

electronics today

MARCH 1978

INTERNATIONAL

45p

Avoid howlround with our
FREQUENCY SHIFTER

INSIDE VCT
LCD PANEL
METER
AUTO
ELECTRONICS
TRUE RMS
VOLTMETER

**FREQUENCY
SHIFTER**




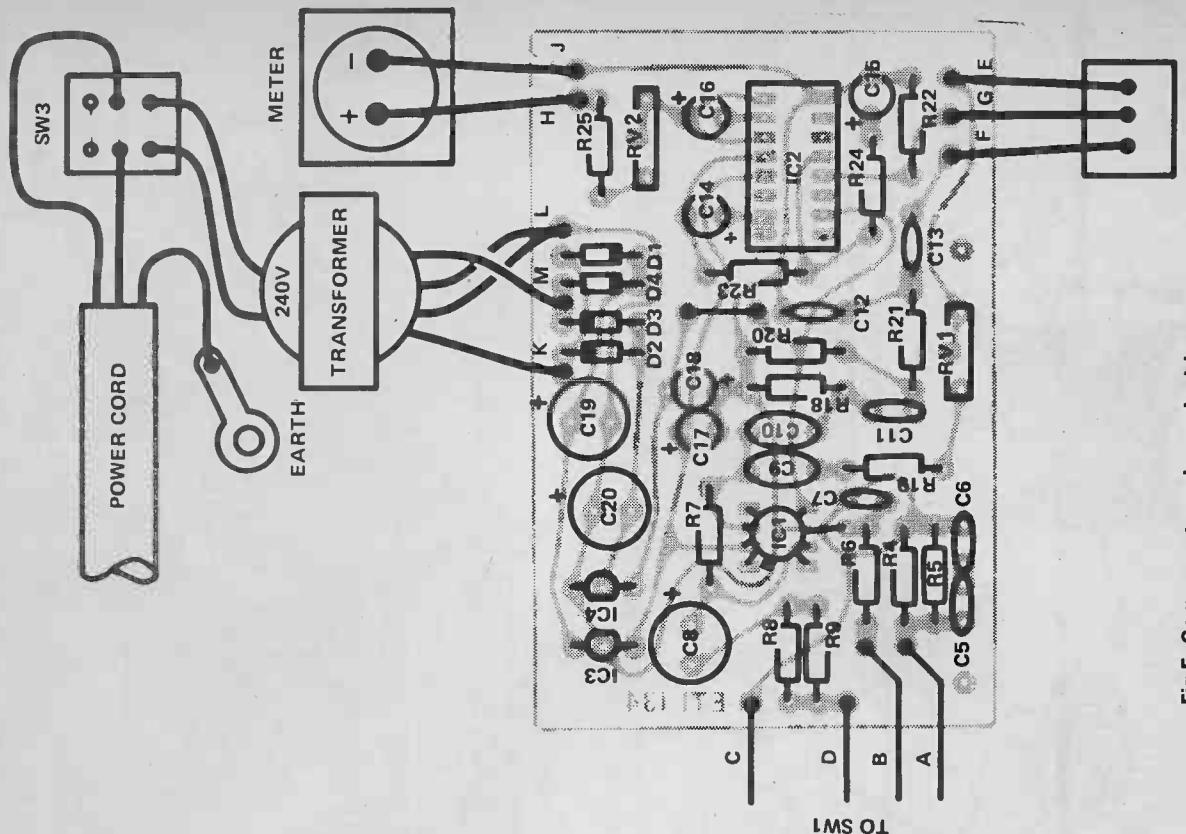


Fig 5. Component overlay and wiring diagram. See Fig 3 for switch wiring.

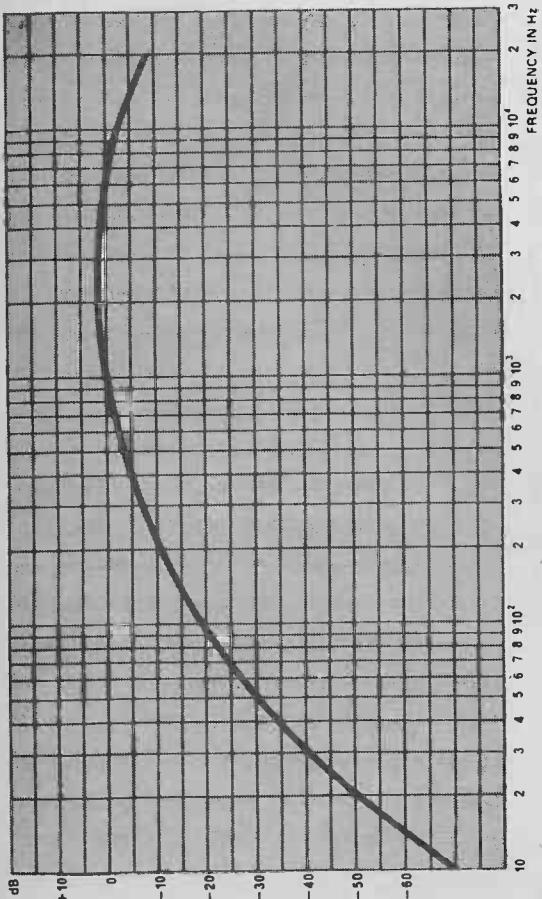

The response in the "A" weight position.

quate shielding and layout, stability was obtained and this final design is presented here.

The spare IC in the LH0091 is normally used to buffer, filter or amplify the output of the converter, but used before so as to buffer the filter network and save an additional op amp (the input impedance of the RMS convertor is only 5k). The output voltage of the convertor is only 500 mV but this is adequate to drive a meter. We could have provided more gain in the buffer stage so giving a higher output but this would lead to greater errors with high crest factor waveforms.

We have limited this instrument to AC signals as this eliminates the need for balance controls to correct for drift when measuring low level signals. This normally is of no consequence as most signals, i.e., output of a tape recorder, sound level meter, etc, have no DC component. If DC capability is needed capacitors C1, 8, 9, 14, 15 and 16 have

to be shorted out, a zero adjustment potentiometer added to IC1 along with the potentiometers needed to offset adjust IC2 (see data sheet).

Construction

The wires associated with the rotary switch should be no longer than necessary to minimise any pickup. The box should be earthed to the mains earth and the front panel earth terminal (left hand one) should also be connected to earth.

Use

When measuring low level signals there may be 50 Hz pickup unless the common side of the input signal is connected to ground. This may be done either in the unit under test or on the meter (hence the earth terminal). Also with the meter terminals open circuited the meter will give some reading. However, as the output impedance of low level signals (0.3 mV and less) is normally relatively low this is normally no problem.. ETI

PROJECT: RMS Voltmeter

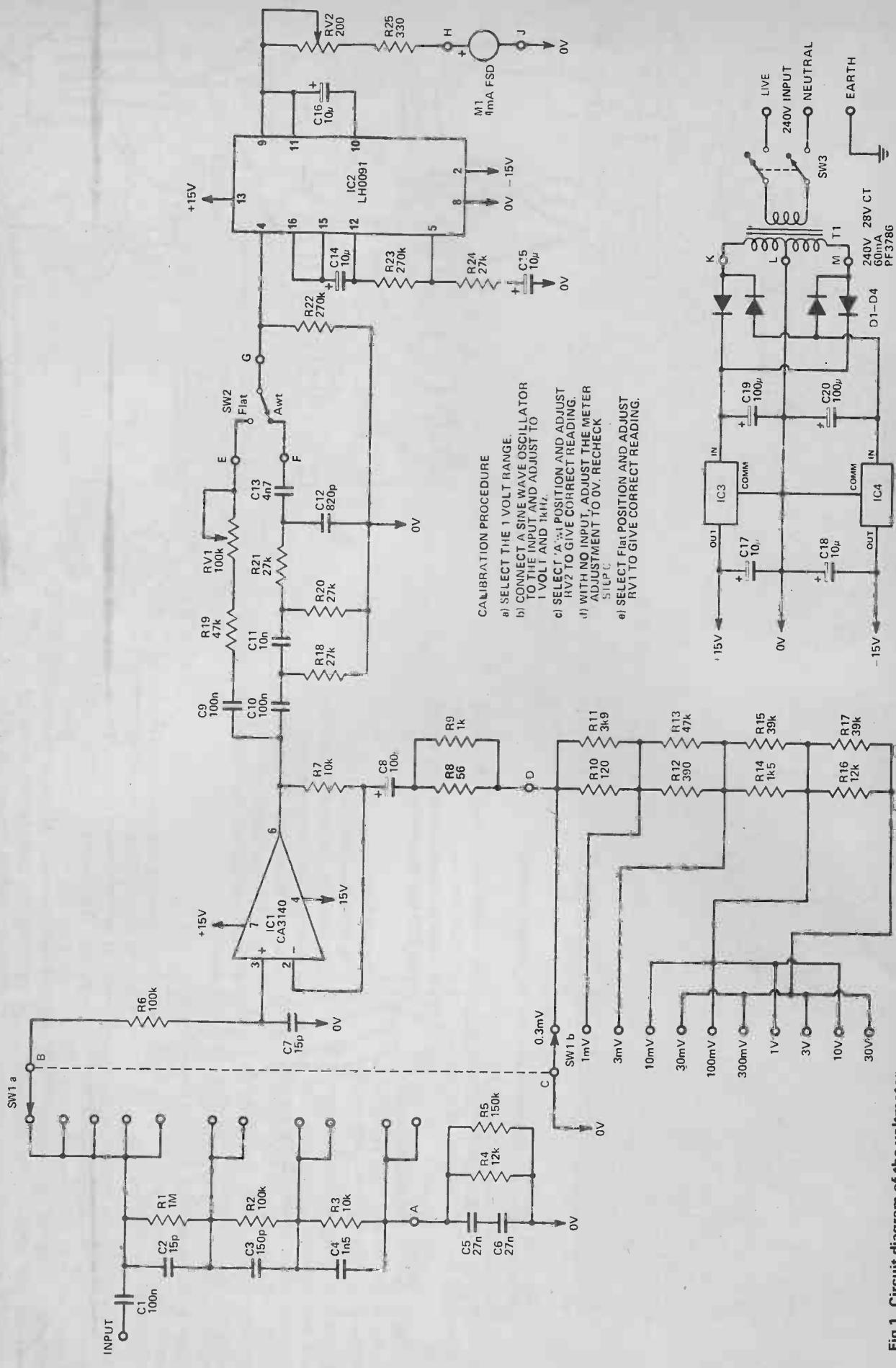


Fig 1. Circuit diagram of the voltmeter.

HOW IT WORKS

The input signal is attenuated by the network R1-R5 and C2-C6; the appropriate attenuation is selected by SW1a. This gives 0 dB, 20 dB, 40 dB and 60 dB. The output of SW1a is buffered by IC1 which is a FET input op-amp. This amplifier has a gain which is switchable giving 5.56 dB, 15.56 dB, 25.56 dB, 35.56 dB and 45.56 dB. By selecting a combination of these two variables the eleven ranges from 0.3 mV to 30 V are obtained. The output of IC1 for full scale reading is 60 mV.

The output of IC1 goes to the 'A' weight filter network and also directly (via R19 and RV1) to SW2. This selects either 'A' weighting or flat response. As the filter has 2.3 dB loss at 1 kHz the "flat" position is also attenuated (hence R19, RV1) to maintain calibration.

The RMS detector IC provides a gain of 20 dB before the detector, the output of the detector is about 500 mV for full scale reading.

The power supply is simply a full wave rectified supply giving both plus and minus voltages of about 20 V, which are then regulated to ± 15 V by IC3 and IC4.

BUYLINES

The only 'hard-to-get' component in this design is the LH0091 true RMS detector. Marshalls have arranged to stock it for ETI readers and can supply most of the other components as well. The PCB will be available from normal suppliers Crofton, Ramar, Tamtronik who advertise at the back of the magazine.


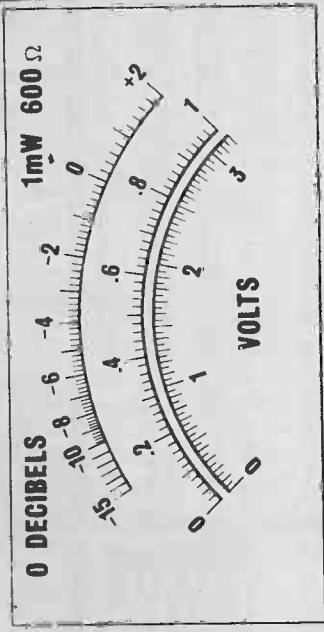


Fig. 2. Meter scale shown full size.

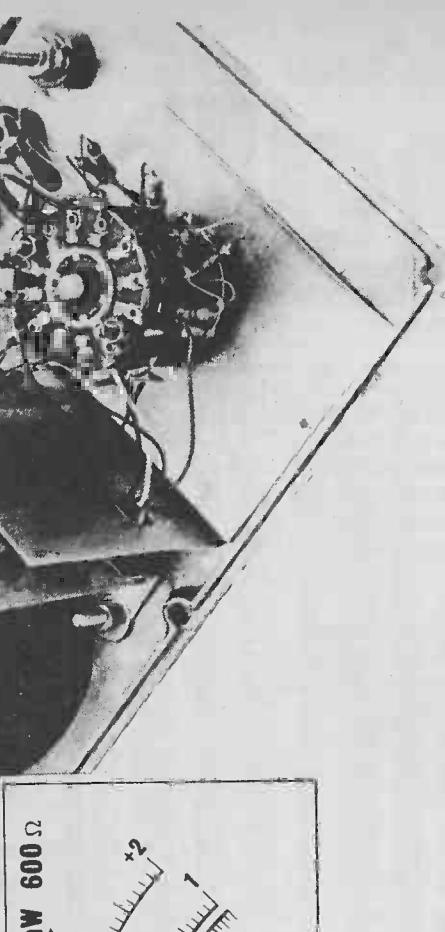

SPECIFICATION

Meter Type	RMS reading AC only
Ranges	0.3, 1, 3, 10, 30, 100, 300 mV 1, 3, 10, 30 V
Accuracy	+3% nominal (crest factors up to 3) -8% at crest factor of 10
Input Impedance	1M in parallel with 25p
Weighting Networks	Flat or 'A' weight
Frequency Response	10 Hz - 20 kHz

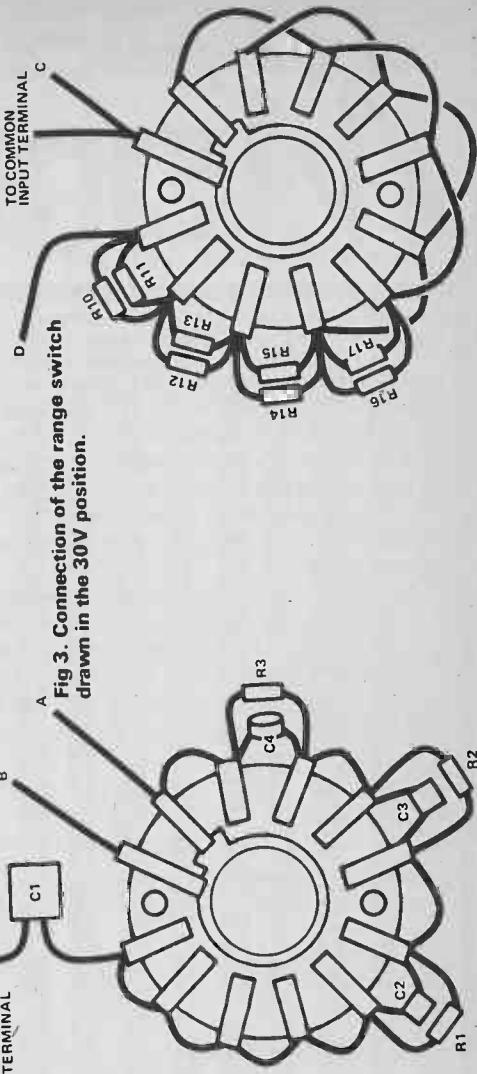


Fig. 3. Connection of the range switch drawn in the 30V position.

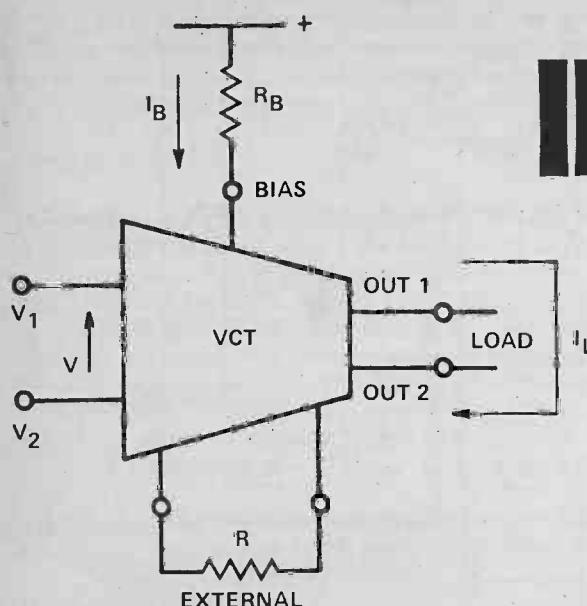


Fig. 1. VCT symbol and external connections.

THE CIRCUIT SYMBOL for the VCT is shown in Fig. 1 along with the necessary bias supply and an external resistor R which determines terminal gain. The name "voltage-current transactor" is derived from the translation of differential input voltage into a proportional output current.

As with the conventional op-amp, the input impedance is made as high as possible to minimise loading of any practical source of input voltage, but the main difference between the VCT and an op-amp lies in the output port. As a current source rather than one of voltage, the port impedance is high rather than low. Furthermore, whereas the op-amp output signal is usually single-ended and referenced to ground, the VCT output is completely floating. The VCT is thus a true four terminal device and either terminal of either port may be used as a common point. It will also be apparent from Fig. 1 that there is no external feedback element involved in a simple amplification application.

The internal circuit is shown in Fig. 3 and as explained in this article there is no overall feedback concealed within

INSIDE VCT

In the January 1977 issue of ETI Ron Harris reviewed the recent development of the Voltage-Current Transistor (VCT), perhaps the most important device innovation of recent years for not only is the VCT expected to perform all the functions we now expect of the op-amp but to perform them either better or with fewer additional components.

The earlier article briefly covered the VCTs development and its terminal properties, together with basic circuit applications. This article describes the VCTs internal functioning. It has been written for ETI by Dr. J. E. Morris of the Department of Physics, Victoria University of Wellington, New Zealand.

the unit. With no feedback, there can be no feedback stability problems and thus a major headache of op-amp design vanishes.

VCT Circuit

Modern ICs are generally very complex and involve many functional blocks. At first glance a circuit diagram often appears to have more relevance as a design for a maze than as a sensible means of serving these required electronic functions. The trick is to identify the functional blocks. Once their patterns are recognized, circuit operation may be deduced. For example it is obvious that the VCT is essentially symmetrical about the centre, so only one side need be considered in detail. And the input transistors ($Q_1 Q_2$ on side 1) clearly form a Darlington pair and may be regarded as a single composite transistor (Q_D say) in any simplified analysis.

Most of the functional blocks in the circuit are derived constant current sources and these will be briefly reviewed before seeing how they fit together to form the VCT.

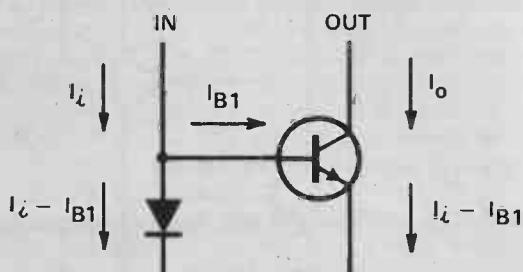


Fig. 2. Basic constant current source. I_o is fixed by injected I_i .

The obvious solution to the impedance matching problem might appear to be the use of a common-base transistor stage which has low input impedance into the emitter and the same high output impedance from the collector as above. In an equivalent situation to Fig. 3 however, a PNP transistor is required and the sign of I_o is reversed. A minimum of three supply voltages would then be required instead of the two implied by Fig. 3.

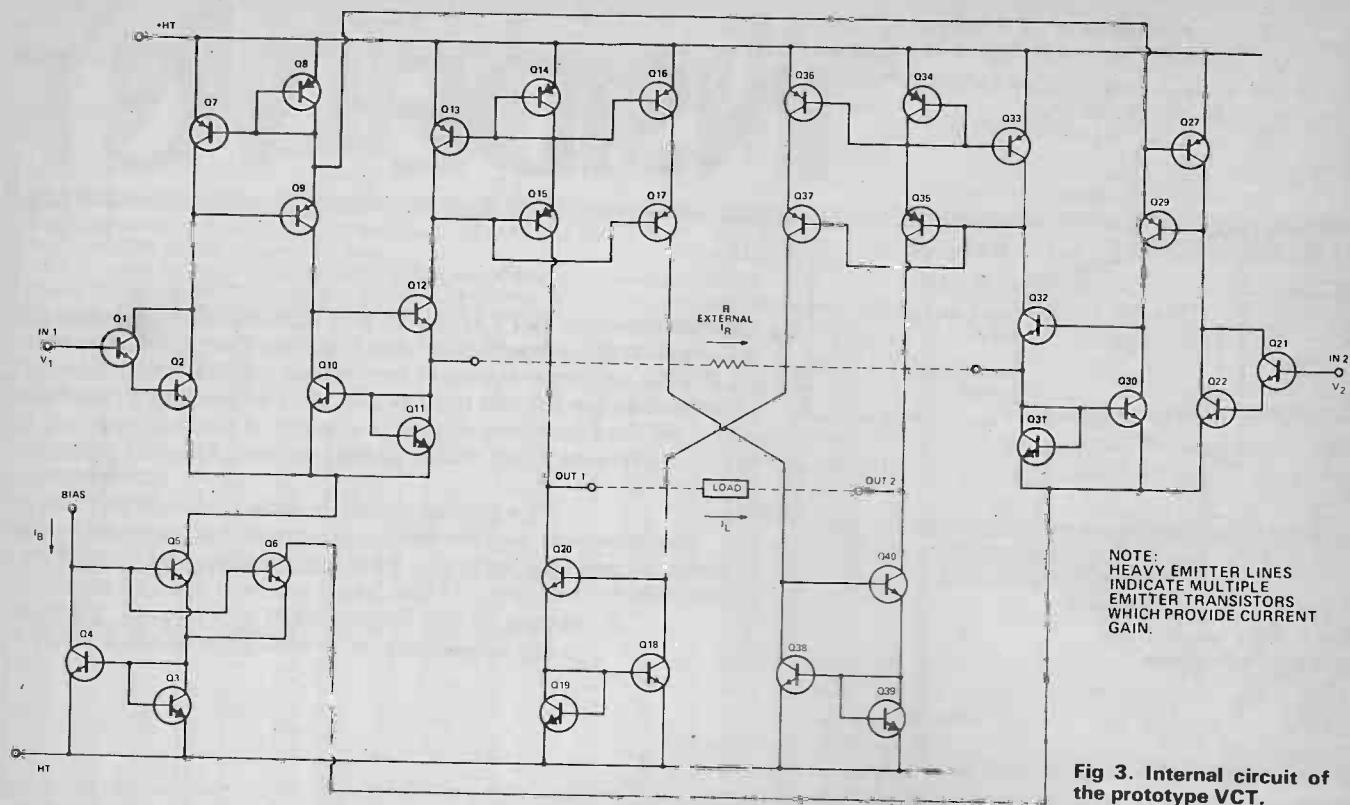


Fig 3. Internal circuit of the prototype VCT.

IC Current Sources

A) Mark I

The derived current source performs a similar impedance matching function with respect to current to that which an emitter follower provides in voltage circuits. A circuit commonly employed in ICs is shown in Fig. 2 where the essential requirement for operation is that the diode is matched to the B-E junction of the transistor. For a given diode voltage equal to the B-E voltage, identical currents must flow through the diode and emitter junction. By inspection $I_o = I_i - 2I_{B1}$ in this case and $I_o \approx I_i$ provided transistor gain β is high. The input impedance is low and the output impedance is high to provide the current in/current out impedance matching required. In addition the input DC level (V_{BE}) is low and the output DC voltage (V_{CB}) will depend upon the nature of the load.

B) Diodes

The crux of the design in Fig. 2 is the matching of the diode to the B-E junction. One major feature of the modern IC is the close matching which may be achieved between adjacent transistors on a chip. Whereas the absolute values may vary quite considerably, and such variation occurs almost identically in nearby transistors. Tight thermal coupling also ensures that the characteristics remain matched independent of external temperature fluctuations and local Joule heating. The diode employed in the VCT is actually a normal transistor with the base shorted to the collector (see Fig. 4). If this transistor is adjacent to the current source transistor and physically identical to it, then the fact that V_{BE} is common to both ensures an identical emitter current in each (Fig. 2). To a first approximation only, the particular configuration also provides

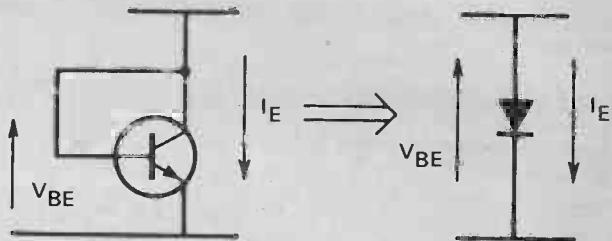


Fig 4. IC diode format.

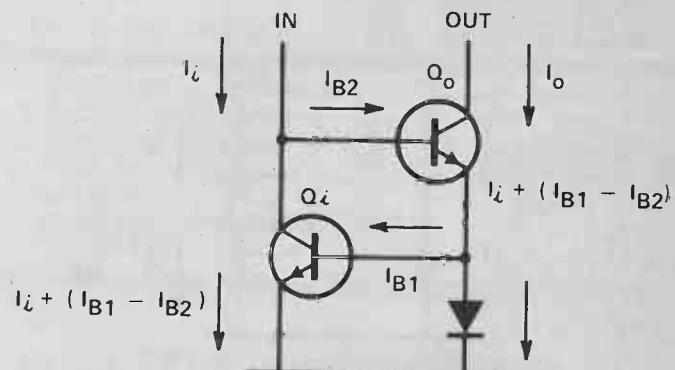


Fig 5. Constant current source employed in the VCT.

for a similar distribution of I_E between I_B and I_C . Truly identical transistors will not, however, possess identical current gains in the circuit due to the differences in V_{CB} (zero for the diode transistor).

C) Mark II

The problem with the single circuit of Fig. 3 is the requirement of high transistor gain. A partial solution is provided by the circuit of Fig. 5 which is the basis of all the functional blocks of the VCT. Here $I_o = I_i + 2(I_{B1} - I_{B2})$ and is made to closely approximate I_i by ensuring that $I_{B1} \approx I_{B2}$ rather than relying only on a large β . Note that the improvement is at the cost of an increased input impedance and DC input level ($V_{BEi} + V_{BEo}$). If $I_{B1} = I_{B2}$ exactly, β must be slightly greater for Q_o than for Q_i (which is reasonable since V_{CBo} will be greater than $V_{CBi} = V_{BEo}$).

Each of the functional blocks involves further modification of this circuit. These will each be described in turn.

D) Multiple Emitters

The multiple emitter structure has been mentioned before. All it means is that the transistor emitter current is increased for a given V_{BE} by increasing the emitter area. In this way the multiple emitter, when used in the output side of a derived current source, can provide current gain. A current gain of two for each of the multiple emitter stages in the VCT leads to the prototype device specifications quoted by Harris and is assumed below.

Bias Circuit

The bias circuit has been redrawn in Fig. 6 where the multiple emitter transistor Q_3 has been split and is shown as two separate diodes. Current amplification leads to the defined bias current $I_B = (V_S - 2V_{BE})/R_B$ being drawn equally from each of the two sides of the VCT.

Note that while the total symmetry shown in the diagram implies that the introduction of a multiple emitter structure requires β_5, β_6 to be twice β_4 , this conclusion is misleading. In fact one would be more likely to vary the multiple emitter area slightly off two, such that (i) all β 's were approximately equal as before (ii) diode currents become $I_B + \frac{1}{2}I'$, and (iii) the base current of Q_4 reverts to $(\frac{1}{2}I') + (\frac{1}{2}I')$.

Differential Input

It should be clear by now that the VCT relies upon defined current sourcing and multiple emitter current amplification to function. The input signal however is defined as a differential voltage ($V_1 - V_2$) and must be converted to a proportional current. This is the purpose of the external resistor R as shown by the simplified view of Fig. 7 where I_R is clearly $(V_1 - V_2)/R$ provided symmetry is maintained. (Q_D is the Darlington combination Q_1 and Q_2 ; Q_{11} functions as a diode).

It will be seen shortly that the existence of a finite I_R upsets the symmetry — in fact this is how the circuit functions. So once again, our ideal is not quite possible since the diodes carry different currents at slightly different voltages. In fact $I_R \approx (V_1 - V_2)/R$.

The next step is to see how I_R is converted to an output current.

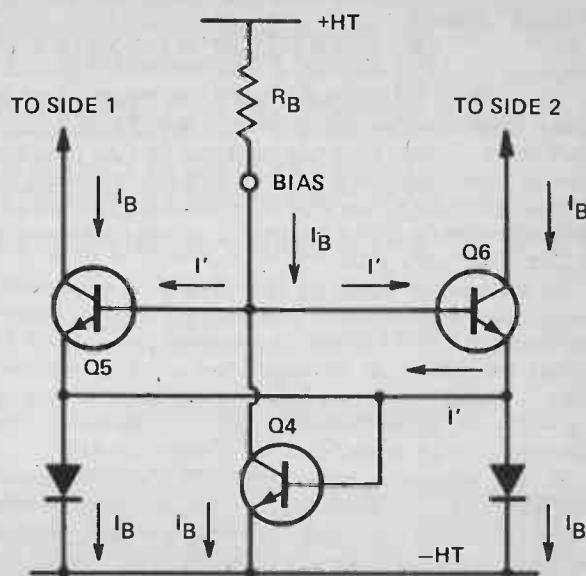


Fig. 6. Bias circuit as an example of the multiple-emitter diode.

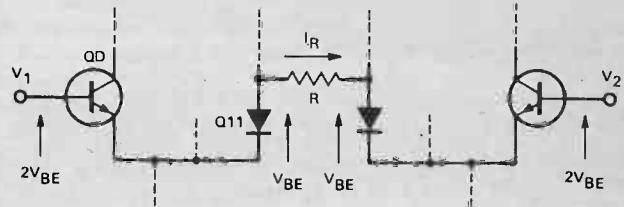


Fig. 7. Simplified view of the differential input circuit.

Input Circuit

The input section of one side of the VCT is redrawn in Fig. 8. Q_8 services both sides of the circuit and has been split in the diagram. Assume for the moment that some current I_x flows down through Q_7 and then the Darlington Q_D . The Q_7, Q_8, Q_9 current sourcing circuit requires I_x to also flow through Q_9 and Q_{10} . Similarly Q_{11} should draw $2I_x$ due to the double emitter. The total $4I_x$ must equal the bias current I_B and hence the currents are as shown with Q_{12} also carrying I_B . The principle of this input circuit is summarised for reinforcement in Fig. 9 which should be compared with Figs. 7 and 8.

It has already been stated that V_{CB} of the source output transistors will vary under operating conditions and cause deviations from ideal behaviour due to resultant in β . In Q_{12} the base current I_{B12} (assuming constant β to first order) can no longer equal I_{B10} . Current source operation must therefore deteriorate under operational conditions.

Output Circuit

The next step is to determine how the input signal current I_R is translated into a proportional floating output. Fig. 10 shows the remainder of side 1 of the VCT, designated as the output circuit. Clearly transistors Q_{18} to Q_{20} form a derived current source with gain equal to two. But it may be more difficult to see that Q_{13} forms part of two similar sources: with Q_{14}/Q_{15} to give a gain of two, and with Q_{16}/Q_{17} for unity gain.

So the current drawn by Q_{12} (Fig. 8) is converted into two proportional currents. The first ($I_B + 2I_R$) flows into the node "OUT 1" while the second ($I_R + I_B/2$) is delivered to side 2. A corresponding current from side 2 ($-I_R + I_B/2$) flows into Q_{18} and the amplified signal ($I_B - 2I_R$) is drawn from the "OUT 1" terminal. The net current delivered to the load (I_L) is therefore $4I_R$.

In the paragraph before last, the detailed operation of Q_{14} to Q_{17} was hurriedly glossed over in order to first cover the principle of the output circuit. The diode function of Q_{14} should be familiar by now, but the reason Q_{15} has also been made with a double emitter is to keep V_{BE15} with $(I_B + 2I_R)$ equal to V_{BE17} with half that current. In this way, the collector and base terminals of Q_{16} are linked by a virtual short circuit and Q_{16} is constrained to also function as a diode.

Overall Principle

When side 1 and side 2 are considered together, as in the simplified equivalent of Fig. 11, one can appreciate the overall concept of the VCT. The input signal ($V_1 - V_2$) causes a current imbalance $(V_1 - V_2)/R$ to be superimposed on the null input bias levels (Fig. 9). With current gain mixed into the process, the bias currents are then balanced out leaving a net differential load current $4(V_1 - V_2)/R$ in the load (Fig. 11).

Device Properties

Each multiple emitter in the prototype VCT has been assumed to give a gain of two. Clearly, it would be simple to vary this; indeed it would appear feasible to provide gain in other parts of the circuit as well as or instead of those shown. Nevertheless, for the prototype as shown, $I_L = 4(V_1 - V_2)/R$. For voltage gain, one might merely insert a load resistor R_L for a totally floating output gain $4R_L/R$. Other elementary circuit configurations have been described by Harris.

The absolute linear range of the VCT is restricted in both current and voltage. Transistor cutoff when $2I_R = I_B$ (See Fig. 10) limits output current $I_L = 4I_R$ to a maximum of $\pm 2I_B$: I_B being set by the circuit designer. Either output current or load is also limited by load voltage and the onset of saturation in the output transistors, i.e the load voltage $I_L R_L$ may not exceed the total power supply range minus $4V_{BE}$. For + 15 V supplies and 10 mA bias current the load impedance limit is 1k4 if the full output current range is to be available. Note also that wide signal excursions from the symmetrical design bias point lead to loss of linearity, since V_{CB} of the current source output transistors are moved off bias values causing β to shift. The need to maintain V_{CB} and β close to design values also limits the acceptable power supply variation — about 10 to 15% according to Harris. These figures would suggest that linearity may be seriously degraded by voltage swing well before the saturation limit is reached.

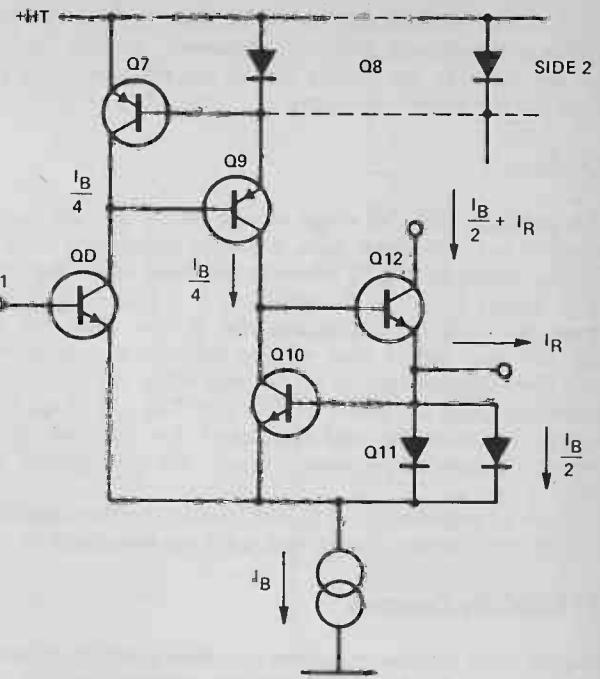


Fig 8. Input circuit — side 1.

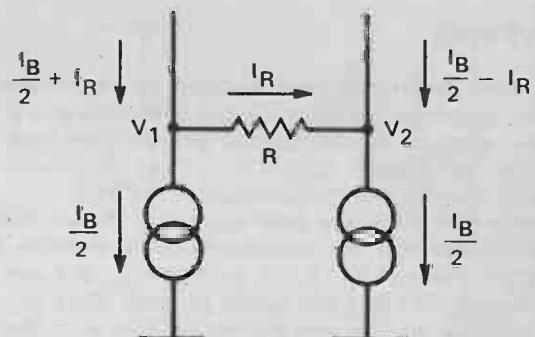


Fig 9. Equivalent input circuit.

High input impedance R_{in} is a fundamental requirement of the VCT concept and is the reason for the use of Darlington inputs. To the grossest of approximations, small signal R_{in} ($=\beta_1 \beta_2 R / \beta_{10}$) is critically dependent upon the input stage current gain and maximising it leads to a whole series of tradeoffs, (e.g. R . should be low for high transconductance, β_{10} high for current source operation)

Common mode rejection ratio and required offset will both depend upon the degree of symmetry attainable in mass production but there is no reason to be pessimistic about them. High slew rates have been reported and are undoubtedly due to the fact that currents vary in only half of the circuit transistors and that the signal only proceeds sequentially through about half of these.

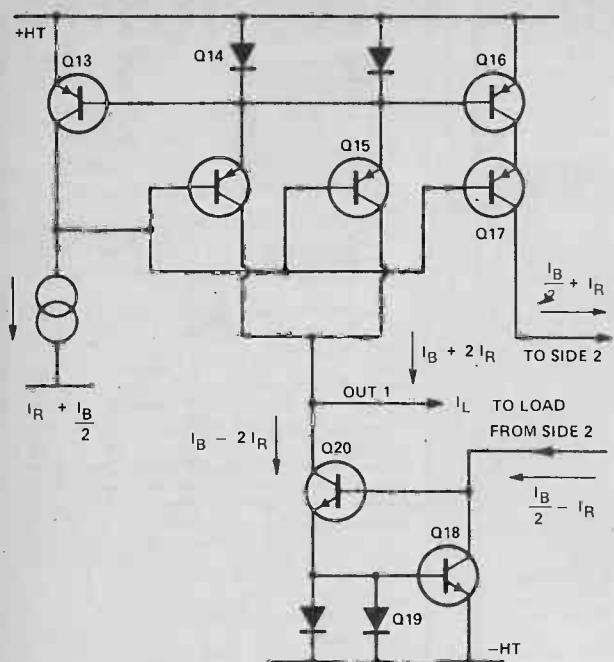


Fig 10. Output circuit — side 1.

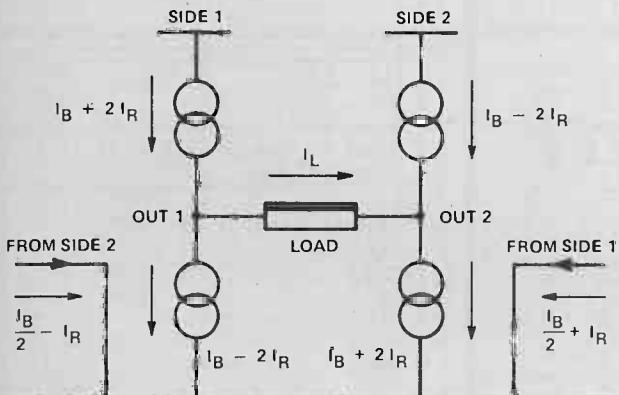


Fig 11. Equivalent circuit of the differential current output.

Conclusion

The main objective of this article has been the explanation of the principles of circuit operation. A secondary aim was to point out some unwanted second order effects and practical limitations. Such limitations occur in all devices and must not be ignored by either the designer or the user.

The immediate question is whether the VCT will survive through to production or remain just another bright idea. Simplicity is a major advantage to any technological innovation and despite the plethora of transistors, the VCT is very simple in principle. Furthermore its implementation will rely totally on existing technology — its future looks bright.

I should like to thank my students whose curiosity and questions led directly to this article.

ETI

**4 WAVE BAND
STEREO RADIO &
STEREO CASSETTE
TAPE RECORDER**
WITH CRO₂ ONLY £117.50
inc. VAT



THIS SUPERB PIECE OF EQUIPMENT HAS EVERYTHING! YOU WOULD WANT AT A FRACTION OF THE NORMAL PRICE AND HAS MORE FEATURES THAN THE MOST SOPHISTICATED AND MORE EXPENSIVE EQUIPMENT.

AN OUTSTANDING SET!

the ORBIT will give you wonderful sound in pure stereo 2.3 watt per channel with stereo volume & tone controls.

STEREO RADIO!

Not only is this a stereo cassette but stereo radio on VHF which you can tape direct!

4 WAVE BAND!

soon to receive all British broadcasts you must have Mw, Lw & VHF NOW! is a golden opportunity to have a 4 wave radio it has short wave as well 6-16MHz with extra fine tuning!

CRO₂

Not only can you use any cassette for recording but for the best reproduction you have CRO₂ head for using CRO₂ tapes.

FEATURES:

Radio	mw	535-1605 khz
	lw	150-350 khz
	sw	6-16 MHz

Tape 4 track stereo. Wow & flutter 0.2% wrms. Fast forward. Fast rewind. Eject button. PA button. AFC button. Stereo indicator. Headphone jack. Ext. mic. & aux. In selector. This set runs off batt./mains, car and has facilities for recording input, output for external sources. Output 2.3 watt at 4 ohms. Total harmonic distortion 3%. Input sensitivity 100nV. Aux/impedance 400k ohm. 405mm(W). 150(7) 255(D).

FANTASTIC EXTRA FEATURES!

These features should be costing you a lot more.

Mixing facilities for having your voice to background music, etc. VU tuning and battery meters to get the exact level of reproduction.

SLEEP!

Just go to sleep with radio or cassette on and it will turn itself off.

MEMORY COUNTER!

To tell you where you are up to. But set the memory button and it will find its way back to where you started.

PAUSE BUTTON!

For catching your breath without the clunk! Two built-in condenser mics for stereo recording, with facilities for external remote control mics.

STEREO SPEAKERS!

Press a button and the speakers come apart to give you that extra sound.

IT'S GUARANTEED

Your ORBIT is fully guaranteed for one year. It is made by a well known Japanese manufacturer with full back-up service here in England.

YES. Send me

Name

Address

ALL PRICES INCLUDE VAT


Add £1.90 for P&P (Mail Order only)

TRITRON

57 BRIDGE LANE, LONDON NW11

Tel: 458 4757

LCD PANEL METER

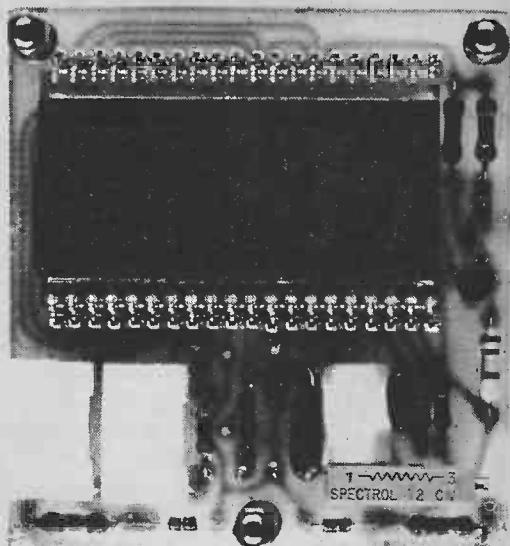

This simple, economical yet highly accurate voltmeter uses a large liquid crystal display for easy reading and low power consumption. It will be the basis of future projects as well as being a useful meter in its own right.

WE INITIALLY purchased a number of Intersil evaluation kits for our own use but soon realised that while they were very good electronically, the physical layout wasn't too hot. We therefore redesigned the PCB, reducing the size dramatically, adding the decimal point drive circuitry and some dropping resistors and zener diodes to allow the board to run from a dual power supply of $\pm 5\text{V}$ or more (e.g. with op-amps). This resulted in a very useful device which we decided to run as a project. While it is basically a panel meter suitable for DC voltages and current (with a shunt) it will be the display module for several future projects.

Construction

To save on real estate, the main IC is mounted under the display. We used the Soldercon pins supplied with the evaluation kit for the display and soldered the IC directly into the board. If you want to mount the IC in a socket a low profile type should be used, with a high one for the display. As a socket is not available for the display a standard 40 pin one can be cut up to fit.

However before fitting either the display sockets or the IC, fit all the other components first. The overlay in Fig. 2 shows the positioning of the components. Most of the components come with the evaluation kit. The large capacitors are laid on their side to minimise height.


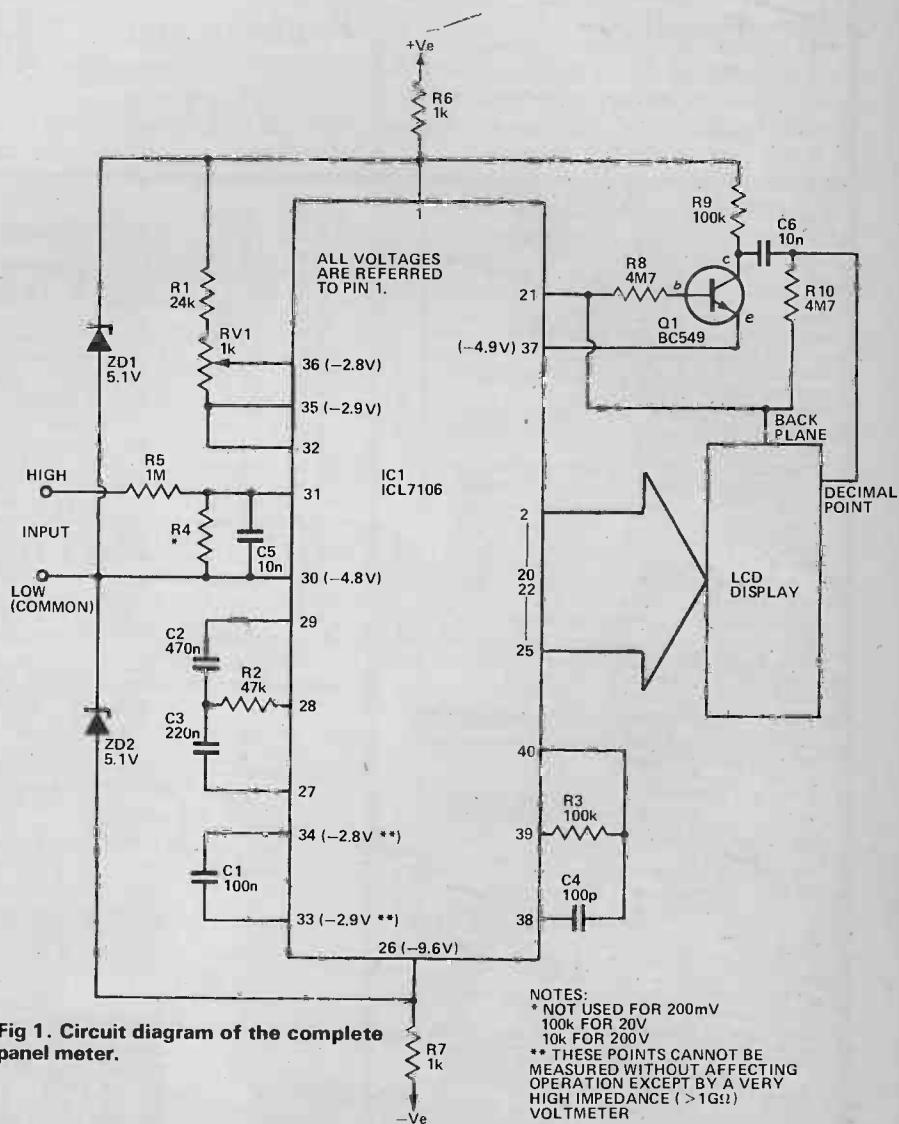


Fig 1. Circuit diagram of the complete panel meter.

SPECIFICATION

Full scale reading	200mV
Resolution	100µV
Accuracy	<1 digit
Display	3½ digit LCD
Input impedance	>10 ¹² ohms
Input bias current	≈2 pA
Polarity	automatic
Conversion method	dual slope
Reference	internal
Power supply	±5V to ±15V DC 1mA @ ±5V

Fig 2. Component overlay with the display in place. Points marked A, B and C are the unused display segments — the vertical part of the + sign, the arrow and the semicolon respectively.

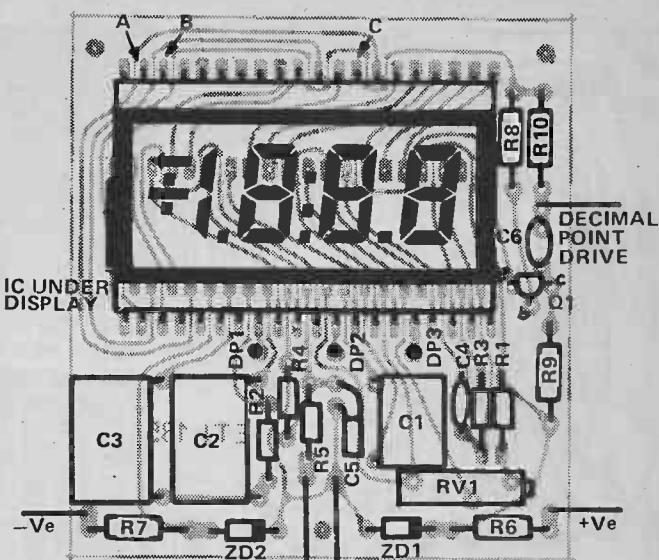

BUYLINES

The Intersil Evaluation kit is available from Rapid Recall, 9 Betterton Street, Drury Lane, London WC2H 9B5 at a cost of £23.29 all inc. If you want to just build the ETI version, Doram and Marshalls stock the chips and display, Watford stock everything as a kit. The PCB is available from all the 'usual' suppliers e.g. Ramar, Tamtronik etc.

PARTS LIST

RESISTORS all 1/2 W 5%

R1*	24k
R2*	47k
R3*, 9*	100k
R4	See circuit diagram
R5*	1M
R6,7	1k
R8,10	4M7

POTENTIOMETER

RV1*	1k 10 turn type
------	-----------------

CAPACITORS

C1*	100n	Polycarbonate
C2*	470n	Polycarbonate
C3*	220n	Polycarbonate
C4*	100p	Ceramic
C5*, 6	10n	Ceramic

SEMICONDUCTORS

IC1*	ICL7106
Q1	BC549 or similar
ZD1,2	5V1 400 mW

MISCELLANEOUS

PCB, LCD 3½ digit display*, soldercon pins*.

* These components are supplied with the Intersil evaluation kit.


HOW IT WORKS


Not much can be said on how this project works as everything is done by one IC and if anything goes wrong it is usually the IC. We have included some waveform diagrams and voltages for reference purposes. The conversion works on the dual-slope integration technique, which is the most reliable of the simple methods available. A capacitor is charged up at a rate proportional to the input voltage for a predetermined time (in this case 1000 clock pulses), then it is discharged at a constant rate until it reaches the starting point again. The time taken to do this (i.e. the number of clock pulses) is proportional to the input voltage.

It is a true dual polarity system where the integration direction depends on the polarity of the input voltage. Provided AC ripple on the input averages to zero over 1000 clock pulses it will be rejected, hence where 50Hz mains is to be rejected a 50 kHz clock should be used, giving 80 ms sample time (4 cycles of 50 Hz). The clock can be adjusted by varying R3 if desired.


For further details of the IC see the data sheet in this issue.

Fig 3. The component overlay without the display showing the positioning of the integrated circuit.

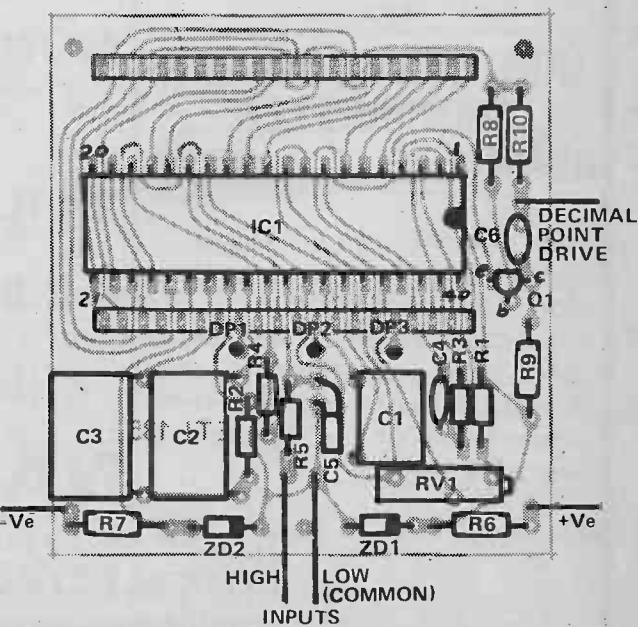

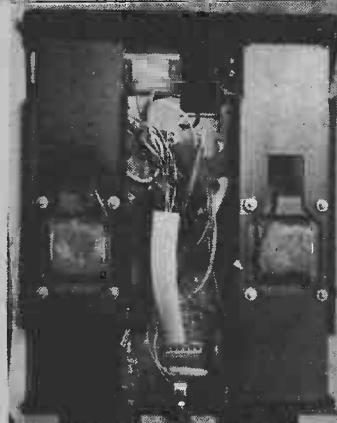

Inside a head p.63

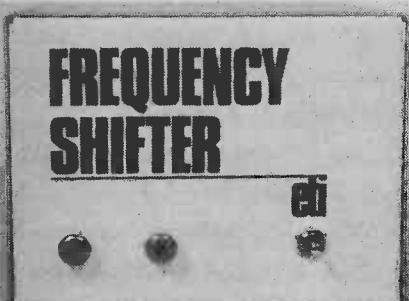

Feel like a move? p.40



Get into top gear p.31

FEATURES

- | | |
|---|---|
| INSIDE VCT
AUTO ELECTRONICS
OP AMPS PART 2
DIGITAL ELECTRONICS PART 6
TECH TIPS | 19 A look beneath the plastic
31 Mixing electrons with Escorts!
49 Circuits galore
66 Do-it-yourself digits
78 More from you to us |
|---|---|

PROJECTS

- | | |
|---|---|
| TRUE RMS VOLTMETER
LCD PANEL METER
FREQUENCY SHIFTER
LIGHT DIMMER
SYSTEM 68 | 13 This meter won't lie to you
26 Easily built, widely applied
40 Move up in the world (by 5 Hz)
55 Tone down the glare
59 Software and all that |
|---|---|

NEWS

- | | |
|--|---|
| NEWS DIGEST
DATA SHEET
AUDIOPHILE
MICROFILE
ELECTRONICS TOMORROW | 7 Who's up to what and where
53 Intersil 7106/7107 display driver
63 The best in heads
71 Womp Rats and Mark 14s
75 Walk in the MPU jungle |
|--|---|

INFORMATION

- | | |
|---|--|
| ETI PRINTS
SUBSCRIPTIONS
ELECTRONICS TOMORROW
ETI APRIL PREVIEW
ETI CLOCK
BOOKS FROM ETI | 9 PCB's the easy way
10 Save yourself the heartache
37 A very special special
39 What's in next month
72 Our longest running special offer
80 Wide range to choose from |
|---|--|

INTERNATIONAL EDITIONS

AUSTRALIA	Collyn Rivers Publisher Les Bell Acting Editor
HOLLAND	Anton Kriegsmann Editor-in-chief
CANADA	Steve Braidwood Editor Graham Wideman Assistant Editor
GERMANY	Udo Wittig Editor

EDITORIAL AND ADVERTISEMENT OFFICE
25-27 Oxford Street, London, W1R 1RF. Telephone 01-434 1781/2 Telex 8811896

Halvor W. Moorshead	Editor
Ron Harris B.Sc	Assistant Editor
Gary Evans	Projects Editor
John Koblanski	Project Development
Jim Perry	Specials Editor
William King	Editorial Assistant
Diego Rincón	Art Editor
Paul Edwards	Technical Drawings
Margaret Hewitt	Administration
Andrew Scott	Office Manager
Kim Hamlin, Tim Salmon, Brenda Goodwin Mark Strathern (Manager), Tom Moloney	Reader Services Advertising




ABC

PUBLISHED BY Modmags Ltd., 25-27 Oxford Street, London W1R 1RF
 DISTRIBUTED BY Argus Distribution Ltd. (British Isles)
 Gordon & Gotch Ltd. (Overseas)
 PRINTED BY QB Limited, Colchester

Electronics Today International is normally published on the first Friday of the month prior to the cover date.

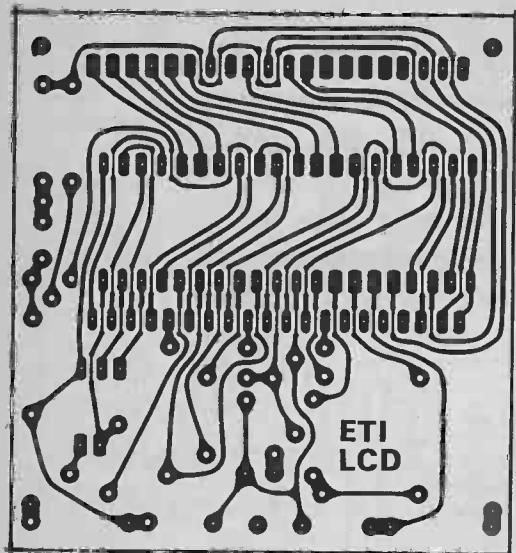COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur a correction will be published as soon as possible afterwards.



Foil pattern for LCD panel meter, shown full size. (65 x 70 mm).

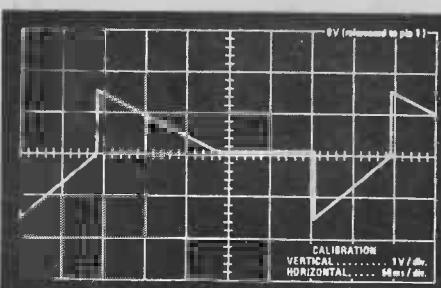


Fig 4. The waveform at pin 27 with a negative input of 170mV.

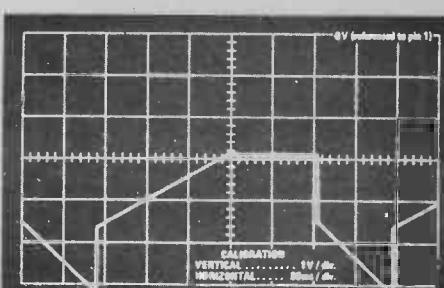


Fig 6. The output of the master oscillator on pin 38.

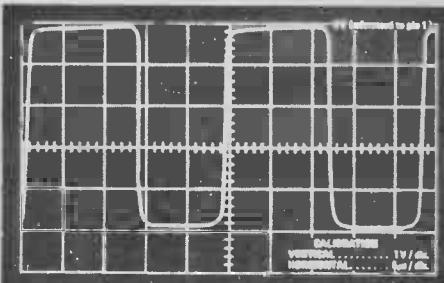


Fig 5. The waveform at pin 27 with a positive input of 170mV.

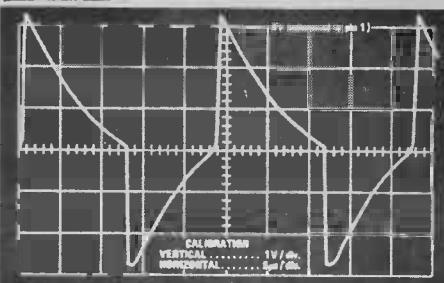


Fig 7. The input of the oscillator-pin 40.

When fitting the IC solder pins 1 and 26 first (the power supply pins) so that the protection diodes on the inputs can operate, thus preventing damage by static electricity. It is necessary that a small tipped iron and fine solder be used

to prevent bridging tracks. The IC sockets can now be fitted in two strips of 20 with the top connecting pieces being broken off using long nosed pliers after they are soldered in.

As there are no polarity marks on the

display it is necessary to hold it at an angle to the light and look for the outline of the digits. The full format of the display is shown in Fig. 3. In this unit the arrow, semicolon and the vertical part of the + sign are not used.

ETI



HOME MICROCOMPUTER

**NORTHERN SEMINAR
MANCHESTER
APRIL 1 £5.50**

After the enormous success of the Wembley Seminar Lynx have been persuaded that there are sufficient Northerners waiting to attend their own show. All day. Microprocessor lectures and presentation of the Nascom I. Only 350 seats.

Z80 QUERTY KEYBOARD
MONITOR PROGRAM
VDU INTERFACE (TV)
2K R.A.M. CASSETTE INTERFACE
P.C.B. TELETYPE INTERFACE

EXPANDABLE SYSTEM

NASCOM I £197.50
+ VAT

**LYNX ELECTRONICS (LONDON) LTD.
92 BROAD STREET, CHESHAM, BUCKS
02405 75151**

Just how will the role of the driver be changed by the rapid advances and increasing implementation of electronics in the motor car? Dr Peter Sydenham examines the most recent equipment to give us a glimpse of the standard accessories of the future.

AUTO ELECTRONICS

IT WAS IN THE LAST DECADE of the nineteenth century that the motor car was born. Most designs of what we now call *veteran* cars used internal combustion engines, for which the main use of electrics was to ignite the fuel in the combustion chamber. Storage batteries were used in some designs of the 1890s to drive the high-tension ignition device and to power an electric warning bell.

Sparkplugs, magnetos, ignition distributors, starter motors, and headlights followed in the 1900 to 1910 era, then a DC generator was added to the engine to keep the battery charged.

Electrical direction signals were in common use by the 1930s, along with stop lights, reversing lights, and courtesy lights. At that time instrumentation of vehicle speed, engine revs, engine temperature and oil pressure almost always used non-electrical methods. Usually the only panel instrument using electrical indication was the ammeter for battery charge or discharge. Regulation of

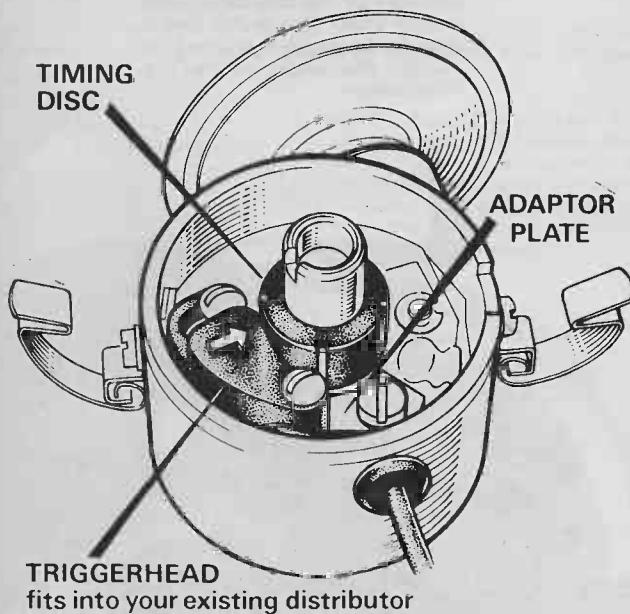


Fig 1. Contactless electronic ignition is available for just about any car. This changeover system is used in the Mobelec system.

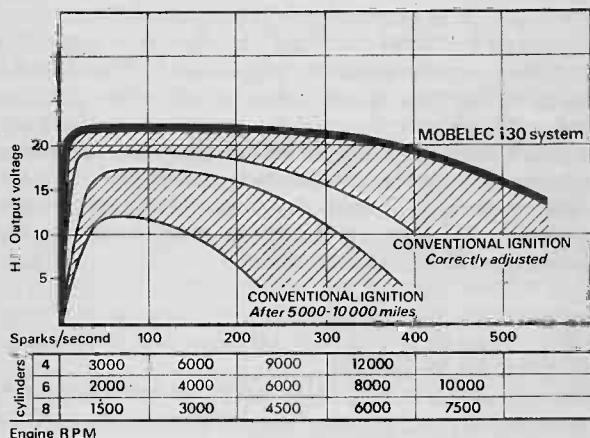


Fig 2. Comparative chart of electronic ignition with the conventional rapidly-dating contact-points method.

battery charge was controlled by moving the "third" brush of the generator and a summer-winter switch position was available to adjust the system for seasonal temperature change.

Cars of the '40s and '50s were little improved. In the 1960s, however, things rapidly began to change. The DC generator was replaced with a much smaller and more efficient AC alternator, which required solid-state diodes for rectification. The day had come when the average do-it-yourself owner could no longer confidently tackle the auto-electrics of the car. Regulators changed from electro-mechanical relays to solid-state circuitry; some cars introduced electronically-controlled fuel-injection, others introduced electronic ignition.

What we saw in the progressive designs of the '60s and early '70s are fast becoming standard equipment today. This study of the 1977 new models and accessory market reveals that there is still a long way yet to go. ▶

Engine And Mechanics

Electronic ignition is becoming standard in an increasing number of cars — Ferrari, Renault, Chrysler and Mercedes use it, while US cars have had it since 1975.

A do-it-yourself kit is available which enables the standard distributor to be used with a change-over "points" component that replaces the contacting points with a non-contact sensor (Fig. 1).

Advantages provided by electronic ignition are lower fuel consumption, easier starting, better idling, improved timing accuracy, and constancy of timing with period of operation, plus no points to need replacing. One maker, Mobelec Ltd, issues a chart showing high-tension voltage output produced by conventional methods compared with their electronic system, shown in Fig. 2. It is seen that the electronic alternative gives the best high-tension performance and holds it over time, unlike the points method that wears.

The next stage of ignition improvement is to replace the rather cumbersome, and not really adequate, automatic vacuum and centrifugal ignition timing control. The latest US Cadillac Seville and Fleetwood Brougham cars have an "electronic spark selection system", which uses electronic logic circuits to monitor engine speed and inlet manifold vacuum, and signal the appropriate spark advance or retard. Thinking it through, it is not hard to see that once electronic ignition is used, with engine speed being measured electronically, it is relatively simple to add a vacuum measuring transducer and use a phase-shift spark time control circuit arrangement. Overall this should be cheaper than the conventional vacuum advance mechanics — and much more reliable and predictable.

Pollution And Economy

Economy is now a strong sales point, so manufacturers are seeking ways to reduce fuel consumption, and the level of pollutants produced by an engine. Fuel injection has been used by a few makers for many years now, and some have reached sophisticated levels of electronic "computer-brain" injector control.

Electronic analysers are used to tune the carburettor for minimum CO emission, but Volvo cars of 1977 now go one step further in the interest of economy and emission control. Their Lambda-Sond electronic air/fuel ratio sensor system uses a "ruggedised" zirconium dioxide oxygen gas content probe in the exhaust manifold. The level of O₂ in the exhaust is measured as an electric signal equivalent that is fed back automatically to control the fuel-injector equipment made by Bosch. This has, it is claimed, enabled the Volvo engines to meet stringent low-emission requirements at less cost than other methods. A snag is that the sensor at present needs replacement at 30 000km periods. They next hope to apply this principle to conventional carburettor control.

A Datsun answer to economy is to provide the driver with a simple "go"-no-go" indicator of the lead-footedness of the driver. "Drive it on the green" is their slogan for the new 1977 Laurel Six saloon. Above the steering column block are two lights — the left green, the right orange. Economy is very much a matter of keeping the inlet manifold vacuum within limits and this

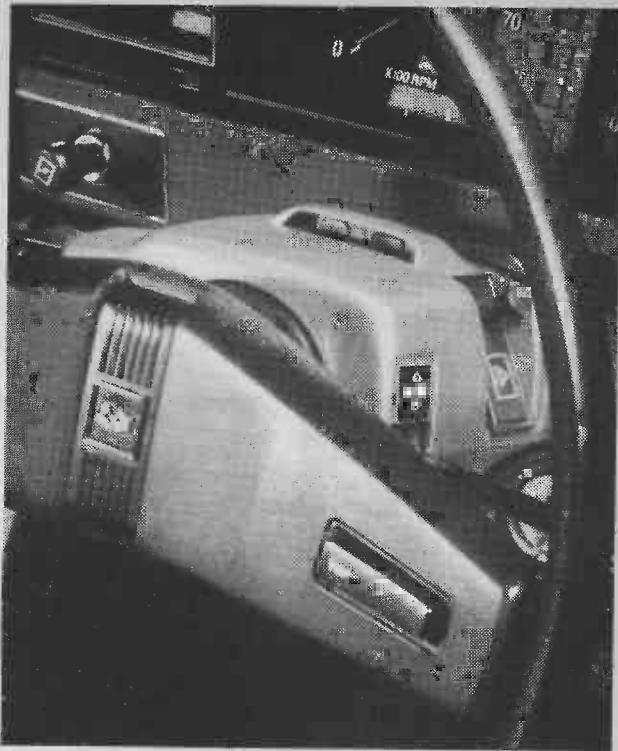


Fig 3. "Drive-it-on-the-green" is the Datsun Laurel slogan. Two lights, seen here above the steering wheel centre, indicate when the driver is operating the engine within good economy limits.

Fig 4. Retrofit cruise control is possible with this kit. The right chain-coupled unit stores the throttle position required. It is operated by the left-hand push button unit. The brake pedal electric connection is used to cancel the position during deceleration.



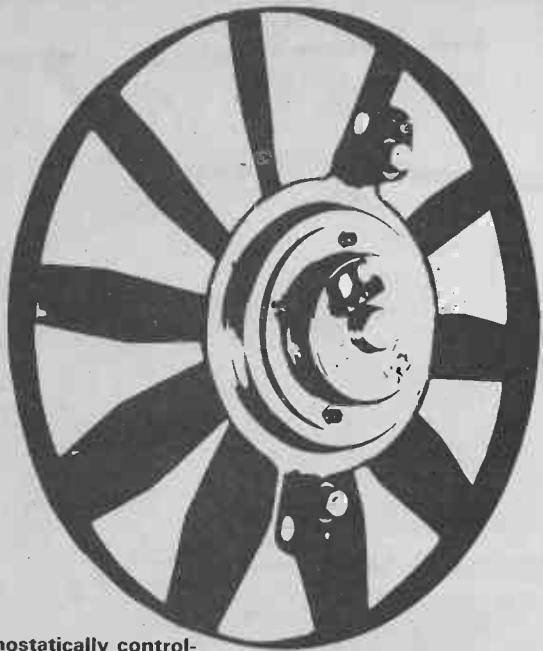


Fig 5. Thermostatically controlled engine cooling fan by Kenlowe.

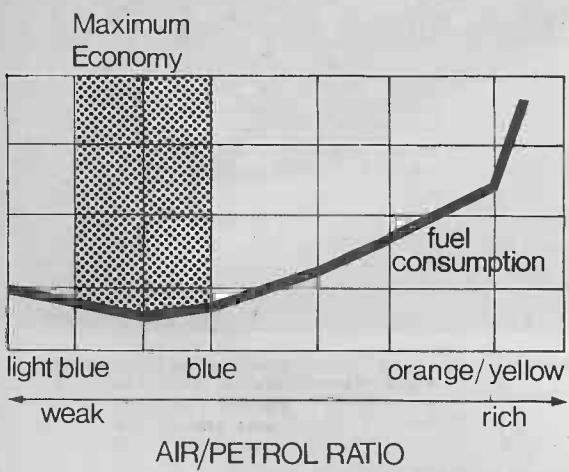


Fig 6. Different air/fuel ratios burn with different colours. Maximum economy is obtained when the colour is in the blue region.

Fig 7. Needle indicators will soon disappear from the dash panel. They will be replaced by solid-state light-emitting diode "scales" that preserve the advantages of the moving-scale method of indication.



is largely decided by the throttle setting for the speed existing.

The 1978 Cadillac Sevilles released in Britain will incorporate the "Tripmaster" facility. This is a central electronic data processing unit. Amongst many other things their display will give digital readout of instantaneous fuel consumption (they call it fuel economy now!) and average trip economy, a calculation which requires the addition of a petrol flow-rate sensor.

Steady driving greatly increases economy, and automatic electronic car speed maintenance — called "cruise control" — is now available on some models. The 1978 US Chevrolet Caprice and some US Ford models have it fitted as a standard addition. The latter have finger-tip touch pads mounted in the crossbar of the steering wheel — to hold the speed reached just touch the button. A retro-fit package produced by Holdspeed Productions Ltd is shown in Fig. 4. The small push-button unit is mounted on the facia and an electro-magnetic throttle "memory" unit is connected in series with the throttle cable to clamp the cable upon electronic demand. Slight movement of the brake pedal releases the unit when the stop light is energised, but it returns to the preset throttle position after acceleration conditions.

The next logical step might be to maintain the car's speed by closed-loops control, using vehicle speed to vary the throttle setting to suit the load. This is, however, yet to be proven as a useful and safe function to provide.

Another way to reduce consumption a little is to replace the engine-driven fan with an electric thermostatically controlled unit. This is not a new idea, but it is at last being adopted to reduce loss and engine noise. The fan still consumes energy, of course, but comes on only when the engine really needs it. It can, it is claimed by Kenlowe Accessories, whose fan is shown in Fig. 5, release up to 9% more engine power. It makes sense to cool the engine this way, and has the added advantage of faster warm-up, and quieter peak engine speed noise.

These systems are thermostatically controlled and, therefore, require a temperature sensor to be added to the water jacket. This can be fitted easily by the use of a special rubber fitting placed under the hose connection, and the temperature control point is set by a dial on the control unit.

Gunson's "Colortune 500" engine tuning system has been on sale for several years now. It is not a complex electronic device but simply a special spark-plug through which the observer can see the colour of the ignition process happening inside the combustion chamber. It is remarkably simple to use, and AA certified tests on five cars made in 1974 showed conclusively that this method could be used to set the carburettor for a better economy. They commented that whilst the drivers could detect no performance difference after tuning, the petrol consumption tests showed fuel consumption was reduced in each case by amounts of 4.45% to 17.39%. Fig. 6 illustrates the colours seen for various mixtures. This device demonstrates the possibility of a closed-loop method that monitors combustion colour using a sensor of this type to control the mixture.

Electronic tuning meters are now marketed in many shapes and forms. Depending on make and model, these enable the setting of breaker points to obtain correct ignition timing, measurement of points contact re-



Fig 8. Stereo speaker equipped headrests can provide better listening. These will also be used for road information services that go only to the driver (or co-pilot!)

istance, and general electrical fault chasing. These are best used in the driver's cabin so that measurements can be checked during actual driving conditions. Once the correct timing is available as an electronic signal, the next stage will be to check this automatically and continuously as one function of a microprocessor diagnostic centre.

Instrumentation

It is clear that the engine will be one significant area of future motor cars in which electronic measurement and control will become a vital part of improving economy, reducing emission, and sensing the need for maintenance.

Electronics will also blossom in the instrumentation of the car. Electric indication of battery charging state, oil pressure, and temperature is now commonplace, the direct hydraulic lines and vapour expansion tubes having been replaced with electrical "senders" many years back. Now also standard are indicators of oil level, seat belts not fastened, brakes not functional, and parking brake on.

Recent additions to the range have been the disc-brake pad-wear warning lights (found in the Renault 20TL), battery condition indication, and a warning light

to tell the driver if all doors are not properly shut.

The Cadillac Seville "Tripmaster" also offers digital readout of estimated arrival time, miles still to go to destination, air temperature, fuel remaining and, of course, speed, the function being chosen via a keyboard mounted on the dash. Many of these functions are provided in the futuristic six-wheel Panther 6 vehicle, which also features a miniature television for the passengers' pleasure, and a panel light-bulb check routine incorporated in the panel.

The days of the electromagnetic instrument movement are numbered. Solid-state analogue-style displays, in which position on a graduated dial is indicated by a lengthening line formed by successively energised light-emitting diodes, are now available. An Austrian tachometer by Intron is shown in Fig. 7.

Utility Without

The motorist's involvement with electrics and electronics does not stop inside the car's compartment. Electronic rear-end levelling is standard in Cadillacs. Height is sensed by an electronic sensor, using photo-electric methods, and this operates an electrically-driven air compressor that alters the height actuators.



Fig 9. This small hand-set is the control for radio-controlled garage doors.

LTs by TEXAS		C-MOS ICs	OP. AMPS
/400 16p	74107 36p	4000 21p	CA1130 108p NE531 V
/401 18p	74119 50p	4001 21p	CA1310 108p 709
/402 18p	74110 50p	4002 21p	CA1360 120p 733
/4C02 25p	74111 75p	1006 127p	LM301A 40p 741
7403 18p	74124 25p	1007 21p	LM318N 175p 747
7404 24p	74116 216p	1008 180p	LM323N 130p 748
7405 25p	74118 160p	1009 180p	LM348N 130p 776
7406 25p	74119 225p	4011 67p	MC1458P 75p 3900
7407 43p	74120 130p	4011 21p	
7408 22p	74112 31p	4012 23p	LINAR ICs
7409 22p	74122 52p	4013 65p	AY-1-012 650p NE555 4
7410 18p	74123 75p	4014 90p	AY-3-8500 775p NE556 97p
7411 26p	74125 70p	4015 90p	CA3028A 112p NE5618 450p
7412 25p	74126 65p	4016 54p	CA3046 85p NE5628 450p
7413 40p	74128 82p	4017 100p	CA3048 250p NE565 200p
7414 85p	74132 81p	4018 110p	CA3053 75p NE566 200p
7416 40p	74136 81p	4019 57p	CA3065 200p NE567 180p
7417 40p	74141 85p	4020 140p	CA3080E 97p RC4151 LDN 432p
7420 18p	74142 300p	4021 120p	CA3D89E 250p SN72710N 54p
7421 43p	74145 95p	4022 140p	CA3090AQ 425p SN76003N 275p
7422 28p	74147 205p	4023 23p	ICL7106 £13 SN76008 280p
7423 36p	74148 160p	4024 82p	ICL8038 400p SN76013N 175p
7425 33p	74150 130p	4025 23p	LM339N 175p SN76013ND 160p
7426 43p	74151 81p	4026 200p	LM377N 200p SN76018 280p
7427 40p	74153 81p	4027 64p	LM380N 112p SN76023N 175p
7428 40p	74154 160p	4028 110p	LM381N 160p SN76023ND 160p
7430 18p	74155 97p	4029 120p	LM389N 160p SP8515 750p
7431 37p	74156 85p	4030 67p	LM3911N 150p TAA621A 310p
7432 37p	74157 85p	4031 100p	M2522A 850p TAA661A 150p
7433 37p	74159 250p	4042 87p	MC1310P 190p TBA001 97p
7434 37p	74160 130p	4043 100p	MC1335P 110p TBA004B 300p
7435 37p	74161 130p	4046 150p	MC1495L 490p TBA651 220p
7440 18p	74162 130p	4047 150p	MC3340P 180p TBA810 125p
7442 75p	74163 130p	4049 64p	MC3360P 160p TBA820 100p
7443 120p	74164 120p	4050 58p	NE540L 225p TDA2020 405p
7444 120p	74165 150p	4054 120p	NE543K 225p ZN414 140p
7445 108p	74166 160p	4055 140p	
7446 108p	74167 320p	4056 145p	VOLTAGE REGULATORS — Fixed
7447 90p	74170 260p	4060 130p	Plastic-T0220-3 Ter- 6.2V 78Lb2 70p
7448 85p	74172 750p	4068 30p	minals 12V 78L12 70p
7450 18p	74173 190p	4069 30p	1 Amp +ve 15V 78L15 70p
7451 18p	74174 130p	4071 30p	
7453 18p	74175 97p	4072 30p	5V 7805 115p
7454 18p	74176 130p	4073 45p	6V 7806 115p 100mA -ve
7460 18p	74177 130p	4078 30p	8V 7808 115p 5V 79L05 80p
7470 38p	74180 160p	4081 30p	12V 7812 115p
7472 32p	74181 324p	4082 30p	15V 7815 115p 12V 79L12 80p
7473 36p	74182 150p	4093 104p	18V 7818 115p 15V 79L15 80p
7474 37p	74183 150p	4101 104p	24V 7824 115p LM309K T03 150p
74C7 70p	74185 190p	4510 150p	LM323K T03 700p
7475 34p	74186 990p	4516 130p	LM327N DIL 275p
7476 34p	74190 160p	4518 110p	5V 7905 160p
7480 54p	74191 160p	4529 110p	12V 7912 160p
7481 108p	74192 160p	14433 E14	15V 7915 160p MC1468 DIL 300p
7482 90p	74193 160p	14533 S540	24V 7924 160p TBA625B T05 120p
7483 99p	74194 160p	14583 150p	7805K T03 150p
7484 108p	74195 110p	Other	Heat sink 1 / W 25p VARIABLE
7485 120p	74196 130p	9301 160p	suitable lo. 10/220 723 DIL 45p
7486 36p	74197 130p	9302 175p	78MGT2C DIL 145p
7489 340p	74198 270p	9308 325p	100mA +ve 1092 T092 LM317T T0220 325p
7490 36p	74199 216p	9310 275p	5V 78L05 70p TL430 T092 70p
7491 90p	74101 175p	9311 275p	
7492 58p	75182 250p	9312 160p	DISPLAYS
7493 36p	5/324 400p	9314 175p	3015f Mintron 200p DRIVERS
7494 90p	5/325 400p	9316 250p	FND500U 50/ Rkt 130p 75-191 84p
7495 75p	9601 175p	9318 275p	DL/00/ DL/0/ Rkt 76492 86p
7496 90p	9602 175p	9321 160p	DL/4/ Rkt Green 250p 9368 200p

When you arrive at the petrol station the fuel is now monitored with advanced metering electronic systems that compute cost and quantity, and which can provide fixed-sum or cash batching. Many countries — Sweden and USA are examples — have banknote recognising, self-service outlets. Credit-card recognisers will ultimately displace these.

When you arrive home there is no need to get out to open the garage door. When you are within 10 m just press the button on your radio transmitter, shown in Fig. 9, and the door will open by remote control. (A licence is required to operate such transmitters.)

Electronics will even help you sell or buy your car. Private car owners in the London area can now market their cars by a computer service. Computacar's sales service, by Unilever Ltd, begins with the owner registering the car for sale. The data are filed in a computer data bank that updates daily until the vehicle is cleared. Buyers have access to a sorted list of the desired car characteristics, thus saving all that hunting through the massive lists of cars offered in published weeklies.

Future Drive

Without a doubt the car of the very near future will be bristling with more and more electronic devices, but, to date, no one car has all the features mentioned in this review.

As many additions are marketed independently of the car maker, it is likely that the overall reliability may fall along with the standard of low-priced expert servicing. Somewhere there will be a trade-off point between complexity of operation, servicing, cost and the benefits gained. Just where this will be will only be found as a result of practical use.

E11

MEMORY I.C.s								
1702A	EPROM	775p	MPF102_3	2N2906	A 22p	DIODES	BRIDGE	
2102-2	RAM	160p	40p	2N2907	A 22p	BY 27	RECTIFIERS	
2112-2	RAM	300p	40p	2N2926B	R 9p	DA47	IA	50V 25p
2708	RAM	£27	MPSA03_6	2N3053	11p	DA81	IA	100V 27p
8080A	CPU	£11	MPSA56_6	2N3054	6.5p	AB45	IA	400V 31p
AV5-1013	UART	600p	MPSU03_7	2N3055	6.5p	AO90	9p	50M 40p
AY5-2376	KB Enc	£13	MPSU05_7	2N3442	15p	AO91	9p	2A 100V 96p
RO3-2513	ROM	700p	MPSU05_8	2N3443	5.4p	AO95	9p	2A 200V 50p
LOW PROFILE DIL SOCKETS BY TEXAS			MPSU05_9	2N3644	5.4p	AO200	9p	3A 200V 70p
8 pin	12p	22 pin	O2C8	2N3702	3.14p	AO202	10p	3A 600V 80p
14 pin	13p	24 pin	O3C5	2N3704	5.14p	I N914	4p	4A 100V 96p
16 pin	14p	28 pin	O3C7	2N3706	7.14p	I N915	7p	4A 400V 96p
18 pin	30p	40 pin	R2008A_225	2N3708	9.14p	I N4003	4.7p	6A 50V 96p
TRANSISTORS	BF167	25p	R2010B_225	2N373.7	320p	I N4005	7.8p	108p
AC125	6.5 20p	BF170	25p	TIP29A	50p	I N4148	4p	6A 400V
AC127	8.20p	BF173	27p	TIP29C	50p	I N5401	3.15p	120p
AC176	2.20p	BF178	30p	TIP30A	60p	I N5404	7.20p	10A 400V
AC187	8.20p	BF179	35p	TIP30C	72p	ZENERS	2.7V-33V	270p
AD149	6.0p	BF180	135p	TIP31A	5.6p	2.7V-33V	400mW	432p
AD161	4.5p	BF184	524p	TIP31C	3.16p	1W	11p	
AD162	4.8p	BF194	13p	TIP32A	63p	2N4058	1.9p	
AF114	5.30p	BF195	11p	TIP32C	85p	2N4062	1.9p	
AF116	7.30p	BF196	17p	TIP33A	97p	2N4123	4.22p	
AF127	4.0p	BF197	19p	TIP33C	120p	2N4125	6.22p	
AF139	4.0p	BF200	40p	TIP34A	124p	2N4401	3.4p	
AF239	4.8p	BF243B	34p	TIP34C	160p	2N4427	9.7p	
BC107	B10p	BF256B	60p	TIP35A	243p	2N4871	6.0p	
BC108	B10p	BF257	34p	TIP35C	290p	2N5179	7.5p	
BC109	10p	BF258	39p	TIP36A	297p	2N5245	4.0p	
BC109	C11p	BF259	48p	TIP36C	360p	2N5295	5.8p	
BC117	27p	BF337	32p	TIP41A	70p	2N5401	6.2p	
BC144	9p	BF340	34p	TIP41C	84p	2N5457	8.40p	
BC148	8p	BF410	134p	TIP42A	76p	2N5459	4.0p	
BC151	11p	BF479	130p	TIP42C	96p	2N5485	4.5p	
BC158	9.13p	BF480	134p	TIP2955	75p	2N6107	7.0p	
BC169	1.65p	BF488	37p	TIP3055	60p	2N6027	6.0p	
BC172	11p	BFW10	0.0p	TIS-3	40p	2N6247	200p	
BC177	20p	BF29	30p	2N597	25p	2N5254	140p	
BC178	17p	BFX30	34p	2N698	43p	2N6292	70p	
BC179	20p	BFX48A	5/50p	2N706	8.22p	3N128	9.0p	
BC182	3.12p	BFX8/6	7.30p	2N838	43p	3N140	9.7p	
BC184	1.4p	BFX88	30p	2N930	19p	3N141	9.0p	
BC187	32p	BFY50	22p	2N131	225p	3N187	1.14p	
BC212	14p	BFY51	22p	2N134	75p	3N201	1.20p	
BC213	12p	BFY52	22p	2N136	7.75p	40360	4.39p	
BC214	16p	BFY90	22p	2N171	22p	40361	2.43p	
BC461	40p	BRY39	48p	2N1883	102p	40411	3.25p	
BC478	32p	BXS19	20.20p	2N2102	60p	40594	9.0p	
BCY70	20p	MJE340	70p	2N2219	60.20p	40595	9.7p	
BCY71	24p	MJ841	175p	2N2229	22p	40635	6.0p	
BD131	2.65p	MJ491	216p	2N2232	22p	40636	14.0p	
BD135	6.54p	MJ501	250p	2N2369	15p	40673	9.0p	
BD139	5.6p	MJ2955	130p	2N2484	35p	40841	9.0p	
			2N2616	5.14p	40871	8.5p		

VAT inclusive prices — add 25p P&P — no other extras
Govt. Colleges etc Orders Accepted

**MAIL
ORDER
ONLY** Govt., Colleges etc Orders Accepted
TECHNOMATIC LTD.

TECHNOMATIC LTD

TECHNOMATIC

TECHNOMATIC LTD

TECHNOMATIC

TECHNOMATIC LTD.
T 1-21-221-4222

54 Sandhurst Road, London NW9

Telex: 922800

Digitized by srujanika@gmail.com

FREQUENCY SHIFTER

A useful device for squeezing a few extra dB out of most PA systems. Designed by our shifty project team.

ANYONE WHO HAS USED a microphone in public address work has come across problems with feedback. These are caused by the level of sound reaching the microphone from the speaker approaching or exceeding that from the person originating the sound. As the reflected sound approaches the level of the original signal, the sound becomes distorted or 'coloured', then audible ringing occurs and finally complete oscillation or howl-round occurs as the reflected sound exceeds the level of the original signal.

The most effective method of eliminating this problem in most cases is to use the correct location for the speakers and the correct choice of microphone.

However in certain environments the 'most effective use and selection of microphone/speakers does not help the problem of feedback. These are the halls and rooms which have little sound-absorbing material on the walls and are very 'live'. If a frequency response curve is drawn for such a room it will be found that there are many peaks and troughs, normally only 4 or 5 Hz apart, along with perhaps major resonances.

Solutions

There are various electronic devices which have been developed to deal with this problem, the main ones being the graphic equalizer, the variable notch filter and the frequency shifter. The first two (especially the notch filter) are ideal for eliminating major resonances. These however also alter the frequency response of the original sound. They can

also help if the offending 'echo' is actually a direct path and not dependent on the room (i.e. if the speakers are behind the microphone). The other method, frequency shifting, is described here.

With a frequency shifter the echo signal is of slightly different frequency on each path round the loop and cannot directly reinforce itself so that while on the first echo it may strike a room resonance the second time it will probably be in a null. This tends to even out the frequency response of the room and allows 5 to 8 dB higher levels to be used in the average room. Also the onset of howl-round is not as dramatic as with

the conventional system and the distortion which normally occurs below the howl-round level is not as noticeable. The system does not however do a great deal for howl-round not associated with room resonances.

Only a small shift is normally required and it does not matter if it is an increase or a decrease. We chose to increase the frequency by about 5 Hz as it is easier to tell if a vocalist is flat rather than sharp. As the frequency response of the unit is good it is suitable for vocal work as well as general public address use. The frequency shift and the slight amplitude modulation cannot be detected by most people.

SPECIFICATION

Frequency shift	5Hz upwards
Maximum input voltage	3V
Frequency response	30Hz - 20kHz
+/- 3dB, -3dB	
Signal-to-noise ratio re 3V output	70dB
Distortion @ 1kHz, 2V out	0.25%
Amplitude modulation	100Hz - 10kHz < 1dB
Phase shift network 50Hz - 20kHz	90° ± 5°

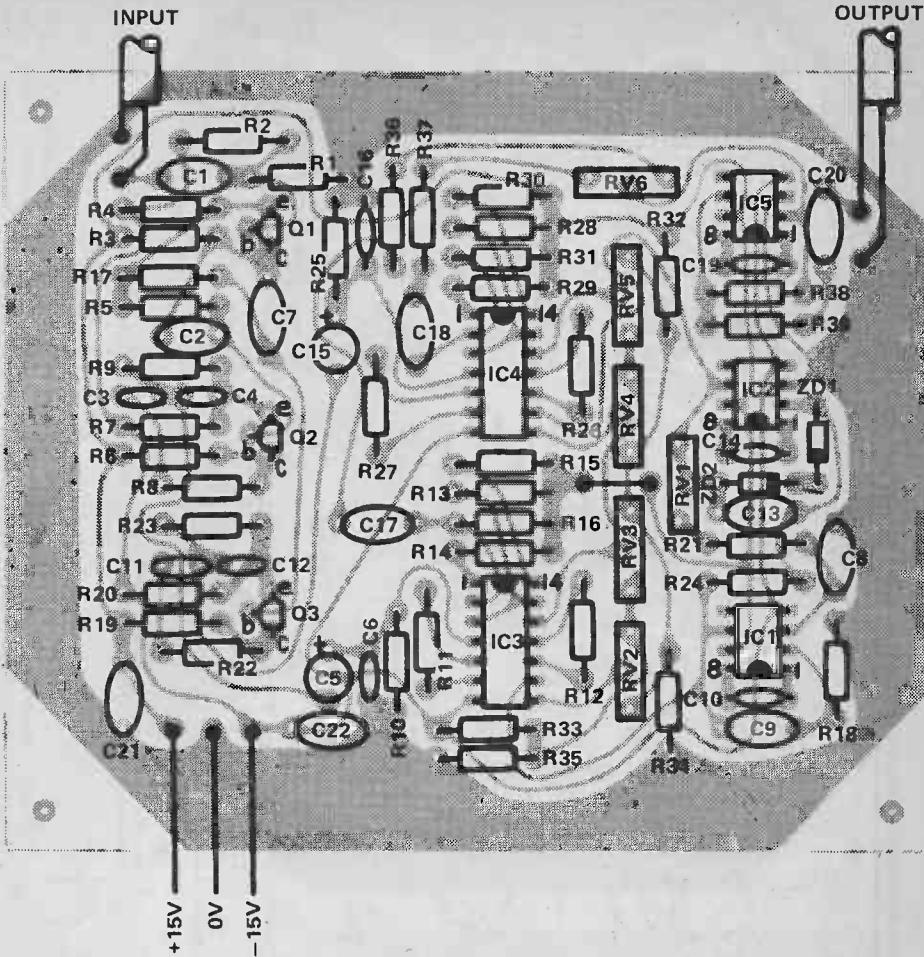


Figure 1. component positioning for the frequency shifter board.

Alignment

Equipment needed — a sensitive AC voltmeter (100 mV or less) or preferably an oscilloscope and an audio oscillator.


1. Check the output of the 5 Hz oscillator and adjust RV1 until it stops. If it cannot be completely stopped, try a link across C9.
2. Apply a signal of about 1 — 2 V amplitude at about 1 kHz to the input and measure the output of IC3 at pin 2. (If your meter does not reject DC, measure at the junction of C17 and R36). Adjust RV3 to give the minimum output.
3. Measure the output of IC4, pin 2 (or the junction of C18 and R37) and adjust RV5 for minimum output.
4. Measure the output of the 5 Hz oscillator on pin 6 of IC1 and adjust RV1 until it starts, then adjust to give about 1.25 V RMS.
5. With no input signal, measure the output of IC3 (or the junction...) and adjust RV2 for minimum output.
6. Measure the output of IC4 (or...) and adjust RV4 for minimum output.
7. If an oscilloscope is available, monitor the output with a 1 — 2 V input signal and adjust RV6 to give the minimum amplitude modulation. Alternatively, by using an amplifier and speaker, RV5 can be adjusted by ear. The unit is now set up.



PARTS LIST

Resistors	all 1/4W 5%	Capacitors	
R1	150k	C1	100n polyester
R2*	100k	C2	56n polyester
R3,4	2k7	C3	6n8 polyester
*R5	32k	C4	1n0 polyester
R6,7	2k7	C5	10u 25V electro
*R8	3k6	C6	1n5 polyester
*R9	24k	C7	100n polyester
*R10	15k	C8,9	100n polyester
R11	4k7	C10	33p ceramic
R12	2k2	C11	22n polyester
R13	15k	C12	4n7 polyester
R14—R16	3k3	C13	100n polyester
*R17	56k	C14	33p ceramic
R18	330k	C15	10u 25V electro
R19,20	2k7	C16	5n6 polyester
R21	330k	C17,18	100n polyester
*R22	2k9	C19	33p ceramic
*R23	27k	C20—C22	100n polyester
R24	330k		
*R25	15k	Semiconductors	
R26	2k2	IC1,2	LM301A
R27	4k7	IC3,4	MC1455
R28	15k	IC5	LM301A
R29—R31	3k3	Q1—Q3	BC549
R32,33	10k	ZD1,2	5.1V 300mW
R34,35	1k		
R36,37	100k	Miscellaneous	
R38	1M	PC board	
R39	100k	Power supply ± 15V, 40mA	
Potentiometers		*For best results the components should be as accurate as possible; preferably 1% tolerance or selected to be within 1%.	
RV1	250k trim		
RV2—RV5	25k trim		
RV6	100k trim		

PROJECT: Freq. Shifter

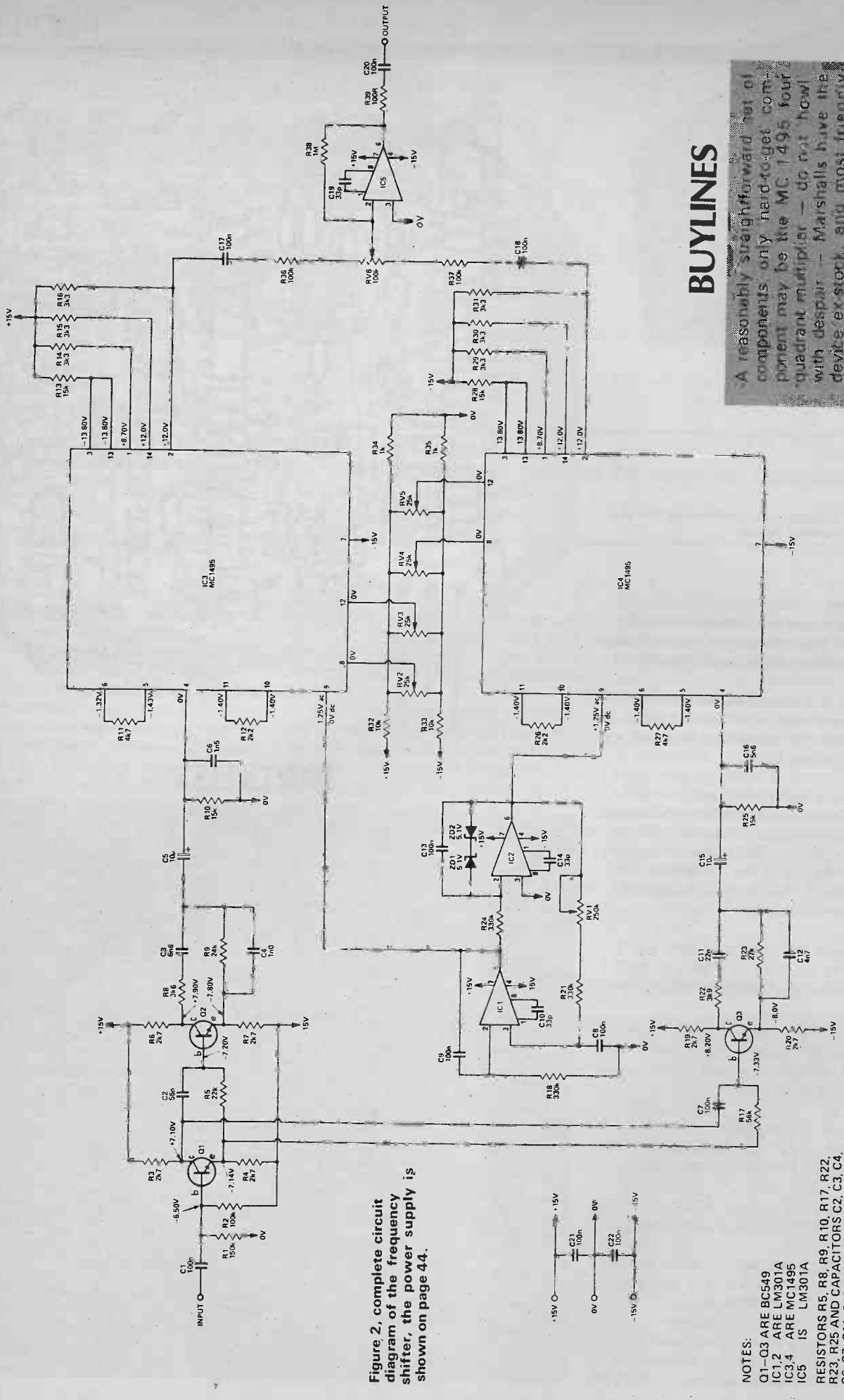

BUYLINES

A reasonably straightforward set of components may be had at component may be the MC 1495 four quadrant multiplier — if not how with despair — Marshalls have the device in stock, and most friendly component stores should be able to supply it to order PCBs from the usual suppliers.

NOTES:
 Q1-Q3 ARE BC549
 IC1,2 ARE LM301A
 IC3,4 ARE MC1495
 IC5 IS LM301A
 RESISTORS R5, R8, R9, R10, R17, R22,
 R23, R25 AND CAPACITORS C2, C3, C4,
 C6, C7, C11, C12 AND C16 SHOULD BE
 1% TOLERANCE OR SELECTED TO BE
 WITHIN 1% FOR BEST RESULTS.
 VOLTAGES GIVEN ARE OF THE PROTO-
 TYPE AND SHOULD BE TYPICAL.

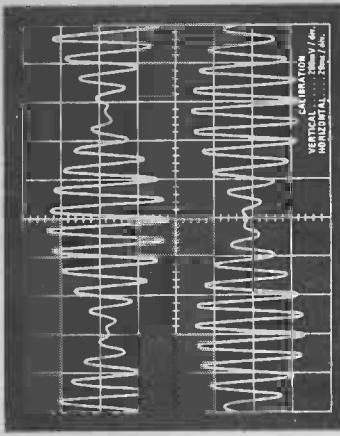


Fig. 3. Oscilloscope showing output of IC3 (upper) and IC4 (lower); signal is 100 Hz, note phase difference. Below, full size foil pattern for the shifter (120 x 100 mm).


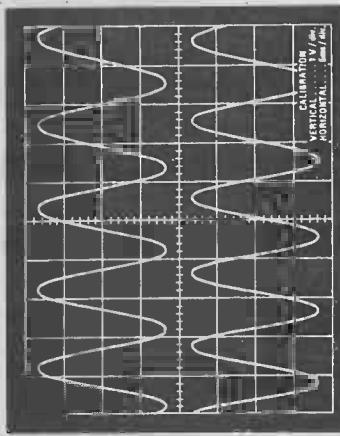
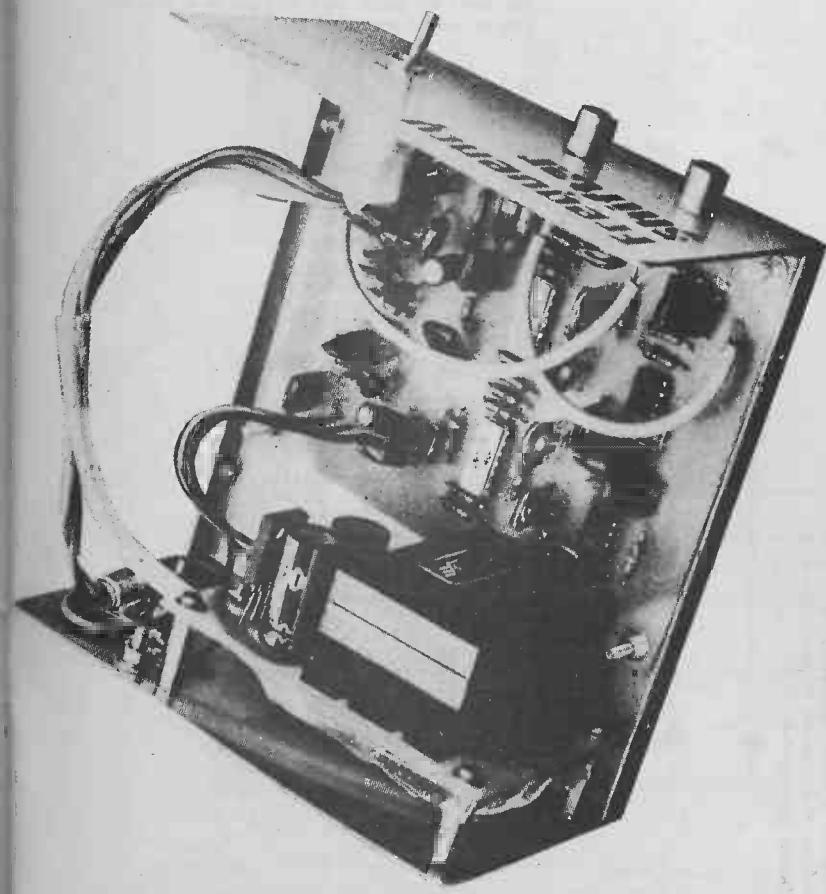


Fig. 3. Oscilloscope showing relationship between input (upper) and output (lower) signals — note change in frequency.

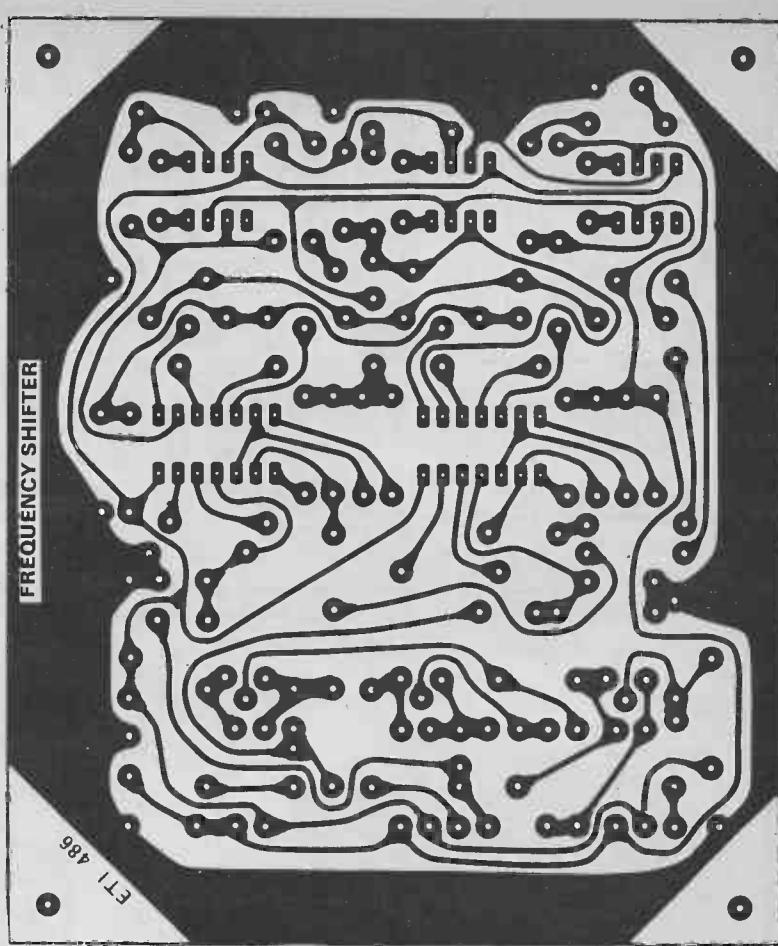

HOW IT WORKS

The audio input is split into two paths which provide a frequency related phase shift, as shown in Fig. 4. The amplitude however remains constant. Due to the different component values in the two networks the phase shift are not the same but differ by 90° at 20 frequencies (50 Hz, 20 kHz, 40 kHz, ...).

IC1 and IC2 form a quadrature sine wave oscillator with the frequency set by R18, R21, R24, C8, C9 and C10. A triangle voltage is provided by ZD1 and ZD2 along with RV1 (see adjustment section). The outputs from these two opamps are the base amplitude for 90% of those shifted. We now multiply one of the audio signals by one of the 50 Hz outputs, at the second node in Fig. 4, the second 5 Hz signal. When we multiply 100 waveforms together the output consists of the sum of the two frequencies and their difference.

This means that if the audio signal is 100 Hz the output will contain a 95 Hz signal and a 105 Hz signal. These will beat with each other to produce a 104 Hz beat note as shown in Fig. 4. Due to the phase shift between the inputs of the multipliers the 105 Hz components of the outputs are in phase while the 95 Hz components are 180° out of phase. They are by adding the outputs of the two multipliers in C5 the 95 Hz components cancel out leaving only the 105 Hz signal. Provided the multiplier inputs have the 90° phase relationship there will always be a 5 Hz shift, independent of frequency.

Due to in inability to multiply exactly the 90° phase relationship, the 95 Hz, or twice selected, will act completely and have the result is a slight beat giving rise to an amplitude modulation effect (we talk about 1 dB). This is not a trivial noticeable on speech or music.

news digest.

RED TAPE GAGS THE QUEEN!

In the wee small hours of January 19th 1903, Marconi established the first two-way communication across the Atlantic. Messages were exchanged between the American president Theodore Roosevelt and the British King Edward VII. To mark the 75th anniversary of this event, the Cornish Radio Amateur Club have organised a team of sixty local amateurs to run GB3 MSA (Marconi's Seventy-fifth Anniversary). The station was run 24 hours a day, from the

14th to the 22nd January, from the lounge of the Poldhu Hotel in sunny Cornwall — only metres away from the spot Marconi used.

Transmitting on 80m, 20m and 2m the team had already made 1 100 contacts in 51 countries when ETI contacted them on the 16th! All the equipment was owned by the club and its members and set up for the week specially. On the American side was another station, KM1 CC, based in Cape Cod. KM1 CC was run by

the local Barnstaple, Mass. radio club with the help of the Radio Club of America.

Now for the red tape... President Carter sent a message via KM1 CC and the Queen wanted to send a reply via GB3 MSA, just like Edward VII did back in 1903. The Home Office said that if she did, it would break a condition in all British amateurs' licences — namely the one about not passing on messages from 3rd parties! So after 2 years preparation the Cornish Amateurs and the Queen were denied permission to reply to President Carter.

Bureaucracy reigns??

now you see it

Following the tremendous success of the 'Light Fantastic' Exhibition in 1977, the Royal Academy of Arts is staging 'Light Fantastic 2' — this time sponsored by Guinness.

Since the first exhibition there have been several innovations in Holographic technique, at long last the public can see 3-dimensional semi-nude dancing ladies — frozen

in mid-air. Other new techniques include experimental 'Head Up Displays' for supersonic aircraft, and multiple exposure Holograms.

Running from 12th January for three months Light Fantastic 2 gives you another chance to see Holograms in real life.

Royal Academy of Arts, Piccadilly, London. W1V 0DS.

the little cb that santa forgot

Citizen Band radio manufacturers around the world are crying into their transceivers after Xmas. They expected a boost to sales to revive their drooping business, and it didn't materialise. Seems no-one wanted to contact anyone else — not even the reindeer.

chrysler lit up

HP have signed a \$400,000 contract to supply Chrysler with LED lamps and displays for this years car ranges. They are to go into digital radios (?) fitted to some prestige models. Twinkle Twinkle little car...?

sounds boxy

the new 36 24 36



This gentlemen is the replacement for all those nubile 'Miss Jones's' cavorting in slinky fashion around the offices in Britain. A right gang of spoilsports called Optimisation intend to replace all of that with all of this. Called the Mind Reader (it's a good job Miss Jones's weren't mind readers) the box is basically a memory system combined with stop watch, calendar and clock. Information and 'things to do' can be filed away under each day with the machine dutifully displaying the required information on the required day.



The keyboard is touch operated it is 10½ by 7½ by 4½ — not a patch on 36-24-36 — it weighs nine pounds and sells for around £300.

Optimisation, 45 South Street, Bishops Stortford, Hertfordshire. P.S. I bet it makes lousy tea and looks terrible in a bikini . . .

The biggest problem with building things is still finding something to build things in. Whenever we hear of a new box (and there aren't all that many are there?) we endeavour to let you know.

This offering caught our attention whilst meandering around Metac in Edgware Road. Constructed in one piece of 3mm thick aluminium, with wooden (REAL!) end-pieces the box has a 75mm by 25mm cut out in the front panel for displays etc, and three pre-punched holes in the box for switches and one for a mains lead. Overall measurements are approx. 120mm x 50mm x 80mm (or four and three quarters by two by three and a quarter if you haven't yet let go of the Empire!) Price is £2.80 all inc. from Metac, 327 Edgware Road, London W2.


PROJECT: Freq. Shifter

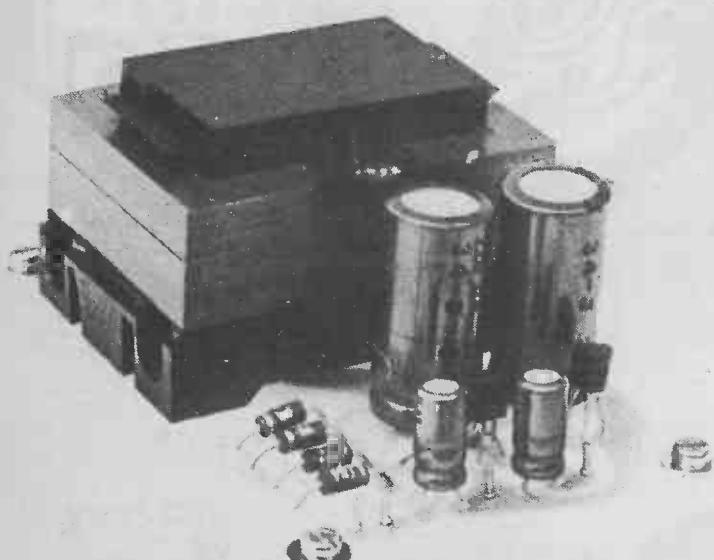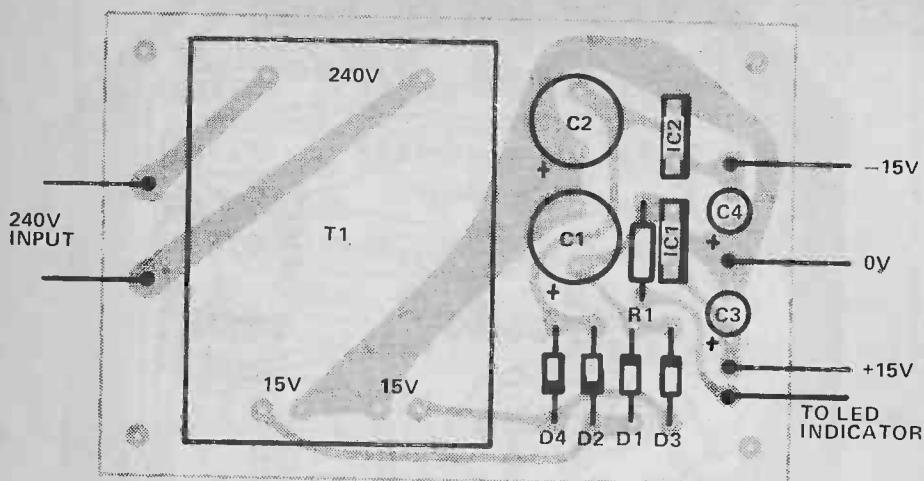

Circuit diagram for suitable power supply, in the prototype the option of LED1 was not used. Note that this power supply can be used by itself and in fact is a useful project in its own right.

PARTS LIST

R1 C1,2 C3,4	Resistor Capacitor	21.2 3W 0% 470 μ 35V 100 25 V
D1-D4 LED1	Diodes Indicator	1N4001
IC1 IC2	Regulator	7815 7915
T1	240V: 15V 0-15V	

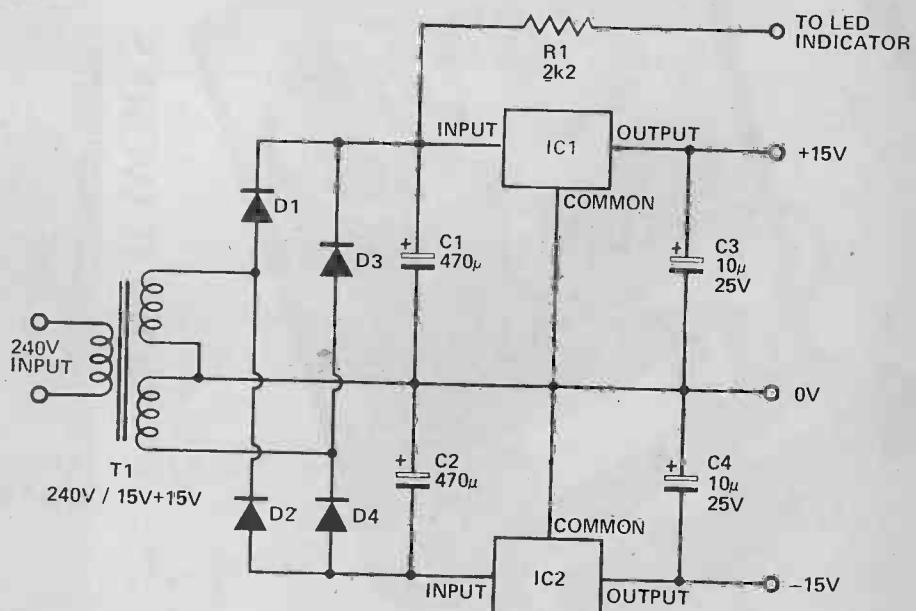



OP AMPS

PART 2

In the first part of this series Tim Orr discussed the theory and operation of op-amps. This month he moves on to give some circuit applications for this ubiquitous device, and explains how and why it can do what it does!

Single Op Amp Oscillator

This circuit has a Schmitt trigger and a 'sort of integrator' all built around one op-amp. The positive feedback is via the 10k resistors. The 'integration', or rather, the timing, is controlled by the RC network. The voltage at the inverting input follows that of the RC charging exponential, except that it is confined to be within the upper and lower hysteresis levels. Thus the hysteresis levels and the RC time constant determine the frequency of the operation. It is possible to make the output square wave have a large mark to space ratio. By closing the switch SW1, the discharge time of the capacitor becomes eleven times faster than the rise time. Thus a square wave with an 11:1 mark space ratio is generated.

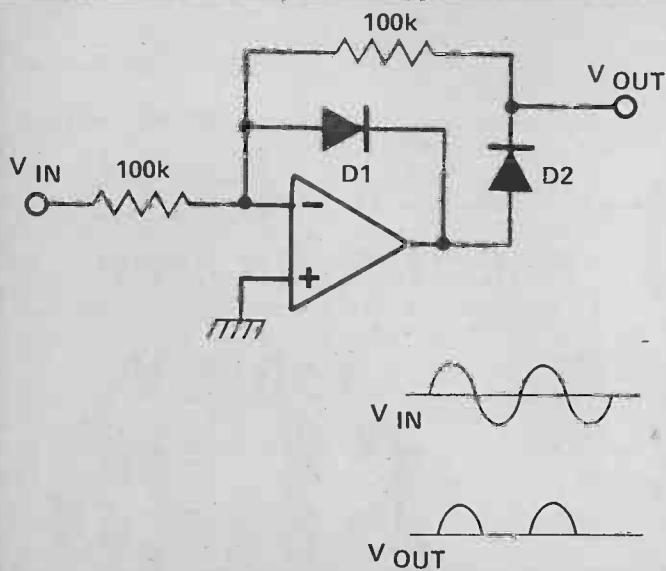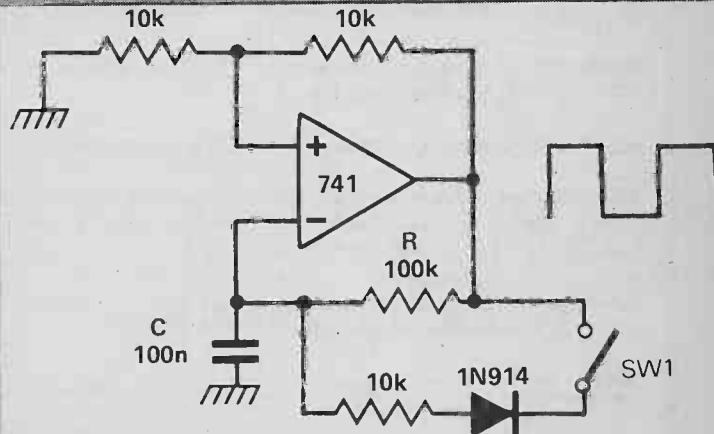



Precision Half Wave Rectifier

Rectifying small signals with any accuracy can be very difficult with just diodes due to their forward voltage drop of about 0.6 V. However, an op-amp can be used to reduce this voltage drop to apparently nothing! Consider the circuit shown. There is negative feedback so that 'virtual earth' circumstances exist. When V_{IN} is positive, D1 conducts to maintain the virtual earth, D2 is reverse biased and so the output is just a 100k resistor connected to 0 V. When V_{IN} goes negative, the output rises positively, D2 is turned on and D1 turned off. As the virtual earth is being maintained, the output voltage is the exact inverse of the input voltage. This is true for all negative inputs. Therefore, the output is composed of positive going half sinewaves. A precision half wave rectification has occurred. In fact the diode error is very small, being equal to

600 mV
(surplus voltage gain)

Therefore as the input frequency increases, and the surplus voltage gain decreases, the amount of precision also falls.

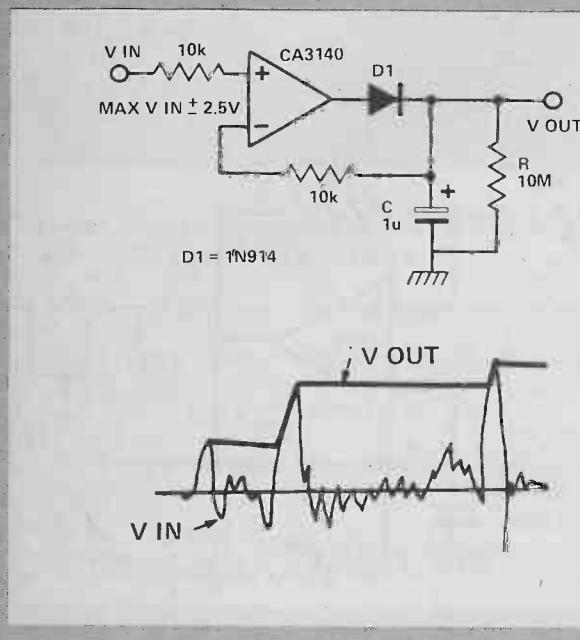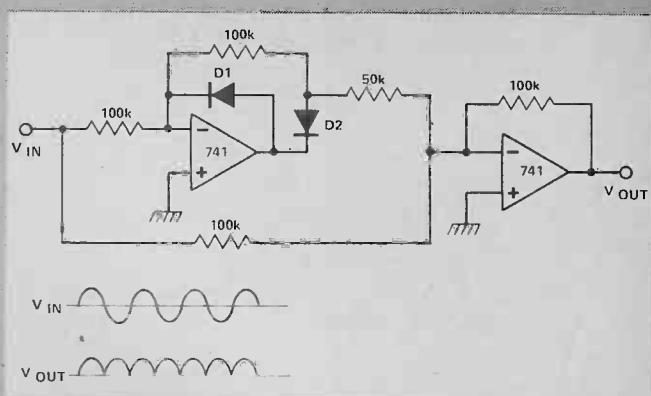By adding the original and the half wave rectified signals together in the right ratio, it is possible to fill in the half cycle gaps and thus to generate a precise full wave rectification. The addition of one summing op-amp and three resistors is all that is needed as shown opposite.




Precision Peak Voltage Detector with a Long Memory Time

The circuit shown has negative feedback only for positive signals. That is, the inverting input can only get some feedback when diode D1 is forward biased and this can only occur when the input is positive. When a positive input signal is applied the output of the op-amp rises until the inverting input reaches the same potential. In so doing, the capacitor C is also charged to this potential. When the input goes negative, the diode D1 becomes reverse biased and so the voltage on the capacitor remains there, being slowly discharged by the op-amp input bias current and the resistor R (10M). The op-amp used has a MOS FET input, having an exceptionally low input bias current of 10 pico amps. Thus the discharge of the capacitor is dominantly controlled by the resistor R, giving a time constant of ten seconds. Thus the circuit detects the most positive peak voltage and remembers it.



Led Bar PPM Display for Audio

The peak voltage detector can be used to control an illuminated audio level monitor displaying the same characteristics as a PPM (Peak Programme Meter). A bar column of LEDs is arranged so that as the audio signal level increases, more LEDs in the column light up. The LEDs are arranged vertically in 6 dB steps. A fast response time and a one second decay time has been chosen so as to give an accurate response to transients and a low 'flicker' decay characteristic. The op-amps that drive the LEDs are being used as comparators. On each of their inverting inputs they have a DC reference voltage, which increases in 6 dB steps up the chain. All of their non-inverting inputs are tied together and connected to the positive peak envelope of the audio signal. Thus as this envelope exceeds a particular voltage reference, that op-amp output goes high and the LED lights up. Also, all the LEDs below this are illuminated.

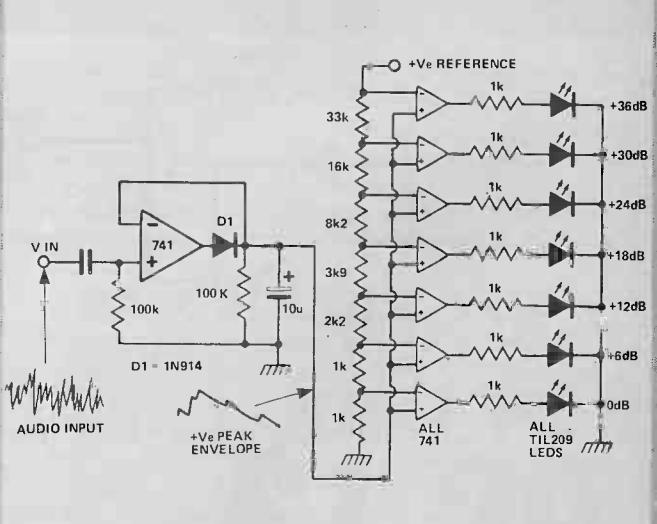

Basic Summing Circuit (Mixer)

A virtual earth amplifier can be used to mix several signals together. The output voltage is a mixture of all the inputs. The amount of an input that appears at the output is inversely proportional to the input resistor. If the input voltages are fed into potentiometers before being fed to the mixer, then their individual levels can be manually adjusted. This is the basis of most audio mixers, although only the cheaper units use op-amps. Most op-amp mixers will degrade the signal to noise ratio of the signals by more than a good discrete component amplifier.

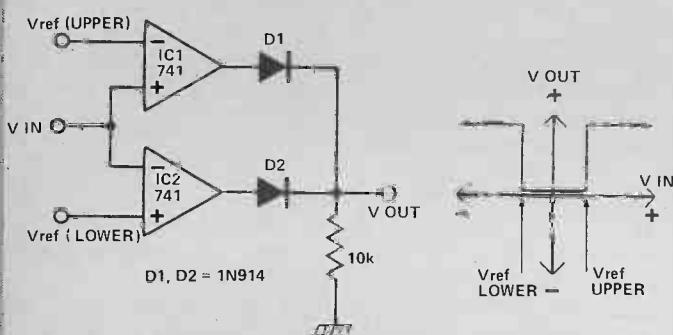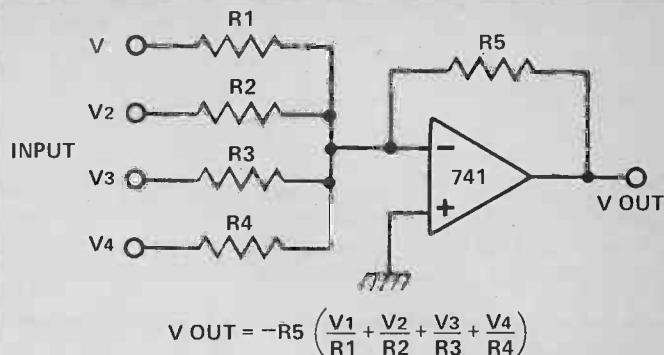


Window Comparator


A window comparator gives an output which in this case is 0 V, when an input voltage lies in between two specified voltages. When it is outside this 'window', the output is positive. The two op-amps are used as voltage comparators. When V_{IN} is more positive than V_{ref} (upper) the output of IC1 is positive and D1 is forward biased. Otherwise the output is negative, D1 reverse biased and hence V_{OUT} is 0 V. Similarly, when V_{IN} is more negative than V_{ref} (lower), the output of IC2 is positive; D2 is forward biased and thus V_{OUT} is positive. Otherwise V_{OUT} is 0 V. Thus only when V_{IN} lies within the window set by the reference voltages is V_{OUT} 0 V.

High Performance Sample and Hold

It is often necessary to have a circuit that will sample an analogue voltage and then remember it for a long time without any significant corruption of that voltage. This is known as a sample and hold circuit and one use of it is to store the voltage from the keyboard connected to an electronic music synthesiser. The voltage is then used to control the pitch of a voltage controlled oscillator and so it is very important to have a high performance sample and hold. A drift of less than one semitone, (80 mV), in ten minutes is required. A sample and hold is simply an electronic switch, a storage capacitor and a high input impedance voltage follower. In the circuit shown, when switch SW1 is positive the FET is turned on, and has a resistance of about 400R. Thus the input voltage charges up the capacitor through the FET. When SW1 is negative, the FET is turned off, (pinched off), and can have a resistance of thousands of Megohms. To get a long storage time the op-amp must have a very low input bias current. For the CA3140, this current is about 10 pico amps, i.e., 10⁻¹¹ amps. Therefore the rate at which the capacitor will be discharged by this current can be worked out from the equation, C(dV/dt) = i

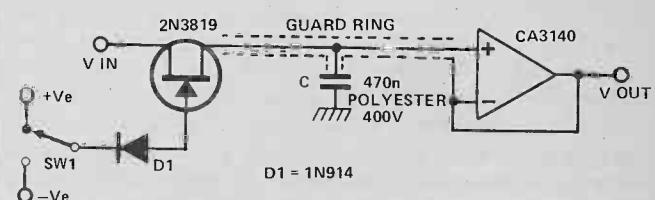

PRINTED CIRCUIT BOARD LAYOUT

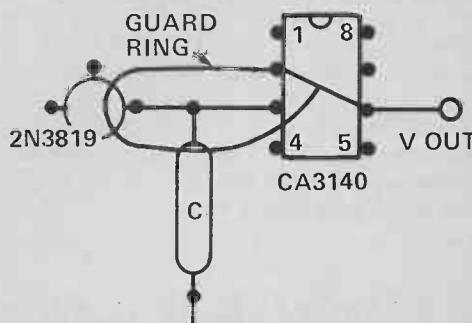

where $\frac{dv}{dt}$ is the rate of change of voltage on the capacitor.
Therefore:


$$\frac{dv}{dt} = \frac{i}{C} = \frac{10^{-11}}{0.47 \times 10^{-6}} = 22 \mu\text{V/s}$$

This is a very low drift rate, much better than we need. However, the actual drift rate will probably be in excess of this, due to surface leakage on the printed circuit board, leakage through the FET, and internal leakage in

the capacitor. It is advisable to use a high voltage, non-polarised capacitor in this circuit to keep the leakage currents to a minimum. Also, to stop surface leakage a simple PCB trick can be used, that of making a guard ring around the sensitive components.

Normally any potential stored on the capacitor may leak to ground across the surface of the PCB, but if we make the surrounding surface a conducting track held at the same potential as that of the capacitor then the potential difference is virtually always zero, and hence the surface leakage is greatly reduced.

Linear Voltage Controlled Oscillator

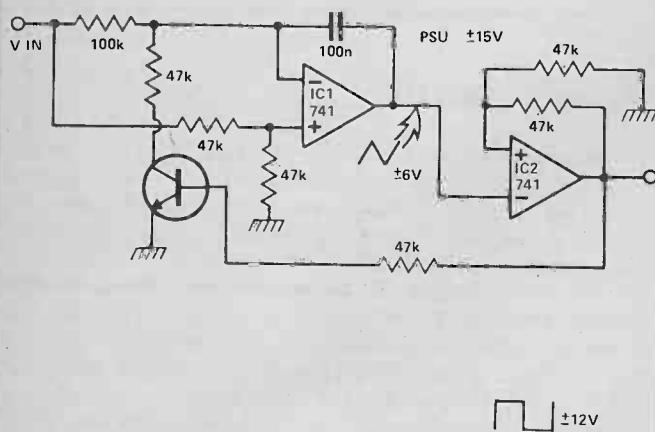


This oscillator is very similar to the triangle square wave oscillator shown in Part 1, except that this one is voltage controlled. The integrator and Schmitt trigger action are the same as before, but the feedback has been altered. The input voltage V_{IN} is applied differentially to the integrator via the resistor network. The larger the value of V_{IN} , the faster the integrator ramps up and down. Thus the frequency of the operation is determined by an external positive control voltage. The frequency is linearly proportional to this control voltage.

When the output of the Schmitt is low, Q1 is off and so all the input voltage is applied to the inverting input. Half of the input voltage is always applied to the non-inverting input. Therefore the integrator's output ramps downward until the Schmitt flips into its positive state. Now, Q1 is switched on and the voltage at the inverting input is negative with respect to the non-inverting input. Hence the integrator now ramps upwards.

Silent Audio Switching

Sometimes electronic switches for audio signals are required. FETs can be used to perform the switching, but they can cause distortion, the resultant output impedance is not very low and clicks generated by the switching signal can break through. The circuit shown virtually eliminates all of these problems. By using an op-amp a very low output impedance is obtained as well as the possibility of selecting or mixing one or more of many input channels. Because of the virtual earth mixing, the voltage across any FET that is switched on is very small. If the input voltage is 1V and the FETs ON resistance is 470R, then the voltage across the FET is about 10 mV. When large voltages are applied to a turned on FET, the distortion is large, but if the voltage is small, (10 mV say), the distortion could be less than 0.1%. Thus the virtual earth mixing enables low distortion operation. Lastly, to stop the generation of switching clicks, a time constant of 47 msec has been enforced at the gate of the FETs.

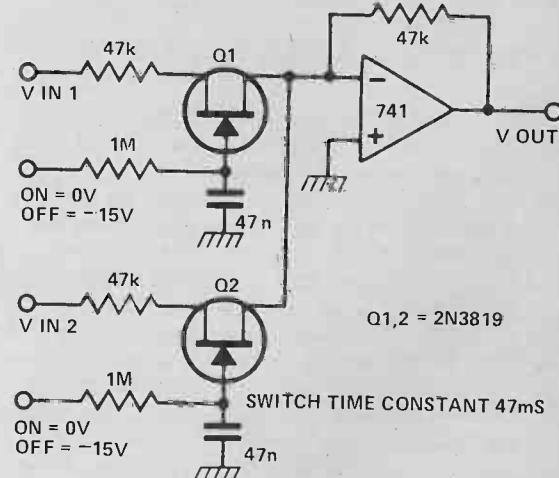

To be continued. Next month sees circuits for exponential voltage to current convertors, musical chime generators, triangle to square wave convertors, squarewave generators with auto level adjustment and variable mark-space ratio — amongst other things.

DATA SHEET

ICL 7106/7107 INTELSIL

DIGITAL PANEL METER

THE ICL7106 and 7107 are high performance, low power, CMOS 3½ digit A/D converters that contain all the necessary active devices on a single monolithic IC. Each has parallel seven-segment outputs which are ideal for use in a digital panel meter. The ICL7106 will directly drive a liquid crystal display including the backplane drive. The ICL7107 will directly drive instrument size LEDs without buffering. With seven passive components, display and power supply, the system forms a complete digital voltmeter with automatic zero connection and polarity. (see figs. 1 and 3).

Both ICs use the time-proven dual slope integration technique with all its advantages, i.e. non-critical components, high noise rejection, non-critical clock frequency and almost perfect differential linearity. Both the ICL7106 and 7107 can be used not only with its internal reference, but true ratiometric reading applications may also be accomplished over a full scale input range of 199.9 mV to 1.999 V.

The accuracy of conversion is guaranteed to plus or minus 1 count over the entire plus or minus 2000 counts and the auto-zero facility provides a guaranteed zero reading for 0 volts input. However, the chip does provide a true polarity output at low voltages for null detection. Both chips have an on-board clock and reference circuitry, as well as overrange detection.

The Clock

The chip carries the active parts of an RC oscillator which runs at about 48 kHz and is divided by 4 for use as the system clock. The integration period (1000 clock pulses) is therefore 83.3 ms. Each conversion requires 4,000 clock pulses, i.e. 3 readings per second. For optimum 50 Hz line frequency rejection, the clock should be set to a multiple of 50 Hz, e.g. 50 kHz.

Fig. 4. Pinouts

(+) SUPPLY	1	40	OSC. 1
D (UNITS)	2	39	OSC. 2
C (UNITS)	3	38	OSC. 3
B (UNITS)	4	37	TEST
A (UNITS)	5	36	+ REF.
F (UNITS)	6	35	- REF.
G (UNITS)	7	34	+ REF. CAP.
E (UNITS)	8	33	- REF. CAP.
D (TENS)	9	32	COMMON
C (TENS)	10	31	INPUT HI
B (TENS)	11	30	INPUT LO
A (TENS)	12	29	AUTO-ZERO
F (TENS)	13	28	BUFFER
E (TENS)	14	27	INTEGRATOR
D (100's)	15	26	(-) SUPPLY
B (100's)	16	25	G (TENS)
F (100's)	17	24	C (100's)
E (100's)	18	23	A (100's)
D (1000)	19	22	G (100's)
POLARITY (MINUS)	20	21	BACKPLANE/DIGITAL GND (7107)

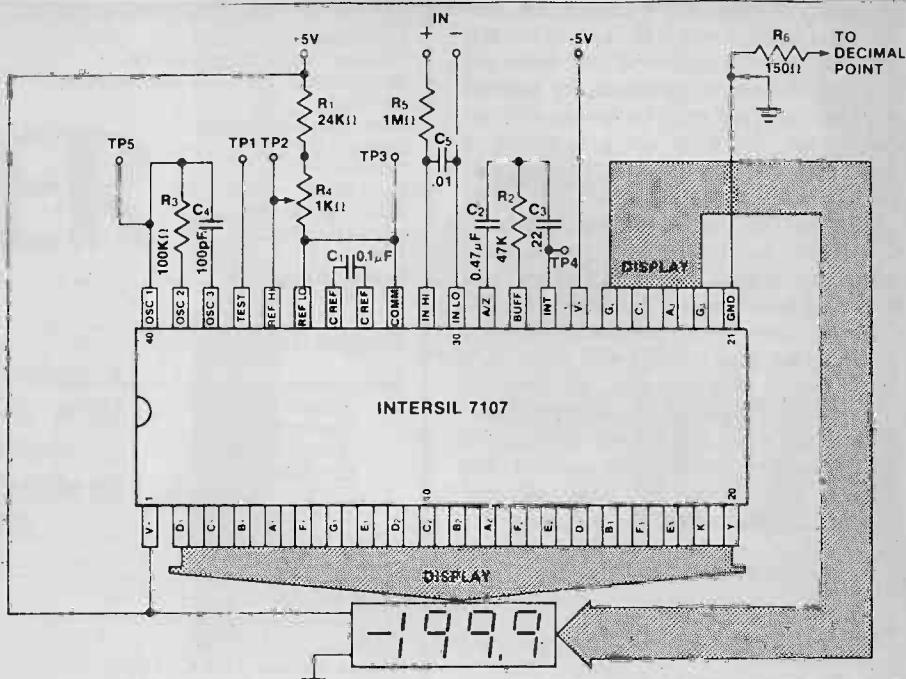


Fig. 1 LED Digital Panel Meter using ICL 7107

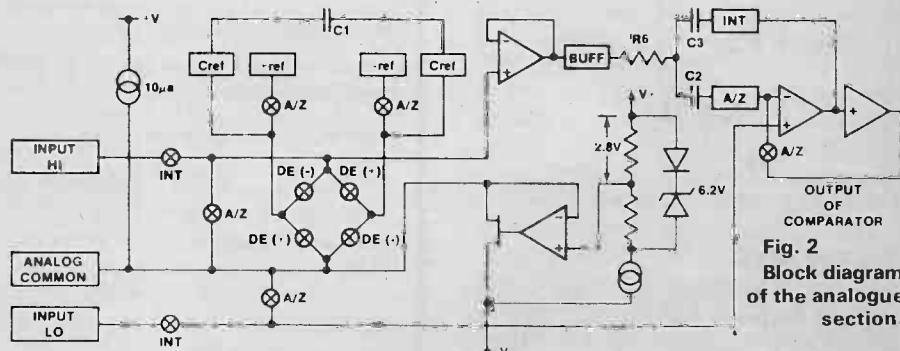


Fig. 2
Block diagram
of the analogue
section.


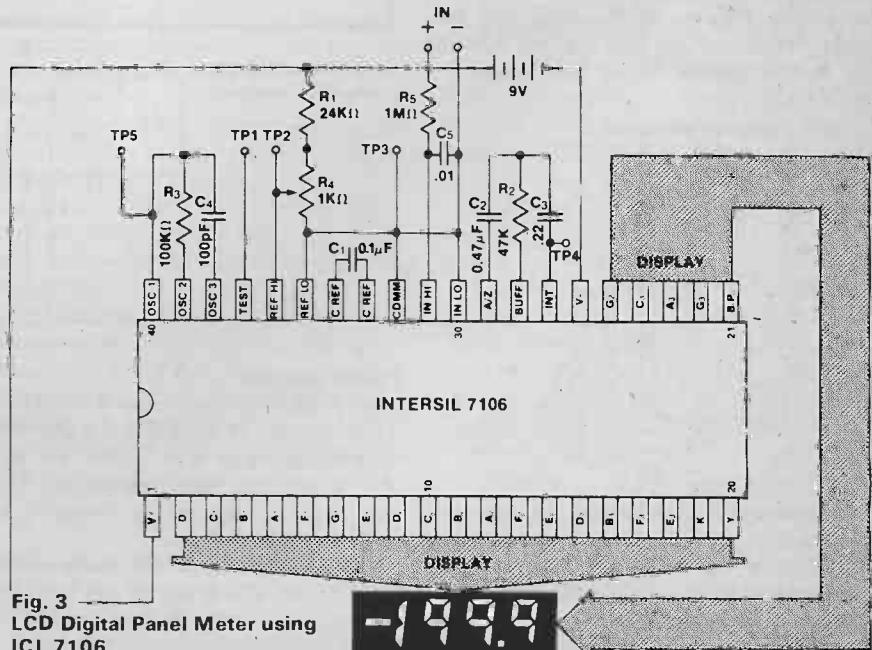


Fig. 3
LCD Digital Panel Meter using
ICL 7106

Displays and DPs

The additional components required to build a DPM are a display (either LCD or LED), 4 resistors, 4 capacitors, and an input filter if required. Liquid crystal displays become polarised and damaged if a DC voltage is continuously applied to them, so they must be driven with an AC signal. To turn on a segment, a waveform 180 degrees out of phase with the backplane drive (but of equal amplitude) is applied to that segment. The 7106 generates the segment drive waveform for all digits internally, but does not generate segment drive for the decimal point. This must be done using an inverter or exclusive-OR logic (see fig. 5 below). For use with LED displays the 7107 pull-down FETs will sink about 8 mA per segment, which produces a bright display suitable for almost any indoor application. A fixed decimal point can be turned on by tying the appropriate cathode to ground through a 150 ohm resistor.


Fig. 5. LCD inverter

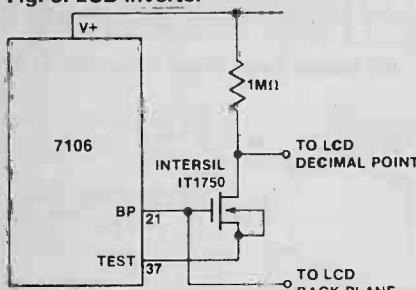

The Reference

For 200.0 mV full scale, the voltage applied between REF Hi and REF Lo should be set at 100.0 mV. For 2.000 V full scale, this should be 1.000 V. The reference inputs are floating, and the only restriction on the applied voltage is that it should lie in the range V- to V+.

Fig. 6. External reference

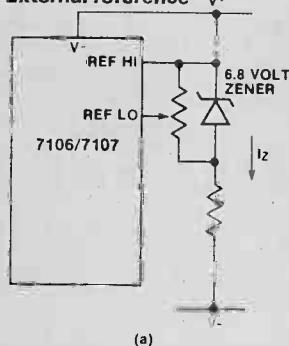


For many applications, the internal reference of 2.8 V between V+ and COMMON is adequate, but power dissipation in the 7107 LED version can wreck this. However, an external reference can be added as shown in Fig. 6.

Electrical Specifications @ +25°C unless otherwise specified

Full Scale Voltage Range	±200mV (5.0V min V+ to V-), ±2.0V (6.0V min V+ to V-)
Full Scale Digital Range	±2.000 Counts
Common Mode Voltage Range	V+ minus 0.5V to V-, plus 1V
Accuracy 10°C to 50°C with external reference	<1/2 Count
Noise referred to Input	15µV typical
Zero width	0-1 transition at .7 to .9 counts
Turnover	<1 Count
Input circuit	Differential
Input Bias Current	2pA
Input Impedance	>10 ¹² ohm
Polarity	Automatic with neg sign displayed
Reference (Internal)	Internal 2.8V, referenced to V+
Reference (External)	Temperature Coefficient 100ppm/°C typical.
Recommended External Components	External reference must be in the range V+ to V-
200mV Full Scale	2V Full Scale
C ₁ =Int Cap 220n	C ₃ =Int Cap 220n
C ₂ =AZ Cap 47n	C ₂ =AZ Cap 47n
C ₁ =Ref Cap 100n	C ₁ =Ref Cap 100n
C ₄ =Clock Cap 100p	C ₄ =Clock Cap 100p
R ₆ =Int Res 47k	R ₆ =Int Res 470k
R ₃ =Clock Res 100k	R ₃ =Clock Res 100k
R ₂ =Short	R ₂ =Short
Clock Frequency	48kHz divided by 4
Display Outputs (LED ICL7107)	An internal divide by 4 counter is provided to count external oscillators down to 12kHz, the internal dual slope clock.
Display Outputs (LCD ICL7106)	22 Current limited segment drives plus one current limited neg sign drive plus LED common
LED (7107) current @ +5.0V	Note: The 2 die in the 1k bit are in parallel
Power Requirements	22 segment drives plus one neg sign drive plus LCD back plane drive
Power supply configuration (7107)	5.5 to 8.0mA
Digital input Signals (7106)	LCD: Ima @ 4.5 - 6V
Read Rate	LED: 1ma @ 4.5 - 6V, plus LED current Dual
	+4.5 to +6V and -3 to -6V @ 1mA
	Note: for inputs that remain within the CM voltage range only a single supply is required
	Test
	Single 5 to 12V
	A high on the test input turns on all segments and the minus sign.
	3 Readings per second with 12kHz internal clock (48kHz external clock).
	Accurate from .1 to 15 reading per second.

Fig. 7. Deriving a negative supply

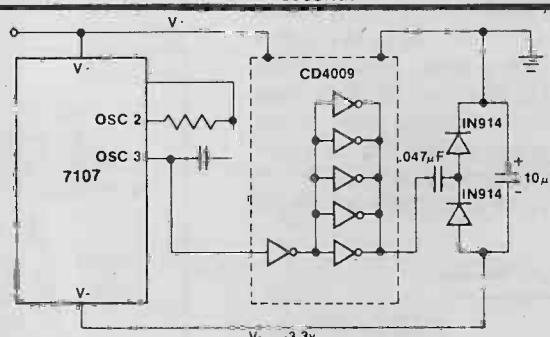

Power Supplies

The 7106 will run from a single 5 to 12 V supply. If INPUT Lo is shorted to COMMON, this will cause V+ to sit 2.8 V positive with respect to INPUT Lo, and V- at 6.2 V negative with respect to INPUT Lo.

The 7107 requires dual supplies, +4.5 to +6 V and -3 to -6 V at 1 mA. A negative supply may be derived from +5 V using the circuit given in Fig. 7.

Evaluation kits for the 7106 and 7107 are available from Rapid Recall, 9 Betterton Street, Drury Lane, London WC2H 9BS. The kits are supplied with full data sheets and an application note, further Intersil application notes are also available on request:

The individual devices are becoming widely available, sources known to ETI include, Audio Electronics, Doram, Marsha's and Watford Electronics.

ETI

LIGHT DIMMER

A versatile design that provides a high quality light dimmer and, with the addition of a simple interface, a building block that forms the basis of many other light effect circuits.



THE DIGITAL LIGHT bulb has been with us for a few years now. What's a digital light bulb you ask — well in case you don't recognise the term it's just a clever, well if not clever, at least obscure, way of describing the common domestic light bulb we all know and love. These bulbs may just about be described as digital as, essentially, they are either on or off — we said we were being obscure and we were not joking.

Light Fantastic

Now this two state nature of the bulb ordinaire can be rather dull, however, the application of electronics makes a number of more interesting things possible. We can, for instance, vary a bulb's brightness smoothly from almost nothing to full output, sequence a number of lights according to a prearranged pattern, turn bulbs on and off in time with music and you can probably think of many other things in this vein. The circuit described here, although presented primarily as a light dimmer, can form the basis of many of these other systems.

Bright Idea

While it would be possible to control the brightness of a lamp by placing a variable resistor of a large power rating in series with same, this type of control would have a number of serious disadvantages, not the

least of which is the large amount of heat that would be generated. The use of phase control provides a means of accomplishing the desired effect that is both simple and efficient.

A Passing Phase

Phase control means simply that power is supplied to the load, in this case a lamp, for only part of each AC cycle. Usually phase control circuits are referred to as "zero crossing" of the AC supply and power is supplied to the load at some time after this point continuing then until the next zero crossing. In this way the energy supplied (light output) can be controlled.

Many domestic controllers use a circuit similar to that shown in Fig. 1. This consists of a simple phase control network with a diac to "fire" the triac that controls the load. We have chosen to use a different type of circuit (Fig. 2) that we feel gives a better and more reliable control. The triac is retained but the triggering circuitry is quite different, consisting as it does of a PUT (Programmable Unijunction Transistor) in a phase control network with triggering of the triac being accomplished by a pulse transformer.

As this unit is intended to form the basic building block of a number of different systems we have chosen not to mount the potentiometer RV1 directly onto the PCB as would have

been the case if this were simply a light dimmer. Instead the pot is connected via flying leads to the PCB as shown in our photos. This leads (please pardon the pun — we cannot resist puns or alterations) to a more versatile board. The basic dimmer can, for instance, depending on the configuration of these leads, either be at full brilliance upon switch on, dimming as RV1 is rotated or alternatively, be at minimum output at switch on bringing the light to full brilliance as RV1 is rotated.

Light Construction

Construction of the light dimmer should pose no problems if the specified components are carefully mounted onto the PCB according to the overlay shown in Fig. 3.

We specify a ready made pulse transformer although those masochists amongst you might like to make this component yourself by evenly winding thirty turns of 32 SWG wire on a half inch long quarter inch diameter ferrite rod to form the primary. After a layer of insulation a further thirty turns of the same wire forms the secondary.

The coil L1 is formed by winding fifty turns of 22 SWG wire on a ferrite rod that is one inch long by quarter inch diameter.

It can then be fixed on to the PCB using quick-set epoxy, after soldering the leads.

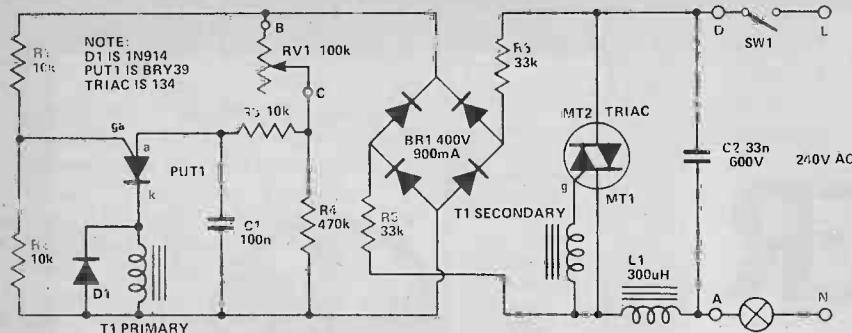


Fig. 2. Full circuit diagram of the light dimmer.

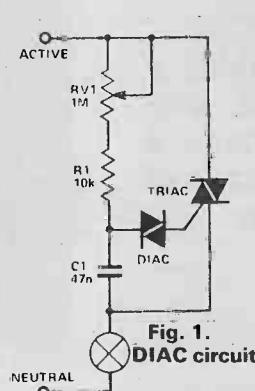
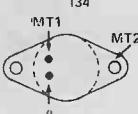


Fig. 1. DIAC circuit

BUYLINES

In order to ensure satisfactory performance of this circuit we recommend that only the components specified in the parts list are used. These components are available from stockists of RS Components, which means most people.

HOW IT WORKS

The light dimmer circuit can conveniently be broken down into two sections, the trigger circuitry and the triac itself that supplies power to the load.

We shall first discuss the trigger circuitry that is formed by PUT 1 and its associated circuitry. The BRY39 PUT (Programmable Unijunction transistor) is a four-layer semiconductor device that is similar in action to a thyristor. The BRY39 has lead-outs connected to each of the four semiconductor layers that make up the device. Our application only requires three of the terminals, the anode (a), cathode (k), and the anode gate (ga) — the cathode gate (gk) is left unconnected. For a full description of this device you should refer to one of the many text books that deal with semiconductor devices.

For our purposes the BRY39 can be thought of as a switch which can either present a high impedance between its anode and cathode terminals (off) or a low impedance (on). The device is switched from the "off" to the "on" state by taking the anode gate negative with respect to the anode which is, of course, the same as taking the anode positive with respect to the anode gate. (The device can also be controlled by the cathode gate.)

When in the "on" state the device can only be returned to the "off" state by reducing the current through the device to a value below the holding current (usually a low value). In this respect the BRY39 is similar to a thyristor.

Thus the BRY39 is turned "on" when the voltage at the junction of R3 and C1 reaches a value that is just greater than that at the junction of R1 and R2.

The trigger circuitry is powered by the unsmoothed full-wave rectified output of

BR1. The bridge is fed via dropper resistors R5 and R6 of which more later.

The relationship between the voltage applied to the BRY39's anode and cathode is dependent upon the value of RV1. A full analysis of the phase control network of the anode circuit (RV1, C1, R2 and R4) would require an article in its own right. However, it can be thought of more simply by considering C1's action as "slowing up" the rise in the full-wave rectified voltage at the PUT's anode. Thus C1 introduces a phase lag at this point. The component values have been chosen to provide the required range of control.

As the PUT is triggered the energy stored in C1 is applied to the primary of the pulse transformer, this induces a pulse in the secondary of T1 which is responsible for firing the triac. D1 prevents any back EMF which could upset circuit operation.

The load is controlled by the triac which can be thought of as a biconducting version of an SCR. The signal applied to the gate controls the triac's action for current in either direction. The pulse induced in the secondary of the pulse transformer causes the triac to conduct, supplying power to the load until the next zero crossing of the mains waveform causes the current in the triac to fall below its holding value thus turning off the triac.

Note that with the triac on there is no power available to the trigger circuit. The only current required by the trigger circuit is that required to charge C1 and a very small amount consumed by R1 and R2 across the supply. The total current is thus very small and the dropper resistors R3 and R4 can be low wattage components.

Capacitor C2 and coil L1 are provided to reduce the effects of RFI.

Loaded Question

So far we have described the basic light dimmer but by connection of the interface (trendy word) circuit shown in Fig. 5 the versatility of the unit can be greatly extended. With this interface circuit installed a DC voltage of between 5 and 7 V applied to the LED that forms the mains and as such should be treated with respect at all times.

Just a couple of final points. The first being that the maximum load we recommend for this circuit is 500 W, which should be adequate for most domestic applications. The second point to note is that this circuit is not isolated from one half of the opto-isolator, provides for full control of the load connected to the dimmer.

The unit can now provide remote control of loads by simply running a length of wire between the control pot and the dimmer (this is not recommended with the basic unit as the control leads are not isolated from the mains). The circuit can now provide a sound to light unit by simply connecting it to an amplifier or a sequencer by driving it from, for example, a clocked CMOS counter.

We are working on a few of these ideas and would hope to present some of them in a couple of months time.

ETI

PARTS LIST

RESISTORS

R1, 2, 3	10 k
R4	470 k
R5, 6	33 k

POTENTIOMETERS

RV1	100 k lin with switch
-----	-----------------------

CAPACITORS

C1	100 n Polyester
C2	33 n 600 V.D.C.

SEMICONDUCTORS

PUT 1	BRY 39
TRIAC	6A 400 V TO86 case

TRANSFORMER

T1	1:1 pulse (see text)
----	----------------------

COIL

L1	See text
----	----------

MISCELLANEOUS

PCB	as pattern
-----	------------

PROJECT: Light Dimmer

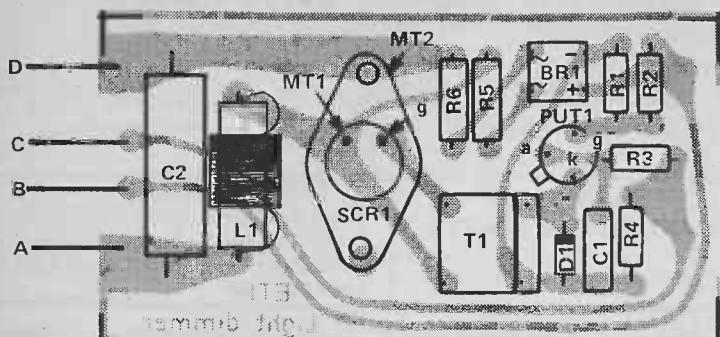


Fig. 3. PCB overlay for light dimmer.

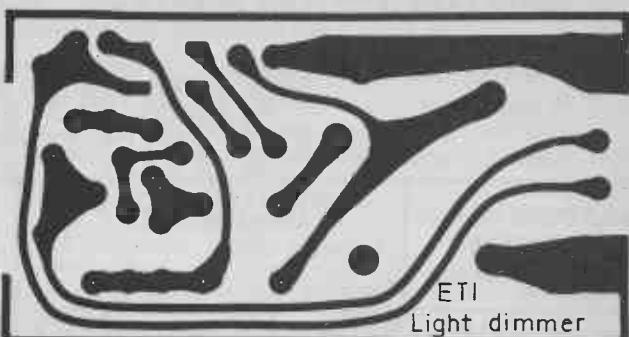


Fig. 4. Foil pattern shown full size.


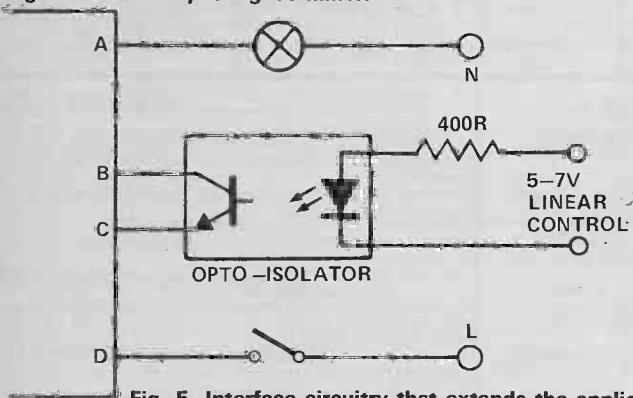


Fig. 5. Interface circuitry that extends the applications of the basic circuit as described in the text.

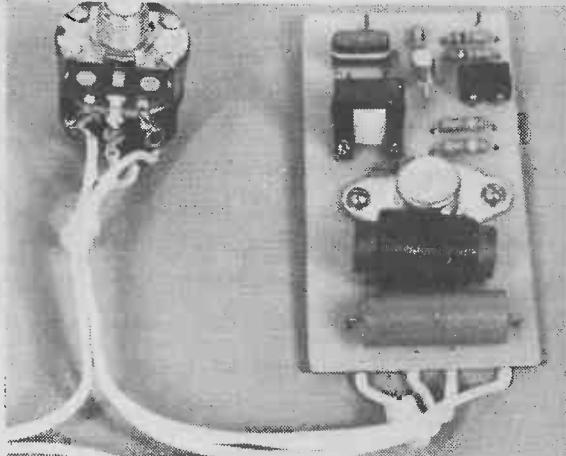

NEW!

STUNT TV MAN

4 EXCITING MOTORBIKE TV GAMES

*Normal and Super Rider Modes at the flick of a switch.
Realistic Throttle and Crash sound effects from the TV Loudspeaker.*

A GAME YOU'LL NEVER BE TIRED OF PLAYING

Super Stunt Cycle

Drag Race

Stunt Cycle

Motocross

HOW MANY BUSES CAN YOU JUMP?

This simple to assemble (1 hour) TV Game Kit comes complete (No extras needed) — just simple soldering. Expected retail price (when available in shops) — over £55.00. **SAVE 50%** by building it yourself. Be one of the first in Europe with this new stunt cycle craze at £28.50 (inc. VAT) + 25p P & P.

Make all cheques or postal orders payable to Teleplay.
Mail Orders: 53 Warwick Road, New Barnet, Herts. EN5 5EQ.
Retail Shop and Demonstrations —
14 Station Road, New Barnet, Herts.
For further Details and Technical Help — phone 01-441 2922.
For extra speed phone your order on Barclay-or-Access Cards.
(French and German spoken)

teleplay

MAINS OPERATED ELECTRONIC DIGITAL ALARM CLOCK

AVAILABLE FROM STOCK ONLY £8.95 EA
VAT 71p POST 30p

- Stylish Design
- Large Bright LED display
- Choice of black or white case
- ALL with red display on black background
- Tilted front panel for easy viewing
- Silent operation, all electronic
- Space age technology L.S.I. circuitry
- Alarm and 9 minute snooze repeater
- P.M. indicator
- Seconds Display
- Size 105mm x 115mm x 50mm high
- Fully guaranteed



Henry's
RADIO

All mail to: Henry's Radio
404 Edgware Rd. London W2

Complete digital clock kits

TEAK or PERSPEX CASE



Non alarm £12.50

Alarm £15.50

NON-ALARM

Complete Kit including case	£12.50
Ready built	£14.50
Module Kit excluding case	£9.50
Ready Built	£10.00

TIMER FACILITY: Stopwatch use up to 9 min. 59 secs. extra 50p

EXCELLENT VALUE

- National Semi. 5 Function LCD Watch. Backlight £15.95
- NOVS 850 Calculator £3.78. Adaptor £2.70.

GUARANTEED

DISPLAYS: FND 500 1/2" LED £1.19 each. 6 for £6.48.	£5.40	
NSB 5430 1/2" red LED stick of 4 .	£4.32	
5LTO2 1/2" green phosphor stick of 4 .	£4.32	
CLOCK CHIPS: 50253N Alarm . 12/24 hr. 4/6 digit .	£5.67	
50362N Calendar clock . £7.75	MM5385N 12 hr. 4 digit. Alarm	£4.32
6 Decade Up/Down Counters: 50395/6/7	£9.45	
MICROPROCESSOR: Z80 CPU	£22.68	
Z80 CTC .	£15.70	
Z80 PIO .	£15.70	
UV PROM Eraser .	£103.00 + £5.00 p&p	
1702A UV Erasable PROM .	£11.35	
2102NA IK Static RAM .	£2.70	
4KX1 16 pin Dyn. RAM .	£7.05	

RECHARGEABLE BATTERY SET

Super Value £8.10
Includes: 4 AA (1.2V) Nickel Cadmium batteries (separately £1.08 each)
3/6/9v switched Universal Mains Adaptor with 4 plug connector
for most calculators (separately £3.78) plus battery holder

ALPHA CLOCK KITS 1/2" Green Display, Perspex Case	£15.50
Alarm Non-Alarm	£12.50

Send payment with order. SAE for details.

BARON
SOUTHVIEW HOUSE
6 GOWER ROAD
ROYSTON, HERTS.
Phone: Royston (0763) 43695



TRANSFORMERS

Panel Meters, Bridge Rectifiers, Power Supply Units
Multimeters - Semi Conductors - Timers - Safebloc

Miniature & Sub Miniature

Volts	Milli-	Ref.	Price	P&P
3-0-3	amps	No.	£	P&P
0.6-0.6	200	238	1.95	.55
9.0-9	1A 1A	212	2.60	.55
0.9-0.9	100	13	1.85	.40
0.8-0.8-0.8	330 330	235	1.95	.40
0.8-0.8-0.8	500 500	207	2.35	.55
0.8-0.8-0.8	1A 1A	208	3.50	.55
0.15-0.15	200 200	236	1.95	.40
0.20-0.20	300 300	214	2.35	.70
0.20-0.20-0.20	700(DC)	221	3.10	.70
0.15-20.0-15-20	1A 1A	206	4.20	.85
0.15-27.0-15-27	500 500	203	3.65	.70
0.15-27.0-15-27	1A 1A	204	4.75	.85

12 AND/OR 24 VOLT

Pri: 220-240 Volts	Amps	Ref.	Price	P&P
12V 24V	Ref.	£	P&P	
0.5	0.25	111	1.95	.55
1.0	0.5	213	2.30	.70
2	1	71	2.90	.70
4	2	18	3.75	.70
6	3	70	5.35	.85
8	4	108	6.25	1.00
10	5	72	6.95	1.00
12	6	116	7.85	1.00
16	8	17	9.25	1.10
20	10	115	12.75	1.30
30	15	187	16.60	1.30
60	30	226	22.90	1.60

30 VOLT (Pri. 220-240V)	Sec. 0.12-15-20-24-30V	Price
0.5	112	2.45
1.0	79	3.05
2.0	3	4.80
3.0	20	5.80
4.0	21	6.85
5.0	51	7.75
6.0	117	9.50
8.00	88	11.35
10.0	89	12.00

CATALOGUE 30p

Please add VAT at 8%
Barclaycard and Access facilities available
Trade and Education Welcome

BAYDIS

54a Mortimer Street
Herne Bay, Kent
Herne Bay 64586

ALL PRICES INCLUDE POST, PACK AND VAT

...news

on the road

Not so very long ago Edgware Road was the place to go for components. The pavements were lined with resistors — any value, any range — and most anything thing the constructor desired was there somewhere.

Even less long ago the road died. Shops closed up, and retailers, with a few notable exceptions, became surly and distinctly unhelpful. Edgware Road was not the place to go to buy anything, except maybe a dead duck or two.

However things seem to have changed yet again. Recently three new component stores have opened, Metac, Audio Electronics and Marshalls. Even a couple of hi-fi emporiums have re-materialised from the ether and things are looking up. Certainly going into Edgware was a shift of more than just the kitchen sink for Metac. Their shops are best known for their range of watches, clocks and TV games. Now however the Edgware Road branch is to major in components, although it will still carry an excellent array of time keeping machinery.

In addition to this the shop acts as an inlet for Metac's TV game service facilities, and will carry a range of MPU equipment when set up.

Anyone who has followed the beaten path to Edgware Road in search of the trappings of our art will have felt the edge of indifference wearing them a little thin at times. We can but hope that Metac and the rest of the reinforcements bring with them their present high standard of service.

horseplay

From Rapid Recalls Stable have come three ICs designed as motor drive devices. The three models have 1 A (8510), 2 A (8520), and 2.7 A (8530) output current capability and a standard 741 input characteristic.

They are of hybrid construction, and consist of a 741, driver chip and complementary output pair with frequency compensation. Short circuit protection is provided

colourfull sounds PAL

The Videograph is a new product that provides a means of displaying colourful "music inspired" patterns on any domestic colour TV set. The basic Videograph circuitry generates a green background upon which blue and orange stripes are superimposed. Each of these stripes can be modulated, rather like the display on a 'scope', by audio signals fed to the Videograph's two audio inputs. The two audio signals will usually be derived from the Left and Right outputs of a stereo amplifier thus turning the TV into a sophisticated sound to light unit.

The circuitry is mounted on two boards, the larger taking care of sync generation, audio signal handling and 'stripe generation' while the other provides the colour modulator.

This latter board is interesting in itself as unlike some colour modulators it does not require complex drive signals, i.e U and V inputs, but operates on three separate R, G and B signals. This modulator, with the addition of a small interface circuit, can provide a colour facility for games based on the ubiquitous AY-3-8500 which means most tele football games.

The Videograph comes in kit form and, if the instructions provided are followed carefully, can be built up in a few hours. If there are any problems with the unit however, the manufacturers will put things right for you at a small fee.

The Videograph is available from:— W. P. Stuart-Bruges at 137, Billericay Road, Herongate, Brentwood, Essex, CM13 3SD.

The complete Videograph costs £15.95 but the modulator is available separately at £5.50.

on chip, with the current into such a load set by external resistors.

One suggested application not to do with controlling actuators, is for a programmable PSU consisting of a D to A converter, 8520 etc, and thumbwheel switches to control the D to A. Output can then be set to ± 0.1V.

Rapid Recall, 9, Betterton Street, Drury Lane, London WC2H 9BS.

Designed by John Miller-Kirkpatrick

SOFTWARE

System 68

ETIBUG 2 is the second software PROM for the System 68 CPU card. The IC fits into socket marked IC9 ready for use. The ETIBUG monitor does an automatic test for the presence of ETIBUG2 (test for an 'E' at location ECO0) during its command, and if it is inserted ETIBUG will automatically branch to it, so there is no need to alter any other part of the card.

New Commands

The new commands included in ETIBUG2 are intended to make machine code programming easier. The first command will dump 128 bytes of memory to the VDU. This command is entered by typing 'H' followed by the hex address from which the dump is to begin. The dump always begins at the top of the VDU 'page' and fills half the screen. If the command is not 'H' then control passes to 'X TEST'.

'X'ecuting your programs

The second new command allows a program to be run without the long-winded procedure of modifying the Stack dump area to change the program counter (PC), to the address where you want execution to begin. The command is operated by entering X and then the hexadecimal address of the start of your program. (This command will not operate if the stack pointer is not pointing to A042 when executed).

More Interruptions

One of the most useful features of the 6800 during Machine Code programming is the Software Interrupt (3F instruction). When this instruction is found it causes a Stack dump of the registers, a display of this data on the VDU and a branch back to the CONTROL loop. Thus you can code several bytes of program followed by a 3F followed by some more coding and another 3F, etc. When the 3F instruction dumps the registers it dumps the address of the 3F instruction as the PC address, thus a subsequent G command from the keyboard causes control to be passed back to that 3F instruction and thus it is re-executed. To continue by using ETIBUG or MIKBUG it is necessary to update the stored PC by 1 and then use the G command. With ETIBUG2 in your system you need only enter the command letter C to Continue executing after the 3F instruction. Like the Xecute command the Continue command updates the stored PC and then branches into the G command.

424F52494E4720535452494E4753 . . .

From the heading of this paragraph you can see how boring and complex it can be to enter a string of ASCII characters into memory using the Memory Examine/Modify command as each character has to be entered by using its ASCII code rather than its keyboard code.

The ETIBUG2 'K' followed by a hex address command allows you to specify a starting address and enter a string of characters from the keyboard into memory until an EOT (Hex 04) character is entered, upon which control jumps back to the Hex Dump Subroutine.

Shifting Memories

The ETIBUG2 S command allows areas of memory to be copied from one location to another. The 'from' address can be any valid hex address covering RAM, PROM, I/O device addresses, etc; the 'to' address can also be any valid hex address but will usually be RAM. A 'Not RAM' check has not been included as it may be possible to use this command to Shift data from memory to a device port (or vice-versa) and thus use the command as for I/O operations.

The Shift command is started by entering the command letter S. ETIBUG2 will then ask for a START ADDR, a TO ADDR and a LENGTH all of which require a valid four digit hexadecimal input. At the end of the copy control returns to the CONTROL loop. As well as the above commands.

Tape Out

This subroutine outputs a block of data to a cassette unit via the TTYOUT subroutine. The parameters for the output must be stored by the user in address locations A018-A021 before using the subroutine.

The routine starts the tape by pulsing the TAPSTRT flip-flop and then waits about 5 seconds before starting the output.

Output first is the Start address, length and six byte label from the parameter area. Data is then output from the Start Addr until the number of bytes specified by the Length parameter have been output. As each data byte is output it is added to the checkdigit byte (which starts at zero), this checkdigit byte is output as the last character of each block. The routine allows a 5 second delay before stopping the tape and returning to the user program which called this subroutine.

The TAPOUT routine can be called from a user program as a sub-routine or can be called by jumping to XED8F.

Tape In

The TAPIN routine does the reverse of the TAPOUT routine. When the routine is executed and the tape started, the first bytes input are read into the parameter area and then the data is read into the area defined by the Start ADDR and Length now defined by the parameter area. As each byte of data is read in a checkdigit is generated in the same way as that generated by the TAPOUT routine. When the Length parameter indicates that all data has been read in the routine reads one more byte which it assumes to be the output checkdigit. Both the output checkdigit (A022) and the generated checkdigit (A023) are stored in the parameter area for user checking.

TAPIN can also be used by previously setting up the Start Addr and Length in the parameter area and executing TAPOUT3 (EDA7). If used in this way note that the length specified should be one less than the length expected and that the last data byte will appear at A022 instead of the location expected. This is because TAPOUT expects the checkdigit to follow the last data byte, if your tape was not generated on a System 68 it may not have a checkdigit following the data (although most tape systems do have one).

Tape In or Out

The cassette I/O routines act on a block of data at each execution, the parameters for the address, length, label, etc for this block have to be set up before output and are also available to the user after input of a block. To save you checking the parameters by dumping the appropriate area of RAM we have included a TAPE CHECK command which is called by entering the command letter T. The data for a tape I/O are stored as follows.

A018,9	Address of start of block of data.
A01A,B	Length of block of data excluding this parameter data.
A01C-21	Six character ASCII label area.
A022	Checkdigit byte for output (Auto-generated).
A023	Checkdigit byte from input (Auto-generated).

For a valid read the checkdigit which was on the tape (A022) should be the same as that generated during the read (A023), the label area is not used by ETIBUG2 but can be used to identify a record by the user.

The T command performs a formatted print of these parameters for use before output or after input.

TTYIN

This subroutine accepts data from a UART whenever the DAV bit indicates that a byte has been received by the UART. After input the DAV flip-flop is reset. Data is input to ACCA and status to ACCB.

TTYOUT

This subroutine outputs data to a UART if the UART is not already BUSY. There are two entry points —

TTYOUT assumes that the index register points to the address of the next byte for output.

TTYOUT2 assumes that the output data is already in ACCA.

Data is output from or via ACCA with the UART status being saved in ACCB.

ETIBUG2 completes the basic PROM software for System 68 for the time-being. Next we hope to bring you a Tiny BASIC or ASSEMBLER.

ETIBUG2 can be obtained in an MM5204 PROM from Bywood Electronics for £25.95 plus VAT.

ETIBUG 2

This is a complete listing of the ETIBUG2 PROM which has been written to make machine code programming on System 68 easier.

Address	Op-code	Label	Mnemonic	Description	Address	Op-code	Label	Mnemonic	Description
EC00	45	H TEST	CMP B H	LETTER 'E' FOR ETIBUG	ED19	42		B	
EC01 C1	48		BNE X TEST	IS COMMAND H?	ED1A	44		D	
EC03 26	31		JSR EE47	NO, JUMP TO X-TEST	ED1B	20		T	
EC05 BD	EE47		LDX 8800	GET ADDRESS FROM KBD	ED1C	54		O	
EC08 CE	8800	H DUMP	STX A014	SET VDU CURSOR TO TOP	ED1D	4F			
EC0B FF	A014		CLR B		ED1E	20			
EC0E 5F			LDX A00C	PRINT ADDRESS	END OF TEXT				
EC0F CE	A00C	NEXT RO	JSR EEC8	LOAD ADDRESS OF BYTE	CARTRIDGE RETURN				
EC12 BD	EEC8		LDX A00C	PRINT BYTE	MESS 4				
EC15 FE	A00C	NEXT H	JSR EECA	STORE ADDRESS OF NEXT BYTE					
EC18 BD	EECA		STX A00C						
EC1B FF	A00C		INC B						
EC1E 5C			BIT B 07	HAVE 8 BYTES BEEN PRINTED?					
EC21 26	F2		BNE NEXT H	NO, LOOP BACK TO NEXT H	ED25	20		C	
EC23 BD	EECC		JSR EECC	YES, PRINT SPACE	ED26	43		H	
EC26 C5	0F		BIT B OF	HAS A ROW BEEN COMPLETED?	ED27	48		E	
EC28 26	EB		BNE NEXT H	NO, LOOP BACK TO NEXT H	ED28	45		C	
EC2A 86	OD		LDA A 0D	YES, LOAD CR CHARACTER	ED2A	4B		K	
EC2C BD	EFD1		JSR EFD1	PRINT CARRIAGE RETURN	ED2B	3B		S	
EC2F C5	7F		BIT B 7F	IS DUMP FINISHED?	ED2C	33		T	
EC31 26	DC	RUN	BNE NEXT RO	NO, DO NEXT ROW	ED2D	54		A	
EC33 7E	EEE3		JMP EEE3	YES, JUMP TO CONTROL	ED2E	41		R	
EC36 C1	38	X TEST	CMP B X	IS COMMAND X?	ED2F	52		T	
EC38 26	09		BNE C TEST	NO, JUMP TO C-TEST	ED30	54			
EC3A BD	EE47		JSR EE47	GET ADDRESS OF PROGRAM START	ED31	20			
EC3D FF	A048		STX A048	STORE ADDRESS AT A048	ED32	41		A	
EC40 EC	7E	EFOF	JMP EFOF	JUMP TO 'RUN' IN ETIBUG	ED33	44		D	
EC43 C1	43	C TEST	CMP B C	IS COMMAND C?	ED34	44		D	
EC45 26	09		BNE K TEST	NO, JUMP TO K-TEST	ED35	52		R	
EC47 FE	A048		LDX A048	TRANSFER PC TO X-REGISTER	ED36	20			
EC4A 08			INX	INCREMENT X-REGISTER	ED37	04			
EC4B FF	A048		STX A048	TRANSFER X BACK TO PC	MESS 5				
EC4E 20	F0		BRA RUN	JUMP TO RUN OUTLINE	ED38	4C			
EC50 C1	4B	K TEST	CMP B K	IS COMMAND K?	ED39	45			
EC52 26	29		BNE S TEST	NO, JUMP TO S-TEST	ED3A	4E			
EC54 CE	ED16		LDX MESS 3	LOAD START OF MESS 3	ED3B	47			
EC57 BD	EE47		JSR EE7E	PRINT MESSAGE 3	ED3C	54			
EC5A BD	EE47		JSR EE47	GET ADDRESS FROM KBD	ED3D	48			
EC5D FF	A018		STX A018	STORE ADDRESS	ED3E	20			
EC60 FE	A018	K LOOP	LDX A018		ED3F	04			
EC63 BD	EFAC		JSR EFAC		ED40	4C			
EC66 A7	00		STA A X	GET CHARACTER FROM KBD	ED41	41		A	
EC68 A1	00		CMP A X	STORE CHARACTER	ED42	42		B	
EC6A 27	03		BEQ K LOOP 2	WAS CHARACTER STORED?	ED43	45		E	
EC6C 7E	EEE3		JMP EEE3	YES, JUMP TO K LOOP 2	ED44	4C		L	
EC6F 08		K LOOP 2	INX	NO, JUMP TO CONTROL	ED45	20			
EC70 FF	A018		STX A018	INCREMENT ADDRESS COUNTER	ED46	20			
EC73 81	04		CMP A 04	STORE NEXT ADDRESS	ED47	04			
EC75 26	E9		BNE K LOOP	WAS CHARACTER EOT?	ED48	43		C	
EC77 7E	EC08		JMP H DUMP	NO, LOOP BACK TO K LOOP	ED49	48		H	
EC7A 00			JMP H DUMP	JUMP TO HEX DUMP	ED4A	4B		K	
				NO OPERATION	ED4C	49		D	
					ED4D	47		I	G

audiophile.


This month Ron Harris lends both ears to the new Koss E-10 electrostatic headphones. Placed at the top of Koss's range, and costing £180 a pair they promise much. Do they deliver? Read on

HEADPHONE LISTENING has much to commend it — isolation from the wallpapered box which produces so much colouration in any loudspeaker system for one thing. Neighbours the world over would be a happier race if we all took to hanging our transducers around our heads instead of knocking down their living-room walls with them.

In terms of absolute quality too, electrostatic (and the better moving coil) units have few if any equals amongst loudspeakers, and their cost will always be lower. So for someone starting down the slippery slope to hi-fi bliss, and who either lives in a flat or yearns for greater accuracy than his budget allows, headphones must provide a serious alternative to those ubiquitous wooden boxes.

Energise . . .

This brings us neatly onto the energiser itself. Superbly finished in black metal with a wood grain panel, the box gives new life to the theory of collapsed matter. For its size it is impossible **heavy**, due of course to the two huge transformers present within. The meter and overload circuitry is contained on a single large PCB, with all connections being made via removable plugs. Although untidy to look at, the internal construction is to a very high standard, and we can envisage no problems being caused here.

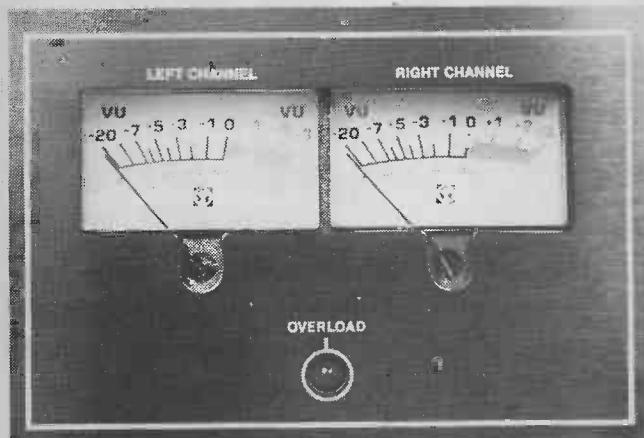

Close-up of the clever bits — VU meters and overload indicator LED

Two VU-meters are provided to monitor signal level, and these operate in conjunction with the overload LED positioned beneath them. Sockets exist for two sets of phones, and the single on/off switch switches the audio back to the speakers once the headphones are switched off. Back panel connections are by spring terminal, and Koss provide four suitable leads to accomplish this.

In practise the overload facility worked well, cutting

off the audio (and lighting the LED) for about ten seconds once the trigger level is exceeded. This level is represented by full scale deflection on the meters, which appear to leap into the red all too readily! We found the cut-off point to be too low for our liking sometimes, but accept that it is a perfectly good compromise.

On heavy rock signals, with any bass boost all (not needed really — see later!) the overload operated at a level which would not always satisfy the devilish tastes for loudness exhibited in this field. In fairness though this is a minor point, and personally I tend to agree with Koss's choice, as sustained listening at even near maximum allowed level amounts to audio suicide of the eardrums.

Down to sound

Now to the sixty-four thousand watt question — how do they sound? In a word they don't! Without qualification the E10s provided the most neutral and uncoloured sound yet to assail our ears. It was very very easy to forget the phones totally, and listen through to the earlier links of the chain and thus to the music itself, assuming high quality source equipment of course.

Expect no mercy — the E10s will ruthlessly expose shortcomings in anything of lesser stature, be it electronics or records, but their even response means that surface noise is not emphasised unduly as is the case with a rising treble characteristic, and no tonal correction was found necessary at any stage in the listening tests.

Here is a transducer to make you question your ideas of fidelity. All speakers possess a character of their own, and probably the E10s do as well. But this is so inobtrusive as to be negligible — and we've waited a long time to be able to say that about any piece of hi-fi!

Pecuniary conclusions



The only possible drawback to the E10 Auditors is their price — £180 all in for phones, energiser, PSU and leads. Quality never comes cheap of course, but we did wonder how much the meters and associated circuitry added to the price.

Still, as we said earlier £180 wouldn't buy a pair of loudspeakers in this class, and so maybe we shouldn't quibble — but seeing as how we're at it — how about some more headroom on the overload?

Overall then, the E10s are probably the nearest thing to transparent transducers on the market, but cost is high and heavy rock fanatics who have a thing for un-natural boom in the bass may not be impressed by their lack of colouration in that area. Definitely a connoisseur's item and one that all hi-fi followers should hear at least once!

Like other electrostatic headphones, the E10 employ the electrostatic push-pull principle. Referring to fig. 1a, the audio is applied across the plates superimposed upon the polarising voltage V_p . Since one plate is fixed and one can move freely, the latter will be vibrated by electrostatic forces much the same as those that hold dust to LPs and LPs to turntable mats. V_p is there to provide an initial displacement about which the audio signal can induce movement. Resistor R loads the polarising signal, and C decouples the audio input.

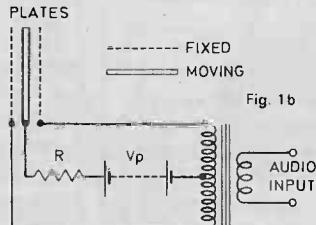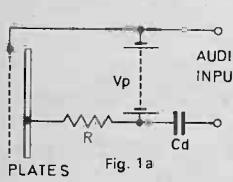The push-pull design overcomes some of the drawbacks of the basic principle and lowers distortion, especially even harmonics. Fig. 1b shows the basis of the design. A second fixed plate is added, so that the moveable plate sits in a sandwich. The audio signal is fed




in through an isolating transformer, the secondary of which is centre-tapped to provide anti-phase signals for the two plates.

This is the task of the energiser, and those transformers can be a limiting factor in the performance. Koss have made their inductors massive, such that a 20 Hz signal can pass unhindered. (In theory).

In the E10 energiser the overloaded sensing is set to operate at around 5 V (pink noise) signal at the input. This represents around 103 dB SPL at the ears, which explains the Koss setting mentioned in the text. The energiser presents a load to the amplifier which varies in phase angle, linearly, from a +30° at 20 Hz to -30° at 15 kHz and an impedance characteristic with minimum of 3 R (20 Hz) and maximum of 180 R at 800 Hz

HOW IT WORKS

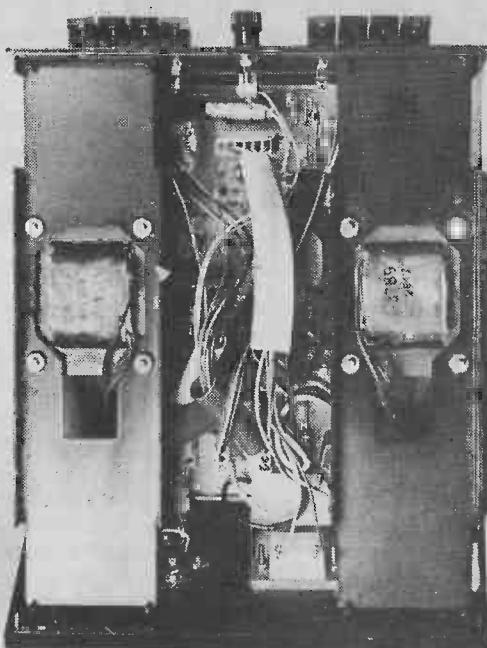

Internal view of the energiser box, note the massive audio transformers.

videocraft


Half price Teletext

You can now buy Texas **Tifax** module Teletext decoder complete with matching cable connected keyboard, power supply, interface board and complete instructions, for installation in most common television receivers for only £180 +VAT and £2.50 postage, packing and insurance.

Since the interface is connected directly to the television's video output circuitry, picture quality is excellent with pure colours — much more so than is possible from decoders which feed the aerial socket.

Due to the compact nature of the **Tifax** module, installation within most receiver cabinets is no problem. Facilities include seven colours, upper and lower case alphanumerics, graphics, time coded display, and newsflash and subtitle inserted in TV picture.

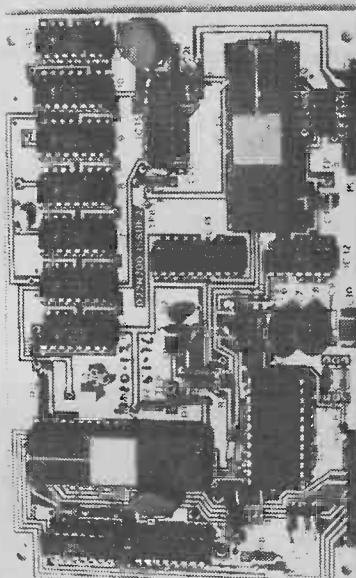To enable us to supply the correct interface board and instructions, we must know your television set make and model and, if possible, chassis type.



videocraft

29-31 Goswell Road
London EC1.
Telex: 896953

DIGITAL ELECTRONICS

RIPPLE COUNTERS are useful and simple, but they are not ideal for high counting speeds, nor for large counter chains. The problem arises from the use of the output of each flip-flop as the clock for the next flip-flop, so that changes must "ripple through" all the stages of the counter. This, as indicated in the previous section, causes difficulties with time delays.

Although these delays are not large, perhaps .60 nS or less per flip-flop, they accumulate to a significant amount over a large number of counter stages and can cause the race hazards mentioned earlier.


Synchronous Counters

A different principle is used for synchronous counters. The input pulses are used to clock *each* flip-flop of a chain, hence the name synchronous. The count sequence is then determined by voltages applied to the J and K terminals, and these voltages must be obtained in such a way that any given count on the flip-flop will cause the J and K voltages to be set to the voltages needed to change to the next digit up or down.

This is much more easily illustrated by an example which we can test on our board. In this example we shall follow the pattern of design steps (with some modifications) which is usually used for synchronous counters.

Basic Two-Step

Let us imagine a very basic counter using two flip-flops and resetting at the count of four. We must start by making a table showing the count, the present state, and the next state for each flip-flop. This means that for each number of the count we list the value of Q (1 or 0) and also the value to which Q will change at the next count. For example, when the count is 1 (01), the next count is 2 (10) and both outputs will change — A from 1 to 0, and B from 0 to 1. On the next count (3), A changes from 0 to 1, and B does not change. The complete table for two flip-flops is shown in Fig 1(b).

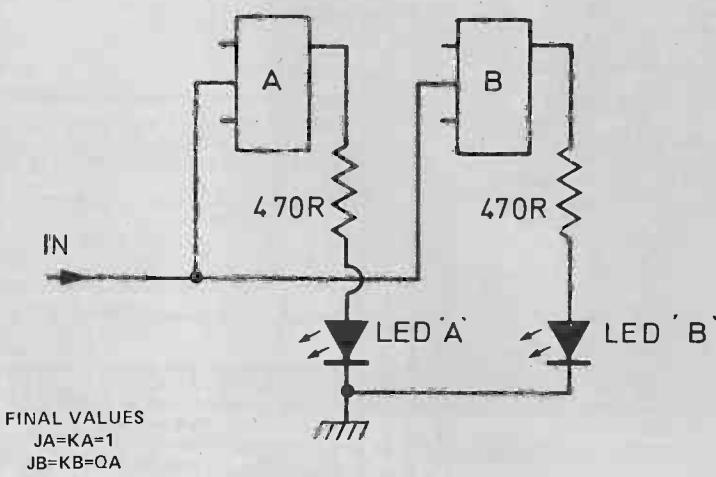

COUNT	A		B		JK VALUES			
	Q PRESENT	Q NEXT	Q PRESENT	Q NEXT	JA	KA	JB	KB
0	0	1	0	0	1	X	0	X
1	1	0	0	1	X	1	1	X
2	0	1	1	1	1	X	X	0
3	1	0	1	0	X	1	X	1

Fig. 1 (Above) A simple synchronous counter, no J-K connections shown.
(a) Circuit. Note that the input clock is taken to each stage.
(b) Table of changes, with J and K values for the changes.

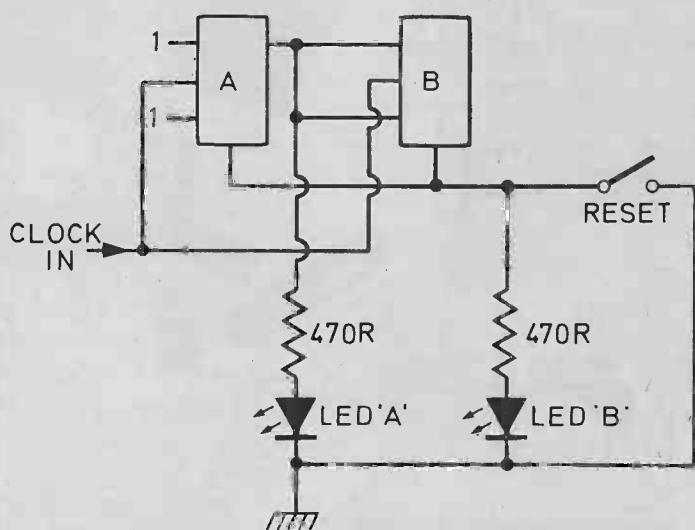


Fig. 2 (Above). Complete two-stage synchronous counter circuit, with J-K connections shown. Try this out on your blob-board.

BY EXPERIMENT PART 6

Now we have to decide what voltages are needed at J and K of each flip-flop to carry out the changes from present state to next state. Here we have some options — for example, if we want to change from 1 to 0, we may have $J=K=1$, or $J=0$ and $K=1$; either state will carry out the change. When this is possible, we can write $J=X$, $K=1$, where X means don't care, since either value of J is equally suitable.

Add more columns to the table to indicate these values of J and K for each flip-flop, and we are ready to start designing. The object now is to obtain the J and K voltages for each flip-flop from somewhere else in the circuit in such a way that all the J and K voltages are correct for each stage of the count. The formal method of doing this involves a technique called *Karnaugh mapping*, but is seldom necessary for only a few counter stages. It is rather difficult to apply for a large number of stages, so only the 'intuitive' look-and-see method will be discussed here.

Table Talk

At the zero count, $Q_a=0$, $Q_b=0$ and the change at the end of the clock pulse will be from $Q_a=0$ to $Q_a=1$. This will happen if $J_a=1$ and for $K_a=0$, or $K_a=1$. We therefore fill in a 1 in the J_a column, and an X (either value) in the K column.

Still at the zero count, $Q_b=0$ and does not change at the end of the clock pulse. This can be done if $J_b=0$, $K_b=X$, so that these values 0 and X appear in the J_b and K_b columns.

These columns are filled in similarly for each change listed — remembering to use X in any case where a value is unimportant — using the J-K table that we used in Part 4 of this series of articles.

We can now inspect the complicated tables to see if any values can be fixed or derived from values of Q_a or Q_b . The tables for J_a and K_a are easily dealt with — since the values are either 1 or X, we can use 1 for all these values, and make $J_a = 1$, $K_a = 1$, as

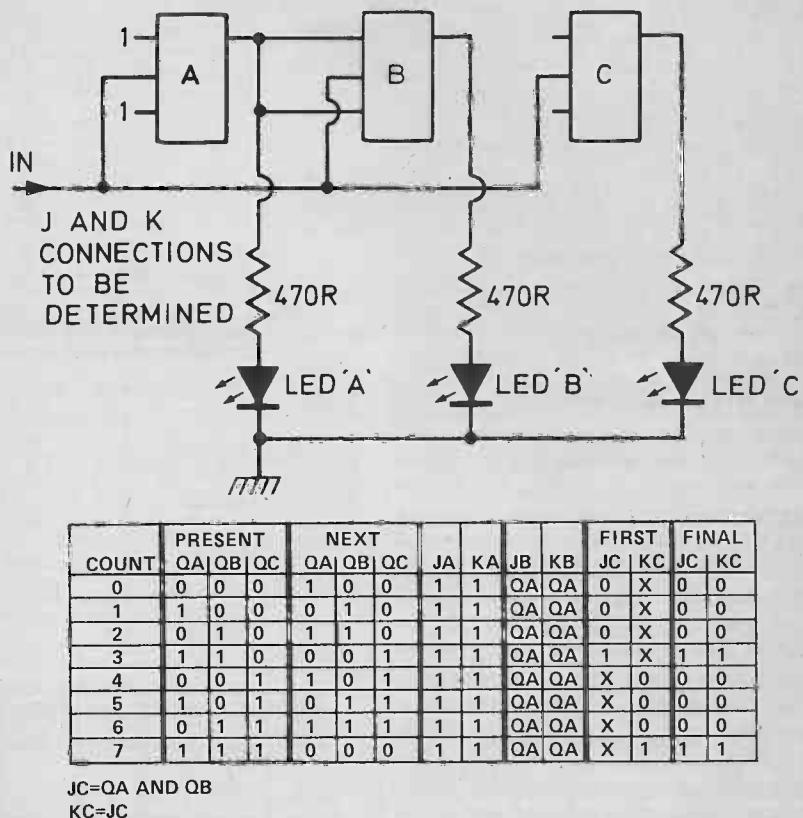


Fig. 3 (Above). A three-stage synchronous counter.

Top: (a) Circuit, J and K connections still to be determined.
Bottom: (b) Table of changes, showing how J and K values are determined.

The "first" Jc-Kc table shows possible values of Jc and Kc, the "final" table shows the most convenient values to use.

for the ripple counter. The J_b, K_b tables are slightly more involved, but for each definite value of one quantity (J or K) there is an X for the other, so that we can again connect J and K. We then find that the values of J and K are identical to the values of Q_a, so that J_b and K_b can be connected to Q_a.

For practical work on synchronous counters it is useful to have a clock pulse line, and one of the spare lines on the board can be used. Connect up the circuit as shown, with a slow clock pulse taken to each clock input, and wire connections linked from Qa to Jb and Kb. Use LEDs as before to check the state of each flip-flop output. Connect a common reset line to each flip-flop and to a switch so that the

counter can be reset. Switch on and check that the count is correct and that resetting to zero is possible.

Third Stage Development

Let us now extend this to a third stage, building on what we have done before. Once again we can build up a table of values of Q, J and K for each stage, but we have made life easier for ourselves by having done the two stage counter, so we can ignore the Ja, Ka and Jb, Kb columns and concentrate on the Jc, Kc column.

Using the same principles as before, we fill in the values of J and K which will be needed at each clock pulse or flip-flop, concentrating on the necessary values, and putting an X

where the value is immaterial. When we do this (Fig. 3b) we find two important states. One is at the count of 3, where J_C must change from 0 to 1; the other is at the count of 7 when K_C similarly changes from 0 to 1.

The change of J_C from 0 to 1 occurs when the count changes to 110 so that we could use an AND gate connected to Q_A and Q_B . The output of this gate will be zero for any count up to 2 and then will be 1 at a count of 3. It will change to zero again to become 1 at the count of 7, but the value of J_C is unimportant beyond the count of 3 anyway.

Looking at K_C we find that the important value of 1 occurs at a count of seven when J_C may also be 1. We can therefore connect J_C and K_C together and feed from an AND gate supplied with Q_A and Q_B .

Third Stage On Board

Making up a three-stage synchronous counter on the circuit board needs some additional connections. Since we are not using AND gates, the gate used will have to be made up from a NAND gate and an inverter. As the 7400 contains four two-input NAND gates and the 7414 contains six inverters, one of which is used for the clock oscillations, there is no shortage of gates. We are working with a low frequency clock, so there should be no ill-effects caused by the number of wires soldered across the board, but a high speed counter would have to be built on a PCB designed for the purpose, using copper tracks on each side and with decoupling capacitors between +ve and -ve lines close to each flip-flop. Such PCBs can be made up quite rapidly by using the new sketch'n'etch technique (P.B. Electronics) for one-off PCBs.

Can you now go one step further to design a four stage synchronous counter and try it out on the board?

Twisted Logic

A different type of synchronous counter is shown in Fig. 5. This is a Johnson, or 'twisted-ring', counter and consists of four flip-flops connected so that the output of one drives the J and K inputs of the next. Three of the connections are made up with Q to J and \bar{Q} to K, but the feedback connection is made with Q to K and \bar{Q} to J — hence the alternative name of twisted-ring. Remembering that \bar{Q} is always the inverse of Q , can you plan out the values of Q and \bar{Q} for each counter? Use the table headings


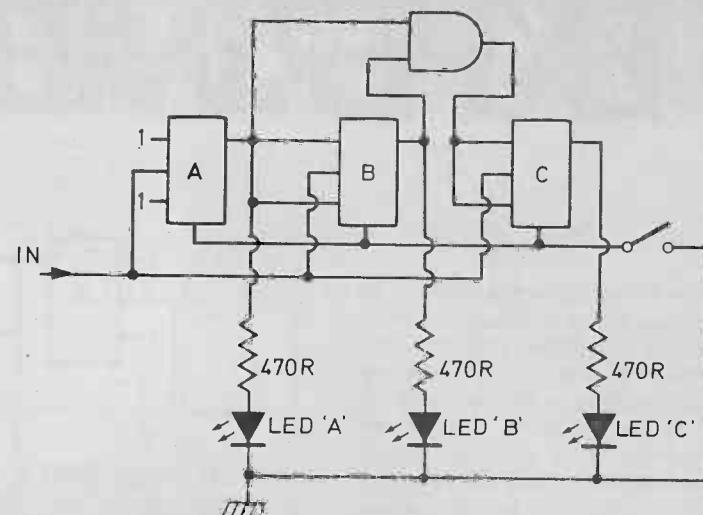


Fig. 4 (Above). The circuit of the three-stage synchronous counter. Try this out on your blob-board.

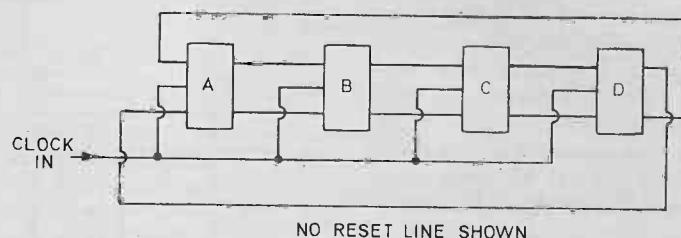

NO RESET LINE SHOWN

CLOCK	JB QA	KB $\bar{Q}A$	JC QB	KC $\bar{Q}B$	JD QC	KD $\bar{Q}C$	KA QD	JA $\bar{Q}D$
0								
1								
2								
3								
4								
5								
6								
7								

shown in Fig. 5(b) and remember that $Q_A = J_B$, $Q_B = J_C$, $Q_C = J_D$, $Q_D = J_A$ and so on.

A Johnson counter uses a completely different count sequence from conventional binary counters, and the maximum count number is twice the number of flip-flops. The counters are synchronous, very easy to design and also very simple to decode for use with lamp indicators.

Build up the four stage (count of 8) Johnson counter of Fig. 5(c) on your circuit board and check that your calculations are correct.



To be continued

Fig. 5. A Johnson counter of four stages.

Top: (a) The circuit, note the "twisted ring" connection.

Bottom: (b) Table to complete so that the counter action can be predicted.

Below: (c) Truth table. Build the circuit on your blob-board and complete this table.

COUNT	A	B	C	D
0				
1				
2				
3				
4				
5				
6				
7				

microfile.....

Gary Evans looks at a couple of earth bound micro systems and then journeys to a stella system for a game of intergalactic proportions.

THE FIRST ITEM WE look at is from a company thought by some to like the cloak and dagger game, but then so do quite a few semiconductor manufacturers, Science Of Cambridge — don't mention Sinclair. At the time of going to press they have just launched their MK14 with an advertisement in a magazine that is generally not associated with a dedicated commitment to micros.

SCAMP and Chips

The MK 14 is described as a keyboard addressable microprocessor. At a price of just under forty four pounds one might not expect all that much but the SCAMP based system provides a hex keyboard, eight digit LED display, 512 bytes PROM with resident monitor, 256 bytes of RAM together with 4MHz crystal plus power supply stabiliser.

I do not have much information of the MK14 and so I can say nothing about the versatility of the monitor, the ease with which the system can be extended, the quality of the documentation and any number of other interesting topics.

The MK14 comes as a thirty-one piece kit and is, apparently, available now. At just less than forty four pounds this kit should, if nothing else, provide the cheapest way of getting hands on experience with a micro which, in my opinion, is the only way to understand these little fellows.

Before leaving the MK14 it is interesting to note that Science Of Cambridge have chosen the

National SCAMP as the heart of their system. This device has been overshadowed by the likes of the 8080, 6800 and lately the Z80. Suffering as it does from a limited instruction set, lack or many on board registers, limited addressing modes and inability to handle stacks it is fair to say that the reception afforded to this MPU by the OEM boys was less than enthusiastic. Despite large campaigns to try and rekindle interest in this area it seems that National are resigned to the fact that SCAMP will forever be known as a Simple Cost effective AMateur Processor.

The fact that demand for the SCAMP has not been overwhelming of late means that there should be plenty of stocks of this device and hopefully Science Of Cambridge will have no supply problems with the MK14.

Zee Micros Mit Z80

Another product launched recently is the latest in micro-computers based on the Z80. The system, from the Micros company, costs £550 and includes a Z80 CPU, monitor in ROM, 2K bytes of RAM, audio cassette interface, video monitor interface, UHF TV modulator,

53 key contactless ASC11 keyboard, power supplies and cabinet. Doesn't sound too bad does it.

The company has under development a BASIC compiler, teletext decoder (I would like to see that — it seems such an obvious move) and a selection of games.

My appetite has been wetted by the above description and I shall try to bring you more information plus photos next month.

Meanwhile, if you want further details contact Micros at 1 Station Road, Twickenham, Middx.

Star Software

Until now there does not seem to have been much point in publishing programs in anything other than the machine language of anything but the most popular of micros. However, the arrival of a range of systems with a BASIC interpreter resident on our market would seem to indicate that there will soon be a demand for programs written in this high level language.

We have been sent a BASIC program which, although too long to publish in full, I feel might be of some interest to many of you. The program provides the opportunity for you to emulate my current hero, that handsome clean cut Luke Skywalker, from the film Star Wars. In case you have been off planet for the last year or so I'll sum up the story for you.

Good guys beat up bad guys.

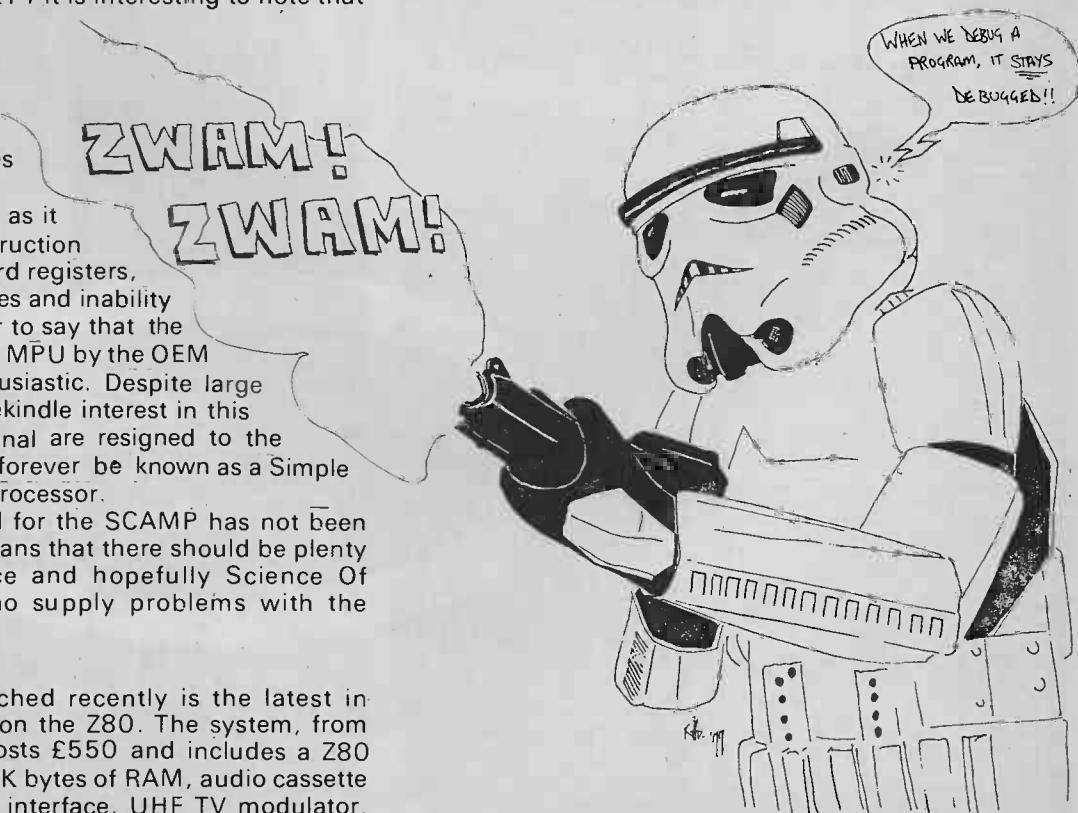


Fig. 1. An extract from Robin Hill's Star Wars program (this talented lad was also responsible for the cartoon). The full BASIC program is available from ETI.

The game program simulates the final bust up that involves a pilot (you) taking his (space) ship down a narrow channel at a (critical) high speed the aim being to release a bomb at the end of the channel at the precise moment in time that will cause it to enter a narrow shaft. While trying this manouvre you can expect to be shot at.

We have only room to show a brief extract from the program, if you want the whole lot please send 25p in

negotiable currency, stamps, POs, cheques (payable to ETI not me)—no live animals please.

Send your monies to:

ETI

Womp Rat Shoot

25/27

London

1

ETI ALARM CLOCK

THE LONG-RUNNING OFFER ON A DIGITAL ALARM CLOCK HAS BEEN ONE OF OUR MOST SUCCESSFUL EVER! OUR PRICE INCLUDES VAT AND POST & PACKING.

£14.50

Our clock shows the time 18Mm high on bright Planar Gas Discharge displays (there is a brightness control on the back) The dot on the left of the display shows AM/PM, and the flashing (1Hz) colon shows that the alarm and clock are working. A bleeping alarm sounds until the clock is tipped forwards. Then the "snooze" facility can give you 5 minutes sleep before the alarm sounds again, and then another 5 minutes, etc., until you switch the alarm off. The clock also features a main-failure indicator and is 12hr ... the alarm beeps 24 hour

We have a large number of units in stock for this offer, but please allow 28 days for delivery.


**CLOCK-OPPER
ETI MAGAZINE
25-27 OXFORD STREET
LONDON W1B 3HP**

I enclose cheque/P.O. for £14.00 (payable to BTI) for an Alarm Clock. Please write your name and address on the back of your cheque.

卷之七


ADDRESS

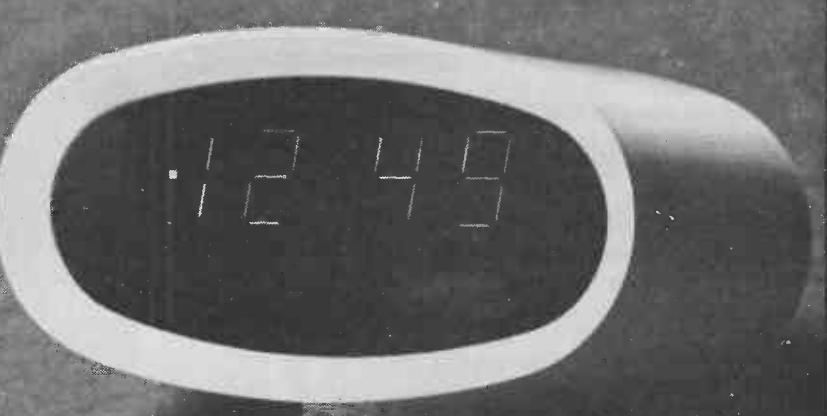Those not wishing to cut their magazine may write on their own notepaper.



Full size is 5in. overall by 1½in. wide.

diges'

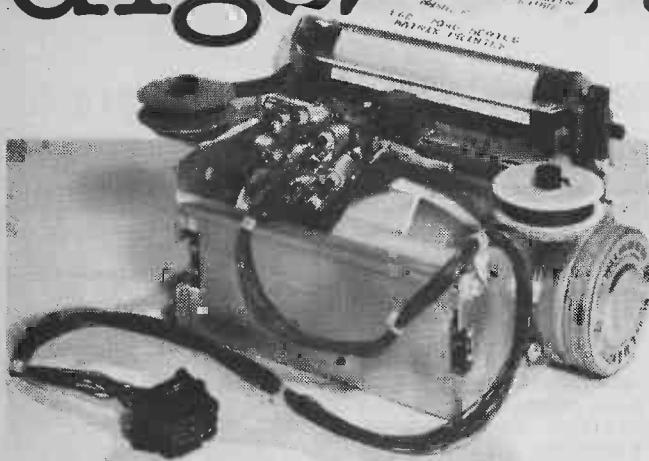


quite a ChArAcTeRXXXXX...

Looking at first glance like a cross between Heath Robinson and IBM, this endearing little machine is actually a compact dot matrix printer introduced by Impecktron Ltd.,

Print speed is one 3.3 in line per second (40 characters) with a character height of 0.123 in. Multiple copies can be arranged, and power supply requirements are 40 V DC at 3.6A peak. (0.8A average). With its small size (8 in x 4 in x 5 in approx.) and low cost the 7040 will probably find many at home. Accessories to extend usage are available. Details from:

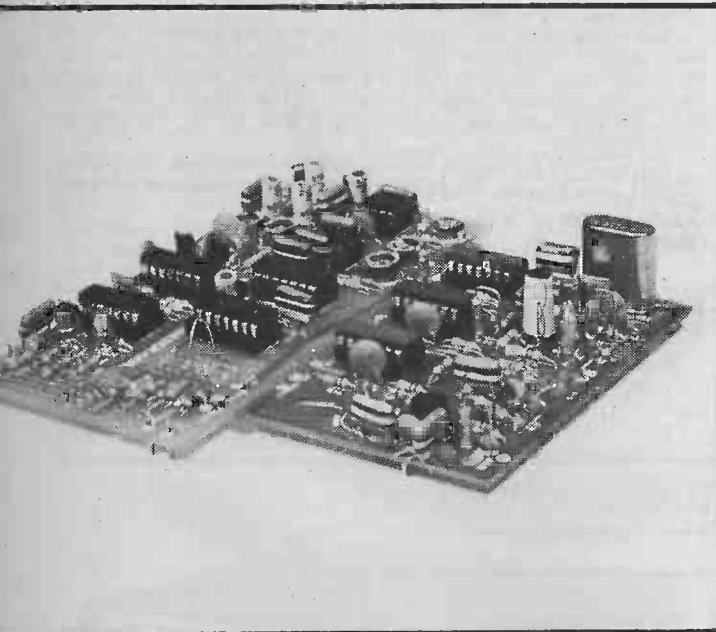Impecktron Ltd., Impecktron House, 23-31 King Street, London. W3 9LH.



amplifying news

A very worthwhile kit of the ETI 100 W amp has come to our attention, using a more compact PCB and output transistors to bring down cost. The board is well made, and top quality components are used throughout. The firm perpetrating the act are Kingsley Services of Newcastle Prices are extremely reason-

able at £16.25 + £2.10 VAT etc. for a built amp module. PSU costs £7.10 + £1.57. Recommended for aspiring 100 W merchants without the confidence to undergo the ritual of the hot iron. Kingsley TV Service, 40/42 Shields Road, Newcastle Upon Tyne, NE6 1DR.

ETIPRINTS

In case you have missed out on ETIPRINTS thus far, they are a complete PCB pattern already to rub down in seconds. The patterns are produced from our original artwork so that the results they produce are nice and sharp.

We think that ETIPRINTS are such a good idea that we have patented the system (Patent numbers 1445171 and 1445172).

ETIPRINTS 005 is now available, and joins 001-004 as part of the regular system.

Details of ordering the ETIPRINTS are shown below.



Lay down the ETIPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!

ORDER TODAY

Send cheque or P.O (payable to ETI Magazine) to:-
ETIPRINT
ETI MAGAZINE,
25/27, OXFORD STREET, LONDON. W.I.R. 1RF.

75p

Inc. VAT and P & P.

Please indicate clearly the ETI PRINTS you require. Those available at present are:

- 001** With patterns for skeet, clock board A, and the compander from Nov 77 plus the spirit level, three-channel tone control, and the digital thermometer from Oct 77.
- 002** With patterns for the burglar alarm from Jan 78 plus clock board B and the rev monitor from Dec 77.
- 003** With patterns for hammer throw and race track from Jan 78 plus the freezer alarm from Dec 77.
- 004** With patterns for the ultrasonic transmitter-receiver, metronome, IB metal locator and porch light from Feb. '78 plus 5/ w stereo amplifier Mk. 2 from Jan. '77.
- 005** March 77 issue projects, including howlround suppressor, RMS voltmeter, LCD panel meter

Readers please note that in earlier ads the contents of 002 and 003 were reversed. Would you please indicate when ordering from which issue the patterns you require were taken.

electronics tomorrow.....

by John Miller-Kirkpatrick

SIT up its the COPS

Regular readers will be able to cast their minds back to the MM57109 calculator chip mentioned a few months ago. This was a programmable calculator chip which could be interfaced to PROM, RAM, LEDs and Flags as well as to an MPU. Well, the MM57109 was part of the Calculator Oriented Processor System (COPS) from National Semiconductor. Two new COPS based chips have now been announced which use calculator style logic to give complex timing applications a new simplicity.

STAC (Standard Timer And Controller) is a 28 pin IC which uses a calculator style keyboard and LED readout to perform the functions of a digital clock and appliance timer. Typically STAC is connected to a 10 position keypad and a four digit LED display. The chip will run from 50 or 60 Hz and in 7 or 8 day cycles. The keys allow fast and slow setting of time and day and alarm times, manual over-ride, test mode and data entry mode.

Alarming Facilities

STAC is basically a four digit mains driven clock which operates from a low power supply of about 9 volts. The first obvious additional feature of STAC is that it has four alarm times and four alarm outputs, but that's not all. At each alarm time each of the four alarm outputs may be switched on, off or left as it is. One of the problems of a central heating system is that at the end of an ON cycle the main tank is full of hot water which will not get circulated as the pump is turned off with the water heating system. With STAC you could program the boiler to turn off at 10.00 but the pump to continue circulating the heated water until 11.00. In this application the boiler could be connected to STAC output 1 and the pump to STAC output 2, your anti-burglar lights are controlled by STAC output 3 and your morning 'wake-up' alarm by STAC output 4.

So far STAC seems to be quite a nice home timing system except that you may not want the anti-burglar lights on every night, perhaps only on Fridays and Saturdays when you are usually out. Similarly you do not want the alarm to wake you on Saturdays and Sundays. No problem for STAC, it has a day counter (1-7 or 1-8) and the facility to switch as per program each day or to ignore switching and simply perform as a clock. This facility opens up applications which should be familiar to many schools and Open University students. Now you can go away for the weekend and program STAC to record your TV or Radio lessons at 10.30 on Friday night and 6.30 on Sunday morning (especially if one is

radio and the other TV). STAC will turn on the radio at 10.25 on Friday, the tape at 10.29, TV 6.25 Sunday and TV recorder at 6.29.

Standard Interval Timer (SIT)

The second COPS based chip is called SIT and like STAC uses the mains frequency, simple power supply, keyboard and display. With SIT the features include 99 hr, 59min, 59.9 secs timing range; count up or down; metronome and relay driver outputs; sequential cycling and 4 event stopwatch mode.

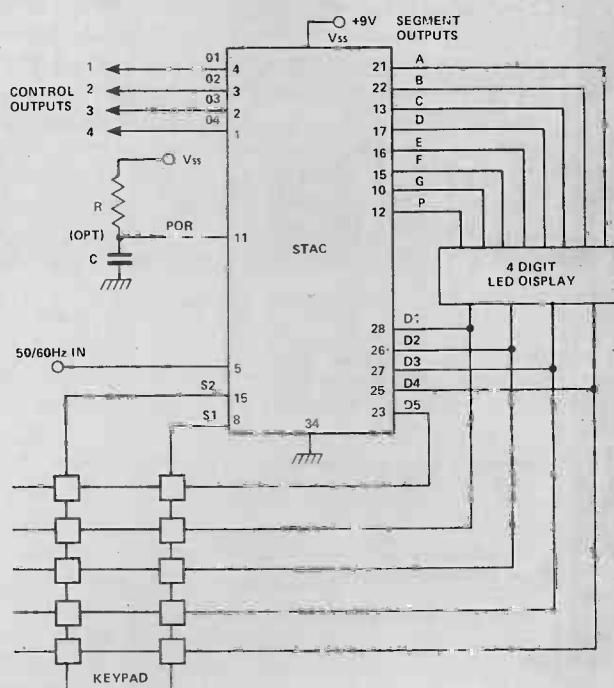


Fig. 1. Typical STAC circuit

The timing period data is entered from a numeric keyboard which is also used to enter commands to indicate up/down counting, stopwatch or timer mode, RUN, CLEAR and HOLD commands.

Keying 'RUN' places the working register on the top of the four entry stack and then rolls the stack to the next entry and the count continues. Thus the last four times at which RUN was enabled are stored for viewing.

'SEQ' is similar to RUN except when pressed the working register is cleared at each enable time. Thus the stack contains the last four times between SEQ enables.

'HOLD' operates in one of two ways depending on whether RUN or SEQ initiated the operation. In either mode it does whatever is required by RUN or SEQ and then stops the count after rolling the stack and clearing the working register if required. The unit will now wait for the next operation of RUN or SEQ.

Four indicator lines are available to show when the stack is at entry a, b, c, or d, each of these lines can directly control an LED lamp. These outputs are also useful in the timing sequence mode to provide activation signals to external equipment.

For further details of STAC, SIT or other COPS chips contact National Semiconductor at 19 Goldington Rd, Bedford. The chips should cost under £10 each and may be available from National outlets.

Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items.

ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for. Drawings should be as clear as possible and the text should preferably be typed. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International, 25-27 Oxford St., London W1R 1RF.

tech


Capacity checker

D. Chivers.

This bridge was originally designed to find values for odd, unmarked or undecipherable capacitors. While not being of great accuracy, it does give a very good indication as to the value of the capacitor.


A known value component is placed across terminals A-A, polarity is not important, but polarised capacitors must not be used, and cannot be tested. The capacitor under test is inserted in B-B, the unit is switched on and VR1 rotated until a maximum value reading is obtained on meter M1. At this point, a reading is taken from the calibration scale on the pot which initially must be calibrated in ratios, ie:

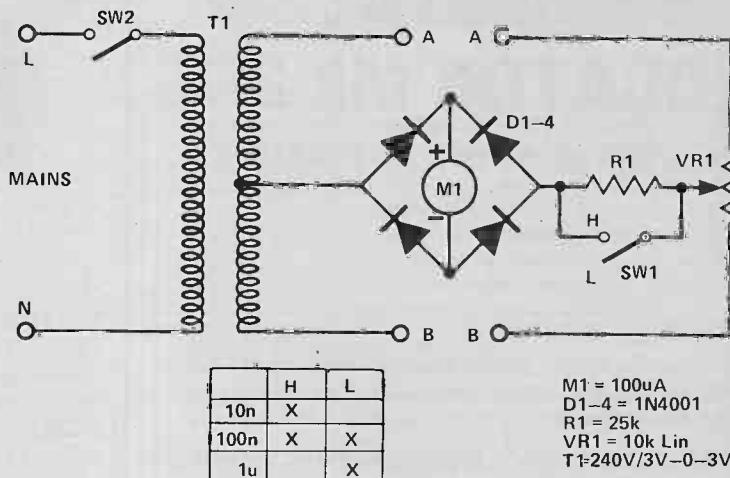1000:1, 100:1, 10:1, 1:1, 1:10, 1:100 etc. The unknown value is then calculated from this reading. Original calibration is from known values.



To increase the range of the circuit switch SW1 has been included to bypass R1. Since the frequency used is 50 Hz from the mains, ranges are limited; if

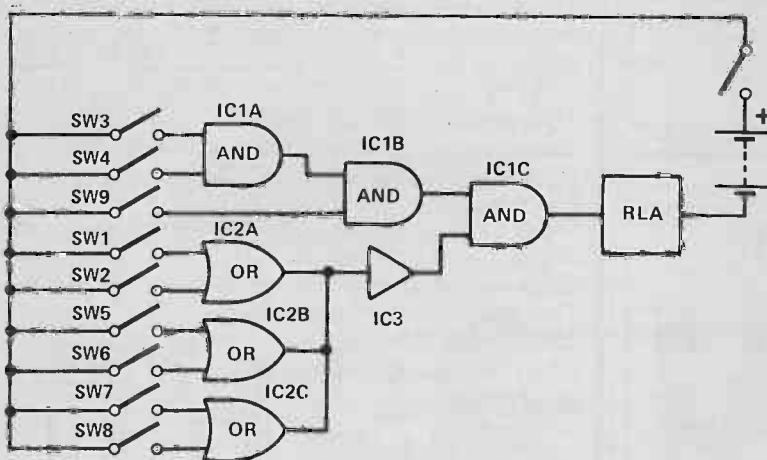another source were used, driving an audio output transformer, the versatility of the unit would then be further increased.




Selective alarm controller

S. Butler.

This circuit provides greater versatility than the simple "in-series" switches mode of alarm, but is still cheap and easy to build.

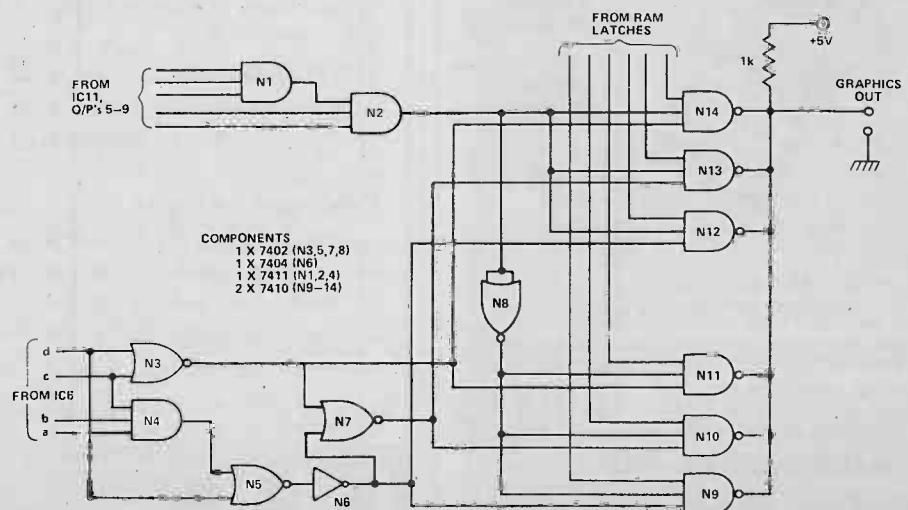When SW3 and 4 are closed, the output of the AND gate goes high. This high is fed to the second AND gate only when SW9 is pressed. The output of this gate goes high and providing no other switches are pressed, it will operate the relay: if any other switches are pressed, the OR gives an output to the inverter and cuts off the power to the AND gate, preventing the coil being energised.




Seven to binary with a special bit!

T. Nash.

This circuit, which uses only four TTL or CMOS ICs, converts a seven segment digit to binary, with indication of the 'special' characters: minus, E (exponent or overflow), and optionally blank. Both types of 6, 7 & 9 can be handled, and for ease of manipulation blank is encoded as binary zero.

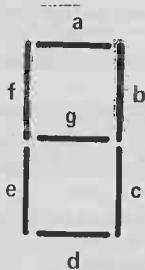For a calculator - microprocessor interface the 'X' output should be fed to the sign position for ease of testing: this method is more economical in time and memory space than testing for a specific binary value. The extra bits needed for the equivalent ASCII character could also be added at the interface.



The segment identification shown above is the standard seven segment lettering system and so should be familiar to most constructors.

The letters also refer in this case to the circuit diagram and the truth table given below on the right hand side of the page.

No power supply connections are shown for the circuit as this depends on which version, TTL or CMOS is constructed.


Graphics for the 560 VDU

M. Jackson

This circuit can be added to the 560 VDU published in ETI in September 1976 to allow the display of simple graphics. The rows and columns of each character position are gated by N1 to N8 to make up the graphic character sections. This information is ANDed with the RAM data to determine whether or not a particular section is on or off.

The graphics/character selection may be controlled by the spare bit in RAM after it has been latched.

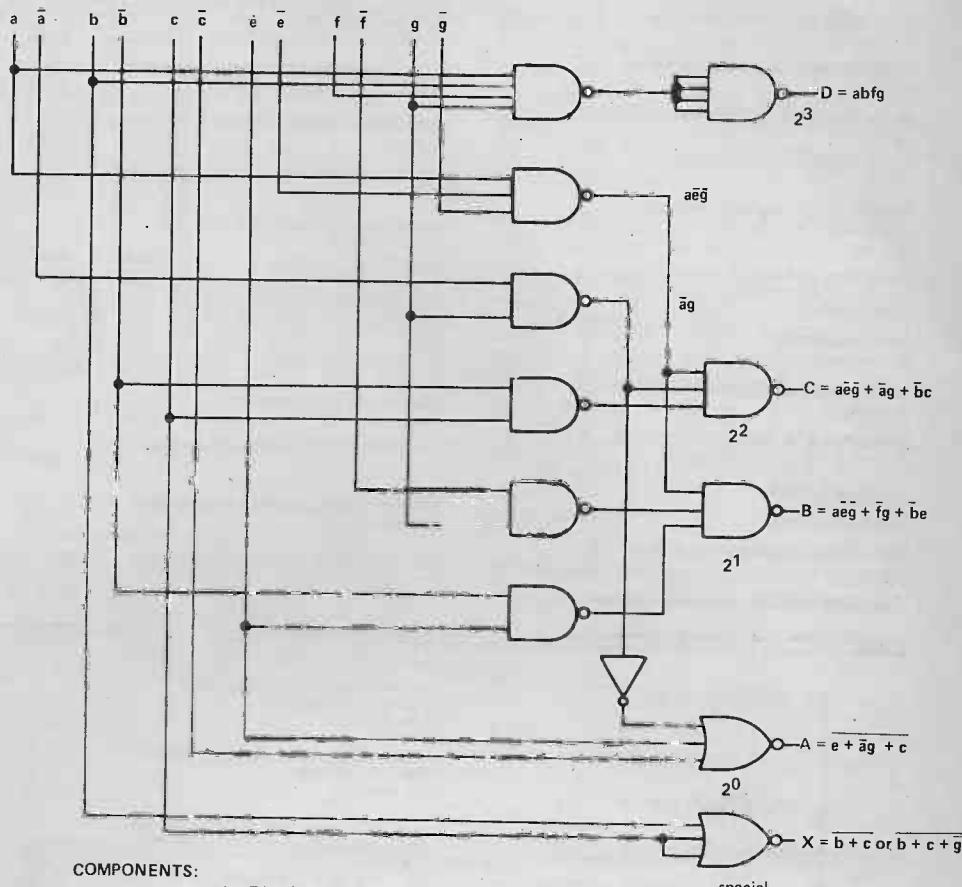Note: RCLK must be disconnected otherwise blank lines will appear in the graphics display.



COMPONENTS:

1 x 7400/4011 FIRST VARIATION SETS X FOR
1 x 7410/4023 BLANK, SECOND DOES NOT.
1 x 7420/4012
1 x 7427/4025/4000 (4000 SHOWN)

* FOR TTL AND 4025 VERSIONS, use 3 input nor.

SEE DIAGRAM

TRUTH TABLE

7-SEG	a	b	c	d	e	f	g	D	C	B	A	X
BLANK	0	0	0	0	0	0	0	0	0	0	0	*
0	1	1	1	1	1	1	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	1	0
2	1	1	0	1	1	0	1	0	0	1	0	0
3	1	1	1	1	0	0	1	0	0	1	1	0
4	0	1	1	0	0	1	1	0	1	0	0	0
5	1	0	1	1	0	1	1	0	1	0	1	0
6	0	0	1	1	1	1	1	0	1	1	0	0
6	1	0	1	1	1	1	1	0	1	1	0	0
7	1	1	1	0	0	0	0	0	1	1	1	0
7	1	1	1	0	0	1	0	0	1	1	1	0
8	1	1	1	1	1	1	1	1	0	0	0	0
9	1	1	1	0	0	1	1	1	0	0	1	0
-	0	0	0	0	0	0	1	0	1	1	1	1
E	1	0	0	1	1	1	1	0	0	1	1	1

Channel splitter for radio control

G. Bathe.

This circuit is designed to replace the electromechanical reed units used as channel-splitters in radio controlled models.

The circuit is based on the MC 1310P integrated circuit, a chip that is primarily a stereo decoder for use in stereo radio tuners. When used as a stereo decoder, the MC 1310P automatically switches itself from the mono mode to the stereo mode whenever its input contains the 10 kHz subcarrier of a stereo multiplex signal at a sufficiently high level (16 mV). It can be triggered by noise if the noise level is greater than 16 mV. Some radio control transmitters tend to transmit noise when they are not transmitting a tone, and if this is the case the transmitter should be modified to prevent noise being transmitted. This could be done by making the transmitter transmit an extra unused tone whenever it is not transmitting one of the used audio tones.

It is this lamp driver facility of the MC 1310P that makes it an ideal chip to use as a channel-splitter. When used as a channel-splitter the circuit is not tuned to the 19 kHz of the stereo decoder but to the audio frequency that the circuit is required to detect, and the lamp driver output from pin 6 is used to drive a power transistor controlling a motor or other device.

The output from the detector of a radio receiver is amplified by the BC 108 and then fed into a series of MC 1030P channel-splitters (connected in parallel) each tuned to a different audio frequency.

The audio frequency to which the channel-splitter responds is determined by the tuning circuit R1, VR1 and C1, and is given by the formula:


$$f = \frac{1}{2\pi C_1 (R_1 + R_{V1})} \text{ Hz}$$

The value of C1 is chosen to give the required tuning range for the preset RV1. For example, if C1 is 10,000 pF, then the tuning range is approximately 750 Hz to 1,000 Hz.

The output is a switched current output between Pin 6 of the chip and the positive supply rail. This current should not exceed 35 mA and so a 470 ohm resistor is inserted in the output connection from Pin 6 as short circuit protection. If a voltage output is required then a resistor can be connected from Pin 6 to the positive supply and the voltage output taken from Pin 6.

The MC 1310P is triggered when the input to Pin 2 contains its tuned frequency at a level greater than 16 mV. It can be triggered by noise if the noise level is greater than 16 mV. Some radio control transmitters tend to transmit noise when they are not transmitting a

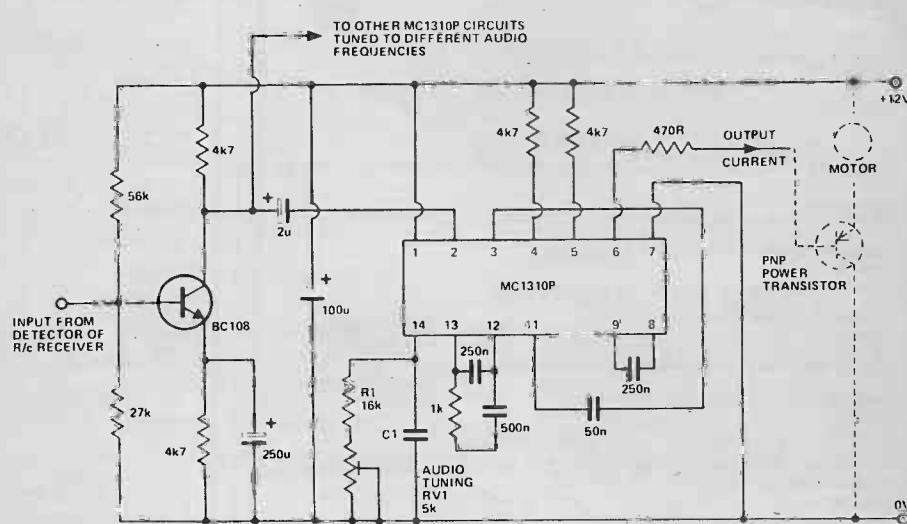tone, and if this is the case the transmitter should be modified to prevent noise being transmitted. This could be done by making the transmitter transmit an extra unused tone whenever it is not transmitting one of the used audio tones.




Novel loudspeaker coupling circuit

P. Mills.

In most amplifier designs the speaker is fed by a high value capacitor to provide DC blocking, but this may result in a heavy switch-on surge, as the capacitor charges up.

An alternative approach, which is worthy of experiment, is shown in the diagram below. Here the ground side of the speaker is connected to the junction of two equal high value capacitors (1000 μ F is typical), across the supply.

The amplifier output voltage will be at $V_s/2$, and so will the voltage across C_1 (if C_1 and C_2 are equal); so as the supply voltage builds up, the DC voltage across the speaker will remain zero, eliminating the switch-on surge. C_1 and C_2 will also provide supply smoothing. The circuit is shown with the LM380, but could be applied to any amplifier circuit, providing that the DC voltage at the output is half the supply voltage.

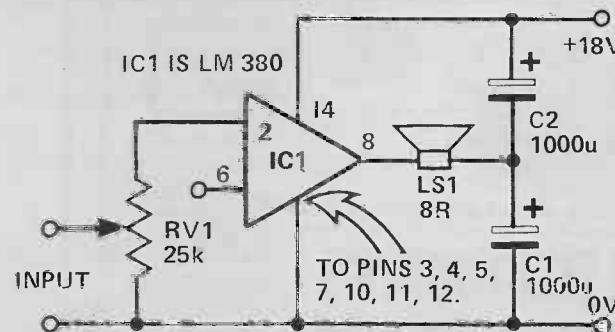



Gaps?



Gaps?

It can be a nuisance can't it, going from newsagent to newsagent? "Sorry squire, don't have it - next one should be out soon."

Although ETI is monthly, it's very rare to find it available after the first week. If it is available, the newsagent's going to be sure to cut his order for the next issue - but we're glad to say it doesn't happen very often.

Do yourself, your newsagent and us a favour. Place a regular order for ETI; your newsagent will almost certainly be delighted. If not, you can take out a postal subscription so there's nothing for you to remember - we'll do it for you.


For a subscription, send us £6.00 (£7.00 overseas) and tell us which issue you want to start with. Please make your payment (in sterling please for overseas readers) to ETI Subscriptions and keep it separate from any other services you want at the same time.

ETI Subscription Service,
Electronics Today International,
25-27 Oxford Street, London W1R 1RF.



... news

key development

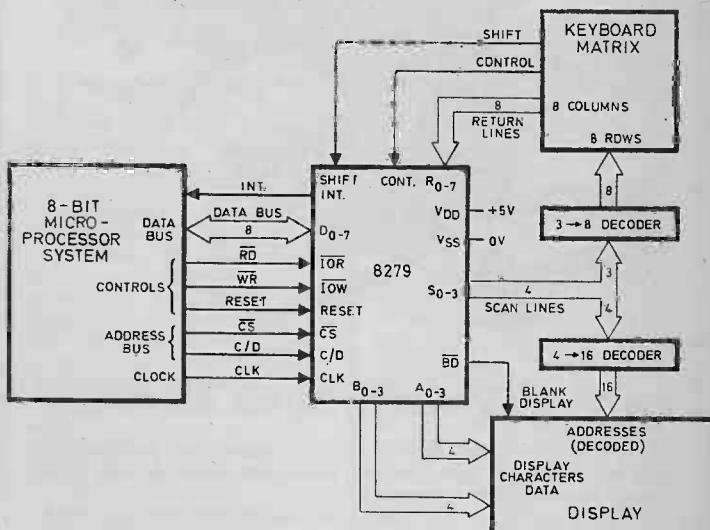

Since Data input and display form an important part of microprocessor systems, a new Intel device, a new programmable single-chip keyboard/display interface device. Known as the 8279 will be of interest to many. The device is suitable for use with 8-bit microprocessors, (such as the 8080A) it relieves the CPU in a system from the task of monitoring and servicing the keyboard, and from updating the output display.

Key depressions can be either 2-key or n-key rollover. All keyboard entries are 'de-bounced' within the chip and are stored in a first-in, first-out memory (FIFO) where they are queued for input to the microprocessor when it has time to read them. If more than eight characters are loaded into the FIFO, the 8279's overrun status flag is set.

The CPU has full access to the display memory and the display memory address can be incremented automatically on memory read or write.

Intel Corporation (UK) Ltd., 4 Between Towns Road, Cowley, Oxford, OX4 3NB.

game set

The FTC in America has come out with a report on tests they conducted which show that normal use of a TV game will not result in damage to a set. And about time, too.

not much scope



The MS15 is a completely new battery oscilloscope manufactured by Non Linear Systems. Sockets are provided for external triggering and X deflection and a one volt internal calibrator is provided. Lawtronics Limited, 139 High Street, Edenbridge, Kent. TN8 5AX.

digest...

bit on the out-side

The BBC has recently been using an experimental 2-channel digital transmission system to assess the feasibility of conveying high-quality stereo sound programme signals from OB sites to London in digital form.

When signals originating at Outside Broadcast (OB) sites are to be propagated throughout the UK, they have to be sent first to London where they are mixed into one or other network programme. Analogue contribution circuits are normally used for this purpose, but their quality is generally inferior to that of the digital distribution circuits that take the signals out from London to the network

of VHF transmitters

The first two broadcasts handled in this way were of a 'Music to Remember' concert at Cardiff on 4th December 1977 and a concert at Lancaster University on 15th December. In both cases the digital signals were transmitted on a radio link from the OB site to a convenient BBC centre, using 4-phase DPSK (differential phase shift keying) modulation. They were then conveyed to London in suitably transcoded form on a television circuit, and mixed into the Radio 4 programme.

This meant that the transmitted signal quality was virtually identical to that at the OB site itself.


its a wide word

Intel, Zilog and Motorola are taking their places in the front rank on the grid for this year's expected race to 16 bit MPU sales. All three have completed development, and will probably show the nature of

On yer marks

their teeth at next month's US Solid State Circuits Conference. The pause between this and letting loose of the hounds as it were will almost certainly mean late autumn production.

driven to LCD?

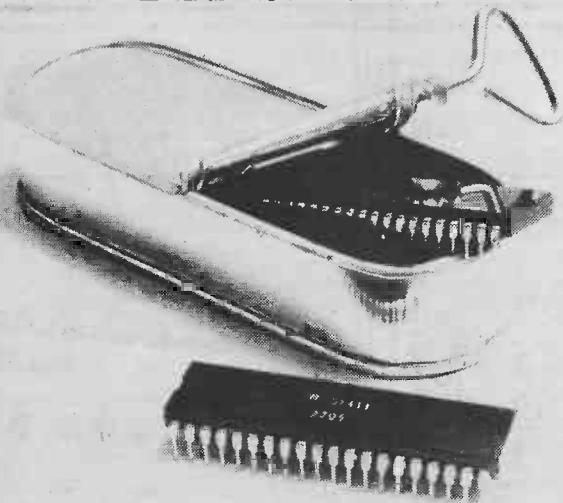

This new DF411 Siliconix chip carries on board all the clever bits necessary to decode and display up to four multiplexed digits of BCD information in liquid crystal fashion. They can be persuaded to gang up if more than 4 digits are required. Supply requirements are 3-8 V.

Siliconix Ltd., Morristor, Swansea, SA6 6NE.

LINES FROM OUR VAST STOCK Please add post 35p per order.
THESE ARE ALL SPECIAL OFFERS BELOW MANUFACTURERS PRICES ALL NEW STOCK. FULLY GUARANTEED All prices inclusive of VAT
EXPORT ENQUIRIES INVITED ON ALL ITEMS

HENELEC
RADIO
CONTROL
SYSTEM

Booklet No. 8
Available 50p

★ INCLUDING PROPORTIONALLY CONTROLLED SWITCH
★ FEATURING COSMOS DIGITAL LOGIC to minimise power consumption and extend battery life.

Six button selector switch with built in 100K pots. Self cancelling buttons. Ideal for use with varicap tuned FM sets and TVs. 120x64x55mm £2.10 for £1.15.

BOWMAR 9 digit calculator display with P.C. connector 0.15" digits. common cathode with red bezel. £1.25. 10 for £10.

TEXAS 19 gold-plated snap key contacts on gold plated P.C. Board — all kinds of useful applications. Size 70x80x2mm Height 65p. 10 for £5. 100 for £40.

OSMOR change over reed relay with 12V coil. Approx. 20mA operating current. 59x17x13mm 95p. 10 for £7. 100 for £50.

Small mains transformers with 240V pri. 12V @ 100mA 60x40x24mm 95p. 10 for £7.50.

Valve type 40.1 Output transformer 61x51x42mm 75p. 10 for £8.

Output transformer for EL84 type valves 80x53x34mm 95p. 10 for £8.

Clocking oscillator PYE DYNAMICS thick film 1MHz 5V supply 19x25x6mm 85p. 10 for £7. 100 for £55.

FAIRCHILD FND 10.0.15" 7 segment display. Common Cathode 50p. 10 for £4.50. 100 for £30.

SPECIAL OFFER BUILT AMPLIFIERS

6+6 WATT STEREO 24/28V 8ohm
Input 50/60 M/V. Into 500K
Tone Controls on P/C £4.95
4 pots £3.50 extra
Size 15.5 x 14 x 4.5 cm
WITH CIRCUIT

10+10 WATT STEREO PAS/25
Input 300 M/V. Into 100K
Size 18 x 7.3 x 4.8 cm
24 volt £5.95
4 ohm
WITH CIRCUIT

Built 5 watt power amplifier Gould-Advance. 4.8 ohms output, up to 24V supply. 500mV into 2K input. Complete with instructions. 11.5x6x3cm £3.00. 10 for £22.50.

Suitable power supply for above, in kit form. £2.20.

HONEYWELL Proximity Detector Integral Amplifier 8V DC £2.50 ea. 10 for £22.

BRAUN Digital 24-hour clock with alarm. Large illuminated numerals, silent running, AC mains. Size 150x60x70mm. Excellent value. £6.50 ea. 3 for £18.50. 10 for £50 less case.

SUPPLY PANEL containing 6 high quality 0.1μF 10% 1KV poly capacitors, 102x19x75mm 35p. 10 for £2.50.

ALMA push-button Reed switches. push to make. High reliability. 18x27x18mm 25p. 25 for £5. 100 for £20.

BURROUGHS 9 digit Panaplex calculator display. 7 segment, 0.15" digits. neon type, with red bezel, socket and instructions. £3.50. 10 for £30.

TV sound converter through your FM tuner module. Complete with instructions £5.50.

I.C. Audio Power by TOSHIBA 35 WATT module. 8 ohms o/p 200mV into 47K for full output. 0.3% distortion (max). 60V power supply required. £8.50. 10 for £75.

10.7MHz crystal filters. Size 35x25x20mm. 25KHz band width for NBFM. £7. 10 for £60.

TEXAS 4+5 Digit C. Cathode Display with 16 pin DIL Base
Pair £1.50. 10 pairs £12.50.

2½" 40 ohm speaker 250 M.Watt — Ideal for that small space. 75p. 10 for £8. 100 for £50.

3 DIGIT 7 SEGMENT DISPLAYS. C cathode pack of 2 with data (one or more segments are missing) 60p pack. 10 packs for £5.

TBA 120s 75p. 10 for £7. 100 for £55.

TTL Pack of 8 gates 7420, 7430, 7451 60p. 10 packs £5. Pack of 6 gates and complex 75p. 10 packs £6.50.

10 Pack of BC171A Transistors BC107 Plastic 75p. 10 packs £6. 100 £50.

SOLDER at half price. 50g pack of 2 metres 18 gauge Servicel £1.20.

AVO meter movements for a military version of the Avo 8 Precision 3/5 micro Amp. 50μA with integral shunt movement. Electronic voltmeter circuit available on request. £8.50.

28 pin calendar/clock chip type MK501 7BB for use with common cathode LED display (with circuit) £4.49.

MK50250 Alarm clock chip for most LED displays. £2.50 with circuits.
5012 12 digit calculator chip. 4 functions, with circuits and data. £2.50.

VITALITY 12V 0.15 amp. MES Bulbs. 100 for £5. 1.000 for £40.

BECKMAN 500KHz triggerable clocking oscillator for use with calculator chips etc. 5V supply. 25x10x12mm £1. 10 for £8. 100 for £65.

Re-settable thermostatic switch. A push button on-off switch which automatically drops out when the ambient temperature exceeds 72°C. 47x29x46mm 75p. 10 for £6.50.

FT243 crystal packs. 10 crystals of mixed frequencies between 5800 and 8500 KHz (Our choice of frequencies. Ideal for re-grinding). £1.50 per pack. 10 packs £10. 100 packs £85.

Ditto. 10X packs of 10 crystals. 250 Kc s-50 mc ~ £1 pack. 12 packs £10. 100 packs £70.

Calculator chip CT5002 12 digit four functions for common cathode multiplex displays. ONLY £1.95 complete with circuit.

1 MHz HC6U quartz crystals. For frequency meters, clocks, frequency references etc. 17x19x7mm £3. 10 for £27.50.

TAPE HEADS 1 track Record Marrott XRP36 £5. XES11 eraser £1.25.

T4/RF LONG-MEDIUM & F/M TUNER WITH MC1310 DECODER ★ 5-BUTTON SELECTOR SWITCHES ★ INPUT SELECTORS FOR GRAM AND TAPE ★ Supplied complete with FRONT-END TUNER AND FERRITE AERIAL ★ SIMPLE INTERCONNECTIONS ★ Size 19x13cm

THIS QUALITY AMPLIFIER £10.95 WITH CIRCUIT


POWER UNIT KIT FOR ABOVE MODELS 25/28 VOLTS £2.95.

FREE ILLUSTRATED EQUIPMENT + VALVE AND TRANSISTOR LISTS
S.A.E. 9½" x 6½" 12½ p stamp



All mail to: Henry's Radio 404 Edgware Rd, London W2

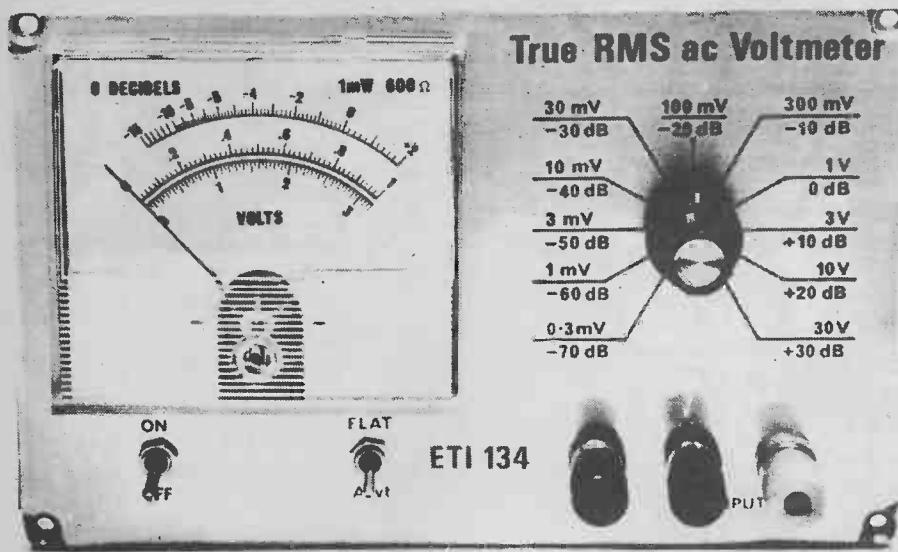LONDON W2 404 6 Edgware Road Tel 01 725 1008



The use of a special IC results in performance greatly improved over conventional designs.

TRUE


RMS VOLTmeter

MOST METERS which can measure AC signals do so by rectifying the signal and then measuring the average voltage. With a sinewave the average voltage is 0.637 of the peak voltage while the RMS value is 0.707 of the peak. Therefore a correction factor of 1.11 is built into the meter to give the RMS value of the signal.

Provided you stick with sinewave signals these meters are adequate. With any other waveform, however, they are not accurate. With a square wave the error is 11% and with pulse wave forms the error increases.

Before continuing we should explain what RMS means and its significance. Without getting mathematical, the RMS value of any wave form is the same as a DC value which would produce the same heating effect in a resistor. For example:

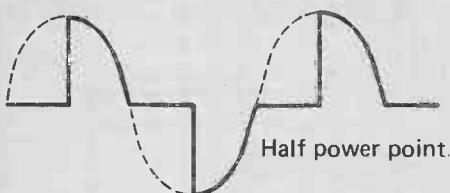Power in a load can be varied by using phase control (i.e., light dimmer) where the time the load is connected to the mains is variable. The RMS value is difficult to calculate except at the point where it is half on-half off. The power then is obviously half power.



If the input voltage is 240 V and the load is 240 ohms the power (maximum) is given by

$$P = \frac{E^2}{R} \text{ or } \frac{240 \times 240}{240} = 240 \text{ W}$$

Half power therefore is 120 W. The voltage corresponding to this is given by

$$E = \sqrt{P \times R} \text{ or } 170 \text{ V (RMS).}$$

On a "normal" meter this will read 120 V or an error of 30%.

This design uses an RMS detector IC, which is basically a small, special-purpose analogue computer to mathematically calculate the true RMS value for any waveform.


Design Features

The design of the voltmeter is basically simple, starting with an attenuator in the front end, then an amplifier with a high input impedance and switchable gain which, with the attenuator, gives the range selection. A filter is then added to give the "A" weighting and the RMS detector IC (LH 0091) does the rest

The output of the input amplifier is 60 mV, independent of range selected, for an input corresponding to the full scale reading. This gives a maximum gain of 46 dB on the 0.3 mV range. There is a loss of about 2.3 dB in the filter (at 1 kHz) and the spare amplifier in IC2 is used to provide a gain of 20 dB giving 500 mV (for full scale reading) before the RMS detection is done. The RMS detector has unity gain with 500 mV RMS in giving 500 mV DC out.

However things are never that simple. With a total of 60-odd dB gain, along with the requirement for a 1 M input impedance, we have an excellent formula for an oscillator. With the third try (yes, we have failures too) with ade-

PROJECT: RMS Voltmeter

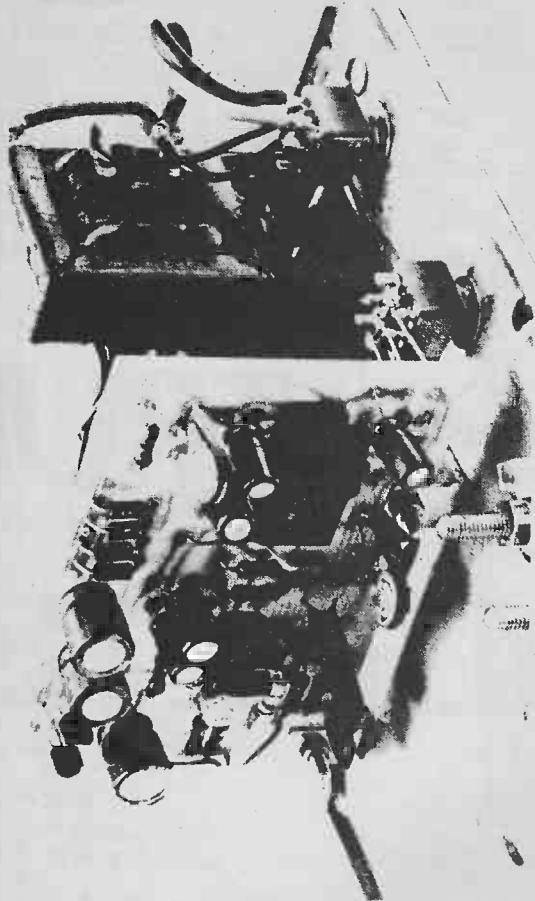

Internal view of the RMS voltmeter, showing how the PCB is mounted within the box relative to the mains transformer.

PARTS LIST

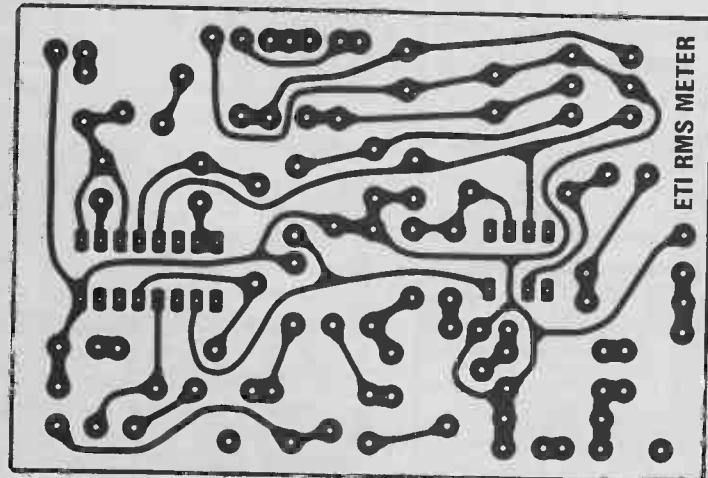


Fig. 4. Printed circuit layout.
Full size 90 x 60mm.

RESISTORS

All $\frac{1}{2}$ W 5%, except where marked.

R1	1M	1%	RV1	100k
R2,6	100k	1%	RV2	200R
R3,7	10k	1%	CAPACITORS	
R4,16	12k	1%	C1,9,10	100n
R5	150k		C2*	15p
R8	56R	1%	C3*	150p
R9	1k		C4*	1n5
R10	120R	1%	D1-D4	1N4001 or similar
R11	3k9			
R12	390R	1%	SWITCHES	
R13,19	47k		SW1	
R14	1k5	1%	SW2	
R15,17	39k		SW3	
R18,20,21,24	27k			
R22,23	270k			
R25	330R			

POTENTIOMETERS

RV1	100k
RV2	200R

All capacitors should be as accurate as possible as they affect accuracy above 10kHz.

MISCELLANEOUS

T1	28 V secondary
M1	Meter 1mA scaled as shown
CA3140	3 terminals (red, black, green). Box to suit,
LMH0091	Metal brackets and shields, 3 core flex and
78L15	plug, 16 pin socket for IC2, Knob,
79L15	
1N4001	
SW1	2 pole 11 position SPDT miniature toggle switch
SW2	DPDT miniature toggle switch
SW3	25 V 100u