

electronics today

INTERNATIONAL


OCTOBER 1985 £1.10

COUNTERTIMER
PULSE GENERATOR
WAVEFORM GENERATOR

MODULAR TEST GEAR TO BUILD



DIGITAL SOUND
SAMPLERS

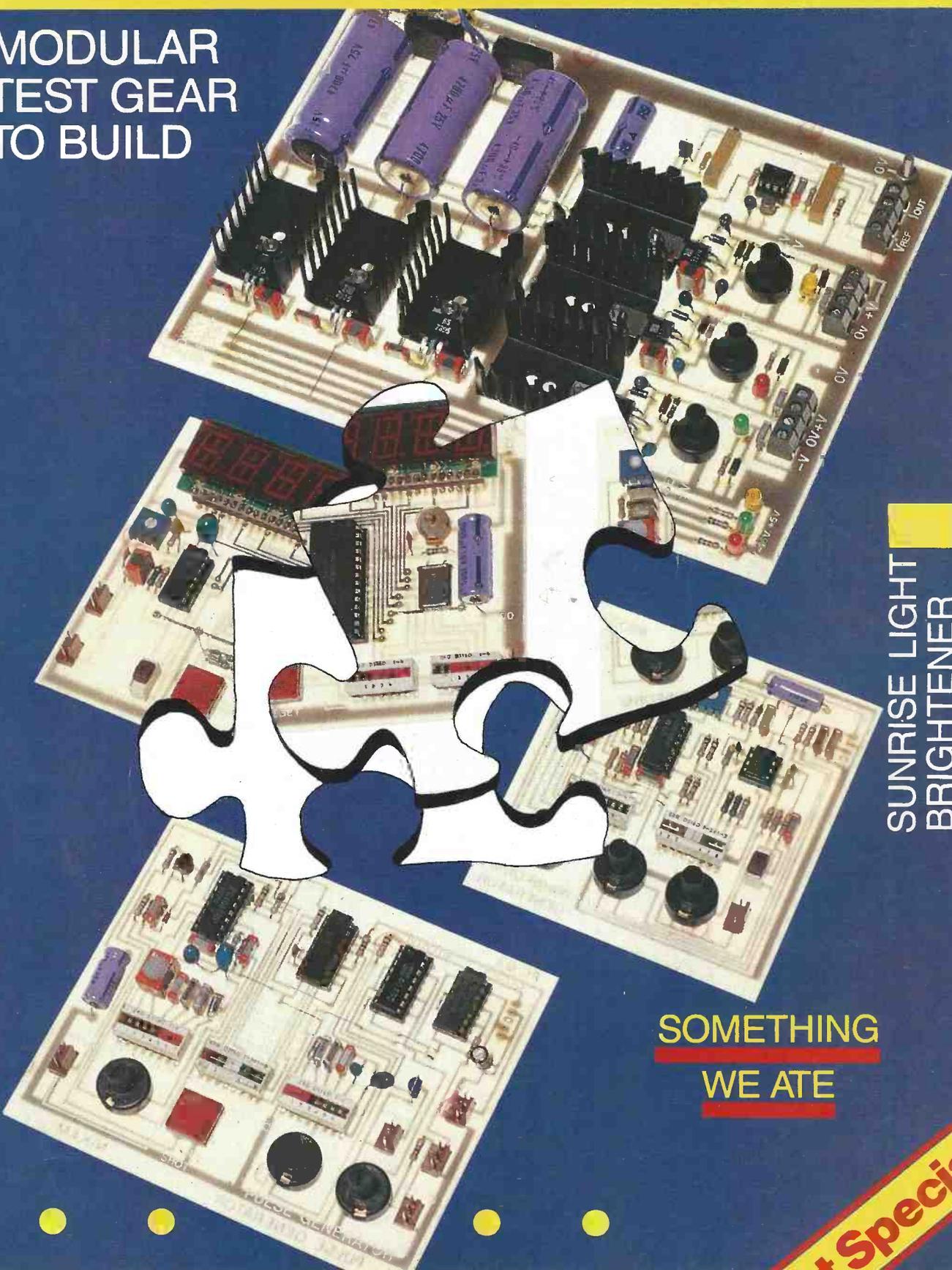

SUNRISE LIGHT
BRIGHTENER

SOMETHING
WE ATE

Test Special

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible VU meter. Open and short circuit proof. **Supplied ready built and tested.**

OMP 100 MkII Amp. Module 110wR.M.S. 4ohms I/P Sens 500mV - 10K. Size: 360 x 115 x 72mm. Price: £32.99 - £2.50 P&P.
OMP/MF100 Mos-Fet. Very high spec: 110wR.M.S. both 4 & 8ohms I/P Sens. 500mV - 10K. Size: 300 x 123 x 60mm. Price: £39.99 + £2.50 P&P.
OMP/MF200 Mos-Fet. Very high spec: 200wR.M.S. 4ohms I/P Sens 500mV - 10K. Size: 300 x 150 x 100mm. Price: £62.99 + £3.50 P&P.
OMP/MF300 Mos-Fet. Very high spec: 300wR.M.S. 4ohms I/P Sens. 500mV - 10K. Size: 330 x 147 x 102mm. Price: £79.99 + £4.50 P&P.
 VU Meter: 11 LED's. Plastic Case. Size: 84 x 27 x 45mm. Price: £8.50 + 50p P&P




MF100

LARGE (28p) S.A.E. FOR CURRENT LIST

PIEZO ELECTRIC TWEETERS — MOTOROLA
 Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.90 each + 40p P&P
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P.
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £6.99 each + 40p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £9.99 each + 40p P&P.
TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £5.99 each + 40p P&P.

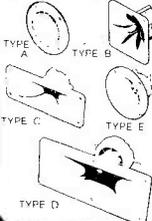


Full specifications available on request.

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV) If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV) Order - Standard or P.A.

19" STEREO RACK AMPS

Professional 19" cased Mos-Fet stereo amps with twin VU meters, twin toroidal power supplies, XLR connections, MF600 Fan cooled. Three models (Ratings R.M.S. into 4ohms).
MF200 (100 + 100W) £169.00
MF400 (200 + 200W) £228.85
MF600 (300 + 300W) £274.85

Securicor Delivery £10.00

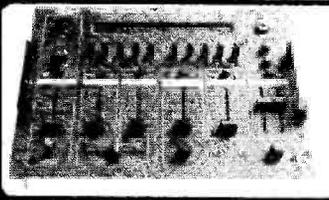

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. VU Meters. Many outstanding features 5 Inputs with individual faders providing a useful combination of the following:—
 3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch, Headphone Monitor Pan Pot. L & R. Master Output controls. Output 775mV. Size 360 x 280 x 90mm.
 Price £134.99 - £3.00 P&P

LOUDSPEAKERS

Cabinet fixing in stock. S.A.E. for details.



LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm. Price £3.99 + 40p P&P.

Loudspeakers 5" to 18". Up to 300W R.M.S. S.A.E. for full lists. McKenzie speakers at advantageous prices. All speakers listed 8 ohm imp.

POWER RANGE
8" 50 WATT R.M.S. Hi-Fi/Disco.
 20 oz magnet. 1 1/2" ally voice coil. Ground ally fixing escutcheon Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £10.99 available with black grille £11.99 P&P £1.50 ea.
12" 100 WATT R.M.S. Hi-Fi/Disco
 50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon Die-cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £28.60 + £3.00 P&P ea.
15" 100 WATT R.M.S. Hi-Fi/Disco
 50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon Die-cast chassis. White cone. Res. Freq. 20Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. PRICE £37.49 + £3.00 P&P ea.
SOUNDLAB (Full Range Twin Cone)
5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £9.99 + £1.00 P&P ea.
6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1 1/2" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 + £1.50 P&P ea.
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 + £1.50 P&P ea.
McKENZIE
12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco.
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £24.99 + £3.00 P&P ea.
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone. Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £24.99 + £3.00 P&P ea.
15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £49.99 + £4.00 P&P ea.

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt). Price: £8.62 x 75p P&P.
3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P.
 3 watt FM Transmitter



POSTAL CHARGES PER ORDER £1.00 minimum

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★



B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX SS2 6TR TEL 0702-527572



MICROBOX II THE 6809 SINGLE BOARD COMPUTER THAT YOU BUILD YOURSELF

VIDEO OUTPUTS KEYBOARD PORT PRINTER PORT SERIAL PORT SERIAL PORT

- SYSTEM EXPANSION BUS
- BATTERY BACKED REAL-TIME CLOCK/CALENDAR
- 128KBYTES SHARED MEMORY RAMDISC
HIGH SPEED SILICON DISC ACTS LIKE A STANDARD 'FLEX' DISC
- ALPHANUMERIC DISPLAY
108 x 24 CHARACTER FORMAT.
USER DEFINABLE CHARACTERS.
STANDARD VDU CONTROL FUNCTIONS
- EXTREMELY FAST, VERY HIGH RESOLUTION GRAPHICS
768 x 576 MONOCHROME DISPLAY
HARDWARE VECTOR GENERATION BY ADVANCED NEC7220 DEVICE. LINE, POINT, ARC, PATTERN, TEXT, AREA FILL ETC.
- POWERFUL 68B09E 8/16 BIT MICROPROCESSOR
- SYSTEM SUPPORT MONITOR (8KBYTES) containing:
DISC AND INPUT/OUTPUT DRIVERS
GRAPHIC PRIMITIVES
TERMINAL EMULATOR
UTILITY AND DIAGNOSTICS
"FLEX" BOOT AND CONFIGURE
- 60KBYTES USER MEMORY
- FLOPPY DISC INTERFACE
SUPPORTS SINGLE OR DUAL, 40/80 TRACK, SINGLE OR DOUBLE DENSITY DISC DRIVES
- EPROM DISC (AND PROGRAMMER)
HIGH SPEED READ ONLY SILICON DISC ACTS LIKE A STANDARD 'FLEX' DISC PROVIDES 'INSTANT' SOFTWARE

*NOTE: MICROBOX II WILL BOOT 'FLEX' FROM ANY STANDARD SYSTEM DISC.

**BARE PCB's AND DOCUMENTATION
 + SYSTEM SUPPORT MONITOR
 + SYSTEM UTILITIES DISC — £95.00
 FLEX + EDITOR + ASSEMBLER £75.00**



Ex VAT

8 SKILLICORNE MEWS · QUEENS ROAD · CHELTENHAM · GLOUCESTERSHIRE GL50 2NJ
 Telephone: Cheltenham (0242) 510525

electronics today

INTERNATIONAL OCTOBER 1985 VOL 14 NO 10



Gary Herman: Editor
Ian Pitt: Assistant Editor
Paul Chappell: Project Editor
Jerry Fowler: Technical Illustrator
Paul Stanyer: Ad. Manager
Caroline Faulkner:
 Classified Sales Executive
Debra Barrie: Copy Control
Dave Bradshaw: Group Editor
 - Electronics
Peter Welham: Publishing Director

PUBLISHED BY:
 Argus Specialist Publications Ltd.,
 1 Golden Square, London W1R 3AB.
DISTRIBUTED BY:
 Argus Press Sales & Distribution Ltd.,
 12-18 Paul Street, London EC2A 4J5
 (British Isles)

PRINTED BY:
 The Garden City Press Ltd.
COVERS DESIGNED BY:
 MM Design & Print.
COVERS PRINTED BY:
 Alabaster Passmore.



Member of the
 Audit Bureau
 of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1985 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

■ Subscription Rates. UK £16.30 including postage. For further details and Airmail rates etc, see the Readers' Services page.

EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.
 Telex 8811896.

FEATURES

- DIGEST**..... 7
 An injunction to eat, or just to chew on the news?
- READ/WRITE**..... 16
 The first and last post.
- REAL COMPONENTS**..... 20
 It could be true or false, but when John Linsley looks at logic chips it's easy (or is that IC?).
- THE SAMPLE LIFE**..... 27
 Music by numbers means an increase in the rates.
- AUTOMATIC TEST EQUIPMENT**..... 43
 W.P. Bond investigATES one of this year's buzz phrases.
- TECH TIPS**..... 53
 Just the tip of the IC-berg.

PROJECTS

- ETI 'SORCERER' STRING SYNTHESISER**..... 32
 Graeme Durant ties up all the loose threads in the final part of this project.
- MODULAR TEST GEAR**..... 38
 These boards form the nucleus of a very versatile test set-up — and you can test that statement for yourselves.
- SUNRISE**..... 48
 Brighten your day gently with Margaret Blake's novel lamp controller.

ETCETERA

- REVIEWS**..... 59
 PCB manufacture and a range of popular microprocessors are looked at in the books under review.
- ALF'S PUZZLE**..... 59
 A teaser for you from the brains in the basement.
- PLAYBACK**..... 60
 In which you find Vivian Capel's views on camcorders.
- TRAINS OF THOUGHT**..... 61
 Roger Amos makes his points.
- OPEN CHANNEL**..... 61
 Keith Brindley's latest electric message.
- PLAYBACK EXTRA**..... 62
 Andy Amrstrong reports from the first British Music Fair to be open to the public.
- SCRATCHPAD**..... 62
 Flea-byte's back and itching to go.

INFORMATION

- PCB SERVICE**..... see page 7
NEXT MONTH'S ETI..... 54
FOIL PATTERNS..... 55
READERS' SERVICES..... 58
ADVERTISERS' INDEX..... 63
CLASSIFIED ADS..... 64

SWITCHES TOGGLE 2A, 250V SPST 35DPDP 84p SP- MIN TOGGLE SPST on off 86p SPDT on off 84p SPDT centre off 88p SPDT biased both ways 105p DPDT 6 tags 80p DPCT centre off 88p DPCT biased both ways 145p DPDT 3 positions on on on 185p 4 on 2 on 220p	DIP SWITCHES (SPST) 4 way 65p; 6 way 80p; 8 way 85p; 10 way 125p (SPDT) 4 way 190p	ROTARY SWITCHES (Adjustable Stop type) 1 pole/2 to 12 way; 3 pole/2 to 6 way; 3 pole/2 to 4 way; 4 pole/2 to 3 way	ROTARY: Mains DP 250V 4 Amp on/off 88p	ROTARY: (Make-a-switch) Make a multiway switch. Shifting assembly has adjustable stop. Accommodates up to 6 wafers (max. 6 pole/12 way with DP switch). Mechanism only 90p
---	---	--	---	---

PUSHBUTTON 6A with 10mm Button SPDT latching 150p SPDT latching 200p SPDT moment 200p	ROCKER SWITCHES ROCKER: 10A/250V SPST 28p ROCKER: 10A/250V DPST 36p ROCKER: 10A/250V DPDT c/off 95p ROCKER: 10A/250V DPST with neon 85p	THUMBWHEEL Mini front mounting switches Decade Switch Module 275p B.C.D. Switch Module 298p Mounting Cheeks (per pair) 75p
--	--	--

GAS/SMOKE DETECTORS TGS812 or TGS813 £6 each Holders for above 40p	JUMPER LEADS (Ribbon Cable Assembly) Length 14 pin 16 pin 24 pin 40 pin Single ended DIP (Header Plug) Jumper 24 inches 145p 185p 240p 380p Double ended DIP (Header Plug) Jumper 12 inches 198p 215p 315p 480p 24 inches 210p 235p 345p 540p 36 inches 290p 370p 480p 525p IC Female Header Socket Jumper Leads 36 20pin 26 pin 34 pin 40 pin 180p 200p 260p 300p 290p 370p 480p 525p
---	--

TRANSFORMERS 3-0-3V, 6-0-6V, 9-0-9V, 12-0-12V, 15-0-15V 100mA 130p PCB mounting. Miniature. Split bobbin 3VA: 2x6V/0.25A, 2x9V/0.15A, 2x12V/0.12A, 2x15V/0.2A 235p 6VA: 2x6V/0.5A, 2x9V/0.3A, 2x12V/0.25A, 2x15V/0.2A 280p Standard Split Bobbin type 6VA: 2x6V/0.5A, 2x9V/0.4A, 2x12V/0.3A, 2x15V/0.25A 250p 12VA: 2x4.5V/1A, 2x9V/0.5A, 2x12V/0.3A, 2x15V/0.2A, 2x20V/0.3A, 2x24V/0.25A 385p (80p p&p) 2x20V/1.2A, 2x25V/1A, 2x30V/0.8A 520p (80p p&p) 50VA Outputs +5V, +5.5V, +12V, -5V, -12V at 1A 820p (80p p&p) 100VA: 2x12V/4A, 2x15V/3A, 2x20V/2.5A, 2x25V/2A, 2x30V/1.5A, 2x35V/1A 955p (75p p&p) P&P charge to be added over and above our normal postal charge	VOLTAGE REGULATORS 1A TO220 Plastic Casing -ve 5V 7805 45p 7905 50p 12V 7812 45p 7908 50p 15V 7815 45p 7912 50p 18V 7818 45p 7915 50p 24V 7824 45p 7918 50p 7924 50p 100mA TO18 Plastic package 5V 78L05 30p 78L05 45p 6V 78L06 30p - - 8V 78L08 30p - - 12V 78L12 30p 79L12 45p 15V 78L15 30p 79L15 45p ICL7660 245p TAA55A..... 50p RC4154 376p TD4142..... 80p RC4195 180p TL97..... 185p LM309A 135p 78H05+5V/50mA..... 850p LM317K 250p 78H12+12V/5A, 655p LM317KP 450p 78HG+5V to +25V LM323K 450p 5A..... 585p LM337 175p 78HG+25V to LM723 Var 30p -24V 5A..... 785p 78S40 225p
--	--

CMOS	4075 25 4541 95	4076 65 4543 65	4077 25 4548 40	4078 25 4549 390	4081 20 4553 210	4082 20 4554 180	4083 60 4555 60	4086 60 4556 50	4089 120 4557 250	4093 25 4558 120	4094 70 4559 340	4095 70 4560 110	4096 100 4561 100	4097 260 4562 350	4098 70 4563 160	4099 110 4564 250	4100 95 4565 180	4181 96 4572 45	4182 96 4573 255	4183 96 4574 125	4184 96 4575 99	4185 105 4576 100	4186 105 4577 100	4187 105 4578 100	4188 105 4579 100	4189 105 4580 100	4190 105 4581 100	4191 105 4582 100	4192 105 4583 100	4193 105 4584 100	4194 105 4585 100	4195 105 4586 100	4196 105 4587 100	4197 105 4588 100	4198 105 4589 100	4199 105 4590 100	4200 105 4591 100	4201 105 4592 100	4202 105 4593 100	4203 105 4594 100	4204 105 4595 100	4205 105 4596 100	4206 105 4597 100	4207 105 4598 100	4208 105 4599 100	4209 105 4600 100	4210 105 4601 100	4211 105 4602 100	4212 105 4603 100	4213 105 4604 100	4214 105 4605 100	4215 105 4606 100	4216 105 4607 100	4217 105 4608 100	4218 105 4609 100	4219 105 4610 100	4220 105 4611 100	4221 105 4612 100	4222 105 4613 100	4223 105 4614 100	4224 105 4615 100	4225 105 4616 100	4226 105 4617 100	4227 105 4618 100	4228 105 4619 100	4229 105 4620 100	4230 105 4621 100	4231 105 4622 100	4232 105 4623 100	4233 105 4624 100	4234 105 4625 100	4235 105 4626 100	4236 105 4627 100	4237 105 4628 100	4238 105 4629 100	4239 105 4630 100	4240 105 4631 100	4241 105 4632 100	4242 105 4633 100	4243 105 4634 100	4244 105 4635 100	4245 105 4636 100	4246 105 4637 100	4247 105 4638 100	4248 105 4639 100	4249 105 4640 100	4250 105 4641 100
-------------	-----------------	-----------------	-----------------	------------------	------------------	------------------	-----------------	-----------------	-------------------	------------------	------------------	------------------	-------------------	-------------------	------------------	-------------------	------------------	-----------------	------------------	------------------	-----------------	-------------------	-------------------	-------------------	-------------------	-------------------

VERO BOARD 0.1" 3/4" x 1' 30p 2 1/4" x 3' 95p 2 1/4" x 5' 110p 3/4" x 3' 110p 3/4" x 5' 125p 3/4" x 17' 420p 4 1/4" x 17' 590p VQ Board 500p VQ Board 395p Vero Strip 95p	VERO WIRING PEN + Spool 380p Spare spool 75p Combs 8p Pen + Spool + Combs 595p	PROTO DECA Veroblock 480p S-Dac 350p Euroboard 590p Bimboard 575p Superstrip S2 1360p	VERO TOOLS Vero Tools Spot face cutters 180p Pin insertion tool 165p
--	--	---	--

FERRIC CHLORIDE 1lb bag Anhydrous 125p 50p p&p	DALCO ETCH RESIST PEN Plus spare 12 100p	EURO CONNECTORS Gold Flashed Contacts Female Smt Angle Pin Male Smt Angle Pin Plug Angle Pin	CRYSTALS Standard 8MHz 975p Wideband 8MHz 450p
---	---	---	---

COPPER CLAD BOARDS Fibre Single Double 3/16" side 4000 6" x 6" 100p 125p 6" x 12" 175p 225p	EDGE CONNECTORS .1" 158" 2x6 way - 75p 2x12 way - 180p 2x16 way - 185p 2x16 way 175p 180p 2x22 way 200p 170p 2x23 way 150p - 2x25 way 250p 245p 2x28 way 180p - 2x30 way 200p - 2x36 way 300p - 2x40 way 320p - 2x43 way 400p - 2x75 way 800p -	DIL PLUG (Header) Solder IDC 14 pin 40p 95p 16 pin 45p 100p 24 pin 85p 135p 28 pin 150p 200p 40 pin 200p 255p	RIBBON CABLE price per foot Grey Colour 10 way 15p 20p 16 way 25p 40p 20 way 30p 50p 24 way 40p 65p 34 way 80p 85p 40 way 70p 90p 50 way 100p 135p 28 pin 85p 64 way 120p 180p
--	--	--	---

ANTEX SOLDERING IRONS C15W 525p C18W 550p Spare Bits 85p Iron Stand 175p	SOLDERING PINS Ideal for making SIL or DIL Sockets 100 pins 45p 500 pins 195p	'D' CONNECTORS Solder IDC 15 25 37 way way way way Male Solder pins 55p 80p 120p 150p Angle pins 110p 175p 225p 300p PCB pins 100p 100p 160p 250p Female Solder pins 90p 125p 180p 275p Angle pins 150p 200p 280p 390p PCB pins 100p 125p 195p 355p Covers 75p 70p 70p 85p IDC 25 way 'D' Plug 385p; Socket 450p	ALUM BOXES 3 x 2 x 1" 85p 4 x 2 x 2" 200p 4 x 2 x 2 1/2" 103p 4 x 4 x 2 105p 4 x 4 x 2 1/2" 120p 5 x 2 x 1 1/2" 90p 5 x 2 x 2 1/2" 130p 6 x 4 x 2 120p 6 x 4 x 3 150p 7 x 5 x 3 180p 8 x 6 x 3 210p 10 x 4 x 3 240p 10 x 7 x 3 275p 12 x 5 x 3 280p 12 x 8 x 3 295p	25 way 'D' CONNECTOR (RS232) Jumper Lead Cable Assembly 18" long, Single ended, Male 475p 18" long, Single ended, Female 510p 36" long, Double Ended, M/M 180p 36" long, Double Ended, F/F 110p 36" long, Double Ended, M/F 95p
---	--	--	---	--

TURNED PIN Low Profile Professional DIL SOCKETS	BT TELEPHONE CONNECTOR
---	----------------------------------

COMPUTER CORNER	SPECTRUM 32K UPGRADE
------------------------	-----------------------------

COMPUTER CORNER	SPECTRUM 32K UPGRADE
------------------------	-----------------------------

PANEL METERS FSD 60 x 48 x 35mm 0-50uA 0-100uA 0-500uA 0-1mA 0-5mA 0-10mA 0-50mA 0-100mA 0-500mA 0-1A 0-2A 0-25V 0-50V 0-300V 485p each	RELAYS Miniature, enclosed, PCB mount. SINGLE POLE Changeover RL-11 205R Coil, 12V DC, (10V5 to 19.5V), 10A at 30V DC or 250V AC 195p DOUBLE POLE Changeover, 6A 30V DC or 250V AC RL-11 53R Coil, 6V DC (5V4 to 9V9) 190p RL-11 111 205R Coil, 12V DC (10V7 to 19V5) 195p RL-11 114 740R Coil, 24V DC (22V to 37V) 200p
--	--

CRYSTALS 32.768KHz 100 100KHz 400 200KHz 370 455KHz 370 1MHz 285 1.008MHz 275 1.28MHz 450 1.6MHz 200 1.8MHz 545 1.8432MHz 200 2.0MHz 225 2.4576MHz 200 3.12MHz 240 3.275MHz 150 3.5734MHz 98 3.8664MHz 300 4.0MHz 150 4.032MHz 290 4.1943MHz 200 4.43361MHz 100 4.608MHz 200 4.80MHz 150 5.185MHz 150 5.2428MHz 390 6.0MHz 140 6.144MHz 140 6.5536MHz 225 7.0MHz 150 7.168MHz 175 7.7328MHz 250 7.68MHz 200 8.0MHz 150 8.08933MHz 395 8.86723MHz 175 9.00MHz 200 10.0MHz 175 10.24MHz 200 10.5MHz 250 10.7MHz 150 12.0MHz 150 12.528MHz 300 14.31814MHz 150 15.0MHz 155 16.0MHz 200 18.0MHz 150 18.432MHz 150 19.868MHz 150 20.0MHz 150 24.0MHz 150 29.530MHz 325 26.5MHz 150 27.648MHz 170 27.145MHz 180 38.6667MHz 240 48.0MHz 240 100.0MHz 295	BUZZERS miniature, solid-state 6V, 8V & 12V PIEZO TRANSDUCERS: PB2720 70p ULTRASONIC TRANSDUCERS 40KHz 475p	LOUDSPEAKERS Miniature, 0.3W-8 2in, 3in, 2 1/2in, 3in 2 1/2in 400; 64tor 80n 8" x 4" 80 7" x 5" 80 8" x 5" 80
--	---	--

MONITORS	SPECIAL OFFER
-----------------	----------------------

MONITORS	SPECIAL OFFER
-----------------	----------------------

MONITORS	SPECIAL OFFER
-----------------	----------------------

MONITORS	SPECIAL OFFER
-----------------	----------------------

MONITORS	SPECIAL OFFER
-----------------	----------------------

Rapid Electronics

MAIL ORDERS:
Unit 1, Hill Farm Industrial Estate,
Boxted, Colchester, Essex CO4 5RD.
Tel. Orders: Colchester (0206) 36412.
Telex: 987756.

ACCESS AND
BARCLAYCARD
WELCOME

MIN. D CONNECTORS

9 way	15 way	25 way	37 way
Plugs solder lugs	55p	65p	90p
Right angle	90p	135p	200p
Sockets solder lugs	90p	100p	135p
Right angle	100p	180p	250p
Covers	120p	90p	100p



SOLDERING IRONS

Antex CS 17W Soldering iron	430
2.5 x 3 1/4"	85
Antex XS 25W soldering iron	530
3.3 and 4.7mm bits to suit	85
Solder pump desoldering tool	480
Spare nozzle for above	70
10 metres 22 swg solder	100
0.5kg 22 swg solder	750

CABLES

20 metre pack single core connect-	
able ten different colours: 75p	
Speaker cable 10p/m	
Standard screened 16p/m	
Twin screened 24p/m	
2.5A 3 core mains 23p/m	
10 way rainbow ribbon 26p/ft	
10 way rainbow ribbon 47p/ft	
10 way grey ribbon 14p/ft	
20 way grey ribbon 28p/ft	

HARDWARE

PP3 battery clips	6
Red or black crocodile clips	6
Black pointer control knob	15
Pr Ultrasonic transducers	350
▶6V Electronic buzzer	70
▶12V Electronic buzzer	70
▶PB270 Piezo transducer	75
▶64mm 8 ohm speaker	70
▶64mm 16 ohm speaker	70
▶20mm panel fuseholder	25
Red or black probe clip	35
4mm terminals	33
12 way 'chocolate' block	21
ultra-min. 8 or 12v rel. SPDT	130
ditto, but DPDT	195

CAPACITORS

Polyester, radial leads. 250v. C280	
type: 0.01, 0.015, 0.022, 0.033 -	
6p; 0.047, 0.068, 0.1 - 7p; 0.15	
0.22, 0.33, 0.47 - 10p; 0.68 -	
20p; 1 - 23p.	
Electrolytic, radial or axial leads:	
0.47/63V, 1/63V, 2.2/63V, 4.7/63V:	
10/25V - 7p; 22/25V, 47/25V - 8p;	
100/25V - 9p; 220/25V - 14p;	
470/25V - 22p; 1000/25V - 30p;	
2200/25V - 50p.	
33 Tag and power supply electrolytics:	
2200/40V - 110p; 4700/40V - 160p	
2200/63V - 140p; 4700/63V - 230p	
Polyester, miniature Siemens PCB:	
1n, 2n2, 3n3, 4n7, 6n8, 10n, 15n, 7p;	
22n, 33n, 47n, 68n, 8p; 100n, 9p;	
150n, 1p; 220n, 13p; 330n, 20p;	
470n 25p; 680n, 29p; 1u 33p.	

CONNECTORS

DIN Plug Skt Jack Plug Skt	
2 pin 9p 9p 2.5mm 10p 10p	
3 pin 12p 10p 3.5mm 9p 9p	
5 pin 13p 11p Standard 16p 20p	
Phone 10p 12p Stereo 24p 25p	
1mm 12p 13p 4mm 18p 17p	
UHF (CB) Connectors:	
PL259 Plug 40p. Reducer 14p.	
SO239 square chassis skt 38p.	
SO239S round chassis skt 40p.	
IEC 3 pin 250V/5A.	
Plug chassis mounting 38p	
Socket free hanging 60p	
Socket with 2m lead 120p	

27128-250	600
6116P3	280
6264P15	680
41256-15	920
41256-15	920
4164-15	300
27286	320
27286	320
2764A-250	350
2764B-350	350

VERO

Verobloc	395
Veroboard Size 0.1 in matrix	
2.5 x 3 1/4"	26
2.5 x 3 1/4"	140
3.75 x 5"	120
3.75 x 17"	350
4.75 x 17"	455
VQ board	190
Veropins per 100:	
Single sided	55
Double sided	110
Spot face cutter	145
Pin Insertion tool	185
Wiring pen	375
Spare spool 75p	6

REGULATORS

78L05	30	79L05	45
CA47	10	1N4007	5
78L15	30	79L15	45
7805	40	7905	45
7812	40	7912	45
LM157	45	7915	45
LM317K	270	LM723	40
LM317T	90	79H05	550
LM323K	420		

EURO CONNECTORS

Gold flashed	Rt. angle	Wirewrap
contacts:	plug	socket
64 way A+B	195	230
64 way A+C	220	270
96 way A+B+C	320	330

TRIACS

400V 6A	65
400V 16A	95
400V 4A	50
BR100	25

DIODES

BY127	12	1N4001	5
CA47	10	1N4002	3
CA30	8	1N4007	7
OAG1	7	1N5401	12
OAG20	8	1N5404	16
OAG28	8	1N5408	17
1N914	4	400mW zen	13
▶1N4148	3	1.3W zeners	6

OPTO

3mm red	8	5mm green	8
3mm green	11	5mm red	11
3mm yellow	11	5mm yellow	11
Clips to suit - 3p each.			
Rectangular:			
red	12	TIL111	60
green	17	TIL78	40
yellow	17	ORP12	85
ILDT94	95	IL074	195
TIL38	35	TIL100	75
2NS777	45	Tri-color Led	35

SWITCHES

Submit photos of SPST 50p, SPDT 60p, DPDT 65p. Miniature toggle: SPDT 80p, SPDT centre off 90p, DPDT 90p, DPDT centre off 100p. Standard toggle: SPST 35p, DPDT 48p. Miniature DPDT slide 14p. Push to make 15p. Push to break 22p. Rotary type adjustable stop. 1P12W, 2P6W, 3P4W all 55p each. DIL switches: 4P5ST 80p, 6PST 80p, 8PST 100p. Min. DPDT slide 14p. Push-make 15p.

MICRO

2716	310	2718	310
2532	380	2728	320
2732	380	2732	380
2732	380	2732	380
2732	380	2732	380
2732	380	2732	380
2732	380	2732	380
2732	380	2732	380
2732	380	2732	380

COMPUTER COMPONENTS

ZX81 2 x 23 way edge connector	150
wrap for ZX81 150	
SPECTRUM 2 x 28 way edge	
connector wire wrap 200	
AMPHENOL PLUGS	
24 way IEEE IDC 450	
36 way Centronix IDC 490	

COMPUTER CABLE

Grey Ribbon cable. Price per foot	
10 way 14	34 way 58
16 way 25	40 way 68
20 way 28	50 way 90
26 way 38	60 way 100

BRIDGE RECTIFIERS

2A 200V	40
2A 400V	45
1A 50V	20
1A 400V	35

SOCKETS

8 pin	7p	28p
14 pin	8p	45p
16 pin	10p	55p
18 pin	12p	60p
20 pin	13p	68p
22 pin	15p	75p
24 pin	17p	82p
28 pin	19p	95p
40 pin	25p	155p

COMPONENT KITS

0.25W Resistor Kit. Contains 1000 0.25W 5% resistors from 4.7 ohms thru to 10M. Quantities depend upon popularity. 1.0x10R, 30x470R, 30x10K, 25x470K. Ceramic capacitor Kit. Total of 250 miniature ceramic capacitors from 22p to 0.1u. Polyester capacitor Kit. Total of 110 miniature polyester capacitors from 0.01u to 0.47u. Preset Kit. Total of 110 miniature preset resistors from 100R to 1M. Horizontal mounting type. Radial Electrolytic Capacitor Kit. A pack containing a total of 93 miniature caps from 1u to 2200u. Nut and Bolt Kit. Contains 800 assorted items. 100 each 6BA 3/4", 3/8", nuts and washers, 4BA 3/4", 3/8", nuts and washers. Just £3.20.

RESISTORS

Carbon film	1+	25+
1/4W 5% 4.7ohm - 10M	2p	1p
1/4W 5% 4.7ohm - 4M7	3p	2p
1/4W 1% 10ohm - 1M	4p	3p
25+ price applies to 25+ per value not mixed.		

CRYSTALS

100KHz	235	500MHz	100
1MHz	275	60MHz	140
1.8432M	200	614MHz	150
2.0MHz	225	70MHz	150
2.4576M	200	80MHz	140
3.225M	195	100MHz	170
3.5785M	95	150MHz	200
4.0MHz	140	16.0MHz	200

BOXES

Aluminium	
3 x 2 x 1 1/2"	65
4 x 2 x 1 1/2"	95
6 x 4 x 2 1/2"	120
95x71x25mm	88
76 x 5 x 2 1/2"	165
140x90x55mm	140

TRANSISTORS

AC125	35	BC158	11	BC556	11
AC127	30	BC159	10	BC557	10
AC128	30	BC160	10	BC558	10
AC176	25	BC168C	10	BC172	16
AC187	25	BC169C	10	BC173	16
AC188	25	BC170	8	BC174	16
AD142	120	BC172	8	BC175	16
AD181	42	BC173	8	BC176	16
AD182	42	BC174	8	BC177	16
AF124	60	BC175	16	BC178	16
AF126	50	BC176	16	BC179	16
AF139	40	BC177	16	BC180	16
AF186	70	BC178	16	BC181	16
AF239	55	BC179	16	BC182	16
BC107	10	BC180	16	BC183	16
BC108	10	BC181	16	BC184	16
BC109	10	BC182	16	BC185	16
BC110	10	BC183	16	BC186	16
BC111	10	BC184	16	BC187	16
BC112	10	BC185	16	BC188	16
BC113	10	BC186	16	BC189	16
BC114	10	BC187	16	BC190	16
BC115	10	BC188	16	BC191	16
BC116	10	BC189	16	BC192	16
BC117	10	BC190	16	BC193	16
BC118	10	BC191	16	BC194	16
BC119	10	BC192	16	BC195	16
BC120	10	BC193	16	BC196	16
BC121	10	BC194	16	BC197	16
BC122	10	BC195	16	BC198	16
BC123	10	BC196	16	BC199	16
BC124	10	BC197	16	BC200	16
BC125	10	BC198	16	BC201	16
BC126	10	BC199	16	BC202	16
BC127	10	BC200	16	BC203	16
BC128	10	BC201	16	BC204	16
BC129	10	BC202	16	BC205	16
BC130	10	BC203	16	BC206	16
BC131	10	BC204	16	BC207	16
BC132	10	BC205	16	BC208	16
BC133	10	BC206	16	BC209	16
BC134	10	BC207	16	BC210	16
BC135	10	BC208	16	BC211	16
BC136	10	BC209	16	BC212	16
BC137	10	BC210	16	BC213	16
BC138	10	BC211	16	BC214	16
BC139	10	BC212	16	BC215	16
BC140	10	BC213	16	BC216	16
BC141	10	BC214	16	BC217	16
BC142	10	BC215	16	BC218	16
BC143	10	BC216	16	BC219	

DIGEST

British Computer Uses The 68020

Durham-Based Integrated Micro Products Ltd have launched a 32-bit multi-user microcomputer which is said to be considerably faster than many minicomputers costing ten times as much.

It owes much of its high performance to the use of Motorola's new 68020 microprocessor (described in ETI October 1984) and is the first British designed and built computer to use the chip.


The IMP-Mentor is available either as a complete super-micro computer or as a series of VME-Bus boards which can be used in other systems. It runs several versions of the Unix operating system and IMP say that it can support thirty-two users simultaneously with virtually no degradation of processing speed.

The main board carries the 68020 and 2M bytes of RAM, expandable up to 8M bytes. There is also provision for a

68881 floating-point co-processor. Two more boards carry the disk controller and the communications controller and each has its own 68000 microprocessor. This leaves the main microprocessor free to operate at the limits of its performance, which can be as high as eight million instructions per second.

To illustrate the speed of the Mentor, IMP quote its performance on the Sieve of Eratosthenes, a test that involves calculating about 2,000 prime numbers. The Mentor takes a mere 0.6 seconds, while a DEC VAX 78 minicomputer takes 1.8 seconds and an IBM-PC XT takes 9.0 seconds.

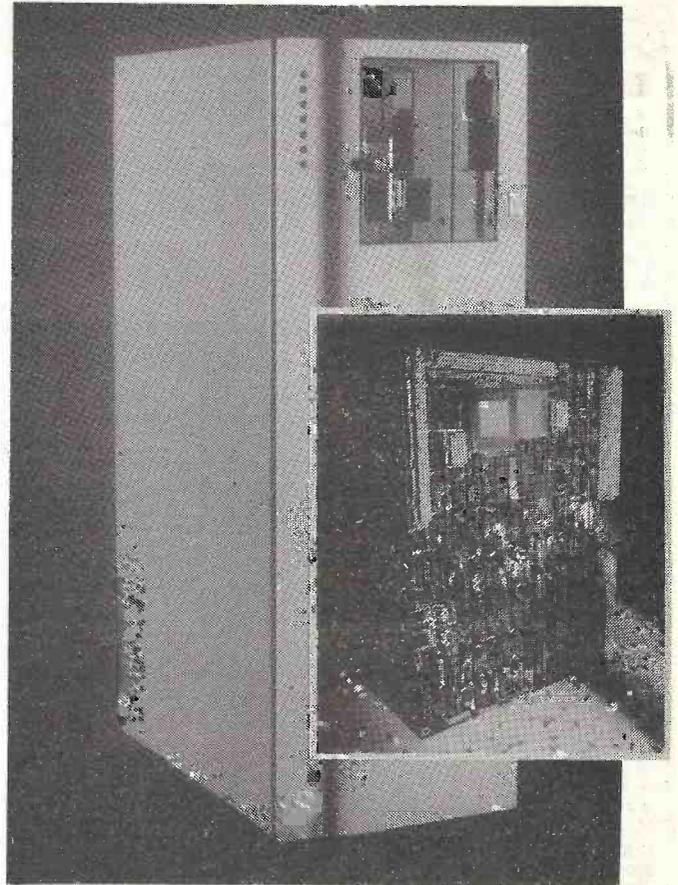IMP say the Mentor is ready for immediate shipment. For more details contact Integrated Micro Products Ltd, Number One Industrial Estate, Medomsley Road, Consett, County Durham DH8 6TJ, tel 0207-503481.



ETI Printed Circuit Board Service

We must again apologise to our readers for the suspension of this service.

As we explained in our last issue, the company who used to supply our PCBs have decided that they no longer wish to continue doing so. Until we find another supplier we cannot send


out any boards.

At the time of going to press we are close to reaching an agreement with a new supplier but nothing has yet been signed. We would hope to be able to start sending out boards again within a few weeks of signing such an agreement.

In the meantime, we will happily refund money to those who have paid but not received boards. However, if readers prefer they can leave their orders with us and we will deal with them as soon as we are able.

We would like to thank our readers for the forbearance many have shown in this matter and once again offer our apologies for the inconvenience.

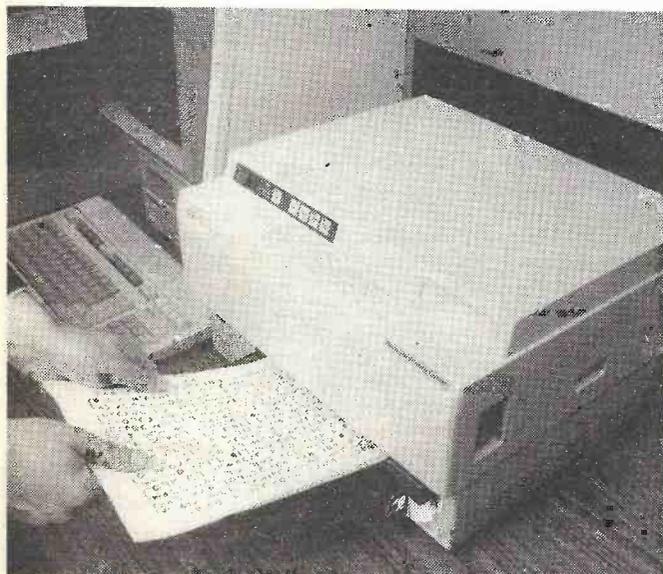● Hitachi have published a sixteen page brochure which describes their HD6305 CMOS microprocessor family. It covers types under development as well as those now available and includes information on support devices, software, etc. Hitachi Electronic Components (UK) Ltd, Hitec House, 221-225 Station Road, Harrow, Middlesex HA1 2XL, tel 01-861 1414.



Bumble Gives Us The Moon — By Laser

A research unit at Brunel University has developed a word processing system which can convert the written word into forms better suited to the needs of blind and partially-sighted people.

The system is called BUMBLE (Brunel University Moon, Braille and Large-print Equipment) and was developed by a team led by Dr. John Gill. It consists of a sixteen-bit microcomputer, specially developed software, and a laser printer.

Because the laser printer uses a non-impact printing system it is able to cope with a wide range of type styles and sizes. The paper can then be heat-treated to produce embossed Braille characters. The system can also print the

less well known Moon language. Developed before Braille, Moon has the advantage that it is very easy to learn, but the difficulty of printing it using traditional typesetting methods has prevented its widespread adoption. The Brunel team hope that their work will lead to a revival of interest in Moon.

Bumble was originally developed for use by social service departments and voluntary associations, but the simplicity of the system should enable it to be used by a wide variety of agencies who currently make no provision for the blind and partially-sighted when preparing information. For further details contact Dr. Gill on 0895-71206.

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE "ALLADINS' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT"

EX-STOCK INTEGRATED CIRCUITS

4164 200ns D RAMS 8 for £14.95 4116 300 ns £1.50
 2112 £10.00 2114 £2.50 2102 £2.00 6116 £2.50
 EPROMS 2716 £4.50 2732 £3.00 2764 £4.95
 27128 £5.50 6800 £2.50 6821 £1.00 66A09 £8.00
 6B09 £10.00 8085 £5.50 8086 £15.00 8251 £7.00
 8748 £15.00.

Thousands of IC's EX STOCK send SAE for list.

RECHARGEABLE BATTERIES

Dry Fit MAINTENANCE FREE by Sonnenschein & Yuasa
 A300 07191315 12v 3ah as RS 591-770 NEW £13.95
 A300 07191312 6v 3ah as RS 591-360 NEW £9.95
 A300 07191202 6-0-5v 1.6ah as RS 591-382 EX Equip
 £5.99 3.6v 100 mah PCB mount as RS 591-477 NEW £10.00

DISK DRIVES

Japanese Half height 80 track double sided disk drives by TEAC, TOSHIBA etc. Sold as NEW with 90 day guarantee ONLY £125.00.
 SUGART SA400 SS FH 35 TRK £55.00
 SIEMANS FDD100 SS FH 40 TRK £75.00 carriage on 5 1/4" drives £5.50
 Brand NEW metal cases with internal PSU etc for above drives, below cost!!
 DSK1 for 2 HH or 1 FH 5 1/4" drive £39.95 + pp £4.50 DSK2 for 1 HH or 1 FH 5 1/4" drive £29.95 + pp £4.50
 8" Refurbished standard units.
 SUGART 801 SS £175.00 + pp £8.50
 SUGART 801 DS £250.00 + pp £8.50
 DRE 700 SS £125.00 + pp £8.50
 TWIN SUGART 881 in smart case, complete with PSU etc, £595.00
 8" DRIVE PSU for 2 drive units £45.00

Hard Disk Drives.
 DRE/DIABLO Series 30 2.5 Mb front load, £525.00, Exchangeable version £295.00
 M3029 PSU for above £95.00
 MEABO 44/DRE4000A, B 5-4 Mb from £70.00
 CDC HAWK 5+5 Mb £795.00
 CDC 9762 80 Mb RM03 etc £2500.00
 PERTEC D3422 5+5 Mb £495.00
 RODIME 10MB ST506 Winchester NEW £299.00
 BASF 6172 23Mb Winchester, as seen £199.00
 Carriage on other drives £10.00.
 Unless stated all drives are refurbished with 90 day guarantee. Many other drives and spares in stock - call sales office for details.

MODEMS

Join the communications revolution with our super range of DATA MODEMS, prices and specifications to suit all applications and budgets...

BRAND NEW State of the art products.
 DACOM DSL123 Multi standard 300-300, 1200-75 Auto answer etc. £265.00
 DACOM DSL123AD Auto dial, smart modem with multi standard AUTO SPEED detect, and data buffer with flow control etc. £365.00
 DACOM DSL123GT The CREAM of the intelligent modems, auto dial, auto call, index, buffer etc etc. £498.00
 STEEBACK SB1212 V22 1200 baud FULL DUPLEX, sync or async, optional auto dial, etc. £485.00
 TRANSDATA 307A Acoustic coupler 300 baud full duplex, originate only, RS232 £49.00

Ex BRITISH TELECOM full spec, CCITT, ruggedised, bargain offers. Sold TESTED with data. Will work on any MICRO or system with RS232 interface.
 DATEL 2B 300 Baud Modem see SPECIAL OFFER.
 MODEM 13A 300 baud unit, only 2" high fits under phone. CALL mode only £45.00
 MODEM 20-1. 75-1200 baud. Compact unit for use as subscriber end to PRESTEL TELECOM GOLD, MICRONET etc. £39.95 + pp £6.50
 MODEM 20-2 1200-75 baud. Same as 20-1 but for computer end. £65.00 + pp £6.50
 DATEL 2412 Made by SE labs for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol etc. Many features include 2 or 4 wire working, self test, auto answer etc.
 COST OVER £800 Our price ONLY £199 + pp £8.00
 DATEL 4800, RACAL MPS4800 baud modem, EX BT good working order, ONLY £295.00 + pp £8.00

SUMMER OFFER
 MODEM TG2393. EX BT, Up to 1200 baud, full duplex over 4 wire or half duplex over 2 wire line. ONLY £85.00 PER PAIR + pp £10.00.

For more information CONTACT OUR SALES OFFICE

HOT LINE DATA BASE

DISTEL

The ORIGINAL FREE OF CHARGE dial up data base. Buy, browse or place YOUR OWN AD for goods or services to sell. 1000's of stock items, spares and one off bargains. Updated daily.
ON LINE NOW. CCITT, 8 bit word, no parity.
 For 300 baud modems call 01-679 1888
 For 1200-75 baud modems call 01-679 6183

PRINTER / TERMINAL SCOOP

A MASSIVE purchase of these attractive stand alone terminal units enables a SUPER BARGAIN offer. Made by the US GENERAL ELECTRIC CORPORATION the GE MODEL 30 features a standard QWERTY 80 key electronic keyboard coupled to a quality built matrix printer with variable 3" to 9.5" forms tractor. The printer is capable of continuous duty printing, with up to 120 characters per line. Standard RS232 interface accepts ASCII data at 110, 150 or 300 baud. Ideal for Terminals, Data loggers, local label printing, or just as a printer! Sold TESTED with data. ONLY £95.00. Also available with TWIN MAGTAPE CASSETTE unit for data capture, data preparation etc £150.00 Carriage £10.00.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of COOLING FANS
 ETRI 126LF21 240v 5 blade equipment fan Dim. 80 x 80 x 38mm £9.95
 ETRI 88XU01 Dim. 92 x 92 x 25mm 240v equipment fan, complete with finger guard NEW £9.95
 GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240v operation. NEW £6.95.
 BUHLER 89.11.22 8-16v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, also silent running and guaranteed 10,000 hr life. Measures only 82 x 22 mm. Current cost £22.00. OUR PRICE ONLY £12.95 complete with data.
 MUFFIN-CENTAUR standard 4" x 4" x 1.25" fans 110v OR 240v NEW at £10.50 or tested EX EQUIPMENT 240v £6.25 or 110v £4.95.
 1000's of other fans EX Stock.
 Call for Details. Post & Packing on all fans £2.00.

QWERTY KEYBOARDS

Manufacturer's BRAND NEW surplus.
 ALPHAMERIC 7204/60 Full travel ASCII, 60 key with parallel output and strobe. £39.95
 DEC LA34 Un-coded keyboard with 67 quality gold plated switches on X-Y matrix - ideal micro conversions etc. £24.95
 AMKEY MPNK-114 Superb word processor chassis keyboard on single PCB with 116 keys. Many features such as On board Micro, Single 5v rail, full ASCII coded character set with 31 function keys, Numeric keypad, cursor pad and 9600 baud SERIAL TTL ASCII OUTPUT!! ONLY £69.00 with data.



Carriage on all Keyboards £3.50

PLESSEY VUTEL

Manufactured by PLESSEY Ltd this compact unit, only slightly larger than a telephone, features an all in one TELEPHONE, 24 x 40 character CRT screen, VIEWDATA - PRESTEL modem, Keypad and electronics to run as a fully fledged PRESTEL terminal or telephone. Ready to plug direct into a BT 600 type jack socket and instantly connect you to PRESTEL etc. Many other features include Memory dialling, Recall button, Off line screen data storage, Picture expand, Standard Mullard LUCY chip set, Integral 5" JVC crt monitor, etc etc. Designed to sell to the EXECUTIVE at over £600!! But from DISPLAY, BRAND NEW and BOXED at only £99.00 for DTMF tone dial or £140.00 for standard DIAL PULSE version. Carr. £8.00.

SPECIAL 300 BAUD MODEM OFFER

Another GIGANTIC purchase of these EX BRITISH TELECOM, BRAND NEW or little used 2B data modems allows US to make the FINAL REDUCTION, and for YOU to join the exciting world of data communications at an UNHEARD OF PRICE OF ONLY £29.95. Made to the highest POST OFFICE APPROVED spec at a cost of hundreds of pounds each, the 2B has all the standard requirements for data base, business or hobby communications. All this and more!!

- 300 baud full duplex
- Full remote control
- CCITT tone standards
- Supplied with full data
- Modular construction
- Direct isolated connection
- CALL, ANSWER and AUTO modes
- Standard RS232 serial interface
- Built in test switching
- 240v Mains operation
- 1 year full guarantee
- Just 2 wires to comms line

BT 600 Jack plug and cable £2.25 Carriage and Ins. £10.00

COLOUR AND MONOCHROME MONITOR SPECIALS

'SYSTEM ALPHA' 14" COLOUR MULTI INPUT MONITOR made in the UK by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future monitor requirements. Two video inputs: RGB and PAL Composite Video, allow direct connection to the BBC and most other makes of micro computers and VCR's. An internal speaker and audio amplifier may be connected to your systems output or direct to a VCR machine, giving superior sound quality. Many other features included PIL tube, Matching BBC case colour, Major controls on front panel, Separate Contrast and Brightness - even in RGB mode. Two types of audio input, Separate Colour and audio controls for Composite Video input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc etc.

This Must be ONE OF THE YEAR'S BEST BUYS
 Supplied BRAND NEW and BOXED, complete with DATA and 90 day guarantee. SUPPLIED BELOW ACTUAL COST - ONLY £149.00

DECCA 80 16" COLOUR monitor, RGB input.

Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only £99.00, a price for a colour monitor as yet unheard of! Our own interface, safety modification and special 16" high definition PIL tube, coupled with the tried and tested DECCA 80 series TV chassis gives 80 column definition and picture quality found only on monitors costing 3 TIMES OUR PRICE. In fact, WE GUARANTEE you will be delighted with this product, the quality for the price, has to be seen to be believed. Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features are: internal speaker, Modular construction, auto degaussing circuit, Attractive TEAK CASE, compact dimensions only 52cm W x 34 H x 24 D, 90 day guarantee. Although used, units are supplied in EXCELLENT condition, ONLY £99.00 + Carr.
 DECCA 80, 16" COLOUR monitor. Composite video input. Same as above model but fitted with Composite Video input and audio amp for COMPUTER, VCR or AUDIO VISUAL use. ONLY £99.00 + Carr.
 REDIFFUSION MARK 3, 20" Colour monitor. Fitted with standard 75 ohm composite video input and sound amp. This large screen colour display is ideal for shops, schools, clubs and other AUDIO VISUAL applications. Supplied in AS NEW or little used condition ONLY £145.00 + Carr.

BUDGET RANGE EX EQUIPMENT MONOCHROME video monitors.

All units are fully cased and set for 240v standard working with composite video inputs. Units are pre tested and set up for 80 column use on BBC micro etc. Even when MINOR screen burn exists - normal data displays are unaffected.
 12" KGM 320-1 B/W high bandwidth input, will display up to 132 x 25 lines. £32.95
 12" GREEN SCREEN version of KGM 320-1 Only £39.95
 9" KGM 324 GREEN SCREEN fully cased very compact unit Only £55.00
 9" HITACHI VM-908E/K Black and White screen £49.95
 Carriage and insurance on all monitors £10.00

D.C. POWER SUPPLY SPECIALS


GOULD OF443 enclosed, compact switch mode supply with DC regulated outputs of +5v @ 5.5a, +12v @ 0.5a, -12v @ 0.1a and -23v @ 0.02a. Dim 18 x 11 x 6 cm. 110 or 240v input. BRAND NEW only £14.95
 GOULD G6-40A 5v 40 amp switch mode supply NEW £130.00
 GREENDALE 19A-BOE Switch mode 60 watt open PCB with a fully regulated DC output of 5v @ 6 amps, and three semi regulated outputs of +12v, -12v +15v @ upto 1 amp. Dim only 11 cm x 20 cm x 5.5 cm. Similar to RS 591-994. 110 or 240v AC input.
 TESTED ex equipment. Only £24.95
 AC-DC Linear PSU for DISK drive and SYSTEM applications. Constructed on a rugged ALLOY chassis to continuously supply fully regulated DC outputs of +5v @ 3 amps, -5v @ 0.6 amps and +24v @ 5 amps. Short circuit and overvoltage protected. 110 or 240 V AC input. Dim 28 x 12.5 x 7 cm NEW £49.95.
 Carriage on PSU's £3.00

VDU TERMINALS

Standard VDU data entry terminals at give away prices!!
 QUME QVT10B. Current product, state of the art terminal with detachable keyboard, 12" green screen, 2 page RAM, TVI 925 emulation, 25 x 80, Clock, Swivel and tilt base, Printer port, Function keys etc. BRAND NEW and BOXED AT ALMOST HALF PRICE ONLY £425.00
 AJ510 - EX RENTAL Z80 controlled, 15" green screen, 24 x 80 display, graphics, cursor addressing, printer port etc. Very good condition TESTED complete with manual only £225.00.
 ADDS 520 - Dumb terminal, used, 12" b/w screen RS232 interface and printer port. TESTED. ONLY £125.00.
 Carriage on terminals £10.00
 100's of other terminals in stock. CALL for more details.

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government Depts., Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30. Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

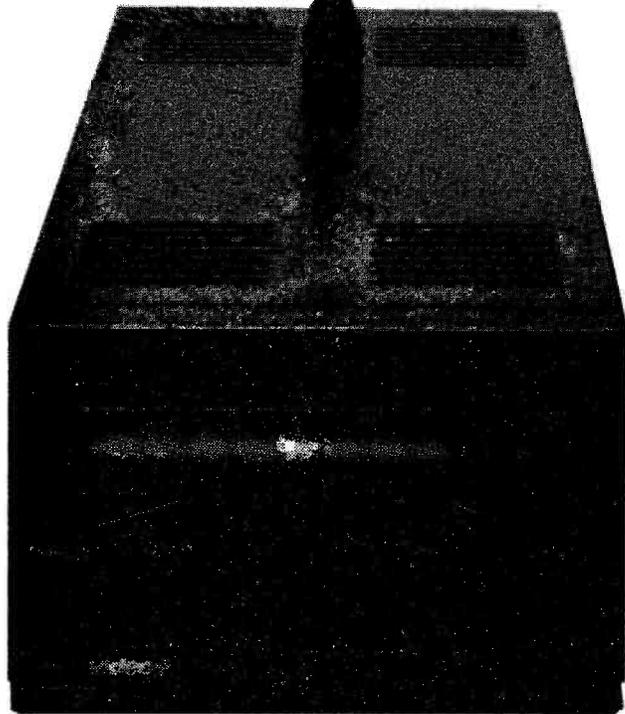32 Biggin Way, Upper Norwood, London SE19 3XF
 Telephone 01-679 4414 Telex 894502 Data 01-679 1888



Short-Range Transmitter For VCRs

Mastertronic have developed a UHF amplifier and aerial unit which will broadcast pictures from a video cassette recorder so that they can be picked up by nearby television sets.

The system has a range of about 45 feet and could be used, for example, to transmit the signal from a centrally placed VCR to a portable TV elsewhere in the house or to enable one VCR to be used with several TV sets simultaneously.

The Video+ takes the UHF signal from the output of the VCR, amplifies it and feeds the output to a short, detachable aerial. Because the final output is only an amplified version of the VCR signal, the transmission frequency will be that to which the VCR is tuned and the programmes can be picked up on the TV channel normally used when the VCR is plugged in directly.

The nominal bandwidth of the amplifier covers UHF channels 32 to 40 with a maximum usable bandwidth extending from channel 21 to channel 60. Two touch panels on the front of the unit increase or reduce the gain, the result being shown on a bargraph type LED display. This makes it possible to select the minimum output power necessary to achieve good reception.

It may come as a surprise to some readers to learn that retransmission in this way is not illegal, but Mastertronic assure us that they have had a team of lawyers working on the case and that even after contacting eighteen Home Office departments they have not been able to find any legal impediment.

Mastertronic are marketing the Video+ with the domestic user very much in mind, but also expect it to be of use in schools, colleges, conference centres, hotels, etc. It will be sold through leading high street electrical shops at a recommended price of £149.95 including VAT, complete with mains lead, aerial and VCR connecting lead.

Mastertronic, Park Lorne, 111 Park Road, London NW8 7JL, tel 01-732 9242.

● MS Components have published a new electronic components equipment catalogue. Its 300 or so pages contain details of around 10,000 products and the company say they can despatch all orders on the day of receipt. Copies are available free-of-charge from MS Components Ltd, Zephyr House, Waring Street, West Norwood, London SE27 9LH, tel 01-670 4466.

● Honeywell have issued the latest edition of their quarterly journal, *Scientific Honeyweller*. It includes an article on secure computers systems which explains how sensitive data can be protected against 'hackers', and also has an article describing an intelligent computer program which can be used in the design of large computer systems tailored to suit particular applications. Copies of the magazine are available free-of-charge from the Information Desk, Honeywell Information Systems Ltd, Honeywell House, Brentford, Middlesex TW8 9DH, tel 01-568 9191.

● There are still areas in which valves reign supreme, some of them very specialised. Among the companies supplying some of the more exotic types are Westinghouse, who have just

published a new, sixteen page catalogue. It covers high-vacuum (triode) amplifiers, high-vacuum (triode) pulse amplifiers and high-vacuum diodes for use in industrial, broadcasting, radar and similar applications, and the guide includes specifications and detailed scale drawings. Copies are available from Peter Collings, Westinghouse Electric SA, Industrial and Government Tube Division, 43 High Street, Marlow, Buckinghamshire SL7 1BD, tel 06284-75876.

● Semiconductor Supplies are distributing an eight-page brochure which describes their range of Kaise and Eagle power supplies and test meters. The power supplies include fixed and variable voltage regulated types and also steplessly variable regulated units. Both analogue and digital meters are available, the analogue types having input sensitivities up to 100,000 ohms-per-volt, and there is also a range of AC and DC clamp meters, insulation testers, earth testers and an analogue light meter. Copies are available from Peter Cresswell, Semiconductor Supplies International Ltd, Dawson House, 128-130 Carshalton Road, Sutton, Surrey, SM1 4RS, tel 01-643 1126.

Key Note


Next time you fancy a little innocent amusement on a crowded bus or train just try clapping three times.

You may be unlucky and elicit nothing more than a few odd looks. On the other hand, you may be rewarded with a cacophony of high-pitched bleeps and a frenzied rustling noise as dozens of embarrassed faces disappear behind their daily papers.

For Dudley Langmead Enterprises have introduced the Key Tracer, an electronic keyring which looks well set to replace the electronic alarm watch as the principal cause of unintended peeping in public places.


The Key Tracer is designed to help those who habitually mislay their keys and behaves like any other keyring until activated by the sound of three claps. It then emits the aforementioned high-pitched tone, alerting the owner to its presence and passers-by to its owner's carelessness.

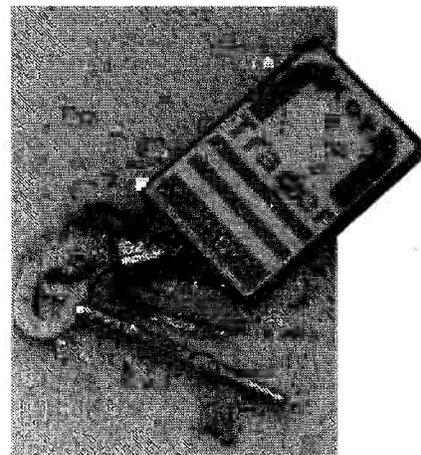The social impact of such an invention may well be out of all proportion to its size. We will probably get used to seeing our public spaces filled with people who wear anxious looks and stride around clapping rhythmically, and unpopular orators will no



doubt come to accept the high-tech accompaniment which starts up shortly after the first few rounds of slow hand-clapping. However, we can only be thankful that Dudley Langmead did not go for voice pattern recognition and that we are spared the sight of distracted owners calling "Here, Keyring, Keyring" as they wander. The cost of this miraculous device is surprisingly modest at £6.95 and the manufacturers are surely to be congratulated on their achievement. But please, no applause. You never know what might result.

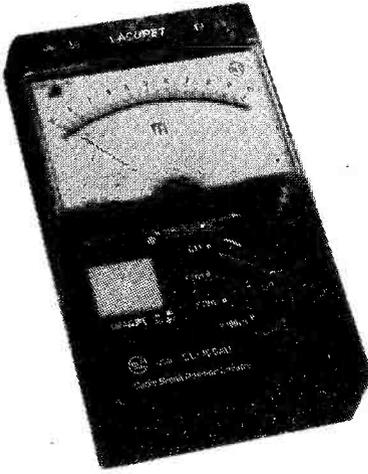Dudley Langmead Enterprises Ltd, 16 Bedford Street, Hitchin, Hertfordshire, tel 0462-35928.



Cable Length Meter

TMK are marketing a portable meter which will measure electronically the length of a piece of cable or the distance to a break or short circuit.

The Lacopet CL-100AU can measure cable lengths from 1 metre to 1000 metres and will work with both two-core and coaxial cables. It works by injecting a 1kHz signal into the line and then measuring the response.

In use, the meter is first calibrated using a 1m piece of cable

identical to the length under test. It can then be connected to the unknown cable and a direct reading of length obtained. It could be used, for example, to measure the amount of cable on a drum without uncoiling it or the distance to a break or short circuit in a buried cable.

The CL-100AU is battery operated and has a basic accuracy of $\pm 5\%$ of FSD. A phono output is provided so that the 1kHz tone can also be injected into cables or equipment for signal tracing purposes.

The meter measures 163 x 100 x 47mm and weighs 300gm. It comes complete with all test leads, batteries, a carrying case

and an instruction manual and has a neck harness which allows it to be supported at a comfortable viewing angle in front of the user whilst leaving the hands free. Optional extras include a signal tracer which can be used to detect the 1kHz output tone.

The CL-100AU costs £199.75 plus VAT and the optional signal tracer costs £125.00 plus VAT complete with case, batteries and earphone. Also available is the CL-100AUK which is generally similar to the CL-100AU but has a measuring range of up to 5000m. It costs £445.00 plus VAT.

TMK Test Instruments, 138 Grays Inn Road, London WC1X 8AX, tel 01-837 7937.

Careers Advice Centre

A Careers In Engineering centre will be one of the features at the Technology Engineering Fair, to be held at the NEC, Birmingham from 8-11th October.

The centre will be staffed by representatives from leading engineering employers and technical institutes and will offer

advice on career opportunities to students and engineers who are currently unemployed. Advice will also be available for engineers who are in employment but feel that their skills are not being fully used.

The centre will be opened by Sir Monty Finnieston. For details contact Juliet Northage, Cahners Exhibitions Ltd, Chatsworth House, 59 London Road, Twickenham, Middlesex TW1 3SZ, tel 01-891 5051.

● The British Standards Institution have issued their BS 6600 entitled Outline Dimensions of Transformers and Inductors for use in Telecommunications and Electronic Equipment. The first section to be issued is part 10 which covers the Q range of C-core transformers and inductors. BSI hope that it will encourage manufacturers to avoid needless variety in producing these parts. BS 6600 part 10 costs £16.20 (£8.10 to members) from BSI,

Linfold Wood, Milton Keynes MK14 6LE.

● The Plessey radio payphone described in News Digest in July has found a customer, but instead of being taken up by poor Third World countries as Plessey expected the first purchasers are the wealthy Swiss. The systems will be installed at fashionable ski resorts in the Alps where a cabled system would be too expensive.

SIREN KIT
Produces a loud swept frequency tone from a 9-15V supply. Enable input for easy connection to alarm circuits. Includes 5in horn speaker **£7.90**
Mini siren (with small speaker & box) **£4.30**

BELL BOX
Brightly coloured and a deterrent by itself 950 130 **£10.00**

PRESSURE MATS
23 x 7ins **£1.70**
29 x 16ins **£2.60**

BT Phone connectors starter pack **£9.50**

VERO

PASSIVE IR DETECTOR
Detects intruders body heat at up to 10m. 12Vdc supply Output N/c contacts 950 135 **£45.00**

XENON BEACON
12V 170mA Orange weatherproof 950 133 **£10.50**

TRIACS

ALARM CONTROL UNIT
4 input circuits, 2 instant 2 delayed. Adjustable entry exist and alarm times. Built & tested. Full instructions supplied.
Size 180 x 130 x 30mm 12 dc supply 950 160 **£26.00**

TOOLS
Side cutters **£2.10**
See Cat. for full range.

PANTEC KITS

BOXES
Plastic, diecast aluminium

MULTIMETERS
Analogue from **£6.50**
Digital from **£26.55**

DIGITAL LOCK KIT
operates from 5 to 18Vdc supply and gives 5040 combinations. 10 way keyboard supplied. 750mA output. Ideal for disabling car ignition or for door lock when used with 701 150 lock mechanism **£11.50**
701 150 **£14.95**

CMOS
4001 16p
4017 39p

LEDs
from 3p

CONTACTS
for doors & windows Magnet & Reed Flush 950 140 **£1.05**
Surface 950 142 **75p**

FREE 28 page catalogue. Send 9x6 SAE NOW!
Telephone orders — Access & Barclaycard **RING 01-567 8910 (24hrs)**

WINDOW TAPE
50m **£2.50**
Terminators **36p/pr**

BATTERIES
NiCADs eg AA **90p** & Chargers

VELLEMAN KITS

HIGH SECURITY IR TRANSMITTER/RECEIVER
Operating from 9-15Vdc, both units have 8 switches and will operate only if these have been set to the same code. Receiver provides latched or momentary output. Ideal for car locks, garage door openers, burglar alarm switches etc. XK119 **£21.75**

ELECTRONICS
13 BOSTON RD
LONDON W7 3SJ
Tel. Orders: 01-567 8910
Enquiries: 01-579 9794
Shop Hours: Mon-Fri. 9am-5pm
Sat. 10am-4pm.

ORDERING INFORMATION:
ALL PRICES EXCLUDE VAT
FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.
LOCAL AUTHORITY AND EXPORT ORDERS WELCOME
GOODS BY RETURN SUBJECT TO AVAILABILITY



Temperature Indicating Paint

Redpoint have introduced an improved version of their Spectratherm paint, a substance which changes colour to indicate the temperature of the surface onto which it is coated. The new formula measures temperatures over the range 58-117°C and can be used to check the temperature of semiconductor packages and other electronic devices.

Spectratherm is available as a kit of three bottles, each of which has a brush built into the cap. It can be applied to any dark surface and the temperature can then be assessed by comparing the paint colour with a printed spectrum chart provided. Redpoint claim that under laboratory conditions the paint can be used to indicate temperature to within 0.5°C.

Spectratherm works best on non-reflective surfaces but shiny semiconductor packages and similar finishes will give reliable readings if they are rubbed over with a black felt pen first.

Redpoint expect the new paint to be of interest to most electronic engineers and especially to test and quality assurance engineers. They plan to introduce an airbrush so that Spectratherm can be used for temperature mapping on large surfaces.

The three bottle kit costs £25.30 including VAT and postage and packing, and further details can be obtained from Redpoint Limited, Cheney Manor, Swindon, Wiltshire SN2 2PS, tel 0793-37861.

● NEC claim to be both a world leader in relay technology and a pioneer in fibre optic communications. To prove it they have published a 122-page guide to their relay products and a 344-page book on fibre optics, both of which are said to contain technical data, reference guides and a glossary of terms and definitions. Copies are available free-of-charge from NEC Electronics (UK) Ltd, Carfin Industrial Estate, Motherwell, Scotland ML1 4UL, tel 0698-732221.

● ECW have an easy-to-build stereo VU meter kit which uses rows of 16 LEDs to give a bargraph-type display. It operates from a 12V DC supply, has an input impedance of 10k and a sensitivity of from 100mV to 10V full scale. The kits costs £20.85 including postage, packing and VAT from

Electronics & Computer Workshop Ltd, 171 Broomfield Road, Chelmsford, Essex CM1 1RY, tel 0245-262149.

● Axiom Electronics have signed an agreement with ITT Cannon under the terms of which they will distribute a wide range of Cannon connectors. They can also provide free copies of technical literature and specifications on the new product lines which include D subminiature connectors, the DIN 41612 range, Solda-D, D*U and low cost plastic connectors, turned-pin IC sockets, chip carrier and pin grid array sockets, and IDC connectors. Axiom Electronics Ltd, Turnpike Road, Cressex Estate, High Wycombe, Buckinghamshire HP12 3NR, tel 0494-442181.

CRICKLEWOOD

ELECTRONICS LTD



It's no secret...

... that there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED

40 Cricklewood Broadway, London NW2 3ET

Tel: 01-450 0995/01-452 0161

Telex: 91 4977



ETI

Happy Memories

Part type	1 off	25-99	100 up
4116 200ns.....	1.25	1.15	1.10
4164 150ns Not Texas99	.89	.84
4128 150ns.....	5.45	4.99	4.70
4258 150ns.....	3.65	3.35	3.10
2114 200ns Low Power.....	1.75	1.60	1.55
2016 150ns.....	2.45	2.30	2.20
6264 150ns Low power	5.00	4.45	4.00
2716 450ns 5 volt.....	3.85	3.45	3.30
2732 450ns intel type.....	4.75	4.25	4.10
2732A 350ns.....	5.25	4.69	4.50
2532 450ns Texas type.....	3.85	3.45	3.30
2764 300ns Suit BBC.....	2.95	2.65	2.50
27128 300ns Suit BBC.....	3.95	3.55	3.35

Low profile IC sockets: Pins 814 16 18 20 24 28 40
Pence 12 13 14 16 18 24 27 38

Available now — The ROAM BOARD for the BBC Micro. Reads Roms via a Low Insertion Force Socket and saves their contents as files, then reloads a file into its sideways Ram as required. Full details on request.

74LS series TTL, wide stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or 'phone for list.

Please add 50p post & packing to orders under £15 and VAT to total. Access orders by 'phone or mail welcome. Non-Military Government & Educational orders welcome., £15 minimum.

HAPPY MEMORIES (ETI),
Newchurch, Kington,
Herefordshire HR5 3QR.
Tel: (054 422) 618

● The autumn issue of Cirkit's component catalogue should be out by the time you read this and will be available from high street newsagents for £1.15. Its 128 pages will carry details of an expanded range of parts and will include a special offer on modems and interfaces for the Amstrad computer at a price which Cirkit say is amazingly low.

● STC have published the 1985 edition of *The Tool Book*, an 80-page catalogue of tools, assembly aids, service aids, storage equipment and cells and batteries. Over 400 products are listed, from screwdrivers to complete soldering/desoldering stations. Also available is *The Electronics Book*, a catalogue of electronic components which runs to nearly 700 pages and contains information on almost 40,000 products. Included are details of Estelle, their on-line ordering and information system which is available to anyone with a computer and modem. Both books are available free-of-charge from STC Electronic Services, Edinburgh Way,

Harlow, Essex CM20 2DE, tel 0279-26777.

● The Institute of Electrical Engineers are planning to produce a **Guide for Industry on the Design and Achievement of Testability in engineering products**. They say that it is debatable whether some of today's sophisticated micro-electronics designs can be tested completely (see our article in this issue for more on this) and hope the Guide will help designers to incorporate test procedures to help overcome the problem. Anyone who feels they have anything to contribute should contact the IEE, Savoy Place, London WC2R 0BL, tel 01-240 1871.


● PSP have updated their free-form literature which contains photographs and information on their range of connectors. They are distributors for ITT Cannon, Thomas & Betts, Transradio, ITT Pomona, Panduit and Souriau and their range covers just about every conceivable application. PSP Electronics Ltd, Unit 2, 2 Bilton Road, Perivale, Greenford, Middlesex UB6 7DX, tel 01-998 9061.

Transformer Design Service

Avel-Lindberg have set up a new department which can produce small quantities of toroidal transformers designed to the requirements of individual customers.

The Small Quantities and Prototype Department can produce transformers in batches of from one to twenty units. They say they can tackle anything within the limits imposed by winding machine and wire technology and offer ratings from 10VA to 3kVA. Finishing options range from Melinex tape winding through to full impregnation and resin filling and they can cope with most special requirements regarding insulation and magnetic shielding. Transformers can be constructed to meet all specifications, including Defence Standard 05-24.

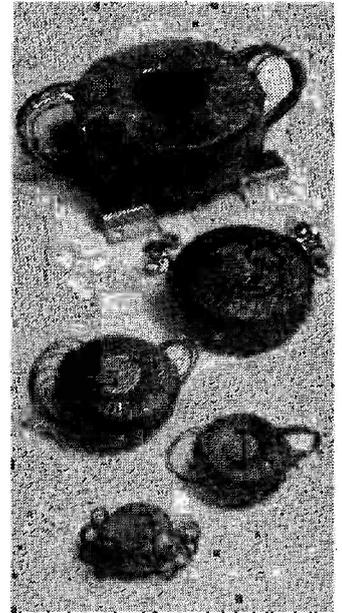Avel-Lindberg use a computer to speed up the design process and can execute the simpler jobs in a few hours. In practice, they feel that most such requirements will be catered for in their standard range and expect the new



service to be used mainly for more complex jobs, some of which may need to be passed back and forth between them and the customer before the design is perfected.

Avel Lindberg Ltd, South Ockenden, Essex RM15 5TD, tel 07080-853444.

CIRKIT AUTUMN CATALOGUE

OUT NOW

- ★ No cover price increase
- ★ 16 extra pages and many new products including ...
 - ★ 25 new radio communication kits and projects
 - ★ New Epson compatible NLQ dot matrix printer for under £200 - including VAT, p&p
 - ★ Acoustic MODEM and interface for Amstrad CPC464/664, supporting Prestel, terminal emulation (BT Gold, glass teletype etc) and data transfer. All this for just £26.00.
 - ★ A new selection of soldering irons and accessories from Weller plus many new hand tools.
 - ★ Test equipment from Black Star and Altai.
 - ★ New range of memory and MODEM ICs
 - ★ Full range of Electrolube aerosols and service aids.

The Autumn catalogue is on sale at your newsagent, or direct from our sales counters in Broxbourne, Herts, Brentwood, Essex and in Portsmouth.

CIRKIT - BIGGER STOCK, BETTER SERVICE

Park Lane, Broxbourne, Herts, EN10 7NQ - 0992-444111

NEWS: NEWS: NEWS:

DIARY

Electronics for Peace: London Group Meeting — September 5th
London New Technology Network, Camden, London, 7.30 pm. For details see September '85 ETI or 'phone 01-541 1825.

Vacation School On Cable Television — September 9-13th
Leeds Polytechnic. For details see September '85 ETI or 'phone 01 - 240 1871 extension 270.

RAE Course Enrolment - September 10th
Bradford & Ilkley Community College, Bradford. For details see September 1985 ETI or contact P. Nurse, Bradford & Ilkley Community College, Great Horton Road, Bradford, West Yorkshire BD7 1AY.

Interconnection Europe — September 10-12th
Cumberland Hotel, Marble Arch, London. For details see February '85 ETI or 'phone 0582 - 417438.

Alarm Training Seminars — September 24-27th
Castle Alarms, Windsor. Four one-day training seminars covering the basic technology, avoiding false alarms, system design and specification and business study. Aimed at engineers, security staff, management and surveyors, the cost is £85 plus VAT per day including lunch and refreshments. Castle Alarms and Electronics, North Street, Winkfield, Near Windsor, Berkshire SL4 4SY, tel 0344-886446.

Programming in C: A Hands-On Workshop — September 24-27th
London: venue to be announced. For details see July '85 ETI or contact ICS at the address below.

Computer Graphics Course — September 24-27th
Venue to be announced. For details see July '85 ETI or contact ICS at the address below.

Semiconductor International — October 1-3rd
NEC, Birmingham. For details see August '85 ETI or contact Cahners at the address below.

System Security Conference — October 2/3rd
Tara Hotel, London. For details see August '85 ETI or contact Online at the address below.

Offshore Computers Conference & Exhibition — October 8-10th
Aberdeen Exhibition & Conference Centre. Conference devoted to the use of computers in petroleum exploration. Thirty-seven papers from seven countries will be presented and the costs range from £160.00 + VAT for one day to £390 + VAT for the full event. Entry to the associated exhibition is free. Contact Offshore Exhibitions and Conferences Ltd, Rowe House, 55-59 Fife Road, Kingston upon Thames, Surrey KT1 1TA, tel 01-549 5831.

Technology Engineering Fair — October 8-11th
NEC, Birmingham. For details see August '85 ETI or contact Cahners at the address below.

Internecon UK — October 10/11th
Metropole Hotel and Brighton Centre, Brighton. For details see August '85 ETI or contact Cahners at the address below.

Computer Graphics '85 — October 15-18th
Wembley Conference Centre, London. For details see August '85 ETI or contact Online at the address below.

Electronic Displays '85 — October 29-31st
Kensington Exhibition Centre, London. For details see September '85 ETI or contact Network Events at the address below.

Addresses:
Cahners Exhibitions Ltd, Chatsworth House, 59 London Road, Twickenham, Middlesex TW1 3SZ, tel 01-891 5051.
ICS Publishing Co (UK) Ltd, 3 Swan Court, Leatherhead, Surrey KT22 8AD, tel 0372-379211.
Network Events Ltd, Printers Mews, Market Hill, Buckingham MK18 1JX, tel 0280-815226.
Online Conferences Ltd, Pinner Green House, Ash Hill Drive, Pinner, Middlesex HA5 2AE, tel 01-868 4466.

ETI

DIGITAL ELECTRONICS

**MADE
EASY**



SUPERKIT £22.00
SUPERKIT II £16.00
(£35.00 if bought together)

The **SUPERKIT** series introduces beginners to practical digital electronics. **SUPERKIT (SUP I)** is the first kit, which contains an instruction manual, a solderless breadboard, and components (7 integrated circuits, switch, resistors, capacitors, LEDs and wire). It teaches boolean logic, gating, flipflops, shift registers, ripple counters and half adders. **SUPERKIT II (SUP II)** extends **SUPERKIT**. It contains an instruction manual and components (10 integrated circuits, 7-segment display, resistors, capacitors and wire), and explains how to design and use adders, subtractors, counters, registers, pattern recognisers and 7-segment displays.

DIGITAL COMPUTER LOGIC £7.00
DIGITAL COMPUTER DESIGN £9.50
MICROPROCESSORS & MICROELECTRONICS £6.50

The **SUPERKIT** series is backed by our theory courses. **DIGITAL COMPUTER LOGIC (DCL)**, the beginners' course, covers the use and design of logical circuits, flipflops and registers. **DIGITAL COMPUTER DESIGN (DCD)**, a more advanced course, covers the design of digital computers both from their individual logic elements and from integrated circuits. **MICROPROCESSORS and MICROELECTRONICS (MIC)** teaches what a microprocessor is, how it evolved, how it is made and what it can do.

GUARANTEE. If you are not completely satisfied, return the item to us in good condition within 28 days for a full refund. All prices include worldwide surface postage (ask for prepayment invoice for airmail). Orders despatched within 48 hours. Overseas payment by international credit card or by bank draft drawn on a London bank.

CAMBRIDGE LEARNING LTD, Unit 15, Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs. PE17 4BR, England. Telephone: 0480 67446.

VAT No. 313026022 Transcash No. 2789159 Reg. No. 1328762

Please send me (initial letters used):

.....	SUP I	@ £22.00	DCL	@ £7.00
.....	SUP II	@ £16.00	DCD	@ £9.50
.....	SUP I + II	@ £35.00	MIC	@ £6.50

Full details of all your courses (please tick)

I enclose a cheque/PO payable to Cambridge Learning Ltd. for £.....

Please charge my credit card.
No. Expiry date

Telephone orders from credit card holders accepted on 0480 67446 (24 hrs).

Name

Address

..... Signature

CAMBRIDGE LEARNING LTD
Unit 15, Rivermill Site, FREEPOST,
St Ives, Huntingdon, Cambs PE17 4BR
England.



BBC Micro Computer System

ACORN COMPUTER SYSTEMS

BBC Model B Special offer	£300 (a)
BBC Model B+Econet	£335 (a)
BBC Model B+DFS	£348 (a)
BBC Model B+DFS +Econet	£399 (a)
BBC B Plus	£409 (a)

UPGRADE KITS

DFS Kit	£80 (d)
Econet Kit	£55 (d)

ACORN ADD-ON PRODUCTS

Z80 2nd Processor	£348 (a)
6502 2nd Processor	£178 (a)
Teltext Adaptor	£190 (b)
IEEE Interface	£282 (b)
Music 500	£173 (b)
RH Light pen	£29 (c)

BBC FIRMWARE

1.2 Operating System	£7.50 (d)
----------------------	-----------

Basic II ROM	£22.50 (d)
View 12.1 Word Processor ROM	£48.00 (c)
Wordwise Plus	£49.00 (d)
BCPL ROM/Disc	£52.00 (b)
Disc Doctor/Gremlin Debug ROM	£26 (d)
EXMON/TOOL KIT ROM	£23 ea (d)
Printmaster (FX80)/Graphics	£28 ea (d)
ULTRACALC spreadsheet ROM	£50 ea (c)
VIEW STORE/VIEW SHEET	£52 ea (c)
ISO PASCAL/LOGIC	£26 ea (c)
Oxford PASCAL/G-FORTH/LISP ROM	£43 ea (c)
ACCELERATOR (BASIC Compiler)	£56 (c)

COMMUNICATION ROM

Termi II	£26 (d)
Communicator	£57 (d)
Commstar	£27 (d)
DATABEB	£25 (d)

TORCH UNICORN products including the IBM Compatible GRADUATE in stock
For detailed specification on any of the BBC Firmware/Peripherals listed here or information on our complete range please write to us.

PRINTERS

EPSON

FX80FT + £220 (a)	FX80T + £210 (a)
FX80T the new NLQ printer	£242 (a)
FX80T £210 (a)	FX100 + £345 (a)
FX100 £430 (a)	
JX80 4 Colour Printer	£499 (a)
HI80 4 Colour Plotter	£399 (a)

KAGA TAXAN:

KP810	£245 (a)
KP910	£339 (a)

DAISY WHEELS:

JUKI 6100	£310 (a)
BROTHER HR15	£315 (a)

Paper:

2000 Sheets Fanfold:	
9.5" x 11"	£13 (b)
14.5" x 11"	£17.50 (b)
Labels: (per 1000)	
3.5" x 17/16" Single row	£5.25 (d)
27/16" x 17/16" Triple row	£5.00 (d)

ACCESSORIES

32K Internal Buffer Parallel £99 (b)

EPSON

Serial Interface: 8143	£28 (c);
8148 with 2K	£59 (c)
Paper Roll Holder	£17 (d);
FX80 Tractor Attachment	£37 (c)
Ribbons: FX/RX/MX80	£5 (d)
FX/RX/MX100	£10 (d)
RX/FX80 Dust Cover	£4.50 (d)

KAGA TAXAN

RS232 with 2K Buffer	£85 (c)
KP810/910 Ribbon	£6.00 (d)

JUKI 6100

RS232 with 2K Buffer	£85 (c)
Ribbon	£2.50 (d)
Tractor Attachment	£99 (a)
Sheet Feeder	£190 (a)
BBC Parallel Lead	£7 (d)
Serial Lead	£7 (d)

BROTHER HR15

Sheet Feeder	£189 (a)
Tractor Feed	£99 (a)
Ribbons Carbon or Nylon	£4.50 (a)

MODEMS

— All modems listed below are BT approved

MIRACLE WS2000:

The ultimate world standard modem covers all common CCITT standards (BELL standards outside the UK) up to 1200 Baud. Allows communication with virtually any computer system in the world. The optional AUTO DIAL and AUTO ANSWER boards enhance the considerable facilities already provided on the modem. Mains powered £129 (b), Auto Dial Board/Auto Answer Board £90 (c) each. (awaiting BT approval) Software lead £4.50.

NEW WS3000 SERIES

WS3000 V2123 (V21E V23)	£295 (a)
WS3000 V22 (as above plus 1200 baud full duplex)	£495 (a)

BUZZ BOX:

This pocket sized modem complies with V21 300/300 Baud and provides an ideal solution for communications between users, with main frame computers and bulletin boards at a very economic cost. Battery or mains operated, £88 (a), Mains adaptor £6 (c), BBC to Modem data lead £7.

Ask for details on WS3000

TECHNOLINE VIEWDATA SYSTEM
Using 'Prestel' type protocols for information and orders phone 01-450 9764. 24 hour service, 7 days a week.

DISC DRIVES

These are fully cases and wired drives with slim line high quality mechanisms. Drives supplied with cables manuals and formatting disc suitable for the BBC computer. All 80 track drives are supplied with 40/80 track switching as standard. All drives can operate in single or dual density format.

Single Drives:

1 x 100K 40T SS :TS100	£85 (b)
1 x 400K 40/80T DS :T400	£125 (b)

With Integral psu:

PS100 with psu	£120 (b)
PS400	£145 (b)

Dual Drives: (with Integral psu)

Stacked Version:	
PD200 2 x 100K 40T SS	£190 (a)
PD800 2 x 400K 80/40T DS	£265 (a)

Plinth Versions:

PD200	£215 (a)
PD800P	£289 (a)

Note: We can supply drives with Shugart mechanisms at considerably lower prices. Please phone for details.

3.5" Drives

TS35 1 x 400K 80T DS	£99 (b)
TD35 2 x 400K 80T DS	£175 (b)

3M 5 1/4" FLOPPY DISCS

High quality discs that offer a reliable error free performance for life. Each disc is individually tested and guaranteed for life. Ten discs are supplied in a sturdy cardboard box.

40T SS DD	£13 (c)
80T SS DD	£22 (c)

40T DS DD	£18 (c)
80T DS DD	£24 (c)

3 1/2" discs Pack of ten £38 (c)

DRIVE ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 20 disposable cleaning discs ensures continued optimum performance of the drives

Single Disc Cable	£8 (d)
10 Disc Library Case	£1.80 (c)
40 Disc Lockable Box	£14 (c)
Dual Disc Cable	£6.50 (d)
30 Disc Case	£8 (c)
100 Disc Lockable Box	£19 (c)

MONITORS

MICROVITEC 14" RGB:

1431 Standard Resolution	£185 (a)
1451 Medium Resolution	£240 (a)
1441 Hi Resolution	£399 (a)
1431 AP Std Res PAL/AUDIO	£205 (a)
1451 AP Med Res PAL/AUDIO	£280 (a)
1451 DQ3 Med Res for QL	£239 (a)

Above monitors are now available in plastic or metal cases, please specify your requirement.

Kaga Super Hi Res Vision III RGB	£325 (a)
Hi Res Vision II	£225 (a)

MONOCHROME MONITORS 12":

Kaga Green KX1201 G Hi Res	£99 (a)
Kaga Amber KX1201 A Hi Res	£105 (a)
Sanyo Green DM8112CX Hi Res	£90 (a)
Swivel Stand for Kaga Monochrome	£21 (c)

All monitors are supplied with leads suitable for the BBC Computer. Spare leads available.

SPECIAL OFFER

2764-25	£2.50
27128-25	£5.00
6264LP-15	£6.00

ATTENTION

All prices in this double page advertisement are subject to change without notice.

ALL PRICES EXCLUDE VAT
Please add carriage 50p unless indicated as follows:
(a) £8 (b) £2.50 (c) £1.50 (d) £1.00

GANG OF EIGHT INTELLIGENT FAST EPROM COPIER

Copies up to eight eproms at a time and accepts all single rail eproms up to 27256. Can reduce programming time by 80% by using manufacturer's suggested algorithms. Fixed Vpp of 21 & 25 volts and variable Vpp factory set at 12.5 volts. LCD display with alpha moving message. £395 (b).

SOFTY II

This low cost intelligent eprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2784. Displays 512 byte page on TV — has a serial and parallel I/O routines. Can be used as an emulator, cassette interface. Softy II. £195 (b)
Adaptor for 2764/2564. £25.00 (c)

UV ERASERS

All erasers with built in safety switch and mains indicator.
UV1 B erases up to 6 eproms at a time. £47 (c)
UV1 T as above but with a timer. £59 (c)
UV140 erases up to 14 eproms at a time. £88 (b)
UV141 as above but with a timer. £71 (b)

I.D. CONNECTORS

(Speedblock Type)			
No of ways	Header	Receptacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	180p	320p
40	230p	190p	340p
50	295p	200p	390p

D CONNECTORS

No of Ways 9 15 25 37

MALE:				
Ang.Plins	120	180	230	360
Solder	60	85	125	170
IDC	175	275	325	
FEMALE:				
St Pin	100	140	210	380
Ang.plins	160	210	275	440
Solder	90	130	195	290
IDC	195	325	375	
St Hood	90	95	100	120
Screw	130	150	175	
Lock				

TEXTPOOL ZIF

SOCKETS	24-pin	£7.50
	28-pin	£9.00
	40-pin	£12

EDGE CONNECTORS

2 x 8-way (commodore)	0.1"	0.156"
2 x 10-way	150p	300p
2 x 12-way (vic 20)	—	350p
2 x 18-way	—	140p
2 x 23-way (ZX81)	175p	220p
2 x 25-way	225p	220p
2 x 28-way (Spectrum)	200p	220p
2 x 36-way	250p	—
1 x 43-way	280p	—
2 x 22-way	190p	—
2 x 43-way	395p	—
1 x 77-way	400p	500p
2 x 50-way (S100conn)	500p	—

EURO CONNECTORS

DIN 41812	Plug	Socket
2 x 32 way St Pin	230p	275p
2 x 32 way Ang Pin	275p	320p
3 x 32 way St Pin	260p	300p
3 x 32 way Ang Pin	375p	400p
IDC Skt A + B	400p	400p
IDC Skt A + C	400p	400p

For 2 x 32 way please specify spacing (A + B, A + C).

AMPHENOL CONNECTORS

Solder		ZDC
36 way plug	800p	475p
36 way skt	550p	500p
24 way plug	—	—
IEEE	475p	475p
24 way skt	175p	—
IEEE	500p	500p
PCB Mtg Skt Ang Pin	—	—
24 way 700p	36way	750p

GENDER CHANGERS

25 way D type	
Male to Male	£10
Male to Female	£10
Female to Female	£10

RS 232 JUMPERS

(25 way D)	
24" Single end Male	£5.00
24" Single end Female	£5.25
24" Female Female	£10.00
24" Male Male	£9.50
24" Male Female	£9.50

DIL SWITCHES

4-way	90p
8-way	120p
6-way	105p
10-way	150p

TELEPHONE CONNECTORS

4 way plug	110p
6 way plug	180p
6 way rt.ang.skt	180p
Flexible cable	
4 way	50p/m
6 way	72p/m

RIBBON CABLE

(grey/metre)		
10-way	40p	34-way 180p
16-way	80p	40-way 180p
20-way	85p	50-way 200p
28-way	120p	64-way 280p

DIL HEADERS

Solder		IDC
14 pin	40p	100p
16 pin	50p	110p
18 pin	60p	—
20 pin	75p	—
24 pin	100p	150p
28 pin	180p	200p
40 pin	200p	225p

MISC CONNS

21 pin Scart Connector	200p
8 pin Video Connector	200p

74 SERIES

7400	30p	74182	140p	74LS162A	75p	74S08	80p	4063	85p
7401	30p	74184	140p	74LS163A	75p	74S10	80p	4066	40p
7402	30p	74185A	180p	74LS164	75p	74S11	75p	4067	230p
7403	30p	74190	180p	74LS165A	110p	74S20	80p	4068	25p
7404	30p	74191	130p	74LS166	130p	74S22	80p	4069	24p
7405	30p	74192	110p	74LS167	100p	74S23	80p	4071	24p
7406	40p	74193	115p	74LS169	140p	74S27	80p	4072	24p
7407	40p	74194	110p	74LS170A	100p	74S28	80p	4073	24p
7408	40p	74195	80p	74LS173A	100p	74S40	50p	4075	24p
7409	30p	74196	130p	74LS175	75p	74S41	45p	4078	25p
7410	30p	74197	110p	74LS181	200p	74S44	45p	4077	25p
7411	30p	74198	220p	74LS183	190p	74S74	70p	4078	25p
7412	30p	74201	110p	74LS190	75p	74S85	300p	4081	24p
7413	50p	74221	100p	74LS191	75p	74S86	100p	4082	25p
7414	70p	74259	150p	74LS192	80p	74S112	150p	4085	60p
7415	30p	74265	380p	74LS193	80p	74S113	120p	4086	75p
7416	30p	74273	200p	74LS194A	75p	74S114	120p	4089	120p
7417	40p	74276	140p	74LS195A	75p	74S124	300p	4093	35p
7418	40p	74278	170p	74LS196	80p	74S132	100p	4094	90p
7419	40p	74279	90p	74LS197	80p	74S133	60p	4095	90p
7420	30p	74283	105p	74LS201	80p	74S138	180p	4096	90p
7421	40p	74285	320p	74LS240	80p	74S139	180p	4097	270p
7422	40p	74290	90p	74LS241	80p	74S140	100p	4099	90p
7423	40p	74293	90p	74LS242	90p	74S151	150p	4501	36p
7424	40p	74298	180p	74LS243	90p	74S152	150p	4502	55p
7425	40p	74351	200p	74LS244	110p	74S157	200p	4503	36p
7426	30p	74356A	80p	74LS245	110p	74S158	200p	4504	95p
7427	30p	74366A	80p	74LS246	110p	74S159	200p	4505	360p
7428	30p	74367A	80p	74LS247	110p	74S163	200p	4506	360p
7429	30p	74368A	80p	74LS248	110p	74S169	350p	4507	360p
7430	30p	74369A	80p	74LS251	75p	74S174	300p	4508	30p
7431	40p	74376	160p	74LS252	75p	74S175	320p	4507/4030	90p
7432	40p	74390	110p	74LS256	90p	74S188	180p	4508	120p
7433	40p	74393	112p	74LS257A	70p	74S189	180p	4510	55p
7434	100p	74490	140p	74LS258A	70p	74S194	300p	4511	55p
7444	110p			74LS259	120p	74S195	300p	4512	55p
7445	100p			74LS260	75p	74S196	350p	4513	150p
7446A	100p			74LS261	120p	74S200	450p	4514	110p
7447A	100p			74LS266	60p	74S201	320p	4515	110p
7448	120p			74LS273	125p	74S225	520p	4516	55p
7449	30p			74LS279	70p	74S240	400p	4517	220p
7451	35p			74LS280	190p	74S241	400p	4518	48p
7453	35p			74LS283	80p	74S242	500p	4519	32p
7454	35p			74LS304	80p	74S251	250p	4520	60p
7455	35p			74LS305	24p	74S252	250p	4521	115p
7456	50p			74LS308	24p	74S258	250p	4522	80p
7457	50p			74LS309	24p	74S260	100p	4526	70p
7458	50p			74LS310	24p	74S261	300p	4527	80p
7459	50p			74LS311	24p	74S283	270p	4528	85p
7460	50p			74LS312	24p	74S287	225p	4529	100p
7461	85p			74LS313	34p	74S288	200p	4531	75p
7462	85p			74LS314	50p	74S289	225p	4532	65p
7463	105p			74LS315	24p	74S299	550p	4534	380p
7464	125p			74LS322	24p	74S373	400p	4536	250p
7465	110p			74LS324	24p	74S374	400p	4538	75p
7466	210p			74LS326	50p	74S375	400p	4539	75p
7467	210p			74LS327	24p	74S387	225p	4540	225p
7468	210p			74LS328	24p				
7469	50p			74LS329	24p				
7470	50p			74LS330	24p				
7471	50p			74LS331	24p				
7472	50p			74LS332	24p				
7473	50p			74LS333	24p				
7474	50p			74LS334	24p				
7475	50p			74LS335	24p				
7476	50p			74LS336	24p				
7477	50p			74LS337	24p				
7478	50p			74LS338	24p				
7479	210p			74LS339	24p				
7480	190p			74LS340	150p				
7481	75p			74LS341	80p				
7482	75p			74LS342	100p				
7483	110p			74LS343	100p				
7484	110p			74LS344	100p				
7485	110p			74LS345	100p				
7486	110p			74LS346	100p				
7487	110p			74LS347	100p				
7488	110p			74LS348	100p				
7489	110p			74LS349	100p				
7490	110p			74LS350	100p				
7491	110p			74LS351	100p				
7492	110p			74LS352	100p				
7493	110p			74LS353	100p				
7494	110p			74LS354	100p				
7495	110p			74LS355	100p				
7496	110p			74LS356	100p				
7497	110p			74LS357	100p				
7498	110p			74LS358	100p				
7499	110p			74LS359	100p				
7400	110p			74LS360	100p				
7401	110p			74LS361	100p				
7402	110p			74LS362	100p				
7403	110p			74LS363	100p				
7404	110p			74LS364	100p				
7405	110p			74LS365	100p				
7406	110p			74LS366	100p				
7407	110p			74LS367	100p				
7408	110p			74LS368	100p				
7409	110p			74LS369	100p				
7410	110p			74LS370	100p				
7411	110p			74LS371	100p				
7412	110p			74LS372	100p				
7413	110p			74LS373	100p				
7414	110p			74LS374	100p				
7415	110p			74LS375	100p				
7416	110p			74LS376	100p				
7417	110p			74LS377	100p				
7418	110p			74LS378	100p				
7419	110p			74LS379	100p				
7420	110p			74LS380	100p				
7421	110p			74LS381	100p				
7422	110p			74LS382	100p				
7423	110p			74LS383	100p				
7424	110p			74LS384	100p				
7425	110p			74LS385	100p				
7426	110p			74LS386	100p				
7427	110p			74LS387	100p				
7428	110p			74LS388	100p				
7429	110p			74LS389	100p				
7430	110p			74LS390	100p				
7431	110p			74LS391	100p				
7432	110p			74LS392	100p				
7433	110p			74LS393	100p				
7434	110p			74LS394	100p				
7435	110p			74LS395	100p				
7436	110p			74LS396	100p				
7437	110p			74LS397	100p				
7438	110p			74LS398	100p				
7439	110p			74LS399	100p				
7440	110p			74LS400	100p				
7441	110p			74LS401	100p				
7442	110p			74LS402	100p				
7443	110p			74LS403	100p				
7444	110p			74LS404	100p				
7445	110p			74LS405	100p				
7446	110p			74LS406	100p				
7447	110p			74LS407	100p				
7448	110p			74LS408	100p				
7449	110p			74LS409	100p				
7450	110p			74LS410	100p				
7451	110p			74LS411	100p				
7452	110p			74LS412	100p				
7453	110p			74LS413	100p				
7454	110p			74LS414	100p				
7455	110p			74LS415	100p				
7456	110p			74LS416	100p				
7457	110p			74LS417	100p				
7458	110p			74LS418	100p				
7459	110p			74LS419	100p				
7460	110p			74LS420	100p				
7461	110p			74LS421	100p				
7462	110p			74LS422	100p				
7463	110p			74LS423	100p				
7464	110p			74LS424	100p				
7465	110p			74LS425	100p				

READ/WRITE

Holey Filing System

Dear Sir,

It is now over a year since I submitted an item for your Tech Tips feature. I can only presume it is among the lost. I shall not moan on about not hearing from you, etc — let him with the perfect filing system cast the first stone. But please, please, let me hear from you soon. I can even take a rejection letter. Of course, I would much rather take a cheque for I am only a poor preacher (as you would realise if you had heard me).

Yours sincerely,
Alan Sharp (Rev.)
Aberdeen

Fear not, Reverend Alan, for that which was lost has been found and is even now among the chosen, in that heavenly place which men doth call the ETI Tech Tips feature. And great shall be your reward (well, almost) for your name is written in the book (in our accounts department) and a small slice of mammon will shortly be winging its way to you.

Thinking Along The Right Lines

Dear Sir,

Further to the article *Trains of Thought* in the September issue, I find Roger Amos' dual controller intriguing.

I would like to experiment along these lines and would appreciate a sight of his circuit. Perhaps we could have a further article on the subject?

Yours faithfully
C.W. Davies
Cardiff

I'm sure a lot of readers would like to experiment along these lines, so as soon as we track down Roger we'll pass on your comments.

Some Cases For John Linsley Hood

Dear Sir,

I read Dr P.A. Joiners letter in the August edition of ETI with great interest, because I have been trying since February to get a copy of Newrad's well advertised catalogue.

I have written on three separate occasions sending a large stamped addressed envelope as instructed. I have also made countless phone calls only to be answered by a phone answering system. I left my name and address and a message. On one occasion the phone was actually answered by a human being and I was told "our catalogues are being printed and you will receive one in two weeks" that was two months ago. Do these people want any customers?

Yours faithfully
M.B. Blight
Basingstoke

Dear Sir,

I greatly enjoyed reading John Linsley Hood's constructional series on his 80W amplifier design. However, for those of us who can't afford to build this design (or who do not require the power output), would it not be possible to persuade him to resurrect and up-date his simple Class-A design?

If the design could be updated to 15 or 20 watts and the high sensitivity input of the 80W design retained, life would be wonderful.

Yours faithfully
Colin Shelbourn
Windermere

The Class A amplifier (a design which was not originally published in this magazine, incidentally) would require significant modification before it could offer the sort of power levels you are talking about and even then the increase in volume level would be negligible. We will pass your comments on to JLLH, of course, but he may not have much time to consider them since he is busy working on his next ETI design!

Dear Sir,

I have recently built the Linsley Hood 80 watt amplifier, not from a kit but by etching my own boards and buying in components from suitable suppliers. I am generally pleased with the results and can confirm the claims for the quality of the

sound. The treble is more open and free from the 'tinselly' sound of my previous amplifier, and the overall sound is more detailed.

I do feel that I must take issue with Mr Linsley Hood on his choice of input sensitivity. The amplifier seems to be too sensitive and I have found it impossible to get rid of the hum induced from the input leads. I feel certain that this problem could be overcome by reducing the sensitivity to 774mV into 600R for full output.

I have tried to do this using a potential divider at the input in place of the volume control (I have a volume control in my pre-amplifier) but the hum problem remains. The most obvious solution would be to increase the negative feedback but I do not have the experience to do this. Would it be possible to prevail upon the designer to produce an alternative input arrangement, with a sensitivity tailored to 774mV at 600R?

I think that, if you consider the sources available today, this is a more realistic input requirement. Compact disc players have a standard output of about 2 volts, and I am sure that anybody who has one will agree that they are the highest quality source available. Radio sources can quite easily be amplified up to the level, and with the passage of time we may well see tuners produced which match the output of CD. The poor old vinyl disc section won't suffer from a bit of extra amplification, the quality being so obviously inferior anyway!

Yours faithfully
D.I. Field
Bath

It seems unlikely that hum problems should arise from JLLH's choice of input sensitivity and impedance. After all, if the input is too sensitive, simply turn the volume control down. If you still suffer from hum problems when the system is used at normal listening levels, the problem is not one of excessive sensitivity.

Too high an impedance can lead to hum pick-up, but the Audio Design amplifier has input impedances of approximately 47k into the disc stage and 100k into the main buffer stage, and both of these figures are perfectly standard. The 600R professional standard does have distinct advantages in the electronically noisy environment of a stage or recording studio (particularly when, as is usual,

the lines are also balanced to ground), but its advantages in a domestic environment are minimal and changing to the system is most unlikely to cure your hum problem. And even were a change of input impedance and reduced sensitivity likely to produce a solution, increasing the negative feedback would not be the best way of going about it. Changing the level of negative feedback in a carefully designed amplifier is guaranteed to have far-reaching and almost certainly unpleasant effects.

It seems more probable that your problem is caused by a hum loop or some similar wiring problem. If in doubt, why not send our Auntie Static a few more details of the problem with a diagram of the present wiring arrangements?

International Electronics

Dear Sir,

Greetings to all Electronics Today magazine staff. Please allow me to say something about myself. My name is Rodney Dulce and I'm 16 years old. I'm studying to be an electronics technician here in the Philippines.

I really like to read Electronics Today because it helps me with the school work. I have used the magazine as a reference for my school assignments and I consider it to be the best of its kind. It's very educational.

Unfortunately, most of the copies of ETI that I see are long out of date and are only borrowed. I would really like to have my own copy each month but I just cannot afford to buy it. My country has been facing an economic crisis for more than a year now and we are greatly affected by it. I don't even have enough to spend on basic needs and am just hoping that I can continue to attend the school.

The reason I am writing to you is that I would like to ask a favour. If possible I would like to have some back numbers of your magazine because I believe they would really help me. Even better would be to have a free subscription. I'm really ashamed at having to ask this but I do believe your magazine could help me a lot. I ask for your kindness and understanding.

Thank you so much and all power to the magazine.

Very respectfully yours,
Rodney Dulce
Cebu City
Philippines


We have sent a parcel of back issues off to Rodney, but we are unable to help him with a free subscription. As you might imagine, we get a lot of requests for such favours and we cannot afford to help all of them, nor have we the time or the ability to determine which are deserving cases and which are not.

Instead, it occurred to us that some of our readers might like to help. If anyone is interested in writing to Rodney and sending him their old copies on a regular basis, we would like to hear from them. It might be best if a group of individuals got together, or perhaps an electronics class in a school or college, and shared the postage costs.

Rather than risk having Rodney buried under a mountain of letters which he might then feel obliged to reply to, we have not printed his address but ask readers to write to us in the first instance. We will then sort through the responses and pass on his address to those who seem best placed to help him. — Ed.




NEWRAD INSTRUMENT CASES LTD
Unit 19, Industrial Estate, Gore Road
New Milton, Hants BH25 6SJ
Tel: New Milton 0425 621195

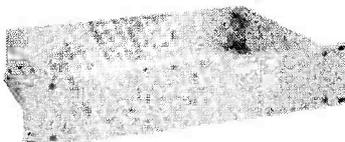	HEIGHT	DEPTH	PRICE
	1U	250	£18.84
	1U	300	21.35
	2U	250	22.05
	2U	300	24.69
	3U	250	25.22
	3U	30	27.99

19 inch Rack Mounting enclosures complete with chassis and top and bottom covers. Front, Side and Rear panels are aluminium and flat for easy machining. These panels are located with heavy duty aluminium extrusions. Front and Rear panels are satin anodised. Covers are finished in cream.

4U heights and depths of 400mm are available in minimum quantities of 10.

PRICES ARE EXCLUSIVE OF VAT. P&P £2.50.

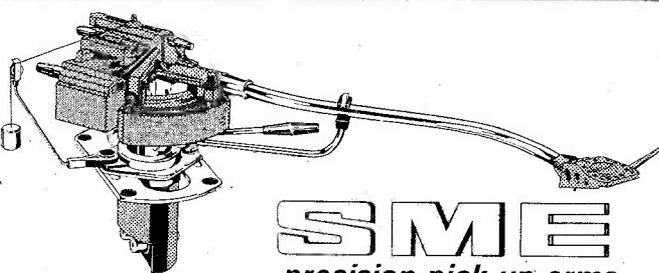

SME

precision pick-up arms

Please call or write:
SME Limited, Steyning, Sussex, BN4 3GY
Telephone: 0903 814321 Telex: 877808 G

AUDIO MODULES AT THE LOWEST PRICES

Now Distributed by Riscomp


POWER AMPLIFIERS

AL 1030 (AL30) - Low cost general purpose 10W/8ohm module, supply voltage range 18-30V.
 **£3.85 + VAT**

AL 1540 - At 15W/8ohm medium power module incorporating over-load protection. Operating voltage range 20-40V.
 **£4.15 + VAT**

AL 2550 (AL60) - Compact 25W/8ohm module for domestic applications with a distortion figure of .06%, operating voltage range 28-50V.
 **£4.95 + VAT**

AL 5070 (AL120) - Top class 50W/8ohm module with self-contained heat sink and built-in protection circuitry, produces really 1st class sound with a distortion level at an incredible .02%.
 **£12.45 + VAT**

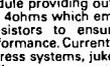AL 12580 (AL250) - A rugged top of the range module providing output powers of up to 125W into 4ohms which employs 4 heavy duty output transistors to ensure a stable and reliable performance. Currently used in disco units, public address systems, juke boxes and even domestic Hi-Fi.
 **£14.70 + VAT**

PRE-AMPLIFIERS & MIXERS

PA 207 - A quality stereo pre-amplifier and tone control unit suitable for driving any of the above amplifiers. Operates from a supply rail of 40-70V.
 **£13.95 + VAT**

MM 100 - 3 input mixer featuring individual level controls, master volume, treble & base controls, with inputs for microphone, magnetic pick-up and tape or second pick-up (selectable). Operates from 45-70V.
 **£12.40 + VAT**

MM 100G - As MM 100 except inputs are for 2 guitar + microphone.
£12.40 + VAT

POWER SUPPLY

SPM50/45/55/65 - A stabiliser module available in 3 voltages, 45/55 & 65V providing a stabilised output of up to 2A and providing a superior performance especially with the higher power audio modules. (Requires an appropriate transformer + reservoir capacitor).
 **£6.85 + VAT**

★ All modules supplied with a comprehensive Data Sheet. ★

Order by post, order by phone  
Add 15% V.A.T. to all prices
U.K. orders add 70p post & packing
Export orders - post & packing at cost

RISCOMP LIMITED
51 POPPY ROAD,
PRINCES RISBOROUGH,
BUCKS
Dept ETI 25
Tel: (084 44) 6326

AUNTIE STATIC'S PROBLEM CORNER

Dear Auntie,

I am at present building a hi-fi pre-amplifier which I hope to make remote-controllable, using the Plessey ML920 remote control receiver. Since I would like the amplifier to be the hi-fi of fi I would appreciate your advice on the following:

1) What would be the best means of input selection? I had thought of using a pair of LM1037 audio switches, but the specified THD of 0.04% seems

rather high. Would using individual FETs or DIL relays be more advantageous?

2) Can you suggest an appropriate IC to decode the 5-bit binary program selection output of the ML920?

3) Is the Mullard TDA1074 of high enough quality to be used as a volume and balance control?

Yours sincerely,

David Tilch,
Sandton,
South Africa

Your letter raises all kinds of interesting questions. On your first point, I can't tell you whether or not a THD figure of 0.04% will be suitable for your purposes — that is for you to decide — but a few general comments may help you to make up your mind.

If you look at the data sheet for the LM107 you will find that 0.04% is a 'typical' distortion figure measured with a 1kHz 1V RMS input-signal. Now, we all know that audio components tend to perform better towards the middle of the audio frequency range than at either end — distortion at 10Hz or 10kHz could well be much higher — but something even more misleading has crept in. What on earth is a typical distortion? If you buy an LM1037, can you be sure that the distortion will be 0.004% even at 1kHz? No, of course you can't

Look again at the data and you'll find a maximum distortion figure of 0.1% quoted (again at 1kHz, 1V RMS). This is a better figure to work with. If you design an amplifier expecting results based on this figure, the chances are you'll do better than you expected, but if you use the typical figure you could well be disappointed. It is just a meaningless number which helps the manufacturer to sell ICs. There is not even a standard way of calculating 'typical' performance figures. Is it the mean of a batch of measurements? The median? Or just a figure chosen at random? I know where I'd place my bets.

You may think I'm rather labouring the point, but 'typical' performance figures are creeping in all over the place, so be on your guard! Engineers will always work with worst case figures — if they can achieve their aims on that basis, any additional performance is a bonus. Taking 'typical' figures is just taking a gamble on whether or not the equipment will perform adequately. Having got that off my chest I will

return to the best means of input switching. As it happens, the distortion figures for the LM1037 are fairly constant from 20Hz to around 100kHz, and for inputs from 100mV RMS to 5V RMS. For good signal-to-noise figures, very small signals from record cartridges and such like should, of course, be amplified before being applied to this switch.

The LM1037 is a bipolar switch, if the circuit schematic is to be believed. It consists of a long-tailed pair for each input, the switching being achieved by turning the tail current sources on or off. You may well be able to achieve better distortion figures by the use of FETs, or the type of analogue switch consisting of FETs and switching logic all in one package. The results you will achieve with this type of device will depend as much on your design skills as on the device itself as the performance depends to a great extent on how it will interact with other components in the circuit.

As for relays, it is generally frowned upon to introduce unnecessary mechanical switching into the path of an audio signal. As hi-fi is an area where designers seem to support their own pet theories much as people of different inclinations might support a football team, I thought it best to attempt to ascertain whether this is a genuine engineering problem or just another piece of esoteric nonsense that surrounds hi-fi in general. After speaking to a number of relay manufacturers and audio engineers, the picture seems to be like this. First of all, new relays don't cause problems. If you use cheap 'n' cheerful relays, however, odd things can happen as they age. Silver contacts can end up with a coating of silver sulphide and unsealed types will gather dust and all kinds of grolly from the atmosphere on their contacts. The result is that if very small signals are applied, the contacts can rectify to some extent, appear to have a high resistance, or even fail to conduct at all.

Remembering that today's bog standard is yesterday's state of the art, engineers ten years ago would have found relays very troublesome. One answer that seems to have been used was to apply a DC 'wetting' current to the contacts and to superimpose the audio signal on top of this. You can imagine the thumps and other noises that would be heard from the speakers any time the relay contacts opened or closed. Naturally enough, relays were generally avoided when possible. Sad to say, instead of keeping up with technology, the idea that relays are no good for audio systems has entered hi-fi mythology as a rule to be followed come what may.

I am assured that a modern sealed relay with precious metal contacts that has been designed for signal switching is as good as, and often better than, solid state switches. There are even relays for very demanding applications such as thermocouple switching where the signal is likely to be a few mV at fractions of a μ A and no thermal offset from the relay's own contact material can be tolerated. In a nutshell, if you buy any old relay the chances are you'll have problems. If you buy one designed for signal switching, you won't.

Now to your second question. The ML920 is one of a series of remote control ICs from Plessey. The transmitter, SL490, responds to a switch matrix by generating one of 32 possible output codes according to the switch pressed. These codes are transmitted via an infra-red or ultrasonic link.

At the receiving end, the ML920 is one of a number of possible decoders. 'Program selection' refers to TV programs, by the way, as these ICs are intended for use in TV remote control. The outputs you can get from the various receiver ICs include a 5-bit binary code corresponding to the switch pressed at the transmitter, a 4-bit code, three analogue outputs and some control signals (from the ML922), also various other combinations of analogue and digital outputs.

Any further decoding you do will depend on the details of your circuit. The digital outputs are CMOS compatible (but not TTL) so any CMOS ICs can be used. You may find a BCD to ten line decoder useful with the ML922, for instance. I can't really be more specific than that.

Now for the TDA1074. Not having any data on the IC, I did the obvious thing and phoned Mullard. They claimed that it is indeed suitable for hi-fi, and since they were honest enough to say that some of their other ICs were not up to the mark, you may choose to believe them. Otherwise, I suggest you get hold of a data sheet and judge for yourself — Auntie.


ETI

Cortex

**HARDWARE
SOFTWARE**

- MDEX disc O/S + BASIC £95
- MDEX Professional Dev. Sys. £275
- CORTEX POWER-BASIC disc extensions £43
- MDEX Extensions**
- Editor £35
- Relocating Assembler/linker £35
- FORTH — screen editor, assembler £55
- graphics — better than BASIC £35
- PASCAL — by Pre Brinch Hansen £35
- QBASIC — fast BASIC compiler £35
- UCSD Pascal, SPL, META, WINDOW, SPELL £150
- CORTEX tape software**
- Pengo — fast machine code action £6
- Golf — excellent animation £6
- Micropede — rampant caterpillar £6
- Space Bugs, Pontoon, Breakout each £6
- Cassette/CDOS word processor £13
- Add £2 for software on CDOS disc
- Disc Drives**
- 80 track double-sided double-density £190
- 40 track single-sided double density £120
- E-BUS Floppy/Winchester Controller £135
- E-BUS 64/128 Kbytes DRAM card £145/£245
- E-BUS Joystick * centronics blakboard £13
- 80*24 Character video blank card £48

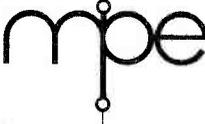State disc format and add VAT to all prices



MICRO PROCESSOR ENG LTD
21 HANLEY ROAD SHIRLEY
SOUTHAMPTON
SO1 5AP
TEL: 0703 775482



FREE CAREER BOOKLET

Train for success, for a better job, better pay!

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.
 Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!
 Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.
 Send for your **FREE CAREER BOOKLET** today — at no cost or obligation at all.

GCE		Choose from over 40 'O' and 'A' level subjects.	<input type="checkbox"/>
COMPUTER PROGRAMMING <input type="checkbox"/>	CAR MECHANICS <input type="checkbox"/>		
BOOK-KEEPING & ACCOUNTANCY <input type="checkbox"/>	INTERIOR DESIGN <input type="checkbox"/>		
POLICE ENTRANCE <input type="checkbox"/>	HOTEL MANAGEMENT <input type="checkbox"/>		
ELECTRONICS <input type="checkbox"/>	COMMERCIAL ART <input type="checkbox"/>		

Please send **FREE DETAILS** for the courses ticked above.

Name _____

Address _____

P. Code _____

ICS Dept. EBSA5, 312/314 High Street, Sutton,
 Surrey SM1 1PR. Tel: 01-643 9568/9 or
 041-221 2926 (both 24 hours)

For help with Reading and Writing

☎ 01-405 4017



Since 1975, 350,000 adults have been helped to read and write better. If you want help look for this sign.

For further information
Adult Literacy & Basic Skills Unit
PO Box 213 London WC1V 7ET

THE REAL COMPONENTS

John Linsley Hood brings his series to a close with a look at digital logic ICs.

The world of electronics is becoming dominated, increasingly, by digital devices and techniques. I suspect that some of my fellow electronics engineers, brought up in a far off time when all things were — more or less — linear, feel a little like medieval knights, beleaguered in their castles and surrounded by a sea of advancing black plastic caterpillars.

For myself, I do not complain. There seems nowadays to be a certain scarcity value in understanding how to handle signals that change gradually and irregularly from one voltage to another. However, I think that it is essential to understand the competition, if only so that it may be made to work for oneself as well. One can, even, make digital ICs function in a linear mode — not marvellously, perhaps, but they are certainly inexpensive. Such are the economies of scale for devices made in very large numbers.

However, to begin at the beginning.

Evolution

From their earliest days — and I can remember when a logic gate was a flip-flop made up from a 6SN7 valve — the desirable qualities of logic gates have been the same. A good gate should operate at high speed, have low current consumption and power dissipation, a good speed/power product, the ability to source and sink a reasonable amount of current, equality of output rise and fall times, good fan-out (the ability to drive many other similar gates), low noise susceptibility, and low noise generation. They should also be cheap!

Resistor-transistor logic (RTL) was one of the earliest forms of IC logic element and derived from the days when such devices were hard wired from discrete components. RTL ICs were created by the simple process of transferring the whole circuit on to the surface of a silicon slice. I have shown a typical circuit block which will operate as a 3-input NOR gate in Fig. 1.

The snags are that it is slow, has poor input noise immunity in the sense of being able to decide when the input signal is a 0 and when it is a 1, and the on-chip resistors are of such a value that they occupy a large chip area. This is now an obsolete system.

Diode-transistor logic (DTL) represents an improvement over RTL in that the number of resistors has been reduced and the input signal selection is performed by diodes, which don't occupy nearly as much space on the chip.

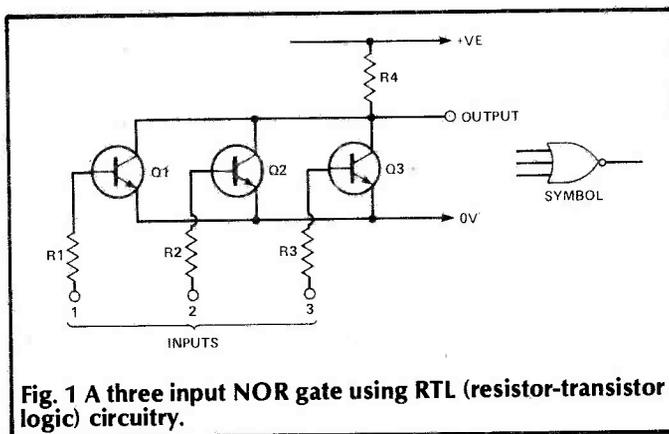


Fig. 1 A three input NOR gate using RTL (resistor-transistor logic) circuitry.

A typical 3-input NOR gate circuit of this type is shown in Fig. 2.

This style of logic gate is still pretty slow and inefficient in terms of power consumed. This is because the maximum pull-up speed at the output, referred to in the data books as T_{off} , is limited by the presence of inevitable output stray (PCB) capacitances, usually in the range 15-50pF. Their effect can be minimised by making R3 very small, but this uses a lot of current in the 'on' condition. They do have a reasonable noise

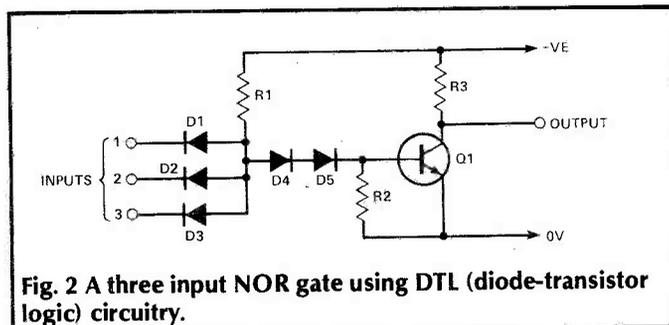


Fig. 2 A three input NOR gate using DTL (diode-transistor logic) circuitry.

immunity, however, and although obsolescent are still available for direct replacement purposes.

High noise immunity logic (HNIL) is also known as high threshold logic (or HTL), and is of the form shown in Fig. 3. This is a version of DTL in which the input 'on' threshold has been lifted by the inclusion of the zener diode, ZD1. Since there are better ways of achieving the threshold requirement, this type of circuit is also obsolete.

Transistor-transistor logic (TTL) in its 54 (military

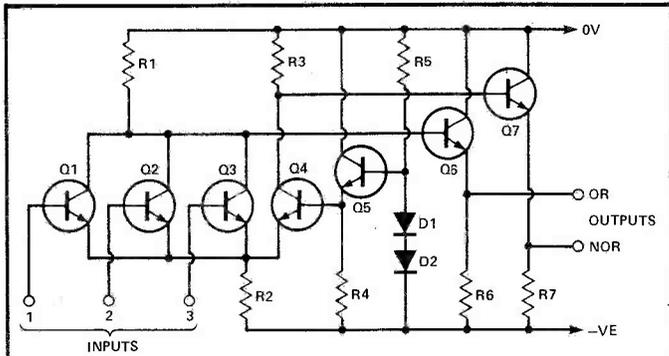


Fig. 8 A three input OR/NOR gate using ECL (emitter-coupled logic) circuitry.

In the particular circuit shown, a 3-input OR/NOR, the input transistors Q1-3 act with Q4 as an input long-tailed pair, in which, if the input goes positive, Q1-3 collectors will fall in potential and that of Q4 will rise. Q5 and diodes D1-2 just act to hold the base of Q4 at a fixed potential. It is fairly typical of ECL that both inverting and non-inverting outputs are provided.

ECL also has the distinction of being the logic system which uses the largest amount of power per gate of all the normal types, and also requires a negative power supply line. The symbol for this type of logic is distinguished by the arrows on input and output, as shown in Fig. 9. The commonly used logic units have the symbols shown in Fig. 10.

Complementary MOS

CMOS is one of the most useful and versatile of all the logic types, and is as much liked by the manufacturers as it is by me. One of its advantages is a very high input impedance, which means that there are no

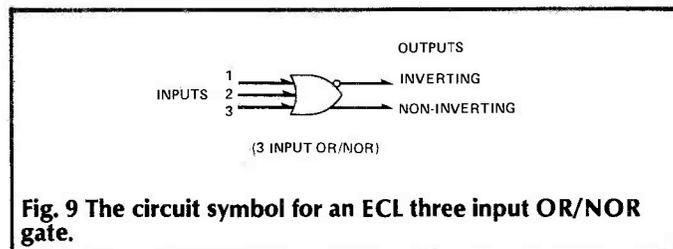


Fig. 9 The circuit symbol for an ECL three input OR/NOR gate.

problems over input drive capability from other logic elements or from outside signal sources. It requires very little operating power — static values of the order of $0.01\mu\text{W}/\text{gate}$ are quoted — and it is also quite tolerant about the supply line voltage. It will accept a supply anywhere in the range +3V to +15V, and I have occasionally had circuits survive careless application of 20-25V!

As with any other logic IC, it is prudent to lessen the possibility of unwanted gate triggering from spurious voltage spikes on the DC supply lines. This is done by liberally strewing small, non-inductive capacitors (ceramic disc or similar) along the +ve rail to decouple this to the ground plane, as close as possible to the supply input to the IC.

Its popularity with the manufacturers is due to the fact that CMOS gates are very easy to fabricate, and use nothing other than P-channel and N-channel MOS transistors. No diodes, no zeners, no resistors! As an example I have shown a simple inverter stage in Fig. 11, and a 2-input NOR in Fig. 12.

Its disadvantages are its relatively slow switching speed and its susceptibility to unwanted signal pick-up due to its high input impedance gate characteristics. However, unless you are in the world of main-frame computers, its relatively slow propagation speed is unlikely to be a major problem. The CMOS gate inputs are, however, a little static sensitive, though often the makers protect them by the incorporation of the diodes D1-4 shown in Fig. 12.

In the 18 or so years since these devices became available, I do not know that I have ever damaged one by careless handling — though I wouldn't go so far as to say that none have ever given up the struggle because I inadvertently wired them up in some particularly idiotic fashion.

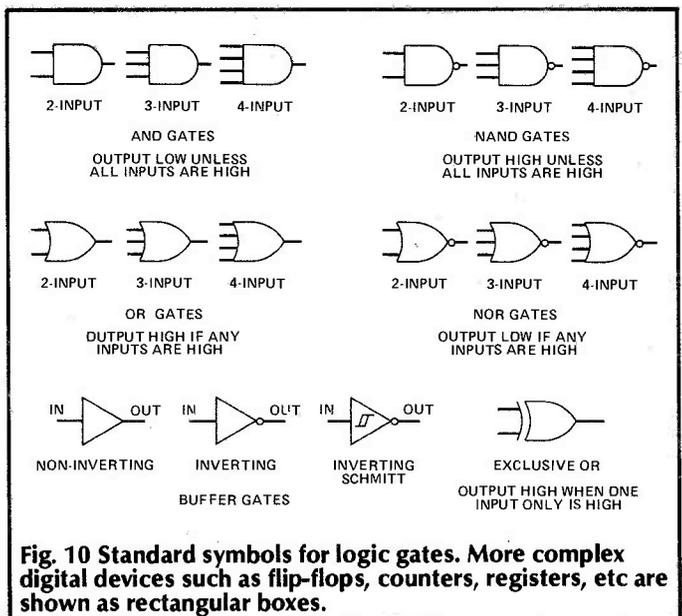


Fig. 10 Standard symbols for logic gates. More complex digital devices such as flip-flops, counters, registers, etc are shown as rectangular boxes.

Construction Methods

To illustrate the advantage of the CMOS structure, I have shown in Fig. 13a some cross sections of a bipolar IC (eg. TTL), showing three of the various circuit elements. At least nine of these would probably be needed to make a functioning gate. In Fig. 13b, for comparison, I have shown the cross section of a complete CMOS inverting buffer.

The more elements there are in an IC, the larger the chip area and the more costly it will be. Also, the more complex the IC is, the greater will be the failure rate for that IC type. Because of this it is understandable that a lot of effort has been put into developing further the simple and compact CMOS structure, which gives good yields and high profits.


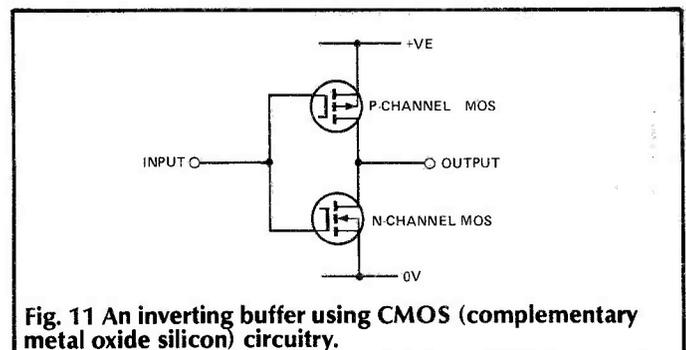


Fig. 11 An inverting buffer using CMOS (complementary metal oxide silicon) circuitry.

Both Schottky TTL and CMOS types have benefitted from a lot of recent development work. In the case of Schottky, the first stage was to reduce the power consumption to something nearer the 1mW/gate figure of low power TTL (74L00), but without the slow response of the 74L00 types (33ns/gate transition). In the event the 74LS00 (Low-power Schottky) types achieve some 9-13ns/gate with a 1mW power outlay.

A further development along these lines has been the Advanced Low Power Schottky types (known as ALS or Fast), which achieve 3-4ns transition speeds and yet only consume 1-2mW/gate. Meanwhile, the Advanced Schottky (AS) types have attained an operating speed approaching that of ECL (1.5ns/gate or 200MHz clock speed) without the associated problem of awkwardness in use. They have a gate dissipation of 20mW, as compared with a 25-60mW/gate dissipation for ECL.

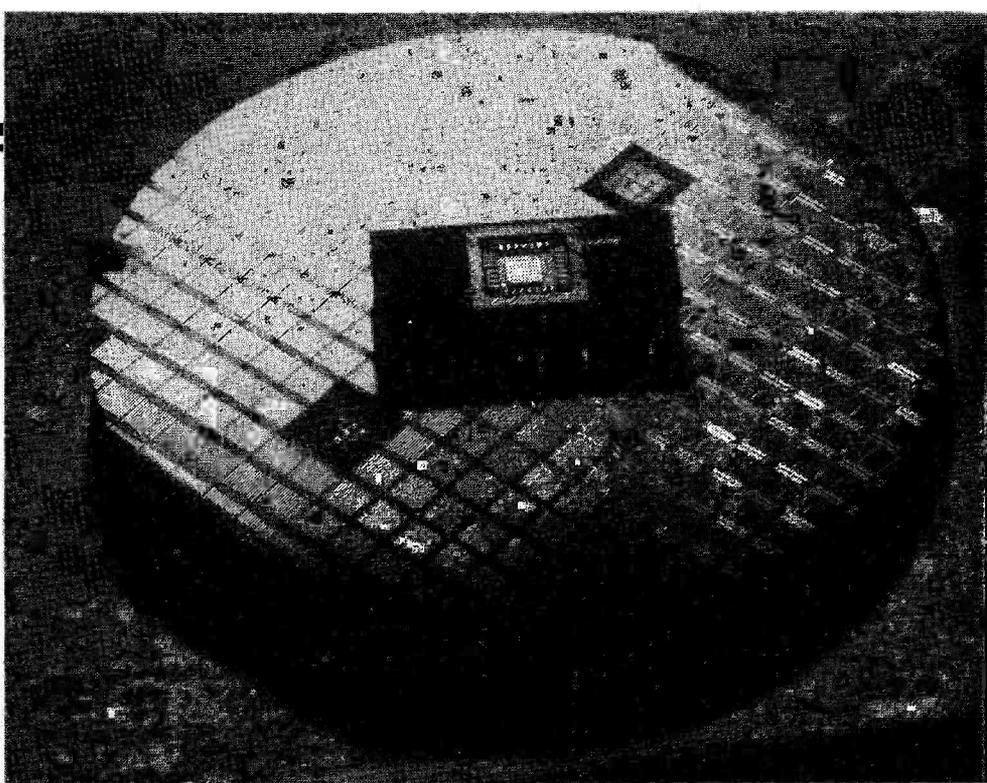On the CMOS front, development has involved replacing the aluminium metallising of the gate elec-



trode with polycrystalline silicon. This can be more precisely deposited, in narrower regions, which allows a considerable reduction in the parasitic gate capacitances. The resulting gate propagation delay is of the order of 7-10ns, which is very similar to low power Schottky and faster than the standard 7400 TTL. The poly gate CMOS (74HC00) is specified for operation in the 4.75-5.25V TTL supply range.

Performance Data

I have summarised the performance characteristics in terms of speed and current consumption in Tables 1 and 2, and I have provided a pecking order list for the various types in Table 3. However, there are some things which must be borne in mind when reading such data, mainly related to the gentle art of specification writing.

I think the statistics quoted for digital ICs are pretty honest (well, relatively so!). This may have something to do with the fact that the digital circuit fraternity tend to be young, and the writers are, perhaps, not yet steeped in guile. Certainly in the field of linear ICs I

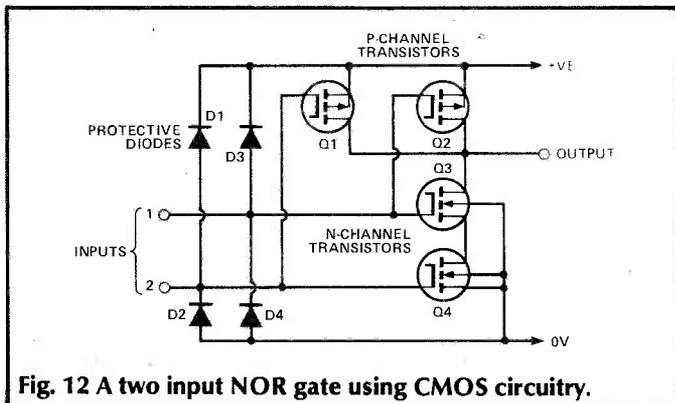


Fig. 12 A two input NOR gate using CMOS circuitry.

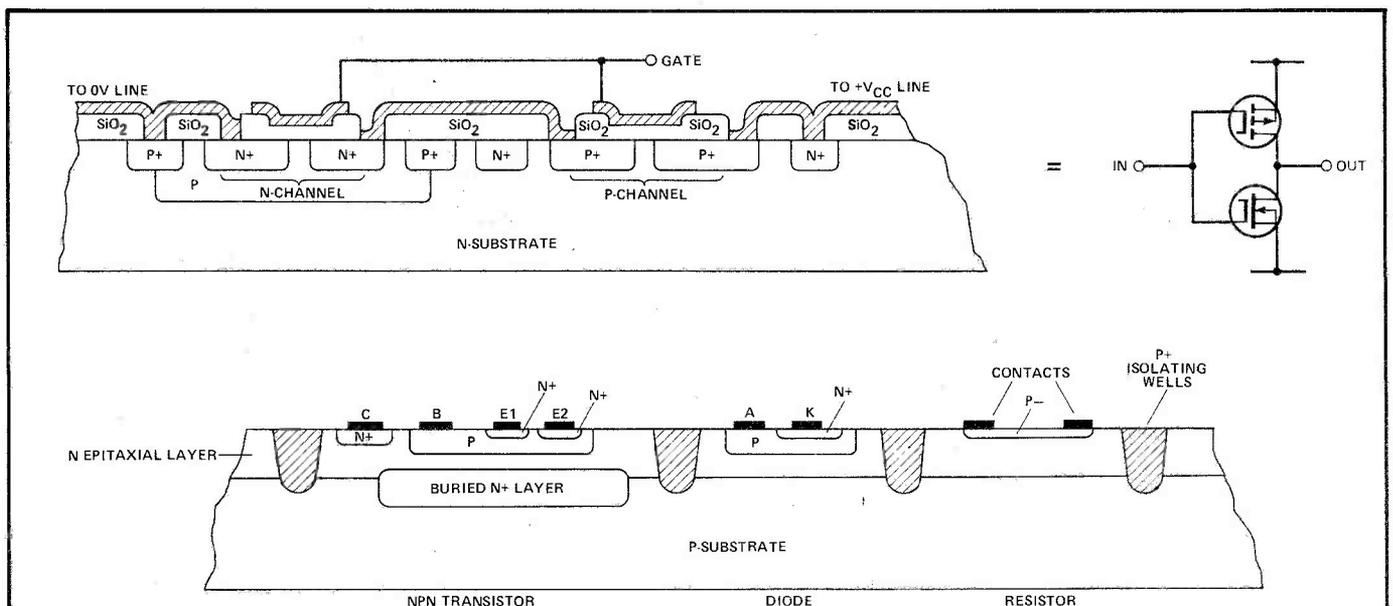


Fig. 13 Cross-sections through a) a CMOS chip and b) a TTL chip.

sometimes get the feeling that the specifications are written by temporarily unemployed science fiction authors.

With regard to the CMOS ICs, the main thing to remember is that the gate propagation delay will be worse at the lower voltages, so the specifications will usually quote the gate delay at 10 or 15V where it is better. There are two types of CMOS IC, the 7400 pin compatible 74C (and now 74HC) varieties, and the generally non-compatible 4000 series. The 4000 series devices will usually be specified for an output (stray capacitance) load value of 15pF, whereas, in practice, 20-40pF is probably nearer the truth. The

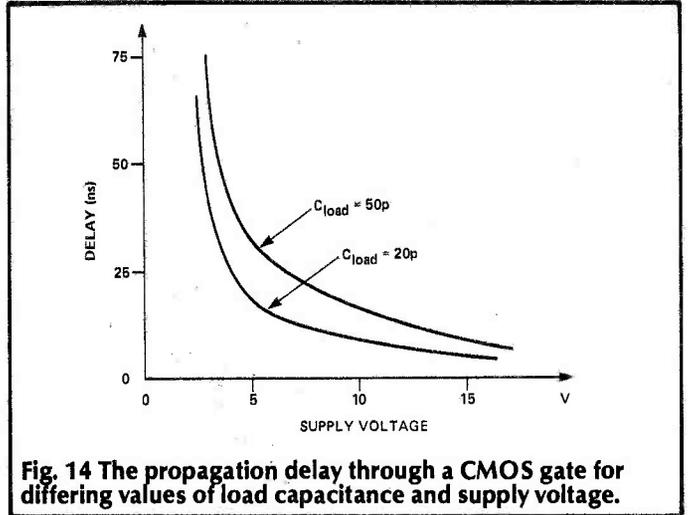


Fig. 14 The propagation delay through a CMOS gate for differing values of load capacitance and supply voltage.

74C types are a bit faster, and are specified for a 50pF output load, but usually at 10V supply voltage.

Another factor which must be remembered is that one gate does not make a logic IC (with the exception perhaps of an inverting buffer). So, IC types quoted at 15ns/gate, such as the 4000 series, may still introduce a considerable delay. For example, the delay from data to output in a CD4013 dual D-type flip-flop operated from 5V is 200ns. The 74C74 is marginally faster at 180ns. The 10V figures are better, at 80ns and 70ns respectively.

The way in which CMOS propagation delay varies with output capacitance and supply voltage is shown in Fig. 14. There will be no significant effects inside the device because the internal circuit capacitances will only be 1-2pF. I have also shown the input/output voltage transfer characteristics of a typical CMOS

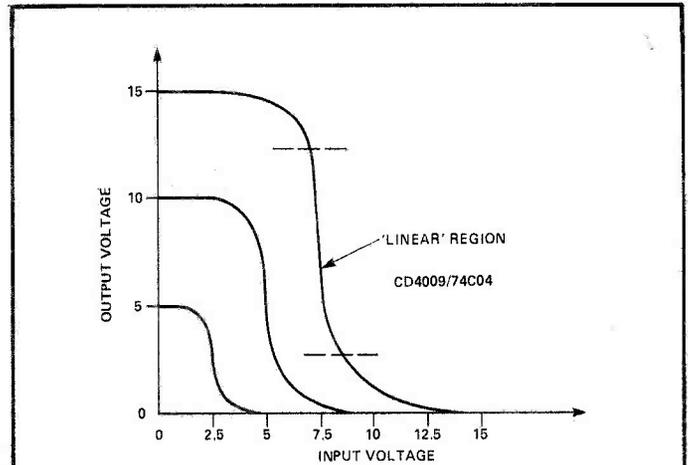


Fig. 15 Transfer characteristics for a CMOS inverting buffer.

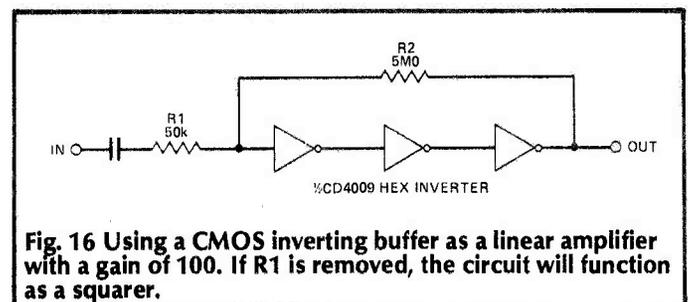


Fig. 16 Using a CMOS inverting buffer as a linear amplifier with a gain of 100. If R1 is removed, the circuit will function as a squarer.

Device Type	Series Code	Maximum Frequency
Low power TTL	74L00	3MHz
Standard CMOS (5V)	4000	5MHz
Standard CMOS (15V)	74C00	15MHz
Standard TTL	7400	35MHz
Low power Schottky	74LS00	45MHz
High speed TTL	74H00	50MHz
High speed CMOS (5V)	74HC00	50MHz
Standard Schottky	74S00	125MHz
Advanced low power Schottky	74ALS00	60MHz
Advanced Schottky	74AS00	200MHz
Emitter coupled logic	MC10100	500MHz

Table 1 Contemporary logic IC types ranked according to maximum operating frequency.

Device Type	Gate Propagation Delay (per gate)	Power Consumption (per gate)
Low power TTL	33ns (50pF)	1mW
	26ns (15pF)	
Low power Schottky	13ns (50pF)	2 mW
	9ns (15pF)	
Advanced Low power Schottky	3-4ns (50pF)	1-2 mW
Standard TTL	15ns (50pF)	10 mW
	10ns (15pF)	
Standard Schottky	4.5ns (50pF)	20mW
	3ns (15pF)	
Advanced Schottky	1.5ns (50pF)	20 mW
Standard CMOS (10V)	20ns (50pF)	Negligible at LF
	15ns (15pF)	
High speed CMOS (5V)	10ns (50pF)	Negligible at LF
	7.5ns (15pF)	

Table 2. Comparison of the speed and power consumption of contemporary logic IC types. Note that buffered devices will always have greater propagation delays.

Logic Family	Speed	Power Dissipation	Fan Out	Noise Immunity	Noise Generation
DTL	6	4	3	4	2
TTL	5	4	3	3	3
S	3	5	3	3	3
LS	4	2	3	3	3
ALS	4	2	3	3	3
AS	2	5	3	3	3
ECL	1	6	2	3	1
NMOS	5	2	2	2	2
CMOS	6	1	1	1	2
HCMOS	4	1	1	1	2


Table 3 A league table of logic IC performance. A '1' indicates the best performance and a '6' the poorest.

FEATURE: Real Components

inverter, such as the CD4009 or 74C04, in Fig. 15. As these characteristics suggest, it is possible to use the device in a linear amplifier mode, as shown in Fig. 16. This particular kind of circuit is useful in amplifying and squaring-off input AC signals of up to 10MHz or so, although the output waveform won't be very square above a few hundred kilohertz due to the absence of the higher harmonics.

A point which must be watched in all CMOS logic ICs is that unused gate inputs must not be left to float. All unwanted inputs should be tied either to the OV or the +Vcc line. Unless this point is remembered, endless problems can arise.

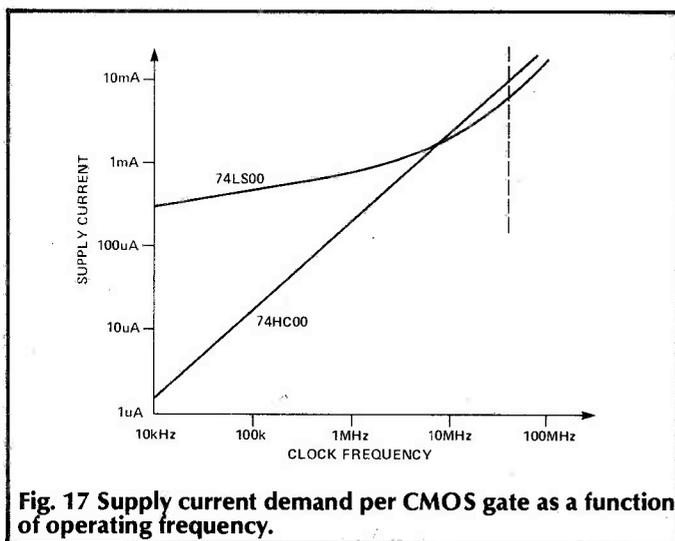Also, while CMOS dissipates very little power when used in static or low frequency switching applications, as the clock frequency rises more and



more power will be required to charge and discharge the output load (stray) capacitance, so the gate dissipation will also increase. I have shown a graph of dissipation versus clock frequency for a CMOS gate in Fig. 17. Other logic systems will follow a similar pattern at the higher frequency end of the curve.

Cost

This is a major factor in the use and choice of ICs and is influenced, to a dramatic extent, by the popularity of the IC in question.

This means that if an IC has been overtaken in performance by a competitive type, not only will the cost of the competitive IC decrease as more are made or as a promotional ploy by the makers, but the price of the IC which it replaces will now increase as the numbers sold decline. So, although I have listed the relative costs of various forms of the same logic IC (a quad 2-input NAND gate) in Table 4, these relative costs

Device Type	Series	Cost (1 off) 1985
CMOS	CD 4011	34-88p
LS	74LS00	40-80p
HCMOS	74HC00	40-123p
	74HCT00	
ALS	74ALS00	49-70p
	74F00	
TTL	7400	57-111p
CMOS	74C00	60-110p
AS	74AS00	71p
ECL	MC10104	160p
S	74S00	176p

Table 4 Comparative cost of different types of quad two input NAND gate.


are changing as time passes. In a year's time, the dearest may no longer be available and the cheapest may no longer be the cheapest.

Large Scale Integration

LSI is the great success story in the digital IC field, allowing very complex functions to be achieved on a single IC chip by joining together very large numbers of relatively simple logic gates.

LSI derives largely from developments in MOS technology, although bipolar Integrated Injection Logic which uses simplified transistor circuitry of the type shown in Fig. 18 has had some success in computer work. However, the main need was for simple, low chip area circuitry with very low power dissipation per gate, and this was provided most effectively by MOS technology, either as NMOS with further NMOS devices acting as load resistors, or, more recently, with CMOS.

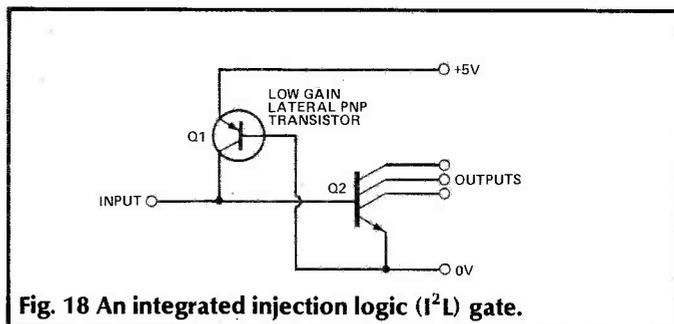Many small personal computers, such as the one on which I am typing this article, are based on NMOS



LSI single chip microprocessor ICs, like the Z80 and the 8080A. However, advanced poly silicon gate CMOS offers higher operating speeds and reduced power consumption, often as little as 5% of that for the equivalent NMOS circuitry.

I have listed some of the current applications of LSI ICs of the CPU/RAM/ROM types in Table 5, in increasing order of chip complexity.


ETI

	Calculators Controllers Printers Sequence timers	Process controllers Automatic instruments Data loggers Games Automotive	Smart terminals Billing/Accounting Point of sale hardware Personal Computers	Minicomputers Advanced instruments Intelligent terminals
ROM	1-2K	1-4K	2-16K	8K+
RAM	32-128	64-256	128-64K	4K++
I/O Lines	10-32	20-64	32-200	128+
Peripherals	0-1	0-3	1-8	5+

Table 5 Typical applications for single-chip LSI (large scale integration) devices ranked according to degree of complexity.

POWER AMPLIFIER MODULES

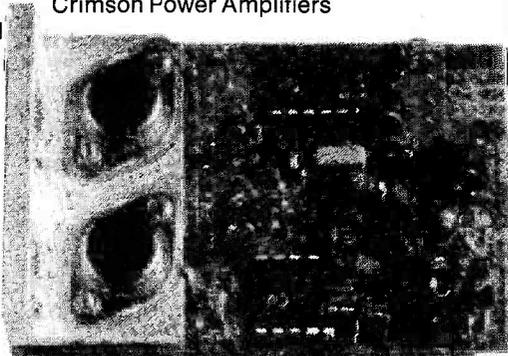After years of extensive tests and empirical research, Crimson have developed the ultimate in Bipolar Power Amplifier Modules, making Crimson Power Amplifiers the most sophisticated and highly protected modules available today.



All of these modules now incorporate the following:

- HP Protection — Automatic shutdown to prevent damage from unstable signal source.
- Thermal Protection — A Thermal Sensor which again causes the amplifier to enter the Shutdown Mode before any danger is reached.
- Power Supply Protection — Diodes have been added to the P.C.B. to prevent reverse polarity damage.

MODULE	POWER/LOAD	PRICE INC. V.A.T. P&P
CE608	60 8Ω	£21.00
CE1004	100 4Ω	£24.50
CE1008	100 8Ω	£27.50
CE1704	170 4Ω	£35.00
CE1708	170 8Ω	£35.00

Full details of our complete range including Power Supplies, Preamps, Mosfets etc available on large sae or contact our agents:

BRADLEY MARSHALL
382-386 EDGWARE RD
LONDON
W2 1EB

WILMSLOW AUDIOS
35-39 CHURCH ST
WILMSLOW
CHESHIRE

CRIMSON ELEKTRIK STOKE
PHOENIX WORKS, 500 KING ST, LONGTON,
STOKE-ON-TRENT, STAFFS. PHONE 0782 330520

You can depend on

ELECTROVALUE

to supply the fine
range of test &
measurement
gear by

thandar


Made
in
U.K.

- counters
- multimeters
- scopes
- signal generators etc.

**FREE 44 PAGE
PRICED AND
ILLUSTRATED
CATALOGUE ON
REQUEST**
● Over 6000 items stocked

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham,
Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475
North Branch, 680 Burnage Lane, Manchester M19 1NA
Telephone 061 432 4945
Please mention this publication when replying

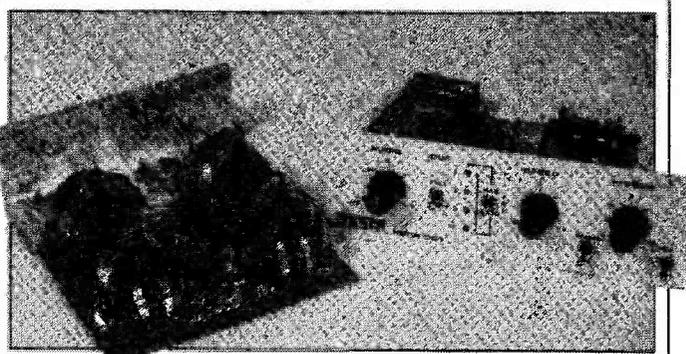BRITAINS FOREMOST QUALITY COMPONENT SUPPLIERS



HIGH QUALITY ELECTRONIC MODULES

- 100W Mono & Stereo professional amplifiers shown in last months issue **£98 & £140.**
 - Disco Lighting Module 750 watts per chan, 4 chan, forward reverse chase **£15.40.**
 - Disco Sequencer Moduel 1024 sequnces, 1000 watts per chan ¼ chan (selectable), zero cross and inductive load. **£40.65.**
 - Amplifier Modules Mos-fet Low distortion .008%, on board protection fuses and power supply requires only transformer & heatsinks, saves **£££'s.**
- Amplifier chassis from 100W Mono to 250W Stereo. Professional Mos-fet for O.E.M. from **£36.95.** All amplifiers are fitted with redpoint black on Heatsinks for reliability. Input Impedance 47K ohm, Input sensitivity 0.775 volts, Total harmonic distortion .008%, Damp factor > 400, frequency response DC - 40KHZ & Slew rate 70 v/us.
- Heatsinks Ex Stock. 2.1 c/w redpoint heatsinks **£2.50.**
 - **Send 20p and a large S.A.E. for specifications & price list on above products and more!!!**

Send to:

TECHNOCROWN LTD
42 Fallowfield, Luton, Bedfordshire LU3 1PX
Tel: 0582-598167
Mail order only.

Postal charges per order £1. Welcome schools, colleges, and Trade. - Securicor £10.00 delivery.

THE SAMPLE LIFE

Paul Chappell tests the water and gives some samples of the problems and solutions facing the designer of a low-cost digital sound sampler.

Several years ago I remember seeing a *Tomorrow's World* which featured a new kind of musical instrument. It looked like an ordinary electronic organ, but instead of generating its own sounds it borrowed them from the outside world. The sound of a violin, say, would be recorded into the instrument's memory through a microphone. Pressing a note on the keyboard would then give the sound of a violin at the appropriate pitch, by varying the speed at which the sampled sound was played back.

Commercial Sound Samplers

Leaving aside instruments such as the Fairlight, which will set you back more than £20,000, and the Emulator at around £7,000, you can now buy a self contained sampler and keyboard, the Ensoniq Mirage, for a mere £1700. To get anything cheaper, you'll have to supply some odds and ends yourself. For instance, the Akai S612 polyphonic sampler at £800 or so has no keyboard, you'll have to provide one, and if you want to store the sounds you've sampled you'll also need a disc drive. Powertran's MCS1 costs around £600 as a kit, but is only monophonic. The MCS1 and S612 can be controlled by a BBC micro, or any computer with a MIDI interface.

At the budget end of the market there are some very low cost devices. The sound quality and features you can expect from these bear very little relation to the price tag, so it's worth taking a good look at the spec sheets to see just what you'll be getting before breaking open your piggy bank. One possibility is the Logitech sampler at £200, a low budget sampler with a low budget sound if the reviews are to be believed. Then there is the Greengate DS3, an add-on for the Apple computer. The sampler box and software will cost you £280 and the music keyboard (as opposed to the computer keyboard) is another £280 on top of this.

The main differences, apart from how many extras you will have to buy, are in sound quality, sound manipulation and editing facilities, and the number of notes you can play at once. The simplest devices, such as the Logitech, use 8-bit linear sampling which implies poor dynamic range and high quantisation noise. They can only play one note at a time. The DS3 also uses linear sampling, but has good editing facilities and is 4-note polyphonic. If 'dynamic range' and 'quantisation noise' are mysterious concepts to you, hold your breath a moment.

Build Your Own

These days it is not particularly difficult to build your own sampler as an add-on for a home computer. A very basic design for the Spectrum appeared in a music magazine not so long ago. It consisted of four ICs for A-D and D-A conversion and address decoding. The Spectrum RAM was used to store the sample. There was no filtering of any kind and the sound would hardly have been super-fi, but no doubt it was

fun to experiment with, which was all it was really intended for.

So what is the ETI design to be? A single chip add-on for the ZX81 or a Fairlight look alike that will still leave you with some change from a second hand Ford Cortina? After much debate ('What do you think we should do, Alf? 'Search me!') we eventually decided on a Spectrum add-on. At the moment you can pick up a brand new Spectrum for the price of a cup of coffee, so there's no excuse for saying you haven't got one. As for the circuit itself, our efforts have been directed towards getting the sound right rather than



The Greengate sound sampler (bottom right) and all the other necessary bits and pieces,


adding extra gadgets. Constructional details will begin next month, all being well, so have your soldering irons warmed up and ready for action.

General Principles

The hardware used to translate analogue signals to digital form and back again has recently been described in the pages of ETI (August, 1985), so I won't go over the same ground again. What this feature on A-to-D and D-to-A conversion didn't mention, however, were the practical consequences of performing the translation. The waveform that is

recovered from a digital sampling process is never quite the same as the waveform that went in. Sampling, by its very nature, breaks continuous waveforms into discontinuous elements. The trick is to get it as close as possible to the original. Without taking any special precautions, you will certainly end up with a sound that is recognisable, but it will be noisy and distorted. Why does it happen, and what can be done about it?

First of all, we have the problem that a fixed number of 'quantisation levels' are available according to the number of bits that will represent the sample digitally. We would like each sample to equal the exact value of the analogue signal at the time. Instead, we must round it up or down to the nearest level for which a digital code is available. A 2V signal, for example, would be okay for an 8-bit sampler, but 2.005V would not.

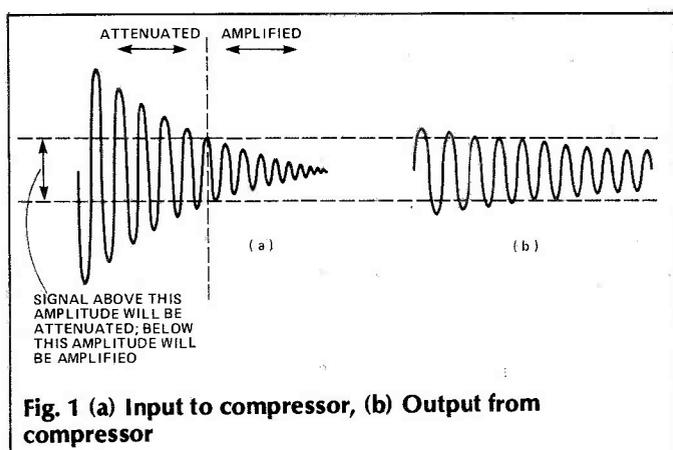

resulting variation between two possible output levels would not track all the nuances of the input with any degree of precision.

Comanding

The simplest solution to this problem is to ask the user to adjust the input so that the ADC is operated as close as possible to its overload level without actually exceeding it. Not very practical, you think? Just take a look at the Greengate sampler, which does exactly this.

Assuming that the sound to be sampled can be repeated a few times to allow the input level to be adjusted, we are still left with the problem that as the sound decays the noise will increase. A piano note, for example, will begin with a high amplitude as the hammer strikes the string. The amplitude will then drop away quickly to a much lower sustain level. A sampler adjusted to accept the initial level would not give very good results during the sustain period.

Another possibility is to adjust the sound level electronically. Devices which do this are called *companders* (compressor/expanders) and are available ready made in the form of ICs. In essence, the compressor section will reduce the amplitude of signals that are above a certain pre-defined level and increase the amplitude of small signals, so that the range of amplitudes is close to a constant level (Fig. 1). Thus output will have a substantially reduced, or compressed, dynamic range and the signal can be kept close to the overload point of the sampler at all times. The expander section returns the dynamic range to normal after the signal has been translated back into the analogue form.

The result of the rounding process is known as *quantisation noise* and sounds very much like the kind of thermal noise hiss that any audio equipment will make to a greater or lesser extent. Intuitively, you can see why it sounds like noise by thinking of the difference between the true value of the audio signal and its quantised value as an extra and unwanted signal that is superimposed on the input.

For an arbitrary input, the value of this extra signal at each sampling will be random, in the sense that it will not be related in any obvious way to the harmonic structure of the input, will not repeat, and so on. There are certain inputs for which this will not be the case, but for general audio signals it's a reasonable way to look at the situation. The main difference between quantisation noise and thermal noise is that quantisation noise is only present when the sound is being reproduced, while thermal noise is there in the background all the time.

For an 8-bit word length, which we are more or less stuck with if we want to make use of Spectrum's memory for storing the samples, the signal-to-noise ratio will be 48dB for a signal which is large enough to make use of all 256 available quantisation levels. This is certainly not hi-fi, but could be tolerated; a cheap domestic tape recorder will give similar results.

Unfortunately, the signal-to-noise ratio degrades very quickly as the amplitude of the input signal drops. For an input 20dB below the overload point (the point at which the A-D converter runs out of codes) the S/N ratio is a mere 28dB. Not too good. The reason for the degradation is fairly obvious; in the extreme case the input may be so small that it only alters the least significant bit in the binary code. The

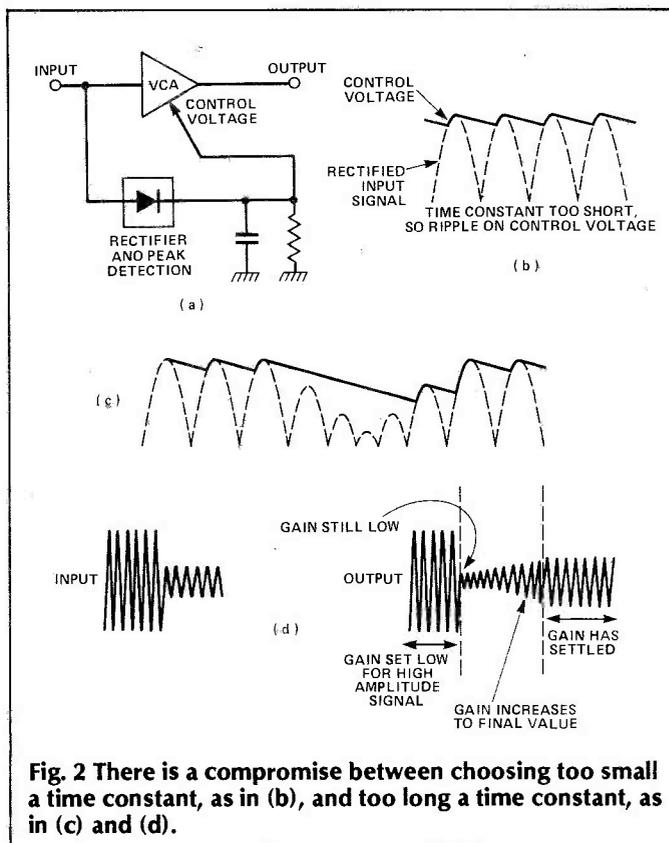


Fig. 2 There is a compromise between choosing too small a time constant, as in (b), and too long a time constant, as in (c) and (d).

This is all very well in theory, but companders work by taking an average of the signal level and using this average to control a VCA which modifies the output

level. The averaging process involves rectifying the input and integrating the result. A short time constant on the integrator will give an accurate average but will result in a good deal of ripple on the VCA control signal, while a long time constant gets rid of the ripple but will make the circuit slow to respond to amplitude changes (Fig. 2).

As rapid changes of gain in the VCA cause considerable distortion, compander circuits tend to err on the side of a slightly longer time constant. The resulting amplitude changes cause an effect often described as 'breathing'.

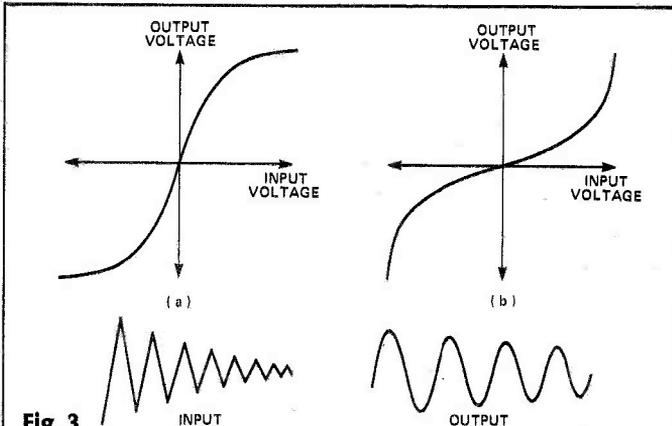


Fig. 3
 (a) 'S'-law transfer characteristic.
 (b) The characteristic needed to restore the original signal.
 The waveforms show a triangular wave of diminishing amplitude before and after processing by (a). Note that the output changes far less in amplitude than the input.

Instead of modifying the signal envelope, as is the case with compressors, another possibility is to modify the waveform itself. Imagine we have a circuit with a kind of 's-law' characteristic as in Fig. 3. Any input to the circuit would be amplified much more around the zero-crossing part than it would be at its peaks. An input of varying amplitude would still be compressed, but this time the compression would be achieved by altering the shape of the wave rather than shrinking it as a whole. The waveform would end up very distorted, but could be restored to its original glory by a circuit with the inverse characteristic.

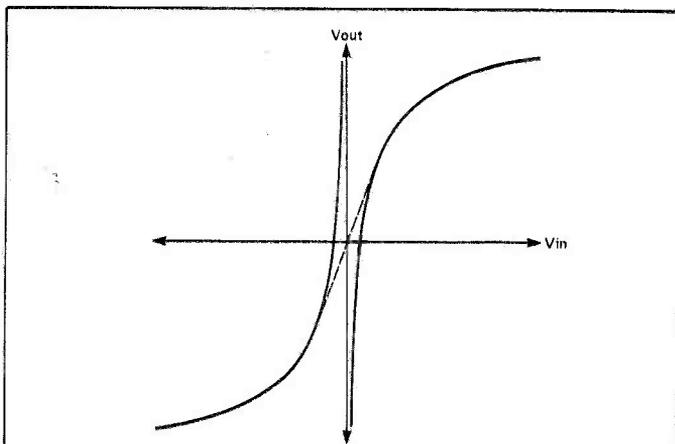


Fig. 4 Making an 'S'-law function from long curves. Note that if transistor junctions are used, the curves are offset along the V_{in} axis and will actually pass through the origin.

A circuit of this nature is not easy to construct as the inverse circuit must be a very precise match to the compressor. I have a feeling that something along these lines could be made by missing out the integrating capacitors on a compander IC, but I haven't really looked into it. If anyone would care to try, please write in and let me know how it turns out.

A circuit I have tried involves using the base-emitter junctions of a pair of transistors to simulate the curved sections (Fig. 4) with a bit of trickery to carry the function across the centre. The results were encouraging, but much more difficult to compensate for the temperature variations than I had anticipated. Log amplifiers exist in IC form (with temperature compensation!) but they only work in two quadrants: you get the right hand side of Fig. 4 or the left, but not both. Perhaps something could be done with two of them? If you have a hot soldering iron and time on your hands . . .

However, all this is short-circuited by the fact that a similar kind of compression can be performed by the ADC. Just tuck the previous ideas away in the back of your mind for a moment because I'd like to approach the idea of 'digital companding' from a slightly different angle.

Short but Sample

The obvious way to increase the dynamic range of the sampling process is to use a high resolution ADC. A 12-bit ADC will give 4096 quantisation levels and a S/N of 72dB at best; for a 16-bit ADC we have over 65,000 levels and a maximum S/N ratio of 96dB. If we're using 8-bit words to store the data we can't use a 12 or 16-bit ADC (assuming we could afford to buy one in the first place in the case of the 16-bit devices) and using two words for each sample would halve our sample time. Bearing in mind that we want to avoid the degraded S/N for low signal levels, suppose we do this instead:

Around the 0V level, we pretend we've got a 12-bit ADC and space the quantisation levels accordingly so that they are 0.025% of full scale apart. After the first eight levels, 0.05% of full scale apart. The next eight levels will be 0.1% FS apart, the next eight 0.2% FS, and so on. The resolution around 0V is now excellent. The penalty is that in the final section which takes care of the wave peaks the resolution is only equivalent to a 5-bit ADC. There are two very strong points in favour of this as opposed to linear conversion. First of all, audio signals generally have an amplitude spectrum concentrated in small signals rather than large ones and will often have crest factors (the ratio of peak to RMS amplitude) of five or more. Secondly, the human ear is much more sensitive to any inaccuracies of the wave around the zero-crossing point than it is to slight variations in the peaks. At the end of the day, the justification for this type of conversion is that it sounds so much better!

In IC form, there are two versions of the companding DAC. The first follows a law known as $\mu 255$, developed by Bell Laboratories. The idealised law is:

$$Y = 0.18 \ln(1 + \mu X)$$

where μ has the value 255 for an 8-bit converter. This law is approximated by seven 'chords' which double in step size as described above. The rival system, the A-law, approximates the function:

$$Y + 0.18 (1 + \ln AX) \text{ for } 1/A < X < 1$$

$$Y + 0.18 AX \text{ for } 0 < X < 1/A$$

Where A has the value 87.6 for an 8-bit converter.

In both these cases, X is the analogue signal level as a fraction of full-scale. The formulae give the magnitude of the signal levels; a sign bit in the DAC is used to say whether they are above or below zero.

The main difference between the two laws is that the approximation of the A-law results in the first two 'chords' having the same step size, so the maximum resolution is only equivalent to an 11-bit linear DAC.

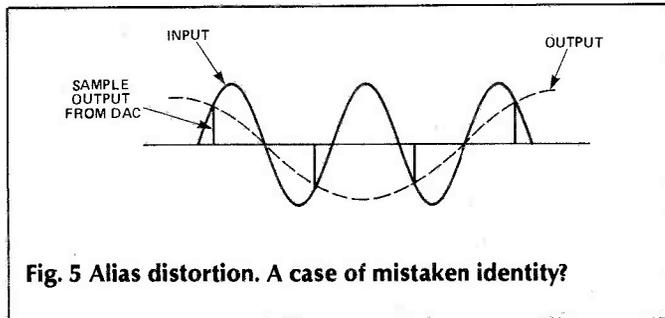


Fig. 5 Alias distortion. A case of mistaken identity?

To tie in with the earlier idea of modifying the waveform with an 's-law' analogue circuit, just imagine that the sample in memory from the variable-step ADC was fed out through an ordinary DAC. With allowances for the chord approximation, the waveform would look just as if it had been processed by the analogue 's-law' circuit!

The advantage of companding during A-D and D-A conversion is that the technology required is just the same as that needed to produce a 12-bit DAC, which is not very difficult these days. To get the same degree of precision in a non-linear analogue circuit would be virtually impossible.

Sampling Rates

A well known rule of thumb is the need to sample at more than twice the rate of the highest frequency component of any waveform that is to be reproduced — the famous Nyquist theorem. If you disobey the rule, you let yourself in for a dose of the dreaded alias distortion.

Alias distortion is often presented as a kind of 'mistaken identity' of the sampled waveform (Fig. 5).

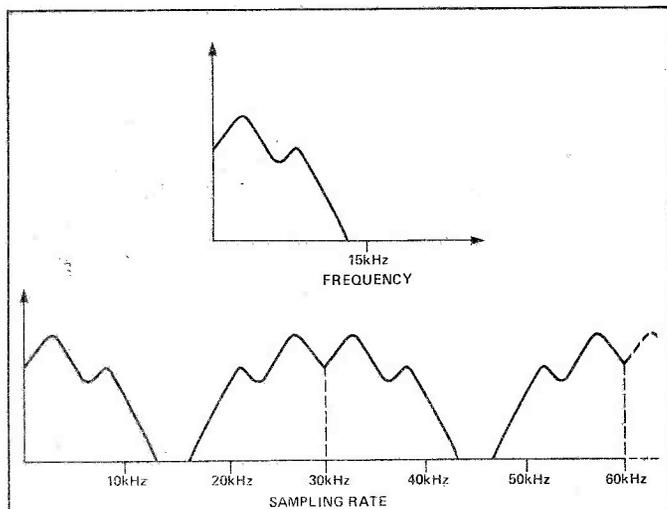


Fig. 6 The frequency spectrum of the input signal (a) and the output from the DAC, (b), showing the additional frequency components generated by sampling.

This is OK for explaining how it might occur, but not much good for deciding what to do about it. A more enlightening view of the situation is to consider the frequency spectrum of the sampled wave, or the output from the DAC.

Two points before we start. First of all, the following discussion assumes that the output from the DAC represents the exact level of the input at the time of sampling. Any practical inaccuracies we have already put into the 'noise' pigeon-hole, and there they can stay for the time being. Secondly, it doesn't matter a damn whether we use linear or log conversion. What we are getting out of the DAC is a stream of voltage levels representing the instantaneous value of the sampled wave, no matter what black magic was used to stuff it into the memory in between.

We'll start off with an analogue input which has a frequency spectrum as shown in Fig. 6a. After sampling at 30kHz, the output from the DAC will have a frequency spectrum as shown in Fig. 6b. No doubt you've seen similar diagrams before. To get a feel for why it should be so, take a look at Fig. 7.

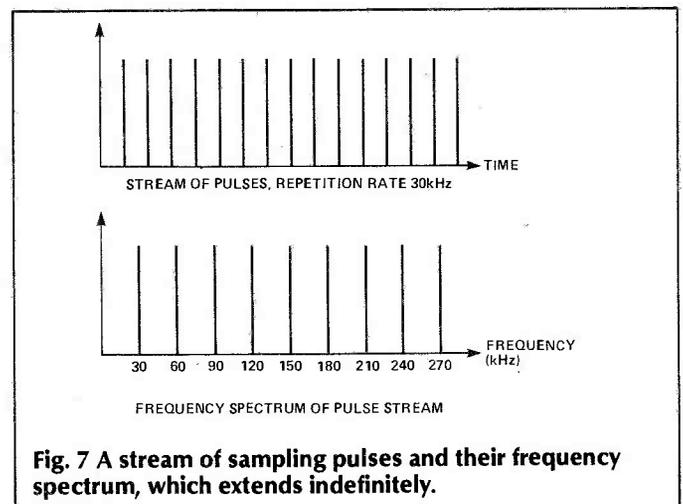


Fig. 7 A stream of sampling pulses and their frequency spectrum, which extends indefinitely.

First of all we have a series of sampling pulses of zero duration. Not very practical? OK, I admit it, it's a mathematical fudge. But bear with me for a moment. It so happens that a string of pulses like that has a frequency spectrum consisting of evenly-spaced sine waves all with the same amplitude. Now, if I took just one of these sine waves and amplitude modulated it, remembering your AM theory, you'd expect to see sidebands on either side, right? And varying the amplitude of the sample pulses in accordance with the amplitude of the input is pretty much like amplitude modulation. So Fig. 6b shows all the 'sidebands'. The argument has as many holes as a string vest, but the conclusions are OK.

So what happens when the DAC output consists of real pulses that have a finite width? Well, if I can lean on the previous rickety argument a little more, the unmodulated output spectrum from the DAC will now be a series of sine waves which diminish in amplitude as their frequency increases. So what we'd expect to see is the amplitude of the higher frequency 'sidebands' of the modulated spectrum decreasing in amplitude, too, as their frequency increases. This is exactly what happens.

The original spectrum of Fig. 6a is all we want to end up with, so it won't cause us any great sadness that the upper frequencies diminish in amplitude. We're going to filter them out anyway. What would

cause us concern would be any alteration to the amplitude of the original spectrum, the part we want to keep.

At this point the intuitive argument collapses under the strain and we must take account of the results of a full mathematical analysis. Yes, the amplitude of frequency components of the part of the spectrum we want to keep will diminish. The wider the output pulses from the DAC, the more significant this effect becomes. With a stair-step output from the DAC, which retains the previous output until another digital code comes along, the frequency response will gently roll off until, at half the sampling frequency, the output will be down by about 4dB. No need to panic, but it should be taken into account. Remember that this has got nothing to do with any filtering or whatever, we're just looking at the raw output from the DAC.

It seems sensible that if we're looking for perfection, the best thing to do would be to return the DAC output to zero in between sample outputs. Sad to say, this can cause more problems than it solves.

We've been looking at nice clean sterilized theory up to now. Unwanted odds and ends creep in, but they stay in their proper place and behave themselves and we know just what to do about them. When you actually come to build a circuit in real life, the results are much less predictable. For instance, DACs don't instantly jump to a new output level when a digital code is applied, they have a certain settling time and what happens at the output during that settling time is anybody's guess. Additional frequency components will be generated and they won't be in predictable places.

The answer is to make them small in comparison with the spectrum we want, which in essence means making the output hold time long in comparison with the settling time. In general, it is often better to put up with a predictable fall in performance that can be compensated for rather than to try correcting it at the expense of introducing factors that can't be removed.

To return to Fig. 6, although there is no frequency component at the input which is above half the sampling frequency, there are already unwanted frequencies from the DAC which occur within the audio range. If we could block off all frequencies above 10kHz at the input, the unwanted frequency spectrum would at least be above 10kHz. This is not very sensible. The unwanted frequencies could burn out tweeters or beat with the bias oscillator of a tape recorder and produce audible products, for instance. There is the more obvious problem of losing bandwidth for no particular reason. Output filtering is the answer here.

Figure 8 shows the situation when frequencies above half the sampling frequency are present at the input. The overlap of wanted and unwanted frequencies is our alias distortion. The practical result is a kind of harshness or coarseness in the reproduced sound. These frequencies could also be eliminated by filtering at the output, at the expense of a good deal of usable bandwidth. Far better to have a filter at the input to prevent frequencies above half the sample rate entering the system in the first place.

The result of all this is that although we could, at a pinch, get away with filters just at the input or output, the maximum system bandwidth and best possible sound will be achieved by filtering both. Obvious, you think? Well, maybe, but a design for a fairly expensive self-contained unit was recently published with no

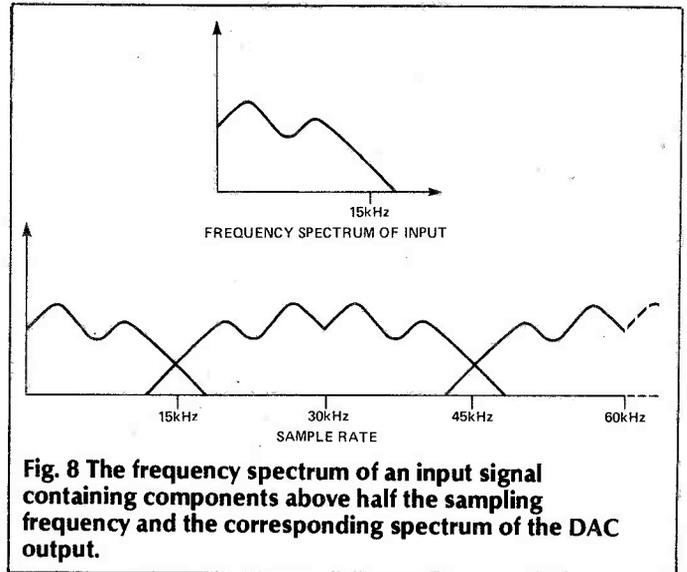


Fig. 8 The frequency spectrum of an input signal containing components above half the sampling frequency and the corresponding spectrum of the DAC output.

input filtering whatsoever and a pathetic and totally inadequate 2-pole filter on the output. The author claims it can 'also be used as a treble control'. Surprisingly often, designers of commercial equipment, who really ought to know better, try to get away with inadequate filtering or even no filters at all.

So, how much practical difference does it make? The answer is that it depends very much on the sampling frequency. At sample rates of 15 to 20 kHz, which are often used in 'sample stretch' or 'double time' commercial devices, the distortion will be very noticeable indeed. We're talking about the potential sound quality of good AM radio as opposed to the achieved quality of a noisy telephone line. At higher sampling frequencies the distortion is still present, however, and is quite obvious when the sampled sound is compared with the original. To extend the previous analogy, you would be settling for AM radio quality without adequate filtering when the system is capable of FM quality sound. The results with a fairly high sample rate can, in some circumstances, sound quite acceptable, but will have as much in common with the original sound as a banana milk shake has in common with bananas.

Pre-emphasis

Yet another way to improve sound quality is to apply pre-emphasis to the input signal. The theory is much the same as that employed in Dolby systems and the like. The higher frequencies of the passband are selectively amplified before A-D conversion, then attenuated after D-A conversion, taking a portion of the noise spectrum with them.

Circuits for this purpose are frequently tacked on to samplers almost as an afterthought. Often the degree of pre-emphasis is limited because the designer has realised that it will mess up the anti-alias filtering. The designer has gone to a lot of trouble to give a nice sharp cut-off to higher frequencies, and here's a circuit amplifying them all up again! There's no doubt that pre-emphasis can be effective, but it must be a part of the overall frequency tailoring, not an add-on.

These are a few of the considerations that led to the design of the ETI sampler. Will it be a revolution in sound sampling, or just another variation on the theme? You'll have to wait and see. 'What do you think, Alf?' 'Dunno.' Well, that about sums it up. **ETI**

ETI SORCERER STRING SYNTHESIZER

Having unravelled the circuit diagrams, Graeme Durant wraps up the project and ties up the loose ends.

Construction of Sorcerer should prove to be quite straightforward, especially if the suggested PCB layouts are used.

Each board requires a number of wire links to be fitted, so these should be tackled first. If you are playing safe and using IC sockets, fit these next. Sockets are recommended for the MOS devices, especially the expensive delay-line chips. Now you can solder in the passive components, remembering that all 213 diodes must go in the correct way round! Note also that some resistors must be mounted vertically. Finally, insert the presets and the panel mounting potentiometers. Since the latter are PC mounting, ensure that they are all straight, so that they will go into the front panel cutouts first time.

After scrubbing off all that nasty flux on the backs of the PCBs, with meths, it is time to fit the boards into the main case, which has by now been drilled and punched to accept them. Note that the VCO board and the envelope board are fixed in only by their front panel potentiometers; they require no further fixing, unlike the other PCBs, which must be bolted into the case. It is recommended that the boards are fitted with veropins or similar terminals, prior to encasing them, to ease the job of interwiring *in situ*.

All power connections should be made from each board to a common point at the power supply board. If power connections are strung from board to board, all manner of nasty noise will be the end result. The power supply itself should be connected

to mains via a suitable panel on/off switch and a 500mA fuse. Be careful to insulate all points at mains voltages with sleeving. If a metal case is being used, a connection should be made between it and earth, using a bolt and solder tag.

Interconnections must be made between the two chorus boards using tinned copper wire (Fig. 10). Connections to the power supply should be made as shown, using Veropins, but with the interconnection wires still soldered underneath. The chorus boards are stacked and bolted, but

plastic spacers must be used to avoid accidental short circuits occurring across the closely spaced tracks on the boards. As a last resort (and I mean a last resort!) use empty plastic biro tubes.

Connections to the front panel switches should be made from the various boards (Fig. 11). The front panel 'Attack LED' is wired between 0V (cathode) and the attack LED pin on the envelope board. Note that none of the connections in Sorcerer are critical and they can all be safely made using ordinary hook up wire.

The keyboard is built on two

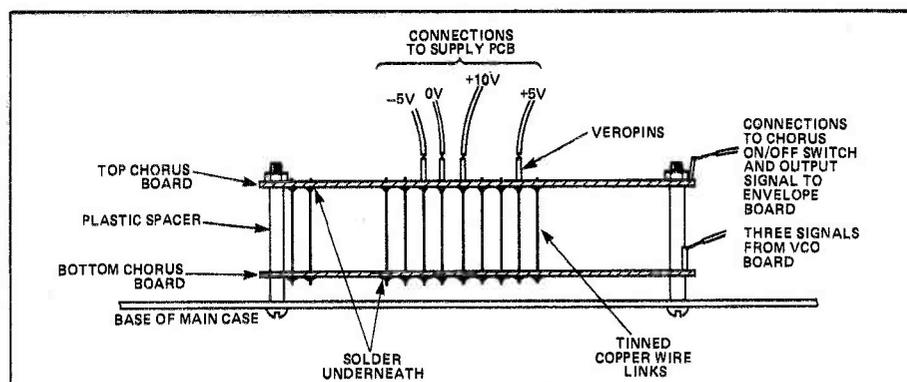


Fig. 10 Interconnecting the two chorus boards.

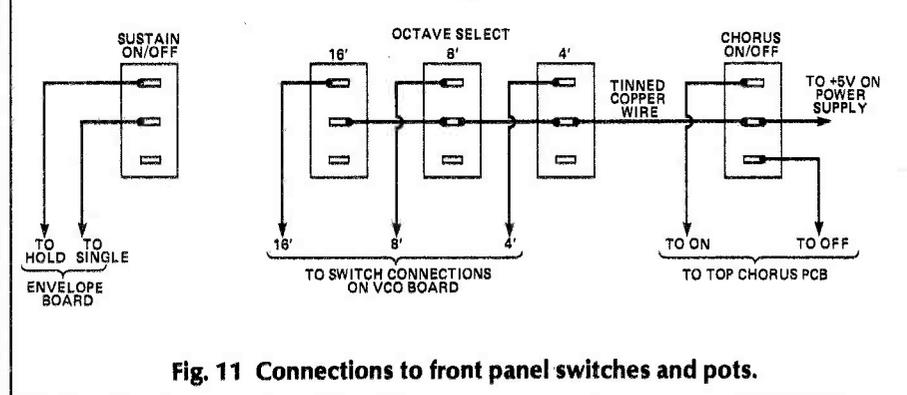


Fig. 11 Connections to front panel switches and pots.

boards. The keyboard interface PCB is the small one, and when complete is stacked about 12mm above the copper side of the main keyboard PCB using spacers and bolts with its copper side up, too. Connections are made to the large board using eleven vertical tinned copper wire links, as on the chorus boards. If the keyboard is to be housed separately to the main electronics, five connections (+5V, 0V, gate, trigger and key voltage) must be made between it and the main unit. In the prototype a five pin DIN lead was used with corresponding DIN sockets, but any suitable method could be employed.

The actual insertion of components is similar to the rest of the boards apart from resistors R60 to R96 and diodes D3 to D39 on the main board. These are soldered together in pairs, in series before insertion into the PCB. (Fig. 12). This was necessary for space reasons.

The keyboard case for the prototype was made from wood and required only simple carpentry skills. The reverse side of the actual keyboard surface of the main PCB was glued, using a contact adhesive, to a strip of chipboard some 12mm thick, the full depth of the keys. From this base, simple wooden ends were glued on, to form the case sides; then a thin strip to form a front edge, to cover up the chipboard, and a rear wider strip to form a back panel, were added. Another thin strip formed the back edge of the keys themselves, then two painted aluminium plates were used as a top and bottom panel. These were fixed using wood screws to allow later removal and access to the circuits inside. Finally, four rubber feet were added to make a stable construction. So, the case is actually built around the main PCB, and should be done carefully after inserting the components.

Modifications

The more serious musician aiming to use the Sorcerer string synthesiser will no doubt prefer to use a real keyboard with moving keys. This will enable the musician to play faster and more reliably, as well as giving a familiar feel.

Such a modification would be quite straightforward. IC9 to IC18 would no longer be required. Instead, a three octave keyboard unit, fitted with single pole 'make'

contacts, would be used. One connection to each switch should be commoned to all the other similar ones, and connected to 0V. Each of the other connections to each switch should be soldered to the appropriate key on the solid-state keyboard PCB. Then, to bypass the spaces left by IC9 to IC18, wire links should be inserted, connecting the tracks which originally went to the op-amp non-inverting inputs, to the tracks which went to their outputs. The result is that each row in the diode matrix can be effectively grounded by pressing a key, thus setting up the keycodes as before. Resistors R20 to R56 pull each row up to five volts when that key is unpressed. These resistors could be reduced in value to 100K, for less susceptibility to noise and faster matrix switching.

The rest of the keyboard circuitry could remain as before, with perhaps a couple of component value changes. R97 to R112 and C7 to C14 can stay, to debounce the mechanical contacts. IC19a and IC19b detect the presence of more than one key being pressed, and having altered the type of keyboard switching, the sensitivity of this detection circuit must be altered to suit. Simply alter the value of R58 until the output of IC19b goes low for two or more keys pressed, but high otherwise — this could be achieved by fitting a 220k potentiometer. The setting could be measured using a

multimeter on the ohms range, and a fixed resistor then put in its place.

Finally, the value of R122 could be experimentally reduced, to allow faster keyboard response. Now that the square pulse signals of the touch detectors have been removed, the reaction delay can be safely reduced whilst still maintaining a reliable response to keys pressed.

Setting Up And Use

Sorcerer contains seven preset potentiometers, so requires a little setting up. Although no test gear is essential, access to an oscilloscope is useful. After having built up all the PCBs, checked for faults and wired up everything except the connections to the power supply outputs, it is time to plug the PSU in to the mains. Check that the PSU outputs are at the correct voltages, then make the final connections between each PCB and the power supply.

Connect the keyboard unit to the main box of tricks and a pair of headphones or an amplifier/speaker set at low volume to the output. Ensure all seven presets are set to their midway positions. Select the middle octave range on the switches, turn off the chorus effect and apply the power. A sound of some kind may be audible, if it is, do not worry. Press a key. The Attack LED should light, and the sound should get louder

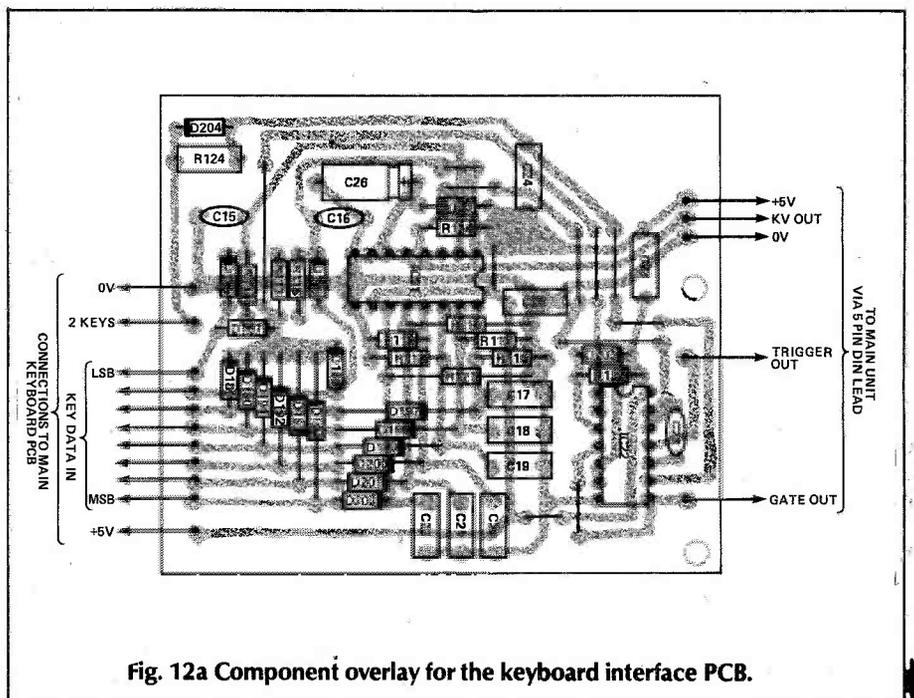


Fig. 12a Component overlay for the keyboard interface PCB.

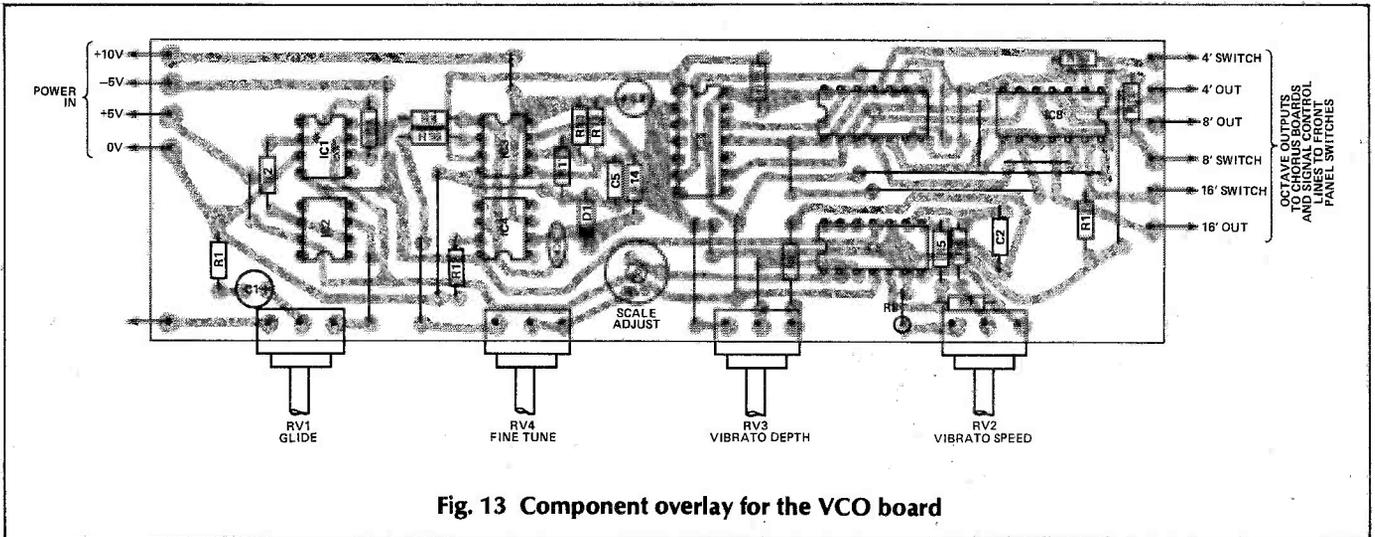


Fig. 13 Component overlay for the VCO board

with an envelope according to the attack and release control settings. If not, turn off. Check your wiring. Check to see if a signal is being produced by the VCO. Check the keyboard output voltage and timing pulses.


If all is OK, try the other octave switches. Try the sustain on/off switch, and different setting of the attack and release controls. Check

the vibrato controls work, and the glide and tune functions. Finally, see that the chorus mode has at least some effect (but do not worry about the din it is probably making!).

Once you are convinced that all the functions have some effect, it is time to set the presets. Switch off the chorus effect, and set the attack and release controls to

minimum. Turn up the amplifier volume control until you can hear the signal breaking through the envelope shaper, then adjust RV8 on the envelope board until the minimum signal is heard.

Switch out all the octave ranges, then, with the sustain set to off, press a key. A sharp click will probably be heard. Turn RV9 also on the envelope board, until

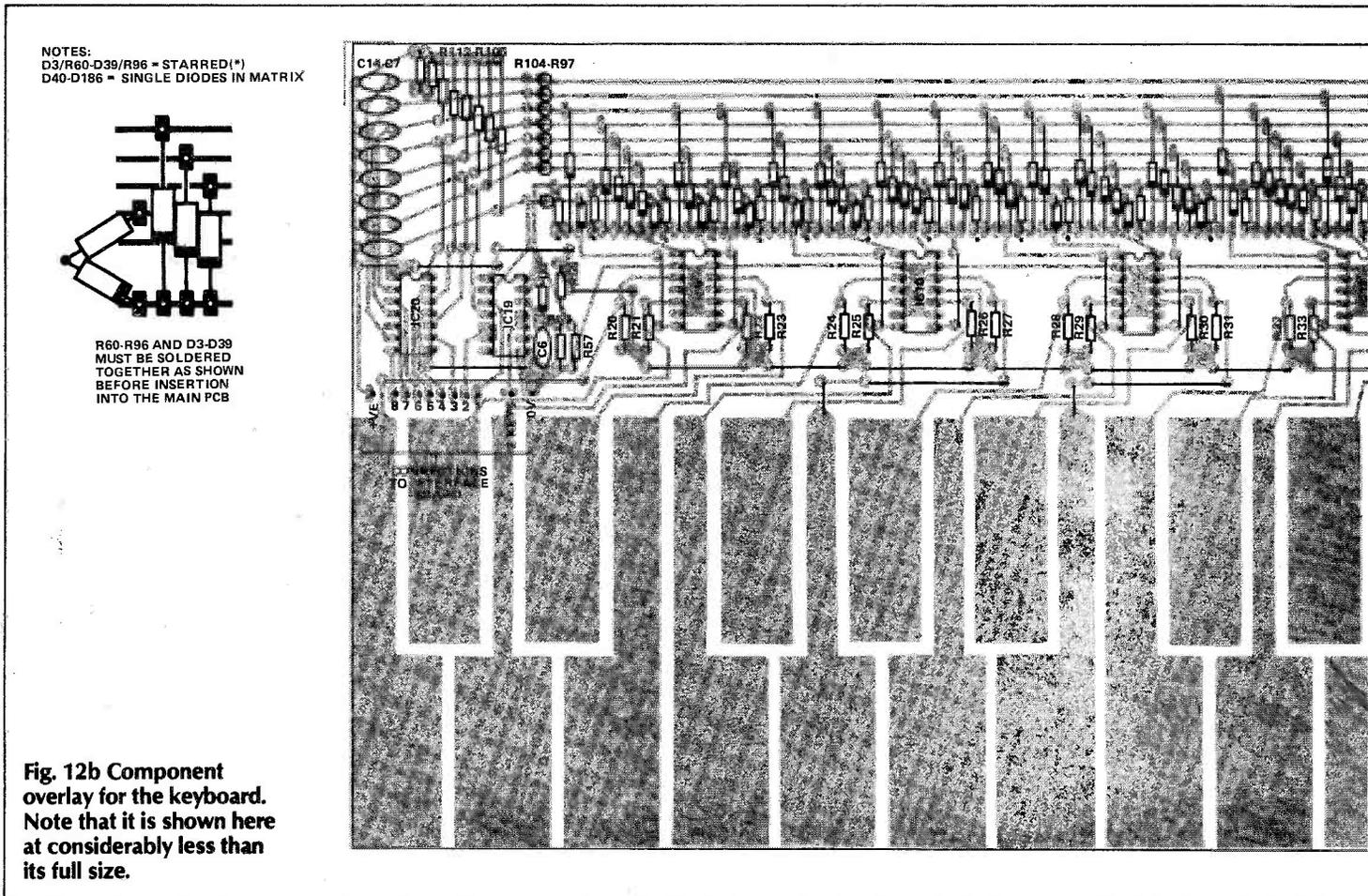

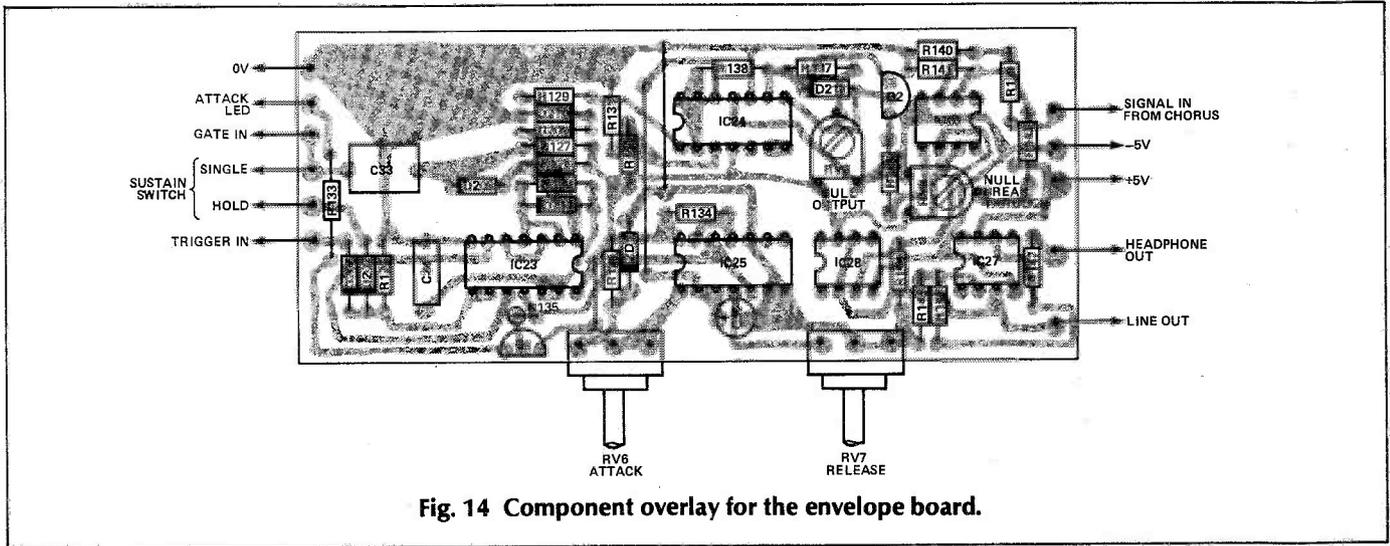


Fig. 14 Component overlay for the envelope board.


pressing a key produces the minimum effect. The envelope shaper is now set up.

Now, reduce the amplifier volume to a reasonable level, and set the attack and release controls about midway. Switch in all the octave ranges. Select the chorus mode, and hold down a note on the keyboard. Turning RV10 through the hole in the top chorus

board should, at one extreme, fuzz the sound and, at the other, stop the signal. RV10 sets the operating point of the delay-line chips and should be in the middle of its undistorted range of travel. Finally, we set up RV11, 12, and 13 on the top chorus board. If an oscilloscope is unavailable, set these midway — they are not too critical. Their function is to cancel

out some of the high frequency clock signals imprinted onto the outputs of the delay line devices. If an oscilloscope is to hand, connect its input to the slider of RV11, and adjust until the minimum high frequency noise appears on the signal. This may be easier to see with all the octave ranges switched off. Repeat for RV12 and RV13. This completes

* D3/R60-D39/R96

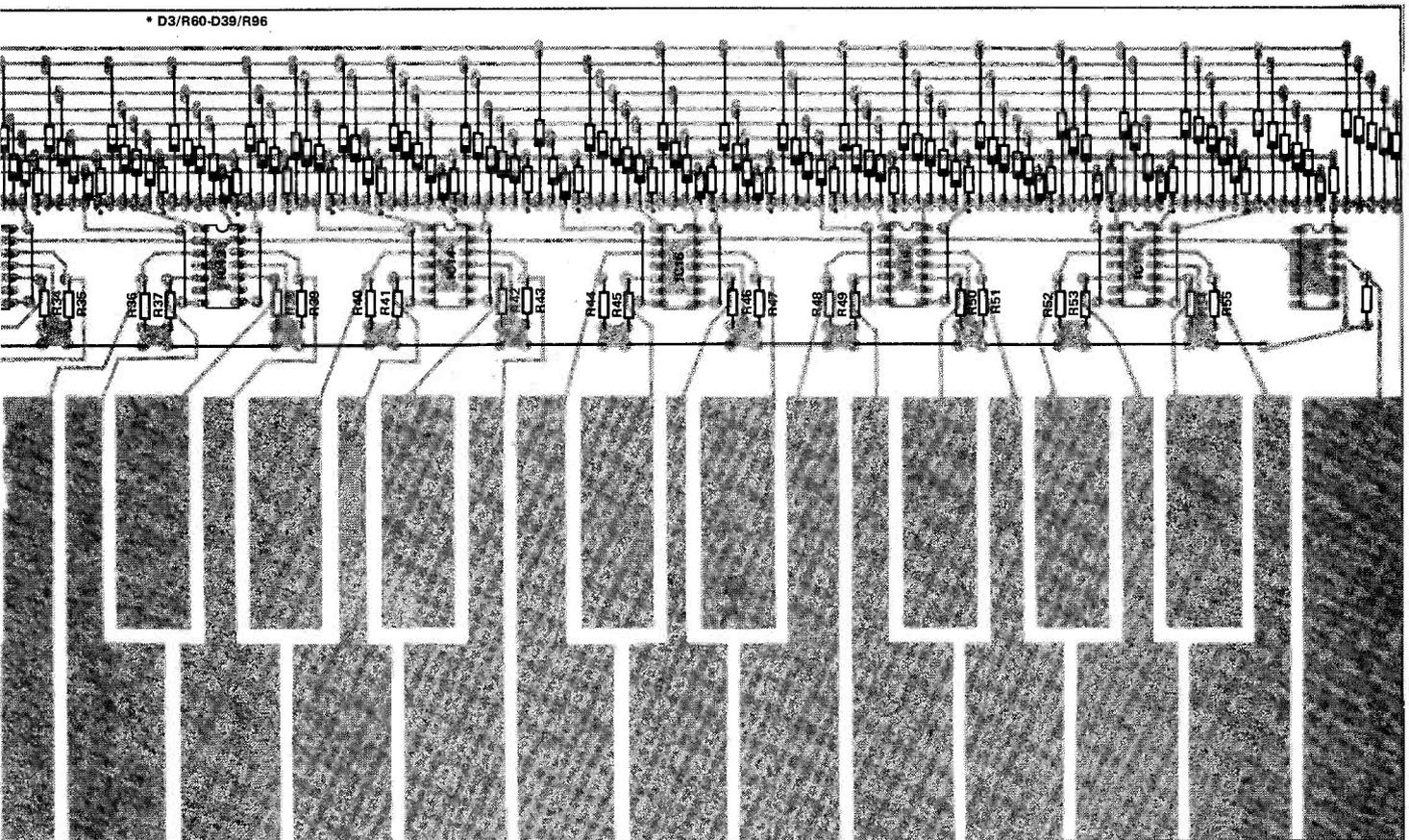

the setting up of the chorus board.

The last preset to deal with is RV5, on the VCO board. This simply acts as a coarse tuning control. Set the front panel tune control to its central position, then turn RV5 until the instrument is in tune with a known reference.

The line output is about one volt peak-to-peak and so should drive most amplifiers, but if it is too high, fit an attenuator. The touch keyboard should work in most environments, provided there is enough mains hum around the place. If problems are encountered, try planting both feet firmly on the floor (I am serious, it does work!). If the problems persist, try removing the 10Mohm input resistors on the keyboard, to increase its sensitivity. Also check earth continuity and connection to the 0V line.

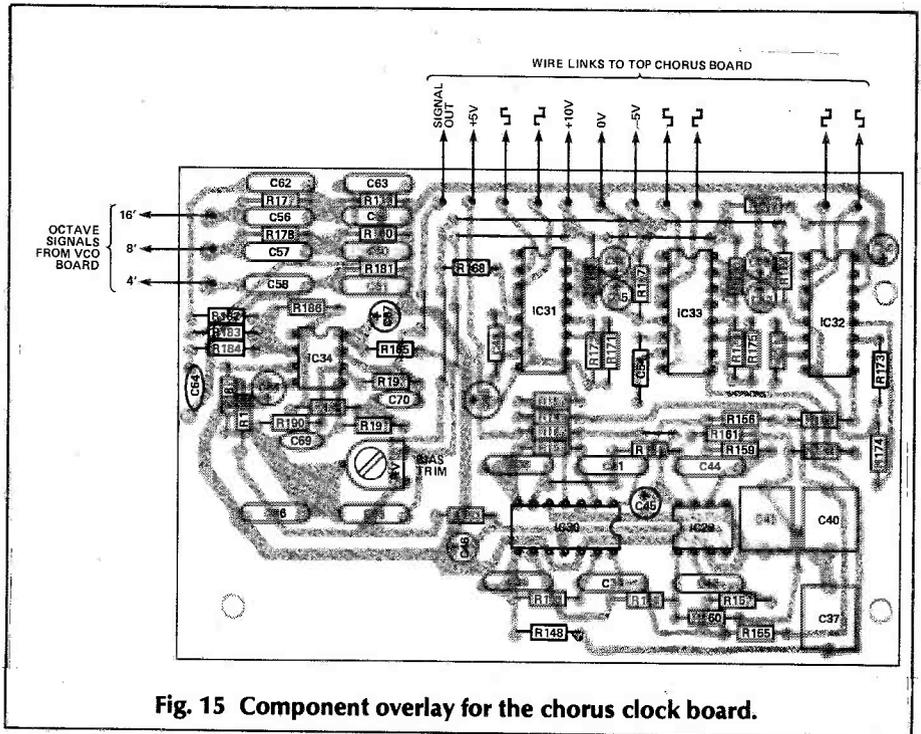


Fig. 15 Component overlay for the chorus clock board.

BUYLINES

Most of the parts used in Sorcerer can be found in any supplier's catalogue, but there are a few more-difficult-to-find parts required. The MN 3010 delay line chips are available from Digisound Limited, 14/16, Queen Street, Blackpool, Lancs FY1 1PQ at a cost of £18.98 for the three all inclusive. The MN3010 delay line chips are available from Maplin, as is the ZN428 keyboard D-to-A converter. The particular sub-miniature single ended electrolytic capacitors used on the chorus PCBs, and the PC mounting potentiometers, were also from Maplin. The case used in the prototype to house the main

electronics is one of the Modular 5 range of enclosures available from West Hyde Developments Limited, 9/10, Park Street Industrial Estate, Aylesbury, Bucks, HP20 1ET. The model used was the MD5 AFL and costs £17.33 including postage, packing and VAT. The encapsulated transformer used in the prototype — Clairtronic type 9641 — can be obtained from Verospeed, Stansted Road, Boyatt Wood, Eastleigh, Hants SO5 42Y (tel: 0703 644555). The price is £3.89 and the order code, 89-35985D. The PCBs are available from the ETI PCB Service, but see the note in News Digest.

PARTS LIST VCO SECTION

RESISTORS	(all 1/4W, 5% unless otherwise stated)
R1,8	1k0
R2,3,4,7,12	100k
R5	47k
R6,9	390k
R10,11,15,17,18,19	10k
R13,16	6k8 1% metal film
R14	2k2
Rv1	100k log. PC mounting
RV2	10k lin. PC mounting
RV3	47k lin. PC mounting
RV4	2k2 lin. PC mounting
RV5	4k7 Cermet preset

CAPACITORS

C1	3u3 16V tantalum
C2	150n polycarbonate
C3	10u 16V tantalum
C4	4n7 mylar
C5	2n2 polycarbonate

SEMICONDUCTORS

IC1,4	LF351
IC2	741
IC3	LM331 or RC4151
IC5	LM324
IC6	4024
IC7	4011
IC8	4081
D1	1N4001

MISCELLANEOUS

PCB; solid tinned copper wire; control knobs; veropins.

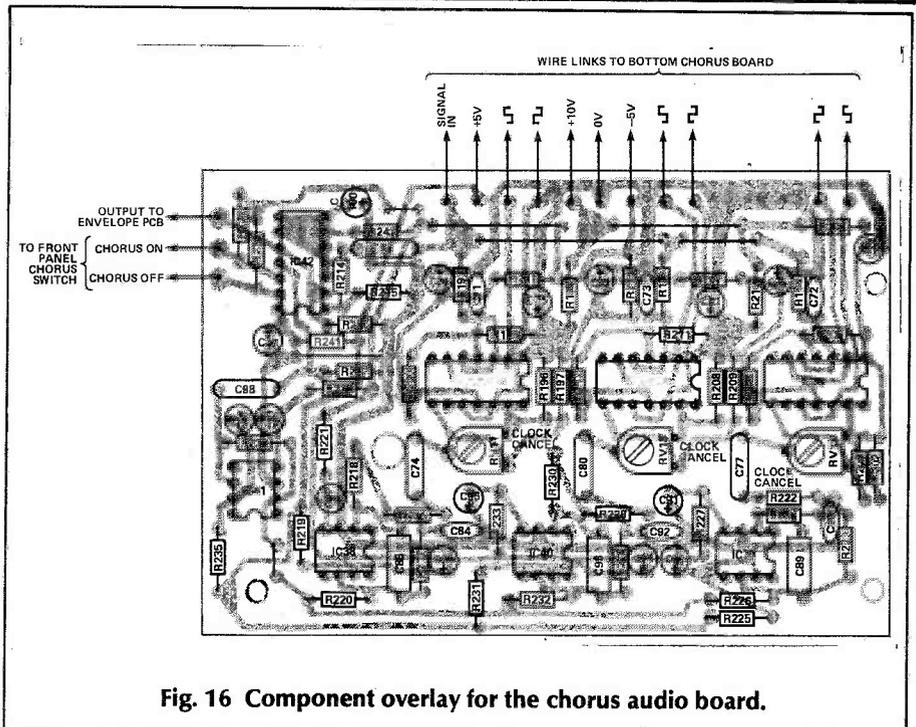


Fig. 16 Component overlay for the chorus audio board.

PARTS LIST

KEYBOARD

RESISTORS (all 1/4W 5%)

R20 to 56	10M
R57,123	470k
R58,60 to 104,113	100k
R59	330k
R105 to 112	820k
R114 to 121	2M2
R122	390k
R124	10k
R125	390R

CAPACITORS

C6,23,24	220n polycarbonate
C7 to 22,25	100n polycarbonate
C26	1u0 axlal electrolytic
C27	1n0 polycarbonate

SEMICONDUCTORS

IC9-18	LM324
IC19,20	40106
IC21	ZN428
IC22	4093
D2 to 204	1N4148

MISCELLANEOUS

PCBs; solid tinned copper wire; IC sockets; spacers; bolts; five way connector for keyboard connection to main unit.

ENVELOPE SHAPER

RESISTORS (all 1/4W, 5%)

R126,128,130,134,137	100k
R127,129,131,132,135,143,144	10k
R133	150R
R136,140,141	470R
R138	4k7
R139,145	47k
R142	1M
R146	82k
R147	100R
RV6	1M0 log. PC mounting
RV7	1M0 log. PC mounting
RV8	10k miniature horizontal preset
RV9	100k miniature horizontal preset

CAPACITORS

C33	33n polycarbonate
C34	220n polycarbonate
C35	2u2 16V tantalum

SEMICONDUCTORS

IC23	4093
IC24	LM324
IC25	4066
IC26	CA3080
IC27,28	741
Q1	BC557
Q2	BC108
ZD1	2V7 400mW zener diode
D206-212	1N4148
LED1	to choice

MISCELLANEOUS

PCB; solid tinned copper wire; control knob; veropins.

CHORUS CIRCUITS

RESISTORS (all 1/4W, 5%)

R148,155,160	680k
R149,156,161	820k
R150,151,157	1M5
R152,158,164,171,173,175,182,183,184,196,197,202,203,208,209,215,237,238,239,240	100k
R153,154,159	150k
R162,163,185,188,198,201,204,207,210,213,241,242	100R
R165,166,167,168,169,170,177,178,187,200,206,212,219,221,225,227,231,233,235,236	1k0
R172,174,176	2M2
R179,180,181	2k2
R186,192,216,217,222,223,228,229	22k
R189,191,193,194,195	10k
R190	39k
R199,205,211	15k
R214,234	47k
R218,224,230	27k
R220,226,232	120k
RV10	22k horizontal miniature preset
RV11,12,13	10k horizontal miniature preset

CAPACITORS

C36,38,39,41,42,44,56,57,58,59,65,66,83,98	100n polyester
--	----------------

C37,40,43 C45,46

C47,49,50,52,53,55,67,68,75,76,78,79,81,82,86,87,90,91,94,95,96,97,99,100	1u polycarbonate
C48,51,54	100p polystyrene
C60,61,74,7,80	47n polyester
C62	22n polyester
C63	10n polyester
C64	4n7 polycarbonate
C69,70	1n5 polycarbonate
C71,72,73,84,88,92	1n0 polycarbonate
C85,89,93	330p polystyrene

SEMICONDUCTORS

IC29,34	LM1458
IC30	LM324
IC31,32,33	4046
IC35,36,37	MN3010
IC38,39,40,41	741
IC42	4066

MISCELLANEOUS

PCBs; solid tinned copper wire; IC sockets; plastic spacers; veropins.

PSU CIRCUIT

CAPACITORS

C28,29	1000u 16V axial electrolytic
C30,31,32	10n mylar

SEMICONDUCTORS

BR1	W005 or similar 1A 50V bridge rectifier
IC43	7805
IC44	79L05
IC45	78L05
D205	1N4148

MISCELLANEOUS

T1 9V-0-9V, 8VA PC mounting transformer.
PCB; solid tinned copper wire; mains on/off switch; fuseholder and 500mA fuse; case; cable and connectors to go between keyboard and main unit; five single pole changeover switches (chorus, sustain, three octave select); hook up wire; mains lead; nuts, bolts, etc.

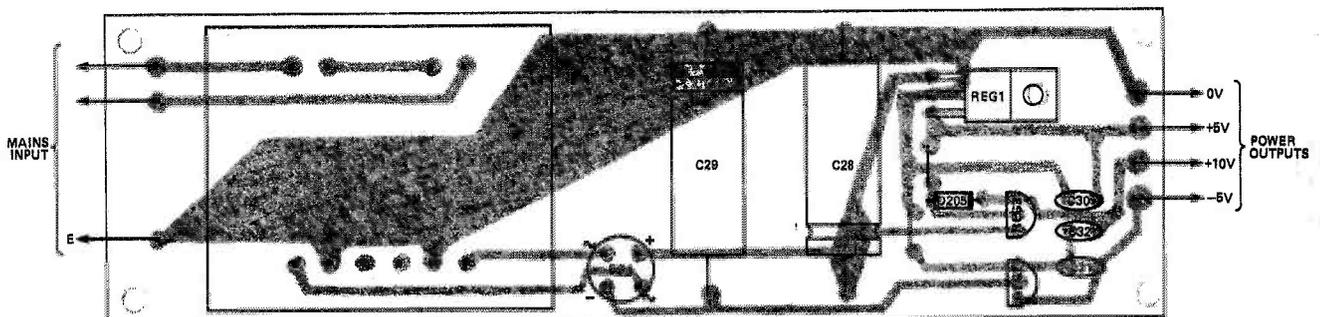


Fig. 17 Component overlay for the PSU.

MODULAR TEST EQUIPMENT

Mike Meakin considers the curious case of the expensive electronics project and suggests a solution.

A look at the average home constructor's workbench will usually reveal a motley collection of test equipment, built as necessity dictated and often in the obligatory biscuit tin with pencilled calibrations! Low cost test equipment is available but often contains little more than an industry standard IC used in the manufacturers' application circuit, and the cost of acquiring a complete system can be daunting.

But where does the cost come from? Have you noticed when budgeting for new projects that the electronics cost very little but the cases, front panels, knobs, hardware and power supplies all add up to a horrifying sum? If these costs could be dispensed with, more money could be spent on the electronics with a consequent improvement in the performance and hence the usefulness of the equipment.

The ETI Workstation has no case, no front panel, and no knobs. It consists of a series of printed circuit boards, each carrying one test instrument and designed to interconnect to form a complete system. The modules include a bench power supply, a pulse

generator, a universal counter-timer and a logic probe cum analogue indicator, and as well as providing voltages for equipment under test the power supply also drives the other modules. This removes the need for individual power supplies on each board and so helps keep costs down.

The constructor can choose to build any or all of the modules as required, if necessary assembling the system over a period of time as finances allow. In theory, the power supply has to be built before any of the other modules can be used, but there is no reason why an existing power supply could not be pressed into service, or even batteries as a temporary measure if one of the other modules is to be built first and the power supply later.

The boards all have a depth of 100mm (or just over 200mm in the case of the power supply) which allows a neat finished unit to be assembled using plastic guides. To avoid the need for external controls and panels, all of the potentiometers mount directly onto the PCB and are of the enclosed preset type with integral knob. PCB mounting switches

have been used throughout and the counter-timer display and power supply LEDs are also mounted directly onto the board. The only part of the system not mounted on a board is the mains transformer, which for safety reasons is housed in a small metal case with only the low voltage AC output fed to the power supply PCB.


Since the power supply is the logical starting point in this project, its design and construction will be dealt with in this first article. The other modules will form the subject of further articles in subsequent issues.

Power Supply Board

The power supply board is of conventional design and provides both fixed voltage supplies for the modules and variable supplies for bench use. Additionally a voltage reference of 10.00V and a constant current source of 10.00mA are available. The voltage reference can be used whilst prototyping circuits and even checking DVMs whilst the current source is most useful for checking LEDs and zeners and can of course be used for ramp generators during breadboarding.

A 4BA screw mounted on the board provides a 0V reference point and something handy to which crocodile clips can be attached. Connection to the fixed supplies for the modules is made by soldering to the underside of the board on the thick bus bars. This may not be particularly elegant but it is simple and above all cheap.

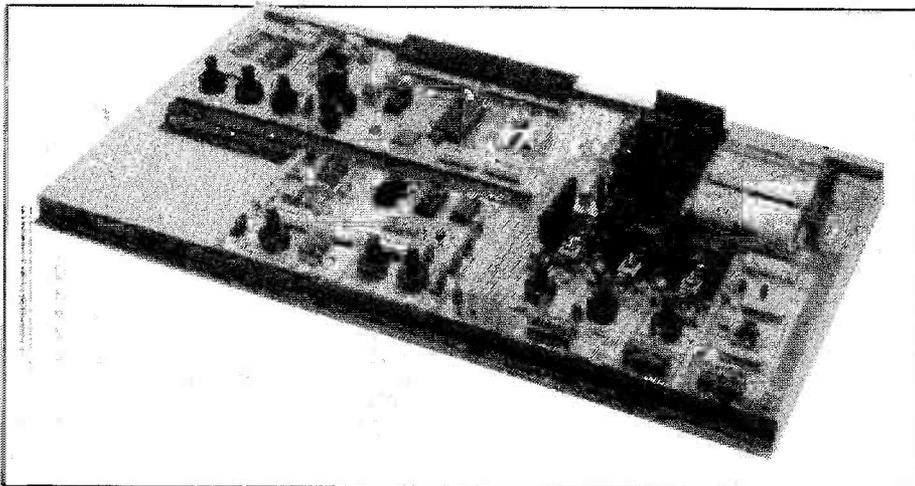The mains transformer is housed in a small metal case along with a fuse, mains on-off switch and neon indicator. The low voltage AC is taken via a DIN connector to the power supply PCB. Housing the mains transformer separately



HOW IT WORKS


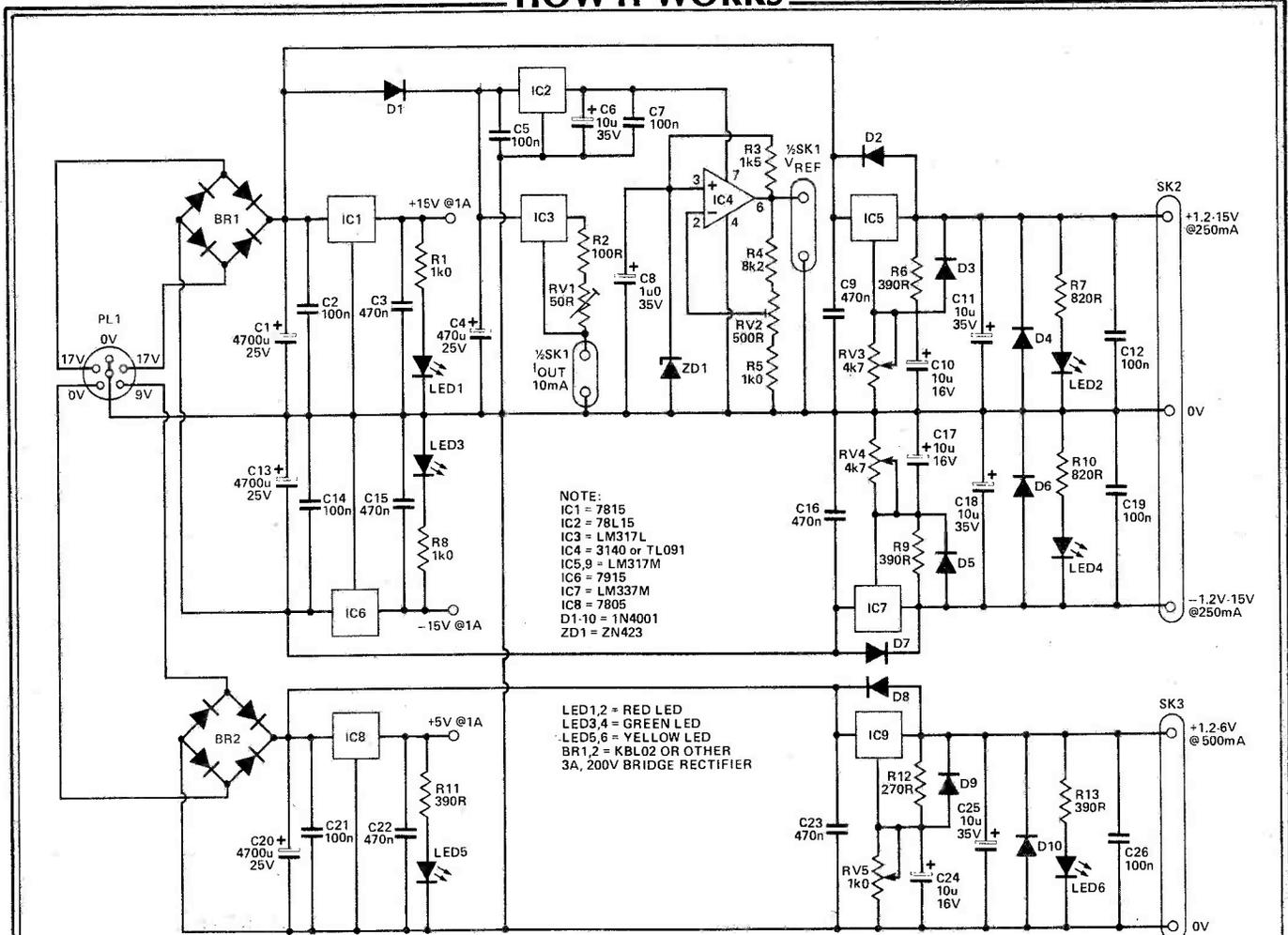


Fig. 1 (above) Circuit diagram of the power supply and Fig. 2 (below) the circuitry inside the transformer box.

The 9V AC supply from T1 is bridge rectified and fed to reservoir capacitor C20. A 5V regulator provides the fixed 5V supply at a maximum current of 1A for the modules and an LED indicates that the supply is present.

The unregulated supply is also fed to IC9, a variable voltage regulator which has additional components around it to provide protection against misuse. The supply can be set to voltages within the range 1.2V to 6.0V by variable resistor RV5. Capacitor C24 provides additional ripple rejection while capacitors C23, C25 and C36 stabilize the IC and improve transient load response. Diode D8 provides a discharge path for any large capacitors that may be hung on the output when the input supply voltage is removed. Diode D9 discharges C24 on switch off and D10 protects the regulator if reverse voltages are fed into its output. An LED again indicates when the supply is present. The input voltage and heatsinking allow this regulator to supply up to 500mA before thermal shutdown.

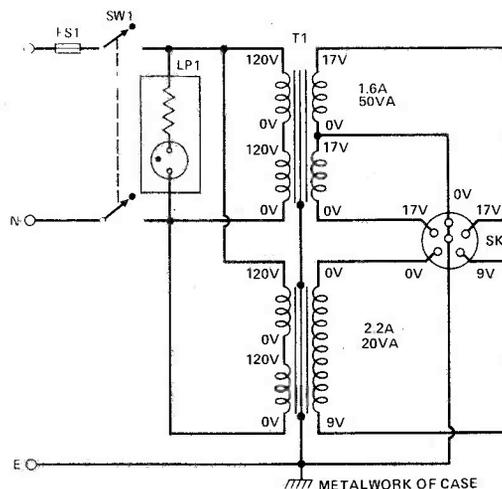The operation of both the fixed and variable plus and minus 15V supplies is similar to that of the 5V supplies described above. However the current drawn from the variable supplies should be limited to about 250mA (dependant on the output voltage) because of heat-sinking limitations.



T1 CAN BE EITHER A SINGLE TRANSFORMER WITH SEPARATE SECONDARY WINDINGS OR TWO TRANSFORMERS CONNECTED AS SHOWN

The unregulated positive supply is also fed via D1 to an additional smoothing capacitor C4 to provide supplies for the constant current source and the voltage reference. This arrangement gives some isolation of transient loads on the main 15V supply. A low power 15V regulator supplies IC4 which is configured in a classic buffered zener arrangement. The bandgap voltage is amplified to give an

adjustable 10.00V reference voltage at IC4 output. As both output and reference voltages are fixed a constant current flows through the reference voltage. The inputs of IC4 operate at 1.2V above 0V and a 3140 or TL091 op-amp must be used in this position. A 317L regulator is used for the constant current source and is set to 10.00mA under short circuit conditions by RV1.


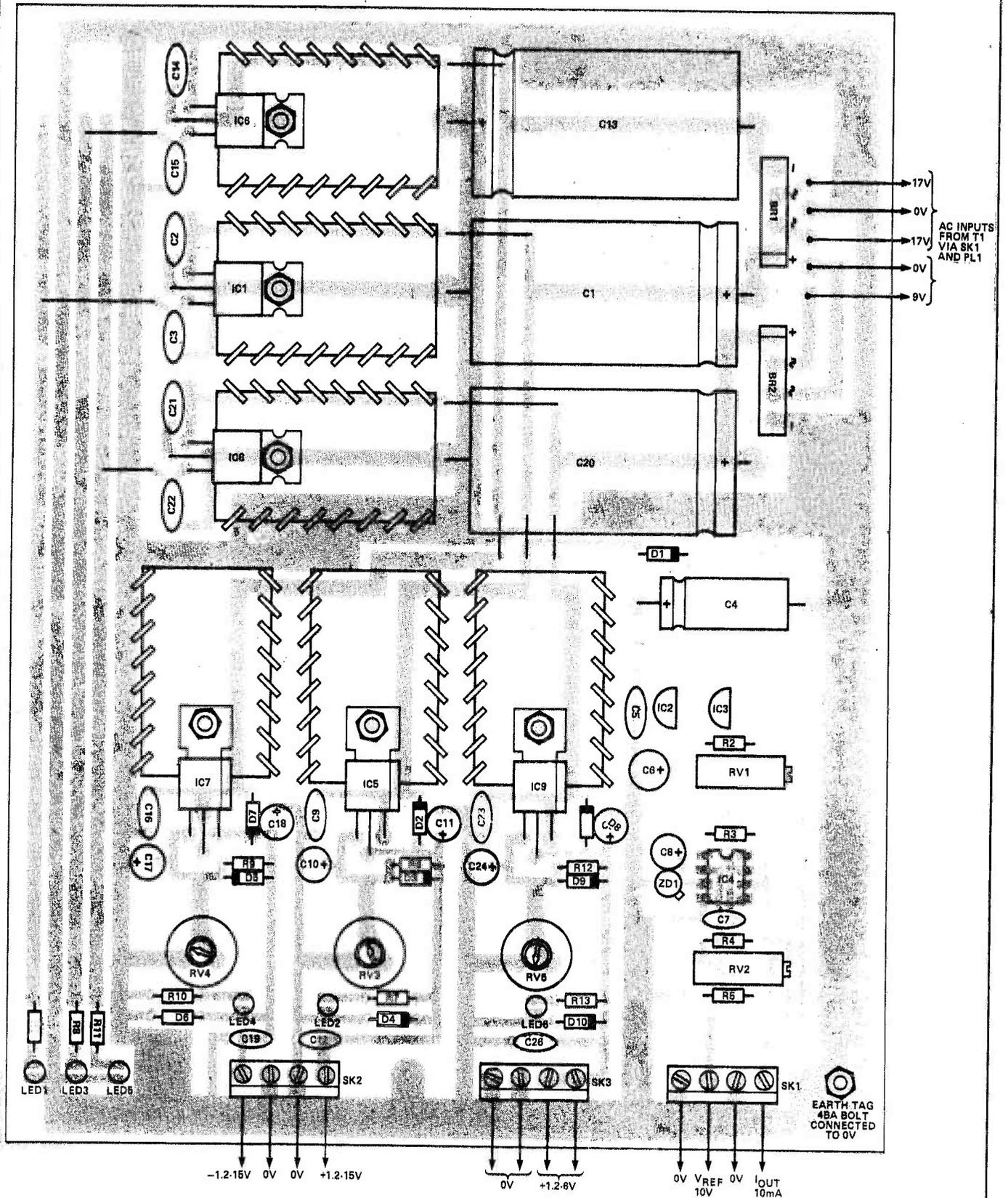


Fig. 2 Component overlay for the power supply PCB.

PARTS LIST

RESISTORS	(all 1/4W 5%)
R1, 5, 8	1k0
R2	100R
R3	1k5
R4	8k2
R6, 9, 11, 13	390R
R7, 10	820R
R12	270R
RV1	50R, 20-turn, 3/4" cermet preset
RV2	500R, 20-turn, 3/4" cermet preset
RV3, 4	4k7 carbon track preset with integral knob
RV5	1k0 Carbon track preset with integral knob
CAPACITORS	
C1, 13, 20	4700u 25V axial electrolytic
C2, 5, 7, 12, 14, 19, 21, 26	100n 100V multi-layer polyester
C3, 9, 15, 16, 22, 23	470n 100V multi-layer polyester
C4	470u 25V axial electrolytic
C6, 11, 18, 25	10u 35V tantalum or radial electrolytic
C8	1u0 35V tantalum or radial electrolytic
C10, 17, 24	10u 16V tantalum or radial electrolytic
SEMICONDUCTORS	
IC1	7815
IC2	78L15
IC3	LM317L (100mA)
IC4	3140 or TL091
IC5, 9	LM317M (500mA)
IC6	7915
IC7	LM337M
IC8	7805
D1-10	1N4001
ZD1	ZN423
LED1, 2	red LED
LED3, 4	green LED
LED5, 6	yellow LED
BR1, 2	KBL02 or other 3A, 200V bridge rectifier
MISCELLANEOUS	
FS1	500mA anti-surge fuse and panel-mounting holder
LP1	mains neon, panel mounting
PL1	6-pin DIN plug
SK1	6-pin DIN socket
SK2-4	4-way 10A PCB-mounting screw terminals
SW1	DPDT mains toggle switch
T1	17-0-17V (or 15-0-15V — see text) 50VA plus 9V 20VA mains transformer

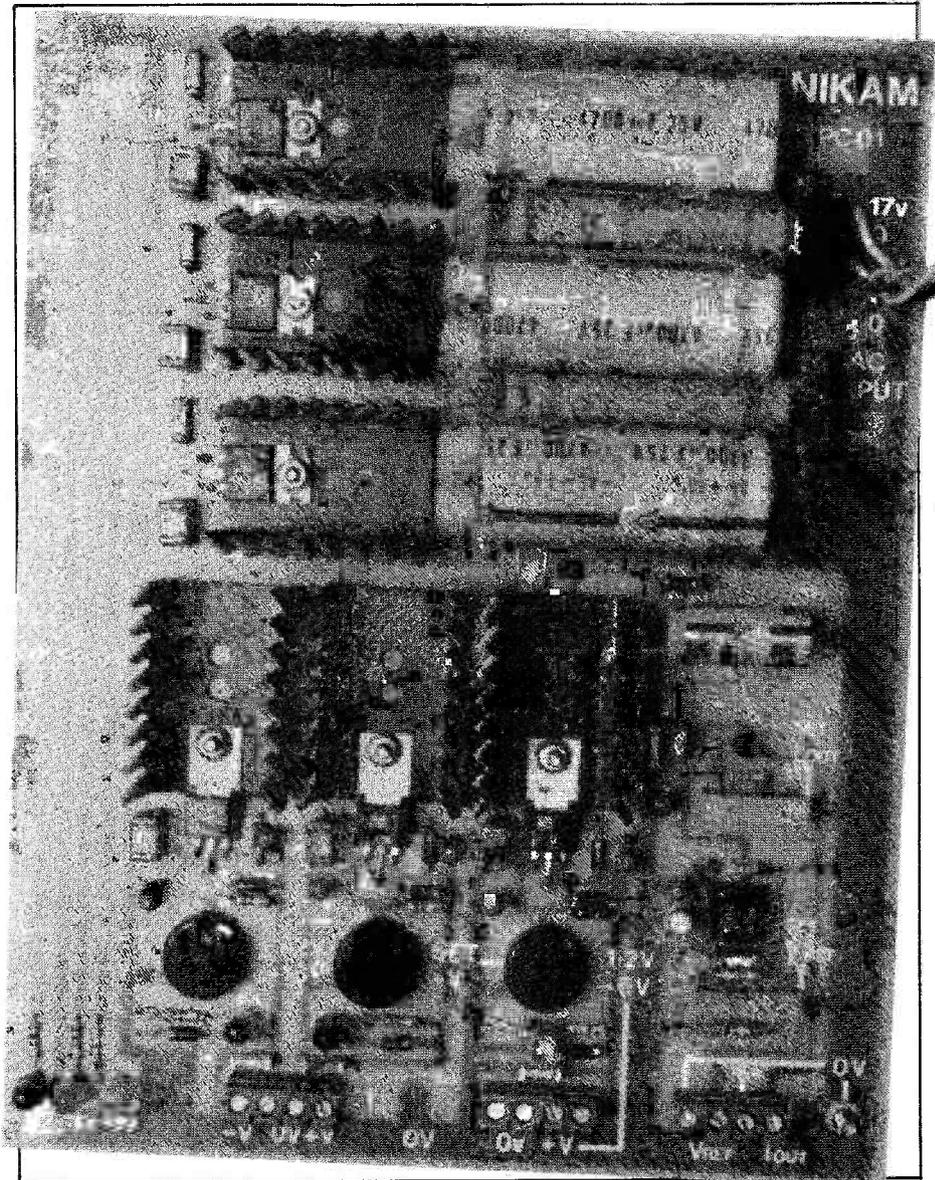PCB; case for transformer; 8-pin DIL IC socket; heatsinks, 6 off; four-core screened cable, heavy duty, for AC connections to power supply board from transformer; mains plug, cable and strain relief bush to suit; 6BA nuts, bolts and washers for heatsinks; 4BA nut, bolt and washer for 0V tag.



and feeding only low voltages to the boards is an essential safety requirement if the system is to be used, as intended, without a case.

Construction

Whilst care has been taken to make the modules easy to construct, the usual precautions are necessary. Frequent reference should be made to the PCB layout diagram and attention to the polarity of diodes, LEDs capacitors and ICs is very important. A socket is recommended for IC4 and LEDs should be spaced away from the surface of the board before soldering. It is not necessary to fit insulating kits on the heatsinks but a little thermal grease should be smeared around each IC tab before mounting to ensure efficient heat transfer.

The mains transformer should be installed in a small metal case,


the exact size of which will be determined by the transformer or transformers you choose. Ideally a single transformer with separate 0-9V and 17-0-17V windings should be used, but these are not widely available. Two separate transformers will work just as well but will, of course, require more space. If a 17-0-17V transformer cannot be found a 15-0-15V one can be used in its place, but this will lead to a loss of regulation if the power supply is used at full load.

Take care with the mains wiring inside the box and make sure that the incoming mains cable is secured by a good strain relief bush. Solder leads from the secondary of the transformer to a six-pin DIN socket mounted in the opposite end of the box to the exposed wiring. In view of the exposed nature of the test equipment boards, it is most

important that there is a good earth connection to the boards. To this end, make sure that the incoming mains earth, the transformer screen (if present), the box metalwork and the DIN socket 0V pin are all reliably connected together. Similar attention should be paid to the DIN plug and lead which carry the transformer output to the power supply board.

Testing

The transformer box should be tested on its own before plugging in the board. Double check the earthing arrangements and then switch on. If all is well, connect to the power supply board and switch on again. You should be rewarded either by twinkling LED's or smoke! If the latter then rapid disconnection of power is recommended. Otherwise, check that the fixed supply voltages are correct to within plus or minus 5%, then check the variable supplies. Finally, adjust the voltage reference against the best DVM you can borrow and adjust the current source under short circuit for 10.00mA.

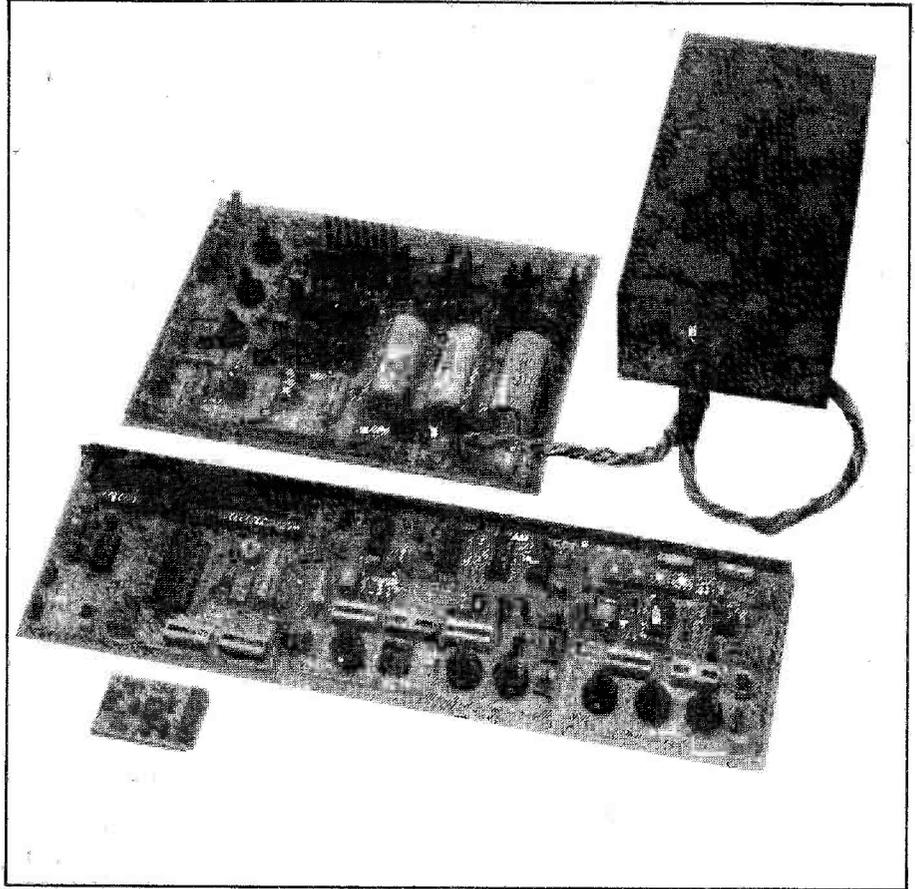

BUYLINES

The resistors and capacitors are all widely available and so are most of the semiconductors. The exception is IC3, the LM317L 100mA variable voltage regulator. The only supplier we know of for these is RS components (stock no. 303-179), who will only accept orders from trade and professional customers. Crew-Allan & Co of 51 Scrutton Street, London EC2 will obtain RS parts for you on payment of a small handling charge, but you may prefer to use another LM317M instead. There is no harm in using the higher-rated device and it should not be too difficult to bend the pins to fit.

RS are also the only source we know of for the moulded presets with integral knob used in the RV3/4 and 5 positions (stock no.s 184-344 and 184-322 respectively). Different types from other suppliers could be used but the PCB may have to be modified slightly to accept them.

We do not know of anyone who stocks a single transformer offering the required voltages, but Maplin have a multi-tapped type which gives 17-0-17V at 2A and RS can supply a 4.5+4.5V type rated at 2.2A (stock no. 207-122). Electrovalue have a 9V 2A type which could be used at a pinch. Some manufacturers

of toroidal transformers claim that their products can be used with the secondaries in parallel, in which case a 0-9 + 0-9 30VA toroid could be used. However, we have our doubts about this practice, so unless it is specifically recommended by the manufacturer we advise against it.

The PCBs will be available from our PCB Service, for details of which see the note in News Digest. Please note that, to save costs, they will not be screen printed as are the prototypes shown in this article.

ETI

★ SECURITY MODULES ★

ALARM CONTROL UNIT
CA 1250
£19.95 + V.A.T.



INFRA-RED SYSTEM
IR 1470



A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

contains:
Control Unit CA 1250
Enclosure & mechanical fixings HW 1250
Key Switch & 2 Keys KS 2801
L.E.D.'s LED 1
5W Horn Speaker HS 508
4 High quality surface mounting Magnetic Switches MS 1025

Order Code: CS 1370

DIGITAL ULTRASONIC DETECTOR US 5063



Only £13.95 + V.A.T.

- * Adjustable range up to 25ft.
- * 3 levels of discrimination against false alarm.
- * Crystal controlled.
- * Low-consumption 12V operation.
- * Built-in delays & fixed alarm time.

An advanced ultrasonic movement detector which employs digital circuit techniques to provide a superior performance for security, automatic light switching and industrial applications.

Suitable metal enclosure £2.95 + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing an installation or simply controlling a single magnetic switch on the front door.

- * Built-in electronic siren drives 2 loud speakers
- * Provides exit and entrance delays together with fixed alarm time
- * Battery back-up with trickle charge facility
- * Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- * Anti-tamper and panic facility
- * Stabilised output voltage
- * 2 operating modes full alarm/anti tamper and panic facility
- * Screw connections for ease of installation
- * Separate relay contacts for external loads
- * Test loop facility

Suitable enclosure for CA 1250 as shown in Complete Security System - HW 1250 Price £9.50 + V.A.T.

The IR 1470 provides an invisible beam of light which, when interrupted energises a built-in relay in order to operate external switches or equipment. Ideal for use in security, photographic, or industrial applications.

Price only £25.61 + V.A.T.

Suitable power supply and timed switching unit for use with IR 1470, etc. Price £13.95 + V.A.T.

EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 + its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided.

Order Code: CS 1480

Add 15% VAT to all prices
U.K. orders at 70p P&P. export postage at cost
Units on demonstration
Shop hours 9.00 to 5.30 p.m.
Closed all day Wednesday
Saturday 9.00 to 1.00 p.m.

Write or telephone for full details of our complete range
Order by telephone or post using your credit card

RISCOMP LIMITED

Dept 51 Poppy Road, Princes Risborough, Bucks HP17 9DD
Tel: (084 44) 6326

AUTOMATIC TEST EQUIPMENT

Love it or 'ate it, automatic test equipment is here to stay. W.P. Bond begins a short series in which all will be revealed.

Automatic test equipment has been around in one form or another for nearly three decades. In recent years, the introduction of LSI and VLSI circuits has totally changed the requirements for ATE, especially since the equipment and procedures must meet the needs of volume production. Cost is perhaps the most important consideration today, and this must be understood in relation to the two general types of test procedure: functional and in-circuit testing.

Functional testing looks at all the functions of a circuit — taken in isolation from a whole system of

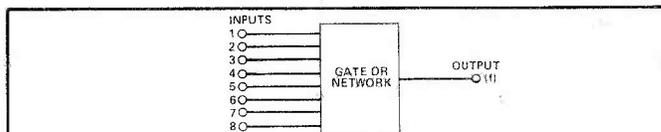


Fig. 1 In the simple case, 256 test patterns would be needed to cover every input combination.

which the circuit may be a part. The circuits involved (and, of course, the test procedures) can be digital or analogue. Digital — or logic — circuits are simpler than analogue circuits from the viewpoint of automatic functional testing. There are simple 'go/no-go' results obtainable with logic circuits, while analogue devices need to be tested within a broad range of acceptable performances. It makes sense to begin an examination of ATE with logic circuits.

Some Logical Steps

There are four main categories of logic circuit:

- ★ Combinational Logic (outputs are dependent solely on the present inputs).

- ★ Sequential Logic (outputs are dependent on present inputs and on previous outputs: circuits with memory or feedback).

- ★ Bus Structured Logic (combined circuitry of the above types on MPU-type boards with components connected by a bus-structure).

- ★ Random Logic (combined circuitry without a bus-structure).

The testing procedure for any given circuit or circuit assembly will depend on the category it belongs to.

There are a number of other considerations that have to be borne in mind when devising test procedures, apart from the categorisation of the circuit concerned. Even in simple cases, functional testing may have to be uneconomically elaborate in order to detect all possible faults. The 8-input gate in Fig. 1 would require 256 test patterns if all input conditions were to be covered. In general, a combinational logic circuit with n-inputs requires 2^n test patterns for

100% truth-testing. Such 'exhaustive testing' (ET) very quickly becomes unwieldy — even with straightforward combinational circuits.

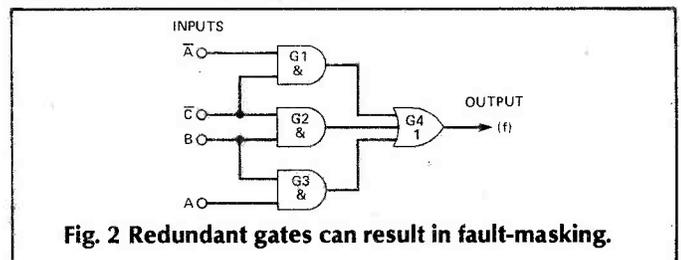


Fig. 2 Redundant gates can result in fault-masking.

Most circuits are not straightforward. One particular problem is caused by the presence of redundant logic, often built-in for reliability. The circuit in Fig. 2, for example, includes a redundant gate (G2) — which can be shown by simplifying the output function, $\bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}B$, using Boolean algebra or Karnaugh mapping. In this case, a fault in the redundant gate may 'mask' faults in the non-redundant circuit elements. For example, in this case if the output from the redundant gate is permanently low ('stuck at 0' or SA0), it will have no effect on the network output. But if it is permanently high ('stuck at 1' or SA1), then the network output will be permanently high regardless of what's happening on the other gates. In effect, the SA1 condition on the redundant gate masks any faults on either of the other gates.

The typical test points are shown in Fig. 3 for a sample circuit. From Fig. 4, it should be clear that the same symptoms can follow from a variety of faults. An SA0 pin fault on the B input to the NAND gate in the figure will be indistinguishable at the output from an SA1 node fault — the same input test patterns will result in the same outputs. To locate faults successfully, it is important to test the circuit in question at more points than its inputs and outputs. Figure 5 shows a small logic circuit with redundancy in which

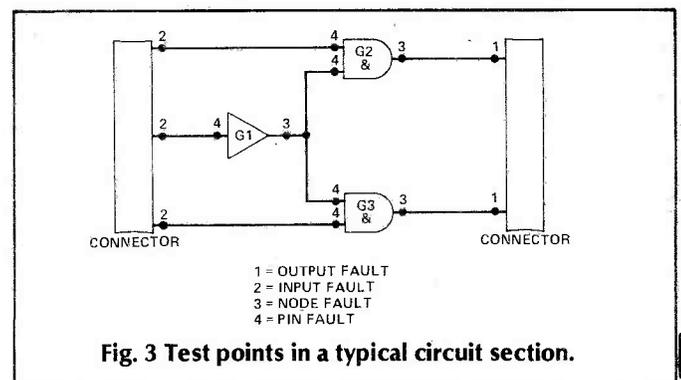


Fig. 3 Test points in a typical circuit section.

an SA1 pin fault would go undetected if the circuit were tested at inputs and outputs only. This sort of fault would be seen where an open circuit existed at the pin, since open circuit inputs float high. Because of this, inputs tied to V_{cc} are sometimes classified as 'undetectable' for fault-finding purposes.

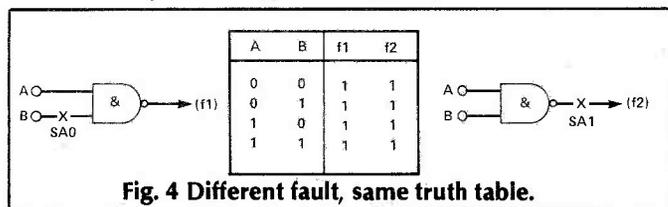


Fig. 4 Different fault, same truth table.

It's worth noting that there are two kinds of redundancy in circuits: fault-masking and self-checking. In the first, faults are masked by multiple circuits performing the same task. In the second, faulty circuits are switched out of the system and good circuits switched in to take their places.

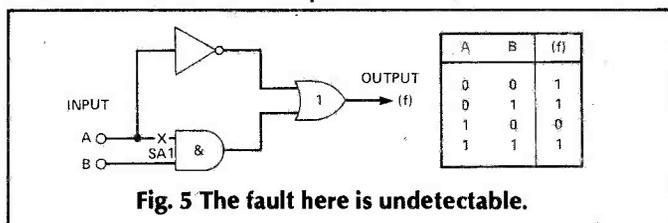


Fig. 5 The fault here is undetectable.

Sequential logic presents the test procedure with yet more problems. Figure 6 shows a circuit configuration in which there is no direct path between the fault (SA0 at input 1) and any output. Here again, the importance of good 'test-pointing' becomes obvious. This kind of fault is described as latent and its detection requires a series of test-patterns to 'walk' it to an output pin. The example shown would require three consecutive test-patterns to clock it through gates G2 and G3. With less than three test-patterns, the fault would simply not appear at any output. The number of patterns required to propagate the fault to the output is called the degree of latency.

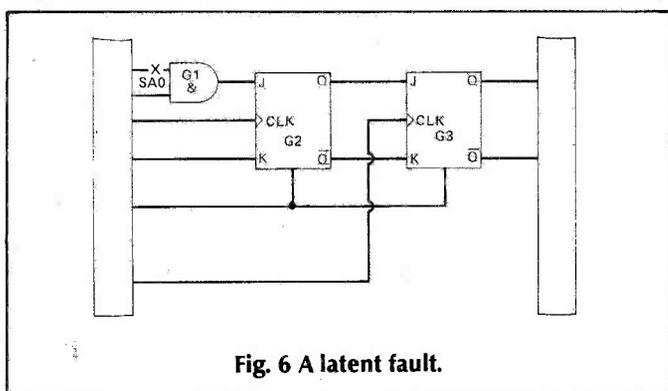


Fig. 6 A latent fault.

Changing inputs can give rise to their own problems. The commonest is called racing. Race hazards take the form of unwanted transients (signal spikes) caused at the output to a logic circuit when two or more inputs change at the same time. These are often known as glitches. In Fig. 7, for example, inputs A and B are meant to change simultaneously from 1 and 0, respectively to 0 and 1. If B reaches the 1 state slightly before A reaches the 0 state, then the output will display the negative-going spike shown. (Such glitches often occur in latching circuits with feedback — dividers, for example). Testing at the output can lead to spurious results in this situation. The simplest solu-

tion is to build-in a time delay at the output test point greater than the propagation delay of the gate.

Untestability Is Detestible

Testability must be designed into electronic modules if they are to be properly tested in the first place. Obvious though this sounds, it is all too often overlooked by circuit designers — perhaps because 'testability' itself is an awkward and ill-understood notion.

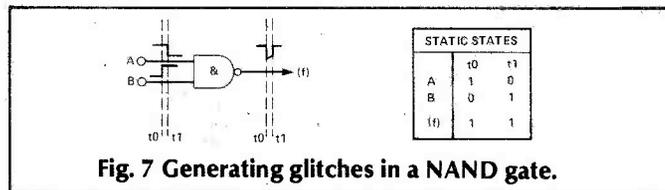


Fig. 7 Generating glitches in a NAND gate.

Testability implies not only the possibility of testing a module or circuit but also the existence of a set of guidelines aimed at maximising test efficiency. Because of the specialized nature of individual complex analogue designs, I will limit the present discussion to functional testing of static digital circuits — although the principles do not lose in generality. (It's worth noting that functional testing, although perhaps more easily understandable, is actually more rigorous than in-circuit testing and as much as ten times more costly).

Test procedures can be considered to have three main aspects: initialising, observing and controlling. For a circuit to be testable, each of these aspects must be catered for.

★ **Initialising.** This is the process by which all nodes of the unit under test (UUT) are set to known states after power-up and before test patterns are applied. Initialising (or initialisation) is essential for reliable and meaningful testing.

★ **Observing.** In the context of ATE, this means minimising the amount of human intervention needed to identify faulty components. Observing entails the correct monitoring of a circuit and involves the provision of suitable 'test points' in the design. Observability is the key to maximising the effectiveness of ATE.

★ **Controlling.** For proper functional testing, the ATE must be capable of controlling the UUT — usually by means of an edge-connector. If all functions of the UUT cannot be exercised, then testing will be inadequate.

In The Beginning

LSI designs are most commonly sequential and the failure to initialise can mean testing circuits in forbidden or indefinite states. There are four main factors in designing-in the ability to initialise a circuit:

★ There should be access to deep sequential circuits — which is a criterion of observability.

★ There should be a means of isolating or breaking feedback loops.

★ There should be access to reset and preset lines in memory elements.

★ In certain cases (for example, VLSI devices where there is no access to reset or preset lines), it should be possible to use 'software initialisation'.

Figure 8 shows a simple sequential circuit — a counter or shift register, for example — without and with testability built-in. If appropriate test points have not been provided on power-up all the memory elements, $f(1)$ to $f(n)$, will be in an unknown state (an x-state). The output will also be in an x-state. Without

access to reset or preset, a 'homing sequence' would have to be provided by the tester. Further, if a fault existed the failure could be observed at the output, but without the use of a guided probe routine and suitable test points fault isolation would be impossible. This is a failure of observability or diagnostic visibility.

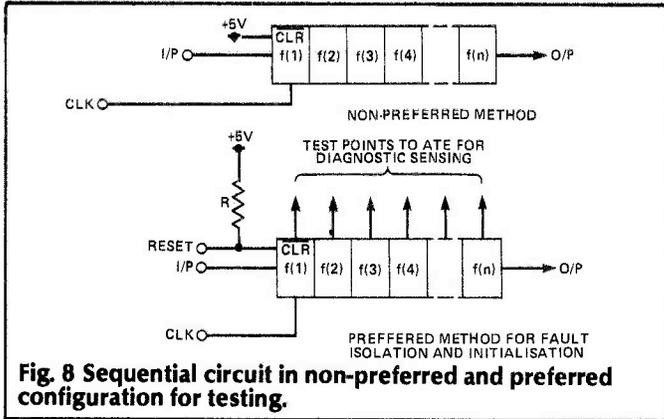


Fig. 8 Sequential circuit in non-preferred and preferred configuration for testing.

In the lower diagram, test points and a reset line have been provided. Since the reset line, in particular, is no longer hard-wired to V_{cc} we need only apply a clear signal to initialise the circuit rather than go through the elaborate motions of a homing sequence.

In Fig. 9, a feedback loop has been introduced to the sequential circuit. Even if test points and the reset line are accessible, so that initialisation — at least — does not require a homing sequence, the problem of fault diagnosis remains. Because of the feedback loop, a fault may be propagated to all points around the loop. To overcome this, the loop must be breakable. The lower diagram shows how this is done — when the control point goes low, the loop is broken.

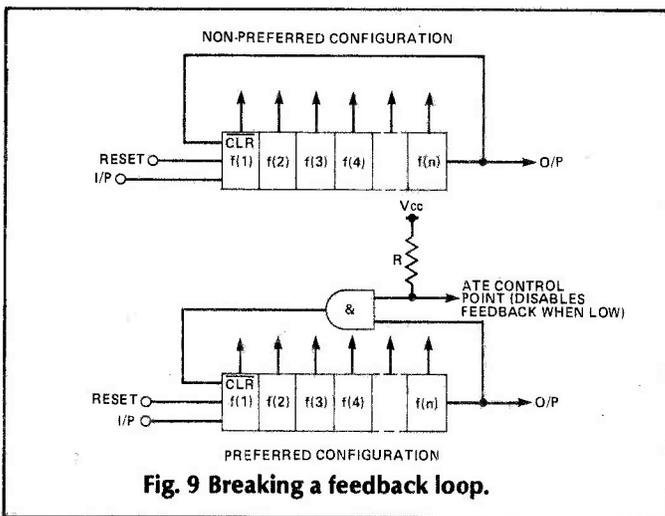


Fig. 9 Breaking a feedback loop.

In Fig. 10, a typical cross-coupled latch is shown. By itself, this poses no initialisation problem, even though the circuit will power-up into an x-state. However, if such latches are deeply embedded in a circuit and if component gates are from different chips, there may be a serious test problem. The preferred method of control, shown in the lower diagram, is to use three-input gates as components so that access points exist to break the feedback loops.

In general, initialising combinational circuits presents no problems, since outputs are purely dependent on inputs. The first test pattern to be applied will

set all nodes to a predetermined state. Initialising sequential circuits is always more complicated since such circuits contain x-states after power-up. These must be flushed out of the system before testing can begin. Since ATE programs must themselves be tested by means of a computer simulation or model circuit, a further problem is encountered. The model circuit will almost certainly power-up into a different state from any other — model or real — circuit.

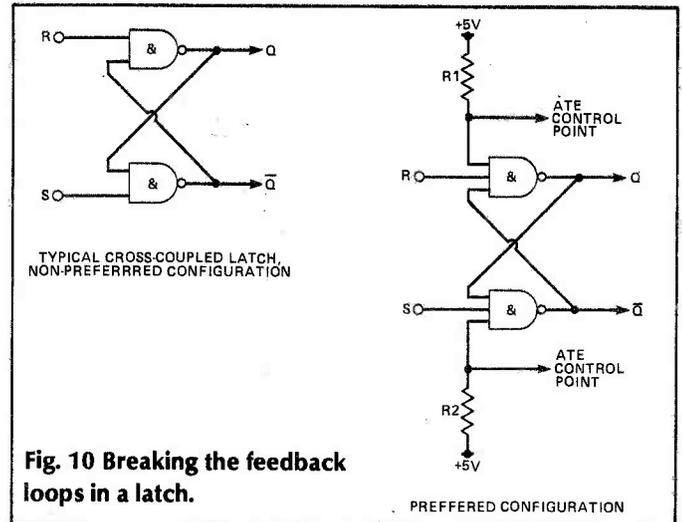


Fig. 10 Breaking the feedback loops in a latch.

A set of test patterns needs to be devised which, when applied to the UUT, will set it to a known state, regardless of its initial condition. This is known as a synchronizing sequence. In a simulation test, the model is then put into the same condition using the same synchronizing sequence before testing proceeds.

The synchronizing sequence can act as a homing sequence in the absence of a reset line. A simple example might involve a synchronous counter — for example, a 74163 — in which all data inputs are set low, the parallel load is enabled and the clock pulsed. Obviously, access to the reset would achieve the same object at a lower overhead.

The difference between a synchronizing sequence and a homing sequence, in general, is that the synchronizing sequence is always the same in each particular, while the homing sequence involves an algorithm to modify its stages in the light of the circuit behaviour. Homing sequences are, in effect, programs with loops and branches and are commonly known by the abbreviation AHS which stands for 'adaptive homing sequence'.

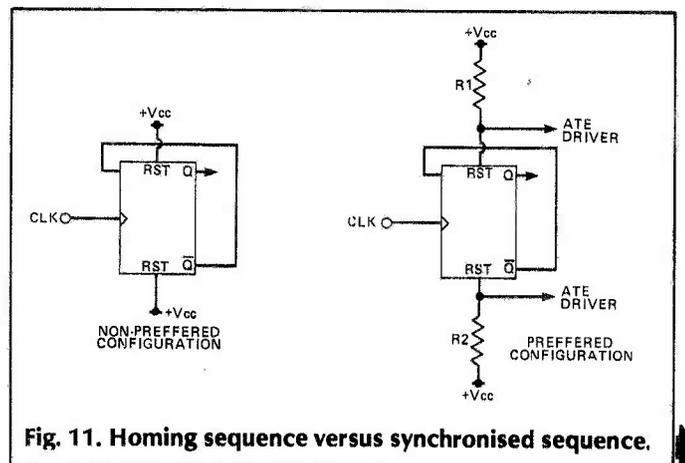


Fig. 11. Homing sequence versus synchronised sequence.

Figure 11 shows a standard divide-by-two circuit. While the right diagram illustrates a simpler arrangement — from a test point-of-view — in which initialisation would require only a single-step synchronizing sequence (reset or preset directly), the left diagram shows a simpler circuit which can be handled by use of an AHS.

The following algorithm would provide a suitable sequence:

1. Set CLK to 0
2. Set CLK to 1
3. If Q is 0, then go to step 1
4. Return to test (output Q, known to be 1).

Bad design is the bane of the tester's life. An example of unhelpful design is shown in Fig. 12 — a section of an actual circuit used in a currently operational ship's navigation system. Basic principles should immediately suggest that it was bad practice to tie J, K and the preset inputs on IC1 (the 7476). Even though the reset lines are available to the tester, close examination reveals another problem. Reset on the 7476 is asynchronous — which is to say, it works independently of the clock — while reset on the 74163 is synchronous — which is to say that it needs an appropriate clock pulse to operate.

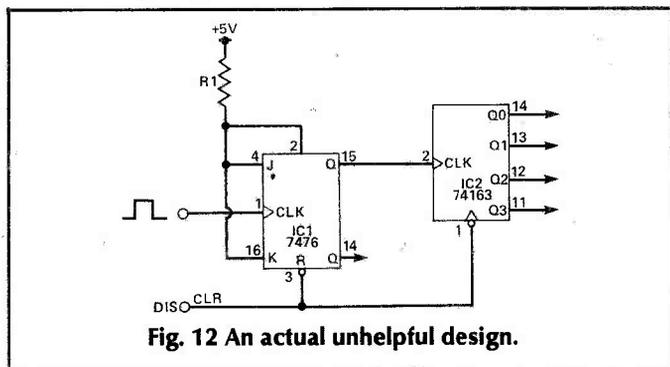


Fig. 12 An actual unhelpful design.

Since the clock pulse for the 74163 is derived from the 7476's Q output, the '163 will never receive a clock pulse when the '76's reset line is low. In other words, in this design configuration it is impossible to reset both ICs at the same time. To make matters worse, there were no direct outputs available from the '163. All of which makes it very difficult to initialise the circuit.

Now You See It

As has been suggested, the observability aspect of testing and the ability to initialise circuits are not totally separable. Observability is really a way of talking about the effectiveness of ATE, which is clearly influenced by the position with respect to initialisation. It's already been shown how feedback loops and the lack of circuit isolation can make it impossible to achieve the desired degree of diagnostic resolution — to use the jargon.

There are three ways in which the circuit designer can improve observability:

- ★ By partitioning circuitry (for example, by function).
- ★ By providing ways to break feedback loops.
- ★ By providing means of isolating faults (for example, the inclusion of suitable test points).

Walking The Dog

Functional testers are, in practice, 'edge connector oriented' and good controllability demands careful

attention to the board design of any circuit. Effective ATE must be able to readily and properly exercise every component on the board. Good design, from the test point-of-view, will reduce the number of steps that need to be taken in order to cover all detectable faults.

The control functions that need to be available to the ATE can be grouped under five headings:

- ★ 1) Reset and preset inputs.
- ★ 2) Tri-state control lines, enable and disable signals.
- ★ 3) Feedback disable.
- ★ 4) Isolation and control inputs for free-running devices, in particular clocks.
- ★ 5) Synchronization signals, especially where microprocessor based modules are being tested, so that the UUT and the ATE may be synchronized.

Reset and preset lines should never be tied together or hard-wired to V_{cc} or GND. They should be 'soft-wired' by use of pull-down or pull-up resistors, to which test-points are connected. CMOS input can be pulled high or low through an appropriate resistor, because CMOS requires only a very small bias current (about $1\mu A$) to establish logic high or low states. TTL, however, can only be successfully pulled high through a resistor, because it requires quite a high sink current (about $2mA$) to establish a logic low state. Active pull-downs should be used, if over-driving is required, as illustrated in Fig. 13. Passive resistors would have to be of too low a value for the ATE's drivers to source a high on to the input. For example, pulling four TTL inputs low would demand a resistor passing $8mA$ across a maximum potential drop of $0.8V$. It would have to be approximately 100Ω .

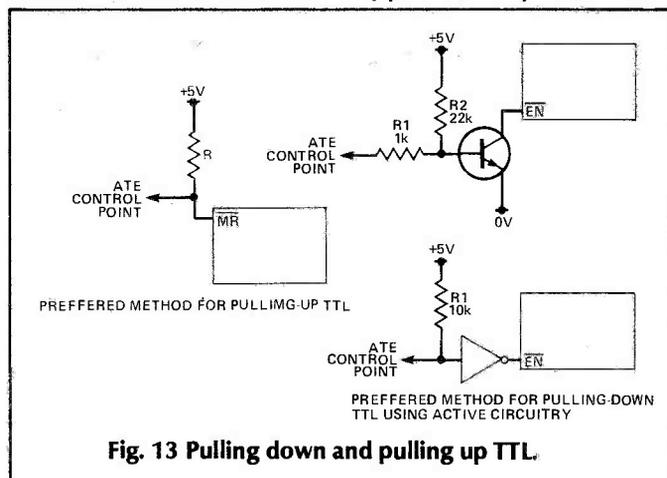


Fig. 13 Pulling down and pulling up TTL.

Access to tri-state control lines is particularly important when testing memory boards or bit-slice processors in which circuit operation depends on ROM contents. Without access to the tri-state lines, it may be very difficult to control the circuit since the ROM contents may make it impossible to exercise all the circuit nodes. The ATE must be able to override such memory-based constraints.

Feedback loops have been dealt with above and the preferred method, shown in Fig. 9, requires no operator intervention but can be handled entirely by the ATE software. Of course, switches or links could be used instead.

Control of free-running devices and synchronization can be treated as two sides of the same problem, since one relates to situations in which the ATE must control the UUT — perhaps, to single-step through a sequence of states — and the other to situations in

which the ATE must simply proceed in step with the UUT.

In the first case, serious synchronization problems will in any case occur where a clock-controlled circuit is operating at a greater rate than the fastest operation of the ATE. Figure 14 shows one way of controlling free-running devices. Under normal operating conditions G1 and G2 would both be enabled allowing the clock pulse through. Under test, control point 1 would disable the clock when taken low by the ATE, allowing an ATE controlled clock to be injected in to control point 2. This is the preferred method, although the same effect could be achieved manually by the use of switches or links.

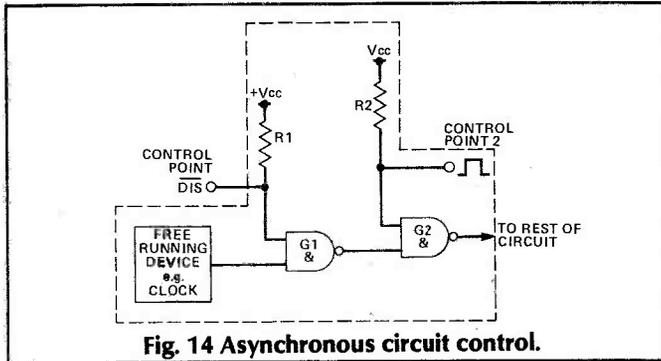



Fig. 14 Asynchronous circuit control.

Synchronization itself is best achieved if the use of multiple clocks is avoided whenever possible. This subject will be dealt with more fully later in this series, when we come to the topic of 'signature analysis'. Multiple-phase clocks present no problems, but multiple clocks cannot be synchronized with. If a multiple clock system cannot be avoided, it should derive each clock signal from a master clock, divided down. This allows a common sync point for the ATE to latch on to.

On The Buses


When testing bus-structured circuits, synchronization alone is not enough. The ATE must be able to force the circuit's controlling microprocessor to relinquish control of its address and data buses.

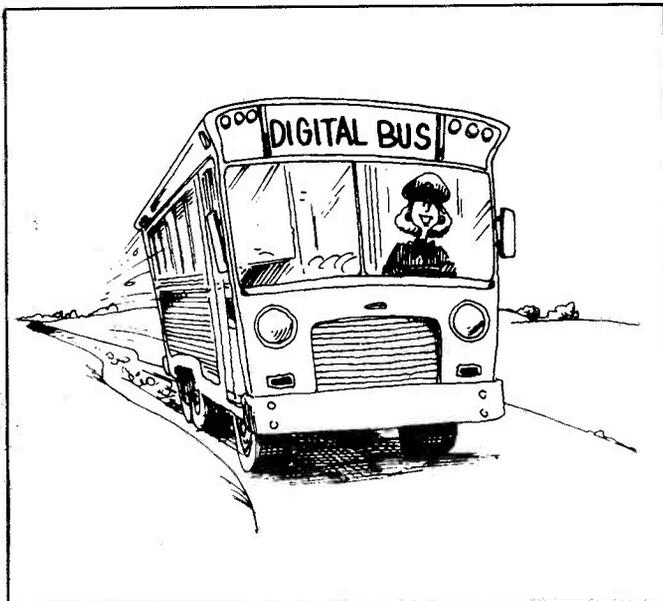If an MPU is used in conjunction with a 'direct memory access' (DMA) device, the DMA device must be capable of instructing the MPU to release its buses



so that I/O or memory block transfers can take place without involving the MPU. Suitable control signals are available on many common MPUs which enable them to put their bus outputs into a high impedance state. Normally, a DMA controller would be used to handle the procedures involved.

The Z80, for example, features a bus request line, BUSRQ, and the 8085 features a similar HOLD line which are used to flag the MPU when the DMA device is about to make a data transfer. On the next cycle, the MPU will finish its present task and flag the DMA device that it has released its buses using — in the above examples — the BUSAK or HOLDKL lines. The DMA device then takes control of the buses. MPUs that do not contain built-in tri-state buffers on the bus lines (for example, the 6502) must be augmented by external tri-state devices if they are to be used with DMA devices or, indeed, with ATE.

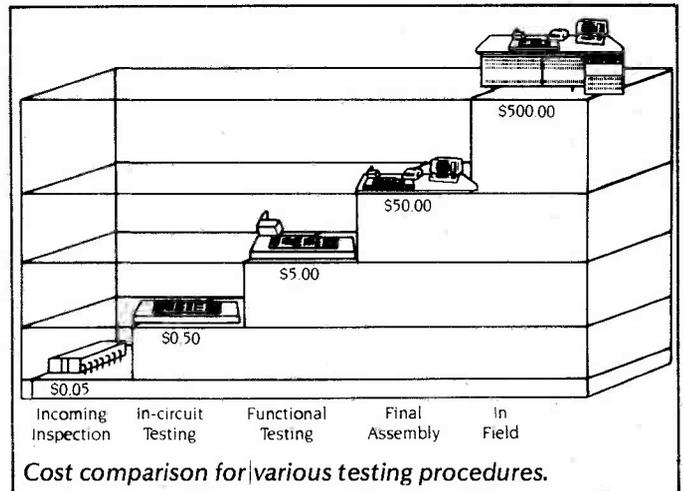

In the case of MPU-controlled bus-structured circuits, effective testing can only be achieved if the ATE has direct memory access either through control lines on the MPU itself or through enable/disable lines on external tri-state buffers.

The Story So Far...

The requirements for testability apply equally to manual and automatic testing. While manual testing can proceed even with a badly thought-out and laid-out module or circuit by the application of a little ingenuity, automatic testing is often impossible with inadequate circuit design. In essence, the circuit designer's responsibility is to provide all the necessary test-points and control lines to enable the ATE to track down all possible faults.

So far, we have only dealt specifically with the functional testing of digital boards. This makes the most rigorous demands on the circuit designer. In subsequent issues, we will turn our attention to in-circuit testing and to analogue circuits and, most importantly of all, to actual test techniques and procedures.

The author and ETI would like to thank the following ATE manufacturers for their help and co-operation in the preparation of these articles. Factron-Schlumberger provided us with the cartoons used in the series and with some valuable information. Zehntel Performance Systems, Genrad Inc., and Hewlett Packard have given permission to re-print details of products and software — Zehntel's Columbia 2000 and their 'timing emulation' technique; Genrad's 'memory emulation' technique; and HP's DTS-70 and 3065 machines, simulation techniques and 'Safeguard' in-circuit software package.

ETI

SUNRISE LIGHT BRIGHTENER

Do you ever get the feeling that rising would be a lot easier if it weren't for the shine? Margaret Blake describes a project to lighten your mornings — gradually!

Picture the scene: it is 7.30 am on a cold and dark Monday morning in winter. The previous evening you were out celebrating with friends and are a bit under the weather. The radio alarm clock switches on and you are awakened gently by its melodic outpourings. All is well until a lone hand ventures from beneath the warm blankets to switch on the table lamp
AAAAAARG!!!

The advent of the clock-radio removed the sudden noisy start to the morning, but what about the switch-on of the bedroom light? Couldn't something be done to remove that shock too?

This article describes the construction of a unit which will gradually illuminate a mains-


powered lamp when it is triggered by an alarm clock or other input. The lamp will take several minutes to progress from darkness to full brightness and will then remain on for either 16, 32, 64 or 128 minutes as desired or until the mains supply is switched off. The circuit is so arranged that the lamp can still be switched on at full brightness in the normal way when required.

The control circuitry is completely isolated from the mains and operation is triggered by a 1.5V pulse to an Enable input. This allows the unit to be used in other applications, for example, in an animal hutch, with a simple switch being used to trigger the lamp brightening process. With a few simple modifications the circuit

can also be arranged to dim progressively when triggered instead of brightening.

If the unit is to be built as a self-contained alarm clock, some sort of timing circuitry and display will be required. Rather than use separate timing ICs or a single clock chip which would then have to be interfaced to a display, the prototype was built around a complete clock module. This consists of a liquid crystal display with an integral clock circuit and comes complete with a mounting bezel. It costs around £16.00 plus VAT but this is probably not a lot more than the cost of using individual components and construction is made a lot simpler.

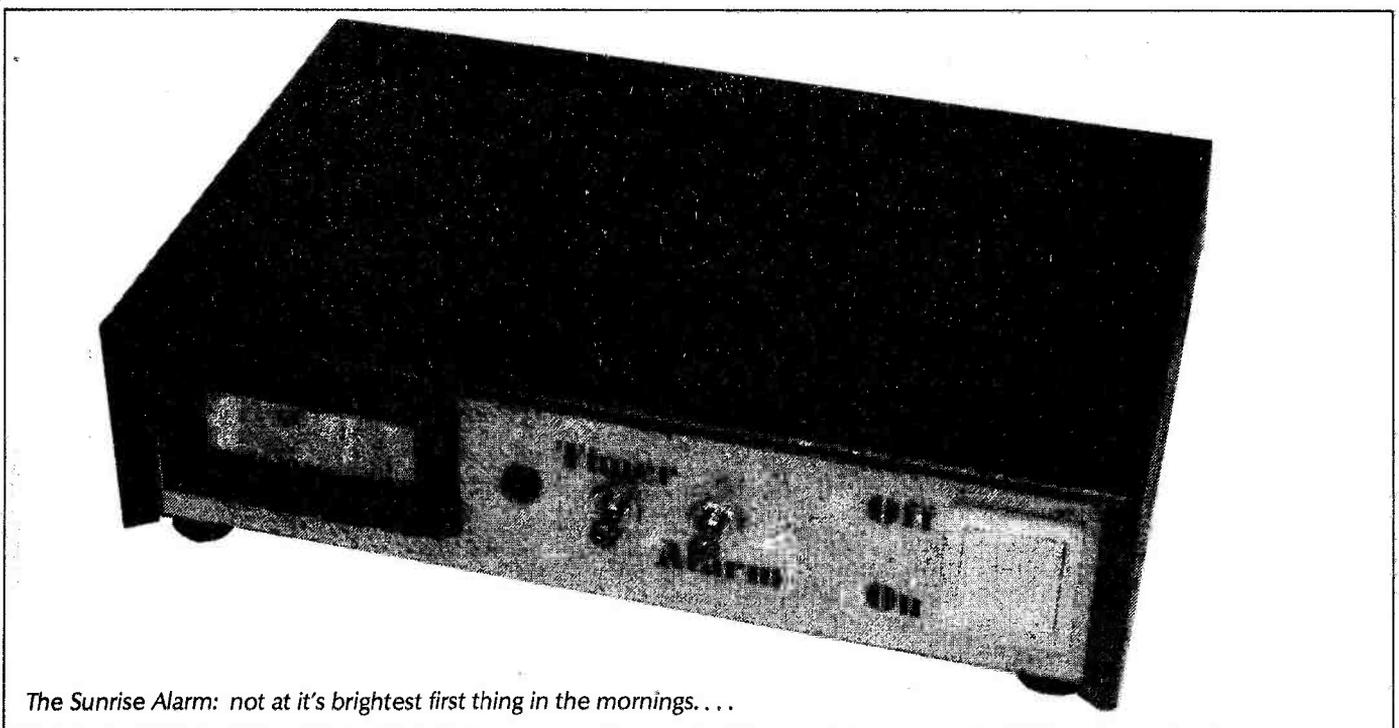The module requires a supply of 1.5V DC. It is advisable to



The Sunrise Alarm: not at it's brightest first thing in the mornings. . . .

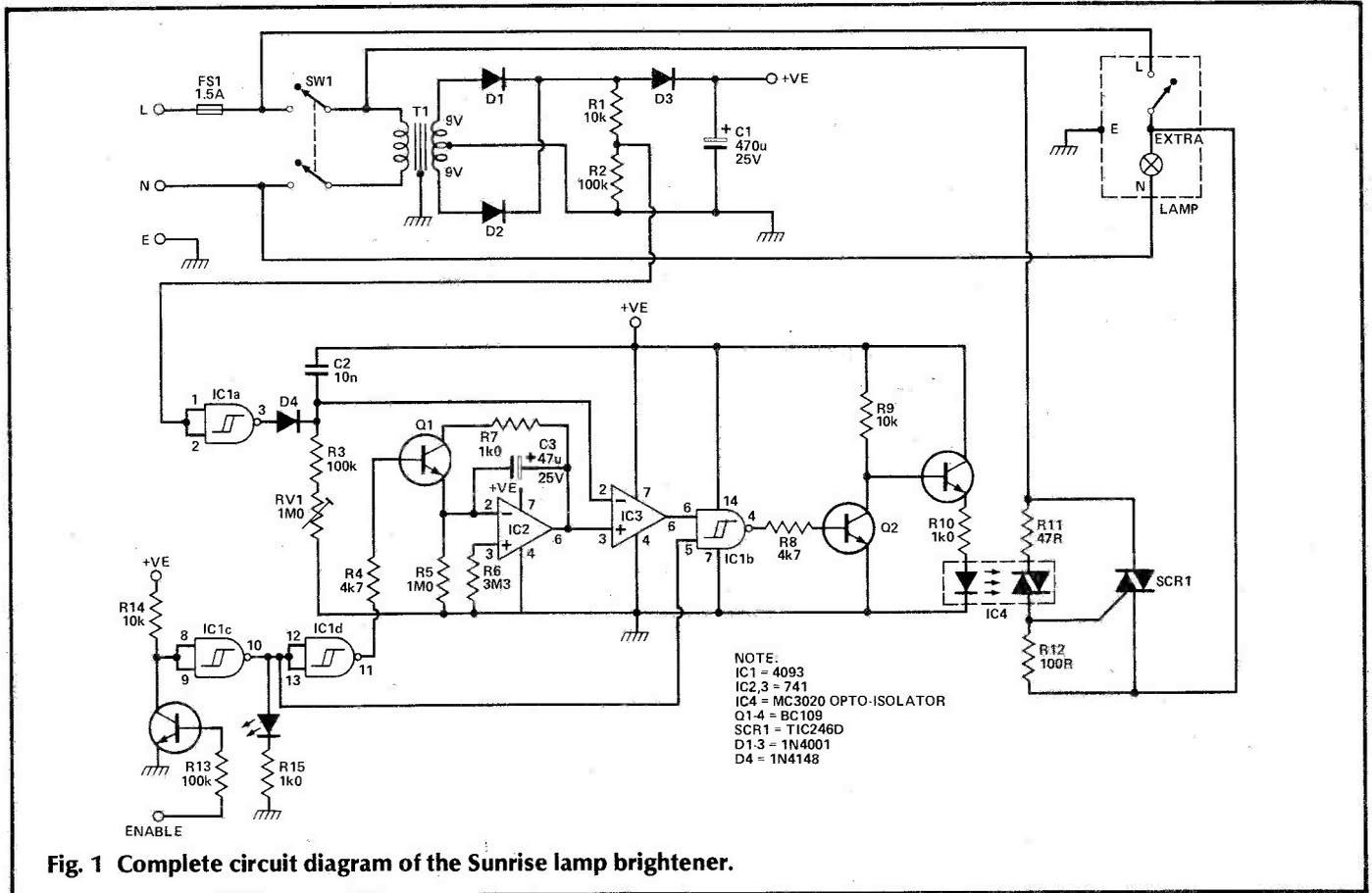


Fig. 1 Complete circuit diagram of the Sunrise lamp brightener.

switch off the lamp brightener when not in use, so, to avoid having to re-set the clock each time the unit is switched on, a 1.5V dry-cell battery is used. A separate mains power supply could be incorporated but the clock consumes so little current that it would be a very long time before the supply paid for itself in saved battery costs.

The clock module includes an incandescent back-light to illuminate the display. This also operates at 1.5V but draws rather more current than the clock. Since the lamp brightener would normally be plugged in overnight ready for the morning, the back light could be connected to the lamp brightener's supply via a suitable dropper arrangement. The

light would then also operate at night when it is most needed. This facility was not included on the prototype but should be simple enough to add.

Construction

The lamp brightener components all mount onto the PCB with the exception of the mains transformer, the LED and, of

HOW IT WORKS

The incoming mains is stepped down by T1 and then full-wave rectified by D2 and D3 before being applied to the voltage divider chain, R1 and R2. The voltage at this point consists of a series of positive half cycles at the mains frequency. A proportion of this voltage is fed from the divider chain to the Schmitt trigger, IC1a, which squares-off and inverts the signal to produce a positive pulse each time the applied mains goes through zero. The full-wave rectified voltage, meanwhile, is fed to C1 which produces a smooth DC output while D3 prevents the action of this capacitor affecting the voltage on the divider chain.

The pulses from IC1a are fed via diode D4 to the network consisting of C2, R3 and RV1. At switch on, the DC supply voltage will appear across R3 and RV1 and the junction of C2 and D4 will be more or less at the same potential as the supply rail. As C2 charges, however,

more and more of the voltage will appear across the capacitor instead of the resistors and the voltage at the junction will drop towards 0V. When the mains next passes through zero and a pulse is delivered by IC1a, the capacitor will be discharged and the process will be repeated. The voltage appearing at the inverting input of IC3 will therefore be a series of ramps synchronised with the mains frequency.

R5, R6, C3 and IC2 form an integrator whose voltage will rise linearly with time over a period of several minutes. When the Enable input is taken above about a volt or so, Q4 will start conducting and pull down the input of IC1c. The output of this Schmitt will then go high and illuminate LED1. The input of IC1d will also be taken high causing its output to go low and this will turn off Q1. The output of IC2 will then start to rise.

IC3 acts as a comparator of the signals from IC2 and the ramp signal from IC1a

and D4. The output of this IC will go high when the voltage coming from D4 is below the voltage from IC2. IC3's output will be mostly low at first, but as the voltage from IC2 rises steadily IC3 will go high earlier in each mains cycle. IC1b is another Schmitt trigger and acts to sharpen up the transient of IC3, its output switching cleanly between the positive supply rail and ground.

R8, R9, Q2, Q3 and R10 provide the drive for the LED which is contained within the opto-isolator, IC4. The other half of the opto-isolator is a small triac which, when triggered by a current through the LED, conducts and causes current to flow from R11 and R12 into the gate of the main triac, SCR1. Thus, as the voltage from IC2 rises steadily, the triac will conduct for a larger percentage of each half-cycle and the lamp will slowly brighten. Swapping over the two inputs to IC3 will cause the lamp to dim gradually instead.

PARTS LIST — LIGHT BRIGHTENER

RESISTORS (all 1/4W, 5%)

R1, 9, 14	10k
R2, 3, 13	100k
R4, 8	4k7
R5	1M0
R6	3M3
R7, 10, 15	1k0
R11	47R
R12	100R
RV1	1M0

CAPACITORS

C1	470u 25V electrolytic
C2	10n
C3	47u 25V electrolytic

SEMICONDUCTORS

IC1	4093
IC2, 3	741
IC4	MC3020 opto-isolator
Q1-4	BC109
D1-3	1N4001
D4	1N4148
LED1	red LED with panel-mounting bush
SCR1	TIC246D

MISCELLANEOUS

FS1	1.5A fuse and PCB-mounting holder
SW1	DPDT mains toggle switch
T1	9-0-9V 100mA chassis-mounting mains transformer

PCB; case; IC sockets if desired, 1 off 14 pin and 3 off 8 pin DIL; four-core mains cable and either four-pole plug and socket or strain relief bush to suit; three-core mains cable and strain relief bush to suit; heatsink for triac (used only if heavy load is being driven); nuts and bolts; veropins; PCB stand-off pillars; connecting wire, etc.

BUYLINES

Most of the parts are widely available from our advertisers and the usual mail-order suppliers and few of the component values are critical anyway. The opto-isolator is available from Watford Electronics and Maplin stock four-core mains cable and plugs and sockets to suit. The clock module is an RS part and can only be obtained directly by trade and professional customers, but Crewe-Allan of 51 Scrutton Street, London EC2 can obtain it for you on payment of a small handling charge. Other clock modules which offer similar functions and operate from a 1.5V supply should be suitable, and there is no reason why a unit built up from individual parts or an existing electronic alarm could not be used provided a 1.5V signal can be obtained from them to drive the brightener circuit. The PCB will be available from our PCB Service, for details of which see the note in News Digest.

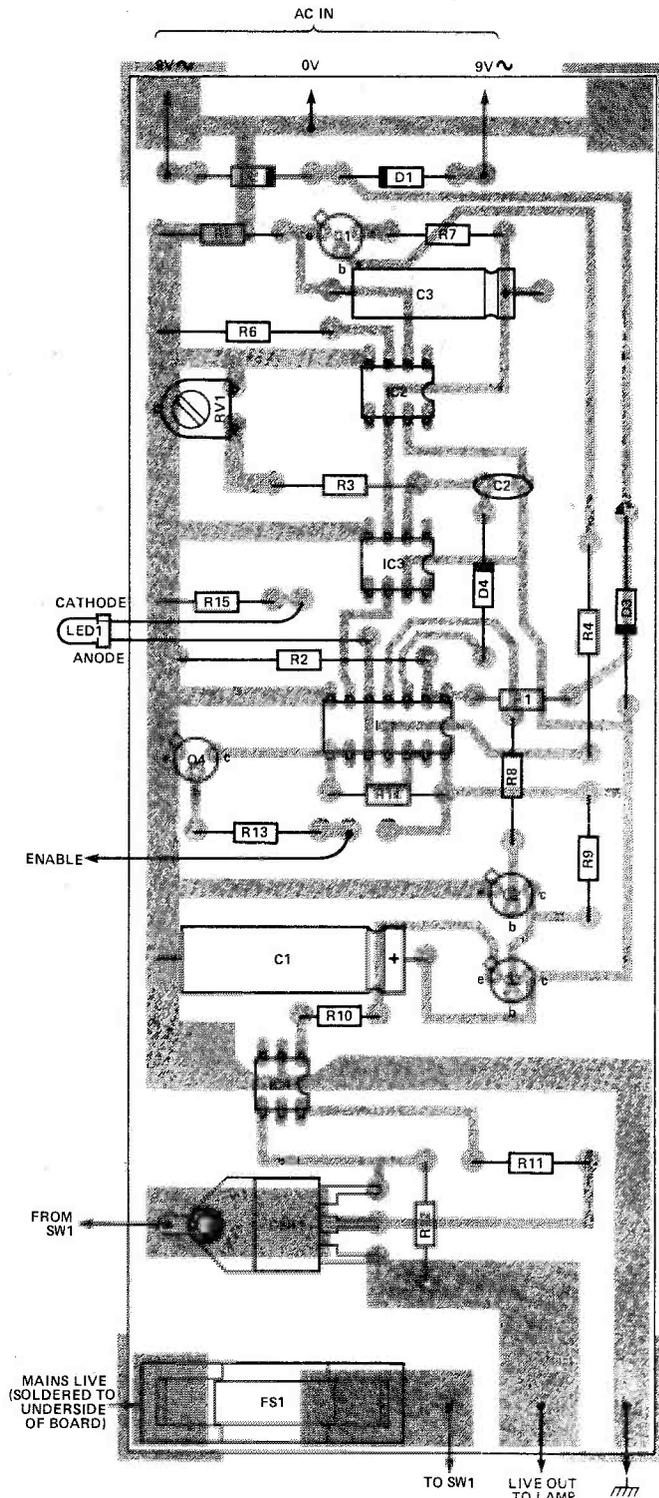


Fig. 2 Component overlay for the lamp brightener PCB.

PROJECT: Light Brightener

course, the on-off switch. The triac is run well within its rating and doesn't need a heatsink so it too is mounted directly onto the PCB.

Begin assembly by soldering into place the hardware items such as the circuit board pins, the fuse holder and the IC sockets (if you are using them), then install the passive components (resistors, capacitors, etc) and finally the semiconductors (the diodes, transistors, triac and ICs). Secure the triac to the board with a nut and bolt and include a solder tag ready for the connection from SW1. If IC sockets have been used, the ICs should be placed in them only when all of the soldering is complete.

Install the PCB in the case, making sure that the end which carries the mains circuitry is well clear of the switches and any other projections with which it might come into contact. If you are using a metal case it should be well earthed, and you should take particular care to ensure that the live end of the board is well clear of the case sides.

Bolt the transformer into place and then install the on-off switch

and the mains wiring. Use a four-core mains cable for the output to the table lamp and route it through a grommet and some kind of strain relief arrangement in the rear panel. Alternatively, if you don't want the table lamp to be permanently attached to the lamp brightener, a four-pole socket can be used on the rear panel and the table lamp fitted with a matching plug. Wire up the LED on the front panel and temporarily attach a bayonet lampholder and bulb to the end of the four-core cable.


Temporarily short the two pins at the timer input on the PCB and then connect the unit to the mains and switch on. The LED should light up to show that the circuit has triggered and the light bulb should come on slowly over the next few minutes. Don't get too worried if nothing seems to be happening early on — even after two minutes the lamp should still only be glowing faintly and it should take a further five minutes to reach full brightness. If that seems a long time, remember that Murphy's law states that five minutes in the morning is longer than five minutes at any other time

of the day! If all is well, switch off to reset the circuit then switch on again and set the initial brightness as desired by adjusting RV1.

Disconnect the unit from the mains and install the clock module, the battery and the push buttons which select the clock functions. SW2, SW3 and SW4 should be mounted on the rear panel and SW5 and SW6 should be on the front panel. The connections to the clock module are shown in Fig. 3.

Break the temporary short circuit across the PCB timer pins and connect the CNT lead from the module to the Enable pin. Don't forget to provide a connection from the negative side of the clock battery to the negative rail of the brightener circuit and the mains earth. The parts all fitted fairly tightly into the case used for the prototype, so if a similar case is used a degree of care is essential if the wiring is not to become a real mess.

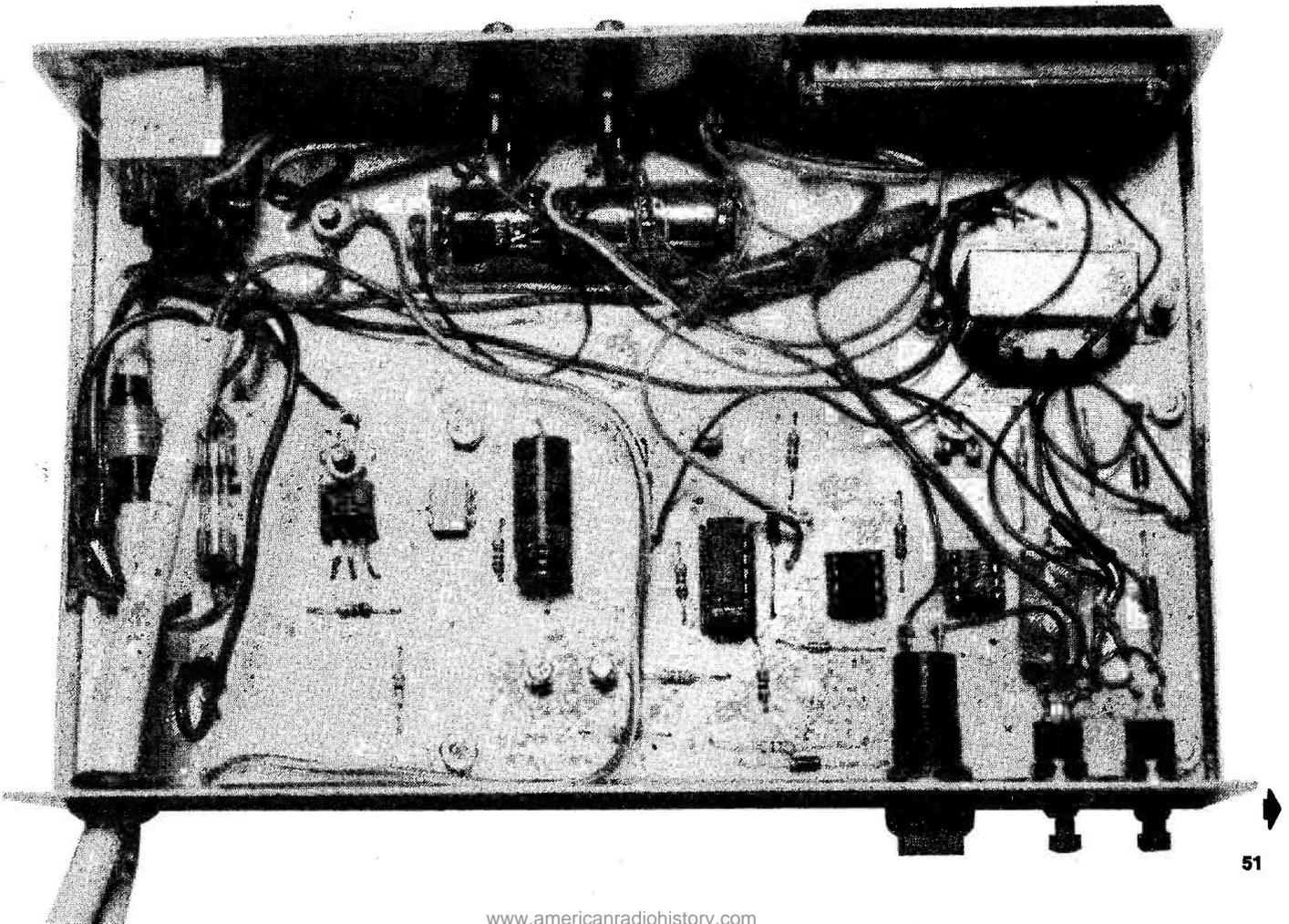The final stage in the construction is to re-wire your table lamp with a four-core lead. The connection arrangement is shown in Fig. 1. The only mains rated four-core




PROJECT: Light Brightener

PARTS LIST — CLOCK

R1-4	100k
SW2,3,5,6	momentary action push-to-make switches
SW4	latching push button switch
B1	1.5V AA battery and holder
Clock module	LCD clock module RS type 304-841 or similar

cables we know of are all 8.5mm diameter or more — rather larger than the three-core leads fitted to many table lamps. Because of this you may have to enlarge the cable entry on the lamp and provide a new strain relief bush. Don't be tempted to use any thinner four-core cables you might happen to have in the junk-box; many of these are only intended for signal applications and are rated at 60V or so maximum.

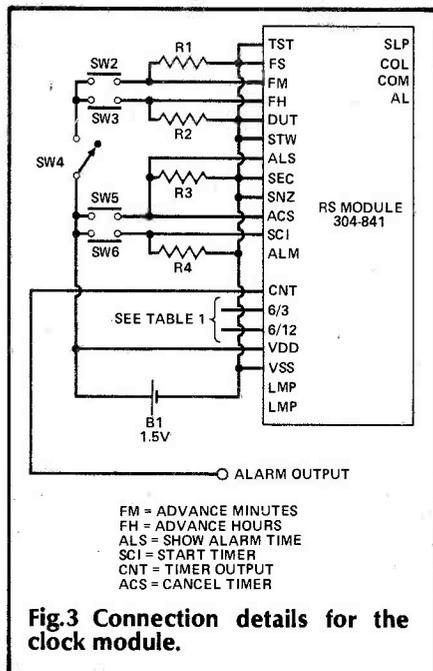With all the wiring complete, begin the final tests by setting the time on the clock module. SW2 sets the minutes and SW3 the hours, and SW4 must be switched on while the setting is taking place.



The inclusion of this switch prevents the time being accidentally altered if either of the other buttons are knocked.

Set the mains switch at off, plug in the lamp brightener and check

that the table lamp can be switched on and off in the normal way using its own switch. Now switch on the brightener and press SW6 until the LED comes on. The table lamp should come on at the previously-set minimum and then progressively brighten until it is fully on.

6/3	6/12	Timing Period
+1.5V	+1.5V	16 minutes
+1.5V	0V	32 minutes
0V	0V	64 minutes
0V	+1.5V	128 minutes

Table 1 Connecting the 6/3 and 6/12 pins on the clock module to select the lamp 'on' period.

In use, the alarm time is set by pressing SW5 and then using SW2, SW3 and SW4 in the normal way. Pressing SW5 at any other time will display the alarm time set. The brightener should be plugged in before retiring at night and will then operate at the pre-set time in the morning. Pressing SW5 will cancel the alarm.

ETI

ROBOTS for EDUCATION TRAINING and INDUSTRY

MENTOR System from £495

NEPTUNE System from £2195

Hydraulic Using water!

SERPENT System from £1515

featured in Practical Electronics Sept. issue

MENTOR DC servo desktop robot; 8 bit control system; 300gm capacity; 420 reach. **Extensive software is supplied free with each robot.**

NEPTUNE I/II 6/7 axes 8/12 bit control system 2.5kg capacity. 1120mm reach. **Leads available for connection to BBC, ZX Spectrum, Apple IIe, Commodore 64 and VIC 20.**

SERPENT I/II 5 axes 12 bit control system 2 kg capacity 400/650mm reach. **Most other micros are also easily usable with these robots.**

Robots programmed from keyboard or hand-held simulator (model robot). **Robots available as kits or ready built.**

Robots may also be taught by 'lead by the nose' method. **FMS (Flexible Manufacturing System) work cell additions also available.**

Please phone for brochure: 0264 50093. **West Portway Industrial Estate, Andover SP10 3ETI.** A private and independent company giving prompt, personal service.

Introducing...

WITH 'PERSPEX' SEE-THROUGH CYLINDERS!

COMPLETE SYSTEM UNDER £1000! including software!

(ni-'ad water nymph)

NAIAD

MICRO ELECTROHYDRAULIC ROBOT

BEING FEATURED IN WIRELESS WORLD November Issue

Please phone for brochure: 0264 50093 **West Portway Industrial Estate, Andover SP10 3ETI.** A private and independent company giving prompt, personal service.


TECH TIPS

COLUMN LOUDSPEAKER DESIGN

Rev. A. Sharp
Aberdeen

Column loudspeakers consist of a number of individual loudspeaker units arranged in a vertical line. They are highly directional and when used in a PA system can be pointed away from the microphone to reduce the risk of feedback. The directional characteristics are enhanced if the units are wired so that the central loudspeaker gives the highest output power and the level tapers off towards the ends. The principle was described in an article by David Hornsby in ETI November 1982.

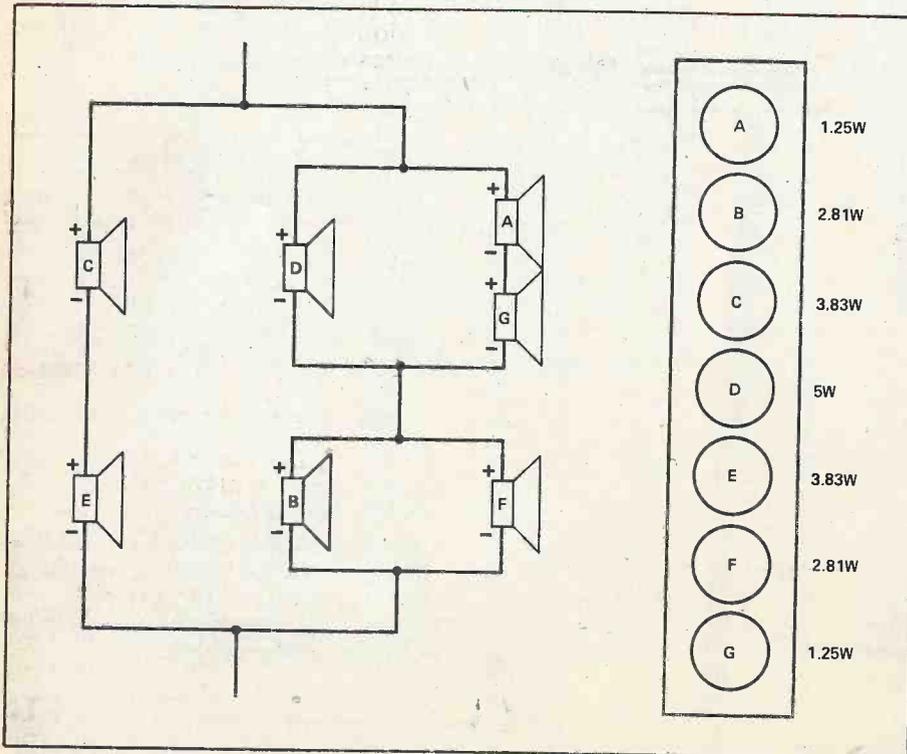This arrangement uses seven 5 watt loudspeakers instead of the five 10 watt ones suggested in the article. This allows cheap 16R car radio loudspeakers to be used and, because of the extra 'speakers and the increased efficiency, still gives almost as much output as the original arrangement. The total impedance of the network is 11.8R. The circuit has proved very effective in a church PA system.



NOVEL INPUT STAGE AND GAIN CONTROL

P. Day
Newcastle



The circuit shown can be used as a general purpose input stage and enables a number of apparently conflicting requirements to be met. It can handle input signals with a wide range of voltage levels without suffering from the noise and overload problems usually encountered.

The potentiometer acts as two rheostats, controlling both the

input level and the negative feedback. When the slider is near A the input is heavily attenuated, allowing high signal levels to be handled without running into overload. The feedback is high so the circuit noise level is low.

When the slider is at B the input signal suffers negligible attenuation. The op-amp has a high gain and the impedance is also high. With the component values given the maximum gain is 30 dB.

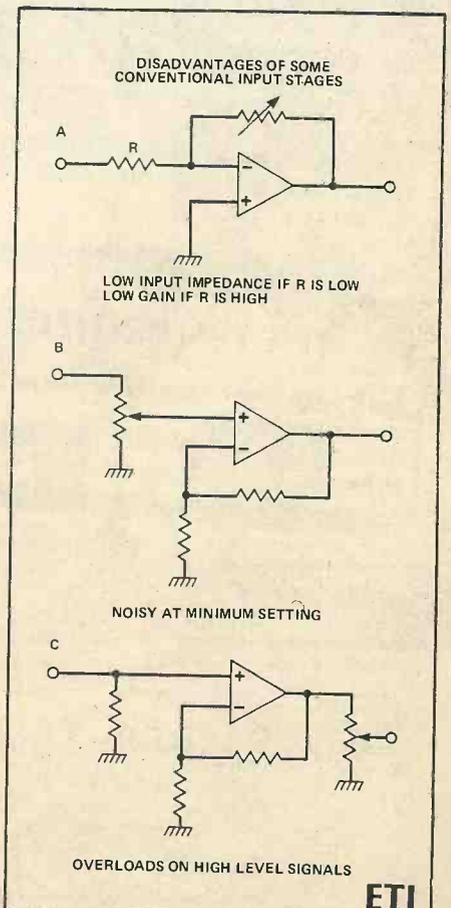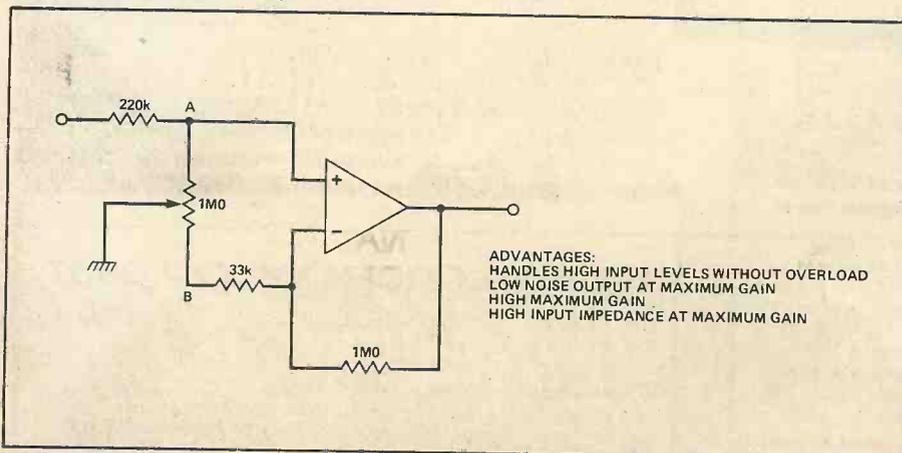I have built and tested a number of these circuits and have been using them as the input stages of a mixer.



**NEXT
MONTH**

AN ARGUS SPECIALIST PUBLICATION

electronics today

INTERNATIONAL

'Well, winter's coming back again.'
'I didn't notice it had ever gone away.'
'Oh, you can always tell.'
'How?'
'The weather...'
'Yes...'
'And the days get longer in the summer...'
'Yes...'
'And the names of the months change.'
'Okay, you've convinced me. But how do you know it's coming back?'
'Well the names of the months change...'
'Yes...'
'And the days get shorter...'
'Yes...'
'And the weather...'
'Why do you keep going on about the weather? It's terrible.'
'That's why I keep going on about it.'
'Of course, there's another way of telling when winter's on its way.'
'Oh, what's that?'
'Well, ETI publishes an issue that's absolutely jam-packed with projects.'
'Oh, yes. The November Ten Project Special.'
'That's the one. Gives you enough projects to keep you occupied all year at a rate of one per month.'
'Hold on. There are twelve months in a year.'
'I know that and you know that, but whatever you do don't tell ETI.'
'Why not?'
'If they find out, they'll have to have this whole page printed again.'

THE TEN PROJECT SPECIAL

This year, the November issue offers more variety than ever before. Among the ten projects lined-up for your delectation are:

The Memory Scope Display

An add-on unit for any oscilloscope which uses digital techniques to slow down the trace and lets you freeze the display. Slow-changing waveforms like sound envelopes and charge-discharge characteristics of capacitors can now be captured and examined without the need to resort to expensive storage devices or long-persistence phosphors.

Switch Mode Regulator

The first project in a series intended to demonstrate the virtues of discrete circuitry, this regulator delivers 5V at up to 1A and hardly gets warm. A perfect replacement for any 7805 with a heat sink large enough and hot enough to fry an egg on.

Rhythm Chip

This canny device uses an EPROM as a metronome or to measure beat-rates directly. All you need to do is tap out a rhythm and the Rhythm Chip will tell you how many beats per minute there are.

Millifaradometer

A voltage window detector, a simple clock and an electro-mechanical counter are the ingredients of this ingenious instrument which will give reliable read-outs of the actual value of large capacitors.

PLUS:


Digital Sound Sampler . . . Electron Interface . . . Chorus Unit . . . Exposure Meter and more.

Oh, we nearly forgot to mention the features, but perhaps we'll leave them until next month.


**NOVEMBER TEN PROJECT SPECIAL EDITION OF ETI.
ON SALE OCTOBER 4TH.
SO YOU KNOW WHAT SEASON IT IS.**

Articles described here are at an advanced stage of preparation. However, circumstances beyond our control may dictate changes to the list of contents.


PCB FOIL PATTERNS

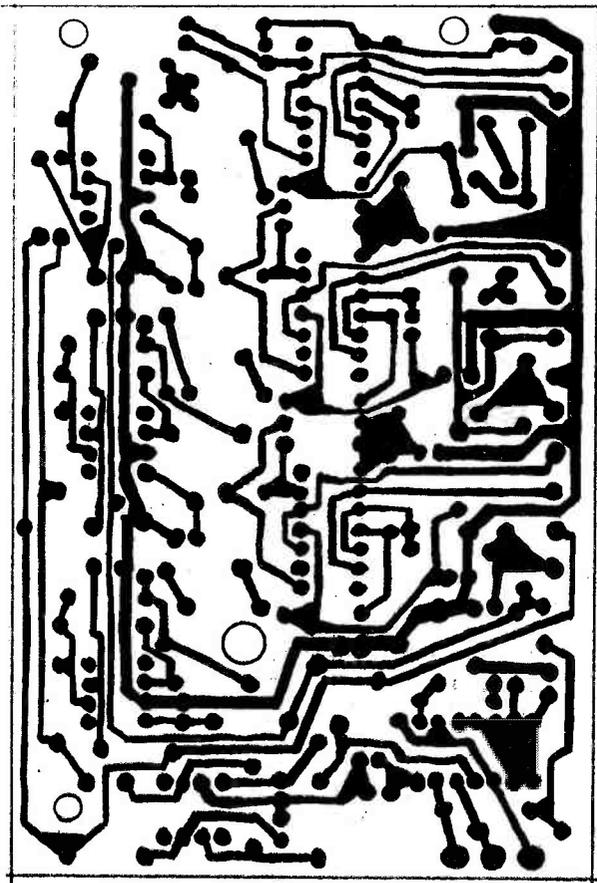

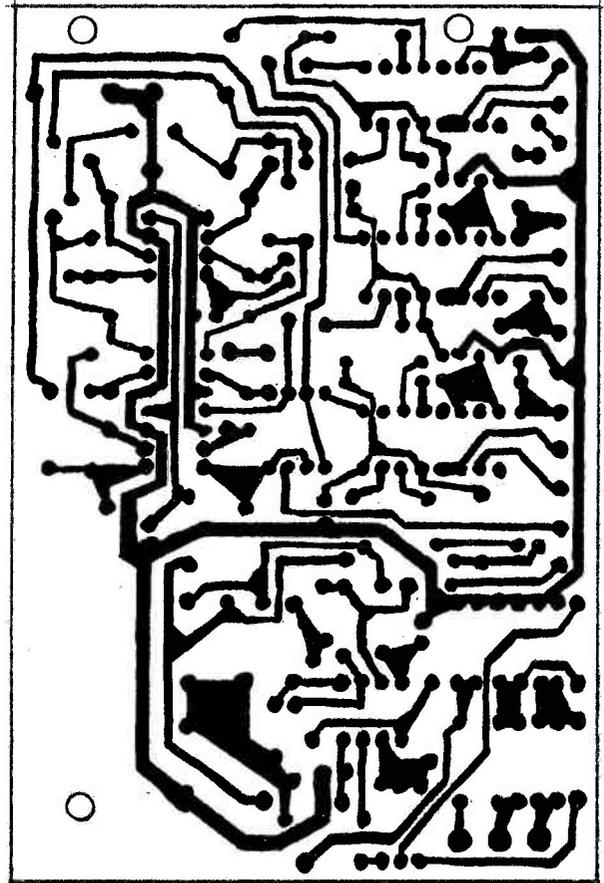
The foil pattern for the Sorcerer chorus audio board.



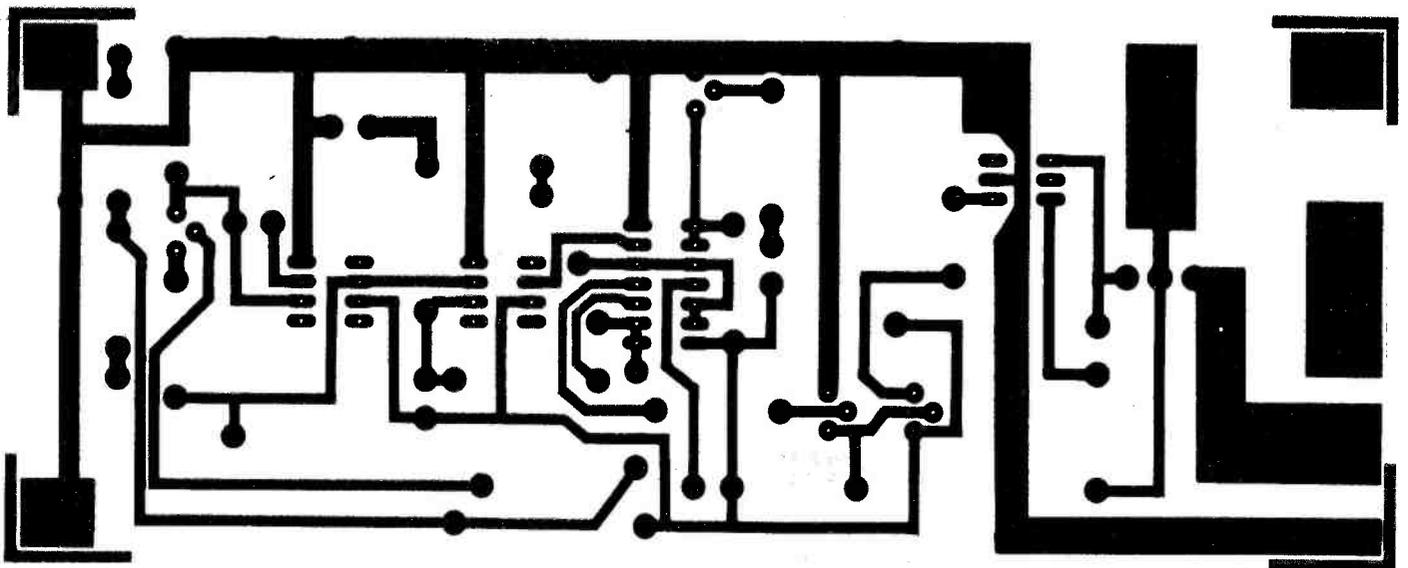
The foil pattern for the Sorcerer chorus clock board.



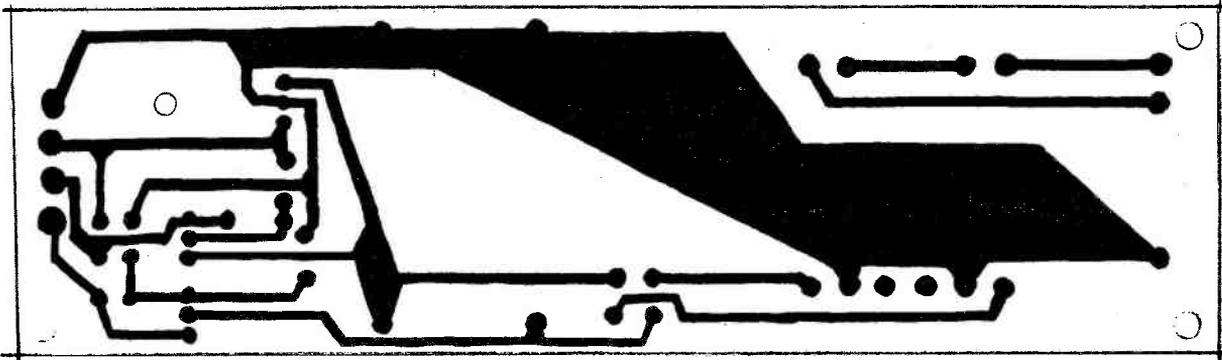
The foil pattern for the Sunrise light brightener.



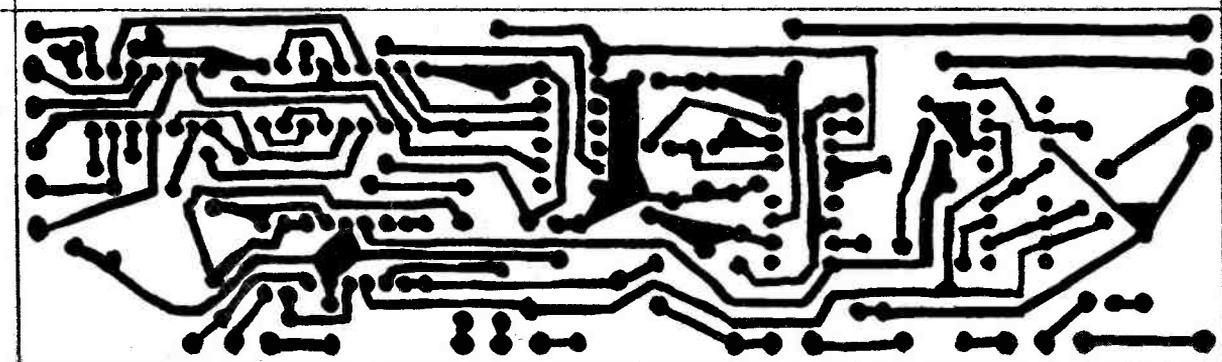
The foil pattern for the Sorcerer power supply board.



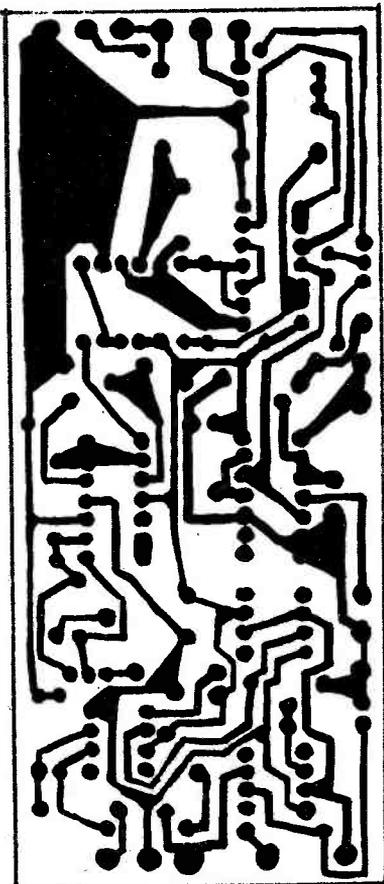The foil pattern for the Sorcerer VCO board.




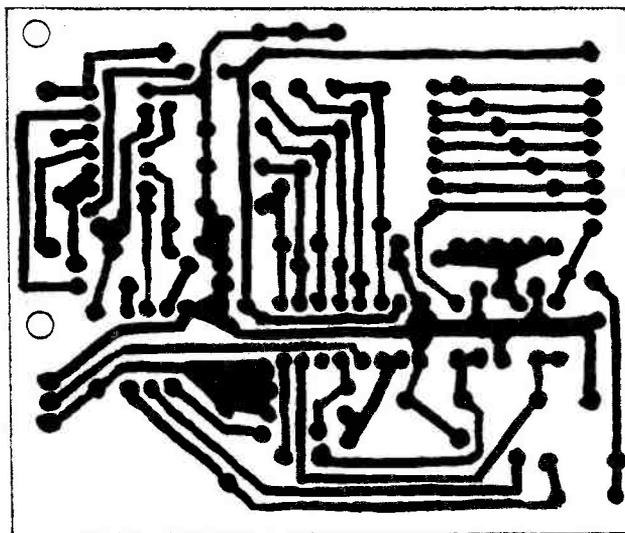The foil pattern for the Sorcerer envelope board.



The foil pattern for the Sorcerer keyboard interface board.

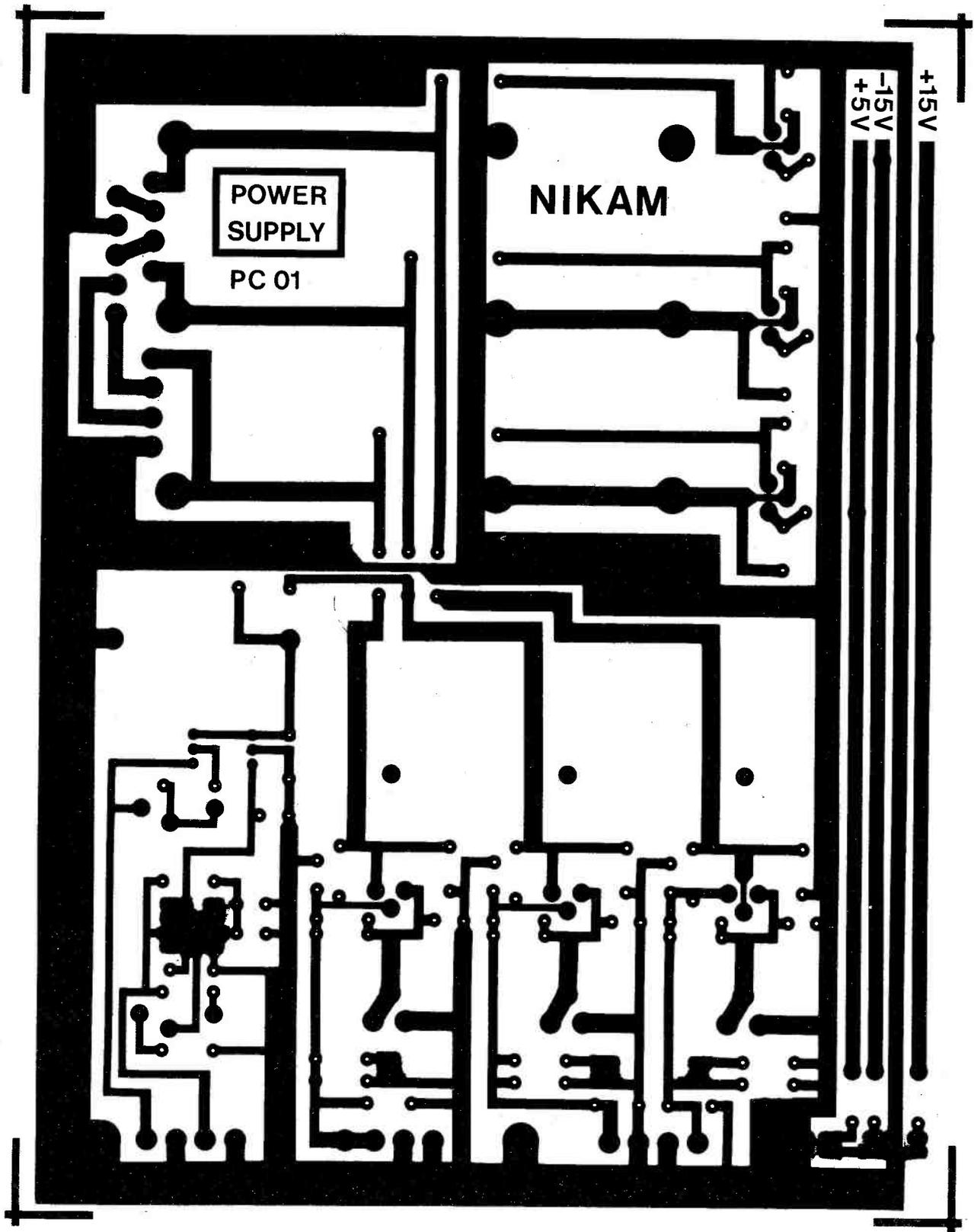The foil pattern for the Sorcerer keyboard is too large to print here (it measures about 500 x 230 mm). It is also too large for us to photocopy. We can prepare clear film copies photographically but the cost is likely to be between £15.00 and £20.00. All in all, it will probably be easier for you to purchase a ready made board from our PCB Service (when it becomes available!)



The foil pattern for the modular test gear PSU board.

SERVICE SHEET

Enquiries

We receive a very large number of enquiries. Would prospective enquirers please note the following points:

- We undertake to do our best to answer enquiries relating to difficulties with ETI projects, in particular non-working projects, difficulties in obtaining components, and errors that you think we may have made. We do not have the resources to adapt or design projects for readers (other than for publication), nor can we predict the outcome if our projects are used beyond their specifications;
- Where a project has apparently been constructed correctly but does not work, we will need a description of its behaviour and some sensible test readings and drawings of oscillograms if appropriate. With a bit of luck, by taking these measurements you'll discover what's wrong yourself. Please do not send us any hardware (except as a gift!);
- Other than through our letters page, Read/Write, we will not reply to enquiries relating to other types of article in ETI. We may make some exceptions where the enquiry is very straightforward or where it is important to electronics as a whole;
- We receive a large number of letters asking if we have published projects for particular items of equipment. Whilst some of these can be answered simply and quickly, others would seem to demand the compiling of a long and detailed list of past projects. To help both you and us, we have made a full index of past ETI projects and features available (see under Backnumbers, below) and we trust that, wherever possible, readers will refer to this before getting in touch with us.
- We will not reply to queries that are not accompanied by a stamped addressed envelope (or international reply coupon). We are not able to answer queries over the telephone. We try to answer promptly, but we receive so many enquiries that this cannot be guaranteed.
- Be brief and to the point in your enquiries. Much as we enjoy reading your opinions on world affairs, the state of the electronics industry, and so on, it doesn't help our already overloaded enquiries service to have to plough through several pages to find exactly what information you want.

Subscriptions

The prices of ETI subscriptions are as follows:

UK:	£16.30
Overseas:	£18.30 Surface Mail
	\$24.00 Surface Mail (USA)
	£43.30 Air Mail

Send your order and money to: ETI Subscriptions Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire, HP1 1BB (cheques should be made payable to ASP Ltd). Note that we run special offers on subscriptions from time to time (though usually only for UK subscriptions, sorry).

ETI should be available through newsagents, and if readers have difficulty in obtaining issues, we'd like to hear about it.

Backnumbers

Backnumbers of ETI are held for one year only from the date of issue. The cost of each is the current cover price of ETI plus 50p, and orders should be sent to: ETI Backnumbers Department, Infonet Ltd, Times House, 179 The Marlowes, Hemel Hempstead, Hertfordshire HP1 1BB. Cheques, postal orders, etc should be made payable to ASP Ltd. We suggest that you telephone first to make sure there are still stocks of the issue you require: the number is (0442) 48432. Please allow 28 days for delivery.

We would normally expect to have ample stocks of each of the last twelve issues, but obviously, we cannot guarantee this. Where a backnumber proves to be unavailable, or where the issue you require appeared more than a year ago, photocopies of

individual articles can be ordered instead. These cost £1.50 (UK or overseas surface mail), irrespective of article length, but note that where an article appeared in several parts each part will be charged as one article. Your request should state clearly the title of the article you require and the month and year in which it appeared. Where an article appeared in several parts you should list these individually. An index listing projects only from 1972 to September 1984 was published in the October 1984 issue and can be ordered in the same way as any other photocopy. If you are interested in features as well as projects you will have to order an index covering the period you require only. A full index for the period from 1972 to March 1977 was published in the April 1977 issue, an index for April 1977 through to the end of 1978 was published in the December 1978 issue, the index for 1979 was published in January 1980, the 1980/81 index in January 1982, the 1982 index in December 1982, the 1983 index in January 1984 and the 1984 index in January 1985. Photocopies should be ordered from: ETI Photocopies, Argus Specialist Publications Ltd, 1 Golden Square, London W1R 3AB. Cheques, postal orders, etc should be made payable to ASP Ltd.

Write For ETI

We are always looking for new contributors to the magazine, and we pay a competitive page rate. If you have built a project or you would like to write a feature on a topic that would interest ETI readers, let us have a description of your proposal, and we'll get back to you to say whether or not we're interested and give you all the boring details. (Don't forget to give us your telephone number).

Trouble With Advertisers

So far as we know, all our advertisers work hard to provide a good service to our readers. However, problems can occur, and in this event you should:

1. Write to the supplier, stating your complaint and asking for a reply. Quote any reference number you may have (in the case of unsatisfactory or incomplete fulfilment of an order) and give full details of the order you sent and when you sent it.
2. Keep a copy of all correspondence.
3. Check your bank statement to see if the cheque you sent has been cashed.
4. If you don't receive a satisfactory reply from the supplier within, say, two weeks, write again, sending your letter recorded delivery, or telephone, and ask what they are doing about your complaint.

If you exhaust the above procedure and still do not obtain a satisfactory response from the supplier, then please drop us a line. We are not able to help directly, because basically the dispute is between you and the supplier, but a letter from us can sometimes help to get the matter sorted out. But please, don't write to us until you have taken all reasonable steps yourself to sort out the problem.

We are a member of the mail order protection scheme, and this means that, subject to certain conditions, if a supplier goes bankrupt or into liquidation between cashing your cheque and supplying the goods for which you have paid, then it may be possible for you to obtain compensation. From time to time, we publish details of the scheme near our classified ads, and you should look there for further details.

OOPS!

Corrections to projects are listed below and normally appear for several months. Large corrections are published just once, after which a note will be inserted to say that a correction exists and that copies can be obtained by sending in an SAE.

Audio Design Buffer (September 1984)

There has been some confusion due to the cases of the various transistors (Fig 4, p.61). Q1 and Q11 are T092(E) (gate, source and drain for pins 1, 2 and 3), while Q2 and Q12 are T092(F) types (gate, drain and source). Q3, Q4, Q13 and Q14 should be 'L' types with a T092(A) case (base, collector and emitter). The pin positions marked on the overlay are correct. The pins themselves may need to be bent to fit the PCB.

Spectrum Centronics Interface (December 1984)

Pin 18 of IC3 on Fig. 1a (page 57) should be marked pin 17. The mistake seems to have been carried over to the PCB (p.58). The track leading from pin 18 to the 0V rail should be cut. A correspondent informs us that he has had success with only this modification — in other words, with pin 17 left floating, too.

Single Board Controller (March 1985)

There were a number of errors in the parts list. RP2 is listed as a 10k SIL pack but is actually four separate resistors, and the same applies to RP3. RP4 is also listed as a SIL pack but should consist of seven common resistors. R13 is always required, not just when a cassette interface is used as stated.

The Real Components (May 1985)

In Fig. 1 on page 20, the connections for the Texas L and 2N transistors are incorrectly shown. They should read B, C and E from the top.

Heat Pen (June 1985)

The instruction in the penultimate paragraph on page 49 should read "... adjust RV2 for 2.73V...", not 2.37V as stated.

Low Cost Audio Mixer (June 1985)

In Fig. 6 on page 39, the PCB foil pattern has been incorrectly shown as though from the copper side. The board is shown correctly from the copper side in the foil pattern pages. In Fig. 10 on page 40, the positive power rail at lower left should be shown connected to pin 8 of the TL072s, IC1-5).

Noise About Noise (July 1985)

In Fig. 5 on page 24, no connection should be shown between the cathode of the diode and the negative side of the 470u capacitor.

Printer Buffer (July 1985)

The case specified is actually larger than the one used for the prototype. It will, of course, work perfectly well, but if you want to a compact unit use a Verocase 202-21038H (180 x 120 x 65mm) rather than a Verocase 202-21035. The regulator IC17 should be bolted to the back of the case to provide heatsinking or, alternatively, fitted with a TO220 heatsink.

Please note that the designer, Nick Sawyer, has been in touch to inform us that the refresh problem we mentioned last month (page 52) is dealt with in the printer buffer software. In this case there is no need to replace the TMS 4416 dynamic RAMs, although as far as we know the replacement parts mentioned (Hitachi HM48416 DRAMs) will cause no problems. The full text of Nick Sawyer's letter will appear next month. Meanwhile, our apologies for any confusion caused.

Intel 8294 Data Encryption Unit (September 1985)

It should be apparent from the text, page 35, that an actual program has been omitted. This program is for use with the SDK 8085 kit only, and copies may be obtained from us on receipt of a stamped addressed envelope.

REVIEWS

A GUIDE TO PRINTED CIRCUIT BOARD DESIGN

Book

Charles Hamilton
The Butterworth Group,
Borough Green,
Sevenoaks, Kent
TN15 8PH.

price: £7.50.

Could there be anything useful here for our own PCB designs? That was my first thought on seeing this book. Let's face it, just like you lot out there in hobby land, we at ETI have to turn our hand to everything from metal bashing to screen printing and a few tips from the experts are always welcome.

As it turns out, the book is aimed at those who intend to make a career of PCB layout in a large company drawing office

and much of the information is not possible to apply to the occasional PCB layout.

The first chapter is a guide to understanding circuit diagrams, which I sincerely hope ETI readers can do already. Next we have advice on how to compile a file of component shapes and sizes - useful in a company that standardises its component stocks, but not much good if you're going to build a circuit with odds and ends from your spares box.

Chapters on the design layout and master artwork have one or two useful hints, but on the whole they are geared to company procedures. For one thing, we wouldn't produce a design layout (with component placing and interconnections all on the same artwork) in the first place. We just plunge straight into the master artwork, and it usually turns out alright on the night.

Other short chapters cover computer aided design (the book assumes you already have £50,000 of CAD equipment and explains how to provide the input), preparing assembly drawings, flow soldering (we use a soldering iron), and so on.

By all means buy the book if you are thinking of making a living from PCB design, but for the general reader I don't think there is enough relevant information to make it worthwhile.

Paul Chappell

INTRODUCTION TO MICROCOMPUTER ENGINEERING

Book

D.A. Fraser et al.
Ellis Horwood, Market
Cross House, Cooper
Street, Chichester,
West Sussex, PO19 1EB

price: £13.75
(student edition).

There are six authors credited for this one book. Since there are nine chapters, either some authors worked harder than others or they wrote 1½ chapters each. Perhaps each author wrote every sixth word? Anyway, no matter how it was written the authors have come up with a very useful book indeed.

There are chapters on four of the most popular 8-bit microprocessors: the 8085, Z80, 6800 and 6502. There is enough detail for the reader to be able to use these devices in relatively simple

systems without reference to any other data - a point I thoroughly approve of. Electrical specifications and timing limits are not included, but unless you're trying to squeeze every ounce of performance from the device you can probably do without them.

Sixteen-bit microprocessors are dealt with in considerably less detail, all in one chapter. Devices mentioned include the 8086, Z8000, 68000 and several others. If you want to use these devices you will certainly have to seek further information from manufacturers data sheets, but the book may help you select the best one for your purposes.

The rest of the book consists of a mixed bag of odds and ends, some of which are not often included in a book of this type. You will find descriptions of the IEEE 488 and S100 buses, some useful ideas on the use of interrupts and DMA, a brief description of fault signature analysis, and much more. If there is any fault in these chapters it is lack of detail, which is understandable in a book that covers so much ground. You get a taste of everything from video graphics to operating systems (CP/M and UNIX) without enough to satisfy you once your appetite has been whetted. However, there is a bibliography of books for further reading at the end...


Paul Chappell

ALF'S PUZZLE

History tells of many men of genius who failed to achieve recognition in their own lifetimes. This could so easily have been the case with Alf. Some of you may know of him as the inventor of the lithium raincoat, or perhaps as the founder of the Snipe Nosed Pliers Owners Club, a very exclusive organisation which to this day has only one member (Alf). To many of you he will be completely unknown.

How can this be when he has been beavering away in the basement of ETI headquarters for the past 15 years, barely taking the time to snatch forty winks in the broom cupboard each night before he's back at the workbench again?

The great tragedy of Alf's

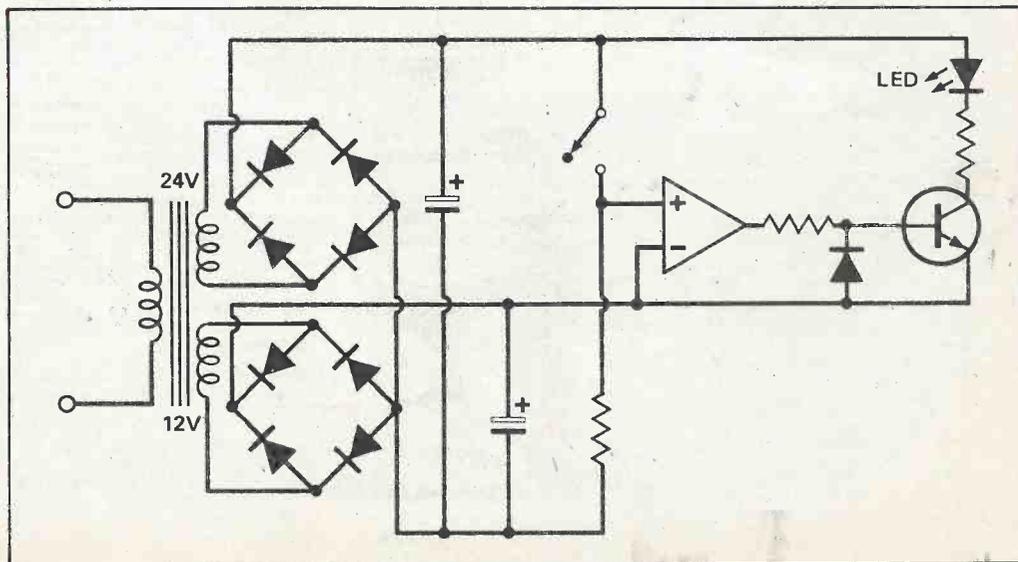

life is that none of his designs ever quite work. The circuit pictured here is one of his finest efforts. The idea is that as soon as the switch is turned on, an LED lights up to remind you to turn it off again. Sad to say, what

actually happens is that the LED turns on for a few seconds and then stays off.

We can't let such a brilliantly conceived idea go to waste, so can any of you fathom out what's wrong with it? If you can, please

don't write in because it would only upset Alf and distract him from work on his welly-bootstrap circuit. We'll let you know our solution next month and you can see if it agrees with your own.

PLAYBACK

Whenever some new development comes along which might become a money-spinner for the makers and a fact of life for the rest of us, it is usually launched with vigor and determination in at least two incompatible formats. We have the manyworld TV standards, the various cassette audio tapes (though fortunately all have fallen by the wayside except the now standard compact cassette) and the still active three video formats.

Now that the CCR (Camera Cassette Recorder) has come along to oust the cumbersome separate camera/recorder outfits, a full-scale format war is once more under way. This has given rise to all the old problems, not least of which is indecision on the part of potential buyers. First-generation CCRs used standard VHS and Beta cassettes and were pretty hefty to lug around, so JVC produced their Compact VHS system. This uses half-inch tape in a tiny cassette, but can be played in a standard VHS machine by means of an adapter shaped like a normal VHS cassette.

That was back in 1981, the year after Sony announced their 8-mm system. Sony obtained the signatures of some 130 manufacturers to give them manufacturing rights and thereby virtually established it as the standard CCR system. However, many of these companies signed just to avoid being left out of the act and were not enthusiastic about the appearance of yet another video system.

When C-VHS appeared, many felt that the Sony system would die. It hasn't, and the new CCD-V8 camera recorder from Sony which fairly bristles with advanced features will undoubtedly ensure that 8-mm video will at least co-exist if not supercede the C-VHS system.

Metal particle tape is required to record video on such a narrow tape-width. There have been problems with metal tape in the past but it seems that these are being overcome. High-quality FM sound is a standard feature of the 8-mm system but may or may not be used with C-VHS, just as with standard VHS. Cassette running time is up to 90 minutes for 8-mm compared with 60 minutes for C-VHS.

So what about the incompatibility of 8-mm? Sony have overcome this one and at the same time upstaged JVC adverts by making a CCR which plugs directly into any TV or video monitor: you don't need another recorder to play their tapes back. JVC's claim that their system has 6 million advantages over 8-mm (these being the number of compatible VHS recorders in use) is therefore trumped by Sony's reply that they have 15½ million, which is the number of colour TV's in the UK. And that, they add, is only counting those who pay their licences.

Those of us who do not have £1000 to spare, — which I suspect is more than a few — can just sit back and enjoy the fun. Can't help thinking though, that an awful lot of effort is being wasted in these skirmishes.


Vivian Capel



GONE TO THE DOGS: the separate camera/recorder system has had its day, but strife dogs its successors.

A METAL Z80A COMPUTER

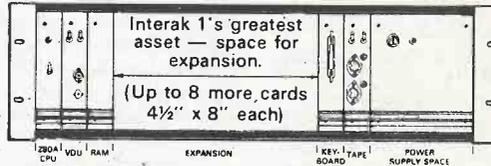Colleges, Universities, Individuals: Build your own modular Z80A-based metal 19" rack and card Interak computer. Uses commonly available chips — not a single ULA in sight (and proud of it). If you can get your own parts (but we can supply if you can't) all you need from us are the bare p.c.b.s and the manuals.



(P.c.b.s range in price from £10.95 to £17.75 + VAT; manuals £1 - £5.)

The Interaktion User Group has 14K BASIC, Assembler, Fig Forth, Disassembler, Debug, Chess and a Book Library, Newsletters etc. No fears about this one going obsolete — now in its fifth successful year! Send us your name and address with a 21p stamp and we'll send you 40 pages of details (forget the stamp if you can't afford it!) You've already got a plastic computer for playing games, now build a metal one to do some real work: Interak, Interak, Interak!

Greenbank

Greenbank Electronics (Dept T9E), 92 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG
Telephone: 051-645 3391

<p>OSCILLOSCOPES TELEQUIPMENT D67. Dual Trace 50MHz. Delay Sweep with manual.....£275 COSSOR CDU 150. Dual Trace 35MHz Solid State. Portable. 8 x 10cm display. With manual.....£200 S.E. LABS SM11. Dual Trace 18MHz Solid State. Portable AC or External DC Operation. 8 x 10cm display. With manual.....£150 TELEQUIPMENT D43. Dual Trace 15MHz. With manual.....£100 TELEQUIPMENT 843. Single Trace 25 MHz. With manual.....£75 EX-MINISTRY CT436. Dual Beam 6MHz. Size 10 x 10 x 16ins. With manual.....£75 NEW PROBES AVAILABLE. Switched x1; x 10.....£11</p>	<p>PROFESSIONAL 9" GREEN SCREEN MONITORS made by KGM for REUTERS. Gives quality 80 x 24 line display/ Composite Video In. Cased. Good Conditiononly £40 each</p> <p>NEW EQUIPMENT HAMEG OSCILLOSCOPES 605. Dual Trace 60MHz Delay Sweep. Component Tester£515 HAMEG OSCILLOSCOPE 203.5 Dual Trace 20MHz Component Tester.....£270</p> <p>BLACK STAR FREQUENCY COUNTERS. P&P £4 Meteor 100-100MHz.....£99 Meteor 600-600MHz.....£126 Meteor 1000-1GHz.....£175 BLACK STAR JUPITOR 500 FUNCTION GENERATOR Sine/Square/Triangle 0.1Hz — 500KHz P&P £4.....£110</p> <p>HUNG CHANG DMM 6010. 3½ digit. Hand held 28 ranges including 10 Amp AC/DC. Complete with batteries & leads. p&p £4.....£33.50</p>
<p>PHILIPS DIGITAL MULTIMETERS 4 DIGIT. AUTO RANGING. Complete with batteries and leads (P&P £5) TYPE PM2517E (L.E.D.).....£75 TYPE PM 2517X (L.C.D.).....£95</p>	<p>ADVANCE AM/FM Sig Gen type SG63 7.5 - 230 MHz.....£75 AVANCE AM Sig Gen type SG62 150KHZ - 220MHz.....£35 LABGEAR COLOUR BAR GENERATOR Type 6037. P&P £5.....£60 LABGEAR CROSSHATCH GENERATOR CM6004. P&P £2.....£15</p>
<p>MULTIMETERS UNBELIEVABLE — AVO 8 MkIV and AVO 8 MkIV. Complete with Batteries & Leads for only.....£85 AVO TEST SET No. 1 (Similar to Avo8 Mk3). Complete with batteries, leads & Carrying Case.....£90 AVO Model 73. Pocket Multimeter (Analogue) 30 ranges. Complete with batteries & leads.....£25 AVO 72 — Similar to above but no AC Current range. With Batteries & Leads.....£18</p>	<p>MARCONI RF MILLIVOLTMETER TF2603. 50KHZ - 1500MHz; 1mV-3V.FSD.....£175 MARCONI ELECTRONIC VOLTMETER TF2604. 20HZ - 1500MHz; AC/DC/OHMS AC 300mV - 300V. FSD.....£95 MARCONI VALVE VOLTMETER TF2600. 10HZ - 10MHz; 1mV - 300V.FSD.....£40</p>
<p>5 1/4" FLOPPY DISK DRIVES TANDON 1/2 Height. Brand New Single Sided Double Density.....£60 Double Sided Double Density.....£100 MPI Double sided, Double Density 80 Track unused.....£100 CHERRY KEYBOARD — SERIAL/ASCII standard QWERTY with numeric pad. New. Cased. With Circuit (P&P £4).....£15 each</p>	<p>AVO TRANSISTOR TESTER TT169 Handheld. GO/NOGO for In-situ Testing. Complete with Batteries, leads & instructions (P&P £3).....NOW ONLY £12 AVO TRANSISTOR ANALYSER CT448. Suitcase style — battery operated. (Batteries not supplied). With informationONLY £20 each</p>
<p>THIS IS A VERY SMALL SAMPLE OF STOCK, SAE Or Telephone for LISTS Please check availability before ordering. Carriage all units £12 VAT to be added to Total of Goods & Carriage.</p>	<p>STEWART OF READING 110 WYKEHAM ROAD, READING, BERKS RG6 1PL Telephone: 0734 68041</p> <p>Callers welcome 9am to 5.30pm Monday to Saturday inclusive</p>

TRAINS OF THOUGHT

To the railway modeller, the equivalent of the Holy Grail is a system that allows independent control of several trains simultaneously on the same layout. The two most frequently encountered methods are command control and cab control.

Command control makes the entire layout permanently live — normally with AC although DC systems have been developed — and each locomotive is equipped with a module which is effectively an on-train controller. This responds to instructions superimposed on the traction voltage by a master control unit.

Probably best known is Hornby's Zero-1 system. This makes extensive use of Texas Instruments TMS-1000 4-bit microprocessors in both the modules and the master control units. Up to 16 trains can be con-

trolled at any of 16 speeds, forwards and reverse. A large number of trackside accessories can also be operated, drawing both power and data requirements from control codes superimposed on the square-wave traction supply.

In contrast to the advanced digital techniques employed by Hornby's system, the Airfix MTC (Multiple Train Control) uses some subtle analogue circuitry. Each on-train module is essentially a radio receiver responding to a pulsed radio-frequency carrier superimposed on the sine-wave traction supply. Again up to 16 trains can be used (though only four at a time), the 16 frequencies being digitally synthesised in the master control. Train direction is determined by the polarity of the traction supply during the RF pulses and speed by the duration of the pulses.

Both systems are reliable and easy to install, except that it can be awkward finding room for the modules in some smaller model

locomotives. A disadvantage is that the system is not compatible with conventional operation — an unmodified locomotive will emit real smoke in a matter of seconds if placed on a live command control track. To adopt the system you must make the changeover and modify all your locomotives at once.

Switching Cabs

The alternative is cab control. In its simplest form this is not electronic but simply an arrangement of switches. The layout is divided into a number of control zones each of which can be connected by switches to any of several conventional (rheostat or electronic) controllers. As the trains progress around the layout passing from zone to zone, the switches are thrown manually so that each train keeps the same controller (or cab) for the whole of its journey.

However, with the availability of reliable train detection systems (discussed in the second article of this series) an auto-

mated version of cab control is feasible. This is called progressive cab control. Its implementation is tedious rather than difficult, requiring banks of logic circuitry (the complexity is proportional to the square of the number of controllers), but it should be possible to arrange for a micro-computer to perform the bulk of the logic. The computer would need a large number of input and output ports — an Apple IIe or BBC Micro with backplane suggest themselves — and also an interface unit containing the train detectors and relays to switch the controllers between sections.

Cab control systems, whether manual or automatic, result in festoons of spaghetti beneath the baseboard and debugging is a nightmare! By contrast, the two-wire command control system is utter simplicity. But an advantage of cab control is its compatibility with conventional control, enabling it to be extended across a layout zone by zone as time and money permit.

Roger Amos

OPEN CHANNEL

A number of press releases landed on my desk recently from British Telecom, announcing the launch of their advanced digital communications service. The service, says the press release, sets a new standard in business communications, with such benefits as:

- an A4 page sent by facsimile in six seconds
- photographic-quality colour pictures on videotex
- slow-scan television
- greater reliability

The new service is called integrated digital access (shortened, thankfully, to IDA). It is part of British Telecom's advancing programme of communications technology which will eventually lead to a digital telephone network providing all these facilities to every business or household in the nation. The complete network is called the integrated services digital network (shortened, again thankfully, to ISDN), and will be accessed by the user through the IDA service. So, you'll have gathered, British Telecom wants every user to have an IDA point through which all digital communications facilities will be routed, in much the same way that existing telephone points allow facilities such as computer

communications (via modems), videotex services (Prestel), answering-phones etc.

IDA will be operated initially from the first System X exchange, opened recently at Baynard House in the City of London. It will cover Euston, the West End, the City and Southbank in London as well as parts of Bracknell, Bristol, Croydon, Reading and Slough. More local exchanges, in London, Milton Keynes, the Midlands and South Lancashire, are expected to be linked in to the network by the end of the year. By the end of 1987, British Telecom hope to have IDA available at 190 centres throughout Britain.

So what advantages are being forced upon us? Well, in the ISDN all communications are digital. That is, the actual telephone which the user speaks into and listens to converts the analogue audio signals directly into digital ones ready for transmission through the network. Contrast this with the existing telephone network where most signals are analogue and only some (over main trunk routes) are digitised for part of the journey. In theory at least, a digital network should provide a more reliable, higher quality and, best of all for the user, a cheaper service.

Anyway, that's the theory. And certainly, I for one, always thought this to be the case. I was looking forward to high quality speech and data communications and was ready to apply for an access point as soon as it

became available (I live in one of those areas which is to get the service by the end of the year). I'm pretty fed up with having to shout down my telephone mouthpiece so that the other party can hear what I'm saying whenever I make anything other than a local call. As a freelance journalist I would also find the data transmission aspects of the network useful to download copy to editors, ready for publication. Perhaps readers have similar feelings. However, the same press release which brings the good news about IDA also gives prices — and these aren't so good.

For example, the cheapest IDA access consisting of a digital telephone with on-hook calling, (known as version NTE1) a keypad, a display, and one data port which can be configured to support a variety of terminals, will be installed for £890. It then costs £710 per year to rent. And if that's not all, customers outside the London, Birmingham, or Manchester areas will be subject to an out-of-area connection charge of either £350 (within the 'A' rate call charge area) or (like me) £700.

Excuse me for being so pessimistic, but if British Telecom thinks it can sell ISDN and IDA to potential customers at these prices, I believe it will have to think again. If the economic benefits of a digital network which British Telecom will derive (ie, lower maintenance costs, lower call costs etc) can't be

passed on to the customer in the form of cheaper rentals and reasonable installation charges, then I can't see many potential customers buying the service. I'll certainly shout down a scratchy analogue line and post my copy to editors if it means I don't have to pay telephone bills of that order. British Telecom can, as the saying goes, stick it!

And There's More!

If you're a typical telephone user and use the 'phone quite regularly, you'll probably just dial a number you want to contact without thinking where the call is going to. After all, even calls to the far end of the country have a cost per unit of only about 5p. At standard rate times this amounts to only about 16p per minute. However, bear these two numbers in mind: 0860 and 0836. If the number you're about to ring is prefixed by either of these, then consider carefully the cost of dialling before you actually do it. These two prefixes indicate numbers that belong to cellphones, ie, telephones which are linked by a radio connection on one of the two existing cellular radio telephone systems. The cost per unit charge when making a call to a cell phone remains the same, but the call is charged at the same rate as it would be if it were a call to the Irish Republic, about 43p per minute for standard rate calls!

Its for yoo-hoo. I'll just reverse the charges!

Keith Brindley

SCRATCH PAD

by Flea-Byte

My most profound apologies for my unexplained absence last month. Many of you may have thought that, like most of the other giants of British electronics, I too had been swept under by the encroaching tide of Japanese goodies, the fickle dollar exchange rate, the ridiculous postures that pass for economic policies in the Cabinet and the general subterranean level of competence among that noble breed - the British manager. No such luck! While the share tumbled, companies teetered, the Daily Maxwell played footsie with Uncle Clive and Sir Kenneth Corfield topped his recent failure to win the British Electronics Personality of the Year award by an even more astonishing failure to steer STC through the stormy seas of his own chairmanship,

good ole Flea-byte was taking a well-earned rest from the solder and the sweat in a small but reasonably well-appointed guest house somewhere on the Costa Packet.

Fortunately, the Sun journalists were too busy identifying miscreants evading the formerly long arm of the law to recognise me. Almost certainly, were I not such a master of disguise, I would have been whisked back to the height of the English 'summer' to rescue Thorn-EMI, STC, GEC, Acorn and Sinclair Research - all of whom, should it have escaped your notice, sailed perilously close to the rocks during the balmy July days.

Now refreshed after many pleasant days spent discussing tax shelters with a man who introduced himself to me as 'A. Bank Robber', I have returned to the fray. To avoid misunderstanding, I must make it clear that, following Sir Kenneth's untimely departure from the helm of STC, I shall not be available to mount one of the economic rescues for which I am so deservedly unknown.

It's not that I have any principled objection to helping STC out of a scrape. On the contrary,

Sir Kenneth Corfield's chairmanship has resulted in this company becoming a flagship for British industry. Among his more notable achievements - to be counted with the acquisition of ICL and the promise that shareholder dividends would be maintained at a time when share prices were going through the floor and profits were disappearing into the negative zone - was his audacious acceptance of a 48% pay rise in 1984. In case you think the labourer should be worthy of his hire, let me tell you that Sir Kenneth's salary at that point amounted to £297,000 a year. Any company that pays that sort of money is alright by me!

No, my reason for not wishing to shoulder the burden of STC's undoubted recovery is simply that I feel it would be far too partisan of me. After all, there are so many companies in need of a guiding hand that to devote all my considerable talent to just one would, I fear, be selfish. Thorn EMI's downturn in profits had already led to the departure of chairman Peter Laister before Corfield announced his resignation. GEC have remained profitable, thanks largely to their

legendary cash-mountain (a billion or more pounds just collecting interest). Even so their recent profit announcement revealed disappointing figures. Acorn and Sinclair seem to have one foot permanently inside the bankruptcy court.


Looking at the way all this news has given the entire British electronics industry the shakes, duty dictates that I remain on the side-lines, egging the teams on to greater things. Readers can rest assured that Flea-byte will not take another holiday until confidence is restored and our electronics industry returns to its former glory. Well....

Crystal Balls

I notice that a company in North London has just launched the first all-British, electronic time machine. Anthony Bassett of NumberOne Electronics claims that the machine generates 'electromagnetic waves' which, apparently, encourage visions of the past to spring before your 'third eye' (that's the one we all have in the middle of our foreheads, you know!). Such machines have, of course, been known for some

Master Electronics - Microprocessors - Now! The Practical Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.

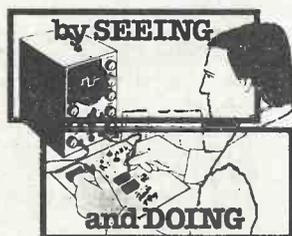

New Job? New Career? New Hobby?

SEND THIS COUPON NOW

FREE! COLOUR BROCHURE
Please send your brochure without any obligation to

OR TELEPHONE US 062 887 2598
OR TELEX 22758 (24 HR SERVICE)



NAME _____ I am interested in

ADDRESS _____ ELECTRONICS

_____ MICROPROCESSORS

_____ RADIO AMATEUR LICENCE

_____ CITY & GUILDS EXAMS

Other Subjects _____

British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ 14 0HS

PLAYBACK PLUS

The British Music Fair

The British Music Fair was open to the public for the first time this year, instead of being confined to the trade. To mark this it was held at Olympia 2, normally the site of computer shows and the Ideal Home Exhibition, in early August.

The big attraction was that you could try out the instruments. Anything from a penny whistle I said. I think I can avoid penny whistles.

Although there were plenty of instruments to try, and in some cases soundproof booths to try them in, you had to wait your turn, and compete with other people using the same demonstration room. Some stands had thoughtfully provided headphones. A friend of mine sensibly took a headphone amplifier and used that all day. The drum synthesizers in the lower hall were definitely not in a soundproof booth! It was noisy, so I wouldn't make a final decision about parting with green stuff there unless I had more patience than I actually have.

Even so there were a number of interesting new electronic instruments and sound modifying boxes there. For yonks I have wondered why musicians on stage don't make more use of radio microphones and guitar transmitters. Maybe their popularity will increase with the introduction of an economically priced guitar transceiver by TOA. They also do a more expensive version with two receiving antennas to remove the problem of RF dead spots. Trantec have produced an even lower cost one, priced at a mere £300.

Home recording addicts are being well looked after these days. Up to four instruments can be recorded at a time, it says, on the new Teczon Multi Dub 4x4 home recorder, and up to thirty three instruments recorded by bouncing from one track to another and overdubbing. It costs £492 from John Hornby Skewes. They were also showing off an Audio Technica machine called the AT-RMX64, four track, six input cassette recorder. Being more steeply priced at £1100, it's probably aimed at professionals or very serious home recordists.

There were lots of new amplifiers, but the most interesting innovation is the Peavy Digital Energy Conversion Amplifiers. Does this mean class D (switched

time - but they only used to work during the summer months when the television companies transmit nothing but repeats. By the way, Number Ones's previous big seller is a crystal ball or, in the technical jargon, gas-filled light-bulb.

* * *

A Knight To Remember

The saga of Sir Clive continues unabated, I'm afraid. Undaunted by the Daily Maxwell's strange will-he? won't-he? dance routine with Sinclair Research, unruffled by a 'Which?' report on the C5 which demonstrated that it would get you from A to B, as long as B was downhill and downwind of A and as long as the traffic fumes and towering juggernauts didn't get you first, the pert, ginger-haired genius is reported to have been observed setting up a new company. Another new company.

My usual reliable sources in the Goat and Feathers tell me that this one will be different. Sinclair Research's Nigel Searle says that, 'the new company will exist to provide services to Sinclair Research, which will primarily be

the availability of Sir Clive himself.' Sir Clive, of whom it has been said that availability is his strongest suit, is currently reassuring the world that the Maxwell's departure from the scene is probably a blessing in disguise. Apparently, several other parties are interested in the possibilities Sinclair Research holds out for losing a great deal of money. Dixons - the high street store - have just agreed a deal with Sinclair and the Spectrum is selling well. In the Goat and Feathers, we nibble on such announcements with our beer - they're saltier than crisps.

Confirmation of Sir Clive's foresight, however, can be obtained from the gist of a speech he made earlier this year to the Radio, Electrical and Television Retailers Association (RETRA). The assembled high street dealers heard him say they could sell as many C5's as video recorders, that his pocket TV would soon be selling over 2 million units a year and that the future of the computer market was a portable with 'a real TV screen'. Sir Clive thinks the Japanese have got it all wrong with their concentration on LCD screens. 'The Japanese will fail,' he said, 'because they have con-

tinued to back LCDs.' At Sinclair Research, they have big plans for the 'no compromise' portable: pocket-sized, no doubt, featuring a high resolution colour monitor and all powered by a single PP3. Well, where would we be if it wasn't for our dreams?

* * *

Old Guard?

The editor tells me an appealing little story about Conservative Central Office, whom he phoned in order to get hold of some pictures to illustrate an ETI article. The pictures in question were photographs of John Butcher, Parliamentary Under Secretary at the Department of Trade and Industry, and Geoffrey Pattie, Minister with special responsibility for Information Technology. The photograph of Butcher was not too much of a problem, despite the fact that it arrived with a rubber-stamp mark threatening to engulf the Under Secretary. Pattie was another matter, however. The man at Central Office wasn't even sure they had a photograph of him. When at length he managed to dig one up it proved to be ten years old, badly focused and scratched.

The Minister was shown in pre-IT days - desporting himself with a small group of Tories from the Chertsey constituency party. Some might say this demonstrates the low regard in which Pattie and, by association, Information Technology are held by the Conservative Party. I prefer to think it has nothing to do with IT or Pattie's position, but rather reflects the man. Butcher, you see, is young, reasonably good-looking and decorated with a full head of hair. Poor Geoffrey Pattie, on the other hand, is old, bald and distinctly odd of aspect. Not at all the image of a Thatcher man!

* * *

Say That Again

Wading through the accumulated press releases on my desk, I came across this shining example of English as she is spoken: This JMS Drum Unit produces sounds which are indistinguishable, and in some cases better, than the real thing. Presumably, this means that some real drum sounds are indistinguishable from their synthesized equivalents and, at the same time, noticeably inferior. And now for the grammar...

mode) we wonder? They claim 90% efficiency and are applying for a stack of patents on the design. Odd, because class D was old when I was at college (many years ago). The DECA 700 and DECA 1200 amplifiers include compression circuits, overload protection and no measurable transient intermod distortion or slew rate distortion.

Then there's the Accessit Aphex aural exciter, a low cost domestic version of a professional product I had never even heard of. Apparently it makes any track of an instrument stand out on the recording, in a way which cannot be simulated by even the most sophisticated equalizer. How it works is secret, but my guess would be some kind of non-linear amplitude response, or perhaps some kind of digitally controlled attack enhancement. It would be interesting to try one out with a variety of waveforms and a scope...

Casio have produced a four channel sequencer with enough memory for 3600 notes in the manual recording mode (and half this in the real time recording mode). It's MIDI compatible, with a metronome built in for real time recording, and costs £295. Their newest, biggest synthesizer has a similar, eight track sequencer built in.

The Roland SRV-2000 reverb unit also offers MIDI, and it can work effectively in conjunction with the Yamaha synth mentioned below. It costs about £1400, and is rather more than your average reverb stuffed into a 100 watt combo. It allows you to program room dimensions, wall covering effects (damping), as well as special effects such as gated reverb. Thirty two different sets of parameters may be stored in memory, and activated via the MIDI connections.

Yamaha have a number of new products. The DX21 programmable synthesizer is one such - the spec reads like that of a computer, but one of the main features is that it is organised so that the 'non-computerate' can make good use of it. In common with the majority of new electronic instruments, it has MIDI. Among many sounds, it can simulate a guitar. Unlike other guitar synth units, the effect of string bending on only one string out of a chord can be simulated. Other synths just let you frequency shift the whole lot.

Let's hope the experiment pays off and the Music Fair stays open to the public. It's only three days out of six, after all - and for £3 you can see a great deal if you are organised.

Andy Armstrong

It's easy to complain about advertisements. But which ones?

Every week millions of advertisements appear in print, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints.

If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code.

Then, if an advertisement bothers you, you'll be justified in bothering us.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 2 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

Lineage:

45p per word (minimum 15 words)

Semi Display: (minimum 2 cms)

£11.80 per single column centimetre

Ring for information on series bookings/discounts

All advertisements in this section must be prepaid.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699 Ext 323

Send your requirements to:
Caroline Faulkner
ASP Ltd.,
1 Golden Square,
London W1.

E
L
E
C
T
R
O
M
A
R
T

LANCASHIRE

ETESON ELECTRONICS

E.E. 15B Lower Green,
Poulton-le-Fyde, Blackpool
Tel: (0253) 885107

Open: 9.30am-12.30, 1.30-5.30. Closed Wed & Sun.
Electronic Component Specialists.

KENT

ONE STOP ELECTRONICS

126a Maidstone Rd., Rochester ME1 3DT
Tel: 0634 400179

Open 7 days a week.

Test equipment, telephones, two-way radios, repairs,
cellular radio and components.

Call and browse anytime except Wednesday afternoon.

MERSEYSIDE

PROGRESSIVE RADIO

93 Dale Street. Tel 051 236 0982
47 Whitechapel, Tel 051 236 5489
Liverpool 2

THE ELECTRONICS SPECIALISTS'

Open: Tues-Sat 9.30-5.30

E
L
E
C
T
R
O
M
A
R
T

COMPUTER
ADD-ONS

*** TANGERINE OWNERS ***
6809 CPU board, Flex O/S, 14K
RAM card overlay Tanex, 32K-
RAM-EPROM-BATTERYBACKED
BOARD address switchable page
selectable all available from
STOCK also all the hard to get
Tangerine chips in stock, loads of
FLEX programmes, power sup-
plies, Access/Barclaycard, s.a.e.
fordetails. Ralph Allen Engineer-
ing, Forncette-End, Norwich,
NR16 1HT. Tel: 095389 420.

**COLOUR GRAPHICS MEMORY
ARRAY.** Professionally designed,
fully buffered, on-board shift
registers 4/8 planes 64K x 16/8
bits (4164). Unpopulated PCB +
App. Circuits £125.00. SAE 65
Northgate St., Colchester, Essex
C01 1EY.

WANTED

TURN YOUR SURPLUS trans-
istors, IC's etc into cash. Con-
tact Coles Harding & Co., 103
South Brink, Wisbech, Cambs.
Tel: 0945 584188. Immediate
settlement.

THREE TMX 9909NL Floppy Con-
troller chips in working order any
reasonable price paid. Tel: 0235
31436. Mr I. Nimmo after 6.00pm.

SERVICES

BOOKS & PUBS.

**WHO NEEDS A LOGIC
ANALYSER?** Illustrated guide
shows you how to decode microp-
rocesses Buff signals using a stan-
dard oscilloscope. Price £4.99 +
40p P&P. Crossed cheques/P.O.'s
to:- Mr M Rimmer 20, Duddle Lane,
Walton-le-Dale, Preston, Lancs
PR5 4UD.

PARAPHYSICS JOURNAL
(Russian translation); psycho-
tronics, kirlianography, heli-
phonic music, telekinetics.
Computer software. S.A.E.
4 x 9", Paralab, Downton,
Wiltshire.

HUNT ELECTRONICS 1985.
COMPONENTS CATALOGUE.
send 50p in stamps. Refunded
with first order, to P.O. 57, Derby,
DE6 6SN. Tel: (0283) 703071.

SERVICES

JBA ELECTRONICS

Specialists in manufacture and
design of:
Microprocessor, Telemetry, and
Audio-based systems.

UNIT 9,

BRECON INDUSTRIAL ESTATE,
BRECON, POWYS, S. WALES

Tel: (0874) 2563

LABEL IT!

PROFESSIONAL QUALITY LABELS AND
BADGES MADE TO ORDER
Low cost • Various colours and styles •
Engraved by us • Very hard-wearing
waterproof plastic or metal
Fast efficient service

Write to Rob Thomson for FREE details

THOMSON

Electronics
Radio Communication Specialists
Basement Office, 5 David Place,
St. Helier, Jersey. Tel: 0534-75170

DESIGN SERVICES, microp-
rocessor, special interfaces, ana-
logue, digital, signalling, alarm
systems, PCB design and artwork.
Prototype and small batch pro-
duction. **ALAB ELECTRONICS.**
Grantham (0476) 860089.

FREE PROTOTYPE of the
finest quality with every P.C.B.
artwork designed by us. Compe-
titive hourly rates, and high
standard of work. Halstead
Designs Limited. Tel: halstead
(0787) 477408.

ETI. VCDO authentic musical in-
struments in EPROM £9.95. O.
Lucas, 45 Fotherby Ct., Maiden-
head, Berks SL6 1SU.

P.C.B. DESIGN and Layout.
Manually taped artwork pro-
fessionally produced at competi-
tive prices. James Gledhill.
01-674-8511.

PCB DESIGN AND LAYOUT.
Contact Elpincrest Ltd, 46 Argyle
St., London N18 2PP. Tel: 01-807-
9276.

Quantum
Technology Products

From

Airwave Communication Ltd.

Manufactures to your design, specification or brief.

From bare boards to systems.

One offs, prototypes and small batch runs.

Projects, Repairs, P.C.B. Service

S.A.E or Phone for details.

Unit 1e

Barbican Rise, Looe

Cornwall PL13 1QQ

(05036) 4739 or 3407

NO JOB
TOO SMALL

NO PLACE
TOO FAR

ALARMS

ALARMS

FREE BOOKLET
on
BURGLAR ALARMS
with
LOWEST U.K. DIY PUBLISHED PRICES
PHONE OR WRITE FOR YOUR COPY
051-523 8440
AD ELECTRONICS
217 WARBRECK MOOR
AINTREE, LIVERPOOL L9 0HU



LOWEST PRICED TOP QUALITY fire and intruder alarm equipment, etc. S.A.E. for catalogue. Security Services, 162 High St., Hythe, Kent CT21 5JR.

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- **LOWEST DISCOUNT PRICES**
- **HIGHEST QUALITY EQUIPMENT**
- **FREE DIY DESIGN GUIDE**
- **FULLY ILLUSTRATED**
- **MICROCHIP CIRCUITRY**
- **QUICK DESPATCH SERVICE**
- **FULL INSTRUCTIONS**

SEND SAE OR PHONE
CTEC SECURITY, Dept E1
Stephens Way, Goose Green,
Wigan WN3 6PH
Telephone (0942 42444)

Trade Enquiries Welcome

POWER SUPPLIES

150W SWITCHMODE PSU + 5V @ 8.4A. + 12V @ 4.8A. + 24V @ 1.7A. - 12V @ 0.2A. Perfect working order over £70 in Henries Radio £29 + Carr. 0245 59027 after 6.00pm.

MISCELLANEOUS

HEATHKIT U.K. Spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewksbury, Glos. Tel: 0684 73127.

COURSES

CONQUER THE CHIP . . . Master modern electronics the **PRACTICAL** way by **SEEING** and **DOING** in your own home. Write for your free colour brochure, now to: British National Radio & Electronics School, P.O. Box 7, Teignmouth, Devon TQ14 0HS.

FOR SALE

100W AMPLIFIER — £9.95 built or use the same board for 50W, 150W, 200W into 4 or 8 ohms, etc., by using alternative output transistors and P.S.U. S.A.E. for full details to:- ESS Amplification, 269 Hessle Road, Hull.

SHEETMETAL FOLDERS. 24" x 166" vice or bench model £50 leaflet 01-890-7838 day/eves.

STEREOAMPS 120 WATT (60+60) . . . Case-D.I.N. sockets anc controls . . . 9.40v/smoothing. . . Protected outputs 3/15 OHM tested and diagrams £10/inc . . . KIA 8 Cunliffe Road, Ilkley . . .

MARCONI TF1058 UHF/SHF Signal Generator with manual, Marconi THF 1HRE distortion factor meter, Solartron AWS 51A lab. amp 15HZ-350KHz. Venner SH1035/ADV counter timer 0.01ms (10KHz). 10 sec (0.1Hz). Ex RAF sweep scope + RF signal generator. Offers? K. Jones. Tel: 01-689-8722.

PRIVATE SALE. Ten years ETI. 1974 - 1983 £5.00 per twelve plus postage. Michael, 465 Blackstock Road, Sheffield S14 1LB.

TECTRONIX OSILLOSCOPES. 8-trace 19 MHz Dual-Beam type 55 1 £235. 556 Dual-beam 4-trace 50MHz Delay sweep £345. 54M Dual trace 50MHz Delay sweep display — switching £250. 585A Dual-trace 85MHz Delay-sweep £250. 502A Dual-beam 100 microvolts 1MHz £105. Philips type 3212 dual-beam 25MHz £335. Storage oscilloscopes, spectrum analysers, semi-conductor curve-tracers, manuals, plug-ins, spares, Nova-3 mini-computer. Other test equipment. Ring 01-868-4221.

EQUIPMENT

ESR

13a Station Road
Cullercoats - North Shields
Tyne & Wear - NE30 4PQ
Telephone 091 2514363


TRANSISTORS - RESISTORS - CAPACITORS - DIODES - LED'S - SCR'S - ICS - VOLTAGE REGULATORS - DISPLAYS - AUDIO & EDGE CONNECTORS - VERO/PCB'S - INSTRUMENT CASES & BOXES - POWER AMPLIFIERS & MODULES - MICROPHONES & STANDS.

WRITE OR PHONE FOR FREE PRICE LIST.

YOU ARE NEVER FAR FROM A

PARTRIDGE COMMUNITY BROADCAST MIXER

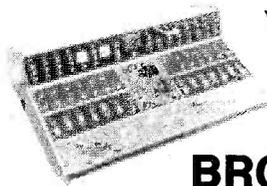56 Fleet Road, Benfleet, Essex SS7 5JN
03745 3381 or 03745 3256 for full details




GRIPMATE

NEW! ELECTRONIC ENGINEERS NEED
'EXTRA HANDS' FOR SOLDERING GLUEING AND ASSEMBLING

This essential compact tool comes complete with 4 croc-clip flexi-arms to hold components positively and rapidly with infinite positioning.....

ONLY **£4.85** USEFUL ACCESSORIES....
48mm 2.5x MAGNIFIER FLEXI-ARM £2.50
MAGNET FLEXI-ARM £1.50
ALL PRICES INCLUDE VAT + POST + PKG

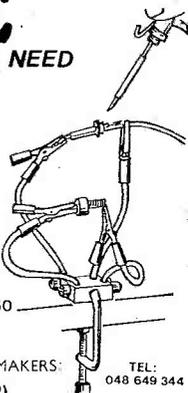SEND NOW! CHQ/PO OR SAE DETAILS DIRECT FROM THE MAKERS:
KEMPLANT LTD (DEPT. 2)
DURFOLD WOOD, PLAISTOW, BILLINGSHURST, WEST SUSSEX RH14 0PN



TEL: 048 649 344

TEST EQUIP.

TOP PRICES PAID for surplus electronic test equipment
ALWAYS a good selection of **SIG-GENS, METERS, and SCOPES** for sale.
Phone 0920-871430

REPAIRS

POWER SUPPLY REPAIRS. We offer a fast repair service on most makers of DC power units in the range of 1 amp to 30 amps. Crow bars etc, also fitted. Full details ring: **0536 743 496.**

Flanger/Chorus parts re E.T.I. Jan 84
Reverb Springs, Pedal Cases, Dummy Keyboards, Microphones, Audioleads and adaptors, clearance bass effects pedal and many more items.
Send S.A.E. for free price list to:-
SOLAR SOUND LTD
18 Berton Way
Croxley Green
Rickmansworth
Herts WD3 3QA

PRINTED CIRCUIT BOARDS one-offs and small quantities supplied. Artwork carried out. Fennel Industrial Electronics, 54 Watling Street, Nuneaton, Wars CV11 6JL. Tel: 0203 382296.

More This Month at Maplin

Colour-coded IDC cables

- 16-way (XR80B) ONLY 32p per metre.
- 20-way (XR81C) ONLY 40p per metre.
- 26-way (XR82D) ONLY 54p per metre.
- 34-way (XR83E) ONLY 70p per metre.
- 40-way (XR84F) ONLY 82p per metre.
- 50-way (XR85G) ONLY 99p per metre.

4-way flat flexible telephone lead (XR86T) ONLY 18p per metre.

Stepper motor 48 steps/rev, 12V 0.13A per phase, 4-phase unipolar, 57g, working torque 8mNm max. ONLY £9.95 (FT73Q).

Driver chip for motor: SAA1027 ONLY £3.75 (QY76H).

★SAVE★ 1 Kit containing everything you need: motor, SAA1027, data sheet and passives ONLY £13.35 (LK76H).

Sounds Terrific



Professional Quality High Power Loudspeakers featuring:

- ★ Virtually indestructible high-temperature voice-coil reinforced with glass-fibre.
- ★ 100% heat overload tolerance.
- ★ Advanced technology magnet system.
- ★ Rigid cast alloy chassis.
- ★ Linen or Plastiflex elastomer surrounds.
- ★ 5-year guarantee (in addition to statutory rights).


Prices from £18.95.

Send S.A.E. for our free leaflet XH625.

Top Ten Kits




THIS/MONTH	LAST	DESCRIPTION	CODE	PRICE	BOOK
1.	(1)	Live-Wire Detector	LK63T	£2.95	14XA14Q
2.	(2)	75W Mosfet Amp.	LW51F	£15.95	Best E&MM
3.	(3)	Car Burglar Alarm	LW78K	£7.49	4XA04E
4.	(7)	Logic Probe	LK13P	£10.95	8XA08J
5.	(5)	U/sonic Intruder Dctcr	LW83E	£10.95	4XA04E
6.	(4)	PartyLite	LW93B	£10.95	Best of E & MM
7.	(6)	8W Amplifier	LW36P	£4.95	Catalogue
8.	(-)	Noise Gate	LK43W	£9.95	Best E&MM
9.	(9)	Computadrum	LK52G	£9.95	12XA12N
10.	(-)	DXer's Audio Processor	LK05F	£9.85	7XA07H

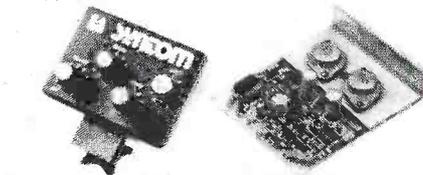

Over 100 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.

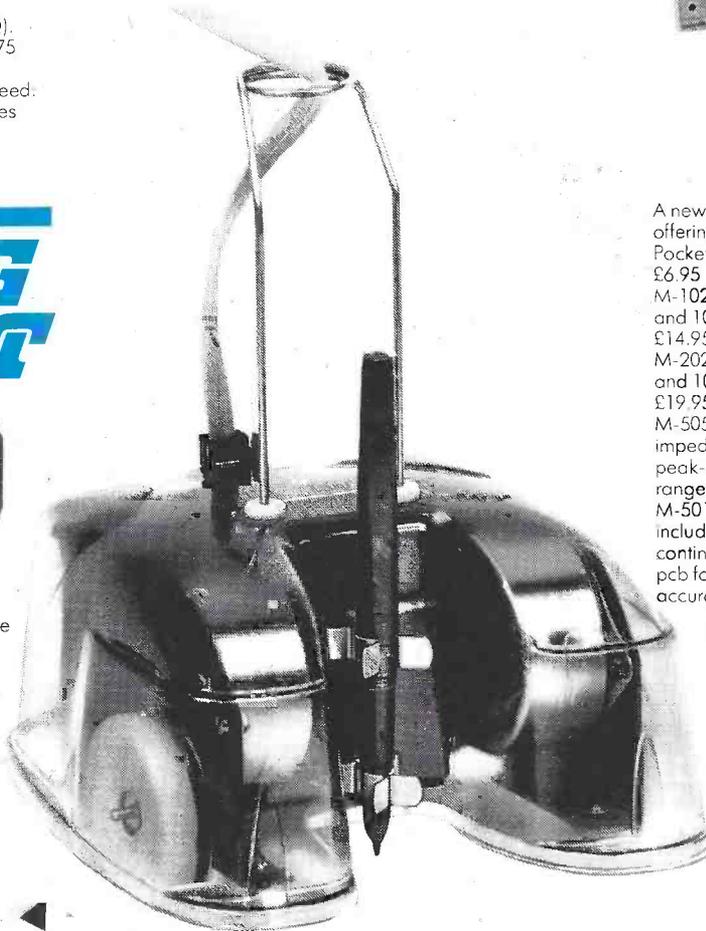Is it a turtle? Is it a robot? Is it a buggy? Yes! it's Zero 2.



- May be used by any computer with RS232 facility.
- Stepper Motor controlled.
- Half millimetre/half degree resolution.
- Uses ordinary felt-tip pens.
- Built-in 2-tone horn, line-follower. LED indicators.

The Zero 2 Robot is the first truly micro robotic system available and remarkably it costs less than £80. Complete kit (only mechanical construction required) £79.95 (LK66W). Full details of power supply and simple interfacing for BBC, Commodore 64 and Spectrum, in Maplin Magazine 15 price 75p (XA15R).

MAPLIN

MAPLIN ELECTRONIC SUPPLIES LTD

Mail-order: P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 552911

SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356-7292.
- LONDON 159-161 King Street, Hammersmith, W6. Telephone: 01-748 0926.
- MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
- SOUTHAMPTON 46-48 Bevois Valley Road. Tel: 0703-225831
- SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex. Telephone: 0702-554000. *Shops closed all day Monday.*

More Choice In Multimeters



A new range of very high quality multimeters offering truly amazing quality at the price. Pocket Multimeter, 16 ranges, 2,000Ω/V DC/AC £6.95 (YJ06G)

M-102BZ with continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95 (YJ07H)

M-2020S with transistor, diode and LED tester and 10A DC range, 27 ranges, 20,000Ω/V DC £19.95 (YJ08J)

M-5050E Electronic Multimeter with very high impedance FET input, 53 ranges, including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95 (YJ09K)

M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated pcb for long-term reliability and consistent high accuracy (0.25% + 1 digit DCV) £42.50 (YJ10L)



The Maplin Service

All in-stock goods despatched same day for all orders received before 2.00 pm.

All our prices include VAT and carriage (first class up to 750g).

A 50p handling charge must be added if your total order is less than £5.00 on mail-order (except catalogue).



Phone before 2.00 p.m. for same day despatch.

Top Ten Books

1.	(1)	Loudspeaker Enclosure Design and Construction	WM82D	£3.25
2.	(4)	Mastering-Electronics	WM60Q	£4.70
3.	(3)	Remote Control Projects	XW39N	£2.75
4.	(9)	How to Build Your Own Solid State Oscilloscope	XW07H	£2.10
5.	(5)	International Transistor Equivalents guide	WG30H	£3.25
6.	(8)	How to Design and Make Your Own PCBs	WK63T	£2.05
7.	(2)	Power Supply Projects	XW52G	£2.10
8.	(-)	Radio Control for Beginners	XW66W	£1.95
9.	(-)	How to Use Op-amps	WA29G	£2.45
10.	(7)	Electronic Synthesiser Projects	XW68Y	£1.95

All offers subject to availability.

Prices firm until 9th November 1985.