

# Be it Known

*THAT* the reader has satisfied the ordinances and regulations of the Magazine and in the month of October 1988 anno Domini has been admitted entry to the

## Careers and Education Special

having satisfied the examiners in the subjects

*Electronics in the Classroom*

*Post A-level courses - full list*

*Careers - what the companies want*

and having completed the required laboratory projects

*Beginners 1st. Class bicycle siren*

*Hi-Fi Peak Programme Meter*

*Powerful Air Ioniser*

Signed and sealed this second day of September in the year of our Lord nineteen hundred and eighty eight. ❖



# OMP POWER AMPLIFIER MODULES

★ PRICES INCLUDE V.A.T. ★ PROMPT DELIVERIES ★ FRIENDLY SERVICE ★ LARGE S.A.E. 28p STAMP FOR CURRENT LIST

## OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

Supplied ready built and tested.



**OMP 1000 Mk II Bi-Polar** Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens for Max. output 500mV at 10K, Size 355 x 115 x 65mm. PRICE £33.99 + £3.00 P&P.



**OMP MF100 Mos-Fet** Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.




**OMP MF200 Mos-Fet** Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 150 x 100mm. PRICE £62.99 + £3.50 P&P.



**OMP MF300 Mos-Fet** Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 147 x 102mm. PRICE £79.99 + £4.50 P&P.

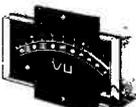NOTE: Mos Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order Standard or P.A.



**Vu METER** Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.F.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 - 50p P&P.

## BURGALAR ALARM

Better to be 'Alarmed' than terrified. **Thandar's famous 'Minder' Burglar Alarm System.** Superior microwave principle. Supplied as three units complete with interconnection cable. FULLY GUARANTEED.

**Control Unit** - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.

**Indoor alarm** - Electronic swept freq siren 104dB output.

**Outdoor Alarm** - Electronic swept freq siren 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £138.00. Usual Price £228.85. **BKE's PRICE £89.99 + £4.00 P&P**

Why buy a collection of self assembly boards!

IDEAL for Work-shops, Factories, Offices, Home, etc. Supplied ready built.



## OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" x 15" x 12". Watts R.M.S. per cabinet. Sensitivity 1W 1mtr dB.

**OMP 12-100 Watts 100dB. Price £149.99**

**OMP 12-200 Watts 102dB. Price £199.99**

per pair. Delivery Securicor £8.00 per pair



## OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. Three models (Ratings R.M.S. into 4 ohms). Input Sensitivity 775mV. MF200 (100 + 100)W. £169.00 Securicor MF400 (200 + 200)W. £228.85 Delivery MF600 (300 + 300)W. £322.00 £10.00

## 1 K-WATT SLIDE DIMMER

- Control loads up to 1Kw
- Compact Size 4 3/4" x 1 1/2" x 2 1/2"
- Easy snap in fixing through panel cabinet cut out
- Insulated plastic case
- Full wave control using 8 amp triac
- Conforms to BS800
- Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.

PRICE £13.99 - 75p P&P

## LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S. Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E. (28p) for free details.

### POWER RANGE

8" 50 WATT R.M.S. Hi-Fi/Disco.  
20 oz magnet. 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea.  
12" 100 WATT R.M.S. Hi-Fi/Disco.  
50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £28.60 - £3.00 P&P ea.

### McKENZIE

12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco.  
2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £29.99 + £3.00 P&P ea.  
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.  
Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £31.49 + £3.00 P&P ea.  
15" 150 WATT R.M.S. C15 Bass Guitar/Disco.  
3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £57.87 + £4.00 P&P ea.  
10" 60 WATT R.M.S. 1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.  
2" voice coil. Res. Freq. 75Hz. Freq. Resp. to 7.5KHz. Sens. 99dB. PRICE £19.99 + £2.00 P&P  
10" 200 WATT R.M.S. C10200GP Guitar, Keyboard, Disco.  
2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 101dB. PRICE £44.76 + £3.00 P&P  
15" 200 WATT R.M.S. C15200 High Power Bass.  
Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. PRICE £62.41 + £4.00 P&P  
15" 400 WATT R.M.S. C15400 High Power Bass.  
Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB. PRICE £89.52 + £4.00 P&P.

### WEM

5" 70 WATT R.M.S. Multiple Array Disco etc.  
1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £22.00 + £1.50 P&P ea.  
8" 150 WATT R.M.S. Multiple Array Disco etc.  
1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £32.00 + £1.50 P&P ea.  
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.  
1" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £36.00 + £2.00 P&P ea.  
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.  
1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £47.00 + £3.00 P&P ea.

### SOUNDLAB (Full Range Twin Cone)

5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.  
1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £9.99 - £1.00 P&P ea.  
6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.  
1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 - £1.50 P&P ea.  
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.  
1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 - £1.50 P&P ea.  
10" 60 WATT R.M.S. Hi-Fi/Disco etc.  
1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 15KHz. Sens. 89dB. PRICE £16.49 + £2.00 P&P

## BSR P295 ELECTRONIC TURNTABLE

- Electronic speed control 45 & 33 1/3 r.p.m.
- Plus Minus variable pitch control
- Belt driven
- Aluminium platter with strobed rim
- Cue lever
- Anti-skate (bias device)
- Adjustable counter balance
- Manual arm
- Standard 1 1/2" cartridge fixings
- Supplied complete with cut out template
- D.C. Operation 9.14V D.C. 65mA


Price £36.99 £3.00 P&P.



ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p
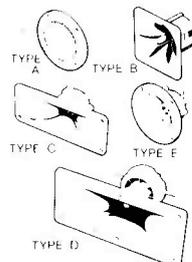
## PIEZO ELECTRIC TWEETERS - MOTOROLA


Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 Watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



**TYPE 'A' (KSN2036A)** 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each - 40p P&P  
**TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each - 40p P&P  
**TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each - 40p P&P  
**TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each - 40p P&P  
**TYPE 'E' (KSN1038A)** 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each - 40p P&P  
**LEVEL CONTROL** Combines on a recessed mounting plate, level control and cabinet input jack socket 85 x 85 mm. Price £3.99 - 40p P&P
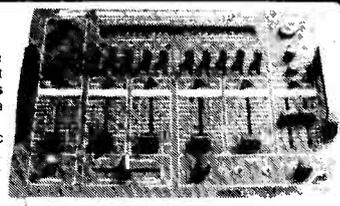
## STEREO DISCO MIXER

**STEREO DISCO MIXER** with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features. 5 Inputs with individual faders providing a useful combination of the following - 3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch. Headphone Monitor. Pan Pot L & R. Master Output controls. Output 775mV. Size 360 x 280 x 90mm. Price £134.99 - £3.00 P&P



## PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

**FM MICROTRANSMITTER (BUG)** 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt). Price: £8.62 + 75p P&P.

**3 WATT FM TRANSMITTER** 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt). Price: £14.49 + 75p P&P.

**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER** 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82 Transmitter 90 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME, SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED.



# B. K. ELECTRONICS DEPT ETI

UNIT 5, COMET WAY, SOUTHBEND-ON-SEA, ESSEX, SS2 6TR TEL: 0702-527572

**For KITS & COMPONENTS -**  
**Choose the easy way - with**

**Send 50p\* & SAE**  
**for CATALOGUE**  
**(AUTUMN 1987)**  
 \*refundable with first order

**TK**

**ORDERS: RING (01) 567 8910 - 24 HRS.**

**ELECTRONIC GUARD DOG KIT**



One of the best deterrents to a burglar is a guard dog and this new kit provides the barking without the bite! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would be intruder think again and try his luck elsewhere. The kit is supplied complete with high quality PCB, transformer, all components and instructions. All you need is a mains supply, intruder detector and a little time. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect.  
**XK125 Complete kit of parts ..... £24.00**

**DISCO LIGHTING KITS**

**DL1000K** This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel ..... **£19.25**  
**DL21000K** - A low cost uni-directional version of the above. Zero switching to reduce interference ..... **£10.80**  
**DLA/1** (for DL & DLZ1000K) Optional opto input allowing audio 'beat'/light response ..... **77p**  
**DL3000K** - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel **£15.50**  
 The **DL8000K** is an 8-way sequencer kit with built in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY - YES 80! different sequences including standard flashing and chase routines. The KIT includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300 W output per channel.  
 And the best thing about it is the price.  
**ONLY £31.50**



**TEN EXCITING PROJECTS FOR BEGINNERS**

This Kit has been specially designed for the beginner and contains a **SOLDERLESS BREADBOARD, COMPONENTS**, and a **BOOKLET** with instructions to enable the absolute novice to build **TEN** fascinating projects including a light operated switch, intercom, burglar alarm, and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.  
**ORDER NO XK118 ..... £15.00**

**MICROPROCESSOR TIMER KIT**

Designed to control 4 outputs independently switching on and off at present times over a 7-day cycle. LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control including different switching time for weekends. Battery back-up circuit. Includes box. 18 time settings.  
**CT6000K ..... £47.20**  
**XK114** Relay kit for CT6000, includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts ..... **£4.30**  
**701115** Additional relays ..... **£1.80**



**VERSATILE REMOTE CONTROL KIT**

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (excluding transformer) 9 x 4 x 2 cms. The companion transmitter is the **MK18** which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available - **MK9** (4-way) and **MK10** (16-way), depending on the number of outputs to be used.  
**MK12** IR Receiver (incl. transformer) **£16.30**  
**MK18** Transmitter ..... **£7.50**  
**MK9** 4-Way Keyboard ..... **£2.20**  
**MK10** 16-Way Keyboard ..... **£5.55**  
**601133** Box for Transmitter ..... **£2.60**

**HOME LIGHTING KITS**

These kits contain all necessary components and full instructions and are designed to replace a standard wall switch and control up to 300W of lighting.  
**TDR300K** Remote Control Dimmer **£18.00**  
**MKS** Transmitter for above **£5.10**  
**TD300K** Touchdimmer **£9.30**  
**TS300K** Touchswitch **£9.30**  
**TDE/K** Extension kit for 2-way switching for TD300K **£2.95**  
**LD 300K** Light Dimmer **£4.75**

**POWER STROBE KIT**

Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz this kit also includes circuitry to trigger the light from an external voltage source (eg. a loudspeaker) via an opto isolator. Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high quality pcb, components, connectors, 5Vv strobe tube and full assembly instructions. Supply: 240V ac. Size: 80 x 50 x 45.  
**XK124 STROBOSCOPE KIT .... £13.75**

**DVM/ULTRA SENSITIVE THERMOMETER KIT**

Based on the ICL 7126 and a 3/4 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches required - details supplied) or a sensitive digital thermometer (-50°C to +150°C) reading 0.1°. The kit has a sensitivity of 200mV for a full-scale reading automatic polarity and overload indication. Typical battery life of 2 years (PP3) **£17.00**

**XK113 MW RADIO KIT**

Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires PP3 9V battery. **IDEAL FOR BEGINNERS £6.60**

**PROPORTIONAL TEMPERATURE CONTROLLER KIT**

Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine-making, etc. Max. load 3kw (240V ac) Temp. range up to 90°C. Size: 7x4x2.5cms.  
**MK4 ..... £7.80**

**BARGAIN COMPONENT PACKS**  
 Refill those empty component drawers at a fraction of the normal price and don't be caught without that odd resistor or capacitor to complete your project. All components supplied are to full spec, and are not seconds or surplus stock.

- Pack A:** 650 x .25 watt resistor 47R-10M **£4.25**
- Pack B:** 60 x Radial electrolytes 1uf-1000uf **£3.25**
- Pack C:** 30 x Polyester capacitors a or 0.01 uf-1uf **£4.50**
- Pack D:** 35 x horizontal presets 1k-1M **£3.00**
- Pack E:** 30 x IC sockets 8, 14, 16 pin **£2.00**
- Pack F:** 25 x Red 5mm LEDs **£1.75**
- Pack G:** 25 x Green LEDs **£2.00**
- Pack H:** 30 x 5mm LEDs 10 Red, 10 Green, 10 Yellow **£2.50**
- Pack J:** 50 x 1N4148 silicon diodes **£1.00**
- Pack K:** 40 x npn/pnp transistors BC182/212 General Purpose **£2.25**

**FREE** Solderless Breadboard (verobloc type). When you buy all ten packs. Prices exclude VAT (15%).

**GIANT SOLAR CELLS**  
 NOW IN STOCK these giant size solar panels 12 x 12ins will deliver over 12 volts 200mA in bright sunlight and 11.5 volts 60mA on a typical British summer day (dull and overcast). In bright sunshine we measured 17 volts (open circuit) and a short circuit current of over 480mA. HUNDREDS OF USES IN THE CAR OR CARAVAN, E.G. Charging NiCads, powering low voltage circuits where mains or battery supplies are inconvenient or coupled to a lead acid battery and a simple inverter you could build yourself a self contained mains supply for low power appliances. **£14.50** (+ £1.75 for p&p on total order)  
 Stock No. 303 145

**MK 14 AC POWER CONTROLLER KIT**  
 This kit uses phase control techniques to vary the power in a mains load by means of a d.c. control voltage. The control voltage (which may be derived from a potentiometer, thermistor, light dependent resistor or a digital to analogue converter) needs to be varied from 0 to 2 volts to vary the load power from zero to maximum and an amplifier is included for smaller voltages. The circuit is mains powered and can control up to 1 kW if the triac is fitted with a heatsink A d.c. supply is also available for powering external circuits. Applications include lighting controllers for stage and theatre, aquariums and avaries, motor speed controls and fast response temperature controllers. The kit includes a printed circuit board, and components together with a circuit diagram, instructions, and applications circuits. **£5.70**

**SOLID STATE RELAY BARGAIN**

- ZERO VOLTAGE SWITCHING: No radio interference problems
- 2.5 KV INPUT TO OUTPUT ISOLATION: No risk of damage to your computer or driver circuits.
- 4 KV TERMINALS TO HEATSINK ISOLATION: Simply bolt onto a heatsink.
- 32V to 32V INPUT VOLTAGE: easily interfaced to TTL or CMOS LOGIC.
- 24V to 240V rms LOAD VOLTAGE: Enabling switching of inductive loads.
- BUILT IN SNUBBER NETWORK: Enabling switching of inductive loads.
- 10A MAXIMUM CURRENT: 4A with no heatsink listed at 40° C CD240/10 **£2.25**

**TOOLS ★ TOOLS ★ TOOLS**

Good quality tools selected to offer outstanding value for money.

- 650 004 6in mini. Snipe Nose Pliers. Serrated jaws and return spring **£2.10**
- 650 005 6in lap jointed side cutters. Insulated handles and return spring **£2.10**
- 650 006 Light duty cutters. Cuttings capacity 0.22 x 1.2mm copper wire. **£1.60**

**TOOL KIT** Contains: side cutters, snipe nose pliers, wire strippers, flat blade screwdriver, Phillips screwdriver in black textured, reinforced and padded case which when opened out measures 240 x 205mm. **£6.80**

- 650 007 Self-adjustable automatic wire stripper with built-in cable cutter. **£3.95**
- 650 012 Watchmakers Screwdriver Set: 1.0/1.4/2.0/2.4/3.0/3.8mm. **£1.75**
- 650 012 Set of a Stainless Steel Tweezers. Straight nosed, straight nosed-reverse action, bent nosed, flat nosed. 110mm long. **£3.55**
- 650 502 Hellam 9-12V dc Drill **£8.90**
- 650 506 Titan 12V dc Drill **£10.25**
- 650 570 Saturn Mains Drill **£16.50**

WE ALSO STOCK ANTEX IRONS AND ACCESSORIES

**AUTORANGING DIGITAL MULTIMETER**

High quality meter with features normally found in meters costing much more e.g. DISPLAY HOLD, MEMORY, CONTINUITY BUZZER and 10A AC/DC current ranges. High accuracy and automatic operation - a must for the professional or serious hobbyist. Size: 127 x 69 x 25mm.

AC Volts: 0-2-20-200-500V  
 DC Volts: 0-200m-2-20-200-1000v  
 AC Current: 0-20m-200mA (1.2%) 0-10A (2%)  
 DC Current: 0-20m-200mA (1.2%) 0-10A (1.5%)  
 Resistance: 0-200-2K-20K-200K-2M (1%)  
 Continuity Buzzer operates @ 20 ohm ..... **£33.00**

**NEW SUPER SENSITIVE FM MICROBUG**

VARICAP TUNED SENSITIVE ELECTRET MICROPHONE. PRINTED CIRCUIT AERIAL COIL. HIGH GAIN AMPLIFIER. HIGH QUALITY SOLDER RESIST (60 x 40mm)

Highly sensitive FM transmitter measuring only 45 x 25 x 15mm, including the built-in microphone. Frequency 88-100MHz enabling reception on a standard domestic FM radio. Range approximately 300m depending on terrain. Powered by 9V PP3 (7mA). Its small size and highly sensitive electret microphone makes it ideal for surveillance, baby alarm, etc. **£5.50**

**RECHARGEABLE SOLDERING IRON**

Powerful cordless iron complete with table-top/wall-mounting charging bracket. Reaches soldering temperature in 10 seconds. Includes lamp which lights when soldering. Comes with mains charging unit and 12V car battery adaptor. **Special Offer £15.95**

**ELECTRONIC WEIGHING SCALES**

This kit contains a Single Chip Microprocessor, PCB, displays and all electronics to produce a digital readout of weight in Kgs, or Sts, and Lbs. In normal use a toothed wheel (pattern provided) is made to rotate when a weight is placed onto the scales, interrupting two infra-red beams. The processor counts the number of teeth passing the sensor (up or down, depending on which beam is broken, first) and shows the reading on the LED display in Sts., Lbs., or Kgms. A PCB link selects the scale for bathroom or two types of Kitchen Scales. A linear version of the toothed wheel could also be used. Other uses include up/down counters. A low cost digital ruler could be made by using a wheel with the correct tooth to diameter ratio. **ES1 ..... £6.50**

**TK ELECTRONICS**  
**13 BOSTON RD**  
**LONDON W7 3SJ**  
**Tel: 01-567 8910**

**SEND 9"x8" S.A.E. & 50p FOR CATALOGUE OR CALL AT SHOP MON-FRI 9-5pm SATURDAY 10-4pm**

**ORDERING INFORMATION: ALL PRICES EXCLUDE VAT**

**FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.**


**LOCAL AUTHORITY AND EXPORT ORDERS WELCOME GOODS BY RETURN SUBJECT TO AVAILABILITY**

October  
1988


VOLUME 17 No 10

Geoff Bains: Editor  
Jez Ford: Assistant Editor  
Paul Chappell: Projects Editor  
Jerry Fowler: Technical Illustrator  
Heather Hopkinson: Design

Mark Warford: Photography  
Julie Capstick: Ad Manager  
Heather Wust: Classified Sales  
Andrew Selwood: Copy Control  
Mark Webb: Group Editor

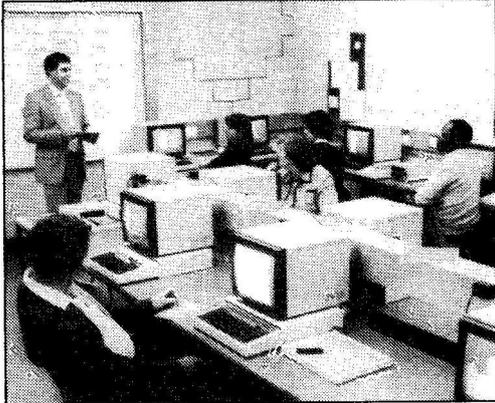


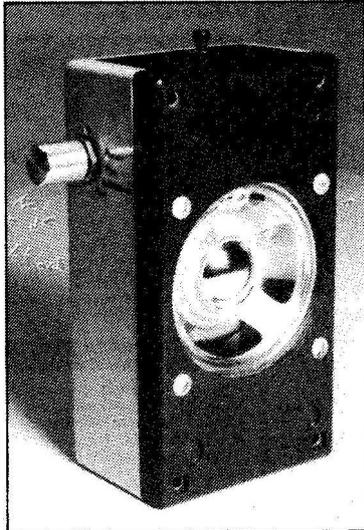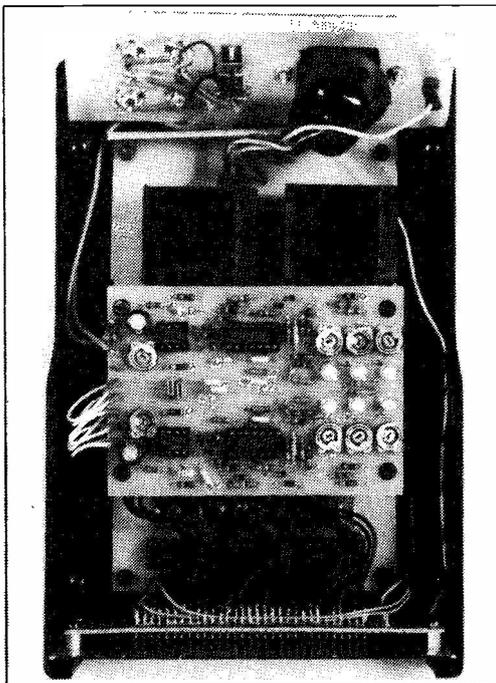Page 12


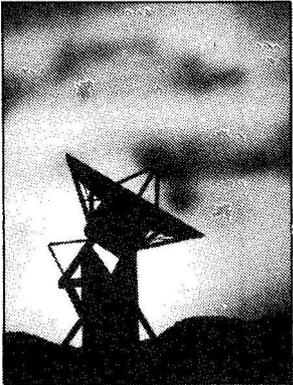


Page 32

Page 34

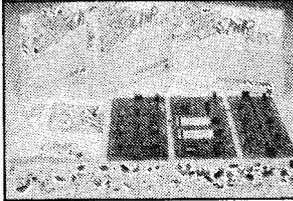

**REGULARS**

<b>News</b>	<b>6</b>	<b>PCB Service</b>	<b>52</b>	<b>Playback</b>	<b>62</b>
<b>Insight</b>	<b>8</b>	<b>PCB Foil Patterns</b>	<b>54</b>		
<b>Diary</b>	<b>8</b>	<b>Oops!</b>	<b>56</b>		<b>62</b>
<b>Read/Write</b>	<b>9</b>	<b>Classified Ads</b>	<b>57</b>	<b>Open Channel</b>	
<b>Next Month</b>	<b>11</b>	<b>Book Look</b>	<b>61</b>		
<b>Keep Regular!</b>	<b>13</b>	<b>APRS Show Report</b>	<b>61</b>	<b>Once Over</b>	<b>63</b>
<b>Competition Results</b>	<b>22</b>	<b>Subscriptions</b>			<b>64</b>
<b>Ad Index</b>	<b>39</b>			<b>Blueprint</b>	<b>66</b>

## FEATURES/PROJECTS

# 12


### Class of 88

Steve Morgan looks at the effects of the new GCSE syllabus on electronics teaching and learning in the classrooms of secondary education

# 14
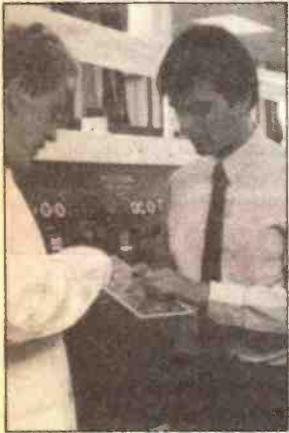
### The Next Step

You've finished your A-levels. You've got three A's in Electronics, Computing and Physics, so what's next? ETI lists all the options with a complete collection of HND and non-university courses.



# 18

### Recruitment In The Real World

The time for job hunting is fast approaching so Jez Ford has done his own milk round to find out what six companies have to offer new employees and how they intend to fill the posts.



# 23


### Going It Alone

Les Sage's Sage Audio has become a shining example of the electronics enthusiast going it alone and making good. Here he tells the story and gives some advice on following his path to fame and fortune

# 28
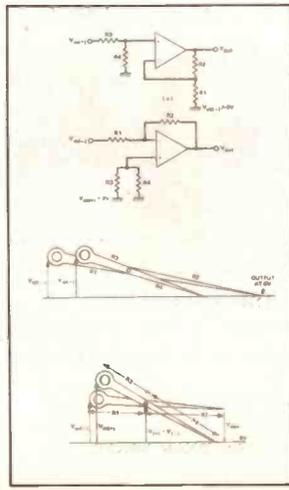
### Op-Amps

Paul Chappell continues the *Circuit Theory* look at op-amps with a discussion of noise reduction using common mode rejection



PROJECT

# 32

### Gerrada Marweh Bikebell

Not content with an appalling homophonic title, Keith Brindley's *1st Class* project is also extremely loud and guaranteed to frighten any living creature in front of the BMX




PROJECT

# 34

### Peak Programme Meter

Ian Coughlan keeps an eye on his hi-fi peaks with this handy, stylish and ultra accurate meter

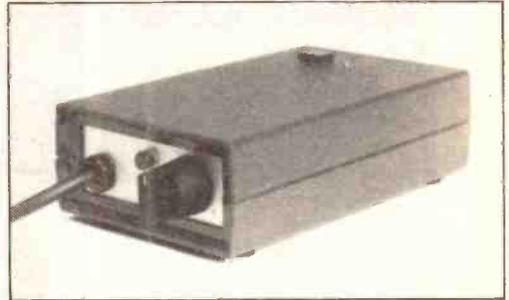

Page 40

Our thanks to Vivien Lunniss for the calligraphy on this month's cover.

# 40

PROJECT

### TV To RGB Conversion

David Lerche shows how to convert your old telly into a more useful RGB monitor to restore crispness and clarity to your computer displays



Page 32

# 45

PROJECT

### Variat-Ion

Paul Chappell has updated his Direct-Ion air ironiser of July 1986 to produce a super-powerful model with fully variable output

## THE PRICE OF POWER

Plans to regulate electricity prices after privatisation are hopelessly over-confident, the Government warned by the area distribution boards.

The pricing policy presently proposed follows the lines of gas and telephone charges which are allowed to increase by inflation less an X-factor. The X-factor for BT has recently been set at 4½% and ministers are intending to fix the electricity X-factor between 1% and 2%.

The area boards are arguing that they will have hardly any scope to reduce costs and that the X-factor should be no more than 0.3%. This figure would prevent ministers from pointing to the price advantages of a privatised electricity industry.

Meanwhile details have been announced of Big G and Little G — the two amusingly titled generating companies to be formed from the break-up of the CEGB. The site listings proposed would give Big G nearly 40000MW capacity compared to Little G's 18800MW. All nuclear generation is included in Big G's allocation. It is possible that these figures may change slightly should some stations be allocated to other private companies.

## PADDINGTON BARE


Paddington College's fight to keep its Radio Amateurs' Examination Course running in the face of ILEA's savaged budgets has led to an empty publicity fund and complete dependency on good enrolment figures for survival. It is likely that all other RAE courses in London will close as a result of the cuts.

ETI is pleased to give a little free publicity. The course not only covers the syllabus for the City and Guilds RAE exam (with an excellent pass rate of close to 90% in recent years) it also makes use of college facilities to provide an elementary grounding in electronics as well as an Amateur Radio Licence.

Attendance is twice a week (terms from mid-September to May).

The enrolment will take place from 5th-9th September between 1 and 4pm and 6 and 8pm on the 3rd floor, Paddington College, Paddington Green, London W2 1NB. Tel: 01-402 6221 for further information.

## ASTRA SKY PALS

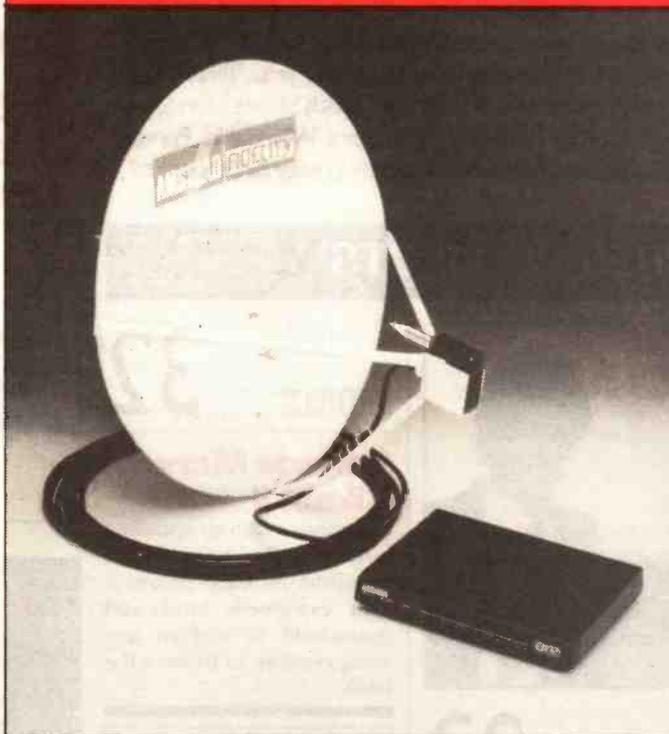

Amstrad has produced its prototype for the £199 receiving equipment for Murdoch's Astra-based PAL satellite channels. Amstrad has already placed orders with Marconi to produce the LNBs for the systems — the dish designs are completed and contracts for the actual receiver units should be finalised in the next month. Amstrad is confident that the equipment will be available by March next year.

There has however been a question mark put over the entire Astra operation by the continued talks between Eutelsat and the consortium headed by Robert Maxwell and WH Smith. Eutelsat plans to have 32 transponders available on two satellites to be launched in 1991.

If the Maxwell consortium were to

withdraw from Astra, the attraction to UK viewers of a single satellite receiver like Amstrad's would be significantly hit. Mr Murdoch is believed to have a get-out clause in his contract with Astra that could be exercised should other English-speaking Astra possibilities go elsewhere.

Meanwhile, BSB is considering countering Amstrad's budget receivers by subsidising sales of its equipment to BSB subscribers.

Several schemes are being considered, with the general idea of maximising the immediate uptake of BSB's channels at its launch next summer. It has also contracted Scottish firm Fortel for exclusive rights to its flat antenna design which could be combined with a budget receiver to retail around £250.

## PCBS FROM PCWS

CADsoft has produced a new version of its printed circuit board design utility. The Amstrad CPC version was reviewed in ETI March 1988 and the program is now available to run on Amstrad PCW8256 and 8512 computers.

As with the CPC version, the program can produce single or double-sided boards, displaying tracks on opposite sides simultaneously. Printout is high quality double-sized onto a normal Epson or equivalent dot matrix printer.

The price is £29.99 fully inclusive and ETI readers can obtain full details and sample printouts by sending an SAE to CADsoft Systems, 18 Ley Crescent, Tyldesley, Manchester M29 7BD. Tel: (0942) 870376.

## ATARI ADD-ONS

Atari ST owners can use their computer as a spectrum analyser or oscilloscope using two new units from Kuma Professional Software.

The K-Spect forms a low frequency spectrum analyser with two channels used as A or B, A+B or B/A. The signal can be locked or free running with a range 0 to 25kHz in 1kHz steps.


The K-Scope oscilloscope is aimed at audio frequency capture up to 30kHz.

Both units consist of an interface box (which connects to the Atari's ROM port) and relevant software.

They cost £149.95 each or £239.90 for the pair.

Contact Kuma, 12 Horseshoe Park, Pangbourne RG8 7JW. Tel: (07357) 4335.

## TV AMP

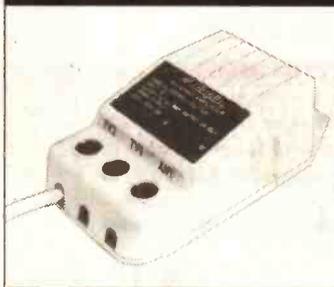


Maplin has added a remarkably cheap aerial amplifier to its range of aerial products.

The amp has a gain of 7dB with an extra co-ax output for driving a second television.

It is mains powered and can be wall mounted if required.

The price is just £11.95 inclusive — Maplin's product code is YP41U. Contact Maplin on (0702) 554161.

## CAPITAL CAPACITORS

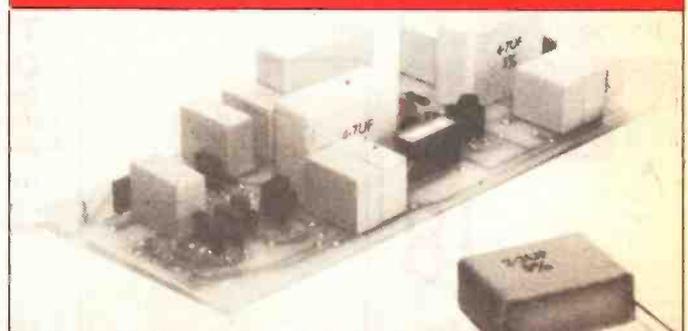


Audiokits of Borrowwash has introduced a new range of high quality audio polypropylene capacitors.

The Audiocap polypropylenes are of radial construction in a rectangular case and their small physical size makes them useful for upgrading amplifiers currently fitted with

polyester or polycarbonate caps (an upgraded Virtuoso pre-amp — ETI June-November 1986 — is shown in the photo).

They are available from 10n to 4µF at 63V rating from Audiokits, 6 Mill Close, Borrowwash, Derby DE7 3GU. Tel: (0332) 674929.

## 2MHz MIDI

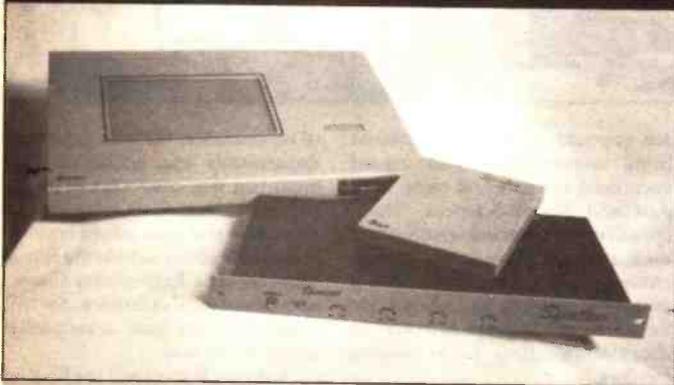

**M**IDI communication at 2MHz is on the way from Syntec Digital Audio in the form of MINI (Musical Instrument Networking Interface).

MINI allows connection of up to 126 instruments at node points around a network ring. A total of 8064 channels (64 for each node) thus become available.

Upgrading a system to use MINI is not easy and certainly not cheap. Each MIDI instrument requires a MINI to MIDI converter and the routing systems get so complex that a master controller is required to implement routing programs.


With a complete ring of instrument nodes formed (including the MINI Master Controller) busses

are specified using instrument names (identified as the nodes are created). The MINI bus information is held by the Master together with Routing Programs (also names rather than numbers) which store combinations of busses.

Once a network is defined it is quite a job to rearrange things so MINI is certainly best suited to permanent studio set-ups. Prices vary from £800 to £3,000 for the Master Controller and a 4-way MIDI converter costs £700.

Contact Syntec Digital Audio, 628 Chester Road, Sutton Coldfield, West Midlands B73 5JR. Tel: 021-373 9858.

## METERS

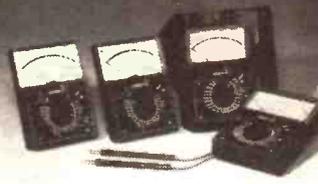

**M**ultimeters at either end of the price scale have been introduced by Universal Instruments this month. In the pocket money and birthday pressie range are four Iskra meters, the cheapest of which is the model 46. This features 23 measurement ranges covering AC and DC volts and amps, plus resistance. It costs £19.50.

The model 45 has wider operating parameters, slightly greater accuracy and an audible short circuit test. The 45 costs £34.33. All four Iskra meters display by analogue moving coil.

Universal has also introduced the latest Hioki digital multimeter, a 4½-digit instrument with resolution to 10µV. It has a wideband frequency response so can give accurate RMS readings even of distorted waveforms. The 3230 costs £318.05.

All prices exclude VAT. For more details contact Universal, Unit 62, GEC Site, Whetstone, Leicester LE8 3LH. Tel: (0533) 750123.

## TRANNY TRAINING

**A** training package for the BBC B and B+ entitled *Understanding Transistors* has been produced by Computer Aided Training of Frizington in Cumbria.

The package is designed for use on GCSE, ITEC and BTECII courses and is supplied with a simple ready built board comprising a transistor switch and common emitter amplifier. A pack of components required for the different experiments is also provided. The board connects to the BBC micro via D-connectors to the joystick port and is powered from the micro's 5V output.

The software supplied monitors the circuit to display two currents and six voltages as numerical values and in graph format, with an option to display values as on an oscilloscope.

A third screen displays the circuit diagram showing the currents flowing and the voltages at each node.

Worksheets for 30 experiments are provided — these are free of copyright so they can be photocopied for multiple or future use.

Computer Aided Training estimates the work could be completed superficially in about 10 hours although some 40 hours of detailed study could be obtained.

*Understanding Transistors* costs £39 inclusive.

Contact J McCormack, CAT, 1 Windergate, Frizington, Cumbria CA26 3QS. Tel: (0946) 810597.

## SUPERTRONIC SHOPPING

**B**irmingham's electronics boulevard, Hurst Street has a new attraction for component shoppers. Supertronics, at 65 Hurst Street, is the third of Marco Trading's retail outlets and will be stocking the whole range of its mail order catalogue from components and ICs through to opto-components and burglar alarms.

Supertronics will also be operating an on-site audio and video repair service with a resident engineer. Contact Supertronics, 65 Hurst St., Birmingham B5. Tel: 021-666 6504.

## PUSH FOR ACTION



**S**ome heavy duty push-buttons and indicators are being marketed by Invader in Swindon, including the pictured chunky mushroom stop button — part of the Highland series 04.

All the range have oil-sealed

contacts and many are panel sealed to standard IP65. The maximum switch rating is 10A at 500V AC.

Contact Invader, Bridgewater Close, Hawksworth, Swindon SN2 1TZ. Tel: (0793) 613201.

## SURVEY WINNERS

**T**he ETI Readers' Survey department was flooded with returned forms following our June issue. Many thanks to all who took part and when the ETI programmers have completed their machinations we'll be taking note of your views.

Meanwhile the 25 winners of the free six month subscriptions are: A J Cunnell, West Norwood. P J Lawro- witz, Stockport. J A Bruce, Braintree. A C Pidsley, Chudleigh. G A Mape, Manchester. Imerio Ballarini, Cricklewood. L Eastwood, Wey- bridge. S Wylie, Burchetts Green. A C Owen, Sheffield. A Hulse, Wigan. G Smith, York. S Eyles, Corsham. A J Perkins, Bracknell. N James, Thornton Heath. P Dooley, Greasby. K Ozwell, Grimsby. S Pearce, Lough- borough. T Hawkins, Southampton. S Coce, Norwich. T Barwick, Clap- ham. D Lewis, Llandaff. A C Booth, Brighton. D Walton, Bracknell. J W Welch, Scunthorpe. G W Peale, Wolverhampton.

These lucky winners will get six free copies of ETI commencing with the November issue (existing subscribers will have their sub- scriptions extended).

## TITCHY TESTER

**A** titchy tester for 6 and 12V batteries is being marketed by Alpha Electronics.

The BQ200A hand-held voltmeter would be suitable for checking vehicle battery and charging systems — power is taken from the system under test so that no internal batteries are used. The 3½-digit display is accurate to within 20mV and indicates polarity signals.

The unit is sealed and guaranteed for twelve months. It costs £26.00+VAT. Contact Alpha Elec- tronics, Unit 5, Linstock Trading Estate, Atherton, Manchester M29 0QA. Tel: (0942) 873434.



## RESISTANCE IS LOW

**L**ow value resistors are part of a new range of components from Welwyn Electronics. The W30 series resistors are designed primarily for current sensing and are available with values between 10 milliohms and 91 milliohms, with wirewound cement-coated construction. Rated dissipation is 3W at room temperature but they can withstand 10 times the rated power for about 5s.

Contact Welwyn Electronics, Bedlington, Northumberland NE22 7AA. Tel: (0670) 822181.

# INSIGHT



Access to higher education must be widened effectively and quickly, otherwise the employers and economy of the UK will be denied the skills and competence necessary to survive. This is the message of a report from the Industry Matters Education Industry Forum, an initiative of the Royal Society for the Encouragement of Arts, Manufacturers and Commerce.

The report challenges the deeply rooted systems for gaining entry to higher education in this country as failing to select those most likely to gain from the studies.

The dominance of A-levels in selection procedures for degree courses has become widely accepted mainly because it provides an easy method for admissions tutors to reduce the piles of UCCA forms to a manageable quantity quickly and with a minimum of effort. A-levels have thus become the standard ticket to universities and polytechnics and have thereby gained dominance in the school curriculum without necessarily providing the breadth and balance of relevant subjects that should be sought in those entering higher education.

This system is positively unhelpful

for mature and non-standard entrants. The A-level ticket is maintaining higher education in a role that nurtures a thin stream of excellence when industry is crying out for a broad highway of competence. Within this, excellence should have its part to play but would not create the current situation where the best become the enemies of the good.

The report however ignores the obvious solution that higher education should be available to more people rather than simply to a different mix. If the system is at present full to capacity and yet produces only a thin stream of excellence, widening the stream can only be achieved by pumping in additional resources — otherwise the results already attained will be lost.

The immediately obvious source of such assistance is the Government but with the present ministerial policies of autonomy in education at all levels additional financing is unlikely to say the least.

A second possibility is a system that positively encourages private company sponsorship of higher education in the form of tax relief and incentives similar to those available in the United States. Many academics

are opposed to such measures as being unavoidably biased toward vocational subjects and away from Arts and Social Sciences. These arguments unfortunately lose much of their strength against the current climate where just this type of bias is exercised annually as colleges are forced to use natural selection to allocate dwindling funds among faculties.

The report from Industry Matters argues that more government money may well be necessary but this is in addition to the attitude changes vital for a more solidly based and broadly trained workforce capable of competing with foreign competitors. Various areas are marked out for attention. Selection procedures should make better use of profiles and experience as well as A-level grades. Entry for mature and non-standard candidates should be simplified and Open University foundation courses more widely accepted.

Modular format courses should be encouraged to assist entry and enable exemption for experienced students, it says. Course objectives should be clearer so that relevant skills in candidates can be identified.

The report also criticises the lack

of co-operation between admission departments and employers. It is important that employers as well as courses understand the advantages of candidates that have gained expertise and qualifications outside the A-level situation. The Engineering Council and Standing Conference on University Entrance have already taken action to this end.

Industry Matters and the RSA are keen that this report does not simply make its recommendations and then gather dust. The national organisation is seeking the assistance of various relevant organisations (notably the Council for Industry and Higher Education) in establishing a working group to seek a method of positively encouraging wider access to higher education.

It stops short of pressing the Government to take action but is refreshing in its admission that a report such as this can only achieve limited objectives and cannot hope to change an entire cultural system through its recommendations alone.

The report *Raising The Standard — Wider Access To Higher Education* is available from Industry Matters, 8 John Adam Street, London WC2N 6EZ. Tel: 01-930 0120.

# DIARY



## Insight On-site — September 6th

Excelsior Hotel, Birmingham. Seminar on electronic security systems. Contact Philips Scientific on (0223) 245191

## Insight On-site — September 7th

Novotel Manchester West, Manchester. Seminar on electronic security systems. Contact Philips Scientific on (0223) 245191.

## Insight On-site — September 8th

Hilton National, Leeds. Seminar on electronic security systems. Contact Philips Scientific on (0223) 245191.

## Conpar 88 — September 10-16th

Manchester. Contact British Computer Society on 01-637 0471.

## Plasa Light And Sound Show — September 11-14th

Olympia, London. Contact the Professional Lighting And Sound Association on (0323) 646905.

## European Conference On Optical Communication — September 11-15th

Brighton Centre, Brighton. Contact IEE on 01-240 1871.

## International Police Exhibition And Conference — September 12-15th

Barbican Centre, London. Mainly radio and communications technology. Contact Major Exhibitions on 01-446 8211.

## Comex 88 — September 13-15th

Sandown Park Exhibition Centre, Surrey. Contact Frametrack on 01-828 2905.

## Personal Computer World Show — September 14-18th

Earls Court Exhibition Centre, London. Contact Montbuild Exhibitions on 01-486 1951.

## Microjoining 88 — September 20-21st

The Welding Institute, Cambridge. Symposium on miniature electronic assembly. Contact The Welding Institute on (0223) 891162.

## International Broadcasting Convention — 23-27th September

Exhibition Centre, Brighton. Contact IEE on 01-240 1871.

## European Gallium Arsenide Conference — September 24-26th

Jersey, Channel Islands. Contact The Institute of Physics on 01-235 6111 for the venue.

## Semiconductor International — September 27-29th

Jersey, Channel Islands. Contact The Institute of Physics on 01-891 5051.

## Electronics In Engineering Design Show — September 27-30th

NEC, Birmingham. Contact Cahners Exhibitions on 01-891 5051.

## BBC Radio Show — 30th-9th October

Earls Court, London. 'Spectacular extravaganza' to celebrate 21 years of BBC Radio 1, 2, 3 and 4. Exhibition, live shows, etc. Contact BBC Radio Show, PO Box 100, Chatham, Kent ME5 8LJ

## Electronic Displays 88 — October 4-6th

Wembley Conference & Exhibition Centre, London. Contact Blenheim Online on 01-868 4466

## Computer Graphics 88 — October 11-13th

Wembley Conference & Exhibition Centre, London. Contact Blenheim Online on 01-868 4466.

## Digital Signal Processing Seminar — October 13th

Heathrow Penta Hotel, London. Contact ERA Technology on (0372) 374151

## Desktop Publishing Show — October 13-15th

Business Design Centre, London. Contact Database Exhibitions on 061-456 8383

## Satellite Systems For Mobile Communications And Navigation — October 17-19th

IEE, London. Conference organised by IEE. Contact IFF on 01-240 1871

## Internecon — October 18-20th

Metropole Exhibition Centre, Brighton. Contact Cahners Exhibitions on 01-891 5051

## Testmex 1988 (Electronic Testing & Measurement) — October 18-20th

Business Design Centre, London. Contact Network Events on (0280) 815 226

## IC Outlook — October 19th

Centre Point Building, London. Market overview seminar. Contact Dataquest on 01-583 9171

## Commercial Awareness And Business Skills For Young Engineers — October 21-23rd

Strand Palace Hotel, London. Contact IEE on 01-240 1871.

# MAKE A NOTE!



September 16th is the day to remember. It's a Friday so slip out of the pub at lunchtime early and nip around to the newsagent to lay your hands on one of the very first copies of:

## The Guide To **Making Music**

This ETI special is 76 pages packed with features and projects for the music maker and home recording enthusiast. There are effects projects for guitarists or anyone else wanting a little control over their sound:

**Chorus**  
**Flanger**  
**Noise Gate**  
**Fuzz**

For the well-connected MIDI enthusiast we have the low down on the ins and outs of the MIDI standard, reviews of the leading budget MIDI keyboards and of Casio's MIDI guitar . . . and more projects:

**BBC Micro MIDI Interface**  
**MIDI Master Keyboard**  
**MIDI Harmoniser**

Build a studio in your bedroom (or living room or garage or fridge) with the help of our brief for budding Stocks (or Aitkins or Watermen) and yet more projects:

**Parametric/Graphic Equaliser**  
**Direct Injection Box**  
**Aural Exciter**

And to finally vent your frustration there's plenty to hit with a couple of extra projects:

**Cymbal Synth**  
**Drum Box**

## ON SALE 16th SEPTEMBER – £1.95

# READ | WRITE

## KUDOS AND PEANUTS

As an occasional contributor to ETI, I feel I must respond to Mr Burton's letter in the August issue. I understand his point of view but suspect he does not appreciate the difficulties involved in preparing a project for publication.

Let us consider the cost of project building. There is no way a home-brew project can compete with mass-market electronics turned out in their hundreds of thousands by factories in Japan or anywhere else. Components are bought in quantity at rock bottom prices and assembled by the cheapest of labour.

The home-brew project cannot compete on quality. Japanese goods are not what they used to be — quality is the main selling point these days. Finish is certainly out — when was the last time you made something that looked as good as even an average pocket radio? Mechanics represent the major difficulty, as anyone who has tried to make a tuning dial will testify. CD mechanisms stand no chance!

Having ruled out 99% of all possible magazine projects as uneconomic, what is left? There are three main areas. Consumer goods

limited to the high cost luxury items, such as high quality audio gear, for example. This section of the market does not sell enough of anything to make economy of scale really count. By building equivalent equipment from constructional articles, you effectively side-step the cost of development by splitting it with everyone else who buys the magazine. What a designer is paid for his article is peanuts compared to industrial development costs anyway. The classical examples of this kind of project are the Linsley Hood audio gear and the various musical projects (keyboards, MIDI and the like).

Test gear also represents a good hunting ground, and there are plenty of those in the pages of ETI. Meters, scopes, analysers, whatever, are all extremely expensive commercially but many are more accurate than the typical hobbyist would require. The hobbyist does not represent a significant market, so there are not many products aimed at him. Where a kit is offered (sometimes to accompany a magazine project), is it any wonder that no-one else can do it much cheaper? No manufacturing costs are involved in marketing a kit.

The last niche where the hobbyist reigns supreme is the odd-ball project. By this I mean the sort of thing that is a gimmick or that wouldn't have a commercial market anyway. There have been dozens of those in ETI and rather than disparage anyone else's project, I might as well castigate my Digibaro as being in this category.

But wait. Who said DIY is about saving money on commercial items? It might be to some but there are plenty of people who would disagree. If you dismiss cost as irrelevant to the fun of making something for yourself (or pain, grief and frustration, more like) that first market of mass imports opens up once more. If you think I'm wrong, how is it that Heathkit has survived all these years? Their kits cost far more than a ready made item on the open market but people make them knowing everything is ready, all the problems have been solved and you get a professional finish.

As a final point, I wish to mention the rewards offered to the contributor of a magazine article. Why have them at all? Mr Burton does not, I am sure, realise how long it takes to develop a fully fledged project. To provide all a magazine such as ETI required would not be economic if entirely done in-house. External contributors don't get paid very much. Usually it works out at just enough to cover the cost of developing a project in the first place.

So why do we do it? Partly it's the kudos of having something in print, of course. It's certainly not the money. In the main, you want to make something and you have the technical skills to design it yourself. Hell and high

water will not stop you building that project and get it working but home-brews cost money and if someone else can be persuaded to foot some of the bill so much the better. It's not that easy, either. First of all you have to persuade the editor that he wants it, then you have to write it, neither of which are necessary if your project is for only private consumption!

When I was starting out, I read the high-flying articles avidly but with no intention of building one. I was getting to understand how the designs were put together, learning my craft as it were. To this day I have never built a magazine project, at least not without bending it out of all proportion. Mr Burton may not have these inclinations but if, after all I have said, he still sees the esoteric article as a waste of space, perhaps he should be reading one of the electronics comics (mentioning no names).

Ken Wood  
Ipswich, Suffolk

*Mostly agree with all that. We must say though that DIY projects can sometimes compete on quality and cost despite what you say. Finish is always a stumbling block.*

*As to the rewards, while we acknowledge that contributors payments are unlikely to ever compete against the pools in the windfall category, they can be a fairly hefty pile of peanuts!*

*Any budding designers out there interested in peanuts, kudos or just supporting the best non-comic electronics mag, please get in touch.*

## POWER CONDITIONER

FEATURED IN ETI  
JANUARY 1988


The ultimate mains purifier. Intended mainly for lowering the noise floor and improving the analytical qualities of top-flight audio equipment.

The massive filter section contains thirteen capacitors and two current balanced inductors, together with a bank of six VDRs, to remove every last trace of impulsive and RF interference. A ten LED logarithmic display gives a second by second indication of the amount of interference removed.

Our approved parts set consists of case, PCB, all components (including high permeability toroidal cores, ICS transistors, class X and Y suppression capacitors, VDRs etc.) and full instructions.

PARTS SET **£28.50 + VAT**

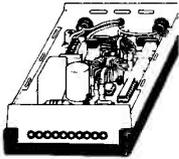Some parts are available separately. Please send SAE for lists, or SAE - £1 for lists, circuit, construction details and further information (free with parts set).



## KNIGHT RAIDER

FEATURED IN ETI JULY 1987

The ultimate in lighting effects for your Lamborghini, Maserati, BMW (or any other car, for that matter). Picture this: eight powerful lights in line along the front and eight along the rear. You flick a switch on the dashboard control box and a point of light moves lazily from left to right leaving a comet's tail behind it. Flip the switch again and the point of light becomes a bar, bouncing backwards and forwards along the row. Press again and try one of the other six patterns. An LED display on the control box lets you see what the main lights are doing.

The Knight Raider can be fitted to any car (it makes an excellent fog light!) or with low powered bulbs it can turn any child's pedal car or bicycle into a spectacular TV-age toy!

The parts set consists of box, PCB and components for control, PCB and components for sequence board, and full instructions.

Lamps not included.

PARTS SET **£19.90 + VAT**

## RAINY DAY PROJECTS



All can be built in an afternoon!

**JUMPIN' JACK FLASH** (ETI March 1988)

Spectacular rock, stage and disco lighting effect! **£6.90 + VAT**

**CREDIT CARD CASINO** (ETI March 1987)

The wicked pocket gambling machine. **£5.90 + VAT**

**MAINS CONTROLLER** (ETI January 1987)

Isolated logic to manage interfaces. **£6.20 + VAT**

**MATCHBOX AMPLIFIERS** (ETI April 1986)

Listen: 50W of Hi-Fi power from an amp small enough to fit in a matchbox!

Matchbox Amplifier (20W) **£6.50 + VAT**

Matchbox Bndge Amplifier **£8.90 + VAT**

L165V Power Amplifier IC, with data and circuits **£3.90 + VAT**

**TACHO/DWELL METER** (ETI January 1987)

Turn your Metro into a Porsche! **£16.40 + VAT**

**HI-FI POWER METER** (ETI May 1987)

Measures Hi-Fi output power up to 100W - includes PCB, components, meters

Mono power meter **£3.90 + VAT**

Stereo power meter **£7.20 + VAT**



FEATURED  
IN ETI  
AUGUST 1988


There's nothing quite so encouraging as having a quantifiable result to show for your training efforts. If you are not particularly fit, your resting heart rate will be around 80 beats per minute. As your jogging, aerobics or sport strengthens your heart, the rate will drop dramatically - possibly to 60bpm or less. With the S101, you can watch your progress day by day.

Breathing is important too. How efficiently do you take up oxygen? How quickly do you recover from oxygen debt after strenuous activity? The S101 will let you know.

The approved parts set consists of case, 3 printed circuit boards, all components (including 17 ICs, quartz crystal, 75 transistors, resistors, diodes and capacitors), LCD switches, plugs, sockets, electrodes, and full instructions for construction and use.

PARTS SET **£33.80 + VAT**

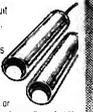Some parts are available separately. Please send SAE for lists, or SAE - £2 for lists, circuit, construction details and training plan (free with parts set).



## THE DREAM MACHINE

FEATURED IN ETI  
DECEMBER 1987



Adjust the controls to suit your mood and let the gentle, relaxing sound drift over you. At first you might hear soft rain, sea surf, or the wind through distant trees. Almost hypnotic, the sound draws you irresistibly into a peaceful, refreshing sleep.

For many, the thought of waking refreshed and alert from perhaps the first truly restful sleep in years is exciting enough in itself. For more adventurous souls there are strange and mysterious dream experiences waiting. Take lucid dreams, for instance. Imagine being in control of your dreams and able to change them at will to act out your wishes and fantasies. With the Dream Machine it's easy!

The approved parts set consists of PCB, all components, controls, loudspeaker, knobs, lamp, fuseholders, fuse, mains power supply, prestige case and full instructions.

PARTS SET **£16.50 + VAT**

AVAILABLE WITHOUT CASE FOR ONLY **£11.90 + VAT**



FEATURED IN ETI  
OCTOBER 1988

**£24.80**  
+ VAT

## THE MISTRAL AIR IONISER

Air ions are as essential to life as food and drink. In sterile city environments the natural ions are wiped out by dirt, dust, pollution and traffic fumes with devastating results.


The Mistral is designed to restore the natural ion balance, and with it your sense of energy, health and vitality. A highly developed circuit combined with an efficient phosphor-bronze emitter fills the most spacious room with life giving ions. You'll feel the difference within hours!

- Variable ionisation potential for maximum ion rush
- Hundreds of phosphor bronze ion thrust points
- Built-in ion counter - see the output level at a glance
- Over 100 top grade components
- Power enough to drive five multi-point emitters
- Feel the difference within hours


Some parts are available separately. Please send SAE for lists, or SAE + £1 for lists, circuit, construction details and further information (free with parts set).

## MAINS CONDITIONER

FEATURED IN ETI  
SEPTEMBER 1986

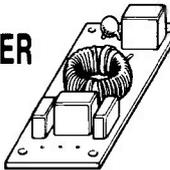

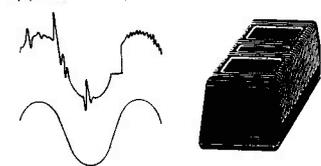Cleans up mains pollution easily and effectively. You'll hardly believe the difference in your Hi-Fi, TV, Video, and all other sensitive equipment.




PARTS SET **£4.90 + VAT**

RUGGED PLASTIC CASE **£1.65 + VAT**

## ARMSTRONG 75W AMPLIFIER

FEATURED IN PE  
JULY 1988

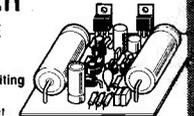

A. J. Armstrong's exciting new audio amplifier module is here at last!

Delivering a cool 75W (conservatively rated - you'll get nearer 100W), this MOSFET design embodies the finest minimalist design techniques, resulting in a clean, uncluttered circuit in which every component makes a precisely defined contribution to the overall sound. You can read all about it in the July issue of PE, but why bother with words when your ears will tell you so much more?

Parts set includes top grade PCB and all components.

**SPECIAL INTRODUCTORY PRICE FOR FULLY UPGRADED MODULES.**

SINGLE PARTS SET **£14.90 + VAT**  
STEREO PAIR **£25.90 + VAT**

Please send SAE + £1 for data and circuits (free with parts set), including diagrams for matching pre-amp and power supply. This amplifier will not be available from your usual audio supplier - we produce the only designer approved parts set.

## BIO-FEEDBACK

FEATURED IN ETI  
DECEMBER 1986



Bio-feedback comes of age with this highly responsive, self-balancing skin response monitor! The powerful circuit has found application in clinical situations as well as on the bio-feedback scene. It will open your eyes to what GSR techniques are really all about.

The complete parts set includes case, PCB, all components, leads, electrodes, conductive gel, and full instructions.

PARTS SET **£13.95 + VAT**

BIO-FEEDBACK BOOK **£3.95** (no VAT)

Please note: the book, by Stern and Ray, is an authorised guide to the potential of bio-feedback techniques. It is not a hobby book, and will only be of interest to intelligent adults.

## POWERFUL AIR IONISER

FEATURED IN ETI  
JULY 1986



Ions have been described as 'vitamins of the air' by the health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than 'dead' air. The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with (better than?) commercial products, was reliable, good to build, and fun! Apart from the serious applications, some of the suggested experiments were outrageous!

We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller printed circuit board, 66 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs about a third of the price of the individual components. What more can we say?

PARTS SET WITH BLACK CASE **£11.50 + VAT**


PARTS SET WITH WHITE CASE **£11.80 + VAT**

## LM2917 EXPERIMENTER SET

Consists of LM2917 IC, special printed circuit board and detailed instructions with data and circuits for eight different projects to build. Can be used to experiment with the circuits in the 'Next Great Little IC' feature (ETI, December 1986).

LM2917 EXPERIMENTER SET **£5.80 + VAT**

## LEDs

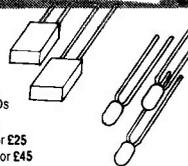

Green rectangular LEDs for bar-graph displays

50 for **£3.50** 500 for **£25**

100 for **£6** 1000 for **£45**

DIGITAL AND AUDIO EQUIPMENT LEDs

Assorted 3mm LEDs: red, green, yellow and orange.

25 of each (100 LEDs) for **£6.80**

Prices shown are exclusive of VAT, so please add 15% to the order total. UK postage is 70p on any order. Carriage and insurance for overseas orders £4.50. Please allow up to 14 days for delivery.

## BRAINWAVE MONITOR



FEATURED IN ETI  
AUGUST 1987

The most astonishing project ever to have appeared in an electronics magazine. Similar in principle to a medical EEG machine, this project allows you to hear the characteristic rhythms of your own mind! The alpha, beta and theta forms can be selected for study and the three articles give masses of information on their interpretation and powers.

In conjunction with Dr. Lewis's Alpha Plan, the monitor can be used to overcome shyness, to help you feel confident in stressful situations, and to train yourself to excel at things you no good at!

Our approved parts set contains case, two PCBs, screening can for bio-amplifier, all components (including three PMI precision amplifiers), leads, brass electrodes and full instructions.

PARTS SET **£36.90 + VAT** ALPHA PLAN BOOK **£2.50**


SILVER SOLUTION (for plating electrodes) **£3.60 + VAT**

Parts set available separately. We also have a range of accessories, professional electrodes, books, etc. Please send SAE for lists, or SAE + £2 for lists, construction details and further information (free with parts set).

Specialist  
**SEMICONDUCTORS**  
LIMITED

SALES DEPT., ROOM 107, FOUNDERS HOUSE, REDBROOK, MONMOUTH, GWENT.

*Next Month  
in*

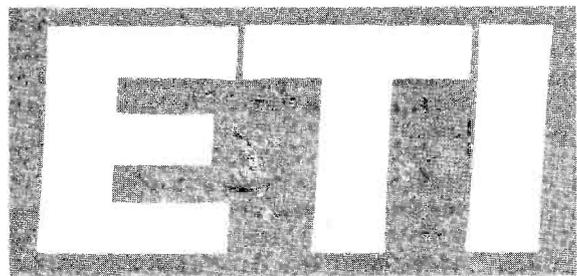

**ELECTRONICS  
TODAY INTERNATIONAL**

# IT'S A STEAL!

**T**he November issue of ETI sees the return of the annual ETI giveaway. On the cover of the November issue you will find a small bag crammed to the gills with valuable components all ready for you to build the ETI Burglar alarm. There have of course been burglar alarms before, but never a free burglar alarm (surprising, really, when you consider that the clear up rate for crimes of breaking and entering is only around 17% and so there are an awful lot of free burglars around!)

As if that wasn't enough from us generous ETI types, the following issue will feature a free PCB on which to mount your components along with a series of expansions to turn your free alarm into a comprehensive protection system.

Meanwhile, back in the November issue, there's a wealth of other goodies, well worthy of protecting! Are you out of control? — not to worry we have the lowdown on control strategies to restore order to your life. Do you not know your digits from your doobries? — our feature on analogue to digital converters will solve all that as well.

Plus, for those long winter nights there's plenty to keep the soldering iron warm and you busy. There's a Chronoscope for the shooting fraternity and a NiCd rechargeable battery charger for the beginners, to name but two.


And there's all the rest that go to make ETI the best electronics magazine to buy this and every month.



## **November ETI — out October 7th**
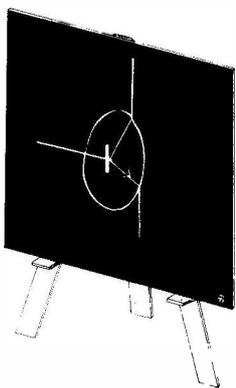
# CLASS OF 88

*Steve Morgan takes a look at the new presentation of electronics in education and sees if there are any lessons to be learned*



# EDUCATION

**E**lectronic Engineering as a subject at degree level has been around for a long time (the microprocessor becomes an adult next year!) but over the last ten years it has slowly been accepted as a subject in its own right at secondary school level.

O-level Electronics has been an option in many schools for at least five years but has often been treated as an extension of Physics with 'the more practically able' pupil being advised to take up this option. This situation has fortunately changed as teachers and pupils have realised the demanding range of design, problem solving and practical skills required in Electronics. Recently talking to a group of 16 year olds who had freshly emerged from this year's exam torture session, it appears that Electronics is rated as close to the top of the list of difficult subjects.

However, despite being rated highly at an academic level and the increasing shortage of engineers in industry, the numbers of students wishing to follow a course at a higher level is considerably smaller than those going into business and accountancy. It's hard for the 'oily overall' image of engineering to compete with a time manager, a Porsche and flat in Chelsea. If the shortage continues perhaps an 'electro-yuppie' will eventually emerge from the oily overall.

This general shortage of engineers and technologists together with the falling numbers of students on science and engineering courses has led the government to introduce a new national curriculum in which science and technology become a compulsory part of education for all in the hope of increasing the level.

The 'new' approach to science teaching will be to provide a 'balanced science course' (useful for weighing up the options) containing physics, chemistry and biology in one subject. Technology subjects like electronics, craft design and technology (CDT) and control technology will be more widely available. Science will also become a larger part of the primary school curriculum.

## GCSEs And AS Levels

The GCSE is the new exam for 16 year olds and for those not taking the exam a national profiling system is being introduced to give information about each pupil's progress across the whole range of compulsory schooling.

The major change in moving from O-levels to GCSEs is the use of more in-course assessment through project work, practical work and written assignments in addition to the usual homework. Feel sorry for the poor teacher who has to set and mark this lot as well as filling in all the new assessment forms and finding time to do the odd bit of teaching!

The GCSE Electronics syllabuses aim to build knowledge, understanding and skills by practical investigations of electronic systems. Design, problem solving, construction, testing and communication skills are developed by following projects through from the initial idea to final realisation. Applications examples are used to show how electronics can help in society and the environment such as aids for the

deaf, blind and handicapped, monitoring pollution, improving the quality of life at work and leisure. The emphasis is definitely on relevance to the world we live in rather than the pursuit of knowledge for its own sake.

Practical activities account for up to 40% of marks obtainable (depending upon the exam board) and there are two written exam papers at the end of the course which together determine the final grade ranging from A to G. A major part of the practical work is the project in which the pupil has to design, construct, test and report on a circuit or system for a particular application.

Pupils are expected to know a range of standard building blocks (amplifiers, logic gates, buffers and so on) and to have a working knowledge of basic components, electrical quantities and fundamental concepts. They examine systems (signals and transducers, interfacing and microcomputers) and systems applications in telecommunications, television and radio. Passive and active components are studied and a logic course is included. There are also more general topics such as electronics in society and safety.

## The As Have It

At A-level more changes are afoot. In order to broaden the subject base and/or reduce the level of specialisation AS-levels have been introduced. These are roughly equivalent to half an A-level and can be taken as complementary subjects to the usual type. A sixth former might for example study two A-levels and two AS-levels.

As far as Electronics is concerned there are A-levels, AS-levels and an A-level electronics endorsement to a normal Physics A-level. The teaching material covered in an A-level electronics course is basically the same as that in the GCSE course and only differs in the depth of treatment. A GCSE pupil would be expected to know the function of logic gates in terms of a truth table and simple applications whereas an A-level student would also learn the characteristics, rise time, propagation delays in quantitative terms and design techniques using Boolean Algebra and Karnaugh maps.

Top-down or Bottom-up is not a reference to the posture to be adopted for GCSE teaching but to the continuing argument about whether to use the systems approach for teaching or to start at component level. Having tried both approaches over a period of ten years there is little evidence to show that one approach is better than another and like a good diplomat I find that a compromise between the two is most agreeable.

One exam board which will remain nameless has obviously been fruitlessly debating the same point since it has cleverly designed its GCSE and A-level syllabuses so that each syllabus leaves teachers free to adopt a bottom-up, top-down or middle-up/down approach to electronics in the classroom!

At a practical level the systems approach uses ready made plug together modules so that a temperature controller, say, can be quickly constructed from a thermistor block, a comparator block, a relay driver block and a small motor acting as a fan.

The problem here is that pupils find component identification difficult since all the boards 'look the same' and they lack practice in use of colour codes and in basic component forming, simple wiring and layout skills. The problem is highlighted in project work where they are suddenly asked to bring together a range of underdeveloped skills.

From the teacher's point of view the systems approach requires a great deal of material in hand since systems can be rapidly and reliably constructed in a short time. There is nothing worse than trying to cope with 30 budding electronics boffins racing each other to plug together as many modules as possible in seemingly random order, having completed your carefully planned practical exercise in 10 minutes.

On the other hand the 'bottom-up' approach using components inserted into some form of prototyping board or breadboard soon becomes limited since the average pupil finds circuit construction beyond a handful of components too time consuming and unreliable. Once again there is little in the way of structured teaching material available for this approach and the burden falls upon the teacher.

This problem was highlighted in a recent report from a task group on assessment and testing methods in secondary education headed by a Professor Black. The group expressed concern over pressures on teacher time, class sizes and resources for practical work.

The reduction of class sizes is a matter for Mr Baker's balance sheet but the provision of teaching material is a matter I have recently had to address as leader of a product design team at the Polytechnic of Wales.

The Polytechnic of Wales recently established an Electronics Centre to provide consultancy and short-course development services to industry. Recognising

the lack of suitable electronics teaching material available, a survey of teachers was undertaken to identify ways of reducing pressures on teacher time and school Electronics budgets. The result was the design of the Chipkits range of electronics teaching aids (see *Once Over*). Chipkits comprise three boards covering the basics of analogue and digital electronics each with a teaching package providing component lists, background theory, practical assignments, extension exercises and homework questions designed to assist teachers and encourage more pupils to take up a career in this exciting field of engineering.

### The TVEI Programme

Although only GCSE and A-levels have been mentioned so far these are not the only courses on offer. Many schools offer a range of TVEI modules in addition to GCSEs. The Technical and Vocational Educational Initiative was set up to develop work related skills (as well as testing pronunciation and memory of its title).

The Certificate of Pre-Vocational Education (CPVE) is also on offer in some schools and colleges and this leads into BTEC (Business and Technical Education Council) courses like ONC and OND (Ordinary National Certificate and Diploma) which can then be used as an entry into HNC and HND courses.

If you've managed to keep a clear head through all those abbreviations you now know that the education environment is about as dynamic as you can get. One certain thing is that whichever route is followed in electronics education and subsequent careers there will always be plenty of interest and opportunity.



# EDUCATION



## OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX • 031 667 2611

- The supplier to use if you're looking for
- ★ A WIDE RANGE of components aimed at the hobbyist ★
- ★ competitive VAT inclusive prices ★
- ★ mail order - generally by return of post ★
- ★ fast, friendly service ★
- by mail order, telephone order or personal call
- 1988 CATALOGUE NOW READY - SEND 2 x 18p STAMPS
- we do try to keep the goods we list in stock.
- Whether you phone, write or call in
- we'll do our best to help you.

Open: Monday-Friday 9.00-6.00  
Saturday 9.00-5.00

### MATRIX SYSTEMS 8052 BASIC 8044 BITBUS Custom Controllers

MATRIX is manufacturing customised controllers using the well proven technology of the Intel 8052AH Basic chip. Prototype hardware and software is easily built onto a MATRIX 8052 board by the customer or by MATRIX themselves. The control system, configured from the MATRIX prototyping board and the application specific circuit, is laid out on a single pcb using a cad system on which the 8052 circuit is already stored. A full product design facility is available from MATRIX including customised case design, ASIC design and sensor development. prototypes, including metal work can be delivered in 10 to 12 weeks.

This service is aimed at customised controllers built-in batches of 10 to 1,000 per annum. For example, MATRIX is supplying products for automatic mailing machinery, vehicle security and colleges of further education.

#### PROTOTYPING PRODUCTS

MX1	8052AH BASIC microcontroller	£200
BT1	8044 BITBUS networked microcontroller	£358
BT2	BITBUS starter kit for a PC system	£932

For further details contact:  
MATRIX SYSTEMS  
Silbury Business Centre  
356 Silbury Boulevard  
Milton Keynes MK9 2LR 0908 604848

# KEEP REGULAR

Don't miss out on your favourite electronics mag. Why search high and low for a copy? Let your newsagent take the strain and reserve you a copy each month.

Fill in your name and address on the form below and hand it to your local newsagent. It will keep you as regular as All-bran. Alternatively, you can eat the coupon. They you'll need the All-bran.



Dear Mr Newsagent  
Please order me a copy of ETI  
and reserve/deliver me a copy  
every month.



Note this magazine is available to your wholesaler through:  
SM Distribution, 6 Leigham Court Road, Streatham, London  
SW16 2PG. Tel: 01-677 8111.

Name \_\_\_\_\_

Address \_\_\_\_\_

*Higher education courses in electronics are many and varied. How to choose between them?*

# COURSES

## THE NEXT STEP

**F**or students starting their second A-level year this month, the time has come to make the decisions that concern life beyond the schoolroom. Applications for university and polytechnic degree courses have a December 15th deadline and although colleges and institutes of higher education will often consider candidates submitting applications in the spring and summer, to make sure of a place applications should be sent early in the new year.

The decisions to make over the next few months are numerous and important — they will decide not only how the next three or four years are spent but which way your career will be heading after that.

The first decision is whether to enter higher education at all or to head into the workplace straight from A-level. This is usually an easy choice to make — and if it isn't then the safest thing to do is apply for higher education anyway. Backing out of a course can be embarrassing but is a whole lot easier than trying to edge in at the last minute. Some colleges may even agree to defer entry for one year or two — although usually only if the job is for a specific period and preferably relevant to the course.

A third option is taking a year out. Many colleges strongly approve of a constructive period in the real world before starting a course. Some even give preferential treatment to such applicants. The year out need not be working in industry — a world tour of crop harvesting shows equal initiative and ambition. Most places will again agree to defer entry until the following year.

The temptation for students planning to take a year off is to sit out of the application process this time around. It is far safer and much more reassuring to get a course established and a place reserved now. After all, this time next year you'll be island hopping in Greece or road building in Tasmania and the last thing you'll want to do is spend hours telephoning home co-ordinating your parents' efforts at course hunting.

Once the decision to enter higher education has been made, the course and the level of qualification must be chosen. As an ETI reader the lure of an electronics qualification is probably strong but do bear in mind the differences between electrical and electronic work, the relevance of the word engineering and also the other more specialised subjects available. If you are certain that it is electronics in sound and music that interests you and little else, for instance, you might be more happy on a course like Salford's Electroacoustics option.

If you have any doubts as to your preferred area, a broader course encompassing Electrical and Electronic Engineering is probably a safer bet. Remember that you will meet many new areas of study which could turn out to be the subject you've been looking for all your life. Take with a pinch of salt the common advice that it is easy to concentrate on your particular interest by selecting relevant options in your third or fourth year — this is not always the case.

### University

Many A-level students (and often teachers) think of a university degree as one rung above those awarded by polytechnics and colleges. Although this is certainly untrue in terms of course content and academic achievement, there does remain a certain prestige value. Competition for university degrees is more fierce than for any other type of establishment and the

grades required for entry are correspondingly high. This year an estimated 160000 students will apply for the 70000 places available. This means that a slip of a single grade in your A-level results and conditional offers may be withdrawn.

### Polytechnics

Polytechnic degrees score over university degrees on a number of points. The first is the control of course content. While universities are autonomous bodies and can run courses with any content they wish, polytechnics have their courses reviewed by the Council for National Academic Awards (CNAA). Electrical and Electronic Engineering degrees are being aligned to provide an emphatic engineering applications orientation and these degrees are marked out by awarding a BEng rather than a BSc (it is possible that some courses may still award a BSc if review is due to take place shortly).

A second advantage is that if your A-levels go horribly wrong, there may be a HND course at the polytechnic on to which you can transfer.

Life at polytechnic is little different to life at university and the degrees count for just as much. Unless you are totally confident of achieving top A-level grades (and few people can truthfully claim that) it is sensible to apply to both.

### Colleges and Institutes of HE

The entry grades for these establishments are significantly lower and the courses are often regarded as an easy option. Yet in some cases degrees are validated by nearby universities and certainly the workload will be at least as high (terms will probably be longer as well). Again colleges and institutes have the advantage of running other electronics courses if A-levels go badly.

### Diploma of Higher Education

A DipHE is equivalent to two years of a degree and has similar entry requirements. There is however only one DipHE in Electrical and Electronic Engineering run in Britain — organised by Thames Poly.

### HND

Higher National Diplomas are offered by the Business and Technical Education Council (BTEC). These courses run at polytechnics and colleges taking two years of full time study, often combined with a year in industry as a three year sandwich. The entry requirement is usually the study of two A-levels — preferably Maths and Physics — only one of which needs a successful pass. BTEC National Certificates (see below) are alternative qualifications to A-levels if the relevant modules have been completed.

It may be possible for outstanding students on HNDs to transfer to degree courses and it is worth checking where this is allowed.

### Conversion Courses

For students who made the wrong choices at A-level and have found themselves unable to apply for engineering degrees and HNDs because their subjects are wrong, there are one year conversion courses called Higher Introductory Technology and Engineering Conversion Courses (HITECC). These run mainly at polytechnics and can be taken as a forerunner of another course there or elsewhere.

## BTEC Qualifications

Apart from HNDs, BTEC validates a variety of courses for students leaving school following GCSEs and for people with previous training in electronics wishing to update their skills or learn new specialisations.

Each BTEC course consists of various units of study organised by the attended college but subject to BTEC validation and moderation. The BTEC First Certificate of Achievement consists of a single module and can be completed in three months (or a year of part-time study). Normal entry requirements for such a course are 3 GCSEs.

The longer courses are BTEC's National Certificate (ONC) and National Diploma (OND). Again studied in modular form, the National Certificate generally takes 15 months of full-time study which can be geared toward desired specialisations by selection of different modules. As with other BTEC courses the study involves substantial practical experience and project work. Entry requires 4 GCSEs or O-levels.

The National Diploma is half as long again as the National Certificate, extended by the study of additional modular units and usually offered as a full-time course with the usual scholastic holidays.

Completion of any ONC or OND course is qualification for entry to BTEC Higher National Certificate (HNC) courses or for the HNDs mentioned above. Note that while ONCs and ONDs can usually be started at the beginning of any of the three terms, HNCs and HNDs start only in September. If you want to apply, get on the phone now!

Colleges offering BTEC courses also run short refresher courses using individual BTEC units.

Details of BTEC courses can be obtained from The London Electronics College, 20 Penywern Road, Earls Court, London SW5 9SU (telephone 01-373

8721) or participating colleges and polytechnics.

## Employment Training

Well worth a mention is the latest training scheme for the unemployed from the Training Commission (the Manpower Services Commission that was). Under the banner of ET (Employment Training) some 600000 places on the scheme will eventually be available each year — it gets under way this month.

The Training Commission is emphasising the structured and strategic study hopefully to BTEC or City and Guilds level — and participation is purely voluntary to ensure commitment on the part of both trainees and training providers.

The scheme is in two stages operated initially by an approved Training Agent who offers advice and support to applicants culminating in an individual action plan to be carried out by the Training Manager in the second part of the scheme.

For full details of ET contact the Training Commission, Room E433, Moorfoot, Sheffield S1 4PQ. Tel: (0742) 703810.

## Non-attendance Courses

It is of course possible to study from home while working full time. Teaching packages exist from open learning enthusiasts' courses such as those offered by the National College of Technology in Bicester (Tel: (0296) 613067) right up to degree level Open University courses requiring extreme dedication and a great deal of time.

## Listings

The lists that follow detail all non-university degree courses and all BTEC HND courses. University courses have been omitted since these are freely available from UCCA (telephone (0242)222444).

# COURSES

## ADDRESSES

CITY OF BIRMINGHAM POLYTECHNIC — Perry Barr, Birmingham, B42 2SU (Tel:021-356 9193)  
BLACKBURN COLLEGE — Feilden Street, Blackburn, BB2 1LH (Tel:0254) 55144  
BOLTON INSTITUTE OF HIGHER EDUCATION — Deane Road, Bolton, BL3 5AB (Tel:0204) 28851  
BRIGHTON COLLEGE OF TECHNOLOGY — Pelham Street, Brighton, BN1 4FA (Tel:0273) 685971  
BRIGHTON POLYTECHNIC — Moulsecomb, Brighton, BN2 4AT (Tel:0273) 693655  
BRISTOL POLYTECHNIC — Coldharbour Lane, Frelchay, Bristol, BS16 1QY (Tel:0272) 656261  
BUCKINGHAMSHIRE COLLEGE OF HIGHER EDUCATION — Queen Alexandra Road, High Wycombe, HP11 2JZ (Tel:0494) 22141 and Newland Park, Gorelands Lane, Chalfont St. Giles, Bucks, HP8 4AD (Tel:02407) 4441  
CAMBRIDGESHIRE COLLEGE OF ARTS AND TECHNOLOGY — East Road, Cambridge, CB1 1PT (Tel:0223) 63271  
THE POLYTECHNIC OF CENTRAL LONDON — 309 Regent Street, London, W1R 8AL (Tel:01-580 2020)  
COVENTRY (LANCHESTER) POLYTECHNIC — Priory Street, Coventry, CV1 5FB (Tel:0203) 24166  
COVENTRY TECHNICAL COLLEGE — Butts, Coventry, CV1 3GD (Tel:0203) 57221  
DERBYSHIRE COLLEGE OF HIGHER EDUCATION — Kedleston Road, Derby, DE3 1GB (Tel:0332) 47181; Western Road, Mickleover, Derby, DE3 5GX (Tel:0332) 514911 and Matlock, Derbyshire, DE4 3FW (Tel:0629) 2383  
DONCASTER METROPOLITAN INSTITUTE OF HIGHER EDUCATION — Waterdale, Doncaster, DN1 3EX (Tel:0302) 22122  
GWENT COLLEGE OF HIGHER EDUCATION — College Crescent, Caerleon, Newport, Gwent, NP6 1XJ (Tel:0633) 421292 and Allt-yr-yn Avenue, Newport, Gwent, NP9 5XA (Tel:0633) 51525  
HATFIELD POLYTECHNIC — P.O. Box 109, Hatfield, Hertfordshire, AL10 9AB (Tel:07072) 79000  
KINGSTON POLYTECHNIC — Admissions Office, Kingston Hill, Kingston upon Thames, KT2 7LB (Tel:01-549 1141)  
LANCASHIRE POLYTECHNIC — Preston, PR1 2TQ (Tel:0772) 22141  
LEEDS POLYTECHNIC — Calverley Street, Leeds, LS1 3HE (Tel:0532) 462903  
LEICESTER POLYTECHNIC — P.O. Box 143, Leicester, LE1 9BH (Tel:0533) 551551  
LIVERPOOL POLYTECHNIC — Rodney House, 70 Mount Pleasant, Liverpool, L3 5UX (Tel:051-207 3561), F.L. Calder Campus, Dowsefield Lane, Liverpool, L18 3JJ (Tel:051-428 4041), I.M. March Campus, Barkhill Road, Liverpool, L17 6BD (Tel:051-724 2321) and C.F. Mott Campus, Liverpool Road, Prescot, Liverpool, L34 1NP (Tel:051-489 6201)  
LUTON COLLEGE OF HIGHER EDUCATION — Park Square, Luton, LU1 3JU (Tel:0582) 34111  
MANCHESTER POLYTECHNIC — All Saints, Manchester, M15 6BH (Tel:061-228 6171)  
MIDDLESEX POLYTECHNIC — Admissions Enquiries, 114 Chase Side, London, N14 5PN (Tel:01-886 6599)  
NEWCASTLE UPON TYNE POLYTECHNIC — Ellison Building, Ellison Place, Newcastle upon Tyne, NE1 8ST (Tel:091-232 6002)

NEWHAM COMMUNITY COLLEGE — High Street South, London, E6 4ER (Tel:01-472 1480)  
NORTH EAST LONDON POLYTECHNIC — Assistant Registrar, Longbridge Road, Dagenham, Essex, RM8 2AS (Tel:01-590 7722) and Information Unit (01-599 5750)  
NORTH LINCOLNSHIRE COLLEGE — Cathedral Street, Lincoln, LN2 5HQ (Tel:0522) 30641  
THE POLYTECHNIC OF NORTH LONDON — Holloway Road, London, N7 8DB (Tel:01-607 2789)  
NORTH STAFFORDSHIRE POLYTECHNIC — Stoke on Trent Site: — College Road, Stoke on Trent, ST4 2DE (Tel:0782) 744531 Stafford Site: — Beaconside, Stafford, ST18 0DE (Tel:0785) 52331  
NORWICH CITY COLLEGE OF FURTHER AND HIGHER EDUCATION — Ipswich Road, Norwich, NR2 2LJ (Tel:0603) 660011  
OLDHAM COLLEGE OF TECHNOLOGY — Rochdale Road, Oldham, OL9 6AA (Tel:061-624 5214)  
OXFORD POLYTECHNIC — Gypsy Lane, Headington, Oxford, OX3 0BP (Tel:0865) 819000  
PLYMOUTH POLYTECHNIC — Drake Circus, Plymouth, PL4 8AA (Tel:0752) 221312  
PORTSMOUTH POLYTECHNIC — Museum Road, Portsmouth, PO1 2QQ (Tel:0705) 827681  
RAVENSBOURNE COLLEGE OF DESIGN AND COMMUNICATION — Walden Road, Chislehurst, Kent, BR7 5SN (Tel:01-468 7071)  
SALFORD COLLEGE OF TECHNOLOGY — Frederick Road, Salford, M6 6PU (Tel:061-736 6541)  
SHEFFIELD CITY POLYTECHNIC — Pond Street, Sheffield, S1 1WB (Tel:0742) 20911  
SLOUGH COLLEGE OF HIGHER EDUCATION — Wellington Street, Slough, SL1 1YG (Tel:0753) 34585)  
SOUTH BANK POLYTECHNIC — Borough Road, London, SE1 0AA (Tel:01-928 9898)  
SOUTH GLAMORGAN INSTITUTE OF HIGHER EDUCATION — Western Avenue, Cardiff, CF5 2YB (Tel:0222) 551111  
SOUTH LONDON COLLEGE — Knight's Hill, West Norwood, London, SE27 0TX (Tel:01-670 4488)  
SOUTHALL COLLEGE OF TECHNOLOGY — Beaconsfield Road, Southall, Middlesex, UB1 1DP (Tel:01-574 3448)  
SOUTHAMPTON INSTITUTE OF HIGHER EDUCATION — East Park Terrace, Southampton, SO9 4WW (Tel:0703) 229381  
SUNDERLAND POLYTECHNIC — Langham Tower, Ryhope Road, Sunderland, SR2 7EE (Tel:0783) 5676231  
TEESSIDE POLYTECHNIC — Borough Road, Middlesborough, TS1 3BA (Tel:0642) 218121  
THAMES POLYTECHNIC — Wellington Street, Woolwich, London, SE18 6PF (Tel:01-854 2030)  
TRENT POLYTECHNIC — Burton Street, Nottingham, NG1 4BU (Tel:0602) 418248)  
THE POLYTECHNIC OF WALES — Treforest, Pontypridd, Mid Glamorgan, CF37 1DL (Tel:0443) 480480  
WATFORD COLLEGE — Hempstead Road, Watford, WD1 3EZ (Tel:0923) 57500  
WEST GLAMORGAN INSTITUTE OF HIGHER EDUCATION — Townhill Road, Swansea, West Glamorgan, SA2 0UT (Tel:0792) 203482)  
WILLESDEN COLLEGE OF TECHNOLOGY — Denzil Road, London, NW10 2XD (Tel:01-451 3411)

**KEY**  
 FT full-time  
 SW sandwich  
 HE higher education

# COURSES

## Electrical and Electronic Engineering

Brighton Polytechnic	B Eng(Hons) and B Eng	FT3
Coventry (Lancaster) Polytechnic	B Eng(Hons) and B Eng	SW4
Hatfield Polytechnic	B Eng(Hons) and B Eng	SW4
Huddersfield Polytechnic	B Eng(Hons) and B Eng	SW4
Liverpool Polytechnic	B Eng(Hons) and B Eng	SW4
Manchester Polytechnic	B Eng(Hons) and B Eng	SW4
Newcastle upon Tyne Polytechnic	B Eng(Hons) and B Eng	SW4
North East London Polytechnic	BSc	SW4
North Staffordshire Polytechnic	B Eng	FT3
Plymouth Polytechnic	B Eng(Hons) and B Eng	SW4
Portsmouth Polytechnic	B Eng(Hons) and B Eng	FT3
South Bank Polytechnic	B Eng(Hons) and B Eng — option in Building Services Engineering	SW4
	M Eng	SW4 <sup>2/3</sup>
Sunderland Polytechnic	B Eng(Hons) and B Eng	FT3
Thames Polytechnic	B Eng(Hons) and B Eng Engineering (Electrical) and Electronic	FT3 (Dip HE FT2)
Trent Polytechnic, Nottingham	B Eng(Hons) and B Eng	FT3
The Polytechnic of Wales	B Eng(Hons) and B Eng M Eng	SW4

## Electronic Engineering

City of Birmingham Polytechnic	B Eng(Hons) and B Eng	SW4
Bolton Institute of HE	B Eng	FT3
Brighton Polytechnic	B Eng(Hons)	FT3
Brighton Polytechnic	BSc(Hons) Microelectronics and Information Processing	SW4
The Polytechnic of Central London	B Eng(Hons) and B Eng	FT3
Gwent College of HE	B Eng Electronic and Instrumentation Systems	SW4
Kingston Polytechnic	B Eng(Hons) and B Eng Electronic systems Engineering	SW4
	M Eng Electronic Systems Engineering	SW4 <sup>1/3</sup>
Lancashire Polytechnic	B Eng(Hons) and B Eng	SW4
Leicester Polytechnic	B Eng(Hons) and B Eng	SW4
Middlesex Polytechnic	B Eng(Hons) and B Eng	FT3
	M Eng Microelectronic Engineering Design and Production	SW4 FT4
The Polytechnic of North London	BSc(Hons) and BSc Electronic and Communications Engineering	FT3
North Staffordshire Polytechnic	B Eng(Hons)	FT3 SW4

## Combined Sciences with electronics option

Brighton Polytechnic	BSc(Hons) and BSc Combined Sciences: Science Majors — permitted pairings from Biology, Chemistry, Computer Studies, Electronics, Energy Studies, Geography, Mathematics, Physics, Statistics	FT3 SW4
Hatfield Polytechnic	BSc(Hons) and BSc Combined Studies — major or twin mode from Chemistry, Computing, Electronics, Human Biology, Applicable Mathematics, Applied Physics, Psychology.	FT3


Kingston Polytechnic	Statistics; twin mode only in Astronomy, Business Operations, Applied Geology, Manufacturing Systems, Philosophy	FT3
	BSc(Hons) and BSc Applied Science — Bioanalytical Science or Earth Science or Mathematical Modelling Science or Applied Physics with Microelectronics and Computing or Resources Science or Chemistry with Microelectronics and Computing	FT3
Leicester Polytechnic	BSc(Hons) and BSc Combined Studies — two subjects in years 2 and 3 from Accounting*, Biology*, Chemistry*, Computing‡, Electronics*, Law, Marketing, Mathematical Sciences*, Medical Laboratory Sciences*, Physics* (*subject available in FT and SW modes. ‡subject available in SW mode only)	FT3 SW4
North Staffordshire Polytechnic	BSc(Hons) and BSc Combined Science — two from Biology, Ceramics and Mineral Products Technology, Chemistry, Computing, Electronic Instrumentation, Geology, Physics, Statistics and Operational Research Methods	FT3
Oxford Polytechnic	BSc(Hons) and BSc Science — Modular degree in two fields chosen from Biology Catering, Computer Studies, Environmental Biology, Food Science and Nutrition, Geology, Mathematical Studies, Microelectronic Systems, Physical Sciences or one arts field listed in the Arts section, or one double field as listed in the appropriate part of the Science section	FT3
West Glamorgan Institute of Higher Education, Swansea	BTEC HND — option in Computer Aided Design Microelectronics, Optoelectronics	FT2

## Electrical and Electronic Engineering

Bolton Institute of HE	BTEC HND	FT2
Coventry (Lanchester) Polytechnic	BTEC HND	FT2 SW3
Derbyshire College of HE	BTEC HND	FT2
Gwent College of HE	BTEC HND	FT2
Huddersfield Polytechnic	BTEC HND	SW3
Leeds Polytechnic	BTEC HND	SW3
Liverpool Polytechnic	BTEC HND	FT2
Manchester Polytechnic	BTEC HND	FT2
Middlesex Polytechnic	BTEC HND Electrical Eng.	FT2
Newcastle upon Tyne Polytechnic	BTEC HND	FT2
North East London Polytechnic	BTEC HND — Electrical Electronic and Telecommunication options	FT2 SW3
North East Wales Institute of HE	BTEC HND	FT2
North Staffordshire Polytechnic	BTEC HND	FT2 SW3
Norwich City College of Further and HE	BTEC HND	SW3



# RECRUITMENT IN THE REAL WORLD

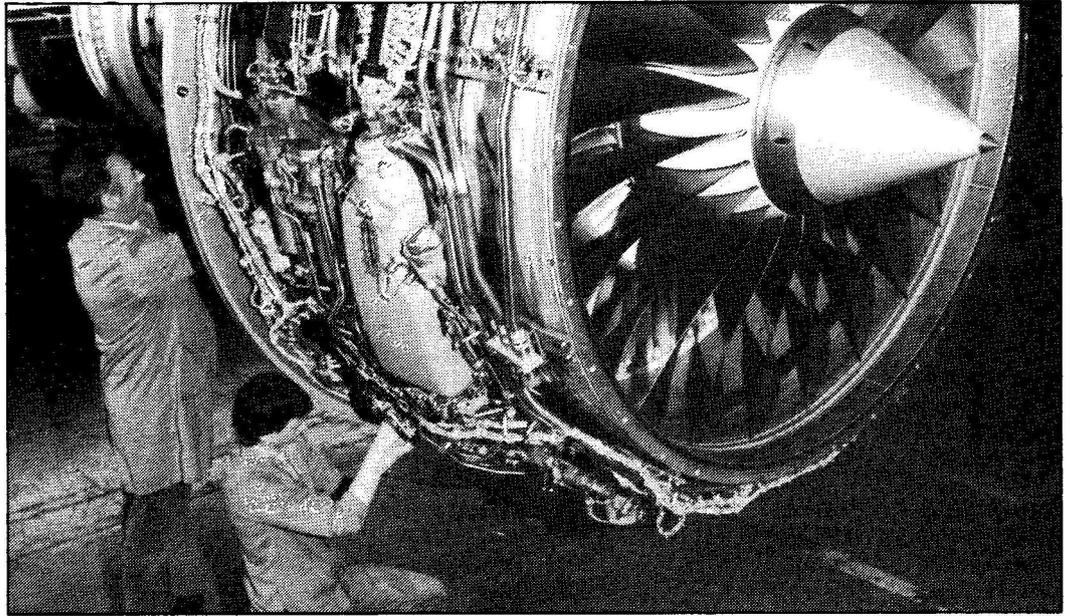

*The time is ripe for undergraduates to reach for their CVs and SAFs. Six companies in the employment market for electronics graduates display their wares and explain their recruitment methods*

## CAREERS

**I**n the final year of most degree courses, electronics students discover that the number of timetabled lectures and courses are drastically reduced from the nine to five arrangement of the first two or three years. Often whole afternoons are left free for the students to spend as they wish. Officially the time is allocated to allow research and work on the final year project (which usually runs over the winter and spring terms) but for many students the first few months pass all too quickly and the extra hours are slept away or spent polishing performances on the squash court.

The following term is then filled with concentrated project work coupled with the growing anxiety nurtured by the ever approaching final exams. On top of this the milk-round starts, with companies touring around the country inviting applications and organising interviews through the busy second and third terms.

Completing application forms takes an enormous amount of time and careful thought — first impressions do count and in most cases it is the application form that provides the initial contact between the employers and potential employees. Forms are best completed individually, partly to show enthusiasm and interest but mainly so that each application can be carefully tailored to show experience relevant to that particular company.

The most common complaint from employers (and the most common cause of failure at interview) is lack of preparation on the part of candidates — not only in finding out about the company but in thinking through personal history and its relevance to employers. All this can be tackled during the first term when time can be spent identifying personal strengths and weaknesses, reading up on prospective companies and preparing a draft CV and application form.

Some companies will accept applications at any time — even in the first and second years — although the main problem here is that it is much harder to compare different companies and keep your options open. Accepting a position is not necessarily an irreversible decision but should be treated with rather more caution than say choosing higher education

courses where having a couple of back-up possibilities is common practice.

By your final year you should have a fair idea of the type of work that interests you. If you haven't, then most careers services operate some kind of computer career matching which questions your interests and skills to produce a list of possible occupations. The results are generally very accurate, invariably hold a few surprises and can be very encouraging for people at a loss for ideas.

A qualification in Electrical and/or Electronic Engineering is a valuable commodity. It should be remembered that any degree opens doors to jobs in all sorts of careers completely disassociated from the subject studied. Engineering subjects are also considered to be among the hardest to study so these degrees are even more valuable for general use. Be prepared to be asked why you didn't pursue that subject as a career — engineering subjects are also among the most job-specific and branching off can be considering indicative of a bad degree choice or even failure.

The other option open is to continue higher education. Electronics provides a great many subjects for post-graduate research and sponsorship can make life as a Ph.D student more comfortable financially. Post-graduate courses are by no means limited to the college attended for the degree (although the process of application is simplified if you stay put).

To give you some idea of how the electronics industry conducts its recruitment, a selection of employers have provided us with details of their recruitment procedures, their requirements for candidates and their most common causes for complaint. This is not the place to go into an analysis of the interview situation, how to sit, what to where and when to laugh. These techniques can be learnt and should be practised unless you are a natural interviewee — again careers services should help.

Practice and preparation bring confidence and hopefully success in establishing your first choice of career. With forty years ahead to regret your decisions, it is worth climbing out of bed and off the squash court to put in some time and effort to get it right.

## AB Electronic Products Group

AB Electronics works in a wide variety of high technology fields, based primarily in South Wales but with subsidiary operations in south-east England and in West Germany, Austria, France and Sweden. It presently employs over 5500 people.

There are various areas of specialisation. AB manufactures components and sub-assemblies for almost every area of the electronics industry and can provide back-up for subcontracting assembly which includes design, development, assembly and testing facilities, sub-contracting work for companies such as IBM and British Telecom.

AB's Automotive Electronics division designs and manufactures vehicle electronics — anything from simple sensors and controls to complete vehicle/driver control systems. Its products are highly regarded in the industry and are used by Jaguar, Mercedes, BMW and Austin Rover among others.

The Microelectronics division has invested heavily in the rise of surface mounted assemblies, keeping the whole company at the forefront of this rapidly expanding technology.

There are also subsidiary companies in cable, satellite, military and aerospace electronics where extreme high quality and reliable operation are essential to meet stringent defence and CAA standards.

AB has recently opened its Technical Centre in Newport where new product ideas and techniques are generated and tested through to the developed stages. The advances achieved in the Centre are then passed to the main AB divisions. This Technology Centre is staffed by a high proportion of graduates.

Recruitment is publicised through ROGET, GET and GO. The company also visits universities and polytechnics during the Spring term, depending on the number and quality of applications already received. AB takes students for work experience and successful placements may lead to permanent posts. There is also a well designed degree sponsorship scheme which includes a bursary and a useful two

week induction training before the degree course begins.

Across the company last year, 450 graduate applicants were considered of which 250 were interviewed. The first interviews are informal two way discussions where the general attitude and flexibility of candidates can be assessed. The most common cause for failure at this stage is lack of awareness of how AB operates and what it is looking for. Another common problem is an inability to communicate in a straightforward non-jargon language.

The second interview stage is more formal. Technical matters are examined and more detailed personal assessment is made. AB's priorities here are to determine technical ability, particularly in areas of specialities relating to current operations and upcoming diversification. Communication skills are also important and adaptability is essential.


The number of successful applicants last year was 25 graduates and 5 postgraduates.

Thanks to the concentration of the company's various activities in South Wales, successful applicants receive a wide variety of basic training without the need to move around the country. Training commences with two weeks of induction followed by four to six months on design and development, four to six months in production engineering and control with some time in purchasing or sales. This follows four months in a test/product engineering department moving through a wide range of short term projects.

During this training programme (usually near the beginning) all recruits spend three months off work attending an Engineering Practice course at college if necessary. Further training as required is arranged on an individual basis. The final stage of training is a first appointment under the supervision of an experience engineer, which is usually completed about two years after joining the company.

Contact AB Electronic Products Group PLC, Abercynon, Mountain Ash, Mid Glamorgan CF45 4SF. Tel: (0443) 740331.

# CAREERS

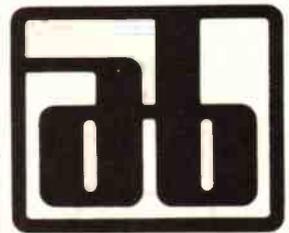

## Geophysical Service International Ltd

Geophysical Service International Ltd is an oil seismic exploration company operating throughout Europe, Africa and the Middle East.

The company is based in Bedford and was originally part of Texas Instruments Ltd as the European branch of TI's geophysical operation (the original TI was set up to use a new method of seismic study for oil in Texas) but now the company is part of the Halliburton group of companies. Data gathered by GSI or provided by its oil clients is processed in a number of GSI centres — the largest of which in this respect is Bedford which has extensive computer data processing technology.

There is a large graduate population at GSI. Recruitment doesn't take place in the usual annual drive, vacancies are advertised throughout the year and there is a rolling run of interviews. It does take part in the university and polytechnic milk run in the second academic term but welcomes applications to its Bedford headquarters at any time.

After preselection from CVs and application forms interviews take place in Bedford. There are separate interviews, with the technical staff (to establish technical background, capability and so forth) and with the personnel department (to examine interpersonal skills).

A good electronics background is essential for applicants in these fields, preferably with an emphasis

on practicality. GSI require candidates with the ability to self-start and to make decisions in the field. Candidates should be confident but not over confident.

Despite this emphasis on individual skills, teamwork is an important quality for employees at GSI. Teams operate in marine data gathering situations as well as in the field so that the ability to operate effectively in an integrated operation is essential.

The majority of electronics graduates taken into Geophysical Service International last year are training as instrument engineers to operate in the field.

For more information contact GSI, Manton Lane, Bedford MK41 7PA. Telephone: (0234) 27011.



## Mars Group of Companies In The UK

The activities of the Mars Group of companies stretch far beyond the manufacturing of sweets that you can eat between meals without ruining your appetite. Mars Incorporated runs eight businesses in Britain, keeping each as a separate company operating with a high degree of autonomy.

Mars Electronics is based in the Reading area and produces a wide range of 'transactional' electronics (mainly electronic systems for cash payment, coin vending and data retrieval). Products are taken from conception right through design, prototyping and manufacture to an international marketplace.

Mars Confectionery needs little introduction. The UK snack market is worth £11 billion a year and in the chocolate arena Mars has six of the top ten brands. Electrical and electronic engineers are employed mainly in manufacture and development.

Master Foods produces brand foods such as the Dolmio range of Italian pasta and sauces, Yeoman and Tyne Brand. Master Foods has achieved dramatic growth in recent years. Electronic engineers work in R&D, control and production.

Pedigree Petfoods has locations in Melton Mowbray and Peterborough and produces Pedigree Chum, Pal, Whiskas, Kit-e-kat and others. Electrical engineering graduates are involved in control, development and production.

Four Square is based around the Klix range of drinks systems, now the market leader. Operations are international and graduates in electronics are required for design of the microprocessor-driven dispensers, research and other areas.

Graduate recruitment is centralised for the Mars Group in Maidenhead. Specific vacancies are advertised in the national press together with the annual graduate recruitment drive through ROGET and university careers services.

Last year the group received about 4000 milk-round applications. The interview rate at Mars is high and some 1500 interviews took place. These are carefully structured to examine applicants for a broad range of skills, not simply those in which they have

been educated. Graduates can and do move between companies in the group so that the ability to adapt and succeed in a variety of environments is essential.

At interview Mars aims to examine a candidate for initiative, decisiveness, planning ability and problem analysis — important skills in both management and research. Equally important are the skills needed to integrate with an open working environment — Mars gives great emphasis to interpersonal skills; the ability to communicate and persuade effectively.

The commonest problem Mars encounters in candidates is lack of preparation. Interviewees are often unaware of the range of qualities required and react badly to unexpected general questions which have not been properly considered beforehand.

From the 1500 graduate interviews conducted for the Mars group last year there were 38 successful applicants, all commencing at salaries not less than £11500.

Once inside the company, graduates are trained for two or three years. This training is both technical and non-technical and will involve several different job functions to give a broad knowledge base to generate both understanding and mobility between different areas of business.

From an early stage, graduates work on a specific project of real and significant impact within the graduate's area of work. A recent example of such a project at Four Square was the design, installation and commissioning of a control system for a new coffee-grinding plant for Klix. Projects may be tackled in a group or alone but either way regular individual reviews are held to assess progress and plan training for the future.

Graduate recruitment is flexible and engineers are welcome in commercial as well as technical functions.

Contact Mars Graduate Recruitment Manager, Shoppenhangers House, Shoppenhangers Road, Maidenhead, Berkshire SL6 2PX. Tel: (0628) 39211.



## NE Technology Ltd

While career hunting among the giants of the electronics and engineering industries, it should be remembered that there are a large number of smaller companies offering graduate opportunities that in many respects cannot be matched by multinationals. Many people find the politics and attitude of large company operations a stifling and daunting atmosphere in which to work and prefer the more friendly attitudes that can be achieved in a smaller company.

NE Technology Ltd is a new company formed following a management buyout of Nuclear Enterprises. The company designs, develops and manufactures instruments involved in the measurement of radiation, primarily for use in the nuclear industry at Sellafield and similar locations and also equipment for medical radiotherapy under contract from the NHS.

NE employs 200 people and is based in Beenham in Reading. It operates four project teams developing its radiation equipment. Vacancies are advertised through the Current Vacancies listings from Central Services and require attributes specific to the posts available. One of the positions available at present for instance is for a software engineer familiar with C and MSDOS for 6800s together with a working knowledge of IBM PCs. Such specific criteria are rare within the sphere of general applications and if your

personal skills and interests match a smaller company's requirements then a successful career can be established very quickly.


NE expects to receive between thirty and forty applications for each post and reduces these through a preselection procedure based on relevant experience and qualifications to around six interview candidates. These are invited to Reading for a 2-stage interview process. A personnel interview is followed by a meeting with the head of department and project team to which the candidate is applying.

Although the quality of candidates by the time interviews are reached is high, the most common failing is the inability of applicants to apply their academic knowledge to practical problems and that subjects studied as part of a degree course are understood only in theoretical terms. Applicants are also often unable to effectively express themselves to demonstrate their particular abilities. This second failing is probably caused by ineffective preparation and inexperience in the interview situation.

Successful candidates at NE Technology Ltd are allocated to the relevant project team and undergo a training program that involves an initial induction in the various operations of NE (finance, marketing, production and so forth) to familiarise the entrant with the operation of the company as a whole.

For further information contact NE Technology Ltd., Bath Road, Beenham, Reading, Berks RG7 5PR. Tel: (0734) 712121.

# CAREERS

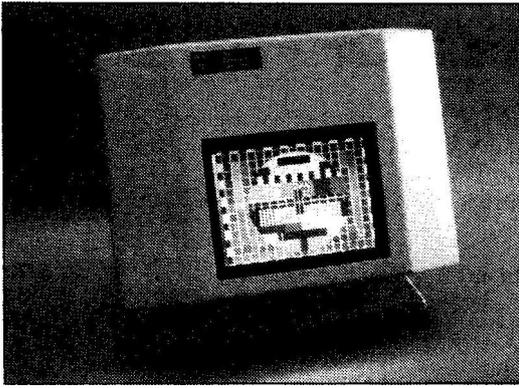

The entire Philips organisation employs over 340000 people worldwide. Over 20000 of these are based in the UK. The Dutch base of Philips has resulted in the company profits suffering from the weakness of the dollar in the last two years. Semiconductor operations were also hit by the slump of 1984 and 1985. Despite these adverse conditions Philips last year achieved a 7% increase in sales and is highly active in the graduate recruitment arena, last year accepting 150 graduates to UK posts.

A certain amount of recruitment also takes place for graduates transferring directly to the Philips bases in the Netherlands, either immediately or after training in the UK.

Graduate recruitment in the UK is centrally organised at Redhill and an annual vacancy booklet is produced entitled 'Graduate Opportunities with Philips' which details all positions available to UK graduates over the following twelve months. The

## Rolls-Royce plc

Rolls-Royce plc needs little introduction. The company has 42,000 employees working at sites in Derby, Bristol, Glasgow, Leavesden (near Watford), Ansty, Coventry and at a number of overseas subsidiaries.

Rolls-Royce is amongst the world leaders in the design, development and manufacture of gas turbine engines. Their engines power airlines, executive jets, fighter aircraft, helicopters, ships and power stations all around the world.

The search for graduate begins early with substantial school liaison to increase young people's awareness of engineering in general and of the variety of training programmes offered by the Company. The actual graduate intake is advertised through the normal recruitment literature (GO, GET, DOG, ROGET and so on) and through autumn visits to universities and polytechnics where students are able to talk informally about the company and the possibilities it offers.

Candidates that are shown by their applications to have the requisite qualifications are usually interviewed on the University and polytechnic milk-round. If successful at this stage they will be invited to attend a Company selection day — Candidates are interviewed by personnel and technical specialists so that their aptitudes and aspirations can be explored in detail.

The important qualities applicants should show at interview are analytical ability, communication skills, enthusiasm and drive. The most common cause for complaint among interviewers is that candidates are inadequately prepared — not only in their knowledge of the work and products of Rolls-Royce plc but in their own attributes and experience.

1989 edition is due for publication in November and is distributed to all universities and polytechnics. It is also available from the address below.

The detail of this booklet ensures that graduates apply for a specific position within the company rather to the group as a whole. Applications are initially examined by the centralised recruitment base — they dealt with 1500 applications during the 1988 milk-round (to April). Candidates with suitable experience are invited either for primary interview there or are referred directly to the section involved.

The milk-round tour of colleges from January to Easter is often the venue for the centralised preliminary interviews and the majority of those interviewed were referred for secondary interviews, which take place in the separate sections of Philips. These in-depth interviews consist of two stages — an initial panel interview relating to technical ability and experience followed by a personal interview to determine communication skills, the aptitude to learn and the candidate's personal strengths and weaknesses. The ratio of second interviews to successful candidates is around the industry norm — about 4:1.

As candidates have applied for specific vacancies it is expected that they will possess some relevant experience to that position either as academic knowledge or practical work experience in the industry (or even both). For successful candidates each job has specific training to augment that experience with internal training facilities recognised by most professional institutions as providing the basis for qualifications further to degree awards where appropriate.


For further information contact Philips Electronics Graduate Recruitment Office, Cross Oak Lane, Redhill, Surrey RH1 5HA. Tel: (0293) 785544.

All engineering graduates undertake a training period of one or two years which includes periods of drawing instruction and workshop training. This is followed by a 'design-and-make' project. Thereafter attachments are arranged in a variety of departments designed to give the graduate a broad understanding of engineering at Rolls-Royce. Those who do wish to specialise in electronics are able to do so. The last of these moves is usually to the area where trainees will take up their first permanent position.

Rolls-Royce is strong on leisure activities and provides sports and social clubs which are extensively used by its many young graduate employees. Graduates entering the company as engineers can expect to start on £9,500.



# CAREERS

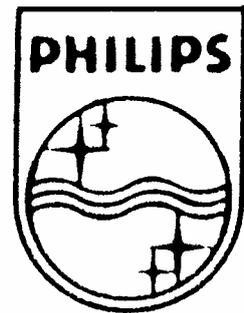

# COMPETITION RESULTS


## REACH FOR THE SKY

The reach for the sky competition in the June and July issues brought in a flood of entries from readers avid to win the £1300 satellite TV system. The judges' decision on the order of importance of the features listed was:

- 1 Unobstructed southerly views
- 2 Receiver bandwidth
- 3 Baseband output
- 4 Single button channel selection
- 5 Receiver remote control
- 6 Parental channel lock
- 7 Receiver styling

The position of the low flying satellite in the part II spot-the-satellite competition is shown below and the lucky winner drawn out of the ETI stetson was: Mr P Burrows of Colliers Wood in London.

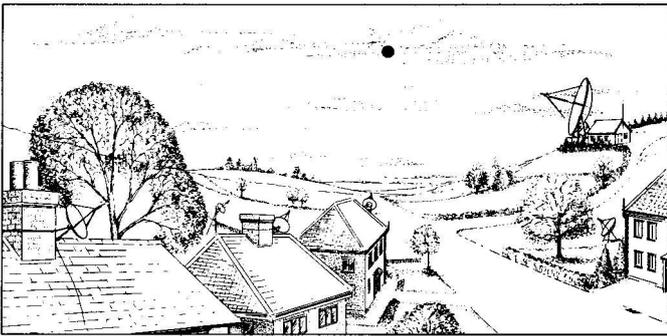Mr Burrows will soon be adorning his garden with a Pace SR640 satellite receiver, Vivor 90cm dish and assorted other bits and pieces to make him the envy of his neighbourhood.



## DEGREES OF FREEDOM

The competition in the July issue to win one of six Maplin maximum/minimum thermometers also attracted a record number of entries. The vast majority of readers had little difficulty deciphering the cryptic temperature descriptions. The answers were:

The body in question	body temperature	98.4°C
Bradbury's burning books	the book 'Fahrenheit 451'	451°F
60% tin 40% lead	melting point of solder	188°C
Downright	absolute zero	-273°C
The old ice	melting point of water	32°F
Gas mark 5	according to the Assistant Editor's Mum's cookbook	193°C

The six lucky winners, first out of the Editor's boot, were:

- Mr T K Parkinson of Hartlepool
- Mr S Hall of Aberdeen
- Mr J R Gray of Manchester
- Mr R P Willis of Northampton
- Mr C Carey of Folkestone
- Sgt Menzies in Gibraltar

Our thanks to all who entered, congratulations to the winners and commiserations to the not-so-lucky-this-time.

### CRICKLEWOOD ELECTRONICS

SUFFERING FROM COMPONENT DEFICIENCY?

**Symptoms:** Frustrated, half-built projects, sleepless nights, non-working equipment, out of stock blues.

SEE YOUR SPECIALIST!

## CRICKLEWOOD ELECTRONICS LTD

The components stock centre — the fast solution to component problems, old, new, rare and common

SERVICE IS OUR OBSESSION

MAIL ORDERS, TELEPHONE ORDERS, CREDIT CARDS, CALLERS WELCOME

## CRICKLEWOOD ELECTRONICS LTD

CRICKLEWOOD ELECTRONICS LIMITED  
40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET  
Tel: 01 450 0995 & 01 452 0161 Telex: 914977



## PROFESSIONAL SURVEILLANCE EQUIPMENT KITS

- **MTX** Micro-miniature VHF transmitter. The smallest kit on the market measuring an incredible 17mm x 17mm including on-board mic. Super sensitive. Fully tuneable over FM band, 9V operation with range up to 1000m. **£10.95**
- **VT500** High power version of the MTX with on-board PA stage providing 250mW of RF. Measures just 20mm x 40mm, power requirements 9-15V. Excellent sensitivity and stability. Fully tuneable over FM band. Ranges over 3000m can be expected. **£12.95**
- **VOX75** Voice-activated transmitter. Variable sensitivity trigger level switches transmitter on when sounds are detected. Stays on for time delay variable between 1-20 sec. Fully tuneable output covers all FM band. Very sensitive and low standby current through CMOS circuitry. 9V operation, range up to 1000m. Measures 30mm x 40mm. **£15.95**
- **CTX900** Sub-carrier scrambled transmitter. Audio is double modulated providing very secure transmissions. Any unauthorised listener will not be able to demodulate signal without DSX900 Decoder unit. Variable modulation on-board. Fully tuneable output covering FM band 9V operation, range up to 1000m. Measures 30mm x 40mm. **£18.95**
- **DSX900** Decoder unit for CTX900. Connects to earphone output of receiver to descramble signal from CTX900. Monitor using small speaker or headphones. Variable decode frequency on-board for best resolution. 9-12V operation. Measures 35mm x 50mm. **£17.95**
- **TLX700** Micro size telephone transmitter. Connects onto line at any point and requires no batteries. Clearly transmits both sides of conversations on both incoming and outgoing calls. Undetectable by phone users. Fully tuneable output covering FM band. Range up to 1000m. Measures just 20mm x 20mm. **£9.95**
- **ATR2** Micro size telephone recording unit. Connects onto line at any point and connects into ANY normal cassette recorder, standard or micro having MIC and REM sockets. Requires no batteries. Switches recorder on silently when phone is used for incoming or outgoing calls, switches off when phone replaced. Clearly records both sides of conversations. Undetectable by phone users. Measures 10mm x 35mm. **£10.95**
- **XML900** RF Bug Detector/Locator. Wide band input circuitry detects presence of RF field and triggers flashing LED and piezo bleeper. Variable sensitivity enables source of transmission to be pinpointed to within 6 inches. Max sensitivity will detect MTX or similar transmitter at around 15-20 feet. 9V operation. Measures 55mm x 55mm. **£21.95**

All kits come fully documented with concise assembly and setting-up instructions. High quality fibreglass PCB and all components necessary to complete the module. All prices are inclusive but please add £1.50 to cover P&P. Orders over £50.00 post free. Please state requirements clearly and enclose cheque or PO to cover.

Phone orders on ACCESS or AMEX accepted. Tel: 0827 714476  
NOTE: It is illegal to operate a transmitter in the UK without a licence  
Send 9x4 SAE for full catalogue of these and other surveillance kits

SUMA DESIGNS (Dept ETI), THE WORKSHOPS, 95 MAIN ROAD  
BAXTERLEY, NR ATHERSTONE, WARCS CV9 2LE. TEL: 0827 714476

# GOING IT ALONE

# BUSINESS

**T**he thought of starting your own business runs through the minds of many people. It has been a dream of mine ever since my school days. In the last few years it has become virtually a fashion to be your own boss with help available from the government, banks and various small firms organisations. Whether you will be successful or not is entirely up to you — probably the best incentive of all!

The business of electronics is quite different to other general businesses such as shopkeepers, hairdressers, builders and plumbers which make up over 40% of new small firms. Electronics covers such a wide area of disciplines that it is essential to know exactly which area you want to concentrate on.

## Your Potential

Right from the start you must have a clear personal objective. Only then will it be possible to direct a company in such a manner as to realise these objectives. Those who simply have a vague feeling that it would be a good idea to start up on their own or have visions of an easy life ahead and plenty of money would be well advised to abandon the idea from the beginning.

It is not my intention to repeat all the information easily available elsewhere but to concentrate on how I personally made the decision and decided to establish Sage Audio, and to eventually build the company into a stable and successful position as a market leader.

## Background

Your background is important to the success of your business. Your business will almost certainly be based on past experiences in one particular field, whether this is audio, radio, computing, design and development or whatever.

I have always at heart been interested in audio sound reproduction from the mid 1960s when I bought a pair of Sinclair Z12 germanium 12W power amplifiers and was suitably impressed by their sound quality.

Prior to setting up Sage Audio, I worked for 12 years for Thorn EMI Ferguson in Essex in the development department designing hi-fi equipment. There I learnt a great deal both technically and in experience and studied for various qualifications.

I have always had a flair for inventiveness and achievement and this was the major influence in the success of Sage Audio. Many new and innovative ideas were born while I was employed by Thorn, including the constant  $V_{ce}$ , constant current distortionless amplification block which was to form the heart of all Sage Audio products.

In 1981 I moved to Bradford and worked for Bradford Engineering Centre — a large research and development laboratory. Here, Sage Audio was finally born. At BEC I was engaged in developing a wide range of products from stereo TV to switch mode power supplies to high frequency video circuits. The experience gained from some of the country's top research engineers combined with my previous audio knowledge and a few short courses on business study armed me with all the tools necessary to 'go it alone'.

My first step into business, and a step I would advise anyone to take, was to start up while still employed. I started by selling high quality components both for the audio market and the power industry. This also involved selecting and grading power components to very tight specifications.

At this time I had been researching for around 18 months into very high speed video amplifiers and SMPS circuitry. I soon realised that in video high performance *means* high performance and anything with a slew rate of less than  $500V/\mu s$  is laughed at.

Using my graded components and some novel techniques I managed to build an amplifier with a staggering performance specification of over  $9000V/\mu s$ , a 3dB power bandwidth of DC to 200MHz at 50V output and a risetime of 1.7ns.


This was for use on a 64kHz line rate high performance VDU monitor. Through my incessant urge for achievement (or possibly just out of curiosity), I often wondered what this high slew rate amplifier would actually sound like if connected to a loudspeaker.

Since MOSFETs were still in their infancy, as output devices I used a couple of T9064 high frequency transistors which use a very special multi-emitter fingered structure and was truly amazed at the clarity and openness of the sound. I was clearly hooked on high slew rate amplification and from then on any other audio amplifier sounded lifeless in comparison.

I decided to design a good audio power amplifier with a high specification based on the video techniques I had pioneered. In 1984, BEC decided to move to London and this finally gave me the incentive to leave full time employment and to really go it alone.

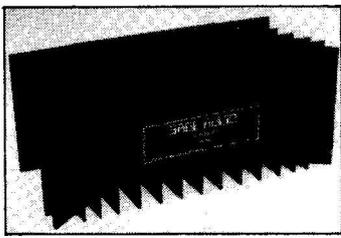*Les Sage talks about Sage Audio — how it expanded out of the bedroom into a 3000 sq ft factory — and gives some insights into starting your own business*





Within one week I had formulated a rough business plan, sought advice from my solicitor and bank and finally made up my mind.

## Product Development

Most ETI readers nowadays firmly associate me with high quality, high specification power amplifiers. However, in 1984 these were still just a dream. I planned right from the start that if a business is to succeed, it must be in manufacturing and not just component distribution. After all we cannot all be shopkeepers or there would be no customers!

A short college course (or three!) on business studies helped me on my way, firmly implanting the notion that a country's wealth is based on its manufacturing capabilities and not just selling imported goods.

To develop a new and highly innovative product such as the Superamp in a professional manner would take at least a year and a great deal of money. As bank loans are difficult to come by for new businesses (usually requiring three year's trading first) I started Sage Audio in 1984 as an electronics consultancy business to build up the required cash to launch the main business of audio power amplifiers. During this time I could do as much market research as I liked.

## Market Research

It cannot be stressed enough how important market research is to a product's success. Information gathered will enable you either to identify an existing market or to accurately estimate whether or not a market could be created.

One market which stood out like a sore thumb to me was the need for good quality audio modules at realistic prices. Market research showed that in the past ten years British hi-fi had flourished in the specialist hi-fi shops overshadowing imported units on the simple basis of good sound quality — names such as Krell, Musical Fidelity, Quad and Naim. Even today much of this equipment remains expensive for the average enthusiast who is left to buy a foreign midi stack system with his limited budget.

My market research revealed a large gap in the market for hi-fi quality power amplifiers. Manufacturers come and go but none offer real hi-fi performance by today's standards. Such names as ILP, Crimson, BK and so forth have filled the gap at the lower end of the market (for discos and the like) with cost effective modules of average technical performance using standard components.

However, the British hi-fi scene has made leaps and bounds in performance in the last ten years and there was a clear requirement for a top quality module at a realistic price to match today's hi-fi systems and to compete with all the big names.

The whole concept of the Sage Audio modular hi-fi is its flexibility, ease of construction and low cost enabling a custom hi-fi system to be built equal to or better than esoteric (and expensive!) units from the big names in hi-fi.

## Question Time

*How did you raise the finance to launch your new power amplifiers?*

I knew I had the product but not the cash to develop it. The Superamp/MOS range of power amplifiers we see today use very advanced circuitry and components including the latest surface mount devices and matched semi-conductors throughout. The cost of introducing SMD technology and the need for special output devices was prohibitive.

Nevertheless I went ahead. I invested £8000 of my own money and a £2000 government grant and took no wage from the business for a year.

During this period I could not easily get a bank loan. I had to earn extra cash to cover the R&D costs.

A stroke of luck came my way in the shape of a US company which I had contact with during my early days as a design consultant. The commission was to design an audio duplex chip for use in some telecommunications equipment. To cut a long story short, the circuitry was designed in just six weeks, the chip mask designed in the US and manufactured in the Far East.

The design was a single chip which encompassed a microphone amplifier, automatic level control, patented duplex control circuitry and an audio output stage. A full 2-wire feedback-free no hands communications system could then be built.

This chip design has been exclusively licensed to them for four years but by January 1989 will be on sale worldwide.

*Could a future ETI project be based around this chip of yours?*

Yes, certainly. I plan to produce such a project early in 1989 especially for ETI.

This chip helped raise the finance to fully develop the Super series power amplifiers you see today.

*At what stage did you acquire premises?*

Most of the early development work was done at home in a bedroom converted to a laboratory and then later moved to the garage. At this time I was doing all the work on my own. However, by late 1985 I managed to acquire premises in Bingley close to the famous Ilkley Moors. These were required for production of the newly designed Superamp.

I started by subcontracting most of the building and assembly work out to private firms. I also took on a part time secretary and part time assistant.

Money was tight despite the royalties received from the duplex chip but more design work for various companies came in, including work for an SMPS which really helped in those days.

*What about the MOSFET amplifiers — How did they evolve?*

Despite the fact we claim our bipolar Superamp module can outperform all other MOSFET modules, market research (and our customers) showed us the hi-fi market was really for MOSFETs (especially for digital audio equipment). Unfortunately at that time the only MOSFETs around were the H-pack types used by most other manufacturers which could not meet our stringent specification requirements.

You see, we wanted to achieve virtually zero distortion of any kind which required extremely accurately matched MOSFETs. The design goal for the SuperMOS was 250V/ $\mu$ s and 0.0001% distortion, although this finally ended up as 0.0002%. To achieve this specification, we managed to find a company to build a special MOSFET to our specifications with tight tolerances on certain parameters.

This was necessary as the SuperMOS amplifier uses class A output circuitry and hardly any feedback at all hence the need for special output devices designed for active class A use. These cost us an arm and a leg each and had to be purchased at a minimum of 5000 pairs per year. This took most of the profits from the Superamp project. From then on the original SuperMOS took off and this has been our steady bread and butter ever since.

*What is your main market for these modules and are these markets those you anticipated?*

The majority of our customers are hi-fi enthusiasts and hobbyists both in this country and abroad. In fact 60% of our trade is abroad and we have sold to just about every country, although the majority of export orders are from Denmark, Sweden, Australia, Hong Kong and (of all places) Japan.

Superamp modules have been sold to schools and Universities, science institutions, physics laboratories, TV and radio stations, banks and even 20 or so SuperMOS modules for use as ultra low distortion power supplies in the Sahara Desert!

Many of the orders, particularly in the last year, have come from sources undreamed of — hotels, PA contract companies, the army and the motor trade.

Export particularly caused us to increase our staff in 1986/7 to four full time and three part time. We also required telex and later fax machines to improve our trading position worldwide.

*What about the SuperMOS MkII — what made you develop such an amplifier in the light of the success of the original SuperMOS module?*

Actually, this came about due to some inaccurate earlier market research. We assumed the SuperMOS I rated at 150W in class A mode would be sufficient for domestic hi-fi systems. This is not so. With modern loudspeakers, the days of 100W hi-fi are long gone. All the big names in hi-fi now produce 250W top of the range systems. People kept asking us if it was possible to obtain more power from the modules.

We decided that to remain the number one power amplifier manufacturer we had to develop a MkII version with an output capacity to cover the range 100-500W still in pure class A mode.

This was a tall order but we achieved it and in the process added six other sound improvements. This module was designed to compete directly with the biggest and best power amplifiers available from Japan and the US such as Krell, Musical Fidelity, Citation and the like, but at a reasonable price compared to these ready built units.

*Has the SuperMOS MkII been as successful as the MKI?*

The SuperMOS II with its higher power capacity has appealed to a much larger market and its phenomenal success has caught us with our pants down. Since its launch in February this year, sales have now outstripped all other modules.

We have now had to move to larger premises in Bradford and have acquired a 3000sq ft factory for production of this and all other units. We do not subcontract out any work now. It is all done in house. This has meant a further increase in staff to eight full time and two part time.

There has been some delay in fulfilling orders in the wake of this massive increase in sales and move of premises but all our customers have been patient and understanding. I'd like to take this opportunity to thank them.

*Have the banks been helpful to you when you expanded?*

As it happens, we have not had to take a bank loan as yet. We have consistently piled all profits back into the business, making it as financially sound as possible before we ask for a loan.

*Now you have expanded, what are the plans for the future of Sage Audio — or are these secret?*

Not at all. There have been many changes within the company over the last few months. The expansion has caused us to flex our muscles a little more. We have gained some loudspeaker cabinet manufacturing capacity and hope to introduce a range of loudspeakers, mainly for export, by spring 1989.

Sage Audio, as it was, does not now exist. For tax reasons, we have split the business into three companies. Sage Audio will continue the main activities of amplification modules. Sage Hi-fi will concentrate on loudspeaker manufacture. Sage Electronics is a pure research company developing new products and ideas, not necessarily relating to audio — such as SMPS.

With fingers in so many pies, we hope to remain a stable company with a steady growth rate.

*Will the speakers continue the Sage tradition and be sold in kit form?*

No, loudspeakers will be ready built but will offer the option of 'bi-amping' with a compartment to house the electronics. They will be called the 'Seven Sages'.

*Will there be a SuperMOS MkIII?*

Definitely not. We have gone as far down the high performance amplifier road as we can. We have had no competition for the SuperMOS I modules in three years and do not expect anyone to compete on the SuperMOS II for a long time to come.

To be launched in January 1989 will be a range of three very high powered modules called the power series. These are 500W, 1000W and 1500W class AB power amplifier modules with a performance specification similar to the SuperMOS I modules. They will not be integral like the Super series but will have a plate construction with only the driver circuitry encapsulated and separate output MOSFETs with a bolt-on heatsink. This gives them the advantage of repairability. These too use specially built output devices and these are aimed at the professional market to whom we currently sell the SuperMOS II.

Also to be released at the same time is a matching pre-amplifier for the Super series modules.

*You mentioned tax earlier. Can you give advice to readers on tackling this problem and where they should go to seek advice on starting up a business.*

Tax is a frightening subject to most people as it is very complicated and few ordinary people understand anything about it.

I found my local tax office to be very friendly, helpful and patient while I learnt about the subject and sorted out their questions. You don't receive a tax demand for at least 18 months from first trading so it is not a worry at the start.

For general advice on running the business I found the 'Small Firms' centres very useful, friendly and helpful, particularly the Small Firms centre in Leeds City Square. They have given me much free advice and guidance on a number of points — premises, law, finance, export and so on.

If you do decide to go it alone, have clear business objectives and make sure you have done your market research. Ensure you have at the very least £1000 spare 'gambling' money to invest in the business. Be prepared to work long hours for apparently little or no rewards at first. Be willing to learn and ensure your spouse is understanding and behind you all the way. Good luck!

# BUSINESS

ETI



## GET INTO ELECTRONICS


## PASS THOSE EXAMS (GCSE)

## MAKE THAT PROJECT

## GO FURTHER, DO BETTER
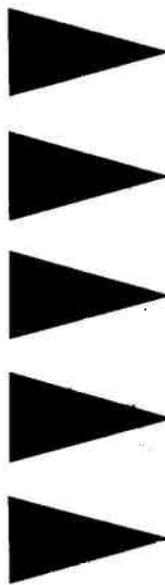
## DESIGN & BUILD WITH PRIDE\*

\***SAFE, NO SOLDERING, BATTERY POWERED.**  
(Battery replacing power supply — price £10.00  
p&p £1.00) — regulated — 5 volts, 300mA —



### THE ELEMENTARY LEARNING PACKAGE

2 Books  
2 WALL CHARTS  
125+ NEW COMPONENTS (5 CHIPS)  
1 RESISTOR COLOUR CODE CALCULATOR

OVER 200 PARTS  
**PRICE £25.00**  
+p&p £5.00

### THE BEGINNER CONSTRUCTOR PACKAGE

5 BOOKS  
350+ NEW COMPONENTS (10 CHIPS)  
1 TEST METER  
1 RESISTOR COLOUR CODE CALCULATOR

OVER 400 PARTS  
**PRICE £55.00**  
+p&p £5.00

### THE SCHOOLS AND PROJECT CONSTRUCTORS PACKAGE

10 BOOKS  
1000+ NEW COMPONENTS (25 CHIPS)  
1 HIGH QUALITY TEST METER  
1 RESISTOR COLOUR CODE CALCULATOR

OVER 1300 PARTS  
**PRICE £95.00**  
+p&p £10.00

### THE ADVANCED CONSTRUCTORS PACKAGE

12 BOOKS  
2000+ NEW COMPONENTS (50 I.C.'s)  
1 V. HIGH QUALITY TEST METER  
1 REGULATED POWER SUPPLY


OVER 2100 PARTS  
**PRICE £160.00**  
+p&p £15.00

### THE COMPLETE CONSTRUCTORS PACKAGE

15 BOOKS  
3000+ NEW COMPONENTS (100 I.C.'s)  
2 PROFESSIONAL TEST INSTRUMENTS  
20+ HIGH QUALITY TOOLS (+ SOLDERING IRON)  
1 REGULATED POWER SUPPLY

OVER 3300 PARTS  
**PRICE £260.00**  
+p&p £20.00


CONSTRUCTORS SOLDERING PACKAGE — TEMPERATURE CONTROLLED IRON, SOLDER, 6 SOLDERING TOOLS — Price £65.00 p&p £10.00  
PROFESSIONAL SOLDERING PACKAGE — PROFESSIONAL TEMPERATURE CONTROLLED IRON, ANTI STATIC MAT, 1/2kg SOLDER, 10 PROFESSIONAL SOLDERING TOOLS PRICE £160.00 p&p £15.00  
CONSTRUCTORS TOOLS PACKAGE — OVER 50 HIGH QUALITY ELECTRONICS TOOLS PRICE £55.00 p&p £10.00  
PROFESSIONAL TOOLS PACKAGE — OVER 100 PROFESSIONAL ELECTRONICS TOOLS — PRICE £160.00 p&p £15.00

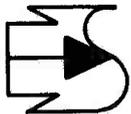

# ELECTRONICS SUCCESS

PO BOX 10  
ST ANNES ON SEA  
LANCS  
FY8 1SA

## PROFESSIONAL GRADE AMPLIFIER MODULES

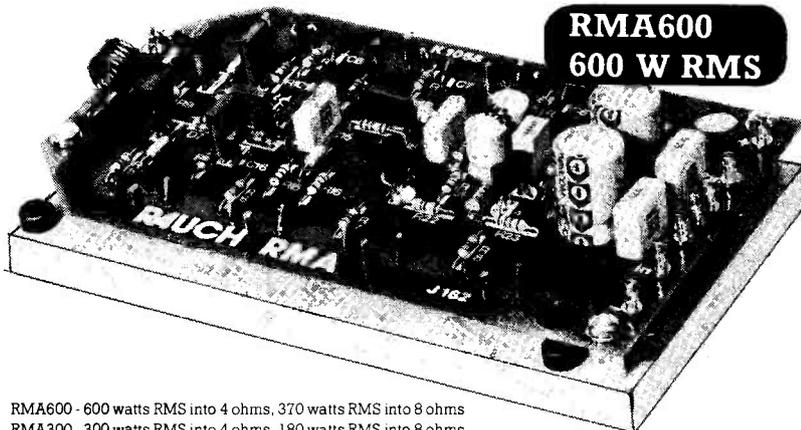

**RMA600**  
**600 W RMS**

RMA600 - 600 watts RMS into 4 ohms, 370 watts RMS into 8 ohms  
RMA300 - 300 watts RMS into 4 ohms, 180 watts RMS into 8 ohms  
RMA150 - 150 watts RMS into 4 ohms, 85 watts RMS into 8 ohms

Available for the first time, **MosFet** power amplifier modules derived from internationally acclaimed **RAUCH** Pro-Audio technology.

The **RMA** series of amplifier modules offer outstanding power handling capability and combine a 'Class A' driver stage with MosFet output devices to give Audiophile performance.

All of the **RMA** modules have been over designed for long term reliability, and are constructed on a glass-fibre solder resisted board with component legging. The power Mosfets are mounted under the PCB and bolted to a substantial 9mm thick aluminium mounting plate. This forms a compact and very robust package which can be easily mounted to the heatsink.

**RAUCH**  
precision

RAUCH PRECISION ENG LTD  
DEPT H  
BLACKHILL IND EST  
SNITTERFIELD  
STRATFORD ON AVON  
WARCS CV37 0PT

#### GENERAL SPECIFICATION FOR ALL MODULES

Frequency response 20Hz - 20kHz, +0dB - 0.2dB  
T.H.D. 0.01% @ 1kHz max,  
typically 0.003%  
S.N.R. -110 db A weighted  
Slew Rate 100v/uS  
Input Sensitivity 0.775v RMS, 0dB  
Dimensions 137 x 76 x 42mm  
Weight 0.375Kg max

Note: the above specifications only apply when the modules are used with the correct power supply and heatsink, which we can supply, see listing below.

#### PRICES excluding VAT and carriage

RMA600 Amp Module	£74.00 built	£65.00 kit
RMA300 Amp Module	£49.00 built	£41.00 kit
RMA150 Amp Module	£37.00 built	£30.00 kit
Toroidal transformer 800 VA 60-0-60v for RMA600	£36.00	
Toroidal transformer 500 VA 60-0-60v for RMA300	£26.00	
Toroidal transformer 200 VA 60-0-60v for RMA150	£17.00	
10,000 uf 100vW PSU capacitors with clamps	£11.80	
600v 35 amp bridge rectifiers	£ 2.90	
Heatsink 300 x 80 x 40mm 0.45 oC/W	£12.00	
24v DC fan 120mm (Papst)	£21.90	
24v DC fan 90mm (Papst)	£20.80	
Thermal switch, re-setting	£ 2.80	
DC protection card	£10.40 built	£ 8.50 kit

CARRIAGE £2.20 FOR ALL ORDERS, CHEQUE OR POSTAL ORDERS ONLY, S.A.E. FOR FURTHER DETAILS, TRADE ENQUIRIES WELCOME!

**BUY WITH CONFIDENCE** - RAUCH PRECISION ARE A WELL ESTABLISHED COMPANY WITH SALES OF PROFESSIONAL POWER AMPLIFIERS EXCEEDING £1,500,000 TO SATISFIED CUSTOMERS WORLDWIDE.


TEL:0789 731133

FAX:0789 731075

TELEX:312242

# SOLDERLESS WIRING

## EASIWIRES

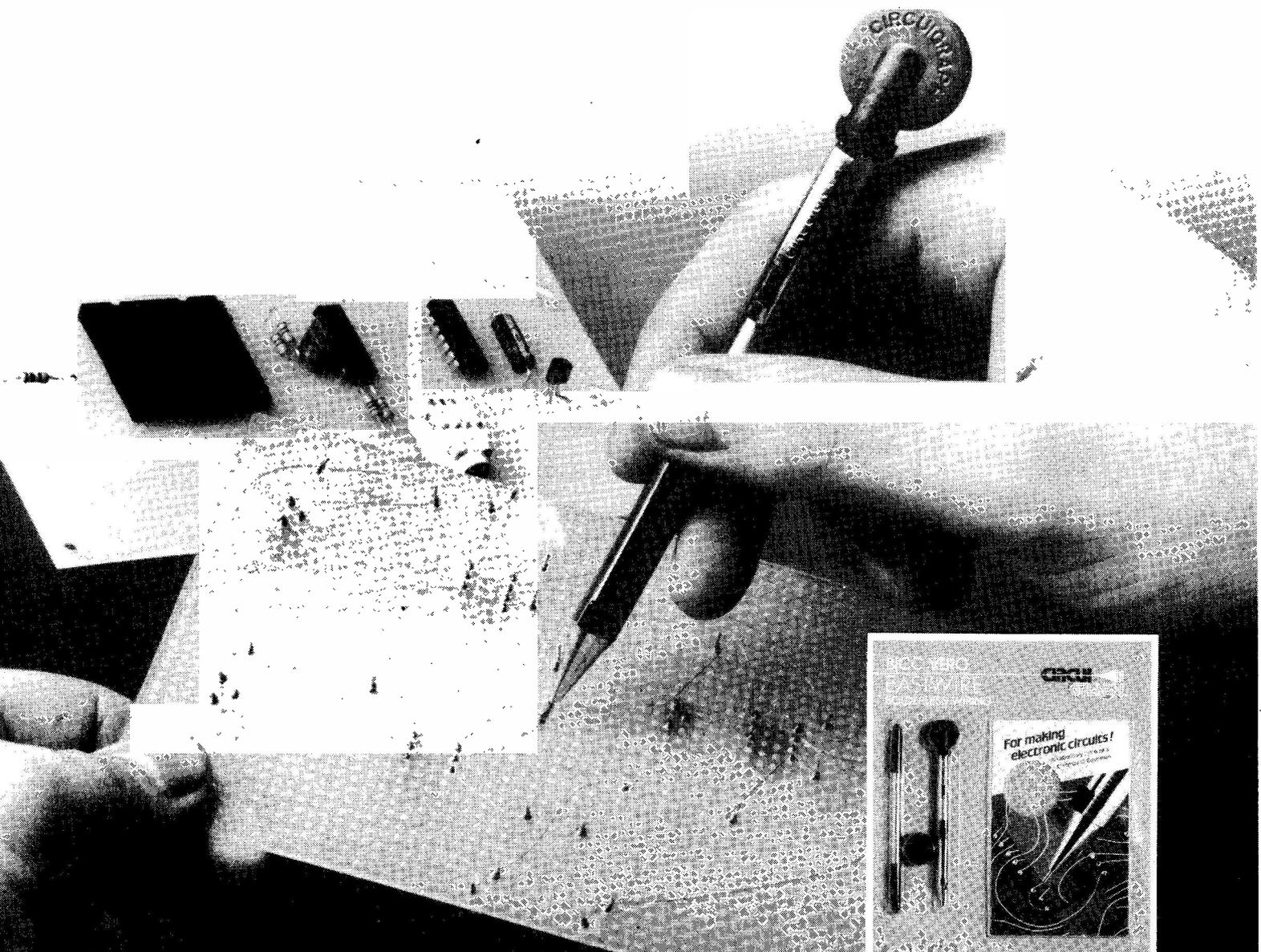

Construct your electronic circuits the new, quick and easy-to-learn way, **WITHOUT** solder: with Circuigraph Easiwire from BICC-VERO

With Easiwire all you do is wind the circuit wire tightly around the component pins. No soldering, no chemicals, no extras, simplicity itself. Circuits can be changed easily, and components re-used.

Easiwire comes in kit form. It contains all you need to construct circuits: a high-quality wiring pen with integral wire cutter, 2 reels of wire, a tool for component positioning and removal, a flexible injection moulded wiring board, double-sided adhesive sheets, spring-loaded terminals and jacks for power connections and an instruction book. Of course, all these components are available separately too.

To take advantage of the special introductory offer, complete the coupon on the right and send it to:

**BICC-VERO ELECTRONICS LIMITED,**  
 Flanders Road,  
 Hedge End,  
 Southampton, SO3 3LG



Please rush me.....Easiwire kits, retail price £18.-;  
**special introductory offer £15.-.** (includes p & p and VAT).

I enclose cheque/postal order for....., made payable to  
 BICC-VERO Electronics Limited

Please debit my credit card as follows:



Card Number .....

Expiry Date .....

Name .....

Address .....

.....

Signature .....

or phone 04892 88774 now with your credit card number  
 (24-hour answering service).

# OP-AMPS

Paul Chappell maintains the balance between noise and signal by rejecting the common mode

So far in this series I have only looked at the way in which the op-amp itself can influence circuit performance (and there's still a lot of ground to cover yet!). This month I'd like to take a break from that aspect of things and take an initial look at another — why one circuit configuration may be preferable to others in a given application when all apparently do the same job.

It's a theme that will crop up frequently as we see more varied and complicated circuits, but for this month I'll kick off with something fairly simple: differential amplifiers.

All the circuits considered so far have expected to see an input with respect to some fixed voltage in the circuit — usually the 0V line. If the input is said to be at 1V it implicitly means 1V with respect to the reference voltage.

It can sometimes happen that a signal to be processed will be in the form of a difference between two voltages, both of which may vary. Sometimes they may vary symmetrically about some voltage, possibly 0V. In other circumstances they will not. Circuits which respond to the difference between two voltages are known variously as subtractors, differential amplifiers or instrumentation amplifiers (although the latter term also carries connotations of high performance).

I will refer to them all impartially as differential amplifiers.

Differential signals can occur in all kinds of situations. When a low level signal has to travel some distance by cable, for example, it is often advantageous to send it as a 'balanced' signal along two wires. The idea is that any radiated noise will affect both wires identically, since they run in close proximity as part of the same cable. As long as the impedances at either end of one cable match those at the corresponding ends of the other, the interference should result in a pure common mode signal at the receiving end. That is to say, both wires will rise and fall in voltage identically, so an amplifier which responds to the difference in voltage will see no noise at all. It can be very effective in practice.

Sometimes it is possible to cancel out certain imperfections in a circuit by driving two identical signal paths in 'opposite directions' or by causing an imbalance in two normally identical voltages or

which detects voltages generated by some function of the body will frequently be arranged to respond to a voltage difference to obtain the benefits of noise cancellation. The list is endless.

One desirable feature of differential amplifiers highlighted by all these applications is that it should respond to the difference in voltage between its inputs while ignoring any voltages common to both. This property is known as common mode rejection and the basic figure of merit for any differential amplifier is its common mode rejection ratio or CMRR. This is simply the amplification it gives to differential signals divided by the amplification (hopefully much less than 1) of common mode signals.

A simple differential amplifier is shown in Fig. 1. The condition for a common mode input to leave the output unchanged is:  $\frac{R1}{R2} = \frac{R3}{R4}$  and an easy way to

achieve this is to make  $R1 = R3$  and  $R2 = R4$ .

## Scissors

The best description I can think of for the way the circuit works is that it's like a pair of scissors. Let me explain. If the table-top in Fig. 2a represents 0V, the action of R3 and R4 is like one half of a pair of scissors with the tip of the blade resting on the table. The input voltage  $v_{in(+)}$  is represented by the height of the handle above the table and the point where the other blade will be joined represents  $v(+)$ , the voltage at the + terminal of the op-amp.

The action of the op-amp is to adjust its output voltage so that the + and - terminals remain at the same voltage, so the second blade is joined at the  $v(+)$  point which now represents both  $v(+)$  and  $v(-)$ .

Now suppose that  $v_{in(+)} = v_{in(-)}$ . This is equivalent to having the two scissor halves closed. (These are special scissors in which both the blades and handles lie side by side when closed. They can also open in either direction!) The effect of a common mode voltage is simply to move the scissors about the blade tips, always in the closed position (Fig. 2b).

Apply a differential voltage (open the handles) and the blades will open, with the tip of the R2 blade representing the output voltage (Fig. 2c). Now apply a common mode voltage again (move the handles, keeping the vertical distance apart the same) and the output voltage (the height of the R2 blade tip above the table) will remain unchanged — the common mode signal is once again rejected (Fig. 2d.)

Suppose that one of the resistor values is changed. Let's say the value of R2 is increased, as in Fig. 2e. If a common mode signal is now applied, even with the two inputs at the same voltage, the output will vary. The common mode signal is no longer rejected.

If you find the scissor analogy helpful, you can extend it to cover any resistor values. Figure 2f represents the situation where the ratio of R1:R2 is the same as the ratio R3:R4, but  $R1 \neq R3$  and  $R2 \neq R4$ , which is the general condition for the common mode signal to be rejected. With a little thought you'll see that the tip of the R2 blade will remain on the table (the output will be at 0V) as long as the two handles are at the same height. If you . . . but I can hear the yawns of those who don't care for mechanical analogies, so I'll have to leave you to work out the details for yourself.

Sooner or later we're going to have to come up with a formula for the output of the circuit in terms of

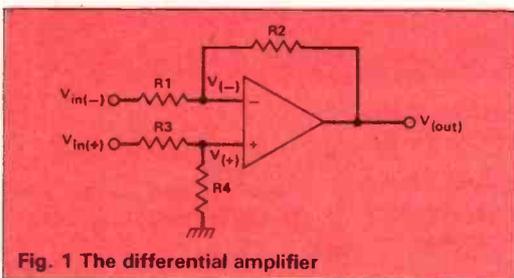


Fig. 1 The differential amplifier

currents. Two types of circuit that frequently use this technique are analogue multipliers and digital to analogue converters.

In theory you can obtain all the information you want by detecting deviations of just one of the outputs from its mean value but using both outputs allows the effects of temperature drift and some circuit non-linearities to be cancelled out.

A whole class of circuits which generate differential signals are bridge networks, which occur in all kinds of guises. Yet again, medical equipment

# CIRCUIT THEORY

the inputs. There's a hard way and an easy way to go about it.

Looking at Fig. 1 again, the output voltage can be calculated by equating the currents through R1 and R2 as we did for the basic shunt feedback circuit way back in June. This gives:

$$v_{out} - v(-) = \frac{v(-) - v_{in}(-)}{\frac{R2}{R1}}$$

Now, we don't want the  $v(-)$  in the equation since we don't know (or care very much) what its value is. In the shunt feedback circuit we recognised that  $v(-)$  would remain as near as dammit at 0V and so set it to zero. In this circuit it will once again be at the same voltage as  $v(+)$ , which will be at some voltage set by  $v_{in}(+)$ , R3 and R4. To be exact, it will be at  $v_{in}(+) \times \frac{R4}{R3+R4}$ . If you substitute this value for

$v_{in}(-)$  in the equation, then rearrange it to give  $v_{out} = (\text{something}) v_{in}(+) + (\text{something else}) v_{in}(-)$ , the job is done. If you reckon I'm going to do it, you can think again! This is the hard way.

What you end up with, in fact, after half a page of algebra is:

$$v_{out} = v_{in}(+) \left( \frac{R4}{R3+R4} \right) \left( \frac{R2+R1}{R1} \right) - v_{in}(-) \frac{R2}{R1}$$

I don't know about you but I don't find that formula very convincing. After all, it's easy to make a mistake, to get a sign wrong, to transcribe a resistor subscript incorrectly or whatever, in half a page of calculations. And it's not immediately obvious from inspection of the circuit whether the formula is correct or not.

Here's the easy way to derive the formula and to see how it works. By superposition, the output arising

from both inputs acting together will be the sum of the outputs from each acting on its own. If we let  $v_{in}(+)$  be the active input, then mentally rearrange the circuit as Fig. 3a, it becomes a series feedback amplifier having a gain of  $\frac{R2+R1}{R1}$

op-amp. The input signal  $v_{in}(+)$  is 'potted down' by R3 and R4 by a factor of  $\frac{R4}{R3+R4}$  before being amplified, so the total contribution to the output is:

$$v_{in}(+) \left( \frac{R4}{R3+R4} \right) \left( \frac{R2+R1}{R1} \right)$$

Now it's the turn of the  $v_{in}(-)$  input. This time the circuit reduces to Fig.3b, and the contribution made by this input we can write down immediately as:  $-v_{in}(-) R2/R1$ .

So the output due to both inputs will be:

$$v_{out} = v_{in}(+) \left( \frac{R4}{R3+R4} \right) \left( \frac{R2+R1}{R1} \right) - v_{in}(-) \frac{R2}{R1}$$

This time, I know what each term means and feel a lot more confidence in the formula. I hope you do too!

If we now apply the condition for the common mode signals to cancel, the cumbersome formula reduces to a much simpler one:

$v_{out} = k (v_{in}(+) - v_{in}(-))$ , where k is the ratio R2/R1 and (since they have to be equal) also the ratio R4/R3. If all the resistors are made equal in value, the result is simpler still:  $v_{out} = v_{in}(+) - v_{in}(-)$ . The circuit will then just generate a signal with respect to ground equal to the difference between the two inputs. Any common mode signal will not affect the output at all.

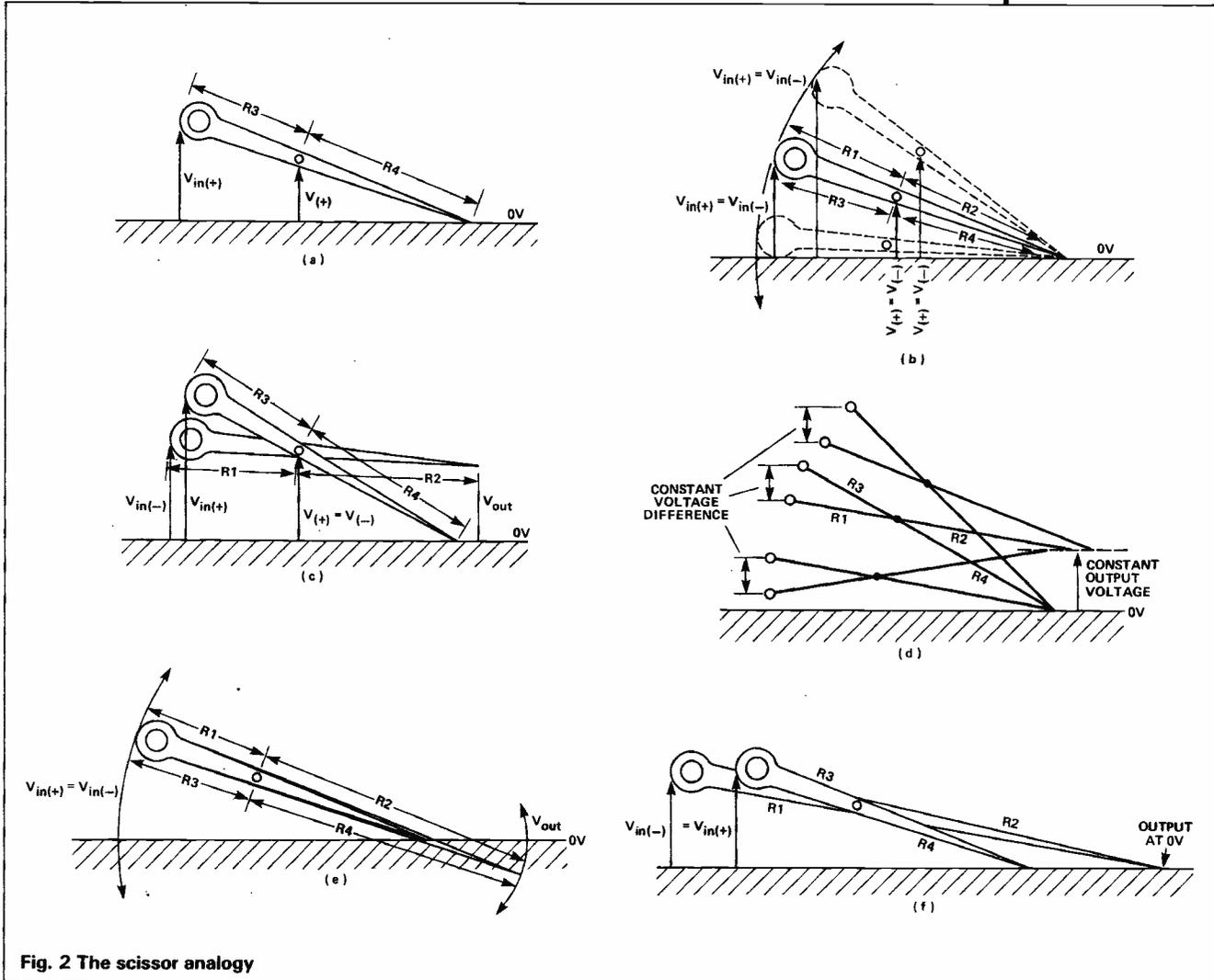


Fig. 2 The scissor analogy

# CIRCUIT THEORY

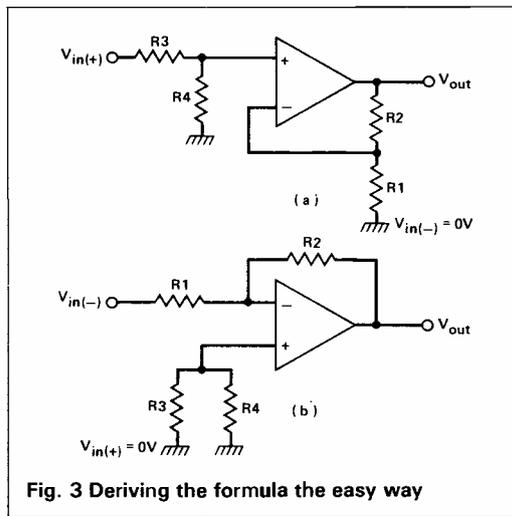


Fig. 3 Deriving the formula the easy way

To get some gain out of the circuit, all that's required is to make the value of  $k$  equal to the gain required by adjusting the resistor ratios. For a gain of 10, for instance,  $R2$  would be  $10 \times R1$  and  $R4$  would be  $10 \times R3$ .

It might seem that we've already found a differential amp that has perfect common mode rejection and can amplify the signal by any amount. Why look any further? The answer is that sooner or later we have to leave the let's-pretend world of theory where if you want resistors to be equal in value all you have to do is to say they are. Trying to build the thing with real components is not so easy.

The first shock comes when you try to calculate just how closely matched the resistors must be to give a respectable common mode rejection. If the resistor ratios are unbalanced by 1%, for instance, the CMR

is reduced from perfection to a mere 49dB. An imbalance of 0.1% will give 66dB rejection, which is certainly good enough for many purposes but not up to the 100+dB that is normally expected of an instrumentation amplifier. The figures are for the unity gain version of the circuit, by the way.

The situation is further complicated by the fact that the output resistances of the drive circuit appear in series with  $R1$  and  $R3$ . If the drive circuit is floating with respect to the differential amp, the effect is to produce a gain error, which may not be a serious matter. If the drive circuit shares a common supply or ground line with the differential amp, the output resistances must be perfectly matched to avoid degrading the CMR.

Yet another point to be considered is the input resistance of the circuit. The resistance seen at  $v_{in(+)}$  is always  $R3 + R4$ , but at  $v_{in(-)}$  the input resistance will depend on what's happening at  $v_{in(+)}$ ! A common mode signal will see an input resistance of  $R1 + R2$  but to a differential signal it will be  $R1(k + 1)/(k + 2)$ , where  $k$  is the gain of the circuit. If the input resistances are balanced for common mode signals (as they must be if these are to be effectively rejected) then the differential drive circuit will be seeing different input resistances at the two terminals, which may cause problems of its own.

To sum up, you might consider this circuit when:

- It is not essential to achieve a very high CMRR.
- It is not important to be able to trim the gain and CMR independently.
- The output resistances of the drivers are equal and very small in comparison to  $R1$  and  $R3$ .

For more demanding applications you will need a better circuit. Since I've spent longer than I intended on this one, the high performance versions will be along next month.

## SPECIAL OFFER

FOR SPECTRUM AND BBC MICRO OWNERS

Now your computer can take control for an affordable price. These tried and trusted interfaces from DCP Microdevelopments are offered at **£20 off** the normal price.

Both units are extremely easy to use from both Basic and assembler/machine code and are supplied ready built and complete with all the documentation you need.

To order by post fill in the form below (or a copy) and send it with your remittance to

**ASP READERS' SERVICES (RO ET5/6)**  
9 Hall Road, Maylands Wood Estate,  
Hemel Hempstead, HP2 7BH

Please make cheques payable to ASP Ltd. Overseas orders add £5 (Interspec) or £10 (Interbeeb) for airpost.

Access and Visa card holders can also place their order by phone on (0442) 41221 Allow 28 days for delivery.

Please supply ..... Interspecs (RO ET5) at £29.95 plus £1.95 p&p per order.  
Please supply ..... Interbeeb (RO ET6) at £49.95 plus £1.95 p&p per order.

Name .....

Address .....


.....

.....

Please debit my ACCESS/VISA card

No ..... to the sum of

£ ..... Signed: .....

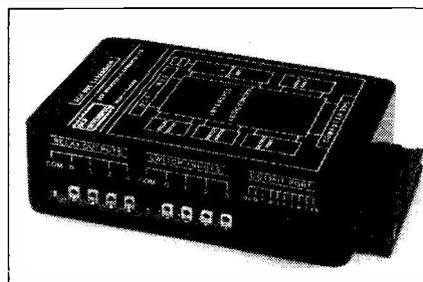

INTERSPEC £29.95

The Interspec unit plugs directly onto the expansion edge connector of the Spectrum to provide a full range of interfacing facilities.

The unit is housed in a plastic case approximately 4½x3x1in which contains the top quality double sided PCB and interface connections.

- 8-bit input port
- 8-bit output port
- four switch sensor inputs
- four relay-switched 12V 1A outputs
- eight channel multiplexed analogue to digital converter
- 15-way expansion bus

All sections of the interface are I/O port mapped and designed for maximum compatibility with existing Spectrum peripherals. Power is supplied through the Spectrum edge connector.

The expansion bus provides all the data and address/control signals for the addition of further DCP modules or home-built devices. Connection is by multi-way PCB connector and all the information required for adding further devices is given.

## INTERBEEB £49.95


The Interbeeb unit connects to the BBC micro's 1MHz bus expansion connector and is supplied complete with its own power supply unit.

The interface unit is housed in a plastic case approx 4½x3x1in which contains the top quality double sided PCB and interface connectors.

- 8-bit input port
- 8-bit output port
- four switch sensor inputs
- four relay-switched 12V 1A outputs
- eight channel multiplexed analogue to digital converter
- precision 2.5V reference
- external power supply
- 15-way expansion bus

All sections of the interface are memory mapped in the 1MHz expansion map for maximum ease of use and compatibility with existing peripherals.

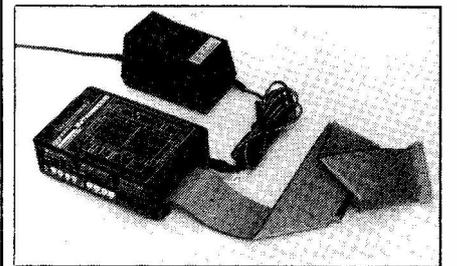The expansion bus provides all the data and address/control signals for the addition of further DCP modules or home-built devices. All the information required for using additional devices is included.



# ULTRA HI-FI — TOP PERFORMANCE PURE CLASS A POWER AMPLIFIERS

Build your own top class Hi-Fi power amplifier superior in performance to all the top big names such as **KRELL, MUSICAL FIDELITY, NAIM, QUAD, EXPOSURE** etc at a fraction of their price using own new Super-Series pure class A power amplifier modules. Three modules to choose from, ALL with so many advanced features that we can't describe them fully in this ad.

SPECIFICATIONS	SUPERMOS	SUPERMOS 1	SUPERMOS 2
Power Output	50-100W	50-100W	100-500W
Harmonic Distortion	0.0002%	0.0002%	0.0001%
Slew Rate	250V/us	250V/us	685V/us
Freq Response — 3dB	5Hz-200kHz	5Hz-200kHz	0.5Hz-350kHz
Damping Factor	800	800	940
s/n Ratio	120dB	120dB	130dB
Price	£65	£78	£140



## AUDIOPHILE PSU COMPONENTS

Top quality capacitors recommend for the Super-Series modules.  
 10,000uF 100V £14.50  
 22,000uF 63V £18.00  
 33,000uF 50V £22.00  
 47,000uF 63V £25.00  
 58,000uF 80V £25.00  
 36amp bridges £4.50. Full range of plugs and sockets inc gold plated phono's 19" rack cases **NEW Monoblock quality finished black anodised cases suit Supermos1 modules £22.00**

### SAGE AUDIO's Super-Series modules feature:-

THE lowest ever harmonic distortion for a cleaner, clearer and more natural sound quality than ever before.  
 THE highest ever slowrate for an audio power amplifier which results in a clearer, crisper, sharply focused stereo image than any other audio power amplifier.

THE best quality components for low sound colourations, including HOLCO and high technology Surface Mount Devices (SMD) featuring exclusive, matched semiconductors throughout with our own custom built output MOSFET's. This enables us to maintain a constant higher quality than any other amplifier module available today. Read how we have used advanced circuitry to eliminate capacitor sound signature colourations inherent in all other power amplifiers.

All modules are fully built and tested and are easily built into a full system with only five simple connections requiring just a simple dual rail PSU, full details supplied with the modules.

**BEWARE** of exaggerated claims made by other module manufacturers with hyped up specifications such as 60 or even 100V/us slewrate and 0.003% THD. Buy with confidence, SAGE AUDIO's modules are the **ONLY** ones to genuinely meet or exceed their specifications and to simultaneously achieve 'Super High' specifications listed above using some new techniques such as high efficiency class A operation, techniques which are not used by any other manufacturer. ALL other modules we know of operate in class AB and do not exceed 25V/us or about 0.01% THD regardless of their sales literature specifications.

### Supermos £65, Supermos1 £78, Supermos2 £140 each.

To receive an 8 page glossy brochure describing these modules inc description of our class A operation and all our products **send £1.50 cheque, PO, coins plus a 9" x 12" 26p SAE** (note we no longer send information without the above money and SAE or 6IRC's overseas) to:



Sue Wilson, Sales Dept.,

SAGE AUDIO, Construction House, Whitley Street, Bingley, Yorks. BD16 4JH. England.

OSCILLOSCOPES	SPECIAL OFFER at ONLY £300 each
TELEQUIPMENT D83 Dual Trace 50 MHz Delay Sweep. Large Tube with manual ..... £350 COSSOR OSCILLOSCOPE CDUI50. Dual Trace 35MHz Delay Sweep. Dual State. Portable 8x10cm Display. With Manual ..... <b>NOW ONLY £180 each</b> Viewing Front Protection Cover. Containing 2 Probes & Viewing Hood ..... £10 S.E. LABS SSM11 Dual Trace 18MHz Solid State. Portable AC or external DC operation 8x10cm display with Manual £150 GOULD/ADVANCE OS255 Dual Trace 15MHz with Manual ..... £225 TELEQUIPMENT D43 Dual Trace 15MHz. With Manual £100 ADVANCE OS250TV. Dual Trace 10MHz. With Manual £150 SCOPEX 4D10A Dual Trace 10MHz. With Manual ..... £150 TELEQUIPMENT S54A Single Trace 10MHz. With Manual ..... £90	TELEQUIPMENT D755 (NATO approved version of D75). Dual Trace. Delay Sweep. 50MHz. TRIO RF SIGNAL GENERATOR type SG402 100kHz-30MHz. Unused (p&p £7) ..... <b>only £75</b> COLOUR PAR GENERATOR type PAL MC-101. 8 patterns. Pocket Size. Rechargeable batteries. Complete with Battery Charger/Mains Adaptor. Unused (p&p £4) ..... <b>only £90</b> COLOUR PAR GENERATOR type PAL MC321. 8 patterns. Video/Sound Output. Unused (p&p £7) ..... <b>only £175</b> AVO TRANSISTOR ANALYSER MK 2 (CT 446) Suit-case style. Complete with batteries & operating instructions <b>only £25 each (p&amp;p £7)</b> <b>AVO TRANSISTOR TESTER TT169</b> Handheld GO/NOGO for in-situ Testing. Complete with Batteries, Leads & instructions (p&p £3) unused. <b>£16 each</b> <b>AVO VALVE TESTER CT160 Suitcase style. 22 Bases only £25 each (p&amp;p £7)</b> DISK DRIVE PSU 240V IN 5V 16V & 12V 1.5A out Size W125mm. H75mm. D180mm. Cased Unused only £10 (p&p £3) QWERTY KEYBOARD (as in LYNX MICRO) must to make Cased ..... <b>£5 each (p&amp;p £3)</b> FARNELL SWITCHED MODE PSU 5V 40A +/-12V 5A £30 each (p&p £4) OTHER SWITCHED MODE PSU available. Please enquire. DISK DRIVES 5 1/4" *Double Sided. Double Density. 80 track ..... <b>From £50</b>
MULTIMETERS	NEW EQUIPMENT
AVO 8 range. Complete with Batteries & Leads ..... <b>from £10</b> ANALOGUE POCKET MULTIMETERS Philips & Taylor etc. With Batteries & Leads ..... <b>from £10</b> MARCONI AF Power Meter TF893A 20Hz-35kHz. 20uW-10W. With Manual (p&p £7) ..... <b>only £35</b> MARCONI RF Power Meter TF1152A2 - DC-500MHz. 0.5 to 25 watts 50ohm. With Manual (p&p £7) ..... <b>only £45</b> MARCONI ATTENUATOR TF2162 DC-1MHz 600ohm. 0-111dB on 0.1dB Steps (p&p £7) ..... <b>£35</b> HATFIELD ATTENUATOR DC-250MHz. 50ohm/0-100dB (p&p £4) ..... <b>£60</b> ADVANCE SG62B AM 150kHz-220MHz ..... <b>£45</b> LABGEAR Colour Bar Generator KG1. 8 Test Patterns (p&p £4) ..... <b>only £40 each</b>	HAMEG OSCILLOSCOPE 604. Dual Trace 60MHz. Delay Sweep. Component Tester + 2 Probes ..... <b>£575</b> HAMEG OSCILLOSCOPE 2036. Dual Trace 20MHz. Component Tester & 2 Probes ..... <b>£314</b> All Other Models Available BLACK STAR FREQUENCY COUNTERS P&P £4 Meteor 100-100MHz ..... <b>£99</b> Meteor 600-600MHz ..... <b>£126</b> Meteor 1000-1GHz ..... <b>£175</b> BLACK STAR JUPITER 500 FUNCTION GENERATOR Sine/Square/Triangle 0.1Hz-500kHz p&p £4 ..... <b>£110</b> BLACK STAR ORION. PAL TV/VIDEO COLOUR PATTERN GENERATOR ..... <b>£199</b> HUNG CHANG DMM 7030. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC 0.1%. Complete with batteries & leads p&p £4 ..... <b>£39.50</b> As above DMM 6010. 0.25% ..... <b>£33.50</b> Carrying Case for above ..... <b>£3</b> OSCILLOSCOPES PROBES. Switched x1: x10 p&p £3/£11
ISOLATING TRANSFORMERS 240V INPUT	ACCESSORIES
240V Out 500VA ..... <b>£15 (p&amp;p £5)</b> 100VA <b>£6 (p&amp;p £3)</b> 24V Out 500VA ..... <b>£6 (p&amp;p £5)</b> 200VA <b>£4 (p&amp;p £4)</b>	■ TV-VIDEO AMPLIFIERS ■ AUDIO ■ TV/VIDEO ■ SECURITY ■ CB RADIO ACCESSORIES
STEPPING MOTORS	
Type 1 200 Steps per rev. 4 Phase (5 wire) 12 24V Torque 25oz inch will run on 5V with reduced torque £15.00 Type 2 612 Steps per rev. 3 Phase. 12/24V (will work on 5V) £2 each 5 off ..... <b>£7.50</b> Type 3 NORTH AMERICAN PHILIPS 24 Steps per rev. 4 wire 5V 3.3Amps 0.250rpm 0.200 PPS ..... <b>£6 each</b> Type 4 200 Steps per rev. 120V (3 wire) Torque 25oz inch ..... <b>£4 each</b> Type 7 WARNER 24 Steps per rev. 3 Phase (6 wire) 28V. Holding torque 45oz. inch ..... <b>£5 each</b>	
Used equipment — with 30 days guarantee. Manuals supplied if possible. This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone or Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.	

### STEWART OF READING

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Tel: 0734 68041. Fax: 0734 351696. Callers welcome 9 am-5.30 pm. Mon-Fri (until 8 pm Thurs)

# HENRY'S

## ELECTRONICS FOR TRADE, INDUSTRY, EXPORT, EDUCATION AND RETAIL

### \*INSTRUMENTS

- SCOPES ■ COUNTERS
- DMMS ■ PSU'S
- GENERATORS ETC.

### COMMUNICATIONS

- INTERCOMS ■ CB RADIO

### \*SECURITY

- PANELS ■ PIRS ■ SIRENS
- DOORPHONES ■ STROBES

### \*PUBLIC ADDRESS

- SPEAKERS ■ AMPLIFIERS
- MIXERS ■ MICS ETC.

### COMPONENTS

- HUGE STOCKS ALSO
- TOOLS ■ CABLES ETC.

### \*ACCESSORIES

- TV-VIDEO AMPLIFIERS
- AUDIO ■ TV/VIDEO
- SECURITY ■ CB RADIO
- ACCESSORIES

## FREE!

ILLUSTRATED  
CATALOGUES WITH  
RETAIL DISCOUNT  
VOUCHERS

- Instruments/Security
- Computer
- General Catalogue

Please state Trade/Education  
or Retail/mail order Send 9" x 4"  
SAE £1.00 each or £1.50 for both

# HENRY'S

404 Edgware Road, London W2 1ED

Tel: 01-724 0323



\*ALSO AT Audio Electronics 301 Edgware Road W2 01-724 3564


SALES OFFICE 01-258 1831 Telex 298102 Fax 01-724 0322

# GERRADA MARWEH BIKEBELL

Fed up with peds in your path? Road hogs clogging up the roundabouts? Build Keith Brindley's electronic bikebell and make 'em jump

To classify this project as a push-bike bell is something of a misnomer, really. It certainly doesn't ring (or even sound like a bell!) and it has no moving parts, either. Nevertheless, it'll help you to be noticed as you pedal along and that's all a conventional bike bell is meant to do.

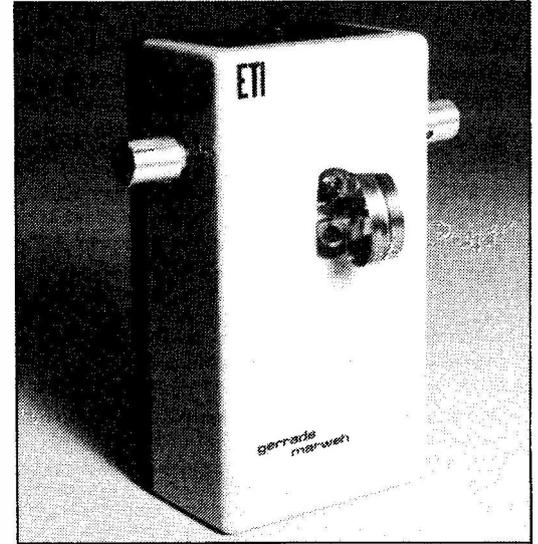Apart from not sounding like a bell, the Gerrada Marweh is significantly louder than any mechanical counterpart fitted to your handlebars can ever be.



we're making is that ordinary dry-cells, which have quite a large internal resistance, won't be able to supply the power demanded. At the very least, the circuit will need an alkaline battery and a PP3-sized battery will give excellent results.

Readers may wish to go to the expense of a rechargeable NiCd battery. Incidentally, next month's *1st Class* project is a NiCd recharger which will be capable of recharging your precious PP3-sized rechargeable battery. (Do we spoon feed you, or do we spoon feed you?)

## Construction

In this project design size was a major criterion. We wanted the project to be as small as possible (small enough to fit to a bike's handlebars) without sacrificing too much volume. The result is a fairly compact project which does need a little care in construction. By and large, development depends on the case you choose to house the project and if you use a different one to the case we used for our prototype, you'll have to adapt.

Start with the bare PCB or stripboard. Carefully saw, cut, file it to shape and make sure it fits into the case and can be bolted down. Next, mount and solder all passive components, that is, the resistors, capacitors, PCB pins, following the component layout shown in Fig. 2 or 3. If you use PCB pins for off-board connections (recommended!) you can leave the battery, speaker, switch, push-button and potentiometer wiring till later. If you don't use PCB pins, now is the time to solder in wires for the above.

Next, fit the semi-conductors in the order transistors Q1, Q2, then the UM3561 IC1. A word of warning about the UM3561 — it's a CMOS device and may be damaged by static discharges. In practice, fitting a CMOS IC merely requires it to be inserted without coming into contact with a large static voltage. Once in circuit it should be OK. Static voltages generated on the human body may be large enough to do damage to a naked chip, so take care. It's probably best to fit the chip into a DIL IC holder soldered into the PCB, as in this way you don't have to solder the chip itself.

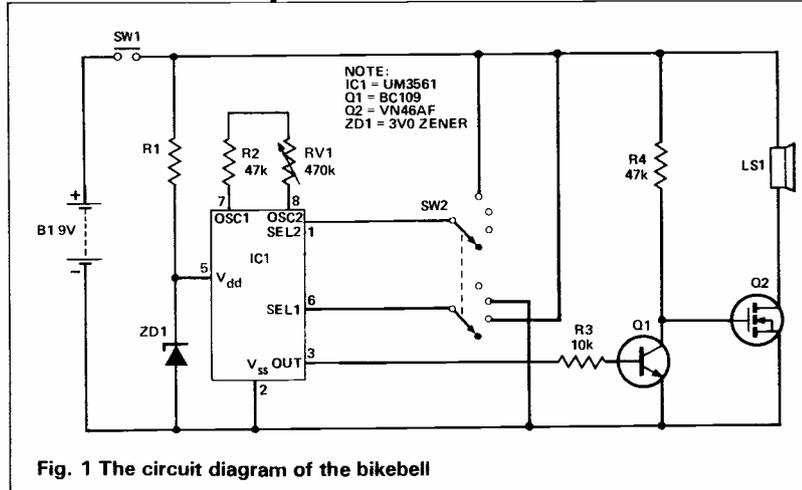


Fig. 1 The circuit diagram of the bikebell

It's based around the UM3561 siren sound generator IC, which allows selectable siren sounds and effects to be produced — namely police, ambulance and fire engine sirens and a laser gun-type effect. The output of the UM3561 is only just sufficient to drive a piezo sounder, though, which wouldn't create enough volume to scare off a fly, so the output's beefed up a little with a VMOS FET device.

The UM3561 is an LSI device (see *How It Works*) which is meant for use in toys and models as a simple-to-use and low-cost tone generator. Readers may have heard toys and models using this chip.

## Power

The Gerrada Marweh is nothing if not power greedy. The circuit itself, in this form, will run from around 4V through to 14V so it is possible to run it from dry-cell batteries or even a car battery. Readers must bear in mind, however, that the circuit positively devours current — it *must* do to be able to produce this much volume for such a low voltage.

At 14V for example, around 600mA must be provided. At 9V around 400mA is required. The point

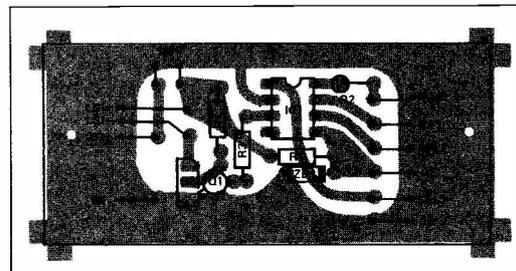


Fig. 2 The PCB component overlay

1st CLASS

## HOW IT WORKS

Figure 1 shows the circuit of the ETI Gerrada Marweh push-bike electronic bell. It's not complicated. Integrated circuit IC1 is a UM3561 siren sound generator requiring a power supply of around 3V, so a voltage regulator comprising zener diode ZD1 with series resistor R1 is used to provide this from the battery voltage.

The UM3561 comprises a number of internal parts (shown in Fig. 2) including an oscillator, control circuit, counter, tone generator and ROM. The oscillator frequency is set by the value of an external resistance connected to the OSC pins of the chip. For defined sirens, the oscillator frequency should be about 100kHz, corresponding to a resistance of 240k. In the Gerrada Marweh a potentiometer and series resistance is used as the external resistance, providing a variable frequency oscillation whose maximum frequency (minimum potentiometer resistance) is set by the series resistance.

Two pins SEL1 and SEL2 on the IC allows a choice of one of four effects depending on how these pins are connected to each power supply rail. Rotary switch SW2 connects the pins accordingly. Table 1 lists the connections to the two selection pins, and the resultant effects.

Stored in the ROM are data patterns relating to the four available effects. As the oscillator output is counted by the counter, one of the patterns is cycled through, selected by the control circuit and then passed to the tone generator.

Output from the UM3561 is a variable frequency squarewave with an amplitude nearly that of the supply voltage (3V). This voltage is amplified to around that of the battery voltage with a single common emitter transistor amplifier formed around transistor Q1. A VMOS FET transistor Q2 is driven directly from Q1's collector giving sufficient current gain to power up a loudspeaker with around 4 watts of power.

## PARTS LIST

### RESISTORS (all 1/4W 5% unless specified)

R1	1k0
R2,R4	47k
R3	10k
RV1	470k lin pot

### SEMICONDUCTORS

Q1	BC109
Q2	VN46AF
ZD1	3V0 zener diode
IC1	UM3561

### MISCELLANEOUS

B1	PP3 battery
SW1	push button
SW2	4-way rotary (at least 2-pole)
LS1	5W 8R 3in mylar speaker

PCB or Stripboard. 8-pin DIL socket. Knobs. Case (150 x 80 x 50mm). Battery clip. Handlebar clamp. Nuts and bolts.

SEL1	SEL2	Effect
NC	NC	Police siren
+	NC	Fire engine siren
-	NC	Ambulance siren
NC	+	Machine gun

Table 1. Connections to the UM3561 siren sound generator IC selection pins and the resultant effects

# 1st CLASS

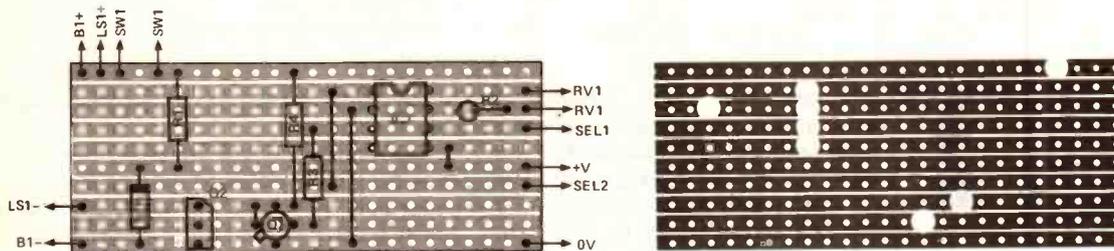


Fig. 3 The Stripboard component overlay and track cutting diagram

Now leave the PCB aside while you drill the case for all controls and fit the speaker. Holes for controls are self-explanatory and depend on how you intend to mount and fasten the project to your bike. Talking of fastening, it's a tricky problem. We found a number of solutions. The best appear to be plumbing clips for 22mm copper or plastic pipes. Another are awning clips found in caravan accessory shops. Inventive readers may have other ideas.


Fixing the speaker into the chosen case is not easy. The inside of the case must be partly milled away to accommodate it.

Once the speaker is shown to fit properly, the holes for mounting bolts and the hole for the cone itself can be drilled and filed out. The speaker used is a mylar cone type and is specifically intended for outside sirens and buzzer applications. The mylar cone provides weatherproofing and splashproofing, making it ideal for this project. With this in mind, the prototype's speaker cone is accessible directly from the underneath, making physical damage to the cone a possibility. It's not essential to fit a protective grill but some readers may feel the need, particularly if the Gerrada Marweh is to be fitted to a young child's bike where prying fingers, lollipop sticks, friends' toys and so on are liable to be encountered.

Once the speaker is fitted, the project can now be put together. Fit the PCB into the case, fit all

controls and wire up the switches according to the wiring scheme shown in Fig. 4. Now, fit a suitable heatsink to the VMOS FET transistor. This must be as large as possible, without obstructing other parts and the controls in the case. Smear the metal face of the transistor with heatsink compound before bolting the heatsink to it, to ensure maximum heat transfer.

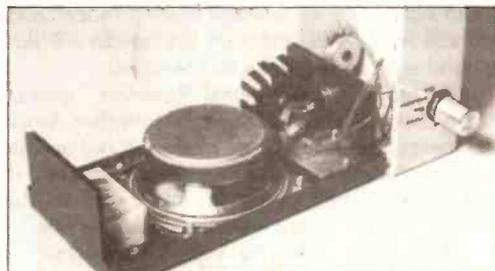No setting up is required. Merely select the effect you require, set the speed control to about mid-position, put in your ear-plugs and press the push-button.



## BUYLINES

The UM3561 and mylar speaker are both available from Maplin. All other components should be available at your local supplies outlet. The PCB is available from the PCB Service.


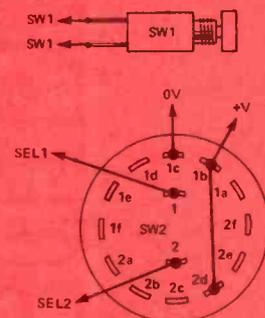


Fig. 4 Wiring up the switches
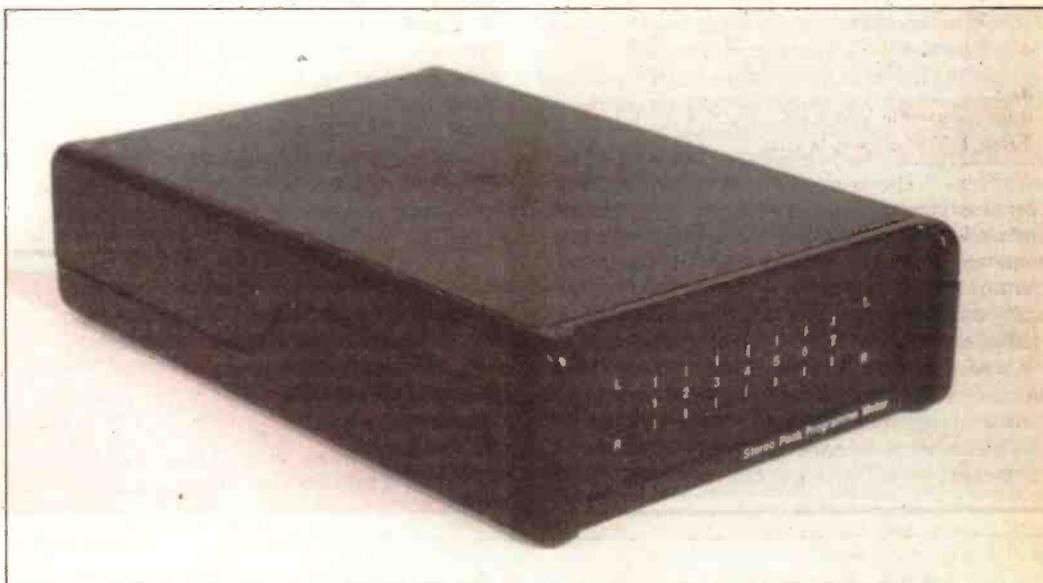
# PEAK PROGRAMME METER

*Ian Coughlan  
peaks at the right  
time with his high  
quality stereo  
meter*



**T**here are two major differences between the typical peak programme meter and the VU meters that are more familiar to most people. The PPM has very different ballistics — it attacks quickly and decays slowly so that peak signal levels are clearly displayed. In addition the PPM's scale is roughly linear whereas the scale of a VU is anything but.

## A Different VU

Let's look at the VU meter in more detail. The audio signal is rectified and integrated to produce a reading corresponding to the average signal level (the PPM shows the peak level). At the left end of the scale is -20, at the right end is +3VU. About two-thirds of the way along is 0VU, which by convention corresponds to +4dBm.

Put a sine wave into the VU meter at a level of +4dBm and it will read 0VU. Simple. Put a typical audio signal in at an average level of +4dBm and it will still read 0VU, although the needle will jump around a bit in response to the signal.

A typical audio signal however, contains peaks that will be rather more than +4dBm. Since a VU meter integrates, these peaks will not produce a proportionate increase in meter reading and the audio system can be driven into overload even though the VU meter says everything is fine.

This may be relatively unimportant — analogue tape recorders for example exhibit a 'soft' overload characteristic and the distortion is not too objectionable. Other media are not always so forgiving. Digital recording systems, radio transmitters and indeed audio amplifiers have very sharply defined upper limits. Drive them even a little above their limits and they simply will not go

— the signal will clip and the resulting distortion is very nasty indeed.

Obviously the best signal-to-noise ratio from an audio path is obtained running as close to the upper limit as you can, short of overload. If all you've got is a VU meter, the peaks are not going to register so you'll have to allow a considerable amount of headroom above the average signal level for these peaks and that's going to compromise the performance at the bottom end.

## Enter The PPM

The fast response of the PPM means that the magnitude of peaks within the signal can be monitored with precision and if you know where your system's upper limit is (it's easy to find — just increase the signal until the output clips), adjust the level so that the peaks are just below the limit. You may want to allow headroom for extra large peaks, but with pre-recorded or broadcast material the recording engineers will have squashed those out long before they get to you!

Not just any old meter can be used for a PPM. Only specialised (and expensive) movements have the necessary ballistics, most ordinary movements being far too slow. The PPM to be described in this article uses LEDs in place of a meter movement and they're as fast as anyone could want! Cheap too — the cost of producing this stereo PPM with built-in power supply is less than the price of one PPM meter with drive card. True, it doesn't have the ultimate accuracy of such a meter but in side-by-side comparisons monitoring typical programme material, no visual differences could be observed. Besides, LEDs look pretty.

The PPM scale is quite distinctive. Unlike the VU meter which tends to squeeze the area of

PROJECT

interest into the top half of the scale, the PPM stretches this area out so that it spans the full width of the scale as shown on the photos.

PPM1 on the left corresponds to -12dBm, PPM7 on the right is +12dBm. In the centre of the scale is PPM4, which is 0dBm. The scale markings are equally spaced, each 4dBm from its neighbours.


PPM	Volts RMS	Volts Peak	dBm
1	0.195	0.275	-12
2	0.308	0.436	-8
3	0.489	0.69	-4
4	0.775	1.095	0
5	1.228	1.736	+4
6	1.946	2.752	+8
7	3.084	4.36	+12

Note:  
0dBm is referred to 1mW in 600Ω, accepted as 0.775V RMS.  
Table 1 PPM display levels

Table 1 shows the PPM numbers with their corresponding dBm levels and voltage levels (RMS and peak). To achieve this linear scale a non-linear amplifier is needed and Fig. 1 shows the desired transfer function of this amplifier. The function is realised in this design by a technique known as discontinuous approximation. The output of the non-linear amplifier does not change in a smooth, continuous manner, instead the transfer function consists of a series of straight lines, designed to approximate the desired curve as shown in the dotted curve. The slope of the amplifier is made to change at each breakpoint and the more breakpoints and slopes there are the more accurate will be the approximation.

This design uses three breakpoints and four slopes, which is quite adequate for the application. Figure 2 illustrates the technique.

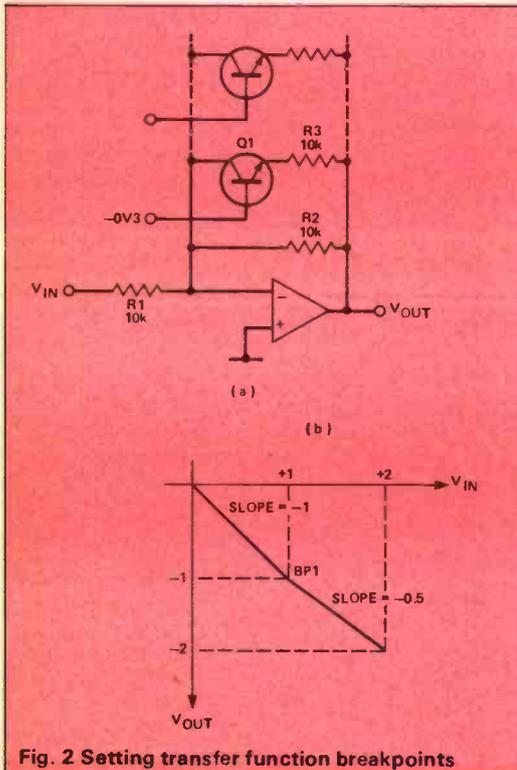For all input voltages up to +1V, the gain of the amplifier will be -1 since Q1 will be non-conducting (its base is held at -0.3V). As the output falls below -1V, Q1 will begin to conduct providing an extra feedback path around the amplifier. The feedback resistance is now effectively R3 in parallel with R2, so the gain becomes -0.5. Further breakpoints can be added as shown.




## Construction

The front and rear panels (supplied with the recommended box) should be cut and drilled as shown in Fig. 5. Drilling the holes in the front panel will not be as easy as it looks. The trick is to drill the four large holes first and fix stripboard to the panel with the holes aligned with the positions of the LED holes. Now drill pilot-holes in the panel, 1mm in diameter, using the strip as a jig. Remove the stripboard and drill the holes out to 2mm. But be warned — don't just rush ahead and do it. Practise on a piece of scrap material first. I ruined four or five pieces before I got it right!

When you're happy with the panels, rub them down with wet 'n' dry paper, clean them and then prime and paint them. Spray-painting gives a much better finish than brush-painting. When the paint is dry, apply dry-transfer lettering and protect this with a light spraying of Letracote or Letfix aerosol varnish.

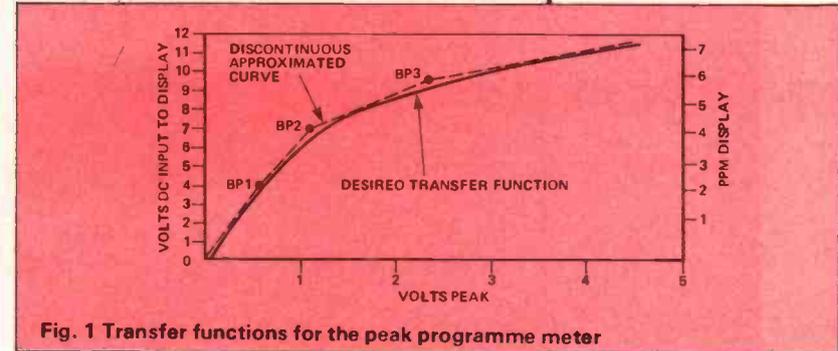Fix the phono sockets, slide switch, and IEC mains inlet to the rear panel. Also, fit a solder-tag to




the rear panel for the earth connection: mains voltages are present within the unit and it's up to you to see that it is safe to use.

Solder R55 and R56 to the slide switch, SW1. Put all the LEDs into a piece of stripboard (observing polarity) but don't solder them yet. Guide the LEDs through the holes in the front panel, and fix the stripboard to the panel using countersunk screws from the front and 6.35mm (1/4in) spacers. Fix a solder-tag to one of the screws — this is the earth connection for the front panel.

If all the LEDs fit snugly, solder them to the stripboard and cut the tracks between the cathodes. The tracks connecting the anodes can be left intact, since all anodes are commoned together anyway.

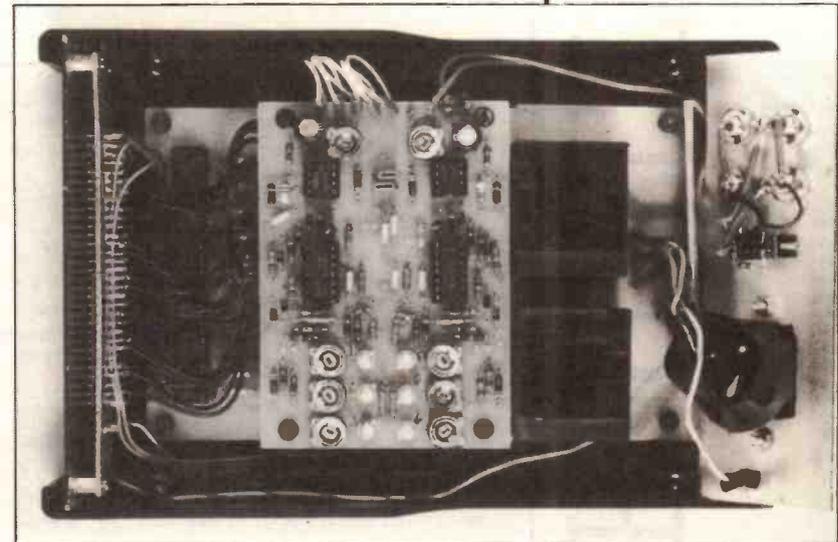Now is a good time to check that all LEDs work using a power supply of about 12V and a



PROJECT



NOTE:  
 IC5-10=LM3914N  
 IC11=78L15  
 IC12=79L15  
 D15-22=1N4002

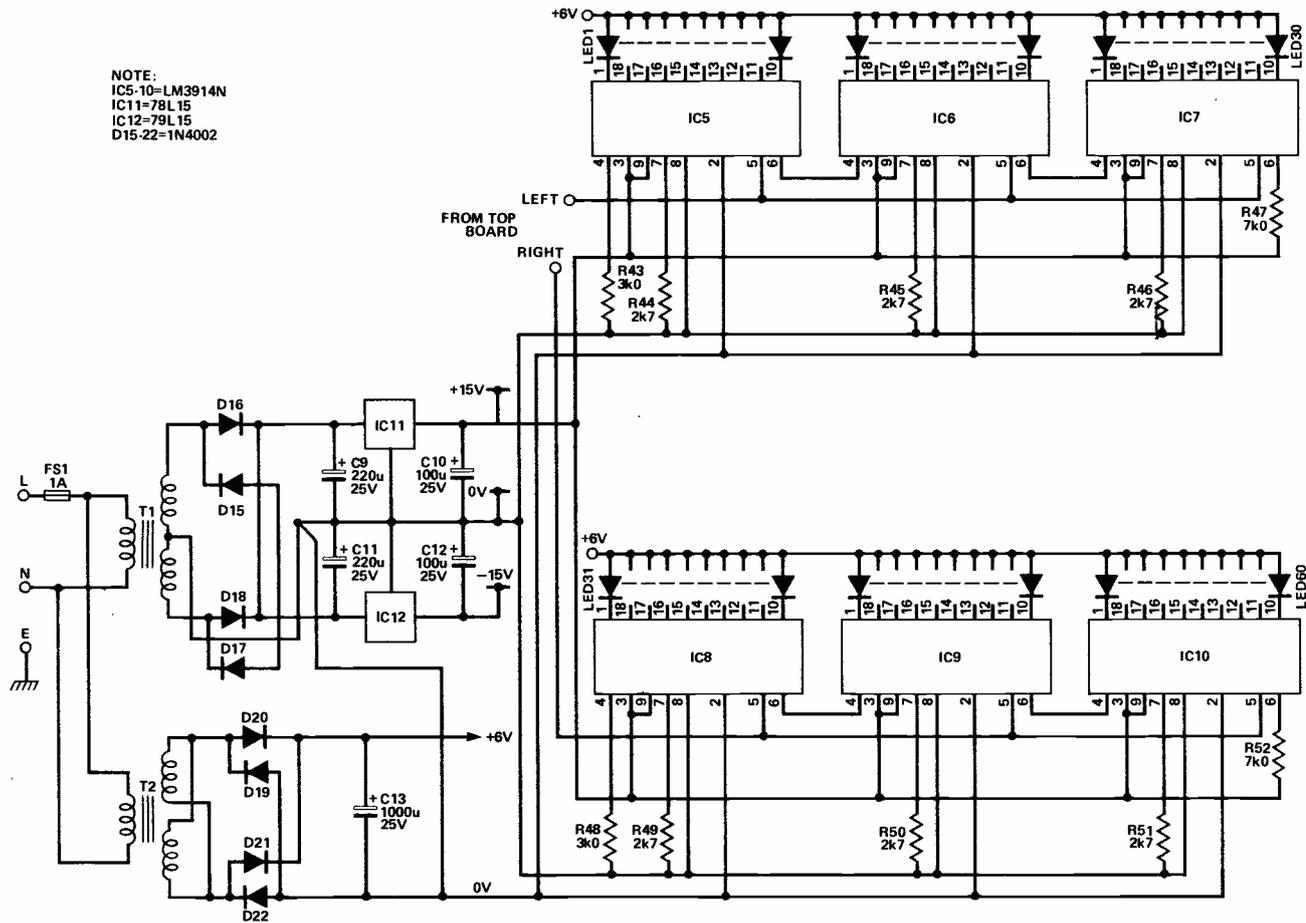


Fig. 4 Circuit diagram of main board

series resistor of say 4k7. If all is well, slide a piece of thin card down between the two rows of LEDs, to prevent light from one row spilling into the next. Put the front and rear panels to one side.

Check both PCBs for short circuits before you start on then. The overlays are shown in Figs. 6 and 7. Insert the through pins from the copper side of the large board and from the component side of the small board. This will keep all the wiring between the boards, resulting in a neater overall appearance.

Fit and solder links, resistors, capacitors, DIL sockets, presets, fuse-clips, transformers and semiconductors (except ICs) to both boards. Connect the lettered points on the underside of the small board, using insulated 7/02 wire, and put this board to one side.

Note that two resistors on the large board (R47, 52) are select-on-test, so these cannot be fitted until their value is known.

Some initial tests should be made at this stage. Pop a 500mA fuse into the fuse-clips and connect a pair of insulated wires to the live and neutral pins. Be careful! A healthy respect for high voltage is a good thing.

Apply power and check for +15V and -15V on the appropriate pins. If all is well, disconnect the power and insert the LM3914s into their sockets, being careful to put them in the right way round (they're quite expensive devices).

Temporarily connect an LED to the LED3 position and another to the LED27 position. Connect a potentiometer (preferably a multiturn preset about 10k) between +15V (clockwise end) and 0V (anti-clockwise). Connect the wiper to the LEFT input pin.

Switch on the power again and adjust the potentiometer for +11.25V on its wiper. R47 must

now be selected so that LED27 is only just on. Another preset (20k) will make this easier. When the value is known, solder R47 into place. It may be necessary to fit two or more resistors in series or parallel. Now check that LED3 is on above a voltage of +1.25V on the wiper of the multiturn preset.

The above procedure must now be repeated for the RIGHT channel, so move the LEDs over to LED33 and LED57 and move the wiper of the multiturn preset to the other input. Once you're

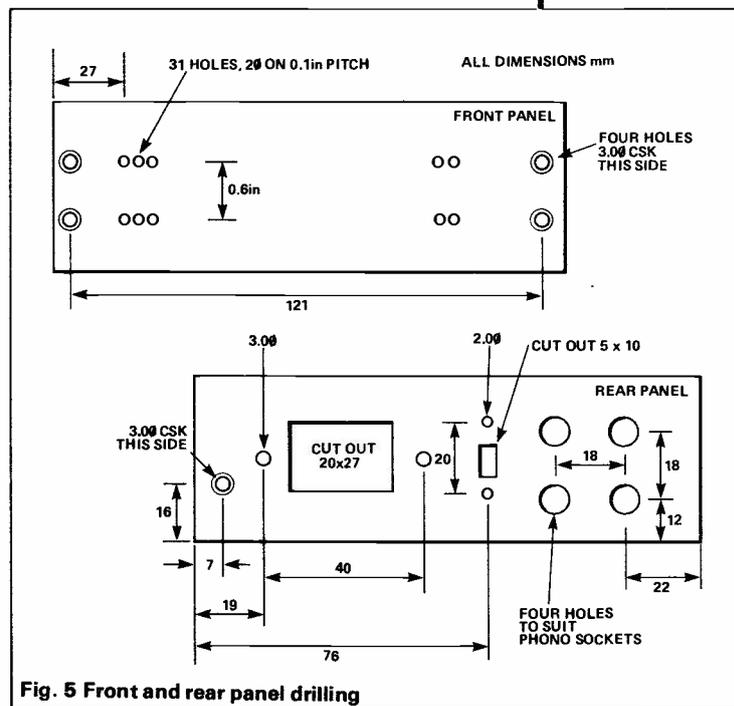


Fig. 5 Front and rear panel drilling

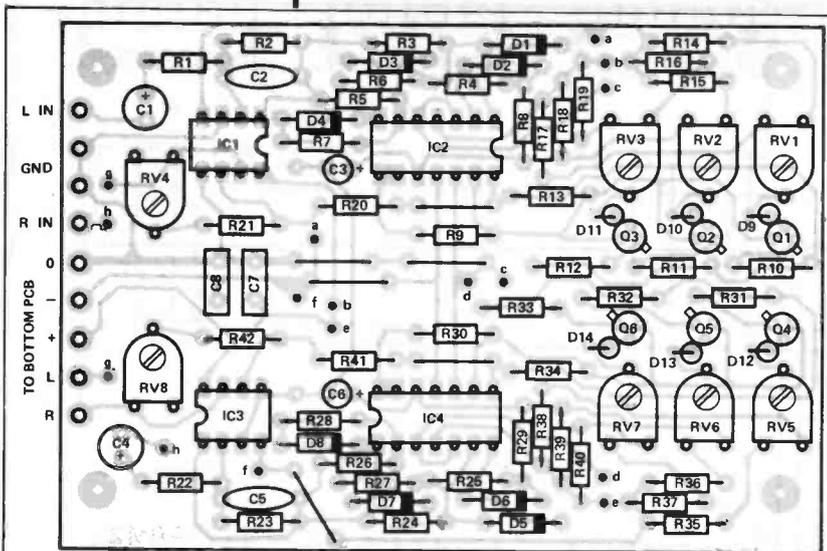


Fig. 6 Component overlay for the small board

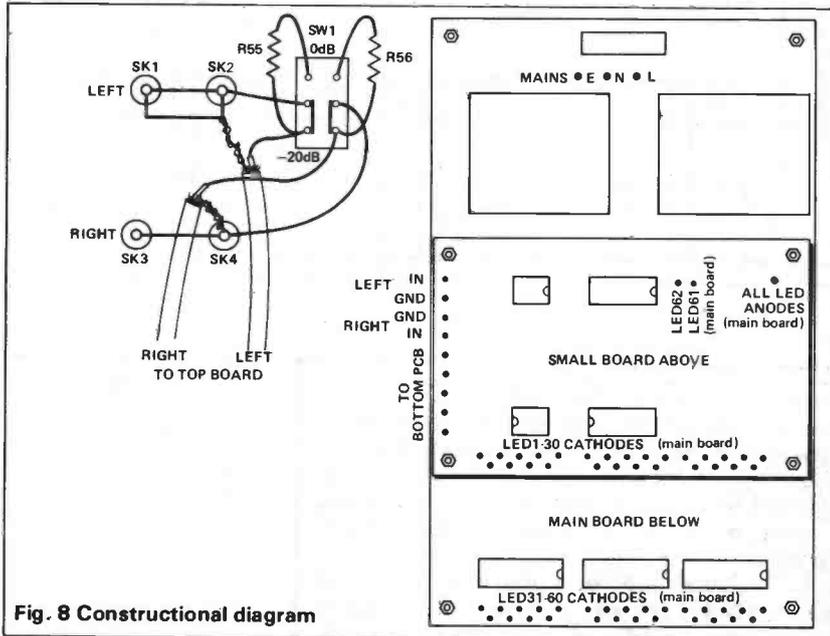


Fig. 8 Constructional diagram

## BUYLINES

Most components should be available from any supplier. The transformers used in the prototype were from Electromail (Tel: (0536) 204555), order codes 207-841 and 207-829. The LEDs are order code 588-689. The case used was from West Hyde ((0296) 20441), code 880710. The prototype was actually built used two lids and no base, but the size of case given here is recommended. Note that voltage ratings given for capacitors represent minimum ratings.

happy with both channels, disconnect the power and remove all the other temporary connections.

Wire in the cathodes of the 62 LEDs. The left hand LED of each channel (LED61, 62) are lit at power on and connect to the centre of the main board. The display for the left channel then runs from LED30 to LED1 and for the right channel from LED60 to LED31.

Fix the two boards together with 1in spacers. Fit the ICs to the small board.

Cut a piece of card and fit it to isolate the input sockets from the mains end of the PCB. Drop the two PCBs into the box and fix the assembly into place. Fit the front and rear panels and wire them to the large PCB as shown in Fig. 8. Remember to fit an insulating boot to the IEC mains connector and to connect the earth wires.

## PARTS LIST

RESISTORS (all 1/4w 5% unless specified)

R1, 22	9k1
R2, 5, 6, 7, 13, 23,	
26, 27, 28, 34	100k
R3, 4, 24, 25	200k
R8, 29	1k0
R9, 30	12k
R10, 31	27k
R11, 32	33k
R12, 18, 33, 39	120k
R14, 21, 35, 42	43k
R15, 51	51k
R16, 37	75k
R17, 38	150k
R19, 40	110k
R20, 41	47k
R43, 48	3k0 2%
R44, 45, 46, 49,	91k
50, 51	2k7
R47, 52	7k0 (Nominal: see text)
R53, 54	3k9
R55, 56	91k
RV1-8	10k skeleton preset

## CAPACITORS

C1, 4, 10, 12, 13	100µ 25V electrolytic radial
C2, 5	10p polystyrene
C3, 6	2.2µ 16V tantalum bead
C7, 8	100n ceramic
C9, 11	220µ 25V electrolytic radial
C10	100µ 25V electrolytic radial

## SEMICONDUCTORS

IC1, 3	TL072
IC2, 4	TL074
IC5-10	LM3914N
IC11	78L15
IC12	79L15
Q1-6	BC107
D1-14	1N4148
D15-22	1N4002
LED1-62	red 2mm flat top LED

## MISCELLANEOUS

FS1	1A 20mm fuse
SK1-4	Phono sockets
SW1	DPDT sub-miniature slide switch
T1	0-15 0-15 3VA PC mounting transformer
T2	0-6 0-6 3VA PC mounting transformer

Case. IEC mains connector and insulating boot. 20mm fuse clips. 20mm spacers. 6.35mm spacers. IC sockets. Solder tags. Stripboard. Cardboard. Pins. Silicone rubber sleeving. 16/02 & 7/02 insulated wire. Nuts and bolts. 22swg link wire.

## Calibration

Calibrating the PPM is very straightforward. You'll need an audio oscillator, capable of producing up to +12dBm (3.08V RMS). The procedure is identical for both channels, so do the left channel as described here and then the right channel, with appropriate changes to component references.

Set the slide switch on the rear panel to the 0dBm position. Apply a sine wave at a level of -8dBm (308.4mV RMS) to the left input, and adjust RV4 until the meter reads PPM2.

Increase the signal level to 0dBm (775mV RMS) and adjust RV3 for PPM4. Increase the signal level to +4dBm (1.228V RMS) and adjust RV2 for PPM5. Increase the signal level again to +12dBm (3.084V RMS) and adjust RV1 for PPM7.

ALL LED ANODES

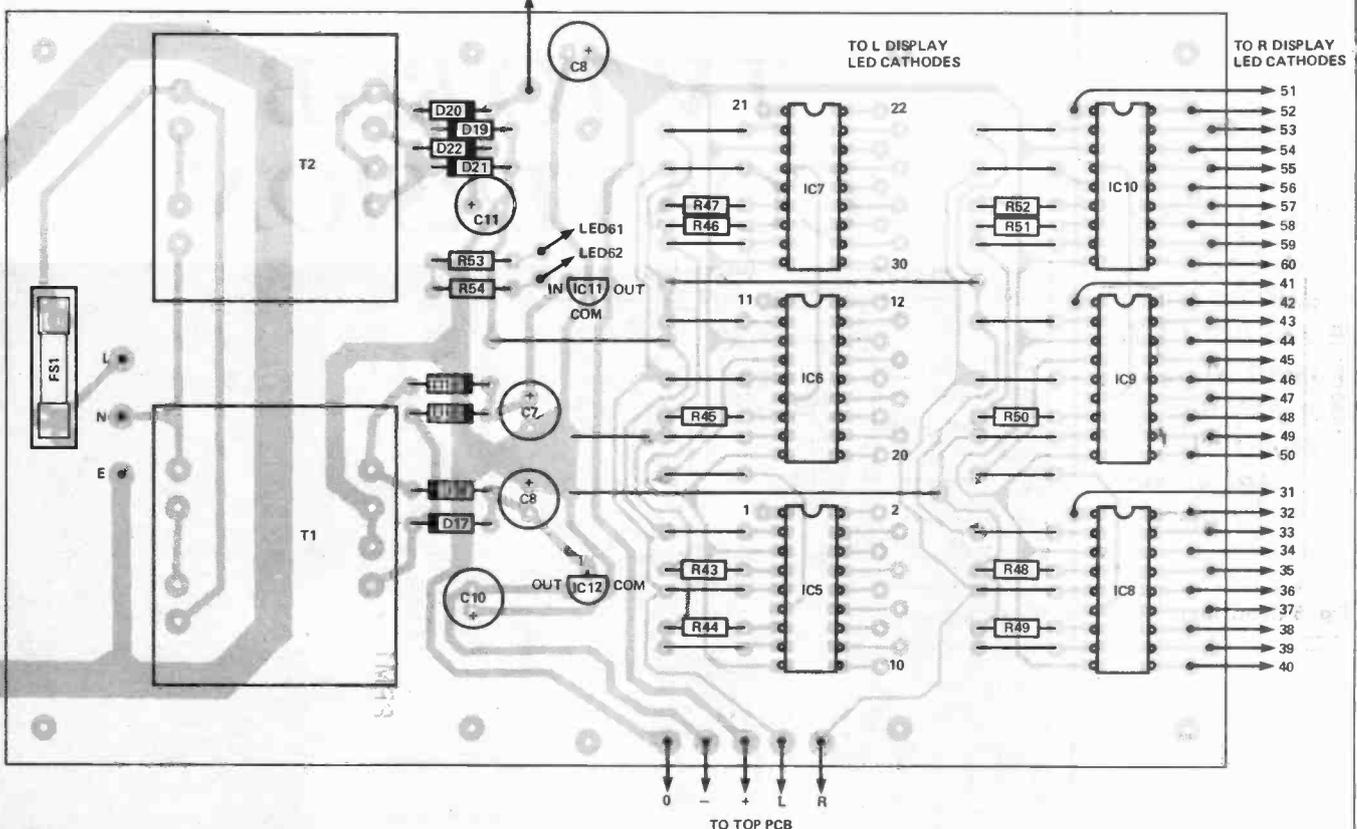


Fig. 7 Component overlay for the main board

Check the PPM points against the signal levels shown in Table 1 and if necessary repeat the above procedure. When you're happy with the left channel, move onto the right.

That's all, calibration is now complete. Fix the lid in place and the PPM is ready for use.

In use, the PPM simply connects into the audio circuit you want to monitor.

# FOR ALL THE DETAILS OF THIS AND MANY OTHER ELECTRONICS PROJECTS, GET

# ELECTRONICS TODAY INTERNATIONAL

Send this form with your remittance, **INFONET**, 5 River Park Estate, Berkhamsted, Herts. HP4 1HL.

made payable to Argus Specialist Publications Ltd.


**SUBSCRIPTION RATES**

12 issues UK	£16.80
12 issues Europe	£21.00
12 issues Middle East	£21.20
12 issues Far East	£22.80
USA	£21.50
Air Mail Rates on Request	\$32.00

Please begin my subscription(s) to ELECTRONICS TODAY INTERNATIONAL with the  issue.  
 I enclose my cheque/postal order for £..... from my Access/Barclaycard No. .... to  
 or debit £..... valid from  to   
**NAME (Mr/Mrs/Miss)** .....,  
**ADDRESS** .....,  
**Postcode** .....,  
**Signature** .....,  
**Date** .....,  
 Please use **BLOCK CAPITALS** and include **post codes**
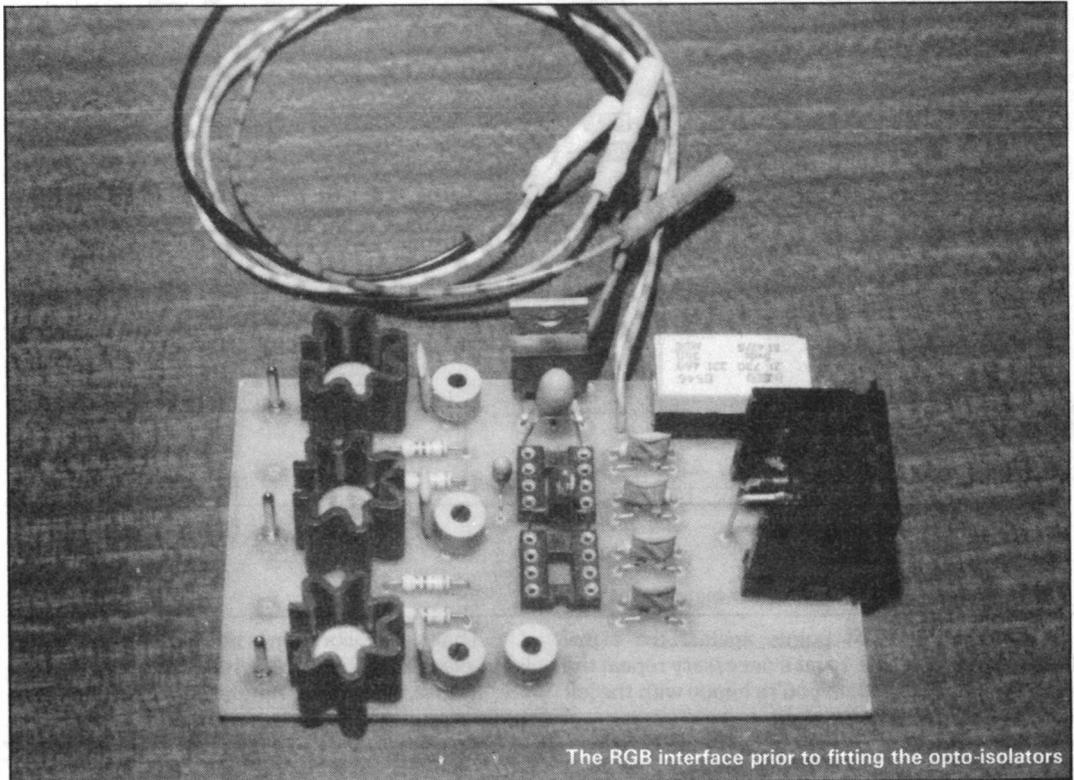
# TV TO RGB CONVERSION

David Lerche has converted his TV to work as an RGB monitor and has provided an RGB buffer board for his Electron for good measure



The RGB interface prior to fitting the opto-isolators

## PROJECT

**T**here have been many designs for TV RGB conversion circuits published in the past. However, they tend to suffer from the one basic disadvantage of requiring a transformer to isolate the TV set from the mains. This component is not only expensive and bulky but it usually won't fit inside your set. This means connecting it into the mains lead where it is probably a hazard and certainly an eyesore. It doesn't make a nice piece of furniture lying around your living room carpet and no doubt the rest of your family will complain about another piece of 'computer junk' cluttering up the living room.

This design overcomes this problem. By using high speed (10MHz) opto-couplers, complete electrical isolation of the computer from the TV set is achieved, as well as providing a video bandwidth greater than the resolution of most TV tubes. The interface is only 2x3<sup>3</sup>/<sub>4</sub>in so it will easily fit inside most sets, while still providing the same degree of safety one expects from a transformer.

The original design was built to interface an old HMV Colourmaster television to an Acorn Electron computer via the RGB DIN socket. Any of the BBC range of computers will work with this interface and it has been tested on both a model B and a Master. It shouldn't take much alteration to make it work with any other type of computer, provided it has the necessary RGB outputs.

As far as the RGB outputs from the Electron are concerned, they are fed directly from a 74LS08 to the RGB DIN socket and not from emitter followers as in the Beeb. This means the Electron can drive short interface leads of two or three feet without too much problem but longer than that and ringing starts to occur on the trailing edge of signals, giving trails on

the screen. An emitter follower circuit which fits inside the Electron is given later.

### Construction

There are no real construction problems. The component overlay is shown in Fig. 2. Transistors Q1, 2 and 3 require small heat sinks. They don't run appreciably hot but as there is anywhere from 0V to 200V on their collectors, it is better to be safe than sorry.

There is not much room for capacitor C5 between IC1 and IC2. It may be necessary to mount it high to allow the ICs to be fitted.

RLA1, D1, RV1, R1 and C1 are only required for automatic switch over of signal from television to computer and can be omitted otherwise.

### Modifying your TV

It is essential you have some expert knowledge before you remove the rear cover from your set to begin the modifications. Remember there are very high voltages involved in generating TV pictures.

The internal workings of TV sets are so varied that it is impossible, within the scope of this article, to cover all the possibilities, particularly with regard to any sync circuit modifications. All I can do is show you how I modified my set. I should say that with many modern receivers it is almost impossible to carry out such modifications, as most, if not all of the video processing is carried out inside one of those large many legged integrated circuits.

The set that I modified (fairly old by today's standards) had a Thorn 3500 chassis so the following description will make references to that.

# HOW IT WORKS

Fig. 1 shows the interface circuit. The R, G, B and sync signals leave the computer through the 6-pin DIN socket, to drive the LEDs inside opto-couplers IC1, 2 via resistors R1, 2, 3 and 4.

The small capacitor across each resistor is needed to improve HF response, although I found it made very little difference subjectively. The sync then goes on to drive the video output and sync operator stages of the TV set.

Although the computer sync signal also drives the video output transistors of the TV set, the sync signal is also the 'colour black' which effectively switches off the video output transistors leaving the interface transistors to drive the tube cathodes on their own.

The outputs from the opto-couplers drive the emitters of the output transistors, by way of presets RV2, 3 and 4. The 'grounded base' configuration is needed to allow a voltage change from the 5V logic level, up to the 100 or so volts necessary to drive the tube cathodes.

The +5V supply from the computer activates relay RLA1. This relay is provided so that the video signal from the TV set can be routed through the interface, which will automatically switch between off air signal and computer syncs every time the computer is switched on.

If you are not sure about the layout of your own set, write down the model number and go to the reference section of your local library to consult *Electrical & Radio Trader* or the *Newnes Radio and Television Service Manuals*.

The open collectors of the RGB interface output transistors Q1, 2 & 3 are connected to the cathodes of the CRT. They are in parallel with the set's own video output transistors and share their collector load resistors. Even though they are left in circuit when the RGB interface is not in use, they have no loading effect on the normal operation of the television.

On the Thorn 3500 the output of the luminance delay line is disconnected from the base of the first video transistor (Fig. 4) and connected by a short fly lead to the interface relay. The output from the interface relay is connected to the base of the first video transistor.

This effectively allows the interface to automatically switch the set between incoming TV signal and RGB signal when the computer is switched on.

## PARTS LIST

### RESISTORS (all 1/4 W 5%)

R1-4	68R
R5-8	560R
RV1	1k0 cermet preset
RV2-4	2k0 cermet preset

### CAPACITORS

C1-4	220p ceramic
C5	4μ7 6.3V tantalum
C6	33μ 6.3V tantalum
C7	220n 6.3V tantalum
C8-10	330p ceramic

### SEMICONDUCTORS

IC1, 2	6N137
IC3	7805
Q1-3	BF259
D1	1N4148

### MISCELLANEOUS

SKT1	6-Pin PCB mounted DIN socket
RLA1	5V 2-pole, 2-way relay
PCB	T03 Heatsinks. Connecting wire.

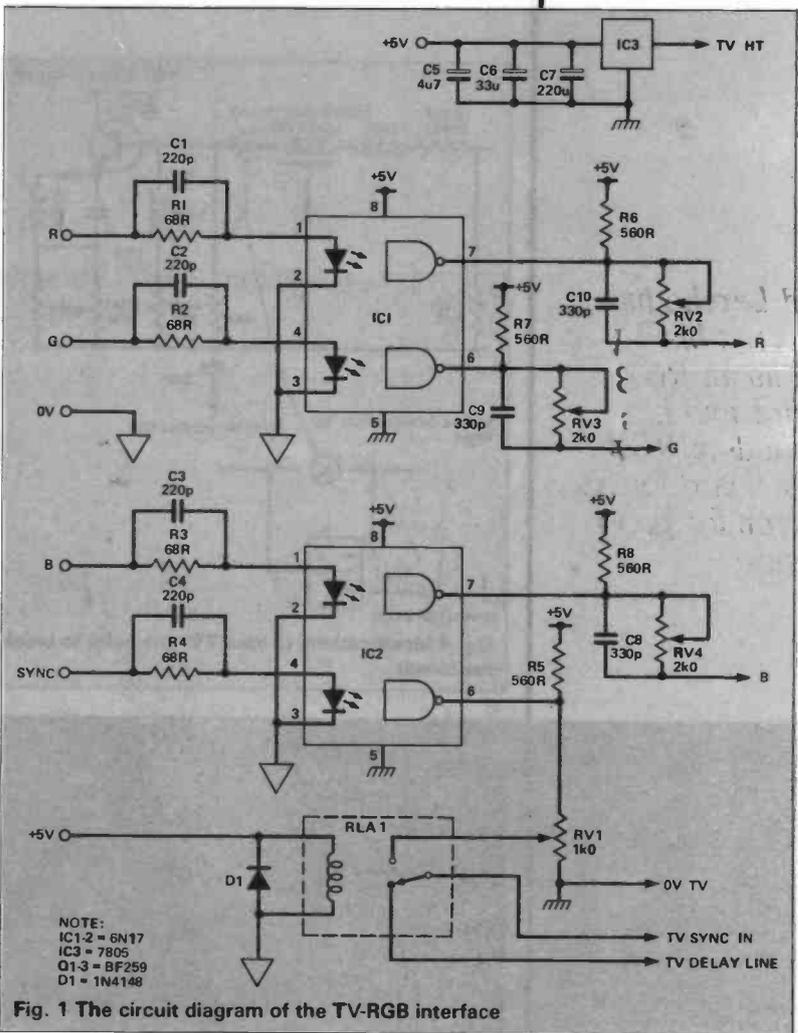


Fig. 1 The circuit diagram of the TV-RGB interface

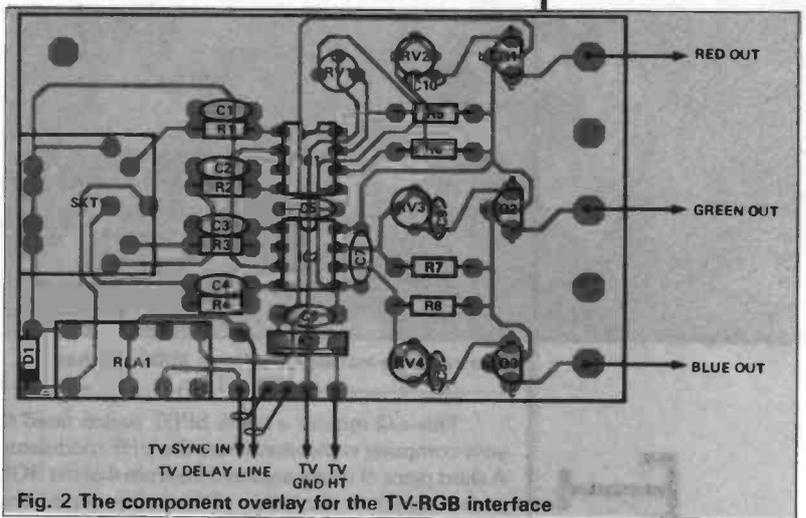


Fig. 2 The component overlay for the TV-RGB interface

or off, or when the RGB lead is plugged in or out.

If the set is receiving an 'off air' signal while the RGB interface is in use, the chrominance component of that signal will break through to give peculiar colour effects on the screen. This problem is easily remedied by either slightly detuning your set so that the colour killer circuit works, or by turning the colour control knob to a position where the colour picture would normally go to black and white.

Apart from the controls mentioned, none of the set's other controls (brightness, contrast and so on) will have any effect on the picture from the computer. RGB picture quality is set only by the 2k0 presets (RV2-4) on the interface board.

Should you consider that breaking into the video circuit of your television is not what you wish to do, a simpler but less automatic approach can be adopted.

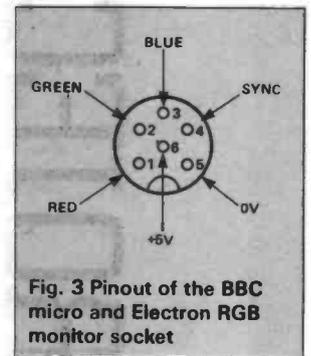


Fig. 3 Pinout of the BBC micro and Electron RGB monitor socket


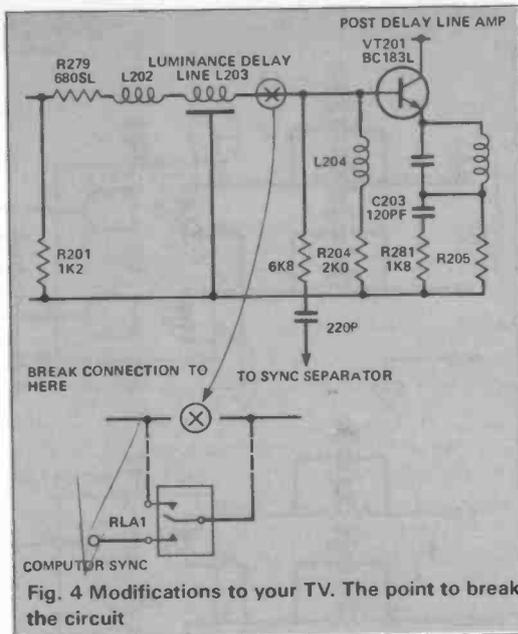


Fig. 4 Modifications to your TV. The point to break the circuit

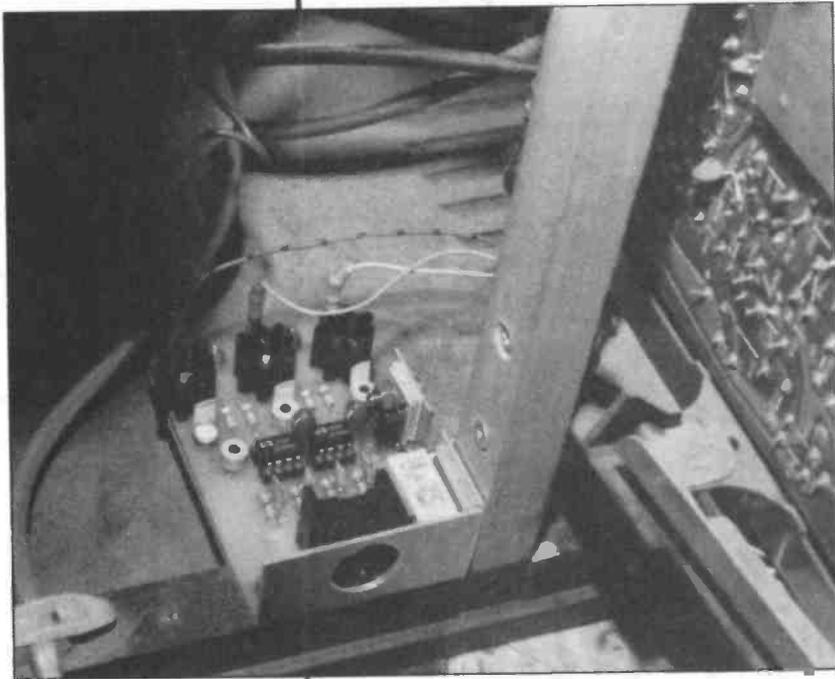

The interface installed in a Thorn 3500 TV chassis

This will require a small SPDT switch fitted to your computer somewhere near the UHF modulator. A short piece of wire is soldered from pin 4 of the RGB socket (sync) on the inside of the computer, to one pole of the SPDT Switch. The video signal that would normally get to the UHF modulator goes to the other pole. The centre contact of the switch now goes to the UHF modulator (Fig. 5).

This will now supply syncs and a black level signal to your television aerial socket when the switch is in the RGB position and standard UHF computer video when it is in the other position. Connect the RGB video outputs as before and connect the RF output of your computer to the aerial input of your TV set.

Tune your TV to your computer (channel 36) and again turn the colour control to black and white. You will now have two leads from your computer to your television. The RF lead providing the sync signals while the RGB lead provides the information.

If you use this method of connection, the sync signal components and the relay on the RGB interface board can be dispensed with.

I derived the +5V supply for the output side of the RGB interface from the TV set's normal HT, if you have difficulty doing this then a separate +5V supply will have to be found. As the current consumption is quite low, one of the mains adapters for personal stereo recorders would be ideal. The 7805 on this interface was dropping about 25V, so it was essential to provide it with a heat sink. I used the RGB interface aluminium mounting bracket for this, bolting the 7805 directly to the aluminium. This puts the bracket at the same potential as the chassis of the set so make sure your DIN plug cannot touch the aluminium. If you are in any doubt use a mica washer under the 7805 to isolate it.

## Testing

Adjust the controls on your set to obtain a black and white off-air signal, set all the pre-sets on the RGB interface to mid-position, connect up the interface to the computer and switch the computer on. You should hear the interface relay click (if fitted) if all is well. If not, switch off and investigate.

Assuming that the relay works, you should have a picture of sorts. If the picture is not locked steady, adjust RV1 until it is, or adjust your tuner if you are using the computer modulator to supply the syncs. Now it is just a case of adjusting RV2-4 for the best possible picture.

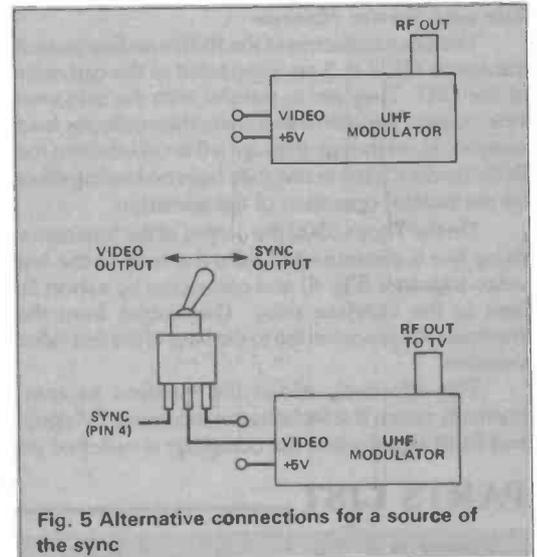


Fig. 5 Alternative connections for a source of the sync

## Electron RGB

For users of the Electron, its RGB output is not buffered with emitter followers as is the Beeb's, and so long monitor cables cannot be used. To solve this small problem I have designed an add-on emitter follower interface to install in the Electron to give it the same RGB output capability as the BBC micro.

## Construction

There should be no problem building the interface (Fig. 6). The only tricky bit is fitting it inside the Electron itself. The pads marked N and S on the component overlay are for wire links to the Electron's PCB. They should have about an inch of 26swg wire soldered in, with the wire hanging down from the under (copper) side of the board.

It is better to put a small loop in the end of the wire on the component side, to stop it from being pulled through the board while it is being soldered in.

Once you have built the interface driver, remove the main PCB from the computer and locate resistors R45, R46 and R47 (68R) situated near the RGB DIN socket (Fig. 8). Unsolder the resistors and fit the six

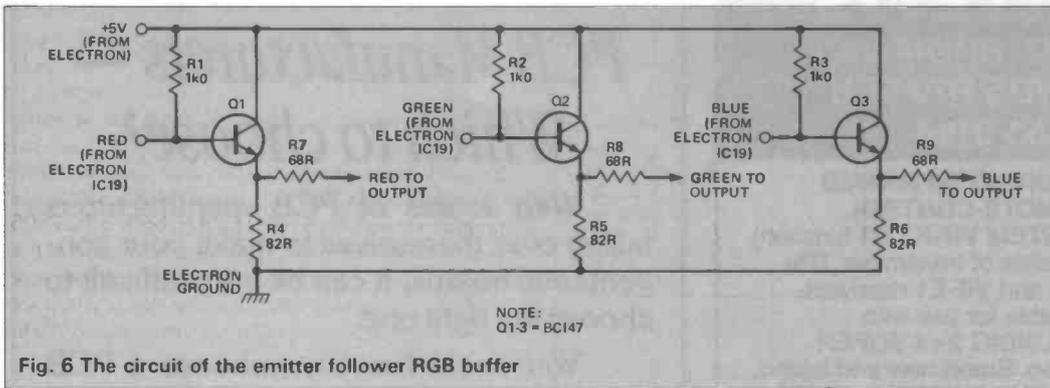


Fig. 6 The circuit of the emitter follower RGB buffer

## HOW IT WORKS

The three transistors Q1-3 are acting as emitter followers for the R, G and B colour signals coming from IC19 (74LS08) within the computer. They provide a lower impedance drive to the DIN socket than IC19 can on its own. This allows you to use a longer RGB lead between your computer and monitor or TV set without ringing occurring. It also gives a much brighter and more saturated picture when driving professional monitors, particularly when it is driving into a 75R load. The 1k0 resistors from the base leads of the transistors to +5V are extra pull-up resistors to assist the outputs from IC19.

wires from the underside of the interface driver into the holes left by the resistors, with the wires from the S pads going to the holes nearest the front of the computer and from the N holes to the rear.

Solder the driver board in position, making sure it sits as low as possible, use a bit of post card underneath for insulation if necessary. This is to make sure that when you re-assemble your Electron, the keyboard cable does not foul the interface board. Connect the +5V lead from the interface board to the collector of transistor Q7 on the Electron PCB and the 0V lead to capacitor C21, soldering the wire to the leg of the capacitor nearest the front of the computer.

Reassemble your Electron, plug in the RGB lead, switch on and you should be rewarded with a much better picture than you had before.

## PARTS LIST

### RESISTORS (all 1/4W 5%)

R1-3	1K0
R4-6	82R
7-8	68R

### SEMICONDUCTORS

Q1-3	BC147
------	-------

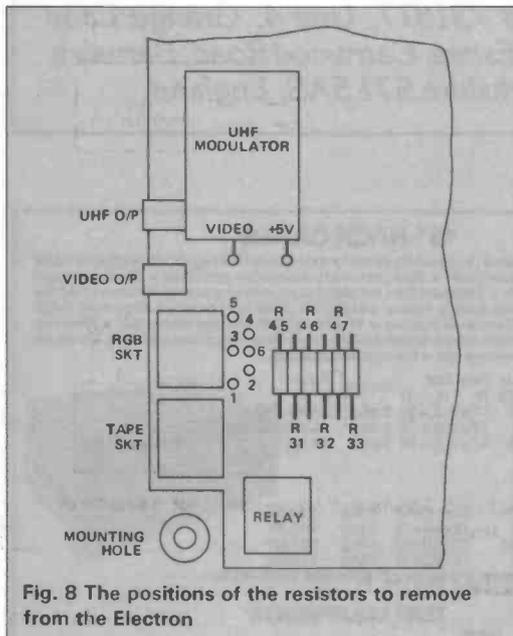


Fig. 8 The positions of the resistors to remove from the Electron



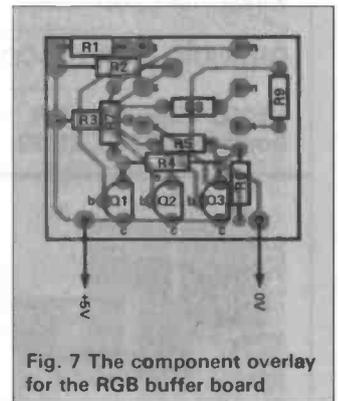


Fig. 7 The component overlay for the RGB buffer board

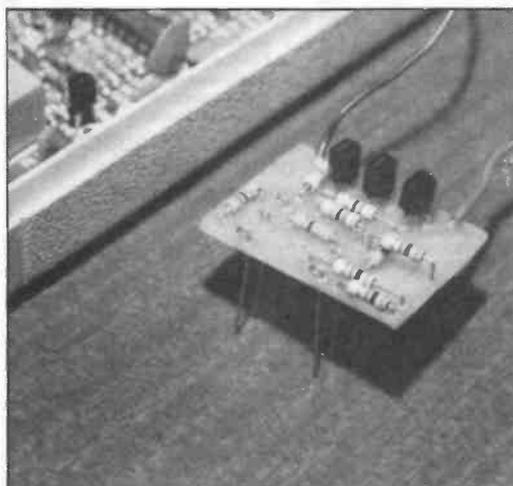

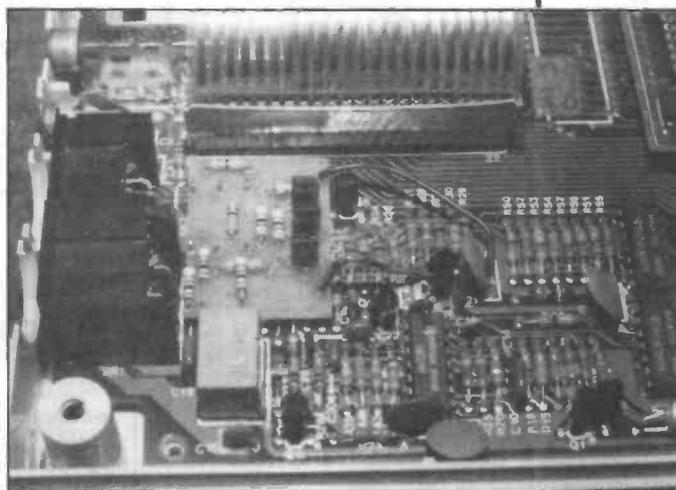The Electron RGB buffer prior to installation



The RGB buffer installed in the Electron

## BUYLINES

Most of the components used in both the TV interface and the RGB buffer board are easily available. The opto-isolators (IC1, 2) are available from Electromail (Tel: (0536) 204555) as part 302-104 as is the relay as part 345-741. The PCBs are available from the ETI PCB service. Details at the end of this issue



# STAN WILLETTS

37 HIGH ST, WEST BROMWICH,  
WEST MIDLANDS B70 6PB

Tel: 021-553 0186



**GRUNDIG INFRA-RED  
REMOTE-CONTROL  
SYSTEM VIF-K1** (13 function),  
consists of transmitter TPV  
355 and VIF-E1 receivers,  
suitable for use with  
GRUNDIG 2x4 SUPER  
Video. Brand new and boxed,  
complete with battery, £4.99  
p&p £2.00.  
VIF-E1 receivers in boxes of  
10, £9.99 p&p £4.

**GRUNDIG 2x4 video heads** complete with head  
assembly, £24 p&p £4. Complete power pack, £19.99  
p&p £4.00.

**2x4 SUPER PANELS = DFT — SERVO VIDEO —  
CROMA — STERITON**, Meter-board, Modulator and  
Tuner, £5.99 p&p £1.00.

**GRUNDIG REMOTE-CONTROL**, £2.99 p&p £1.00.

**V2000 VIDEO TAPES**, "MEMOREX", brand new and  
boxed; VCC360, £6.99; VCC480, £7.99.



**VHS VIDEO TAPES:  
"VIDEOLAB" PREMIUM  
QUALITY** brand, which we  
recommend and guarantee,  
one for one exchange, £1.99  
p&p £1.00.  
**TDK, SCOTCH, FUJI**, £2.99;  
**MEMOREX**, £2.69.

**VIDEO HEAD CASSETTE  
CLEANERS**  
£1.99, with full instructions.  
VHS or BETA, p&p £1.00.



**VIDEO HEAD CASSETTE  
DEMAGNETISER**  
Electronic circuit, LED  
indication degausses one  
second.  
£7.99 p&p £1.00.

**VIDEO RECORDER, SONY C5  
AND C7 SANYO**, etc, perfect  
working order, £39.99 (caller only).



**THERMOMETER-  
COMPASS AND CLOCK**  
(detachable), brand new.  
£1.99 p&p 75p.

**FREQUENCY TRANSLATOR**  
8 Channel UHF and tunable  
mains voltage, used but in  
working order, £4.99 p&p  
£5.00.



**PLEASE NOTE WE ARE INTERESTED IN  
PURCHASING ALL TYPES OF EQUIPMENT**

Advertisement

## PCB Manufacturers — Which to choose?

With scores of PCB manufacturers falling over themselves to make your conventional boards, it can be very difficult to choose the right one.

You could however, choose a PCB manufacturer with more to offer. Such as, assembly, panel printing, final build and design.

Slee Electro Products can provide you with these services and will still offer you competitive prices on your PCB's.


"We're hot on quality and delivery too. And being a member of the Printed Circuit Association, means we have to try harder."

*Slee Electro Products, Tel: 0226 200717,  
Fax: 0226 731817, Unit 4, Grange Lane  
Industrial Estate, Carrwood Road, Barnsley,  
South Yorkshire S71 5AS, England.*

### 19" RACK CASES

★ Suitable for instruments, high quality amplifiers and many other applications that demand strength and professional finish ★ New improved construction and finish ★ Black anodised aluminium front panels ★ Separate front mounting plate, no fixing screws visible on the front and the side of the enclosure ★ Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet ★ Rear box manufactured from 1.1mm steel finished in black. Rack mounting or free standing. Comes in quick assembly flat package spare front panels available.

Order Code	Panel Size W H (inch)	Rear Box W H D	Weight	Price £
1U-10	19 x 1.75	17 x 1.5 x 10	2.4kg	23.50
2U-10	19 x 3.5	17 x 3.0 x 10	2.9kg	24.50
3U-10	19 x 5.25	17 x 5.0 x 10	3.5kg	26.50

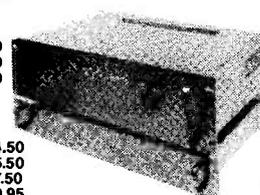


1U-12	19 x 1.75	17 x 1.5 x 12	2.8kg	£24.50
2U-12	19 x 3.5	17 x 3.0 x 12	3.3kg	£25.50
3U-12	19 x 5.25	17 x 5.0 x 12	4.0kg	£27.50
4U-12	19 x 7.0	17 x 6.5 x 12	4.6kg	£29.95

Please add £3.00 P&P for the first item and £1.50 for each additional item.  
No VAT to be added to the price.

### TEST EQUIPMENTS

NEW

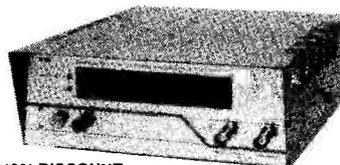

#### C550 8-DIGIT 550MHZ FREQUENCY COUNTER

- ★ Auto channel selection
- ★ Dual Decimal Points Indication
- ★ Selection of Gate Times
- ★ Complete with RF Cable and Technical Manual

**SPECIAL INTRODUCTORY  
OFFER £79.50**  
offer ends 31.10.88

10% DISCOUNT  
ON TEST EQUIPMENTS  
WITH THIS ADVERT  
(not valid for C550)

C550 550 MHZ Frequency Counter	£94.50
C83A Digital Power Supply/Voltmeter (0/35 Volts 1.5 A)	£49.50
C83B Digital Power Supply (0/30 Volts 1 A)	£40.50
C89A Function Generator (2 Hz to 200 KHz)	£43.50
C86A 60 MHz Counter/Timer	£55.50
C87A Autoranging Capacitance Meter (0.1 pF to 999 mF)	£55.50
MV338 Metal-mains detector	£4.99


High quality test equipments at an incredibly low price. Customers who have bought from us are delighted with the quality and found them excellent value for money. Place an order now. We will give you your money back if you are not completely satisfied and return the unit within 14 days. Please add £3 p/p per item (50p for MV338).

To order send cheque/postal order. Quantity discount available. Customers who require further information please send S.A.E. Trade and overseas orders welcome. Mail order only.

**T.J.A. DEVELOPMENTS**  
Dept. ETI, 19 Welbeck Road,  
Harrow, Middlesex HA2 0RN.

# THE VARIATION

# PROJECT

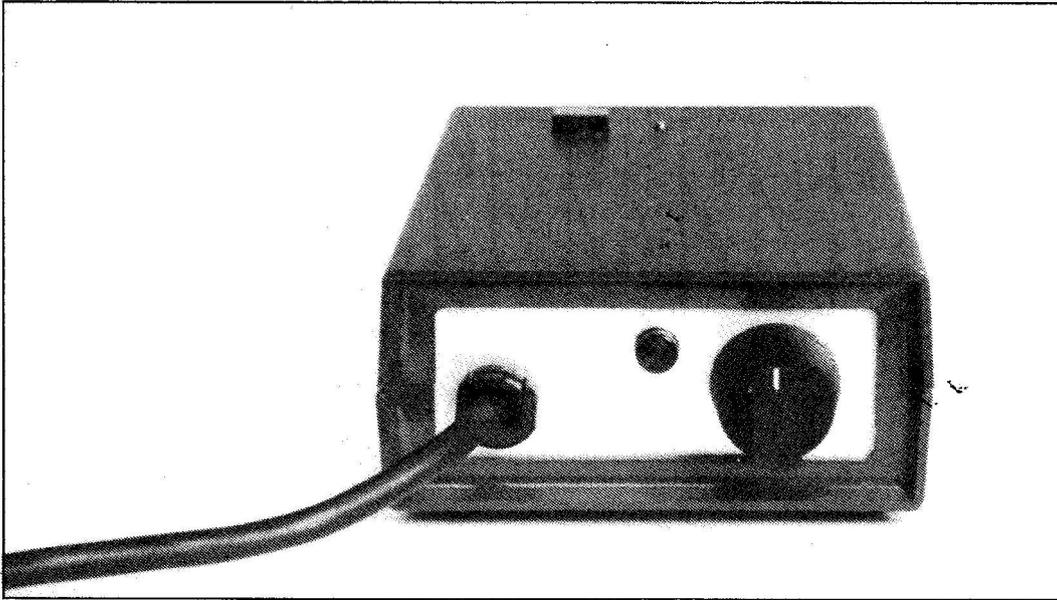

**T**he most spectacular demonstration of an ioniser's powers has got to be the vanishing smoke trick. It's what got me hooked, anyway. Ionisers are usually promoted as health aids — they heal the sick, make the blind see, cause the lame to dance the hornpipe and probably raise the dead too if some of the more frenzied hype is to be believed. But it's the odd way they behave that really grabs your attention.

You don't need to be a member of the magic circle to baffle people with the smoke trick. The only equipment you need is an ioniser, a glass jar and a cigarette. Pass the ioniser around your audience. Look: no fans, no filters, no moving parts. Puff cigarette smoke gently into the glass jar until the air inside is a thick, grey smog. Invert the jar over the ioniser. The smog swirls around for a few seconds and suddenly the air is crystal clear again!

This, you explain to your audience, is one of the ioniser's minor powers. For an encore it will cause the blind to dance, the dead to see and may even heal the hornpipe. Or will it?

The Great Ion Debate has been aired (pun slightly intended) at one time or another in just about every science publication from *New Scientist* to the *International Journal of Biometeorology*. Research papers on the subject have appeared in almost any medical journal you care to name. Air ions have been investigated by such diverse bodies as NASA (when looking at the environment needed in space capsules), Mercedes Benz (ditto in cars) and the World Health Organisation. Yet still there's no overall agreement on what ions can do for you or just how important they are.

## Ions In The Air

Air ions are nothing more than gas molecules which have either gained or lost an electron. Add an electron and you get a negative ion, or neg-ion for short. Subtract an electron and you end up with a pos-ion.


Ions occur naturally from a variety of causes: by the friction of one layer of air on another (like school electrostatics experiments where charges are generated by rubbing glass or plastic rods with a cloth), by the action of ionising radiations (ultra-violet rays

from the sun or nuclear 'background' radiation from naturally occurring minerals), from the electrical discharges associated with thunderstorms, from waterfalls and from many other sources.

The natural ion density in open countryside, far from city pollution, varies from around 300 to 1000 ions/cc of air. Close to vast ion generators, like the Niagara falls or the sea, levels of 2000 ions/cc and above can be measured.

In man-made environments the ion count is likely to be much lower. In cities, the life of each ion is much shortened by air pollution — smoke, dirt, traffic fumes and so on. In houses, whether in town

*Paul Chappell is fit and healthy thanks to this super powerful, variable and ion-counting air ioniser*

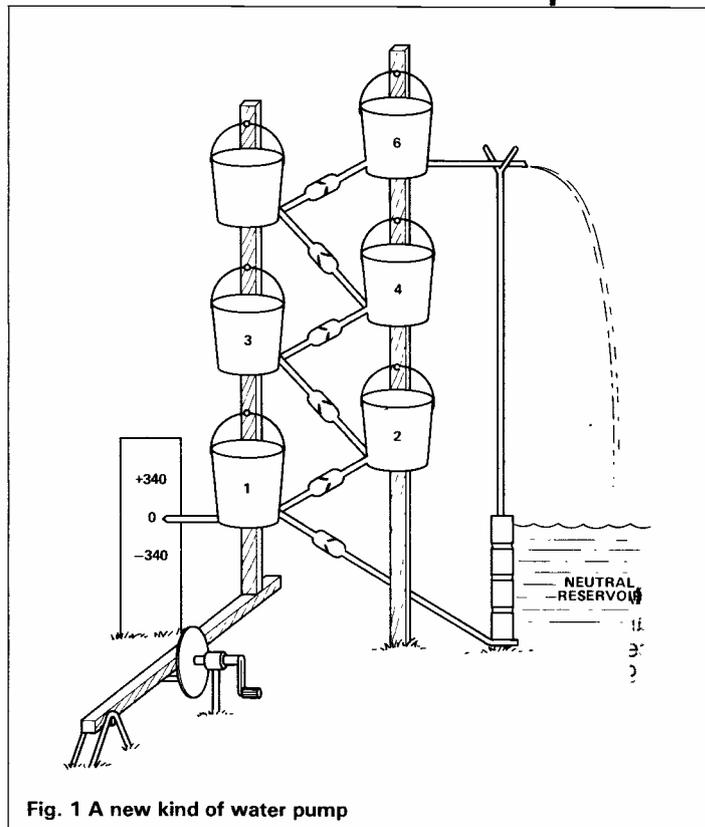

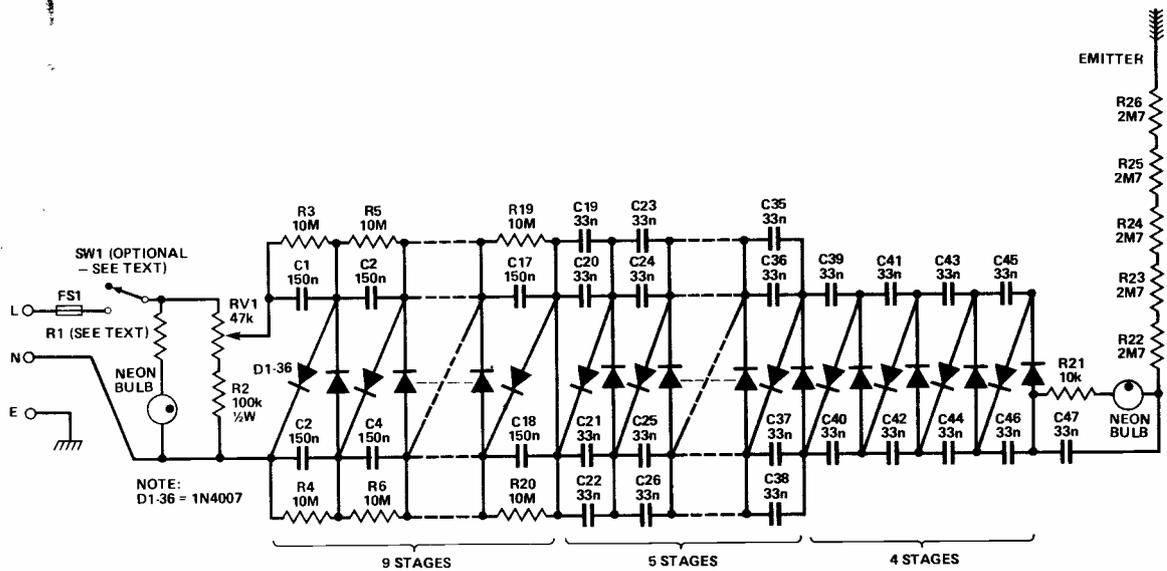


Fig. 2 The circuit of the Variat-Ion

or country, the effects of modern building and furnishing materials all act to remove ions from the air quicker than natural processes can replace them. The undisputed result is that most people spend most of the time breathing ion impoverished air. The case for owning an ioniser, then, is that living in ion-starved air has bad effects, whereas breathing ion-rich air has good ones.

### Vitamins Of The Air

A demonstrably beneficial effect of ionising the air is the one you've already seen. Ionisers remove dirt, fumes and dust that might otherwise end up in your lungs. What happens is that as the particles come into contact with air ions, they pick up a greater and greater negative charge until they are drawn, by electrostatic attraction, to the nearest uncharged surface. Inside a jar, with an ioniser producing half a billion ions every second, this happens very quickly indeed. In a room the process takes a little longer, perhaps half an hour to remove most of the dust but it happens just the same. In a city street the pollution producers (cars, for instance) work so fast that the process doesn't stand a chance.

The effects of the neg-ions themselves are so profound that they are often described as 'vitamins of the air'. In a normal healthy person they seem to bring about feelings of tranquility and freedom from stress and worry — general state of well-being. In short, breathe in those ions and you'll feel great!

The evidence is partly anecdotal (people who have ionisers say they feel good and who am I to argue with them?) and partly physiological. The two main demonstrable effects are a reduction in serotonin levels and an increase in alpha activity in the brain.

Serotonin is a neurohormone which is produced in response to emotional stress. It has its part to play in the normal functioning of our bodies but when too much is produced too often the results can be counter-productive. The effects range from depression and irritability to (at worst) migraine headaches, nausea and vomiting.

Neg-ions help to prevent over production of serotonin — the hormone responsible for these unpleasant feelings. The way this is measured, if you're interested, is by detection of serotonin itself and a harmless by-product known as 5HA in urine samples

(don't you wish you hadn't asked?). Measurement of the quantities of these two substances shows how much serotonin is being produced and how effectively the body is breaking it down. The effects of neg-ions in reducing serotonin levels and aiding its breakdown are well documented.

As far as alpha activity is concerned, ions have the effect of increasing the duration and amplitude of this type of brain activity. Broadly speaking, electrical brain activity (as picked up by electrodes on the head) can be split (on the basis of frequency) into four main types: beta, the highest frequency associated with active thought; alpha, linked to pleasure and relaxation; theta, which indicates a state of reverie and delta, which only appears during sleep. For choice, unless you're driving a car or doing something else that needs your full attention, alpha is the state to be in.

Neg-ions have been recommended for all kinds of specific complaints but the strongest evidence for their beneficial effects is in the treatment of respiratory complaints (asthma, hay fever, bronchitis), migraine and, surprisingly, burns. The action of cleaning the air has to be of benefit in itself for any kind of respiratory disorder and the further effect of speeding up the action of the cilia (the cleaning cells in the respiratory tract) helps too. As far as burns are concerned, the rapid healing and reduced scar tissue seems to arise from ions absorbed directly by the skin rather than inhaled. Next time I burn my finger on the soldering iron I'll hold it above the ioniser and let you know. . .

My latest ioniser is one for the connoisseur. If you just want a small ioniser for your bedside the Direct-Ion (ETI, July 1986) will fit the bill admirably (and is quite a lot cheaper in parts). If you want one with enough power to run several multi-point emitters, variable ionisation potential and a built-in ion counter, the Variat-Ion is the ioniser for you.

There are all kinds of ways of producing ions, from radioactive sources to water sprays but by far the most convenient, predictable and safe method is to do it electrically. The principle is to create a high voltage and to apply it to one or more sharp points. Since charge density increases as radius of curvature gets less, the surplus electrons will be crammed tightly into the points and will gladly step off onto any passing air molecule. The molecule, now negatively charged, will be repelled from the point to make way for the next.

This accounts for the 'ion breeze' you feel if you put your hand close to the emitter.

Positive ions have an initial stimulating effect but after a while feelings of tiredness and irritation set in, which is why ionisers go for the negative ones.

## A Novel Water Pump

I really must tell you what happened to me earlier this week. I was passing the Neutral reservoir when I saw a group of people gathered around what looked like a lot of buckets hung on a pair of wooden posts. I stopped to take a closer look and discovered that the water board were trying out a new kind of manual pump. From memory, it looked something like Fig. 1.

Close to the reservoir was a tall wooden post on which had been hung a number of buckets, one above another. A few feet from the first post was a second one, similarly hung with buckets. The first post had been driven into the ground, whereas the second was supported on a kind of lever arrangement so that it would move up and down as the operator turned a crank. With the crank in the resting position, the bottom bucket was at just the same level as the water in the reservoir.

When the operator turned the crank, the second post fell and the bottom bucket immediately began filling with water through a hose from the reservoir. By the time the post was at the lowest extent of its travel, the bucket was full. As the crank lifted the post to its highest level with bucket 2 at the same height, the water began to transfer from bucket 1 to bucket 2 until the levels in each were the same. I asked why the water didn't simply go back the way it came into the reservoir and was told that each hose was fitted with a non-return valve which only let the water through in one direction.

With each movement of the post, a quarter of the water in each stationary bucket was moved into the one above. After three complete cycles of the crank, the bottom of the top bucket had just a little water in it. It will never catch on, I thought. Too much work for too little water! Now, if they made the lower buckets bigger than the higher ones...

## The Circuit

The internal workings of the ioniser are shown in Fig. 2. It is based on a Cockcroft-Walton diode and capacitor ladder, which is similar in some ways to a string of buckets (capacitors) connected by hoses (wires) with non-return valves (rectifiers) in them. The action is not as inefficient as the water pump analogy might lead you to believe — each capacitor is 'floating' on the voltage of the one before, so a more accurate analogy would have a load of nested buckets, each floating on the water contained in the one below! The analogy gives a general idea of the circuit in operation, though — enough for you to work out the details for yourself if you're interested.

The circuit is quite tricky to analyse in any detail but one principle that does emerge, and is applied in the Variat-Ion, is that the circuit is at its most efficient when the capacitors lower down in the chain are as

## PARTS LIST

### RESISTORS (all 1/4W 5%)

Note: All resistors, with the exception of R1, R2 and R21, should have a proof voltage of at least 1kV and a working voltage of 500V or more.

R1	150k (not needed if complete panel lamp used)
R2	100k 1/2W
R3-R20	10M (33M slightly better, if you can get them)
R21	10k
R22-26	2M7
RV1	47k 1in pot

### CAPACITORS


C1-C18	150n X2
C19-C46	33n X2
C47	47n 250V

### SEMICONDUCTORS

D1-D36	1N4007
--------	--------
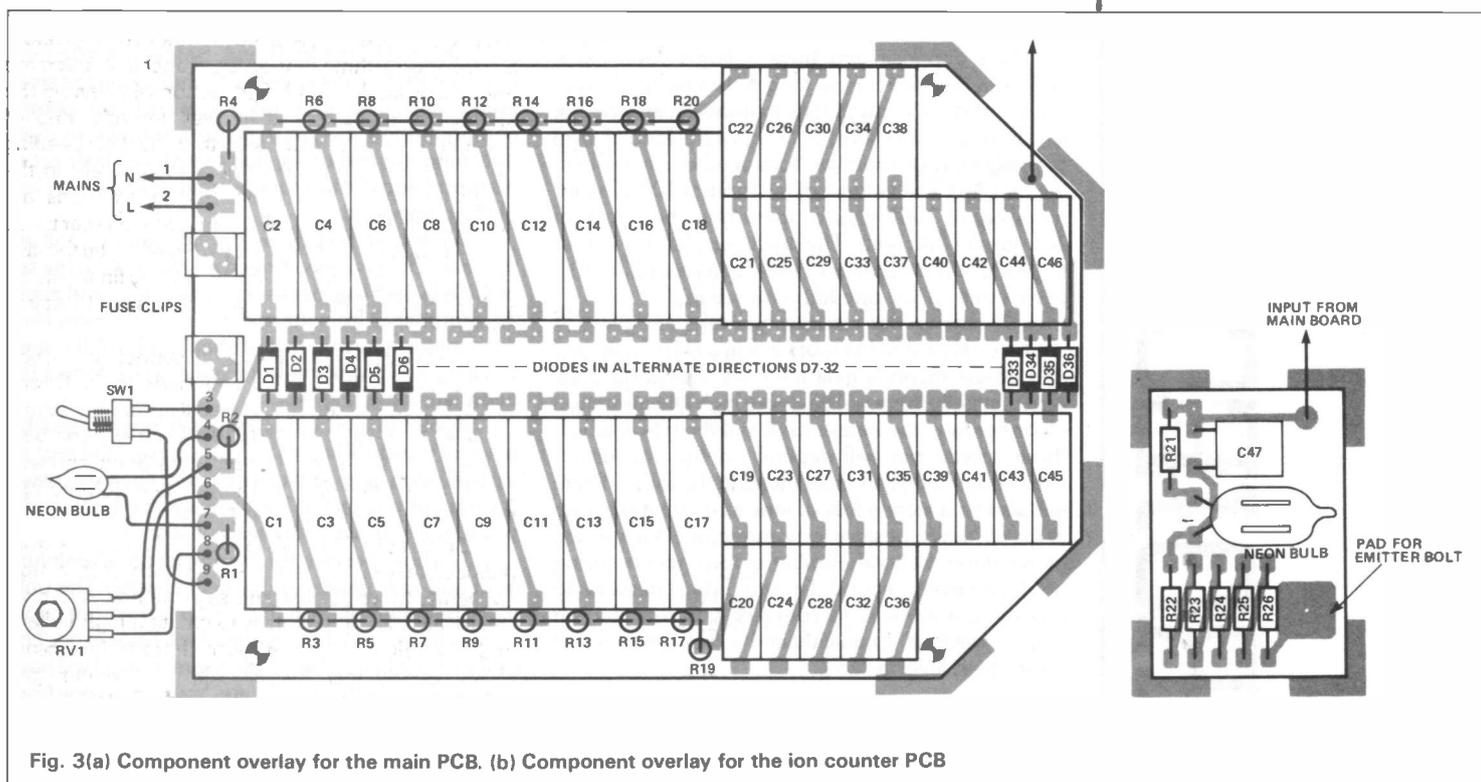
### MISCELLANEOUS

PCBs. Retex 'Elbox' 145x90x41mm case. Neon lamp. Plastic lens. Fuse and clips. Knob. Strain relief bush. Mains flex. Connecting wire. Emitter brush. Plastic offcut for rear panel. Nuts and bolts.





The original Direct-Ion ioniser (July 1986) on which the Variat-Ion is based

# PROJECT

large as possible. Increasing the value of the higher capacitors has diminishing effect, so the place to spend your available space and money is at the beginning of the chain where the effects are enormous! The first 18 capacitors in the chain are 15 times as large as those used in the earlier Direct-Ion, giving this ioniser plenty of spare power — enough to drive several multi-point emitters.

At the very top of the chain (the junction of D36 and C46) comes the ion counter. As the emitter ionises the air, the electrons attached to passing molecules are supplied by a current drawn through the resistor chain R22 to R26. The more ions created, the higher the current.

Most of the time the emitter current is supplied by C47, giving a steadily rising voltage across it. Sooner or later the voltage will rise high enough for the neon bulb to strike. The bulb draws current from C47 for a short time until the voltage across the capacitor will no longer sustain conduction. The neon, having discharged the capacitor by about 50V, goes out and will not conduct again until the voltage across C47 has once more risen to its striking voltage.

The value of C47 should be somewhere between 10n and 100n. If it's less than 10n, the flashing will barely be bright enough to see. If it's much above 100n, the time between flashes is too long — you have to sit by the ioniser for minutes at a time to judge the output. The value I've specified in the parts list is 47n, which will give about one flash every thirty seconds with an average emitter — a lot quicker with a good emitter and quicker still if you bring your hand or face within a foot or so of the tips to draw the ions away.

Assuming that each electron emerging from the emitter results in the creation of one ion, the number of ions generated between successive flashes of the counter is easily calculated. To bring a 47n cap from the neon's extinguishing voltage to its striking voltage — a difference of 50V — requires a total charge of  $2.35 \times 10^{-6}$  Coulomb (this is just calculated from  $q = CV$ ). The number of electrons which will have a total charge of 1 Coulomb is  $6.24 \times 10^{18}$ , so multiplying this by  $2.35 \times 10^{-6}$  gives the total number of ions created:  $1.47 \times 10^{13}$  or roughly fifteen billion ions. If the counter flashes at its average rate of once every thirty seconds, the Variat-Ion is creating thirty billion ions every minute!

Let's suppose you have a larger than usual bedroom of  $100\text{m}^3$ . How long will it take the Variat-Ion to produce enough ions to establish an average ion density of 1000ions/cc? (This is the kind of level you might find on mountain tops or other areas of high ion density.) The volume of the room is  $10^8\text{cc}$ , so for a density of 1000 ions/cc there must be a total of  $10^{11}$  ions in the room. The time taken for this ioniser to produce this number of ions, at a rate of  $3 \times 10^{13}$  per minute, is just one fifth of a second!

Of course, this assumes the ions are going to diffuse to all parts of the room within a fifth of a second and unless there's a gale force wind blowing, they won't. Initially there will be a very high concentration of ions around the ioniser itself and the rate at which these spread out will depend on the convection currents and other air movements in the room. There will also be a steady loss of ions as they hit particles in the air, walls, positive ions and so on. But at a rate of five times the total number of ions needed being produced every second, I'm sure I don't need to do any more arithmetic to convince you that the ion density will built up quickly and will be sustained at a very high level indeed.

## Construction

The component layout for the main PCB is shown in

Fig. 3a. Put in the rectifiers first or you'll find yourself trying to poke them between two tall rows of capacitors, which ain't easy. The rectifiers at the narrow end of the PCB are fairly close together — whether they will all lie flat against the board or not depends on the manufacturer of the particular rectifiers you buy. The diameter of 1N4006/7s varies from one make to another. The best way to proceed to put in every second diode (which will all point in the same direction so it's easy to check for one pointing the wrong way) and then fill in the gaps with the rectifiers pointing in the opposite direction, letting them sit a little above the PCB if necessary.

When you come to solder the diodes (and all the other components for that matter) it's a good idea to cut the leads to size first and solder afterwards. The bugbear of any EHT circuit is power loss through corona discharge from sharp points or edges which encourage discharge. If your soldering iron is too hot, you can also get spikes of solder when you remove the iron from the joint. Soldering along a row of leads one after another should keep the iron cool enough.

After the rectifiers, put in the capacitors. With encapsulated types it usually happens that the leads are not exactly central when they emerge from the case. The PCB allows for a slim gap between adjacent capacitors, but if one seems to be a tight fit, turning it around should cure the problem. Finally, solder in the resistors and a few inches of insulated wire to join the 'hot' end of the board to the emitter board.

At this stage, clean the board thoroughly with isopropyl alcohol or a proprietary board cleaner of some kind, then spray on a few coats of anti-corona compound. This isn't absolutely essential but if you want to prevent unnecessary losses in the circuit it's a good idea. Spray both sides of the PCB and give it at least fifteen minutes to dry between coats. It will try your patience but it's well worth the bother.

While you're waiting for the anti-corona spray to dry, you can assemble the emitter and ion counter board (Fig. 3b). Leave a little slack in the neon bulb leads to allow it to be positioned under the lens later on. Once again, cut the component leads before soldering. After soldering the components, push a 20mm M3 bolt through the hole in the large, square pad, with the head on the copper side of the board (Fig. 4a), put on a nut to hold it in place, then solder the bolt head to the PCB pad. Solder the wire from the main PCB to the small PCB, then clean the small board and give it a few layers of anti-corona compound too. Before you spray, put two or three nuts onto the end of the bolt (which will later act as a support and contact for the emitter) to keep it clear of the compound.

While both boards are drying, you can drill out the case. The emitter will need a 1/8in hole in the top of the box, half way between the two sides and about 1in (not critical) from the end. Half an inch away from the emitter, towards the left-hand side of the case (looking at it from the front panel end) comes the neon lens hole (Fig. 4b).

If you can't get hold of a separate lens or a suitable piece of translucent plastic, you can saw the end off a panel neon lamp and use that. It's a shame to waste a lamp but you can at least salvage the bulb (and if you're really miserly, the resistor too!).

The box specified for the project has aluminium front and rear panels and a steel chassis. The only metal part allowable on the ioniser is the front panel — the chassis and the rear panel will have to go. The chassis is not needed at all, but the rear panel will have to be replaced with a plastic one. You can cut one from the plastic case of a retired project, using the metal panel as a template or you may use some other suitable material.

The front panel has to be drilled for the mains lead (which must be fitted with a strain relief bush), the neon lamp and the pot RV1. If you use a separate resistor R1, neon bulb and lens (wired as in Fig. 3a), the 'mains on' indicator can go in any convenient position. If you use a panel neon assembly (wired as in Fig. 4c — note that R1 is no longer required) the hole must be mid-way across the panel and fairly high up so that the neon body is well clear of the components on the PCB. The pot and mains inlet positions you can arrange according to taste but wiring is a darn sight easier if you put the inlet to the left and the pot to the right. It also helps if you bolt the pot to the panel with its tags facing upwards.

Now that the boards are dry you can solder the fuse holder clips to the PCB (if you'd soldered them earlier they'd be covered in goo by now!) Also solder three 3in lengths of insulated wire for the pot connections and a similar length for the neon lamp connection. Push the mains wire through the strain relief bush, then push the bush through the panel hole, squeezing the bush with pliers to clamp the wire firmly. There should be about 4in of mains lead on the inward side of the panel. Strip off all but 1/4in of the outer insulation and cut the live and neutral wires back to about 1 1/2in length. Strip the ends and solder them to the PCB.

By this time you will feel more like a snake handler than an electronics enthusiast, with several feet of mains wire connected to the large PCB connected to the small PCB and a metal panel dangling somewhere along the way. To tidy everything up, screw the main PCB into the case (using four no.4 6.4mm self tapping screws), slot the front panel into the lower section of the case and tape the small PCB temporarily to the main PCB to prevent the link wire from flexing and maybe breaking.

Now the front panel has to be earthed. In the prototype I used a neon lamp with a metal body which fixed to the front panel with a nut and shakeproof washer. A 0BA solder tag fitted neatly over the body and was held between the washer and the panel. The earth wire was soldered to the tag.

Now solder the neon lamp wires and the pot wires (makes it much easier with the terminals facing upwards, doesn't it?) and check out your wiring carefully with Fig. 4c. There is provision on the PCB for an on/off switch if you want to fit one. I didn't — the ioniser is left on day and night and I've never wanted to turn it off! There is also provision for fitting a separate neon bulb and resistor if you prefer this to using a complete lamp assembly. Connections are shown in Fig. 3a.

Remove the tape holding the small PCB to the large one. Twist another nut onto the emitter bolt and rest a shakeproof washer on top of it. Push the end of the bolt through the hole in the case lid and adjust the position of the nut so that when it is pushed against the lid the PCB will be level with the neon bulb just underneath the lens. Above the case top, drop another washer onto the bolt, put on another nut and, holding the PCB so that it doesn't twist around, tighten up the nut to hold the PCB firmly in place (Fig. 4d). Just to make sure the nuts don't work loose, you can apply a little Loctite or Superglue or some similar preparation.

Push the back panel into the bottom case section and bring the two halves of the case together. Put in the case screws, tighten them up, push on the plastic feet and you're done. Apart from the emitter, that's it.

## Emitters

The emitter used on the prototype was an airgun cleaning brush. It works well, but a rifle cleaning brush

is better, and a brush with 'V' shaped wire soldered to the top is best of all (Fig. 6a). The wire is sharpened by cutting it with a pair of flush-cutting wire cutters used 'upside down' — that is, with the flat side of the cutters pointing away from the brush and the bevelled side towards it. The brush simply screws onto the emitter bolt — the chances are that the thread won't quite match (I took my brush along to the local hardware shop and they couldn't find any thread to match it!) but it should screw down far enough to be held firmly. As a last resort you could solder an M3 nut to the bottom of the brush, but it shouldn't be necessary.

If you fancy experimenting with different emitters (and since the effectiveness of the ioniser depends very much on the quality of the emitter it's certainly worth doing) there are all kinds of things you can try. A very effective emitter, although it doesn't look very pretty, is a length of stranded connecting wire with about 1/2in of insulation removed and the strands separated out so that they point upwards, sideways, all directions. If you remove 2in or so of insulation, you'll find the strands will be attracted to your finger. With 6in of bared wire, you've got an electric forest that will wave about if you pass your hand above it!

I have been told that carbon fibres make a very effective emitter. Rumour has it that it's possible to buy reels of the stuff in a kind of carbon rope from which the individual strands can be separated out. So far I've been unable to track down a source so I can't give a first hand report. If you find any — try it!

Sewing needles can make fairly good emitters, especially if you use several of them. Outside the case they would be a menace — imagine having a restless night and impaling your hand on one — but inside the case they'd be fine. The way to arrange it is to get hold of an offcut of copper clad board, solder the needles along one edge (stainless steel doesn't solder too well, so you may need to fix the needles in place

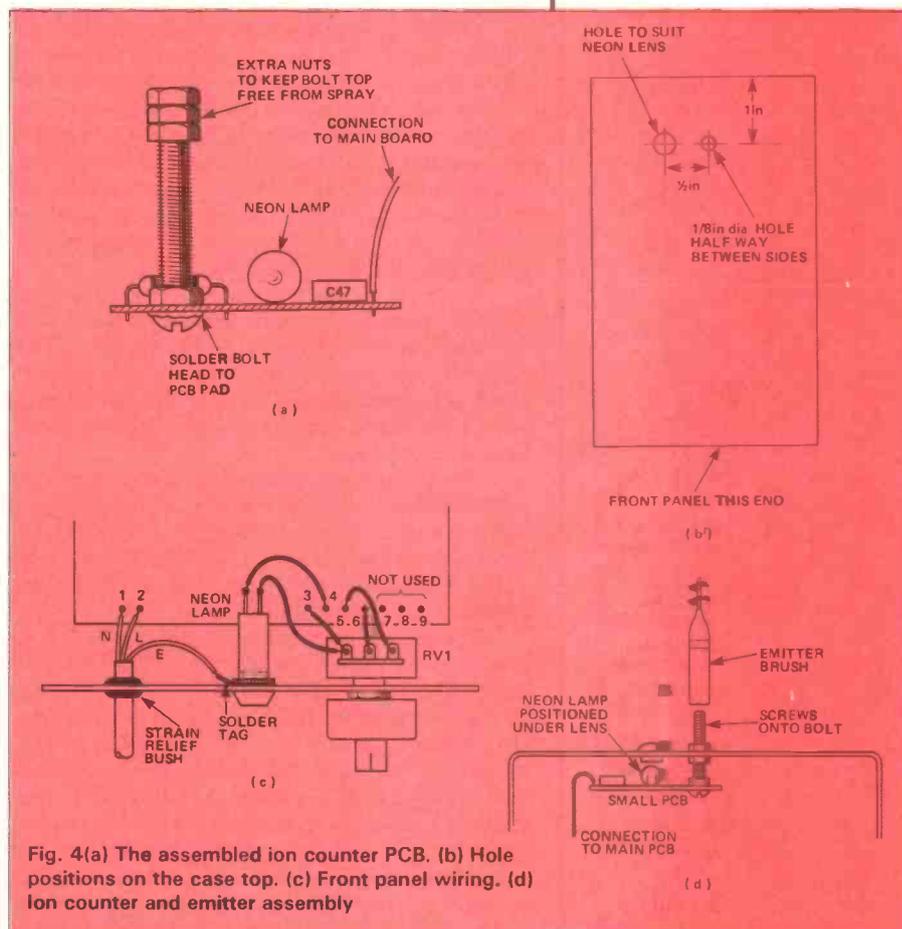


Fig. 4(a) The assembled ion counter PCB. (b) Hole positions on the case top. (c) Front panel wiring. (d) Front panel ion counter and emitter assembly

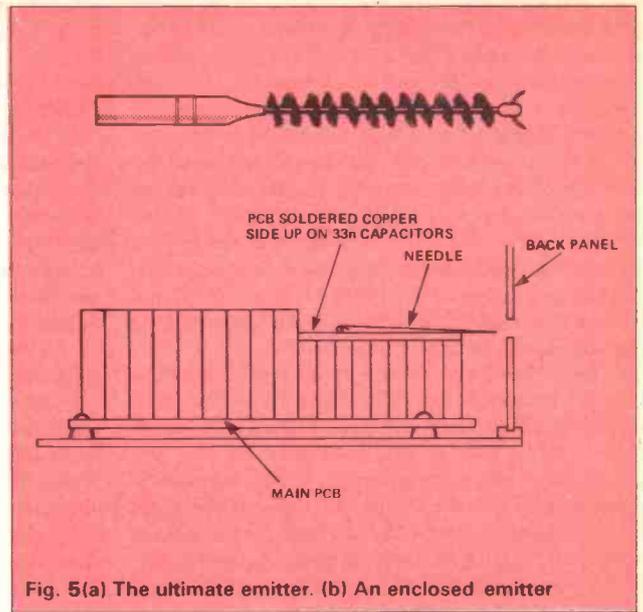
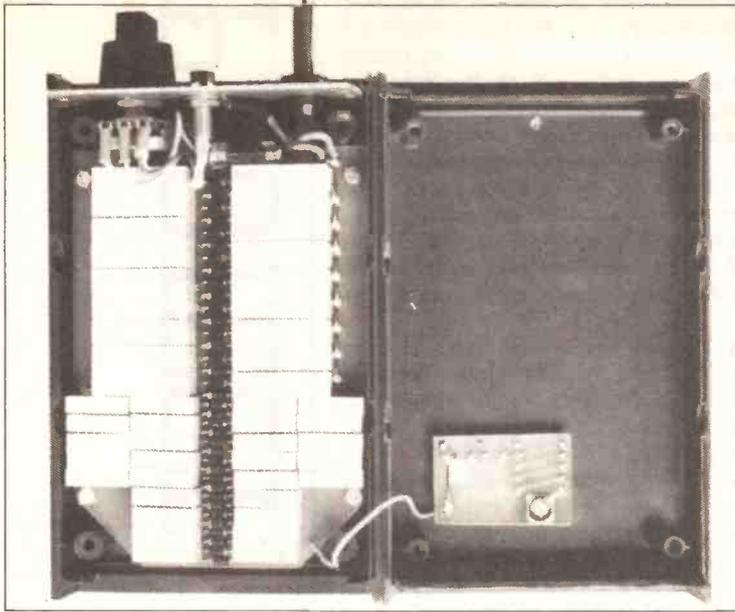


Fig. 5(a) The ultimate emitter. (b) An enclosed emitter

some other way) then glue the board copper side up onto the 33n caps at the end of the main PCB. Drill a 3/16in hole for each needle in the plastic end panel of the case and you have a completely enclosed ioniser (the needle tips should be about 1/4in behind the holes). This won't give you a better ioniser but if it is to be used by children it may be preferable to having an exposed emitter. (Fig. 5b).

The general rule is that anything with sharp points or edges will make a good emitter. Come to think of it, a razor blade would probably work well, although comments about pins outside the case should be multiplied by a factor of 99 billion where razor blades are concerned. Inside the case — why not?

Certain types of houseplant make excellent ion emitters. I remember hearing once that somebody was actually making plant pots with an ioniser built into the base, although I've never actually seen one. Have to be a bit careful watering the plants with a 5kV ion generator in the vicinity, I should think. If you want to try it out, choose a plant with sharp, pointy leaves, stand it on a polythene bag, run a wire from the ioniser's output bolt to the soil in the plant pot and you've got your very own triffid.

If you put your hand close to one of the leaves, it will be drawn towards you. Let the leaf touch you and it will spring back again. A very shy triffid. The reason is, of course, that the leaf discharges as soon as it touches your hand. Plants don't seem to mind being ionisers and some say they grow better when treated in this way.

The Variat-Ion is quite powerful enough to run several emitters — you can spread empty plastic boxes with gun brushes attached all round the room and run them all from the one ioniser. The best scheme is to give each brush a separate series resistor so that it can select its own operating voltage.

The ionisation potential control can be left at maximum for most types of emitter. The time you need a lower potential is if the emitter has very fine points, like the carbon fibres, needles or (possibly) the razor blade! If you use too high a potential, all that happens is that the current density in the point will melt it, round it off and make the ion emission less efficient. The best thing is to bring the control up from minimum until you feel a distinct breeze from the points and leave it on the setting where that first occurs. If you can afford to waste a few emitters, you can try setting the control higher, then check an hour

later to make sure that the ionisation rate is just as strong. If the ion counter is flashing less frequently, you've got the control set too high, so start again. Keep the windows open while you're doing this to keep the ion density in the room fairly low, since the rate of emission will drop off in any case as the room becomes saturated with delicious neg-ions.

### Safety

The Variat-Ion works by raising a piece of metal to several thousand volts above its surroundings. In the version with the external emitter it is possible to touch both the high voltage part and an earthed object (such as the front panel of the ioniser itself) simultaneously. For any healthy adult this experience is not in the least dangerous, or even shocking, if you'll excuse the pun, since the current available is very small. The circumstances where I would advise caution are either if you have any reason to suppose your heart is dodgy, if you (or anyone else who may come into contact with the ioniser) have a pacemaker or if young children are likely to have access to it. In any of these cases, the safest thing would be to make the fully enclosed version where the ionising points cannot be touched.

The current available from the ioniser will depend to some extent on the quality of the mains earth in your house. In mine, I measured 75 $\mu$ A on the prototype. The maximum current from the ionising tip to mains neutral (which is the maximum current available no matter how good your earth) was 110 $\mu$ A. The current needed to have any effect on a healthy adult is well over 100 times as great so there's a good safety margin.

The main problem with young children is not that the current itself may harm them but that the surprise of a sudden tingle (which they will feel more keenly through sensitive skin than you will through your tough fingertips) might cause them to drop the ioniser or knock it onto the floor, with who knows what results? If in doubt, enclose the points, OK?

If you have to dismantle the ioniser for testing or any other reason after it has been turned on, be sure to discharge it thoroughly by touching the neutral prong of the mains plug to the emitter. There are resistors to bleed away the charge on the larger caps but with any EHT circuit you can't be too careful.

### Living With Ions

When you try out the ioniser the first thing you might notice in a quiet room is a gentle hiss from the emitter.

If you don't — put it a bit closer to your ear! The gentle breath you feel on your hands or face a few inches from the emitter is the ion breeze I spoke of earlier.

It's quite understandable if you feel a little way of the ioniser at first. The best thing is to approach it boldly. Touch the emitter with the back of your hand. You'll hear a little squeak as you make contact but you shouldn't feel anything at all. The only way you can get a tingle from the ioniser is to touch some earthed surface (like the front panel of the ioniser itself) and to hold a finger about 1/8in from a flat part of the emitter — the shaft of the gun brush. Alternatively, you can touch the emitter and hold a finger close to the front panel. The sensation comes about because conduction in your finger takes place in a series of quick pulses as your body charges and discharges. Touch the emitter and earth without leaving a gap and you'll feel nothing again. So now you know, and there'll be no surprises!

The Variat-Ion is designed to run continuously, day and night. If you don't want the bother of moving it around the house, the best place for it is by your bedside where you will have the benefit of ionised air for eight hours or so at a time. Because its strong action in precipitating dirt and dust from the air, it's a good idea to stand the ioniser on a washable surface a few feet away from the nearest wall. The dust will then fall in the carpet and be swept up during normal household cleaning. Too close to a wall and it may taint the paint or wallpaper, which will not be too popular with the Mizz.

The lightest and most active ions are found close to the emitter, so the nearer the ioniser is to your bed, the better. This is particularly important when it is being used to treat respiratory complaints, which seem

to need the small, highly mobile ions. If you're just looking for a general improvement in mood and brain function, put it anywhere in the room.

Some people like to hold the ioniser quite close to their face and breathe deeply for minutes at a time. This, they say, makes them feel fresh and alert. Others just like to know there's an ioniser around the place and may not touch it for weeks at a stretch. Some move it from room to room during the day, and even take it to work with them. Others prefer to let the ions build up in one single room. Some say their ioniser has changed their life. Others say they can't be sure but look uncomfortable if you suggest turning it off!

There are as many ways to live with an ioniser as there are individuals, but one thing's for sure: anybody who's ever owned an ioniser would never again want to be without one.

**ETI**

## BUYLINES

The Retex case for the project is available from West Hyde Developments (standard version) or Specialist Semiconductors (with plastic rear panel). Suitable resistors can be obtained from a number of suppliers but the rule is to check before ordering since most 1/4W types are only rated for 300V. Half watt resistors are a better bet. Gun cleaning brushes can be obtained from any hunting, shooting and fishing shop (look under 'Arms and Ammunition' in Yellow Pages). Class X capacitors will be available from any large component catalogue, as will board cleaning preparations and anti-corona compound. A complete parts set for the project can be obtained for £29.32, inclusive of postage and VAT from Specialist Semiconductors, Founders House, Redbrook, Monmouth, Gwent NP5 4LU. Components are available individually from the same source.

# PROJECT

## ZENITH KITS - FOR THE ELECTRONICS ENTHUSIAST



The following is a selection from our catalogue:

- Black Ice Alarm (for Winter Motorists).....Kit **£17.53**
- Negative Ion Machine, complete with case.....Kit **£24.11**
- Miniature F.M. 'BUG' transmitter 60-145MHz.....Kit **£6.95**
- 3-Watt F.M. transmitter 80-108MHz 12-Volt.....Kit **£13.99**
- Running light sequencer 10-channel, varispeed...Kit **£15.89**
- Audio Power Meter 10-LED indication.....Kit **£12.94**
- VU-Meter 10-LED indication P.P.M. display.....Kit **£13.63**
- Electronic Door chime 3-note - variable freq.....Kit **£9.85**
- Infrared transmitter/receiver system.....Kit **£33.09**
- Light Activated Relay, 9-12Volt opp.....Kit **£8.91**
- Metal and Voltage Detector.....R/Built **£11.00**
- Tone Generator - Pulse or Warble tones.....Kit **£5.50**
- Loudspeaker Protector 5-100Watts.....Kit **£11.40**

■ All Kits are available **READY BUILT** please see latest Catalogue.

■ All Kits contain full instructions PCBs and components ■ All prices include VAT and postage and packing ■ Overseas orders add 10% to above prices ■ Please send Cheque or Postal Order with Order.


**ZENITH ELECTRONICS** Dept. 1  
Cortlandt Business Centre  
Hailsham, East Sussex, UK BN27 1AE  
Telephone (0323) 847973  
Telex 878334 Fax 647204

**Access & Barclaycard Orders**  
Telephone (0323) 847973

**S.A.E.**  
(A4 + 26p)  
for  
**FREE**  
Catalogue
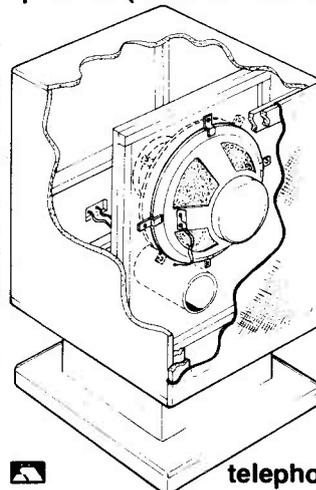
## £150 + £125 = £1000?

Add our £125 sub-bass unit to your £150-per-pair "Best Buys" and your system will sound as if it has **LARGE** (and expensive!) speakers. Although very compact, this ingenious Push-Pull design will fill-in that missing "Bottom Octave" and can be sited almost anywhere in the room — without affecting the stereo image. It can be connected directly into systems with medium sized speakers (87-90 dB sensitivity).



The Wilmslow Audio CPP sub-bass speaker kit contains 2 10" drive units, flatpack cabinet kit (inc. stand) machined from smooth MDF for easy assembly, low pass filters, grille fabric, reflex port etc.  
Dims. (inc stand):  
571x366x336mm  
Amp. suitability:  
20-120 watts  
Impedance: 8 ohms  
PRICE £125 inc. VAT  
plus carr/ins £11

☎ telephone credit card orders ☎


**WILMSLOW AUDIO LTD.**  
35/39 Church Street, Wilmslow, Cheshire  
SK9 1AS Tel: 0625 529599  
Call and see us for a great deal on HiFi  
(Closed all day Mondays)

DIY Speaker catalogue £1.50 post free (export \$6)




E8504-3	Framestore Control	N	E8705-5	Budget Power Meter	E
E8504-4	Buzby Meter	E	E8706-1	Hi-fi Power Meter	N
E8504-5	CCD Delay	F	E8706-2	MIDI Keyboard CPU	U
E8505-5	Stereo Simulator	F	E8706-3	MIDI Keyboard Front Panel	O
E8506-1	Audio Mixer Main	J	E8706-4	Flame Simulator	G
E8506-2	Audio Mixer PSU	F	E8707-1	MIDI Keyboard PSU	H
E8506-3	Audio Mixer RIAA	D	E8707-2	Telephone Alarm	J
E8506-4	Audio Mixer Tone Control	D	E8707-3	Nuclear Strategy Simulator	J
E8506-5	EPROM Prog MKII	O	E8708-1	Remindalite	F
E8507-1	Noise Gate	H	E8708-2	Rear Wiper Alarm	G
E8508-1	RCL Bridge	N	E8708-3	Rev Counter	F
E8508-2	EX42/BBC Interface	E	E8708-4	Car Alarm	F
E8508-3	EPROM Emulator	L	E8708-5	Knight Raider	J
E8509-1	Spectrum EPROM card	F	E8709-1	Boiler Controller	G
E8509-2	Direct Injection Box	E	E8709-2	Amstrad Sampler (2 bds)	P
E8510-9	Sunrise Light Brightener	K	E8709-3	Portable PA	G
E8511-1	MTE Waveform Generator	H	E8709-4	EEG Monitor (2 bds)	L
E8511-2	Millifaradometer	H	E8710-1	Concept CPU board	N
E8511-3	Cymbal Synth	J	E8710-2	Concept Power board	K
E8511-5	Chorus Effect	H	E8710-3	Concept display board	G
E8511-7	Enlarger Exposure Meter	F	E8710-4	Hyper-Fuzz	F
E8511-8	Switching Regulator	E	E8710-5	Big Digits digit board	N
E8511-9	Second Line of Defence	M	E8710-6	Big Digits minute board	F
E8512-1	Specdram Connector	F	E8710-7	Big Digits battery board	G
E8512-2	MTE Pulse Generator	H	E8711-1	Quiz Controller	E
E8512-3	Specdram	L	E8711-2	256K Printer Buffer	N
E8601-2	Walkmate	L	E8712-1	Heating Management System	O
E8601-3	MTE Counter-timer	M	E8712-2	SWR Meter	H
E8602-1	Digibaro	O	E8712-3	Dream Machine (free PCB)	D
E8603-2	Programmable Logic Evaluation Board	H	E8801-2	Passive IR Alarm	H
E8603-3	Sound Sampler Analogue Board	R	E8801-3	Deluxe Mains Conditioner	G
E8604-1	JLLH PA PSU	H	E8801-4	RGB Dissolve	L
E8604-2	Matchbox Amplifier	C	E8802-1	Electric Fencer	E
E8604-3	Matchbox Amp Bridging Version	C	E8802-2	Telephone Intercom	L
E8604-4	MTE Analogue/Digital Probe	M	E8802-3	Transistor Tester (2 bds)	L
E8605-1	Microlight Intercom	E	E8802-4	Spectrum Co-processor CPU	N
E8605-2	Baud Rate Converter	M	E8803-1	Co-processor RAM board	N
E8605-3	Baud Rate Converter PSU Board	C	E8803-2	Beeb-Scope (3 bds)	O
E8605-4	Portable PA	H	E8803-3	Jumping Jack Flash	E
E8606-1	MIDI-CV Converter Board	H	E8804-1	Spectrum Co-processor Interface Board	N
E8606-2	MIDI-CV Converter PSU	D	E8804-2	Combo-lock	E
E8606-3	Troglograph	F	E8804-3	Kitchen Timer	E
E8606-4	80m Receiver	H	E8805-1	Virtuoso 2U PSU	M
E8606-5	Sound Sampler	R	E8805-2	Virtuoso 3U PSU	N
E8607-1	Direction	E	E8805-3	Bicycle Speedometer	F
E8607-2	Upgradeable Amp, MC stage (Stereo)	G	E8805-4	Dynamic Noise Reduction	E
E8607-3	BBC Motor Controller	F	E8806-1	Universal digital panel meter	L
E8608-1	Digital Panel Meter	G	E8806-2	Universal bar graph panel meter	K
E8608-2	Upgradeable amp, MM stage (mono)	H	E8806-3	Virtuoso power amp board	N
E8609-1	Mains Conditioner	E	E8806-4	Virtuoso AOT board	G
E8609-2	Experimental pre-amp	F	E8806-5	Metal detector	E
E8609-3	Upgradeable amp, Tone board (mono)	H	E8806-6	Bicycle dynamo backup	D
E8609-4	Upgradeable amp, Output board (mono)	F	E8807-1	Bar Code Lock (2 bds)	N
E8610-1	Audio Analyser Filter Board	L	E8807-2	Analogue Computer Power Board	L
E8610-2	Audio Analyser Display Driver	K	E8807-3	Bell Boy	F
E8610-3	Audio Analyser Display	H	E8807-4	Logic Probe	C
E8610-4	Audio Analyser Power Supply	F	E8807-5	Updated FM stereo decoder	J
E8611-1	Audio Switcher (2 bds)	H	E8807-6	Breath Rate display board	F
E8611-2	PLL Frequency meter (4 bds)	Q	E8808-1	Breath rate main board	H
E8611-3	Upgradeable Amp PSU	J	E8808-2	Breath rate switch board	C
E8611-4	Call meter, main board	O	E8808-3	Telephone recorder	D
E8611-5	Call meter, interface board	N	E8808-4	Analogue computer main board (2 bds)	M
E8612-1	Bongo Box	J	E8808-5	Random number display	O
E8612-2	Biofeedback monitor (Free PCB)	E	E8809-1	Spectrum EPROM Emulator	M
E8701-1	RGB Converter	F	E8809-2	Frequency meter (2 bds)	P
E8701-2	Mains Controller	D	E8809-3	Travellers' Aerial Amp	E
E8701-3	Flanger	H	E8810-1	Gerrada Marweh Bikebell	E
E8701-4	Audio Selector main board	M	E8810-2	Peak Programme Meter (2bds)	N
E8701-5	Audio Selector PSU	H	E8810-3	Variat-Ion ioniser	K
E8701-6	Tacho-Dwell	F	E8810-4	TV-to-RGB converter	E
E8702-1	Ratometer main board	K	E8810-5	Electron RGB buffer	C
E8702-2	Ratometer ranging board	F			
E8702-3	Photo Process Controller (3 bds)	O			
E8702-4	LEDline display board (2 off)	K			
E8702-5	LEDline PSU and controller (2 bds)	G			
E8703-1	Capacitometer	F			
E8703-2	Geiger Counter	L			
E8703-3	Credit Card Casino	E			
E8704-1	BBC micro MIDI interface	L			
E8704-2	ETIFaker patch box	H			
E8704-3	24Hr Sundial	E			
E8705-3	MIDI Keyboard keyswitch boards (3 bds)	W			
E8705-4	Batlite	C			


# PCB FOIL PATTERNS

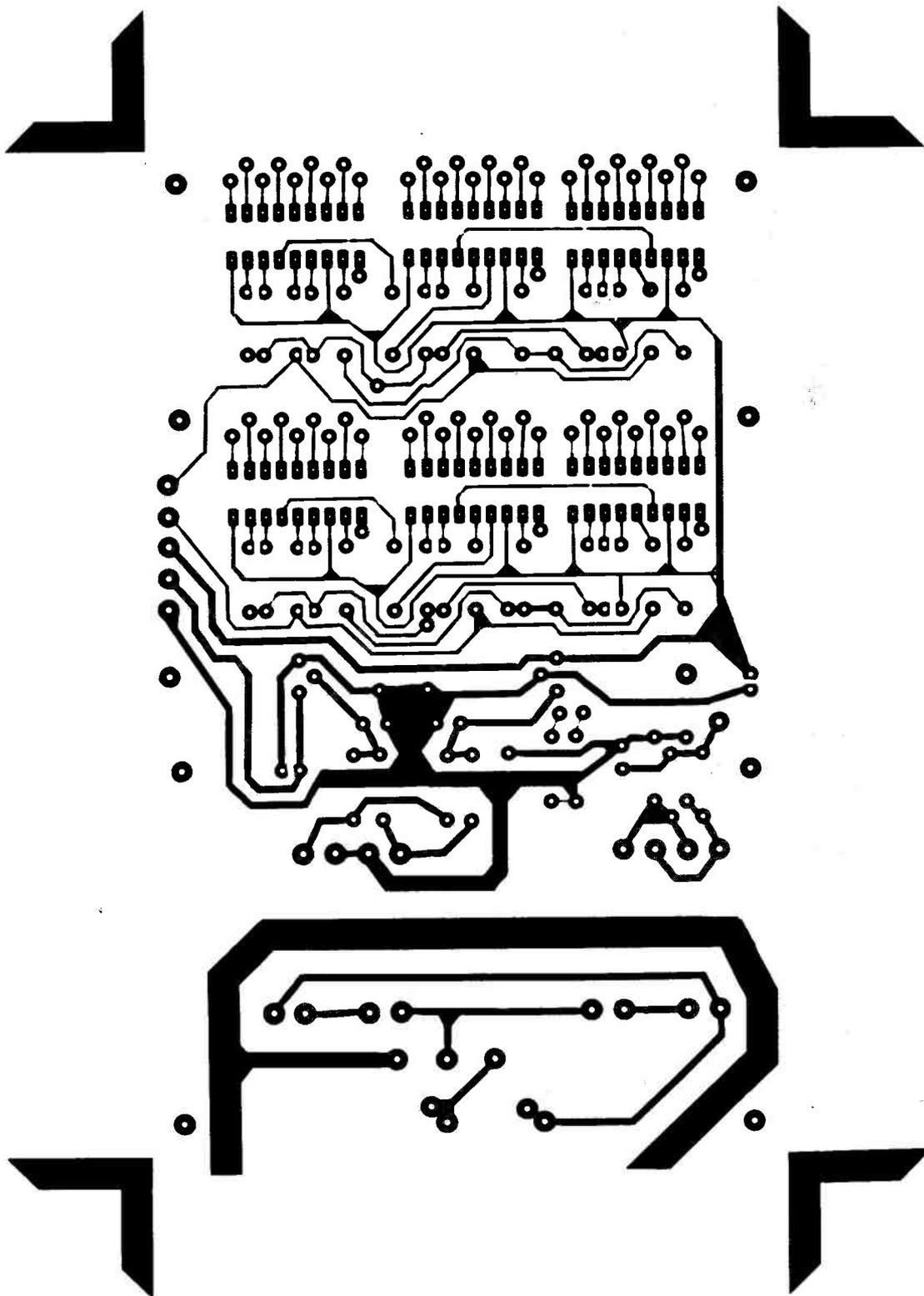


The Peak Programme Meter main board

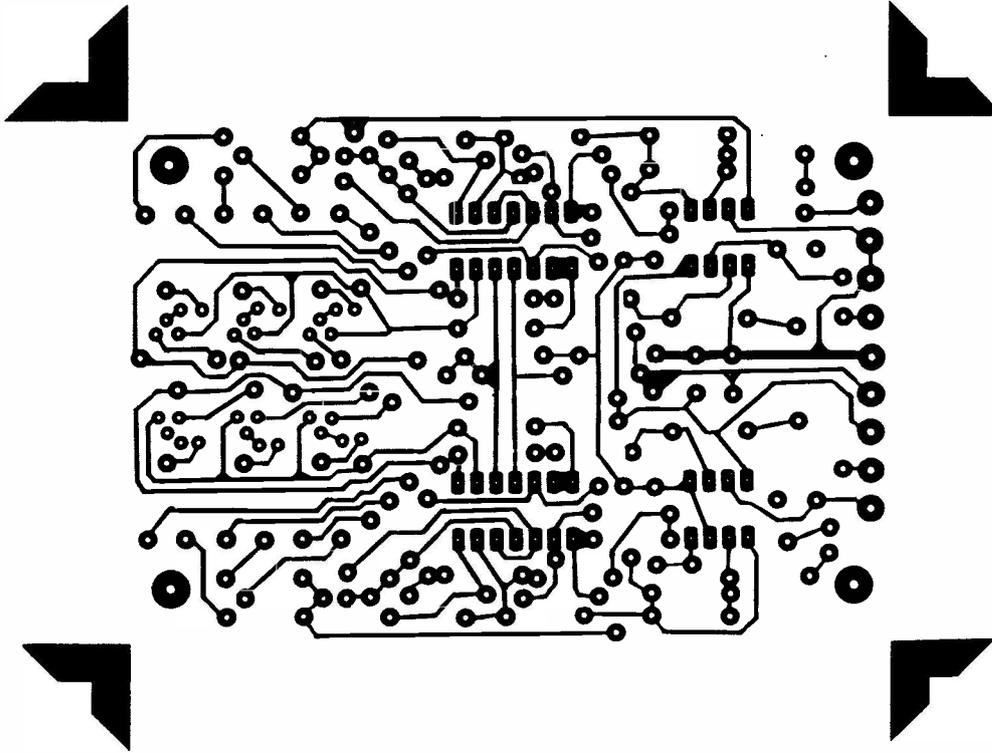


The Peak Programme Meter small board

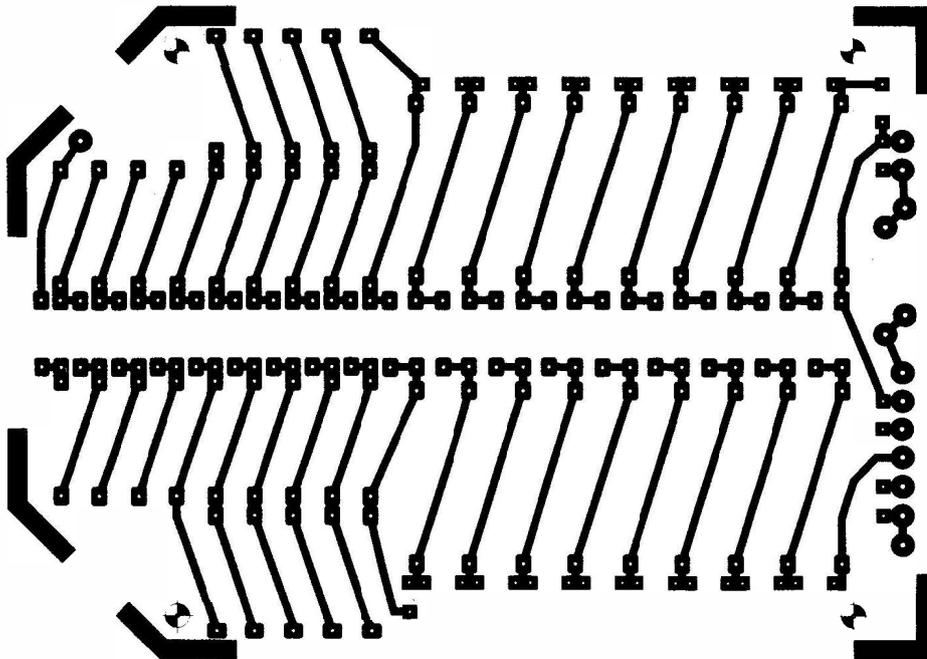


The Variat-Ion ioniser main board

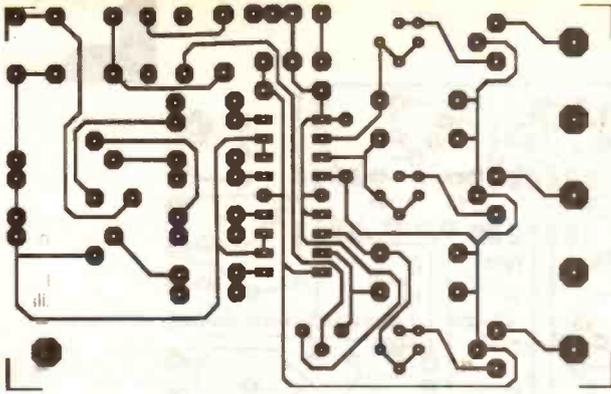


The TV-RGB converter board

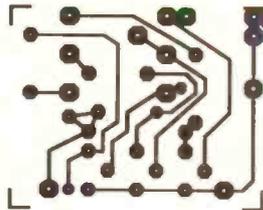

The Electron RGB booster board

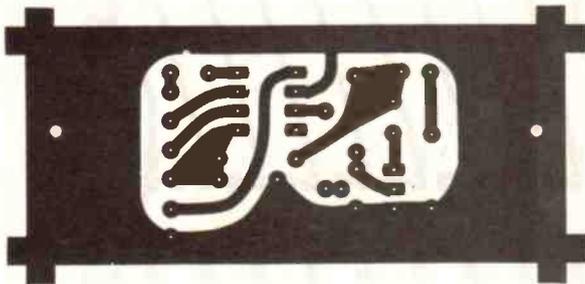

The Gerrada Marweh bikebell foil

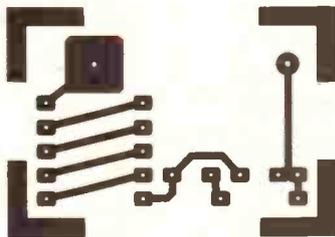

The Variat-ion emitter board



**Dream Machine** (December 1987)

The transistors used in this project are ST1702. BC108s can be substituted.

**Heating Management System**

(December 1987)

A 4116 is not a suitable alternative to the 6116 specified. A 4016 RAM chip will suffice. In Fig. 1 the junction of R1/D5 should connect to D1-4/C1 and not cross. The zener diodes above the temperature sensor ICs (IC16-19) should be deleted. C4 should be 220n and not 220μ. C7-10 should be 10μ. Q2-7 should be 2N3904 and not BC3904.

**RGB Auto-Dissolve** (January 1988)

In Fig. 5 there are marked two D6's. The right hand one should be D5 (they are both 1N148's anyway). In the text the reference to zener diode D5 should read ZD1.

**Power Conditioner** (January 1988)

There is confusion between the values of R7 and R8 in the Parts List and Fig. 1. These should be: R7-27k, R8-10k and not as given in the Parts List. In addition, ZD1 is incorrectly orientated in Fig. 3. The positive terminal should be at the southern end.

**Passive Infra-Red Alarm**

(January 1988)

Fig. 2(a) shows the base of Q1 connected to ground and to R14. It should be connected only to R14.

**Transistor Tester** (February 1988)

The foil pattern for the main board was printed reversed left-right on the foil pages.

**Spectrum Co-processor** (March 1988)

Mogul Electronics, given in the Buylines as suppliers of the RAM chips, have moved to: Unit 11, Vestry Estate, Sevenoaks TN14 5EU. Tel: (0732) 741841.

**Dynamic Noise Reduction** (May 1988)

The LM1894 is no longer available from the sources listed but it can be obtained from the author. Please address orders to Manu Mehra, 88 Gleneagle Road, Streatham, London SW16 6AF.

**QL Output Port** (Tech Tips May 1988)

Several problems with the diagram for this one. A5 should read AS — that is, address strobe. Pins 22 and 24 should be connected to +5V and the junction of the (only) resistor and diode connected to VPA on the QL.

**QWL Loudspeakers** (August 1988)

Some dimensions were missing from Fig. 7. The bass driver port centre should be 3 3/4in above the base of the baffle panel. The notches in the side of the tweeter cut-out are 1/2in wide. The top plate is missing from the cutout diagram (Fig. 6). This is 7 x 4 5/8in.

# ETI

## ELECTRONICS TODAY INTERNATIONAL



### CLASSIFIED

**Heather Wust**  
01-437 0699 Ext 292

Send your requirements to:  
**Heather Wust, ETI Classified Department, ASP Ltd.,**  
1 Golden Square, London W1.

Lineage: 54p per word VAT inclusive (minimum 15 words)  
Semi Display: (minimum 2 cms)  
£12.80 per single column centimetre + VAT

Ring for information on series bookings/discounts  
All advertisements in this section must be prepaid.  
Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

### COMPONENTS AND EQUIPMENT

#### F.J.P. KITS-COMPONENTS

Tel: 05435 6487  
No VAT prices. Wholesale/Retail components. By return of post. We are new to ETI and offer a personalised service to readers/professional user alike. Electronic components and amateur radio components is our business and will be looking at kits for ETI projects. We stock ICs, plugsockets, transistors, capacitors, switches, opto. solder, cable, boxes, pcb material.  
Semiconductors inc lcs: BC107 to 9 14p ea. BFY 50-51 28p, 2N3819 30p, 2N3054 90p, 2N3055 60p, 2N3773 £1.80, BC547-9 10p, BCY73-71 18p, BD131-2 45p, RCA 40673 £1.50, 40361-2 50p, 2N5496 50p etc.  
Op amps: CA3130e 99p, CA3140e 50p, CA3240e 92p, CA741 20p, TL071 50p, TL072 89p, TL074 85p. Audio: TBA 800 72p, TBA 810s 80p, TBA 820m 80p, UA723reg 52p, 78L05-15v 0.1a 35p, la 78 series 48p.  
Resistors: 1/4 watt 5%, 100m-100ohm ohm all 1p ea, 0.6W watt 5p all carb film. Metal film 1%. CF series ALL 5p. Electrolytics 0.33-100uF 8p, 10-25v radial axial 5p. Phone plugs 15p sockets (m) 20p.  
Terms: Cheques, P.O.s, cash, Access, Visa with order. To: F.J.P. Kits-Components, 63 Princess Street, Chadsmoor, Cannock, Staffs WS11 2JT, Dept ETI. Generous discounts for Education, Businesses on above plus test gear. Cata A4 & 50p refundable on 1st purchase. £5 or over. Postage £3 plus free, other 60p.

#### PROMs - EPROMs - PALS ANY PROGRAMMABLE IC SUPPLIED OR BLOWN

Typical prices (excluding VAT)  
(Data Entry P&P extra)  
2716 £4.20 ..... 2732 £3.85  
2764 £2.85 ..... 27128 £4.40  
**BIPOLAR PROMs from £1.35**  
e.g. 82S123, 18S030, 74S288  
**PALs, PLDs etc. from £3.26**  
e.g. 82S153, 16L8, EP310  
Full design and prototyping service.  
Any quantity programmed - SAE or phone for details.  
**P.L.S., 16 Central Road,  
Worcester Park, Surrey, KT4 8HZ.  
Phone: 01-330 6540**



**DISTRIBUTORS OF ELECTRONIC COMPONENTS**  
2 Elder Way, Langley Business Park, Slough, Berkshire SL3 6EP  
Telephone: 0753 49502 Fax: 0753 43812 Telex: 848132

#### CHANGE OF ADDRESS FROM LONDON OFFICES

We wish to advise you that BONEX LTD have moved to new and larger premises, and are now situated at the above address. We would take this opportunity of thanking you for your past support which has enabled us to achieve this expansion, and trust we may be of service to you in the future.

#### THE FOLLOWING PRODUCTS ARE AVAILABLE FROM BONEX

- I.F. Transformers
- Fixed Inductors
- Axial Inductors
- Chip Inductors
- High-Power Inductors
- Moulded Coils
- Variable Coils
- Quadrature Coils
- Ceramic Filters
- Helical Filters
- Linear Filters
- Pilot Tone Filters
- U.H.F. Filters
- Toroidal Rings
- Ferrite Cores/Beads
- Quartz Crystals
- Signal Diodes
- Varicap Diodes
- Zener Diodes
- Double Balanced Mixers
- Ni-Cads, Cables
- Silver/Enamelled Wires
- Full Range of Capacitors
- Variable R.F. Trimmers
- Full Range of Connectors
- BNC/PL259/TNC/F/Adapters
- Hardware, Boxes, Heatsinks
- CMOS, TTL, Linear I.C.'s
- Voltage Regulators
- Small Signal Transistors
- Audio/Power Transistors
- R.F. L. Power Transistors
- R.F. H. Power Transistors
- Field Effect Transistors
- Gas F.E.T.'s
- VMCS, MOSFETS, Darlingtons
- Switches, Test Equipment
- Expo Drills, Antex Irons
- Tools, Cutters, Reamers
- Drake Transformers
- Vero Board, Bread Boards



Ring **HEATHER WUST** on  
01-437 0699 for details of  
series discounts

**TRANSFORMERS**, one off specials, prototypes, your spec. N. E. Peart, 20 Langley Avenue, Grotton, Oldham OL4 5RA.

## T-systems Ltd

COMPUTER SYSTEMS AND COMPONENTS

Min. toggle switch, on/off .....	60p
Min. toggle switch, single pole, changeover .....	69p
Min. toggle switch, as above with centre off .....	75p
Min. toggle switch, double pole, changeover .....	80p
Min. toggle switch, as above with centre off .....	89p
Slide switch, double pole, changeover .....	25p
Slide switch, as above with centre off .....	29p
LED's, 3 or 5mm, red, green or amber/yellow .....	10p
Bulb, 12V, 3mm, red, green, amber or clear .....	22p
Resistors, 0.25 watt, 5% E12 series .....	2p
DIN plug or socket, 5, 6 or 7 pin .....	25p
25 way D plug, socket or shell .....	85p

\* Prices include VAT, add 25p P&P if under £2. Cheques payable to T-systems Ltd. \*  
Exclusively for ETI readers, 15% off all prices shown above for the August issue only.  
**61 High Street, Orpington, Kent BR6 0JF**  
\* ACCESS Card sales accepted on Tel: 0689 22196 \*

Components are the biggest selling item in ETI so why not advertise yours here?

- Series X Mixer Kits
- up to 1,000 inputs
- on-board mic input
- 6 auxiliaries
- versions for recording PA, radio, disco
- From £9.92



Send 18p for catalogue to:


K. Tek, P.O. Box 172A, Surbiton, Surrey KT6 6HN. Tel: 01-399 3990

**WOULD YOU BUY A CAR WITHOUT A TEST DRIVE? THEN WHY BUY A MIXER WITHOUT A TEST DRIVE?**

Thinking about a new project — from a small Mixer to a large studio complex — come and talk over ideas with the people who offer manufacturing and user experience at our new premises:

**Unit D, 318 High Road, Benfleet, Essex SS7 5HB**  
TO TAKE THAT TEST DRIVE —  
PHONE 0268-793381

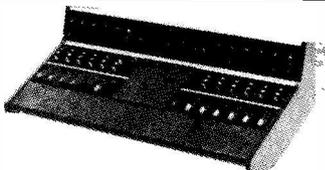(Weekend Committee visits welcome by prior arrangement)



**PARTRIDGE ELECTRONICS**

Head Office, 56 Fleet Road, Benfleet, Essex SS7 5JH  
Telephone 0268-793256

### TERMS & CONDITIONS

#### CLASSIFIED ADVERTISING TERMS & CONDITIONS

Our terms for new advertisers (semi-display and lineage) are strictly pro-forma payments until satisfactory reference can be taken up (excluding recognised advertising agencies Cheques and P.O.s should be crossed and made payable to ARGUS SPECIALIST PUBLICATIONS LTD and sent together with the advertisements to:

The Classified Dept.,  
No. 1 Golden Square,  
London W1R 3AB.

There are no reimbursements for cancellations. Advertisements arriving too late for a particular issue will be inserted in the following issue unless accompanied by instructions to the contrary. It is the responsibility of the advertiser to ensure that the first insertion of every series is published correctly, and corrections must be notified in time for the second insertion, otherwise the publishers will not accept liability or offer any reduction in charges.

All advertising sales are subject to Government Regulations concerning VAT. Advertisers are responsible for complying with the various legal requirements in force, e.g. The Trade Description Act, sex discrimination act & the business advertisements (disclosure) order 1977. Full Terms & Conditions of Advertising available on request.

### ALARMS

**NEIGHBOURHOOD WATCH BURGLAR ALARM D.I.Y. KIT**  
will offer a professional system at a DIY price

Ham mini beam 10, 15, 20 metres. Parts integrated circuits, transistors, diodes, valves, resistors, etc.

Service Manual and parts for *Spectrum and Amstrad*  
Send a 8" x 5" SAE for list.

**M.J. SEAWARD (Mail Order)**

Dept. (ET), St. Olafs Road, Stratton, Nr. Bude, Cornwall.  
Telephone: 0288 4892

## KITS



### I-TRON'S TOP SELLING KITS



**BUG-87** Matchbox sized surveillance transmitter - can be received by any FM/VHS radio .....£4.95  
**ROBO-VOX** Instantly transforms your voice into Dalek/Robot type - also amazing sound effects possible .....£11.95  
**ROBOT CIRCULAR** Unique radio controlled robot - can also be converted to control via computer.£18.95  
**EDU-SCOPE** Build your own oscilloscope with solid state display .....£39.99  
**EDU-SCOPE CASE KIT** .....£11.99  
**THERAMIN MUSIC GENERATOR** An electronic device based on an legendary mystical instrument.£12.75  
**RAD-X CONTROL** A complete ready built 2 output RADIO CONTROL SYSTEM .....£19.75  
**SUPER SOUND-FX MICROCOMPUTER** An easy to use and program single chip sound effects Micro completely self contained - Incredible sound routines possible with this unit.☆☆STAR VALUE☆☆ ..£9.95  
**SOUND-FX PRO CONSOLE CASE KIT** .....£3.99

Please add £0.95 per order for P&P. For FREE Datapack on all our Products/Kits send SAE.

Cheques/Po's payable to:-  
**IMAGINA-TRONICS**

Aberdeen House, The Street, Charlwood, Surrey RH6 0DS.

## COURSES

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on

REF: ETI/6/88

06267 79398



**NAME** \_\_\_\_\_  **Telecomms Tech C&G 271**  
 \_\_\_\_\_  **Radio Amateur Licence C&G**  
 \_\_\_\_\_  **Micro-processor Introduction to Television**

**Radio & Telecommunications Correspondence School, 12, Moor View Drive, Teignmouth, Devon. TQ14 9UN.**

### MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	Radio, Audio and TV Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds) -	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
<b>GCE</b> over 40 'O' and 'A' level subjects			<input type="checkbox"/>

Name \_\_\_\_\_  
 Address \_\_\_\_\_ P. Code \_\_\_\_\_  
**ICS** International Correspondence Schools, 312/314 High St., Sutton, Surrey SM1 1PR.  
 Tel: 01-643 9368 or 041-221 2926 (24 hrs.) Dept. EB558

## SPECIAL OFFERS

FREE MEMBERSHIP TO THE

### NATIONAL COMPONENT CLUB

For details and a free gift of components worth over £10 send only £1 p&p to:

Higher Ansford, Castle Cary, Somerset BA7 7JG

**STEREOAMPLIFIERS £13.95 INCLUSIVE!!** 60 + 60 watt, case, controls and sockets. Glass/PCB plus heatsinking and smoothing. Fr 20Hz to 30KHz -3dB. — K.I.A., 8 Cunliffe Road, Ilkley LS29 (SAE).

**ETI Classified now accepts**

**ACCESS & VISA**



Telephone Bookings  
**01-4370699**

or write to the  
 Classified Department  
 1 Golden Sq, W1R 3AB

### J.P.G. ELECTRONICS

Resistors 1/4w 5% carbon E12 1P 1% metal fm E243P  
 Resistor Pack 85 different E12 values plus ohm link, total content of resistor 1,000 .....£8.95  
 LED's Red/Green 3/5mm 6p each; Yellow 11p each  
 Cable Ties 75mm 1p ea. £5.95/1000; £49.50/10000  
 Power Transistors 1T1 35C, TIP36C, 100V, 25A TOP3  
 Plastic case .....£1.56 each  
 100db Piezo Buzzer ... £1.50; Standard Buzzer ... 80p  
 Solar Cells 0.45v 100mA .... £1.48; 700mA ... £3.50  
 Stepping motor 4 phase 12v 7.5 step 500ohms £8.95  
 SAA 1027 Stepping motor drive chip ..... £3.95  
 Miniature FM Transistor kits 100/108MHz high quality sound ideal for cordless microphones or guitars etc £7.48  
 Metal Latching XLR line plug ..... £1.35  
 Line Socket ..... £1.48  
 Ferric Chloride pack for mixing with 1/2 litre water £1.40  
 Flux cord solder 500g ..... reel £4.95  
 Automatic Squeeze action wire ..... stripper £3.45

#### SPECIAL OFFERS

Computer grade capacitors with screw terminals 58,000 uf 60v £4; 4,700 uf 63v £1.50; 38,000 uf 20v £1.95; 87,000 uf 10v £1.50.  
 Stereo LW/MW/FM tuner, pre-amp complete with volume/tone control and tuning scale Brand new in makers box £5.95; Faulty £1.95  
 Circuit diagram, description and setting up procedure for tuner assemble described above 50p  
 LCD display 16 digit 7x5 dots matrix ..... £2.50  
 Qwerty keyboard 58 key uncase good quality switches £5  
 CMOS TTL 74 HC 74F linear transistor kits, capacitors, resistors, tools etc, always in stock.  
 Please add 75p + p per order VAT inc.  
**J.P.G. ELECTRONICS, 276 Chatsworth Road, Chesterfield S40 2BH. Callers welcome. Access orders (0246) 211202**

**CASSETTE MOTORS** large and small 2 for £1.00. Mono and stereo cassette tape heads. 2 for £1.00. Microphone small for cass. tel. etc. 2 for £1.00. Telephone buzzers at £2.50 each. Please add 75p p&p no VAT. Access card accepted. Golden Orange Supplies, Brockhollands Road, Woodside, Bream, Lydney, Glos. Tel: 0594 563009.

## ELECTRONICS TECHNICIANS FULL-TIME TRAINING

(Full-time Courses Approved by the Business & Technician Education Council)

**2 Year BTEC National Diploma (OND) ELECTRONIC & COMMUNICATIONS ENGINEERING**  
 (Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

**1 Year BTEC National Certificate (ONC) ELECTRONIC ENGINEERING**  
 1—INFORMATION TECHNOLOGY (Electronics, Satellite TV, CD, Networks, Telecomms)  
 2—ELECTRONIC EQUIPMENT SERVICING (Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)  
 3—SOFTWARE ENGINEERING (Electronics, Assembler, BASIC, PASCAL, CAD/CAM)  
 4—COMPUTING TECHNOLOGY (Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

**10 Months BTEC Higher National Certificate (HNC) COMPUTING TECHNOLOGY & ROBOTICS**  
 (Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

These courses include a high percentage of college based practical work to enhance future employment prospects. No additional fees for overseas students. Shortened courses of from 3 to 6 months can be arranged for applicants with previous electronics knowledge.

Courses commence 12th/19th September and 2nd/9th January

FULL PROSPECTUS FROM

**LONDON ELECTRONICS COLLEGE (Dept EE)**  
 20 PENNYWERN ROAD, EARLS COURT,  
 LONDON SW5 9SU. Tel: 01-373 8721.

The next copy deadlines are

November issue — 22 August

December issue — 20 September

Ring or write today — 01-437 0699

## PCB'S

### QUALITY PRINTED CIRCUITS

- ★ Established 15 years ★
- ★ Single or double sided boards ★
- ★ Plated through hole boards ★
- ★ Personal service ★

**PAYNE ELECTROPRINT LTD**  
 Marcus Road, Dunkeswell  
 Nr Honiton, Devon EX14 0RA  
 Tel: Sales 040 489 646/664

**PRINTED CIRCUIT BOARDS** At very competitive rates: 4 pence per square centimetre (less for orders of 10 plus) 1 off; 100 offs. Enquiries: Watling Wires, 52 Watling Street, Nuneaton, Warwickshire, CV11 6JL. Telephone (0203) 382296.

**HAVE** your electronic ideas become a reality. Let Highland Itec develop and manufacture your circuits at a low cost for prototype and small production runs with comprehensive documentation which includes: Silk screen layouts, photo-artworks, pad-masters, solder-masks, bill of parts. Manufacture includes: Sizes up to 300 x 200mm single or double-sided. Finish: Roller-tinned and drilled. For more details Tel: (0463) 226505 or Fax (0463) 226506.

## WANTED

Turn your surplus transistors, IC's etc., into cash. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. Contact:

**COLES HARDING & CO.**  
 103 South Brink  
 Wisbech, Cambs.  
**ESTABLISHED OVER 10 YEARS**  
 Tel: 0945 584188  
 Fax Number: 0945 588844

- Kits
  - Courses
  - Surveillance
  - Switches
  - Plans
  - Designs
- Market your Expertise in ETI by calling 01-437 0699**

Advertise your Products and Services in ETI: The magazine with the largest market share

## Labcenter electronics PC-B £80

At last, an affordable PCB design tool for your Amstrad PC. Plotting service available. Send SAE for further details, or £2 for demo disk.

**Labcenter Electronics**  
 14 Marriner's Drive,  
 Bradford, BD9 4JT.  
 Tel: 0274 542868

## PCB Manufacturers Which to Choose See Page 15

## SURVEILLANCE

### ESKAN ELECTRONICS

LEADING MANUFACTURERS AND SUPPLIERS OF SURVEILLANCE AND SECURITY EQUIPMENT.

MINIATURE TRANSMITTERS, TELEPHONE MONITORING EQUIPMENT, AND MANY OTHERS.

Send stamped addressed envelope for your free catalogue to:

172 Caledonian Road,  
 London N1 0SG.

Telephone 01-278-1768

Trade Enquiries Welcome

## FOR SALE

**MOVEMENT DETECTOR.** Protect your videos, TVs, hi-fi's, etc. The ultimate protector, supplied in kit form including PCB at only £7.50. — Cheques/POs to: Rashid Adat, 20 High View Street, Bolton BL3 4DQ.

## SERVICES

**ADS REPAIR AMPLIFIERS!!!** 1 Regent Road, Ilkley LS29. 100 watt, slave chassis's, 240 volt, £23. +/-50v reg/psu, failsafe, Fr 20Hz to 30KHz +/-3dB, wood surround, j/sockets!!

## KITS

### VHF MICROTRANSMITTER KIT


Tunable 88-115 MHz, 500 metre range, sensitive electret microphone, size 25mm x 20mm.

#### SPECIAL OFFER

Complete kit ONLY £3.95 POST FREE  
 Access orders telephone 021-411 1821 (24 hours)  
 Cheques/POs to Quantek Electronics Ltd (Dept ETI),  
 45a Station Road, Northfield, Birmingham B31 3TE.
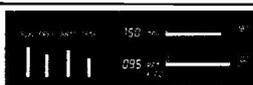
## PLANS AND DESIGNS

**ELECTRONIC PLANS,** laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue. SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.



Design and build your own electronic dashboard. Plans, instructions, circuits, parts lists £4.95 inc p&p

**BURLINGTON MOTOR CO. LTD.**  
 (G9) ARCH 39M, BATH PLACE,  
 LEAMINGTON SPA, CV3 3AQ.

## MISCELLANEOUS

**HEATHKIT U.K.** Spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. 0684 73127.

**GWM RADIO LTD,** 40/42 Portland Road, Worthing, Sussex BN11 1QN. Tel: (0903) 34897. Special purchase power supplies. Power-one international series type HB15 — 1.5A output 15 VDC at 1.5A, unused boxed with spec sheet, open frame psu. £15 inc p&p. Gould Econoflex type EX5-20/n, open frame — switch mode — output 5V at 20A, unused boxed with spec sheet, £30 inc p&p.

**S.H. COMPONENTS** presents 18 pages of very competitively priced semi-conductors, switches, optoelectronics, etc. plus sample, send 85p to: 17 Beeley Road, Grimsby, S. Humberside.

## SCOPES

### MENDASCOPE LTD

REPAIR & RECALIBRATE OSCILLOSCOPES

ALL MAKES ALL MODELS  
 NATIONWIDE COLLECTION & DELIVERY

FREE ESTIMATES

Phone 069-172-597

## BOOKS

### FULL WORKSHOP SERVICE MANUALS

Any Video Recorder — £10.00 + LSAE.  
 Any Colour/Mono TV, Any Audio, Music System — £5.00 + LSAE Amateur Radio, Test, Vintage, Military etc.  
 State Make/Model/Type with order.  
 FREE Catalogue Unique Repair and Data Guides with all orders.

**MAURITRON TECHNICAL SERVICES** (ETI), 8 Cherry Tree Road, Chinnor, Oxfordshire, OX9 4QY.



Advertise your Books and Publications in ETI today  
 01-437 0699

## SWITCHES

**VOICE/SOUND ACTIVATED SWITCHES** easy to follow diagrams and uses only £1.00. Components and P.C.B's available: **Herrington, 63 Home Farm Rd, Hanwell, London W7 1NL.**

## GOVERNMENT SURPLUS EQUIPMENT

### ANCHOR SURPLUS LTD.

The Cattlemarket, Nottingham NG2 3GY Tel 0602 864902  
 The UK's Largest Genuine Government Surplus Dealer


Always a large stock of Radio, Test, Service and General Equipment in stock. Pye, Racal, Marconi, Tek Redifon, Plessey, Mullard.



**Special:** Eddystone 730/4 1-30MHz RX £75 - £110. Pye PF2 LB FM from £25.  
**Phone Rob (G4ROB) For Details.**

Mail Order, Access/Visa Welcome



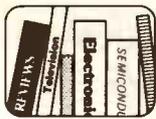

**Video Techniques (2nd ed) by Gordon White. £30. Heinemann Professional Publishing, Halley Court, Jordan Hill OX2 8EJ.**

With a title like *Video Techniques*, you could be forgiven for thinking that this was yet another book of hints for the amateur videographer — and an expensive one at £30 a throw. But you'd be wrong.

A closer look reveals a well thought-out guide to the history of video and its transformation since it all started (over 50 years ago) with Baird and Scheonberg.

The author, Gordon White, has written the book to help the young engineer with only the new technical knowledge to understand the reason why the system operates as it does' and he shows how today's methods of operation and design have been influenced by the experiences of yesterday.

Each chapter covers a wide area of subject. For example, *The Television Waveform* starts with its basic principles, the first scanning method (amazingly patented by Nipkow in 1884!) through its development by the Baird company in the early thirties until the acceptance of the EMI system by the Beeb in 1937.

It deals with present day standards and conversion systems right up to the latest enhanced and extended definition television. There are plenty of easy-to-understand circuits and block schematics but White avoids technical explanations 'unless it is to illustrate a principle, *Video Techniques* does not describe circuitry or individual pieces of equipment as these rapidly change'.



He always reminds you of the origins of each subject, be it cameras, recording techniques, post production, studio design, transmission and reception methods and takes you through all the stages of research and development, finally giving his considered view of the future.

Even the enthusiastic semi-technical amateur who might not understand all the circuits and schematics will find plenty to interest and inform in the easy-to-read pages.

This second edition brings us into the world of digital television and White points out how the very nature of broadcasting is changing as the new technology gives the producer and viewer more and more sophisticated facilities, making the point that the engineer is once again having to adjust and re-educate himself.

This book will certainly help to make that task easier and, at the same time, make him aware of those early pioneers whose achievements still influence today's *Video Techniques*.

**James Talbot**

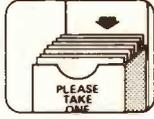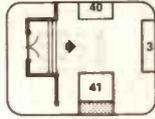

June of this year saw the annual exhibition for all those people in the professional audio market at London's Olympia 2, organised for the 21st time by the Association of Professional Recording Studios — the APRS. This year 174 exhibitors showed some 6000 visitors to the show exactly what all the best equipped studios will be sporting during the next year.

The show saw some interesting developments which, although only available to those people whose annual income looks like a telephone number at present, will no doubt filter down to the rest of us in the foreseeable future.

**Let's Get Digital**

Yes folks, 'digital' is this year's buzzword. Just about everything at the show was in some way digital or at least 'equipped for the digital age' — whatever that means. Most directly relevant was the launch of several DAT recorders from several of the major manufacturers, most notably Sony and Casio with their portable DAT models.

Not surprisingly the Casio model has set out to be the cheapest on the market retailing for about £800. However much of the broadcasting industry has or are about to opt for Sony's PCM-2500 which is considered to be more 'in the field reporter' proof.

At the other end of the spectrum comes the Sony PRODAT 1 and 2 which sport electronically balanced analogue inputs as well as both domestic and professional EBU digital inputs.



To compliment this wave of digital mastering we find ourselves with digital replacements for just about everything that you would normally find in a studio. It all stems from the fact that the end result is only as good as the weakest link in the audio chain — something the industry is taking great delight in telling us as it means they can sell virtually complete new set-ups to existing studio owners.

Many of the mixing desk manufacturers have taken the easy option of taking last year's model, cleaning up the circuitry a bit and calling them 'digital ready'. However, an equal number of companies have actually made important steps forward in audio technology.

Yamaha's DMP-7 eight-into-two digital mixer is not only totally digital

from input to output stage but has four effects processors built-in and motorised faders. All this and MIDI control to allow automated mixdown as well. Watching the unit in action is quite amazing; seeing the faders reposition themselves within the blink of an eye certainly made me feel like robbing a bank in order to get the £4000 needed to buy it.

To make life even easier Yamaha has teamed up with Steinberg (best known for their sequencer software) to produce an on-screen editor package which allows you to save and load various mixer settings via an Atari ST. Furthermore you have full control over all parameters at the click of a mouse. In a similar vein was the



Matchless Mixing desk from TAC. This is a conventional desk with a MIDI interface on it allowing software such as the JMS (Jellinghaus Music System) C-Mix package on the ST to change volume level and EQ settings via MIDI allowing synchronisation between a sequencer and the recording console.

Harman Audio is excited about the launch of its new desk. The whole exercise comes under the title of the REMIS project — (rather like a Fredrick Forsythe novel). It is a British designed, SMPTE automation assisted mixing console which is hoped to blow away the competition in the £10-25,000 price bracket.

**Be Direct**

Another area of activity is Direct to Disk recording — the process of multitrack recording directly on to a hard disk drive. This allows digital sound quality, precise yet non-destructive editing facilities and as many as 200 individual tracks, depending on the size of the song and the memory. In effect these are incredibly large samplers with much more control.

New England Digital was first to produce such a system called the Synclavier which has built up quite a reputation for itself not to mention a large user base of musicians such as Trevor Horn, Paul Hardcastle and Frank Zappa.

However, there is some competition from Digital Audio Research with the Soundstation II, selling itself as a total music production console.

If we may I'd like to get back to the analogue world of tape (remember

tape?). In particular Tascam and TOA, who are both launching new 8-track recorders. They've managed to squeeze eight tracks onto a standard audio cassette and I have to admit that it sounds quite respectable.

**Little Boxes**

It wasn't all expensive large boxes at the show. There were many expensive small things as well! The new Rebis Multigate gives you up to four different noise gate treatments at any one time. From Citronic we have the SPX7-21 15-band graphic equaliser, the MPX9-11 background music mixer and zoning unit and the SPX5-41 active crossover each costing between £340 and £450.

Sound Technology had nothing really new on their stand but as distributor of Alesis effect units in this country an insider reliably informed me of a new MIDlverb which will allow four different effects running at the same time. The unit will be called the Quadraverb.

**Mr Speaker**

Loudspeaker manufacturers were also in evidence. HH Electronics had the TA series of PA monitors complete with the C1 system controller. From Tannoy we have a sneak preview of the new AV Pro series designed for control room monitoring. These should be available by October.

With such chunky speakers coming onto the scene you may well be after a sound analyser and it just so happens that Electromusic has just released a nice one christened the Scanalyser which thanks to its unique sweep filter can display detail that the competition can't manage.

**Bits And Pieces**


Sifam Ltd were showing off their range of audio meters, knobs and faders



whilst Ampex displayed various formats of magnetic tape including the new Ampex 478 featuring better than average wind characteristics, improved low print performance and a new high speed backcoating. Not only that but it sounded good as well! Klotz had all 58 varieties of cable on show in addition to the Neutrik connectors as well as the Mikro and Nano PA speaker ranges which they also distribute.

Obviously the current wave of digital equipment on show points the way towards how we will be composing and recording in the future. All we have to do now is wait.

**Darrin Williamson**

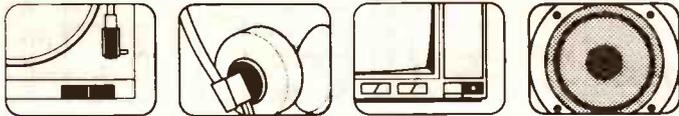

Recently the *New Scientist* published an article concerning the much reduced longevity of certain compact discs, a story seized upon and later sensationalised by the good old non-technical popular press (one paper even claimed an 'exclusive!') Embellishments aside, the true nature and potential seriousness of the problem may well have been blown out of proportion.

To some extent the originators of the CD format have laid themselves open to such a broadside by virtue of their initial claims of 'perfect sound forever'.

Nothing lasts forever, especially if it is a plastic/aluminium sandwich destined for a considerable amount of abuse.

Bringing things up to date this latest scare concerning the life-expectancy of CD's is generally attributed to the specialist Nimbus and Mobile Fidelity pressing plants. Both companies have highlighted the alarmingly high failure rate of certain discs derived from some other (competing) plants.

Long-term archiving experiments have indicated that 95% of all conventional discs offer a stable and acceptably low error-rate over a three year period, while some 5% of discs show an increase in the digital error rate of up to 200 times after just two years of careful storage.

Some discs have apparently deteriorated so rapidly as to be rendered useless after just a few months!

Current evidence suggests a gradual oxidation of the aluminium reflector layer is responsible. The gradual build up of fibrous residues conceal the minute  $0.4 \times 0.1 \mu\text{m}$  'pits'. However, this aluminium reflector layer is vapour deposited onto the encoded portion of the CD's polycarbonate window, the rear surface being quickly sealed by a thin layer of lacquer.

#### Air

Air should therefore be excluded from the inside of the disc, severely hampering any oxidation mechanisms. However, a degree of uncertainty is thrown into the equation by the actual thickness and durability of the lacquer itself, especially when some pressing-plants are employing inappropriate solvent-based inks to decorate this thin layer.

Considering this rear surface may be less than  $30 \mu\text{m}$  thick, many halogenated solvents would easily penetrate the lacquer before fully volatilising from the ink itself. Even if this only occurred on the microscopic level, the aluminium surface would still be sufficiently exposed for a gradual, parasitic oxidation.

This leads onto another variable: the actual thickness of the aluminium reflector itself. To all intents and purposes the amount of aluminium used is determined by the required reflectivity of the finished system but a quick examination of different discs reveals that this 'requirement' has been loosely interpreted. In fact the layer inside some discs is so thin as to be completely transparent, while other discs remain totally opaque when held up to the light.

#### Pin Holes

This situation is quite removed from the obvious loss of information caused by 'pin-holes'. It seems to me the thinner the layer the more readily will it be consumed by oxidation. This is particularly important if oxidation is actually occurring from the rear surface, the digitally encoded information being stored on the front surface of the aluminium.

Adding fuel to the long-term archiving tests, other researchers have employed short-term accelerated aging techniques, extrapolating the results to predict failure in 'real' time.

This generally involves a periodic cycling of both temperature and humidity, stressing both the chemical and physical stability of the materials to their limits. While this may be a trifle OTT and perhaps unrepresentative of domestic abuse, the results concerning the premature demise of some discs is consistent. These methods have provided an excellent proving ground for the protagonists of gold and platinum-layer discs.


#### Physics & Chemistry

It would appear reasonable to assume that some pressing plants have not examined the physics and chemistry of CD manufacture in sufficient depth, their own poor products reflecting badly on the remainder of the industry. I have no doubt that names will be named in the very near future!

Meanwhile, certain uncharitable individuals have suggested that the manufacturers of such noble-metal discs have a vested interest in disparaging the conventional aluminium varieties. However, gold-coated CD's cost two to three times the amount of ordinary discs and currently offer only a very limited repertoire. At £11 a throw the silver-coloured discs are a bitter pill to swallow. I can hardly envisage £20-£30 equivalents selling like hot cakes.

Unfortunately then, this kind of ill-considered scare-mongering may end up back-firing on the very pressing plants that 'leaked' the information in the first place.

Paul Miller

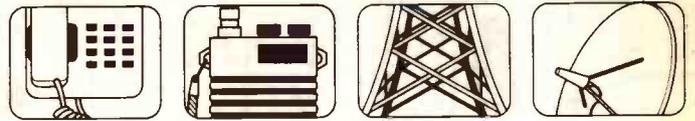

Get Smart! Yeh. I used to watch it, too! But the Smart I want to talk about here isn't the TV prog of yesteryear. It's the little piece of plastic which we'll all be carrying around in our wallets before too long, which looks set to replace existing credit cards and give us a few extra features as well.

Smartcards, on the face of it, are just like credit cards but embedded into them is semiconductor memory or processing power, which enables them to hold information. If the holder of a Smartcard wishes to buy something, the shopkeeper now doesn't need to telephone for authorisation because all relevant financial details are held digitally on the card. Merely reading the information with the use of a cheap card reader is sufficient to show that funds are available and the transaction can go ahead.

But purchases aren't the only use to which Smartcards can be put. Medical details, car log book, drivers' license, library ticket, etc ad infinitum can all be held and manipulated on the smartcard. For example, in South Wales a DHSS-financed experiment is underway to investigate the potential of smartcards in medicine-management. Doctors' patients are issued with smartcards holding prescription history, allowing patients to purchase drugs and medicines at chemists. The smartcard used in the experiment is manufactured in the UK by Cumana and holds up to 128K of information.

The amount of information which can be stored depends largely on technology, with 256K smartcards being common but the Japanese are in on the act, with current smartcards of 1Mb storage capabilities. It seems the sky's the limit.

So what are the technical problems in smartcards? The major one appears to be the method of getting all the information on in the first place and off when required. Such large amounts of data into such a small card require highly accurate read/write methods — the most common being magnetic, optical and, most recently, radio transceivers (used by GEC).

The introduction of all these varieties of smartcards will mean we will need more wallet space (already bulging) but if service providers get their technical heads together to define a single standard, it could be that all current plastic cards can be incorporated into a single smartcard.

What about cost? Smartcards cost around £3 to produce at present, while plastic cards with simple magnetic stripe information cost only around 10p. Greater numbers of smartcards will cause the price to tumble. Anyway, the cost is but a small



price to pay for the added security against card fraud. Estimates have already been made that the use of smartcards will prevent at least 60% of current card frauds — which means savings of many £m over existing plastic cards.

#### Defining A Standard





Until recently, it has been generally assumed that when the medium-powered television satellite Astra starts to transmit it will do so using the MAC (multiplexed analogue component) standard. SES, the Luxembourg-based organisation launching and running the Astra satellite have always said the Astra is transparent to television standards — whatever standard the programme providers beam-up will be beamed back down again to the users.

It has looked likely that the D2-MAC standard would be common (more by default than design) whereas the future British Satellite Broadcasting DBS satellite is planned to transmit according to the D-MAC standard. Use of either of these standards requires that users will need either (1) a new television capable of receiving and displaying the high quality MAC pictures or (2) a decoder to convert the received MAC signals to the PAL format common in terrestrial television receivers throughout most of Europe.

However, Rupert Murdoch's recent decision to use four of Astra's 16 transponders to broadcast his Sky Television channels to the PAL format has upset the apple-cart somewhat and has some far-reaching effects to the industry.

First, being on the PAL standard transmissions can be received by users owning existing televisions, for the price of an aerial (the infamous dish — around 60cm in diameter) and a simple receiver. Such receivers have been around for a few years now, in the small but growing satellite TV market, merely receiving the microwave transmissions from the satellite and converting them into UHF PAL signals directly receivable by an existing television. Current satellite TV receivers start at around £600, and go

## ONCE OVER

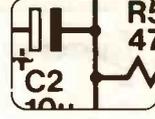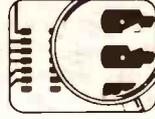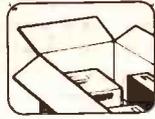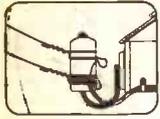

up to around £2000. The high cost is partly because they use a much larger dish (1-2m) but mainly because they sell in low quantities.

The idea with Astra and following satellites is that the smaller dishes and higher volume production will make the receivers much cheaper and so more accessible by Joe Public. To this end Alan Sugar's Amstrad has indicated a commitment to produce £200 systems, enabling us all to receive satellite transmissions extremely cheaply. In effect, Rupert Murdoch and Alan Sugar will tap a market which hitherto appears to have gone unnoticed.

Alan Sugar's part in all this is worthy of note. Amstrad, as readers will know, produces cheap and cheerful hi-fi, television, video cassette recorders and so on in large quantities. Alan Sugar was, until recently, a founder of BSB and the DBS venture. As I noted in this column when he pulled out of the consortium (September 1987) his going indicated that he did not wish to be part of an organisation producing low-to-medium volume equipment, at a high price.

In retrospect, it would appear that Alan Sugar was aware of Rupert Murdoch's intention to create four channels of satellite broadcast television using the PAL standard, knowing that high-volume, low-priced equipment is his forte.

Second, the Sky/Amstrad combination will mean that other potential programme providers will probably consider transmitting in PAL too. I am willing to put my money on this. Lead times in writing, editing and production of ETI will mean that readers may already have heard of other such channels on Astra which haven't yet got off the ground as I pen this.

Effectively, in a single, seemingly innocuous move, Murdoch and Sugar must have delayed European DBS plans, will have left DBS providers with a product they may not be able to sell and may have scuppered DBS altogether in its present form.

If Astra launches successfully in November as planned, for £200 Mr and Mrs Public could be sitting down after their Christmas lunch to around an extra 20 television channels (16 on Astra and a handful more on existing satellites) on their existing TV set. For Joe, his wife and the kids, the question will not have been whether to wait and pay more for three channels of high quality pictures and stereo sound (which DBS/MAC will give) but will have been the more poignant question, why wait at all?

Keith Brindley

Chipkits, produced by the Polytechnic of Wales, are a series of modules intended to assist training in electronics. Three main modules are currently available: the Transistor Module, the Op-amp Module, and the Logic Module. In addition, an I/O Module of two PCBs with parts ready mounted, (including a loudspeaker, a motor, a microphone and so on) is also available for all three. Each main module consists of a printed circuit board, components and an instruction book and each kit is supplied in a smart plastic briefcase-style carton.

The printed circuit boards are fitted with sockets suitable for the type of components used in each module. The sockets, some test pins and screw connectors for power, inputs and outputs are interconnected to permit circuits to be built up without being so interconnected as to constrain the type of circuit.

Legend printing on the top face of the boards shows what is connected to where and labels some of the components, for example 'op-amp 1'. The bottom faces of the boards are fitted with rubber feet so that they do not scratch the table top.

The instruction books provide some basic information such as resistor colour codes, component identification information and so on. They explain how to bend a component lead and insert it in the socket. There is also some background information — for example, the op-amps book shows the internal equivalent circuit of a 741. Most of each book, however, is devoted to experiments designated Lab 1, Lab 2 and so on.

A fair amount of information on each experiment is provided for the student but these are definitely not

self-teaching kits for the beginner. The layout of the course clearly expects an experienced tutor to be present, to explain the results of the experiments and to teach the student how to operate any test equipment required. For each experiment there are tables to fill in with results, questions to answer and diagrammatic oscilloscope screens for copying the observed waveforms. The manual which comes with each kit is therefore the basis of the student's lab notebook, rather than a textbook.

The experiments at the beginning of each book are extremely basic and suitable for the beginner who may have some background in physics but has never built a circuit in his or her life. The first experiment in the transistor module is to connect a diode and a resistor in series, with a signal generator across the two ends and measure the resulting waveforms on an oscilloscope. The experiment goes on to show what happens when capacitors of various values are added to this classic half wave rectifier circuit. Other experiments include a common emitter AC coupled amplifier stage, astable and bistable flip-flops, etc.

In the op-amps module I was slightly surprised to see that the initial experiments were based on the use of an op-amp as a comparator rather than as a linear amplifier. This makes some sense in that an op-amp without external components to provide negative feedback has such a high gain that it works as a comparator for most practical purposes but I think I would have started with linear circuits.

Most of the circuits shown are not practical in the sense that, although they will work in the context of an experiment, nobody would actually

design with them in that form. For example, a push-pull audio output stage is shown using two transistors with their bases and emitters connected together to boost the current output of an op-amp. A circuit for serious use would normally include biasing for the transistors to reduce crossover distortion, and emitter resistors to improve temperature stability.

The logic module first covers the basic combinational logic functions, NAND, NOR etc. It proceeds via the 555 timer (which I had always classified as an analogue IC) to sequential logic circuits, using a 555 monostable circuit to provide a clean clock pulse from an ordinary push button switch.

All the logic ICs used are 74LS series TTL. This type of logic is going out of fashion but is probably a good choice for the training modules because it is hardy and cheap to replace.

Correct wiring of the experiments is aided by the way the connections are arranged, with the IC connections brought out to large rectangular arrangements of pins over which cardboard push-out pin diagrams can be laid.

The general presentation of the kits is good. The PCBs are coated with solder resist on both sides and the top face is printed with connection information. Closer inspection shows that the quality of etching is poor, many of the tracks having ragged edges. Some of the soldered joints would not pass normal industrial inspection, either.


It is not likely, though, that these points would affect the utility of the kits in most cases. In a few cases I can envisage a unit having a short between two tracks or a non-functional soldered joint but for the most part the effect is cosmetic. The boards and sockets on the whole are spacious, visually clear and much easier to use than the normal type of push-in breadboard.

The level at which the subject is covered is probably most suitable for school sixth forms or first-year higher education students and their equivalents. The flexibly structured PCB and step-by-step workbooks impose a certain clarity on the subject in hand and, as my guinea-pig pointed out to me, structured courses like this are useful for keeping the instructor to the point as well as the students.



Transistor Module £32.41, Op-Amp module £33.68, Logic Module £37.39, IO kit £26.23, all plus VAT and carriage. Available from: The Electronics Centre, The Polytechnic of Wales, Pontypridd, Mid Glamorgan, CF37 1DL.

Andrew Armstrong



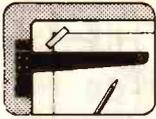

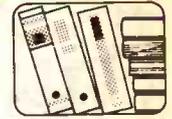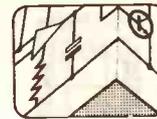This column is a service to readers to provide electronic designs to order. Many a project never gets further than the drawing board because of difficulties with one small part. If you are stuck for a circuit or a technique, let the ETI expert help you out. Send your requirements, with as much detail as possible, to ETI Blueprint, 1 Golden Square, W1R 3AB.



This month's Blueprint request comes from Mark Cox of Derby. I would like a circuit to provide battery backup to a 62256 (256K) static RAM, using a 3V6 100mAH NiCd. The battery should recharge but not overcharge from the 5V power supply when this is present. How long would the battery take to discharge when providing the 40µA standby current of the RAM and how long would it take to recharge!

You haven't given me enough details about your application to design a specific solution — for example I don't know whether there is any circuitry in the main unit which could write data to the RAM without the operation of a manual toggle switch. For this reason and to make the answer of wider relevance, I have provided a general solution to the problem. You can leave out any parts which you do not need.

For general reference the first diagram shows the internal arrangement of the 62256 RAM. When active, this chip is rated to draw a maximum of 15mA.

The chip also has two standby modes. When the chip select line is at the logic 1 minimum level (2.2V) a maximum of 3mA is drawn. If the chip select is within 200mV of the positive supply voltage, the standard version of the chip is rated to draw typically 40µA at 5V. No maximum is given but one might estimate a figure of 100µA as a working maximum. A low power version of the chip is also available. This is rated to draw 2µA typically at 5V.

The standard device is not rated for battery backup operation, though it is likely that many standard devices will work in this mode. The low power device is rated for memory retention down to a supply voltage of 2V.

### Battery Consumption

If you were to use a standard power chip in memory backup mode and if it drew the typical 40µA over the battery voltage range then the battery life could be calculated. It is not usually possible to recover all the rated capacity from a NiCd partly because it will self discharge gradually so not all the current goes to the memory chip. If we assume that 80% can be recovered then the sum is  $80\text{mAH}/40\mu\text{A} = 2000$  hours. To allow a further safety margin, because even if a standard chip works on memory backup it may not work down to such a low voltage as the low power type, you could assume the battery will last for at least two months.

This calculation is pessimistic in its assumptions. If you are particularly lucky the battery could last for a year.

Using the low power chip, the current consumption is so low as to render the self discharge of the battery the main factor in determining the life. One particular type of memory backup battery is rated at 50% charge retention after 12 months. Normally the self discharge slows as the battery becomes discharged so it is likely that a battery life of two years would be possible using the low powered chip.

Most memory backup batteries are rated at 10mA charge for cyclic applications, 1mA trickle charge rate. While a charged battery is on charge, its voltage rises above the nominal voltage, so in the circuit shown in the second figure, the charge rate will be above 1mA for a deeply discharged battery but under 1mA when the battery is well charged. The battery will be fairly well charged after three days with power applied and fully charged after five days.

### The Circuit

The circuit diagram shows a typical power supply, with a voltage detector circuit on the input to the voltage regulator. This is to detect when the voltage regulator has barely enough input voltage to function correctly and to provide a signal to deselect the RAM to prevent spurious data writes from occurring if another chip in the

circuit goes berserk as the power fails.

The comparator compares the voltage on the storage capacitor with the reference voltage. The ratio of the potting down resistors gives switching levels of 7V to switch the PSU OK signal off and 8.5V to switch it back on again. The hysteresis between these switching levels is intended to take account of ripple on the capacitor. If more than about 1.25V ripple is expected then the hysteresis should be increased.

Continuing the story of the PSU OK signal, the chip select ( $\overline{\text{CS}}$ ) is gated together with PSU OK by the two NOR gates shown. The RAM is only selected if the PSU OK signal and the externally generated  $\overline{\text{CS}}$  signal both agree that it should be. The  $\overline{\text{CS}}$  signal to the RAM is controlled by a transistor so that, when the transistor is off the  $\overline{\text{CS}}$  pin will be held at the supply voltage, thus minimising standby power consumption.



If the NOR gate IC1 gives an invalid output when the power supply fails, a spurious write will still be impossible. The values of R8 and R9 ensure that Q1 cannot be switched on when the power supply falls below approximately 3V.

If the PSU OK signal is not needed and if the externally  $\overline{\text{CS}}$  signal can be changed to logic 1 to select instead of logic 0 then IC1 can be omitted.

The power supply to the RAM is via a Schottky diode which prevents the battery supply from powering other circuitry while giving minimum voltage drop when the RAM draws power from the main supply. The charging rate of the battery is limited to approximately 1mA by R10, while the RAM is powered via D2. At a current drain of 40µA the voltage drop of a 1k2 resistor is only 50mV so D2 could be omitted with little effect but it is included to take account of any brief pulse of current which may occur at switch on or off.

R11 is included to limit the short circuit current. This is not strictly necessary but it may prevent damage in case a track is accidentally short circuited in the course of experimentation.


**Andrew Armstrong**

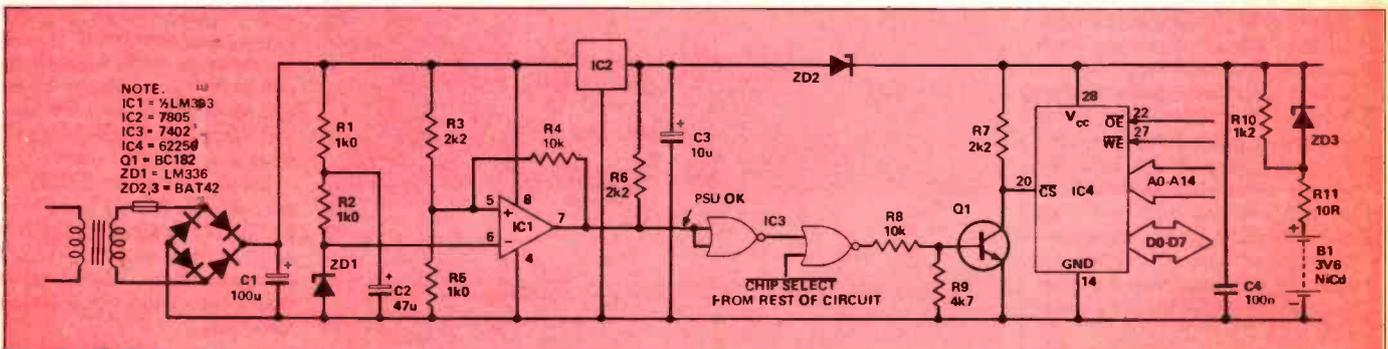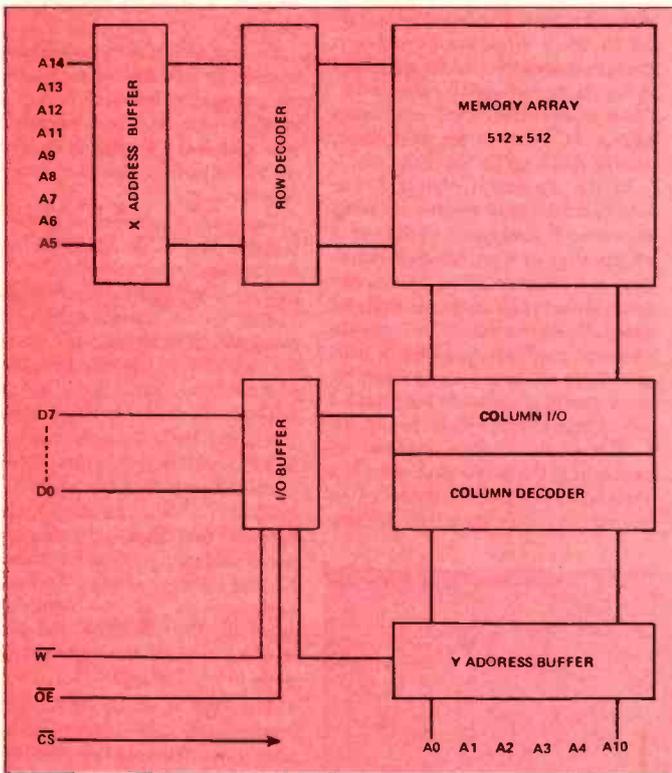

# ILP TRANSFORMERS FROM JAYTEE
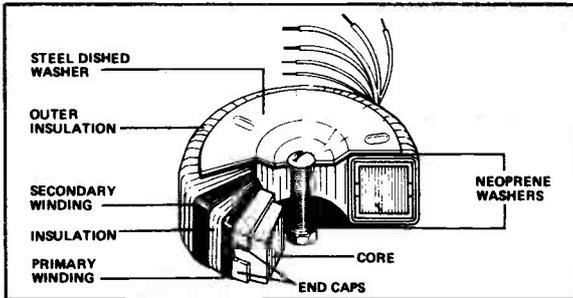
## The UK Distributor for the Standard Toroidal Transformers

- \* 106 types available from stock
- \* Sizes from 15VA to 625VA



Write or phone for free Data Pack

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL  
Telephone: (0227) 375254

# ILP AMPLIFIERS FROM JAYTEE

## The UK Distributor for the complete ILP Audio Range

- \* Bipolar Modules – 15 watts to 180 watts
- \* Mosfet Modules – 60 watts to 180 watts
- \* Power Booster – 15 watts (for 12v dc supply)
- \* Power Supplies
- \* Pre-amplifier and Mixer Modules
- \* 100 volt Line Transformers
- \* Loudspeakers – 12" 350 watt Bass and 200 watt Wideband Bass
- \* Power Slave Amplifiers

Write or phone for free Data Pack

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL  
Telephone: (0227) 375254

## Electronics - Build and Learn 2nd Edition · RA Penfold

June 1988 · 120 pages · 216 × 138 mm  
72 line dwgs · 18 photos  
ISBN: 1 870775 15 5 · £5.95

- \* For enthusiasts/students starting in electronics \*
- \* Explains principles involved \*
- \* Tests and experiments to aid understanding \*
- \* Practical guidance for construction \*
- \* Lists all components required \*

Electronics is a practical subject, but a certain amount of theoretical knowledge is necessary if you are to become proficient in it. This book combines theory and practice so that you can 'learn by doing'.

Gives full constructional details of a circuit demonstrator unit used to introduce common electronic components — resistors, capacitors, transformers, diodes, transistors, thyristors, fets and op amps — and describes how these components are built up into useful circuits — oscillators, multivibrators, bistables and logic circuits.

An essential book for the beginner in electronics!

**Contents:** Circuit demonstrator unit; Passive components; Semiconductor devices; Operational amplifiers; Oscillator and radio circuits; Pulse and logic circuits; Index.

Send cheque or postal order for £6.45 (£5.95 + 50p P&P), made payable to PC Publishing, to: PC Publishing, 139-141 High Street, Edenbridge, Kent TN8 5AX (tel 0732 866896).

## 19" RACK MOUNTING EQUIPMENT CASES

This range of 19" rack equipment cases have been designed with economy and versatility as their objective. These cases are supplied as a flat pack kit with assembly instructions. The ★ NEW IMPROVED DESIGN ★ now features a black powder coat 16SWG (1.5mm) steel front panel with the rear box constructed from .9mm PVC coated steel.

All units are 10" (254mm) deep and are available in the following popular sizes:-

TYPE	HEIGHT	PRICE
U1	1" (44mm)	21.85
U2	3" (88mm)	23.00
U3	5" (133mm)	25.30
U4	7" (178mm)	27.60
M6U Sloped mixer case		28.75

DELIVERY INCLUDED

All prices INCLUDE VAT


Blanking Panels, Racking Consoles and Rack Cabinets are also available.

Please send S.A.E. for details.

★ TRADE ENQUIRIES WELCOME ★

TEL: 0275 823983 FOR ACCESS/VISA SALES  
OR CHEQUE WITH ORDER TO:-

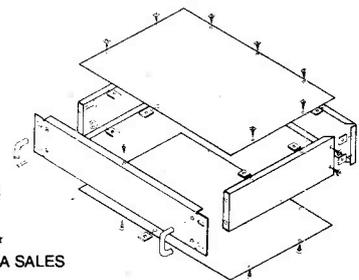RACKZ PRODUCTS PO BOX NO. 1402, MANGOTSFIELD, BRISTOL  
ENGLAND. BS17 3RY



## BINDERS

**FOR YOUR VALUABLE COLLECTION OF ELECTRONICS TODAY INTERNATIONAL MAGAZINES**

• SMART • EASY TO USE • TOP QUALITY

To ASP Readers Services, PO Box 35, Wolsey House, Wolsey Road, Hemel Hempstead, Herts HP2 4SS (0442-41221)

£5.95  
inc.  
P&P

Please supply .. Electronics Today International Binders £5.95 inc. P&P

Total £ ..... (Please make cheques payable to ASP Ltd.)

Years Required — 198.....198.....198.....198.....

Name .....

Address .....

Please allow 21 days for delivery

## ADVERTISERS INDEX

ASP READERS SERVICES	17
BENCHMARK BOOKS	66
BK ELECTRONICS	IFC
CRICKLEWOOD ELECTRONICS	22
DISPLAY ELECTRONICS	IBC
ELECTRONICS SUCCESS	26
EMINENCE AUDIO	65
GREENBANK ELECTRONICS	66
HART ELECTRONICS	66
HENRY'S AUDIO ELECTRONICS	31
JAYTEE ELECTRONICS	65
MAPLIN ELECTRONICS	OBC
MATRIX SYSTEMS	13
NATIONAL COLLEGE OF TECHNOLOGY	17
OMNI ELECTRONICS	13
PC PUBLISHING	65
RAUNCH PRECISION ENGINEERING	26
SAGE AUDIO	31
SLEE ELECTRO PRODUCTS	44
SPECIALIST SEMICON DEVICES	10
STEWARTS OF READING	31
SUMA DESIGNS	22
TJA DEVELOPMENT	44
TK ELECTRONICS	3
STAN WILLETS	44
WILMSLOW AUDIO	51
ZENITH ELECTRONICS	51

## NEW BOOKS ON ELECTRONIC DESIGN

### KEY TECHNIQUES FOR CIRCUIT DESIGN

G C LOVEDAY

Deals with designing electronic circuits from scratch covering concepts such as target specifications, component selection (passives, discretes and ICs), the design cycle, derating etc. Numerous design examples are given and several reader exercises all with fully worked solutions. The approach is essentially non-mathematical.

ISBN 1 871047 00 5 Pbk 128pp Price £6.95 + 60p p&p

### DESIGNING DC POWER SUPPLIES

G C LOVEDAY

Covers all aspects of the design of regulated power units, using discretes, IC regulators and switched units. It also covers protection circuits and reference supplies. Many design examples and exercises all with fully worked solutions are given.

ISBN 1 871047 01 3 Pbk 136pp Price £6.95 + 60p p&p


Order direct from:

**THE BENCHMARK BOOK COMPANY**

59 Waylands, Swanley, Kent BR8 8TN

Interak 1

## BUILD YOUR OWN COMPUTER

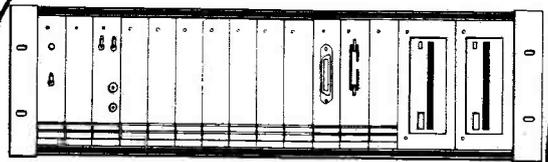

INTERAK can be commenced with the minimum of outlay. Bare boards from £10.95; beg borrow or steal the components, or buy from us - all parts available separately. No special or custom chips (ie PALS, ULAs, ASICs etc) used - no secrets.

Go as fast or as slowly as your funds and enthusiasm permit.

Made for those who must know what goes inside. Full circuit diagrams and descriptions are provided. And honestly, can you really use a computer effectively if you don't know what's inside and nobody will tell you?

Solid engineering construction - something to be proud of. 19" 3U rack mounting, plus in circuit boards and modular construction keeps obsolescence at bay.

Flourishing Independent Users Group, and newsletter. Hundreds of programmes on disk at little or no cost from the Users Group. Program in machine code (Assembler), Basic, "C", Forth, etc. Database, Word Processing, Scientific applications.

Cassette tape operation or disk (up to 4 drives, 1 Megabyte 3.5" available from us, but you can add 3", 5.25", 8" if you want). Disk operating system CP/M Plus.

64K RAM, Z80 based at present with potential for expansion to a 16 Megabytes address space and Zilog's latest Z80280 in the future. Needs no specialised knowledge to construct, and we will happily get you out of a jam if you get into one.

Availability of personal and individual after sales service, impossible to obtain from large companies, who are only after your money. Security of supply - from Greenbank Electronics, established in 1970.

**Greenbank**


For more details write or phone us:

**Greenbank Electronics, Dept. (T9E), 460 New Chester Road, Rock Ferry, Birkenhead, Merseyside L42 2AE. Tel: 051-645 3391.**

# HART

HART ELECTRONICS are specialist producers of kits for designs by JOHN LINSLEY-HOOD. All kits are APPROVED by the designer
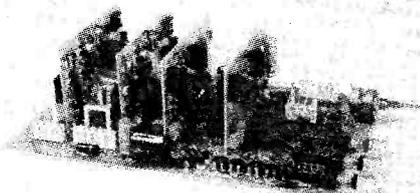
### LINSLEY-HOOD CASSETTE RECORDER CIRCUITS



Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.


Complete Stereo Record/Play Kit ..... £33.70  
 VU Meters to suit ..... £2.30 each  
 Reprints of original Articles ..... 75p no VAT  
 860X Stereo Mic Amplifier ..... £8.70

### LINSLEY HOOD 300 SERIES AMPLIFIER KITS

Superb integrated amplifier kits derived from John Linsley-Hoods articles in Hi-Fi News. Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

K300-35. 35 Watt. Discount price for Complete Kit ..... £98.79  
 K300-45. 45 Watt. Discount price for Complete Kit ..... £102.36  
 RLH485. Reprints of Original Articles from Hi-Fi News ..... £1.05 no VAT
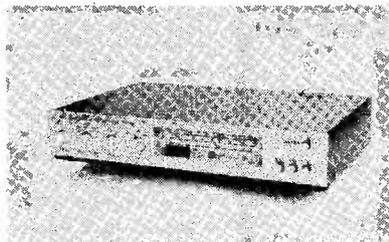
### LINSLEY-HOOD SUPER HIGH QUALITY AM/FM TUNER SYSTEM.



Our very latest kit for the discerning enthusiast of quality sound and an exotic feast for lovers of designs by John Linsley-Hood. A combination of his ultra high quality FM tuner and stereo decoder described in "ELECTRONICS TODAY INTERNATIONAL" and the Synchronyne AM receiver described in "Wireless World". The complete unit is cased to match our 300 Series amplifiers. Novel circuit features in the FM section to include ready built pre-aligned front-end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together make a tuner which sounds better than the best of the high-priced exotica but, thanks to HART engineering, remains easy to build. The Synchronyne section with its selectable bandwidth provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real HiFi listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of it's sound it is incredible value for money. To cater for all needs four versions are available with variations up to the top of the range full AM/FM model, with any unit being upgradeable at any time. Send for our fully illustrated details.

### STUART TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life.  
 K900W Stereo Kit with Wound Coils and Twin Meter Drive ..... £65.67  
 RJ51 Reprints of Original Articles ..... £1.30 no VAT

## HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks ..... £7.66  
 HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response ..... £14.86  
 HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head ..... £14.60  
 HX100 Stereo Permalloy R/P head. Special Offer £2.49  
 MA481 2/2 Language Lab R/P head ..... £13.35  
 SM166 2/2 Erase Head. Standard mounting, AC type ..... £8.85  
 SM150 2/2 Erase Head, DC Type ..... £3.60  
 HQ751E 4/4 Erase Head for Portastudio etc. .... £46.80  
 Full specifications of these and other special purpose heads in our lists.

## HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback ..... £4.54  
 Curved Pole Type for inaccessible heads ..... £4.85

Send for your free copy of our LISTS. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add part cost of post, packing and insurance as follows:

**INLAND**  
 Orders up to £10 - 50p  
 Orders £10 to £49 - £1  
 Orders over £50 - £1 50

**OVERSEAS**  
 Please send sufficient to cover Surface or Air Post as required

Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE  
 (0691) 652894

ALL PRICES EXCLUDE VAT UNLESS STATED

**HART**  
 HART ELECTRONIC KITS LTD  
 4 PENYLAN MILL  
 OSWESTRY, SHROPSHIRE  
 SY10 9AF

**RACKS CABINETS & FANS** **SURPLUS BOUGHT & SOLD** **ELECTRONIC COMPONENTS & OBSOLETE IC'S** **MONITORS VDU'S & PLOTTERS** **1000'S OF ITEMS IN STOCK** **COMPUTER SYSTEMS & PERIPHERALS** **RELAYS MOTORS & STEPPERS** **POWER SUPPLIES & INVERTORS** **ALL TYPES OF TEST EQUIPMENT** **PRINTERS DISK DRIVES & KEYBOARDS** **VIDEO EQUIPMENT & CAMERAS**

# THE 'ALADDINS' CAVE OF ELECTRONIC & COMPUTER EQUIPMENT

## COLOUR MONITORS

16" Decca, 80 series budget range, colour monitors, features include: PIL tube, attractive teak style case, guaranteed 80 column resolution, only seen on monitors costing 3 times our price, ready to connect to a host of computer or video outputs. Manufacturers fully tested surplus, sold in little or hardly used condition with 90 day full RTB guarantee. 1000's Sold to date.  
 DECCA 80 RGB TTL + SYNC input for BBC type interface etc. £150.00 (E)  
 DECCA 80 COMP 75 1 composite video input with integral audio amp & speaker ideal for use with video recorder or TELEBOX ST or any other audio visual use. Only £99.00 (E)

## HIGH DEFINITION COLOUR

BRAND NEW CENTRONIC 14" monitors in attractive style moulded case featuring hi res Mitsubishi 0.42 dot pitch tube with 669 x 507 pixels, 28Mhz bandwidth. Full 90 day guarantee.  
 Order as 1004-N2 for TTL + sync RGB for BBC etc £150.00 (E)  
 1003-N1 for IBM PC etc fully CGA equiv £189.00 (E)  
 1005-N2 RGB interface for QL 85 columns. £169.00 (E)

## 20" & 22" AV Specials

Superbly made, UK manufacture, PIL tube, all solid state colour monitors, complete with composite video and sound inputs, attractive teak style case, ideal for a host of applications including Schools, Shops, Disco's, Clubs etc. Supplied in EXCELLENT little used condition with 90 day guarantee.  
 20" Monitor £165.00 (F) 22" Monitor £185.00 (F)

## MONOCHROME

MOTOROLA M1000-100 5" CRT black & white compact chassis monitor measuring only cm 11.6h, 12w, 22d, ideal for CCTV or computer applications. Accepts standard Composite video or individual H & V syncs. Operates from 12v DC at approx 0.8a. Some units may have minor screen marks, but still in very usable condition. Fully tested with 30 day guarantee & full data. Only £29.00 (C)  
 Fully cased as above, with attractive moulded, desk standing swivel and tilt case Dim. cm 12h, 14.5w, 26d. £39.00 (C)  
 JVC type 751-7 5" ultra compact black & white chassis monitor for 12v 0.7a DC operation Dim cm 11h, 14w, 18d. Simple DIY circuit data included to convert data and separate sync input to composite video input. Ideal portable equipment etc. Supplied with full data. Brand New £65.00 (B)  
 KGM 324 9" Green Screen, Little used fully cased, mains powered high res monitors with standard composite video input. Fully tested and in excellent condition. Only £49.00 (E)  
 20" Black & White monitors by AZTEK, COTRON & MATIOLINI. All solid state, fully cased monitors, ideal for all types of AV or CCTV applications. Units have standard composite video inputs with integral audio amp and speaker. Sold in good, used condition-fully tested with 90 day guarantee. Only £85.00 (F)

## FLOPPY DRIVE SCOOP

A MASSIVE purchase of standard 5.25" disk drives enables us to offer you prime product at all time super low prices. All units unless stated are removed from often BRAND NEW equipment, fully tested and shipped to you with a full 120 day guarantee. All units offered operate from +5 and +12 volts DC, are of standard size and accept the common standard 34 way interface connector.  
 TANDON TM100-2A IBM compatible 40 track FH double sided £39.95 (B)  
 TANDON TM101-4 FH 80 track double sided Only £49.95 (B)  
 JAPANESE Half Height double sided drives by Canon, Tec, Toshiba etc. Specify 40 or 80 track Only £75.00 (B)  
 TEAC FD55-F 40-80 track double sided Half Height Brand New £115.00 (B)

## DISK DRIVE ACCESSORIES

34 Way interface cable and connector single £5.50, Dual £8.50 (A)  
 5.25" DC power cable £1.75, Fully cased PSU for 2 x 5.25" Drives £19.50 (A) Chassis PSU for 2 x 8" drives £39.95 (B)

## 8" DISK DRIVES

SUGART 800/801 single sided refurbished £175.00 (E)  
 SUGART 851 double sided refurbished £260.00 (E)  
 MITSUBISHI M2894-63 Double sided switchable Hard or Soft sector. BRAND NEW £275.00 (E)  
 SPECIAL OFFER Dual 8" drives with 2mb capacity in smart case with integral PSU Only £499.00 (F)

## COMPUTER SYSTEMS

TATUNG PC2000. Big brother of the famous EINSTEIN, the TPC2000 professional 3 piece system comprises: Quality high res GREEN 12" monitor, Sculptured 82 key keyboard and plinth unit containing the Z80A CPU and all control electronics PLUS 2 integral TEAC 5.25" 80 track double sided disk drives. Many other features include Dual 8" IBM format disk drive support. Serial and parallel outputs, full expansion port, 64k ram and ready to run software. Supplied complete with CPM, WORDSTAR, BASIC and accounts package. BRAND NEW Full 90 day guarantee. Original price OVER £1400 Only £299(E)

EQUINOX (IMS) S100 system capable of running either TURBO or standard CPM. Unit features heavy duty box containing a powerful PSU, 12 slot S100 backplane, & dual 8" double sided disk drives. Two individual Z80 cpu boards with 192k of RAM allow the use of multi user software with upto 4 RS232 serial interfaces. Many other features include battery backed real time clock, all IC's socketed etc. Units in good condition and tested prior despatch, no documentation at present, hence price of only £245.00 (F)  
 S100 PCB's IMS A465 64K dynamic RAM. £55.00 (B) IMS A930 FDC controller £85.00 (B). IMS A862 CPU & I/O £65.00 (B)  
 SAE for full list of other S100 boards and accessories.

## PRINTERS

Bulk purchase brings you incredible savings on a range of printers to suit all applications. Many other "one off bargains" can be seen at our South London Shop  
 HAZELTINE ESPRINT Small desktop 100 cps print speed with both RS232 and CENTRONICS interfaces. Full pin addressable graphics and 6 user selectable type fonts. Up to 9.5" single sheet and tractor paper handling. Brand New Only £199.00 (E)  
 CENTRONICS 150 series. A real workhorse for continuous use with tractor feed paper, either in the office, home or factory, desk standing. 150 cps 4 type fonts and choice of interfaces. Supplied BRAND NEW Order as:  
 150-SN up to 9.5" paper handling £185.00 (E)  
 150-SW up to 14.5" paper handling £225.00 (E)  
 150-GR up to 14.5" paper plus full graphics £245.00 (E)  
 When ordering please specify RS232 or CENTRONICS interface.

## Ultra Fast 240 cps NEWBURY DATA NDR 8840 High Speed Printers Only £449 !!

A special purchase from a now defunct Government Dept enables us to offer you this amazing British Made, quality printer at clearance prices. SAVING YOU OVER £1500 !! The NDR8840 features high speed 240 cps print speed with integral, fully adjustable paper tractor, giving exceptional fast paper handling for multi part forms etc. The unit features 10 selectable type fonts giving up to 226 printable characters on a single line. Many other features include internal electronic vertical and horizontal tabs, Self test, 9 needle head, Up to 15.5" paper, 15 million character ribbon cartridge life and standard RS232 serial interface. Sold in SUPERB tested condition with 90 day guarantee. Only £449.00 (F)  
 EPSON model 512 40 column 3.5" wide paper roll feed, high speed matrix (3 lines per second) printer mechanism for incorporation in point of sale terminals, ticket printers, data loggers etc. Unit features bidirectional printhead and integral roll paper feed mech with tear bar. Requires DC volts and simple parallel external drive logic. Complete with data. RFE and tested. Only £49.95 (C)  
 EPSON model 542 Same spec as above model, but designed to be used as a slip or flatbed printer. Ideal as label, card or ticket printer. Supplied fully cased in attractive, small, desk top metal housing. Complete with data. RFE and tested. Only £55.00 (D)  
 PHILIPS P2000 Heavy duty 25 cps bidirectional daisy wheel printer. Fully DIABLO, QUME, WORDSTAR compatible. Many features include full width platen - up to 15" paper, host of available daisy wheels, single sheet paper handling, superb quality print. Supplied complete with user manual & 90 day guarantee plus FREE dust cover & daisy wheel. BRAND NEW Only £225.00 (E)

## POWER SUPPLIES

All power supplies operate from 220-240 V AC. Many other types from 3v to 10kV in stock. Contact sales office for more details.  
 PLESSEY PL12/2 Fully enclosed 12v DC 2 amp PSU. Regulated and protected. Dim cm 13.5 x 11 x 11. New £16.95 (B)  
 AC-DC Linear PSU outputs of +5v 5.5a, -5v 0.6a, +24v 5a. Fully regulated and short proof. Dim cm 28 x 12.5 x 7. New £49.50 (C)  
 POWER ONE PHC 24v DC 2 amps Linear PSU fully regulated. New £19.95 (B)  
 BOSHERT 13088 switch mode supply ideal disk drives or complete system. +5v 6a, +12 2.5a, -12 0.5a, -5v 0.5a. Dim cm 5.6 x 21 x 10.8. New £29.95 (B)  
 BOSHERT 13090 same as above spec but outputs of +5v 6a, +24v 1.5a, +12v 0.5a, -12v 0.5a. New £39.95 (B)  
 GREENDALE 19A06 60 Watt switch mode outputs +5v 6a, +12v 1a, -12v 1a, +15v 1a. D 11 x 20 x 5.5. RFE Tested £24.95 (B)  
 CONVER AC130-3001 High grade VDE spec compact 130 watt switch mode PSU. Outputs give +5v 15a, -5v 1a, + & -12v 6a. Dim 6.5 x 27 x 12.5 Current list price £190. Our price New £59.95 (C)  
 FARNELL G6/40A Compact 5v 40 amp switch mode fully enclosed. New £140.00 (C)  
 FARNELL G24 5S Compact 24v 5 amp switch mode fully enclosed. New £95.00 (C)

## Special Offer EXPERIMENTORS PSU

ONLY £16.95 (C)

Made to the highest spec for BT this unit gives several fully protected DC outputs most suited to the Electronics Hobbyist. +5v 2a, + & -12v 1a, +24v 1a and +5v fully floating at 50ma. Ideal for school labs etc. Quantity discount available. Fully tested with data RFE = Removed From Equipment

## The AMAZING TELEBOX Converts your monitor into a QUALITY COLOUR TELEVISION

Brand new high quality, fully cased, 7 channel UHF PAL TV tuner system. Unit simply connects to your TV aerial socket and video monitor turning same into a fabulous colour TV. Don't worry if your monitor doesn't have sound, the TELEBOX even has an integral audio amp for driving a speaker plus an auxiliary output for headphones or Hi Fi system etc. Many other features: LED Status indicator, Smart moulded case, Mains powered, Built to BS safety specs. Many other uses for TV sound or video etc. Supplied BRAND NEW with full 1 year guarantee. Carriage code (B)



TV SOUND & VIDEO TUNER ONLY £29.95

TELEBOX ST for monitors with composite video input £29.95  
 TELEBOX STL as ST - but fitted with integral speaker £34.95  
 TELEBOX RGB for use with analogue RGB monitors £59.95

Colour when used with colour CRT. RGB version NOT suitable for IBM-CLONE type colour monitors. DATA sheet on request. PAL overseas versions CALL.

## \*\* South London Shop \*\*

Located at 215 Whitehorse Lane, London SE25. The shop is on the main 88 bus route and only a few miles from the main A23 and South Circular roads. Open Monday to Saturday from 9 to 5.30, parking is unlimited and browsers are most welcome. Shop callers also save the cost of carriage.

## MODEMS

Modems to suit all applications and budgets. Please contact our technical sales staff if you require more information or assistance.

## SPECIAL PURCHASE V22 1200 baud MODEMS ONLY £149 !!

MASTER SYSTEMS type 2/12 microprocessor controlled V22 full duplex 1200 baud. This fully BT approved modem employs all the latest features for error free data comms at the staggering speed of 120 characters per second, saving you 75% of your BT phone bills and data connect time !! Add these facts to our give away price and you have a superb buy !! Ultra slim unit measures only 45 mm high with many integral features such as Auto answer, Full LED status indication, RS232 interface, Remote error diagnostics, SYNC or ASYNC use, SPEECH or DATA switching, integral mains PSU, 2 wire connection to BT line etc. Supplied fully tested, EXCELLENT slightly used condition with data and full 120 day guarantee.

LIMITED QUANTITY Only £149 (D)

CONCORD V22 1200 baud as new £330.00 (E)  
 CONCORD V22 1200-2400 BIS £399.00 (E)  
 RIXON Ex BT Modem 27 V22 1200 £225.00 (E)  
 DATEL 4800 / RACAL MFS 4800 EX BT modem for 4800 baud sync use. £295.00 (E)  
 DATEL 2412 2780/3780 4 wire modem unit EX BT fully tested. £199.00 (E)  
 MODEM 20-1 75-1200 BAUD for use with PRESTEL etc EX BT fully tested. £49.00 (E)  
 TRANSDATA 307A 300 baud acoustic coupler with RS232 I/O. Brand New £49.00 (E)  
 RS232 DATA CABLES 16 ft long 25w D plug to 25 way D socket. Brand New Only £9.95 (A)  
 As above but 2 metres long £4.99 (A)  
 BT plug & cable for new type socket £2.95 (A)

## RECHARGEABLE BATTERIES

Maintenance free, sealed long life LEAD ACID  
 A300 12v 3 Ah £13.95 (A)  
 A300 6v 3 Ah £9.95 (A)  
 A300 6-0-6 v 1.8 Ah RFE £5.99 (A)

## NICKEL CADMIUM

Quality 12 v 4 Ah cell pack. Originally made for the TECHNICOLOR video camera, this unit contains 10 high quality GE nicad, D type cells, configured in a smart robust moulded case with DC output connector. Dim cm 19.5 x 4.5 x 12.5. Ideal portable equipment etc. BRAND NEW £24.95 (B)  
 12v 17 Ah Ultra rugged, all weather, virtually indestructible refillable NICAD stack by ALCAD. Unit features 10 x individual type XL1.5 cells in wooden crate. Supplied to the MOD and made to deliver exceptionally high output currents & withstand long periods of storage in discharged state. Dim cm 61 x 14 x 22. Cell and industry standard SMD interface. Ultra high speed data transfer and access times leave the good old ST506 interface standing. Supplied BRAND NEW with full manual. Only £399.00 (E)  
 Dual drive, plug in 135 Mbs sub system for IBM AT unit in case with PSU etc. £1499.00 (E)  
 Interface cards for upto 4 drives on IBM AT etc available. Brand new at £395.00

## BRAND NEW 85 Mb Disk Drives ONLY £399

End of line purchase enables this brand new unit to be offered at an all time super low price. The NEC D2246 8" 80 Mb disk drive features full CPU control and industry standard SMD interface. Ultra high speed data transfer and access times leave the good old ST506 interface standing. Supplied BRAND NEW with full manual. Only £399.00 (E)  
 Dual drive, plug in 135 Mbs sub system for IBM AT unit in case with PSU etc. £1499.00 (E)  
 Interface cards for upto 4 drives on IBM AT etc available. Brand new at £395.00

## COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of IBM AND NEW cooling fans.  
 AC FANS Specify 240 or 110 v  
 3" Fan dim 80 x 80 x 38 £8.50 (B)  
 3.5" ETRI slimline 92 x 92 x 25 £9.95 (B)  
 4" Fan Dim 120 x 120 x 38 £9.95 (B)  
 As above - TESTED RFE Only £4.95 (C)  
 10" round x 3.5" Rofron 10v £10.95 (B)  
 DC FANS  
 Papst Miniature DC fans 62x62x25 mm Order 812 6-12v or 814 24v £15.95 (B)  
 4" 12v DC 12w 120 x 120 x 38 £12.50 (A)  
 4" 24v DC 8w 120 x 120 x 25 £14.50 (B)  
 BUHLER 12v DC 62 mm £12.95 (A)  
 1000's of other fans and blowers in stock CALL or SAE for more details

## SPECIAL INTEREST

Please call for availability or further info.  
 RACAL-REDAC real time, colour drafting PCB layout system £3950  
 DEC VAX11/750 inc 2 Mb Ram DZ, and full doc. Brand New £8500  
 HP7580A 8 pen digital A1 drum plotter with IEEE interface As New £4750  
 CHEETAH Telex machine £995  
 1.5 kw 115v 60 Hz power source £950  
 500 watt INVERTER 24v DC to 240v AC sine wave 50 Hz output £275  
 SOLDER SYSTEMS tin lead roller tinning machine for PCB manufacture £360  
 CALLAN DATA SYSTEMS multi user INTEL based UNIX SYSTEMS multi user software and 40 Mb Winchester disk etc. £2750  
 WAYNE KERR RA200 Audio, real time frequency response analyzer £3000  
 TEKTRONIX 1411/R PAL TV test signal standard. £6500  
 TEKTRONIX R140 NTSC TV test signal standard. £875  
 HP 3271A Correlator system £350  
 PLESSEY Portable Microwave speech / data link, 12v DC, 70 mile range. The pair £275.00  
 19" Rack cabinets 100's in stock from £15.00

All prices for UK Mainland. UK Customers must ADD 15% VAT to total order value. Minimum order, cash £25, Credit Card £10. Official account orders from Government Depts, Universities, Schools & Local Authorities welcome - minimum account order value £25. Carriage charges (A) £1.50, (B) £3.50, (C) £6.50, (D) £8.50, (E) £10.00, (F) £15, (G) Call. All goods are supplied subject to our standard conditions of sale. All guarantees given on a return to base basis. We reserve the right to change prices & specifications without prior notice. Bulk trade & export enquiries most welcome.

MAIL ORDER & OFFICES  
 Open Mon-Fri 9.30-5.30  
 32 Bignin Way,  
 Upper Norwood,  
 London SE19 3XF

LONDON SHOP  
 1000's of Bargains for callers  
 Open Mon-Sat 9-5.30  
 215 Whitehorse Lane,  
 South Norwood, London SE25

DISTEL © The ORIGINAL  
 FREE of charge dial up data base  
 1000's of items + info ON LINE NOW!!  
 300 baud 01 679 1888, 1200/75 91 679  
 6183. 1200 FDX 01 679 8769

ALL ENQUIRIES  
 01 679 4414  
 FAX 01 679 1927  
 TELEX 894502



DISPLAY ELECTRONICS

## SINGLE-ACTION WIRE-STRIPPERS

Extremely quick and easy to use. Just place wire in jaws and squeeze handles. Wire is neatly stripped in one simple action. Also includes tension adjustment and cutter.

**NEW LOW PRICE**

**£2 95**  
FT4CX

**YOU CAN'T BUY CHEAPER**



## HELPING HANDS

Remarkably low price on this most useful piece of equipment. Two fully adjustable crocodile clips hold pcb's etc. firmly and glass magnifier allows close inspection.



**SUPERB VALUE**

**£4 95**  
YK53B

# Maplin

## SUPPLY THE TOOLS! SO YOU CAN FINISH THE JOB WITH EASE!

☎ SALES 0702 554161

## HOBBY VICE

Lever operated suction grip base holds tightly to smooth non-porous surfaces. Ideal for holding small components and assemblies. Metal faced jaws 37 x 11mm, open to 35mm. Base 60 x 60mm. Height 68mm.



**UNBELIEVABLE PRICE**

**ONLY**

**£1 95**  
YP38R

## SOLDER by ADEPTO

**INCREDIBLE LOW-PRICE TRIAL OFFER TO LAUNCH OUR NEW BRAND**

½kg reel **18 swg**

**£6 89**  
YJ92A

(=£5.99+VAT)  
**PER REEL**  
or in boxes of  
20 reels (10kg)

**£4 99**

(=£4.34+VAT)  
**PER REEL**  
(SC20W price £99.80).



Top quality standard flux-cored solder designed for hand and machine soldering of electronic components. Manufactured to BS219 Grade KP, BS441 Grade 2 and BS5625 Class 5a. The solder is a 60% tin, 40% lead alloy containing a non-corrosive flux. Solder starts to melt at 183°C and is fully molten at 188°C. Available on ½kg reels in 0.7mm dia. (22 swg) and 1.2mm dia. (18 swg). Perfect for use with all hand soldering irons including Antex, Weller etc.

**UNBEATABLE TRIAL OFFER PRICE ON ADEPTO FINE QUALITY SOLDERS.**

½kg reel **22 swg** or in boxes of 20 reels (10kg)

**£7 99**  
FY70M

(=£6.95+VAT)  
**PER REEL**

**£5 74**

(=£4.99+VAT)  
**PER REEL**  
(SC21X price £114.80).

## "The finest soldering irons in the world." - Maplin recommend Antex.

Precision soldering irons that are a pleasure to use. Low leakage currents, ceramic element, shatterproof handle. It all adds up to the number one soldering equipment for the hobbyist. Use CS type for very fine work. XS for general use.



17W TYPE CS  
**£7 25**  
FY62S

25W TYPE XS  
**£7 45**  
FR12N

## SOLDERING IRON STAND

Suitable for most soldering irons.

**SUPER LOW PRICE**

**£2 95**  
FR20W

## SOLDERING IRON KITS

CS or XS Iron complete with stand, solder and 'How To Solder' booklet.

**IDEAL GIFT**

CS KIT  
**£9 95**  
FY68Y

XS KIT  
**£10 15**  
FY69A

ALL ITEMS SUBJECT TO AVAILABILITY

**ALL PRICES INCLUDE VAT. PLEASE ADD 50p TOWARDS POSTAGE. IF ORDER BELOW £5 PLEASE ADD 50p**

## DESOLDER PUMP

Powerful pump action and plunger guard.

**INCREDIBLE LOW PRICE**

**NOW ONLY**

**£2 95**  
FR26D

## Maplin ELECTRONICS

P.O. Box 3, Rayleigh, Essex, SS6 8LR.

**MANY MORE PRODUCTS INSIDE!**



Pick up a copy of our giant 512 page catalogue from W.H.SMITH for just £1.60.

Shops at: Sutton New Road, Erdington, Birmingham. 302 Gloucester Road, Bristol. 159-161 King Street, Hammersmith, London. 8 Oxford Road, Manchester. 46-48 Bevois Valley Road, Southampton. 282-284 London Road, Southend-on-Sea.