


SEPTEMBER, 1964

50 CENTS



PHOTOFACT REPORTER

including **Electronic Servicing**

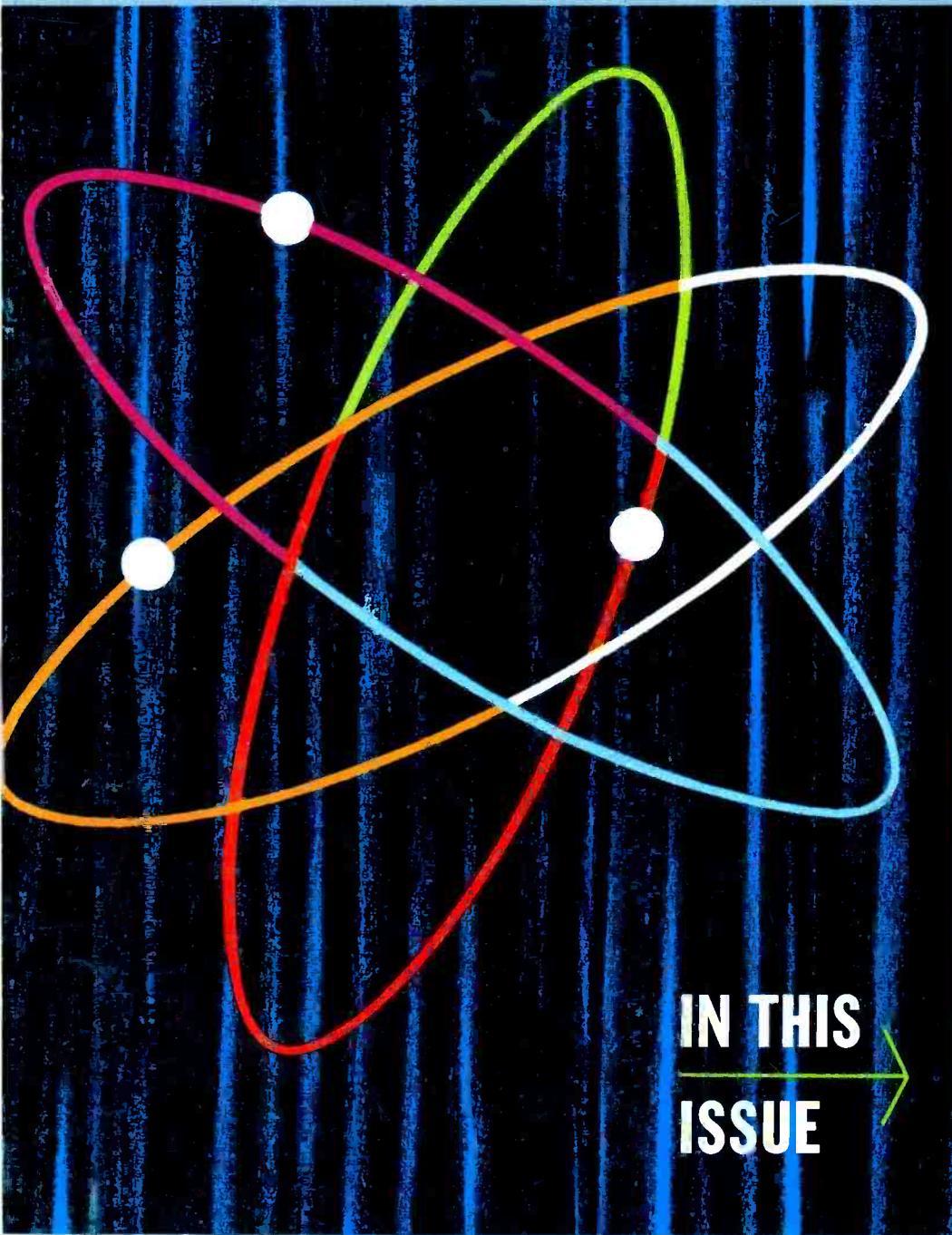

**IN THIS
ISSUE** →

Sync Simplified

**TV Circuit-
Protection Devices**

**AGC Troubles
and Solutions**

**Radio Amateurs
Aren't So Bad**

**Curing Aircraft
Radio Troubles**

JA 2L 1104 1266
WM. M. DAVIS
RAD. & TV SERV.
118 RIVERSIDE AVE.
CANON CITY, COLO.

*and many
others*

why **two** JFD UHF log-periodic TV antennas?

Because our engineers realize that **no** single antenna design is the answer to **all** UHF reception conditions.

UHF frequencies are more adversely affected by surroundings. Degradation due to receiver noise is greater on UHF. Also, UHF signal losses are greater than VHF.

Consequently, our R & D Laboratories in Champaign, Illinois, have developed **two** new UHF antenna concepts based on the acclaimed patented Log-Periodic formula of the Antenna Research Laboratories of the University of Illinois:

JFD LPV-U LOG-PERIODIC UHF ANTENNAS

1

for reception of UHF Channels 14 to 83 and VHF 7 to 13 in cluttered city or hilly areas where high gain and sharp directivity is needed for crisp ghost-free UHF reception in B/W or COLOR!



40" x 31"

model **LPV-U15**
For Fringe Areas up to 50 miles
\$18.95, list

26° to 29° narrow "E" plane (horizontal) beamwidths eliminate ghosts resulting from horizontal reflections—and combine with . . .
"H" plane (vertical) beamwidth, as low as 40°, to give over-all high gain.


- Exclusive new UHF Log-Periodic frequency independent design provides flat, high gain across the band—excellent 300 ohm match gives below 2:1 VSWR.
- 30% to 50% more effective gain and directivity than corner reflectors and stacked bowtie-screens on UHF channels 14 to 83—plus a bonus VHF gain of up to 6 db on channels 7-13.
- Inline solid aluminum rod construction for least wind and ice loading area.
- Beautifully gold alodized for lasting eye-appeal.
- 100% pre-assembled—nothing to swing out or tighten—no movable joints.
- Stainless steel take-off terminals.

FOUR JFD LPV-U LOG-PERIODICS TO CHOOSE FROM:				
	Model	Range	Outperforms	List
	LPV-U21	up to 80 miles	12-bay bowtie-screen	\$27.95
	LPV-U15	up to 60 miles	8-bay bowtie screen	18.95
	LPV-U9	up to 40 miles	4-bay bowtie-screen	12.50
	LPV-U5	up to 25 miles	corner reflector	6.95

2

JFD UHF ZIG-A-LOG LOG-PERIODIC UHF ANTENNAS

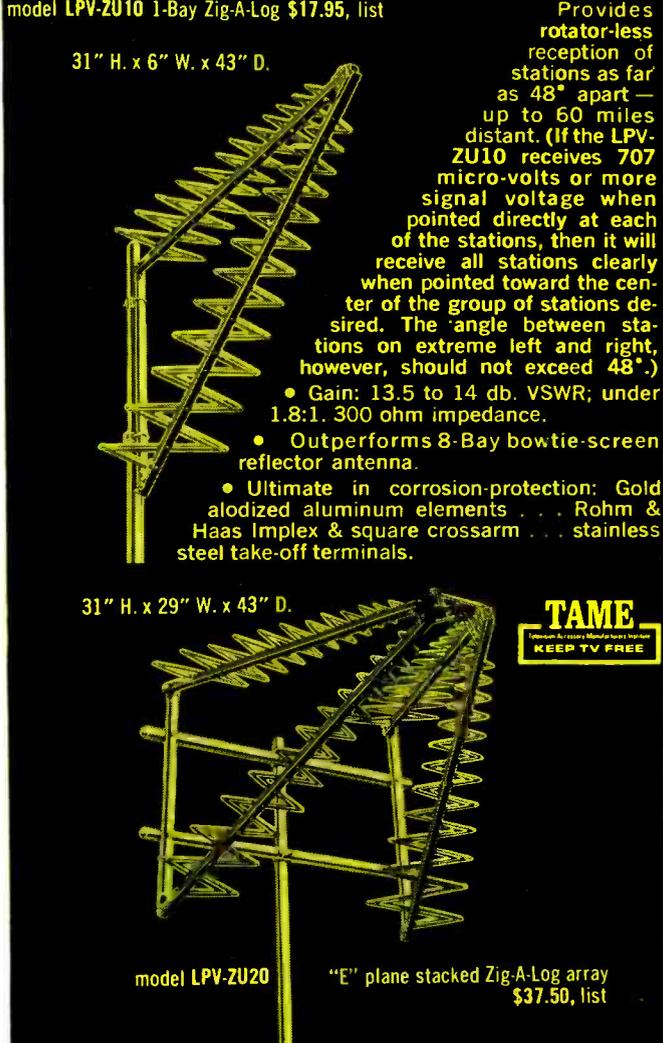where the "ultimate" in UHF color, and black and white reception is required.



model **LPV-ZU10** 1-Bay Zig-A-Log \$17.95, list
31" H. x 6" W. x 43" D.

Provides rotator-less reception of stations as far as 48° apart—up to 60 miles distant. (If the LPV-ZU10 receives 707 micro-volts or more signal voltage when pointed directly at each of the stations, then it will receive all stations clearly when pointed toward the center of the group of stations desired. The angle between stations on extreme left and right, however, should not exceed 48°.)

- Gain: 13.5 to 14 db. VSWR; under 1.8:1. 300 ohm impedance.
- Outperforms 8-Bay bowtie-screen reflector antenna.
- Ultimate in corrosion-protection: Gold alodized aluminum elements . . . Rohm & Haas Implex & square crossarm . . . stainless steel take-off terminals.

31" H. x 29" W. x 43" D.

model **LPV-ZU20** "E" plane stacked Zig-A-Log array \$37.50, list

TAME
The American Television Manufacturers Association
KEEP TV FREE

Narrow 25° "E" (horizontal) and 30° "H" (vertical) plane patterns minimize ghosts caused by horizontal and vertical reflections in flat fringe terrain up to 90 miles from transmitters.

- Gain: 16-17 db, VSWR: under 2:1. 300 ohm impedance.
- Today's most powerful UHF array—matches effective gain of large parabolics—with much less wind, snow and ice-loading area.
- Locks on transmitter signal—no need to re-orient.
- Ultimate in corrosion-protection: Gold alodized aluminum elements . . . Rohm & Haas Implex & square crossarm . . . stainless steel take-off terminals.

Whether the location calls for VHF . . . or UHF . . . or FM . . . or VHF/UHF/FM—there is a JFD Log Periodic antenna to suit your installation needs—perfectly.


WRITE FOR BROCHURES 624 & 711 FOR FULL DATA.

BETTER YET, GET THEM FROM YOUR DISTRIBUTOR TODAY!

JFD JFD ELECTRONICS CORPORATION
15th Avenue at 62nd Street, Brooklyn, N. Y. 11219
JFD Electronics-Southern Inc., Oxford, North Carolina
JFD International, 64-14 Woodside Ave., Woodside 77, N. Y.
JFD Canada, Ltd., 51 McCormack Street, Toronto, Ontario,


LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,958,081; 2,985,879; 3,011,168; 3,108,280 AND ADDITIONAL PATENTS PENDING IN U. S. A. AND CANADA. PRODUCED BY JFD ELECTRONICS CORPORATION UNDER EXCLUSIVE LICENSE FROM THE UNIVERSITY OF ILLINOIS FOUNDATION.

Circle 1 on literature card

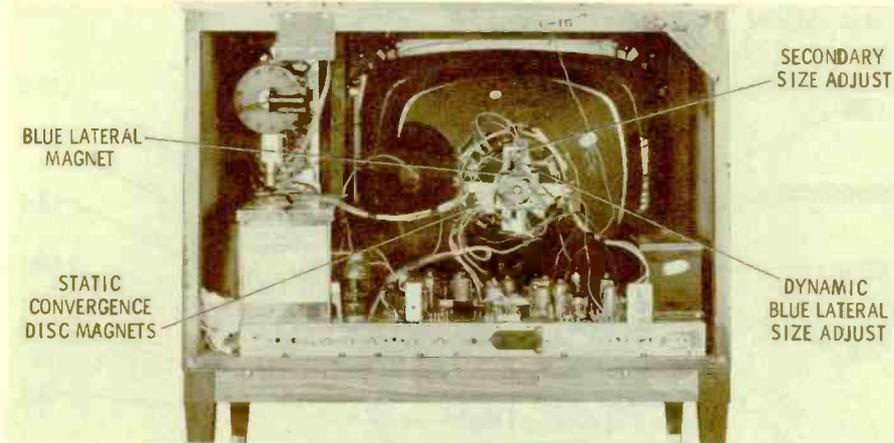


Motorola
Model Y23CK38M-2
Chassis TS908Y

The console color receiver pictured above uses a 23EGP22 picture tube. Design of both monochrome and chroma circuits is much the same as that found in 21" sets; however, some additional adjustments are provided for convergence of this 23" rectangular tube. An assembly located to the rear of the convergence yoke has a dynamic blue lateral size adjustment for converging the blue vertical line with the red and green lines near the left and right edge of the screen. Some models also have a secondary size adjustment in case additional movement of the blue vertical line is required.

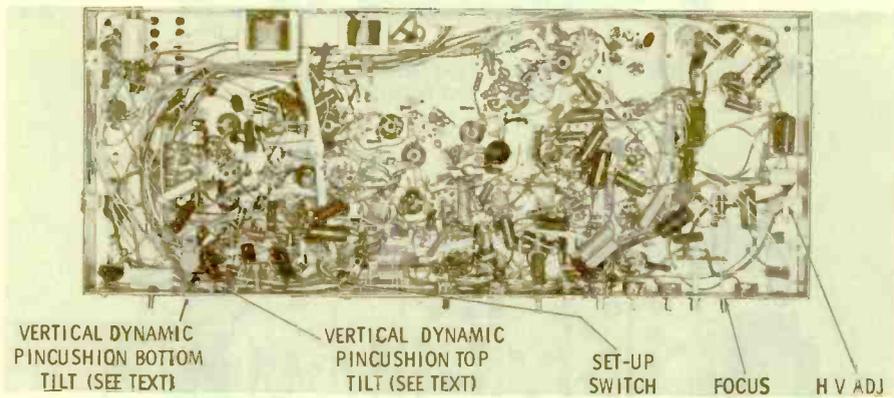


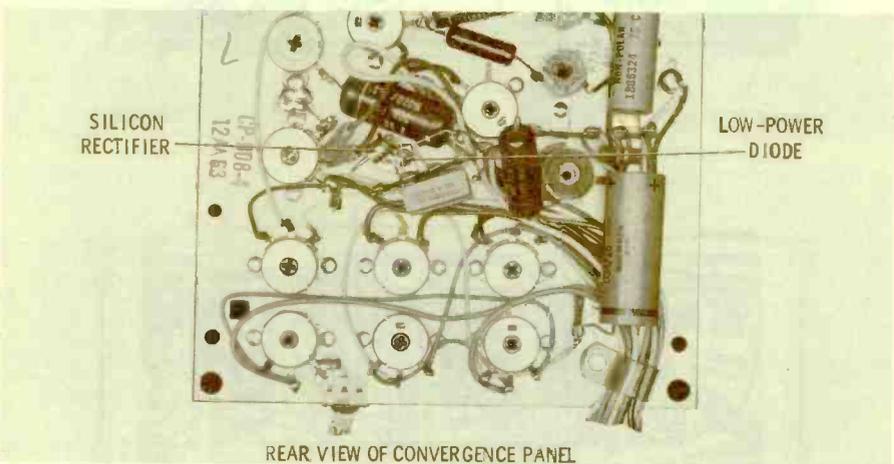Static convergence is accomplished in the usual manner, except that disc magnets are rotated for center-dot convergence and two pincushion tilt adjustments are provided on the chassis. The "vertical dynamic pincushion bottom tilt" control straightens the horizontal line at the bottom of the screen; the top tilt has the same effect at the top of the screen.



Convergence controls are located on a hand-wired assembly behind a removable speaker panel on the front of the receiver. The two latches that hold the panel may be reached from underneath.

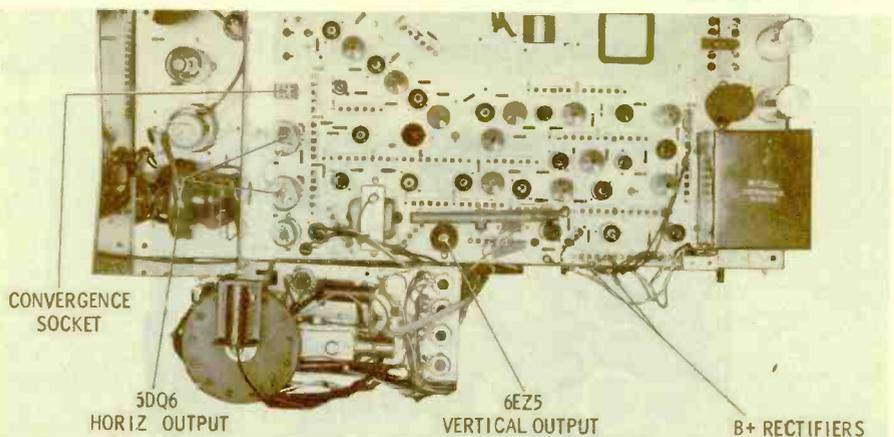Most of the tubes used in this chassis are familiar types; an exception is the 6EZ5 vertical output. The horizontal output circuit uses two 6DQ6's in parallel.




B+ is developed by two silicon rectifiers wired as a voltage doubler and protected by a circuit breaker. The parallel filament circuits are fused with #24 wire, except for the picture tube and high-voltage regulator which operate from a separate winding and are not protected.

Recent productions of the chassis use a low-power diode (shown in photo) to correct for a shift in DC convergence. The silicon rectifier shown in these convergence circuits is a departure from the usual selenium.

The small-neck CRT has its own basing configuration and a special-type socket is required when making tester connections to this tube.

PF REPORTER, for September, 1964. Vol 14, No. 9. PF REPORTER is published monthly by Howard W. Sams & Co., Inc., 4300 W. 62nd St., Indianapolis 6, Indiana. Second-class postage paid at Indianapolis, Indiana. 1, 2 & 3 year subscription prices: U.S.A., its possessions, and Canada: \$5.00, \$8.00, \$10.00. Other countries: \$5.00, \$10.00, \$13.00. Current single issues 50¢ each; back issues 65¢ each.

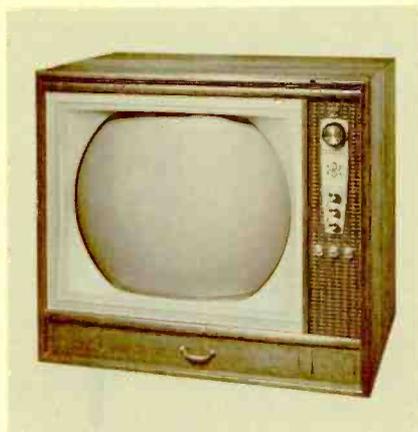




**Setchell Carlson
Model 3C64
Chassis U800**

This unitized chassis is used in all 1964 color television receivers produced by Setchell Carlson. This company has offered a chassis design of this type in black-and-white sets in the past, but this is a first in color television. Nine individual plug-in units, including the RF tuner assembly, are used in this 21" receiver. Stages contained in the individual units are: unit CB-1—first, second, and third video-IF amplifiers, and video and 4.5-mc detectors; unit CC-1—first and second sound-IF amplifiers, ratio detector, audio amplifier and phase inverter, and push-pull audio output; unit CD-1—three stages of video amplification, AGC keyer, and sync separator; unit CE-1—vertical sweep; unit CF-1—horizontal AFC, oscillator, and output, plus high voltage; unit CG-1—low-voltage power supply; unit CY-1—all chroma circuitry.


Any of the above sections may be replaced by a substitute unit in a matter of minutes, thereby in most cases eliminating the need for taking the entire chassis to the shop for service. Also, the chassis is designed so that a monochrome picture can be obtained even though the CY-1 section is removed.

Setup and service controls, along with the convergence panel, are located beneath and to the left of the picture tube and are accessible from the front by opening the hinged panel. The bottom of the chassis is covered by a screen which can be removed for minor servicing and checks without disassembling the chassis.


B+ for this transformer-powered set is developed by two silicon rectifiers connected as a full-wave voltage doubler. Protection is provided by a circuit breaker in series with the secondary winding of the power transformer. A separate 8.3-volt winding on the transformer furnishes heater voltage to the picture tube and the 6BK4 high-voltage regulator; this winding is protected by a wire-link fuse. An additional filament winding—12.6-volt, center-tapped—supplies the remaining filaments, and both legs are protected by wire link fuses. A fourth such fuse is found in series with the primary winding.

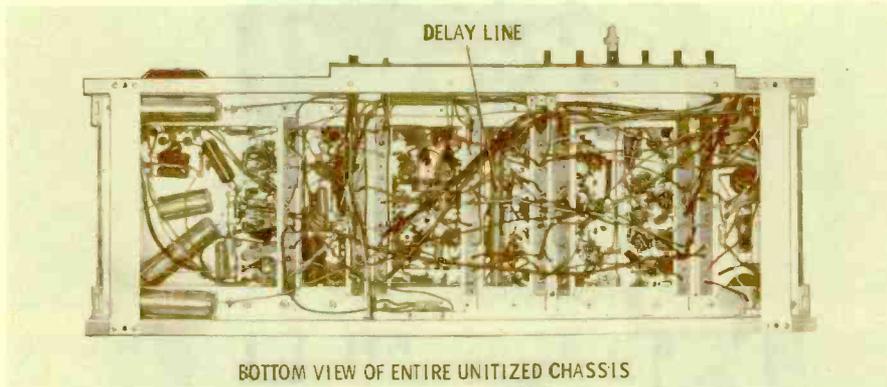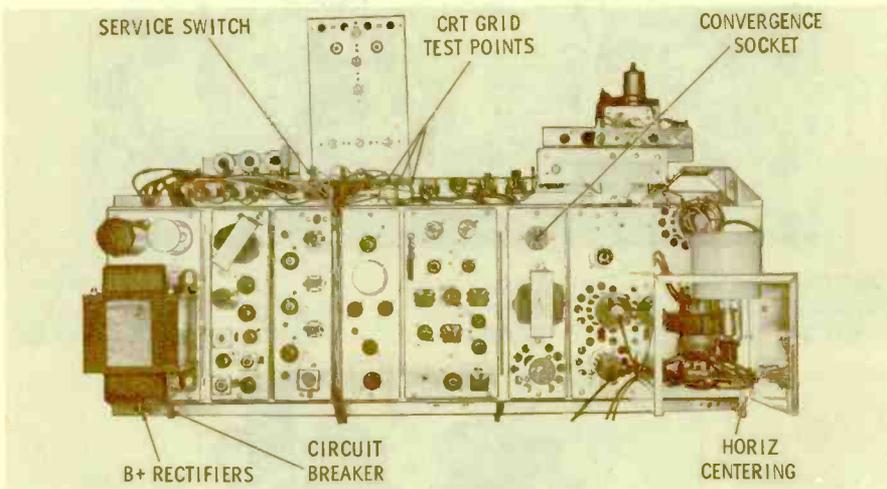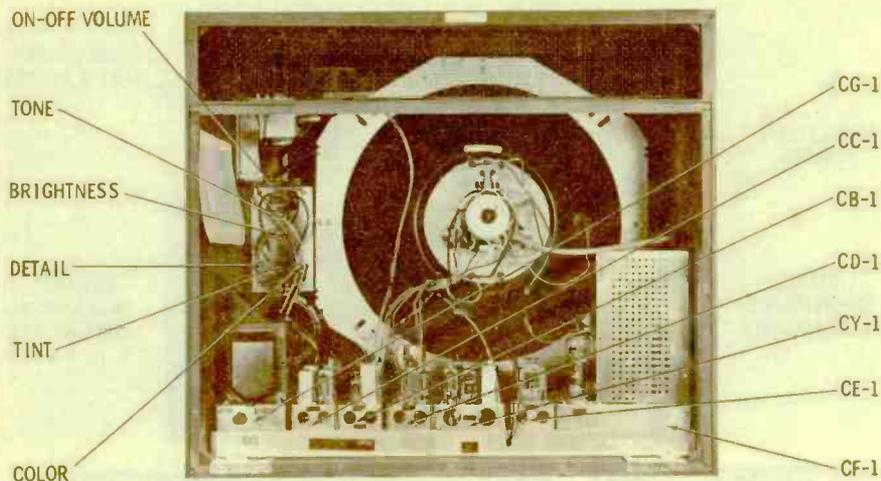

BOTTOM VIEW OF ENTIRE UNITIZED CHASSIS

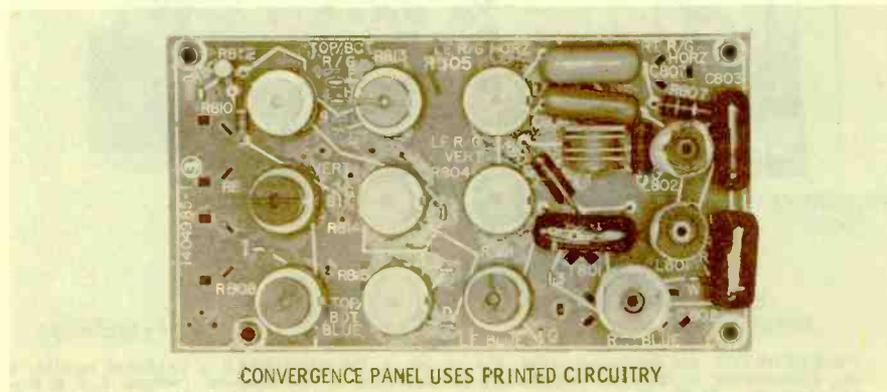

CONVERGENCE PANEL USES PRINTED CIRCUITRY

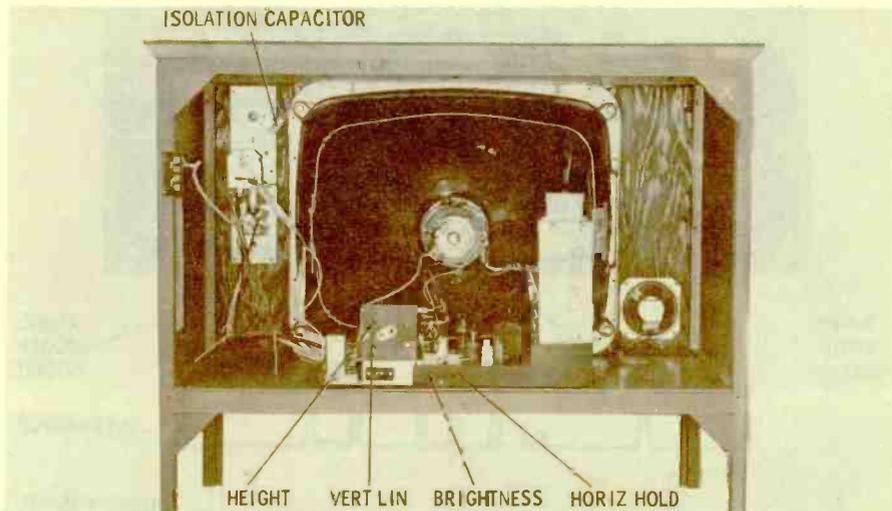

Sonora
Model S64K236W




A new physical chassis, with both common and newly introduced tubes, is the highlight of this 23" console. The lightweight horizontal chassis has only one printed-circuit board with the majority of components mounted on top. Circuits in this receiver aren't changed drastically from those previously used. However, slight changes in connections and component values have been necessitated by the low-B+ tube lineup.

Tubes worth mentioning are the 23FWP4 picture tube, 3HQ5 RF amplifier, 6HB7 mixer-oscillator, 4EH7 first video-IF amplifier, 4EJ7 second video-IF amplifier, 10GK6 video output, 10CW5 vertical multivibrator-output, 21GY5 horizontal output, and 17BE3 damper. The remaining tubes are conventional types that should cause no replacement problems.

This transformerless chassis has no protection for the series filament string. However, a 4.5-ohm, 10-watt surge-limiting resistor and a circuit breaker protect the single silicon rectifier that develops the 130 volts of B+. Most circuits are supplied directly from the 130-volt line, with these exceptions: The sound detector plate is fed from boost, as is the CRT focus anode (in one position of the focus jumper); a 125-ohm, 4-watt resistor lowers the tuner B+ voltage somewhat.

A 1N295 crystal diode, located under a shield covering the final IF transformer, is used as the video detector. A common-cathode dual selenium diode is utilized in the horizontal AFC section. This diode plugs in and may be replaced without dismantling the chassis.

Operating controls are located on the tuner-mounting bracket and are accessible from the front; these include on-off-volume, contrast, and vertical hold. Adjustable from the rear of the chassis are the height, vertical linearity, brightness, and horizontal hold. The width may be varied by a plastic sleeve located between the yoke and the picture-tube neck; slide the sleeve in or out of the yoke to obtain correct width.

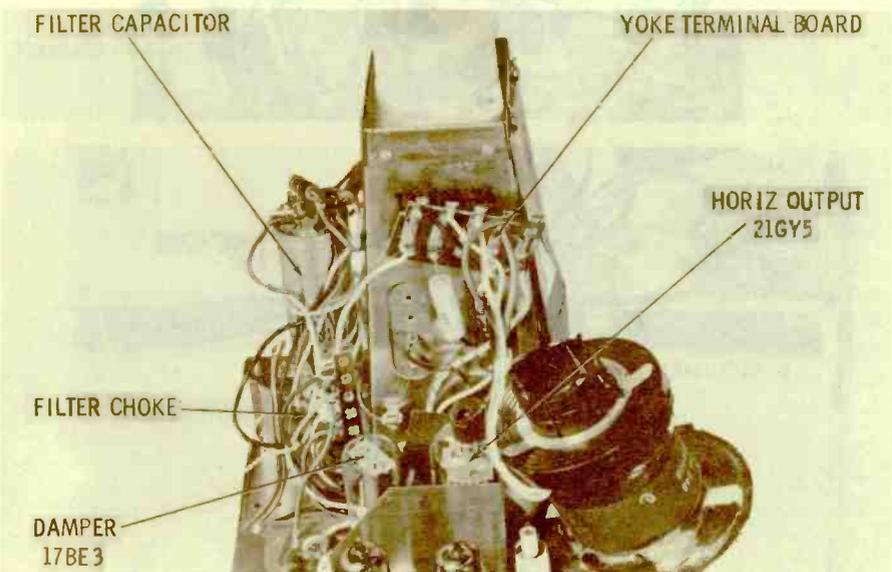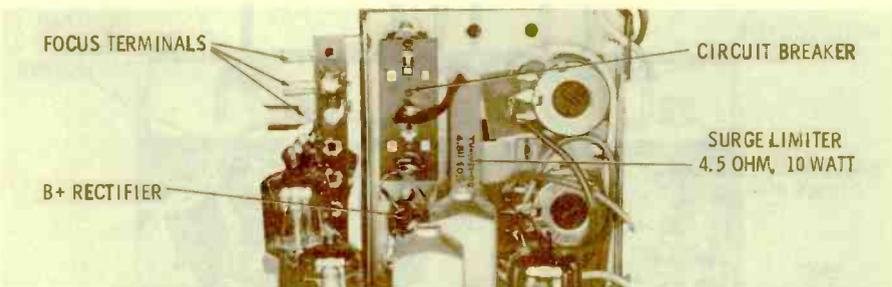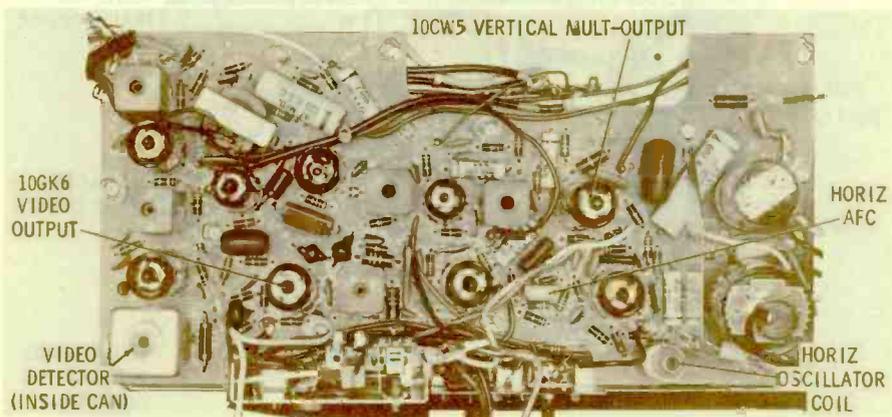



Zenith
Model ML2784W3
Chassis 16L24





The combination model shown here contains a 23" television, AM-FM-FM MPX radio, and four-speed automatic phonograph. The TV chassis is similar to last year's model both physically and electrically.

The VHF tuner uses a 6HA5 RF amplifier and 6GJ7 mixer-oscillator. Tubes in the three-stage video-IF strip include 6EH7's for the first and second amplifiers, and a 6EJ7/EF184 for the third. The video output section uses the pentode portion of a 6JT8, with the triode half of this tube as a sound-IF amplifier. A 6BN6 works as a sound discriminator, and its output is fed through an interconnecting plug and socket to the radio chassis for amplification by the triode section of a 12AX7A in both the left and right channel. A pair of 6BQ5's, located on the TV chassis, operate as a push-pull audio output stage for TV, radio, or phono operation. A 6HS8 performs the functions of sync separator, AGC keyer, and noise limiter, while a 6FM7 operates as vertical multivibrator-output. The tube complement of the horizontal circuit includes a 6KD8 (6GH8 alternate) AFC-oscillator, 6GE5 output, 6AY3 damper, and 2AS2 high-voltage rectifier. The picture tube is a bonded 92° 23ECP4.

B+ is derived from two silicon rectifiers within the voltage doubler network. Silicon protection is afforded by a circuit breaker in series with the primary winding of the power transformer; a 1½" length of #24 wire serves as a fuse link for the parallel filament circuit.

The quadrature coil, buzz control, and AGC control are located on the rear apron of the chassis, while the remaining controls and the horizontal oscillator coil (used for hold control) are on the front of the chassis and are accessible by opening the panel door beneath the picture tube face.

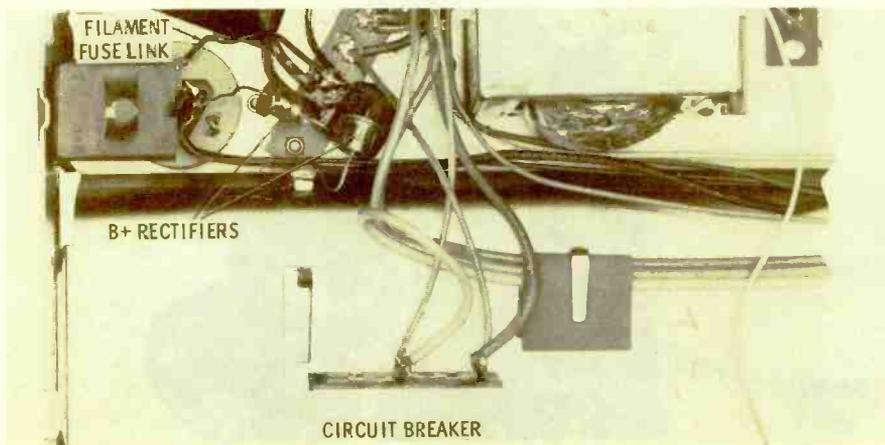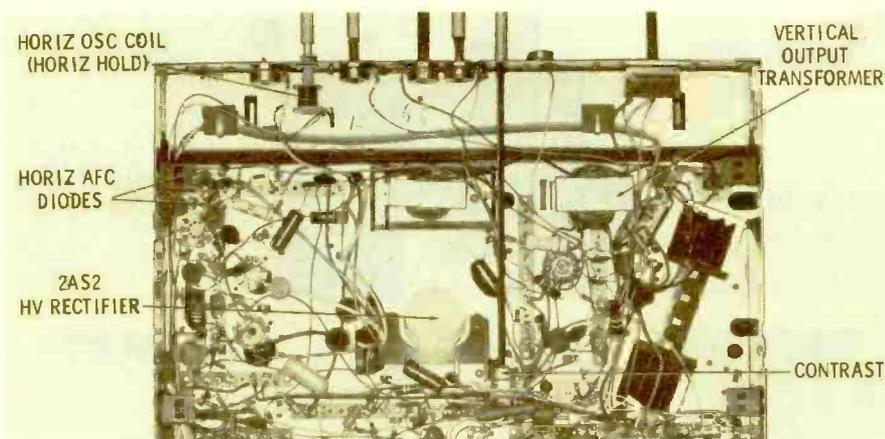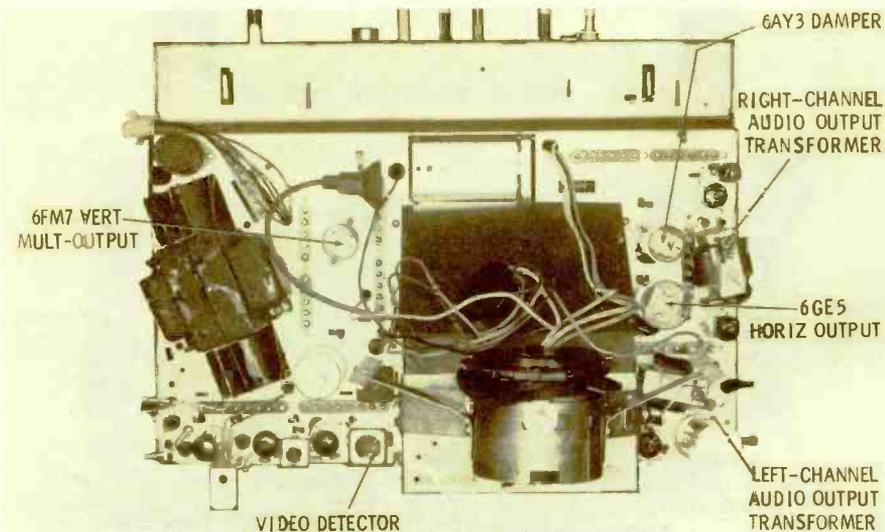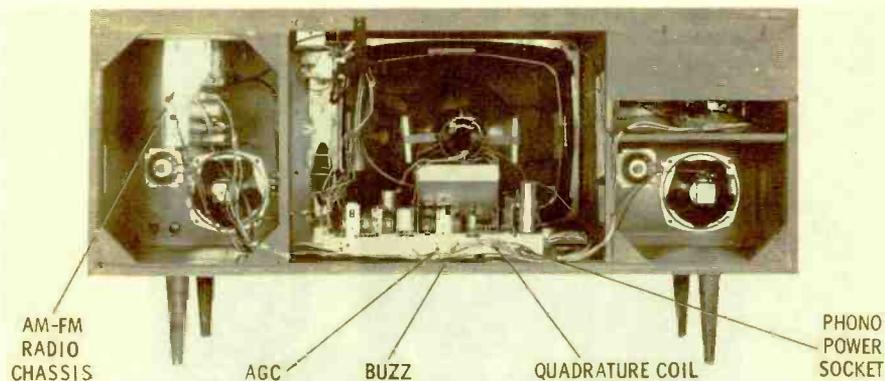Radio, phono, or TV operation may be selected by a function switch on the radio chassis; the loudness, bass, and treble controls are also on the radio chassis.



See PHOTOFACT Set 505, Folder 1

Mfr: Admiral Chassis No. 18B7


Card No: AD 18B7-1

Section Affected: Pix and sync.

Symptoms: Video overload; poor sync; low voltage on screen grid (pin 2) of V5 (6BU8).

Cause: Sync separator screen grid resistor overheated.

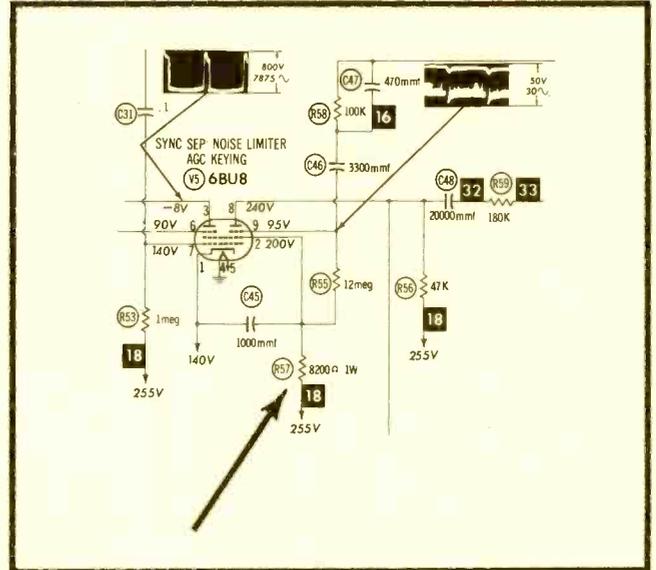What To Do: Replace R57 (8200 ohms—1W); also V5 (6BU8).



Mfr: Admiral Chassis No. 18B7


Card No: AD 18B7-2

Section Affected: Horizontal sync.

Symptoms: Horizontal frequency drifts out of range. Reduced voltage at plate (pin 1) of V9 (6CG7).

Cause: Leaky bypass capacitor in horizontal multivibrator.

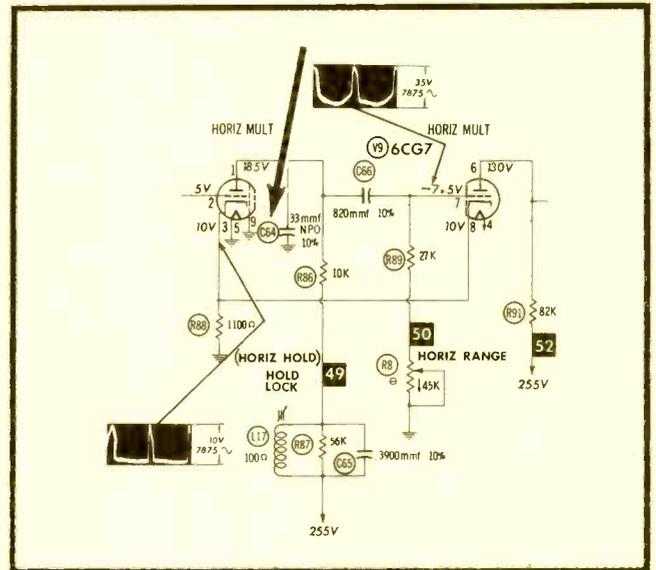What To Do: Replace C64 (33mmf—NPO, 10%).



Mfr: Admiral Chassis No. 18B7


Card No: AD 18B7-3


Section Affected: Raster.

Symptoms: No raster; boost voltage is low.

Cause: Shorted boost circuit filter capacitor.

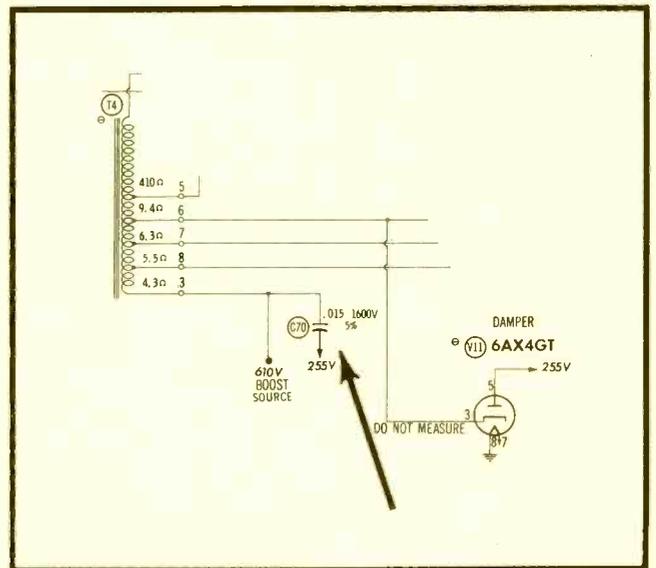What To Do: Replace C70 (.015 mfd—1600V, 5%).



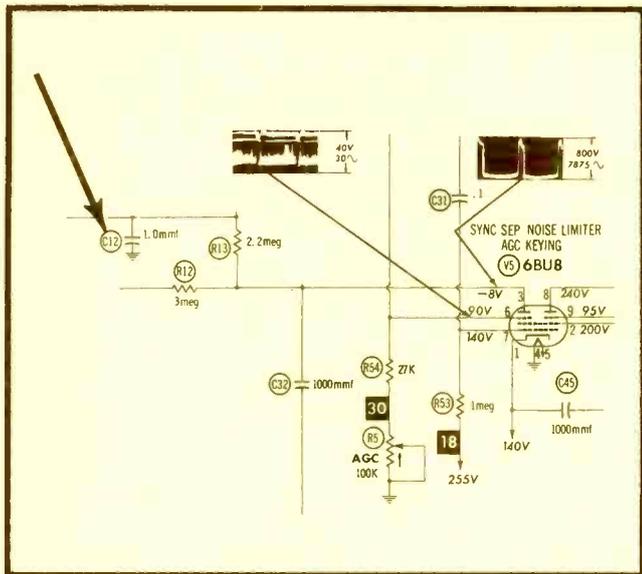

See PHOTOFACT Set 505, Folder 1

Mfr: Admiral Chassis No. 18B7


Card No: AD 18B7-4

Section Affected: Pix and sync.

Symptoms: Picture bends; sync unstable.

Cause: AGC filter capacitor open.

What To Do: Replace C12 (1 mfd).

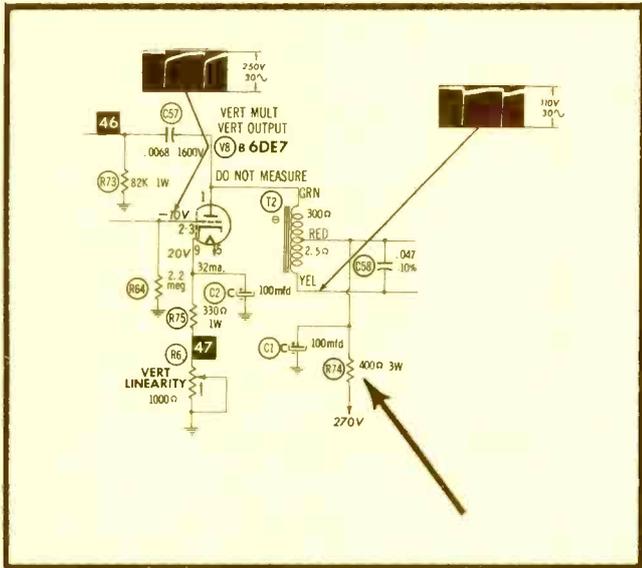

Mfr: Admiral Chassis No. 18B7


Card No: AD 18B7-5

Section Affected: Raster.

Symptoms: Vertical sweep collapses.

Cause: B+ resistor in vertical output circuit overheated.

What To Do: Replace (R74—400 ohms).

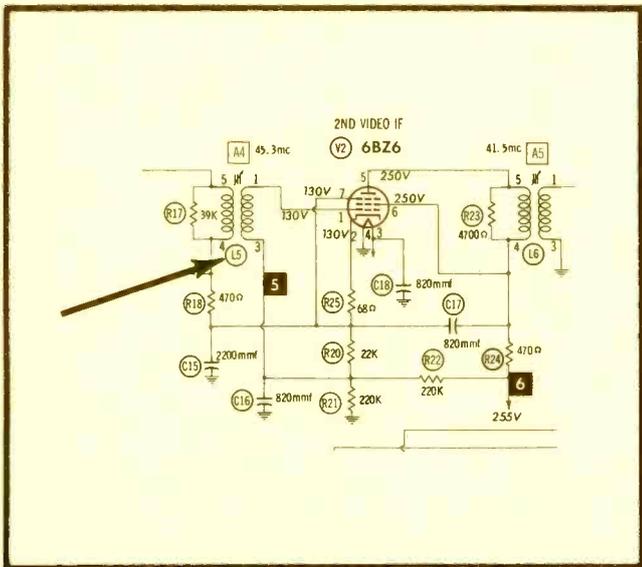

Mfr: Admiral Chassis No. 18B7

Card No: AD 18B7-6

Section Affected: Pix.

Symptoms: Weak and washed out pix.

Cause: Poor connections to transformer in grid circuit of second video IF; no voltage on grid (pin 1) of V2 (6BZ6).

What To Do: Resolder all connections on L5. (Poor connections on L6 cause same symptoms, but grid voltage on V3 is unaffected.)

See PHOTOFACT Set 628, Folder 2

Mfr: General Electric

Chassis No. MW Compactron


Card No: GE MW-1

Section Affected: Raster.

Symptoms: 120 cps modulation in raster; sound and pix okay. Bridging C1A and C1B improves but does not correct condition.

Cause: Leakage between C1A and C1B power supply filters effectively shorts filter choke L20.

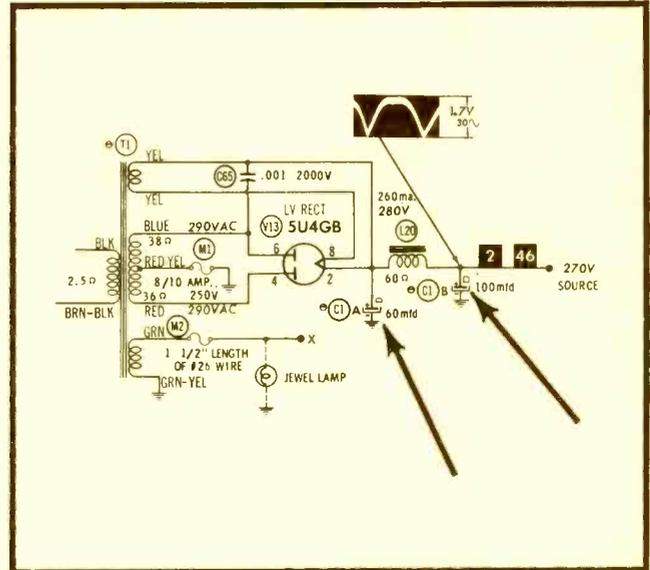What To Do: Replace C1 (60-100-100-5 mfd —350-350-150-200V).



Mfr: General Electric

Chassis No. MW Compactron


Card No: GE MW-2

Section Affected: Sound.

Symptoms: Buzz in sound; adjusting fine tuning control varies amount of buzz. Buzz cannot be eliminated by normal procedure.

Cause: Secondary winding of sound takeoff coil open.

What To Do: Replace L12.

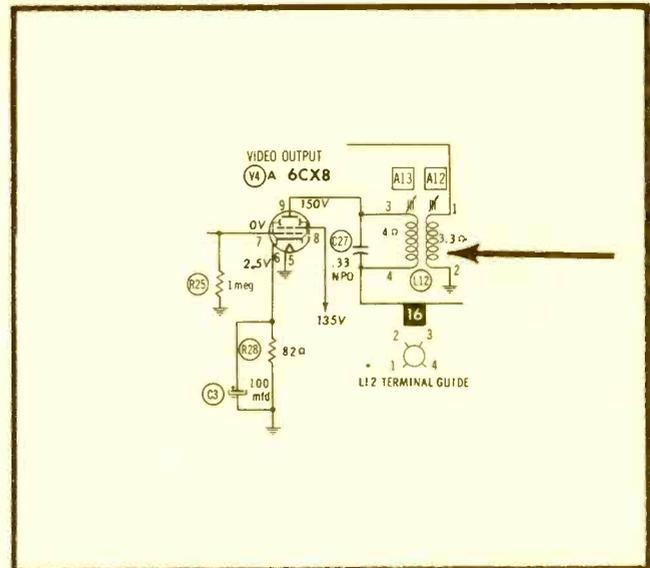

Mfr: General Electric

Chassis No. MW Compactron


Card No: GE MW-3

Section Affected: Pix and Raster.


Symptoms: Vertical foldover. Insufficient width and height; low high voltage; raster blooms.

Cause: Leakage develops in vertical component pack. Bias on grid (pin 3) of V8 (6FJ7) may be low.

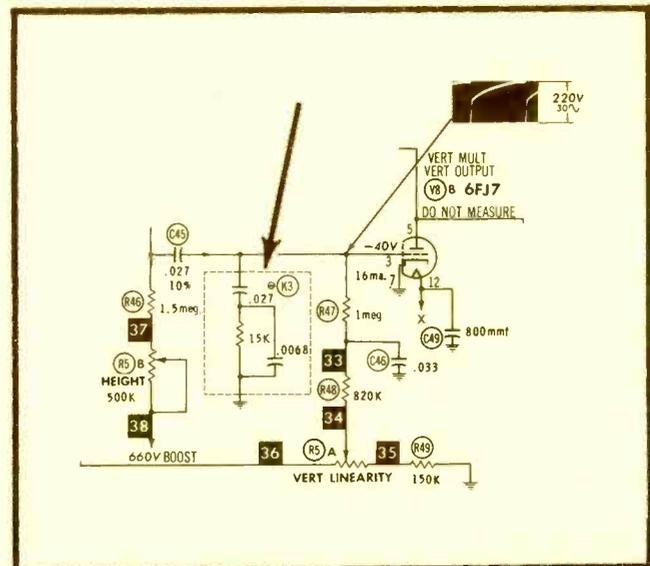What To Do: Replace vertical component pack K3.



TUNER REPAIRS

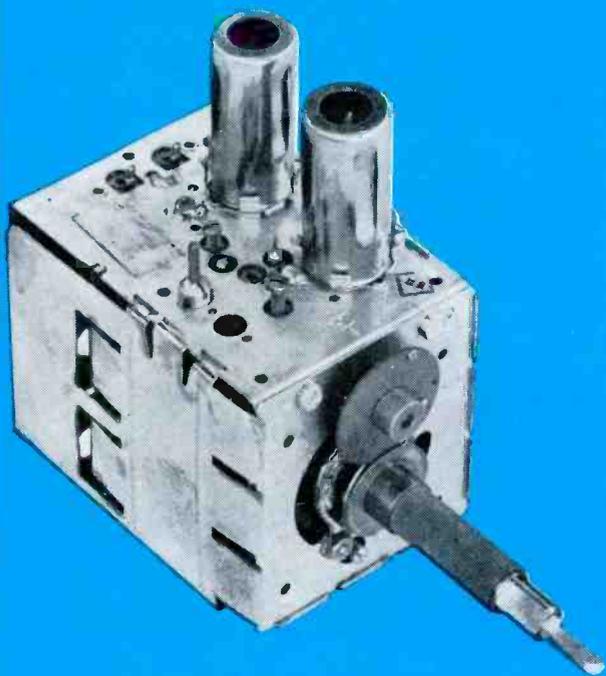

\$9.50

FOR COMPLETE OVERHAUL

**Includes ALL parts (except tubes)
ALL labor on ALL makes**

**24-HOUR SERVICE with
FULL YEAR WARRANTY**

Sarkes Tarzian, Inc., largest manufacturer of TV and FM tuners, maintains two completely-equipped Service Centers to serve YOU. Both centers are staffed by well-trained technicians in this specialized field and are assisted by engineering personnel to assure you of FAST, DEPENDABLE service.

Ⓢ Tarzian-made tuners—identified by this stamping—received one day will be repaired and shipped out the next. A little more time may be required on other makes. Every channel is checked and re-aligned per manufacturer's specifications, not just the channels which might exist in any given area.

You get a 12-month guarantee against defective workmanship and parts failure due to normal usage. Cost to you is only \$9.50 and \$15 for UV combinations, including all labor and parts except tubes. No additional costs. No hidden charges. All tuners repaired on approved, open accounts. You pay shipping. Replacements on tuners beyond practical repair are available at low cost.

When inquiring about service on other than Tarzian-made tuners, always send TV make, chassis and Model number. Check with your local distributor for Sarkes Tarzian replacement tuners, parts, or repair service. Or, use the address nearest you for fast factory repair service.



SARKES TARZIAN, INC.
TUNER SERVICE DIVISION

See your distributor, or use the address nearest you

537 South Walnut St.,
Bloomington, Indiana
Tel: 332-6055

10654 Magnolia Blvd.,
North Hollywood, Calif.
Tel: 769-2720

Manufacturers of Tuners . . . Semiconductors . . . Air Trimmers . . . FM Radios . . . AM-FM Radios . . . Audio Tape . . . Broadcast Equipment

Circle 2 on literature card

September, 1964/PF REPORTER 9

QUESTION:

ANSWER:

When it comes to electrolytic capacitors, why do more than half of the nation's Radio-TV Service Technicians prefer to do business with Sprague Distributors?

Because they don't want makeshift substitutions or multi-rating "fits-all" capacitors. They insist on exact replacements, which are always available through Sprague Distributors everywhere.

SPRAGUE **TWIST-LOK**[®] CAPACITORS...

1863 different ratings and sizes...

the world's most complete selection

of **EXACT** replacements!



We don't have to tell you that it's easier to service with exact replacements. And we don't have to tell you that it's better, too. When sets are designed, specific capacitance values are used for peak operation, so it takes exact replacements to restore original set performance.

And who better than Sprague knows which values and sizes are needed in the replacement market? Sprague, the world's largest component manufacturer, has the most complete specification file on original set requirements. That's why you're always right when you service with Sprague TWIST-LOK exact replacements!

Wouldn't you really rather have what the set manufacturer recommends? An exact replacement in capacitance, voltage, and size is easier to install and less expensive, in most cases, than substitutes!

GET YOUR COPY of Sprague's comprehensive Electrolytic Capacitor Replacement Manual K-107 from your Sprague Distributor, or write Sprague Products Company, 105 Marshall Street, North Adams, Massachusetts.



WORLD'S LARGEST MANUFACTURER OF CAPACITORS

65-127-83 R2

Circle 3 on literature card



PF REPORTER

including Electronic Servicing

VOLUME 14, No. 9

SEPTEMBER, 1964

CONTENTS

Previews of New Sets	1
Zenith, Model ML2784W3, Chassis 16L24 Motorola, Model Y23CK38M-2, Chassis TS908Y Setchell Carlson, Model 3C64, Chassis U800 Sonora, Model S64K236W	
Video Speed Servicing	5
Service hints on Admiral, Chassis 18B7 and General Electric, MW Compactron	
Letters to the Editor	12
The Electronic Scanner	16
The Troubleshooter	21
Symfact: Horizontal Oscillator	23
(Transistor Type) See what happens to voltages and waveforms when troubles occur.	
AGC Troubles and Solutions	28
Shop Talk—Pinpoint elusive AGC faults when trouble seems to be in other circuits. <i>Allan F. Kinckiner</i>	
Sync Simplified	30
Straightforward analysis of sync circuits speeds servicing. <i>Thomas A. Lesh</i>	
ABC's of Convergence	32
Picture Story—Step-by-step instructions give pictorial support for color setup.	
Curing Aircraft Radio Troubles—Part 1	34
Explore this airborne avenue to additional profits. <i>Keith Bose</i>	
Solid-State Rectifiers Come of Age	36
Servicing Industrial Electronics—A survey that includes type designations and applications. <i>Forest H. Belt</i>	
Chasing Distortion	38
Quicker Servicing—Techniques and tools used for eliminating this bothersome bugaboo. <i>Larry Allen</i>	
Death Stalks the Rooftops	56
A potential killer may wait for you on your next antenna repair job.	
TV Circuit-Protection Devices	58
A review of the components that stand silently by to prevent overload destruction of circuits and components. <i>Rufus P. Turner</i>	
Transistorized UHF Tuners	64
Who's afraid of the little "block box"? <i>Allen B. Smith</i>	
Audio—Sideline or Mainline?	72
Dollar and Sense Servicing—If you're considering audio servicing, this article will give you many good tips. <i>James M. Moore</i>	
Radio Amateurs Aren't So Bad	78
Two-Way Talk—Improved relations between the serious hobbyist and the service technician can have many benefits. <i>Howard S. Pyle</i>	
Notes on Test Equipment	82
Lab reports on the B & K Model 1074 TV Analyst, and Seco Model RPS-5 Power Supply.	
Book Reviews	95
Product Report	98
Free Catalog & Literature Service	100
Monthly Index	on free literature card

publisher

Howard W. Sams

editor

Forest H. Belt

managing editor

George F. Corne, Jr.

associate editors

James M. Moore

Allan B. Smith

Stuart N. Soll

Norman D. Tanner

consulting editors

William E. Burke

Joe A. Groves

C. P. Oliphant

production manager

Robert N. Rippy

circulation manager

J. A. Vin

circulation fulfillment

Pat Tidd, Mgr.

Katherine Krise, Ass't.

Cora La Von Willard, Ass't.

art directors

Gene La Rue

Robert W. Reed

advertising & editorial assistants

Hazel Boyer

Rebecca Clingerman

photography

Paul Cornelius, Jr.

advertising sales offices

Dave Milling, advertising sales manager

midwestern

Hugh Wallace

PF REPORTER

4300 West 62nd Street,

Indianapolis 6, Ind.

AXminster 1-3100

eastern

Gregory C. Masefield

Howard W. Sams & Co., Inc.

3 West 57th Street,

New York, N. Y.

MUrray Hill 8-6350

western

The Maurice A. Kimball Co., Inc.

2550 Beverly Blvd., Los Angeles 57, Calif.

DUnkirk 8-6178; and 580 Market Street,

Room 400, San Francisco 4, Calif. EXbrook 2-3365

Address all correspondence to
PF REPORTER, 4300 W. 62nd Street,
Indianapolis, Indiana 46206



Copyright© 1964 by Howard W. Sams & Co., Inc.
PF REPORTER is a trademark of Howard W. Sams
& Co., Inc. No part of PF REPORTER may be
reproduced without written permission. No potent
liability is assumed with respect to use of
information herein. Acceptance of advertising does
not in any manner signify the products, policies
and services so advertised have been approved,
endorsed or recommended by this magazine.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00,
3 years—\$10.00, in the U.S.A., its possessions and Canada.
All other foreign countries: 1 year—\$6.00, 2 years—
\$10.00, 3 years—\$13.00. Single copy 50¢; back copies 65¢.

Indexed in *Lectrodex*.

Printed by the Waldemar Press Div.
of Howard W. Sams & Co., Inc.

ABOUT THE COVER

The varied list of titles shown
on this month's cover illustrates the
ever-increasing complexity of electronic
servicing. Profits in the field require
a constantly-expanding and timely
knowledge of new techniques and concepts.
The successful technician knows that his
greatest allies are up-to-date procedures
and informative articles like
those in this issue.





**NOW...
THE FABULOUS
*G. E. COMBO**

PLAYS ANYWHERE
ON 110 AC OR 12V DC
BATTERY CURRENT

For
Auto • Boat • Plane
Camps • Picnic • Trailer

ATR MODEL 12T-RME-1 INVERTER .. \$39⁹⁵

*G.E. MODEL M110Y 11" PORTABLE TV \$99⁹⁵

*Available at G.E. TV Dealers

Both Only **\$139⁹⁰** Retail
THE **ATR** MODEL 12T-RME-1 ONLY ONE
OF A FAMILY OF FAMOUS DC-AC **INVERTERS**

Also NOW...

HAND WIRED—
NO PRINTED
CIRCUITRY

ATR ALL-TRANSISTOR
ULTRA COMPACT
UNIVERSAL MODEL 707



Karadio
IN DASH...
UNDER DASH...

Complete with variable tone control . . . R. F. stage
. . . Built-in speaker . . . and External speaker jack.

ATR MODEL 707 \$29⁹⁵ Retail



ATR ALL-TRANSISTOR
ROOF-MOUNT and
IN-DASH MODELS

TRUCK
Karadio
MODEL TR-720

FITS ALL TRUCKS • BOATS •
STATION WAGONS
INSTANT PLAY . . . POWERFUL

Complete with patented antenna-yoke assembly.
(U.S. Patent No. 3,087,118. Canadian Reg. 575,567)

ATR MODEL TR-720 \$44⁹⁵ Retail



ATR "A" Battery
ELIMINATOR

For Demonstrating and
Testing Auto Radios—
TRANSISTOR or VIBRATOR
OPERATED!
Designed for testing D.C.
Electrical Apparatus on Reg-
ular A.C. Lines.

MAY ALSO BE USED AS A BATTERY CHARGER
MODEL 610C-ELIF . . . 6 volts at 10 amps. or 12 volts
at 6 amps. Shipping weight 22 lbs.

USER NET PRICE \$55⁰⁰

ATR AUTO RADIO and
COMMUNICATION
LONGER-LIFE
VIBRATORS
"The Best by Test!"



SEE YOUR ELECTRONIC PARTS DISTRIBUTOR OR
WRITE FACTORY FOR LITERATURE & DEALER PRICES

ATR ELECTRONICS, INC.

Quality Products Since 1931
St. Paul, Minnesota 55101—U.S.A.

Circle 4 on literature card

**Letters to
the Editor**

Dear Editor:

Your June "Guide to Importers" should aid technicians greatly. However, I've found that many of the importers listed will not provide any information; indeed, some of them will not even reply to a letter sent to them.

WAYNE BLACKWELL

Amarillo, Tex.

Many other readers have voiced this conclusion, too, Wayne. Watch for a future listing, similar in format, but showing which importers and manufacturers will supply service information and parts for their transistor sets.—Ed.

Dear Editor:

On page 34 of the May issue, I noticed especially the article "TV Waveforms Save Analysis Time." This is the first time I have noticed this feature in PF REPORTER. I think you should put these enlarged waveforms in the magazine every month, showing those in different parts of the television set like you do SYMFACT. With a better understanding of waveforms, we wouldn't keep our scopes sitting at the back of the bench as an ornament. SYMFACT has been a great help, and this feature could, too. How about it?

H. RUTHERFORD

Brooklyn, N.Y.

We're preparing a series of these articles, showing servicemen how to analyze the various portions of waveform traces seen on their scopes. Do any other readers have suggestions for information they'd like to see included in this type of feature?—Ed.

Dear Editor:

Your June article "Scoping in Transistor Radios" was very interesting, but I just can't buy the solution to the formula on page 71. Maybe I missed something, but I'd like to know for sure.

JIM PRINDELL

Circle, Mont.

The formula is solved incorrectly, Jim, but the 1-to-1 ratio still holds true. The solution is as follows:

Formula: $W = E^2 / R$
Substituting: $.35 = E^2 / 3.2$
Multiply both sides by 3.2: $3.2 \times .35 = E^2$
Combine terms: $1.12 = E^2$
Solving: $\sqrt{1.12} = E$
Solution: $1.058 = E$ (rms)

Because the scope reads peak-to-peak voltage instead of rms values, multiply E by 2.8, equalling 2.96 volts. Thus, getting back to our reason for working the formula in the first place, we can use the rule-of-thumb that approximately 3 volts on the scope, measured across a 3.2-ohm voice coil, will indicate approximately 300 mw of power being delivered. By corollary, then, each peak-to-peak volt on the scope equals .1 watt or 100 mw.—Ed. ▲



FOR THE MAN WHO KNOWS . . .

THE

Excelsior

BY

OAKTRON

NO. FEBKW

THE BLUEPRINT TO BETTER SOUND

- 10.10 OUNCE MAGNET
- 1 1/4" ALUMINUM VOICE COIL
- 20 WATT CAPACITY
- NICKLED SOLDERLESS TERMINALS
- MATCHED TWIN CONES
- EXCELLENT WOOFER
- FLAT MID-RANGE
- SUPERB HIGH END
- AVAILABLE IN 8 OR 12 INCH
- A CLASSIC FOR HI-FI
- ECONOMICALLY PRICED
- SEND FOR FREE CATALOG



LOOK TO OAKTRON
FOR QUALITY . . .

OAKTRON
INDUSTRIES, INC.
MONROE, WISCONSIN

Circle 5 on literature card

you get **PRODUCT PLUS** from your Sylvania Distributor



The value of a name Dealers have long found that SILVER SCREEN® 85 picture tubes move off the shelves fast. Why? One big reason is the tube's precision-engineered features. Another is that through the years these same features have created the guaranteed acceptance of a *name*—SILVER SCREEN 85. ■ In picture tubes no brand name approaches the assured recognition of SILVER SCREEN 85 tubes. To your customers, the name means built-in quality and long life dependability. To you, SILVER SCREEN 85 picture tubes mean sales, profits, fewer callbacks, better satisfied customers. ■ Sylvania values that acceptance and safeguards it by applying every new research and development technique for product improvement. That's why the newest SILVER SCREEN 85 picture tubes have longer life and greater product uniformity. ■ Stay with the *quality* name in TV picture tubes—SILVER SCREEN 85. See your Sylvania Distributor.

SILVER SCREEN 85 picture tubes are made only from new parts and materials except for the envelopes which, prior to reuse, are inspected and tested to the same standards as new envelopes.

SYLVANIA
SUBSIDIARY OF
GENERAL TELEPHONE & ELECTRONICS **GTE**

NEW CAPABILITIES IN: ELECTRONIC TUBES • SEMICONDUCTORS • MICROWAVE DEVICES • SPECIAL COMPONENTS • DISPLAY DEVICES

Circle 6 on literature card

Now, JERROLD's great new line of **12 POWERMATES** gives you a transistor amplifier for every job

Leave it to Jerrold! We've expanded our fast-selling *Powermate* line of transistorized antenna amplifiers and indoor amplified couplers to give you a *Powermate* tailored to every VHF, UHF, and FM stereo reception problem you're likely to run into.

Now, from deepest fringe to suburban and metropolitan reception areas, you can offer TV viewers and FM listeners the perfect *Powermate* amplifier or coupler for their needs and their budgets. The chart here, designed to be hung on your wall, tells you which *Powermate* to recommend for each customer.

Ask your Jerrold distributor for complete information, or write *Jerrold Electronics, Distributor Sales Division, Philadelphia, Pa. 19132*.

CUT OUT THIS CHART AND SAVE FOR


INDOOR POWERMATES



Model TA-24 List price \$24.95

NEW!

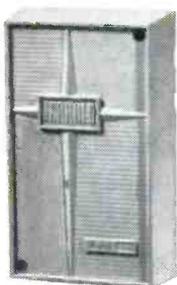For four-set (VHF) indoor coupling in suburban to fringe areas—new economical one-transistor Indoor Powermate supplies up to four TV and FM sets from a single antenna.



For maximum indoor amplification of up to four VHF TV sets and FM receivers—indoor version of the twin-transistor Super Powermate SPM-102, featuring the industry's best gain-overload characteristics and low noise figure.

Model TA-66
List price \$34.95



NEW!

For two-set (VHF) indoor coupling in suburban to fringe areas—new Indoor Powermate Special supplies two VHF TV sets or a TV and an FM set from a single antenna.

Model TA-12
List price \$17.95
Available November.



NEW!

For FM stereo indoor amplification—new Stereo Range Extender is the Indoor Powermate for the FM band. Extends FM broadcast range and splits FM from TV signals to permit use of single broadband TV antenna for both.

Model SRX
List price \$29.95



NEW!

For UHF set coupling indoors—new UHF Indoor Powermate Special supplies clean signals to two UHF sets from a single UHF antenna. High isolation between outputs minimizes interference between sets.

Model TAU-12
List price \$29.95
Available October.



HANDY REFERENCE, OR HANG ON THE WALL OF YOUR SERVICE SHOP.

OUTDOOR POWERMATES



For snow-free VHF TV and noise-free FM where overload is no problem—the original Powermate has been improved with new power-supply circuitry. Unparalleled gain throughout hi and lo VHF bands, coupled with exceptionally low noise figure. Dual outputs.

Model APM-102

List price \$39.95



For bringing in weak VHF signals without overloading from strong local signals—the famous twin-transistor Super Powermate introduced last year. Exceptional gain-overload capabilities permit it to deliver signals from far-distant stations bright and clear, without overloading from strong signals "in your back yard."

Model SPM-102 List price \$44.95



For best color and b&w reception in weak-signal areas—new Super Powermate Coaxial is the coax-downlead version of the famous twin-transistor Super Powermate Model SPM-102 described above. Coax downlead assures superb color and b&w reception by prevention of interference from auto generators and other transients... also is not affected by corrosion and bad weather.

NEW!

Model SPC-103

List price \$47.95



NEW!

For low-cost VHF TV and FM reception in no-overload areas—the new Powermate Special delivers plenty of crisp, bright pictures and sound throughout the VHF and FM band—even from distant stations.

Model LPM-102

List price \$29.95



NEW!

Model SPC-132

For deepest fringe areas—Transistor successor to the famous "De-Snow" model DSA-132, this is the mightiest Powermate of them all. Works where all other units fail. Ideal for small public buildings as well as homes. Coax downlead assures excellent impedance match and minimum interference pick-up. Available October.

List price \$97.75



NEW!

Model UPM-104

For UHF reception in fringe to deep-fringe areas—new super-gain antenna-mounting UHF Powermate. Twin transistors bring in excellent clear pictures even in the most difficult UHF reception areas.

List price \$49.95



NEW!

For low-cost UHF antenna preamplification—antenna-mounting UHF Powermate Special with single transistor provides enough gain to bring poor UHF signals in out of the snow.

Model ULP-104

List price \$34.95

JERROLD
ELECTRONICS

DISTRIBUTOR SALES DIVISION, Philadelphia, Pa. 19132

A subsidiary of THE JERROLD CORPORATION

Circle 7 on literature card

www.americanradiohistory.com

NOW, MORE THAN EVER...

THE FINEST SERVICE IN TV TUNER OVERHAULING

CASTLE TV TUNER-EAST HAS MOVED TO NEW LOCATION WITH IMPROVED FACILITIES

In Long Island City near Postal Concentration Center to provide faster service by mail.

All other U.S. and Canadian Servicemen will get the same fast service from **CASTLE-CHICAGO** and **CASTLE-CANADA**.



**ALL MAKES
ALL LABOR
AND PARTS
(EXCEPT TUBES)*
ONE PRICE**

995

THIS ONE LOW PRICE INCLUDES ALL UHF, VHF AND UV COMBINATION* TUNERS

Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. 90 Day Warranty.

Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

*UV combination tuner must be of one piece construction. Separate UHF and VHF tuners must be dismantled and the defective unit only sent in.

Pioneers in TV



Tuner Overhauling

CASTLE TV TUNER SERVICE, INC.

EAST: 41-90 Vernon Blvd., Long Island City 1, N. Y.

MAIN PLANT: 5701 N. Western Ave., Chicago 45, Illinois

CANADA: 136 Main Street, Toronto 13, Ontario

*Major Parts are additional in Canada

Circle 8 on literature card



The Electronic Scanner

news of the servicing industry

Makes Move




The Parts and Accessories facility of **Radio Corporation of America** has been moved from its former location in Camden to a new building at 2000 Clements Bridge Road, Deptford, New Jersey 08096. Telephone numbers remain the same, except that extension numbers now begin with a PT prefix; the teletype number is 609-845-4962. A new RCA 301 computer is to be installed in the building to provide improvement in service to customers.

Education at the World's Fair

Local and foreign educators participated in the somewhat belated dedication of the **Communications Demonstration Center** in the Hall of Education at the New York World's Fair. Programs of an educational nature will originate from the fully equipped Center daily throughout the two years of the Fair. The integrated facility consists of an auditorium area for groups of up to 400, an area for demonstrating classroom or seminar instructional programs, individual student study stations, a backstage area from which rear-screen projection of film, slides, and television can be presented on multiple screens, a studio facility where television programs and demonstrations can be produced for recording on video tape or for direct live broadcast, and a master control room which is the nerve center for all audio-visual and broadcasting equipment. The demonstration stresses that, although the latest technological equipment for education is being shown, the role of the equipment is not to replace teachers; instead, it is to provide aid in presenting diverse materials, measuring student response, and performing routine, monotonous tasks which would become impossible to do with the vastly increased number of students anticipated in future classrooms.

Tuner Replacement Program

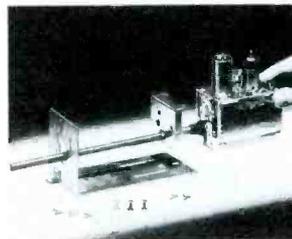

A new parts-distributor merchandising program to replace tuners needing repair has been started by **Standard Kollsman Industries, Inc.**, Melrose Park, Ill. The program is being started with RCA tuners because of their wide usage. The new SKRCA mounting bracket, included in the replacement tuner kit, facilitates replacement of tuners in most RCA receivers. The kit allows substituting SKI tuners for 68 different RCA tuner models of the KRK series. The dealer or service technician will be offered a \$6.00 trade-in on the old RCA tuner when he purchases an SKI replacement kit.

New Acquisition

KTV Tower and Communications Co., of Sullivan, Ill., has been acquired by **Rohn Manufacturing Co.** The KTV company, formerly known as Kuehne Tower Company, manufactured home-television and amateur towers. The line will now be available from Rohn representatives. ▲

WHY... SERVICE COLOR TV ?

**WHY WAIT?
YOU CAN MAKE
MONEY NOW!**

**...IF YOU'RE EQUIPPED - AND
A WIDE BAND SCOPE IS A MUST**



**1,000,000 SETS IN 1964
65% OF NBC PROGRAMMING*
IN COLOR
NEW 25" SETS COMING
THIS FALL
2,000,000 ALREADY IN USE**

*PRIME TIME

This Hickok-quality, full 5", wide-band scope — factory assembled, wired and calibrated can put you in color TV service... for less than \$200.00.

- Rise time—less than 0.08 μ sec.
- AC response—5 cycles to 4.5 MC within 3 db
- Vertical sensitivity—40 MV RMS/inch
- 5 times horizontal sweep expansion
- Sharp, bright (1600 volts anode potential)
Trace with full astigmatic correction
and, of course, it's...




THE COMPLETE COLOR LINE



MODEL 615



MODEL 656XC

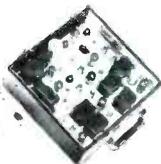


MODEL 660



MODEL 661



MODEL 675A

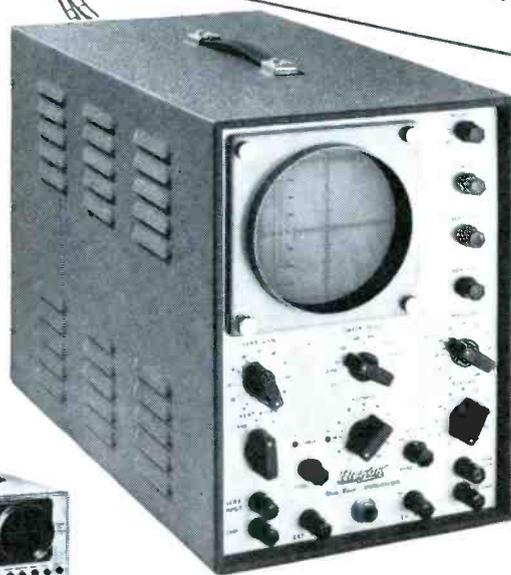

THE **Hickok**

ELECTRICAL INSTRUMENT CO.
10566 DUPONT AVENUE • CLEVELAND 8, OHIO

The antenna that challenges


NEW Swept Element

"COLOR-VE-LOG"

BY

FINCO

Finco's Color Ve-Log challenges all competition on color or black and white reception and stands behind this challenge with a "Guarantee of Supremacy". ■ The swept element design assures the finest in brilliant color and sharply defined black and white television reception — as well as superb FM monaural and stereo quality. ■ FINCO precision-engineered features make these advanced-design antennas indispensable to good home sight-and-sound systems. And, of course, they carry the famous unconditional guarantee from the leading manufacturer in the field — FINCO. ■ Promote the Color Ve-Log Antennas with pride, sell them with confidence, and profit handsomely.

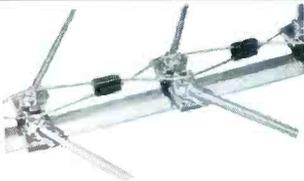


One-piece cross-over drive line assembly has no joints between adjacent driven elements. Eliminates loose connections, shorts, broken drive line sections. Polystyrene snap-lock spacers, with center 'air insulator' space.



Elements are made of triple thick aluminum to stand up in severe weather. Die stamped bracket fastened with tough, thick-gauge rivet holds proportional length sleeve reinforcing shell into which element fits.



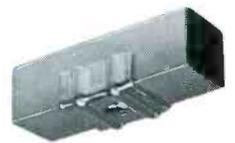First from Finco and exclusive — double contact between drive line and driven element bracket assembly for perfect drive-line support and electrical continuity. Positive, vibration-free, non-corrosive contact.



Boom reinforcing back up brackets at elements add triple strength to the riveted assembly, mounted on a rigid, non-crushable I" heavy duty square boom. Boom rolled square from 1 1/4" diameter round aluminum for increased strength.

Write for color brochure #20-307, Dept. 310 .

all competition!



VL-10
 9 driven elements
 1 parasitic element
 List price \$34.95

Featuring Finco's Exclusive Gold Corodizing



Finco's boom-mast bracket, rust-proofed by zinc plate-gold di-chromate dip process, is the finest available. It has positioned cleats to assure sag-free positive direction of the antenna. Locks tight. Can't tilt. Antenna stays in proper position at all times.



High impact polystyrene insulators are reinforced with strong aluminum shields. This gives quadruple strength in supporting triple-thick snap-in elements. Lifetime assembly with fitted aluminum cup to hold oversize aluminum rivet.



VL-5
 5 element VHF-FM
 5 driven elements
 List price \$16.95



VL-7
 7 element VHF-FM
 7 driven elements
 List price \$23.95




VL-15
 15 element VHF-FM
 9 driven elements
 6 parasitic elements
 List price \$46.95



VL-18
 18 element VHF-FM
 9 driven elements
 9 parasitic elements
 List price \$54.50

The FINNEY Company • 34 Interstate Street • Bedford, Ohio

Circle 10 on literature card

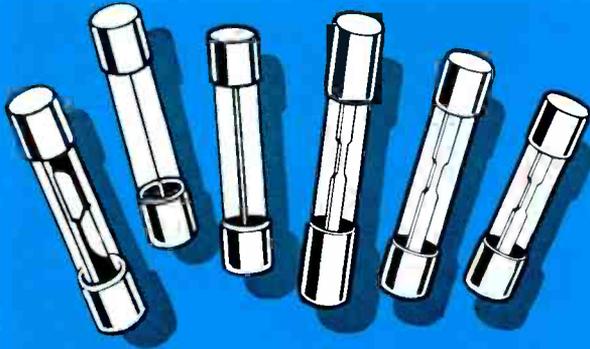

BUSS quick-acting Fuses

"Fast Acting" fuses for protection of sensitive instruments or delicate apparatus;—or normal acting fuses for protection where circuit is not subject to starting currents or surges.

BUSS

Write for BUSS
Bulletin SFB

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

R54 (820K resistor) had increased in value. The voltage on the cathode (pin 8) remains normal even though the resistor is defective.

THURMAN E. WILKES

Goldenrod, Florida

This time we've shown the schematic of the complete vertical multivibrator section of the receiver. To understand how a defective R54 can cause vertical roll but no apparent change in cathode voltage, note that R3A, R53 and R54 form a cathode voltage-divider network. Adjusting the vertical hold control changes the cathode voltage. As the set warms up and R54 changes value, the cathode voltage also changes slightly; the grid bias is thus affected, the tube conduction is changed, and the picture rolls. Once the set is warmed up and R54 settles to a certain value, the cathode voltage may be restored to normal with the hold control. If any of you have trouble of this nature, thank reader Wilkes for this tip.

Distorted Stereo

I am having trouble with a General Electric Model RC1710 multiplex adapter. When I adjust the stereo balance control for proper separation, the output becomes distorted. The distortion can be eliminated by resetting the balance control, but at this point there is no separation between channels. I have aligned and realigned this set but have been unable to correct the trouble.

PAUL M. SELL

Media, Pa.

This multiplex receiver is covered in PHOTOFAC T Folder 620-9. The symptoms seem to indicate either incorrect adjustments or defective components in the L+R channels. Since you have already tried alignment, it would be wise to check capacitor C35 by substitution if necessary. Make sure that the components in printed-circuit unit K3 are okay and that X5 and X6 have precisely the same front-to-back char-

BUSS: 1914-1964, Fifty years of Pioneering....




The Troubleshooter


answers your servicing problems

Cure for Hot and Cold

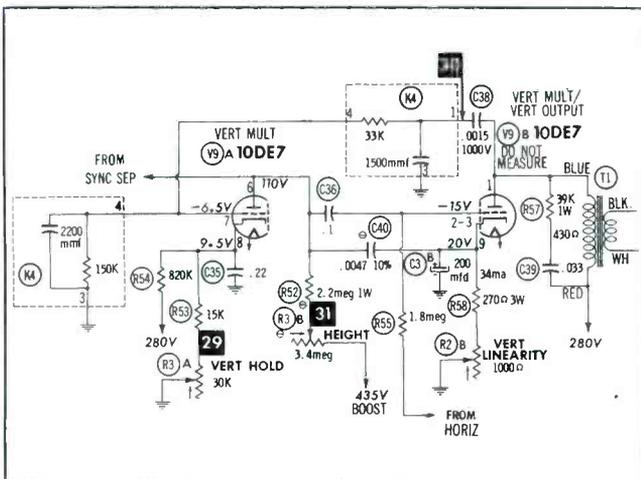With reference to Mr. Meyer's vertical roll problem in a Philco Model G4242M (Troubleshooter, May, 1964, PF REPORTER, page 20), I have had this same problem in several sets of this particular model and found in most cases that



BUSS MBO
1/4 x 1-1/4
inch

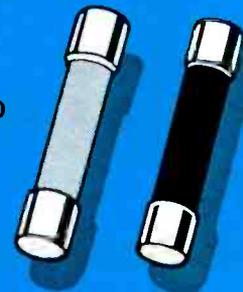

BUSS ABC
1/4 x 1-1/4
inch

BUSS high interrupting capacity Fuses

For the protection of circuits capable of delivering currents as high as 25,000 amps. at 125 volts or 10,000 amps. at 250 volts.




BUSS

Write for BUSS
Bulletin SFB

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis, Mo. 63107

Mallory Distributor Products Company
 P.O. Box 1558, Indianapolis, Ind. 46206
 a division of P. R. Mallory & Co. Inc.

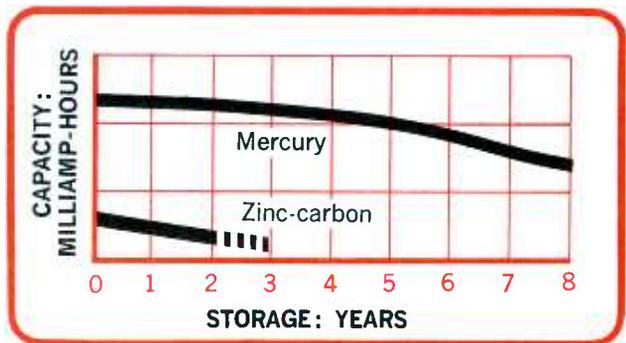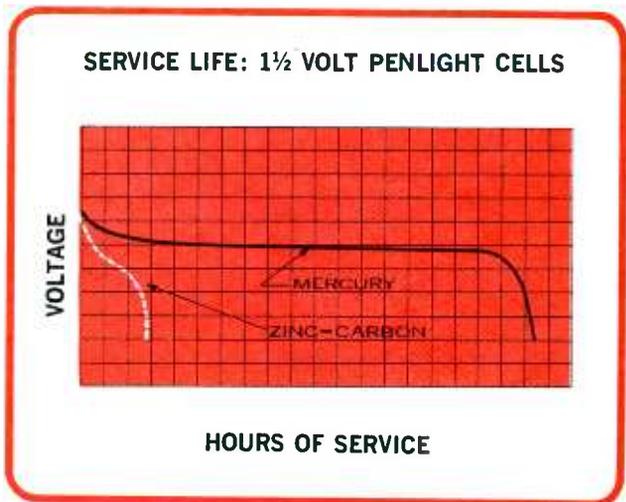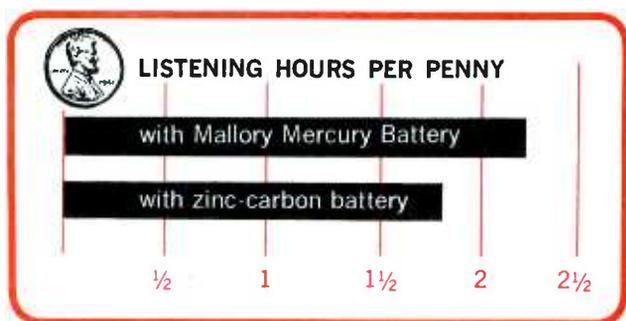Why Mallory Mercury Batteries work better in transistor radios



There are a lot of good reasons why more and more people are using mercury batteries in their transistor radios. And the reasons boil down to this—they're a better value, and they give better performance.

To get a comparison between mercury batteries and ordinary zinc-carbon batteries, let's look at a typical transistor radio. This radio uses size "AA" penlight batteries and has a current drain of 15 milliamperes. The Mallory Mercury Battery is the ZM9 and the zinc-carbon type would be the NEDA type 815. The ZM9 retails for 75¢ versus 20¢ for the 815. Got the picture?

Here's where the fun begins. The ZM9 will operate the radio for 165 hours versus only 35 hours for the zinc-carbon battery. This means that for one penny you'll get 2.2 hours of listening pleasure using the ZM9 versus 1.75 hours for the zinc-carbon battery. In other words, it costs you 0.57 cents per hour to use the zinc-carbon compared to only 0.45 cents for the mercury battery.


We're not through yet. Let's get back to *listening pleasure*. The mercury battery has essentially a flat discharge curve. This means that it presents a more constant voltage to the transistors. Result: you don't have to keep turning the volume control up while you're listening AND the radio *sounds* better because there's far less distortion.

Had enough? There's one more important point. Suppose you put the batteries in the radio and use it only slightly. Those 20¢ zinc-carbon batteries go "dead" in a few months whether you use them or not. But the mercury batteries can be stored 2 to 3 years and still deliver dependable power. Plus the fact that Mallory Mercury Batteries are guaranteed* against leakage in your transistor radio.

We've used this "Tip" to illustrate the superiority of Mallory Mercury Batteries in transistor radios. But this superiority extends to *thousands* of other applications. So whether you're building test equipment, heart-pacers, or satellites, see your Mallory Distributor. He has a Mallory Mercury Battery that will do exactly the job you want done.

*We guarantee to repair the radio and replace the batteries, free of charge, if Mallory Mercury Batteries should ever leak and damage a radio set. Send radio with batteries to Mallory Battery Company, Tarrytown, New York.

Blocking Oscillator With Diode AFC

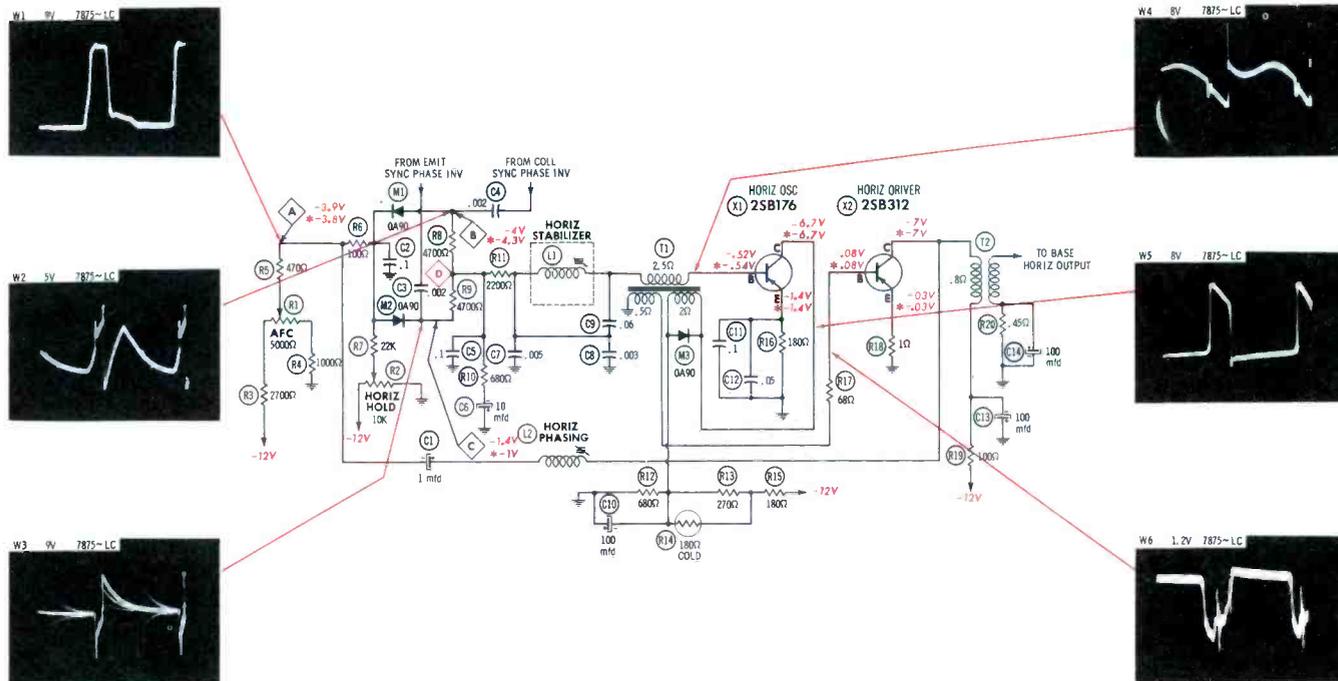

DC VOLTAGES taken with VTVM, on inactive channel; antenna terminals shorted. *Indicates voltages taken with signal present—see "Operating Variations."

WAVEFORMS taken with wideband scope; TV controls set for normal contrast (50 volts p-p at CRT). Low-cap probe (LC) used to obtain all waveforms.

Normal Operation

AFC-oscillator circuit shown here (from Panasonic Model *Mitey 5*) is typical of imported transistor TV's. Sync pulses are coupled from both emitter and collector of sync phase splitter to balanced diode AFC arrangement. Sample pulses from collector of driver arrive via L2-C1 for comparison with incoming sync. Average conduction (without signal) of M1-M2 and therefore base bias of X1 depends on content of W1 and setting of AFC and horizontal hold controls (voltage-divider networks across power supply). M2 conducts only on positive-going pulses of W1; less negative voltage appears at C than at B. Incoming sync (W2, W3) combines with sample W1 and causes diode conduction to change from average value. Resulting positive or negative shift at point D keeps oscillator in sync via path through R11, L1, and T1. C5, C6, C7, C8, R10, and R11 serve as AFC filter (anti-hunt) network. L1 and C9 form parallel-resonant tank to improve oscillator stability and noise immunity. Regenerative feedback (collector to base) via blocking-oscillator transformer T1 sustains oscillation. M3 limits overshoot on trailing edge of feedback pulse. X1 appears reverse-biased, but only because meter reads *average* DC voltage; reverse bias actually exists only during cutoff, but this is major portion of waveform W4. R12, R13, R14, R15, and C10 form voltage divider and decoupling network for X1 collector. Thermistor R14 holds collector voltage fairly constant during operation. T2 is collector load for X2, R19 is supply resistor.

Operating Variations

- A** DC voltage varies from -1 to -7.5 volts (with or without signal) depending on setting of AFC control. Horizontal hold control produces approximate 2-volt swing at this point.
- B** DC voltage, with or without signal, changes from -1 to -6 volts with adjustment of AFC control; bias at minimum setting (least negative voltage at A) may be sufficient to kill oscillator. With AFC set at center of range, adjustment of hold control swings voltage from -3.8 to -4.8 volts. Voltage at C follows variations at B—goes positive at minimum setting of AFC control.
- X1B** Horizontal hold control shifts voltage from -.2 to -.7 volts. As AFC control is rotated toward minimum, voltage swings through zero to about .2 volts positive.
- X1E** Emitter voltage changes from -1.3 to -1.8 volts with full rotation of hold control. X1 collector voltage will vary slightly, but deviations from normal are not very noticeable.
- WAVEFORMS** Horizontal phasing coil (L2) shifts phase of sample pulse slightly, but change is almost unnoticeable with scope; affects picture very little. L1 should be adjusted for equal peaks of W4 in same manner as for tube sets.



Horizontal Sync Unstable

SYMPTOM 1


Phasing Bar in Picture

C1 Open

(AFC Feedback Capacitor—1 mfd)

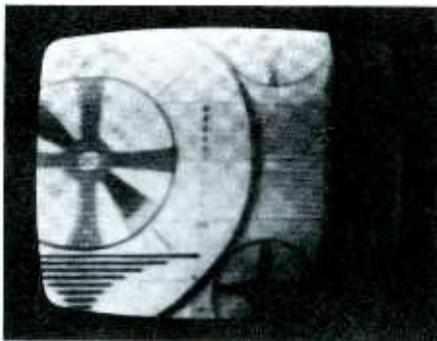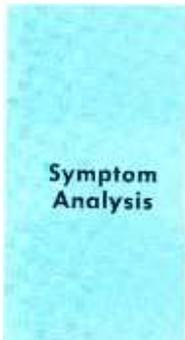

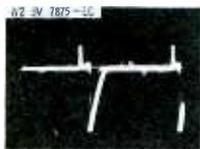
Bars may be sloping in either direction, depending on setting of horizontal hold control; at one setting, stable picture can be obtained, but phasing bar still appears in right side of picture. Adjusting L1 or L2 has little effect on symptom; defect on screen remains.




Waveform Analysis



W2 (shown) and W3 (not shown) contain normal sync, but both are without sample feedback pulse. Abnormal W1 confirms loss of sample pulse. This indicates trouble must be in feedback path. Presence of raster proves driver output pulse is present. Scoping at junction of C1 and L2 indicates pulse is present there. Since signal path is okay through L2, C1 must be open. Scope is necessary instrument here.

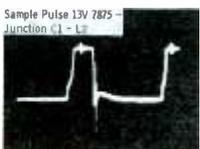

Voltage and Component Analysis

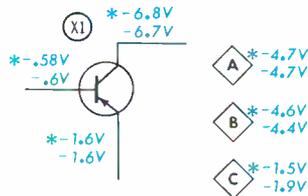

Voltage clues at points A, B, and C are of little help because all vary quite extensively with setting of AFC or horizontal hold control. Voltages on X1 are no help, because oscillator is working (even though off frequency); voltages are thus within tolerance. X2 seems okay, since its voltages are normal. Circuit must have sample pulse for comparison with sync pulses to control frequency of oscillator; this is true of any AFC circuit. Open L2 or broken printed-circuit board could cause symptom that is similar on the screen.

Best Bet: Scope will pinpoint trouble.


No Raster

Sound Not Affected

SYMPTOM 2

R15 Increased in Value

(X1 Collector Load Resistor—180 ohms)


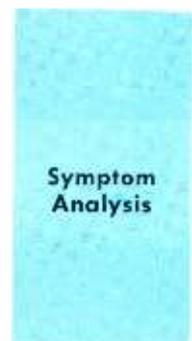


No raster appears on screen; neon lamp held next to HV anode doesn't glow, indicating loss of high voltage. Lack of change when brightness control is rotated proves picture is not blooming out due to overloading of high-voltage section at high brightness setting.


Waveform Analysis



Absence of pulse in W6 hints strongly at trouble in oscillator circuit; eliminates need for further troubleshooting in driver or output stages. W4 offers more evidence of oscillator trouble. Normal p-p signal at this point is 8 volts. Collector-to-base feedback is necessary for oscillation. R17 and interstage winding of T1 can be disregarded. Possible faults are R16, X1 collector bias network, or winding of T1.

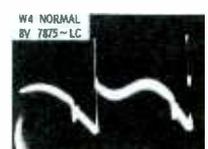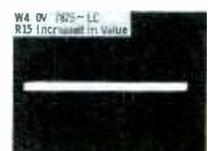

Voltage and Component Analysis

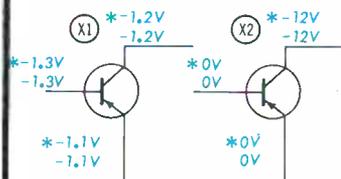

Full supply voltage at X2 collector, and absence of voltage at X2 base and emitter, indicate transistor is cut off. Wrong voltage at X1 collector (-1.2 volt) points to oscillator trouble. Emitter voltage (-1.1 volt) proves X1 is not overconducting—excessive collector current would increase negative emitter voltage. Higher value of R12 would make collector voltage more negative; increased R15, less negative. If R13 or R14 increased in value, parallel resistor would limit combined resistance; voltage change would be slight.

Best Bet: Scope; then VTVM.

Horizontal Frequency Off


SYMPTOM 3

When Synced With AFC Control, Still Unstable


C9 Open

(Stabilizing Capacitor—.06 mfd)

Symptom Analysis

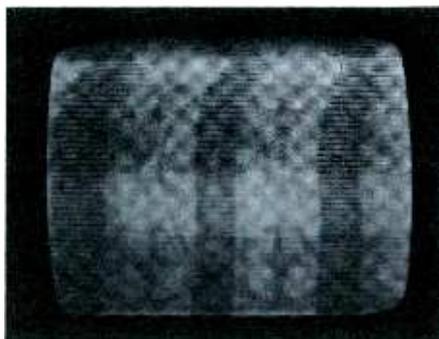


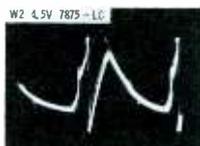Three images—resembling Christmas-tree effect—can be seen, indicating extreme shift in oscillator frequency. AFC control straightens picture, but instability is still apparent. Drift over extended period requires continued readjustment of AFC.




Waveform Analysis

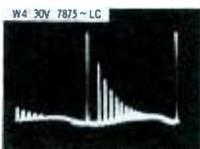With picture in sync, normal waveforms W2 and W3 indicate sync stages and feedback path are okay. Excessive, slowly damped ringing in W4 shows oscillator is being upset between incoming sync pulses. L1 and C9 form tank circuit producing sine wave that reduces effect of noise pulses on oscillator. Normally, sine wave combines with feedback pulse to supply oscillator base with correct signal.



Voltage and Component Analysis

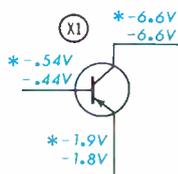

X1 base voltage is normal (with signal); emitter voltage is more negative than normal due to irregular waveform at base. With C9 open and no signal applied, oscillator is operating off frequency, causing X1 base voltage to go less negative. Best clue to actual fault is that adjustment of stabilizer coil has little effect on picture—quite unusual; this coil should shift oscillator frequency considerably. Any component that affects free-running frequency of blocking oscillator stage could cause similar symptom on the screen.

Best Bet: Scope and careful analysis.

No Raster

Sound Normal

SYMPTOM 4

R19 Increased in Value

(Driver Collector Supply Resistor—100 ohms)

Symptom Analysis




Screen is blank; raster may appear intermittently as set is turned on and off. Symptoms indicate trouble in horizontal-deflection or high-voltage section of receiver, but they give no good clue to help pinpoint trouble to one specific stage. More analysis is needed.

Waveform Analysis

Waveform to output stage has nearly correct shape, but amplitude is low (1 volt); normal level is 3.5 volts. Output and flyback thus probably aren't in trouble. Driver collector pulse, normally 10 volts, is greatly reduced (2.5 volts), narrowing search to oscillator or driver stage. Reduced W6 isn't enough to account for weak collector pulse; driver stage is probably cause of trouble.



Voltage and Component Analysis

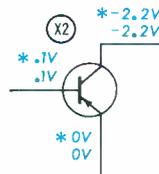

Scope indications suggest voltage checks in driver stage. X2 emitter and base voltages—normally very small—offer little help in locating trouble spot. X2 collector voltage is greatly reduced, leads to suspicion of supply network in collector circuit. Leaky C13, leaky C1, or increased R19 could lower voltage. Also check X2 for possible shorts. Driver and output circuits in transistor sets are easier to troubleshoot than in tube receivers. No boost voltage is involved; simple networks develop voltage for all transistor elements.

Best Bet: Scope; then VTVM.

Oscillator Off Frequency


SYMPTOM 5

High Voltage Low

R1 Wiper Arm Open



(AFC Control—5000 ohms)

Symptom Analysis

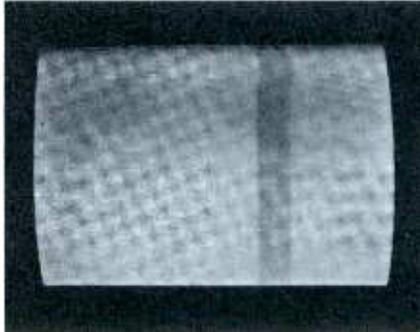


No raster when set is first turned on. Rotation of hold control produces dim raster; two pictures are obtained. Further adjustment of hold control gives sloping bars. Oscillator is running at approximately 1/2 normal frequency; loud whine can be heard. AFC is ineffective.

Waveform Analysis

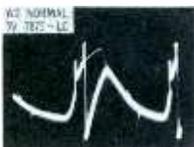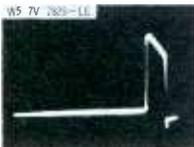

Presetting scope to exactly 7875 cps is valuable aid in troubleshooting oscillator suspected to be at wrong frequency. W5 looks almost normal, but single pulse means oscillator is at 1/2 correct frequency. W2 sync looks normal, but sample pulse occurs only with every other sync pulse (see accompanying normal W2). Waveforms show sync stages are okay and trouble is in either AFC or oscillator circuit.

Voltage and Component Analysis

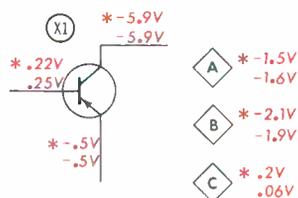

Change of voltage at X1 base from normal -0.5 volt to positive $.22$ volt explains why oscillator is running off frequency; also directs suspicion toward AFC circuitry. Readings at points A, B, and C are significantly smaller than normally; this explains why oscillator base is positive and confirms suspicion of AFC defect. Voltage at arm of AFC control is -1.5 volts and does not change with rotation. Arm must be open; otherwise voltage variation would be noted. Faulty R3 or R5 could show similar symptom.

Best Bet: Scope isolates stage; VTVM pinpoints trouble.

Intermittent Raster

SYMPTOM 6

Critical Horizontal Sync
(When Raster Is Present)

X1 Leaky

(Oscillator Transistor—25B176)

Symptom Analysis




When set is first turned on, raster isn't visible. Adjusting AFC and hold controls to near end of range causes raster to appear, but horizontal sync is unstable. Constant readjustment of AFC and hold controls is required as set warms up or as channels are changed.

Waveform Analysis



With raster absent, W2 shows only sync pulses (no sample pulse); this indicates trouble isn't likely in output or high-voltage section. W5 (with no raster) further isolates trouble to AFC or oscillator by excluding possible defect in driver. W5 (even with raster) has proper amplitude, but duration of pulse is much too short, indicating greatly reduced conduction time of X1. Scope eliminates certain stages.


Voltage and Component Analysis

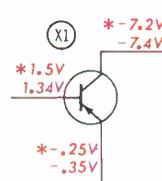

Logical point for voltage measurements, considering information gained from scope, is oscillator transistor. Collector voltage, though slightly increased, gives no definite clue. Base voltage (positive 1.5 volts) explains why no raster is present; transistor ceases to conduct at all if base voltage rises above about 1.4 volts positive; even a small amount of positive base voltage causes oscillator instability. Extent of leakage in X1 determines actual voltage at base; consequently raster may or may not be present.

Best Bet: Voltage analysis followed by component tests.

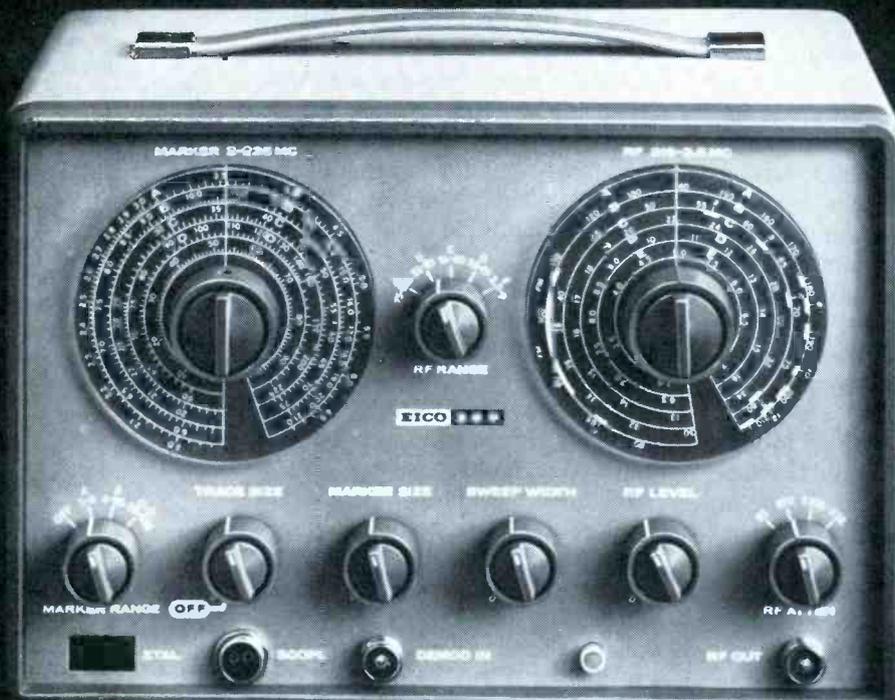post-injected markers
 —do not distort response
 —are not diminished by traps



EICO 369 tv-fm sweep & post injection marker generator

With the 369, circuit response is not affected by markers and markers are not affected by circuit response. The 369 feeds only the required sweep signal to the input of the circuit being aligned or tested. At the output end, a demodulator cable picks off the signal and feeds it to a mixer stage inside the generator, where the markers are added. The combined signal is fed to the oscilloscope. This means that circuitry under test or alignment is not affected by the marker signal, and that traps in the circuitry will not reduce or eliminate the marker.

The EICO 369 has a controllable inductor sweep circuit—all electronic, with no mechanical parts to wear and give trouble later. The sweep generator is independent of the marker generator. It has five ranges: 3.5–9 mc; 7.5–19 mc; 16–40 mc; 32–85 mc and 75–216 mc. All five ranges are fundamentals; tuning to the desired center frequency is simplified by a 6:1 vernier dial and a 330° scale. Output impedance is 50 ohms. Retrace blanking is obtained by both direct grid cut-off and indirect B+ cut-off (via the AGC chain) of the oscillator with a blanking tube that conducts during the negative excursion of the 60 cps sine sweep. A three-stage AGC circuit keeps the level of the swept signal constant over its entire frequency range, even when the widest sweep width of 20 mc is being used. A phasing control at the rear of the EICO 369 adjusts permanently the horizontal sweep signal fed to the scope.

The marker generator in the EICO 369 has 4 ranges covering 2–225 mc. The highest range, 60–225 mc, is the third harmonic of the next lower range. All other ranges are fundamentals. Frequency setting is simplified by a 6:1 vernier dial and a 330° scale. As a rapid check of marker generator alignment a 4.5 mc crystal is supplied with each generator. When plugged into a front panel socket it automatically turns on a fixed frequency marker oscillator. The 4.5 mc signal produced by this oscillator is mixed with the variable frequency marker. The 4.5 mc crystal is used also for alignment of sound circuitry in TV Receivers.

The demodulated wave form with the post injected marker is fed to the vertical input of the "scope", and the horizontal sweep to the horizontal input of the "scope" through one shielded two-conductor cable. Separate level controls for trace size and marker size on the front panel can be used independently. Kit \$89.95; Wired \$139.95



EICO ELECTRONIC INSTRUMENT CO., INC., 131-01 39th Avenue, Flushing, N.Y. 11352
 EXPORT: ROBURN AGENCIES INC., 431 GREENWICH STREET, N.Y. 13, N.Y.

Circle 13 on literature card



PUT THE BEST ON YOUR BENCH

EICO 667 dynamic conductance tube and transistor tester will earn money for you by catching the bad tubes an emission tester would miss. The EICO 667 combines a mutual conductance test with a peak emission test to give a single reading of tube quality. Bad transistors can be spotted easily. Gain and leakage tests will find the defective ones.

TESTS ALMOST EVERY DOMESTIC OR FOREIGN RECEIVING TUBE MADE. The EICO 667 checks 5 and 7-pin Nuvistors; 9-pin Novars; 12-pin Compactrons; 7, 9 and the new 10-pin miniatures; 5, 6, 7 and 8-pin subminiatures; octals and loctals. It will also check many low-power transmitting and special purpose tubes, voltage regulators, cold-cathode regulators, electron ray indicators, and ballast tubes. And by inserting pilot lamps into the special output in the center of the Novar socket you get an instant good-bad test of these lamps.

TESTS MADE UNDER ACTUAL TUBE OPERATING CONDITIONS. When one section of a multi-purpose tube is being tested, all sections are drawing their full rated current. Pentodes are tested as pentodes rather than combining all the elements for a simple emission check. Leakage between tube elements is read directly on a 4½-inch meter in ohms.

TRANSISTORS CHECKED IN TWO STEPS. First for leakage, then for beta or current amplification factor. Both are read directly off the meter dial and both n-p-n and p-n-p transistors can be checked. Price, \$79.95, kit, \$129.95, wired.

Tests all Color, B & W CRT's—70, 90 and 110°!

EICO CRU universal crt test adapter—New CRT adapter for models 667 and 628 has 12-pin socket for 70° and early 90° deflection black and white tubes. Three additional back-to-back plug-socket adapters for 7- and 8-pin 90 and 110° and color CRT's. Adaptable to many other tube testers. Wired \$9.95

Write for Free catalog to Dept. PF-7

Add 5% in West.

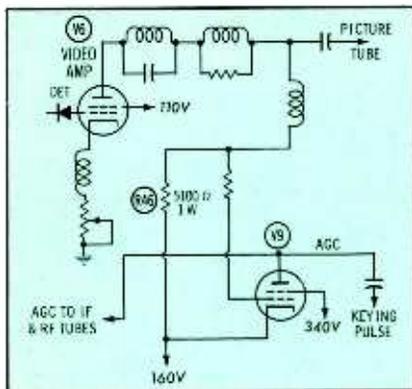


Fig. 1. Voltage drop across video-amplifier load resistor controls AGC tube conduction.

Quick and accurate decisions, indicating which section or circuit is responsible for receiver troubles, invariably reduce troubleshooting and repair time. But troubles arising from AGC-circuit defects are not subject to quick and accurate judgment, because the symptoms are often identical to those produced by defects in other circuits. Sync instability often results from distortion of the composite signal by an AGC defect. Weak or excessive contrast can result from excessive or insufficient AGC voltage. Contrast distortion, in which either the black or white picture contents are compressed, is sometimes caused by abnormal AGC voltages. In some cases, raster shading or unwanted signals of various forms results from AGC defects. Even sync buzz in the sound can sometimes be attributed to an AGC abnormality.

Since most of these conditions tend to indicate trouble in other circuits, AGC troubleshooting is often delayed until these other circuits are



Fig. 2. White compression from reduced AGC.



Fig. 3. Overdriving of video amplifier results in compressing white portion of video signal.

vindicated by extensive and time-consuming tests. Even more confusion results from those cases in which a slight AGC defect combines with a mild defect in another section to produce symptoms that neither defect by itself would cause.

AGC-System Limitations

Sometimes inherent limitations of the AGC system are not entirely compatible with reception conditions at the receiver location. Such incompatibility can be better understood if the limitations of various AGC systems are recognized. *Simple AGC* cannot prevent extremely strong inputs from overloading the video amplifier. This system also develops a small potential (called residual voltage) with weak signals and thus tends to attenuate such signals.

Supplemented AGC can handle stronger signals, but residual voltage is still a problem on very weak signals. Tie-in of the AGC with sync circuits may result in sync instability in some cases of very minor AGC faults.

In noise locations, *peak AGC* develops excessive control voltages, which in turn lowers contrast. This type provides control of very strong signals, but on weak signals the residual voltage still reduces receiver sensitivity.

Nonkeyed tube-conduction AGC (amplified AGC) responds poorly to weak signals because of noise in the AGC tubes, but it provides good control of strong signals. It is also sensitive to minor current-drain variations throughout the receiver.

Keyed, or gated, AGC shows good sensitivity in low-signal areas and good control in strong-signal areas—it works well almost anywhere.

Servicing

Because of the many variables involved, many different troubleshooting techniques are used for AGC defects. One of the most common starts with the use of a voltage source to override the AGC voltage (if any). However, after the picture has been returned to normal by this method (called clamping), a number of voltages may have to be read to find the defective component. Actually, the defective component or abnormal condition can often be

detected by carefully analyzing voltages before resorting to overriding the bias. When keyed or nonkeyed AGC is used, the bias voltage of the AGC tube should be critically examined. The following cases concerning AGC systems of all types illustrate troubleshooting procedures.

Keyed AGC

A Hoffman receiver using a Model 187 chassis was brought into the shop. The complaint was of an extremely weak picture. Tube substitution in the picture-signal stages didn't help, so a scope check was made at the video-amplifier grid. A composite signal amplitude of less than 1 volt indicated trouble in either the IF or RF stages, most likely the former because of the absence of snow. Checking these stages revealed that the plate and screen voltages were slightly high, caused by excessive bias on the

AGC

AGC-controlled tubes.

The circuit (Fig. 1) is such that the amount of AGC voltage depends on conduction of the AGC tube; this conduction is controlled by the voltage drop across plate load resistor R46 in the video amplifier. With no signal applied to the video-amplifier grid, V6 draws a large amount of plate current, and a voltage drop of about 40 volts is developed across R46. The AGC tube is biased beyond cutoff, and no AGC voltage is produced. With a signal applied to the video-amplifier grid, the average plate current of the negative DC component of the signal. A smaller voltage across R46 leads to increased conduction of the AGC tube and development of AGC voltage.

In the receiver under discussion, even though the DC signal component was only a fraction of a volt, the drop across R46 was less than 20 volts. A video-amplifier defect

was thus indicated, but tube substitution produced no change, and checks of the screen and cathode circuits revealed nothing wrong. These tests left only one possibility—decreased resistance of R46. An ohmmeter check showed that this 5100-ohm 2-watt resistor had reduced in value to a mere 2000 ohms. Replacing it with a 5-watt wirewound unit restored normal operation.

Problems With Simple AGC

An RCA set being serviced for a variety of complaints was found to have white compression (Fig. 2) on one of the three stations available. Waveforms observed at the grid of the first video amplifier were normal, except that the amplitude for the offending station was about 5 volts compared to 4 volts for other stations. Moving the scope to the output of the first video amplifier gave a trace (Fig. 3) which clearly

overloading and poor sync at moderate settings of the contrast control. The chief cause of the condition is slight grid emission or gas in tubes controlled by the AGC. These tubes often require heating in a tube checker for as much as an hour before the gassy condition is indicated, yet these very same tubes will cause trouble in a receiver in less than ten minutes.

For example, consider an AGC circuit similar to the one shown in Fig. 5. When the range switch is in the "Strong" position, any voltage drop across R33 indicates one or more gassy IF, mixer, or RF tubes. With the range switch in the "Normal" (center) setting, AGC is applied only to the IF tubes, and a voltage drop across R33 indicates a gassy IF tube. When the range switch is in the "Weak" setting, however, one end of R33 returns to ground through R34, and a voltage difference is normal.

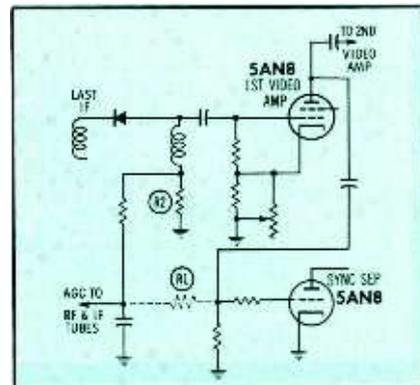


Fig. 4. Adding resistor in circuit helps prevent video overloading from strong signals.

ratio, but the overall amplitude was about twelve volts, more than twice normal. Severely compressed sync was observed at the video output (Fig. 7B). The AGC voltage measured -9 volts at the source and only -3 volts at the terminal end of the AGC filter resistor. Replacing one of the IF tubes decreased the voltage difference to about 3 volts, but it didn't noticeably improve the sync compression of the video output signal. Replacing the mixer tube reduced the DC drop across the AGC filter resistor to less than 1/2 volt and also restored the video output signal to normal (Fig. 7D). Fig. 7C shows the much cleaner waveform at the video-amplifier grid after replacing the two tubes.

Controlled tubes having gas or grid emission produce excessive amplification; this results in excessive

• Please turn to page 90

TROUBLES AND SOLUTIONS

by Allan F. Kinckiner

showed white compression; note the compression along the bottom edge of the video. Substitution of several 5AN8 video amplifier tubes produced no improvement.

Finally the technician observed another factor—the offending station was transmitting a signal in which the sync pulses formed a higher percentage of the composite signal than in the signals from the other stations. Since simple AGC, as used in this set, normally develops a voltage somewhere between the picture-signal level and the sync-pulse level, the offending signal generated a slightly lower AGC voltage than the others. A cure was achieved merely by adding 4.7 meg resistor R1 (Fig. 4). Several early RCA chassis (KCS87, 93, etc.) use this or a similar circuit, so make a note of this cure for white compression.

One of the most common problems in sets using simple AGC is

In circuits with a voltage divider network, and in circuits where one end of the filter resistor is connected to a slight positive AGC delay voltage, determining gas quality of the controlled tubes is not so simple. It is still possible however: Replace the tubes in controlled stages, tune in the strongest station, and read the voltage drop across the AGC filter resistor. Use this voltage drop as a standard for comparison with that using the original tubes. It's a good idea to mark the schematic with this voltage value.

An excellent example of the results of gassy IF tubes occurred in a Motorola TS-410 (Fig. 6). This set played acceptably for about ten minutes after being turned on. Then excessive contrast developed and gradually became more severe until the picture started to bend and slip vertically. The signal at the video-amplifier grid (Fig. 7A) was perfectly normal in shape and sync-to-picture


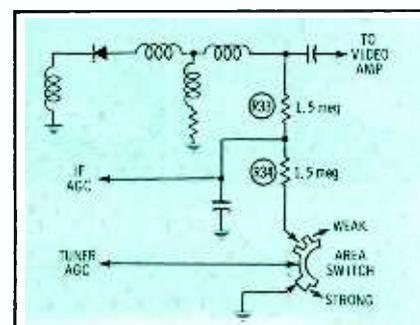


Fig. 5. Voltage drop across R33 can give useful info concerning RF, IF, mixer tubes.

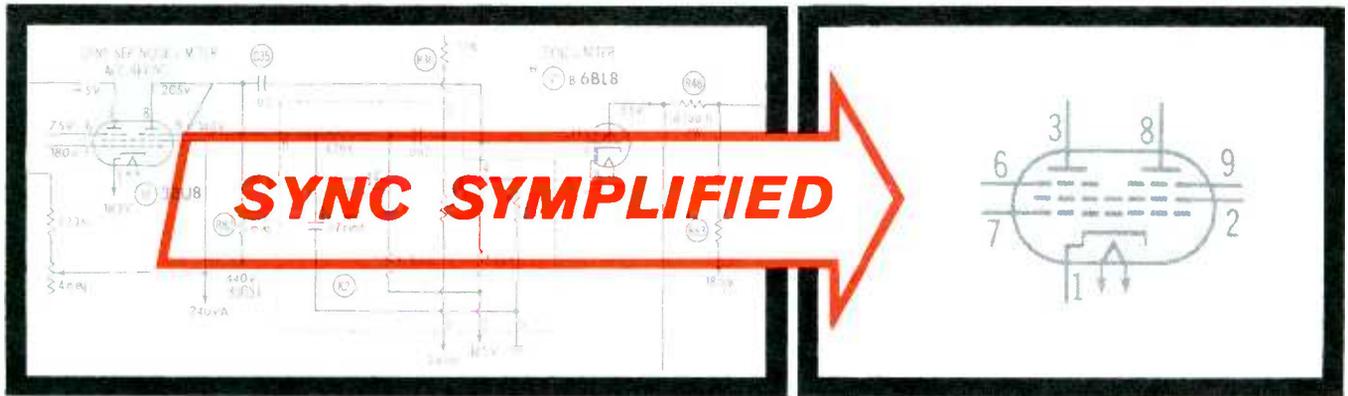

Fig. 6. Example of excessive contrast resulting from loading of AGC line by gassy IF.



Here's an easily understood version of control circuits . . . by Thomas A. Lesh

Troubleshooting in sync circuits is becoming simpler all the time. Most of the late-model sets have just one sync stage, so there is not much circuitry to check, and faults show up quite definitely. But there are still plenty of older sets that have complicated sync circuits, of unique design, and it's a problem to figure out how they should normally work—let alone troubleshoot them. (They must be at least No. 4 on the "headache list" of most technicians—outranked only by horizontal sweep, AGC, and vertical sweep.)

The secret of minimizing such sync problems lies in analyzing the *essential* points of the circuit's operation, and checking the actual signals in the set to see if the sync circuit seems to be carrying out these essential functions.

We can show you what we mean, by describing a recent problem in a 10-year old DuMont Chassis RA-170 (PHOTOFACT Folder 216-2). This set has a total of *five* sync stages, with four of them tied together by a common cathode network (see Fig. 1). The set on our

bench had a wild horizontal jitter and vertical jumping of the picture—quite plainly a sync fault. In the preliminary test, waveforms throughout the sync and video stages were all so jumpy and confused (like Fig. 2, which represents W6) that we knew we wouldn't get far by using conventional test techniques. So, we eased back from the lab bench to do a little pondering.

We decided to see what we could do with DC voltage clues. This isn't our usual way of going at a sync problem, because DC voltages can

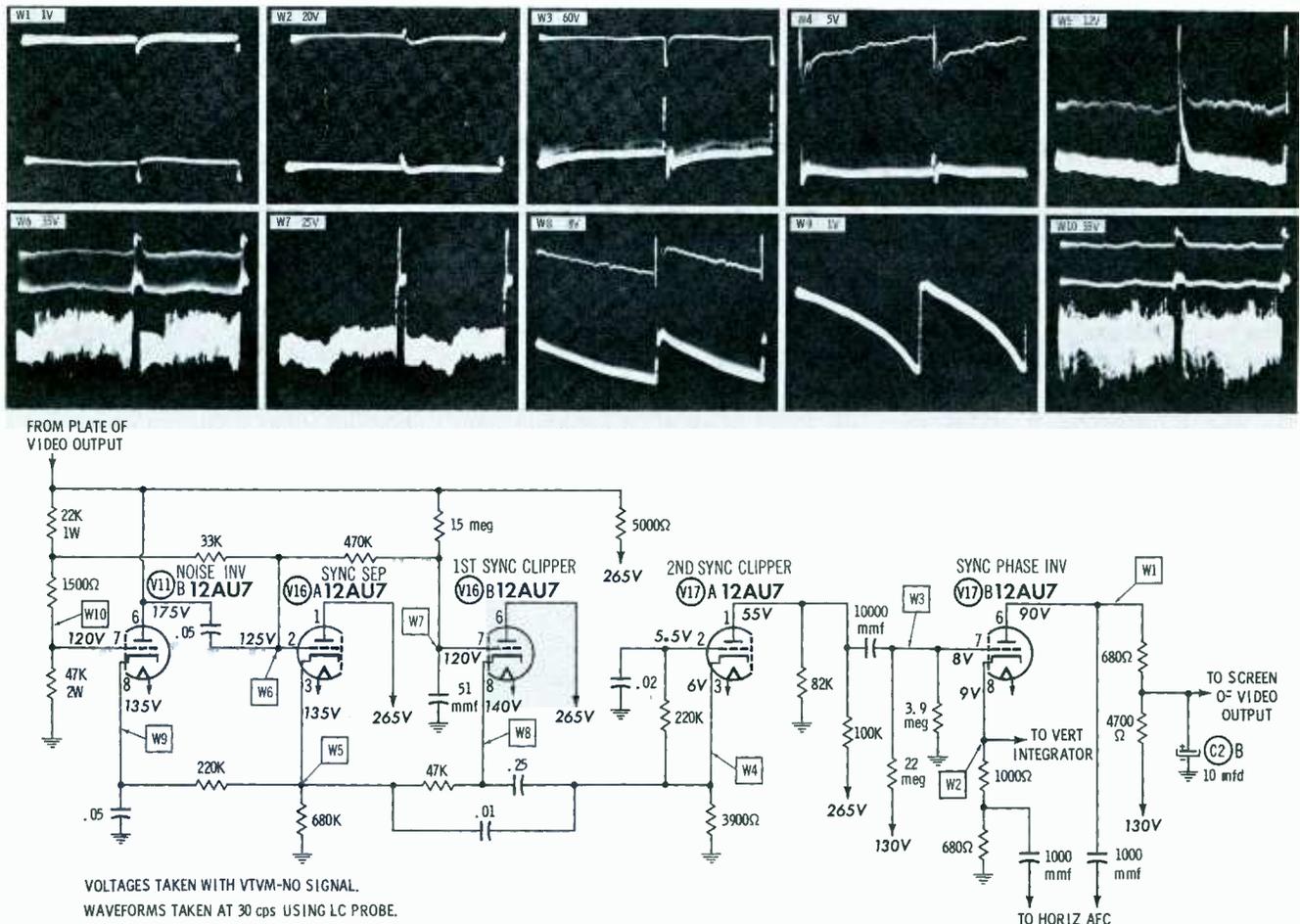


Fig. 1. Five-stage sync circuit in DuMont Chassis RA-170 poses unusually tough problem in trouble isolation.

vary tremendously in sync circuits without causing really significant distortion of the signals. In our experience, trying to find the cause of moderate voltage “discrepancies” usually winds up in a wild goose chase. Nevertheless, there was a chance we might find some really outrageous reading that would clue us in to a dead-shortened capacitor, open resistor, or other clear-cut fault.

But such was not to be. There were only a few voltage readings that aroused any real suspicion, and a few quick resistance checks removed all question of significant voltage errors due to component faults.

What next? Well, after some thought, we decided to consider the AGC system as a possible part of the problem. True, the picture didn't seem overloaded, and there were no other indications of actual trouble in the AGC circuit. But the set had *keyed* AGC leaving room for a “vicious circle” of feedback that could aggravate any existing sync faults. Jittery horizontal sync would cause wild variations in timing of the AGC keying pulses from the horizontal sweep circuits, and erratic conduction of the AGC tube would develop fluctuating bias on the RF-IF stages. This would make hash of the video signal, further aggravating the sync trouble, and so on into desperation.

As an attempt to tie down the feedback loop, we clamped the AGC line, using a variable bias supply. We found that the picture would settle down a great deal if enough AGC bias were applied to reduce the contrast slightly below the normal viewing level. But there was still a definite tendency toward horizontal jitter, even though the vertical hold now seemed quite good; so, some sort of trouble was still present. The signal fed from the video output stage to the keying tube was in good shape now, though a little weak because of the reduced contrast. Also, video waveforms W6 and W10, the inputs to the sync section, now looked normal—again allowing for a little less than ordinary amplitude.

To begin to “box in” the trouble, we followed our usual technique of inspecting the final output of the sync section—W1 at the plate of


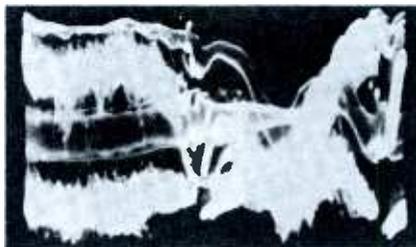



Fig. 2. Sad results of first attempts at scoping signals in sync section to find trouble.

V17B, the sync phase inverter. When we scoped it (Fig. 3A), the vertical sync pulses looked just fine—but that's just about all we could find in the waveform. It showed only an occasional flicker along the base line to suggest that horizontal pulses might be trying to come through, too.


Okay, then: the horizontal pulses were being lost somewhere in that maze of sync circuitry, without great effect on the vertical pulses. This sort of selective distortion happens a lot—quite a bit oftener than you'd think! Our next phase of the job was to make a stab at further localizing the trouble. We weren't even sure, as yet, how to trace the signal path; but we decided to start scoping and taking notes on the waveforms. (At that time, we didn't have the full set of normal waveforms shown in Fig. 1 available for reference.) After accumulating a good

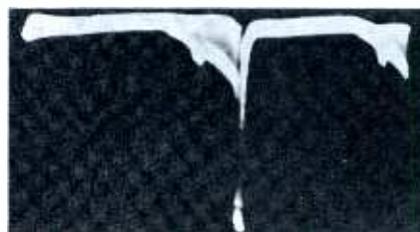

(A) W1 — 12V p-p

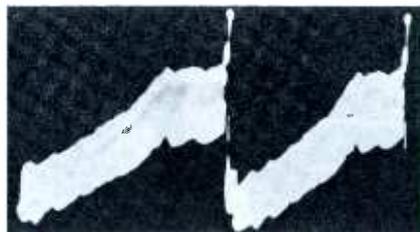

(B) W3 — 50V p-p

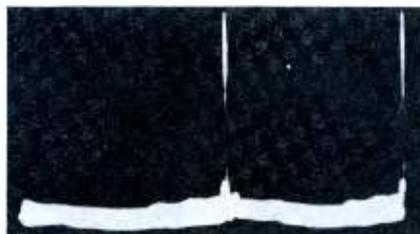

(C) W4 — 3V p-p

Fig. 3. Abnormal signals found on V17.

set of findings, we'd review them and try to draw clues from them. (For instance, we'd ask ourselves: Should the signal at this point really look the way it does?)

Going back to W3 at the grid of V17B, we found a wild-looking sawtooth wave (Fig. 3B). It included good, strong vertical sync pulses, which were being inverted by the stage in normal fashion. (They were not being amplified, but maybe they were not supposed to be.) That ragged mess between the vertical pulses, on the sloping base line, could contain horizontal pulses—but only the last ones in each group were at a high enough voltage level to get through V17B.



Well, back to the plate of V17A. Same thing here as at the following grid—so the interstage coupling circuit must be okay. At the cathode of V17A, there wasn't much but vertical spikes (Fig. 3C). This waveform must be abnormal, since it's so empty of horizontal pulses.

Rather puzzled by the peculiar coupling circuit that goes back to the cathodes of both V16A and V16B from the cathode of V17A, we proceeded to find out what was going on in both sections of V16. On the cathode of the “A” side, labeled “Sync Sep,” there was a video waveform (Fig. 4A) almost as large as W6. That didn't seem right; the stage seemed to be operating like an ordinary cathode follower. No sync separation here!


Now, on V16B's cathode, there was another oddball signal (Fig. 4B). It included prominent vertical pulses, like the output waveform; it also had a sawtooth slope, but in a direction opposite from W3. This waveshape was hard to figure out in light of the label “1st sync clipper” for V16B on the schematic. But things cleared up just a bit when we checked the grid waveform, shown in Fig. 5. This had big, strong vertical pulses, and a very low-level video signal in the spaces between. Apparently V16B was being driven into conduction on just the vertical pulses. The sawtooth slope between pulses in W8 must be just a result of the discharge of the big .25 mfd capacitor at the cathode.

A quick check of V11B didn't reveal much—just normal video at

•Please turn to page 87

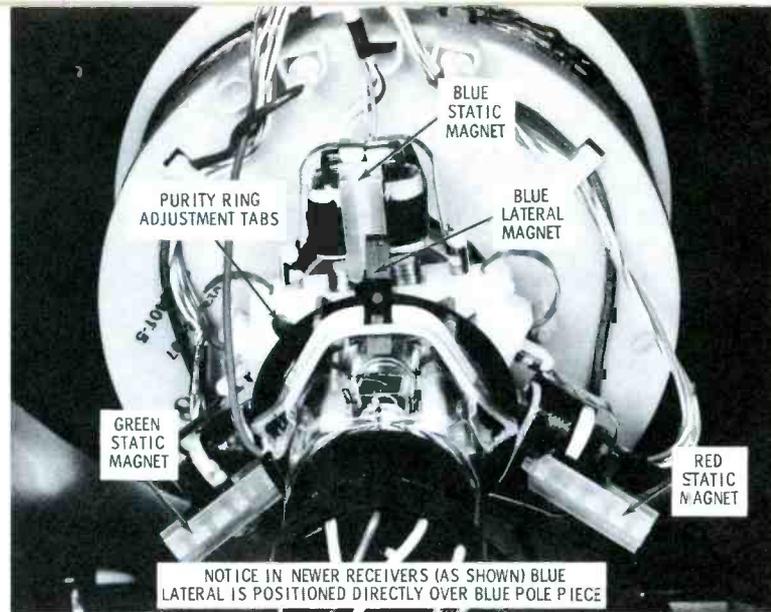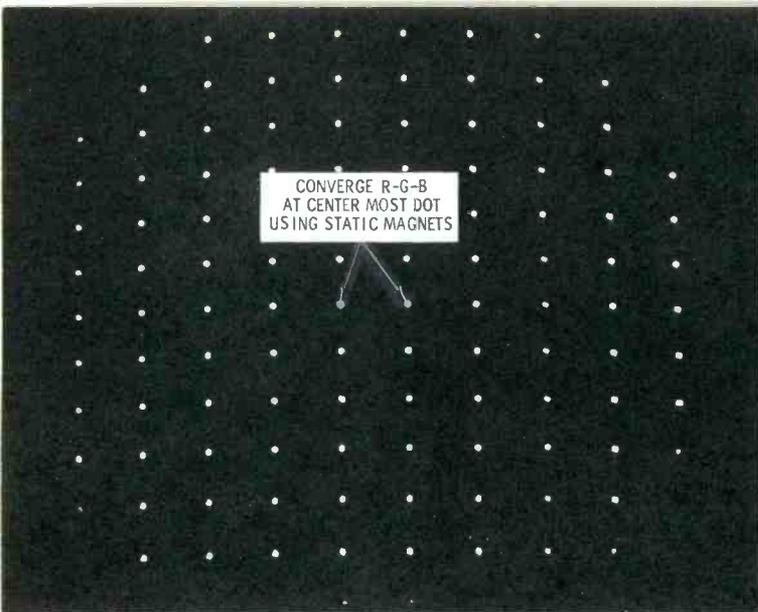


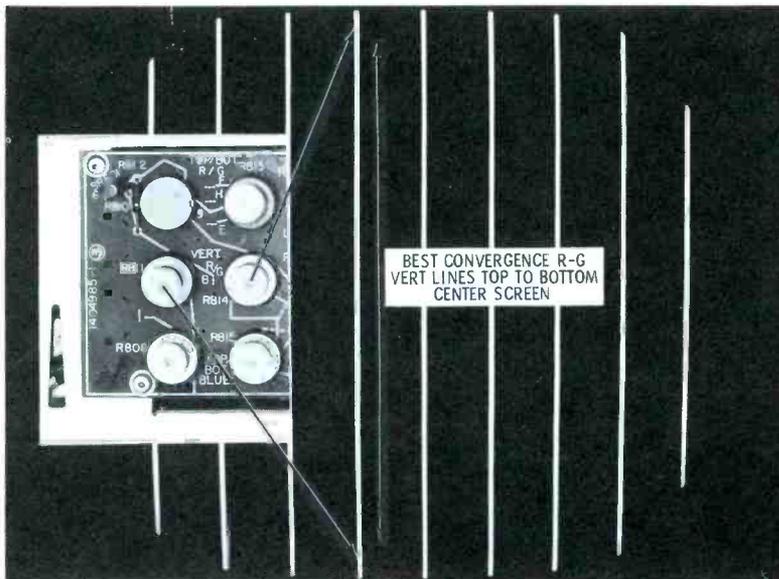Black and white setup procedures, CRT degaussing, and purity checks should be performed previous to convergence. Use the red, green, and blue magnets and the lateral magnet for center dot convergence.




Use R-G vert lines top (Master Tilt) and R-G vert lines bottom (Master Amp) to converge the vertical red and green lines top to bottom center screen.

ABC's OF

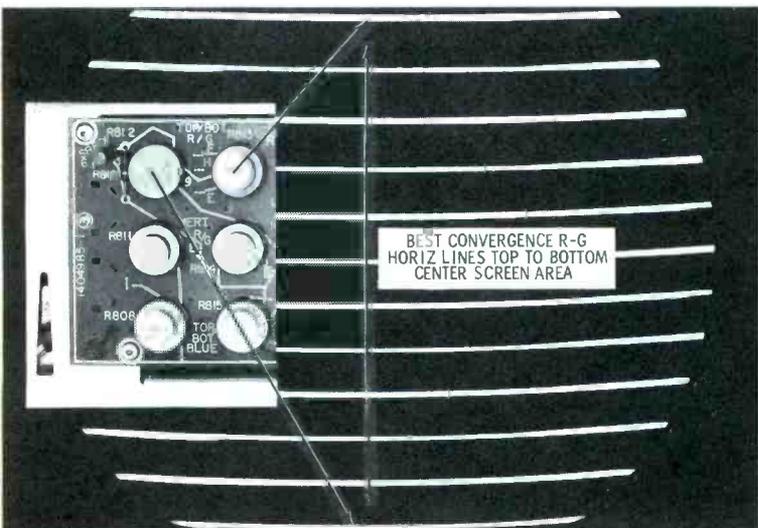

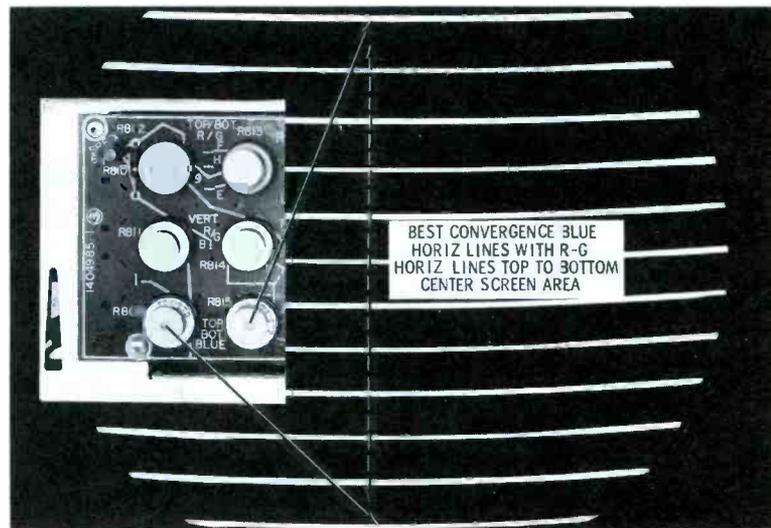Use R-G horiz lines top (Diff Tilt) and R-G horiz lines bottom (Diff Amp) to converge red and green horiz lines top and bottom at the center of screen.



Use Blue horiz lines top (Blue Tilt) and Blue horiz lines bottom (Blue Amp) to converge blue horiz line with red and green lines at the center of the screen.




Use the R-G vert lines right (R-G-1) and R-G horiz lines right (R-G-2) to converge red and green vert and horiz lines at the right center screen area.






Use the R-G vert lines left (R-G-3) and R-G horiz lines left (R-G-4) for convergence of the red and green vert and horiz lines left center screen area.

CONVERGENCE

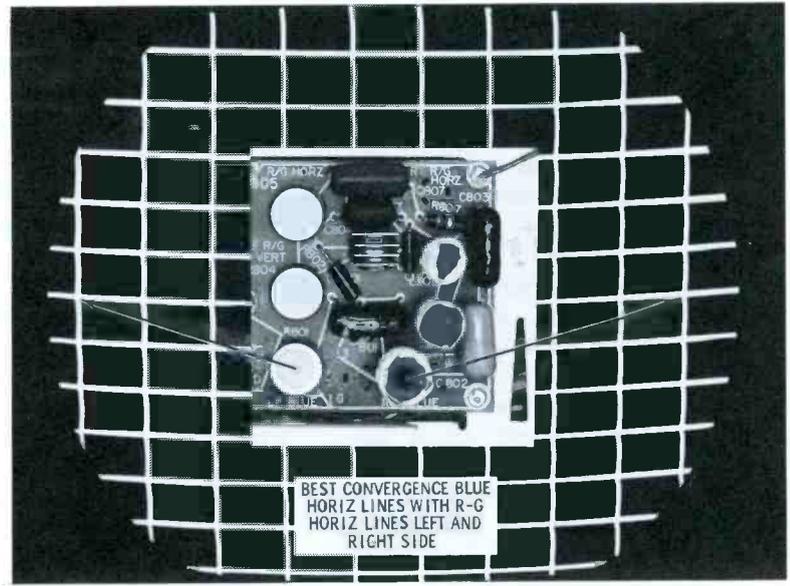

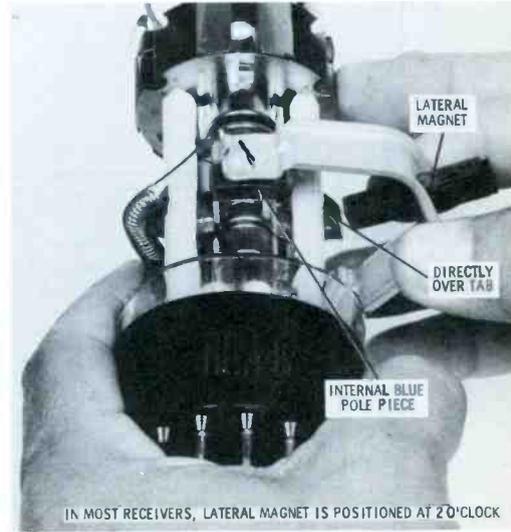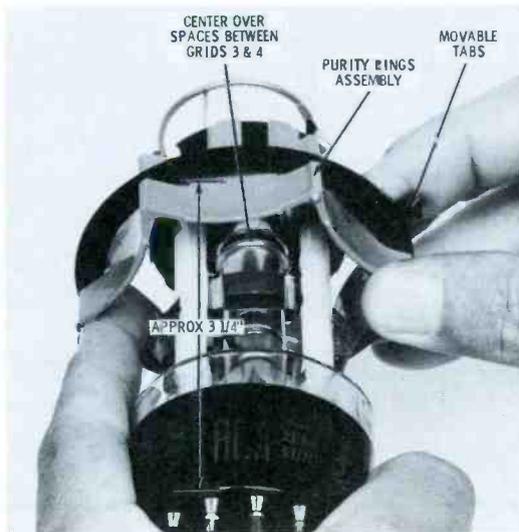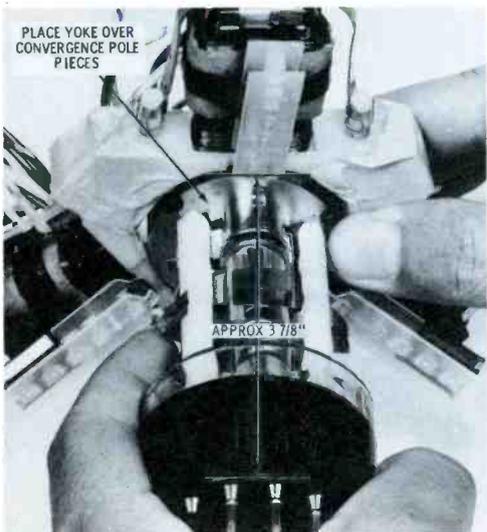Use the blue horiz lines right (B-1) and blue horiz lines left (B-2) to converge blue horiz lines with red and green at the left and right center area.



Poor convergence may result from improperly positioned elements; convergence yoke directly over pole pieces $3\frac{7}{8}$ " from CRT base, purity ring $\frac{5}{8}$ " rearward, and the lateral magnet over internal pole piece.

curing aircraft radio troubles

Part 1



Radio communication plays a vital part in modern aviation. At large airports, airplanes are controlled prior to flight by special ground communication channels. Airport towers control takeoff and landing by radio, and other special channels are used to maintain contact during the flight.

In the early days, aviation radio communication was carried out in the band from about 180 kc to 450 kc. Sections of this band are still reserved for aviation and marine radio and are classified as low frequencies. Emissions at these frequencies are characterized by strong ground waves which are best suited for radio direction finding. These low frequencies are not limited to line-of-sight communication; in fact, powerful very-low-frequency stations are used to transmit ground-wave signals around the world. Some airport towers still transmit at low power in the LF band for traffic control in emergencies or for aircraft equipped only with an LF receiver.

"Radio range" and so-called "beacons" are an important part of aircraft navigation, and these devices account for most of the use of the LF aviation frequencies. Beacons are low-powered omnidirectional transmitters which continuously transmit an identification code and which are accurately located on the pilot's aeronautical chart. The directional loop of the plane's navigational system locates this radio-signal beacon.

HF Communication

It should be noted that LF transmitters are no longer used aboard aircraft. One obvious reason for this is that it would be impossible to devise an antenna long enough to be efficient at low frequencies. At 3 mc and above, however, antenna dimensions come within the range useable for airborne transmitters. Several years ago, a wire was trailed behind an airplane for communication in the high-frequency band (the frequencies from 2 to 30 mc). This method is now seldom used, and ingenious antenna systems are required in order to provide HF communication aboard highly-streamlined aircraft which can no longer tolerate external wires.

High-frequency sky waves readily reflect from ionospheric layers. Radio amateurs pioneered long-distance HF communication by means of "skip" in the years between World War I and World War II when the HF bands were referred to as "short waves." During the thirties, HF was the primary means of both airport-tower and long-distance communication. Today, HF is used primarily for long-distance communication either for over-water routes or as a means of company communication between an airplane and its home base.

There is one important exception to the preceding statement. After World War II, and before the development of suitable VHF equipment, many private airplanes were

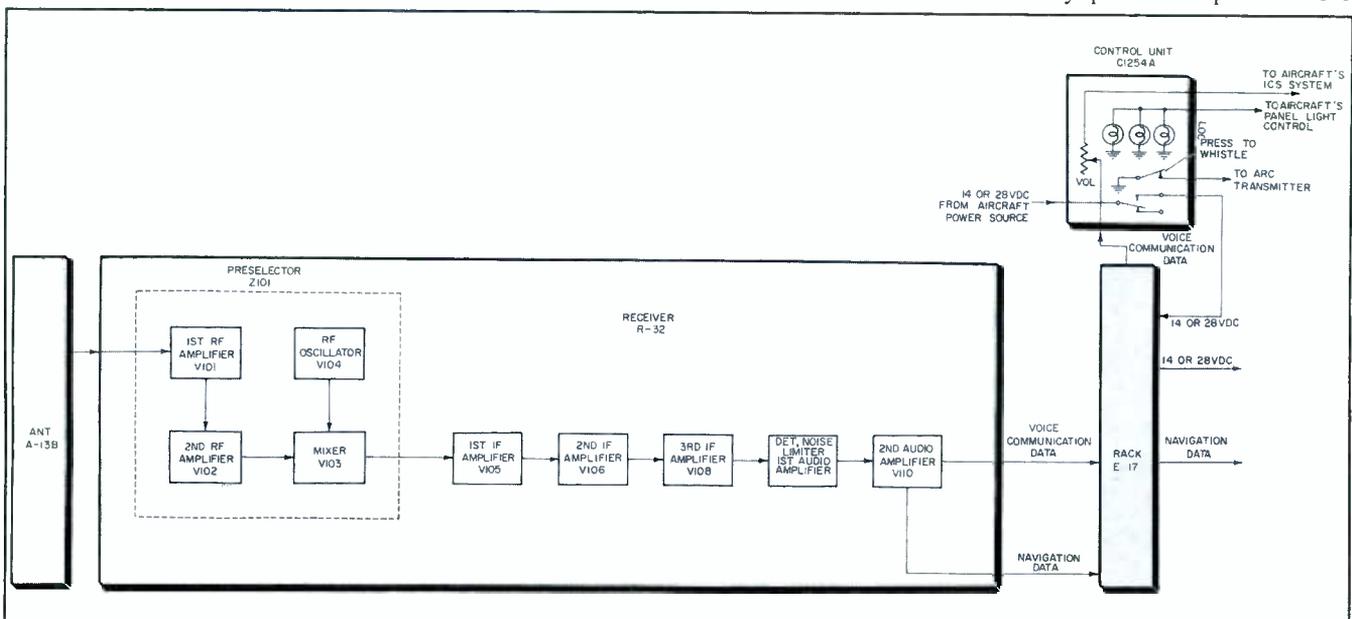


Fig. 1. Block diagram of a continuously tuned VHF-AM superheterodyne aircraft receiver.

Introduction to equipment used in airborne communications.

by Keith Bose

equipped with low-power HF transmitters for tower communication. The FCC now sets aside 3023.5 kc to provide contact with airport towers for landing and other instructions using transmitters developing a fraction of a watt. Reception in the airplane is usually on the LF band on frequencies around 270 kc. Although transistors now make possible very inexpensive LF-HF transceivers, there is little interest in such equipment at the present time.

In order to provide continuous long-distance HF communication utilizing the skip effects of the ionosphere, it is necessary to change frequencies as changes occur in the ionosphere. Correct frequencies can be predicted and assigned in advance, but this means that HF equipment must be designed to operate at several different frequencies. Several years ago, trained radio operators were carried aboard most long flights, and these crew members were responsible for tuning and operating HF equipment which greatly resembled the designs used on the ham bands. Today, however, equipment is tuned by the pilots. Efficient antenna loading is obtained by a servo loop which automatically obtains an optimum standing-wave ratio. Combinations of crystals are switched to derive desired frequencies, and servo loops are employed to tune the various resonant elements.

VHF Systems

The use of HF for routine air-ground communication in the face of unusual ionospheric reflections

could conceivably contribute to dangerous situations. Moreover, high frequencies require long antennas, and crowded bands necessitate the best possible receiver selectivity. For air-ground work, a radiation pattern which affords positive reception at all points except those beyond a certain radius of interest would be ideal; this would allow operation on the same frequency at distant, unrelated points. The behavior of radiations at *Very High Frequencies* meets these requirements. Since power to VHF is more efficiently propagated from aircraft antennas to the ground station, less power is required. Also, more channels are available in the VHF range. Because VHF is limited to horizon-distance transmission, there is little interference, although an airplane at 20,000 feet has a VHF range of 200 miles if sufficient power is used. By the use of remote, centrally controlled VHF ground stations along airways, it is possible for airplanes to remain in constant touch with Air Traffic Control by VHF.

By the end of World War II lightweight VHF equipment became commercially available. The VHF band now set aside for aviation use extends from 108 mc to as high as 152 mc. The area between 108 mc and 118 mc is used for VOR, or omnirange, navigational ground stations. Most aircraft transmitters operate between 118 and 135 mc.

Localizers (ILS) and low-powered terminal VHF omni stations (TVOR) are assigned frequencies

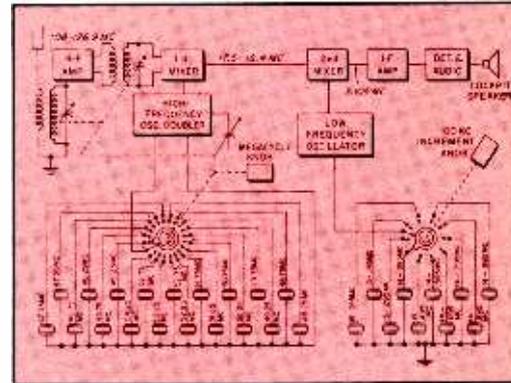


Fig. 2. Block diagram of a crystal-tuned VHF receiver in which frequency synthesis is used.

between 108 and 112 mc. The more powerful enroute VOR stations operate from 112 to 118 mc. VHF communication frequencies run from 118 to 135 mc and are now assigned in increments of .05 mc. Frequencies from 118 to 121.4 mc include towers, departure control, etc. The frequency 121.5 mc is the universal emergency frequency isolated on either side by a 100-kc "guard band." 121.7, 121.8, and 121.9 mc are used for airport ground control. FCC assignments are tabulated in Table 1.

VHF Receivers

Receiving equipment for VHF may be classified as either continuously tuned or crystal-tuned. Continuously tuned equipment is capable of receiving any frequency within its range, and it is usually the least expensive. Crystal-tuned receivers allow quick, positive tuning which is worth a lot in many flight situations.

Circuits of continuously tuned re-
 • Please turn to page 96


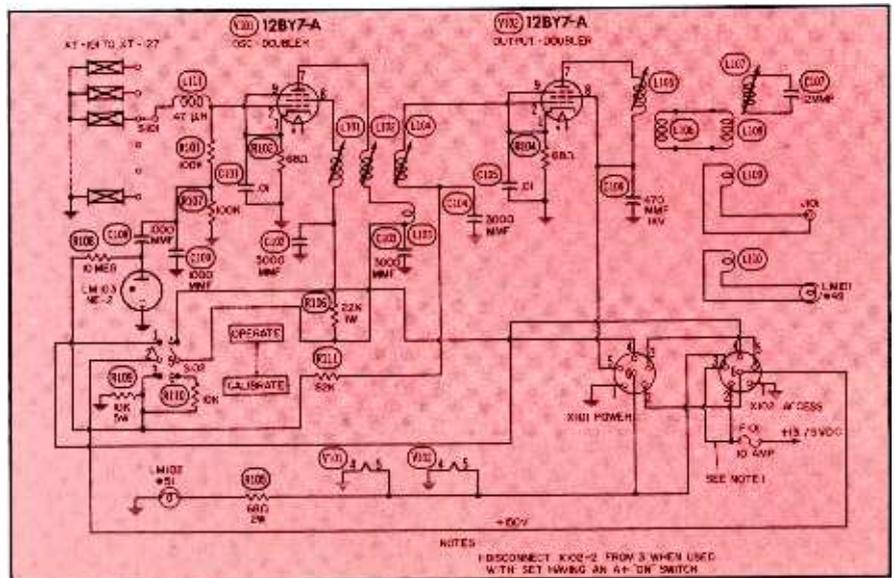


Fig. 3. Schematic of VHF transmitter. Separate modulator and power supply are required.

SOLID STATE RECTIFIERS come of age

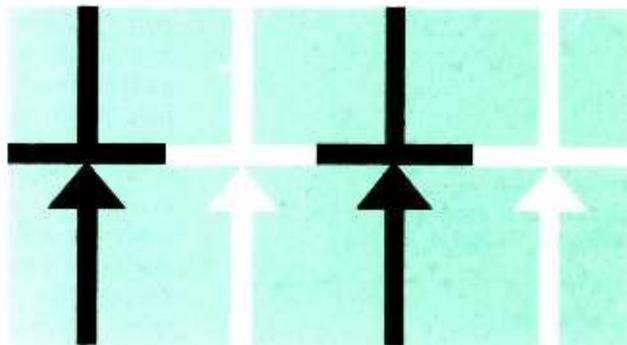

For many years, radio and television servicemen have been accustomed to servicing receivers that use selenium rectifiers to change AC power-line voltages to DC potentials. Technicians working on heavy-duty electronic equipment are also familiar with copper oxide rectifiers used to rectify heavy currents. These devices have been commonly referred to as metallic rectifiers, because one side of each rectifying junction consists of a metal disc or plate.

More recently, it has been discovered that devices made of other elements, such as the semiconductors silicon and germanium, also display the ability to conduct in only one direction—if the elements are mixed with slight amounts of impurities. And along with these developments has come a new terminology; metallic and semiconductor rectifiers are called *solid-state* devices, to distinguish them from those rectifiers of open-element construction—such as vacuum and gaseous tube rectifiers.

There are a large number of solid

state devices—including transistors, tiny signal diodes, bulky silicon rectifiers for heavy duty, and other special devices such as thermistors, thyrectors, *Varicap* diodes, and silicon controlled rectifiers. There are even solid state relays to replace electromechanical types. For the present, we're most interested in rectifiers, those solid state devices that possess the characteristic ability to change AC to pulsating DC.

The Power Race

Always, design engineers have been looking for ways to increase the efficiency of rectifiers. The discovery of new techniques for creating semiconductor junctions, and new materials to use, has triggered significant advances in this area. The use of silicon has permitted manufacture of rectifiers that match selenium units for power-handling capability, but are only a fraction of the physical size. Even the cost has been reduced considerably.

For extremely heavy-duty rectifier systems, such as industrial battery chargers, copper-oxide rectifiers are still being used. To date, they are less expensive than other units; one serious limitation, however, is that they can economically be used only with low voltages. Consequently, solid state rectifier packs are becoming preferred, and will probably replace metallic units completely.

Selenium units, too, are still being used in many rectifier systems. Where high current is not a requirement, and operating temperature is not important, seleniums are generally less expensive. Low-current silicon rectifiers are not common, for other materials lend themselves better to low-current applications. For current requirements above 200 ma, silicons are rapidly replacing seleniums, for two reasons: Silicon rectifiers often achieve operating efficiencies approaching 98%, while equivalent selenium units are only 65% to 75% efficient; besides this, the characteristics of seleniums change during an extended period of operation, while those of silicons are comparatively constant throughout their life.

There are disadvantages to silicons that partially account for the fact that seleniums are still in extensive use. Silicon units are not as capable of withstanding temporary overloads as are seleniums. Power line surges, transient load changes, and spurious voltage "spikes" that have little effect on a selenium may destroy a silicon junction. Thus, some equipment manufacturers use the less sensitive selenium unit in preference to building surge protection into the circuit for silicons.

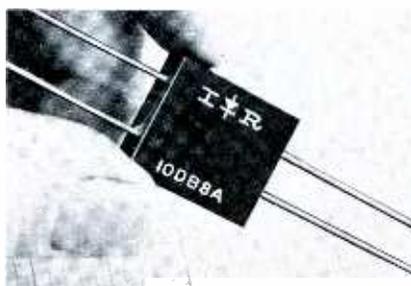


Fig. 1. Large bulky seleniums have been displaced by smaller-size silicon rectifiers like these.

More and more, however, the advantages of silicon rectifiers are outweighing those of seleniums, and set builders are switching to silicon power supplies.

Silicon Devices

A significant number of different solid state units use silicon as the primary material. These include plain silicon rectifiers of many styles, shapes, sizes, and ratings; silicon controlled rectifiers; silicon planar diodes; and silicon zener diodes. Silicon junctions have the advantage of being able to withstand greater voltage surges than those of germanium, notwithstanding their susceptibility to damage from voltage extremes. The low junction temperatures in silicon units (compared with selenium) permit higher current ratings and lesser cooling requirements. Thus, devices made of silicon are "middle class" in the society of solid state devices. And they have extreme versatility.

Silicon Rectifiers

As mentioned above, many styles, shapes, and sizes of silicon rectifiers are available. These characteristics are determined largely by the power ratings—current capability versus operating voltage. Some units are stud-mounted in heat sinks; others mount simply by axial leads; still others are press-fitted into heat sinks. In some small units, the heat sink is merely a single fin around one end of the unit—giving the familiar "top hat" appearance. Other types, without built-in heat sinks, are fuse-clip types, epoxy-impregnated types, and cylinder types (single-ended or axial). See Fig. 1.

In ratings, silicon rectifiers range from tiny encapsulated units, capable of handling currents between 5 ma and 750 ma, to large stud-mounted ones that can handle up to 250 amps. Voltage ratings usually begin around 5 or 6 volts (although .5 volt is about the minimum practical voltage for a silicon unit) and range as high as 1000 volts rms.

The actual current that can be expected from a silicon rectifier supply depends on the type of load placed on the supply. An inductive or resistive load can demand almost 50% more current from a silicon unit than can a capacitive load. Thus, a unit rated at 750 ma for an inductive or choke-input filter system can sup-

ply only 500 ma into a capacitor-input filter network.

This brings up the matter of protection for silicon rectifiers. There are three major areas of common failure in these units: voltage overload, too-high operating temperature, and too much current. The first can be, and usually is, eliminated by proper circuit design; a circuit that is too inductive often creates this problem by forming transient pulses that overload the forward or reverse rating of the unit. The second is the result of poor cooling, and is a factor that can be eliminated by careful selection of case style for each application; if heat sinks are needed, they must be provided.

The third problem is of much more importance to you, particularly when you replace silicon units or substitute them in place of selenium rectifiers. This problem is a result of initial surge current. For comparison purposes, solid state rectifiers in the silicon class are rated at an operating potential of 1 volt forward bias.

Semiconductor junctions will conduct only after a certain minimum forward bias voltage is exceeded; for most, this point is just above .5 volt. Above this point, junction resistance may be only 2 or 3 ohms; at 150 volts, the resistance is only a few thousandths of an ohm. Consequently, series resistance is needed to limit the current to a reasonable value during the peak excursion of each forward cycle. Why doesn't the load resistance prevent overcurrent? Because we are talking about a capacitor-input filter. Until the capacitor accumulates a charge, it acts as a short across the output of the rectifier—during the first cycle after power is applied.

Let's compute the size of the lim-

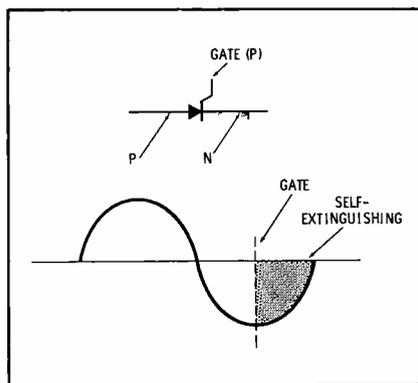


Fig. 2. SCR gate junction is control element.

iting resistor. The instantaneous voltage at the peak excursion of a 130 volt AC power line (the maximum likely to be encountered) is almost 184 volts. As an example, consider a silicon rectifier that has a capacitor-input current rating of 500 ma. A typical unit might be rated to withstand a surge current of 25 amps for 1/120 second—one half-cycle at power line frequency. The protective resistor for this rectifier would have to drop the 184 volts to no more than 1 volt, for that instant, if it is to protect the rectifier. Using Ohm's law, divide 184 by 25; the result is 7.5 ohms—the value of the surge resistor.

Another common rectifier has a surge rating of 35 amps for one half-cycle at 60 cps. Ohm's law would indicate a need for a surge resistor of 5.25 ohms.

Since the surge across the resistor takes place during only 1/120th of a second, at the instant when power is first applied, the wattage requirement is much less than you might suppose. To compute the wattage dissipated during the surge, you would multiply the voltage by the current, and then multiply the resultant by the duty-cycle factor of 1/120. In our first example, this would indicate an instantaneous dissipation of 40 watts. But remember that it is *instantaneous*. The actual wattage of the resistor should be chosen according to the constant demand of the power supply, in this case not to exceed 500 ma (the rectifier rating). Computing power, we find a constant dissipation of about 2 watts. Allowing a safety margin, you'll find a 5 watt resistor sufficient.

Silicon Controlled Rectifiers

You've seen how silicon rectifiers are used and protected from overload; now, let's look at a close cousin—the silicon controlled rectifier. This rectifier is a multijunction device that is actually a triggered rectifier. If you're familiar with thyatron tubes, you can compare the action of the SCR to that of the thyatron.

The junction primary in the SCR is very similar to that of the ordinary silicon rectifier. However, the SCR contains another junction designated as the *gate*. The unit cannot function as a rectifier until this gate is

• Please turn to page 93



TECHNIQUES OF Distortion CHASING

each particular transistor; one pitfall of this system is that not all transistors of a particular type operate the same, even with the same bias. The second method—substituting an adjustable bias voltage and setting it for linear operation—has the advantage of *showing* an immediate and definite result; besides, only a general knowledge of bias values is needed.

Measuring Bias

To set the stage for our dynamic techniques of troubleshooting distortion problems, let's first take a look at the two ways bias is measured.

Fig. 1 shows an audio stage using a PNP transistor. Bias can be measured by a sensitive voltmeter connected between the base and emitter as shown in Fig. 1A. The voltmeter, preferably a VTVM, must be able to indicate voltages as small as a few hundredths; some transistors operate with less than .1 volt bias. Fig. 1B shows another way to determine bias on a transistor—by measuring the voltage at the emitter and then at the base; the difference between the two readings is the bias voltage.

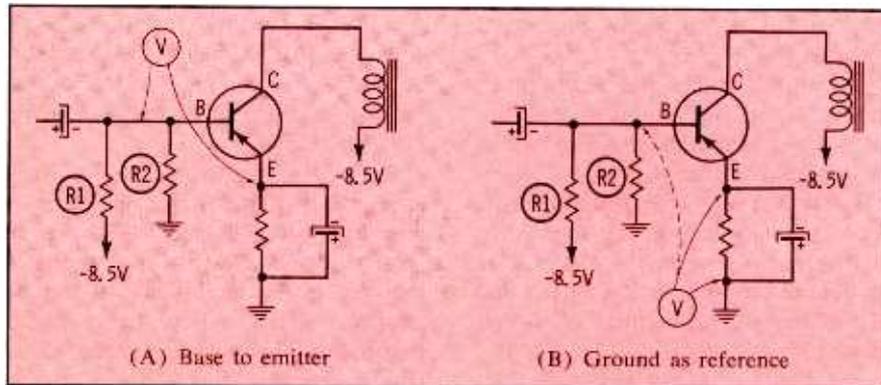


Fig. 1. Methods of measuring transistor bias.

It can be generalized that distortion in transistor receivers and audio amplifiers is the result of some defect that upsets bias in an audio stage. It naturally follows, then, that distortion in these units can be cured by correcting the bias problem. Carrying this logic a step further, we can assume that if altering the bias on an audio stage clears up any distortion we hear (or see, with a scope) the fault must lie within that stage. It matters not from a standpoint of troubleshooting, whether we clear up the distortion artificially—by supplying the correct bias from some external source—or

in the usual manner by replacing the defective component. Naturally, the latter is too time-consuming and parts-wasting to be practical as a troubleshooting procedure.

Let's examine this idea from another viewpoint. We can consider two methods of finding in which stage distortion originates: by measuring voltages on each transistor or by artificially altering the bias in each stage until one of them clears up the faulty sound emanating from the speaker. The first method—measuring voltages—makes it necessary for the service technician to know in advance the correct bias for

Developing Bias

Next, let's examine how bias is normally applied to transistor stages. We can still use Fig. 1 as an example.

The emitter voltage is primarily a function of total collector current, although a very insignificant amount of base current affects it. The base voltage is determined by divider resistors R1-R2 connected across the main power supply. The ratio of R1 to R2 sets the amount of the supply voltage that is applied to the base of the transistor. Base-emitter current in this PNP unit also has some effect on the final value of base voltage, so the operating value may vary slightly different from that computed by the mathematical ratio of R1:R2. Nevertheless, the ratio is a usable clue to the approximate value to be expected.

A similar biasing system is shown in Fig. 2A; the divider system is connected in this stage directly across the collector supply. In Fig. 2B, a still different arrangement is used, but the divider principle remains. You'll find that base-biasing arrangements in most transistor audio

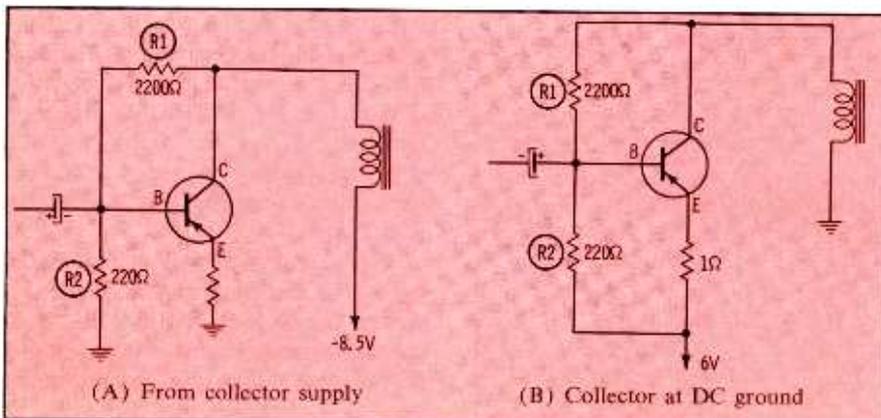


Fig. 2. Here is how bias is derived for base.

• Please turn to page 47

TWO NEW HIGH-PERFORMANCE CB TRANSCEIVERS FROM LAFAYETTE... *Leader In CB Equipment*

NEW! LAFAYETTE 23-CHANNEL CRYSTAL-CONTROLLED DUAL CONVERSION 5-WATT CB TRANSCEIVER



Model HB-400
169⁵⁰

With Advanced "Range-Boost"

- ✓ Ruggedly Built For Reliable 2-Way Radio Communication
- ✓ Easy To Use... Easy To Maintain. With Every Feature CB Users Want!
- Frequency Synthesis Offers 23 Crystal Controlled Transmit/Receive Channels—No Extra Crystals Needed!
- "Range-Boost" Circuit for Increased Sideband Power... Greater Range!
- 17-Tube Performance With 13 Tubes
- Low Noise Nuvistor "Front End"
- 5 Double-Tuned IF Transformers
- Sensitive 3/10 μ V Dual Conversion Receiver
- Built-in 117V AC & 12V DC Power Supply
- Plug-in Facilities For Lafayette Selective Call Unit ■ Imported

NEW! LAFAYETTE ALL-TRANSISTOR DUAL CONVERSION 5 WATT CB TRANSCEIVER With Mechanical Filter For Ultra-Sharp Selectivity

- ✓ 100% Solid-State... Full 5-Watt Performance!
- ✓ 11 Rugged Silicon Mesa Transistors Used In Critical Areas
- ✓ Small, Compact—Only 3" High!
- ✓ Low Battery Drain—Less Than 350 ma on Receive, 850 ma on Transmit!

- 12 Crystal Transmit & Receive Positions
- 23 Channel Tunable Receiver with Spotting Switch
- 15 Transistors, 5 Diodes
- Sensitive 5/10 μ V Dual Conversion Receiver
- Variable Squelch, plus ANL
- For 12V DC, or 117V AC with Optional Solid State AC Power Supply ■ Imported



Model HB-500
139⁵⁰

**Dealerships
Now Available for**

LAFAYETTE'S NEW "HOT-LINE"

Lafayette Radio Electronics, "World's C.B. & Electronics Center" has available dealerships for its new "Hot Line" of Citizens Band equipment. A leader in the C.B. field, Lafayette equipment has been performance proven and customer accepted.

Lafayette is now introducing its new C.B. "Hot Line" etc. Engineer-designed, precision-crafted and field-tested to make Lafayette THE NAME in Citizens Band.

Be the first one to hook-up with Lafayette's

NEW "HOT-LINE."

Get complete information without obligation—mail the coupon today.

LAFAYETTE RADIO ELECTRONICS CORP.
Dept. ASPF1-4
111 Jericho Turnpike
Syosset, L. I., N. Y. 11791

Mr. Robert Laub:
Please send me full information on how I can become an exclusive Lafayette dealer. I understand there is no obligation.

Name

Address

City


State

Zip

Here's the **NEW** Jensen Electronic Musical Instrument Concert Series Loudspeakers

Jensen electronic musical instrument loudspeakers are highly special devices designed to give (1) exactly the correct musical quality or "voicing" required for the particular instrument; (2) the power capability to reproduce the characteristic wave shapes of the instrumental notes without distortion at loud volumes, and (3) unprecedented ruggedness for unusually long life under the severe peak load conditions imposed in these demanding applications. All designs are new and are based on recent research and development culminating our years of experience as the original and predominant source of speakers for musical instruments. Among the many features which insure better performance and trouble-free service are (1) special voice coils with high temperature enamel coatings and phenolic bobbins for dependable high power operation, epoxy cemented for permanent adhesion to the radiator; (2) formed, flat-sheet specially-processed fibre cone material which is extra stress resistant and immune to sub-harmonic breakup; (3) unique elastomer edge treatment to resist cracking; (4) breakage-proof leadout connections that multiply service life; (5) higher efficiency SYNTAX-6[®] magnet material.

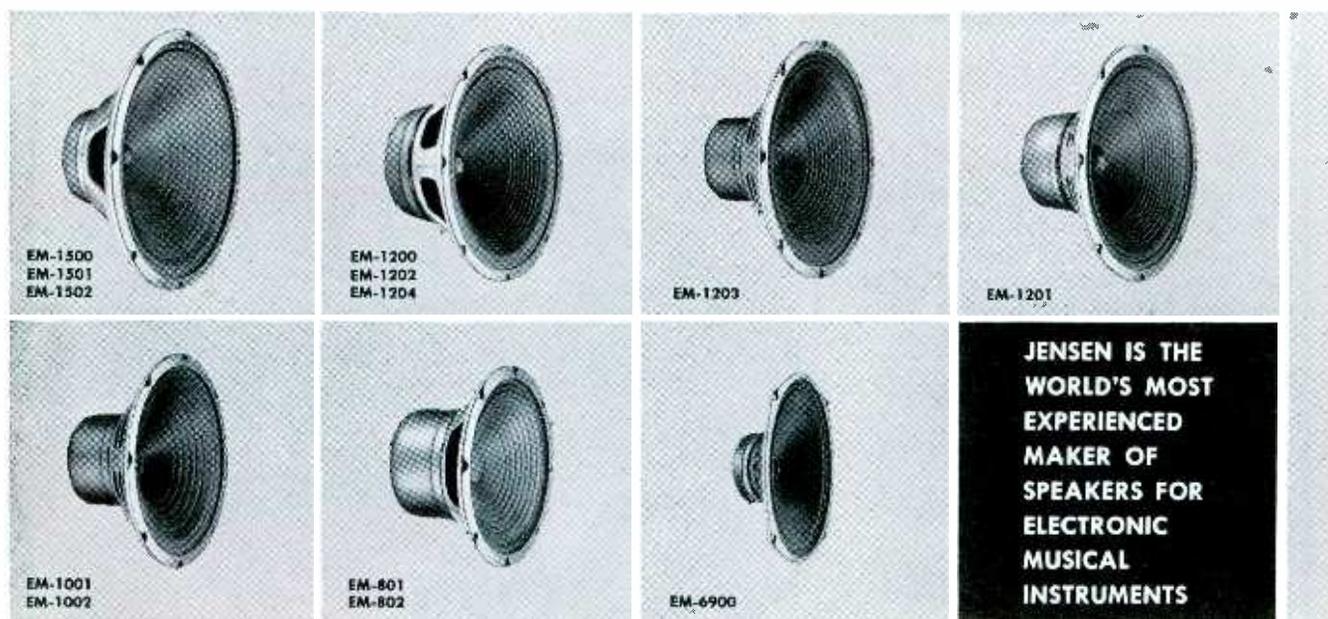GET THE COMPLETE JENSEN CONCERT SERIES STORY—SEND FOR CATALOG 1090




Type	Nominal Size, Inches	List Price	Model Number	Magnet* Wt. Oz.	Voice Coil			Dimensions, Inches		
					Imped. Ohms	Power Watts**	Dia. Inches	H & W	Depth	Baffle Opening
Bass Guitar	12	\$35.95	EM-1200	16	8	50	1½	12¼	6¼	10½
	15	52.00	EM-1500	27	8	60	1½	15¼	7	13¼
Guitar	8	19.95	EM-801	10	8	25	1	8¼	4½	6¼
	10	21.50	EM-1001	10	8	30	1	10¾	5¼	8¾
	12	29.50	EM-1201	11	8	40	1¼	12¼	6½	10½
	12	35.95	EM-1202	16	8	50	1½	12¼	6¼	10½
	15	52.00	EM-1501	27	8	60	1½	15¼	7	13¼
Accordion	12	35.95	EM-1202	16	8	50	1½	12¼	6¼	10½
	15	52.00	EM-1501	27	8	60	1½	15¼	7	13¼
Organ	6 x 9	14.75	EM-690G	10	8	12	1	6¼ x 9¼	3	5¼ x 8½
	8	19.95	EM-802	10	8	15	1	8¼	4½	6¼
	10	21.50	EM-1002	10	8	18	1	10¾	5¼	8¾
	12	22.50	EM-1203	10	8	20	1	12¼	6¼	10½
	15	52.00	EM-1204	16	8	25	1½	12¼	6¼	10½
			EM-1502	27	8	30	1½	15¼	7	13¼

*All models have Syntox-6[®] ceramic magnets. **Program power. Peak power is twice program rating.

JENSEN MANUFACTURING COMPANY / DIVISION OF THE MUTER COMPANY / 6601 SOUTH LARAMIE AVENUE, CHICAGO 38, ILLINOIS
Canada: Radio Speakers of Canada, Ltd., Toronto • Argentina: Ucoa Radio, S.A., Buenos Aires • Mexico: Fapartel, S.A., Naucalpan, Mex.

Circle 75 on literature card

How to deliver the best signal...

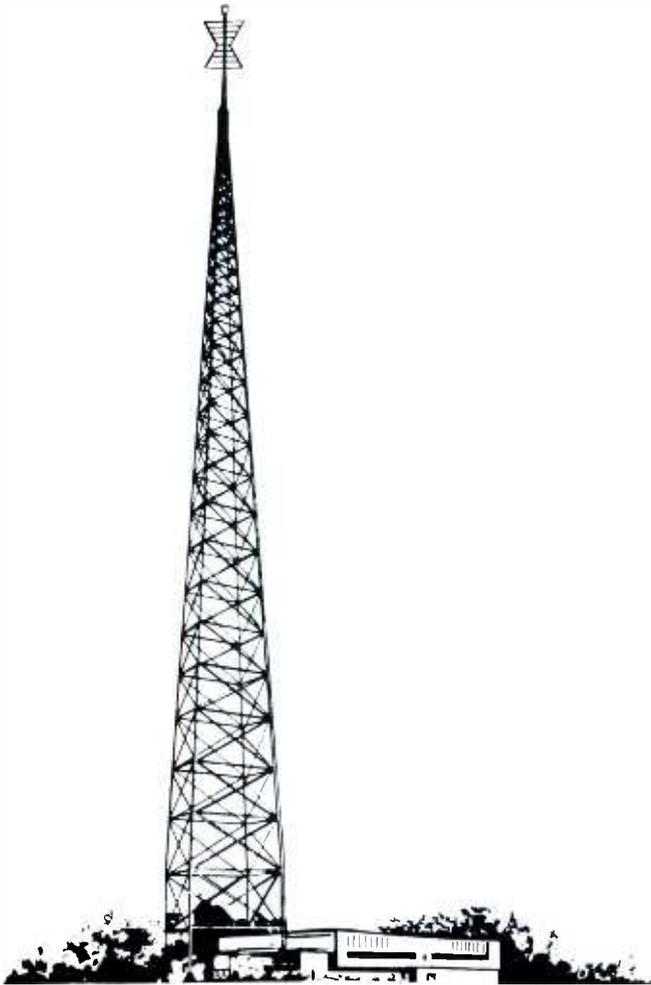

from here...



to here

BLONDER-TONGUE leader in UHF and VHF product design
dedicates Fall, 1964 to better TV reception with the

BLONDER-TONGUE VAL·U·RAMA

How TV signal amplifiers improve reception

by Ben H. Tongue

(President, Blonder-Tongue Laboratories)



TV amplifiers can improve TV reception in many cases. There are, however, situations where no improvement is to be expected. This article will cover both situations to help you recognize potentially profitable installations.

Amplifier performance is determined by the level of internally generated noise (snow), amplification level, and degree of freedom from overload by strong local signals. Amplifiers are used as follows:

1. INCREASE CONTRAST Low cost TV sets generally have insufficient gain for weak signal reception. Old TV sets (low or high cost) often have aged tubes and insufficient gain. Low gain generally is the cause of poor contrast on weak signals. If the contrast of "snow" when the TV set is operating at full gain (no signal input) is much less than picture contrast on a strong signal, low gain is at fault. A good amplifier, indoor or outdoor, will improve poor contrast caused by low gain. Contrast is reduced if the transmission line from antenna to TV set has a high loss. Noise (snow) is also increased by this condition. Let us assume that a good antenna is well installed and that quality transmission line is used (flat twinlead for VHF and round foam-filled twinlead for UHF).

TABLE 1	FREQUENCY	Length for 3db Loss	
	Low Band VHF (Ch 3-6)	50' Wet	300' Dry
	High Band VHF (Ch 7-13)	26' Wet	158' Dry
	Low Half UHF (Ch 14-48)	45' Wet	90' Dry
	High Half UHF (Ch 49-83)	37' Wet	74' Dry

2. REDUCE SNOW Snow appears when the TV signal-to-noise ratio is reduced. A good antenna reduces snow because of increased signal pickup. Transmission line loss increases snow because it reduces the signal reaching the first amplifier stage (booster or tuner RF stage). This reduces the signal-to-noise ratio. Here's how snow can be minimized:

- Increasing signal pickup by using a higher gain antenna.
- Using an amplifier which generates less noise than the TV input stage.
- Amplifying at the antenna. If the amplifier has the same noise figure as the TV set tuner, the amplification overcomes transmission line loss, and the picture signal-to-noise ratio is nearly the same as if the TV set were at the antenna.

Point "A" applies at all times. Point "B" generally applies to low cost (tetrode tuner) and older TV sets when the amplifier is mounted near the set. Point "C" applies when the transmission line loss is appreciable. (See table 1). In this case we can improve the initial signal-to-noise ratio by using a low noise mast-mounted amplifier.


3. OVERCOME SPLITTING LOSSES Splitting a signal to drive several TV sets causes loss to each set. If the signal power is divided among two sets, each will receive 1/2 the original power (3db loss). This is equivalent in points "1" and "2" to an extra 3db of transmission line loss. The solution is amplification before splitting. This can restore contrast and re-establish signal-to-noise ratio (or even improve it).

One transistor amplifiers are most susceptible to overload. Two transistor amplifiers are much less susceptible, performing about the same as single tube units. Two tube and dual section tube amplifiers overload least. Frame-grid tubes provide exceptionally low noise and last longer than ordinary tubes. If interference occurs, attenuation filters can be used.

BLONDER-TONGUE TV/FM SIGNAL AMPLIFIERS

Brilliant color TV, sharp black and white TV and lifelike FM stereo reception require strong, clean signals. To provide TV viewers with the best possible reception in any area of the country, Blonder-Tongue offers the world's largest selection of signal amplifiers. There are VHF amplifiers, UHF amplifiers, FM amplifiers. And, for the first time, all-channel TV amplifiers covering every channel from 2 to 83.

When you select a Blonder-Tongue amplifier, you can always be sure of getting the best amplifier for your specific reception problem. There are mast-mounted amplifiers designed to take advantage of the best signal-to-noise ratio available at the antenna for weak signal areas. There are indoor amplifiers, that offer convenient installation and can provide excellent results where there are relatively strong signals. You also have a choice of either tubed or transistor amplifiers. For example, transistor amplifiers offer greater gain and are most effective in weak signal areas where there are no strong local channels to cause overload.

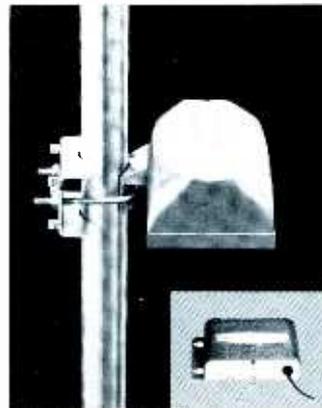

The finest signal amplifiers in the world are also the easiest to install. Many of the mast-mounted amplifiers feature the exclusive 'Miracle Mount'. All mast mounted amplifiers feature a separate remote power supply which can be installed easily indoors near the set. Finally, secure, positive 300 ohm connections can be made in a jiffy with Blonder-Tongue patented stripless terminals.

The chart on the right hand page will serve as a guide that will help you select the best signal amplifier for your area.

ALL CHANNEL



UHF



Blonder-Tongue amplifier that's best for you

BLONDER-TONGUE SIGNAL AMPLIFIERS—VHF, UHF, VHF-UHF, FM

MODEL	DESCRIPTION	COVERS CHANNEL	OUTPUTS	NET	
MAST MOUNTED	U/Vamp-2	World's first mast-mounted UHF/VHF amplifier. 2 transistors. Built-in FM filter. Remote AC power supply. Separate inputs for UHF and VHF. Single 300 ohm input at power supply accepts combined UHF/VHF twinlead.	2-83	1	\$33.25
	Vamp-2	Mast-mounted VHF amplifier. 2 transistors. Separate remote AC power supply. Strong overload handling capability. 2 or more sets.	2-13	2	\$25.85
	Vamp-1	Mast-mounted transistor VHF amplifier. Separate remote AC power supply. FM trap.	2-13	1	\$17.10
	Vamp-2-75	Mast-mounted 75 ohm VHF home TV amplifier system. 2 transistors. Uses coax cable. Single 75 ohm output can be split to 2 or more TV sets. Strong overload handling capability. Remote AC power supply. FM trap.	2-13	1 (75 ohm)	\$29.55
	AB-3	Deluxe, mast-mounted TV/FM amplifier. Low noise frame-grid tube. Can be used up to a mile from AC source. 75 and 300 ohm outputs.	2-13, FM	1 (75 or 300 ohms)	\$78.50
	ABLE-U2	Mast-mounted UHF amplifier. 2 transistors. Uniform response on all UHF channels. Remote power supply. Miracle Mount.	14-83	1	\$26.95
	INDOOR	V/U-ALL2	World's first indoor UHF/VHF amplifier. 2 transistors. FM filter. Single 300 ohm input accepts combined VHF/UHF twinlead. 2 sets.	2-83	2
B-24c		Indoor VHF/FM amplifier. Uses high gain, low-noise frame-grid dual-section tube. 4 sets.	2-13, FM	4	\$17.25
IT-4		Indoor transistor VHF/FM amplifier. Excellent interset isolation. Up to 4 sets.	2-13, FM	4	\$19.95
B-42		Indoor VHF/FM using high gain, low noise, frame-grid tube. Up to two sets.	2-13, FM	2	\$14.25
U-BOOST		Indoor tuneable UHF amp Frame-grid tube.	14-83	1	\$17.35
HAB		Deluxe, indoor VHF/FM amplifier for professional home installations.	2-13, FM	1 (75 ohm)	\$49.65
FMB		Indoor FM amplifier. Ideal for stereo and regular FM. Uses frame-grid tube.	FM	1	\$14.55

VHF



Vamp-2-75



HAB



B-24c



Vamp-1



IT-4



B-42



Vamp-2



AB-3



FMB

UHF converter and antenna guide

Selection of right converter and antenna critical for UHF

by I. S. Blonder

Chairman of the Board,
Blonder-Tongue Laboratories, Inc.



There has been a long-standing prejudice against UHF. Since the band opened in 1952, many otherwise knowledgeable technicians have considered UHF reception to be inferior to VHF. Yet the recent New York City tests conducted by the FCC have proved that this is simply not so.

There is a reason for this paradox — equipment. In 1953, the state of the UHF art was relatively primitive. Today, experienced manufacturers like Blonder-Tongue are able to produce equipment capable of providing UHF reception that is, in many ways, superior to VHF.

Today's Blonder-Tongue UHF converters reflect the improvements drawn from our experience in every UHF area of the country. The consumer has the opportunity to buy a converter which has withstood the most critical test of all, performance in nearly 3 million homes. Blonder-Tongue provide brilliant color pictures and sharp black & white reception on *all* UHF channels.

As for antennas, UHF has a definite advantage over VHF. Because the UHF wavelength is so small, high gain, efficient antennas are small and cost little. The periodic principle

proved so successful in the U.S. Satellite program is especially applicable to UHF. The Blonder-Tongue Golden Dart (outdoor) and Golden Arrow (indoor) antennas utilize this principle. While they are compact, these antennas provide more gain than the large VHF yagis. What's more important, their patterns are clean, rejecting unwanted "ghost" signals. With a little extra care in selecting and installing UHF equipment, you can often provide your customers with better UHF pictures than they've been watching on VHF.

Blonder-Tongue UHF converters

These all-channel UHF converters, your best investment in TV enjoyment, add channels 14-83 to your present set. They are particularly suited to meet the critical demands of color TV. The famed BTU-2T and 99S converters feature peak performance on all UHF channels, easy installation, reliable, long-term operation. Maximum stability for drift-free performance and a low noise figure for snow-free reception. The BTU-44 employs a tunnel diode circuit for excellent, low cost battery operation.

Blonder-Tongue UHF antennas

The UHF antennas are designed to match the high performance standards on all UHF channels of our famed UHF converters. They employ the well-known Periodic principle, to provide uniform, high gain across the entire UHF spectrum for sharp, ghost-free pictures. Full bandwidth makes these UHF antennas excellent for color and black & white TV.

The Golden Dart is an outdoor UHF antenna which comes completely pre-assembled with nothing to snap out, no screws to tighten. The Golden Arrow is an indoor UHF antenna, which outperforms all other available indoor UHF antennas.



ALL-CHANNEL UHF CONVERTERS

DESCRIPTION	EFFECTIVE RECEPTION RANGE*	INPUT CHANNELS	OUTPUT CHANNELS	NET
BTU-2T —Deluxe all-channel, UHF converter/amplifier. Adds all UHF channels to any set. Triples TV signal strength. Easiest tuning with dual-speed channel selector. UL approved.	Used with an outdoor antenna anywhere up to 50 miles from station. With indoor antenna, up to 25 miles.	14-83	5 or 6	\$26.95
BTC-99S —All-channel, UHF converter. Adds all UHF channels to any set. Provides maximum signal power. Drift-free, distortion-free. UL approved.	Can be used with indoor antenna for prime signal areas and outdoor antenna up to 25 miles from station.	14-83	5 or 6	\$19.50
BTU-44 — All-channel, tunnel diode UHF converter. Utilizes tunnel diode for maximum reliability. Operates on ordinary flashlight battery which lasts from 6 to 9 months.	Can be used with indoor antenna for prime signal areas and outdoor antenna up to 25 miles from the station.	14-83	5 or 6	\$13.20

ALL-CHANNEL UHF ANTENNAS

DESCRIPTION	EFFECTIVE RECEPTION RANGE*	FRONT-TO-BACK RATIO	NET
GOLDEN DART outdoor UHF antenna Uses Periodic principle, 11 working elements for uniform high gain across the entire UHF spectrum.	Up to 50 miles.	20db min.	\$3.55
GOLDEN ARROW indoor UHF antenna Employs 10 working elements to provide constant high gain and matched impedance. Full Bandwidth — flat response.	Up to 20 miles.	20db min.	\$2.70

*In weak signal areas, use a model Able-U2 UHF amplifier.

**ENJOY BETTER
TV RECEPTION WITH
BLONDER-TONGUE.**

**SAVE DURING
THE VAL-U-RAMA
NOW GOING ON.**



BLONDER-TONGUE

9 Alling Street, Newark, New Jersey 07102

Canadian Div.: Benco Television Assoc., Ltd., Toronto, Ont.

home TV accessories • closed circuit TV
• community TV • UHF converters • master TV

RCA Calibration Center's Resistance Standard — accuracy 0.0002%.

RCA Frequency Standard being used to calibrate an oscillator

Recertifying Calibration Tubes on the RCA Static Characteristic Standard.



Calibrating portable Standard Cell on the RCA Primary Voltage Standard

Voltmeter being calibrated on the RCA AC Voltage and Current Standard.



RCA ELECTRON TUBE RELIABILITY BEGINS HERE

DEPENDABLE PERFORMANCE



IS THE END RESULT

No reliability program for receiving tubes can be better than the test instruments and equipments it employs.

That's why RCA maintains the extensive Calibration Center in its Harrison, N. J., tube manufacturing plant (see photos above). The Center's responsibility: to assure that all measuring instruments and equipments, used in tube development from initial design through volume production, are accurate within rigidly specified limits. Here is how this is accomplished:

1 The Calibration Center's own equipments are calibrated by standards (voltage, resistance, capacitance, frequency) whose values are regularly checked against standards of the National Bureau of Standards.

2 Measuring instruments used in all research, design, development and application laboratories are calibrated directly from the Center's equipments.

3 Sets of Calibration Tubes, selected to cover every type and family of tubes, are measured in the Calibration Center and used by the Center's personnel to periodically verify the accuracy of all factory tube-testing equipments.

4 Sets of Control Tubes, evaluated under the supervision of the Calibration Center, constantly monitor the repeatability of factory tube-testing equipments.

Our Harrison Calibration Center is another example of the effort we make to assure the specified and dependable performance of every receiving tube that bears the emblem of RCA...performance that benefits you through customer satisfaction.

**SEE YOUR
AUTHORIZED RCA DISTRIBUTOR
FOR TOP-QUALITY
RCA RECEIVING TUBES**

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



The Most Trusted Name in Electronics

fast, accurate, never lets you down . . .

New Burn-out,
stick proof meter!

NEW
SPEEDY
SET-UP
BOOKLET



only

NEW TC 130

\$7450

Checks them all . . .

including Novars, Compactrons,
Nuvistors, 10 pin tubes — plus
Picture Tubes!

Only 7 Lbs. . .
Smaller Than A Portable Typewriter

Here's the famous MIGHTY MITE, America's fastest selling tube checker, with an all-new look and many new exclusive features. MIGHTY MITE III brings you even greater portability, versatility and operating simplicity beyond comparison. Controls are set as fast and simply as A-B-C right from the speedy set-up cards in the cover. The new functional cover can be quickly removed and placed in a spot with more light for faster reading of the set-up data or "cradled" in the specially designed handle as a space saver as shown above. New unique design also prevents cover from shutting on fingers or cutting of line cords as in older models.

In a nut shell . . . the MIGHTY MITE III is so very popular because it checks for control grid contamination and gas just like the earlier "eye tube" gas checkers (100 megohm sensitivity) and then with a flick of a switch, checks the tube for inter-element shorts and cathode emission at full operating levels. Sencore calls this "the stethoscope approach" . . . as each element is checked individually to be sure that the tube is operating like new. User after user has helped coin the phrase "this checker won't lie to me". Most claim that it will outperform large mutual conductance testers costing hundreds of dollars more and is a real winner in finding those "tough dogs" in critical circuits such as color TV and FM stereo.

See Your Parts Distributor -- And See
The Mighty Mite III For Yourself!

NEW

IMPROVED

MIGHTY
MITE

NEW

Lower voltage checks for
Nuvistors and all new frame
grid tubes, as demanded by
tube manufacturers, but not
found on other tube checkers.

NEW

Speedy indexed set-up cards
to reduce "look-up" time.
No more cumbersome booklets,
or incomplete charts.

NEW

Simplified panel layout
reduces set-up time — prevents
set-up errors.

NEW

Streamline styling
with rounded corners
and rubber feet, prevents
marking Furniture — presents
that "Professional look".

SENCORE
"Quality at its finest"

426 SOUTH WESTGATE DRIVE
ADDISON, ILLINOIS

Chasing Distortion

(Continued from page 38)

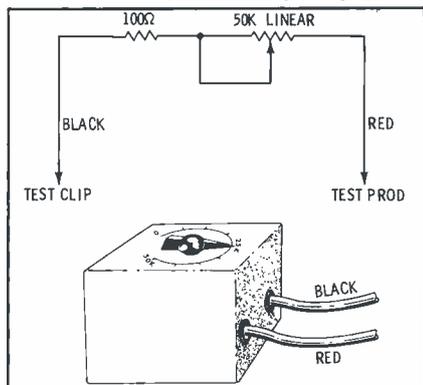


Fig. 3. "Bias-changer" will trace distortion.

stages resemble the divider systems shown here. This being the case, it is easy to alter the bias simply by changing the ratio of the divider resistors. Find an easy way to change this ratio, and you'll have an easy way to change the bias; change the bias without much effort, and you can check the stage for distortion without much effort. Therefore we need procedures for doing this job quickly, and without a lot of intricate desoldering and resoldering on tightly packed printed boards.

The Bias-Changer

The "tool" we use for distortion-chasing in transistor audio amplifiers—be they hi-fi units with barely measurable distortion or tiny portable radios with fuzzy sound—is shown schematically and sketched in Fig. 3. (The device can be mounted in a box as shown, but we've used one for several years without ever going to that much trouble.) The 50K potentiometer has a linear taper, and the 100-ohm resistor is added to prevent inadvertently shorting some point through the test unit.

Fig. 4 shows an example of how the unit can be used to ascertain what bias is necessary to keep the transistor amplifier operating in the linear region. By opening the base-bias supply connection (a razor-

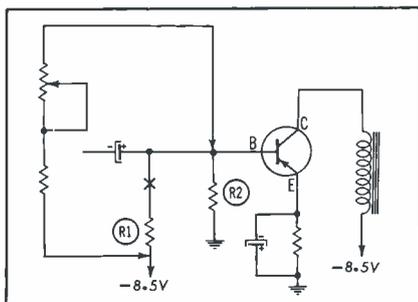


Fig. 4. Tester can substitute variable bias.

BOOK REVIEW



Communication Satellites

George E. Mueller and Eugene R. Spangler; John Wiley & Sons, Inc., New York, N.Y.; 280 pages, hard-bound, \$10.00. In modern global communications, orbiting satellites are becoming one of the more dependable, although expensive, means of relaying voice and television messages directly to any part of the world. Here's a book that tells about two important aspects of the subject—communications via satellites and the technology of placing a satellite in a communications-capable orbit. As outstanding engineers in the space program, both Dr. Mueller and his former assistant, Mr. Spangler, easily qualify as experts in both areas.

Chapters 1, 2, and 3 introduce problems and choices facing those who design satellite relay systems. Chapter 3 elaborates on the relative merits of passive satellites compared with active relay systems. Considering losses and other factors inherent in passive systems, it isn't difficult to

conclude—as do the authors—that active repeaters are the more practical.

From here, the organization of the book seems a little indeterminate, but the information is all there. Chapters 4, 7, 8, and 10 treat of the satellites themselves, while chapters 5, 6, 9, and (part of) 10 are concerned with the communications systems and equipment—the payload and its functions. Chapters 11 and 12 deal with applications and reliability.

Concerning satellites, the reader is familiarized with the effects of, and interrelation among: altitude; micrometeorite activity; radiation such as cosmic, gamma, X-, and ultraviolet rays, plus other little-known radiation phenomena; and time delay in various orbits. Attention is given to problems of attitude and orbit control, and the systems now used for solving them. Satellite structure, methods of temperature (environmental) control, tracking provisions, and command (control) systems also receive their portion of discussion.

Obviously, you're not going to be servicing satellites, at least not right away. However, for the technician whose curiosity about communications satellites is more than merely passive, this book offers a lot of information.

Get Your First Class Commercial F.C.C. LICENSE QUICKLY!

Career opportunities in *communications electronics* are almost unlimited. Prepare now. Let Grantham train you — by correspondence, or by classroom and laboratory instruction. Get your *first class commercial F.C.C. license* in as little as 3 months, or at a slower pace if you prefer. Then, continue in more-advanced electronics training if you wish. Diploma awarded. Our catalog gives full details.

Learn how our training can prepare you for your F.C.C. license; write or telephone the School at any one of the teaching divisions listed below, and ask for "Catalog 41."

Grantham School of Electronics


1505 N. Western Av., Los Angeles, Cal. 90027
(Phone: HO 9-7878)

408 Marion Street, Seattle, Wash. 98104
(Phone: MA 2-7227)

3123 Gillham Road, Kansas City, Mo. 64109
(Phone: JE 1-6320)

818-18th St., NW, Washington, D.C.
(Phone: 298-7460)

Circle 63 on literature card

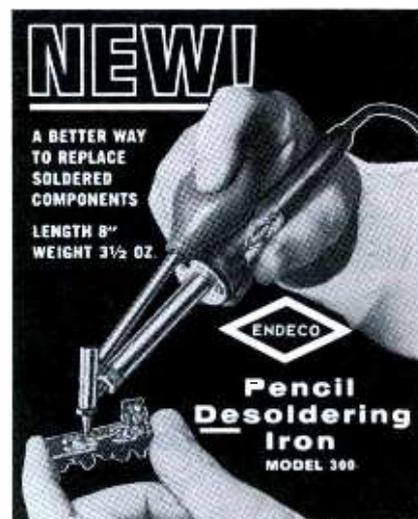

Now—remove miniature soldered components in seconds—without damage

Hollow tip fits over connection; vacuums all solder for easy removal of component. Leaves terminals and mounting holes clean. Then, with 360° contact, it resolders even faster and better than regular irons. Handles miniature and standard components in printed circuit boards and conventional wiring. Self-cleaning. All parts replaceable. 40 watts, 115-v. 5 tip sizes. Pays for itself in time saved. \$9.95 net East of the Rockies.

Larger model available. See your distributor or write:

ENTERPRISE DEVELOPMENT CORPORATION
1102 E. 52nd • INDIANAPOLIS, IND 46205

Circle 64 on literature card

September, 1964/PF REPORTER 47

helps you make more money
than any other test instrument

Checks CRT emission, interelement shorts and grid cutoff in a jiffy.

NEW

IMPROVED

CRT

CHECKER

and rejuvenator

Only tester that checks all black and white and color tubes without adaptors.

Uses DC on all tests as recommended by tube manufacturers. Exclusive automatic controlled rejuvenation (ACR) insures just the right amount of rejuvenation for each job. You just push the button: The ACR circuit takes over and applies rejuvenation voltage for just the right amount of time.

All hand-wired — all American made.



COLOR CABLE

B&W CABLE

Weights only 10 lbs. — Unbreakable all steel case for home or shop.

SENCORE CR128

\$69⁹⁵

Here is a new CRT checker and rejuvenator with the latest in design but at a price far below testers that check round color tubes only. The CR128 checks them all; conventional black and white tubes, new low drive B&W tubes, round color tubes and the recently announced rectangular color tubes.

Tests made are standard in the industry, using DC for all checks to prevent damage and erroneous readings. Color guns are tested individually as recommended by CRT manufacturers. Procedures for color gun tracking tests are explained on back cover of instruction manual.

Exclusive automatic controlled rejuvenation applies rejuvenation voltage for a longer period of time to guns that are lowest in emission. Merely push the rejuvenation button and the RC timer takes over to automatically rejuvenate cathodes, clear shorts or weld open cathodes. A must for equalization of beam currents in poor tracking color tubes. Once RC timer discharges, new rejuvenation voltage cannot be re-applied until button is released and depressed again. It really works; you merely push the button and the automatic circuit takes over.


New all steel portable carrying case protects meter and panel when carried in a service truck. Removable cover can be used as a handy parts tray in the home and fitted to the back while in the shop.

Let your SENCORE Distributor show you how the CR128 will pay for itself the very first month in picture tube sales.

SENCORE

426 SOUTH WESTGATE DRIVE
ADDISON, ILLINOIS

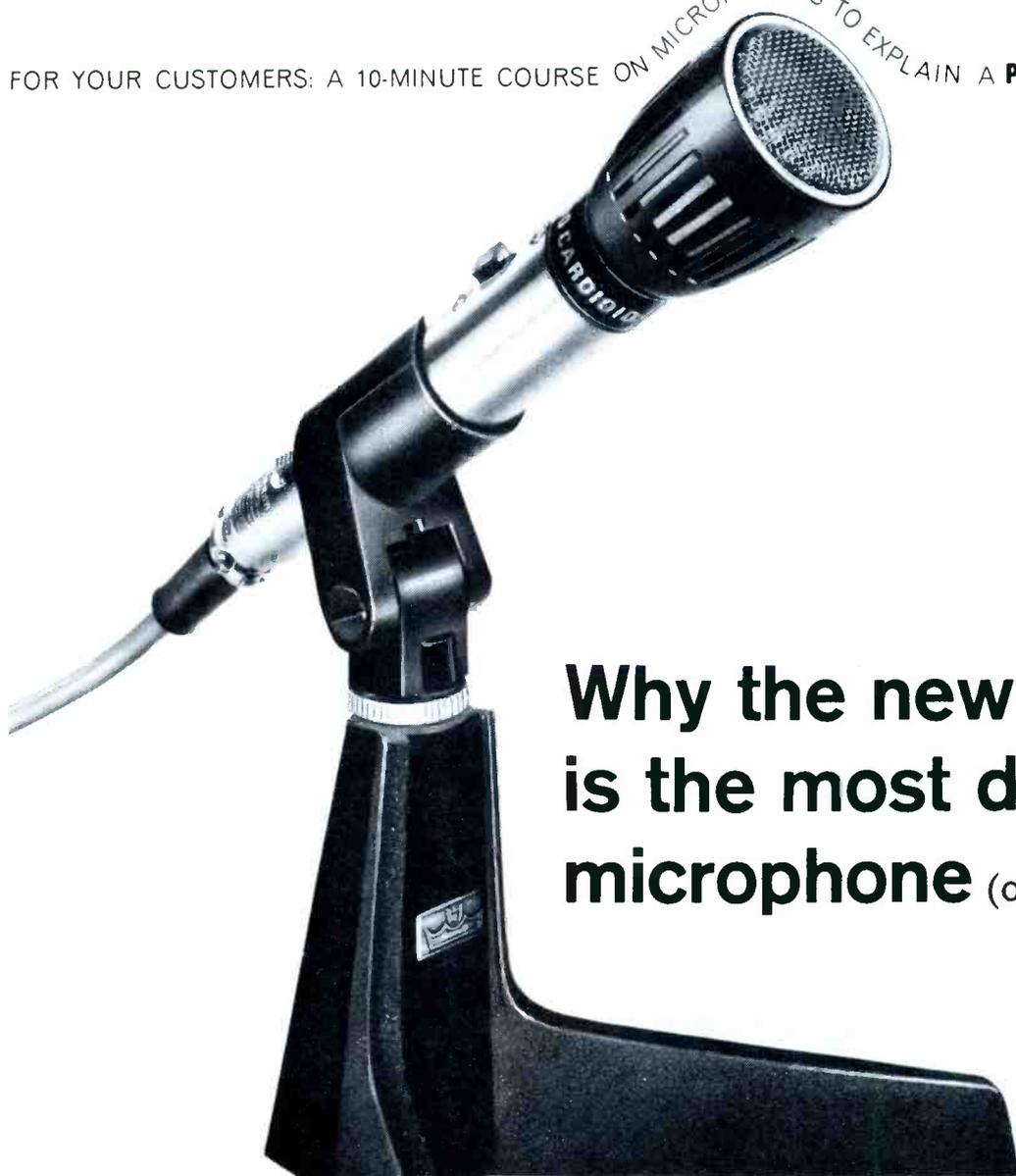FOR YOUR CUSTOMERS: A 10-MINUTE COURSE ON MICROPHONES TO EXPLAIN A PHENOMENAL SUCCESS STORY



Why the new 8000 is the most demanded microphone (of its kind!)

New University 8000: \$29.95.
With slide switch (the 8100): \$31.50.
Model DS-10 Desk Stand: \$6.95.

It's a cardioid. It's dynamic. It's shock-mounted. It offers variable impedance and uniform wide-range response. It's designed and made by LTV/University and it's less than \$50.00. Less than any other cardioid! It's only \$29.95. And it's sold with the world's only five-year microphone warranty!

The new University 8000 is a "first" and "only." For those who like to be exclusive, that's one reason for buying it. The important reasons may be found in the following microphone buyers' guide!

There Are Cardioids... and Cardioids. All cardioids are essentially "deaf" to sounds originating from the rear. They're invaluable for eliminating background sounds, for use in noisy and reverberant areas, for reducing feedback and for permitting a higher level of sound reinforcement before feedback would normally occur. BUT—not every cardioid uses rugged dynamic generating elements. There are crystal cardioids which offer high sensitivity and output. But their response is limited; deterioration is rapid due to heat, humid-

ity, rough handling. The University 8000—a cardioid dynamic—is virtually indestructible.

Tape Recording. Cardioid mikes are essential for quality recordings. They pick up only the performer over a wide frontal area. They prevent the output of speakers from affecting the mike, thus eliminating feedback squeal, and permit recordists to work from far or near. For stereo, only cardioids can assure proper balance, if both are matched. *University quality control makes any two 8000's absolutely identical "twins" to assure full stereo effect.*

Public Address. Cardioids make microphone placement far less critical; permit greater amplifier output—without feedback—than possible with omnis; assure superior intelligence indoors and out. For public address use, however, they must be extremely rugged. The 8000 can be handled without care. It can take extreme heat and humidity. The user can hit it, shout into it—even shoot a gun near it! It's also corrosion-proof.

Realism. Wide-range response is important. Uniform response is even more important. The new 8000 offers wide-band response, extremely uniform to eliminate sibilants (hissing S's), bass boom and tinny treble. Its reproduction quality is virtually indistinguishable from the live performance.

Cables, Long and Short. The 8000 has variable impedance—30/50 to 20,000 ohms. With high impedance mikes, a 10-foot cable is maximum to avoid response loss and hum pickup. The 8000, sold with a 15-foot cable, can also be used with longer cables to record without recorder noise; to monitor recordings through speakers instead of headphones, and make recordings with recorder out of sight.

For complete specifications on the fabulous 8000 series, ask your dealer for literature or write Desk PR-9



**LTV
UNIVERSITY**

A DIVISION OF LING-TEMCO-VOUGHT, INC.
9500 West Reno, Oklahoma City, Okla.

blade slit across the printed foil will do it) and substituting the connection shown, the amount of bias can be adjusted or varied while you listen or watch the scope to see when the transistor reaches normal operation. The test potentiometer should be set at maximum resistance for the beginning of each test. After the connection is made and the set turned on, slowly rotate the 50K control so the bias on the transistor is increased.

When a point is reached that clears any distortion, the values of R1 and R2 can be changed to pro-

vide this same bias for the transistor; if it is obvious the new values would be considerably different from the original design of the set, you can safely assume the transistor or some other circuit component is causing the problem.

Our "bias-changer" can be used without disconnecting any components or cutting across any printed-circuit foils. How? . . . simply by connecting it across one of the existing resistors, thus reducing the value. Lowering the value of the series resistor in the divider (R1 in Fig. 4) will increase the base bias; reducing

the value of the shunt resistor (R2 in Fig. 4) will reduce the value of bias voltage applied to the transistor base.

In many transistor circuits, the technique shown in Fig. 4 can be used without the precaution of opening the foil connection to the voltage supply—the "bias-changer" device will override the existing bias network. If there is any doubt of your results, however, play it safe and take time to slit the foil.

Rapid Component Analysis

Assuming the bias-changing technique has revealed the faulty stage, you'll want next to determine what has caused the unwanted change in bias. Long experience in troubleshooting receivers has shown that their most common fault is a defective capacitor. The electrolytic capacitors generally used in transistor sets cause more cases of distortion than any other single component.

You are now in need of a technique for locating a defective capacitor quickly, and it would be nice if the same technique would point out any faulty resistors or transistors in the process. One useful technique involves monitoring the input current drawn by the set from its power supply (usually a battery). If a capacitor is leaky or shorted, merely disconnecting one end will generally cause a very noticeable change in the total input current. This is easy to understand if you consider the capacitors in the partial schematic in Fig. 5.

Any unusual leakage in C5, C6, or C7 would provide a direct drain on the power supply of the receiver and would appear as a higher-than-normal reading on the milliammeter across the input switch. Disconnecting one end of any faulty capacitor would considerably reduce the drain. The effect of a leaky or shorted C6

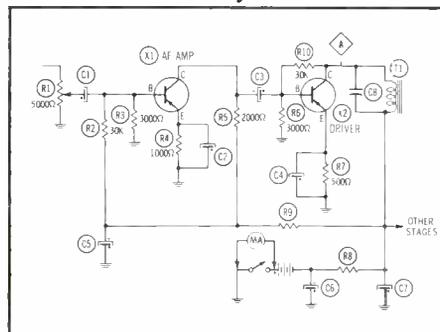


Fig. 5. Audio stages in transistor receiver.


B&K PROFESSIONAL QUALITY AT LOW COST

Model 600 Compact Portable Dyna-Quik Makes Tube Testing Quick, Accurate, Profitable!

It's amazing how quickly you can accurately check out tubes on every call—sell more replacements, and make more money—with this up-to-date, low-cost professional quality tube tester. Checks for all shorts, grid emission, leakage, and gas. Checks each section of multi-section tubes separately. Checks tube capability under simulated load conditions. Rejects bad tubes, not good tubes. Quickly reveals tube condition, saves customers, stops call backs, increases servicing profit.

Exclusive adjustable grid emission test. Sensitivity to over 100 megohms. Phosphor-bronze socket contacts. Complete tube listing in handy reference index. Handsome, sturdy leatherette-covered carry-case. Size 8½" x 11" x 4½". Net, \$74⁹⁵

QUICK, DIRECT, ERROR-FREE READINGS WITHOUT MULTIPLYING

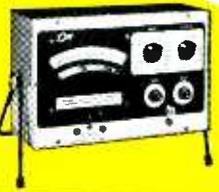	Model 375 VTVM Net, \$89.95		Model 360 V O Matic Net, \$59.95
---	--	---	---

See Your B&K Distributor or Write for Catalog AP21-R

B & K MANUFACTURING CO.
Division of DYNASCAN CORPORATION
1801 W. BELLE PLAINE - CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.

Circle 21 on literature card

NOW

*convergence and color adjustments
are easier, faster, more accurate!*

NEW B&K MODEL 1240 LOW PRICED PORTABLE COLOR GENERATOR

with crystal-controlled keyed rainbow color display!



Thinnest Horizontal Lines! Smallest Visible Dots!
(Just one raster scanning line thick)

**Simplifies In-Home (or Shop)
Color TV Set-Up and Servicing**

only
\$134⁹⁵_{NET}

You're the color TV expert when you use the "1240." You have the advantage of B&K quality—with features not available before at such surprisingly low cost.

Provides crystal-controlled keyed rainbow color display on TV screen to test color sync circuits, range of hue control, and align color demodulators. Shows ability of TV receiver to display color values.

Provides dot pattern, crosshatch, horizontal and vertical lines. Highly stable crystal-controlled count circuit with small-step count assures greater reliability and stability of color, dots, and lines. All horizontal lines and

dots are just one raster scanning line thick. Lines begin off-screen and end off-screen, with no break in line. Dot brightness is adjustable with easily accessible control. Chroma Level Control simplifies color sync trouble-shooting.

Operates on channels 3, 4, and 5, and adjustable without removing cabinet. No connection inside TV set is needed. Power transformer operated and line isolated to prevent shock hazards. Operates reliably on 105-125 VAC, 60 cps. (Color Gun Killer is available as optional accessory.) Extreme lightness and portability (9 lbs.) make it ideal for in-home servicing.



*See it at your B&K Distributor
or Write for Bulletin AP21-R*

B & K MANUFACTURING CO.
DIVISION OF DYNASCAN CORPORATION
1801W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.

Circle 22 on literature card

designed and
produced to the
highest standard
of excellence...

NORTRONICS

laminated core, all-metal face heads are now available for more than 500 different tape recorders! Nortronics complete replacement line includes:



miniature heads for use with compact audio-visual equipment



record, play and erase heads for use with home and professional tape recorders



multi-channel heads for use with video tape machines

Find out how you can increase your sales and service business! Write for your FREE copy of Nortronics Tape Head Replacement Guide.

Nortronics 

8161 Tenth Ave. N., Minneapolis, Minn. 55427

Circle 23 on literature card

would be the most notable, because current through C5 or C7 would be limited slightly by resistors R8 and R9. In either case, however, current drain would be sufficient to result in some change in the milliammeter reading when the defective capacitor was disconnected.

A shorted C1 would upset the bias on transistor X1 since current could easily leak to ground through C1 and control R1. Lowering the bias on transistor X1 would reduce collector current and decrease total input current. A shorted C1 would not affect the current drain directly, even with the R1 tap at ground, because of the limiting effect of R2, a comparatively high resistance. Nevertheless, disconnecting one lead of the capacitor would produce an obvious change in the DC current drawn from the power supply and would be a definite clue if C1 is defective.

A shorted C2 would be noticeable mostly in the collector current of X1. As with C1, the effect on input current is indirect—caused by a change in transistor bias. And again the input current diminishes when the capacitor is disconnected. If the capacitor is normal, there will be practically no change in drain from the power supply. The same applies to C4 in the emitter of X2.

The effect of a leaky C3 on current drain could be considerable, because the current path through R5 and R6 would greatly increase forward bias and thus the collector current in transistor X2. It is even possible that a completely shorted C3 could apply so much forward bias to transistor X2 as to ruin it. Disconnecting C3 will greatly reduce the input current drain, if the unit is faulty. If you find the current is still

too high, you'd want to investigate the possibility of a defective X2. To test this, the circuit would have to be broken at point A; but remember that even with a normal transistor some current reduction would occur upon disconnecting divider network R6-R10. To ascertain the exact point of excess current drain, the collector lead could be disconnected right at the transistor, by unsoldering or by the razor-blade method.

Faulty resistive networks can easily be checked out with the bias-changer potentiometer, often simply by bridging a suspected resistor with the test device. Bias faults caused by faulty resistors can thus be checked and eliminated. To determine the exact value for a suspected resistor, simply remove it from the circuit and connect the test device in its place. Adjust the potentiometer until normal operation is resumed. Then it is a simple matter to measure the resistance of the test device and put a correct-value resistor in place of it.

Summary

The techniques set forth in this article are far from the only way to go distortion-chasing in transistor audio stages. However, they have the advantage of being quick and not requiring an undue amount of unsoldering parts for testing. The less soldering you have to do on some of those tiny printed boards, the better.

We've found from our own experience that the bias-changing (or divider-substituting) system is a very quick way to bring a nonlinear stage back into line, thus ascertaining whether it truly is the stage at fault. This method will work well in some of the little transistor sets

PRECISION TUNER SERVICE

P. O. BOX 272

1200 S. WALNUT ST.

BLOOMINGTON, IND.

EDISON 99653

7.50
V or U
COMBO PLUS
9.95 POSTAGE

6 MONTH WARRANTY



All Types T.V. Tuners Cleaned, Repaired and Aligned to Factory Specifications. Same day in shop service on most Tuners. Price Includes Minor Parts, Major Parts at Cost Price. We use Original Parts if possible. State Make Model and Enclose all Parts and Tubes. Pack Well and Insure.

ALSO HAVE LARGE STOCK OF EXCHANGE TUNERS, WRITE FOR TYPES AND PRICES.

Circle 24 on literature card

ANOTHER GREAT ADDITION TO THE
FAMOUS SERIES OF B&K ANALYSTS

SIMPLIFIES AND SPEEDS TV SERVICING

NEW!

B&K

Compact Model 1074 TELEVISION ANALYST FOR BLACK & WHITE and COLOR



Dot Pattern




Crosshatch



Vertical Lines



Horizontal Lines

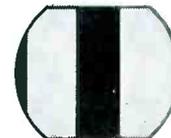

Color Pattern

Here is an exciting new addition to the famous B&K series of Television Analysts—*designed to give every service technician a faster, easier way to service more TV sets!*

The compact "1074" gives you a complete TV signal generating source of your own. Using the B&K *point-to-point signal injection technique*, you can isolate and pinpoint any performance problem for quick correction.

By injecting your own signals, with a visual check on the TV screen, *you can easily signal-trace and troubleshoot any stage* throughout the video, audio, r.f., i.f., sync and sweep sections of black & white and color television sets.

It becomes much easier to find and fix "tough dogs," and troublesome intermittents, as well as to solve other general TV set troubles—to the satisfaction of your customer, and to your own profit.

Net, \$249⁹⁵

Supplies complete r.f. and i.f. signals, with pattern video and tone audio. Video signals are switch selected for fast, visual troubleshooting. Provides FM modulated 4.5 mc sound channel, with built-in 900 cycle tone generator. Provides composite synchronizing signals. Provides separate vertical and horizontal plate and grid driving signals to check complete output circuit and interrelated components. Many other features.

Makes it Easy to Set-up and Service Color TV

Provides dot pattern, crosshatch, vertical lines, horizontal lines, burst signal and individual colors (Green, Blue, B-Y, R-Y, Red, I, and Q) one at a time on the TV set—all crystal controlled for maximum accuracy. Color phase angles are maintained in accordance with NTSC specifications. Thin lines and high stability assure fastest, easiest convergence and linearity adjustments. Color display makes demodulator alignment extremely simple.

Time-Saving, Money-Making Instruments Used and Preferred by Professional Servicemen Everywhere.



Model 375 Dynamatic Automatic VTVM



Model 360 V O Matic Automatic VOM



Model 700 Dyna-Quik Tube Tester



Model 850 Color Generator



Model 445 CRT Tester Rejuvenator

See Your B&K Distributor
or Write for Catalog AP21-S

B&K

B&K MANUFACTURING CO.

DIVISION OF DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.

Circle 25 on literature card

that "don't sound too good" even when new. It will work with sets that sound poor after batteries are only slightly used. In almost any case of distortion, you'll find this technique fast and accurate for pinning down the stage at fault (and often giving a clue how to fix it).

For detecting leaky capacitors, without having to unsolder both ends for testing or substitution, the input-monitoring system is quick and effective. With the meter connection so easy to make, and having already localized the trouble to a single stage, this technique has prov-

en itself popular among all who have learned to use it.

Distortion chasing is not nearly so difficult with these easy techniques. Use them a few times with your next audio jobs; they'll help make the jobs profitable and the customer happy.

Stabilized Variable AC

Have you ever been irritated by fluctuations in line voltage on the bench, or received an AC shock when servicing a transformerless set? The Heath IP-22 isolation transformer is intended to eliminate



these annoyances. This unit reduces shock hazard by providing isolation between the AC line and the chassis being serviced. The stable output voltage can be set to a number of values between 90 and 130 volts and can be monitored with the front-panel meter. A meter switch also permits checking the line voltage. Fine- and coarse-voltage output switches are provided to vary the output voltage in steps of .75 or 5.2 volts. A 3-watt lamp (used as a current-limiting resistor) and an OC2 gas regulator tube maintain a constant output voltage.

The variable-voltage feature is often handy for finding the cause of intermittent operation. For example, slightly increasing the input voltage may make the symptom appear—and stay—making it possible to test the set while a defect is present. This method works exceptionally well if the problem is caused by thermal changes during operation.

An output capacity of 300 watts continuously or 500 watts intermittently makes this transformer suitable for operating equipment with heavy current demands—a color television receiver, for example. An 8-amp fuse protects the isolation-transformer components and the power-line fuses in the event of a short circuit in the equipment under test.

This instrument operates from 105-125 volts AC, 50-60 cps. A 3-conductor line cord is provided, with the ground wire connected to the case. The IP-22 (available in kit form) measures 9½" x 6½" x 5", weighs 18 lb, and sells for \$54.95. ▲

For further information, circle 72 on literature card




MODEL A-106 CONVERSION KIT ADAPTER

FOR PREVIOUS* B&K MODEL 1076 TV ANALYSTS

CRYSTAL-CONTROLLED CIRCUIT
provides keyed rainbow color display
improves horizontal oscillator sync

*

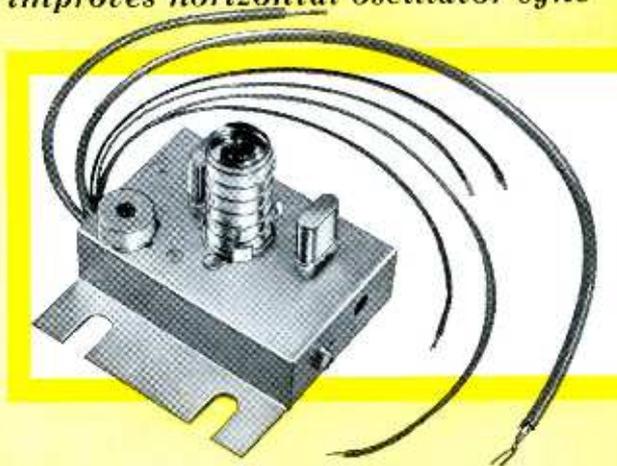Designed for easy conversion of all Model 1076 Television Analysts before Serial No. 425301 and from Serial Nos. 505001 to 506100



Now built into the current Model 1076 Television Analyst, this new Adapter is made available for in-chassis installation on previous* Model A-106. Net, \$35⁹⁵

DELUXE MODEL 1076 TELEVISION ANALYST

with Flying Spot Scanner

Includes crystal-controlled keyed rainbow color display and improved horizontal oscillator synchronization. Makes servicing of black and white and color TV easier, faster, more profitable. Net, \$329⁹⁵



See your B&K Distributor, or Write for Bulletin AP21-R



B & K MANUFACTURING CO.
DIVISION OF DYNASCAN CORPORATION
1801W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.



JUST TRY AND MAKE US

...buy any indoor antennas but Channel Master!

The line that moves in new directions. Once you discover it you'll never give it up, either.

As the gentlemen above have learned, Channel Master indoor antennas are worth fighting for. Worth holding onto. Worth featuring BIG.

Because Channel Master really blazes new trails. It's the most complete, most effective, most beautiful, most profit-packed line in the world.

It offers the best series of step-up choices in the business: 14* all told...one for every purpose and price. The customer chooses from either UHF/VHF all-channel/FM Stereo,

or VHF/FM Stereo models; all of them great for color.


Know what you'll particularly like about most of the "all-channel 82's"—besides their looks and price? The **outdoor-type elements. Yagis. Stacked Bow-Tie.** Really revolutionary for indoor antennas.

And each model is truly 2 antennas in 1—made with 2 separate and distinct UHF and VHF transmission lines. The VHF models? Time and again, they've proved their claim to be called best.

Honestly—wouldn't it be a crime to buy anything but Channel Master? Write for our full-line catalogue: *New Directions in Indoor Antennas.*

CHANNEL MASTER

hands you
the keys
to the city...

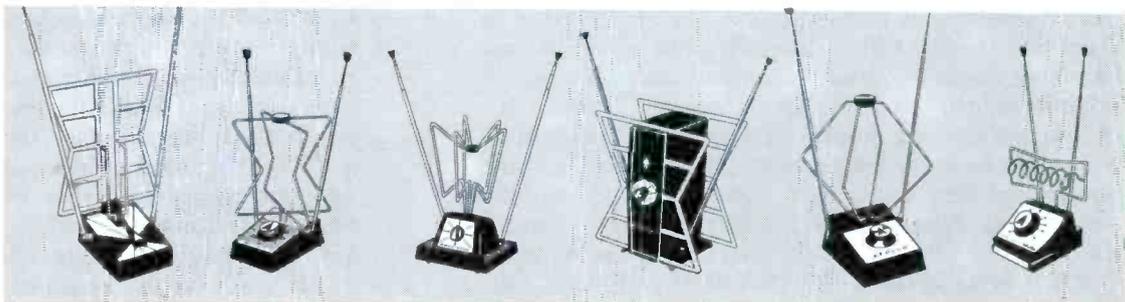

New! Canaveral-82, Model 4006. All-channel and FM. VHF Dipole; plus more UHF gain than stacked dipole. \$10.95*

Canaveral, Model 3720. VHF/FM Stereo. Best-seller at \$9.95*

New! Gamma, Model 3723. VHF/FM Stereo. \$5.95*

YU-82, Model 4000. All-channel and FM. Exclusive Beam-Reversing Circuit \$14.95*

Transistor-Amplified Apollo, VHF only. Model 3721. World's lowest noise level amplified indoor antenna. \$29.95*

Transistor-Amplified FM/Stereo. Top stereo reception. Model 3731. \$19.95*

...plus eight other models from \$4.98* up. Including: In main photo above, extreme right, Aurora-82, \$5.95*. Second from right, Gamma-82 with 3-element UHF yagi, Model 4007, \$6.95*. Second from left, Alpha, VHF/FM Model 3722, \$7.95*. Left, Gamma.*

Circle 27 on literature card

CHANNEL MASTER • ELLENVILLE, N.Y.

*Fair-traded

Death Stalks the Rooftops

by Forest H. Belt

One recent hot day in July, on a rooftop in Pendleton, Indiana, a 22-year-old technician received a severe electrical shock when he cut into a television lead-in with his diagonal cutters. Subsequent investigation of the situation, led by Mr. Jack Clouse of Rodefeld, Inc., Indianapolis, disclosed a potentially serious danger to every television serviceman who works with antennas and lead-ins.

The young technician had climbed to the roof to replace an antenna lead. (As is common with rooftop installations, the mast was grounded.) He stood on a ladder, gripped the mast with one hand for added support, and reached upward with his other hand to cut the lead-in. As he cut, a strong AC voltage coursed through his arms and chest, and he was unable to relax his grip from either the mast or the cutters. Fortunately, the lady of the house, watching from the ground, had enough presence of mind to run inside and throw the main service switch. The young man collapsed, and subsequently spent many hours under oxygen before he was revived.

To determine the cause of such an unexpected event, investigators removed the chassis from the transformer-powered set and took it to a nearby service shop where it was thoroughly checked. Line filters were examined carefully, as were the interlock, the on-off switch, and all wiring associated with the input power circuits. There was absolutely no indication of any short, nor *any* clue as to why there had been an AC voltage of any kind on the lead-in. In fact there was no trace of voltage at the antenna terminals!

When the chassis was reinstalled in its wooden cabinet at the house and plugged in, a 100-watt light bulb connected between the antenna lead and earth ground burned brightly. A licensed electrician was called in to check the house wiring carefully, but no fault was found. It was determined further that the bulb was also brightly lighted when connected directly between the chassis and an earth ground. Successively disconnecting the lead-in from the set, the plug from the wall, and the power cord from the chassis produced a most startling and baffling result: With the set *completely* disconnected from all line power and from the antenna, **THERE WAS ENOUGH VOLTAGE PRESENT BETWEEN THE CHASSIS (now apparently isolated) AND THE GROUND TO LIGHT THE BULB!**

This uncanny event triggered an even more intensive examination, and shortly investigators found a tiny gray wire that lead from beneath the set to a tiny hole


in the floor. Inspection revealed that one of the molded pair was connected across the speaker voice-coil. The other end, the investigators found, was connected to the speaker of a small AC-DC table radio in another part of the house.

At last they had the answer to this deadly booby-trap. The power cord of the AC-DC set was plugged in so that the chassis was hot when the set was off (reversing the plug would merely have resulted in a hot chassis when the set was on). In line with common practice, one side of the speaker circuit was grounded, and so was one side of the speaker circuit in the TV set (also not unusual). With the TV chassis thus connected directly to the power line through the hot-chassis AC-DC set, the lead-in became energized through the balun ground connection at the antenna input terminals. This potential killer had existed for a number of months, just waiting for an unsuspecting serviceman to start working on the antenna. The usual precaution of pulling the power cord provided no protection from this dangerous situation.

Considering the many different home-entertainment and intercom systems in which a common speaker buss might be used, and because the condition or configuration of the accessory equipment hooked to such a system is often unknown, it occurs to us that a few words of extra caution are in order for the many readers who might be unwittingly confronted with such a stealthy adversary in one of their customers' homes. Here are some precautions that could minimize the dangers of such servicing:

- (1) Disconnect *every* lead from the receiver before attempting any servicing of the antenna or lead-in. This especially means disconnecting the lead-in itself from the antenna terminals.
- (2) Connect a voltmeter from the disconnected lead-in to an earth ground. (A water pipe will do. Properly installed conduit boxes are grounded, but don't merely assume they have been correctly installed. The antenna ground system is another good ground point for your VOM while you check each conductor of the lead-in.)
- (3) Use only diagonal cutters with insulated handles. (This is a good idea under any circumstances.)
- (4) Always suspect any "extra" wiring that isn't a normal part of the installation. Even if *you* install the "extra" wiring, be absolutely sure you're not setting up a booby-trap for yourself, one of your helpers, or some other unsuspecting technician. ▲

GHOST TOWN!

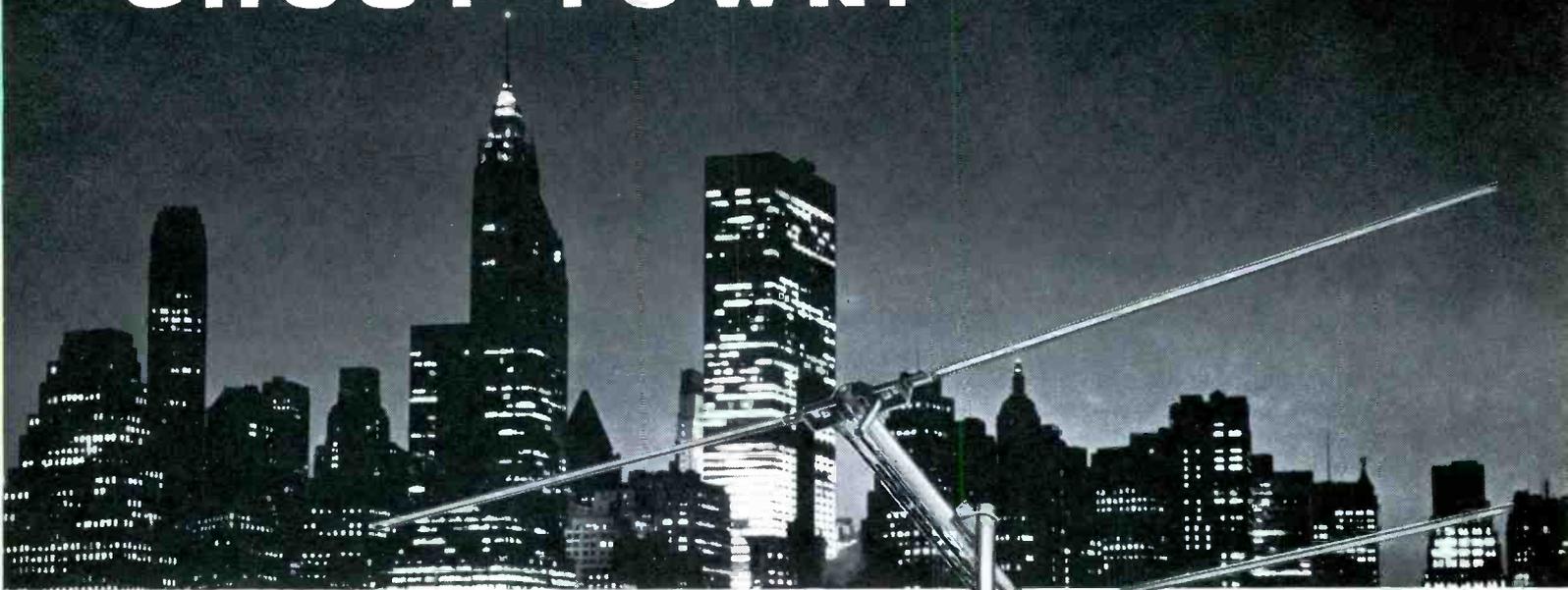

Clean it up...take it over... with this unique new Channel Master antenna


The Coloray. A new kind of antenna **GUARANTEED** to make city (and suburban) TV sets give up the ghost, knock out interference. And has proved it time after time. Right out there in the field—among the tall buildings that cause 80% of the city's TV troubles.

The Coloray is so effective, in fact, that we dare guarantee it to do a better ghost-killing job than any other antenna on the market . . . regardless of size, type, or price . . . or your money back! It is the only antenna in the world backed by such a guarantee.

Enjoy Fringe-Area-Type Profits! No longer are you forced to sell metropolitan antennas on a low price, low profit basis. No longer need you envy fringe-area dealers their high profits on expensive antennas.

The Coloray gives you a real **performance** advantage . . . that means big new profits from a waiting market willing to pay a little more for it. Model 3110-G. Includes E.P.C. protective "Golden Overcoat." Also available in kit form, Models 3115-G, 3116-G.

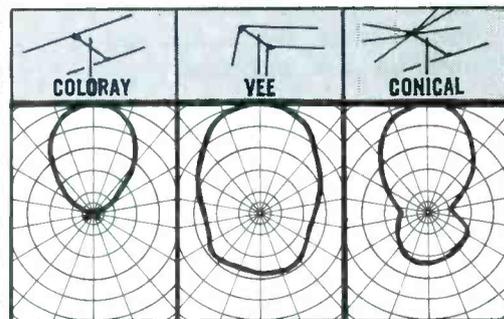Higher Front-To-Back Ratio Than
a 10-Element Single-Channel Yagi.



Compare polar pattern of Coloray with those of most commonly used city antennas.



The secret! A transposed phasing harness with an impedance balancing Power Equalizer Circuit that is really unique.

CHANNEL MASTER COLORAY *

hands you the key to the ghost city

Circle 28 on literature card CHANNEL MASTER • ELLENVILLE, N.Y. *Patent Pending

Automation is really nothing new to the electronics serviceman. Simple automatic control devices of one sort or another have been used in many circuits for years. Often these silent sentinels are used for protective purposes—to prevent self-destruction of the equipment in case of an overload. One example is the group of protective devices employed in TV receivers.

Television protective devices include fuses, fusible resistors, peak-limiting resistors, thermal relays, circuit breakers, and thermistor-type surge-protection resistors. These ordinary two-terminal components carry out their function automatically and dependably. Because of them the TV set owner, the design engineer, and the service technician are saved many headaches.

Some protective devices outlast the receiver; others need to be replaced occasionally since they destroy themselves to save the rest of the circuit. It is important that the service technician be familiar with these devices, their roles, and the rules for their replacement.

Fuses

The simplest and oldest of all automatic protective devices is the fuse. Whatever its size or shape, the fuse operates on the simple principle that excessive current will generate enough heat to melt the fuse wire or link, opening the circuit and disconnecting the equipment from the power source. Nothing in the fuse wears out unless the circuit is overloaded (except in rare cases of failure due to metal fatigue).

When a fuse is used in the low-voltage power-supply section of a TV set, it usually appears in one of two places—in series with the power line (Fig. 1A) or in series with the B-lead (Fig. 1B). To discourage tampering by laymen, the fuse often is soldered into the circuit and located under the chassis or otherwise concealed.

Tiny, glass-tube-type fuses are supplied in a wide range of ratings to suit various operating requirements. Typical quick-acting fuses are supplied with current ratings of $\frac{1}{4}$, $\frac{1}{2}$, $\frac{3}{4}$, 1, 2, and 3 amps at 250 volts maximum. In some circuits, harmless surges blow the fast-acting fuse and unnecessarily deactivate the circuit; a slower-acting fuse is

TV

CIRCUIT PROTECTION DEVICES

Many different types with one primary purpose.

by Rufus P. Turner

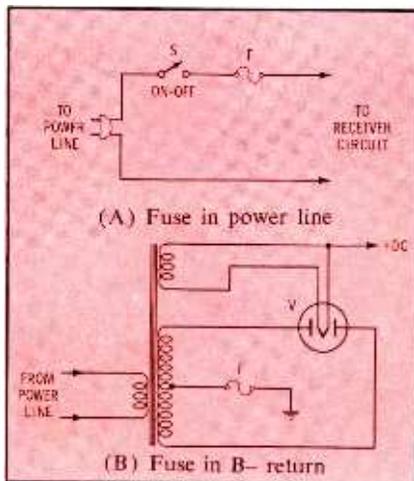


Fig. 1. Locations of some protective devices.

more practical for these applications. Fuses of this latter type have a long time-lag and can withstand a heavy surge or high starting current; however, they will open in the event of a short circuit or continued overload. This type is available in many current ratings between 10 ma and 30 amps at 125 volts maximum. Obviously, the use of a slow-acting fuse is inadvisable in a circuit which must be protected against surges.

A blown fuse shows that something went wrong in the circuit to cause excessive current (find the fault and fix it before replacing the fuse) or that the fuse was too small or of an incorrect type in the first

place (consult service data for the correct size and style).

The rules for fuses are simple and clear: Always use an exact replacement; use neither the next higher nor the next lower rating. Never substitute a piece of wire or other conductor for a fuse. To avoid electric shock, disconnect the power and discharge all capacitors in the fuse line before removing the fuse. Remove a clip-in fuse with a fuse puller designed for the purpose.

Circuit Breakers

In doing its job, a fuse destroys itself, and it must then be replaced. A circuit breaker, on the other hand, opens an overloaded circuit without damaging itself and may be reset automatically or manually. As long as the overload remains, however, the circuit breaker will refuse to remain closed. Manual-type breakers are reset by hand; automatic types reset themselves after a brief interval.

The so-called thermal-cutout switch is one type of circuit breaker. Fig. 2 shows a miniature, thermally-activated circuit breaker of the automatic-reset type. The heat-sensitive element is a thin U-shaped metal strip (A) with a contact (B) on its free end. The strip is mounted so that its contact normally rests against a fixed contact (C) to complete the circuit. When excessive current flows through the device, the strip is heated and expands as indicated by the dotted lines; the circuit is thus opened. When the strip cools and relaxes to its initial position, the contacts reclose the circuit.

A typical device of this kind is mounted in a glass bulb and resembles a small neon lamp. It measures .30" in diameter and is 1.26" long. Pigtail leads are pro-


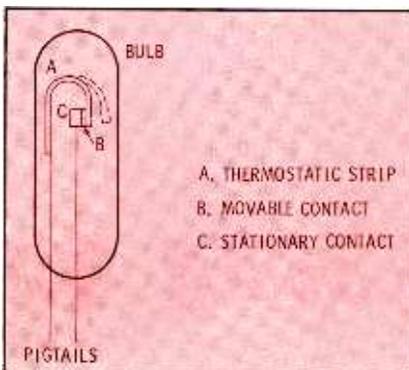


Fig. 2. A typical thermally-activated breaker.

SNOW COUNTRY!

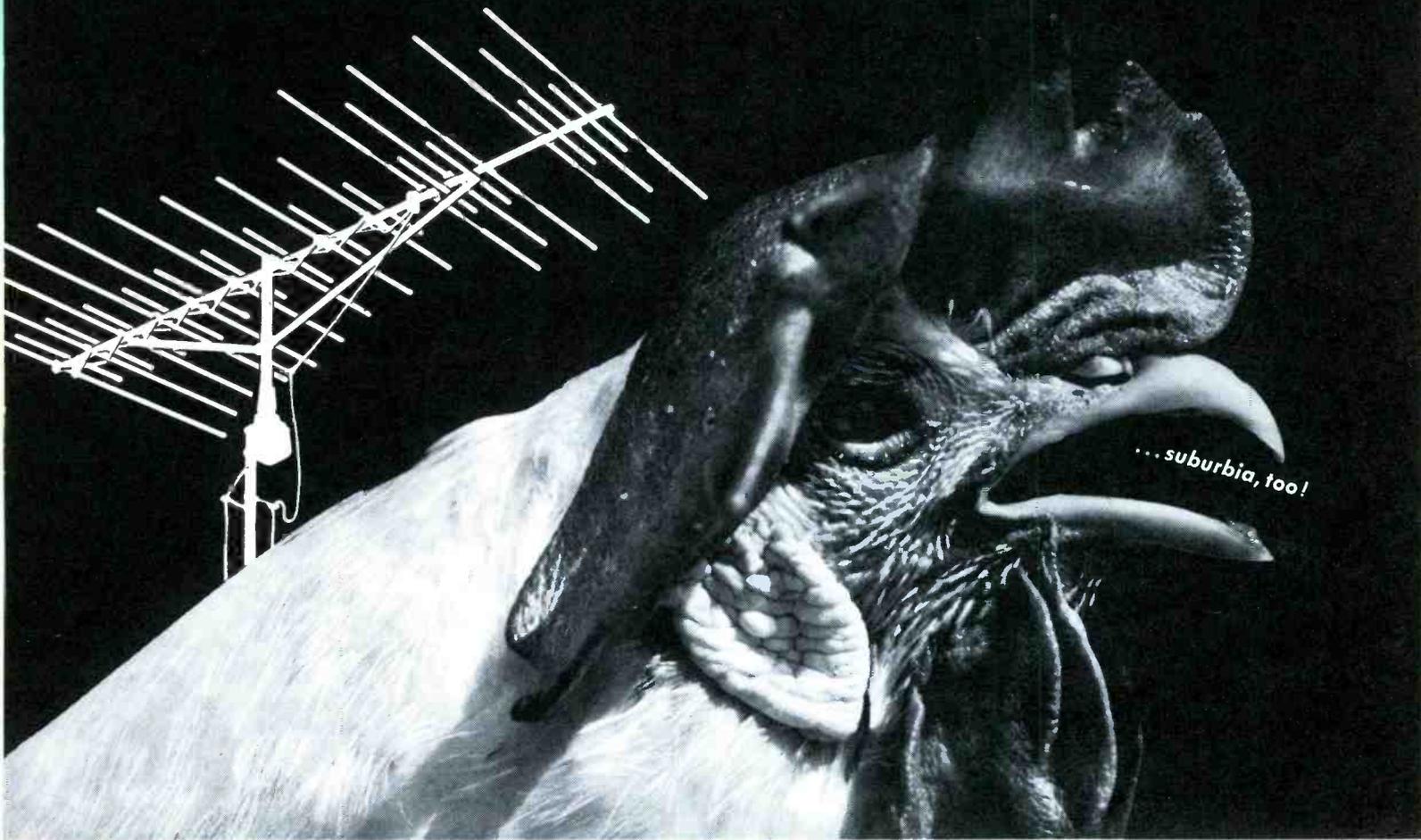

Clean it up...take it over... with **CHANNEL MASTER CROSSFIRES**

The world's most powerful TV/FM antennas. Way-out farm country is snow country. Real weak signal. Without the right antenna, there's a good chance viewers are seeing "spots" on their TV screen. Near fringes and often suburbia are also weak signal. Smart watchers know what to do about this problem in all these areas. They get the right Crossfire.

Top snow removal team! The revolutionary Golden Crossfire alone works on the principle of Proportional Energy Absorption. Meaning? There are more driven elements working with greater efficiency on the Crossfire than in any other antenna. It actually delivers the highest antenna gain of all time. Cleanest, too. The unique transposed feed line cancels rear pick-up beautifully. Perfect for color. And exclusive E.P.C. "Golden Overcoat" protects against every type of corrosion.

8 rugged, handsome Crossfire models are available... 1 for every area and budget. Feature them and you've got the snow country, the near fringes, and the commuter belt... right where you want 'em! In your money belt. Shown above: 28-element Crossfire for deep-fringes. Model 3600.

**Now! Channel Master
Reduces Booster Prices
Up to \$10.**


World's most effective antenna amplifiers.

... Because no boosters anywhere give you more extra signal power when and where you need it. Plus lowest possible noise figure. Built-in lightning resistance. Complete line covers model for every purpose and area... including an all-in-one rotator-TV amplifier. Write for catalog.

WAS \$39.95

NOW! \$29⁹⁵

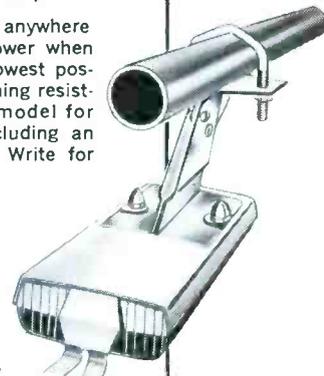Transistorized Telstar TV/FM,
with 4-set coupler. Model 0023B.



Model 3604, 11-element
Crossfire Suburban
... for high gain and
top directivity.

CHANNEL MASTER hands you the keys to the snow country

ELLENVILLE, N.Y.

Circle 29 on literature card

www.americanradiohistory.com

Devant "1"

The All NEW
DEVANT-1
From MOSLEY

The result of
continuous research
and development to bring you
Superior Quality at a

NEWEST ADVANCE IN CB COMMUNICATIONS

A field tested base station antenna that will equal or outperform anything available on the CB market today. Many of the features of the DEVANT "1" are built into the base section. The vertical element terminates in a phenolic sleeve which has greater strength than the aluminum element. Radials terminate into a high strength "Cyclac" base, which again, has more strength than the aluminum element. The Coax female connector is part of the (weather-proof) radial support assembly. Antenna mounting is simplified, just mount the antenna on your mast, tighten two screws and lock nuts.

Tapering the ends of the aluminum tubing (called swaging) is designed to reduce wind load, and any possibility of vibrations which would cause metal fatigue. Loading and impedance matching of the DEVANT "1" is accomplished with loops of one eight inch aluminum rods.

Available Nov. 1st.

New Low Price
\$22.76

\$14.50

The Traveling Companion of
the Base Station DEVANT "1"
is the New Mosley DEVANT "2"

This stainless steel mobile antenna has
the world famous Mosley performance.

A slim line beauty with built-in durability.

Cash in on these outstanding engineering efforts
wherever Mosley antennas are sold.

For detailed specifications and performance data on
the DEVANT "1" and / or DEVANT "2"
clip coupon below and mail.



27 Mcs.
CB Mobile Ant.

Please send me (FREE of charge & obligation) literature on the following
antennas. DEVANT "1" DEVANT "2"

Name

Address

City/State

Mosley Electronics Inc.

4610 N. Lindbergh Blvd.,
Bridgeton, Mo. 63044

vided to allow the breaker to be wired into the circuit it protects. It is an automatic-reset type of breaker that trips when the circuit current reaches 200% of the breaker rating. This particular breaker is available in two types, indicating and non-indicating. The indicating type lights when tripped and remains lighted until the trouble is corrected and the breaker resets; breakers of this type are connected in series with the power line and the load.

Peak-Limiting Resistors

In a typical low-voltage supply employing solid-state rectifiers, heavy current rushes through the rectifier into the uncharged filter capacitors when the set is first turned on. At that instant the input capacitor appears as a short circuit, and the resulting current surge could destroy the rectifier. To prevent this, a peak-limiting resistor is connected in series with the rectifier, capacitor, and AC source. This resistor then limits surge current through the rectifier to a safe value.

The presence of the peak-limiting resistor must not, of course, interfere with normal operation of the circuit. Hence, its resistance must be quite low in order to minimize the voltage drop at normal operating current. In usual practice its value seldom exceeds 7.5 ohms.

Fig. 3 shows a half-wave circuit employing a solid-state rectifier, D. Here, R1 is a 3-ohm, 5-watt peak-limiting resistor. If the power supply normally delivers 100 ma at 100 volts, the voltage lost across this resistor ($3 \times .1 = .3$ volt) is not enough to be noticeable. A 1 1/4-amp slow-acting fuse (F) is included for regular circuit protection.

Fusible Resistors

The circuit shown in Fig. 3 contains both a peak-limiting resistor (R1) and a fuse (F). It is common in TV sets, however, to combine the resistance and fusing functions in a single component—the fusible


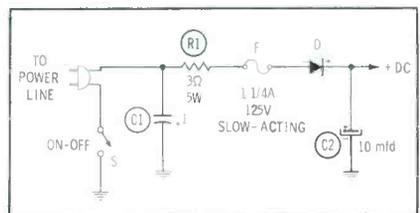
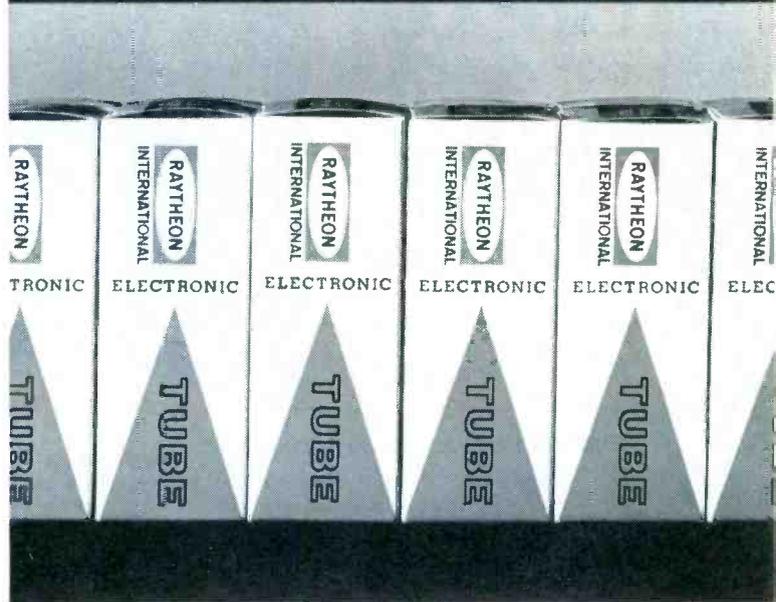
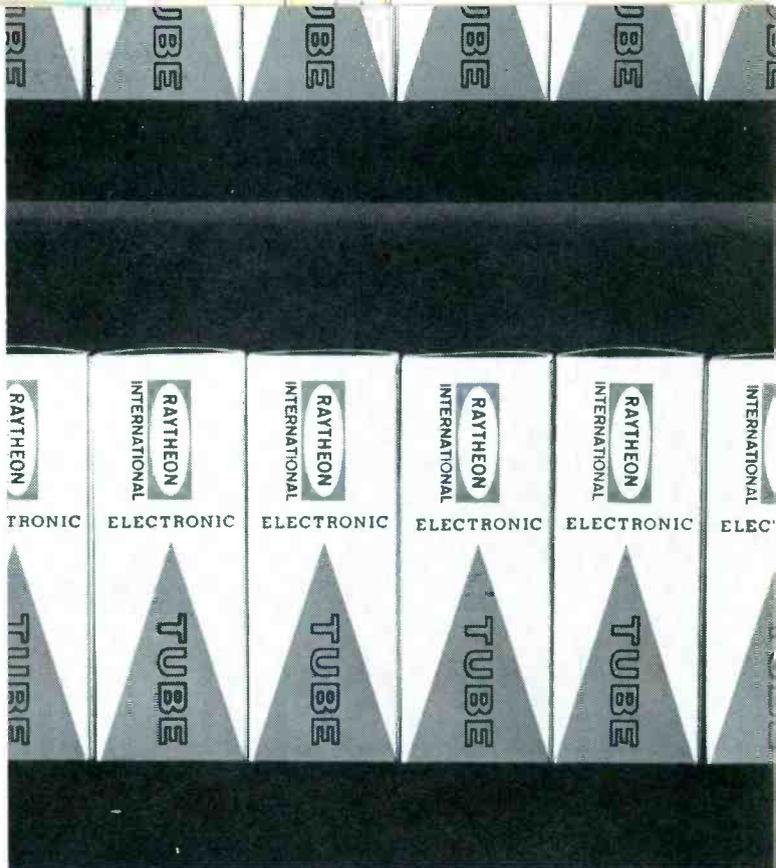


Fig. 3. Peak-limiting resistor in supply filter.

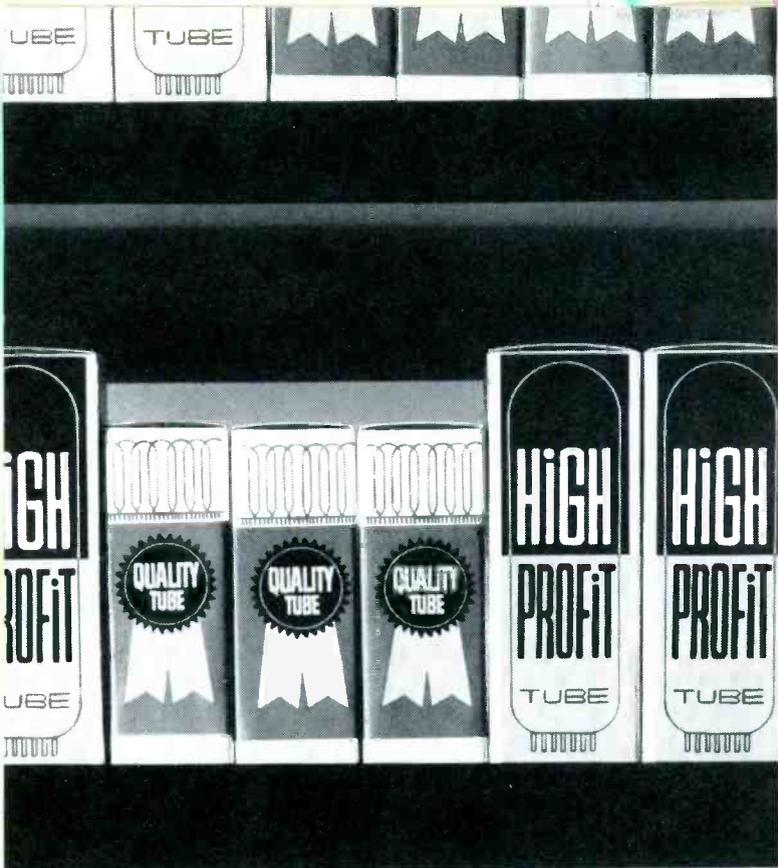

why stock two? Raytheon gives you both in one carton

Raytheon's International line puts high quality and high profits in one neat package — where they belong! Raytheon International tubes are designed, manufactured and tested by selected foreign producers in accordance with Raytheon specifications and U.S. industry standards. Characteristics are controlled for exact interchangeability and newer types are continually being developed to keep pace with your replacement needs. Right now, for example, 92% of all socket requirements

can be filled immediately by Raytheon International's 284 types.

Raytheon's 40 years of experience plus the Good Housekeeping Seal of Approval provide your customers with the finest warranty in the business. Add a good healthy profit margin for you and you have all the reasons for stocking and selling Raytheon's International line. See your Raytheon Distributor for complete details.

Circle 31 on literature card



resistor. As its name signifies, this device has a resistive element which opens when excessive current passes through it. Such resistors are often of plug-in design, such as R2 in the voltage-doubler power supply shown in Fig. 4. In other cases, they have pigtailed which allow them to be soldered into the circuit.

Common resistance values for fusible resistors are 4.7, 5, 5.6, 7.5, 9, and 22 ohms. Always replace a fusible resistor with one of the same type and identical resistance; never replace one with a conventional resistor.

Thermistor-Type Protective Devices

The resistance of a tube filament is low when the tube is cold and high when it is hot. This variation introduces a problem in sets employing series-connected filament strings; when the set is first turned on, the current can be high enough to burn out one of the tubes or at least to shorten their life. As the tubes come up to normal operating temperature, their filament resistance rises, and the current settles to normal.

A filament-protective resistor au-

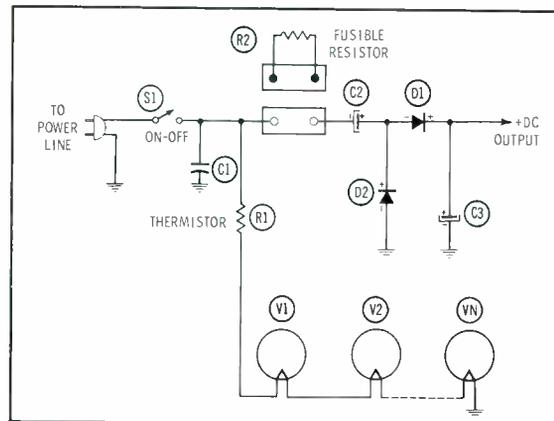


Fig. 4. Two types of protective resistors are often used in television power supplies.

tomatically prevents such a damaging initial surge of current. This component is a type of thermistor (thermally-sensitive resistor). It has a resistance-temperature characteristic opposite to that of the tube filaments; its cold resistance is high, and its hot resistance is low. When the set is first switched on, the thermistor limits the filament current to a safe value. As the filaments come up to temperature their resistance increases. At the same time, the resistance of the thermistor decreases, and the current is allowed to reach its normal level. A resistor of this type is shown as R1 in Fig. 4. Such filament-protective devices are available from most manufacturers of standard resistors and resistor elements. Always use an exact replacement for a broken or defective filament protector.

Sometimes an entire receiver is protected by a thermistor-type regulating resistor connected in series with the power line and the entire receiver circuit. This type of protector limits a potentially destructive voltage surge to about 25% of normal, but still allows full voltage to be applied to the circuit after warm-up. These protective resistors are invaluable when selenium rectifiers are replaced with silicon diodes, because of the higher voltage output.

Conclusion

While much of the information presented in this article may seem obvious and elementary, the very nature of protective devices makes them easy to overlook or treat lightly. Such a lapse on your part can result in damage to the equipment and expenditure of excessive time, both of which cost you money. Let these devices do their job, and you'll receive the benefits. ▲

More useful than ever!

ALL New!
COMPLETELY INTEGRATED
B&K
CRT 445
Checks and Corrects
B & W and COLOR
Picture Tube Troubles

THE INDUSTRY'S STANDARD

*Most Widely Used Today
by Professional Servicemen*

Includes all desired features. Does the job in a few minutes right in the home without removing tube from TV set.

**SAVES CUSTOMERS—ADDS SERVICE INCOME
MAKES NEW TUBE SALES EASIER**

Gives new life to weak or inoperative tubes. Checks for leakage, shorts, open circuits and emission. Removes inter-element shorts and leakage. Repairs open circuits and low emission. Restores emission and brightness. Life Test checks gas content and predicts remaining useful life of picture tube. Quickly pays for itself. Net, \$74.95

TESTS AND REJUVENATES

all picture tubes at correct filament voltage from 1 to 12 volts.

TESTS AND REJUVENATES

all Hi G-2 and Lo G-2 picture tubes, including tubes that require as low a G-2 voltage as 30 volts. Supplies all three necessary voltages: Hi G-2, Low-1 G-2, and Lo-2 G-2.

TESTS AND REJUVENATES


110° tubes and the new 19" and 23" tubes.

TESTS AND REJUVENATES

color picture tubes, including the new 90° 23" 23BG22. Checks and corrects each gun of color tube separately.

<p>Subscribe to New Picture Tube Information Service</p>	<p>UP-DATE YOUR B&K CRT WITH THESE ACCESSORIES</p>
	<p>Model C40 Adapter. For use with previous Models 400 and 350 CRT's—to test and rejuvenate TV color picture tubes and 6.3 volt 110° picture tubes. Net, \$9.95</p> <p>Model CR48 Adapter. For use with previous Models 400 and 350 CRT's—to test and rejuvenate 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. Net, \$4.95</p>
<p>See Your B&K Distributor, or Write for Catalog AP21-R</p>	<p>B&K MANUFACTURING CO. DIVISION OF DYNASCAN CORPORATION 1801 W. BELLE PLAINE AVE. - CHICAGO 13, ILL. Canada: Atlas Radio Corp., 50 Whiggold, Toronto 19, Ont. Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.</p>

Circle 32 on literature card

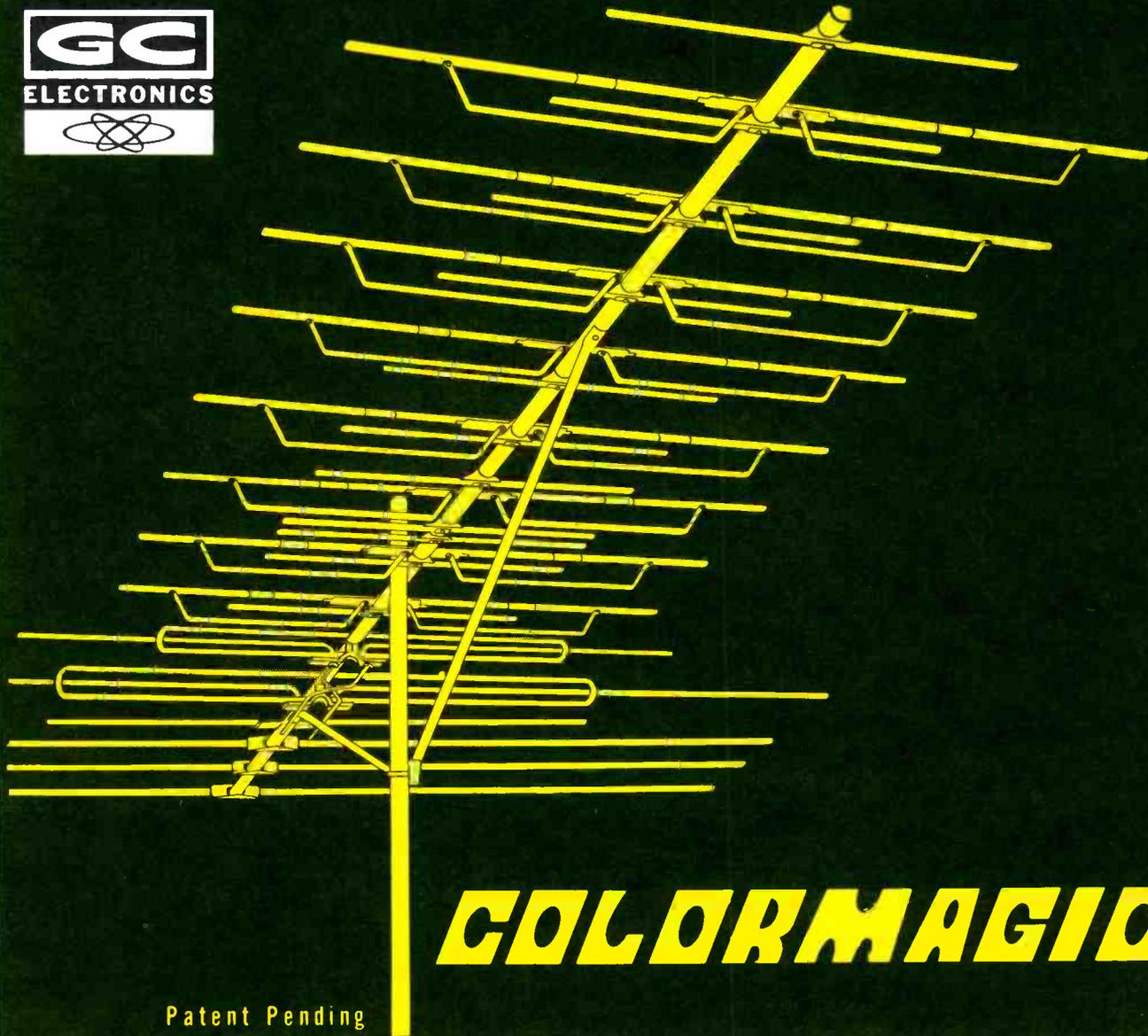

COLORMAGIC

Patent Pending


FHR

FUNDAMENTAL HARMONIC RESONANCE...GC'S EXCLUSIVE DESIGN PROCESS! Colormagic elements resonate on the fundamental harmonics within both the high and low bands. Colormagic FHR outperforms the average second harmonic TV element by producing a tight, laser-linked directivity of signal...higher gain! It's in the elements!

GC "GOLD-GUARD" anodizing process guards against pitting, chipping, rust and corrosion...makes the Colormagic series the best protected, all-weather line available!

GC "SOLID-SEMBLED" construction insures quick, easy installation...rigid-lock elements snap securely into place!

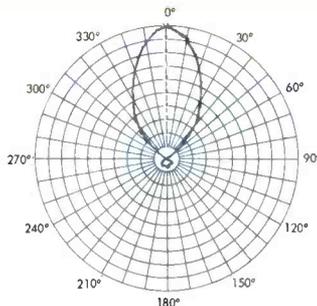Compare! Colormagic Antenna Systems offer pencil-point polar patterns...laser-linked directivity...flat plateau response curve...no traps or peaks...excellent for color or black & white TV reception.



15 All-New Colormagic Combo-Couplers permit cross-direction reception of UHF-VHF-FM antenna combinations...each unit encased in high-impact polystyrene case...supplied with stainless Steel mounting strap. Complete sales program available.



See your GC Distributor! He'll fill you in on this "prestige" package. **CONSIDER THE ELEMENTS INVOLVED!** ...then GO COLORMAGIC! If not stocked locally, write us for name of Distributor nearest you.

GC ELECTRONICS CO.
Division of Textron Electronics, Inc.

Western Plant: 3225 Exposition Place, Los Angeles 18, Calif.
MAIN PLANT: 400 S. Wyman St., Rockford, Ill., U.S.A.

Circle 33 on literature card

Transistorized

UHF TUNERS

A servicing analysis of the newest tuners . . . by Allen B. Smith

The all-channel ruling which became effective on April 30 this year has many implications of interest to the television serviceman. The most important of these implications is undoubtedly the fact that we are going to be faced with a little "black box," the UHF tuner, with which some may be unfamiliar. Most of the VHF-only sets will have been sold by early Fall, and from that time on, UHF tuners will be increasingly evident in shops throughout the country.

Most of the UHF tuners that have reached the market so far have used tube-type oscillators, but transistorized tuners are becoming more popular. This is true for several reasons, not the least of which is that the advent of economical high-frequency transistors has brought the cost of transistorized tuners in line with that of tube types, allowing manufacturers to ride the crest of solid-state consumer enthusiasm.

There are other practical reasons, some mechanical and some electrical, which will increase the number of transistor UHF tuners. A transistor soldered directly into the oscillator circuit eliminates several

potential problems in mechanical orientation and does away with the socket, feedthrough capacitor, and heater choke. Cooler operation reduces the effects of heat on frequency-determining components, all of which are relatively critical at ultra-high frequencies. A single model of a transistorized tuner may be used with either series-string filaments or transformer-powered ones, as the tuner requires only one power connection. Finally, since most of the troubles in earlier UHF tuners can be traced to the oscillator tube, the increased reliability and longer life expectancy of planar-epitaxial NPN transistors promise greater trouble-free operation. With the certainty, then, of more transistorized tuners, let's examine them a little more closely.

UHF Fundamentals

Perhaps it would be advisable to review a few of the peculiarities inherent in working with ultra-high frequencies. The most characteristic difference between UHF and VHF circuits is the manner in which UHF signals react to standard inductors

and capacitors. At frequencies in the region from approximately 450 mc to 900 mc, the familiar helical-wound inductors not only exhibit excessive inductance and distributed capacitance, but also fail to provide a suitably high Q for efficient tuned circuit use. Similarly, the usual multiplate capacitor suffers from excessive capacitance and internal inductance, and its physical design contributes to high circuit losses. Since the UHF-TV band is in the rather awkward region where tuned cavities are too large and standard tuned circuits are too inefficient, UHF tuners utilize inductors and capacitors of specialized configuration. Generally speaking, an inductor at ultra-high frequencies will be a single rod or bar, and its companion capacitor will consist of two or three adjustable plates adjacent to an extension of the inductor.

Fig. 1A shows the construction of a typical series-tuned resonant circuit in which the inductor is a rod with two flattened portions which form the stator plates of the capacitor. The rotor plates are mounted on the tuning shaft. The schematic

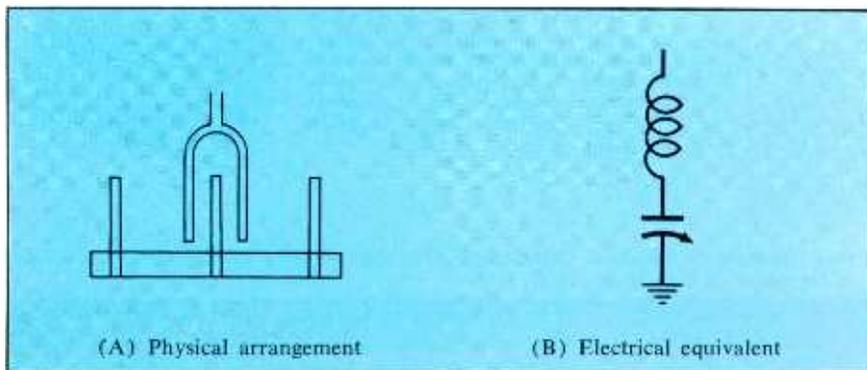


Fig. 1. Physical and electrical arrangement of a typical series-tuned UHF tank circuit.


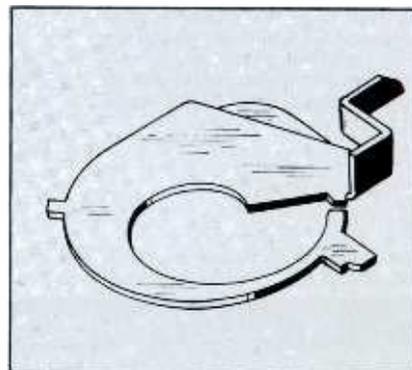


Fig. 2. Ring inductor found in some tuners.

HIGH FIDELITY SERVICING...

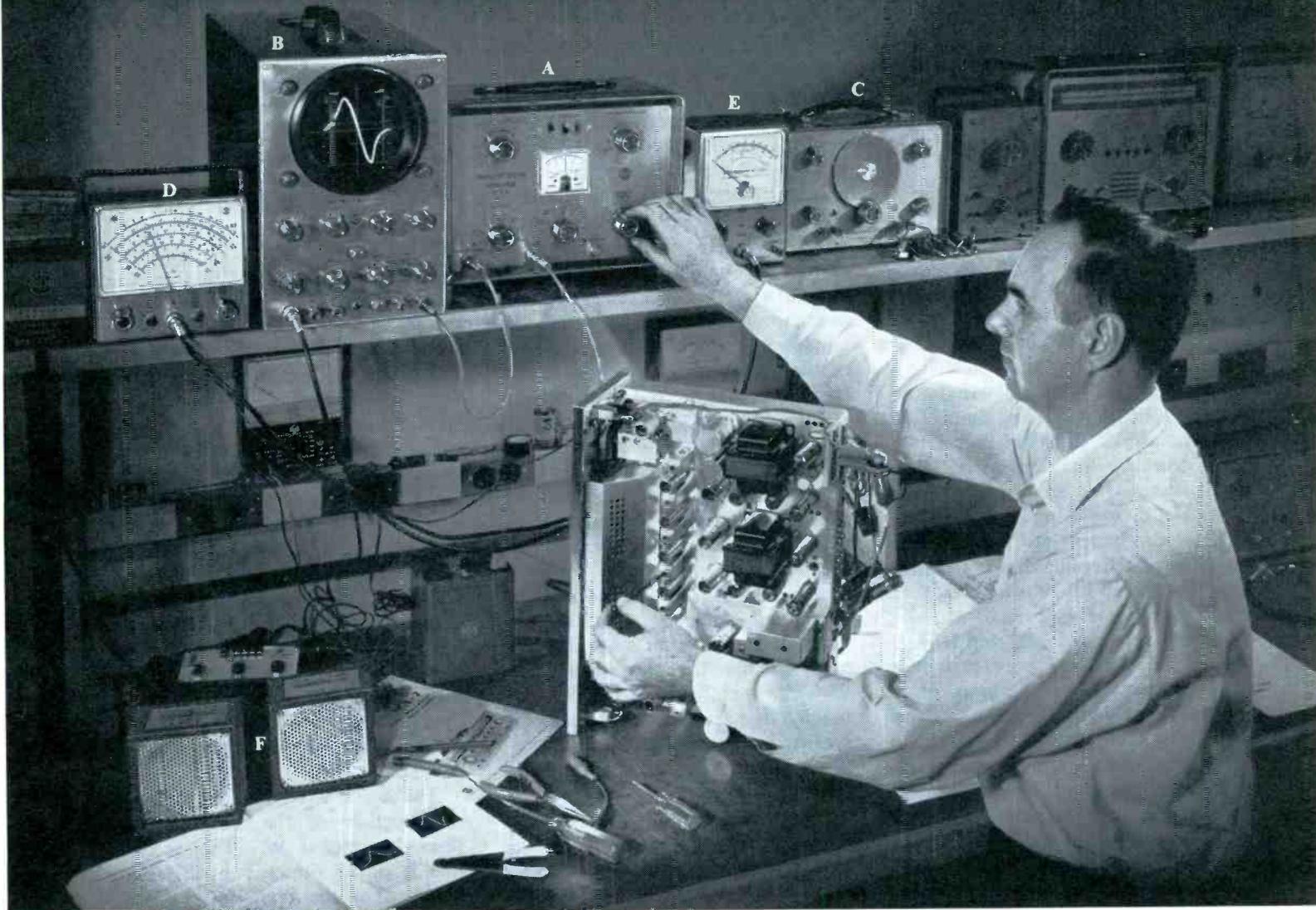FAST, EASY, SURE AND PROFITABLE WITH RCA TEST INSTRUMENTS



Aligning the discriminator in an FM multiplex stereo receiver, using an RCA WR-51A Stereo FM Signal Simulator and an RCA WO-91A Oscilloscope. Display on scope screen is the trace obtained at the output of a properly aligned discriminator.

(A) RCA WR-51A FM STEREO SIGNAL SIMULATOR

Generates: 4 FM signals—Left Stereo, Right Stereo, Special Phase Test, Monaural FM • 8 sine-wave frequencies available separately or for modulating FM signals • 100 Mc carrier tuneable ± 0.8 Mc to permit selection of a quiet point in the FM band. 19Kc subcarrier, crystal-controlled within ± 2 cps • 100 Mc sweep signal adjustable from 0 to 750 Kc at 60 cps rate • 3 composite stereo output signals. **\$249.50***

(B) RCA WO-91A 5" OSCILLOSCOPE


A high-performance, wide-band 'scope—serves as a display type VTVM. Choice of wide band (4.5 Mc—0.053-volt rms/inch sensitivity) or narrow, high-sensitivity band (1.5 Mc—0.018-volt rms/inch sensitivity). **\$249.50***

(C) RCA WA-44C AUDIO GENERATOR

Generates sine-wave and square-wave signals over range of 20 to 200,000 cps to test audio systems. Used to measure intermodulation distortion, frequency response, input and output impedance, speaker resonance, transient response, and phase shifts. **\$98.50***

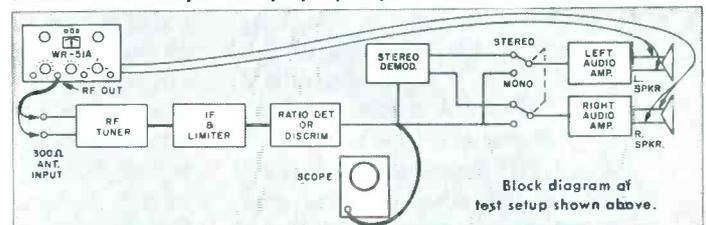(D) RCA WV-98C SENIOR VOLTOHMYST®

For direct reading of peak-to-peak voltages of complex waveforms, rms values of sine-waves, DC voltages, and resistance. Color-coded scales differentiate peak-to-peak from rms readings. Special 0.5-volt full scale DC range for use in low-voltage transistor circuits. $5\frac{1}{2}$ " meter. **\$79.50***



(E) RCA WV-76A AC VTVM

Measures AC voltages down to 0.0002 volt. Decibel scale for measurements from -40 to +40 db. Built-in amplifier which may be used separately as a pre-amplifier. Typical applications: frequency response tests; signal tracing; measurements of audio level, power level, and gain; amplifier balancing and general audio voltage measurements. **\$79.95***

(F) RCA WG-360A STEREO PHASE CHECKER

A quick, simple, positive way to check phase alignment of low and mid-range speakers in stereo systems. Completely "sound-powered". For use with a VOM, VTVM, or oscilloscope. **\$14.95*** See them all at your Authorized RCA Test Equipment Distributor.

**Optional Distributor Resale Price All prices are subject to change without notice. Prices may be higher in Alaska, Hawaii and the West.*

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



The Most Trusted Name in Electronics

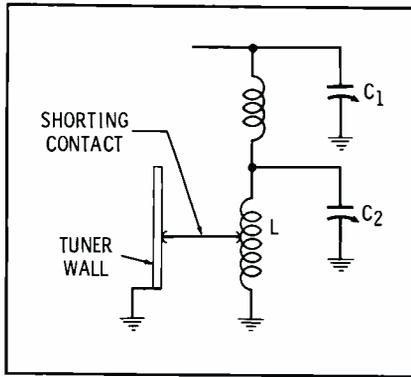


Fig. 3. Schematic of inductance-ring type.

equivalent is shown in Fig. 1B. Both the inductor rod and the capacitor plates are silver plated to minimize losses by "skin effect."

In a second type of UHF tuned circuit, the inductor is shaped as shown in Fig. 2. This inductance ring normally functions as one side of a tuned line of approximately one-twelfth wavelength at 470 mc. The other element of the tuned line is a flat plate mounted near the ring and parallel to it. In usual practice, the plate is one wall of, or a partition in, the tuner. The ring is then tuned by a rotary contact which progressively shorts portions of it to the wall. The radial width of the ring is tapered to provide a straight-line frequency characteristic. The ring, the adjacent wall, and the wiper are all silver plated; the ring has an additional gold flashing to aid in controlling wear and to avoid electrochemical erosion of the elements in the inductance circuit. A schematic representation of this circuit is shown in Fig. 3. Tracking adjustment at the low edge of the band (470 mc) is accomplished with C2, while C1 adjusts tracking at the high end (890 mc).

Most UHF tuners use some form of one or the other of these two

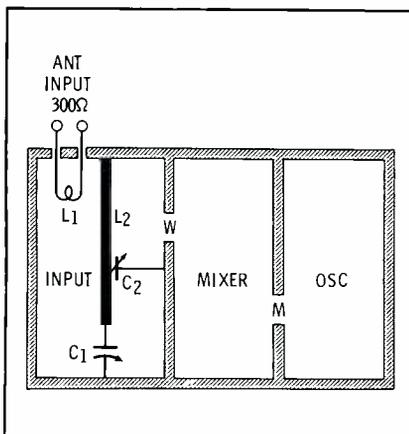


Fig. 4. Case configuration of typical tuner.

basic configurations, differing primarily in mechanical characteristics.

Mechanical Considerations

A typical UHF tuner is constructed in a rigid, three-compartment case formed from heavy-gauge copper. Since tuned UHF circuits depend heavily upon mechanical rigidity for their stability, this type of construction provides the required ruggedness and additionally offers a means of isolating each stage: the unamplified preselector input stage, the mixer, and the local oscillator. Radiation from the oscillator is minimized, and shielding of the preselector is also enhanced by the compartmented approach.

Fig. 4 shows typical case construction along with a schematic representation of the input or preselector circuit. Each compartment is approximately the same size as the others and will contain the tuned-circuit components for that stage and some or all of the remaining circuit elements. Coupling between the preselector stage and the mixer is capacitive, through window W. The mixer circuit itself is not tuned; the second tuned line increases image rejection by the preselector and matches the antenna circuit to the mixer.

Since the mixer diode is located in the same compartment as the second tuned antenna circuit, the input signal is usually coupled inductively to the diode. In some tuners, however, the signal is direct-coupled to the mixer by means of an autotransformer. The diode itself (usually a 1N82A or equivalent) is most often mounted in a pair of clips to facilitate replacement or testing, but may be soldered into the circuit. A bent loop projecting into the oscillator compartment through window M couples the injection signal from the oscillator to the mixer.

The oscillator compartment contains the tuning circuit, the trimmers, and—in most tuners—the oscillator transistor itself with its related components. In some tuners, the oscillator transistor and its companion circuitry are mounted externally.

Basic Circuitry

For a typical UHF tuner incorporating a tuned passive input, a diode

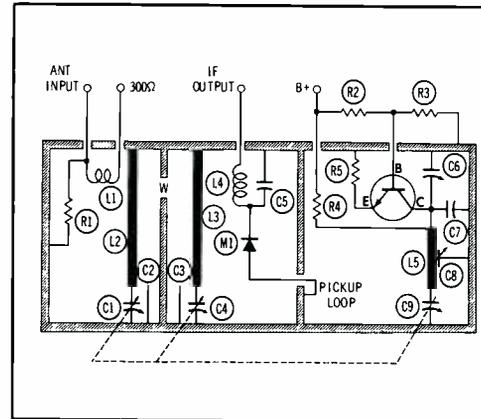


Fig. 5. Schematic of a typical UHF tuner. mixer, and an internally mounted transistor oscillator, the schematic will resemble that shown in Fig. 5. Other types of tuners are essentially similar—enough so that a single explanation should serve for most basic circuit functions.

A station signal in the range of 470 mc to 890 mc is coupled to the first tuned antenna line through L1, which consists of a few turns of wire in a loop mounted adjacent to inductance (rod) L2. The input line is tuned to frequency by C1; capacitor C2 is a trimmer for the high end and consists of a narrow metal tab which can be bent toward or away from the electrostatic field of C1.

The signal is coupled to the second section of the antenna line through window W. The second line is tuned similarly by C4 and trimmed at the high end by C3. Coupling to mixer diode M1 is inductive since the diode lead is located in the field of the tuned line.

The oscillator section is mechanically similar to the others, and is fairly simple electrically. A tuned line (L5, C9) tunes the modified Colpitts oscillator; capacitor C6 trims the low end, and trimmer C8, the high end. Operating voltage is obtained from the low-voltage supply in the set through a series dropping resistor. The supply voltage varies among different tuners, generally ranging between 12 and 20 volts DC. RF voltage from the oscillator is coupled to the anode of the mixer diode by means of the pickup loop which projects into the oscillator compartment. IF output from the mixer is generally around 40-45 mc.

It is apparent, then, that this little box which at first seemed a bit perplexing is really a pretty simple

ALLIANCE C-225...

THE ONLY SOLID STATE TENNA-ROTOR®



TV's better color getter...

Distributors and dealers are enjoying amazing sales results with the solid state C-225 Tenna-Rotor®.

Its patented phase-sensing bridge circuit is patterned after scientific test equipment to afford the TV and FM stereo owner life-like 'studio' reception.


Alliance Tenna-Rotors are built to handle today's larger new antennas. They will support, hold and turn any antenna that can be lifted and placed on them. Careful workmanship and precision components provide longer life and dependable, trouble-free operation.

Check the C-225 "plus" features

- accurate repeatability
- constant synchronization
- silent operation
- greater sensitivity

Quality features you expect from the world's leading manufacturer of antenna rotating devices. Sell the line you sell with confidence—Alliance Tenna-Rotor®!

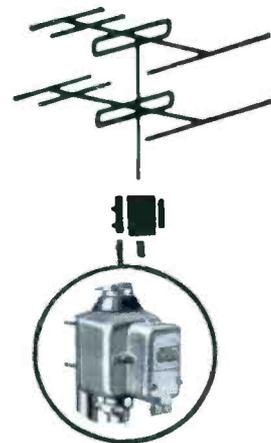Order the C-225 and other quality Alliance models today.



The **ALLIANCE** Manufacturing Co., Inc., Alliance, Ohio

(Subsidiary of Consolidated Electronic Industries Corp.)

Circle 36 on literature card

component once a few basic considerations are established.

Servicing Hints

Because the basic tuner case is sturdy, and all components are firmly mounted to it, we can reasonably expect few mechanical problems. The rotor elements of the ganged tuning capacitors, as a rule, will also remain trouble free. Barring outright mistreatment, therefore, mechanical faults should be minimal. The simplicity of the circuitry also suggests that we could expect few

problems from components. This is generally true, except in the case of the transistor itself, and in that of the diode to a lesser extent.

The 1N82A mixer diode, commonly used in many tuners, has a good noise figure and high conversion efficiency. In cases where the picture becomes snowy (sound remains good), the diode should be suspected. Since most tuners use a double clip to hold the diode, replacement is easy; and no realignment will be required.

While mixer faults are relatively

uncomplicated, those contributed by the transistor are in a different category. Because most manufacturers solder the transistor into the circuit, the serviceman is faced with a variety of prospects. Its location in a rather cramped space means that, should replacement be required, extreme caution must be exercised to keep from damaging nearby components and to avoid physical misalignment of frequency-critical circuit elements. The use of a soldering aid and the application of heat for short periods only (no more than five seconds) is recommended by some tuner manufacturers. Most service bulletins also stipulate the use of 3% silver solder in all replacement operations involving RF components, including silvered-button capacitors and feed-throughs. Voltage measurements to determine proper operation of the oscillator should be taken from the manufacturer's service data.

Alignment

Extremely important to the proper servicing of UHF tuners is the realization that efficient UHF tuner operation (and therefore proper operation of the entire set) depends heavily upon correct tuner alignment. Since replacement of any component in the oscillator compartment will in all probability detune the entire stage, a complete realignment is in order whenever replacements are made. Time consuming? Perhaps yes, initially, but once the proper equipment setup and procedure has been established, you'll find it takes only a few minutes; the rewards in increased tuner efficiency and customer goodwill will be large and profitable.

Various manufacturers have different suggestions regarding alignment, but the basic procedure is the same and requires a UHF sweep generator with a 300-ohm matching pad, an oscilloscope, a marker generator, and a milliammeter to check the mixer-diode injection current. The steps prior to alignment are simple:

1. Allow about 15 minutes warmup time.
2. Make all adjustments with oscillator cover in place.
3. Check service data for location of adjustments and for specific procedures.

A NEW CONCEPT IN COLOR TV ANALYZING PUTS YOU IN THE PROFITABLE COLOR TV SERVICE PICTURE AT A VERY LOW COST



**Model 900
COLOR TV
ANALYZER**

- Checks color, video and picture tube circuits
- Checks the overall performance of color TV sets
- Provides for fast purity, convergence and gray scale tracking adjustments

Color TV set sales are booming all over the country! To help progressive servicemen get their share of the color service business Mercury has developed a highly efficient instrument based on an ingenious new engineering concept in color TV analyzing. The Model 900 Color TV Analyzer enables you to tackle color TV servicing in the home and in the shop with ease and confidence at a minimum cost.

FEATURES

- ✓ Makes all tests dynamically while color set is in operation
- ✓ Exclusive circuit eliminates need of range switches. Just set element selector and meter is automatically on right range
- ✓ Connects as easily as a picture tube brightener...no need to get under TV chassis
- ✓ Safety feature...circuit allows safe measurement up to 7000 volts on focus grid

See your electronics parts distributor or write for complete Mercury catalog

\$4495 Slightly higher in the West

MAKE ANY ONE OF THESE TESTS IN MINUTES

- TEST each control grid voltage... indicates shorts or gas in each color gun
- TEST each color gun screen voltage and screen current... indicates trouble in power supply or boost circuits
- TEST focus voltage... indicates high voltage or horizontal deflection circuit trouble
- TEST each cathode voltage... indicates circuit trouble
- TEST each control grid emission current... indicates shorts or gas in each color gun
- TEST each color gun cathode emission... indicates dynamic quality of each color gun.

The Model 900 enables you to cut-out color guns in any combination and adjust for proper PURITY—CONVERGENCE—and GRAY SCALE TRACKING.

NEW



Mercury ELECTRONICS CORPORATION
manufacturers of quality electronic products
 111 Roosevelt Avenue, Mineola, New York
 IN CANADA: R. C. Kahnert Sales Ltd., 359 Entford Rd., Richmond Hill, Ontario

Circle 37 on literature card

1958...the RCA Radio-Phone Series

1959...the RCA Mark VII

1963...the RCA Mark VIII

and now 1964...

THE NEW RCA MARK NINE

the latest and greatest RCA CB radio of them all

Look at some of the new features...



NEW! Combination "S" Meter and Relative RF Output Meter

"S" Meter indicates the relative strength of incoming signal in "S" units. RF Output Meter (EO) indicates relative strength of the signal being transmitted.

NEW! Spotting Switch

Permits precise manual tuning of receiver without use of receiver crystals. Receiver can be tuned (or "spotted") quickly to any incoming channel. This means, when you buy crystals for extra channels, you can (if you wish) omit the RECEIVE crystals and buy only TRANSMIT crystals.

NEW! External Speaker Jack

Lets you connect an external speaker to the set, so incoming calls can be heard in remote locations.

RCA, a pioneer in the development of citizens' band radio, has been providing quality equipment since the inception of the Class D Citizens' Radio Service in 1958. Now, these years of experience culminate in the great new RCA Mark Nine.

- 9 fixed crystal-controlled TRANSMIT/RECEIVE channels, separately controlled
- All-channel continuously tunable receiver
- Illuminated meter and working channel indicator
- Push-to-talk ceramic mike with coiled cord

ONLY \$13475*

AC UNIT

*Optional User Price



The Most Trusted Name in Electronics

Get all the Facts Before You Buy.
Mail Coupon Today. Paste on 4¢ Post-Card


RCA ELECTRONIC COMPONENTS AND DEVICES
Commercial Engineering Dept.133R....
415 South Fifth Street, Harrison, N. J.

Please send more information on the RCA Mark
Nine CB Radiophone

Name _____

Address _____

City _____ Zone _____ State _____

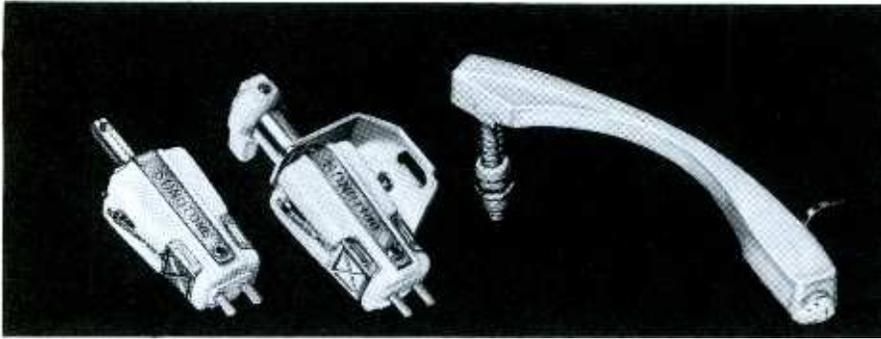

How to turn crystal



into gold

You can strike it rich with the new Sonotone line of crystal cartridges. It offers direct replacements for "Ronette," "Vaco" and "BSR" models with typical Sonotone quality.

Here are the extras you get—New improved crystal elements for longer pickup life. Mono ("14T") and stereo ("20T") models. High output voltage. Modern turnover type for LP, 45 and 78 rpm records. Available with or without mounting brackets or turnover knobs to fit most arms.

Oh yes, they come in a slim, lightweight plastic tonearm, too. You have a choice of the mono ("14T") or stereo ("20T") cartridge. It's easy to install because it's prewired. It has a shielded cable, spring mounting post and a plated finger lift. It's complete with arm rest and all necessary hardware. Get details today. Write:

SONOTONE
audio products

Sonotone Corp., Electronic Applications Div., Elmsford, New York
Cartridges • Speakers • Microphones • Headphones • Hearing Aids • Batteries

Circle 39 on literature card

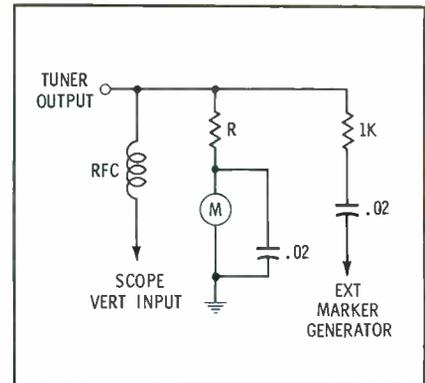


Fig. 6. Setup for sweep alignment of tuner.

4. Use matching pad between sweep generator and tuner input terminals.

Actual alignment is nearly as straightforward:

1. Connect tuner output to scope through circuit similar to that shown in Fig. 6. Meter has 0-5 ma range. Resistance of R plus that of the meter should total 20 ohms.
2. Set tuning control to low end and set marker generator to specified center of bandpass curve (check service data). Set sweep generator at 468 mc. Adjust low-end trimmer until marker is centered on curve as seen on scope.
3. Set tuning control to high end and sweep generator to 900 mc. Marker generator remains at same specified center frequency as in Step 2. Adjust high-end trimmer to center marker as in Step 2.
4. With all controls as in Step 3, adjust mixer pickup loop by bending in or out of oscillator compartment for milliammeter reading of .75 to 2.25 ma (for 1N82A).
5. As final check, tune through entire range (channel 14 to 82) to see that mixer injection current stays within manufacturer's tolerance. If it does not, re-adjust pickup loop until it does.

Conclusion

All-channel transistorized tuners can mean increased problems for any serviceman who leaps before he looks. A few moments spent in a review of UHF fundamentals and with the manufacturer's service suggestions can make the "little boxes" a means of creating among your customers increased respect for and confidence in your ability. ▲

NEW . . . JUST \$119.50 FOR A COMPLETE COLOR BAR GENERATOR WITH EXCLUSIVE SECO STABILITY!

- 15-second warmup for your convenience
- Day-long performance without variation
- Simple sync control—just vertical and horizontal hold
- Work-a-day ruggedness—crystal controlled in heavy metal case

JUST IN TIME FOR THE BIG BOOM IN COLOR TV!

Cash in on the bigger volume coming from the new lower cost color TV's. Here are two color bar generators built to take the toughest use in truck or shop. Fast hookup—just clip on two antenna leads. Foolproof crystal controlled color bars. Fast warm up. Highly stable, after just 15 seconds and all day long—speeds work in home or at bench. Factory set to Channel 3 and can be tuned to Channels 2 or 4. Steel case. See your electronic supply dealer or write for information.



MODEL 980 does everything you need to set up a color TV set

- **KEYED COLOR BARS** for aligning and trouble shooting color circuitry—10 standard bars.
- **DOT PATTERN** for DC or static convergence—54 dots.
- **CROSSHATCH** for dynamic convergence, overscan and linearity adjustments—6 horizontal bars, 9 vertical bars.
- **VERTICAL BARS** for adjusting dynamic horizontal convergence controls—9 vertical bars.
- **HORIZONTAL BARS** for adjusting dynamic vertical convergence controls—6 horizontal bars.

ONLY \$119.50 net

MODEL 990 gives you all the deluxe features!

- **ALL** the tests of the Model 980—with these extra advantages—
- **COLOR GUN KILLER** to actuate any combination of guns.
- **RAINBOW COLOR PATTERN** to supplement keyed color bar tests.
- **VARIABLE DOT PATTERN** with 54 or 144 dots of adjustable size.
- **VARIABLE CROSSHATCH** with 6 or 16 horizontal bars.
- **VARIABLE HORIZONTAL BARS** with 6 or 18 lines.
- **GREY RASTER** for tests required on older sets.

ONLY \$149.50 net




SECO also manufactures a full line of tube testers

SECO ELECTRONICS, INC.

Circle 40 on literature card

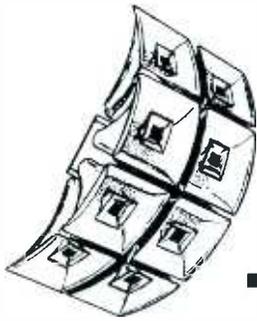1221 S. CLOVER DRIVE • MINNEAPOLIS, MINNESOTA 55420
A DIVISION OF DI-ACRO CORPORATION



AUDIO —SIDELINE or MAINLINE?

Whenever you contemplate adding a new line to your present servicing (or selling) business, there arises the immediate question—is the new undertaking to be a sideline or mainline? That is to say, will it merely be an addition to your present activities, or do you plan to make the new line your predominant one? In arriving at a decision, a number of factors must be considered: Is there a lasting demand for this particular product or service? If such a demand doesn't already exist, can it be created? If new investments are necessary, can they be reconciled with the expected volume of business? By arriving at honest answers to these questions, you can determine how extensively you should go into the new business activity.

Is There A Market?

Obviously, you can't expect a new business line to be successful if nobody is interested in buying your goods or services. Therefore, the first step in deciding whether to start such an enterprise is to analyze the potential market.

Types of Markets

The reproduction of sound finds application in many different ways. The one that first comes to mind is the area of home entertainment—high fidelity. Several factors influence the demand for high-fidelity equipment in a given area. The people's tastes in music influence how fidelity-conscious they are. If most of the people in a community have modest incomes, the market for costly stereo systems will be small. On the other hand, in an area of high-income families there is a good prospect of selling and servicing expensive stereo high-fidelity equipment. In an area of the latter type, the technician who really knows audio can earn a sizeable income by making custom installations. Naturally, these factors are variable, but as a member of the community you should have a pretty good idea about conditions in your locality.

A demand for public-address and intercom systems can be encouraged in most communities. Churches, manufacturing plants, and schools are prime prospects

in this regard. A little investigation will enable you to make a good estimate of the number of customers you can expect to attract. You may find that a considerable market for rental equipment exists.

Schools in particular are making extensive use of sound equipment. Complex intercom and audio-distribution systems are finding increased use. Audio teaching aids of numerous types are being used for language instruction and other purposes. Even though such systems may already be installed, they represent potential servicing jobs in the event you decide to go into that phase of the business. If you decide to establish a really ambitious audio department, you may want to seek some design and/or installation projects as well. Keep in mind, though, that activity of this sort requires highly specialized skills and tools. If you enter such a field poorly prepared, you will very likely be in for trouble.

One good way to build up an audio servicing business is to sign a contract to do service work for one or more retailers, discount houses, etc., who sell audio equipment. This can bring you a sizeable portion of the market in one stroke. You may also choose to collect the results of your market survey and use them as a selling point in obtaining service contracts or dealer franchises from one or more manufacturers or suppliers of audio equipment.

Competition

Another important factor to be considered in evaluating your potential market is the nature of the competition. If a competitor is already catering to the audio trade, you must be especially careful in evaluating the demand. Is there really enough business for more than one shop? Remember that when you enter the picture your competitor is going to step up his efforts, and he will have the advantage of being already established. Also consider the possibility that other shops not now engaged in the audio business may follow your lead in entering the field. You must be prepared to do a competitive selling job. If you can't reconcile the effort required with the expected results, you would be well advised not to enter the field at all.

If you are in a one-shop community, you may really have no choice about being in the audio business, particularly as far as servicing is concerned. People will naturally bring their audio-equipment problems to you. You may find that you can increase this business with a little promotion. Furthermore, you may be able to use this service activity to launch the sale of audio equipment.

In case you are in a small community, you should be watchful for one further element of competition: The fact that you have no local competitor doesn't mean that you'll have no competition at all in the audio business. In a specialized field such as this, dealers and servicemen frequently extend their activities to neighboring communities, especially to the suburbs of larger cities. Sometimes they operate over rather wide areas. Of course, this principle can work both ways; you may decide to expand the geographic scope of your own activities.

Other Factors

When evaluating your market, consider whether it



Quick cure for focus problems in color television sets

SYMPTOMS:


- The colors have become indistinct, smeared, or "washed out."
- You agree with the customer that it is impossible to focus the television receiver by normal controls.

CAUSE:

- Focus control has been lost because the selenium Focus Rectifier has "aged," upsetting circuit parameters.

CURE:

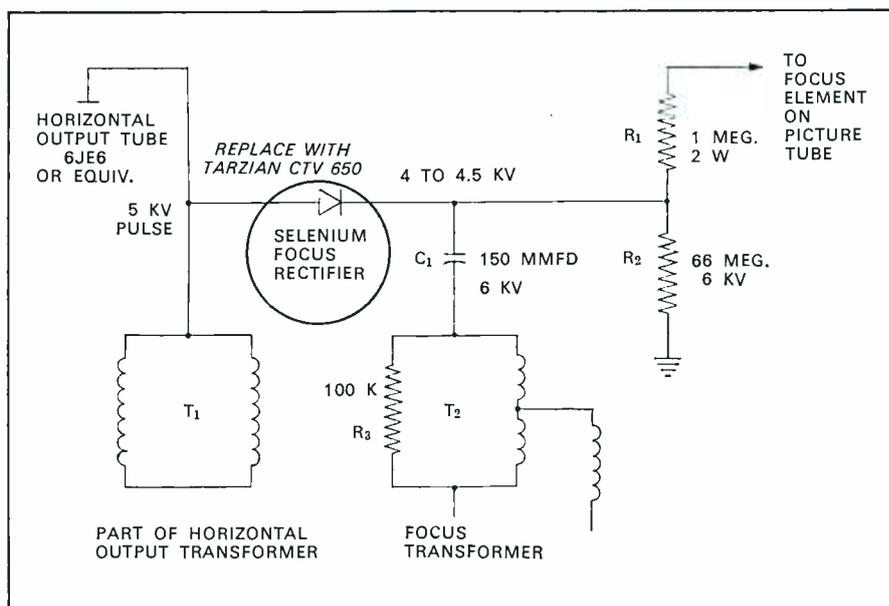- The selenium Focus Rectifier must be replaced. To do the job, select a Sarkes Tarzian Type CTV650 silicon rectifier. Because these devices exhibit no aging characteristics, they will continue to deliver full performance for the life of the set.



Insertion of Tarzian Silicon Rectifier CTV650 provides improved focus control for the life of the set.


Tarzian Silicon Rectifier Type CTV650

Is a Direct Replacement For:

Color TV Receiver	Part No.	Color TV Receiver	Part No.
Airline (Wells Gardner)	66X0035-001	Magnavox	530096-1
Dumont	1440977-1	Packard Bell	72110
Olympic	1440977-1	Philco	34-8053-2
RCA	1440977-1	Silvertone (Warwick)	86-44-3
Emerson	817123	Sylvania	16106-1
		Zenith	212-48

Tarzian CTV650 replacement rectifiers are available from your distributor. List price for this life-of-the-set device is only \$8.35.

The complete Tarzian replacement line includes silicon rectifiers and conversion kits for a variety of electronic jobs, plus tube replacement silicon rectifiers and "condensed stack" selenium rectifiers. All are immediately available from distributors throughout the United States and Canada, in the quantities and ratings you want most. FREE CATALOG 63-SI-6 is crammed with 48 pages of interesting technical information and product specifications about Tarzian Silicon Rectifiers. Send for your copy today—be sure your files (and your shelves) are up to date on the rectifier line voted first choice among service technicians year after year.

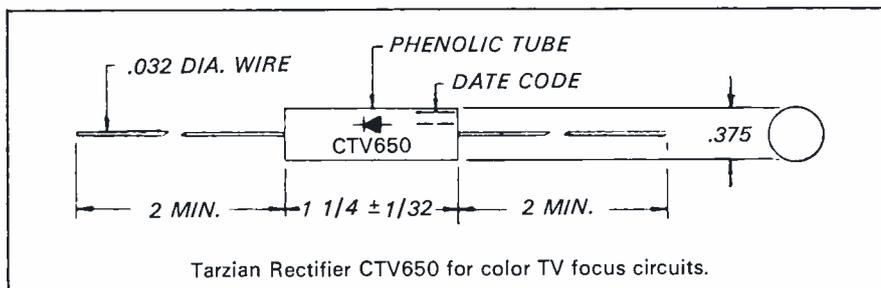

Tarzian Rectifier CTV650 for color TV focus circuits.



SARKES TARZIAN Inc.

World's Leading Manufacturers of TV and FM Tuners • Closed Circuit TV Systems • Broadcast Equipment • Air Trimmers • FM Radios • Magnetic Recording Tape • Semiconductor Devices


SEMICONDUCTOR DIVISION • BLOOMINGTON, INDIANA

Canadian Licensee: Marsland Engineering Limited • 350 Weber Street North, Waterloo, Ontario

Circle 41 on literature card

NEW
AND MOST
VERSATILE

TRIPLETT

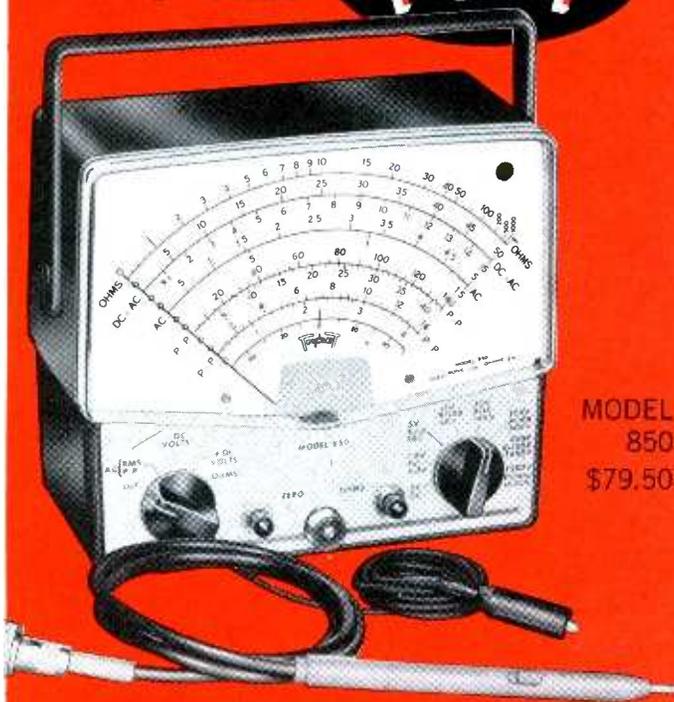

MODEL
850
\$79.50

MODEL 850
ELECTRONIC VOLT-OHMMETER
IS BEST FOR YOU

FACTS MAKE FEATURES:

- 1 Long 7" easy-to-read scale.
- 2 .5 D.C. volt range for transistor circuits.
- 3 HIGH STABILITY. Meter connected in cathode circuit of 12AU7.

High Input Impedance (11 MEGOHMS) and wide Frequency Ranges give this extremely versatile Electronic Volt-Ohmmeter considerable advantage in the measurement of DC voltages, AC RMS and Peak-to-Peak voltages. It measures directly the Peak-to-Peak values of high-frequency complex wave forms and RMS values of sine waves on separate scales.

ADDED PROTECTION. Meter is shorted out in OFF position for greater damping, meter safety during transit, electrically protected against accidental overload. ZERO CENTER mark for FM discriminator alignment, plus other galvanometer measurements.

New pencil thin test probe used for all functions: DC, AC, and ohms. No need to change cables. Beautifully styled case for professional appearance and functional utility, 7⁵/₈" x 6⁷/₁₆" x 3³/₄".

Carrying handle can be used as a tester stand to place the tester at 25° angle for ease in reading.

Frequencies to 250 MC may be measured with auxiliary Diode Probe, \$7.50 extra. DC voltages to 50 KV may be measured with auxiliary High Voltage Probe. \$20.50 extra.

TRIPLETT ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO

Circle 42 on literature card

74 PF REPORTER/September, 1964

is of a temporary or long-term nature. In a highly specialized endeavor, business may boom for a time, but then the market may become saturated. This condition is unlikely to arise in servicing (unless the particular type of equipment becomes obsolete), but it should be given some thought with regard to sales.

You can obtain useful information about the extent of the market by talking to your present customers, to retailers, etc. Try to estimate in terms of dollars and cents the amount of business you can expect from each category you investigate. As you study your market, other important factors may become evident. Investigate each of them carefully. Your estimate of potential business volume provides the basis for giving more intelligent thought to some other important considerations.

Special Requirements

Even though all electronics equipment is based on the same general operating principles, each type presents its own peculiar servicing problems. In audio you may encounter some unusual circuits; and if you are in the business very long, you are bound to be faced with mechanical devices, such as tape transports, turntables, and record-changer mechanisms. These are high-precision machines and must be treated as such.

In most audio applications, a higher level of equipment performance is demanded than is usually required in TV. This is especially true of high-fidelity installations; the really serious enthusiast will not settle for anything less than the best possible performance from his entire system. Don't be surprised if this customer hears distortion or other abnormalities that you can't. You'll find that routine methods aren't sufficient to produce the extra reduction of distortion or hum that he demands. In summary, audio servicing, if done right, requires special equipment, knowledge, skills, and tolerance of the customer's viewpoint.

Equipment

If you are going to limit your activities to servicing amplifiers and tuners alone, you may be able to get by with the test equipment you already have. However, you'll need some specialized test aids to service tape machines. A few other specialized test instruments will enable you to do a thorough job on amplifiers and tuners as well.

With these requirements in mind, a fully equipped audio service shop should have, in addition to the usual equipment: a good-quality scope, a low-distortion audio generator, a good RF generator (preferably a sweep generator), a distortion meter, an audio volt-meter (covering 1 mv to 300 volts), a wow and flutter meter, a stroboscopic speed gauge, and at least one alignment tape.

Most of these items are moderately priced and are available from several sources. Even so, and even if you already have some of the equipment, a sizeable equipment investment is indicated. If you set up a separate audio department, the equipment you already have will probably need to be duplicated. As you add up your projected equipment costs, the value of a thorough market investigation will become increasingly apparent.

Many successful shops do servicing work without, say, a wow and flutter meter. You will have to evaluate your need for each test instrument with respect to the kinds and number of repair jobs you expect to handle. Keep in mind that if you are going to undertake this type of work, you should try to provide the best service possible.

Training and Experience

As a serviceman, you know that the best test equipment made is of no value unless the technician knows how to operate it, what tests to make, why he makes them, and how to interpret the test results. To be fully competent in the field of audio—particularly in system design and installation—the technician must have knowledge of electronics, mechanics, acoustics, and sometimes even interior decorating. All this knowledge cannot be acquired overnight. You will have to read—and study—publications on the subject, talk to others in the business, enroll in a formal training course, or undertake a combination of these. All of this, of course, involves the expenditure of time and money. You'll have to weigh the expense against the results you expect to achieve.

There is, of course, a quicker way to obtain the advantages of audio-servicing training and experience: Hire a new man for the department. Obviously the amount of new business must do far more than offset the expense of paying this added employee; and if he is competent, you'll have to pay him well. Furthermore, you may have some difficulty finding such a man. Nevertheless, if you decide that you can attract enough business to keep a full-time audio man busy, this may be your best approach.

Other Considerations


An important factor to consider in both service and sales is the inventory you'll have to maintain. Do you have the necessary space? Can you justify tying up a substantial amount of money in parts and merchandise? From time to time you'll have need for unusual replacement parts. Can you afford to stock a variety of these? Will you have to stock them, or can they be obtained with relative speed from a distributor or other source?



Communications, mobile radio...

A First Class FCC License

...or Your Money Back!

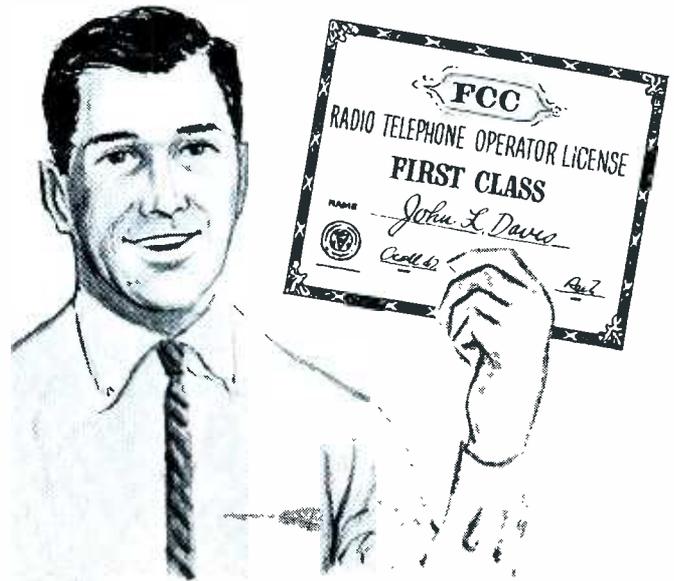

Your key to future success in electronics is a First-Class FCC License. It will permit you to operate and maintain transmitting equipment used in aviation, broadcasting, marine, microwave, mobile communications, or Citizens-Band. Cleveland Institute home study is the ideal way to get your FCC License. Here's why:

Our training programs will *quickly* prepare you for a First-Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination after completing your course, you will get a *full refund* of all tuition payments. You get an FCC License . . . or your money back!

You owe it to yourself, your family, your future to get the complete details on our "proven effective" Cleveland Institute home study. Just send the coupon below TODAY. There's no obligation.

Mail Coupon TODAY For FREE Catalog

Cleveland Institute of Electronics

1776 E. 17th St., Dept. PF-16
Cleveland, Ohio 44114

Please send FREE Career Information prepared to help me get ahead in Electronics, without further obligation.



CHECK AREA OF MOST INTEREST—

- | | |
|---|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> First Class FCC License |
| <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering | <input type="checkbox"/> Advanced Engineering |

Your present occupation _____

Name _____ (please print) Age _____

Address _____

City _____ State _____ Zip _____

Accredited Member National Home Study Council

new!

CAN MEAN EXTRA PROFITS FOR YOU!



\$6.95 DURA-GOLD FINISH **MODEL Y-7-G**

The Y-7-G is an excellent all channel UHF YAGI antenna. Sold in a "Big 6 Pack" carton that contains 7 antennas (one free) completely factory pre-assembled. Stacking kits are also available for the Y-7-G.

2 NEW GOLD UHF ANTENNAS



GUARANTEED FOR BLACK AND WHITE OR COLOR

Antennacraft's famous Model G-1483, UHF antenna operates on an extremely efficient, patented principle. It is available in several different models and can also be stacked for fringe area reception.



A dependable antenna that is completely factory pre-assembled. Saves time and "call backs."

DURA-GOLD FINISH

Pat. No. 2918672

\$9.95

See your distributor about these two big antenna values. Be ready for the UHF boom.



Circle 44 on literature card

Whether you engage in sales, service, or both, your shop must present a neat and clean appearance. If you plan to sell audio equipment, you must make provisions for displaying it. To do this effectively may require revamping your display area. First be sure you have enough space; then consider the best display method to use. In the case of high-fidelity equipment, you'll want to be able to give some sort of demonstration of systems and components. This means that the room should have reasonably good acoustics and be as free as possible from extraneous noise.

How Much Audio?

With your data collected and organized, you are ready to sit down and do some figuring. For each alternative you consider, compare your income estimate with the total projected cost. In this way you can evaluate how extensive an audio effort, if any, you should undertake. When listing estimated expenses, don't forget increased expenditures for taxes, insurance, rent, heat, light, interest, etc., where applicable. Make allowance too for extra advertising and promotional expenses.


There are several degrees of involvement you may wish to consider. You may want to try promoting audio servicing with no additional investment, using your present facilities. In most instances you will be limited in the results you can achieve with this method. You may be operating very near to capacity already, and have little time to do justice to a sideline. It may develop that you will not be able to handle all the jobs that come into your shop, and you may have to turn some customers away. This is no way to expand business. On the other hand, if the potential servicing volume seems small, you may be able to absorb it into your operation with little trouble.

At the other extreme, a large market potential may indicate the need for a complete audio sales and service department. Since you stand to lose a great deal here if you fail, great caution is indicated in considering this possibility.

No matter how good the prospects might appear, it would be inadvisable—if not downright foolhardy—to completely abandon your present, successful business in favor of a new, untried venture. However, if your new department proves successful, you may decide to make a complete transition later. This is not to say you should avoid all risk; there is a degree of risk involved in every business venture. That is what justifies a profit on your investment.

Conclusion

There is no mathematical formula you can use to determine whether or not to add a new line of business to your present activities. Similarly, no magazine article can give you a foolproof answer to this question. We have presented here some ideas to provide a starting point for your thinking. As you study the problem, other aspects peculiar to your own situation will present themselves. Consider them all carefully in terms of dollars and cents. Don't plunge blindly into a new line of business just because you feel you must try something new. Think first; weigh the pros and cons, and then make a decision according to your best judgment. ▲

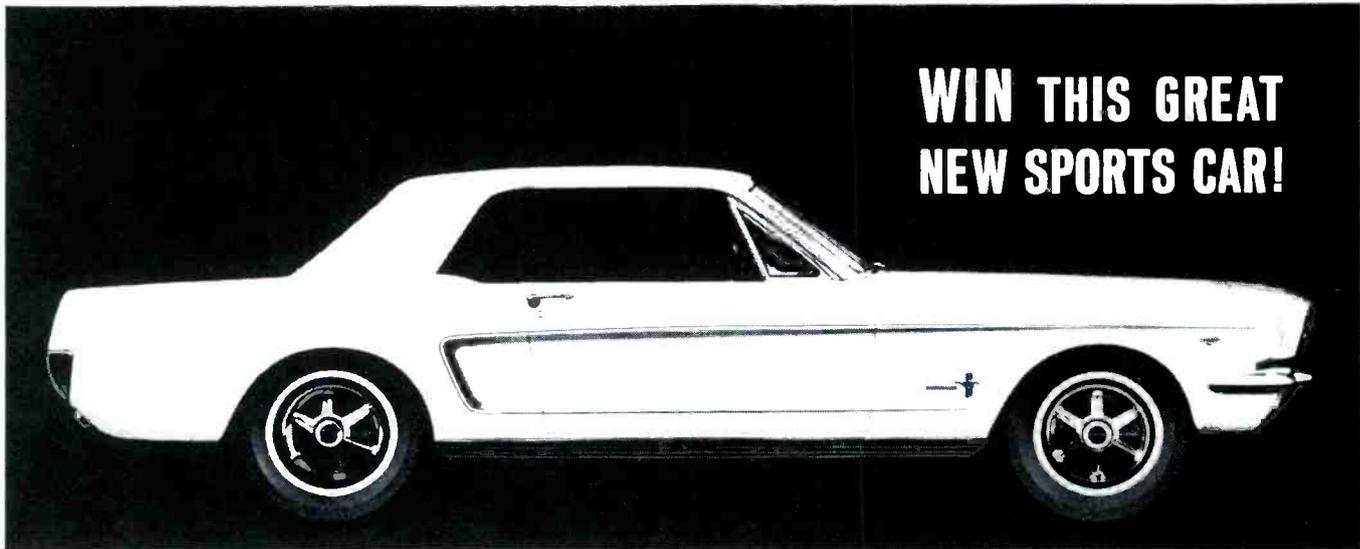

**WIN THIS GREAT
NEW SPORTS CAR!**

Photo Courtesy Ford Motor Co.

ENTER THE BIG PHOTOFACT[®]
"WIN-A-MUSTANG" CONTEST!

**EVERYONE WHO ENTERS
IS A WINNER!**

FIRST PRIZE

New 1964 Mustang Sports Car
(as illustrated)

SECOND PRIZE

Luxurious Mink Stole

THIRD PRIZE

Ladies Elgin Diamond Wrist Watch

**All entrants will receive a
special gift just for entering
this PHOTOFACT contest...**

Contest period is open between September 1, 1964 and December 31, 1964. Entry forms are available from your Sams Distributor or from Howard W. Sams & Co., Inc. (only one entry per contestant accepted). All you do is fill out the entry form, and have it validated by your Distributor. Winners will be determined by a drawing. (Contest limited to U.S.A.; not valid where prohibited by State or local laws.)

DRAWING WILL BE HELD ON

JANUARY 15, 1965

winners will be notified

YOU'RE ELIGIBLE IF YOU USE PHOTOFACT
the world's finest TV-Radio service data

The contest is open to everyone who: **1**— is a subscriber to PHOTOFACT or one of the new PHOTOFACT Specialized Series—or—**2**—owns a PHOTOFACT Library of 60 or more Sets. There is nothing to do except fill out the entry form. Everyone has an equal chance to win at the drawing. Contest closes December 31, 1964, and all entry forms must be postmarked before January 1, 1965. Enter this worthwhile contest now!

**GET YOUR ENTRY FORM FROM YOUR
SAMS DISTRIBUTOR OR SEND COUPON**

**DO IT
TODAY!**

HOWARD W. SAMS & CO., INC., Dept. PFF-9
4300 W. 62nd St., Indianapolis, Indiana 46206

- Send my entry form for the "Win-A-Mustang" Contest
 - I am presently a subscriber to a PHOTOFACT Service
 - I am not a subscriber to a PHOTOFACT Service

Name _____

Shop _____

Address _____

City _____ State _____ Zip _____

My Distributor is: _____



HOWARD W. SAMS & CO., INC.
INDIANAPOLIS, INDIANA 46206

RADIO AMATEURS AREN'T SO **BAD!**



by Howard S. Pyle

Relations between service technicians and amateur radio operators are frequently far from cordial. Hams receive the blame for all kinds of radio and TV interference problems, and the word "amateur" is often taken to mean "careless" or "incompetent." Contary to the views of more than a few owners of radio-TV sales and service shops, the radio amateur is not just a kid playing around with a toy about which he knows little. Many hams have investments which equal or surpass those in many commercial shops, and they have technical knowledge and experience which often rival those of many shop owners and technicians. There is no reason why the electronic service-

man and the amateur can't be friends, and there are some good reasons why they should be.

During many years as a traveling salesman for wholesale distributors of radio and TV equipment, it was more or less incumbent on me to make suggestions to my customers that could conceivably increase their own sales possibilities. Since I was a radio amateur, it occurred to me that here was a field which the owners of radio-TV sales and service shops had more or less neglected. Many of them seemed to have adopted the attitude that the radio ham was just a nuisance who caused snow or wiggles on the customers' screens.

A few dealers, however, ap-

proached what the others considered to be a problem from a different angle. Instead of simply blaming their interference problems on the "— radio ham next door," they took a more realistic viewpoint. Where the source of interference with either radio or TV reception appeared to boil down to a neighboring amateur radio station, these dealers first approached the amateur and, in an amiable mood, discussed the situation with him. In the majority of cases, cooperation was immediately forthcoming. The amateur was not at all anxious to be guilty of interfering with his neighbor's radio or TV reception.

When interference difficulties began to take on alarming proportions, amateurs, dealers, and manufacturers of radio and TV receivers worked out a method whereby all concerned were satisfied. Manufacturers of TV equipment, for example, cooperated to the extent of changing the intermediate frequencies of their equipment to avoid pickup from near-by amateur radio stations. Many others supplied their retail dealers with filter systems which were installed on the customers' sets; the manufacturer and the dealer cooperatively absorbed the small cost involved. Where this was not effective, the amateur radio enthusiast himself, when shown that *his* equipment was at fault, spent the few dollars necessary to modify his own apparatus to eliminate the annoyance. In many instances, particularly in localities having amateur radio clubs, "interference committees" assisted the individual amateur in locating the source of trouble.

True, malicious or repeated interference did, at one time, constitute enough of a problem to warrant the setting up of strict regulations by the Federal Communications Commission. Such regulations, carrying rather severe penalties for offenders, are still very much in existence. Fortunately, through the cooperation of the amateur-radio fraternity as a whole, instances of flagrant violations have become quite rare even though the growth of amateur radio activity has become almost phenomenal in recent years. Thus the amateur isn't so bad after all.

From a sales-promotion standpoint, how many dealers take



Amateurs have—and are entitled to—many social contacts over the air, but they also perform many valuable public services when they are needed; often during emergency situations.



your next customer:

You can't know if he'll be smiling or angry, wearing a suit or a sports shirt, or driving a 6 or an 8. One thing you can be reasonably sure of, though. You'll be able to service his radio with Delco parts. That's because nearly half the

cars on the road—around 25,000,000 of them—have Delco radios. And you can service most other kinds of radios with Delco parts, too. The line is that broad. What does this mean? Simply that it makes good sense to stock and use genuine Delco parts. For better servicing. For fewer customer complaints. For the convenience of getting most of the parts you need quickly and reliably from *one* source: your United Delco supplier.

Call him today for our big detailed catalog. (To learn who your nearest United Delco supplier is, phone any of the numbers listed below. Ask for the Zone Service Manager.) Delco Radio electronic service parts and electro-mechanical devices are distributed nationally through United Delco.


simply say Delco



Atlanta.....Cedar 7-1501	Dallas.....Fleetwood 2-8471	Cincinnati.....Cherry 1-2310
Boston.....Wells 3-3100	Cleveland.....671-6460	Charlotte.....Edison 4-8671
Chicago.....437-5300	Denver.....Keystone 4-0273	Jacksonville.....Exbrook 8-5755
Detroit.....584-1025	Indianapolis.....Melrose 6-4351	Houston.....Jackson 6-4338
Los Angeles.....Dunkirk 5-6487	Buffalo.....TF 2-5362	Washington, D.C.....Juniper 8-7494
Minneapolis.....331-4811	Philadelphia.....Garfield 3-8200	El Paso.....Keystone 3-1651
Newark.....297-3300	St. Louis.....Jefferson 3-4230	New York.....Judson 2-3824
San Francisco.....Landscape 6-8221	New Orleans.....523-4281	Kansas City.....Fairfax 1-3900
Seattle.....Parkway 2-4477	Pittsburgh.....Court 1-6551	
	Omaha.....558-0225	
	Memphis.....Jackson 5-6471	

Circle 46 on literature card

Coming in the
OCTOBER issue . . .

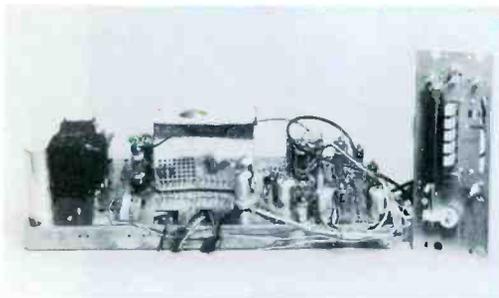

Highlights of 1965 TV Lines

Read our popular annual report on the new black-and-white chassis.

Shrunk Rasters

Be armed with answers when this trouble appears.

Applied Reasoning for Auto Sets

Use these proven techniques to save time and temper.

2-Way Transistor Power Supplies

Understand these circuits so you can service them quickly and easily.

New Sound From Old Cabinets

Don't throw old cabinets away—bring them back to life.

Make the Most of Your Attorney

What you don't know can hurt you; don't let ignorance of the law cause you trouble.

plus . . .

Symfact

The Troubleshooter

Notes on Test Equipment

. . . and many more features to ease your job and raise your profits.

Enter my subscription to PF REPORTER and send me free book(s) checked.

3 Years \$10.00 2 Years \$8.00 1 Year \$5.00

The Troubleshooter's Handbook No. 2

Servicing Industrial Electronics

Servicing TV from Tuner to Picture Tube

Symfact Handbook

Check one of above for each year you subscribe

Bill Me Remittance Enclosed

Extend Present Subscription

Please Check Your Business Classification

Owner, Mgr. Employee Service Mgr.

Independent Radio, TV Serviceman Retailer with Service Department

Industrial Electronics Service Other (Specify occupation and title)

Name _____


Firm _____

Address _____

City _____ State _____ Zip Code _____

Take this coupon to your distributor, or mail to: Howard W. Sams & Co., Inc., 4300 W. 62nd Street, Indianapolis, Indiana

964

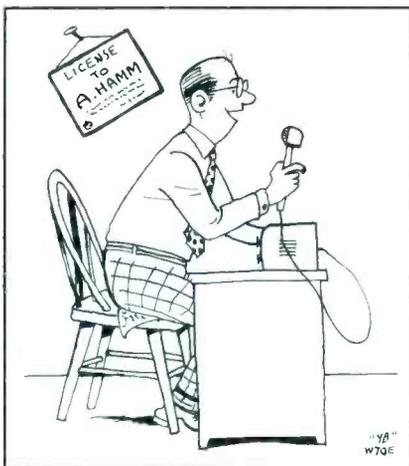

Most amateur radio operators assemble their stations from quality components, and they have the technical know-how required to operate and maintain their station properly.

advantage of the opportunity to establish acquaintanceships in this "other world" of radio — amateur communication? This is where a considerable number of radio-TV dealers "miss the boat." Consider for a moment that the average radio amateur is just another guy like you. Perhaps he is a "white-collar worker" at an industrial plant. When the whistle blows, he can come home, eat his dinner, look at the paper, and then take off for his ham shack. Or, perhaps he is a high school student; after finishing his homework, he can converse, via radio, with a buddy a thousand or more miles away.

If you show an interest in any of these hams — help him with his minor technical problems, test his tubes, or check his gear for a loosely soldered connection — you've made a friend. When he needs professional electronics service, where will he go, or whom will he suggest? *You*, if you have befriended him.

Perhaps a neighbor will consult your ham friend, feeling that a radio amateur has knowledge of all there is to know in the field of electronics. If this neighbor wants to buy a new TV or radio set, hi-fi or stereo equipment, etc., who is the radio ham going to mention? His friend, the local radio-TV dealer-serviceman.


Get the picture? Isn't it about time that you cashed in on this opportunity? The radio ham can be not only one of your best friends but also one of your greatest business boosters. ▲

DON'T REPAIR STEREO PHONOS!



(Modernize them with the Positive Scratch Protection of a new E-V featheride!)

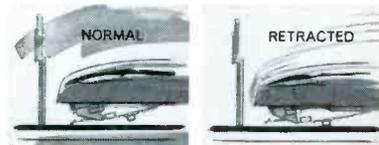It's as easy as exact replacement—and much more profitable! Upgrade your stereo phono customers to featheride performance and record protection—until now only available with high-priced console phonographs and custom hi-fi systems.



Exclusive E-V featheride mechanism lifts needle off record before accidents can damage grooves. Unique soft felt pad absorbs all shocks.

featheride high compliance design keeps tracking pressure low for longer record life—two models match all modern changers. Specially designed mount permits tracking even badly warped records every time!

If a featheride cartridge prevents damage to just one record, your customer has saved the slight extra cost. Start installing today's most wanted phono feature—E-V featheride—available at your E-V distributor's today.

ELECTRO-VOICE, INC., Dept. 947R.
Buchanan, Michigan 49107

featheride
ElectroVoice[®]
SETTING NEW STANDARDS IN SOUND

Circle 47 on literature card

Quality is no gamble!



when you specify **ELMENCO** dipped Mylar* paper

Every time you make a call ... service a circuit ... change a component — you bet on the parts used. Make sure the odds are in your favor with miniaturized Elmenco Dipped Mylar-Paper (DP) capacitors. Over 100 million are in use now, because Elmenco DP capacitors give missile quality at commercial cost. Whether for radio-TV repairs, or critical industrial circuitry, reliable, dependable, rugged Elmenco capacitors eliminate profit-killing callbacks and customer complaints. Elmenco DP capacitors operate at 125°C without derating, are completely moisture proof, and are up to 50% smaller than comparable types. You can substitute values in a capacitor, but never virtues. Ask for Elmenco, and be sure you get it. Elmenco DP capacitors are available from stock only at authorized ARCO distributors throughout the U.S.A.

*Reg. Du Pont Trademark



ARCO
electronics inc.

ARCO'S RESERVE WAREHOUSES

You can get your Elmenco (DP) capacitors in any quantity within 24 hours from coast to coast. They're stocked in depth at Arco's reserve warehouses serving authorized Arco distributors throughout the nation. Call your Arco distributor today!

Community Drive, Great Neck, N.Y. ☐ 516 HU 7-0500
Branches: Dallas 7 ☐ Los Angeles 35

Circle 48 on literature card



For your
background
music installations

5. new Quam speakers

Over the hubbub of other sounds, background music has to be audible without being obtrusive. Ordinary public address speakers, designed for capturing the primary attention of the audience, are *not* the answer. These new Quam Speakers—especially designed to handle background music—are.

Quam offers you five background music speakers, three eight-inch models and two twelve-inch. All have ceramic magnets; four of these new units are extended range units with dual cones; two of the new speakers offer very shallow construction. (Complete specifications are given in the new Quam Catalog 63... now available on request.) They meet the traditional Quam standards of utmost quality and performance satisfaction.

Remember Quam—for forty years the Quality Line for all your speaker needs.

QUAM

QUAM-NICHOLS CO.

234 EAST MARQUETTE ROAD • CHICAGO 37, ILLINOIS

Circle 49 on literature card

82 PF REPORTER/September, 1964



Notes on Test Equipment

analysis of test instruments... operation... applications

by Stephen Kirk

Color Generator



Fig. 1. Versatile unit provides wide selection of signals for use in servicing color TV sets.

The B & K Model 1074 (Fig. 1.) is a streamlined version of the 1076 TV *Analyst*, except that it does not have a flying-spot scanner for reproducing transparencies on the TV screen. Instead, it uses crystal-controlled oscillators and multivibrator frequency-divider circuits to develop crosshatch lines, dots, verti-

cal lines, horizontal lines, and color signals. The video signals are either applied directly to a receiver circuit or used to modulate a carrier injected into the TV set at the IF or on any one of several channels (2, 3, 4, 5, 6, 7, 8, 12, 13).

In addition to the pattern signals, the following outputs are available at panel jacks: horizontal and vertical grid-drive signals, a bias voltage adjustable from 0 to plus or minus 25 volts, a 900-cps audio signal, a 4.5-mc carrier frequency modulated at 900 cps, color-burst signals, a color-subcarrier signal of adjustable amplitude, and sync signals of adjustable amplitude and either polarity. Provision is also made for a signal to directly drive a vertical yoke and for a shorted-turns tests.

The circuits of the 1074 are laid out on three separate printed boards. One board contains the 189-kc crystal oscillator and the frequency dividers, the second contains the color and sound cir-

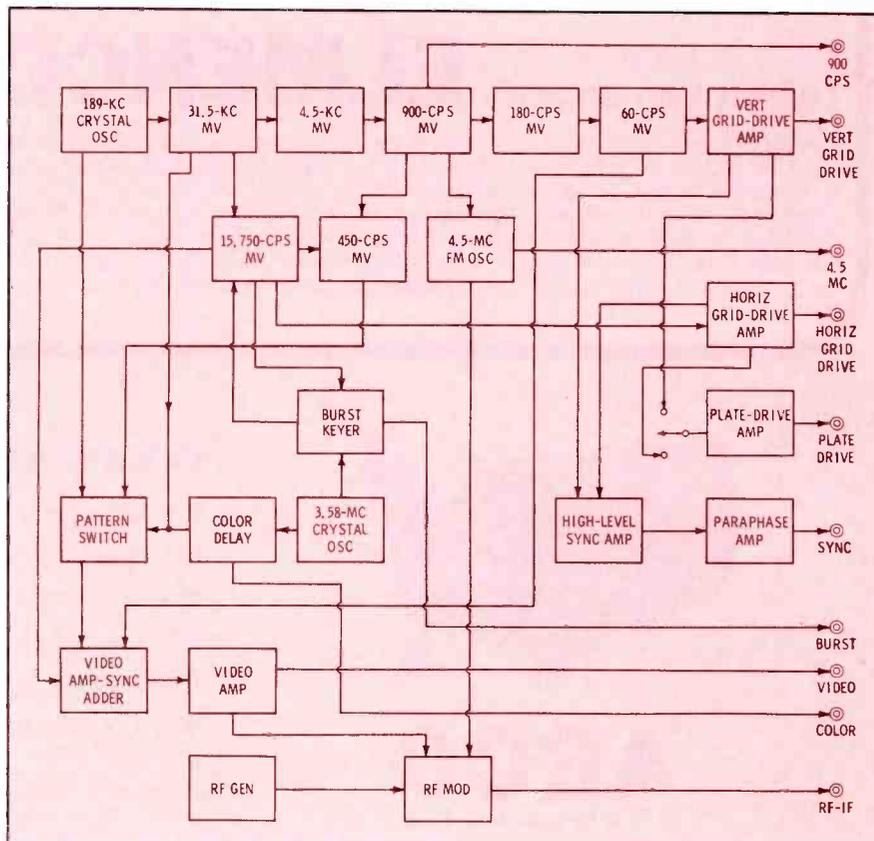


Fig. 2. Simplified functional diagram shows how signals are generated in B & K 1074.

uits, and the third contains the RF-oscillator, modulator, and sync circuits.

The functional block diagram in Fig. 2 shows the signal-generating portions of the 1074. One output of the 189-kc crystal oscillator is used to synchronize a 31.5-kc multivibrator, and another output is shaped and used to produce vertical lines. This output goes to the pattern switch. The 31.5-kc multivibrator synchronizes the 15,750-cps and 4.5 kc dividers and is used to set the phase of color information in the color-bar display. The 15,750-cps divider feeds the horizontal grid-drive amplifier, provides horizontal sync pulses, keys the color burst, and controls the phase of the 450-cps multivibrator.

The 4.5-kc divider between the 31.5-kc and 900-cps stages is used only as an intermediate divider to increase long-term stability. Four outputs are taken from the 900-cps multivibrator: One controls the frequency of the 450-cps horizontal line source. (The two inputs to the 450-cps stage insure that each horizontal test line is one raster-line wide and coincides with the beginning and end of a horizontal scan interval.) The second 900-kc output is used as a direct audio source, the third is used to frequency modulate the 4.5-mc oscillator, and the fourth synchronizes the 180-cps intermediate divider and stabilizing counter for the 60-cps multivibrator. The 60-cps divider is the source of vertical sync pulses and also excites the vertical grid-drive amplifier.

Video information is a composite of pattern components and necessary sync signals selected with the pattern switch. The composite output is obtained from a paraphase amplifier that has either positive or negative output. The composite signal is also fed to the RF modulator.

The sync signals are fed separately to a paraphase amplifier to provide either positive or negative output. The sync control varies the amplitude from 0 to 50 volts at the SYNC OUTPUT jack.

The color signal is generated by a 3.58-mc crystal-controlled oscillator. A sample of this signal is fed through the horizontal multivibrator (15,750 cps) so it will start (as far as the output is concerned) during the horizontal sync interval; thus the color burst portion of the composite video signal is formed. Another output from this crystal oscillator is fed to a delay line. The amount of delay, controlled by a panel switch, determines which of seven different colors is transmitted to the receiver. For example, when the color switch is set to RED, the screen color on the TV set should be red if the hue or tint controls on the set are correctly adjusted. Whatever color is selected, there is a black vertical reference bar (keyed by the 31.5-kc divider) in the center of the screen. This makes it easy to check or set up color demodulators.

It is impossible to discuss here all the possible tests and checks that you can make with the 1074. The outputs



EASY TO SELL... EASY TO USE... EASY TO MAINTAIN 2-WAY RADIO FOR THE BOOMING CB MARKET!

Never before this performance breakthrough! Never before this big chance for you to cash in on the fast-growing 2-way radio market . . . for car, boat, home, business, office. The Courier 23 has unequalled performance with dollar for dollar value others can't match. It features dual conversion, transistor power supply, 23 crystal controlled channels and more features CB users want. It is priced at \$189.50 . . . and that includes all crystals, mounting brackets, power cords and noise-cancelling microphone. Best of all, the Courier 23 is "hot" . . . with wide acceptance everywhere!

CAN YOUR FIRM QUALIFY AS AN AUTHORIZED e.c.i. DEALER?

A sound knowledge of radio and/or communications equipment . . . the desire to install and service this equipment . . . an established business reputation and a good credit rating . . . a real interest in a dynamic new product with dramatic profits. These are the requirements. Write today for details!

e.c.i. electronics communications inc., Dep't Q
56 hamilton ave., white plains, n.y.

Please send full details on the Courier 23 and an e.c.i. dealership.

name

firm name

address

city zone state



Be a wise owl!

How to simplify installation, increase profit on all-channel UHF converters!



Model UC100A. Modern, 2-tone design with brushed gold knobs.

Improved for greater reliability... priced for greater profits! New Admiral UHF Converters use a 2-speed ball-bearing planetary drive for easy single-knob channel selection. Trouble free 3-gang tuning provides years of dependable service.

The latest nuvistor I.F. amplifier circuits give power to spare. Even fringe area reception can be clearer with added picture power. We've tested all makes—here's the best!

Installation is easy, too. Use just a screwdriver to connect the antenna lead and 300 ohm lead to any TV set.

And the remarkable Admiral price makes your "profit picture" look better than ever before.

Economy model UC100B also available... contact your Admiral Distributor now... start pocketing bigger profits right away!

Be wise... standardize on

Admiral[®] ALL-CHANNEL UHF CONVERTERS

Always Precision Crafted Quality
Circle 51 on literature card

are so flexible and varied that they become even more useful as you learn more about what to expect in various situations. The examples that follow illustrate typical applications of the instrument.

One case involved a color set used in an apartment building equipped with an antenna distribution system. Black-and-white could be received okay, but color could not. In a situation like this it is almost natural to suspect the distribution system, but the technician decided to connect the 1074 to the receiver antenna terminals to make sure. Color appeared and remained in sync even when the RF gain control of the 1074 was turned low enough to produce a snowy picture on the screen. This indicated that the color circuits were okay. The technician was on the verge of condemning the antenna distribution system when he noticed that the lead-in from the antenna to the set had been neatly bundled, tied with a cord, and placed inside the cabinet of the set. Removing the excess lead restored normal operation.

In a set that had no high voltage, we disconnected the plate cap from the 6BQ6 horizontal amplifier and inserted a signal from the 1074 PLATE DRIVE jack. The high voltage came on. Next, we moved to the grid of the 6BQ6 and inserted a signal from the HORIZ GRID DRIVE jack. Again there was high voltage. This pointed definitely to trouble in the horizontal oscillator or phase detector. A couple of voltage measurements in the oscillator stage revealed that the plate resistor had changed value.

We were particularly interested in the patterns for setting up color sets. We converged several sets made by different manufacturers. In every case there was no tendency for the patterns to move, weave, or jitter. Lines and dots both were thin and clearly defined, which made convergence much less of a chore.

The modulated 4.5-mc signal is a boon in troubleshooting audio IF stages. We had no trouble tracing a loss of sound to a defective takeoff trap in the video circuit of a receiver with a reflex sound circuit.

We had no trouble in locating the defective tuner in a set that was without

sound or picture. Injecting an IF signal from the 1074 into the first IF grid of the set produced a pattern on the screen; this furnished all the proof we needed.

The 1074 can be put to good use in aligning tuners on sets that are to be used on a cable TV system. The range of fine tuning can be checked to make sure that a slight drift in frequency will not prevent the customer from tuning in a good picture.


It appears that overall sensitivity of a particular set can be checked with fair accuracy, especially if the settings of the RF GAIN control are noted for sets that are in good working order. By turning the control until snow first appears in the picture, a pretty good reference point can be established for two-IF sets, three-IF sets, and sets with various tuner types.

One thing we've not mentioned so far is the shorted-turns indicator circuit. This is essentially the same circuit that is used in the 1076. It is rather sensitive and may occasionally indicate that a good transformer is bad. However, we



TV TUNERS * REBUILT OR EXCHANGED

* ALL TYPES

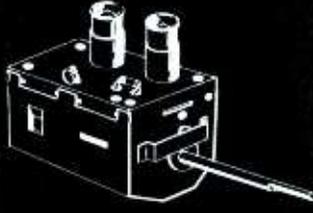

\$9.95 Including all parts and labor
(except broken wafers—billed at cost)

- Normally shipped same day received
- 90 day full guarantee
- U/V combinations \$17.95

FREE—If Mailing carton sent to you on request

Phone REpublic 3-9189

L. A. TUNER EXCHANGE
4611 West Jefferson Blvd.
Los Angeles 16, California

Circle 52 on literature card

found no case where a flyback checked good that was really defective. (This might sometimes happen if the transformer were breaking down only under high-voltage stress.)

For further information, circle 73 on literature card

Low-Voltage Supply



Fig. 3. This compact power supply provides DC voltages for variety of transistor devices.

The Seco Model RPS-5 (Fig. 3) is a regulated power supply that delivers voltages suitable for powering transistor equipment. Its maximum rated power output is 4 watts. In addition to stabilizing the average output voltage, the transistor regulator circuit also reduces the ripple content.

Outputs are available between the common (—) jack and three other jacks. The output range depends on the setting of the METER RANGE switch. In

the 1.5v/15v position, these voltage ranges are available: 0 to 1.5 volts at the LOW jack, 0 to 7.5 volts at the INT jack, and 0 to 15 volts at the HIGH jack. When the switch is in the 30v position, 0 to 28 volts is available at the HIGH jack, and the other outputs are disabled. Two current ranges, 0 to 30 ma and 0 to 150 ma, are included. These measure current drawn from the HIGH jack only. A panel lamp indicates when excessive current is drawn and serves as a fuse in the event of severe overload or failure of a component in the supply.

Two half-wave rectifiers are operated from a tapped transformer (Fig. 4). One of these rectifies the DC output; the other, in conjunction with a zener diode and a control potentiometer, supplies reference voltage to the base of the regulator transistor.

The METER RANGE switch turns the unit on and off, selects the meter range, and in the 1.5v/15v position completes the voltage-divider circuit for the low-voltage outputs. On the 1.5v/15v range, the voltmeter is connected across the 1.5-volt output. (As the voltage at the LOW jack varies from 0 to 1.5 volts, the voltage at the HIGH jack varies from 0 to 15 volts.) On the 30v range, the meter is connected between the HIGH and — jacks. On the current ranges, the meter is connected across resistors located on the supply side of the transistor; thus the meter resistance is not actually in the supply lead to the unit being powered. A diode clamping arrangement protects the meter and shunt resistors from damage by overload.

Only the HIGH output of the supply is directly regulated. The other two outputs are regulated only to the extent that they are obtained from a voltage divider connected across the regulated source. Thus, the divider resistors will affect current-

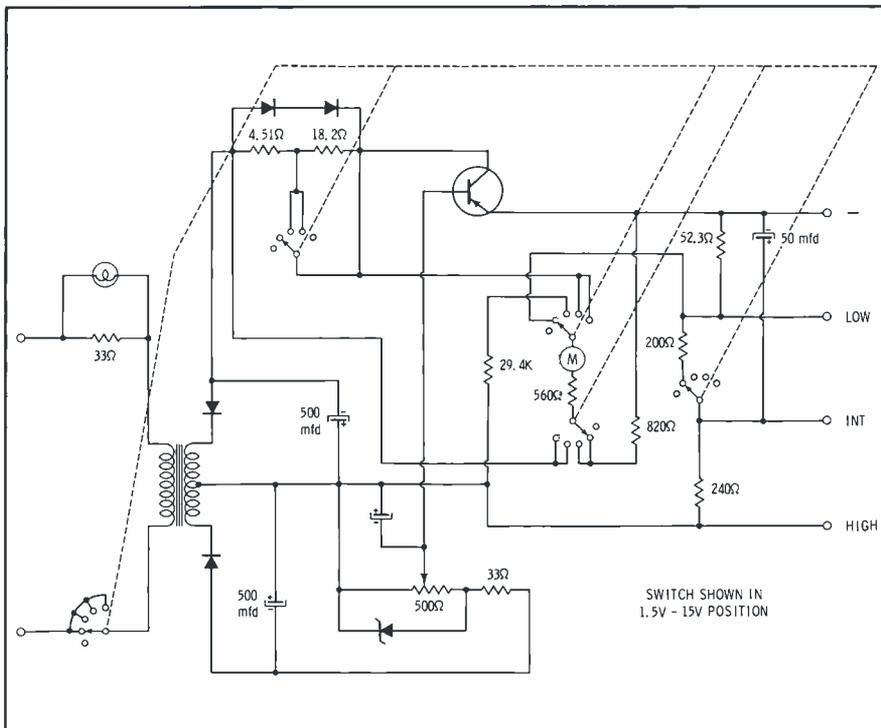


Fig. 4. Circuit diagram of the Seco Model RPS-5 shows how outputs are obtained and metered.



Be a wise owl!

How to cut inventory, increase profit on picture tubes!



Save space, save dollars! Reduce your basic tube inventory to the 5 Admiral Ensigns. They replace 43 different tube types.

Each Admiral Ensign picture tube must pass rigid quality controls for finest performance.

Call your Admiral Distributor now . . . start cutting inventory cost; pocketing new profits right away!

ENSIGN 17BJP4 REPLACES	17ATP4 17ATP4A 17AVP4	17AVP4A 17BUP4 17CBP4	17CLP4
ENSIGN 21AMP4A REPLACES	21ACP4 21ACP4A 21AMP4	21AQP4 21AQP4A 21CUP4	21BSP4
ENSIGN 21CBP4A REPLACES	21FLP4 21ALP4 21ALP4A 21ALP4B 21ANP4 21ANP4A	21ATP4 21ATP4A 21ATP4B 21BAP4 21BNP4 21BTP4	21CBP4B 21CMP4 21CVP4 21CWP4 21DNP4 21CBP4
ENSIGN 24CP4A REPLACES	24ADP4 24CP4 24QP4	24ATP4 24VP4 24VP4A	24XP4
ENSIGN 24AEP4 REPLACES	24DP4A 24YP4	24ANP4 24ZP4	

Be wise . . . standardize on

Admiral
ENSIGN
REPLACEMENT PICTURE TUBES

Always Precision Crafted Quality
Circle 53 on literature card

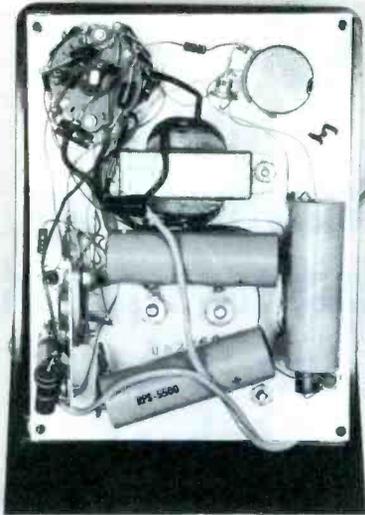


Fig. 5. Internal view Seco RPS-5 power unit.

vs-voltage at the two lower-voltage outputs.

We used this unit to power a number of transistor radios. In so doing, we found no evidence of motorboating or hum. The switch-selected milliammeter proved to be a handy feature for this type of service work. We noticed, however, that if the switch is turned from the 30-volt range to the 15-volt range while the output voltage is greater than 15 volts, the meter will "pin," or strike the stop. A little caution is therefore advisable in switching ranges.

The operating portion of the unit can be removed from the case for servicing by removing only four screws. Hand-wired construction is used throughout the unit. As can be seen in the photo (Fig. 5) the transistor is a high power type, similar in physical shape to those used in auto radio output stages. A thin strip of metal serves as a heat sink. The

remaining circuit components seem readily accessible.

The unit operates from a 115-volt AC supply, measures 3½" x 5½" x 7½", and weighs 3 lbs. ▲

For further information, circle 74 on literature card

now in our lab . . .

The latest test instruments being analyzed for future "Notes" columns:

Cornell-Dubilier Model BF-71

Capacitor Checker

Hickok Model 470A VTVM

Standard Kollsman VHF-UHF

Translator

RCA Model WV-76A AC

VTVM

EICO Model 667 Tube Tester

SENCORE Model PS127 Oscilloscope

TWIN TRANSISTOR SUPER COLORTRON

Not 10 DB, not 15 DB but a whopping
33 DB gain on the low band and FM—
33 DB gain on the high band actually
amplifies the signals 45 times

**TWIN TRANSISTOR
STANDARD COLORTRON**

18 DB gain on the low band and FM—
18 DB gain on the high band



NEVER BEFORE — 33 DB gain!
NEVER BEFORE — Same gain on every channel 2—13 plus FM!
NEVER BEFORE — 3.5 DB noise figure or less on all channels!


Sync Simplified

(Continued from page 31)


both the grid and the plate. We remembered that this type of noise inverter isn't even supposed to conduct, except when noise pulses more positive than sync tips appear in the video signal coming into the sync section. Then the noise inverter conducts, produces a negative pulse at the plate, and thus cancels out the noise at the grid of the sync separator. If it conducts at any other time, it murders the sync signal. But in this case, W6 was as good as gold, so V11B must not be misbehaving.

Circuit Study

Right now was a good time to

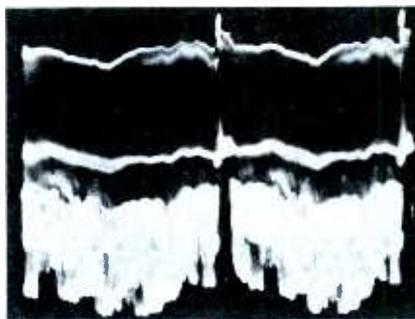

(A) W5 — 20V p-p

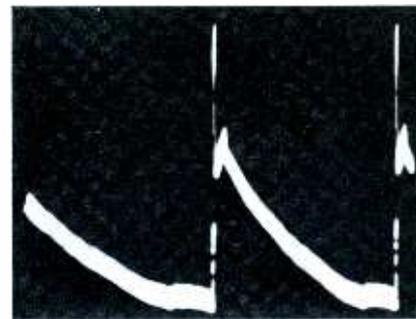

(B) W8 — 7V p-p

Fig. 4. Odd waveforms were present at V16 cathodes.

take our findings and try to tie them together into an understanding of how the circuit works. The first problem, as in any complicated sync circuit, was to distinguish the really essential components from those which are incidental to the main

job. We started our analysis by trying to define how the circuit performed three main functions:

1. Prepare the video signal for separation.
2. Separate the sync pulses from the video.

POTENT NEW PRE-AMPS from Winegard with Super High Gain

- First Pre-amps That Have Same Gain on Both TV Bands plus FM.
- Will Take Highest Signal Input of Any Twin Transistor Antenna Amplifiers Made.
- Have Lowest Noise Figure Ever Obtained on TV Antenna Pre-amps.
- Can Be Used on Any TV Antenna for Black and White, Color or FM.

Up to now there have been two serious drawbacks to *all* antenna pre-amps (including our own)—

First—there have never been antenna pre-amps that had enough gain for *every* application. Second—all antenna pre-amps have had from 4 to 6DB gain less on the high band. This is unfortunate because the high band channels normally need pre-amplification more than the low band due to greater reception losses at the higher frequencies.

NOW Winegard has created two big solutions to this problem—the Super Colortron with a flat 33 DB measured gain on all channels 2—13 and the Standard Colortron with a flat 18 DB gain on all channels 2—13. For example, the Super Colortron will blow up a 50 microvolt signal to 2250 microvolts even on 13, the highest channel. Compare this with the best twin transistor pre-amps previously available where a 50 microvolt

signal would be amplified only to 175 microvolts—a tremendous difference in signal power. This increase in amplification will cover *all* applications—particularly for *fringe* area color. (See comparison charts to the right).

Of equal importance to gain is the noise figure of a pre-amp. Winegard engineers have lowered the noise figure on these new pre-amps as much as 2 DB over any other TV pre-amp available. They will bring perfect color even to deep fringe areas.


Compare these new Winegard antenna pre-amps with any others on the market today. Compare construction—totally weather-proofed polystyrene case, even the terminals are protected . . . convenient, rugged mounting bracket that snaps-on boom. Compare performance—highest gain . . . lightning protected circuit . . . lowest noise! Then try a new Twin Transistor Colortron and see it in action!

The Super Colortron (AP75T) uses a 75 ohm system with RG59U Coaxial cable. Has three RG59U Connectors. For runs of over 70 ft., RG11U is recommended. The AP75T supercedes the AP215N. Model AP75T lists for only \$79.95.


SPECIFICATIONS: GAIN: +33 DB per band. BAND PASS: 54MC-108MC, 174MC-216 MC. RESPONSE $\pm\frac{1}{2}$ DB per 6 MC channel. VSWR: Input 1.5:1. Output: 1.75:1. MAX. SIGNAL INPUT: 55,000 MV. MAX. SIGNAL OUTPUT: 2,000,000 MV. INPUT IMPEDANCE: 300 ohm. DOWNLEAD IMPEDANCE: 75 ohm. OUTPUT IMPEDANCE 75 or 300 ohm. 117V 60 CPS 1.8 watts.

The Twin Transistor Colortron Antenna Amplifier (AP220T, 300 ohm) lists for only \$44.95. The AP275T (75 ohm) amplifier lists for \$49.95.

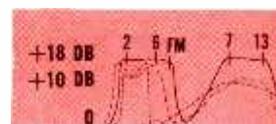SPECIFICATIONS: GAIN: +18 DB per band. BANDPASS: 54 MC-108 MC, 174 MC-216 MC. RESPONSE $\pm\frac{1}{2}$ DB per 6 MC channel. VSWR: Input 1.5:1. Output: 1.75:1. MAX. SIGNAL INPUT: 80,000 MAX. SIGNAL OUTPUT: 660,000 MV. INPUT IMPEDANCE: 300 ohm. OUTPUT IMPEDANCE: AP-220T—300 ohm, AP275T—75 ohm. 117V, 60 CPS. 1.8 Watts.



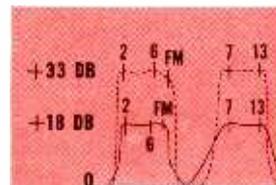COMPARE THESE GAIN CURVES AGAINST COMPETITIVE MAKES. CURVES TAKEN FROM SCOPE PHOTOS.
--- BRAND J
--- BRAND B
--- WINEGARD COLORTRON (AP220T)



ACTUAL MEASURED CURVES PROVE A FLAT 18 OR 33 DB GAIN . . . HIGH BAND, LOW BAND, FM, TOD.
--- WINEGARD AP75T
--- WINEGARD AP220T

<p>COLORTRON TWIN NUVIATOR (AP220N). 300 ohm. Input: 400,000 microvolts . . . highest of any amplifier. tube or transistor. List \$39.95. AP275T (75 ohm) List \$44.95.</p>	<p>TWIN NUVIATOR FM AMPLIFIER ONLY. (AP320). 18 DB gain. 180,000 Microvolts Input. List \$39.95. AP375—same, but coax. List \$44.95.</p>	<p>REDHEAD SINGLE TRANSISTOR ANTENNA AMPLIFIER (RD300) Most reliable, highest gain single transistor model available. Input: 20,000 microvolts. 300 ohm input and output. List \$29.95.</p>	<p>UHF 212—Twin Transistor UHF antenna amplifier has 12 DB gain on all UHF channels 14-83. Noise figure 8 DB at 960 MC. List \$44.95.</p>	<p>UHF 110X Single transistor UHF antenna amplifier has +8 DB gain on channels 14-72. List \$34.95. UHF 110T (translator model) —same, but has 12 DB gain on channels 72-83. List \$34.95.</p>
--	---	--	--	---



Winegard Co.

ANTENNA SYSTEMS

3009-I Kirkwood, Burlington, Iowa

World's most complete line of TV&FM reception equipment.

Circle 54 on literature card

www.americanradiohistory.com

it's here! most advanced
color TV test instrument
ever developed



- OBSOLETES ALL OTHERS
- ELIMINATES ALL GUESSWORK

LECTROTECH V7*

A sensational new color generator with 4 major Lectrotech exclusives . . . plus all of the time-proven standard features . . . in one compact, portable unit. For the first time you can install and service color TV completely, accurately and faster! Here are the facts:

EXCLUSIVE—COLOR VECTORSCOPE—Until now, available only in \$1500 testers designed for broadcast. Accurately measures color demodulation to check R-Y and B-Y plus all 10 color bars for color phase angles and amplitude. A must for total color and those hard to get skin tones.

EXCLUSIVE—SELF-CALIBRATING — Adjust timing circuit without the use of external test equipment. No need to return unit to a factory for adjustment.

EXCLUSIVE—DIAL-A-LINE — Now, you can adjust horizontal line to any width desired from 1 to 4 lines wide.

EXCLUSIVE—SOLID STATE RELIABILITY — Only two tubes are used in combination with fully transistorized diode-rectifier circuit.

PLUS— the V7 produces all Crosshatch, Dots, Vertical only, Horizontal only and Keyed Rainbow Patterns. RF at channels 3, 4 or 5. Video Output (Pos. and Neg. adjustable) for signal injection trouble-shooting. Red-Blue-Green Gun Killer. All transistor and timer circuits are voltage regulated to operate under wide voltage ranges. Lightweight, compact — only 8¼" x 7½" x 12½". Net..... **189.50**

*Designed and produced by the men who introduced and developed the modern approach to TV testing — Bill Grossman and Bob Karet.

For the full story on the V7, write for complete catalog or see your distributor.

Distributors: Phone or Wire Collect.



LECTROTECH INC.

1737 Devon Ave. • Chicago, Ill. 60626 • Area 312 465-2622

Circle 50 on literature card

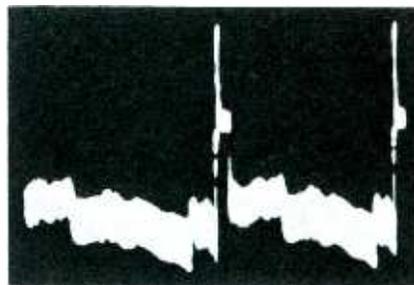


Fig. 5. W7 taken at V16B grid (18V p-p) consisted mostly of the vertical sync pulses.

3. Shape the separated sync pulses —clip them to constant amplitude, and establish the desired amplitude and polarity.

To follow up on the first point, we looked for the exact path of the input signal from the video stage to the stage labeled "Sync Sep." In this case, the input path is short—through two resistors, a 22K and a 33K, to the grid (pin 2) of V16A. The circuit of V11B is in parallel with the input path, but we'd cleared it pretty well of suspicion. We had a good signal in V16A, so we checked off function 1 as OK.

Now, how about the second point —separation? The only signal output from V16A was at the cathode, and it was video! Surely it shouldn't be. . . . On further pondering, it seemed that V16A and V16B should both be working in parallel as sync separators—receiving video inputs at their grids and feeding pulse-signal outputs from their cathodes to the cathode of V17A. Nothing like having a spare sync separator! Actually, we mused, the two circuits must work somewhat differently and complement each other's action.

Suppose the *normal* W4 were a complete, fully separated sync signal. It should be passed through V17A without inversion (cathode to plate), but we could expect it to be amplified quite a lot. When it's fed to V17B, it's probably strong enough to drive that tube into both saturation and cutoff—this would partially take care of point 3 in the above list (trimming the pulses to size). There are outputs from both the cathode and the plate of V17B—that takes care of the "polarity" requirement of function 3.

Beautiful theory, isn't it! Now, why didn't the actual circuit measure up to it? There seemed to be a defect somewhere ahead of the cathode of V17A; vertical sync pulses were getting through to here, but

not horizontal pulses. We decided to operate on the assumption there were two sync separators in parallel—one for vertical pulses and one for horizontal. V16B tended to bear out this idea—its input waveform would consist largely of vertical pulses, because the 51 mmf capacitor at the grid would partially bypass the higher frequencies in the video signal to ground. If our theory were correct, V16A would be responsible mostly for horizontal pulses. Therefore, these pulses should be the main component of W5. At any rate, one would think most of the video would have been removed. But it wasn't—and this looked suspicious.

Not much in this circuit to go wrong. . . . We checked the 680K cathode resistor, finding it okay. As another idea, we unsoldered the output (V17A) end of the .01 mfd capacitor; then, with the set running, we held a VTVM probe and a scope probe (in turn) on the loose lead. Neither the meter nor the scope gave any reading. The capacitor was open! Putting in a new .01 restored beautiful sync.

The waveforms all became as shown in the photos of *normal* signals. W5 no longer had video in it. There were vertical sync pulses, but—more important—there were also clean horizontal pulses. And now, with a normal W5 being coupled to the grid of V17A, we found *both* horizontal and vertical pulses in W4. The horizontal sync tips were still a bit ragged and uneven in amplitude, but the action of V17 improved this situation. Look at all the gain V17A gave the signal, and look at the clean waveshape of outputs W1 and W2! On V16B, W8 still had its screwball sawtooth slope; as we previously had suspected, this is normal. The input to V16B was also the same as before.

Just out of curiosity, we checked all DC voltages again, and could not find more than 2% deviation from any of the former readings! This case had involved strictly signal troubles, with one of two parallel signal paths becoming open—resulting in selective-frequency coupling of the signal. If we'd relied on hit-or-miss methods instead of trying to reason this one out, wonder how long the job would have taken? ▲

Weller® for all soldering

Dual Heat Soldering Guns

Weller dual heat soldering guns give time-saving instant heat. Two trigger positions let you switch to low heat, for soldering near heat-sensitive components, or high heat when needed. Spotlight illuminates work. Three models available.

100/140 watts—Model 8200—\$5.95 list
145/210 watts—Model D-440—\$9.95 list
240/325 watts—Model D-550—\$10.95 list



Soldering Gun Kits

"Expert" Kit (shown) includes 100/140 watt gun, 3 soldering tips, tip wrench, flux brush, soldering aid and solder in a plastic utility case. Model 8200PK—\$8.95 list.

Heavy-Duty Kit features 240/325 watt gun; soldering, cutting and smoothing tips; tip-changing wrench; solder; plastic utility case. Model D-550PK—\$12.95 list.



"Pencil" Soldering Iron

For miniature type soldering. A 25 watt, 115 volt soldering pencil that's small and lightweight. So efficient it does the work of irons that are much heavier and require much higher wattage. Rapid recovery. Cool handle. Complete with 1/8" screwdriver tip and cord set. Model WP—\$5.20 list.

Temperature-Controlled Low-Voltage Soldering Pencils



Temperature control of this new Weller soldering pencil is in the tip. Interchangeable tips give a choice of 500°F, 600°F, or 700°F controlled temperatures. Operates on 24 volts. Small, lightweight, highly efficient. Complete with 3/16" 700°F tip and 60 watt, 120 volt, 50/60 cycle power unit with stand for soldering pencil attached. Model W-TCP—\$26.00 list.

Also available: a soldering pencil controlled by thermistor and SCR (silicon controlled rectifier) circuit. It gives a choice of controlled temperatures between 200°F and 450°F. Highly efficient. Model W-TCP-2.

AT YOUR ELECTRONIC PARTS DISTRIBUTOR
WELLER ELECTRIC CORP., Easton, Pa.
WORLD LEADER IN SOLDERING TECHNOLOGY

In Canada: Grant Brothers Sales Co., 18 Hook Ave., Toronto 9; A.C. Simmonds & Sons, 100 Merton St., Toronto 7.
In Europe: Weller Elektro-Werkzeuge G.m.b.H., 7122 Besigheim Am Neckar (Postfach 140), West Germany.

Circle 56 on literature card

AGC Troubles

(Continued from page 29)

input to the video amplifier and too much contrast in the picture. The excessive input level also results in compression of the sync portion of the composite signal, and since the video output signal is fed to the sync separator, it's easy to see how the compressed video output signal creates unstable sync.

Supplemented AGC Systems

This type of AGC circuit derives the control voltage from two sepa-

rate sources. On weak signals, the DC component of video across the detector load resistor (R1 in Fig. 8A) is the main source of control voltage. On stronger signals, the negative voltage developed through signal rectification by the grid and cathode of the sync separator increases, and a portion of this negative voltage is coupled into the AGC line. Because of the connection between the sync separator and the AGC line, a controlled tube with slight gas or grid emission can result in sync instability before excessive

**FOR UNEXCELLED PERFORMANCE
FOR CUSTOMER SATISFACTION**

**These two will do
the best job for you!**



HALLMARK 3000

**30 WATT TRANSCEIVER FOR BUSINESS AND INDUSTRIAL SERVICE:
FCC TYPE ACCEPTED.**

A top performer for dependable, long range business communications in the 25 to 50 MC band. The compact, rugged design make best use of the features of tubes and transistors. Receiver sensitivity is 0.3 μ v for 10db S+N/N ratio. Selectivity is better than 30db. Transistorized modulator gives maximum "talk power." Power to antenna is 20 watts. Transistorized mobile power supply. Available in 115 VAC and 12 VDC models. Suggested list: \$269.50.



HALLMARK 1250

**12 CHANNEL, CRYSTAL
CONTROLLED CB DESIGNED
LIKE A 15 WATT UNIT.**

A unique hand-wired modular chassis gives a new small size that fits any vehicle. The sensational 1250 features a silicon rectifier full wave bridge, electronic switching and an improved ferrite speaker. Four rugged latches provide easy access for maintenance and to crystal sockets. Sensitivity is 0.3 μ v for 10db S+N/N ratio. Adjacent channel rejection better than 45db. Modulation exceeds 95%. RF power output is 3.4 watts or better. Dual powered. Suggested list: \$169.50.


SPECIAL OPTION: Model 1250X—Has plug-in transistorized power supply. Suggested list: \$189.50.

Write for complete information.

HALLMARK INSTRUMENTS

2620 Freewood • Dallas, Texas 75220 • FL 7-0184


Circle 57 on literature card

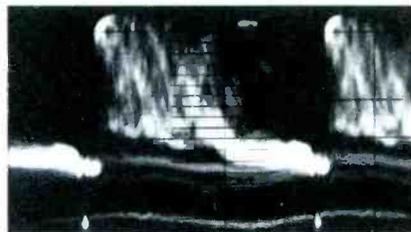


(A) Video-amplifier grid (abnormal)



(B) Video output (abnormal)

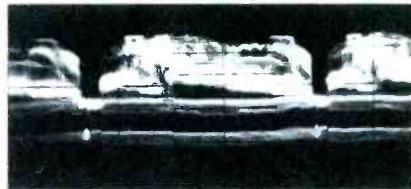

(C) Video-amplifier grid (normal)

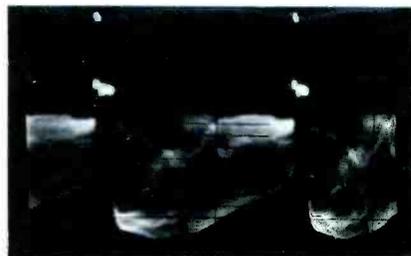

(D) Video-output (normal)

Fig. 7. Receiver waveforms shown in Fig. 6.

contrast becomes noticeable.

Troubles produced by gassy tubes are so varied they are almost impossible to catalog. For example, Philco uses the supplemented AGC arrangement shown in Fig. 8 in several models. In one case, a 10H25 chassis with gassy tubes in the first and second IF stages produced a negative picture (Fig. 9) due to overloading of the third IF stage. In this receiver, the voltage drop across AGC filter resistor R49 was more than 10 volts. When new IF tubes were installed, there was still a drop of 3 volts across R49, but this is normal because R47 is connected to a 20-volt source to provide a delay voltage.

Just as troubles in the AGC portion of this circuit can act to produce sync troubles, defects in the sync portion can also produce AGC troubles. For example, in early General Electric sets using a circuit similar to Fig. 8B, a slightly leaky coupling capacitor feeding the

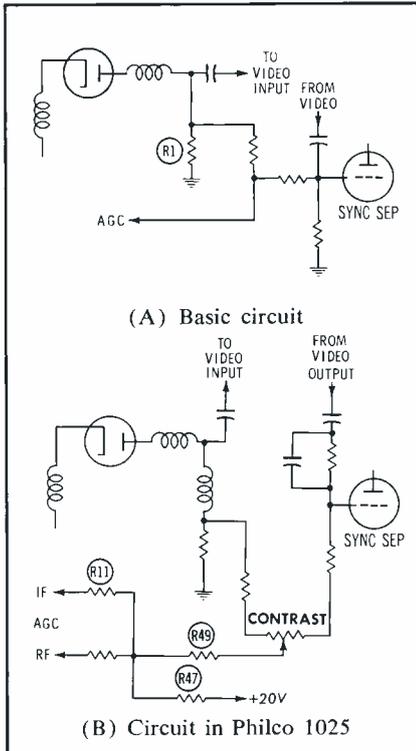


Fig. 8. Circuits producing supplemental AGC.

grid of the sync separator resulted in excessive contrast along with disabling of the contrast control.

Trouble With Peak AGC

In peak AGC, the control voltage is developed by an additional diode fed by the same signal that feeds the detector diode. A simple circuit of this type is shown in Fig. 10A. The signal at the final IF transformer is capacitively coupled through C1 to an AGC diode. A negative voltage proportional to the peak amplitude of the signal is developed across load resistor R1 and is fed through filter resistor R2 to the controlled tubes. For a given signal at the IF output, the peak-developed AGC voltage is greater than the simple AGC voltage (developed across the detector load resistor) would be.

Peak AGC is prone to develop excessive control voltage when the incoming signal has a high noise content. Thus, in noisy locations, receivers using peak AGC may be over-controlled to the point that contrast is below normal.

The circuit shown in Fig. 10B, used in Hoffman 326 chassis, operates exactly like a peak AGC circuit and has the same weakness in noisy



Fig. 9. Negative picture, poor sync resulting from gassy tubes in IF strip of TV receiver.

locations. One of these Hoffman sets exhibited poor contrast and the presence of interference, as shown in Fig. 11. The dark interference bar appeared to be the result of replacing the selenium rectifier with a silicon unit.

With the assumption that the interference could be cleared up easily, we turned our attention toward the weak-contrast condition. The weakness was caused by excessive AGC voltage, but the reason for this excessive voltage could not be determined. Finally the technician decided to clear up the interference by shunting the silicon rectifier with a .002-mfd capacitor. Immediately

SENCORE

SIMPLIFIES SWEEP CIRCUIT TROUBLE SHOOTING

SS117 SWEEP CIRCUIT ANALYZER

For Color and Monochrome Testing

A professional trouble shooter that helps you methodically walk the trouble out of "tough-dog" sweep circuits in monochrome and color receivers. The SS117 provides a positive but simple push button test on all circuits indicated in the block diagrams. These time-consuming circuits are checked step-by-step with tried and proven signal injection and substitution methods. All checks can be made from the top of the chassis or from under the chassis when it is removed from the cabinet.

TV horizontal oscillator check is made by substituting a universal oscillator known to be good. Horizontal output check consists of a cathode current and screen voltage test. The TV horizontal yoke is checked by substituting a universal yoke from the SS117 and viewing brightness or restoration of 2nd anode voltage. Horizontal flyback is checked dynamically in circuit by measuring the power transfer to the yoke when TV is turned on. TV horizontal sync can be used to control the SS117 horizontal oscillator, providing a positive check on sync from the video amplifier to the TV oscillator. Vertical circuits are tested by simple signal injection from vertical yoke to oscillator for full height on CRT. The SS117 with the CA122 Color Analyzer provides a complete TV analyzer for virtually every stage in monochrome or color receivers.

External checks for AC, DC, peak to peak voltage readings and DC current in the upper right hand corner save using a separate VTVM. Accurate 2nd anode measurements up to 30,000 volts are made with a sensitive 300 microamp meter and the attached high voltage probe. AC outlets, all steel construction and mirror in the cover makes every servicing job easier.

Size: 10 1/4" x 9 1/4" x 3 1/2". Wt. 10 lbs.

Dealer Net..... 89.50

Circle 58 on literature card



The SS117 checks them all

	SYNC. CIR. & H. SYNC. DISCRIM.	VERT. OSC.	VERT. OUTPUT	VERT. OUTPUT XFMR	VERT. DEFLEC. YOKE
	HORIZ. OSC.	HORIZ. OUTPUT	HORIZ. FLYBACK XFMR	2nd ANODE VOLTAGE CIRCUIT	HORIZ. DEFLEC. YOKE

FREE—A 33 RPM half hour permanent record packed with every unit explains each test.

NEW SAMS BOOKS

Two-Way Mobile Radio Handbook Newly Revised and Enlarged Edition

by Jack Helmi. Describes and analyzes the latest developments in 2-way communications equipment. The most comprehensive coverage of mobile radio for new buyers, present users, and those interested in servicing this type of equipment. Covers operational theory of basic systems; types of receivers available; transmitters, control systems; power; servicing and maintenance (includes pointers on setting up a mobile-radio service shop). Invaluable for practical understanding of 2-way radio circuitry and equipment. 256 pages; 5 1/2 x 8 1/2". **\$395**
Order **MRS-2**, only.....

TV Receiver Tube Usage Guide

by the Howard W. Sams Engineering Staff. Available for the first time—a complete guidebook for TV technicians, listing the tubes, fuses, and semiconductor diodes required to repair individual TV models. Receivers are listed by manufacturer, chassis and model numbers—data provided tells you exactly what to take along to repair a specific set. Covers over 25 different manufacturers of hundreds of TV models (including color receivers). Tubes and functions are listed for each model, along with fuses and diodes used. This real time-saver belongs in every tube caddy and on the workbench. **\$195**
96 pages; 5 1/2 x 8 1/2". Order **TUR-1**, only.....



ONLY COURSE OF ITS KIND
5-Volume HOWARD W. SAMS

Basic Electricity/Electronics

New, unique positive training worth hundreds of dollars. First completely new course to be published in the last 10 years...using the latest programmed method for quick, effective learning.

- Vol. 1. Basic Principles & Applications
- Vol. 2. How AC & DC Circuits Work
- Vol. 3. Understanding Tube & Transistor Circuits
- Vol. 4. Understanding & Using Test Instruments
- Vol. 5. Motors & Generators—How They Work

(Complete Set contains over 1300 pages; 1250 illustrations; 51 chapters; in sturdy slipcase)
Order **ECY-50**, only..... **\$1995**

Technical Writer's and Editor's Stylebook

by Rufus P. Turner. The first practical and complete guide for technical writers and editors. Describes the fundamentals of technical writing for magazine articles, books, reports, etc. Explains in text and examples the basics of good writing techniques; use of tech symbols, mathematics, technical phraseology, punctuation, capitalization, prefixes and suffixes, devices for emphasis, etc. Tells how to prepare an outline, how to ready a manuscript for publication. Has appendices showing symbols from various technical fields. An invaluable reference for writers in any technical field. 192 pages; 5 1/2 x 8 1/2". **\$395**
Order **TWS-1** (softbound), only.....
Order **TWH-1**, (hardbound), only..... **\$4.95**

Handbook of Algebraic & Trigonometric Functions

by Allan Lytel. A complete selection of basic formulas and tables of mathematics at the high school and beginning college level. The first part of the book includes formulas for geometry, algebra, trigonometry, and calculus; the second part is devoted to 24 sections of mathematical tables and conversions. An extremely practical reference for students, technicians, and engineers. 160 pages; 5 1/2 x 8 1/2". Order **ALG-1**, only..... **\$295**

Replacement Guide for TV & Auto Radio Controls

Vol. 6. Bigger and better than ever—covers over 38,000 TV and 1500 auto radio models. Lists recommended replacement controls made by Centralab, Clarostat, CTS-IRC, and Mallory. 192 pages; 8 1/2 x 11". Order **RGC-6**, still only..... **\$100**

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. PF-9, 4300 W. 62nd Street, Indianapolis, Ind. 46206

Send me the following books:

- MRS-2 ECY-50 TWH-1 RGC-6
 TUR-1 ALG-1 TWS-1

\$_____ enclosed. Send FREE Booklist

Name _____

Address _____

City _____ State _____ Zip _____

My Distributor is _____

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

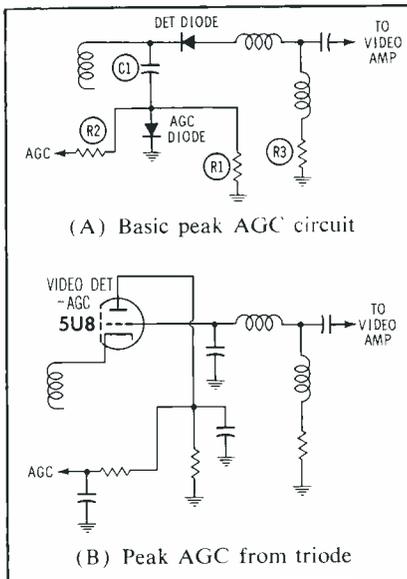


Fig. 10. Circuits in which AGC voltage is determined by peak level of video IF signal.

the contrast increased to normal; the AGC voltage was found to be reduced by about 2 volts. The installation of the silicon had provided the set with its own built-in noise generator, and the AGC voltage was being determined by the peak amplitude of the noise.

Summary

The examples of troubles in each of these AGC systems are representative of abnormalities that can affect AGC action. The bleeding off of AGC voltage by gassy tubes parallels the effects of a leaky AGC filter capacitor. Insufficient AGC voltage in supplemented circuits can be due to other sync-separator components than those in the specific cases presented. Generation of excessive AGC in peak circuits may result from other types of noise than the one described; a particular offender is pulse feedback from the horizontal-deflection circuit.

By recognizing these circuit types and by knowing their characteristics and limitations, the service technician is better prepared to find solutions to AGC troubles. ▲



Fig. 11. Horizontal interference caused low contrast in receiver using peak AGC circuit.

NEW PRICES from QUIETROLE

the oldest, most widely proved and sold radio and TV lubricant



	LIST
2 oz. bottle with dropper	\$1.49
	LIST
4 oz. bottle	2.54
	LIST
4 oz. bottle (brush-n-cap)	2.64
	LIST
8 oz. bottle	5.07
	LIST
6 oz. spray can — with extender	2.79
	LIST
3 oz. spray can — with extender	1.79

Quietrole is your guarantee of the most effective, quick silencer of noisy radio and TV controls — the quality product that is a top value. Get Quietrole at quality jobbers. Some territories available for Experienced Representation.



manufactured by **QUIETROLE Company**
Spartanburg, South Carolina

Circle 59 on literature card



TYPE L . . . for long, long years of service life ask your distributor for **PLANET LYTICAPS**, the universal replacement type electrolytic capacitor. Available in a wide range of capacities in voltages from three to five hundred. LYTICAPS are "Engineered for Quality".

PLANET SALES CORP.

225 Belleville Ave.
Bloomfield, New Jersey

Circle 60 on literature card

Solid State

(Continued from page 37)
 triggered. Take a look at the diagram in Fig. 2. When normal AC voltage is applied, but no gate current is injected, the SCR will not conduct in either direction. When a positive voltage is applied between the gate and the cathode (N), a slight forward current flows and triggers the unit into action. The function of the unit is then merely that of a rectifier; current can flow from cathode (N) to anode (P) but not the reverse.

The SCR has another characteristic that is strangely reminiscent of the tube thyatron. Once the gate current has started forward conduction across the main junction, the primary junction will continue to conduct after the gate pulse is removed. Thus, the junction maintains a very low resistance as long as the forward current remains above a certain *holding* level. The forward conductance can be stopped only by extinguishing the main junction current.

When the current thus ceases, the junction will no longer permit current to flow in either direction, until

another gate pulse arrives. This action can be set to useful tasks, by merely using the gate to control the primary action of rectifying. By timing the gate to occur at 270° in the cycle, 60 cps power could be made effective during only one-fourth of its total time, as shown in Fig. 2. This would have the same effect on a load as using a step-down transformer or a voltage-dropping resistor to reduce power; the SCR is infinitely more compact and is less wasteful of power.

SCR's are expensive by comparison with less efficient methods of controlling power, but increased use and production are rapidly driving prices downward. Very soon, you'll be encountering these devices in all sorts of controls for home and industrial use.

Zener Diodes

These devices, some of selenium but mostly of silicon, are the true voltage regulators of the solid state family. Their function is simple to explain. Zener diodes are constructed so that they do not conduct at all until a certain specific voltage is reached; beyond this point the

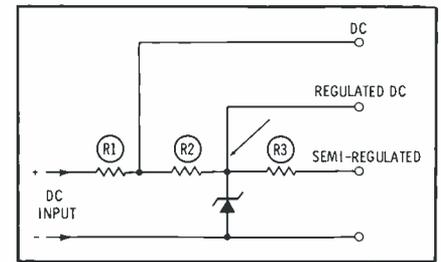


Fig. 3. Zener diode simple voltage regulator.

amount of their conduction is dependent on the voltage applied. Thus, if a 7.5 volt zener diode is connected as shown in Fig. 3, the voltage at that point will be held at exactly 7.5 volts. Current in the zener unit will be just sufficient to drop any excess voltage across R2, maintaining a constant potential at the point indicated by the arrow. Voltage following R3 will depend on the load, but can in no case exceed the voltage set by the zener diode.

The cost of zener diodes is low enough to make them attractive in all sorts of low-voltage regulation applications. They can be used to protect equipment, meters, and other semiconductor devices from overload caused by voltage surges or

ALL NEW SENCORE component substitutor



All your favorite Sencore Substitution Time-Savers in One Compact Unit

A complete range of carbon resistors, wire wound power resistors, capacitors, electrolytics, and universal selenium and silicon rectifiers.

Imagine, all of these hard to locate parts at your finger tips for on the spot substitution. Say goodbye to messy, crumpled parts, unnecessary unsoldering and soldering of components for testing purposes only. Save valuable servicing time and be sure, by substituting.

NEW . . . each section operates independently with a value close enough for every substitution need. Components in each section are isolated from chassis and from the other sections. For example, a complete power supply can be constructed using the RC121 Components only.

NEW . . . dual electrolytics provided. A new circuit enables you to substitute up to 25 single electrolytic values or 9 duals. Exclusive surge protector provides protection on both singles and duals for both you and the circuit.

You save space and money. Equivalent Sencore substitution pieces purchased individually (H36, PR111, RS106, ES106) cost you \$54.00

RC121 (all hand wired, all American made) only 3995
RC121K (Kit) 27.95

Now in stock at your Sencore Distributor. See him today!
 Circle 61 on literature card

S E N C O R E

ADDISON 2, ILLINOIS

1

Genuine, fresh Little Devil® resistors (on "Tally Tape" or in Cabinet Assortments)

2

Quality 2-watt pots. Type AB

3

Gold-bonded germanium diodes at "entertainment diode" prices.

3 WAYS TO MAKE SURE IT STAYS FIXED

You're always safe, always sure with any of these three quality replacements. Why be otherwise? Repair jobs that boomerang cost you hard-earned profit. Little Devil® resistors come in 1/10, 1/4, 1/2, 1, and 2 watts from 2.7 ohms to 22 Megs . . . AB Pots from 50 ohms to 5 Megs in several shaft lengths and styles . . . gold-bonded diodes in ninety 1N types off the shelf.

Call your distributor for the latest Ohmite Stock Catalog 30.

Be right with



Circle 62 on literature card

transients. They can even be used back-to-back to clip both positive and negative waveform peaks.

Zener diodes are usually classified primarily by the voltage at which "zenering" begins, and within a broad category of power ratings. Low-power units start at about 500 mw, with zener voltages ranging from 6.2 volts through 200 volts. Thus, these solid-state voltage regulators can be used in almost any circuit that you are likely to encounter in electronics. They can even be wired in series to increase the total voltage rating. Industrial types up to 50 watts are generally available, with zener ratings comparable to the low-power units.

In appearance, zener diodes are very similar to other silicon units. They are available as epoxy- or ceramic-encapsulated, top-hat, and stud-mounted units. The type of case used depends, as with silicon rectifiers, on the power that must be dissipated; heat sinks are often necessary.

A Touch of the Old

As mentioned earlier, selenium rectifiers are still used extensively, and thus deserve some consideration as solid state devices. Many of the selenium unit's characteristics are similar to those of silicon rectifiers. They both require a certain level of forward voltage before they begin to conduct—usually around .5 volt. Selenium cells, however, do not show nearly so sharp a decrease in forward resistance as do silicon; furthermore, the resistance of a selenium rectifier increases noticeably with age, reducing efficiency considerably.

Selenium rectifiers are primarily rated according to the amount of DC output current they will produce. Power-supply seleniums start at about 10 ma and are available in sizes up to 2 or 3 amps. Higher-rated units are made, but cost and efficiency are sacrificed; other types can do that job better in many instances.

Like silicon rectifiers, seleniums are usually protected from surges that occur at the time of initially applying power to the circuit. Series resistance usually is chosen in the same manner as for silicon, and ranges in value from 3.3 ohms with one typical TV unit to 47 ohms for

the small-current rectifiers used in many radio power supplies.

Selenium Diodes

Another common use for selenium is in small, low-power diodes for circuits such as the horizontal AFC of television sets (Fig. 4). Computers make extensive use of selenium diodes, as do many other instruments and industrial electronic assemblies. They are even found in communications equipment as balanced modulators and in similar applications.

Selenium diodes of this type are usually designed to handle very small currents. One typical unit is rated at 250 ua average current, with a peak capability of only 2.5 ma. Peak reverse voltages applied to these units can rarely exceed 75 volts.

Thyrectors

These specialized solid state devices also use selenium as the basic junction material. Their principal use is for suppressing transient voltages, in somewhat the same as the zener diodes already described. The difference is that thyrectors act much more quickly, and will withstand higher momentary currents.

There are two general types. One is similar to the "back-to-back" configuration familiar in dual diodes, and is called an AC thyrector. The other is symbolized as an ordinary solid state diode, and is called a DC thyrector because it clips only transients that occur in one direction.

Ratings are by voltage range. For example, one group of AC thyrectors is designed to suppress transients in the range of 0-25 volts, while another group fills the range from 25-50 volts. DC thyrectors are rated in the same manner.

Some thyrectors require cooling fins; physically, they look exactly like selenium power rectifiers. Others appear similar to miniature electrolytic capacitors, but appearance is where the resemblance ends.

Signal Diodes

Last, but not least, are the "little people" of the solid state family—the small-signal diodes. These are made principally of germanium. They are delicate miniature units that require deliberate and careful handling in both design and operation.

Ratings begin with current levels

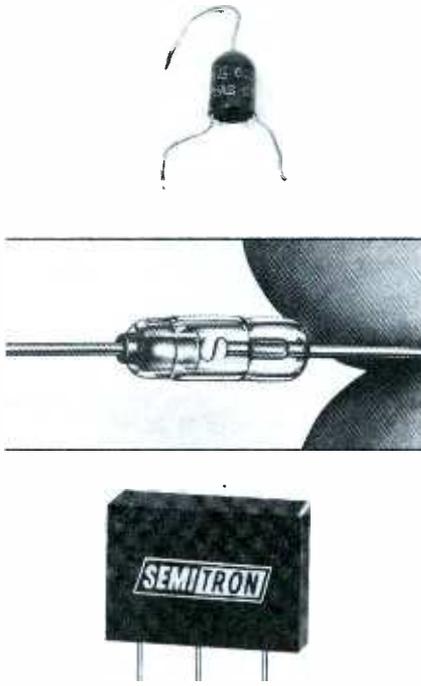


Fig. 4. Selenium diodes used in horizontal AFC circuits come in various shapes, sizes, of a few microamps, and extend to a few hundred milliamps. Peak inverse ratings—the amount of reverse voltage the unit can withstand—seldom exceed 150 volts, except in special units.

Germanium diodes are used extensively as video detectors, AGC rectifiers, metering rectifiers—in short, any application where the applied DC voltage is slight and the signal voltages are low. They are responsive to much higher frequencies than other types of solid state rectifiers, and thus are used in almost all RF or supersonic applications.

Heavy-duty units are available, but the cost is usually great enough that the application must be a very special one to justify the expense.

What's For Tomorrow?

Solid state rectifiers are indeed coming into their own. From the small number of "fixed-detector" germanium crystals available just over a decade ago, solid state diodes have been diversified to take almost every form imaginable, and almost every job available. Some perform well as oscillators—the Esaki or tunnel diode is an example. Others regulate and control the actions of other solid state devices—and even tube devices.

Make it a point to increase your familiarity with solid state rectifiers; they represent the electronics of tomorrow, and you'll need to know all you can about them. ▲

I. F. & R. F. COILS

30,000 O.E.M. Replacement Parts in our Catalog No. 164
Even non-listed items receive our same day service
Just send us model no., part no. or defective unit

across the nation
it's

J. W. MILLER

J. W. MILLER COMPANY

Factory: 5917 S. Main Street Los Angeles 3, Calif U.S.A. Phone ADams 3-4294—FAX No. XCM

Circle 18 on literature card



MAKE EXTRA PROFITS WITH THIS NEW HEATHKIT® FM STEREO GENERATOR

ONLY \$99.00

- Everything you need for fast, simple servicing & alignment
- Produces all signals required for mono & stereo FM servicing

Enter the profitable field of mono & stereo FM servicing now! This new Heathkit FM stereo generator offers complete facilities for every alignment and trouble-shooting need. Signals generated by the IG-112 include audio or composite stereo signals for tuner, receiver and multiplex adapter adjustments . . . phase test for accurate alignment of subcarrier transformers . . . special SCA frequencies (65 & 67 kc) for aligning even the most advanced-design tuners . . . a crystal-controlled 19 kc (± 2 cps) pilot signal, adjustable from 0 to 10% to check the lock-in range of stereo receivers . . . sweep function with built-in markers for overall IF & RF alignment . . . a 100 mc RF carrier (adjustable ± 2 mc) mono or stereo modulated . . . and many more! Balanced 300 ohm RF output permits direct connection to the antenna terminals of unit under test without complicated matching networks! Complete with test leads and detailed stereo alignment instructions. Order your Heathkit IG-112 now for faster, easier servicing and extra profits in this greatly expanding field of stereo FM!

Kit IG-112 . . . 10 lbs. . . \$10 dn., \$9 mo. \$99.00
Export model available for 115/230 VAC, 50-60 cps; write for prices.

FREE CATALOG
Over 250 exciting Heathkits available in easy-to-build kit form. Save 50% or more by doing the easy assembly yourself! Send for your free catalog today!

HEATH COMPANY, Dept. 25-9-1
Benton Harbor, Michigan 49023

Name _____ (Please Print)

Address _____

City _____ State _____ Zip _____

Prices & specifications subject to change without notice. TE-130R



send for NEW FREE
CRYSTAL CATALOG
with NEW TRANSISTOR
OSCILLATOR CIRCUITS

**3 PLANTS TO SERVE YOU BETTER
HERMETICALLY SEALED
PRECISION GROUND
CUSTOM-MADE
NON-OVEN CRYSTALS**

Gold or silver plated, spring mounted, vacuum sealed or inert gas, high freq. stability, 10 milliwatt max. current cap. Meet mil. specs.

- 1000KC to 1600KC (Fund. Freq.) Prices on Request
1601KC to 2000KC (Fund. Freq.) \$5.00 ea.
2001KC to 2500KC (Fund. Freq.) 4.00 ea.
2501KC to 5000KC (Fund. Freq.) 3.50 ea.
5001KC to 7000KC (Fund. Freq.) 3.90 ea.
7001KC to 10,000KC (Fund. Freq.) 3.25 ea.
10,001KC to 15,000KC (Fund. Freq.) 3.75 ea.
15MC to 20MC (Fund. Freq.) 5.00 ea.

OVERTONE CRYSTALS

- 15MC to 30MC Third Overtone \$3.85 ea.
30MC to 40MC Third Overtone 4.10 ea.
40MC to 65MC Third or Fifth Overtone 4.50 ea.
65MC to 100MC Fifth Overtone 6.00 ea.

DRAKE 2-B Receiver Crystals \$4.00
(All Channels—Order by Freq.)

OVEN-TYPE CRYSTALS

For Motorola, GE, Gonset, Bendix, etc.

Add \$2.00 per crystal to above prices

SUB-MINIATURE PRICES slightly higher

ORDER FROM CLOSER PLANT
TEXAS CRYSTALS

DEPT. PF
1000 Crystal Drive
FORT MYERS, FLORIDA
Phone 813 WE 6-2109



AND
4117 W. Jefferson Blvd.
LOS ANGELES, CALIF.
Phone 213-731-2258

Circle 66 on literature card



**NEED A 110 V.
A. C. OUTLET?**

**IN CAR, BOAT OR TRUCK,
YOU HAVE IT WITH A**

**terado POWER
INVERTER**

Actually gives you 110 volt, 60 cycle A.C. from your 6 to 12 volt D.C. battery! Plug inverter into cigarette lighter, and operate lights, electric shavers, record players, electric tools, portable TV, radios, testing equipment, etc. Frequency stable within one cycle.

See Your Electronics Parts Jobber, or Write:

Models from 15 to 300 watts, priced as low as **\$12.95** LIST



Circle 68 on literature card

Aircraft Radio

(Continued from page 35)

ceivers resemble conventional superheterodynes with tunable local oscillators. Fig. 1 shows a block diagram of the type R-32 receiver manufactured by Aeronautical Radio Corp, a typical unit. This receiver employs two RF amplifiers for high selectivity, tunes from 108 mc to 135 mc, and has an IF of 15 mc. The receiver itself is separated from the tuning dial which usually is on the instrument panel. A flexible cable connects the two for rotation of the tuning capacitors.

A disadvantage of the continuously tuned receiver is that it must be tuned to the station in the manner of a conventional household radio. Thus, unless a carrier is being transmitted, it is difficult to set the dial correctly. Furthermore, pilots are generally busy with other duties at the critical moment when a radio must be tuned. Crystal-tuned receivers eliminate this disadvantage of continuously tuned receivers as well as that of questionable stability.


Fig. 2 shows the block diagram of a typical crystal-tuned superheterodyne receiver (the Collins 51X3). A local frequency is synthesized by doubling the frequency of a third-harmonic crystal and adding in a second mixer the output of another oscillator. By proper choice of frequencies, the lower-frequency oscillator can be switched to ten different crystals providing steps of 100 kc, and the higher-frequency oscillator-doubler can be switched to provide steps of 1 mc throughout the desired band.

The tuning capacitor shafts in the RF stage are ganged to the crystal switch. When the switch snaps to another position, the common shaft moves the capacitor rotor to the proper position for resonance at the chosen frequency. It can be seen

Table 1. Aviation Frequency Assignments (mc)

118.00-121.40	(Every 50 kc) Airport control.
121.50	Emergency.
121.65-121.95	Air Traffic Control (ATC).
122.00-123.05	(Every 50 kc, except 122.80 and 123.00) General aviation air-to-ground.
122.80	Advisory (UNICOM).
123.00	Advisory.
123.60-128.80	(Every 50 kc) ATC.
132.05-134.95	(Every 50 kc) ATC.


SAVES
your back ...
SAVES
your time ...

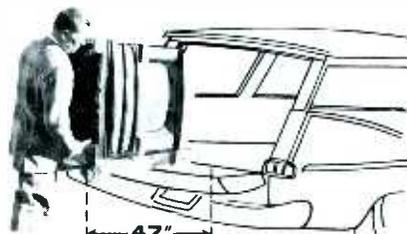

YEATS

SHORTY DOLLY
for
RADIO and TV

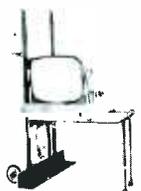just 47 inches high for STATION WAGONS
and PANEL PICK-UPS



FOLDING PLATFORM
15 1/4" x 24 1/2" top.
Snaps on or off.
(Platform only)
\$11.95

Designed for TV, radio and appliance men who make deliveries by station wagon or panel truck ... the short 47 inch length saves detaching the set for loading into the "wagon" or pick up. Tough, yet featherlight aluminum alloy frame has padded felt front, fast (30 second) web strap ratchet fastener and two endless rubber belt step glides. New folding platform attachment, at left, saves your back handling large TV chassis or table models. Call your YEATS dealer or write direct today!



YEATS
Model No. 5
Height 47"
Weight 32 lbs.



FURNITURE PAD

"Everlast" COVER AND PADS

YEATS semi fitted covers are made of tough water repellent fabric with adjustable web straps and soft, scratchless white flannel liners. All shapes and sizes — Write



TV COVER



APPLIANCE DOLLY SALES COMPANY

1307 W. Fond du Lac Ave. • Milwaukee, Wisconsin

Circle 67 on literature card

that the design problems of such a receiver are as much mechanical as electrical. Lead dress becomes a matter of mechanical design, and capacitor-switching arrangements are carefully integrated.

VHF Transmitters

VHF transmitters all use crystal oscillators because no other convenient means is available for maintaining the FCC frequency tolerance of $\pm 0.01\%$. A typical VHF transmitter for light planes is the NARCO VTA-3 shown in Fig. 3. The circuit consists of a 12BY7A electron-coupled oscillator-doubler employing as many as 27 third-overtone crystals in the 30-mc range. The crystal frequency is doubled in the plate circuit of the 12BY7A. The resulting signal is coupled to the next stage which acts as final amplifier and doubler. The tank circuits are fixed-tuned to a frequency just above the highest frequency to be used. This causes some spurious radiation, but it is tolerable under normal circumstances.

More sophisticated transmitters utilize crystals arranged in a digital fashion similar to that used for synthesizing the local oscillator frequencies in VHF receivers.

As pointed out previously, VHF transmitters in airplanes are required to emit relatively little power because airborne antennas are capable of transferring relatively greater amounts of power in the VHF range to a distant receiving antenna. This is a great advantage of VHF, and transmitted power ranges from only .5 watts in many private aircraft to no more than 25 watts in airline service. Maximum VHF reception distances are listed in Table 2.

The first part of this series has been concerned primarily with aircraft communication systems. The concluding part of the series will discuss radio navigation systems. ▲

Table 2. VHF Reception Distances

Feet Above Ground	Reception Distances (Miles)
1000	45
3000	80
5000	100
10,000	140
15,000	175
20,000	200


With the introduction of the Outdoor Specialist Series and the Model OH-10 weatherproof high fidelity sound system, Oxford has the most advanced, most imaginative units on the market.

The Outdoor Specialists (Models OP-6 and OP-8) incorporate new materials and design innovations that result in indestructible paging and talkback speakers with the highest efficiency available. This new series also features the most versatile mounting bracket — Oxford's LEVER-LOCK* swivel bracket which has complete freedom of motion to position the speaker and locks tight with the flip of a lever.

The OH-10 is a masterful blending of the most advanced acoustic and mechanical design. Its woofer-tweeter speaker system reproduces the entire audio range with comparable quality to expensive speaker systems used in the home. Mechanically, its die-cast aluminum construction will withstand severe abuse and so attractive is its decorator design that it will blend with almost any surrounding.

If you want public address speakers incorporating today's advanced design and newest techniques — write today for complete information and specification sheets.

*patent pending

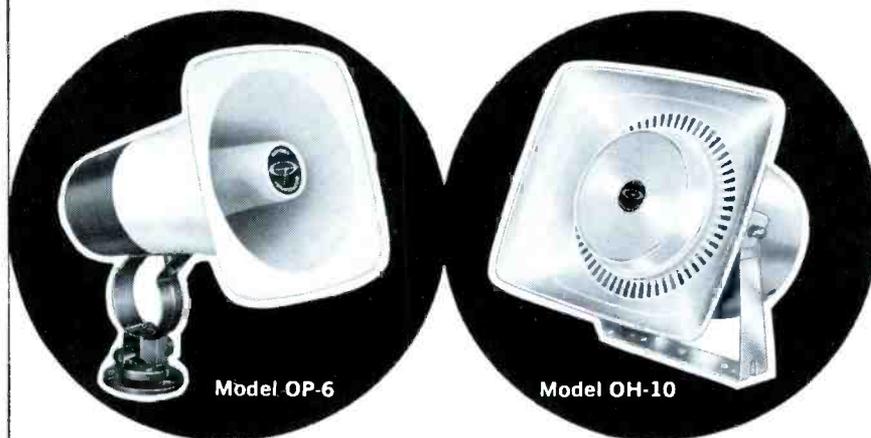

**NOW, IT'S OXFORD FOR
ADVANCED OUTDOOR
SPEAKERS**



OXFORD TRANSDUCER CORPORATION

A Subsidiary of OXFORD ELECTRIC CORPORATION

2331 North Washtenaw Ave. • Chicago 47, Illinois

Circle 69 on literature card



Product Report

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.



Rectifier Offer (143)

The "Combination Pak" No. HDR1000 contains ten heavy-duty silicon rectifiers and one gold-plated man's Lucerne wrist watch. The top-hat silicon rectifiers in the **Semitronics** package are rated at 1 amp, 500 PRV, and are universal replacements for TV, radio, phono, and hi-fi use. The Swiss-made antimagnetic watch has a sweep second hand, unbreakable lifetime mainspring, and luminous dial. Normal retail value of the package is \$29.95, but it is available in this special offer for \$14.95.



Dynamic Microphone (144)

A shock-mounted cardioid dynamic microphone, the Model 8000 was designed basically for home-recording applications; however, it is also suited for use in churches, schools, location broadcasting, etc. The cartridge produces a smooth frequency response from 70 to 15,000 cps. Under normal operating conditions, the diaphragm retains its original level of performance throughout the life of the microphone. This **LTV University** product sells for \$29.95 and carries a five-year warranty against faulty material and workmanship.



Selective Communications (145)

Two-way radios may be equipped to receive only desired calls, on an all-unit or a selective basis, with the **Cadre** Model 524. This transistorized unit operates with the company's 5-watt solid-state transceivers and other 12-volt two-way radios. Connections are made through the speaker and power supply of the transceiver. A microphone adapter plug is furnished. Unit cost for base or mobile stations is under \$70, and installation takes only a few minutes.



Portable Amplifier (146)

The all-transistor "Ampli-Vox" Model S-700 is powered by flashlight batteries and is designed to deliver professional-quality sound. A single control turns the unit on and off and adjusts the volume. This **Perma-Power** amplifier is rated at 25 watts EIA music power, 40 watts peak. Its two inputs make it suitable for use with a microphone and a tuner, phonograph, or tape recorder; outputs are provided for two 8-ohm speakers. The amplifier measures 8 3/8" x 3 1/2" x 8 3/4" and weighs 7 lb. with batteries. Net price is \$69.95 without batteries.

Mobile Antennas (147)

A new "Band Spanner W-600" line of 13 antennas developed by **Webster Mfg. Co.** covers frequencies in the 25-to-54 mc and 144-to-470 mc bands. The selected antenna can be tuned to match a particular transmitter by rotating the lower barrel of the antenna base for lowest



possible VSWR and then locking the barrel in place with a setscrew. Metal parts are chrome-plated solid brass. The transformer coil is moisture-proof, and the trapping of moisture within the antenna base is eliminated by a triple washer arrangement with a drain hole. The suggested list price is \$34.95.



GC Counter Model
ELECTRONICS AUTOMATIC
No. 36-802 TUBE TESTER

Automatic Tube Tester (148)

Automated tube testing and simplicity of operation are provided by the Model 36-802 counter-model tube tester. The **GC Electronics Co.** unit tests 7-, 9-, and 10-pin miniatures, 5- and 7-pin nuvistors, novars, compactrons, octals, loktals, fuses, panel lights, and vibrators. Grid-cathode leakage up to 6 megohms or filament-cathode shorts up to 500K ohms can be detected. A leakage and quality test for multisection tubes is also provided. A shorted tube actuates a flashing sign; at the same time, the tester is automatically deactivated to prevent damage. The tester is warranted for 90 days and has a suggested net price of \$325.00.

Power Supply (149)

A new dual-voltage power supply, of low cost and high stability, provides both positive and negative voltages from individual outputs. Up to 300 ma can be drawn from the two outputs simultaneously; adjustable output voltages range from 0 to 15 volts. Ripple and noise are less than 5 mv at 15 volts and 300 ma.



The instrument, intended for use by transistor circuit designers and experimenters, requires a maximum input of 100 watts at 117 volts, 60 cps. The **Buckeye Stamping Co.** Model PS-100 measures 7" x 5" x 4", weighs 2½ lb, and sells for \$49.95.



Transistorized Inverter (150)

The 12.6-volt output from a storage battery can be changed to 115 volts AC by use of **Merit's** new inverter, Model INV-12-40. The inverter uses two 2N234A power transistors to supply 50 watts intermittent or 40 watts continuous output power. The unit is housed in a steel case with a green finish. A 3-foot cord with attached plug is provided for connection to a cigarette-lighter receptacle.



Stereo Ceramic Cartridge (151)

Positive scratch protection is one of the prime features of the new "Featheride" stereo ceramic cartridge from **Electro-Voice**. The protection is assured by a spring-suspension mechanism that permits the cartridge to pivot when sudden force is applied, bringing the front end (and therefore the stylus) up off the record surface and bringing a soft "sole" to bear on the record surface. The "Featheride" is offered in two types, usable in phono units tracking at any force between 2 and 6 grams. It can be mounted in any tone arm having standard ½" or 7/16" mounting centers.



Space-Saver Fuseholder (152)

A new compact, miniature space-saving fuseholder has been developed by **Bussmann**. The panel-mounted unit is only 1½" long and extends just 29/32" behind the front of a panel. It accepts ¼" x 1¼" fuses and can easily be converted to take 9/32" x 1¼" fuses by changing the screw-type knob. ▲

Winegard

Dealer of the month

No. 25 of a Series

Irv Beringhaus says: "Here, at the base of the Rockies, we have a tremendous problem with wind and reception. Winegard Colortrons solve both problems."



Winegard salutes Mesa T.V. & Radio, Boulder, Colorado

Irv Beringhaus has been in the rugged country around Boulder for just two years after spending five years as a dealer under the warm Miami sunshine. In both locations he has been a Winegard booster, and now finds the tremendous power and rugged construction of Winegard even more advantageous.

In servicing all of Boulder and the three surrounding towns of Lafayette, Louisville and Nerdeland, Irv has installed Winegard antennas in homes, motels and a variety of business locations. Says Irv, "The performance of Winegard antennas and antenna systems in this extremely rugged terrain has pleased both me and my customers tremendously."

The confidence Irv Beringhaus has shown in Winegard comes from installing Winegard antennas for seven years and seeing them in action under the most taxing conditions. He's one more important service man who knows Winegard's standards of excellence first hand.

Winegard Co.
ANTENNA SYSTEMS

D30091 Kirkwood • Burlington, Iowa

Circle 70 on literature card

INDEX TO ADVERTISERS

ATR Electronics, Inc.	12
Admiral Sales Corp.	84, 85
Alliance Mfg. Co.	67
Antennacraft Co.	76
Arco Electronics, Inc.	81
B & K Mfg. Co.	50, 51, 53, 54, 62
Div. of Dynascan Corp.	
Blonder-Tongue Labs.	41-44
Bussmann Mfg. Div.	20, 21
Castle TV Tuner Service	16
Channel Master Corp.	55, 57, 59
Cleveland Institute of Electronics	75
Delco Radio Div.	79
EICO Electronic Instrument Co., Inc.	27
Electro-Voice, Inc.	80
Electronics Communications, Inc.	83
Enterprise Development Co.	47
Finney Co.	18, 19
GC Electronics Co.	63
Grantham Schools, Inc.	47
Hallmark Instruments	90
Heath Co.	95
Hickok Electrical Instrument Co.	17
JFD Electronics Corp.	Cover 2
Jensen Mfg. Co.	40
Jerrold Electronics	14, 15
L.A. Tuner Exchange	84
Lafayette Radio Electronics Corp.	39
Lectrotech, Inc.	88
Littelfuse, Inc.	Cover 4
Mallory, P. R. & Co., Inc.	22
Mercury Electronics Corp.	68
Miller, J. W. Co.	95
Mosley Electronics, Inc.	60
Nortronics Co., Inc., The	52
Oaktron Industries, Inc.	12
Ohmite Mfg. Co.	94
Oxford Transducer Co.	97
Planet Sales Corp.	92
Precision Tuner Service	52
Quam-Nichols Co.	82
Quietrole Co.	92
RCA Electronic Components and Devices	Cover 3, 45, 65, 69
Raytheon Co.	61
Sams, Howard W. & Co., Inc.	77, 92
Sarkes Tarzian, Inc. Semiconductor Div.	73
Tuner Service	9
Seco Electronics, Inc.	71
SENCORE, Inc.	46, 48, 91, 93
Sonotone Corp.	70
Sprague Products Co.	10
Sylvania Electric Products, Inc.	13
Terado Corp.	96
Texas Crystals	96
Triplett Electrical Instrument Co.	74
University Loudspeakers, Inc.	49
Weller Electric Corp.	89
Winegard Co.	86, 87, 99
Yeats Appliance Dolly Sales Co., Inc.	96



FREE Catalog and Literature Service

*Check "Index to Advertisers" for further information from these companies.

Please allow 60 to 90 days for delivery.

ANTENNAS & ACCESSORIES

76. **ALL CHANNEL PRODUCTS**—New catalog showing *Rembrandt* Model 283 outdoor antenna for VHF, UHF, and FM reception.
77. **ANTENNACRAFT**—Latest information on FM antennas, featuring new omnidirectional model for multiplex or monophonic broadcasts.*
78. **CLEAR BEAM**—Catalog listings for an additional line of indoor antennas.
79. **FINNEY**—Catalog No. 20-307 listing four newly announced multielement, single-boom, VHF-FM antennas.*
80. **G. F. WRIGHT**—Catalog sheets on guy wire used with outside antenna installations.
81. **JERROLD**—Illustrated brochure describing full line of new antenna preamplifiers and *Paralog* antennas.*
82. **JFD**—Literature on complete line of VHF, UHF, FM, and FM-stereo antennas. Brochure showing converters, amplifiers, and accessories; also complete 64-65 dealer catalog.*
83. **MOSLEY ELECTRONICS**—Illustrated catalog giving specifications and features on large line of antennas for Citizens band, amateur, and TV applications.*
84. **TRIO**—Brochure on installation and materials for improving UHF translator reception.
85. **WINEGARD**—"Factfinder" describes new channel coupler that mixes, equalizes, and transforms to 75-ohm cut-channel antennas.*
86. **ZENITH**—Informative bulletins on universal loudspeakers and new line of log-periodic vee-type antennas for FM and monochrome or color TV.

AUDIO & HI-FI

87. **ACTION**—Brochure titled "We make sound work for you" shows how sound fits into every type of business.
88. **ADMIRAL**—Parts and accessories catalog listing replacement components; also includes cross reference for phono needles and cartridges.*
89. **ASTATIC**—Catalog on microphones, phono cartridges, and needles; also cross-reference indexes for needles and cartridges.
90. **ATLAS SOUND**—New 1964 catalog No. 564 contains illustrations and specifications on PA speakers, microphone stands for commercial and industrial installations, and other new products.
91. **GIBBS SPECIAL PRODUCTS**—Folders describing principles of sound reverberation and *Stereo-Verb* reverberation units for automobiles.
92. **GROMMES-PRECISION**—Specification sheets on AM, FM, FM-MPX tuner and stereo amplifier; also sheets on public-address line.
93. **NUTONE**—Two full-color booklets illustrating built-in stereo music systems and intercom-radio systems. Includes specifications, installation ideas, and prices.
94. **OKAKTRON**—"The Blueprint to Better Sound," an 8-page catalog of loudspeakers and baffles giving detailed specifications and list prices.*
95. **OXFORD TRANSDUCER**—Product information bulletin describing complete line of loudspeakers for all types of sound applications; including replacements for public address and intercom systems.*
96. **PHILMORE**—Information concerning two-way loudspeaker system with built-in crossover network.
97. **QUAM-NICHOLS**—New catalog listing replacement speakers for background music, public address, and hi-fi applications.*

98. **SONOTONE**—Specification sheet on new stereo and mono crystal replacement cartridges.*
99. **SWITCHCRAFT**—Product Bulletin 141 describes new Q-G audio receptacles.
100. **WILDER**—Literature describing matching stereo hi-fi speaker system.

COMMUNICATIONS

101. **CADRE**—Catalog sheets on complete line of Citizens band radios, including Model C-60 two-channel, 100-mw transceiver.
102. **ELTEC**—Information concerning FM communications monitor-receiver and frequency-standard calibrators.
103. **GENERAL RADIOTELEPHONE**—Brochures describing two-way radio systems for all types of applications.
104. **PEARCE-SIMPSON**—Specification brochures on *Companion II* and *Escort* Citizens band transceivers.
105. **REGENCY**—Information on newly introduced Citizens band transceivers and *Monitoradio*.

COMPONENTS

106. **BUSSMANN**—Bulletin SFUS listing complete line of Buss and Fusetron small-dimension fuses by size and type. Indicates proper fuse holders and gives list prices.*
107. **CENTRALAB**—8-page catalog listing *Fastatch II* exact replacement controls and accessories.
108. **GC ELECTRONICS**—Updated Walsco phono drive chart #FR-236-W.*
109. **JEH**—Transistor interchangeability list; also cross-reference chart for auto-radio transistors.
110. **ONEIDA**—Catalog on line of electronic components and replacement items.
111. **PERMACEL**—Bulletin describing line of plastic tape and plastic parts box.
112. **RCA BATTERIES**—Manual BDC-111 includes battery theory and applications, electrical and mechanical characteristics, and terminal connections on all types in the RCA line.*
113. **TRIAD**—10-page color-TV replacement guide for yokes, flybacks, vertical-output, and power transformers.

SERVICE AIDS

114. **CASTLE**—How to get fast overhaul service on all makes and models of television tuners is described in leaflet. Shipping instructions, labels, and tags are also included.*
115. **PRECISION TUNER**—Literature supplying information on complete, low-cost repair and alignment services for any TV tuner.*
116. **YEATS**—The new "back-saving" appliance dolly Model 7 is featured in a four-page booklet describing feather-weight aluminum construction.*

SPECIAL EQUIPMENT

117. **ATR**—Descriptive literature on selling new, all-transistor *Karadio*, Model 707, having retail price of \$29.95. Other literature on complete line of DC-AC inverters for operating 117-volt PA systems and other electronics gear.*
118. **GREYHOUND**—The complete story of the speed, convenience, and special service provided by the Greyhound Package express method of shipping, with rates and routes.
119. **LECTROTECH**—Bulletins on new color-TV test instrument, meter-protective devices, and substitute for VTVM battery.*
120. **PERMA-POWER**—Catalog sheet on transistorized garage-door opener.

121. **TERADO**—Bulletin on *Galaxy* Model 50-205 transistorized DC-AC power inverter.*
122. **VOLKSWAGEN**—Large, 60-page illustrated booklet, "The Owner's Viewpoint," describes how various VW trucks can be used to save time and money in business enterprises; including complete specifications on line of trucks.

TECHNICAL PUBLICATIONS

123. **CLEVELAND INSTITUTE OF ELECTRONICS**—"Pocket Electronics Data Guides" with handy conversion factors, formulas, tables, and color codes. Additional folder, "Choose Your Career in Electronics," describes home-study electronics training program, including preparation for FCC-license exam.*
124. **RCA INSTITUTES**—64-page book, "Your Career in Electronics," detailing home study courses in TV servicing, communications, automation, drafting, and computer programming; for beginners and experienced technicians.*
125. **HOWARD W. SAMS**—Literature describing popular and informative publications on radio and TV servicing, communications, audio, hi-fi, and industrial electronics; including special new 1964 catalog of technical books on every phase of electronics.*

TEST EQUIPMENT

126. **B & K**—Catalog AP-21R describing uses for and specifications of new Model 1074 Television Analyst, Model 1076 Television Analyst, Model 850 Color Generator, Model 960 Transistor Radio Analyst, new Model 445 CRT Tester-Rejuvenator, new Model 250 Substitution Master, Model 375 *Dynamatic* VTVM, Model 360V-O-Matic VOM, Models 700 and 600 *Dyna-Quit* Tube Testers, and Model 1070 *Dyna-Sweep* Circuit Analyzer.*
127. **EICO**—New 32-page, 1964 catalog of test instruments, hi-fi components, tape recorders, and Citizens band and amateur radio equipment.*
128. **HICKOK**—Complete description and specification information on newly introduced equipment—Model 662 installer's color generator; Model 580 portable tube tester; Model 727 multiplex generator; Model 235A portable field-strength meter.*
129. **JACKSON**—Complete catalog describing all types of electronic test equipment for servicing and other applications.
130. **MERCURY**—Description and specification brochure on Model 1400 in-circuit capacitor tester; also information on line of other test equipment.*
131. **SECO**—12-page instruction manual for Model 980 and 990 color-bar generators; includes schematics, waveforms, and specifications.*
132. **SENCORE**—Question-and-answer bulletin on new Model MX-129 *Multiplex Analyzer* and Model CR-128 *Picture-Tube Tester-Rejuvenator*.*
133. **SIMPSON**—Latest series of VOM's is described in test-equipment bulletin; also information on line of automotive test equipment.
134. **SPRAGUE**—Catalog on TO-6 Tel-ohmic capacitor analyzer.
135. **TRIPLETT**—Sheets giving basic information on complete line of VOM's.*
136. **WATERMAN**—Technical data and photos on pocket-size OCA-11A industrial oscilloscope.

TOOLS

137. **ACME LITE**—Descriptive bulletin on line of *Magniflex* fluorescent lamps.
138. **ADEL**—Literature on "Nibbling Tool" that cuts, notches, and trims round or irregular holes to any size over 7/16"; ideal for radio chassis, templates, or shims.
139. **ENTERPRISE DEVELOPMENT**—Time-saving techniques in brochure from Endeco demonstrate improved desoldering and resoldering techniques for speeding up and simplifying operations on PC boards.*
140. **LUXO LAMP**—Catalog on line of "touch-and-stay-put" lamps.

TUBES & SEMICONDUCTORS

141. **INTERNATIONAL ELECTRONICS**—New listing includes Mullard range of electron tubes for TV, Radio, and Hi-Fi replacements; includes cross-reference guide.
142. **SEMITRONICS**—New updated 16" x 20" wall chart CH10 lists replacements and interchangeability for transistors and diodes.



WHERE THE SILVERAMA® SCREEN BEGINS

TV picture quality depends on precise control of phosphors

Television picture quality depends on the quality of the phosphor screen inside the faceplate. That's why every RCA Silverama replacement picture tube is completely rescreened—in the same painstaking manner and with the same precision—as RCA picture tubes produced for use in original equipment. Before receiving their new Silverama screens, reused glass envelopes are scrubbed completely clean and given a series of chemical baths internally to restore them to the peak of their optical capabilities.

RCA produces and develops its own screen phosphors. These are

formed by reacting solutions of zinc sulfate and zinc and cadmium sulfates with hydrogen-sulfide gas in this complex precipitator, (above). The resulting zinc sulfide and zinc-cadmium sulfide are then activated, fluxed, fired, washed, dried, and screened to form phosphors which emit blue and yellow light, respectively. These are carefully blended to produce phosphors that possess the pleasing "white", high light output, and uniform smoothness, which characterize RCA Silverama picture tube screens.

Make RCA Silverama your first choice in picture tubes.



Drying ovens remove moisture from phosphor



Phosphors are blended for best screen quality



Base materials are fired to form the phosphors

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.



The Most Trusted Name in Electronics

In Electronic Circuits . . .

ALL AROUND PROTECTION

NEW MICROFUSE
 THE PIGTAIL VARIETY (278000) SERIES
 THE PLUG-IN VARIETY (272000) SERIES
 THE SUB-MINIATURE FUSE HOLDER (No. 281001)

New Indicating 3AG Fuse Posts

It GLOWS when the FUSE BLOWS

Labels around the circle include: SOLDER TERMINAL MOUNTING, 4AG FINGER OPERATED POST, TERMINAL CLIP, FUSE CLIP EARLESS, FUSE CLIP, LC FUSE HOLDERS, MOUNTINGS FOR ACOTI/FI/PS, 3AG FUSES, 3AG SLO-BLO, 3AB FUSE U/L, LC FUSES 250V TYPE C, LC FUSES 125V TYPE C, LC SLO-BLO 125V TYPE N, 8AG INSTRUMENT FUSES, 8AG U/L FUSES, AIRCRAFT FUSES, 4AG SLO-BLO, IN LINE FUSE RETAINERS, 3AG POST SCREWDRIVER OPERATED, 3AG POST FINGER OPERATED, 3AG POST MINIATURE, CAN COVER MOUNTING, THROUGH PANEL MOUNTING, and SCREW TERMINAL MOUNTING.

It's **LITTELFUSE** First!
 DES PLAINES, ILLINOIS

Circle 71 on literature card