

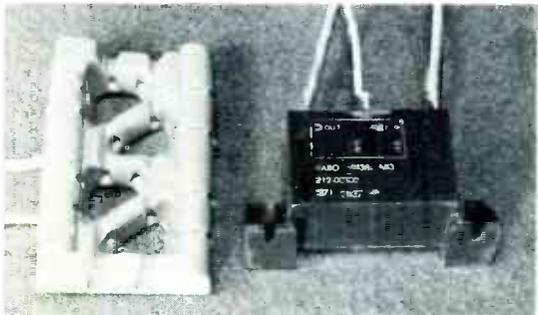
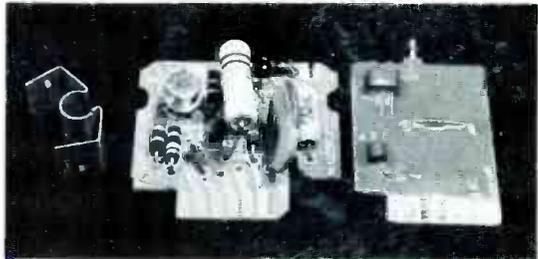


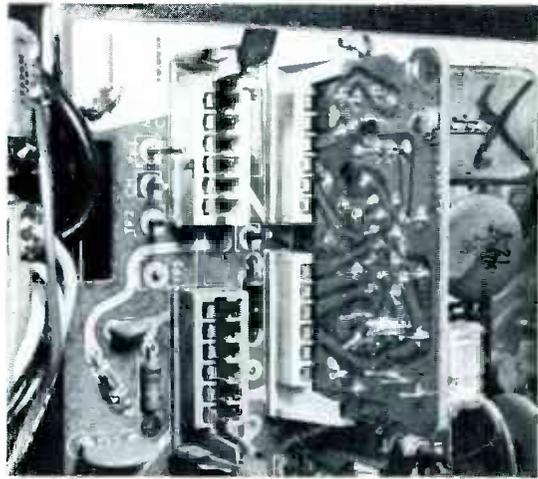

# Electronic Servicing

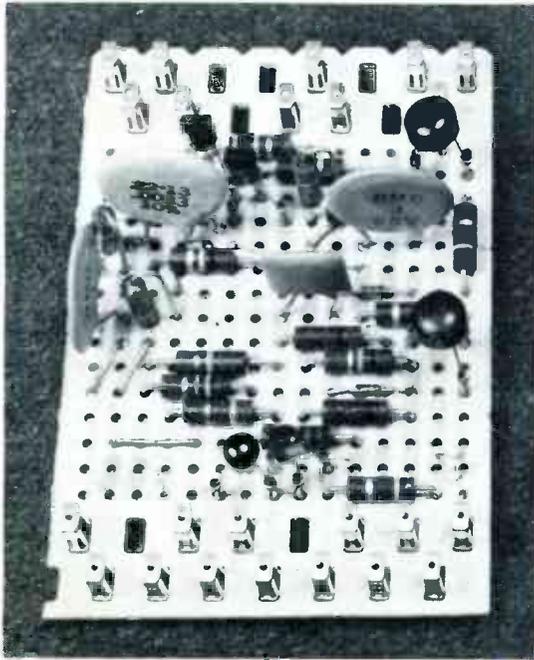

## NEW CIRCUITRY IN '71 COLOR TV

Articles beginning on  
pages 16 and 38

Updated and expanded  
Source Guide to Imports,  
page 50

# Cut your time

## With "QT." The Quick Turnover Parts Inventory System from RCA.

How much time do you spend in the shop searching for parts? And if you don't have them, how long does it take you to get them?

If you're doing more than your share of looking for parts or ordering them on the phone, you're wasting time.

Time that's cutting down your efficiency and preventing you from doing the really important things.

That's where our Quick Turnover Parts Inventory System ("QT" for short) can help.


It's a system that puts 250 of the fastest moving RCA parts for TV sets, radios and phonographs at your fingertips. Parts selected by RCA's computers.

You'll also know when the supply is running low. And should any of the parts be dropped from the "top-mover" list, simply return them through your "QT" distributor.

Talk to your RCA Parts & Accessories Distributor about putting in a "QT" Inventory System.

The sooner you do the faster you'll start saving time.

**RCA** Parts and Accessories

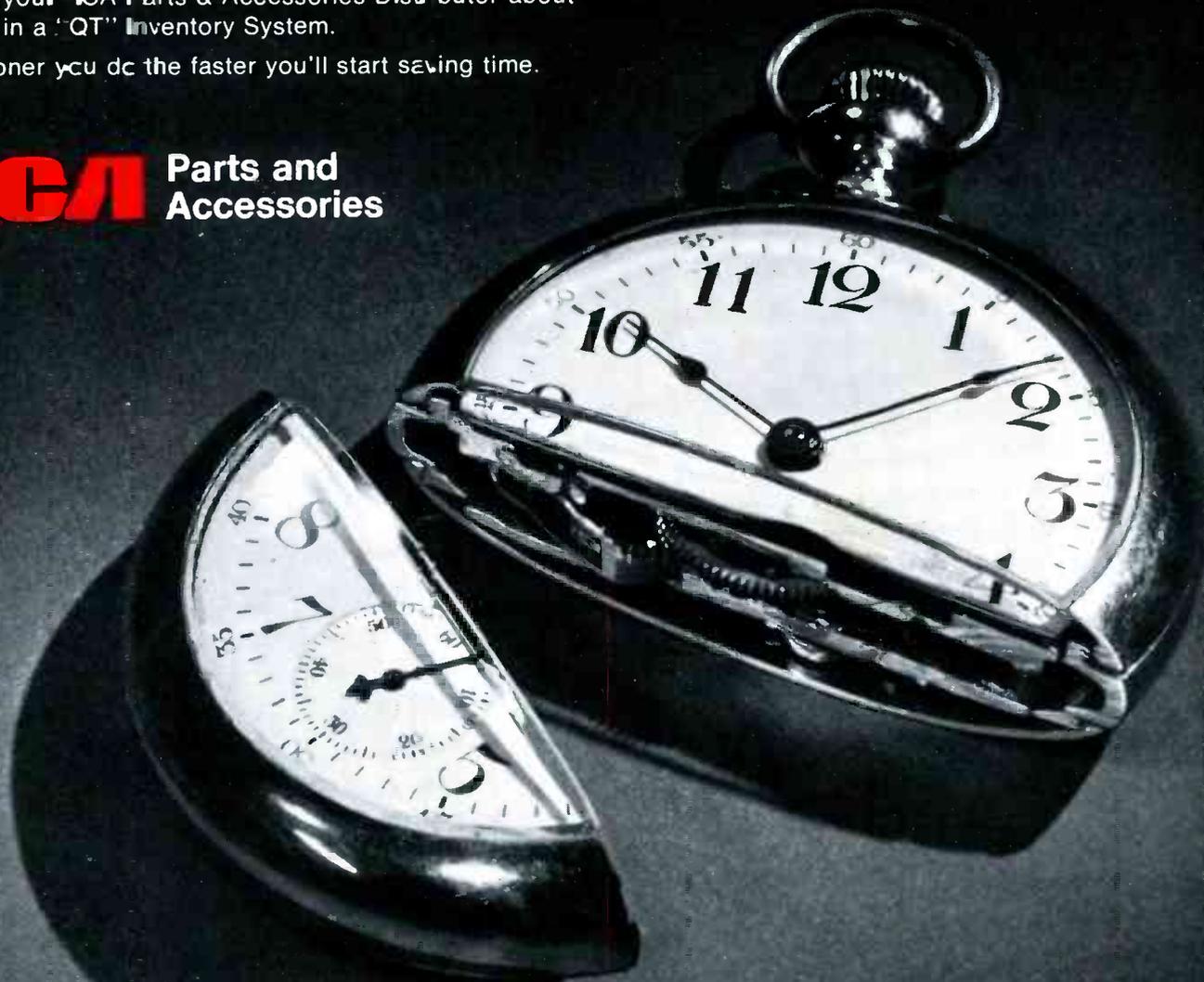

# FREE! YOUR FIRST CAN OF TUN-O-BRITE IS ON US!



We say TUN-O-BRITE is head and shoulders above any other tuner spray you've ever tried. You say you've heard that song before.

It's time for us to put our money where our claims are. Tell you what we're gonna do. Buy a can of TUN-O-BRITE from your favorite distributor — at the regular price.

When you've used the TUN-O-BRITE up, send the empty can to us. We'll send you a new can *OF YOUR FAVORITE TUNER SPRAY FREE!*

There are no strings attached to this offer. If you ask for TUN-O-BRITE, we'll be delighted to send you another can absolutely free. If you ask for a competitive brand, we'll be disappointed, but we'll send it to you anyhow. Either way, you can't lose. You get to try TUN-O-BRITE at our expense because you can swap the empty can for a free can of your favorite tuner spray.

Of course, we're betting that once you try TUN-O-BRITE, you simply won't settle for any other product, no matter how cheap you can buy it. After all, you can tell a professional TV technician by the tools he uses.

**CHEMTRONICS** INC.  
1260 RALPH AVE.  
BKLYN., N.Y. 11236



Circle 3 on literature card

December, 1970/ELECTRONIC SERVICING 1

ONLY ONE  
FREE CAN  
TO A  
TECHNICIAN.

This offer expires  
February 1, 1971

← Circle 1 on literature card

# Electronic Servicing

Formerly PF Reporter

## *in this issue...*

- 16 **Shop Talk—New and Changed Circuitry In '71 Color TV, Part 1.** ES's technical editor explains the operation of both new and modified circuitry you'll encounter in this year's crop of color receivers. **by Carl Babcoke.**

---

- 26 **Dale's Service Bench—1-2-3-4 Servicing.** Dividing circuitry into functional, bite-size elements which can be checked in a definite, logical sequence is the basis of one veteran technician's successful diagnostic technique. **by Allan Dale.**

---

- 32 **Troubleshooting Video IF With Sweep Alignment Gear, Part 1.** The time-saving designs of modern TV alignment equipment—such as Sencore's Model SM152 and B & K's Model 415 sweep/marker generators—make them particularly efficient aids for both alignment and troubleshooting. How you can use these instruments for speedier troubleshooting is the primary subject of this series. **by Larry Allen.**

---

- 38 **The All-Electronic Tuner.** It is probable that "mechanicless" tuners eventually will be used in all TV receivers. To service them, you will have to be familiar with how they function. This article explains the fundamental principle of operation of RCA's new electronically switched TV tuner. **by Bruce Anderson.**

---

- 50 **Source Guide to Imported Consumer Electronic Products.** A cross reference of brand names to importers, distributors or manufacturers. Over 700 brand names of foreign-made sets are listed in this updated and expanded edition of an annual ES feature.

---

- 64 **Simple X-Ray Detection Instruments For TV Service Technicians.** Two proven designs developed by the Radiation Measurement and Calibration Branch of the Bureau of Radiological Health specifically for construction and use by electronic service technicians. Either design reportedly can be built from commonly available, low-cost components, and without specialized radiation measurement instrumentation experience. **by Richard K. Stoms & Edward Kuerze.**

### DEPARTMENTS

Electronic Scanner . . . . .	4	Audio Systems Report . . . . .	48
Readers' Exchange . . . . .	10	Advertisers' Index . . . . .	62
Troubleshooter . . . . .	12	Antenna Systems Report . . . . .	62
Letters to the Editor . . . . .	14	Product Report . . . . .	72
Test Equipment Report . . . . .	44	Catalog and Literature . . . . .	75

Second class postage paid at Kansas City, Mo. and additional mailing offices. Published monthly by INTERTEC PUBLISHING CORP., 1014 Wyandotte St., Kansas City, Mo. 64105. Vol. 20, No. 12. Subscription rates \$5 per year in U.S., its possessions and Canada; other countries \$6 per year.

Copyright, 1970, Howard W. Sams & Co., Inc. All rights Reserved. Material may not be reproduced or photocopied in any form without written permission of publisher.

#### EDITORIAL

GEO. H. SEFEROWICH, Director  
J. W. PHIPPS, Managing Editor  
CARL BABCOKE, Technical Editor  
BARBARA L. SMITHSON, Editorial Assistant  
DUDLEY ROSE, Art Director

#### CONTRIBUTING AUTHORS

Bruce Anderson  
Joseph J. Carr  
Allan Dale  
Robert G. Middleton

#### TECHNICAL CONSULTANT

JOE A. GROVES

#### EDITORIAL ADVISORY BOARD

LES NELSON, Chairman  
Howard W. Sams & Co., Indianapolis

#### CIRCULATION

EVELYN ROGERS, Manager

#### ADVERTISING SALES

Kansas City, Missouri 64105  
Tele: 913/888-4664  
E. P. LANGAN, Director  
R. JACK HANCOCK, Manager  
JAKE STODCKWELL  
S. F. WILSON, Production

#### REGIONAL ADVERTISING SALES OFFICES

Indianapolis, Indiana 46200  
ROY HENRY  
2469 E. 98th St.  
Tele: 317/846-7026

New York, New York 10016  
CHARLES C. HORNER  
3 W. 57th St.  
Tele: 212/688-6350

Los Angeles, California 90005  
JOHN D. GILLIES  
3600 Wilshire Blvd., Suite 1510  
Tele: 213/383-1552

London W. C. 2, England  
JOHN ASHCRAFT & CO.  
12 Bear Street  
Leicester Square  
Tele: 930-0525

Amsterdam C. Holland  
JOHN ASHCRAFT & CO.  
W.J.M. Sanders, Mgr.  
for Benelux & Germany  
Herengracht 365  
Tele: 020-240908

Tokyo, Japan  
INTERNATIONAL MEDIA  
REPRESENTATIVES LTD.  
1, Shiba-Kochohicho, Minatoku  
Tele: 502-0656



ELECTRONIC SERVICING (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., 1014 Wyandotte Street, Kansas City, Missouri 64105.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00, 3 years—\$10.00, in the U. S. A., its possessions and Canada.

All other foreign countries: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00. Single copy 75¢; back copies \$1.




Robert E. Hortal, Publisher

Intertec Publishing Corp.  
Subsidiary of Howard W. Sams & Co., Inc.

Do you want the  
same things  
Dick DeVroeg wants in capacitors?

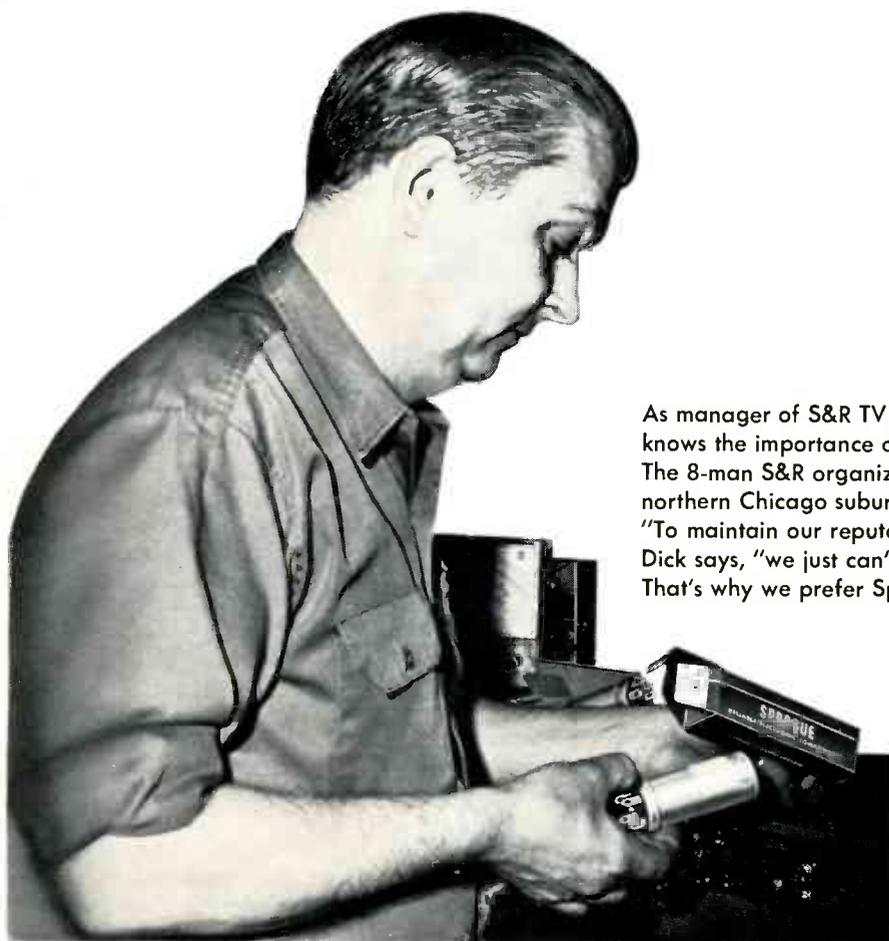Then you'll ask for  
Sprague Twist-Lok<sup>®</sup> Capacitors when  
you need twist-prong electrolytics.



As manager of S&R TV in Lake Forest, Illinois, Dick DeVroeg knows the importance of using quality components. The 8-man S&R organization has built a name for itself in northern Chicago suburbs over the past 18 years. "To maintain our reputation in servicing everything in electronics," Dick says, "we just can't compromise on dependability. That's why we prefer Sprague Twist-Lok Capacitors."

Ask your Sprague distributor for a copy of Sprague's Electrolytic Capacitor Replacement Manual K-109 or write to:  
Sprague Products Company, Marshall St., North Adams, Mass. 01247.

**P.S.** You can increase your business 7½% by participating in EIA's "What else needs fixing?" program. Ask your distributor or write to us for details.

*Circle 4 on literature card*



### Business Consultation Offered By NATESA

A direct consultation service "on all phases of home electronic service business problems" is being offered members by the National Alliance of Television and Electronic Service Associations (NATESA).

There is no charge for the service except for those problems that require extensive and costly research. In such cases, the member will be advised of the cost before research of the problem begins.

Under this plan, the member is asked to submit his question in a typed, double-spaced letter, providing as many related details as possible. The member also must include his NATESA license number and a self-addressed, stamped #10 envelope.

Each question reportedly will be studied and, if necessary, researched and answered as soon as possible, depending on the complexity of the problem.

The service is not meant to replace members' own legal or accounting agencies, states Frank Moch, Executive Director of NATESA.

### EIC Formed to Unite Electronics Industry and Solve Mutual and Related Problems

The Electronics Industries Council (EIC) was formed in Chicago on Sept. 29 to serve in a liaison capacity between all electronics trade associations. The group formulated plans for industry-wide cooperation encompassing all segments of production, service, merchandising, broadcasting, research and technical applications.



Associations represented at the first formal meeting of the council were: The Electronic Industries Association, Distributor Products division; National Electronic Associations; National Association of Broadcasters; National Alliance of Television and Electronic Service Associations; National Electronic Distributors Association; Electronic Representatives Association and the International Society of Certified Electronic Technicians.

Invitations to participate in the EIC are being extended to nine other trade groups: the National Appliance and Radio Dealers association; the Association of Electronic Manufacturers; the Western Electronic Manufacturers Association; the Society of Broadcast Engineers; the Institute of High Fidelity; the National Cable Television Association; the American Loudspeaker Manufacturers Association; and the National Association of Music Merchants. Other interested trade groups also are invited to send representatives to the Dallas meeting in February and to consider participating on a permanent basis.

The Chairmanship of the group will be rotated each succeeding session. Gene Hill, Kaiser Broadcasting Co.,

(Continued on page 6)

## COLOR TV CONTROLS

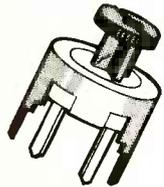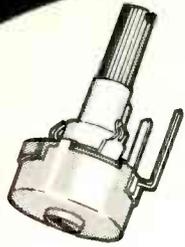

- CONVERGENCE
- Audio • Color
- A.G.C. Delay • Focus
- Brightness • Sensitivity
- Horizontal Frequency
- Horizontal Centering
- Vertical Linearity
- Vertical Centering

105 DIFFERENT EXACT REPLACEMENTS

RCA • SILVERTONE  
ADMIRAL • ZENITH  
G.E. and others

ASK FOR FREE CROSS REFERENCE NO.X67

MANUFACTURED FOR THE OEM MARKET. NOW AVAILABLE FOR REPLACEMENT PARTS...

MANUFACTURED BY  
**WORKMAN** Electronic PRODUCTS INC.  
SARASOTA, FLORIDA

Circle 5 on literature card

## FREE CATALOG



## CRT COLOR CHAMPION

### TV PICTURE TUBE REBUILDING EQUIPMENT

C.R.T. Equipment Company, Inc.  
2740 Old Lebanon Road  
Nashville, Tennessee 37214

Telephone (615) 883-0215

### Mail Coupon Today

(Please Print)

Name \_\_\_\_\_

Firm Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Clip Me Out

Circle 6 on literature card



# \$975

## TUNER SERVICE CORPORATION

**PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS AT ONE PRICE.**

### TUNER REPAIR

VHF Or UHF Any Type \$9.75.  
UHF/VHF Combo \$15.00.

In this price all parts are included. Tubes, transistors, diodes, and nuvistors are charged at cost.

Fast efficient service at our 4 conveniently located service centers.

1 year guarantee backed up by the largest tuner manufacturer in the U.S.—SARKES TARZIAN INC.

All tuners are cleaned inside and out, repaired, realigned and air tested.

### TUNER REPLACEMENT

Replacement Tuner \$9.75.

This price buys you a complete new tuner built specifically by SARKES TARZIAN INC. for this purpose.

The price is the same for every type of universal replacement tuner.

#### Specify heater type

Parallel 6.3V  
Series 450 mA  
Series 600 mA

All shafts have the same length of 12".

#### Characteristics are:

Memory Fine Tuning  
UHF Plug In  
Universal Mounting  
Hi-Gain Lo-Noise

If you prefer we'll customize this tuner for you. The price will be \$18.25. Send in original tuner for comparison purposes to our office in INDIANAPOLIS, INDIANA.



## TUNER SERVICE CORPORATION

**FACTORY-SUPERVISED TUNER SERVICE**

**MIDWEST** . . . . . 817 N. PENNSYLVANIA ST., Indianapolis, Indiana . . . . . TEL: 317-632-3493  
(Home Office)  
**EAST** . . . . . 547-49 TONNELE AVE., Jersey City, New Jersey . . . . . TEL: 201-792-3730  
**SOUTH-EAST** . . . . . 938 GORDON ST., S. W., Atlanta, Georgia . . . . . TEL: 404-758-2232  
**WEST** . . . . . SARKES TARZIAN, Inc. TUNER SERVICE DIVISION  
10654 MAGNOLIA BLVD., North Hollywood, California . . . TEL: 213-769-2720  
*Circle 7 on literature card*

who presided at the initial meeting, will continue as Chairman at the next session, to be held in Dallas, Texas, on February 10, 1971. The Chairmen for the following two sessions will be Frank J. Moch and M. L. Finneburgh, Sr., respectively.

Groundwork for activation of the Council was laid in St. Louis in July, and Hill, the acting Chairman, followed through by setting up the organizing session, held at suburban O'Hare Inn in an all-day meeting.

Among projects and actions recommended by the Council were: Exchange of statistical, research and survey data among the trade groups; a parts availability survey; a census of electronic service technicians to determine future needs and an analysis of the industries' manpower.

The group also voted to recommend to the trade associations a study of the present Electronic Hall of Fame with a view to its expansion as an all-industry honor.

A permanent administrative staff was named, to consist of Dick Glass (NEA), Secretary; Bob Flanders (NAB), Records Coordinator and S. I. Neiman (Electronics Information Bureaus), Information Coordinator. Bill Woodbury, Sprague Products Co., will coordinate the parts availability survey.

### **GE Introduces First Combo Horizontal Output/Damper Tube for Color TV**

The Y-2014 Compactron tube—reportedly the first combination of horizontal output and damper tube functions in one envelope rated for color TV—has been announced by General Electric's Tube Department.

The new Compactron combines the conventional 6KD6 horizontal output tube (pentode) and the conventional 6CJ3 damper (diode) tube in one T-14 enve-



lope, offering ratings compatible with requirements for horizontal service in 18-inch, 90-degree color chassis.

### **GE Halts B-W Picture Tube Production**

General Electric has announced discontinuation of black-and-white TV picture tube production, according to a recent report in **Merchandising Week**.

The reason given for the halt of b-w CRT production is increased importation, which reportedly is expected to account eventually for as much as 50 percent of the domestic market.

### **NFIB Survey Reveals Trends of Interest Rates Paid by Small Independent Businesses**

Whether or not the cut in the prime interest rate charged by banks will benefit smaller business firms remains to be seen.

Data from the September continuous field survey of the National Federation of Independent Business (NFIB) showed the average interest rate paid by small business on bank loans remained steady at 8.6 percent for the second consecutive month.

However, because the cut in the prime rate did not occur until late in September, any decline in the interest rate to the smaller borrowers would not be reflected in the September data.

But casting uncertainty over whether or not the drop in rate charged to blue chip borrowers will be passed along further down the line is the fact that the cut in the prime rate from 8½ to 8 percent earlier in the year failed to be reflected in subsequent Federation surveys.

There is evidence that cutting the prime rate has slowed down the rate of increase in interest rates to independent firms. The average interest rate being paid banks reported by independents at the first of the year was 8.4 percent. This jumped to 8.5 percent at the end of the second quarter of the year, and now stands as 8.6 percent. Last year the increase in the national bank interest rate to small business was at the rate of 1/10th of one percent per month.

While the highest small business rate remains in the Pacific Coast states, followed by the Mountain states, the increase so far this year in those areas has not been as high as in some other regions. In the Pacific states the current bank rate reported by smaller firms is 9.6 percent, up from 9.2 percent in January. In the Mountain states it is 8.9 percent, up from 8.8 percent the first of the year.

The movement upward in the average bank interest rate so far this year has been more pronounced along the Atlantic Seaboard, with the exception of New England. In the Mid-Atlantic states the reported average rate has gone from 7.9 percent in January to 8.4 percent in September, and in the South Atlantic also from 7.9 percent to 8.4 percent, or a full half percent. In New England the increase reported over this period was only from 8.7 percent to 8.9 percent.

Among independent businessmen borrowing from

*(Continued on page 8)*

# BUSS

THE COMPLETE LINE OF SIGNAL-INDICATING,  
ALARM-ACTIVATING FUSES AND FUSEHOLDERS

FOR USE ON COMPUTERS, MICROWAVE UNITS, COMMUNICATION EQUIPMENT, ALL ELECTRONIC CIRCUITRY




BUSS Grassopper Fuse, Visual-Indicating, Alarm-Activating.



BUSS MIN-13/32 x 1 1/2 in. Visual-Indicating.



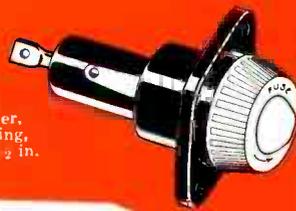FMA FUSITRON Fuse 13/32 x 1 1/2 in. slow-blowing, Visual-Indicating, Alarm-Activating. (Also useful for protection of small motors, solenoids, transformers in machine tool industry.)



HPC-C panel mounted holder, visual-indicating, for 13/32 x 1 1/2 in. fuses.




BUSS ACH Aircraft Limiter, Visual-Indicating.




BUSS Series 70, Visual-Indicating, Alarm-Activating. (Used in telephone and similar applications.) Ask for Bulletin 765-C.



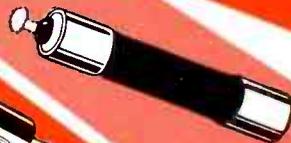
HLD panel mounted holder, visual-indicating, for 1/4 x 1 1/4 in. BUSS GBA fuses (or GLD fuses) 3/4 to 5 amp.



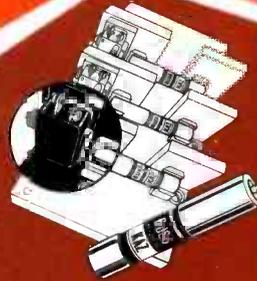BUSS GBA-1/4 x 1 1/4 in. Visual-Indicating.



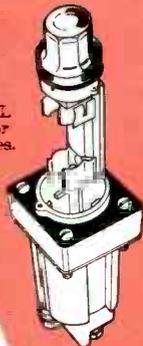
BUSS KAZ Actuator 13/32 x 2 in. Signal-Indicating, Alarm-Activating Device. Use to call attention to the opening of a fuse of 50 amp or larger. Can be mounted "piggy-back" on large fuse or in special block with micro-switch. Ask for Bulletin KAPS.



HGC panel mounted holder lamp indicating Military type FHL 12U Single pole for 13/32 x 1 1/2 in. fuses.



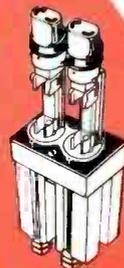Signal fuse block No. 3839 for 13/32 x 1 1/2 in. indicating fuse.




HGA-C panel mounted holder lamp indicating Military type FHL10U Two pole for 1/4 x 1 1/4 in. fuses.



FEB-C panel mounted holder lamp indicating Military type FHL11U Single pole for 1/4 x 1 1/4 in. fuses.



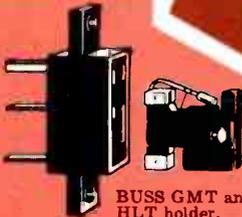Signal fuse block No. 4178 for 1/4 x 1 1/4 in. indicating fuse.



BUSS GMT and HLT holder, Visual-Indicating, Alarm-Activating.



HFA panel mounted holder, lamp indicating, signal activating, for 1/4 x 1 1/4 in. BUSS GLD fuse. 3/4 to 5 amp.



HKL panel mounted holder, lamp indicating, for 1/4 x 1 1/4 in. fuses.

WRITE FOR BUSS BULLETIN SFB

SUPPLIED THE ECONOMICAL WAY  
THRU DISTRIBUTORS  
**BUSS QUALITY**  
FUSES

BUSSMANN MFG. DIVISION,  
McGraw-Edison Co., St. Louis, Mo. 63107

Circle 8 on literature card

finance companies, the average interest rate reported had remained fairly constant over the year so far. In January it was 12.4 percent, compared to 12.7 percent in September. The lowest rate from this source was the 10.3 percent reported in February and the highest 13.6 percent reported in July.

### Sylvania To Phase Out Most of Semiconductor Production

Sylvania Electric Products, Inc. announced today it will phase out most of its semiconductor manufacturing operations over the next three months.

This action will have no effect on components for Sylvania Entertainment Products; the Semiconductor Division has directed its product lines almost totally to defense needs and the computer industry.

Garlan Morse, Sylvania President, said "the decision was made to terminate much of our semiconductor manufacturing because there is no indication that, within the foreseeable future, stability will supplant the disorderly conditions that have characterized this branch of the electronics industry for many years."

The semiconductor operations to be phased out represent slightly more than two per cent of Sylvania's total sales of a wide range of electronic and lighting products. The semiconductor products to be discontinued are integrated circuits, diodes, and rectifiers. Not included in the phasing out is the microwave diode department, which produces highly specialized semiconductor devices.

No other Sylvania operation will be affected by the semi-conductor phase out, and advanced semiconductor research will be continued at General Telephone & Electronic's Laboratories Incorporated, in Waltham, Mass.

Mr. Morse said the decline in defense spending and extreme price competition in sales to the computer industry have had a particularly severe impact on semiconductor profitability.

### Merger to Create Giant CATV Setup Approved by FCC

The Federal Communications Commission (FCC) has put its stamp of approval on the creation of a cable antenna television (CATV) system having outlets in 28 states, according to a report in **Home Furnishings Daily**.

The merger of H & B American Corporation, formerly the nation's largest CATV company, and TelePrompter Corporation, the fourth largest, will establish the giant CATV system. The merged firms reportedly will operate under the TelePrompter name. (The largest stockholder in TelePrompter is Hughes Aircraft Corporation.)

TelePrompter reportedly told the Commission that the merger will enable it to originate high-quality programming. The FCC, earlier this year, ruled that CATV systems must originate programming, to keep their licenses.

### North American Philips Offers Tape Recorder Servicing Seminars

A series of two-day seminars, conducted for its nationwide network of more than 300 authorized independent repair stations, has been inaugurated by the Home Entertainment Products Division of North American Philips Corporation.

The work-study classes—limited to 25 participants each—cover all aspects of service, repair and adjustment for the growing line of Norelco tape recorder products.

The first session was held the latter part of October at Norelco House, the firm's service facility in Skokie, Ill., according to Rudolph G. Kroupa, the division's general manager for service. It is being followed by seminars in factory service centers in New York, and Los Angeles, making a total of 18 meetings.

### Audio Technician Seminars


Professional Audio Technician Seminars (PAT) are scheduled for successive sessions in all major cities of the U.S., according to Fisher Radio Corp., sponsors of the seminars.

All service technicians within each market area are invited to attend.

Details and specific dates and locations can be obtained by writing:

PAT Service Center  
P. O. Box 1  
Long Island City, N.Y. 11101

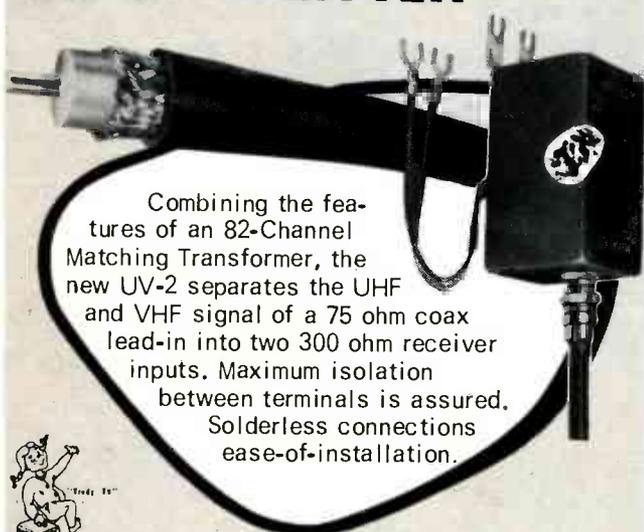**NEW COAX UHF & VHF**  
**MATCHING TRANSFORMER**  
**INPUT-SPLITTER**



Combining the features of an 82-Channel Matching Transformer, the new UV-2 separates the UHF and VHF signal of a 75 ohm coax lead-in into two 300 ohm receiver inputs. Maximum isolation between terminals is assured. Solderless connections ease-of-installation.

Write Dept. 168 for FREE detailed brochure

**Mosley Electronics, Inc.** 4610 N. Lindbergh Blvd.,  
Bridgeton Missouri 63042

Circle 10 on literature card

# CUT TV ALIGNMENT TIME

# IN HALF!



with the all new  
SENCORE SM158

## SPEED ALIGNER

and at \$120.00 less  
than competition!  
only \$275.00

*Here are 7 Reasons why we call the SM158 the Speed Aligner*

**AUTOMATIC ALL CRYSTAL CONTROLLED MARKERS:** You will never spend any more time looking up marker frequencies or interpreting them when you own an SM158; they are automatic. For example, want the chroma carrier on any RF curve, IF curve, or chroma curve, simply push the chroma carrier marker button. Want the sound, video, adjacent carrier markers or any other marker on any curve, just push the button as directed on the panel. The SM158 is fast and saves you time . . . that's why we call it the speed aligner.

**UNLIMITED MARKER AMPLITUDE:** The marker height control is like a powerhouse; crank it up as far as you want, even to the point where the markers are larger than the scope screen, without upsetting the response curve. Each marker is crystal controlled on fundamental frequencies and post-injected so that you may place all markers on the curve at unbelievable heights without affecting the curve in the least. That's why we call the SM158 the speed aligner.

**EASY TO CONNECT:** Just four connecting cables clearly marked TO TV and TO SCOPE. It takes just seconds to connect . . . that's why we call the SM158 the speed aligner.






**TWO EXTRA VHF CHANNELS:** Competition has only two VHF channels; the SM158 has an extra high channel and an extra low frequency channel to prevent any co-channel interference. The SM158 is interference-free . . . that's why we call it the speed aligner.

**PLENTY OF SWEEP WIDTH:** A full 15 megahertz sweep signal, constant on all IF, chroma and RF curves, provides adequate sweep width to cover new solid state IF amplifiers. Competition covers only 12 megahertz. The SM158 gives you the full picture the first time . . . that's why we call it the speed aligner.

**GENERATES A ZERO REFERENCE BASE LINE:** You know where zero is with the SM158. All alignment instructions show a base line, yet some competitors do not generate a base line. You can follow TV manufacturers' instructions to the "T", easier and faster with the SM158 . . . that's why we call it the speed aligner.

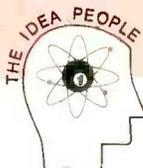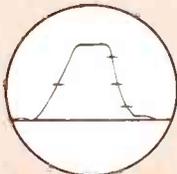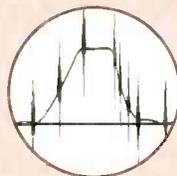**SWITCHABLE HORIZONTAL OR VERTICAL MARKERS:** want to tilt markers 90 degrees so you can view markers better in traps or for leveling? Merely pull the MARKER HEIGHT control out and markers appear horizontally — a real plus feature.



# SENCORE

3200 Sencore Drive  
Sioux Falls, South Dakota 57107

Circle 11 on literature card

Electronic technicians and owners or managers of electronic service shops who need assistance obtaining a part, service literature or any other item related to the servicing of electronic equipment, or who have for sale such an item, are invited to use this column to inform other readers of their need or offer. Requests or offers submitted for publication in this column should be sent to: Readers' Exchange, ELECTRONIC SERVICING, 1014 Wyandotte St., Kansas City, Mo. 64105. Include a brief but complete description of the item(s) you need or are offering for sale, your complete mailing address and how much you are willing to pay or want for the item(s). Individuals responding to a request or sale offer in this column should write **direct** to the requestee or seller.

### Test Equipment for Sale

I have a 5-inch, wide-band oscilloscope, Model 555, manufactured by General Electronic Equipment Co., Easton Pennsylvania. It is in good condition with operating instructions and schematics. I would like \$50.00 for it.

James C. Williams  
519 South 7th St.  
Wilmington, N.C. 28401

I have the following test equipment for sale at a very reasonable price (one owner—all originally purchased brand-new by myself):

RCA Rider Chanalyst Model 162-C;  
Hickok Dynamic Mutual Conductance Tube Tester combined with VOM, Model 534-A;  
EICO grid dip meter, Model 710.

B. J. Brown  
Box 548  
Trion, Georgia 30753

I have the following TV test equipment for sale:

RCA Oscilloscope Type WO-91B;  
Jackson-Sweep & Marker Generator Model TVG-2;  
Sencore-DeLuxe Color-Bar Generator Model CG-141.

Low, bargain prices. All test leads, probes and instruction manuals are available. If anyone is interested, please write:

W. D. Shevtchuk  
One Lois Avenue  
Clifton, New Jersey 07014

I want to sell all of my test equipment, still in very fine condition, in one package for the best offer (express collect).

I have the following items:

- 1) Heath Laboratory 5" Oscilloscope Model 10-12, plus two probes
- 2) Heath Vacuum Tube Voltmeter, Model 1M-

- 11, plus two probes
- 3) Superior Genometer signal generator
- 4) Superior Cathode Ray Tube Tester and Rejuvenator
- 5) Superior Rapid Tube Tester
- 6) Radio Shack Tube Tester
- 7) One tube caddy complete with 218 Radio and TV tubes, all new.

I also have for sale all issues of *Electronic Technician/Dealer and Electronic Servicing/Formerly PF Reporter* which date from 1961 to the present.

Charles C. Ramirez  
306 West 15th St.  
San Angelo, Texas

I have written many articles in different electronic magazines in the past years about test and hobby type equipment, and now I have a closet full of models, built especially for these articles all brand-new but bearing some signs of the extensive shipping. I would like to sell them for the price of the material. I will give the copy of the manuscript with each one, in case the article can not be located.

- 1) "Triggered sweep for any scope" model and Heath 0-10 Scope
- 2) Transistor tester
- 3) Power supply, variable 0-50V
- 4) FET DC voltmeter
- 5) Studio microphone, Dynamic, Astatic 77-A
- 6) Horn and Hailer for Jeep/Boat 12 V, 5W
- 7) Professional Sun Gun with SCR dimmer, 1000W
- 8) Flashmeter
- 9) Stereo amplifier, solid state with preamp, 35W/ch.

The manuscript contains all schematics so later repairs will not cause any problems.

Imre Gorgenyi  
7807 E. Diamond St.  
Scottsdale, Arizona 85257

### Info About TV Technician Employment Opportunities Needed

I am training to be a TV technician and will complete my training in about one year. I would like any information that readers would care to give concerning which areas of the country opportunities for trained technicians are most lucrative.

Leonard P. Root, Jr.  
15473 Patricia Dale Drive  
Baton Rouge, Louisiana 70815

### Help Needed

Can anyone help me obtain circuit information on a Superior Instrument Co. Genometer model TV50? The one I have is very weak.

L. H. Gray  
212 Thoroughman  
Ferguson, Missouri  
63135

I need some help in finding some 12FR8 tubes, which seem to be out of production, with no sub-

(Continued on page 12)

# Sylvania's declaration of independence.

We're all for independence.

In fact, some of our very best friends are independent. Independent distributors and service technicians. And they've done a lot for us.

Here's how.

As a manufacturer, we figure the best way for us to spend our time and resources is in developing new and better products. Which means we leave the selling and servicing of those products to somebody else. (Except, of course, we service only our own television sets and even that is only in selected areas.) But it can't be just anybody. It's got to be somebody who'll really work at it.

A long time ago we found out that nobody, but nobody, works harder than somebody who's independent.

An independent doesn't have any Big Daddy to fall back on if things get a little rough. To make it, he's got to produce, whether it's sales or service.

That's just what our independent distributors and service technicians have done. Produced. And made it.

In making it for themselves, they've made it for us. Which is one selfish reason we're so proud of our partnership with our independents.

It's also a good reason for not changing that relationship, for not disturbing a good thing. We don't compete with our independents. We'll continue to support them. Anything else would be self-defeating.

You might say that at Sylvania, we're perfectly happy to be dependent on our independents.

Electronic Components  
100 First Avenue  
Waltham, Mass. 02154

**SYLVANIA**  
GENERAL TELEPHONE & ELECTRONICS

*Circle 12 on literature card*

stitute listed. If any of your readers can help me, I would like to know quantity and price.

John L. Wiersma  
1819 Chamberlain SE  
Grand Rapids, Michigan  
49506

I need information on a Crosley regenerative receiver Model 5-50. It uses Armstrong patents dated October 6, 1914, and has five GW 201A tubes.

I also need an FM 1000 tube or a substitute tube or a solid-state device. It is a pentagrid type used as an FM detector in a Philco Model 48-482 (PHOTOFACT Folder 30-472-24).

Durward Dostie  
54 Academy St.  
Amsterdam, New York

I would like to obtain a schematic for a Lowery Organ Model .07, built in the 1930's by a Chicago manufacturer.

I would appreciate any help or assistance anyone could give me.

J. Corcoran  
515 Skylark Dr.  
Rockford, Illinois

I have been unable to locate a tube for a Philips TV set that was made in Canada. The tube is a 13CM5. I have tried all over the San Francisco and Oakland Bay area with no success. The tube is a Rogers brand, made in Canada.

Can someone please tell me where I can purchase this tube or where I might obtain the address of Rogers in Canada.

Monson TV  
438 43rd St.  
Richmond, California

#### Photofacts for Sale

I am working for a TV dealer now, and do not use my own Sams Photofacts.

I have folders No. 158 to No. 1037 inclusive with file cabinets.

I would like to sell them.

Tony Braidic  
5831 Marra Drive  
Bedford Heights, Ohio 44146

#### Radios for Sale

I have for sale two Majestic console radios, Model 70, manufactured by Grigsby-Grunow of Chicago.

Robert S. Rash  
Custom TV  
2962 Brockton Ave.  
Riverside, California

**If its about servicing consumer  
electronic products, you'll find it in  
ELECTRONIC SERVICING**

# troubleshooter


## Yoke Resistor Smokes; High Voltage Will Not Vary

The 4.7K-ohm resistor inside the yoke of a GE Model M907 color TV runs so hot it smokes. R10, the pincushion control, also overheats. In addition, the high voltage doesn't change when the high-voltage control is adjusted; it remains at 26KV.

I have replaced all the horizontal tubes, checked all capacitors, and replaced the boost and focus rectifiers. The pincushion transformer tests normal on an ohmmeter.

My guess is that the flyback is bad. I hope you can prove me wrong.

Willie Buendia  
Planada, California

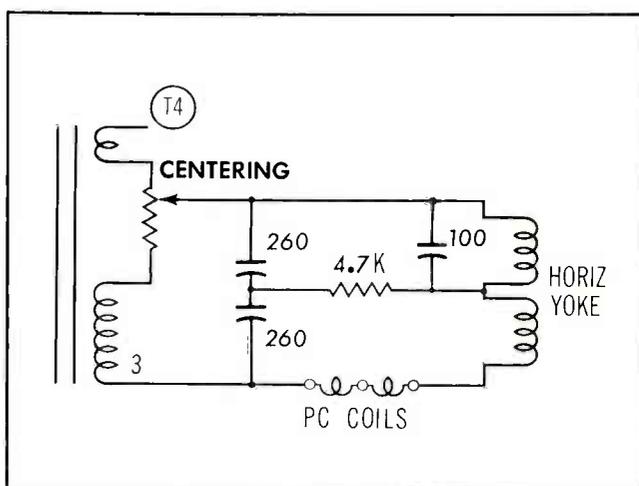

During normal operation, the two 260-pf capacitors (see diagram) and the two horizontal yoke windings form a balanced bridge. No voltage appears across the 4.7K-ohm resistor, except for a slight unbalance, and the resistor operates with very little heat.

Any unbalance of the 260-pf capacitors or the yoke windings will cause the resistor to overheat and burn up. Excessive leakage in the 100-pf, anti-ringing capacitor also will cause the resistor to burn.

An open in one of the yoke windings, shorted turns in one of the yoke windings or leakage in the 100-pf capacitor will cause a trapezoidal picture.

An open in either one of the 260-pf capacitors will cause the 4.7K-ohm resistor to burn up and the yoke current to increase.

Check for the remote possibility of a defect in the pincushion circuit by simply shorting across the PC transformer winding that is in series with the cold end of the yoke. If there are no defects in it, nothing should change except the pincushion correction. If the overheating of the 4.7K-ohm resistor ceases, a defect in the pincushion circuit should be suspected. After the defective part is located and replaced, the high voltage should be readjusted. ▲

# NOW you can measure resistors accurately

# IN CIRCUIT!

## in solid state devices



**FE20 HI-LO**  
with hi-voltage probe and large  
six-inch meter **\$129.50**




**FE21 HI-LO**  
with 4½-inch  
meter **\$99.50**

## WITH THE NEW HI-LO FIELD EFFECT MULTIMETERS

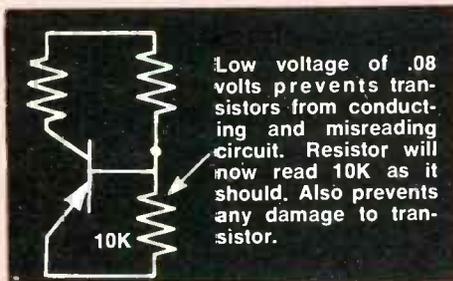
**USES ONLY .08 VOLTS TO POWER OHMMETER TO PREVENT TRANSISTORS FROM CONDUCTING AND UPSETTING READINGS**

Look at these extra features to see why the Hi-Lo meter belongs on your want list:

- Unbelievable specifications of 15 megohm input impedance on DC and 12 megohms on AC
- Laboratory accuracy of 1.5 percent on DC and 3 percent on AC
- 9 DC voltage ranges from as low as .1 volts full scale to 1000 volts
- 3 hi-voltage ranges of 3 KV, 10 KV and 30 KV
- 9 DC zero center ranges from .05 volts to 500 volts . . . a must for delicate transistor bias measurements
- 7 resistance ranges from 1000 ohms full scale to 1000 megohms
- 9 DC current ranges from 100 microamps to 1 amp
- Automatic built-in battery test . . . never a worry about rundown batteries, just push the switches under the meter and read.
- Standard .6 amp fuse to protect the ohms and milliamps scales if voltage or overload is accidentally applied. No more need to return the meter to factory for repair . . . just replace the fuse.
- Special probe with 100K isolation resistor in probe to prevent AC pickup or to prevent loading oscillator circuits. Leave in normal position for most tests.



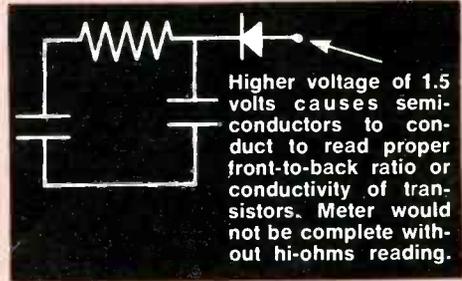**Here is why you should have both Hi and Lo battery voltages for correct in-circuit resistance measurements in solid state circuits:**



**SENCORE** INC. 3200 Sencore Drive • Sioux Falls, South Dakota 57107

Circle 13 on literature card

## Changes Stand on Technician Licensing

I wrote a letter to *ELECTRONIC SERVICING* some time ago favoring the licensing of television technicians. Now, I believe licensing is a mistake.

I have looked around quite a bit and found that those who have a license actually are more free to cheat the public than unlicensed technicians because most customers are naive enough to believe that a license makes him the most honest man around. Certainly licensing should encourage a technician to be honest, but there are few individuals who will not try to get a fast buck if they can. With a license the technician is free to get it. The license does not make the best man, either; it only indicates that he should be the best man.

Licensing to some extent does restrict free enterprise—the freedom of servicers to deal with each other on a competitive basis to keep prices within reach of all consumers. The licensed man usually is the highest-priced man around, and no one can force his prices down.

My business gets so slow in the summer that I have to close up my shop and seek other sources of income. Everyone is either on vacation, working in the field or lounging around lakes. Consequently, I am a part-timer. But don't knock it. A part-timer is not necessarily a "sorry" technician . . .

I am considering shutting down altogether, except in my spare time, and taking a supervisory position with a company.

Billie W. Fowler  
Memphis, Texas

## Views on RCA's "Service America"

In reviewing the recent article on RCA's entrance into the all-brand servicing with "Service America" I have suddenly realized that the "Independents" may not be long for this world.

Qualified technicians are few in quantity and quality and greater effort should be put forward to recruit and train new technicians for the ever increasing service market. Is "Service America" truly the answer to the "Independents" quest for relief? What would happen if other large companies such as Zenith, Magnavox, Sylvania, Motorola, Westinghouse, etc. were to jump on the bandwagon with similar service centers?

Robert L. Crutchfield  
Torrance, California

I was much amazed and amused by the "All-brand Servicing" article in your September issue.

Why RCA feels obligated to apologize for or relinquish cost saving advantages in providing repair service amazes me.

The main reason for entering the "all-brands" servicing field should be to make a profit. This can only

be accomplished by superior management minimizing operating expenses, while maximizing servicing skills and customer awareness. If deemed necessary by RCA, this should include recommending RCA products, without apology, and use of RCA facilities, whenever cost advantages may be realized.

It is amusing, though unfortunate, that certain entities, apparently prodded by an appeal to weakness, feel compelled to band together and exert pressure to reduce the capabilities of others to a common level. How much more worth-while if this vast energy were directed inward toward self-improvement and proficiency!

I am a one-man operation because I want to be, but I can effectively compete in many ways through my own efforts.

May I never cultivate a desire to mind the other fellow's business, large or small, or expect to succeed in business without really trying.

Here's hoping RCA Service America and all electronic servicing entities, including my own, always receive exactly what they earn.

Robert N. Woodcock  
Manhattan Beach, Calif.

## Parts Availability

In answer to George Savage of Grand Island, Nebraska: Not all companies delay sending parts.

In August of 1970, I needed a transistor for a Magnavox TV. I ordered the part from the company in Skokie, Illinois, after finding that it could not be purchased locally. I figured what I thought to be a reasonable amount for the part, and added for postage and handling. I then sent a signed blank check good for no more than a specified amount. Five days later, I had the part—and a satisfied customer.

It seems that if one is willing to trust a manufacturer, one gains by it.

L. J. Pederson  
Kansas City, Missouri ▲

## Change of Address

To receive *Electronic Servicing* at your new address, send an address label from a recent issue and your new address to:

**Electronic Servicing**, Circulation Dept.  
1014 Wyandotte St., Kansas City, Mo. 64105

## New Service Literature

**TV TECH AID**, Edward G. Gorman, Kings Park, L.I., New York 11754; printed monthly; yearly subscription \$7.95.

A monthly summary of actual color and b-w TV trouble symptoms, their possible causes and the cure for each. Where needed, a schematic of the circuitry involved is included.

The troubles and cures are grouped according to manufacturers, which, in turn, are listed alphabetically. The format of the publication is designed to facilitate filing the troubles and cures according to manufacturer and chassis number—a **definite aid to quicker servicing.**

# The replacement picture tube no other color tube can replace!



Simulated TV picture

**ZENITH**  
**CHROMACOLOR**

Now you can install the revolutionary Chromacolor picture tube in almost any brand of 23" (diag.) color TV. And let your customer see the difference: a new, sharper Chromacolor picture with greater brilliance, contrast and color definition.

Zenith pioneered, developed and patented (U.S. Patent No. 3146368) the Chromacolor picture tube. And only Zenith has Chromacolor.

Chromacolor is an easy sale because people already know of Chromacolor's superiority. (Last year, after the revolutionary new Chromacolor system was

introduced, Zenith giant-screen color TV sets became the No. 1 best-seller!)

### Full two-year warranty.

Here's your sales clincher: Chromacolor replacement color tubes are warranted for two full years. Exactly double the warranty period for most other replacement color picture tubes.

Give your customers the best — Chromacolor replacement color tubes. Only your Zenith Distributor has them.

## TWO-YEAR WARRANTY

Zenith Radio Corporation warrants the replacement CHROMACOLOR picture tube to be free from defects in material arising from normal usage for two years from date of original consumer purchase. Warranty covers replacement or repair of picture tube, through any authorized Zenith dealer; transportation, labor and service charges are the obligation of the owner.



Zenith Chromacolor picture tube pinpoints the color dots on a jet black background and for the first time fully illuminates every dot.

**ZENITH**  
The quality goes in  
before the name goes on

Circle 14 on literature card

December, 1970/ELECTRONIC SERVICING 15

# shop talk

With Carl Babcock  
ES Technical Editor



## New and Changed Circuitry In '71 Color TV

General trends in the designs of new color TV circuits for 1971 are almost identical with those reported in the December '69 issue of *ELECTRONIC SERVICING*. These major trends are:


- Increased use of solid-state components in both hybrid and all-solid-state designs. Integrated circuits show a small increase in usage, but the increase is less than had been predicted by some sources.
- Solid-state high-voltage tripler and quadrupler rectifier assemblies,

which include both the diodes and capacitors, are found in nearly half of the new chassis. Two such assemblies, employed in Zenith chassis, are shown in Fig. 1. High-voltage regulators of the 6BK4 type are used only in about 15 percent of the new chassis designs.

- Automatic tint control (ATC) circuits are in fashion now; most of the major manufacturers offer at least a few models equipped with one of the two basic types of ATC.

- Varicap- or varactor-tuned circuits in both VHF and UHF tuners have received much publicity, but, as yet, few new color receivers have this feature.
- The use of plug-in modules is increasing slowly, but the trend is well established and probably will eventually be adopted by most major manufacturers.

Despite the undeniable fact that the major trends differ only in degree from those of last year, a varied assortment of completely new and modified versions of previously existing circuits are incorporated in the new color receivers. The new and most-changed circuits are analyzed for you in the following paragraphs.

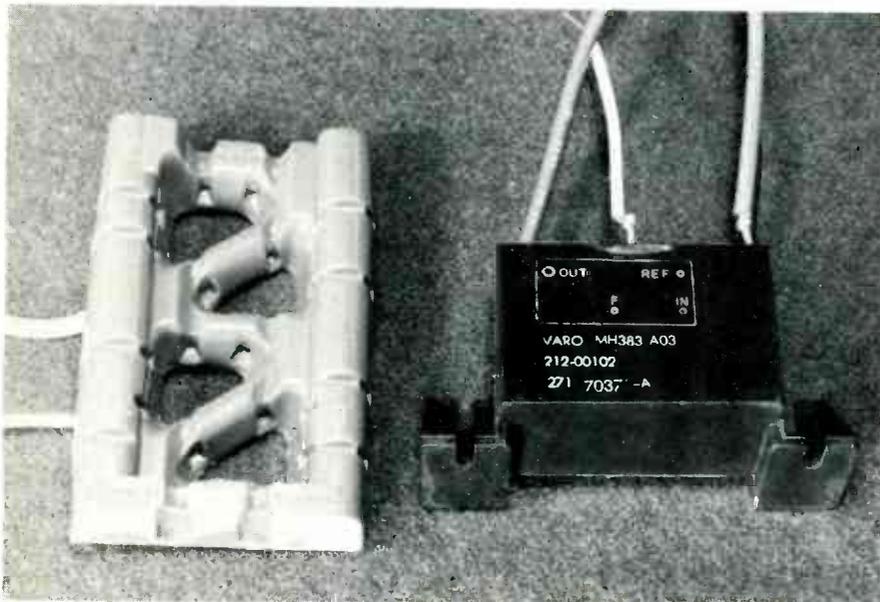

**Fig. 1** Two of the several types of high-voltage rectifier and filter assemblies used in new Zenith color TV receivers.

### Automatic Tint Controls

Automatic tint control (ATC) circuits are intended to offset the undesirable and frequent changes in tint, or hue, caused by variations in the broadcast signal. Because green or purple skin colors are the most displeasing flesh tints, all of the ATC circuits increase the amount of orange in the picture. Color-bar patterns, when the ATC is switched on, show as many as four orange bars instead of the usual one. Because some false hues will result from any ATC action that broadens the range of orange

skin tones, only enough ATC should be used to keep the flesh tones relatively consistent and of an acceptable hue.

When servicing ATC-equipped receivers, remember that ATC action will change the null, or crossover, points of the color-bar signal viewed on a scope connected to the CRT, or the actual color-bar pattern viewed on the screen of the picture tube.


### Magnavox and Admiral ATC

The ATC system in the new Magnavox T951 color TV chassis changes the phases of the yellow or red chroma signals to a 57-degree orange, which is satisfactory as skin color to most people. This is accomplished by gating on and off two transistorized channels, each of which has fixed amounts of phase shift. This correction signal then is


combined with the normal chroma signal just before it is applied to the demodulators.

Vector patterns offer the fastest and most dramatic proof of this circuit action, as shown in Fig. 2. With the ATC switch in the FULL position, the first three petals are

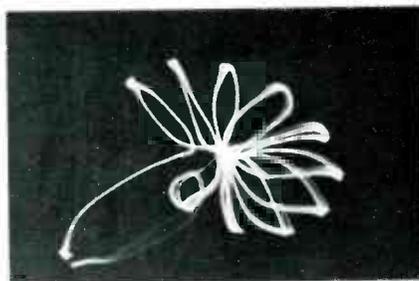all at 57-degrees, and even petals 4 and 10 are moved nearer to 57-degrees. Petals 6, 7 and 8 are not affected at all; these are the hues in the cyan region. (Refer to page 26 of the October '69 issue of ELECTRONIC SERVICING for a more detailed explanation of this



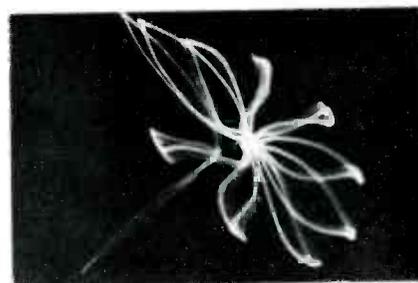(A) Normal vector pattern with the third petal at 90 degrees (red.)



(B) The first three petals all are at 57 degrees (orange) when the ATC switch is in the FULL position.

Fig. 2 Vector patterns illustrating Magnavox's ATC action.

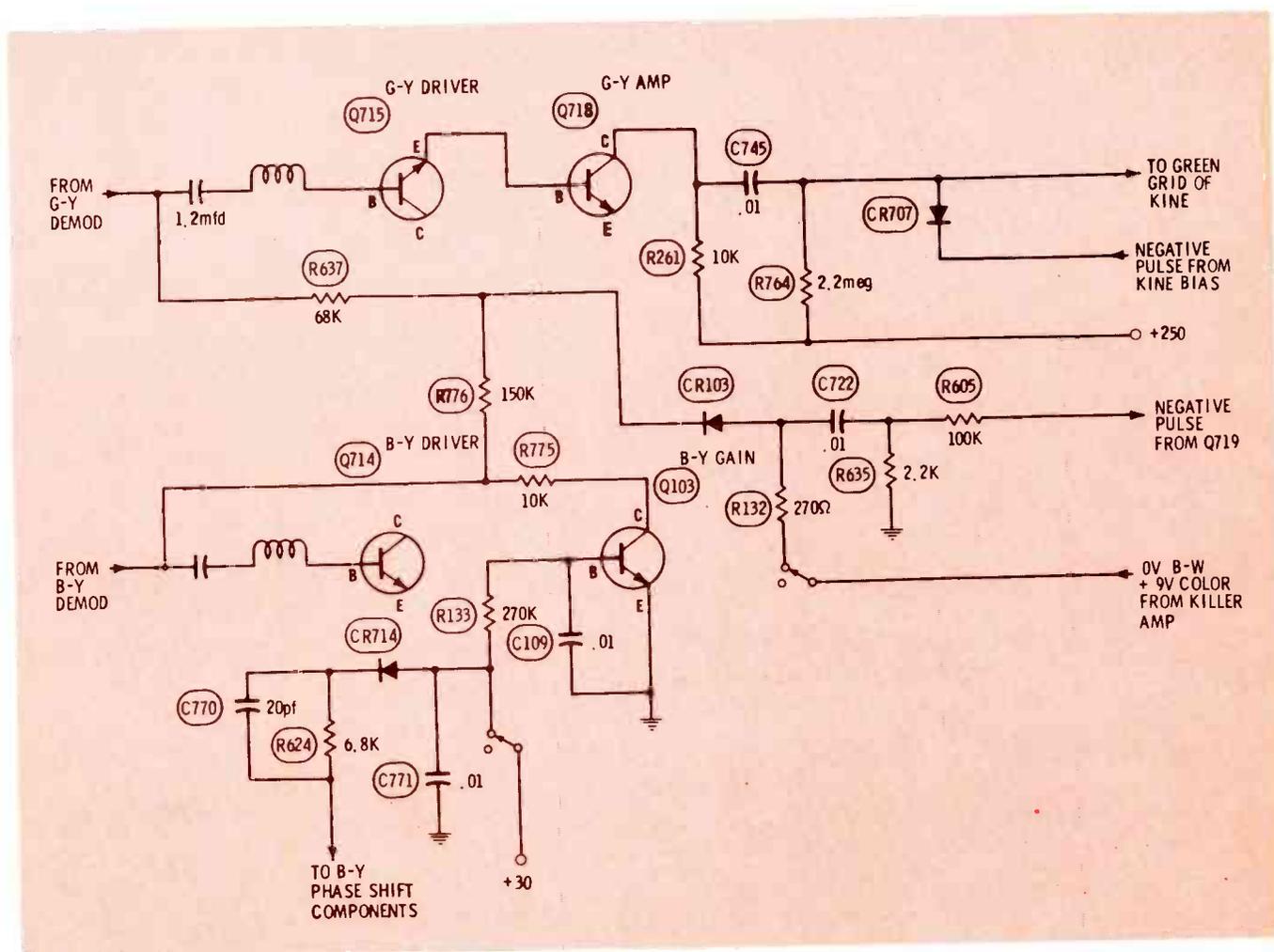


Fig. 3 The switching action of diodes and one transistor controls the ATC circuit of the RCA CTC44 chassis.

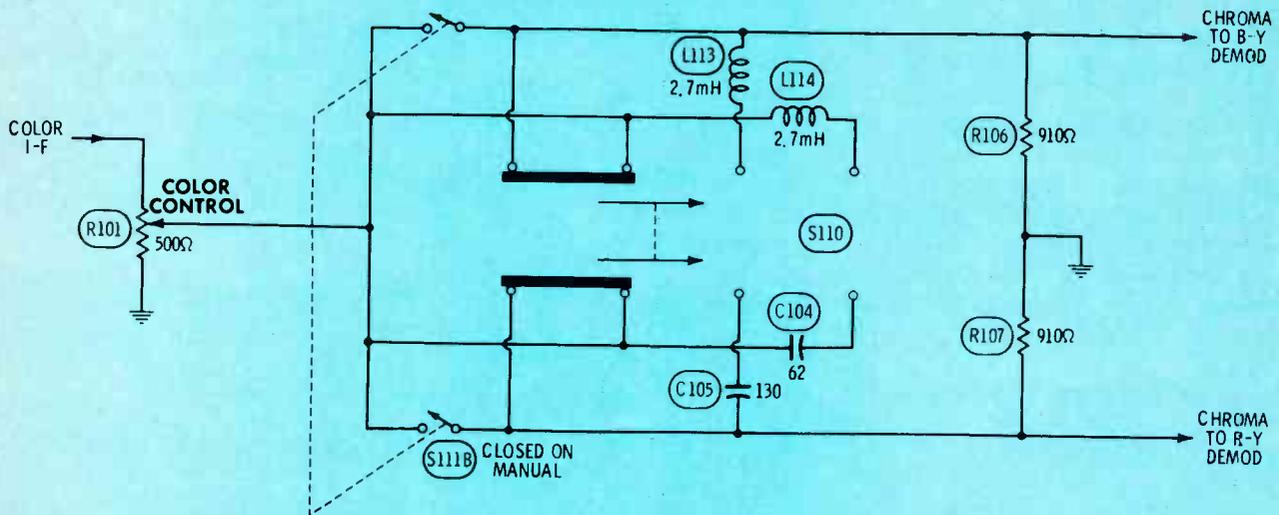


Fig. 4 Schematic of the Customatic Tint Lock circuit included in the General Electric KE-2 chassis.

particular ATC system.)

Magnavox color TV chassis T950 employs an ATC circuit, the operation of which is based on the same principle as that used in their other models, but in which several significant changes have been incorporated.

Chroma signals from the color control are applied to the base of QA5. Output from the collector supplies the main 3.58-MHz signal to the demodulators, while the signal from the emitter goes through "Partial" and "Full" switching diodes (controlled by DC voltages) to the Red and Yellow gate transistors. It is important to notice that QA5 is the stage whose gain is eliminated by the color killer. A varicap (or varactor) diode is used in the phase-shifting network of the Preference Control. The diodes and varicap apparently are used to avoid signal radiation or degradation that could be caused by the long leads between the ATC board and the front panel, if direct switching were used.

Admiral's Color Monitor employs almost the same circuit as the one found in Magnavox color chassis T951, except a chroma driver (emitter-follower) is inserted before the "Partial" and "Full" switch and the gate transistors.

#### RCA Accu-Tint

An analysis of the version of the RCA Accu-Tint (A-T) system used in the CTC39X color chassis was presented in an article which begins on page 30 of the July '70 issue of

ELECTRONIC SERVICING. As explained in that article, three basic changes occur in the chroma channel when the A-T switch is turned to the ON position. These changes are:

- The phase of the 3.58-MHz car-

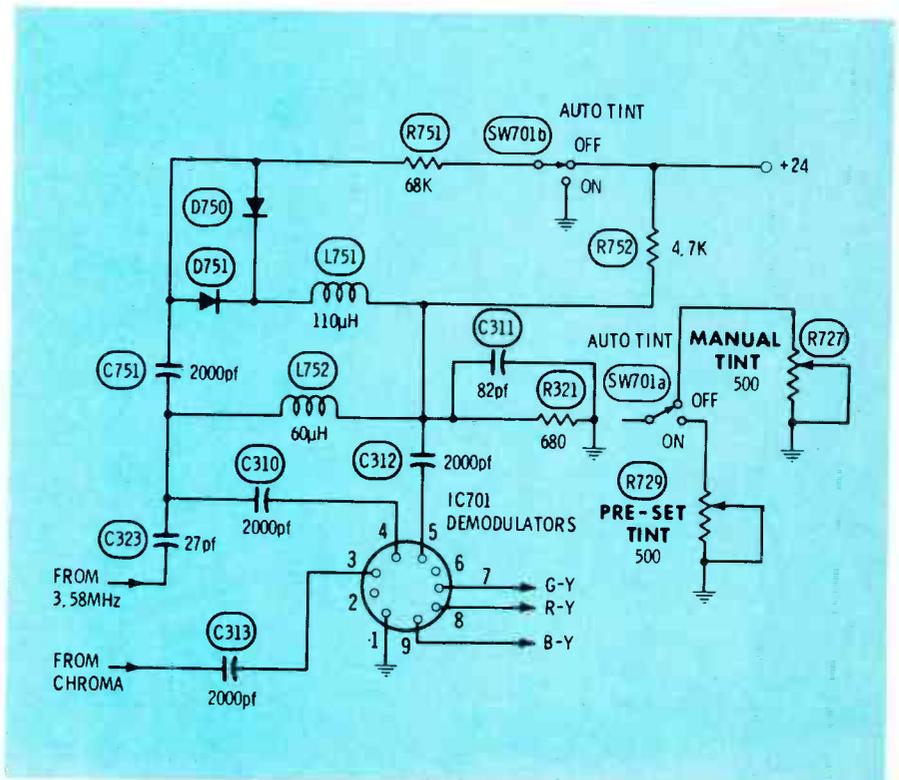


Fig. 5 The Auto Tint circuit designed into Electrohome's C9 chassis employs diode switching.

rier applied to the B-Y chroma demodulator is changed so that the output from this demodulator is separated from the R-Y signal by 124 degrees. Previously, beginning with their CTC16 chassis, RCA has used 105 degrees as normal phase difference between B-Y and R-Y signals. When a color-bar pattern is viewed on the screen of the TV and the Accu-Tint is switched to the ON position, the blue bars move about a half bar to the right (away from the red bars). This multiplies the number of color bars that are orange, or nearly orange.

- The output from the B-Y demodulator circuit is reduced about 33 percent.
- The hue, or gray-scale, of the blue screen is changed from the normal blue-white to a brownwhite (sepia). This "warming" of the screen color "temperature" occurs

only when the A-T switch is in the ON position during reception of a color signal (color killer inoperative).

These same changes occur in the chroma section of the RCA all-solid-state CTC44 chassis, but are the result of different ATC circuit actions. The schematic in Fig. 3 shows this part of the chroma circuit. When Accu-Tint switch S112 is turned to the ON position, +30 volts is applied to the anode of CR714, and, because its cathode is returned to ground through R624, L710 and the secondary of the tint transformer, it is forward biased and becomes a near-short circuit. This action connects C770 and R624 (through C771) in parallel with phase-shift components C758 and R778, which increases the phase shift of the 3.58-MHz signal that is applied to the B-Y demodulator.

The same +30 volts which is

applied to the anode of CR714 also is applied, through R133, to the base of Q103. This forward-biases Q103, and the near-zero collector-to-emitter resistance grounds R775, reducing the output from the B-Y demodulator.

Warming of the screen color temperature is accomplished by adding opposing pulses to the grid clamp diodes connected to the green and blue control grids of the CRT. The +9 volts that appears at the collector of Q705 the killer amplifier transistor, when a color program is received is applied through S112 and R132 to the anode of CR103. This positive voltage forward biases CR103, which passes the clamping pulse (obtained from R605, R635 and C722) on to R637 and R776. The negative pulses through R637 and R776 are amplified and inverted by the G-Y and B-Y amplifiers and finally applied to the anodes of CR707 and CR708, which are connected to the green and blue grids of the CRT, respectively. The positive-going pulse on the green grid of the CRT and the anode of CR707 adds to the negative-going clamping pulse at the cathode of CR707 and drives the grid a few volts less positive than it would be without ATC action. Identical action takes place at CR708 and the blue grid of the CRT. Consequently, the brightness of both green and blue is reduced, while red remains the same.

### GE Customatic Tint Lock

Phases of the chroma signals applied to the B-Y and R-Y demodulators of the GE KE-2 color chassis are changed by the switch positions of the Customatic Tint Lock circuit. "Manual" and "Automatic" pushbuttons on the tilt-out control panel switch on the AFC and ATC functions in the "Automatic" position, and switch them off in the "Manual" position. Switching of the ATC action is shown in Fig. 4. In addition, S110 can be adjusted for no ATC action (110 degrees between R-Y and B-Y demodulators), moderate action (130 degrees) or maximum action (150 degrees).

Because of the weaker signal and the shorter length of lead, less radiation occurs when the chroma sig-

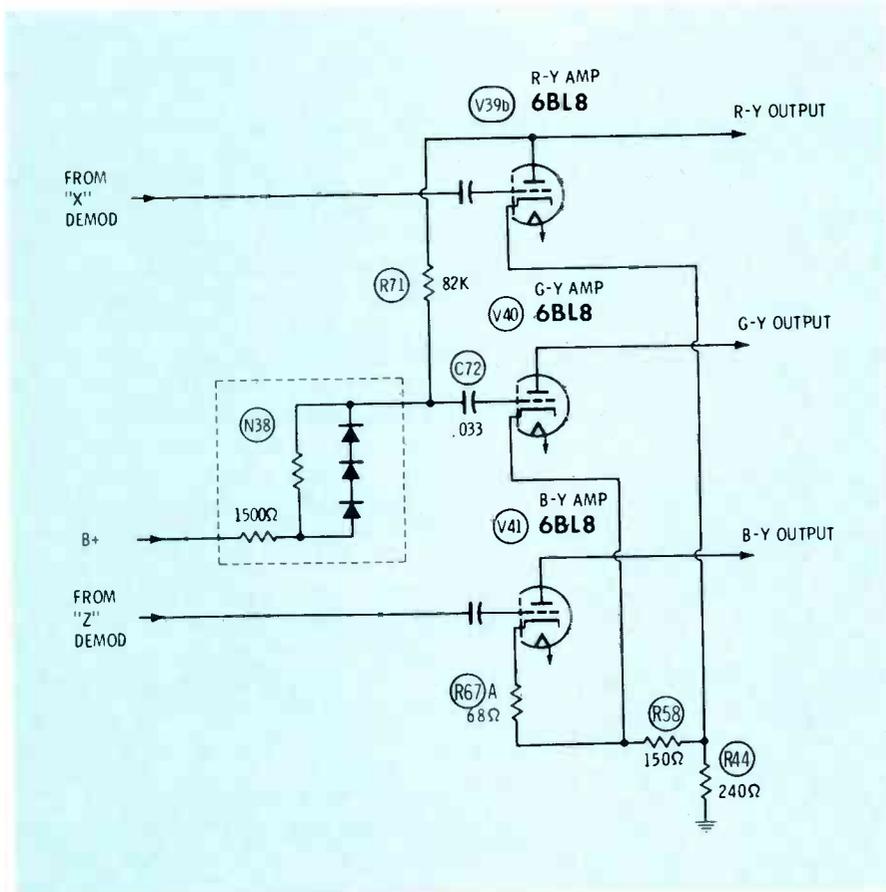


Fig. 6 A new type of matrixing is used in the production of the G-Y signal in Philco's 21ST90 chassis.

nal, instead of the 3.58-MHz carrier, is phase shifted by ATC adjustments.

### Electrohome Auto Tint

Diode switching is used in the Electrohome hybrid chassis C9 to change the phase of the 3.58-MHz carrier applied to the integrated-

circuit chroma demodulator, as shown in Fig. 5. The ON position of the Auto Tint switch (SW701, a front panel control) also switches in factory pre-set color and tint controls. These pre-set controls can be readjusted by a TV technician, if the customer is not pleased with the factory setting.

In the OFF position of SW701, the cathodes of D750 and D751 are more negative than the anodes; consequently, both diodes are a near-short, and L751 is connected in parallel with L752.

When SW701 is placed in the ON position, R751 is grounded and no DC voltage is applied to the anodes of the diodes. Because about +5 volts still is applied to the cathodes, the diodes are reverse-biased, opening the circuit so that L752 is the only reactive element in the phase-shifting network. Consequently, the phase change is less than that produced with the switch in the OFF position.

Outputs from the R-Y and B-Y demodulators differ by 105 degrees in the OFF position of the Auto Tint switch and by 125 degrees in the ON position.

### Philco Auto Tint

Philco does not have a switch or control for changing demodulator phasing, color balance or screen color of its new color receivers, but some of these features are built in.

Circuit features which produce actions that correspond roughly to a change in demodulator phasing are shown in Fig. 6. Most of the G-Y signal is developed in the common cathode circuit of the three tubes. R58 has been added to make the cyan hues less blue, and R67A slightly reduces the B-Y output. The G-Y amplifier needs additional signal from the R-Y stage to give proper matrixing, and this is obtained easily through R71. However, a better color reproduction of degraded picture information is produced if the R-Y signal fed through R71 is more negative than positive. The diodes and resistors in network N38 supply such a logarithmic voltage. Philco product information states that the interim quality of skin color is greenish; however when the tint control is readjusted to produce correct orange face hue, the green hues will have less blue contamination.

Philco also has an Automatic Color Temperature Control (ACTC) circuit which makes the raster color more sepia during reception of color signals. Fig. 7 shows the simplified schematic. Color-killer voltage is used to "identify" b-w or

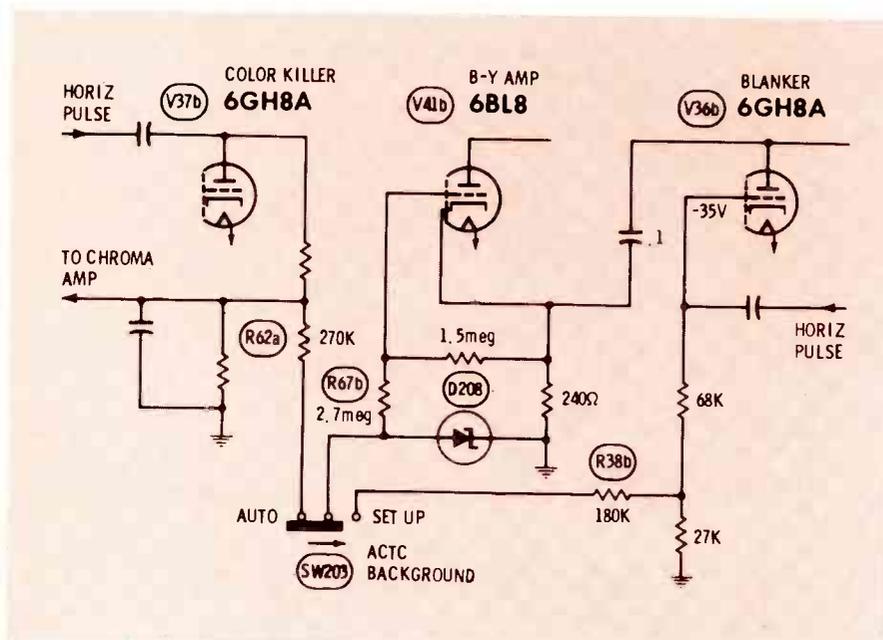


Fig. 7 Killer action in the Philco 21ST90 chassis during reception of color signals also changes the screen color to sepia.

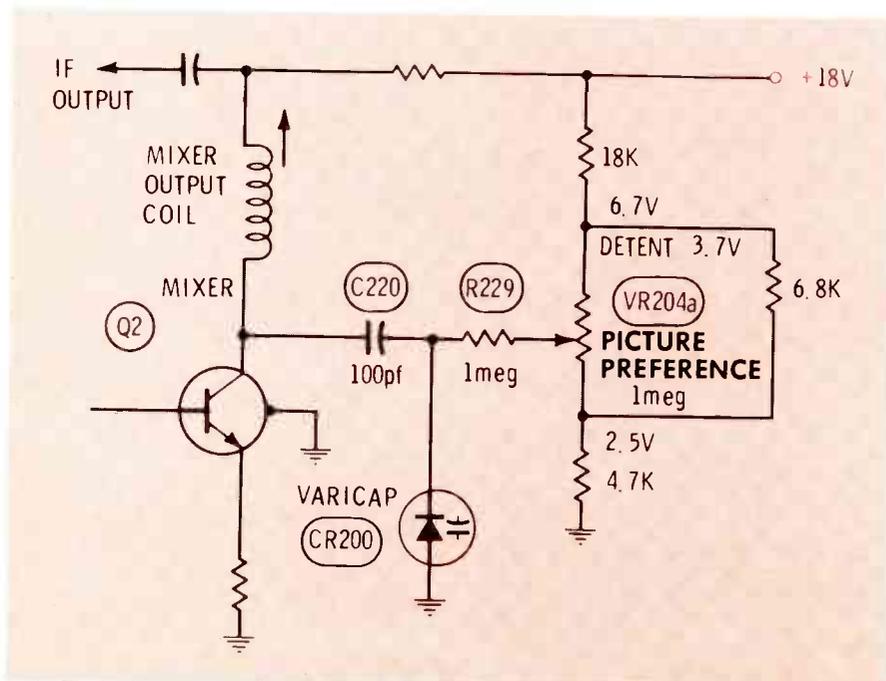


Fig. 8 A slight change of IF alignment by varicap tuning in the Philco 21ST90 chassis gives an effect similar to video peaking.



## The story on RCA SK devices is told in confidence

Since top quality is assured in all SK-Series Devices, they are bought and used in total *confidence*...key to the success of RCA's comprehensive replacement line.

This SK line is precisely engineered. Each device—transistor, rectifier, or integrated circuit—is manufactured and tested to tight, premium specifications. And the SK line is designed especially to fit a broad number of applications in entertainment-type electronic equipment.

No wonder RCA SK's are among the industry's top performing replacements!

This line now numbers 47 devices that can replace more than 14,000 units—foreign, domestic, even unbranded part-number types! All are backed by electrical parameters that make them comparable to—often better than—original devices.

Featuring only premium types—no cast-offs, no factory seconds, no unbranded culls, RCA SK devices cover most jobs you face—from small signal applications to TV deflection circuits to the latest in 100-watt audio amplifier outputs.

All RCA devices, after careful checking and rechecking of the types they replace, are cross-referenced in the current RCA SK Replacement Guide. It also includes:

- A new, quick-selection chart by application
- A new, technical data selection in tabular form
- A new listing of types recently added to the line



For more information on RCA SK replacements and your copy of the RCA Replacement Guide, see your local RCA Distributor.

RCA | Harrison, N.J. 07029

# RCA

color programs for the circuit, and an ACTC set-up switch (SW203) is provided to switch in a standard voltage in place of the killer voltage, which might be undependable because of signal conditions during the adjustment.

In the SET-UP position of SW-203, a small amount of negative voltage, taken from the grid of the blinker tube, is supplied to the grid of the B-Y amplifier. To establish the desired b-w color temperature, the ACTC control is placed in the SET-UP position, and the screen color, or gray-scale, is adjusted in the usual way using the CRT drive and screen controls. Then the ACTC switch is returned to the AUTO position, in which the same amount of voltage established in the SET-UP position is supplied the grid of the B-Y amplifier by the color killer when b-w programs are received. Thus, the b-w screen color is the usual blue-white.

Because no negative voltage is generated in the color-killer circuit during reception of color signals, the grid of the B-Y amplifier is less negative than during b-w reception or when the ACTC switch is in the SET-UP position. The less-negative grid causes the B-Y plate to become less positive, and because the blue grid of the CRT is coupled direct to the B-Y plate, less blue is seen in the raster and picture. Part of this same effect also is transferred to the green, because of the common cathode connections. Less blue plus slightly less green makes the raster more orange, to emphasize

skin hues.

The next Philco feature to be discussed is not strictly an ATC circuit (see Fig. 8), yet it is intended to relax the rigid grip that automatic fine tuning has on the b-w picture quality. In the VHF tuner, a varicap diode is used to change the tuning of the mixer-output IF coil when the reverse voltage on the diode is changed by means of the Picture Preference Control (PPC), which is located on the front panel.

Color quality is changed very little by this feature because, as Philco states, the change in alignment is stopped before the color is degraded. A detent is provided, and the receiver has been factory aligned with the PPC control set at the detent. Visible effect on the picture quality is somewhat the same as that produced by a video peaking control, with normal sharpness obtained at the detent. However, it is possible that better vertical and horizontal locking might be obtained on weak or poor signals with the PPC control set to smear slightly the b-w detail, compared to normal locking obtained with a video peaking control.

### Zenith Auto-Tint Guard

Several of the new Zenith models use the circuit shown in Fig. 9 to improve the varying skin hues produced by some color broadcasts. Operation is straightforward: The demodulation angle between R-Y and B-Y is increased when SW204 is closed and connects C262 in parallel with C1016.

### Plug-in Circuits

The expanding use of plug-in circuit boards, panels or modules could prove to be one potential source of help in relieving the added burden imposed on TV technicians by miniaturization and the added complexity of solid-state designs.

Motorola Quasar removable panels and Zenith Duramodules (shown in Fig. 10) are well known and seem to have been well accepted.

RCA for some time has been testing the module concept in selected models of their b-w receivers. Recently, RCA announced their CTC49 all-solid-state portable color TV chassis, which uses eleven modules. The locations of these modules and other major parts are shown in Fig. 11. Fig. 12 shows the socket on board PW300 with its associated module (MAC) removed. Sound module PM22 and its socket can be seen in the back-ground.

Pre-CRT matrixing for each color is accomplished in the three MAD modules. Fig. 13 shows both the original type, which uses conventional discrete components, and the newer version, which is an encapsulated "computer card" type that eventually will replace all the original versions of all the modules. RCA states that the latter type gradually will be phased into production during the next few months.

Warranty on the different brands of modules varies. Motorola still has a replacement warranty on the entire panel. Zenith warrants only the individual parts on the Dura-

Fig. 9 The Automatic Tint Guard circuit in Zenith 40BC50 and 12B14C50 chassis adds a capacitor to the circuitry to alter demodulator phasing.

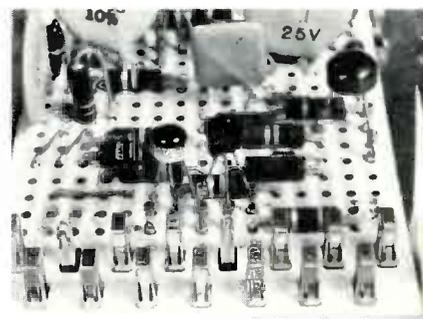
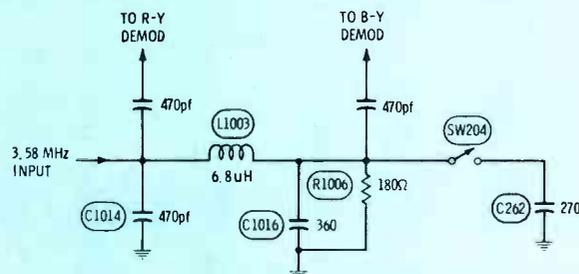


Fig. 10 Plug-in Duramodule used in Zenith's 4B25C19 chassis also features plug-in transistors.

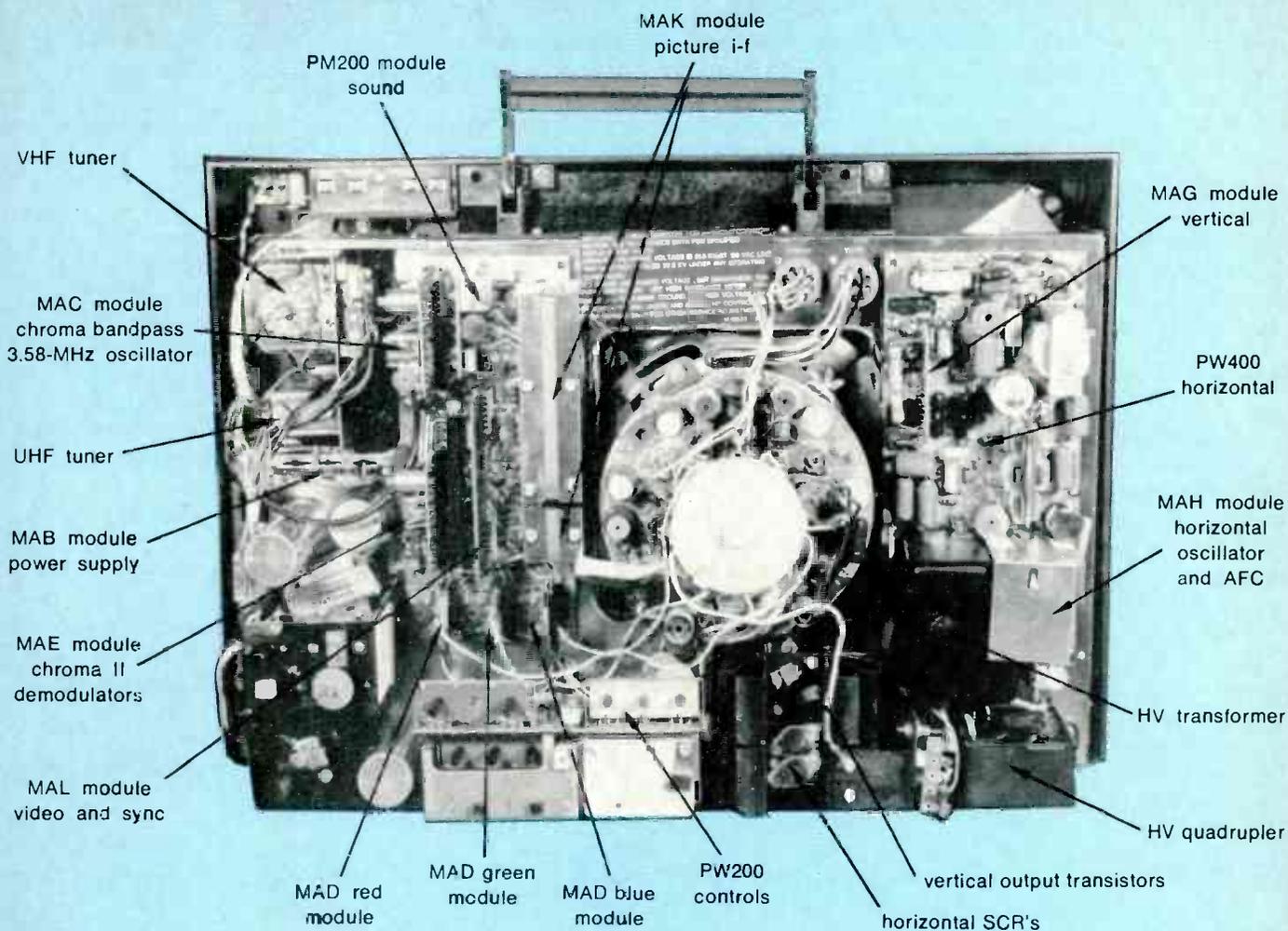


Fig. 11 Photo showing location of major components and the eleven modules that comprise the RCA CTC49 chassis.

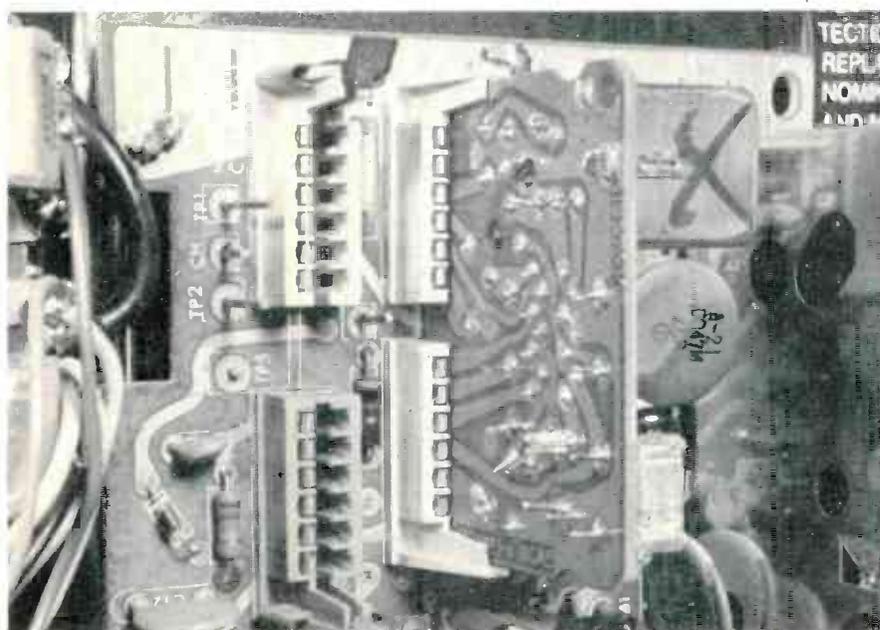


Fig. 12 Upper and lower sockets with module MAC removed from the RCA CTC49 chassis. Module PM200 and sockets are shown at right in background.

module (the transistors plug-in, as shown in Fig. 10). RCA provides a complete panel in exchange.

Motorola panels, Zenith Duramodules and the present type of RCA modules can be serviced by normal troubleshooting and repair techniques if the modules are out of warranty, or if repair seems desirable for any other reason. RCA encapsulated modules cannot be repaired with reasonable effort; therefore, replacement is necessary.

#### High Voltage and Automatic Brightness Control

Fewer tube-type, high-voltage rectifiers and regulators are being used because of the possibility of radiation if the high voltage becomes abnormally high.

Fail-safe circuits, tripler and quadrupler rectifier assemblies with capacitors and semi-conductor di-

odes in one unit, elimination of the high-voltage DC shunt regulator tube and a search for new methods of high-voltage regulation are the order of the day.

Automatic Brightness Control (ABL) circuits help high-voltage regulation indirectly by preventing excessive CRT current and, thus, any excessive decrease in high voltage (which, if severe enough, causes a noticeable amount of picture blooming).

### Extra Admiral Diodes

Several chassis which regulate horizontal sweep and high voltage by changing the negative voltage applied to the grid of the horizontal output tube have added an extra diode in series or parallel with the one necessary for pulse rectification. The ultimate in such cautious design is the circuit in Fig. 14, an Admiral design that employs four diodes in series-parallel. Failure of any one diode (or in certain specific failures, up to three diodes) will not affect the regulation.

### High-Voltage Regulation

Sweep/high-voltage regulation and ABL circuits employed in Hitachi CFA-450 and CSU-690 models are shown in Fig. 15. T703 is a saturable core reactor which changes impedance in accordance with the load on the high-voltage circuit. The Japanese-to-American translation of specifically how this circuit functions was too garbled to understand, and the actual physical construction of the reactor, which obviously is of an unusual design, was not ascertainable from the material supplied us. The Hitachi ser-

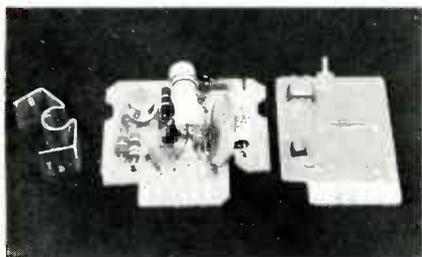


Fig. 13 Early-production MAD module and heat sink on the left, and a new type of encapsulated MAD module on the right.

vice data says that the impedance of T703 varies as the current through it changes. Thus, LX winding of T703 is in parallel with the primary of T704, the high-voltage transformer. Any reduction in the impedance of T704 because of increased load should be offset by an increase in the impedance of LX.

Understanding the operation of the ABL circuit is relatively easy if you imagine that R724 is connected to ground instead of +120 volts, and then realize that the voltage at the low end of the high-voltage transformer secondary is the source of negative voltage which varies in direct proportion to the average amount of rectified current passing through the tripler.

(Also of help in understanding this circuit is the following rule, which was stated in the Shop Talk column in the September '70 issue of ELECTRONIC SERVICING: "When rectified DC is obtained from a diode, the polarity of the voltage will be negative if it is taken from the anode, and positive if it is taken from the cathode.")

In the Hitachi ABL circuit, the negative voltage at the junction of C723 and R724 partially cancels the steady DC voltage through R724 from the +120-volt source. The more CRT current, the lower the positive voltage that is applied to the CRT grids. Since the cathodes of the CRT are operated at a fixed positive voltage, the CRT is biased more negatively with increased CRT current; therefore, the CRT is prevented from drawing an excessive amount of current.

### Zenith Automatic Brightness Limiter

The ABL system in Zenith 40BC50 and 4B25C19 chassis does not monitor the actual high-voltage current; instead, the operation depends upon the amount of ripple in the focus voltage supply. The more high-voltage current drawn from the rectifier-filter assembly, the higher this ripple will be. Ripple (AC content) from the focus supply voltage (see Fig. 16) is coupled through C277 (inside the rectifier assembly, in some cases) and R338 to the base of Q204, which has no


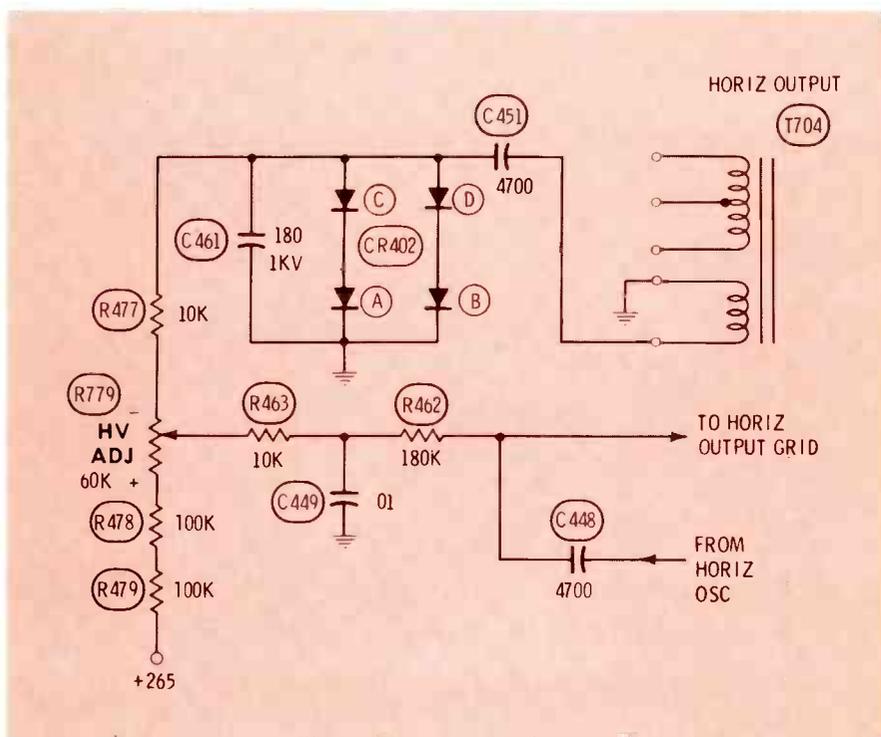


Fig. 14 To help insure adequate high-voltage regulation regardless of failure, four diodes are wired in series-parallel in the high-voltage regulator of Admiral's 19H10 chassis.

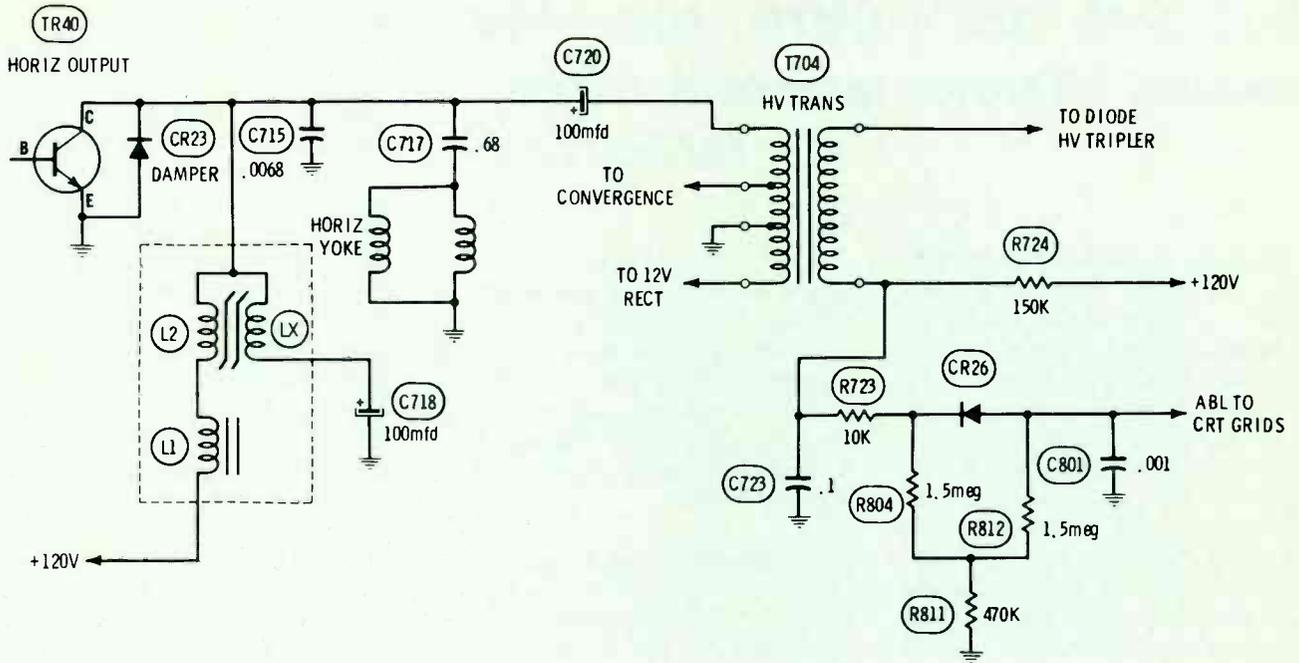

**Fig. 15** Hitachi models CFA-450 and CSU-690 employ a saturable-core reactor as the high-voltage regulator. CRT current through the high-voltage tripler determines the amount of bias supplied the CRT by the automatic brightness limiter (ABL) circuit.


bias applied to it except for the ripple. If the ripple at the base is low, Q204 does not conduct and, consequently, the collector voltage, which is connected to a video amplifier stage, remains at almost the same value as the supply voltage.

When the ripple amplitude is high because of increased high-voltage current, Q204 is saturated by the large forward bias developed by the ripple, and the collector-to-emitter junction becomes a low-value resistance, which causes the collector voltage to drop, thereby increasing the negative bias on the CRT via the video amplifiers.

CRT current is limited to about 1.5 milliamperes by this ABL action.

### Next Month

Because space available in this issue has not permitted discussion of all new circuitry and significant modifications of existing circuit designs used in the 1971 color chassis, this article will be continued next month, and for as many issues as necessary to insure complete coverage of this most-important topic. ▲

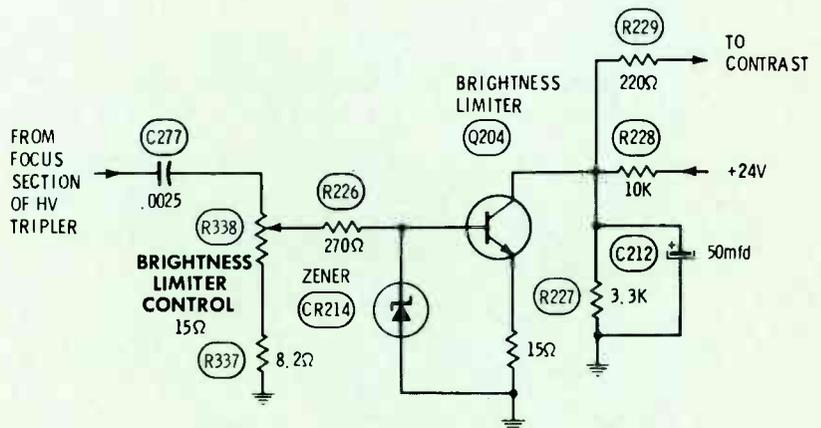

**Fig. 16** The ABL circuit in Zenith's 40BC50 and 4B25C19 chassis senses the increased ripple amplitude of the focus supply voltage (resulting from excessive brightness). The change in ripple amplitude is used to control Q204, the collector voltage of which varies the conduction of the video amplifiers and, consequently, also varies the bias applied to the CRT. Q204 functions as both a rectifier and amplifier. The video amplifier voltage is directly coupled to the CRT, in the correct polarity to reduce the brightness level.

by Allan Dale

# 1-2-3-4 Servicing Adds up to improved efficiency because it reduces Service Time

A couple of books I saw recently made me think, "Wish I'd thought of that." They're about a carefully organized method of troubleshooting called **1-2-3-4 Servicing**.

Using this four-step system, you break down a set into four successively smaller divisions. Before you're through, you've run the trouble down to the faulty part. The idea works for anything—color set, amplifier, record player, cassette machine, radar. You apply the same principles no matter what kind of electronics.

Both books are published by Howard W. Sams & Co., Inc. They're written by Forest H. Belt. The titles are "1-2-3-4 Servicing Automobile Stereo" and "1-2-3-4 Servicing Transistor Color TV."

The 1-2-3-4 Servicing system works so well, I got permission to tell you about it briefly in this department. It's the most basic and effective method I've seen. Yet it includes some techniques you've been using for years. Anyway, look it over and try it. You'll find it highly effective.

## Dividing Up A Set

The basic premise is "divide and conquer." You first consider the set as divided up into its various **sections**. Once you diagnose what section is faulty, you divide that section into **stages**. Having located which of those stages is defective, you divide that one stage into **circuits**. Now you can isolate the the faulty circuit, and divide it up

into **parts**. By this divide/divide/divide method, you end up with only a few parts to test, one of which is sure to be the bad one.

The first important thing to know is what constitutes a **section**. The block diagram in Fig. 1 should help clarify it for you. Each section handles one kind of signal. For example, in the diagram a radio is shown divided into RF, IF, and audio sections. The TV set consists of RF, IF, video, sync, sweep, and audio sections.

Whenever the nature of the signal is changed, it goes into a different section. The RF section of a TV handles modulated station signals. Once their character is changed by conversion to an intermediate frequency, they enter another section—the IF section.

The same thing is true further along. The composite video signal is handled in the video section. Once the sound IF is extracted, a different section handles it. Ditto the sync. And sweep signals are in a section all their own.


You can get a little better idea of a section once you see how a section is divided up. It's broken down into whatever **stages** are in it.

For example, in Fig. 2A you see the RF section of a radio. The stages in it are an RF amplifier, an RF oscillator, and a mixer. All stages in the RF section handle RF signals.

The section in Fig. 2B is the audio section of an FM radio. Stages in this section are the audio amplifier and power output.

The FM detector occupies a special position. It's an **interface stage**. It takes the IF signal from the IF section, and changes its character. It "changes" modulated IF into plain sound signals. The FM detector interfaces the IF section to the audio section. In Fig. 2A, the mixer is the interface stage between the RF section and the IF section which follows.

A third example is shown in Fig. 2C. The video section of this b-w receiver has only one stage, the video amplifier. If it had more than one video amplifier, they'd all be part of the video section. The video detector is a multiple interface stage. It interfaces the IF section with the video section and with the audio and sync sections. It does **not**

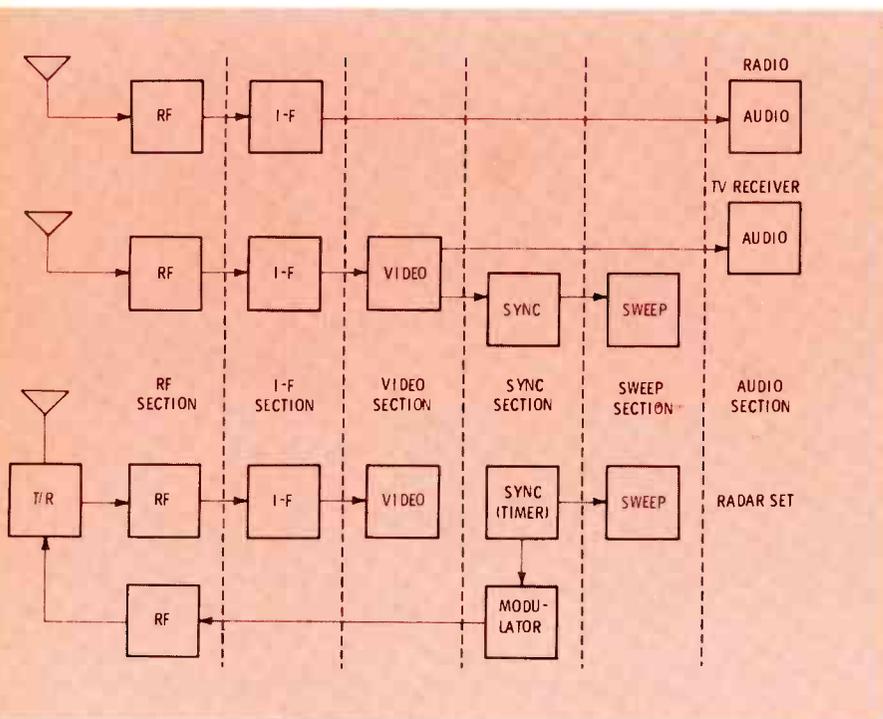

**Fig. 1** Sections are the largest division of electronic equipment. Each section handles one kind of signal. When the nature of the signal changes, it's handled in a different section.

interface the audio, video, and sync sections with each other.

Stages break down into **circuits**. There's a tendency to call whole stages circuits, but it's a bad habit. A circuit is one group of parts that have a **specific function** within a stage.

Take a look at Fig. 3. It helps explain what circuits are. The pentode tube stage in Fig. 3A has four main signal circuits and five DC circuits. **Signal** circuits are input, output, and two bypass circuits. Circuits that supply **DC** operating voltages and currents are cathodes, grid, screen, suppressor, and plate circuits—one for each tube element.

The transistor stage in Fig. 3B has only three circuits of each kind (**signal** and **DC**). The signal circuits are input, output, and emitter bypass. Operating voltages and currents reach and leave the transistor through the base, emitter, and collector DC circuits.

Circuits break down into **parts**. You get a clearer understanding of circuits if you examine the parts in them. An individual part might be used in several different circuits, depending on how you're looking at the stage.


Fig. 4 shows labels for the parts in the stage of Fig. 3A. From a DC standpoint, R1 is a grid return resistor. Yet, if you consider signal, R1 is the input-circuit load. C1, for the signal, is input coupling; for DC, it's a blocking capacitor.

Consider the plate circuit. T1 and R3 form the DC path. The screen supply path shares R3. For signals, however, R3 doesn't even enter the picture. T1 is tuned by C4, and C3 is a bypass (sometimes called decoupling) capacitor. These three parts form the output circuit.



The screen DC circuit follows a path through common (plate and screen) supply resistor R3 and screen supply resistor R2. For signal, the screen has only a bypass circuit straight to ground, through C2.

### The 1-2-3-4 Procedure

That tells you how to divide up a set. For 1-2-3-4 Servicing, you first divide into sections. Then divide sections into stages, stages into circuits, and circuits into parts. Realize, while you're at it, that you

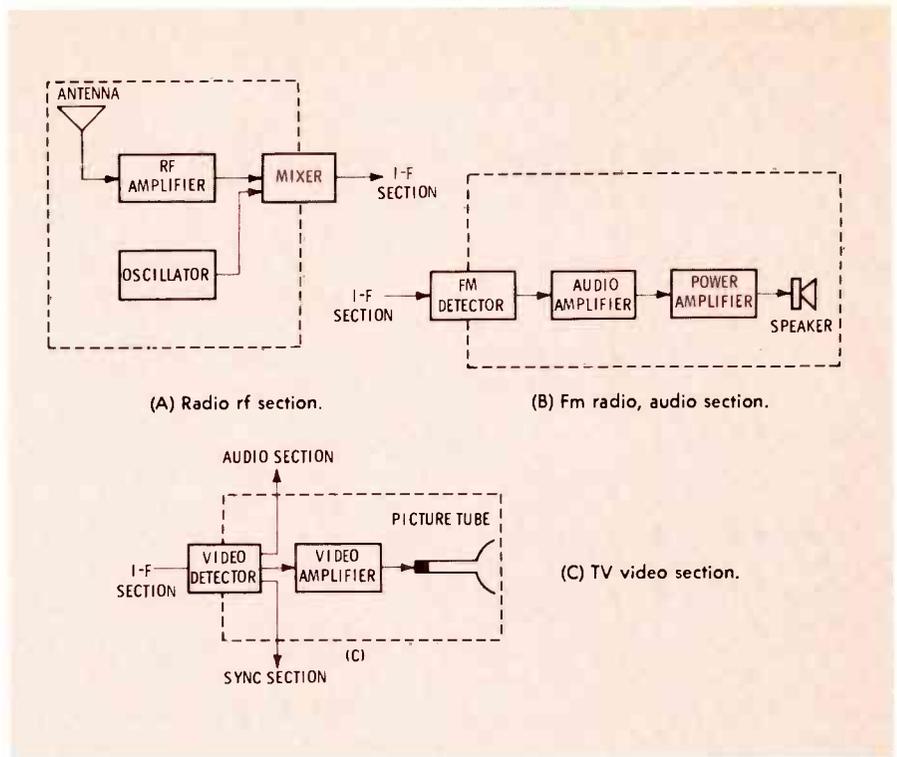

**Fig. 2** Examples of how sections are divided into stages. Interface stages are the ones that change the signals, in preparation for feeding the signal on to the next section.

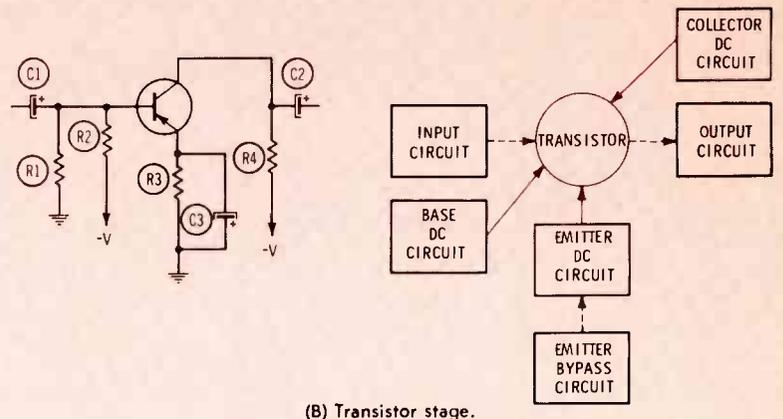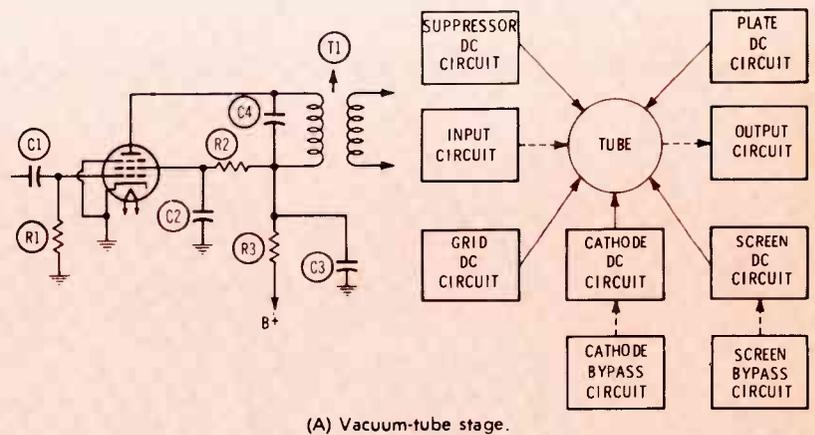

**Fig. 3** Circuits in typical amplifier stages. Other signal circuits include feedback circuits, tuned circuits. Bypass circuits are often called decoupling circuits.

can do this with **any** piece of electronic equipment.

What then? Well, as you probably guessed, you don't have to divide up **all** the sections, stages, and circuits. What you do is first **diagnose** which section isn't functioning as it should. From there on, you only worry about the stages, circuits and parts **in that section**. There are several recommended diagnosis methods, but I'll get to them later. The point is that your first step is to **diagnose** which **section** is bad.

Knowing what stages are in the faulty section, your next move is to **locate** which stage isn't functioning properly. That's why you have to be able to recognize all the stages of each section. What you're doing at each step is narrowing down the amount of testing by eliminating parts of the chassis.

Having located the faulty stage,

step three is to **isolate** which **circuit** in that stage isn't doing what it should. Specific tests help you do that. There are only a few circuits to check, because you test only the ones in the bad stage you've located during step two.

Finally, you **pinpoint** the defective **part** in that faulty circuit. To do it, you only have to test a few parts.

Now, review those four steps. (1) You diagnose the faulty **section**, so you don't have to worry about stages in other sections. (2) You locate the faulty **stage**, so you don't waste time on circuits in the good stages. (3) You isolate the faulty **circuit**, so you have only a few parts left to test. (4) You pinpoint the faulty **part**, and replace, repair or readjust it.

### Ways To Do The Testing

Now all you need to know is the

techniques for diagnosing, locating, isolating, and pinpointing. Then you can put 1-2-3-4 Servicing to work for you. You want **efficiency**, and the way to get that is with **quick tests**.

One thing may be a surprise: **You probably are familiar with most or all these tests**. 1-2-3-4 Servicing merely organizes them for you. Pick the tests or combinations of tests that suit you best for each step. No one test is best for all cases.

The chart in Fig. 5 gives the most effective methods for diagnosing the faulty **section**. It's relatively self-explanatory.

Familiarity with equipment is a big help, although not absolutely necessary. The chart tells how you can become familiar quickly. Another way to diagnosis is thorough observation—of how the set looks, sounds, smells, and feels, and of what symptoms are present. When you've completed this step, you should know in which section you can expect to find the faulty stage.

The chart in Fig. 6 names the best methods for locating the faulty **stage**. There are three groups: symptoms observation, signal tests, and DC tests.


Signal tests are carried out from stage to stage in the section you diagnosed as faulty. You can begin with injection tests at the output and work your way backward, or trace signals from the input up to where they become abnormal. This tells you which **stage** is faulty.

Some technicians prefer to make voltage tests on all stages in the faulty section. That's okay in some cases. But a lot of stages that test okay for DC still are faulty for signals. A combination of signal and DC tests usually is best.

Fig. 7 is the chart that tells how to isolate the faulty **circuit**. The tests are grouped into those for signal circuits and those for DC circuits. The lists in the chart remind you what circuits to check. Signal and DC tests for stages are described in Fig. 6, and they work as well in circuits. You go from circuit to circuit in the faulty stage.

Methods of pinpointing the faulty part are spelled out in Fig. 8. Again, the chart listings are self-explanatory.

Some technicians overlook the time-saving possibilities in the two

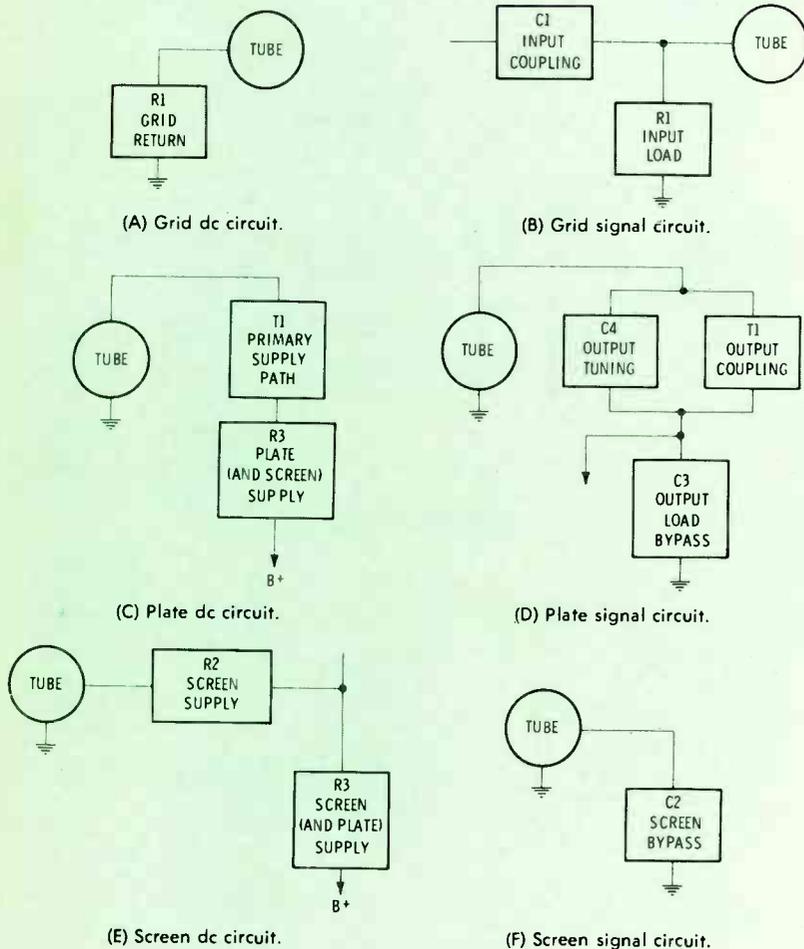

**Fig. 4** Parts, the smallest division for 1-2-3-4 Servicing, often serve in more than one circuit. Examples are shown here for both signal and DC circuits in Fig. 3A.



## Who said B & K couldn't improve the only complete Television Analyst?

Now there is a new model... the 1077-B, with solid state sweep drive.

The B & K Television Analyst has become standard equipment in repair shops everywhere. And for good reason. It's the quickest, simplest way to test every stage of any TV.

But even classic instruments have to keep up with the times.

That's why we've added a solid state sweep drive in our latest model. It can check any new transistorized color set on the market today.

It's so easy, too. Because the unique B & K signal substitution technique eliminates the need for external scopes or wave-form interpretation.

Whether it's tubes or transistors, VHF or UHF, simply inject the appropriate test pattern or any other known signal. The new Model 1077-B, with its exclusive flying spot scanner, checks everything from the antenna terminals to the input of the picture tube.

Ask your distributor about the new Television Analyst. Only B & K makes it. And now B & K makes it even better.

Model 1077-B \$389.95



Product of DYNASCAN CORPORATION  
1801 W. Belle Plaine, Chicago, Illinois 60613  
*Circle 16 on literature card*

methods listed last. **Individual parts testing** is quick, after you've isolated the fault to one circuit. You're taught in electronics school not to make haphazard parts tests. But the key word is "haphazard." Testing the parts in only **one** circuit you know is faulty is not haphazard.

**And substitution.** It's not practical for expensive or hard-to-reach parts. But for small parts, substitution often is faster than testing. A commercial substitution box, with a variety of parts and values, can save you countless minutes—and eventually hours—of testing time.

### Shortcuts

This method is so quick and direct in most cases, it seems silly to bother with shortcuts. But there are a few I'd like to at least mention. What often happens is that you move through a couple of steps at a time.

For example, look back at Fig. 3A. Suppose you've diagnosed a faulty IF section, and with the RF

probe of a signal tracer are working your way through the IF stages. Probably, you're jumping from grid to grid, or maybe grid-plate-grid-plate and so on. At the grid of the pentode shown, signal is okay. But at the plate it's very weak. That locates the faulty stage, completing step two.

Checking the signal circuits in that stage, you find no further clue. But DC voltage checks at the screen and plate tell you the screen circuit is okay but the plate circuit is open. Merely isolating that faulty plate circuit also pinpoints the faulty part—the transformer. It's the only part that's in the plate but not the screen circuit. You've completed steps three and four simultaneously.

Other similar happenings occur. Suppose the signal is okay at the plate of the stage preceding Fig. 3A, but your tracer detects none at the grid of this pentode. The input coupling circuit must be open. You've virtually skipped step two.

No need to worry about what stage; you've already isolated the bad circuit. What's more, you've pinpointed the faulty part—the capacitor is the only part in that input circuit. So, while working on step two, you've actually finished steps three and four.

The only rule about these shortcuts is: Don't vary from the sequence. Start with step one, and proceed to steps two, three, and four in that order. You'll find the whole procedure surprisingly fast. And any skips that occur **naturally** are bonuses.

### Next Month

What better subject to follow simplified servicing than how to troubleshoot one of the toughest sections in the whole TV receiver? No one likes horizontal sweep or high-voltage problems. But everyone is confronted with them at one time or another. Next month, I'll tell you how I keep them from driving me up the walls. ▲

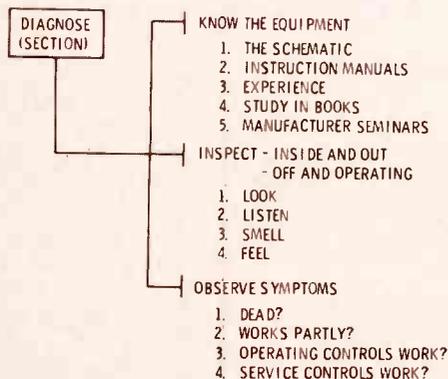


Fig. 5 Step One of 1-2-3-4 Servicing.

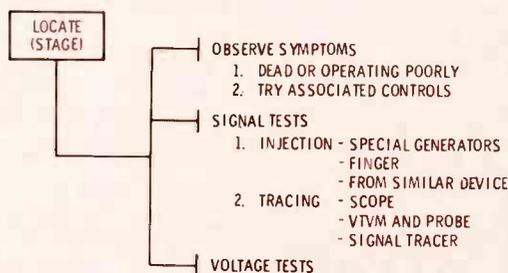


Fig. 6 Step Two of 1-2-3-4 Servicing

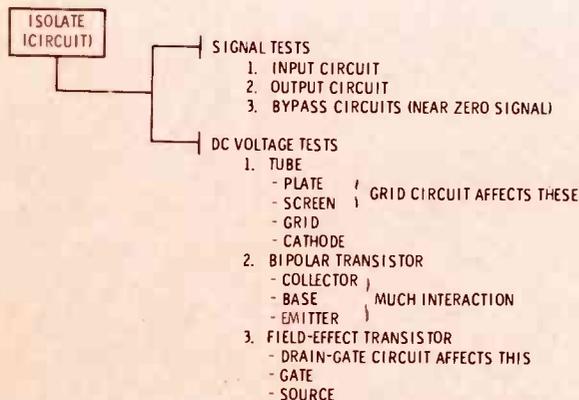


Fig. 7 Step Three of 1-2-3-4 Servicing.


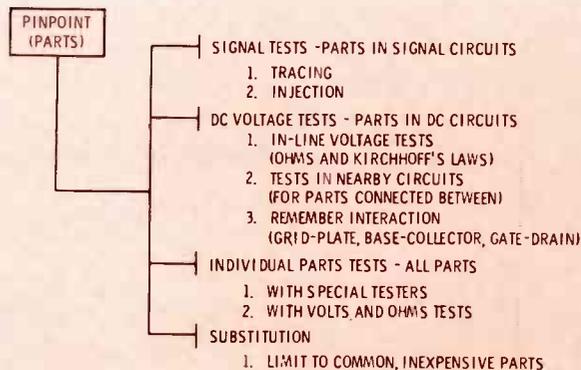


Fig. 8 Step Four of 1-2-3-4 Servicing.

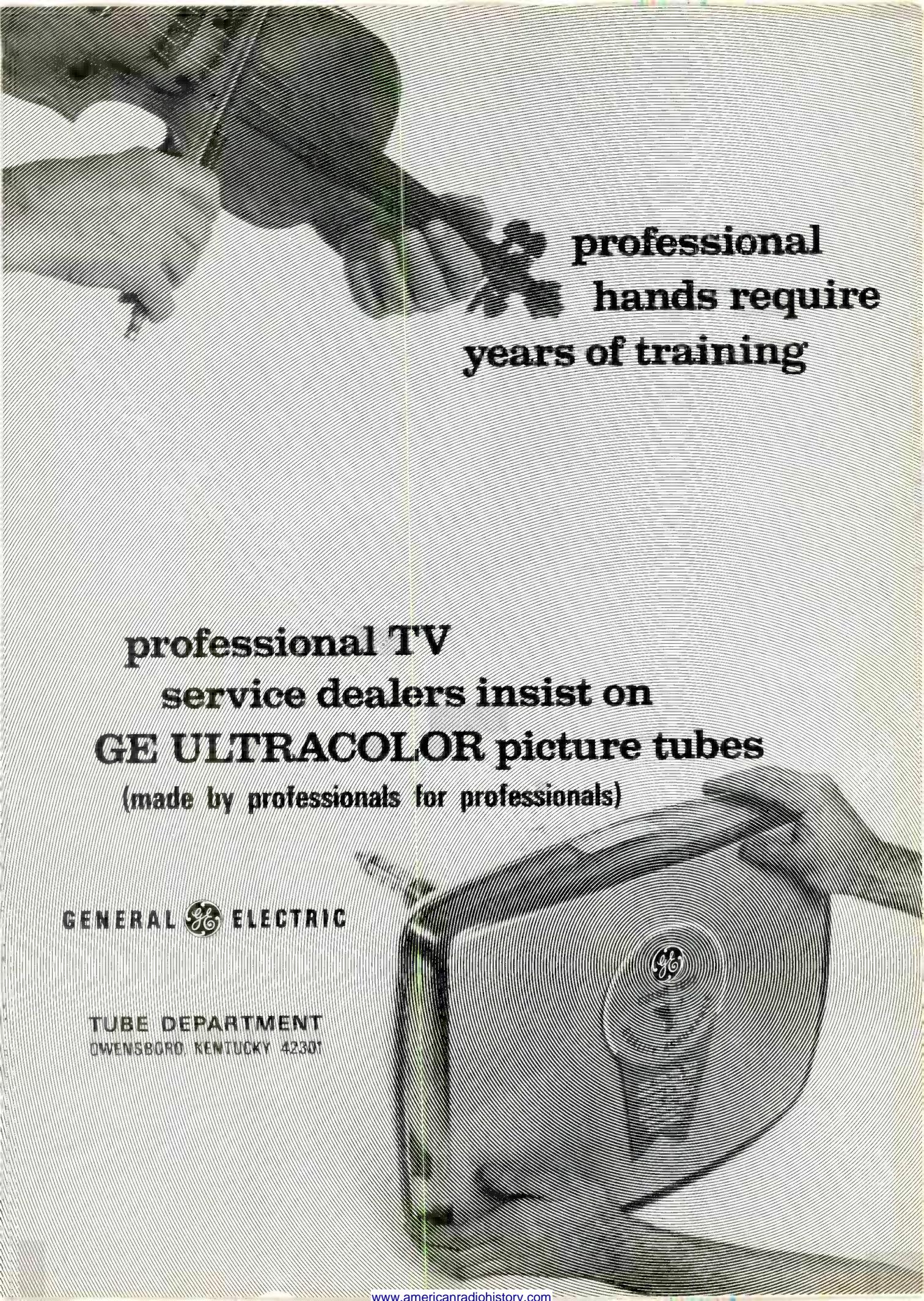

**professional  
hands require  
years of training**

**professional TV  
service dealers insist on  
GE ULTRACOLOR picture tubes  
(made by professionals for professionals)**

**GENERAL  ELECTRIC**

**TUBE DEPARTMENT  
OWENSBORO, KENTUCKY 42301**

# Troubleshooting video IF with sweep alignment gear

## Part 1

New test equipment has simplified sweep alignment—and IF troubleshooting.

by Larry Allen

Nowadays, with color so popular, and with so many sets operating from cable TV and MATV systems, alignment is more important than ever.

Oh sure, a set can get by without it, some of the time. But TV characteristics such as adjacent-channel performance, color bandwidth, and chroma sync depend on correct IF alignment. Even today's high-gain, black-and-white sets don't look right unless the IF and RF stages are properly aligned. Most technicians will admit that half the sets they see could use an alignment touchup.

### Simplifying Sweep Alignment

Of course, the reason some technicians pass over minor alignment is easy to understand. Sweep alignment takes time—or it once did. Also, it requires a lot of special equipment hookup—or it once did. And it demands you know the set rather intimately—or it once did. I keep saying "once did" because none of these is true anymore.

Take the time element. In earlier days, I used six instruments and sev-

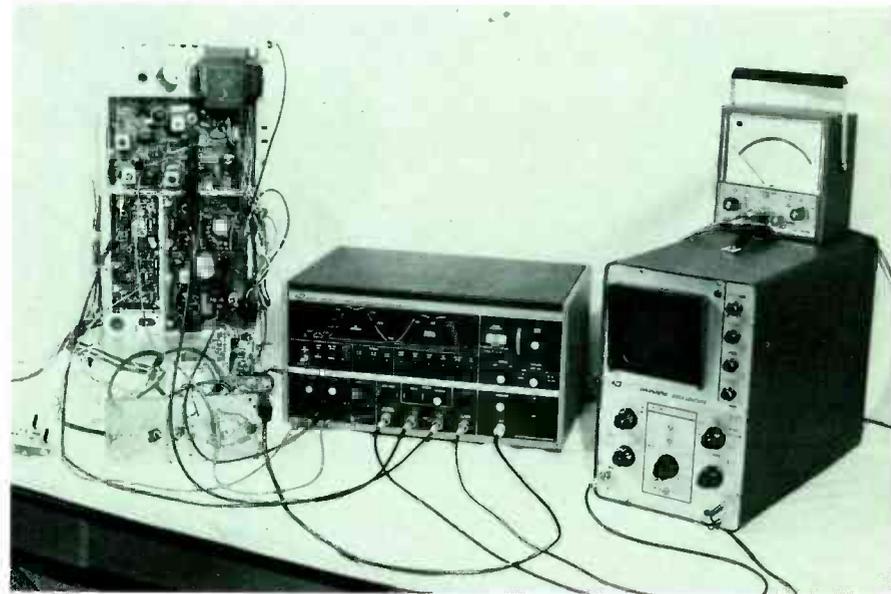


Fig. 1 With modern equipment, sweep alignment is much simpler than it was in the old days, when it took many instruments and a couple dozen connections to get hooked up and ready to view a response curve.

eral little gadgets to do a sweep alignment. My setup had a scope, sweep generator, marker generator, marker adder, VTVM, and dual bias box. It usually took 18 separate connections—and even more for a color alignment. No wonder some technicians hesitated. Hooking up and getting everything adjusted for that first response curve could take half an hour. In all fairness, that's too much time to spend for just a touchup.

And the equipment. Today, the instruments in Fig. 1 are all I need—a scope, a modern TV alignment generator, and a VTVM. Even for color, there are less than a dozen connections to make. Hookup and turn-on time: 10 minutes, if I'm not familiar with the TV chassis. And I don't have to figure out an octopus of interconnections between instruments.

And that brings to mind the problem I used to have with alignment: I needed to know the set, because almost nothing was standard. Now, I can align a strange set al-

most as quickly as I can a familiar one. There are two reasons: One, the instrument hookup is so simplified and standard, all I need is the chassis schematic so I can find the connection points. A layout chart, with the coils marked, is a help but not an absolute necessity. And two, the IF strips and tuners are fairly standard in chassis nowadays. Chroma sections are too, to some extent. You get familiar with standard alignment fairly easily. These factors make alignment much easier.

### Troubleshooting Quick and Easy

But let's not get too far off the track here. This isn't basically an article on alignment. I'm writing about troubleshooting the IF strip.

Nevertheless, it's important that you know how easy TV alignment has become. Why? Because the fastest and most **uncomplicated** troubleshooting method I've ever found for IF stages is based on principles you use in alignment.

You may have to try this method to believe it. If you're like I was a

few years back and avoid anything resembling sweep alignment, you'll find it hard to believe that word "uncomplicated." Really, the word fits. And because this way is so uncomplicated, it's also fast. You can spot almost instantly exactly what coil is bad, exactly which bypass capacitor is open, or exactly what trap isn't trapping. Can you do that with any other method?

Here, in a nutshell, is the secret: You set up a response curve of the IF strip with a sweep generator and scope. Using post-injection markers, you identify any improper peaks or dips by their location on the curve. Knowing the frequency of the bad spot on the curve, you can easily deduce what's causing it.

Think that's difficult? It isn't. Let me prove it's not, by an example. Then I'll tell you how to set up your own gear for a quick look at IF response.

#### The Case of the Dud Decoupler

This TV set came in looking like it needed alignment bad. It had all the ghosts and ringing you see in Fig. 2. No amount of fine tuning could get rid of the multiple images, although it did move them around

a lot. And the sound had some buzz in it that fine tuning couldn't clear up.

Since I've had this modern alignment setup, there's no "getting-out-hooking-up, and turning-on" to do. I keep it connected and warmed up all the time. I just connect the two leads to my scope, and I'm ready to clip them to the chassis. In less than 5 minutes I am looking at a curve showing the response from IF input to video detector.

What I saw in this particular case is the waveform in Fig. 3A. I wasn't sure what the shape should be, so I got out the manufacturer's alignment instructions. I had alignment curves drawn. With the sweep generator connected at the mixer test point, the response curve at the video detector of this set should look like Fig. 3B.

Particularly note the five markers. I activated markers at 39.75, 41.25, 42.17, 45.75, and 47.25 MHz. These are at the adjacent picture, sound, chroma subcarrier, video and adjacent sound points on the overall response curve, respectively. In the generator I use, all these markers are crystal-controlled and ex-

tremely accurate.

Compare the two waveforms of Fig. 3. Note the differences, because they are what is important.

The left side of the curve in Fig. 3A seems okay. It's just about the same as the left side of 3B (the correct curve). The 39.75 adjacent-picture marker is at zero level at the left, and the 41.25 sound marker is in its slot near the beginning of the skirt. The 42.17 chroma subcarrier marker is hard to see on the steep left skirt, but it's there—about halfway up—in both curves.

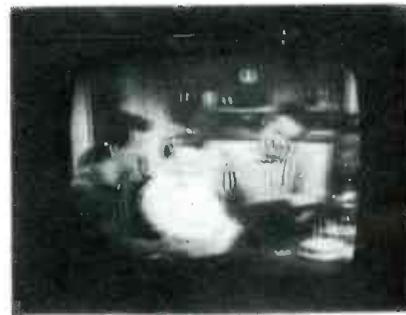


Fig. 2 Typical screen symptom of very bad alignment in the IF strip. Fine tuning usually moves the ghosts around a lot but doesn't clear them up. Sound may have buzz, too.

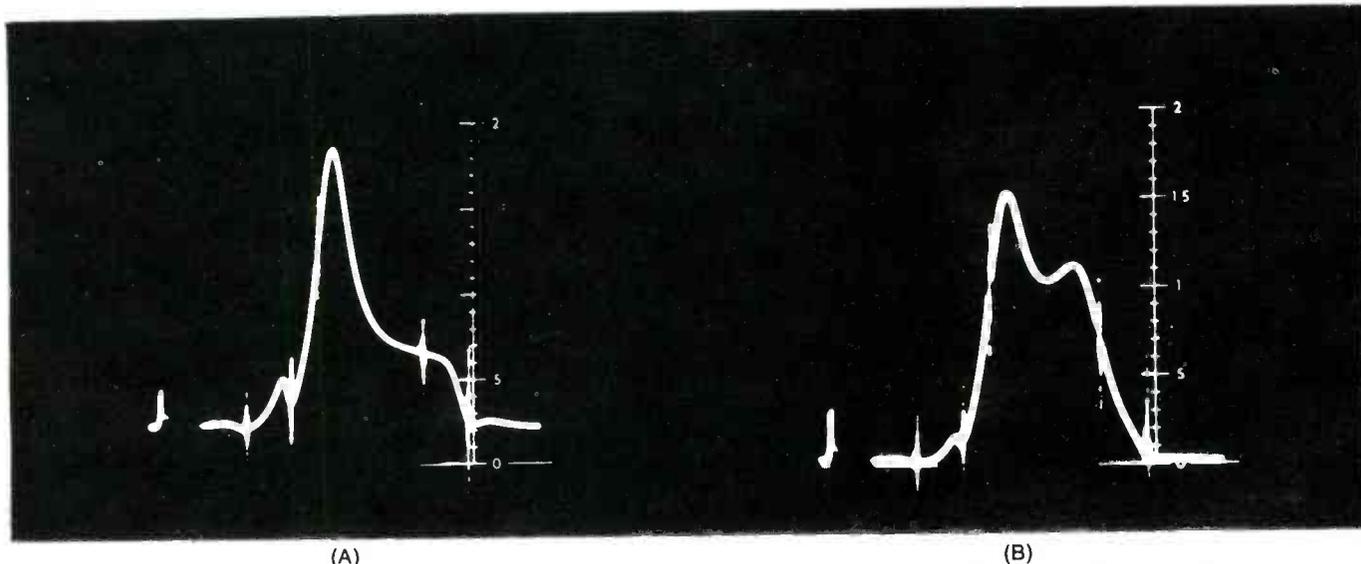


Fig. 3 The waveform at left (A) is the response curve the author saw when the set was first brought into the shop. The curve at right (B) is the correct one, after the trouble had been found and cured.

It's after the curve goes "over the top" that it changes shape. In the normal curve in Fig. 3B, the upper-frequency skirt of the curve is positioned so that the 45.75 video marker is about halfway down it. The right-hand peak is a little down-frequency from the 45.75 marker.

But in the bad curve of Fig. 3A, the response has dropped way down before it reaches the 45.75 marker. The down-frequency peak is no longer there. The only distinct peak remaining is the first one, just up-frequency from the 42.17 marker.

So, what conclusion do you draw from this? Well, for one thing, you can deduce that the IF strip gain is deficient from around 44.0 or 44.5 MHz on up past 45.75 MHz. Since tuned coils peak the gain at different frequencies across the IF response band, chances are one of the coils isn't peaking like it should.

You probably have reasoned that out for yourself. If so, you already have a fair grasp of this unique troubleshooting method.

Now, as I did, carry your reasoning a bit further. It'll save you "twiddling" around with several of the coils.

A schematic of two of the IF stages is drawn in Fig. 4. This is

the popular "stacked" IF. That is, the two tubes are in series for B+. The plate of V1 goes to the cathode of V2 (through T2, R7, and R8). The plate of V2 goes to the 250-volt supply.

As far as IF signals are concerned, the stages are cascaded. Capacitors C1, C2 and transformer T1 couple signal to V1. T2 couples it on to V2. T3 takes it on to the stage that follows. The grid and cathode of V2 are well above ground for B+ voltage, but C6 and C7 hold the bottoms of the T2 windings at ground for IF signals. Capacitors C4 and C9 do the same decoupling job for T1 (with L2) and T3.

Each transformer—often just called "IF coil"—is tuned to a different frequency. That's why this kind of IF strip is called stagger-tuned. Each transformer peaks a portion of the overall IF response. A fourth tuned transformer, beyond the third IF amplifier, isn't shown in this schematic.

The sketch in Fig. 5 shows the responses of T1, T2, and T3 side by side. The heavy line is their combined response. Notice how closely it resembles the curve in Fig. 3B. (The effects of traps L1 and L2 are included in the heavy line but

are not drawn separately.)

In case you're wondering where I got the coil peaking frequencies, it was from the alignment data. The sheet doesn't always label each adjustment by frequency, but you can figure them out by noticing which markers the instructions say are affected by which adjustments.

Since the right side of the curve is affected, the coil **not** doing its job must be T2. The peaking frequency for T2 is 45.0 MHz. There are several possible defects. But you now know the trouble is in the immediate vicinity of T2.

The coil could be badly mistuned by a defect, or just by misalignment. But if it were tuned to some other frequency, there should be some sign of **overpeaking** somewhere else on the curve. So that isn't the trouble in this example.

The coil might be shorted or open. If it was open, however, you'd know by the DC voltage missing on pin 5 of V1. If T2 were shorted, it also would load down the trapping effect of the third winding; the response curve wouldn't look right at the 39.75 marker. Also, the tuning slug for that coil would produce no change in the curve as you adjust it.

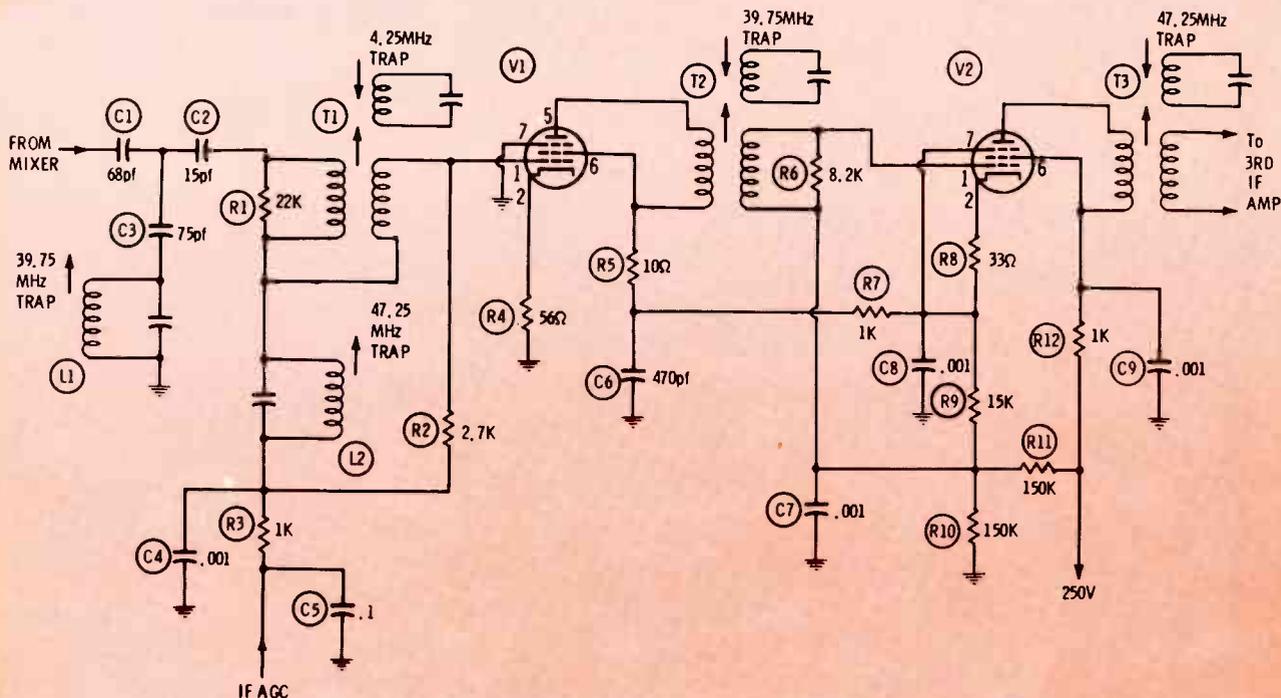


Fig. 4 Part of stagger-tuned IF strip that is used in many TV brands and models. This one is "B+ stacked" version, in which two tubes are in series across B+ line. Cathode and grid of V2 have high positive voltages.

FROM THE COMPANY WHO GIVES YOU  
THE STRONGEST GUARANTEE IN THE BUSINESS

# BUY AN INSTRUMENT. GET AN INSTRUMENT FREE.\*

## SIGNAL TRACER PROBE



Gain 3000 at 2 KHz. Bandwidth 50 Hz to 200 MHz. Z 3500 $\Omega$  to 350 K $\Omega$ . Output 0.3 p-p volts. Noise -45db. Supplied with anti-overload probe tips: Eico PST-2, Kit \$19.95, Wired \$29.95.

## NEW TRANSISTOR ANALYZER



Tests trans-conductance and Beta in and out of circuit. Measures FETs, bipolars, diodes, rectifiers, SCRs, UJTs. Built-in voltmeter, ohmmeter. 50 $\mu$ a taut band meter movement. Eico 685, Kit \$99.95, Wired \$149.95.

## NEW CURVE TRACER



New professional transistor/diode curve tracer enables any general-purpose oscilloscope to display direct readouts of the most meaningful data. Eico 443, Kit \$99.95, Wired \$149.95.

## SOLID STATE COLOR GENERATOR



Standard offset carrier type stable 10-bar display plus precision dots, crosshatch, individual series of V & H lines; gun killers. Feeds to ant. terminals. Portable, battery/AC. Eico 385, Kit \$79.95, Wired \$109.95.

## NEW OSCILLOSCOPE/VECTORSCOPE



DC-8MHz (usable to 10 MHz). 5" flat-face CRT. Sensitivity 12 MV RMS/CM. Negligible relative H & V phase shift. Excellent curve tracer with Eico 443 (below). Eico 465, Kit \$179.95, Wired \$249.95.

## CRT TESTER AND REJUVENATOR



For all B-W & Color Picture Tubes. Each gun of Color Tube measured individually and numerically, provides required gray scale tracking information. Eico 633, Kit \$79.95, Wired \$109.95.

## NEW SOLID STATE SINE/SQUARE WAVE GENERATOR



Provides simultaneous sine and square wave outputs. Covers 20 Hz-2MHz, 5 bands. Max. distortion 0.25%. Rise time at 20 KHz <0.1  $\mu$ sec. Eico 379, Kit \$69.95, Wired \$99.95.

## NEW SOLID STATE FET-TVM'S



AC RMS/DCV: 0-1, 3, 10, 30, 100, 300, 1000V. P-P ACV: 0-2.8, 8.5, 28, 85, 280, 850, 2800V. DC Input Z 11 M $\Omega$ . Ohmmeter 0.2 $\Omega$  to 1000 M $\Omega$ . 4 1/2" 200  $\mu$ A meter. Eico 240, Kit \$59.95, Wired \$79.95. With 6 1/2" meter & AC/DC Current readings.

Eico 242 FET-TVOM, Kit \$69.95, Wired \$94.50.

## TUBE TESTER



Tests all standard tubes plus decals, magnovals, 7-pin nuvistors, popular TV picture tubes. Professional, compact, lightweight, and modest price. Eico 635, Kit \$44.95, Wired \$69.95.

## NEW SOLID STATE SIGNAL TRACER



Output 400mw. Inputs: 1mv RF; 63 mv AF; Hum >60 db below 400 mv. 200  $\mu$ a meter. Provides substitution output Xfmr & spkr. Eico 150, Kit \$59.95, Wired \$79.95.

## THE TECHNICIAN'S CAUSE EICO helps it. With . . .

1. The first and only instruments with the MOST capability-per-dollar. They do more, faster — save you more time, effort, money.
2. The first and only solid state instruments guaranteed for 5 years.
3. Now, in the teeth of inflation, EICO makes your dollars buy even more TOTAL VALUE than ever before.

OUR 25th YEAR. LABORATORY PRECISION AT LOWEST COST.

## \*FREE EICO TRUVOHM™ MULTIMETERS (with purchases as described)



Model 1A1  
1 K  $\Omega$ /V



Model 4A3  
4 K  $\Omega$ /V

After purchasing any instrument on this page from your local EICO Distributor, mail EICO the sales slip, Registration Card and coupon at right. We'll ship you prepaid an EICO Truvohm Multimeter as follows: For each purchase up to \$100, the Model 1A1; for each purchase over \$100, the Model 4A3. Offer expires Jan. 31, 1971. Void where prohibited or taxed.

For latest catalog on EICO Test Instruments, Stereo, EICOCRAFT Projects, Environmental Lighting, and name of nearest EICO Distributor, check Reader Service Card or use coupon.

Circle 18 on literature card

[www.americanradiohistory.com](http://www.americanradiohistory.com)

ES-12 Offer expires Jan. 31, 1971.  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



EICO • 283 Malta Street • Brooklyn, N.Y. 11207

The third possibility is an open C6 or C7. They must keep the bottom ends of the T2 windings grounded for IF signals. If either one opens, there's degeneration in that winding. It can't peak; in fact, it **cuts down** the IF gain at all frequencies, but more so at T2's frequency.

In the set on my bench, C6 was open. It left the primary of T2 more-or-less floating. The transformer couldn't efficiently pass the 45.0-MHz portion of the sweep signal, so the curve at that point was reduced from normal.

Just for added information, Fig. 6 shows what the response looks like if C7 opens. This defect causes the same degeneration at the 45.0-MHz portion of the curve. The drop-off isn't quite as bad, but it's enough to make correct alignment impossible. And it produces the same screen symptom you saw in Fig. 2.

### Setting Up Your Own Equipment

You know how much trouble it would be to find that bad capacitor ordinarily. Once you saw the symptom, you'd probably check around the tuner. Finally, you'd spend a lot

of time messing around with all the coils.

Eventually, you might notice T2 doesn't tune right. But even if you do, you might be tempted to replace the coil. And, of course, a new one would tune just as poorly. So you're better off by far with the visual troubleshooting method which uses the sweep setup.

You can do this special troubleshooting with **any** sweep alignment equipment. However, if you're not using post-injection for the markers, you ought to consider updating your instrument lineup. For years I used a marker adder, which is just a complicated way of doing the same thing: injecting the marker **after** the response curve has already been developed. The advantage is that the marker doesn't distort the curve, no matter how big you make it.

Your marker generator must be fairly accurate. That's why I like crystal-control . . . no fumbling around with the dials. And if you can show several markers at a time, you can visualize the frequency positions better. But you can manage with a single-marker, tunable generator. Just set the dial at each frequency, one at a time, and remem-

ber that marker's position on the curve.

No matter what instruments you use, I have one strong suggestion. As I said earlier, hooking them together is an aggravation as well as a time-waster. And they need to be warmed up 15 minutes, too. My suggestion: Keep your sweep-alignment gear all hooked up and turned on, at least on standby. It's also better for the instruments, because they are not alternately hot and cold.


If you only have one scope, it's okay to keep it separate for regular use. There are only two connections to make when you connect it into the sweep alignment setup, anyway.

Hooking the instruments together is a minor detail. If you haven't done it recently, the instruction manuals will remind you what goes to what. And if you're fortunate enough to have modern equipment, there's very little hookup to be done.


### Analyzing Curve Shapes

If you hesitate to start using this professional troubleshooting method for IF's, it's probably because you haven't had any experience figuring out wrong curve shapes. This is something that usually is not covered in electronics school. You are taught only to recognize a **correct** curve when you get it.

I want you to feel more at home with this unique method. So, in the next issue, I'll take you through several actual cases that were solved using the sweep alignment method. In the process, you'll come to understand: (1) How to determine which coil should peak at what frequency, (2) how to recognize a response curve that's not shaped right, and (3) how to reason out what's wrong with the curve. ▲

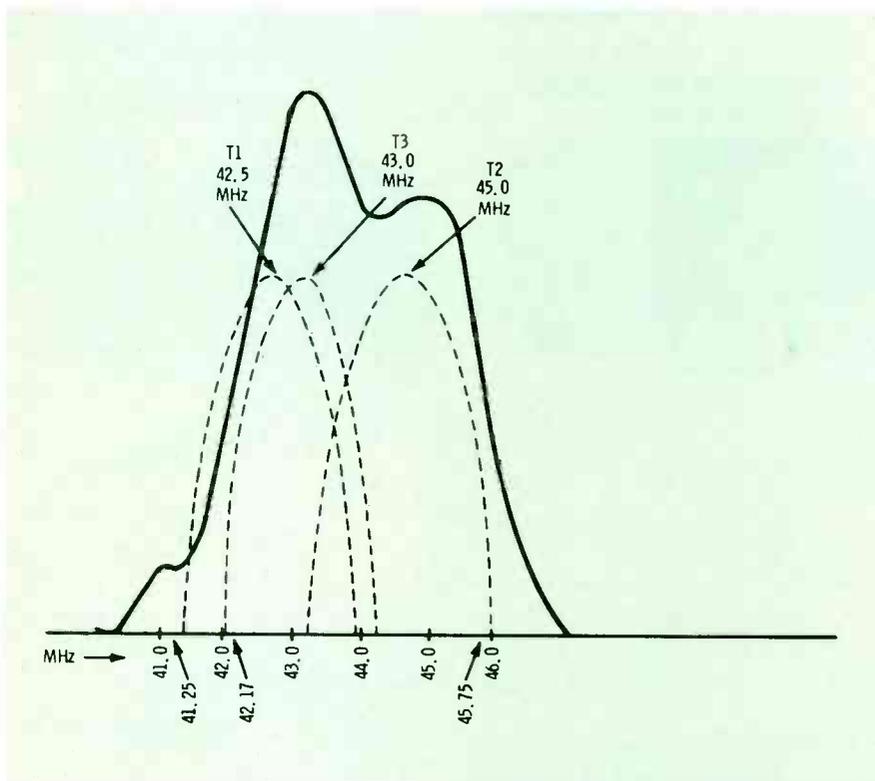

**Fig. 5** Individual responses of stagger-tuned IF transformers combine to form IF response curve. Heavy line is the net response traced at all frequencies in the IF passband. It is the same curve you see traced by the sweep generator and scope in Fig. 3B.

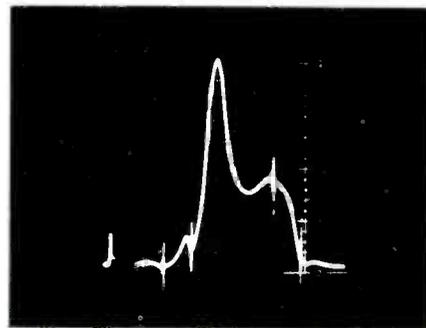

**Fig. 6** This is what the response curve of Fig. 3B would look like with decoupling capacitor C7 open; degeneration isn't quite as bad as with C6 open (Fig. 3A).


IT REALLY ISN'T CHRISTMAS WITHOUT THEM.



Use Christmas Seals.

It's a matter of life and breath. †

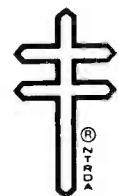Fight emphysema, tuberculosis, air pollution.



Space contributed by the publisher as a public service.

# The All-Electronic Tuner

by Bruce Anderson

Until recently, all television VHF tuners had one thing in common: A shaft had to be rotated to change channels. All-electronic tuning has changed this.

In the following paragraphs we will discuss the actual process by which a channel is selected mechanically, point out some of the inherent deficiencies in the mechanical method, and then consider an alternative—electronic tuning.

The concepts of electronic tuning are still being developed, and, undoubtedly, new refinements will be forthcoming; however, one such system has been in existence for the past year in the RCA CTC47 chassis. While a consideration of this system might be principally of academic interest, since it was a

limited-production design employed in a "prestige" receiver, it does merit some attention as a forerunner of things to come.

## The Conventional Tuner

At the present state of the art, the superhetrodyne receiver is considered to be the only type of receiver suitable for television reception. For this reason, all tuners are basically similar. As illustrated in Fig. 1, the usual tuner configuration employs an RF amplifier, a mixer, and a local oscillator as its essential elements. The four tunable circuits are the input and output circuits of the RF amplifier, the input of the mixer, and the tank circuit of the local oscillator. The conventional tuner also has an input-matching circuit, or balun, which matches the impedance of the transmission line to the input impedance of the tuner; and an IF rejection filter, which pre-

vents the entry of IF radiation into the RF amplifier; and a tuned circuit which develops the output voltage and matches the mixer to the IF strip.

To the servicing technician, the four tunable circuits might appear to be incremental parts of the RF amplifier, mixer, and local oscillator; however, their functions actually are quite separate from the functions of the active devices themselves. In this discussion, the RF amplifier, mixer, and local oscillator can be considered simply as black boxes, while the tunable circuits themselves are the real interest.

The tunable circuits take two forms. In some tuners a separate resonant circuit is used for each channel; in others an inductance is tapped at twelve points to make it resonant at each of the channel frequencies. (A total of 13 frequencies is required, one for each VHF chan-

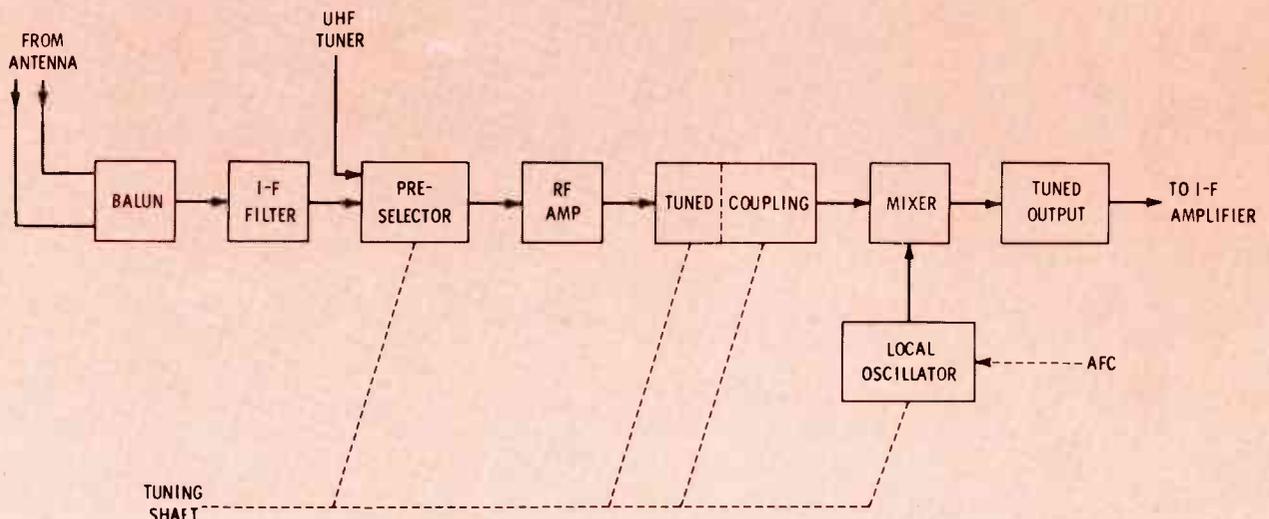


Fig. 1 Location of the tunable circuits in a typical conventional color television tuner.

**Elimination of mechanical switching of signal circuits has been accomplished by replacing the bulky "mechanics" of conventional tuners with diodes, which are switched electronically.**

nel and one for the output of the UHF tuner, which is normally at the IF frequency.) Regardless of which type of resonant circuit is used, a four-function, 13-position switch is required to select the proper tuner circuits.


It might come as a surprise to find that the shaft and knob of the tuner have three distinct functions. The first of these is to provide a link between the switches themselves and the hand of the individual who operates the receiver. This is called the "interface" function. The

second function is to hold the switches in the position selected after the operator removes his hand. This is the "memory" function. Third, the shaft or knob is fitted with an indicating device to tell the operator which channel has been selected. This is the "indication" function. In the conventional tuner, these functions are seldom of any interest, but in an electronic channel-selection system, each function must be performed by an operating system, or the receiver cannot function.

### The Electronic Switch

To change from mechanical to electronic tuning, it is necessary to substitute electronic devices for each of the four switches which select the taps of the tuned circuits. For the sake of simplicity, the arrangement of Fig. 2 shows only enough of a tuning system to allow the selection of two channels. Additional banks of diode switches are required for each remaining channel.

In Fig. 2, the switch, S1 could be a double-pole, two-position switch. If this system of tuner con-

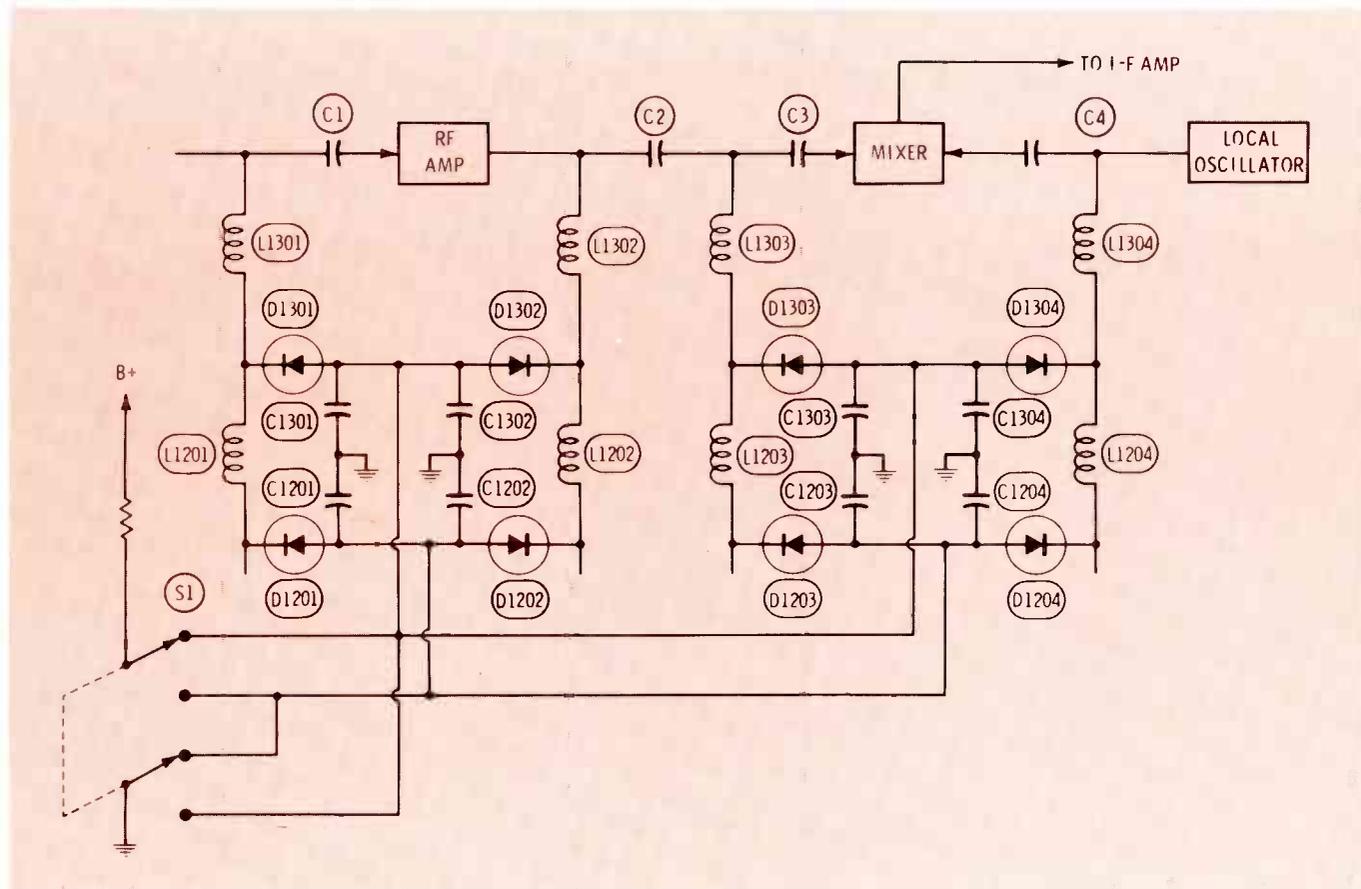

**Fig. 2** Partial schematic of the electronically controlled tuner, showing the components for channels 12 and 13. An additional set of diodes and capacitors is used for each of the other channels.

trol were to be used, naturally, it would have thirteen positions, one for each channel. In the position shown, positive voltage is fed to the anodes of each of the 1300-series diodes, biasing them into conduction. The result is that the impedance of these diodes is made very low, effectively placing the lower ends of the 1300-series coils at RF ground through the 1300-series capacitors. This produces the same result as having a closed mechanical-switch contact in the same location as each diode.

Since the 1300-series diodes are forward biased, whatever voltage is applied to their anodes also appears at their cathodes (less the .7-volt barrier drop). The positive voltage is conducted to the cathodes of all the other diodes, 1201, 1101, 1001, etc., holding these diodes at cutoff. The grounding section of S1 is essential; without it, the anodes of the other-channel diodes would "float". If these diodes were allowed simply to "float", their inter-element capacitance would vary, causing the tuning of the resonant circuits to drift. Naturally, this is true only of those diodes in chan-

nels higher than the one selected; the others are isolated from the resonant circuits by the conducting, on-channel diodes.

To equip a tuner having electronic channel selection with a fine-tuning knob is illogical to the engineer; to the prospective buyer, it would be absurd. Unfortunately, a conventional automatic fine-tuning circuit is inadequate in the electronic tuner.

All present-day AFT circuits depend on a variable capacitance connected across the oscillator tank to maintain the correct frequency. A simplified circuit is illustrated in Fig. 3. If the local oscillator tends to drift, the frequency of the video carrier from the mixer begins to shift. This causes an error voltage to be generated in the discriminator. The error voltage changes the effective capacitance of the diode and returns the local oscillator tank to the correct resonant frequency.

In a conventional tuner, the user expects to fine tune the local oscillator into the operating range of the AFT system when the need arises; in an electronic system he would not. Because of this, the

range of the AFT system of the electronic tuner must be broad enough to preclude the oscillator ever drifting outside the range of correction, without sacrificing so much gain that tuning will be "sloppy" on some channels.

A characteristic of any variable-capacitance frequency control is that a given amount of capacitance change produces much more frequency change if the operating frequency is increased. Consequently, a given amount of corrective voltage will have much more effect on the high channels than it has on the low channels. In effect this causes the loop gain of the AFT system to increase as the operating frequency increases, making it difficult to design an AFT-controlled oscillator which will perform well on all channels.

The solution to this problem is to use separate local oscillators for the high-band and low-band channels. The circuit in Fig. 4 shows how this is done. By using the diode control voltage as the power source for the two local oscillators, band and channel are selected simultaneously.

Assume that channel 13 has been selected. The channel 13 diode is forward biased, placing the end of L1304 at ground through the capacitor connected to the anode of the diode. The remainder of the tapped inductance is out of the RF circuit, but DC power for the collector of Q1 is supplied through these windings, the channel-7 diode, R1, and L1.

If channel 9 were selected, the RF ground would still be supplied to the transistor through the balance of the inductor.

If a low-band channel were to be selected—channel 5, for example—Q1 no longer would be energized, but Q2 would be. The tuner circuit would consist of that portion of the inductor between the channel-5 diode and the collector of Q2; the balance of the inductor would provide the DC path for collector power. During UHF reception, a local oscillator is not required, so neither Q1 nor Q2 is energized.

Automatic frequency control of


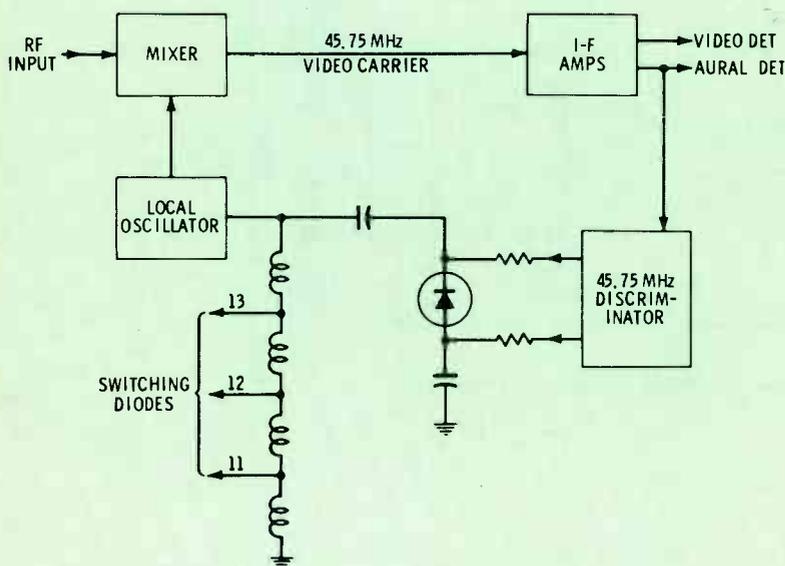


Fig. 3 The basic automatic-fine-tuning (AFT) loop.

# Sams Books

famous for

## Servicing Know-How

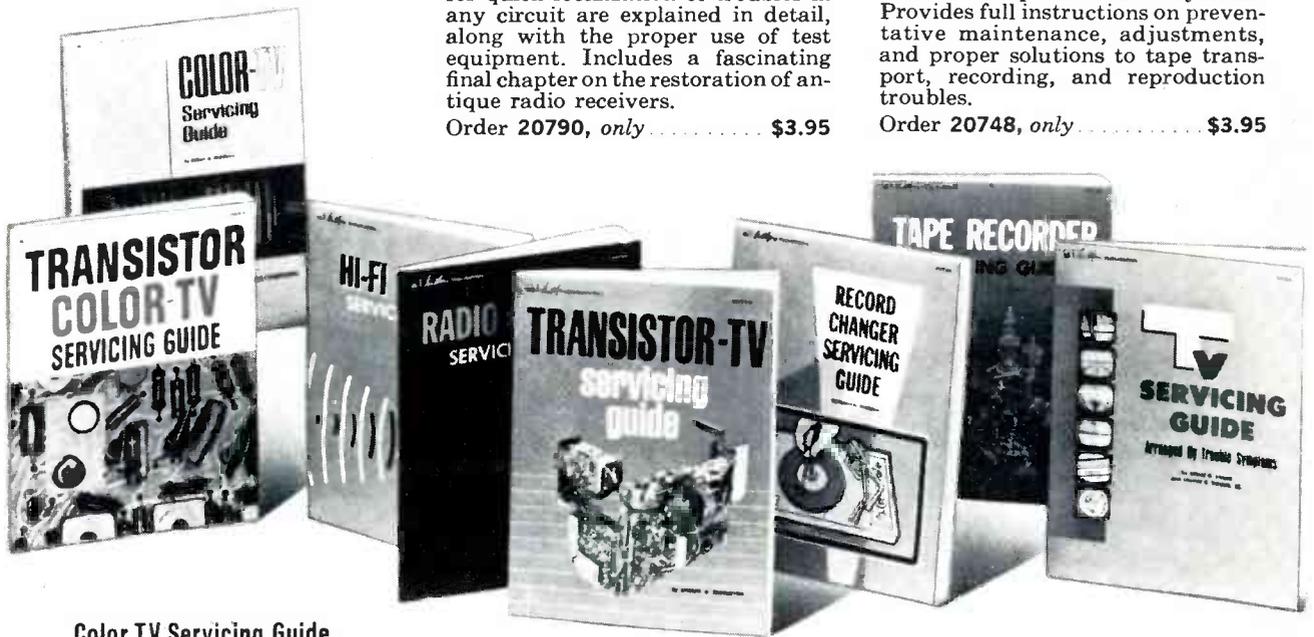

### Hi-Fi Stereo Servicing Guide

by ROBERT G. MIDDLETON. A complete guide to effective servicing of a-m tuners, fm tuners, stereo-multiplex units, and audio amplifiers (all components, except record players and tape recorders). Includes hi-fi speaker system installations, trouble localization, and overall system evaluation. Also gives testing methods for verifying performance.  
Order 20785, only ..... \$3.95

### Record Changer Servicing Guide

by ROBERT G. MIDDLETON. Presents the general principles of record changer design, followed by a detailed analysis of the working parts of changer mechanisms. Explains adjustment and lubrication procedures, diagnostic techniques for operating troubles, and the corrective measures required to remedy them. This is a thoroughly practical guide.  
Order 20730, only ..... \$3.95

### Radio Receiver Servicing Guide

by ROBERT G. MIDDLETON. Presents the professional technician's approach. Covers troubleshooting and repair of a-m radio receivers, both solid-state and tube type. Methods for quick localization of troubles in any circuit are explained in detail, along with the proper use of test equipment. Includes a fascinating final chapter on the restoration of antique radio receivers.  
Order 20790, only ..... \$3.95

### Tape Recorder Servicing Guide

by ROBERT G. MIDDLETON. Tells how to repair tape recorders profitably. Thoroughly explains the principles and characteristics of magnetic recorder circuitry, describing the various components and systems. Provides full instructions on preventative maintenance, adjustments, and proper solutions to tape transport, recording, and reproduction troubles.  
Order 20748, only ..... \$3.95

### Color TV Servicing Guide

by ROBERT G. MIDDLETON. Shows how to apply fast troubleshooting techniques to color-TV repair using the famous Middleton system based on analysis of trouble symptoms illustrated by actual full-color picture tube photos. Clearly-written text explains possible trouble causes and diagnostic procedures. Final chapter explains in detail how to use color-bar generator.  
Order 20358, only ..... \$4.25

### Transistor Color-TV Servicing Guide

by ROBERT G. MIDDLETON. Clearly explains the basics of the various circuits used in transistor color-TV receivers, including the most recent developments. Shows how to apply proper troubleshooting procedures based on analysis of trouble symptoms. Includes a wealth of circuit diagrams, charts, and picture tube and waveform photographs.  
Order 20693, only ..... \$4.50

### Transistor-TV Servicing Guide

by ROBERT G. MIDDLETON. Second edition. Updated to provide full information on latest circuitry and many additional new test procedures. Clearly explains general transistor circuitry and servicing techniques and then proceeds through the receiver, section by section, describing various picture and or sound trouble symptoms and their remedies.  
Order 20696, only ..... \$3.95

### TV Servicing Guide

by LESLIE D. DEANE and CALVIN C. YOUNG, JR. This is the famous guide used by more than 100,000 service technicians. Shows you how to apply quick troubleshooting procedures based on analysis of trouble symptoms illustrated by picture tube photos. Fully explains possible causes for each trouble symptom and then details proper diagnostic and repair procedures.  
Order 20361, only ..... \$3.25

### HOWARD W. SAMS & CO., INC.

Order from your Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc., Dept. ES-120 4300 W. 62nd St., Indianapolis, Ind. 46268

Send books checked at right. \$\_\_\_\_\_ enclosed

Send FREE 1970 Sams Book Catalog

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

- 20785
- 20730
- 20790
- 20748
- 20358
- 20693
- 20696
- 20361

Circle 20 on literature card

the oscillators is performed by the two varactors, VAR 1 for Q1 and VAR 2 for Q2. Each of these will have approximately the same amount of capacitance change for a given amount of control voltage; however, the two 2.2-pf capacitors in series with VAR 1 make the total variation in capacitance of this circuit considerably less than that produced by the swing of VAR 2 and its two 4.7-pf capacitors. At the centers of the upper and lower bands, the ratio of frequency change to voltage change is about the same for both oscillators.

### Merits of the Tuner

Aside from the fact that the electronic tuner has appeal to the consumer because of its ease of operation, quiet operation, rapid action, etc., it also has advantages from the engineering point of view. Because

there is no mechanical connection between the tuner and the control for it, the location of the tuner can be anywhere inside the cabinet. There are no more gear trains, detents, indicator drums, mounting assemblies, etc. It is entirely possible that, sometime in the not-too-distant future, the tuner will become simply another part of the main chassis.

Another advantage of the electronic tuner is that the actual switching of signal voltages is done without a mechanical device. Dirty switch contacts in the tuner have been a constant servicing headache since television was introduced. Obviously, the insides of the switching diodes cannot get dirty. Even if some type of mechanical switch were to be used to control the tuner, it would interrupt only a control voltage, not RF signals.

### Interfacing

The simplest interface between an electronic tuner and the operator is a 13-position switch with two poles, one which energizes the diodes of the selected channel, and one which grounds the other 12 sets of diodes. The system would have the advantages of allowing the tuner to be located wherever it is convenient and of switching only a control voltage instead of RF signals. Operation of the switch could be reasonably rapid and quiet, although never approaching the limitations of the tuner itself, and a drive motor could be used for remote control.

By substituting an all-electronic control switch, the speed of operation can be increased to the point that channel selection appears to be instantaneous, and the system is completely silent. Of greater significance, the motor, always an undesirable feature in remote-control systems because of original cost as well as servicing problems, can be eliminated. The electronic system described here incorporates all these advantages, with the exception of cost. This is the first system to be produced; it is reasonable to expect that future designs will be simpler and more economical, just as the television receiver has become simpler and more economical over the years.

### Summary

An electronically controlled tuner is much the same as a mechanically operated tuner, except that diodes are used to switch the tuner circuits. This has several advantages, including freedom of location of the tuner, no possibility of dirty or corroded switch contacts in the RF circuitry, and the aesthetic appeal of rapid and silent channel selection, limited principally by the control systems which might be used in conjunction with the tuner.

In the next of this series, the control system for the electronically controlled tuner of the RCA CTC47 chassis will be discussed. In preparation for that description, there will be a short discussion of binary numbers and their application to logic circuits. ▲

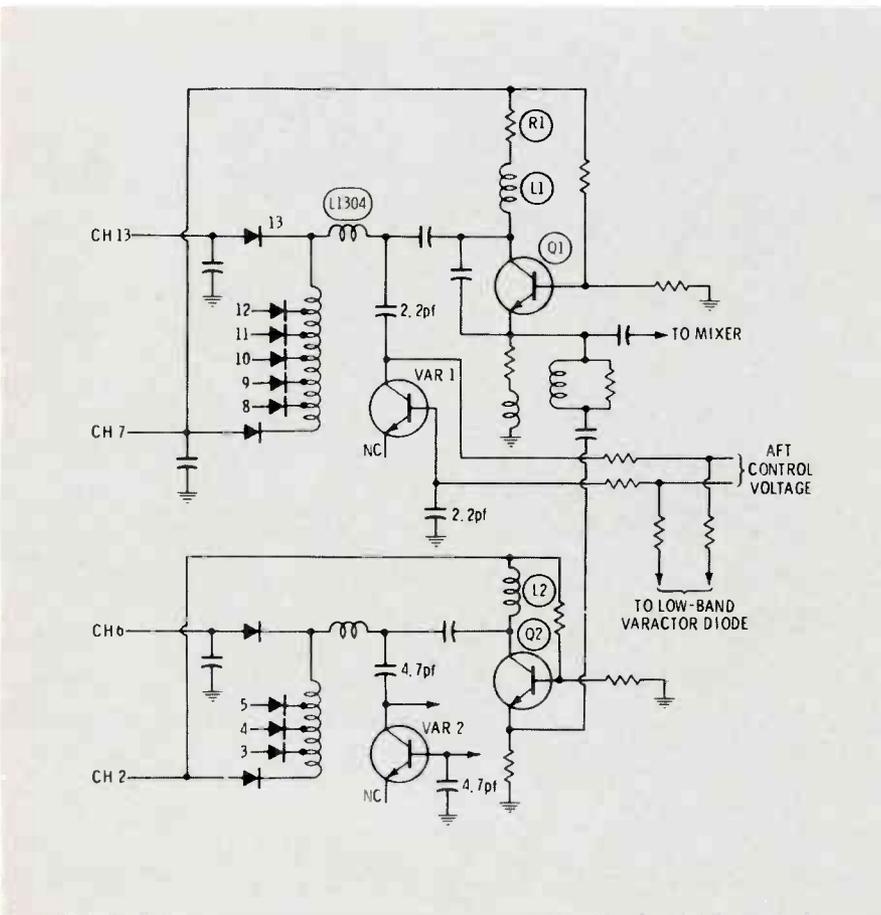


Fig. 4 The dual local-oscillator configuration, which is necessary to insure optimum AFT performance on all channels.

IT REALLY ISN'T CHRISTMAS WITHOUT THEM.



Use Christmas Seals.  
It's a matter of life and breath.

Fight emphysema, tuberculosis, air pollution.



A-1 Communications Supply Co.  
 AB&B Electronics  
 A F Electronics Parts  
 A G Radio Parts Co.  
 A & J Distributing, Inc.  
 A & N Bella Electronics  
 A & W Electronic Supply  
 Abbot Electronics Co.  
 Acro Electronics Dist.  
 Adleta Electronics Co.  
 Admiral Corporation  
 Advanced Electronics  
 Aikins Electronic Supplies, Inc.  
 Akron Electronic Supply  
 Wm. B. Allen  
 All State Electronics  
 Alltronic Distributors  
 Almo Radio Co.  
 Alpha Electronic Distributors  
 Alpine Electronics  
 Cass Altshuler  
 Amarillo Hardware  
 American Distributing  
 American Electronics  
 Amerling Co.  
 Anahem Electronics  
 Anchor Electronics  
 Anderson Electronic Supply  
 Ange Electronics  
 Appleton Radio Supply  
 Arby Electronics  
 Arlington Electronic Distributors  
 Associated Radio Distributors  
 Atlas Electronics  
 Atkinson & Smith  
 B B & W, Inc.  
 B & S Electronics  
 Badger Electronics  
 Baldwin Part Electronics  
 Ballard Supply  
 Barstam Electronics  
 Burkner Higbee, Inc.  
 Burma Radio  
 H. R. Bastford Company  
 Bashum-Christiansen, Inc.  
 Bay Electronics  
 C. E. Beckman Company  
 Belco Distributors  
 Bell Radio  
 Berger Electronics  
 Black Hills Electronics  
 Bluff City Distributing  
 Bond Radio Electronics, Inc.  
 Bondurant Bros.  
 Bore Electronics  
 Jess Bowman & Associates  
 Braid Electronics  
 J. Brandwin Company  
 Bristol Distributing Co.  
 Brooks Electronics  
 Brookshire Radio Supply  
 Bruno New York, Inc.  
 Brutonics Communications  
 Buff's Electronics  
 G. & W. Burkin Electronics  
 Burma Radio  
 Burstein-Applebee Company  
 Byron's Radio & TV Wholesale  
 C R T Electronic Supply  
 Cand S Electronics  
 California Radio & TV Supply  
 Cam Electronics Dist. Corp.  
 Camden Distributing  
 Cantrell Wholesale Products  
 Capewide Electronics  
 Capitol Electronics  
 Capital Electronics, Inc.  
 Capital Radio  
 Carl's Electronics  
 Carlton-Bates Company  
 Carmichael Wholesale Supply  
 Carolina Radio Supply Company  
 Carson Electronics  
 Carter Supply  
 Central Distributors  
 Certified Electronics  
 Chief Electronics  
 Clark Radio Supply  
 Cole Distributors  
 Collins Company  
 Color Vision Electronics  
 Columbia Radio & Supply  
 Commercial Distributors  
 Consumer Electronics  
 Joe Coomes Dist.  
 Corr & Johns  
 Covington Distributing  
 Craft Radio  
 Crescent Electronics  
 Cumberland Electronics  
 Curle Radio  
 D & H Distributing  
 D & M Electronics  
 D & S Electronics  
 Dale Electronics  
 Dalis Radio  
 H. L. Dalis, Inc.  
 Deal Tron Electronics  
 Dean's Electronics  
 B. J. De Jarant Wholesale Co.  
 Dell Electronics  
 Del Padre Supply  
 Denison Supply  
 Distributors TV Service  
 Dixie Radio Parts  
 Dow Electronics  
 Dugger Electronics  
 A. Dukis Appliance Dist.  
 J. V. Duncombe Electronics  
 Dunlap Electronics  
 E D C Electronics  
 E S I  
 Eastco  
 Eastern Radio  
 Eburger Electronics  
 Edisco  
 Bill Erger  
 El-A-Company  
 Electronic Equipment Co.  
 Electric City  
 Electron Sales  
 Electronic Center  
 Electronic City  
 Electronic Communication  
 Electronic Components  
 Electronic Distributors Corp.  
 Electronic Equipment  
 Electronic Materials  
 Electronic Parts Co., Inc.  
 Electronic Service Supply  
 Electronic Supply Co.  
 Electronic Tubes  
 Electrotex  
 Elliott Electronics  
 Emerald Electronics  
 Emerson Dumont Southern Cal.  
 Emerson-Midwest

Emerson-Northwest  
 Emerson Radio of N. E.  
 Emerson Radio of Pa.  
 Emerson Radio of Ohio  
 Emerson TV of Indiana  
 Emerson of W. Pa., Inc.  
 Empire Sales  
 Emco Electronics  
 Engleman Electronics  
 Erie Electronics  
 Euclid Radio  
 F & M Electronics  
 Ferguson Electronics  
 Fidelity Northwest, Inc.  
 Fisher Electronics  
 Fissett's Electronics  
 Fleming Supply  
 Forbee's Electronics  
 Fordham Radio  
 Fox Radio Parts  
 Frances Electronics  
 Frankel Co.  
 Freck Radio & Supply  
 Frontera Electronics  
 Ft. Wayne Electronics  
 Fullers Sound Electronics  
 General Electronics  
 General Radio

Main TV Supply  
 Mannfred Electronics  
 Mar Vac Electronics  
 Marcus & Klausner  
 Marietta Radio & TV Supply  
 Martin Distributing  
 Masine Electronics  
 Master Electronics  
 Albert Mathias Co.  
 May Electronics  
 May & Jackson Dist.  
 Melville Radio Corp.  
 Mesco Electronics  
 Metronix - Detroit  
 Midland Specialty  
 Mid-Ohio Electronics  
 Mid State Supply  
 Mid State Radio  
 Midwest Electronics  
 Miller Jackson  
 Millers Electronic Supply  
 Missouri Cable Co.  
 Mitchell Electronics

Ralph's  
 Randolph, Hale & Matthews,  
 Randolph & Parks, Inc.  
 Randolph & Rice  
 Rankin & Houser  
 Ritec Company  
 Risher Electronics  
 Reed Radio Supply  
 Rein Distributors  
 Remcor Electronics  
 Resco Electronics  
 Rim Electronics, Inc.  
 Risher Electronics  
 Robertson Electronics  
 Rodefelf Co., Inc.  
 E. A. Ross & Co.  
 Round-Up Electronics  
 Route Electronics  
 L. K. Rush Co.  
 Ryan Supply Co.  
 S S Electronics  
 Saco Electronics  
 Santa Cruz Electronics  
 Sawyer Electronics  
 Servex Electronics  
 Seyberts Radio Supply  
 Sherwood Distributors  
 Shields Electronics  
 Shuler Electronics  
 Signal Center  
 Signal Supply Co.  
 Silberne Radio  
 Skyline Electronics  
 Smith Electronics  
 Soundco Electronics  
 Southeastern Electronics  
 Southern Electronics Corp.  
 Southwestern Wholesale  
 Southern Radio  
 South Hills Electronics  
 Southside Distributors  
 Specialty Distributing  
 Standard Electronics  
 Standard Parts  
 Standard Supply  
 Starr's Electronics  
 State Electronics  
 Sterling Electronics  
 A. T. Stewart  
 Stoddard Supply  
 J. L. Stone Co.  
 Stotts-Friedman Co.  
 Stuart Electronics  
 Suddreth Electronics  
 Sunland Supply  
 Superior Electronic Parts  
 Superior Picture Tube  
 Swan Electronics  
 Sylvania Electronics  
 TV Specialists Co.  
 TV Parts, Inc.  
 T V Wholesale Supply  
 T & W Electronics  
 Edwin E. Taylor  
 Teague Electronics  
 Tee Vee Supply  
 Television & Electronic Supply  
 Television Parts  
 Television Radio Parts  
 Television-Radio Supply  
 Television Supply  
 Ward Terry & Co.  
 Three-Way Electronics  
 Thunderbird Electronics  
 Torrance Electronics  
 Triangle Electronics  
 Trice Wholesale  
 Tri State Electronics  
 Trojan Electronic Supply  
 The Tube Mart  
 Frank Uffer Co.  
 U. S. Radio & TV Supply  
 Union Electronics  
 Union Supply  
 United Electronics  
 United Radio & TV  
 United Teltronics  
 Universal Components  
 Vidco Electronics  
 Sid Wagner's  
 Walder Electronics  
 Walck's Electronics  
 Walkers Radio  
 L. B. Walker Radio Co.  
 Warren Radio  
 Walco, Inc.  
 Wedemeyer Radio  
 Westchester Electronics  
 Wescon Electronics  
 Western Electronics  
 Westside Electronics  
 David White  
 Wheelhead Radio  
 Wholesale Electronics  
 Wible Radio Supply  
 Wicks Radio  
 Wilco Radio Distributors  
 H. A. Williams  
 Wilkinson Bros. Co.  
 Wise Radio  
 Witmal Electronics  
 Womack Co., Inc.  
 Woodland Electronics  
 Wesco  
 Yonkers Electronics  
 Young Bros. Electronics  
 Zenith Radio

# BLUE STUFF IS IN GOOD COMPANY

Genesee Radio  
 Geophysical Supply  
 Giant Electronics  
 League Electronics  
 Glen Electronics  
 Goldcrest Electronics  
 Grace Electronics  
 Guaranteed Maintenance  
 Gunter Wholesale  
 Hesco Supply  
 Halley Electronics  
 Hamburg Bros.  
 Hamilton Electronics  
 Handley Electronics  
 Harco Electronics  
 Hargis Austin  
 Hatry Electronics  
 Hawk Electronics  
 E. A. Helwick Electronics  
 Hemco Radio  
 Henshaw TV Supply  
 Hialeah Electronics  
 Hollander Company  
 Holt Electronics  
 Hooper Electronics  
 Hope Electronics  
 Houston Electronics  
 Howard Electronics  
 Howe Electronics  
 Hughes Supply  
 Hurley Electronics  
 Huston Electronics

Mobile Electronics  
 Modern Electronics  
 Monmouth Radio Supply  
 Matronics, Inc.  
 Morley Bros. Dist. Co.  
 Morris Electronics  
 Morris Electronics of Rochester  
 Morris Electronics of Syracuse  
 Morrison's Radio Supply  
 Morton Supply Co.  
 Moyer Electronics  
 National Radio  
 N. H. Electronics  
 Newark-New Orleans Elect.  
 Nidasco, Inc.  
 Norcal Electronics  
 Norman Electronics  
 Northeastern Radio  
 North Pacific Supply Co.  
 Northwest Distributors  
 Northwest Radio Supply  
 Norwest Electronics  
 Nuvo Electronic Co.  
 Oakley Wholesale, Inc.  
 O'Donnell Electronics  
 Ohio Radio Parts  
 Ohio Valley Sound  
 Oline Electronics Supply  
 Opelousas Radio  
 Orvac Electronics  
 Oxibow Electronics  
 Pacific Radio  
 Pacific Teletronics  
 Pan American Electronic Co.  
 Payless Wholesale Electronics  
 Peerless Electronics  
 Pelican Electronics

and here are some of the good  
 companies where you can get it!

Hutch & Son  
 Hygrade Electronics  
 Industrial Electronics  
 Inland Electronics  
 Interstate Electronics  
 John Iverson Company  
 J & B Electronics  
 J & M Electronics  
 J & S Electronics  
 Johnson Electronics  
 Jackson Distributors  
 Jason Electronics  
 Jayso Electronics  
 Jenkins Supply Co.  
 Jersey Electronics  
 Johnson Electronic Supply  
 Jordan Electronics  
 Joseph Electronics  
 Kass Electronics  
 Kaseo Electronics  
 Robert Kay Co.  
 Kearns Electronics  
 Keith Electronics  
 Kellip Disc Electronics  
 Keith Electronics  
 Kentron Corporation  
 Kentucky Electronics  
 Kiesub Corporation  
 Kimball & Stark Electronics  
 Kinde Distributing Co.  
 Klausper Electronics  
 Knight Distributors  
 L. M. Electronics  
 L & M Sales  
 L M L Distributing Corp.  
 L & S Electronics  
 Lake Charles Electronics  
 Land Electronics  
 Laurel Electronics  
 Lavender Distributing  
 Lazar Electronics  
 Leader Electronic Dist.  
 M. Lefl Radio  
 George Lehtleiter & Co., Inc.  
 Lektrotron, Inc.  
 Lifetime Radio  
 Lima Radio  
 Aaron Lippman  
 Long Island Electronics  
 Long Distributing Co.  
 Lowe Electronics  
 Lurtz Electric  
 Lykes Financial Corp.  
 McAllen Radio  
 McChung Appliances  
 McCulloch Electronics  
 R. P. McDavid Co.  
 McGeer Radio  
 McNichol, Inc.  
 McWhorties Weaver & Co.  
 M & M Electronics  
 M & R Electronics  
 Main Line Distributors

Peninsula Electronic Supply  
 Penn Electronics  
 A. A. Peters  
 Philadelphia Electronics  
 Philco Parts Co.  
 Philco-Ford Corp.  
 Pilgrim Electronics  
 Pioneer-Standard Electronics  
 Poe's Electronics  
 G. M. Popkey Co., Inc.  
 Precision Electronics  
 Pringle Electronics  
 Purchase Radio Supply  
 RCA Victor Dist. Co.  
 Radio Distributing Co.  
 R K Distributing Co.  
 R P C Electronics  
 R & R Electronic Supply  
 R S L Distributors  
 Radio & Appliance Dist., Inc.  
 Radio Electric Supply  
 Radio Electronic Equipment  
 Radio Electronic Service Co.  
 Radio Equipment Co.  
 Radiolab, Inc.  
 Radio Maintenance Supply  
 Radio Parts, Inc.  
 Radio Supply Co.  
 Radio Supply & Engineering  
 Radio Supply Co.  
 Radio & TV Essentials  
 Radio TV & Refrigeration

## test equipment report

**High-Voltage Probe**  
 Eico announces the Model  
 HVP-5 high-voltage probe.



The HVP-5 reportedly measures voltage up to 30,000 volts with complete safety, and because it has a built-in voltmeter, eliminates the need for additional bulky equipment. Special barriers isolate the high-voltage tip from the probe handle and meter.

The HVP-5 sells for \$22.95, wired.

Circle 50 on literature card

### CRT Tester/Rejuvenator

B & K has announced release of the new Model 466 CRT Tester/Rejuvenator for b-w and color picture tubes. The 466 test CRT's for opens, shorts or leakage between elements, and rejuvenates guns and repairs shorted or leaky tubes.

Key CRT elements are connected to test points, with all others shorted to ground; this reportedly provides

If we've left anyone out let us know and we'll run an ad for them

**TECH SPRAY** P. O. Box 949  
 Amarillo, Texas

makers of BLUE STUFF and other  
 chemical tools for technicians

Circle 22 on literature card



greater accuracy and eliminates CRT damage. Heater, G1 and G2 voltages are continuously variable and metered. G1 voltage can be set with accuracy under all conditions, according to the manufacturer. Heaters are monitored at tube pins.

The 466 is supplied in a light-weight case measuring 13¼ inches X 9½ inches X 5¼ inches and weighs 8 lbs. The price is \$129.95.

Circle 51 on literature card

#### CRT Checker and Rejuvenator

A picture tube color-tracking analyzer and rejuvenator, which is designed to check all color tubes in accordance with CRT manufacturers' recommended procedures, has been made available by Mercury Electronics Corp.



Model 880 contains universal sockets and adapters, including complete black-and-white sockets. Mercury states that each gun of a color tube is adjusted to cutoff before the beam current reading is taken, to simulate actual conditions in the television set. It also checks shorts or inter-element leakage.


The unit, which comes complete with a picture tube data book, sells for \$79.95.

Circle 52 on literature card

(Continued on page 46)

## BLUE STUFF

Doesn't Rattle  
when you shake it

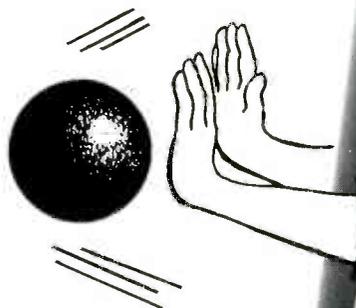

and it's a good  
thing it doesn't



Here's why - Continuous polishing compounds like BLUE STUFF must be free to migrate on the tuner contacts as the channel selector rotates. If the compound were to thicken and harden (cake up) it would prevent good contact from being made and you'd have a callback.

How can you tell if a product will harden on the contacts? Chances are that if it will cake up on contacts it will also cake up in the can. So, just shake the can and see if it rattles. If it doesn't rattle that means it didn't need a marble to keep the compound from settling out and hardening, and that's a good indication that it will not harden on the tuner contacts.

Pick up a can of BLUE STUFF and shake it. . . .  
What you don't hear tells you a lot.

**TECH SPRAY** better chemical tools for technicians

P. O. Box 949 Amarillo, Texas • Canada: Wm. Cohen, Montreal • Export: Empire Exporters, N.Y.C.

Circle 23 on literature card


**NEW**

# TV/radio/Hi Fi

# fix-it tools



make tricky jobs easy

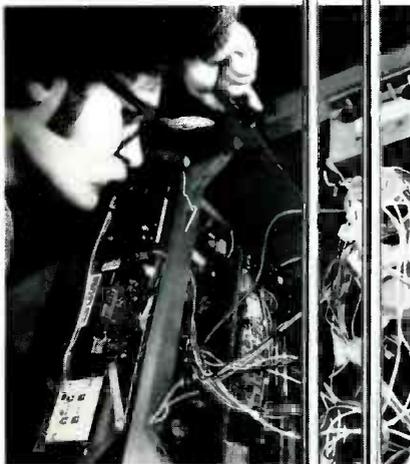

### SUPER LONG NUTDRIVERS

Over 20" long with 1/4" and 5/16" hex openings, color-coded plastic (UL) handles, full length hollow shafts.

Eliminate skinned knuckles and the frustration of trying to reach tuners, bezels, other up-front components from the back of a TV set with ordinary tools.

Extra length means more convenience, greater driving power for many other "fix-it" jobs.

### INVERTED PALNUT DRIVER SHANKS

Fit all Xcelite "99" handles, including Tee and ratchet types. Popular 7/16" and 1/2" external hex sizes, hollow shanks.

Save time, prevent damage to fastener or equipment when removing Palnuts on balance controls, on-off switches, volume control shafts of most TV sets, record players, portable radios.



nationwide availability through local distributors

REQUEST BULLETIN N470



XCELITE INC., 18 BANK ST.,  
ORCHARD PARK, N. Y. 14127  
In Canada contact Charles W. Pointon, Ltd.

Circle 24 on literature card

### Insulation Tester

The new Hitachi E-17 insulation tester has been introduced by General Electric Supply Co., for the Japanese Products Corp.



The E-17 detects insulation leakage and breakdowns in motors, outdoor and indoor wiring, lighting fixtures, switchboards, receptacles, appliances, circuit breakers, cables and panels.

The E-17 is self-powered and weighs only 5½ lbs.

Test voltage outputs to 2,500 VDC are available. Prices start at \$165.00.

Circle 53 on literature card

### Solid-State Field-Strength Meter

A new solid-state, portable field-strength meter for cable TV (CATV) and master antenna TV (MATV) systems is available from JFD Electronics Corp.

The unit provides direct readings on all UHF and VHF picture and sound carriers. Inputs from 10 µV to 2 volts can be measured with a stated accuracy of ±1.5 dB. The VHF frequency range is from 54 to 216 MHz, and the UHF frequency range is 470 to 890 MHz.

A special phone-scope jack is provided to give a detected signal



output which can be used to drive a high-impedance crystal earphone, a tape recorder or an oscilloscope. The unit automatically turns off when the cover is closed.

Model 1720 operates on four 9-volt batteries. Price is \$395.00.

Circle 54 on literature card

### Portable Triggered Oscilloscope

Philips Electronic Instruments introduces a portable triggered-sweep oscilloscope, Model PM 3200.

The design of PM 3200 has eliminated the need for the following controls: DC balance, trigger stability, and manual trigger level. The instrument has a 10-MHz band-



width, sensitive to 2mV/Div. The signal-derived triggering is automatic over the entire nominal 10-MHz bandwidth.

Model PM 3200 has two control settings: vertical amplitude and time base. A battery power pack also is available. The basic price is \$495.00.

Circle 55 on literature card

### Pulse Generator Adapter

The new Blulyne, Model APG-150, pulse generator reportedly allows the calibration of scopes at high frequencies (50-MHz rise times), and the testing of amplifier frequency response, control chopper circuits, and any other electronic circuits that require fast rise times,



variable pulse widths and amplitudes.

The generator features variable pulse widths from 100 nanoseconds to 5 milliseconds, with added capacitance to 500 milliseconds (50% duty cycle maximum); pulse amplitude is variable from 0 to 12 volts, and rise and fall times are up to less than 20 nanoseconds, reports the manufacturer.

Two models are available: the APG-100, with 100-ohms output impedance and 0-6 volts amplitude, and the APG-150, with 50-ohms output impedance and 0-12 volts amplitude. Price of the APG-100 is \$49.95; the APG-150 sells for \$59.95.

Circle 56 on literature card

### 50K-ohm/Volt VOM

Unimetrics introduces the Omnimeter-50K, a 50K-ohm/volt VOM.

Specifications of the unit include: Mirror-scale meter, single-selector switch, easy access battery com-



partment, diode-protected meter movement and a pre-calibrated AC rectifier.

The Omnimeter-50K measures 4½ inches X 2¾ inches X 5¾ inches and weighs 22 ozs. with batteries. The price is \$27.95.

Circle 57 on literature card

### Solid-State Electronic Multimeter

A new solid-state electric multimeter has been introduced by Simpson Electric Co.

Model 2795 has 68 switch-selectable functions for measuring AC

# RMS BEST PERFORMING UHF CONVERTERS




### RMS SOLID-STATE TWO TRANSISTOR DELUXE UHF CONVERTER HAS BUILT-IN AMPLIFIER!

Updates any VHF TV Set to receive any of the 83 UHF/VHF Channels. Low noise, drift-free operation. Simple hook-up. Charcoal Gray Hi-Impact Plastic Housing has Silver-matte finish front panel. Features accurately calibrated UHF dial, UHF/VHF antenna switch, on/off switch, advanced pilot light indicator and tuning control.

Model CR-300

List \$34.95

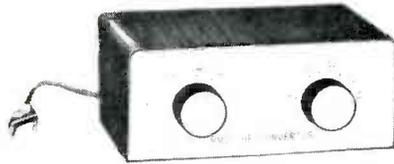

### RMS SOLID-STATE ECONOMICAL UHF CONVERTER

Two transistor advanced circuitry. Durable metal housing has wood grain finish and Satin Gold front panel with Black knobs having Gold inserts. #CR-2TW

List \$27.95



### RMS UHF ANTENNAS . . .

Top performers for all areas! Brings clearest Color and Black and White Reception on all UHF Channels 14-83. Features Reynolds Aluminum COLORWELD!

# RMS ELECTRONICS, INC.

50 ANTIN PLACE, BRONX, N. Y. 10462 • Tel. (212) TY 2-6700

Write for FREE Information on these and other Profit Building Products. . . .

Circle 25 on literature card

and DC voltage in 13 ranges, AC and DC current in 14 ranges, resistance in 6 low-power ranges, capacitance in 6 ranges, temperature in 2 ranges and output in 12 ranges.

The manufacturer reports a rated accuracy of  $\pm 1.0\%$  for AC and DC.

The 2795 features an anti-parallax mirror dial and a linear scale for all AC/DC voltage and current measurements. Separate scales are provided for resistance, capacitance, temperature and decibels.

The new model 2795 is battery operated and sells for \$230.00, complete with test leads, batteries and instruction manual. ▲

Circle 58 on literature card



**ELECTRONIC SERVICING . . .**  
the country's only magazine  
devoted 100% to the  
**ELECTRONIC SERVICING**  
industry . . .

# TV TECH AID

Takes you right to the source of the trouble... without guesswork and wasted time!

You receive each month OVER 40 ACTUAL CAUSES AND CURES OF COLOR AND B-W TV TROUBLE SYMPTOMS . . .

reported by leading TV manufacturers, technicians and field reps . . . each presented in a concise, brief format, including a clearly marked schematic diagram of the associated circuitry . . . no wading through unnecessary details!

You also receive timely and complete information about CIRCUIT MODIFICATIONS AND OTHER VALUABLE SERVICE DATA relating to both new and existing TV models.

Start or expand your own file of causes and cures with TV TECH AID . . . arranged so you can file them by make and model, by trouble symptom or use your own system.

**SUBSCRIBE  
or  
RENEW NOW!**

only \$7.95 per year (12 issues)  
(that's less than 67¢ per month!)

**WHILE THEY LAST . . .  
ALL 12 1969 ISSUES  
OF TV TECH AID FOR  
ONLY \$4.95!**

TV TECH AID  
P.O. BOX 603  
KINGS PARK, N.Y. 11754

ENCLOSED IS A CHECK OR MONEY  
ORDER FOR \$.....  
PLEASE SEND:

- 1971—12 ISSUES—\$7.95  
 1970—12 ISSUES—\$7.95  
 1969—12 ISSUES—\$4.95

TO:  
NAME .....

ADDRESS .....

CITY .....

STATE ..... ZIP.....

Circle 26 on literature card

# audio systems report

## Speed-Test Strobes

A pair of tape player speed-test strobes in cassette and cartridge formats are available from Robins Industries Corp.

The function of the strobes is to help guard against the pitch changes that result from player speeds that are either too fast or too slow. Also, they can be used to determine sporadic speed changes: flutter, when the repeated speed change is fast; or wow, when the irregularity changes slowly.



Both units have integral strobe light and tape for testing by simply sliding the case into the player. Instructions are on the face of the case for ready reference. Operation is on standard house current.

The cassette version of the new Robins strobe, Model TSC-9, is built into a standard compact-cassette case and sells for \$6.50. Its eight-track counterpart, Model TSC-8, comes in a standard cartridge case and sells for \$7.90.

Circle 59 on literature card

## Dual Voice-Coil Speaker

A new speaker, designated the 69HU8WD, has been introduced by Oaktron Industries, Inc.

Because of the unique double voice coil on the unit, special switching arrangements and wiring reportedly are not required. The dual voice coil enables use of both regular radio and stereo tape on the same speaker. This unit is 6 inches X 9



inches with a maximum depth of 3 3/16 inches. It has dual 8-ohm voice coils, rated for 10 watts.

The price is \$12.80.

Circle 60 on literature card

## Microphone for PA Systems

A new omnidirectional dynamic microphone for public-address system and recording-studio radio/TV applications has been introduced by Shure Brothers, Inc.

The Vocal Sphere Model 579SB is a low-impedance unit that reportedly delivers a peak-free, linear, wide-range response. Shure states that its uniformly omnidirectional pickup pattern minimizes unnatural voice coloration that often occurs when the speaker moves from side to side in front of the microphone.

Built-in wind and "pop" filters are incorporated in the unit. Handling and mechanical noises are sharply reduced by its shock-mounted, isolated cartridge. It reportedly is lightweight and well-bal-




anced, with a modified "ball" head and a 3/4-inch body diameter. It features a built-in on/off switch and comes with a 20-foot detachable cable with a Cannon connector on the microphone end.

The price is \$75.00. ▲

Circle 61 on literature card

# 35,000 parts for a dollar.

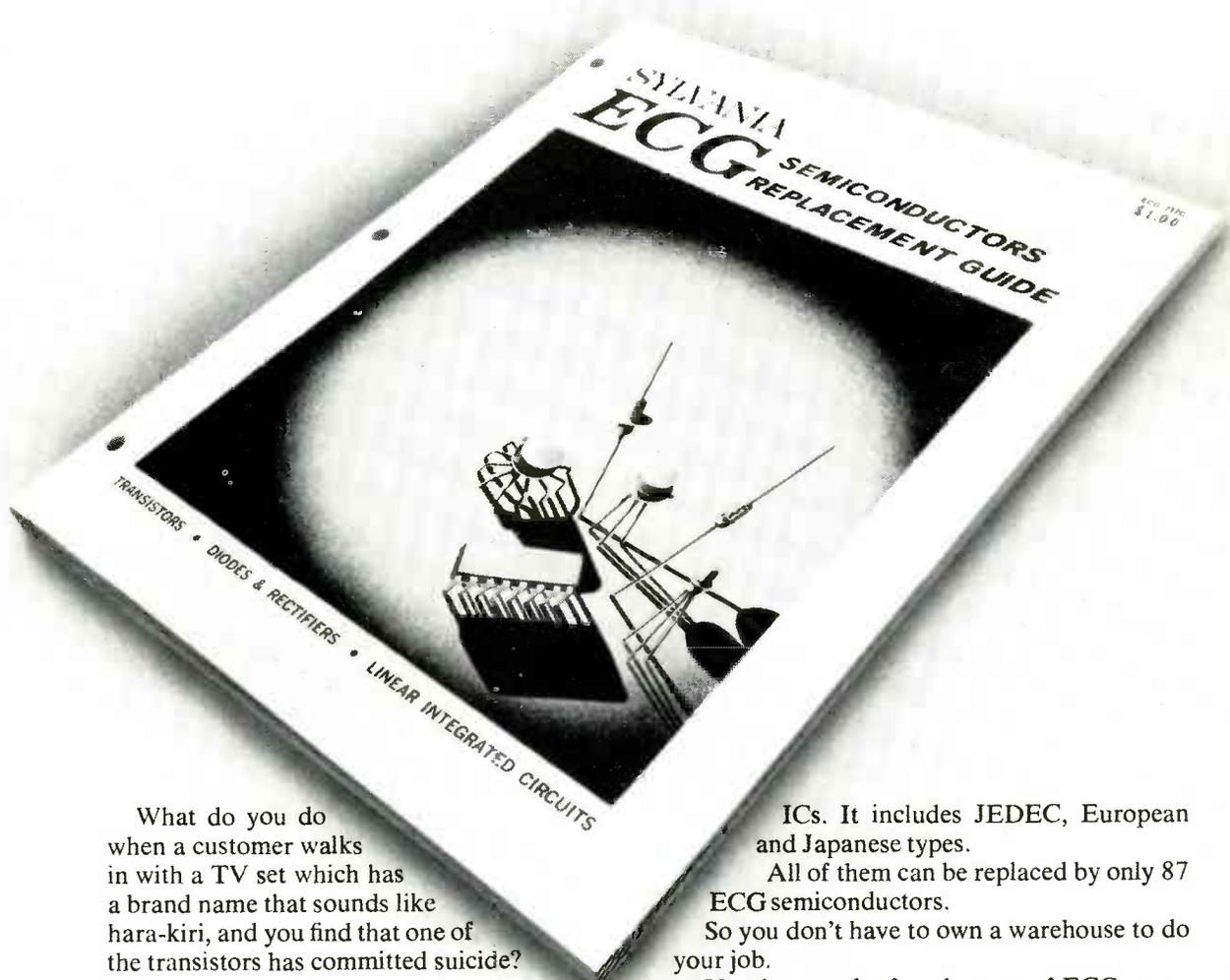

What do you do when a customer walks in with a TV set which has a brand name that sounds like hara-kiri, and you find that one of the transistors has committed suicide?

You can tell him to throw the set away.

Or, if the transistor has a number, you can look it up in Sylvania's ECG Semiconductor Replacement Guide and pop in an ECG replacement.

The Guide lists over 35,000 transistors, FETs, diodes, rectifiers, Zener diodes and linear

ICs. It includes JEDEC, European and Japanese types.

All of them can be replaced by only 87 ECG semiconductors.

So you don't have to own a warehouse to do your job.

You just need a few drawers of ECG parts. And one buck...

*for which your Sylvania Distributor will gladly sell you the Guide. He also has the entire ECG replacement line. Remember: Sylvania supplies you; we don't compete with you.*

**SYLVANIA**  
GENERAL TELEPHONE & ELECTRONICS

Circle 27 on literature card

December, 1970/ELECTRONIC SERVICING 49

# Source guide to imported consumer electronic products

A source guide to imported consumer electronic products was published in the November '69 issue of ELECTRONIC SERVICING. Since then, we have learned of many new brands. After considerable research, we now have determined the manufacturer, importer and/or distributor(s) of these new brands and have included them all in this updated Source Guide to Imported Consumer Electronic Products.

This guide correlates the brand name of an imported product with the manufacturer, importer and/or distributor of that product and indicates whether or not that brand name is or has been covered in Howard W. Sams specialized series of transistor radios, auto radios and tape recorders (TSM, AR and TR series) or in PHOTOFAC.

The number following each brand name indicates the most likely source from which service information and/or parts may be obtained, or to which a set may be sent for repair service. Before shipping a set, it is best to write the company indicated to determine if repair service is available, and if it is, what the company rules are concerning shipment of the set.

We have attempted to list only those brand names that are still being marketed in this country.

To provide continuous updating of this source guide, the editors of ELECTRONIC SERVICING would appreciate receiving from readers other brand names that are being used but do not appear here. If the manufacturer, importer and/or distributor is known, please include it. If it is not known, we will attempt to trace it and publish the information in ELECTRONIC SERVICING.

**Complete  
Manufacturer/Importer/Distributor list beginning on page 56**

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
ACME	251	yes
AFCO	3	no
AITC	200	no
AMC (Aimcee)	10	yes
AMC (York)	506	no
AMD	497	no
AGS	418	no
APF	4	no
Adell	7	no
Admiral	8	yes
Adonis	5	no
Advanco	9	no
Aimor	2, 47	no
Aircastle	411	yes
Aircorder	358	no
Airline	281	yes
Aiwa	11	yes
Aiwa (Rand)	359	yes
Aiwa (Selectron)	384, 385	yes
Akai (Camart)	62	no
Akai (Roberts)	364	no
Alaron	42	yes
Alfred	66	no
Alliance	13	yes
Allied	15	yes
Alpha	301	no
Alps	17	no
Ambassador	16, 268	yes
Amertone	18	no
Amico	132	no
Ampex	21	no
Angel	27	no
Annabel	42	no
Apolec	2	yes
Aristo	25	no
Aristocrat	38	yes
Aristo-Tone	25	no
Arrow	27	no
Arvin	29	yes
Astrex	473	no
Astrotone	230	yes
Audio-Lite	93	no
Audio Magnetics	34	no
Audio-Stereo	284	yes
Audion	36	no
Audiopak	33	no

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Audiotape	33	no	Califco	60	yes	Crown	92	yes
Audition	496	no	Cameo	29	yes	Crown (Ansafo)	22	no
Aud-I-Tone	205	yes	Candle	63	yes	Crown (Industrial Supp.)	195	yes
Audiovox	35	yes	Capehart	65	no	Crowncorder	92	no
August Moon	149	no	Capri (Nason)	292	no	Curtis-Mathes	94	yes
Auto Music	335	no	Capri (Toepfer)	446	no	Daltone	97	no
Automatic	37	yes	Captain	502	no	Dart	492	no
Autosonic	259	yes	Car Pal	35	no	Data Packaging	98	no
Aztec	40	no	Car Tapes	67	no	Dec	96	no
BASF	41	no	Cathedrel	492	no	Decca	99	yes
BSR	43	yes	Cathy	309	no	Dejay	100	no
Barkleigh	44	no	Channel	72	no	Delmonico	101	yes
Baron	52	no	Channel Master	73	yes	Dempa	102	no
Baylor	481	no	Chemicon	300	no	Denon	302, 303	no
Belaic	148	no	Chinon	376	no	Denon (Sheraton)	389	no
Belair (Hamway)	176	no	Cipher	269	yes	Dia	311, 312	no
Belair (Mason)	261	no	Citation	178	no	Dimension	441	no
Belair (Toko)	450	no	Clairtone	77	yes	Dokorder (Pengo)	343	no
Belair (Toyo)	458, 459	no	Claricon	497	yes	Dekorder (Wilson)	494	no
Belaire	148	no	Clarion	497	yes	Dolphin	104	no
Belcor	46	no	Clark	79	no	Domino	312	no
Belcorder	176	no	Clasonic	78	no	Doral	164	no
Bell & Howell	48	yes	Coach	103	no	Dorset	444	no
Benjamin	50	yes	Color Volt	404	no	Douglas	406	yes
Berlitz	32	no	Columbia	81	yes	Drexel	105	yes
Big Bem	452	no	Commodore	82	yes	Dual	475	no
Bigston	229	no	Communica	453	no	Durpoint	106	no
Billion	383	no	Concertone (Monarch)	279	no	Dyn	107	no
Birch	438	yes	Concertone	83	yes	Dyn-Sonic	107	no
Blaupunkt	53	yes	Concord	84	yes	Dynakits	108	no
Boeing	52	no	Conion	85	no	Dynavox	109	no
Boman	58, 59	no	Constant	64	no	Eagle	454	no
Bowman	58, 59	no	Consul	158	no	Ebner	140	no
Bozak	122	no	Consul Delux	162	no	Echo	224	no
Bradford	168	yes	Contelcee	87	no	Echo Radio	110	no
Brand 5	365	no	Continental	58, 59	no	Edge	406	no
Bravo	361	no	Coral	88	no	Editall	122	no
Brenell	140	no	Coronado	409	yes	Eico	111	no
Brightone	1	no	Coronet	27	yes	Eicocraft	111	no
Broadmoor	56	yes	Cortina	111	no	Eiwa	112	no
Browni	74	no	Corvair	466	yes	Eiwacorder	112	no
Bulova	57	yes	Corvette	273	yes	Elac	50	no
Bush	464	no	Country	221	no	Eldorado	80	no
CBC	74	no	Craig	90	yes	Electra	113	no
CEC	76	no	Crest	446	yes	Electro	114	yes
Caisonic	356	no	Crest-Line	64	no	Electro-Brand	114	yes

# Source guide, continued . . .

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Electrohome	199	yes	GRT	159	no	Hokuyo Musen	187	no
Electrophoneic	119	yes	GW	160	no	Honey Tone	30	yes
Electro-Wipe	106	no	Galaxy	30	no	Hosho	84	yes
Elgin	120	yes	Garrard	161	yes	IEM	190	no
Elite	121	no	Gaytone	176	no	ISCO	195	yes
Embassy	123	no	Geloso	19	yes	ITC (Ikegami)	192	no
Emerald	202	no	Gema	30	no	ITC (Int'l. Transistor)	200	no
Emerson	124	yes	General	464	yes	ITT	191	yes
Emi	50	no	General Electric	163	yes	Ideal	198	no
Empire	461, 126	no	Gibson Girl	365	no	Imperial	193	yes
Encore	61	no	Gidget	37	no	Imperial Delux	193	no
Engineers	367	no	Global	164	yes	Impex	194	no
Englishtown	411	yes	Globe	157	yes	Inland	196	yes
Epicure	128	no	Goer	166	no	Inmont-Cass/8	72	no
Espo	130	no	Goer 8	71, 72	no	Intermart	197	no
Essex	236, 237	yes	Golden Shield	165	no	Intersonic	201	no
Estey	131	no	Goodmans of England	121	no	Invico	69	no
Ever-Play	171	yes	Goodway	166	no	Invicta	460	yes
E-Z Splice	106	no	Gotham	167	yes	Irish	202	no
Fabulloyds	236, 237	no	Granada	148	no	J. B. Hunter	16	no
Facom	155	no	Grand Prix	74	no	JFD	204	yes
Faircrest	141	yes	Gregory	169	yes	JIL	207	no
Fairfax	134	no	Grenadier	125	no	JJJ	205	no
Fairmont	136	yes	Grundig	170	yes	JVC	206	no
Falcon Sergeant G-2	118	no	Gusdorf	172	no	JVC (Delmonico)	101	no
Fanon	137	yes	Guy Barry	136	no	Jade	360	no
Fantavox	257	no	HTV	175	no	Jaguar	294	yes
Fanuc	155	no	Halco	174	no	Japarc	208	no
Federal	139	no	Hammerlund	116	no	Jeolco	210	no
Fen-Tone	140	no	Harmon-Kardon	178	no	Jerone Speer	492	no
Ferrograph	122	no	Harlie	177	no	Jensen	209	no
Fidela	289	no	Harp	147	no	Juli-Corder	451	no
Fidelity	367	no	Hatsune	180	no	Juli-Phone	451	no
Fisher	142	no	Hemisphere	369	yes	Juliette	455	yes
Fix Tuned	144	no	Heritage	181	no	Juliette (Miami)	454	yes
Fleetwood	468	yes	Hi-Deilty	346	yes	KCK	211	no
Foster	146	no	Highsky (Paros)	203	no	KLH	212	no
Four Star	145	no	Highwave (Delmonico)	101	yes	Katone	215	no
Fuji	150	no	Highwave (Marvel)	260	yes	Kaysons	217	no
Fuji Ricoh	152	no	Hinode	182	no	Kensington	444	no
Fujiden	153	no	Hit	181	no	Kent	218	yes
Fujion	151	no	Hitachi	184, 185	yes	Kenwood	219	yes
Fujitsu	155	no	Hitachi (New York Ltd.)	184	yes	Kenwood (Trio)	470	yes
Fujitsu Ltd.	154, 155	no	Hitachi (Hitachi Maxwell)	183	yes	Keystone	32	no
Funia	156	no	Hitachi (Thal)	445	yes	Kilts	103	no
GC	157	no	Hiwave	261	no	Kitaron	222	no

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Kits	223	no	Major	250	no	Morse	282	yes
Kleen-Sweep	106	no	Majorette	250	yes	Mortone	202	no
Kodam	224	no	Mantone	251	no	Motorola	283	yes
Koronette	143	no	Marantz	252	yes	Muntz Stereo-Pak	284	yes
Korting	4	no	Mar-Lin	253, 254, 255	no	Murata	285	no
Koss	225	no	Mars	256	no	Musicolor	286	no
Koss-Acoustech	225	no	Martel	259	no	Muskat	49	no
Koss-Rek-O-Kut	225	no	Marvel	251	yes	NAC	291	no
Kowa	226	yes	Mascot	367	yes	NAL	314	no
Koyo	227	yes	Master Control	498	no	NACO	313	no
Kron	193	no	Mastercraft	262	yes	NDK	305	no
Kroy	506	yes	Masterwork (Columbia)	81	yes	NGK	287	no
Kuba	348	no	Masterwork	263	yes	NTK	287	no
Kupi-Tone	493	no	Matsushita	264	yes	Nakamichi	289, 290	no
Kyocera	228	no	Maxell	183	no	Nanaola	456	no
LIC	240	no	Mayfair	28, 45, 266	yes	Nassau	437	no
L.W.E.	6	no	Mecca	258	no	National	339	yes
Lafayette	230	yes	Megatone	5	no	Nec (Kanematsu)	213	yes
Lamie	429	no	Melodian	220	no	Nec (Nippon)	304	yes
Lark	61	no	Melo-Sonic	492	no	Nemco	288	no
Leader	231	no	Mercury (Pax)	267, 341	no	Net	295	no
Lear Jet Stereo 8	232	yes	Message Minder	54	no	Newell	2	no
Le-Bo	233	no	Metex	312	no	Nichicon	298	no
Levtron	481	no	Metro	270	no	Nikka	75	no
Lexington	352	yes	Mexko	353	no	Nitto	310	no
Liberty	234	yes	Micro	272	no	Nivico (Challenge)	69	no
Lion	235	no	Microsonic	356	no	Nivico (Delmonico)	101	no
Little Pal	251	no	Midland	273	yes	Nobility	296	no
Lloyd's	236, 237	yes	Miharu	274	no	Nocturne	178	no
Loben	447	no	Mikado	275	no	Nordmende	419	yes
Longines Symphonette	238	yes	Mingon	429	no	Norelco	315	yes
Lord Barkleigh	44	no	Mini-Swinger	438	no	North American	313	yes
Loyal	239	no	Miny (Tape Players)	258	no	Novel	150	no
Lucky	240	no	Miny	313	no	NuVox	316	no
Lulu	340	no	Miracord	50	yes	OKI	70	yes
Luxtone	241	no	Miradon	348	no	OMGS	313	yes
Lynn	242	no	Mirandette	14	no	Ocean	173	no
McIntosh	122	no	Mitsubishi	276	yes	Ocean & Transonic	467	no
MYM	245	no	Mitsumi	277	no	Olson	321	no
Macrosonic	505	no	Miyakawa	278	no	Omg's	313	yes
Magatone	311	no	Mody-Kit	55	no	Omron	333	no
Magnatone	131	no	Monarch	279	yes	Onkyo	337	no
Magnavox	248	yes	Monarch (BSR)	43	yes	Oral	334	no
Magnecord	439	no	Monacor	279	yes	Orion	336	yes
Magnifique	367	no	Mondo	280	no	Orion (Fried Trading)	148	yes
Magnus	249	no	Moore	317	no	Ortofon	122	no

# Source guide, continued . . .

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Oscar	95	no	Robins	365	no	Silver	398	no
Pacific	338	no	Rolecor	366	no	Singer	402	yes
Panasonic	339	yes	Romar	351	no	Shin-ei	396	no
Panger	441	no	Ross	367	yes	Skandia	403	no
Paros	203	no	Rota	363	no	Skyfon	322	no
Pax	267, 341	no	Rotacorp	363	no	Skymaster	296	no
Peerless	342	yes	Rotel	366	no	Solo-Phone	401	no
Pencorder	352	no	Roxy	318	no	Sonics	405	no
Penncrest	344	yes	Royal	250	yes	Sonoco	407	no
Perfection	345	no	Rozinante	368	no	Sonoramic	365	no
Perpetuum-Ebner	122	no	Rutherford	94	yes	Sony-Superscope	423	no
Pet	375	no	Ryth-O-Matic	492	no	Sony	408	yes
Petely	346	no	SD	427	no	Sound	308	no
Peter Pan	438	no	SMK	400	no	Sound 'N Color	111	no
Petite	419	yes	Samac	382	no	Soundesign	360	yes
Philco	347	yes	Sampson	199	yes	Sovereign	389	no
Philips	492	no	Sandhurst	5	no	Spica	420	yes
Phoenix	61	no	San-ei Instrument	370	no	Spico	410	no
Pianola	399, 59	no	Sankoh	372	no	Spinola	406, 412	no
Pickering	349	no	Sankyo	20	no	Sportmaster	463	yes
Pioneer	350	no	Sanrin	373	no	Squealer	72	no
Plata (Dyn)	107	yes	Sansui	377, 378	yes	Stanbrooke	444	no
Plata (Kaysons)	217	yes	Sanyo	379	no	Standard	414, 415	yes
Playtape	91	no	Satellite	51	yes	Stanford	416	no
Poly-Planar	247	no	Saxony	463	yes	Stanton	122	no
Poly-Sonic	247	no	Scene	166	no	Starfire	253	no
President	342	no	Scene Tuner	72	no	Star-Lite	262	yes
Princeton	26	no	Scotch	244	no	Startone	189	no
Qatron	354	no	Scott	380	no	Stereo-Magic	417	no
Quickmount	247	no	Seavox	148	no	Stellar	31	no
Radiant	356	no	Seeburg	381	no	Stereo-Dyn	107	no
Radiomaster	357	no	Selecto	106	no	Stereo Dynetic	401	no
Raleigh	217	yes	Seminole	374	yes	Stereomatic	5	no
Ranger	441	yes	Sentry	32	no	Sterling	418	no
Realistic	355	yes	Setico	386	no	Stewart	242	yes
Realtone	360	yes	Shamrock	202	no	St. Moritz	251	no
Record-Matic	106	no	Shannon	103	no	St. Mortiz	251	no
Recoton	361	no	Sharp	387	yes	Sublime	358	no
Rembrandt Antennas	12	yes	Sharpe	122	no	Summit	420	no
Rhapsody	42	yes	Sharpe (Scrintrex)	388	no	Sun Bird	207	no
Rising	187, 188	no	Sheraton	389	yes	Sun Bird (Katoh)	214	no
Rivera	293	no	Sherwood	390	no	Sun Glass	19	no
Roberts	364	yes	Shibaden	391, 392, 393, 394	yes	Sunny-vox	397	no
Roberts Ross	445	no	Shimadzu	395	no	Sunsonic (Sankei)	371	no
Robette	179	no	Shin-Shirasuna	398	no	Sunsonic (Sunsonic)	421	no
Robin	261	yes	Shure	401	no	Suora	105	no

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Super Dynamic	427	no	Three-Star	292	no	Venice	319	no
Superex	422	yes	Tobi-Sonic	28, 45, 266	no	Versatek	123	no
Superscope	424	no	Toho	452	no	Vesper	448	yes
Supersonic	411	yes	Tokai	448	no	Viking	439	no
Supre-Macy	246	yes	Tokai (Japan)	449	no	Vikoa	480	no
Sylvania	425	yes	Tokai (Audiovox)	35	no	Viscount	86	yes
Sylvano	24	no	Toko	450	no	Vision	481	no
Symphonette	238	yes	Tonecrest	271	yes	Vista	90	yes
Symphonic	426	yes	Tonemaster (Broadmoor)	56	yes	Voca	482	no
Synchronex	356	no	Tonemaster (TAC)	464	yes	Vornado (Automatic)	37	no
TDK	427	no	Tonex	61	no	Vornado	483	yes
TDK (Cassette)	427	no	Toshiba	456	yes	Wald	484	no
TMK	460	no	Toshiba (Trans World)	466	yes	Waltham	485	no
TWI	468	no	Toshri	138	no	Waltham (Int'l.)	199, 369	yes
Tact (Fried)	148	no	Townley	127	no	Watts	122	no
Tact (Hamway)	176	no	Trancel	466	yes	Wealth (Funai)	156	no
Taico	428	no	Transcriber	465	no	Wealth (Toyomenka)	460	no
Takt	430	no	Transette	273	yes	Weather Ear	123	no
Tamradio	431	no	Transicorder	307	no	Weltron	488	no
Tamura	432	no	Transonic	466	yes	Webcor	487	no
Tandberg	433	yes	Transworld	117	no	Westinghouse	490	yes
Taya	457	no	Trio	469	no	Wharfedale	491	no
Teac (Teac)	434	no	Triumph	471	no	Wilco	379	yes
Teac (Repair Center)	362	no	Tropicana	47	no	Wilson	494	no
Technicorder	320	no	Troubador	125	no	Windsor	495	no
Tel	441	yes	Truetone	489	yes	Winston	460	no
Telecon	435	no	Tussah	472	no	Wollensak	243	no
Telefunken	436	yes	Twin XX Twenty	247	no	XAM	384, 385	no
Tele-Tone	438	yes	USAC	476	no	Yamaha	499	yes
Telex	439	no	Uher	259	yes	Yamatake-Honeywell	501	no
Telex-Phonola	486	no	Ultra-82	480	no	Yaskawa	503	no
Telmar	440	no	Unelco	473	no	Ye	500	no
Telmar (Martel)	259	no	Unicord	19	no	Yec	507	no
Tempest	39	no	Unidyne	401	no	Yew	504	no
Ten (Fujitsu)	155	yes	Unimetrics	230	yes	York	506	yes
Ten (Sanyo)	379	yes	Union	474	no	York (N.Y. Transistor)	297	yes
Ten Brand	35	no	Unisphere	401	no	Zenon	508	no
Tenna	441	no	United Audio	475	no			
Tennac	442	no	Valencia	207	no			
Tennamatic	441	no	Valiant	477	yes			
Tenphonic	443	no	Vantage	133	yes			
Thorens	122	no	Velk	478	no			

---

**Complete  
Manufacturer/Importer/Distributor list  
beginning on page 56**

# Manufacturer/Importer/Distributor List

1. A & A Trading Co.  
23 East 26th St.  
New York, N.Y.
2. ABC Import & Export  
47 West 30th St.  
New York, N.Y.
3. AFCO Electronics, Inc.  
P.O. Box 973  
Oakland, Calif. 94604
4. APF Electronics, Inc.  
515 Madison Ave.  
New York, N.Y. 10022
5. A & S Trading Co.  
124 West 30th St.  
New York, N.Y. 10001
6. Acoustron Corporation  
2418 Bartlett  
Houston, Tex. 77006
7. Adell International, Inc.  
43700 Adell Blvd.  
Novi, Mich. 48050
8. Admiral Corporation  
3800 West Cortland St.  
Chicago, Ill. 60647
9. Advance Transistor Co.  
1225 Broadway  
New York, N.Y.
10. Aimcee Wholesale Corp.  
1440 Broadway  
New York, N.Y. 10018
11. Aiwa International Corp.  
One East Wacker Drive  
Chicago, Ill. 60611
12. All Channel Prod. Corp.  
47-75 48th St.  
Woodside, N.Y.
13. Alliance Mfg. Co., Ltd.  
Lake Park Blvd.  
Alliance, Ohio
14. Allied Impex Corp.  
300 Park Ave. South  
New York, N.Y.
15. Allied Radio Corp.  
111 N. Campbell Ave.  
Chicago, Ill. 60680
16. Allied Stores Purchasing  
401 Fifth Ave.  
New York, N.Y. 10016
17. Alps Electric Co., Ltd.  
c/o Kanematsu-Gosho (USA),  
Inc.  
One Whitehall St.  
New York, N.Y. 10004
18. Amerex Trading Co.  
417 Fifth Ave.  
New York, N.Y. 10016
19. American Gelsolo Electronics, Inc.  
251 Park Ave. South  
New York, N.Y. 10010
20. American Sankyo Corp.  
95 Madison Ave.  
New York, N.Y. 10016
21. Ampex Consumer Equip. Div.  
2201 Lunt Ave.  
Elk Grove Village, Ill. 60007
22. Ansafofne of New York  
41 East 11th St.  
New York, N.Y.
24. Apex Repair Center  
1141 Broadway  
New York, N.Y.
25. Aristo-Tone Electronics  
240 Fifth Ave.  
New York, N.Y. 10001
26. Arlans Dept. Stores, Inc.  
393 Seventh Ave.  
New York, N.Y. 10001
27. Arrow Trading Co.  
7 West 26th St.  
New York, N.Y.
28. Artic Import Co.  
(Bee Electronics)  
(Mayfair Electronics Corp.)  
666 West Kinzie St.  
Chicago, Ill. 60610
29. Arvin Industries, Inc.  
1531 13th St.  
Columbus, Ind. 47201
30. Associated Importers  
34 Dore St.  
San Francisco, Calif.
31. Astra Trading Co.  
175 Fifth Ave.  
New York, N.Y. 10010
32. Atlas Rand Corp.  
One Keystone Rd.  
Paramus, N.J.
33. Audio Devices, Inc.  
235 East 42nd St.  
New York, N.Y.
34. Audio Magnetics Corp.  
14600 S. Broadway  
Gardena, Calif. 90247
35. Audiovox Corp.  
156 Fifth Avenue  
New York, N.Y. 10010
36. Audion Corp.  
200 Fifth Ave.  
New York, N.Y.
37. Automatic Radio Sales  
Two Main St.  
Melrose, Mass.
38. Automotive Assoc.  
551 Fifth Ave.  
New York, N.Y. 10017
39. Azad International  
22 West 27th St.  
New York, N.Y.
40. Aztec Sound Corp.  
2140 South Lipan St.  
Denver, Colo.
41. BASF Systems, Inc.  
Crosby Drive  
Bedford, Mass. 01730
42. B&B Import & Export Co.  
15755 Wyoming Ave.  
Detroit, Mich. 48238
43. BSR (USA), Ltd.  
Route 33  
Blauvelt, N.Y. 10913
44. Barker Stores  
815 Hutchinson River Pkwy.  
Bronx, N.Y. 10465
45. Bee Electronics  
666 W. Kinzie St.  
Chicago, Ill.
46. Belcor Corp.  
457 Chancellor Ave.  
Newark, N.J.
47. Bell Electronics  
1180 Broadway  
New York, N.Y. 10009
48. Bell & Howell Co.  
7235 North Linder  
Skokie, Ill. 60076
49. Bel-Mar, Inc.  
1942 N.E. 151st St.  
North Miami Beach, Fla. 33160
50. Benjamin Electronic Sound Co.  
40 Smith St.  
Farmingdale, L.I., N.Y. 11735
51. Best of Tokyo  
11 West 42nd St.  
New York, N.Y.
52. Boeig Electronics Co., Ltd.  
1-9, Ryocho Sakata-City  
Yamagata, Japan
53. Robert Bosch Corp.  
40-25 Crescent St.  
Long Island City, N.Y. 11101
54. Boston Worldwide  
148 State St.  
Boston, Mass.
55. Bowman Electronics  
155 East First Ave.  
Roselle, N.J.
56. Broadmoor Industry, Ltd.  
530 Santa Rosa Dr.  
Des Plaines, Ill. 60018
57. Bulova Watch Co.  
630 Fifth Ave.  
New York, N.Y. 10020
58. California Auto Radio, Inc.  
9426 Stewart & Gary Rd.  
Downey, Calif. 90241
59. California Auto Radio, Inc.  
1229 South Woodruff St.  
Downey, Calif.
60. California Trading Co.  
P. O. Box 3164  
Torrance, Calif.
61. Caltrade Mfg. & Trading Co.  
360 Ninth St.  
San Francisco, Calif. 94103
62. Camart Products  
Repair Center  
1845 Broadway  
New York, N.Y.
63. Candlé America, Inc.  
1457 Venice Blvd.  
Los Angeles, Calif. 90006
64. Canton-Son, Inc.  
12 West 27th St.  
New York, N.Y.
65. Capehart Corp.  
770 Lexington Ave.  
New York, N.Y. 10021
66. Capin Mercantile Corp.  
109 Nelson Ave.  
Nogales, Ariz. 85621
67. Car Tapes, Inc.  
320 West Ohio St.  
Chicago, Ill. 60610
68. Cardinal Electronics  
5069 Broadway  
New York, N.Y.
69. Challenge Corp.  
150 Fifth Ave.  
New York, N.Y.
70. Chancellor Electronics, Inc.  
457 Chancellor Ave.  
Newark, N.J. 07112
71. Channel Marketing, Inc.  
26 Springdale Road  
Cherry Hill, N.J. 08034
72. Channel Marketing, Inc.  
342 Madison Ave.  
New York, N.Y.
73. Channel Master  
Elienville  
New York, N.Y.
74. Charles Brown & Co.  
1170 Broadway  
New York, N.Y. 10001
75. Chiyoda Electronic Co., Ltd.  
3-9, Soto Kanda 3-chome.  
Chiyoda-ku  
Tokyo, Japan
76. Chuo Denki Co., Ltd.  
1767 Aza Higashidaria,  
Higashi Matsuyama  
Saitama, Japan
77. Clairtone Electronic Corp.  
681 Fifth Ave.  
New York, N.Y. 10022
78. Clarion Shoji Co., Ltd. (USA)  
2306 Cotner Ave.  
Los Angeles, Calif. 90064
79. David Clark Co., Inc.  
360 Franklin Street  
Worcester, Mass. 01604
80. A. Cohen & Sons, Inc.  
27 West 23rd St.  
New York, N.Y. 10010
81. Columbia Records Corp.  
51 West 52nd St.  
New York, N.Y. 10019
82. Commodore Import Corp.  
507 Flushing Ave.  
Brooklyn, N.Y. 11205
83. Concertone, Inc.  
3962 Landmark St.  
Culver City, Calif. 90230
84. Concord Electronics Corp.  
1935 Arnacost Ave.  
West Los Angeles, Calif. 90025
85. Coney Onkyo Co., Ltd.  
1-23, Iwaya Kita-machi 5-chome,  
Nada-ku  
Kobe, Japan
86. Consolidated Merchandising Corp.  
520 West 34th St.  
New York, N.Y. 10001
87. Continental Telephone  
Answering Devices  
17 West 46th St.  
New York, N.Y.
88. Coral Audio Corp.  
8-9, Soto-Kanda 3-chome,  
Chiyoda-ku  
Tokyo, Japan

89. Craig Panorama, Inc.  
2302 East 15th St.  
Los Angeles, Calif. 90021
90. Craig Corp.  
Cardinal Electric  
5069 Broadway  
New York, N.Y.
91. Craigston Corp.  
1115 Broadway  
New York, N.Y.
92. Crown Radio Corp.  
755 Folsom St.  
San Francisco, Calif. 94107
93. Curtis-Electro Lighting, Inc.  
1536 South Paulina St.  
Chicago, Ill. 60608
94. Curtis-Mathes Sales Co.  
414 Elizabeth Ave.  
Newark, N.J. 07112
95. Daishin Electric Ind. Co., Inc.  
2-5 Ohmori-minami, Ohta-ku  
Tokyo, Japan
96. Daiwa Ltd.  
1, Nihonbashi, Edobashi  
2-chome, Chuo-ku  
Tokyo, Japan
97. Dalamal & Sons  
107 Franklin  
New York, N.Y. 10002
98. Data Packaging Corp.  
205 Broadway  
Cambridge, Mass. 02139
99. Decca Distributing  
445 Park Ave.  
New York, N.Y. 10022
100. Dejay Industries  
90 North Washington St.  
Boston, Mass.
101. Delmonico International  
50-35 56th Rd.  
Maspeth, L.I., N.Y. 11378
102. Delta International, Ltd.  
Box 1946  
Grand Junction, Colo.
103. Dictotape, Inc.  
9090 Krier Place  
Brooklyn, N.Y. 11236
104. Dolphin Sansho, Ltd.  
11-13, Shimoigusa 5-chome,  
Suginami-ku  
Tokyo, Japan
105. Drexel Radio Corp.  
P. O. Box 15156  
New Orleans, La.
106. Duotone Co., Inc.  
6875 S.W. 81st St.  
Miami, Fla. 33143
107. Dyn Assoc. Importers, Inc.  
270 West 22nd St.  
Hialeah, Fla. 33010
108. Dynaco, Inc.  
3060 Jefferson St.  
Philadelphia, Pa. 19121
109. Dynavox Electronics Corp.  
40-05 21st St.  
Long Island City, N.Y. 11101
110. Echo Tsushin Kogyo Co., Ltd.  
29-9, Shimo Sueyoshi 1-chome,  
Tsurumi-ku  
Yokohama, Japan
111. Eico Electronic Instr. Co., Inc.  
283 Malta St.  
Brooklyn, N.Y. 11207
112. Eiwa Sangyo Co., Ltd.  
6-11, Nishi Shinbashi 2-chome,  
Minato-ku  
Tokyo, Japan
113. Electra Radio Corp.  
30 West 23rd St.  
New York, N.Y.
114. Electro-Brand, Inc.  
210 West Chestnut  
Chicago, Ill. 60610
115. Electrohome, Ltd.  
809 Wellington St. North  
Kitchener, Ontario, Canada
116. Electronic Assistance Corp.  
20 Bridge Ave.  
Red Bank, N.J. 07701
117. Electronic Ind., Inc.  
901 Daniel St.  
Kenner, La. 70062
118. Electronic Research &  
Development, Ltd.  
6th Floor, Shiozaki Bldg. 7,  
Hirakawa-cho 2-chome,  
Chiyoda-ku  
Tokyo, Japan
119. Electrophonic Corp.  
9200 Atlantic Ave.  
Ozone Park, N.Y.
120. Elgin National Watch Co.  
841 West Jackson Blvd.  
Chicago, Ill.
121. Elite Electronics  
195 East Central Ave.  
Farmingdale, N.Y. 11735
122. Elpa Marketing Ind., Inc.  
Thorens & Atlantic Ave.  
Garden City Park, N.Y. 11040
123. Embassy  
5330 East 38th St.  
Indianapolis, Ind. 46218
124. Emerson TV & Radio Co.  
51 West 51st St.  
New York, N.Y.
125. Empire Scientific Corp.  
1055 Stewart Ave.  
Garden City, N.Y. 11530
126. Empire Ultrasonics, Ltd.  
1199 Broadway  
New York, N.Y. 10001
127. The Englishtown Corp.  
42 Broadway  
New York, N.Y. 10004
128. Epicure Products, Inc.  
185 Somerville Ave.  
Somerville, Mass. 02143
129. Ercona Corp.  
432 Park Ave. South  
New York, N.Y. 10016
130. Espo Engineering Corp.  
5334 West 65th St.  
Chicago, Ill. 60638
131. The Estey Co.  
Div. of Electro-Learner Corp.  
Ziegler St.  
Harmony, Pa.
132. Exhibit Sales Co.  
South 3rd St.  
Philadelphia, Pa. 19106
133. Fairfax Dist. Co., Inc.  
1328 New York Ave. NW  
Washington, D.C.
134. Fairfax Ind., Inc.  
165 Ward St.  
Paterson, N.J. 07505
135. Fairmont Electronics, Inc.  
55 West 39th St.  
Suite 506  
New York, N.Y. 10018
136. Fairmont Electronics  
12 Crescent St.  
Holyoke, Mass.
137. Fanon Electronic Ind.  
439 Frelinghuysen Ave.  
Newark, N.J. 07114
138. Fedco, Inc.  
P.O. Box 2605  
Terminal Annex  
Los Angeles, Calif. 90054
139. Federal Transistor Co., Inc.  
519 South Broadway  
Los Angeles, Calif. 90013
140. Fen Tone International  
106 Fifth Ave.  
New York, N.Y. 10011
141. J. M. Fields  
111 Eighth Ave.  
New York, N.Y.
142. Fisher Radio Corp.  
11-40 45th Rd.  
Long Island City, N.Y. 11101
143. Fisher Sonic Co., Inc.  
405 44th St.  
Brooklyn, N.Y.
144. Fix Tune Solid State Electronics  
One West 30th St.  
New York, N.Y. 10001
145. Fortune Star Products  
1207 Broadway  
New York, N.Y. 10001
146. Foster Electric Co., Ltd.  
230 North Michigan Ave.  
Chicago, Ill. 60601
147. L. K. Franklin Co.  
8912 West Olympic Blvd.  
Beverly Hills, Calif.
148. Fried Trading Co.  
425 Bedford Ave.  
Brooklyn, N.Y. 11211
149. Fuji Electronics Co., Ltd.  
Nikko Mita Bldg., 26-4 Takanawa  
1-chome, Minato-ku  
Tokyo, Japan
150. Fuji Electrochemical Co., Ltd.  
437 Fifth Ave.  
New York, N.Y. 10016
151. Fuji Onkyo Co., Ltd.  
15-13 Shimomaru 1-chome,  
Ohta-ku  
Tokyo, Japan
152. Fuji Ricoh Co., Ltd.  
1046-2 Ikebukuro Toshima-ku  
Tokyo, Japan
153. Fujiden International Corp.  
Hase Bldg., 25, Bingomachi  
3-chome, Higashi-ku  
Osaka, Japan
154. Fujitsu California, Inc.  
16410 South Figueroa St.  
Gardena, Calif.
155. Fujitsu Ltd.  
680 Fifth Ave.  
New York, N.Y. 10019
156. Funia Electric Co., Ltd.  
3004 West Logan Blvd.  
Chicago, Ill. 60647
157. GC Electronics Co.  
400 South Wyman St.  
Rockford, Ill.
158. GCL Mercantile Corp.  
36 Utter Ave.  
Hawthorne, N.J. 07507
159. GRT Corp.  
1286 N. Lawrence Station Rd.  
Sunnyvale, Calif. 94086
160. GW Electronics, Inc.  
1647-4 West Sepulveda Blvd.  
Torrance, Calif.
161. Garrard  
Div. of British Ind. Co.  
Westbury, N.Y. 11590
162. General Consolidated  
87 Dell Gen Ave.  
Lodi, N.J.
163. General Electric  
Electronics Park  
Syracuse, N.Y. 13201
164. Global Import & Export  
858 West Flagler St.  
Miami, Fla. 33130
165. Golden Shield Corp.  
680 Fifth Ave.  
New York, N.Y. 10019
166. Goodway, Inc.  
11401 Roosevelt Blvd.  
Philadelphia, Pa.
167. Gotham Electronics, Inc.  
170 Michael Dr.  
Syosset, N.Y. 11791
168. W. T. Grant Co.  
1441 Broadway  
New York, N.Y. 10018
169. Gregory Amplifier Corp.  
3650 Dyre Ave.  
Bronx, N.Y.
170. Grundig Electronic Sales  
Corp.  
355 Lexington Ave.  
New York, N.Y.
171. Gulton Ind.  
212 Durham Ave.  
Metuchen, N.J.
172. Gusdorf & Sons, Inc.  
6900 Manchester Ave.  
St. Louis, Mo. 63143
173. Hachiyo Electric Sound Co., Inc.  
3-6, Higashigaoka 2-chome,  
Meguro-ku  
Tokyo, Japan
174. Halen Associates  
125 Fifth Ave.  
New York, N.Y. 10003
175. Hamamatsu TV Co., Ltd.  
c/o Kinsho-Matachi Corp.  
80 Pine St.  
New York, N.Y. 10005
176. Hamway Import Co.  
40 West 29th St.  
New York, N.Y. 10001

# Manufacturer / Importer / Distributor List continued . . .

- |   |   |   |   |
|---|---|---|---|
| 177. Harlie Transistor Prod.<br>393 Sagamore Ave.<br>Mineola, L.I., N.Y.                              | 199. International Importers<br>2242 South Western Ave.<br>Chicago, Ill. 60608                  | 221. King Korn Marketing<br>Div. of Fullview Ind., Inc.<br>6001 North Clark St.<br>Chicago, Ill. 60626  | 243. 3M Company Mincom Div.<br>3M Center<br>St. Paul, Minn. 55101                                   |
| 178. Harman-Kardon, Inc.<br>55 Ames Court<br>Plainview, New York 11803                                | 200. International Transistor<br>1206 South Maple<br>Los Angeles, Calif.                        | 222. Kitaron Electric Co., Ltd.<br>1-13, Arakawa 1-chome,<br>Arakawa-ku<br>Tokyo, Japan                 | 244. 3M Company Magnetic<br>Prod. Div.<br>3M Center<br>St. Paul, Minn. 55101                        |
| 179. Haskel Howard Co.<br>21 Hazelton Rd.<br>Yonkers, N.Y.  | 201. Intersonic Corp.<br>P.O. Box 215<br>Rockaway, N.J. 07866                                   | 223. Kits Industries, Inc.<br>729 Ceres Ave.<br>Los Angeles, Calif. 90021                               | 245. MYM Trans-World Corp.<br>1165 Broadway<br>New York, N.Y.                                       |
| 180. Hatsune Electric Ind. Co., Ltd.<br>Yatsurugi, Iwakure-cho, Niwa-gun<br>Aichi, Japan              | 202. Irish Tape Div.<br>Morhan National Sales Co., Inc.<br>458 Broadway<br>New York, N.Y. 10013 | 224. Kodama Chemical Ind. Co., Ltd.<br>7-3, Soto Kanada 6-chome,<br>Chiyoda-ku<br>Tokyo, Japan          | 246. Macy's Dept. Store<br>Herald Square<br>New York, N.Y. 10001                                    |
| 181. Heritage International Trading<br>1330 Stuyvesant Ave.<br>Union, N.J. 07083                      | 203. Izumi Co., Ltd.<br>9-13, 1-chome, Meauro Honcho,<br>Meauro-ku<br>Tokyo, Japan              | 225. Koss Electronics, Inc.<br>2227 North 31st St.<br>Milwaukee, Wis. 53208                             | 247. The Magitron Co.,<br>Div. of Era Acoustics Corp.<br>311 East Park St.<br>Moonachie, N.J. 07074 |
| 182. Minode Electric Works<br>13, Kamiyama-cho, Kita-ku<br>Osaka, Japan                               | 204. JFD Electronics Corp.<br>62nd St. at 15th Ave.<br>Brooklyn, N.Y.                           | 226. Kowa American Corp.<br>276 Fifth Ave.<br>New York, N.Y.  | 248. Magnavox Co.<br>270 Park Ave.<br>New York, N.Y.  |
| 183. Hitachi Maxell, Ltd.<br>501 Fifth Ave.<br>New York, N.Y. 10005                                   | 205. J.J.J. Merchandise<br>15 West 26th St.<br>New York, N.Y. 10010                             | 227. Koyo International<br>Inc. of America<br>330 Madison Ave.<br>New York, N.Y. 10017                  | 249. Magnus Organ Corp.<br>1600 West Edgar Rd.<br>Linden, N.J. 07036                                |
| 184. Hitachi New York, Ltd.<br>333 North Michigan Ave.<br>Chicago, Ill. 60601                         | 206. JVC America, Inc.<br>50-35 56th Rd.<br>Maspeth, N.Y.                                       | 228. Kyocera International, Inc.<br>510 South Mathilda Ave.<br>Sunnyvale, Calif. 94086                  | 250. Major Electronics Corp.<br>649 39th St.<br>Brooklyn, N.Y.                                      |
| 185. Hitachi Sales Corp.<br>New York Branch Office<br>666 Fifth Ave.<br>New York, N.Y. 10019          | 207. Japan Industry, Ltd.<br>Kawazu Bldg., 4 Kitayacho,<br>Shibuya-ku<br>Tokyo, Japan           | 229. Kyokuyo Electric Co., Ltd.<br>605, Oazo Idogi Ageo<br>Saitama, Japan                               | 251. Manhattan Novelty Co.<br>263 Canal St.<br>New York, N.Y. 10013                                 |
| 186. Hitachi Sales Corp. of<br>America<br>48-50 34th St.<br>Long Island City, N.Y. 11101              | 208. Jappac Co., Ltd.<br>21-21, Joban 9-chome, Urawi-shi<br>Saitama, Japan                      | 230. Lafayette Radio & Electronics<br>111 Jericho Turnpike<br>Syosset, L.I., N.Y.                       | 252. Marantz Co., Inc.<br>8150 Vineland Ave.<br>Sun Valley, Calif. 91352                            |
| 187. Hokuyo Musen Kogyo Co., Ltd.<br>6, Shikishima-cho 4-chome,<br>Johto-ku<br>Osaka, Japan           | 209. Jensen Mfg. Div. The Muter Co.<br>5655 West 73rd St.<br>Chicago, Ill. 60638                | 231. Leader Instrument Corp.<br>24-20 Jackson Ave.<br>Long Island City, N.Y. 11101                      | 253. Mar-Lin Enterprises<br>1472 Broadway<br>New York, N.Y.   |
| 188. Hokuyo Musen Co., Ltd.<br>80-26 138th St.<br>Kew Gardens, N.Y.                                   | 210. Jeloco (USA), Inc.<br>477 Riverside Ave.<br>Medford, Mass. 02155                           | 232. Lear Jet Stereo, Inc.<br>13131 Lyndon Ave.<br>Detroit, Mich. 48227                                 | 254. Mar-Lin Radio Corp.<br>45 West 27th St.<br>New York, N.Y. 10001                                |
| 189. Hotta Clock & Watch Co., Ltd.<br>23-12, Ueno 5-chome, Taito-ku<br>Tokyo, Japan                   | 211. KCK Co., Ltd.<br>528 West Wellington Ave.<br>Chicago, Ill. 60657                           | 233. Le-Bo Products Co., Inc.<br>71-08 51st Ave.<br>Woodside, N.Y. 11377                                | 255. Mar-Lin West Ltd.<br>1515 Santee St.<br>Los Angeles, Calif. 90015                              |
| 190. IEM<br>187, Kominato-cho 3-chome,<br>Naka-ku<br>Yokohama, Japan                                  | 212. KLH Research and Development<br>Corp.<br>30 Cross St.<br>Cambridge, Mass. 02139            | 234. Liberty Trading Co., Ltd.<br>Nippon Bldg., 8, Ohtemachi<br>2-chome, Chiyoda-ku<br>Tokyo, Japan     | 256. Mars Radio Corp.<br>79, Hanazonocho, Shinjuku-ku<br>Tokyo, Japan                               |
| 191. ITT Distributor Prod.<br>250 Broadway<br>New York, N.Y.  | 213. Kanematsu New York<br>One Whitehall St.<br>New York, N.Y.                                  | 235. Lion Electronics Corp.<br>194 South 8th St.<br>Brooklyn, N.Y.                                      | 257. Marshall Field & Co.<br>111 North State St.<br>Chicago, Ill. 60690                             |
| 192. Ikegami Electronics Inds.,<br>Inc. of New York<br>35-27 31st St.<br>Long Island City, N.Y. 11106 | 214. Katoh Co., Ltd.<br>Oaawa Bldg., 2-13,<br>Motohama-cho,<br>Naka-ku<br>Yokohama, Japan       | 236. Lloyd's Electronics Corp.<br>59 North Fifth St.<br>Saddlebrook, N.J. 07662                         | 258. Maruwa Electronic & Chemical<br>Co., Ltd.<br>1-18, Nishiura-cho, Higashi-ku<br>Nagoya, Japan   |
| 193. Imperial Import Co.<br>1199 Broadway<br>New York, N.Y. 10001                                     | 215. Katone Corp.<br>37 West 28th St.<br>New York, N.Y.   | 237. Lloyd's Electronics of California,<br>Inc.<br>6651 East 26th St.<br>City of Commerce, Calif. 90022 | 259. Martel Electronic Sales<br>1199 Broadway<br>New York, N.Y. 10001                               |
| 194. Impex Electronics<br>213 South Robertson Blvd.<br>Beverly Hills, Calif.                          | 216. Kay Jewelers<br>1328 New York Ave., NW<br>Washington, D.C. 20005                           | 238. Longines Symphonette<br>200 Myrtle Ave.<br>Larchmont, L.I., N.Y.                                   | 260. Marvel International<br>30 East 42nd St.<br>New York, N.Y.                                     |
| 195. Industrial Suppliers<br>755 Folsom St.<br>San Francisco, Calif. 94107                            | 217. Kaysons International Ltd.<br>250 West 57th St.<br>New York, N.Y.                          | 239. Loyal Sangyo Co., Ltd.<br>28-1, Sekiguchi 1-chome,<br>Bunkyo-ku<br>Tokyo, Japan                    | 261. Mason Camera Corp.<br>1141 Broadway<br>New York, N.Y. 10001                                    |
| 196. Inland Trading Co.<br>111 Hackensack Ave.<br>New Jersey  | 218. Kent Overseas, Inc.<br>38 West 33rd St.<br>New York, N.Y.                                  | 240. Lucky International<br>1155 Broadway<br>New York, N.Y. 10010                                       | 262. Mastercraft Electronic Corp.<br>1115 Broadway<br>New York, N.Y. 10010                          |
| 197. Intermart Corp.<br>147 West 42nd St.<br>New York, N.Y.   | 219. Kenwood Corp.<br>69-41 Calamus Ave.<br>Woodside, N.Y.                                      | 241. Luxor International<br>39 West 29th St.<br>New York, N.Y.  | 263. Masterwork Audio Prods.<br>1080 Graftle Rd.<br>Hawthorne, N.J. 07506                           |
| 198. International Distributors, Inc.<br>1178 Pope St.<br>Memphis, Tenn. 38102                        | 220. Keystone Electronics Corp.<br>11, Hirakawacho 1-chome,<br>Chiyoda-ku<br>Tokyo, Japan       | 242. Lynn Stewart Co.<br>439 East Illinois St.<br>Chicago, Ill. 60611                                   | 264. Matsushita Electric Corp. of<br>America<br>200 Park Ave.<br>New York, N.Y. 10017               |

265. M.E. Parts & Repair  
43-30 24th St.  
Long Island City, N.Y.
266. Mayfair Electronics Corp.  
666 West Kinzie St.  
Chicago, Ill.
267. Mercury Record Corp.  
35 East Wacker Dr.  
Chicago, Ill.
268. Metasco  
401 Fifth Ave.  
New York, N.Y. 10016
269. Metric TV Parts  
Repair Center  
65 Lexington Ave.  
Passaic, N.J.
270. Metro of California  
4861 Santa Monica  
Los Angeles, Calif. 90029
271. Metro Wholesale Corp.  
53 West 43rd St.  
New York, N.Y. 10036
272. Micro Seiki Co., Ltd.  
19 Fujimicho, Itabashi-ku  
Tokyo, Japan
273. Midland International Corp.  
1909 Vernon St.  
North Kansas City, Mo. 64116
274. Miharu Shoji Co., Ltd.  
P. O. Box 4  
Ellenville, N.Y. 12428
275. Mikado Electronics Corp.  
34 Dore St.  
San Francisco, Calif.
276. Mitsubishi Electric Corp.  
119 East Lake St.  
Prudential Plaza  
Chicago, Ill. 60601
277. Mitsumi Electronics Corp.  
11 Broadway  
New York, N.Y. 10004
278. Miyakawa Shoko Co., Ltd.  
13-1, Hagashi Azabu 1-chome,  
Minato-ku  
Tokyo, Japan
279. Monarch Electronics Corp.  
7035 Laurel Canyon Blvd.  
North Hollywood, Calif. 91605
280. Mondo Electronic Corp.  
19-3, Kami Ochiai 1-chome,  
Shinjuku-ku  
Tokyo, Japan
281. Montgomery Ward  
619 West Chicago Ave.  
Chicago, Ill.
282. Morse Electron Prods.  
9200 Atlantic Ave.  
Ozone Park, N.J. 11416
283. Motorola, Inc.  
9401 West Grand Ave.  
Franklin Park, Ill. 60131
284. Muntz Stereo-Pak, Inc.  
1715 Densmore Ave.  
Van Nuys, Calif. 91406
285. Murata Corp. of America  
Two Westchester Plaza  
Elmsford, N.Y. 10523
286. Musicolor Prods. Visionics, Inc.  
4332 Artesia Ave.  
Fullerton, Calif. 92633
287. NGK Spark Plugs (USA), Inc.  
4010 Sawtelle Blvd.  
Los Angeles, Calif. 90066
288. Nagata Electric Mfg. Co., Ltd.  
240, Hanakawaminamino-cho,  
Nishiyodogawa-ku  
Osaka, Japan
289. Nakamichi Research, Inc.  
153, Suzukicho 1-chome, Kodaira  
Tokoyo, Japan
290. Nakamichi Research (USA), Inc.  
130 Woodbury Rd.  
Woodbury, N.Y. 11797
291. Nakayama Denshi Co., Ltd.  
13-5, Nishimagome 2-chome,  
Ohta-ku  
Tokyo, Japan
292. Nason Trading Co.  
230 Fifth Ave.  
New York, N.Y.
293. National Electronics  
38-20 SE 8th St.  
Miami, Fla.
294. National Silver Co.  
241 Fifth Ave.  
New York, N.Y.
295. Net Electronics  
8315 East Firestone Blvd.  
Downey, Calif. 90241
296. New York Merchandise Co.  
32 West 23rd St.  
New York, N.Y. 10010
297. New York Transistor Co.  
New Jersey
298. Nichicon Capacitor, Ltd.  
3941 North Pine Grove Ave.  
Chicago, Ill. 60613
299. Nichimen Co.  
60 Broad St.  
New York, N.Y.
300. Nippon Chemical Condenser  
Co., Ltd.  
86-16 60th Ave.  
Rego Park, N.Y. 11373
301. Nippon Alpha Electric Co., Ltd.  
200 Park Ave.  
New York, N.Y. 10017
302. Nippon Columbia Corp. of  
America  
Suite 1001-3  
501 Fifth Ave.  
New York, N.Y. 10017
303. Nippon Columbia Corp. of  
America  
6 East 43rd St.  
New York, N.Y. 10017
304. Nippon Electric New York, Inc.  
200 Park Ave.  
New York, N.Y. 10017
305. Nippon Densan Co., Ltd.  
Morita Bldg., 15, Shitanishkubo,  
Hiromachi, Minato-ku  
Tokyo, Japan
306. Nippon Gakki Co., Ltd.  
10-1, Nakazawacho, Hamamatsu  
Shizuoka, Japan
307. Nippon Sound Equipment  
Co., Ltd.  
55-1, Kamiishihara 3-chome,  
Chafu  
Tokyo, Japan
308. Nippon Sound Co., Ltd.  
5-12, Shinsayama 1-chome,  
Sayama City,  
Saitama, Japan
309. Nissho Electronic Corp.  
225, Hirano Babacho, Higashi  
Sumiyoshi-ku  
Osaka, Japan
310. Nitto Gramophone Co., Ltd.  
5, Higashi Irifuneco,  
Nishinari-ku  
Osaka, Japan
311. Noam Electronics Corp.  
60 West 45th St.  
New York, N.Y. 10036
312. Noam Electronics Corp.  
118-21 Queens Blvd.  
Forest Hills, N.Y. 11375
313. North American Foreign  
Trading Co.  
1115 Broadway  
New York, N.Y. 10010
314. North American Leisure Corp.  
1776 Broadway  
New York, N.Y. 10019
315. North American Philips Co.,  
Inc.  
100 East 42nd St.  
New York, N.Y. 10017
316. NuVox Electronics  
150 Fifth Ave.  
New York, N.Y. 10011
317. OTC International, Inc.  
205 West Wacker Dr.  
Chicago, Ill. 60606
318. Ofuna Electronics Ind. Co., Ltd.  
526, Kamikashio-cho, Totsuka-ku  
Yokohama, Japan
319. Oikawa Kogei-sho Co., Ltd.  
9-9, Minamidai 5-chome,  
Nakano-ku  
Tokyo, Japan
320. Oki Electric Ind. Co., Ltd.  
202 East 44th St.  
New York, N.Y. 10017
321. Olson Electronics, Inc.  
260 South Forge St.  
Akron, Ohio 44308
322. Omiya Electric Co., Ltd.  
866, Sakaemachi 3-chome,  
Funabashi City,  
Chiba, Japan
323. Omron Tateisi Electronics Co.  
166 Forbes Rd.  
Braintree, Mass. 02184
324. Oral Denki Kogyo Co., Ltd.  
Ginza Midori Bldg., 11-9, Ginza  
5-chome, Chuo-ku  
Tokyo, Japan
325. Original Ind. Corp.  
529 Jericho Turnpike  
Mineola, N.Y. 11501
326. Orion Electric Co.  
1199 Broadway  
New York, N.Y.
327. Osaka Onkyo Co., Ltd.  
230 East 44th St.  
New York, N.Y. 10017
328. Pacific Import Co.  
37 West 23rd St.  
New York, N.Y.
329. Panasonic Repair  
43-20 24th St.  
Long Island City, N.Y.
330. J.J. Paulson Associates  
24 Brooklyn Ave.  
Freeport, N.Y. 11520
341. Pax, Ltd.  
5125 Church St.  
Skokie, Ill. 60076
342. Peerless Telerad, Inc.  
162 Fifth Ave.  
New York, N.Y. 10010
343. Pengo Traders  
234 Fifth Ave.  
New York, N.Y.
344. J. C. Penney Co., Inc.  
1301 Ave. of the Americas  
New York, N.Y. 10019
345. Perfect Sound Mfg. Co., Inc.  
5-16, Ginza 6-chome, Chuo-ku  
Tokyo, Japan
346. Petely Enterprises  
441 Lexington Ave.  
New York, N.Y.
347. Philco-Ford Corp.  
Tioga & "C" St.  
Philadelphia, Pa. 19134
348. Phillips Audio, Inc.  
29-28 41st Ave.  
Long Island City, N.Y. 11101
349. Pickering and Co., Inc.  
101 Sunnyside Blvd.  
Plainview, N.Y. 11803
350. Pioneer Electronics (USA),  
Corp.  
140 Smith St.  
Farmingdale, L.I., N.Y. 11735
351. D. Plough Dist., Co.  
P.O. Box 2266  
Memphis, Tenn. 38102
352. Ponder & Best, Inc.  
58-20 Broadway  
Woodside, N.Y.
353. Puchi Properties, Inc.  
405 Grand Ave.  
Nogales, Ariz.
354. Qatron Corp.  
12000 Old Georgetown Rd.  
Rockville, Md. 20852
355. Radio Shack Corp.  
730 Commonwealth Ave.  
Boston, Mass. 02215
356. Radiant Corp.  
8220 North Austin Ave.  
Morton Grove, Ill. 60053
357. Radiomaster, Inc.  
1314 Blondell Ave.  
Bronx, N.Y. 10461
358. Ramson Trading Co.  
1185 Broadway  
New York, N.Y.
359. Rand Associates  
1270 Broadway  
New York, N.Y.
360. Realtone Electronics Corp.  
34 Exchange Place  
Jersey City, N.J. 07302
361. Recoton Corp.  
46-23 Crane St.  
Long Island City, N.Y. 11101
362. Repair Center  
404 Jericho Turnpike  
Syosset, N.Y.

# Manufacturer / Importer / Distributor List continued . . .

- |   |  |   |   |
|---|--|---|---|
| 363. Risui Corp.<br>3-2, Hongo 3-chome, Bunko-ku<br>Tokyo, Japan  | 384. Selectron International Co., Inc.<br>55 Veteran Blvd.<br>Carlstadt, N.J. 07072                                | 405. Sonics Corp.<br>2, Kojimachi 3-chome,<br>Chiyoda-ku<br>Tokyo, Japan                                    | 426. Symphonic Radio & Electronics<br>Corp.<br>470 Park Ave. South<br>New York, N.Y. 10016                      |
| 364. Roberts Electronics, Inc.<br>5922 Bowcroft Ave.<br>Los Angeles, Calif. 90016                               | 485. Selectron International Co., Inc.<br>4215 West 45th St.<br>Chicago, Ill.                                      | 406. Son Lee Electronics<br>1227 Broadway<br>New York, N.Y.   | 427. TDK Electronics Corp.<br>82 Wall St.<br>New York, N.Y. 10005   |
| 365. Robins Inds. Corp.<br>15-58 127th St.<br>Flushing, N.Y. 11356  | 386. Setico Import Co.<br>2321 Liberty St.<br>Jacksonville, Fla.   | 407. Sonorac Co., Ltd.<br>1-10, Shimomeguro 1-chome,<br>Meguro-ku<br>Tokyo, Japan                           | 428. Taisei Co., Ltd.<br>Kyodo Blvd., 6, Takaracho<br>3-chome, Chuo-ku<br>Tokyo, Japan                          |
| 366. Roland Electronics Co., Ltd.<br>36-8, Ohkayama 1-chome,<br>Meguro-ku<br>Tokyo, Japan                       | 387. Sharp Electronics Corp.<br>178 Commerce Rd.<br>Carlstadt, N.J. 07072  | 408. Sony Corp. of America<br>47-47 Van Dam St.<br>Long Island City, N.Y. 11101                             | 429. Taiyo Koki Co., Ltd.<br>427, Oaza-Iida, Ohmiya<br>Saitama, Japan   |
| 367. Ross Electronics<br>2834 South Lock St.<br>Chicago, Ill.   | 388. Sharpe Instruments Div. of<br>Scintrex, Inc.<br>Amherst Industrial Park<br>Tonawanda (Buffalo), N.Y.          | 409. Sound Design Corp.<br>34 Exchange Place<br>Jersey City, N.J. 07302                                     | 430. Takt Denki New York<br>1170 Broadway<br>New York, N.Y. 10001   |
| 368. Rozinante, Inc.<br>878 Wing St.<br>Plymouth, Mich. 48170   | 389. Sheraton Electronics Co., Inc.<br>401 Broadway<br>New York, N.Y.  | 410. Spico Electronics<br>Div. of Spirling Products<br>Henrietta St. & Duffy Ave.<br>Hicksville, N.Y. 11802 | 431. Tamradio Co., Ltd.<br>241-20 Northern Blvd.<br>Douglaston, N.Y. 11363                                      |
| 369. The Sampson Co.<br>2244 South Western Ave.<br>Chicago, Ill.  | 390. Sherwood Electronic Labs., Inc.<br>4300 North California Ave.<br>Chicago, Ill. 60618                          | 411. Spiegel, Inc.<br>1061 West 35th St.<br>Chicago, Ill. 60609   | 432. Tamura Electric Works, Ltd.<br>437 Fifth Ave.<br>New York, N.Y. 10016                                      |
| 370. San-ei Instrument Co., Ltd.<br>Canterbury House, Apt. D-15<br>15 Canterbury Road<br>Great Neck, N.Y. 11021 | 391. Shibaden Corp. of America<br>21015-21023 South Figurroa St.<br>Torrance, Calif. 90502                         | 412. Spinola International Corp.<br>315 Fifth Ave.<br>New York, N.Y. 10016                                  | 433. Tandberg of America<br>8 Third Ave.<br>Pelham, N.Y. 10803  |
| 371. Sankei Mfg. Co., Ltd.<br>21-3, Shimomarucho 4-chome,<br>Ohta-ku<br>Tokyo, Japan                            | 392. Shibaden Corp. of America<br>1725 North 33rd Ave.<br>Melrose Park, Ill. 60160                                 | 413. Sportsmaster Radio<br>2570 Devon Ave.<br>Des Plaines, Ill.   | 434. Teac Corp. of America<br>1547 18th St.<br>Santa Monica, Calif. 90404                                       |
| 372. Sankoh Electric Co., Ltd.<br>25-11, Nishi Ochiai 1-chome,<br>Shinjuku-ku<br>Tokyo, Japan                   | 393. Shibaden Corp. of America<br>9848 Monroe Dr.<br>Dallas, Texas 75220   | 414. Standard Radio Corp.<br>60-09 39th Ave.<br>Woodside, N.Y. 11377  | 435. Telecon Corp.<br>4-6, Osaki 5-chome,<br>Shinagawa-ku<br>Tokyo, Japan                                       |
| 373. Sanrin Electric Co., Ltd.<br>1-152, Kashiwagi 1-chome,<br>Shinjuku-ku<br>Tokyo, Japan                      | 394. Shibaden Corp. of America<br>58-25 Brooklyn Queens Expwy.<br>Woodside, N.Y. 11377                             | 415. Standard Radio Corp.<br>1934 South Cootner Ave.<br>Los Angeles, Calif. 90025                           | 436. Telefunken Sales Corp.<br>South St./Roosevelt Field<br>Garden City, L.I., N.Y. 11530                       |
| 374. Sans & Streiffe, Inc.<br>8400 Brookfield Ave.<br>Brookfield, Ill. 60513                                    | 395. Shimadzu Seisakusho Ltd.<br>c/o Ataka America, Inc.<br>633 Third Ave.<br>New York, N.Y. 10017                 | 416. Stanford International<br>569 Laurel St.<br>San Carlos, Calif. 94070                                   | 437. Telephone Dynamics Corp.<br>1333 Newbridge Rd.<br>North Bellmore, N.Y. 11710                               |
| 375. Sanshin Electric Co., Ltd.<br>35-20, Koenji Minami 5-chome,<br>Suginami-ku<br>Tokyo, Japan                 | 396. Shin-ei Electric Co., Ltd.<br>6-8, Tagara 4-chome, Nerima-ku<br>Tokyo, Japan                                  | 417. Stereo Magic<br>Div. Eastern Specialties Corp.<br>5 Richard Dr. West<br>Mt. Arlington, N.J. 07856      | 438. Tele-Tone Co., Inc.<br>444 South 9th Ave.<br>Mount Vernon, N.Y.  |
| 376. Sanshin Optical Co., Ltd.<br>21-17, Takashima 1-chome, Suwa<br>Nagano, Japan                               | 397. Shinkyo Co., Ltd.<br>3, Kanda Kaji-cho 3-chome,<br>Chiyoda-ku<br>Tokyo, Japan                                 | 418. Sterling Hi Fi, Inc.<br>22-20 40th Ave.<br>Long Island City, N.Y.                                      | 439. Telex Communications Div.<br>9600 Aldrich Ave. South<br>Minneapolis, Minn. 55420                           |
| 377. Sansui Electronics Corp.<br>32-17 61st St.<br>Woodside, N.Y. 11377   | 398. Shin-Shirasuna Electric Corp.<br>60 Broad St.<br>New York, N.Y. 10004   | 419. Sterling Hi-Fidelity, Inc.<br>24-40 40th Ave.<br>Long Island City, N.Y. 11101                          | 440. Telmar<br>2339 South Cotner Ave.<br>Los Angeles, Calif. 90064  |
| 378. Sansui Electronics Corp.<br>2301 South Grand Ave.<br>Los Angeles, Calif. 90007                             | 399. Shintokyo Musen Co., Ltd.<br>1146, Minawa-cho, Kohoku-ku<br>Yokohama, Japan                                   | 420. Summit International<br>1140 Broadway<br>New York, N.Y. 10001  | 441. Tenna Corp.<br>19201 Cranwood Pkwy.<br>Cleveland, Ohio   |
| 379. Sanyo Electric, Inc.<br>221 North LaSalle St.<br>Chicago, Ill. 60601                                       | 400. Showa Musen Kogyo Co., Ltd.<br>c/o Kanematsu-Gosho (USA)<br>Inc.<br>One Whitehall St.<br>New York, N.Y. 10004 | 421. Sunsonic Corp.<br>10-5, Ginza 4-chome, Chuo-ku.<br>Tokyo, Japan  | 442. Tennac Antennas<br>P.O. Box 1005<br>Burlington, Iowa 52601   |
| 380. H. H. Scott, Inc.<br>111 Powder Mill Rd.<br>Maynard, Mass. 01754   | 301. Shure Brothers, Inc.<br>222 Hartrey Ave.<br>Evanston, Ill. 60204  | 422. Superex Electronics<br>4 Radford Place<br>Yonkers, N.Y.  | 443. Tensho Electric Ind. Co., Ltd.<br>Electronics Div.<br>3-3, Koyama 1-chome,<br>Shinagawa-ku<br>Tokyo, Japan |
| 381. Seeburg Corp.<br>1500 North Dayton St.<br>Chicago, Ill. 60622  | 402. Singer Consumer Products<br>30 Rockefeller Plaza<br>Room 6228<br>New York, N.Y. 10020                         | 423. Superscope, Inc.<br>8150 Vineland Ave.<br>Sun Valley, Calif. 91352                                     | 444. Terra International<br>3 East 28th St.<br>New York, N.Y. 10016   |
| 382. Seidai Mfg. Co., Ltd.<br>Oaza-kubo, Koga-machi,<br>Kasuya-gun<br>Fukuoka, Japan                            | 403. Skandia Electronics Corp.<br>4260, Nyoj-Gemba, Kusunoki-cho,<br>Kita-ku<br>Nagoya, Japan                      | 424. Superscope Pre-Recorded Tape<br>Div.<br>8150 Vineland Ave.<br>Sun Valley, Calif. 91352                 | 445. J. H. Thal Associates<br>200 Fifth Ave.<br>New York, N.Y.  |
| 383. Sekii Ind. Co., Ltd.<br>11-11, Kuramae 3-chome,<br>Taito-ku<br>Tokyo, Japan                                | 404. Sola Electric Div. of Sola<br>Basic Ind.<br>1717 Busse Rd.<br>Elk Grove Village, Illinois 60007               | 425. Sylvania Entertainment Products<br>700 Ellicott St.<br>Batavia, N.Y. 14021                             | 446. Alfred Toepfer<br>One Broadway<br>New York, N.Y. 10004   |

447. Toho Boeki Kaisha Ltd.  
7-14, Uchikanda 2-chome,  
Chiyoda-ku  
Tokyo, Japan
448. Tokai Corp. of America  
500 Fifth Ave.  
New York, N.Y. 10036
449. Tokai Communication Apparatus  
Corp.  
816, Nakahara, Shizuoka City  
Shizuoka, Japan
450. Toko New York, Inc.  
350 Fifth Ave.  
New York, N.Y. 10001
451. Tokyo Rokuon Kogyo Corp.  
17-11, Daita 4-chome,  
Setagaya-ku  
Tokyo, Japan
452. Tokyo Sansel  
1170 Broadway  
New York, N.Y. 10001
453. Tokyo Wireless Corp.  
33-37, Tokumaru 3-chome,  
Itabashi-ku  
Tokyo, Japan
454. Topp Electronics, Inc.  
4201 N.W. 77th Ave.  
Miami, Fla. 33166
455. Topp Import & Export, Inc.  
40 Whelan Rd.  
East Rutherford, N.J.
456. Toshiba America, Inc.  
477 Madison Ave.  
New York, N.Y. 10022
457. Toshiba Denshionkyo Co., Ltd.  
Third Wako Bldg., 12-1, Shiba  
Nishikubo Aketune-cho,  
Minato-ku  
Tokyo, Japan
458. Toyo Radio Co., Ltd.  
9-12, Osaki 2-chome,  
Shinagawa-ku  
Tokyo, Japan
459. Toyo Radio Corp. of America  
1842 B. West 169th St.  
Gardena, Calif. 90247
460. Toyomenka, Inc.  
Two Broadway  
New York, N.Y.
461. Trade Distributors, Inc.  
1199 Broadway  
New York, N.Y. 10001
462. Trade Unlimited  
75-03 Main St.  
Flushing, N.Y.
463. Trans-Aire Electronics Corp.  
393 Sagamore Ave.  
Mineola, N.Y.
464. Trans America Electronics Co.,  
Inc.  
6479 North Avondale  
Chicago, Ill. 60631
465. Transcriber Co., Inc.  
P.O. Box 478  
Attleboro, Mass. 02703
466. Transistor World Corp.  
52 Broadway  
New York, N.Y.
467. Transocean Electronics, Inc.  
Tojo Bldg., 14 Shinjuku 4-chome  
Shinjuku-ku  
Tokyo, Japan
468. Transworld Ind. Corp.  
5204 Hudson Ave.  
West New York, N.J.
469. Trio Corp.  
212 Fifth Ave.  
New York, N.Y.
470. Trio Corp.  
(Kenwood Electronics, Inc.)  
3700 South Broadway Pl.  
Los Angeles, Calif. 90007
471. Triumph Electronic Inds.  
515 East Jarvis  
Des Plaines, Ill. 60018
472. Tussah Corp.  
1412 Broadway  
New York, N.Y. 10018
473. Unelco Electronics Corp.  
Subsidiary of Astrex, Inc.  
32 North Eutaw St.  
Baltimore, Md. 21201
474. Union Co., Ltd.  
22-31, Kamisueyoshi 5-chome,  
Tsurumi-ku  
Yokohama, Japan
475. United Audio Products, Inc.  
535 Madison Ave.  
New York, N.Y. 10022
476. United States Antenna Corp.  
P.O. Box 46462  
Cleveland, Ohio 44146
477. Vallant Radio Corp.  
380 Second Ave.  
New York, N.Y.
478. Velk Electric Corp.  
33-14, Zenukujji 3-chome,  
Suginami  
Tokyo, Japan
479. Venfome Enterprises  
212 Fifth Ave.  
New York, N.Y.
480. Vikoa, Inc.  
400 Ninth St.  
Hoboken, N.J. 07030
481. Vision Electronics, Inc.  
1116 East Houston St.  
San Antonio, Texas 78206
482. Voca Dictating Machine  
274 Madison Ave.  
New York, N.Y.
483. Vornado, Inc.  
174 Passaic St.  
Garfield, N.J. 07026
484. Wald Sound  
11131 Dora St.  
Sun Valley, Calif. 91352
485. Waltham Electronics Ltd.  
Toyokawa Bldg., 12-13, Ginza  
8-chome, Chuo-ku  
Tokyo, Japan
486. Waters Conley Co., Inc.  
A Subsidiary of the Telex Corp.  
645 North Michigan Ave.  
Chicago, Ill. 60611
487. Webcor Div. of Consolidated  
Merchandising Co.  
59-50 Queens Midtown Expwy.  
Maspeth, N.Y. 11378
488. Weltron Co., Inc.  
514 East Peabody  
P.O. Box 217  
Durham, N.C. 27702
489. Western Auto Supply  
2107 Grand Ave.  
Kansas City, Mo. 64108
490. Westinghouse Electric  
3 Gateway Centre  
P.O. Box 2278  
Pittsburg, Pa. 15230
491. Wharfedale  
Div. of British Ind. Co.  
Westbury, N.Y. 11590
492. Whippany Electronics, Inc.  
1275 Bloomfield Ave.  
Fairfield, N.J. 07006
493. Whitehall Overseas Corp.  
1140 Broadway  
New York, N.Y.
494. Wilson Import Co.  
1157 Broadway  
New York, N.Y. 10029
495. Windsor Inds., Inc.  
88 Third Ave.  
Brooklyn, N.Y. 11217
496. F. W. Woolworth  
233 Broadway  
New York, N.Y. 10010
497. World Mark Electronics  
663 Dowd Ave.  
Elizabeth, N.J.
498. World Mart, Inc.  
201 N.W. 21st St.  
Miami, Fla. 33127
499. Yamaha International Corp.  
7733 Telegraph Rd.  
Montebello, Calif. 90054
500. Yamano Electric Mfg. Co., Ltd.  
12-27, Iwats 3-chome,  
Higashi Osaka City  
Osaka, Japan
501. Yamatake-Honeywell Co., Ltd.  
c/o Honeywell, Inc.  
24-30 Skillman Ave.  
Long Island City, N.Y. 11101
502. Yashima Electric Ind. Co., Ltd.  
314, Kamifuda, Chofu  
Tokyo, Japan
503. Yaskawa Electric America, Inc.  
100 Bilss Dr.  
Oak Brook, Ill. 60521
504. Yewtec Corp.  
1995 Palmer Ave.  
Larchmont, N.Y. 10538
505. Yokohama LPG Trading Co., Ltd.  
80, Onocho 5-chome, Naka-ku  
Yokohama, Japan
506. York Radio Corp.  
15 Empire Blvd.  
South Hackensack, N.J. 07606
507. Yutaka Electric Mfg. Co., Ltd.  
c/o Marubeni-Iida (America)  
Inc.  
938 Merchandise Mart  
Chicago, Ill. 60654
508. Zenon Corp.  
12-4, Takanawa 1-chome,  
Minato-ku  
Tokyo, Japan

The sure way to  
**ELIMINATE  
CALLBACKS**



Only Injectorall's new **BLUE LUBE** foam spray contains Oxidant -- an anti-oxidation chemical that cleans contacts, keeps them permanently clean and prevents callbacks. Eliminates picture streaking and intermittents with one application.



**INJECTORALL  
ELECTRONICS CORPORATION**

Great Neck, N.Y. 11024

In Canada:  
CANADIAN GENERAL ELECTRIC LTD.  
Ontario

Circle 28 on literature card

**SAVE MONEY**

WITH THE



**COLOR  
ECONO JIG  
KIT**



Use your 19" color tube easily assembled metal cabinet for portable, bench, or hanging operation all components — less picture tube.

**SERVICE ALL MAKES**

OF COLOR SETS WITH THE ECONO-JIG OR ANY COLOR TEST JIG. SEND FOR FREE CROSS-REFERENCE

**TELEMATIC DIV., U.X.L. CORP.**  
2245 PITKIN AVE.  
BROOKLYN, N.Y. 11207

Circle 29 on literature card

**advertisers'  
index**

B & K Manufacturing Co. ....	29
Bussmann Mfg. Div. McGraw Edison Co. ....	7
C.R.T. Equipment Co., Inc. ....	4
Chemtronics, Inc. ....	1
Eico Electronic Instrument Co. ...	35
General Electric Co. ....	31
Heath Company ....	72
Injectorall Electronics Corp. ....	62
Leader Instruments Corp. ....	63
Littelfuse, Inc. ....	Cover 4
Loral Corporation ....	74
Master Appliance Corporation ...	76
Mosley Electronics Inc. ....	8
RCA Electronic Components. Cover 3	
RCA Electronic Components ....	21
RCA Parts & Accessories ...	Cover 2
RMS Electronics, Inc. ....	47
Howard W. Sams & Co., Inc. ...	41
Sencore, Inc. ....	9, 13
Sprague Products Company ....	3
Sylvania Electric Products Inc. ...	11, 49
Tech Spray ....	44-45
TV Tech Aid ....	48
Telematic Div., UXL Corp. ....	62
Tuner Service Corporation ....	5
L. A. Tuner Exchange ....	43
Vikoa Inc. ....	73
Workman Electronic Products, Inc. ....	4, 74
Xcelite, Inc. ....	46
Zenith Radio Corporation ....	15

**antenna systems  
report**

**Indoor/Outdoor TV Antenna**

The Winegard Company has introduced a new TV antenna which can be used inside as well as out.

The new Sensor antenna is 46-inches long, measures 6-inches at its widest point and reportedly performs as well as larger antennas up to 40 miles and more from TV transmitters.



The Model SR-20 has two flat "wing-like" anodized exterior signal collectors, with solid-state circuitry enclosed in an ultra-sonically sealed Cyclocac housing, which, like the signal collectors, is totally weatherproof, according to the manufacturer.

Winegard has made available three mounts for easy installation. The first, the SRM, is a universal tripod roof mount measuring 30 inches high. The SWM is a combination wall, window and chimney mount, and the third, STM, is designed for travel trailers, mobile homes, houseboats, cruisers and other similar installations.

The list price for Model SR-20 is \$49.88, complete with a 2-set power coupler.


Circle 62 on literature card

**Tapoff/Line Stretchers**

Two new combination MATV tapoffs and line extender amplifiers have been introduced by JFD Electronics Corp./Systems Division.

Model SL-6302 provides 13.5 dB gain at VHF frequencies (channels 2 through 13) and unity (1) gain at UHF frequencies (channels 14 through 83). Model SL-6312

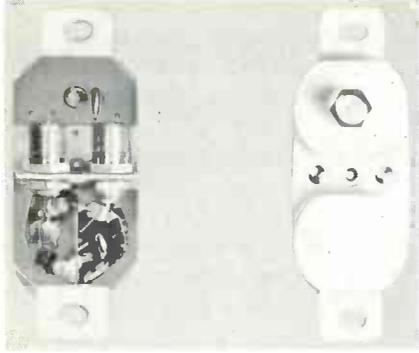provides 12.5 dB gain at UHF frequencies and passes VHF with unity gain. Both units provide an 82-channel "F" output tapoff.



Each unit can be cable-powered from any 17-volt DC, 24-ma source; however, they are designed primarily for use in JFD Smooth-line cable-powered systems. The flush-mounted line extenders reportedly can be installed anywhere on an MATV trunkline.

The units both sell for \$47.50 each.

*Circle 63 on literature card*

#### Antenna Preamplifier Series


Jerrold Electronics Corp. has made available a complete line of its 4000 Series "Powermate-Plus" preamplifiers for antenna or mast-mounting, including super-gain and super-overload versions in both 300-ohm and 75-ohm models.

These units reportedly improve picture quality in locations of normally poor TV reception and give color pictures with greater contrast, less noise and less background snow.

Designed especially for master antenna television (MATV) and home distribution systems, the units are easy to install on antenna masts in conjunction with mating indoor-mounting power supplies, according to the manufacturer. Each device is housed in an unbreakable plastic cover that also forms a natural water shed, with electrical connections located on the underside of the outdoor preamplifier.

#### 300-Ohm Models

Model 4238-S offers higher gain

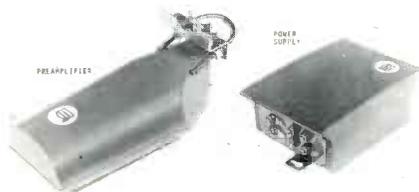

and overload for VHF, UHF and FM amplification, and sells for \$49.95. Model 4203-S is designed for VHF television and FM reception, and also passes UHF signals. It is list priced at \$46.50. Model 4083 is a special model for UHF television that also passes VHF and FM, and sells for \$38.25. All three models have two separate outputs from the power supply.


#### 75-Ohm Models

Model 4287-S has a 300-ohm

input and a 75-ohm output and is designed for all-channel reception. The price is \$47.25. Model 4207-S is for VHF and FM, but also passes UHF television. Also equipped with a 300-ohm input and a 75-ohm output, it is list priced at \$46.50. Model 4087-S7 is recommended for UHF television, although it also passes VHF and FM. It is equipped with 75-ohm output and input, and sells for \$54.95. ▲

*Circle 64 on literature card*

# Make the wiggly test.

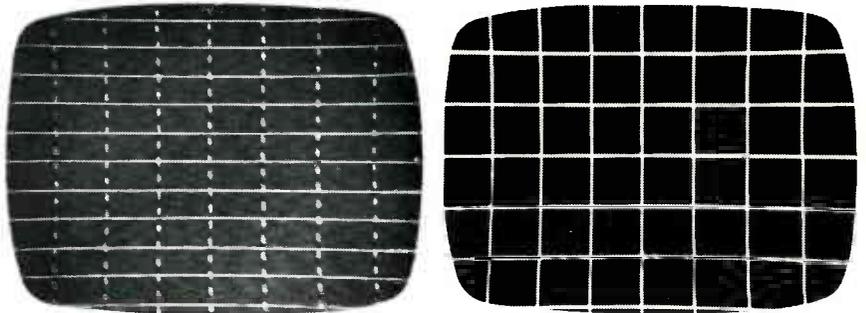


On the left, a pattern\* produced by an ordinary color bar generator. On the right, the equivalent pattern\* produced by Leader's LCG-388. Perfectly stable, the instant you turn the power on.

Flip the switch, and you can select from 15 patterns. Including the single dot, single cross, single horizontal and single vertical.

The magic is in Leader's binary counters and gates. Nobody else has them, and what a difference they make.

\$149.00, and you can make the wiggly test at your distributor's. For the one nearest you, just drop a line or call.

## Seeing is believing.

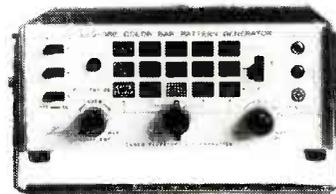

#### LEADER INSTRUMENTS CORP.

24-20 Jackson Avenue, Long Island City, N. Y. 11101/(212) 729-7411

\*As photographed.

*Circle 30 on literature card*

# Simple X-Ray Detection Instruments For TV Service Technicians

Two simple X-ray detection  
devices you can build easily  
with conventional components.

by Richard K. Stoms  
and Edward Kuerze

The development of instrumentation for measuring radiation exposure from electronic products is a major responsibility of the Division of Electronic Products, Bureau of Radiological Health. When adequate or suitable instruments for a particular application are not available, it is the responsibility of the Division's Radiation Measurements and Calibration Branch to develop them. This article describes the results of an effort to design simple and inexpensive instruments that could be used by service technicians to detect x-ray emission from television receivers.

The devices described in this article were designed to be constructed by television and electronic technicians without specialized radiation measurement instrumentation experience. The circuits can be built from commonly available, low-cost components. The use of one of these detection devices will enable a service technician to determine whether a television receiver emits excessive x-radiation and, hence, whether repair or adjustment is necessary.

The construction and use of these detection devices by service technicians will provide a partial solution to the problem of detecting excessive x-ray emission from television receivers which are now in the hands of consumers.

Robert L. Elder, Sc.D.  
Acting Director  
Division of Electronic Products  
Bureau of Radiological Health

## Purpose and Types Of Instruments

Because of the relatively high cost of instrumentation and the skills and radioactive sources needed to ensure calibration, the measurement of x rays emitted from home color television receivers has been restricted primarily to health agencies and television manufacturers. Television service personnel have not become involved in the problem other than to be advised to replace shunt regulator tubes with approved types, adjust high voltage to manufacturers' specifications, and ensure that all covers in the high-voltage section are properly installed. The question does arise as to whether the service industry should become more involved in making measurements of x-ray emission and taking any indicated corrective action. Measurements could be made on both sets housed in cabinets and chassis on service benches.

An instrument would be adequate if it were designed to indicate only whether x rays are emitted at a rate that approaches the 0.5 mR/hr rate specified as a limit by Federal regulation. The instrument need not be calibrated with a high degree of accuracy and, additionally, need not require a meter readout. Availability of such an instrument would enable service personnel to identify radiating sets and provide assurance that corrective action had reduced the radiation well below the specified 0.5 mR/hr.

This article describes two basic instrument designs. The first is a low-cost instrument capable of indicating whether a television receiver is emitting sufficient x rays to warrant corrective action. This instrument is easily assembled with low-cost components, many of

This article has been adapted from a U.S. Department of Health, Education and Welfare publication titled "Simple X-Ray Detection Instruments For TV Service Technicians." Copies of the publication can be obtained for \$3.00 each from the Clearinghouse for Federal Scientific and Technical Information, Springfield, Virginia 22151. Technical questions pertaining to X-radiation should be addressed to the Office of Information, Bureau of Radiological Health, 12720 Twinbrook Parkway, Rockville, Maryland 20852.

which are found in the ubiquitous "junk box". The instrument requires no calibration, and the readout is clear and unambiguous.

The second instrument is considerably more complex and designed for those who wish to construct a high-quality Geiger-quality Geiger-Mueller instrument for which checkout and calibration in terms of counts per minute require only commonly available service shop instrumentation.

### Operation of Geiger-Mueller Tube

There are several methods one might choose to measure x rays emanating from television receivers. One of the best from the standpoint of sensitivity and economy uses a Geiger-Mueller (G-M) tube as the sensing device.

The G-M tube instrument may be broken down into three basic sections: the sensor, high-voltage supply, and readout. G-M tubes consist of a cathode, anode, and filling gas. The filling gas is usually a mixture of a noble gas and a quenching gas such as alcohol vapor or one of the halogens. If a positive voltage is applied to the anode, the electric field is highest around the thin-wire anode and decreases rapidly as the distance from the wire increases. This high electric field gradient around the wire permits operation in the Geiger region, as described below, with a lower applied voltage than would be the case with a thick-wire anode.

Quanta of ionizing radiation, such as x rays and cosmic rays, enter the tube, and a small percentage reacts with either the tube wall or the filling gas to produce free electrons in the gas. As the voltage on the anode is raised from the cathode voltage, some of the free electrons will be collected on the positive anode and some will recombine with gas molecules. As the anode voltage is increased further, more electrons will be collected and less will recombine. If the voltage is raised even higher, a point is reached where the electrons are accelerated to a high enough velocity to knock electrons (secondary elec-

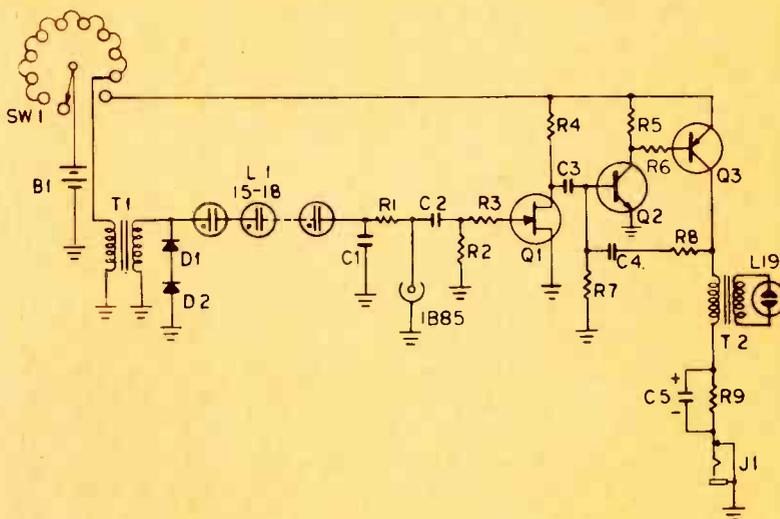


Fig. 1 Circuit diagram of circuit No. 1, a simple X-ray detection instrument.

### Parts List For Circuit In Fig. 1

B-1	—	6 volt (4 AA cells)
R1	—	10 M ohm
R2, R3	—	100 k ohm
R4, R7	—	10 k ohm
R5, R9	—	1 k ohm
R6	—	560 ohm
R8	—	15 k ohm
C1	—	0.047 $\mu$ fd 1600 V
C2	—	0.001 $\mu$ fd 2 kV
C3	—	100 pfd
C4	—	0.1 $\mu$ fd
C5	—	20 $\mu$ fd 15 V
D1, D2	—	F8 Sarkes-Tarzian
Q1	—	2N5457 (MPF 103), or 2N4221 (Motorola)
Q2	—	2N635A, 2N697, 2N706, 2N1605, 2N3567, 2N3646 or 2N5133
Q3	—	2N404, 2N414, 2N652, 2N741, 2N1038, 2N1193, 2N3133, 2N3638, 2N3645, 2N5140 or MA206
T1	—	6.3 volt filament transformer (Allied 54-1416) or output transformer (Allied 54-1449) or input transformer 100/98500 ohm (Triad A-1X) or many others typical of the above.
T2	—	Same as T1, plus input transformer (Calectro D1-719) or input transformer 10 K/2 k ohm (Lafayette 99-6124).
L1 to L18	—	Ne-2
L19	—	Ne-2 or Ne-51
SW1	—	Any 3-11 position switch, "break before make".

trons) from the gas molecules with which they collide. Thus, more electrons are collected than were originally produced by the radiation. At an even higher voltage, the electrons reach such high velocities that they cause very many secondary electrons, which are in turn accelerated to high enough velocities to produce even more electrons. Thus, an avalanche of electrons is formed and the tube is said to be operating in the Geiger region. In this case, the final number of electrons collected is approximately a constant and independent of the number and energy of the original electrons produced by the radiation. It depends only on the applied voltage within the Geiger region.

The quenching gas operates in such a way as to cause the tube to revert to its previously deionized state after the avalanche occurs. At a sufficiently higher voltage, the G-M tube will go into a state of continuous discharge which generally produces permanent damage. (An additional and more detailed description of G-M tubes is given in the source of this article.)

### Description of Circuits

Circuits for instruments useful to television technicians for indicating x-ray emission from television receivers have been designed with low cost and ease of construction as criteria. The Geiger tube chosen for the instruments to be described is the Victoreen 1B85 (available from many parts houses). The choice of the 1B85 is based upon its thin wall (36 mg/cm<sup>2</sup>, aluminum) which permits measurements of low-energy x rays. The projected area is quite close to the 10 cm<sup>2</sup> over which Federal regulations specify that the x-ray exposure rate from television receivers be integrated.

The high-voltage supply for the 1B85 should provide between 800 volts and 1000 volts DC. This is the voltage range over which the tube will operate in the Geiger region. The current required from the high-voltage source is quite minimal. A 0.047-microfarad capacitor charged to 900 volts is sufficient to

operate the G-M tube for over an hour at normal background count rates. The high-voltage supplies for the survey meters described need not be highly regulated since the variation in counting rate expected from the lowest to highest

voltage over which the tube will operate is only about 5 or 6 percent. However, some form of regulation is provided, not so much to ensure accuracy in count rate, but to protect against a catastrophic overvoltage.

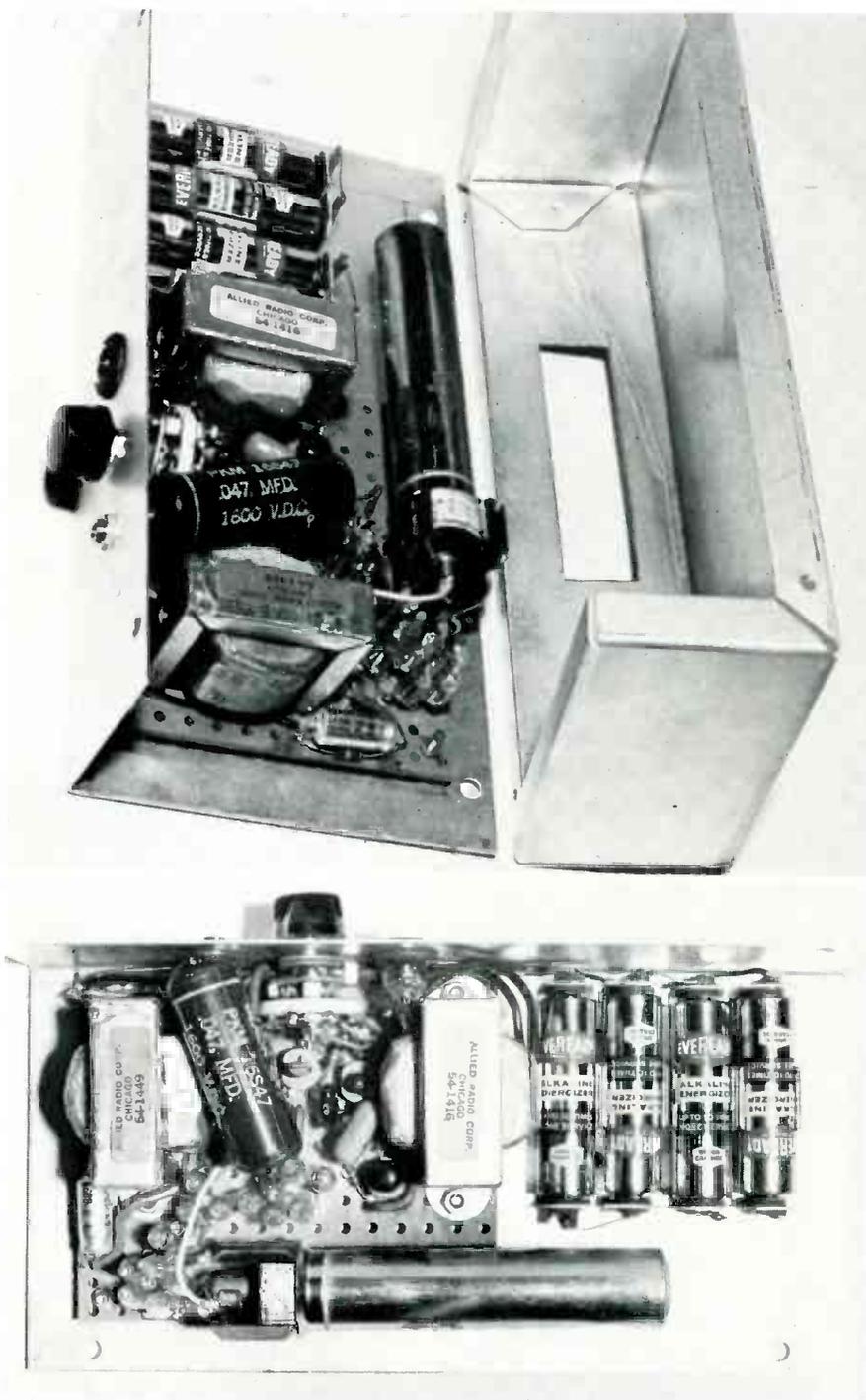


Fig. 2 Two views of an instrument built using the circuitry diagrammed in Fig. 1.

The transformers and other components for these power supplies are rather common in "junk boxes". A large number of filament, output, or interstage transformers will work. Regulation is provided by a series of low-cost NE2 neon lamps. Readout of the number of pulses per unit time, which is related to the x-ray exposure rate, may take many forms. The exact form and design of the readout affect the accuracy. For personnel or shops not equipped with radiation standards or the specialized skills necessary to properly calibrate radiation instruments, high precision and accuracy are not attainable. That is not to say that the use of an uncalibrated G-M instrument is meaningless.

Any of the instruments to be described will determine whether a television receiver is emitting x rays and indicate in a general way the source of the x rays (i.e., picture tube or high-voltage component). In all known cases of x-radiation the emissions could be reduced to near zero by high-voltage adjustments (to manufacturers' specifications), replacement of either the shunt regulator or rectifier tubes, or in a few cases, replacement of high-voltage cages or covers which had been left off. These instruments can determine whether or not a television set emits significant radiation and whether or not corrective action has eliminated that radiation.

If the detection of significant x-ray emission rather than an accurate determination of x-ray exposure rate is our goal, then a meter readout is not necessary. Most people are familiar with the popping sound from a set of headphones or small speaker associated with the use of a G-M counter. This type readout is not accurate, but it will certainly indicate large changes in count rate. The average count rate due to normal background radiation will be between about 40 and 150 counts per minute, depending on geographical location, elevation, and possible presence of slightly radioactive materials.

An x-ray field of 0.5 mR/hr produced by a shunt regulator or high-

voltage rectifier tube inside a television cabinet will produce a count rate in a 1B85 tube of about 4000 counts per minute. It is therefore obvious whether a television receiver is emitting x-rays with an exposure rate significantly above background.

#### Circuit No. 1

A very simple instrument is shown in Fig. 1. High voltage is developed by repetitively operating switch SW1. The transformer T1 can be selected from a wide range of filament, output, input, and interstage transformers that may be found in "junk boxes". Any of those shown on the parts list is adequate. Several operations of SW1 should suffice to charge capacitor C1 to its terminal voltage. Once capacitor C1 is charged, it will power the 1B85 for about an hour at background rates and over 10 minutes at 4000 counts per minute. This allows ample time to check a television set for radiation emission.

The phasing of the transformer T1 must be such that when SW1 is operated, the increasing current in the primary (low turns side), which occurs each time the wiper makes contact, induces a negative voltage at the high side of the secondary. This forward biases diodes D1 and D2 which clamp the T1 secondary to ground, and no voltage appears across the NE2 lamps. When the wiper moves off of a contact, current is suddenly cut off, producing a high positive voltage at the high side of the secondary. The diodes D1 and D2 are now back biased and the positive voltage is applied to the NE2 lamps. Note that SW1 is any type of rotary switch that has a "break before make" action. Thus, rotating SW1 will alternately close and open the primary circuit of T1. An 11-position, single-deck switch is desirable, although any number of positions will work well. SW1 should never be left in an intermediate position so that T1 primary current flows continuously, as this will rapidly discharge the batteries.

The voltage from an adequate transformer is sufficient to cause conduction in the string of NE2

lamps. Current through the lamps charges C1. When the C1 voltage is below the extinguishing voltage of the NE2 string, C1 will charge with every pulse. However, when C1 is charged to about the extinguishing voltage, the next pulse will charge it above this voltage. In this case, C1 will charge to a higher voltage during the pulse and then discharge back through the NE2 lamps until their extinguishing voltage is reached. Thus, the terminal voltage on C1 will be determined by the extinguishing voltage of the NE2 lamps.

In selecting a transformer, all one has to do is set up the high-voltage circuit as shown. An acceptable transformer will produce noticeable flashes in the NE2 lamps every time the SW2 is rotated. If no flashes occur, either the primary or secondary leads should be reversed. Also to provide some safety margin, 18 NE2 lamps should be used in selecting a transformer. D1 and D2 used by the authors are Sarkes-Tarzian F8 diodes at 800 volts peak inverse. They are avalanche protected which undoubtedly is the reason they work in this circuit. The voltage appearing across the combination is approximately the voltage on C1 (about 900 volts) plus the voltage required to ignite the NE2 string (about 1100 volts). This adds up to about 2000 volts. To allow for some safety margin, nonavalanche protected devices should be rated at about 3 kv peak inverse. Stacking nonavalanche-protected diodes in pulse circuits of this type does not usually prove satisfactory unless bleeder resistors are used. Bleeders in this circuit are not recommended.

As mentioned above, 18 NE2 lamps are used in selecting a transformer. Space should be provided on the circuit board for 18. The exact number to be used in the final circuit will depend on the specific lamps used. The method of selecting the final number is described below.

The high voltage is applied to the 1B85 through the anode load resistor R1. The value of R1 is not critical, and any value between

about 1 megohm and 10 megohms can be used. The signal produced by a Geiger discharge at the 1B85 anode is a negative pulse as shown. Its amplitude and width are primarily functions of the high voltage, load resistor, coupling capacitor, and following-stage input impedance. Typically, it is about 2 volts peak and 20 microseconds wide with the values shown. Many service oscilloscopes will not reproduce it.

Q1 is an amplifier used to in-

crease the signal level and invert the pulse to drive the monostable multivibrator Q2 and Q3. The use of a field-effect transistor (FET) in this stage is not mandatory although it performs the required function well with few components and without substantially loading the 1B85 output. A standard bipolar transistor properly biased and with an adequate frequency response will suffice in lieu of an FET.

Q2 and Q3 compose a one-shot or monostable multivibrator. Nor-

mally, R7 will cause Q2 to be cut off so that the voltage drop across R5 is zero. This in turn causes Q3 to be cut off. A positive pulse at the base of Q2, derived from the preceding stage (Q1), will start to turn Q2 on. The falling voltage at the collector of Q2 and hence at the base of Q3 will start Q3 to conduct. The increasing voltage at the Q3 collector is coupled to the Q2 base through R8 and C4 which further tends to cause Q2 to conduct. This positive feedback action will cause the collector current of Q3 to increase rapidly and remain until C4 becomes fully charged and positive feedback action ceases. This causes Q2 and Q3 to revert to the nonconducting state. The magnitudes of R7, R8, C4, and collector load of Q3 will determine the output pulse width.

A neon lamp and an earphone are shown in Fig. 1 for readout. Either or both may be used. The transformer T2 can be selected from a wide variety of types, some of which are shown in the parts list. The earphone is a low-impedance type generally sold with transistor radios, tape players, etc. Most speakers will also work quite well. Fig. 2 shows one way to assemble the meter and the method of mounting the G-M tube.

#### Circuit No. 2

For those who prefer not to operate a switch to obtain high voltage, the circuit of Fig. 3 will prove useful. This is not the most efficient circuit, but it does permit flexibility in the selection of components. The free-running multivibrator, Q1 and Q2, is quite similar to the one-shot multivibrator (MV) shown in Fig. 1. In fact, the only difference is that R7 in Fig. 1 is deleted and replaced by R1 in Fig. 3. R1 is selected so that Q1 conducts slightly. This slight conduction sends a signal through Q1 collector to Q2 base and hence through Q2 collector back to Q1 base. This positive feedback action turns Q2 on hard until C1 is fully charged and positive feedback action stops, at which time Q1 and Q2 turn off and the cycle is repeated. The on-

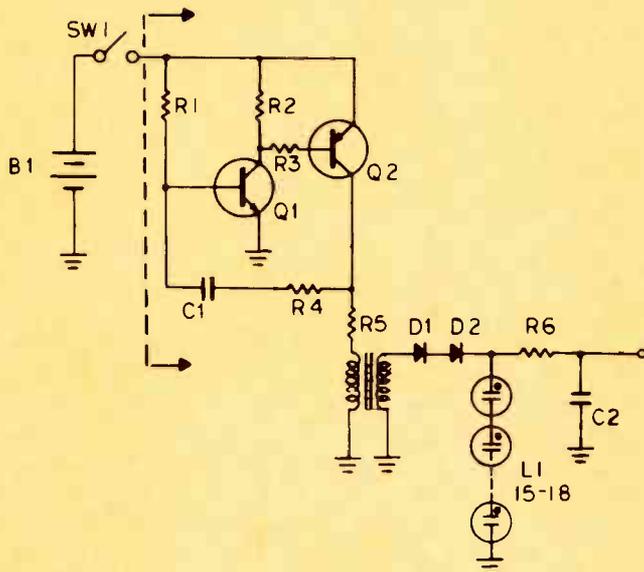


Fig. 3 Oscillator high-voltage supply employed in circuit design shown in Fig. 4.

#### Parts List For Circuit In Fig. 3

R1	—	See text
R2	—	1 k ohm
R3	—	560 ohm
R4	—	15 k ohm
R5	—	22 ohm
R6	—	100 k ohm
C1	—	0.1 $\mu$ fd
C2	—	0.047 $\mu$ fd 1600 V
D1, D2	—	F8 Sarkes-Tarzian
Q1	—	2N3567 (Fairchild)
Q2	—	2N3638 (Fairchild)
L1 to L15 or L18	—	Ne-2
Transformer	—	100 ohm/98.500 ohm (Triad A-1X)
Battery	—	12 volt

and off times of this circuit are not necessarily equal. With a fixed C1, the on time is determined primarily by R4 and the repetition rate by R1. The transformer is more critical than the one in Fig. 1 because Q2 cannot interrupt current as quickly as a mechanical switch nor can it supply as much current to the transformer as the switch.

The Triad A-1X transformer is effective in this circuit and is reasonably priced. Other transformers have worked but at the expense of a much higher battery drain, marginal voltage output, or considerably higher price. Note that the secondary operates into a standard halfwave rectifier circuit. D1 and D2 are Sarkes-Tarzian F8 diodes. The peak inverse voltage (PIV) in this case is limited by the breakdown voltage of the NE2 string (about 1200 volts). Earlier comments in regard to diode stacking also apply here, although the diodes now will have only about a 1200 PIV rating.

All the circuits, including the one in Fig. 4, should be enclosed in and grounded to a metal box since they are sensitive to electro-magnetic fields, especially that caused by the horizontal output circuit in a television receiver. A rectangular hole is cut in the side so that the G-M tube is exposed. The hole should be  $2\frac{3}{4}$  by  $\frac{3}{4}$  inch. If any RF sensitivity is evident, the hole may be covered with one layer of aluminum foil glued in place. It is recommended the high-voltage section be located as far from the input circuitry as possible.

The G-M tube poses some problems. "As received" it will have a black coating over the glass seal on the anode end. This coating can become scratched, allowing light to enter the tube. Light, especially sunlight, can cause ionization and hence the tube will count as though irradiated by x-rays. If the tube counts in the light but not in the dark, the paint should be removed with acetone or a paint remover and thoroughly cleaned with either acetone or high-purity alcohol. When dry, the glass seal should be recovered with a black silicone rub-

ber such as GE RTV-103.

The tube may be mounted in a  $\frac{3}{4}$ -inch fuse clip which is grounded. The anode connection may be made with any type of grid connector that will fit a  $\frac{1}{4}$ -inch-diameter connector, or several turns cut from a spring can be pushed over the anode connector. Connection should not be made by soldering to any part of the tube.

The thin wall and low internal pressure make the tube susceptible to crushing and denting. No attempt should be made to remove dents, since a tube may work satisfactorily if the central wire is not disturbed or the tube did not suffer an air leak. If the dent damaged the tube, it cannot be repaired. The tube should be handled only at the anode end, especially when inserting the mounting clip.

As previously mentioned, provision should be made on the circuit board for 18 NE2 lamps. The high-voltage circuit should work with all 18 lamps in series. The G-M tube should not be connected to the high voltage until the entire circuit is finished. At this time, 5 of the NE2 lamps should be shorted out with a jumper so that 13 are in series (applies to either version of the high-voltage circuit), the G-M tube should be inserted, and the circuit turned on (operate SW1 in Fig. 1 circuit). The high voltage should be too low, and there will be no output indicated on either the NE2 or earphone. The circuit should then be turned off, the jumper reconnected to place 14 NE2 lamps in series, and the circuit turned on. This should be repeated, increasing the number of neons by one each time until an output indication is obtained from background radiation. It will be necessary to wait up to 15 seconds to determine if the tube is counting since the background count rate is low and random. One more NE2 should be added in series after counting starts.

A word of caution: the high-voltage capacitor should not be shorted when it is charged and transistor Q1 (Figs. 1 and 4) is in the circuit. The resulting sudden change

in voltage can damage the gate of Q1. The transistor should either be removed if sockets are used or a lead should be connected from the gate to ground when working on the high-voltage circuit. An alternate method to bleed down the high voltage is to short it to ground through a 10-megohm resistor. This can be done with Q1 in the circuit.

### Circuit No. 3

The circuits described above are adequate for the purpose of detecting x rays that may emanate from color television receivers. They are not capable of very accurate measurement of the count rate produced by a G-M tube.

The circuit shown in Fig. 4 is capable of more accurate measurement of G-M tube counting rate. The power supply shown in Fig. 3 is used to generate the high voltage. The transistor Q1 and monostable multivibrator Q2 and Q3 are as previously described except for a change in the collector circuit of Q3.

The accuracy of this count-rate meter depends on maintaining a fixed output pulse width with decreasing battery voltage. The zener diode, D1, ensures a fixed pulse width under this condition.

The monostable output pulse is applied through D2 to an integrating circuit composed of Q4, R11, R12, R13, and C4. Q4 is a constant-current generator whose output is independent of the supply voltage, in this case the amplitude of the monostable output pulse. The current through Q4 is adjusted to approximately 0.8 ma by selecting R11. A 6-volt battery is connected to the cathode of D2 with the minus side of the battery grounded (no other voltages in circuit). R11 is selected so that a 0-1 ma meter connected across R12 and R13 reads about 0.8 mA. Changing the 6-volt battery to 12 volts should not change the 0.8 ma reading. Because of this and the zener diode D1, the supply voltage need not be regulated.

The input to the integrating network could be taken from the top of D1 rather than R9, but this

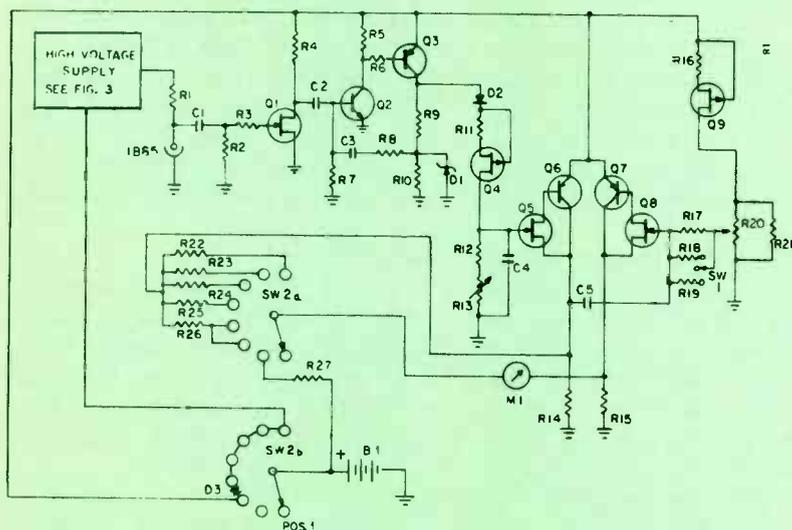


Fig. 4 Circuit diagram of Circuit No. 3, an X-ray detection device that provides more accurate measurement than the design shown in Fig. 1.

#### Parts List For Circuit In Fig. 4

R1	—	10 M ohm
R2, R3	—	100 k ohm
R4, R7	—	10 k ohm
R5-R14, R15	—	1 k ohm
R6	—	560 ohm
R8	—	6.8 k ohm
R9	—	100 ohm
R10	—	470 ohm
R12	—	82 k ohm
R13	—	50,000 ohm pot
R17	—	10 M ohm
R18	—	220 k ohm
R19	—	2.2 M ohm
R20	—	1,00 ohm pot
R11, R16, R18, R19, R21 through R27	—	See text
C1	—	0.001 $\mu$ fd 2000 V
C2	—	100 pfd
C3	—	0.001 $\mu$ fd
C4	—	0.1 $\mu$ fd
C5	—	1 $\mu$ fd paper
D1	—	1N713A
D2	—	1N914B
D3	—	1N99
Q1, Q5, Q8	—	2N5457 (MPF103) (Motorola)
Q2	—	2N5133
Q3	—	2N3638 (Fairchild)
Q4, Q9	—	2N4360
Q6, Q7	—	MPS. A66 (Motorola)
SW1	—	Single pole, double throw, center-off toggle switch
SW2	—	2 pole, 8 position rotary switch

would not provide any better regulation and would provide a lower voltage to the integrating circuit, limiting its range

In operation, C4 is charged by current pulses through Q4. Each pulse from the G-M tube results in a constant-amplitude (due to constant current Q5) and constant-width (ensured by D1) current pulse into C4. In other words, a constant amount of charge is delivered to C4 for each pulse. Constant current will flow into C4 with a voltage on C4 of the order of 6 or 8 volts. If, as is often done, C4 is charged through a resistor rather than a constant-current generator, the change in voltage on C4 is substantially different for various C4 voltages. R13 is provided to adjust the voltage output.

The C4, R12, R13 network cannot be loaded by a succeeding stage if proper operation is to be maintained. A high-impedance voltmeter is required to read the voltage on this network. A standard 10-meg-ohm-input vacuum tube voltmeter (VTVM) is satisfactory but not very portable. Commercial FET voltmeters should prove adequate, and most are portable.

If such a meter is not available, the measurement can be made with the circuit shown connected to this network. Q5 through Q9 constitute an FET voltmeter. This circuit has several advantages. The input impedance is high, linearity up to about 8 volts (with a 12-volt supply) is excellent, and about any meter with 1-ma full-scale sensitivity or better may be used. A 10-ma movement could probably be used if R14 and R15 were to be reduced to 100 ohms. This is in contrast to most FET voltmeter circuits that require a 50- or 100- $\mu$ a movement.

Q9 and R16 constitute a constant current generator. R16 is selected to produce a constant voltage drop of one volt across R20, which is used to set zero. R21 is shunted across R20 after the circuits have been completed and are operational. R21 is selected so that adjustment of R20 moves the pointer of the meter about plus or

minus 20 percent when the selector switch is on "zero" position. In operation, a voltage will appear across R14 and R15 which is dependent on the characteristics of the specific transistors used. A voltmeter connected from R14 to R15, with the gates of both Q5 and Q8 grounded (or at zero voltage), will show that one voltage is higher. If the voltage on R15 is higher, the transistors should be interchanged so that R14 voltage is higher. This is done so that the zero adjustment R20 can bring the R15 voltage up to zero the meter.

When the voltage on the gate of Q5 is increased, the voltage on R14 also increases. The voltage on R15 remains fixed so that the difference in voltage between R14 and R15 is a measure of the gate voltage of Q5. If the gate voltage of Q8 were to increase with that of Q5, the difference across R14 and R15 would be zero. The time-constant capacitor C5 couples fast changes in voltage to the gate of Q8 so that the meter reading for fast changes is zero, allowing only slow changes to cause a meter reading. Three ranges of "slowness" may be obtained with the time-constant switch SW1.

The selection of meter ranges will depend on the use of the instrument and on the selection of a meter movement. If, for example, ranges (full scale) of 1000, 3000, 10,000, 30,000, and 100,000 counts per minute are desired, the total range is 100 to 1. If a 50-millivolt meter movement is available, the upper voltage to be delivered by the integrating circuit and voltmeter circuit is 5 volts, which is well within their capabilities. A 100-millivolt movement would require a 10-volt upper range which could be obtained by an 18-volt supply voltage to the monostable multivi-

brator, integrating circuit, and voltmeter circuits. Meters with a higher millivolt requirement would necessitate restricting the ranges or arranging to switch in various values for R12 and R13 (or alternately R11).

The instrument is calibrated (in counts per minute) by disabling the high voltage or by removing the G-M tube. Resistors in the meter circuit, R22 through R26, should be selected to provide full-scale meter readings for the desired set of full-scale input voltages at the Q5 gate (e.g., 0.050, 0.150, 0.50, 1.50, and 5.0 volts full scale for the 1000 to 100,000 count-per-minute ranges mentioned previously). Input voltage can be obtained from a battery and potentiometer applied directly to the Q5 gate without disconnecting previous circuitry.

A pulse generator (negative pulse of about 0.5 to 2.0 volts peak with a rise time on the order of 0.1 microsecond and a width less than 100 microseconds) may be connected to the junction of R2 and R3. The pulse rate can be related to the meter reading by adjustment of R13. Only one point need be adjusted. The circuit in figure 5 is a convenient way to obtain 3600 counts per minute. The clip is connected to the R2-R3 junction. Usually no ground is required. If so, touching the chassis is usually sufficient.

The battery test resistor R27 on the range switch is selected to provide a full-scale meter reading with fresh batteries.

#### Operation of Instruments

Normal background count rates will probably fall between about 40 and 150 counts per minute. Any x-ray emission high enough to justify corrective action will increase this count rate substantially. If there is any question or doubt that the rate has increased, it has not.

In a conventional color television receiver, x rays are generated by the picture tube, shunt regulator, and high-voltage rectifier. Thus, a quick pass, say 30 seconds, across the picture tube face will suffice for this area. Some cathode ray tubes

(CRT's emit x rays from the funnel. In some cases these will be transmitted through the cabinet. If the tube emits from the face, it will emit over most of the face area.

The regulator tube and rectifier are usually placed on the opposite side of the cabinet from the tuner. Hence, a pass around the rear, top, side, and, if accessible, the bottom of the set in the vicinity of the high-voltage components and CRT should be all that is necessary. Sometimes the x-rays exit in a narrow beam so that it is desirable to sweep as great a percentage of the surface in the high-voltage component area as possible. Until familiarity with the measurement is acquired, it is suggested that the instrument be moved across the surface at a rate of about 1 foot in 15 seconds.

#### Summary

A simple Geiger-Mueller tube instrument may be built with inexpensive components, many of which can be found in "junk boxes". The instrument avoids the problem of calibration and interpretation of results by not having a meter display. A neon lamp or earphone, or both, are used to indicate the presence of x rays. An increase in flash rate or sound-pulse rate indicates that a television receiver emits sufficient radiation to warrant corrective action. Any definitely noticeable increase of background count rate may be judged sufficient to require correction to reduce the radiation. The instrument will also locate the area from which radiation is being emitted, thus facilitating location of the radiation source.

For those wishing more detailed information about the x-ray field, a more complex instrument is described. This instrument can be constructed and calibrated in counts per minute using equipment found in all service shops.

Neither instrument is specifically adapted for large-scale production. Instead, the emphasis is placed on an instrument design that facilitates construction by service shops and technicians without specialized equipment. ▲

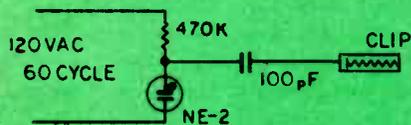


Fig. 5 Test pulse generator.

# how to get a \$400 frequency counter for \$199<sup>95\*</sup>



## ...build the new Heathkit® IB-101

- Accurate counting, 1 Hz to over 15 MHz
- Automatic trigger level for wide range input without adjustment
- Five digit readout with Hz/kHz ranges & overrange indicators give eight digit capability
- High Z input
- Computer-type integrated circuitry eliminates divider chain adjustment

The latest Heath breakthrough in low cost, high quality instrumentation. New IB-101 counts from 1 Hz to over 15 MHz; advanced integrated circuitry eliminates blinking readout & divider chain adjustment.

Overrange indicator & Hz/kHz switch give the IB-101 8-digit capability. Set the range switch to kHz & the display reads out to the nearest kHz... push the range switch to Hz and read down to the last Hz. Overage & Hz/kHz indicators light up to give error-free measurement & correct range at all times. Automatic decimal locator eliminates interpolation & figuring.

Exclusive Heath-designed input circuit uses a dual-gate, diode-protected MOSFET... provides proper triggering without adjustment from less than 100 mV to over 200 V. Input Z is 1 megohm shunted by less than 20 pF to minimize circuit loading & error. Other features include sockets for all 26 IC's & 5 display tubes... 120/240 V AC operation & convenient handle/tilt stand.

Compare the new Heathkit IB-101... then order yours. **Kit IB-101, 7 lbs. . . . \$199.95\***

**IB-101 SPECIFICATIONS:** Frequency Range: 1 Hz to greater than 15 MHz. Accuracy:  $\pm 1$  count  $\pm$  time base stability. Gate Times: 1 millisecond or 1 second with automatic reset. **INPUT CHARACTERISTICS** — Sensitivity: 1 Hz to 1 MHz, less than 100 mV rms. 1 MHz to 15 MHz, less than 250 mV rms, after 30 minutes warmup. Trigger Level: Automatic. Impedance: 1 Megohm shunted by less than 20 pF. Maximum Input: 200 V rms, DC — 1 kHz. Derate at 48 V per frequency decade. **TIME BASE:** Frequency: 1 MHz, crystal controlled. Aging Rate: Less than 1 PPM/month after 30 days. Temperature: Less than  $\pm 2$  parts in  $10^7$ /degree C. 20 to 35 degrees C after 30 minutes warmup.  $\pm .002\%$  from 0 to 50 degrees C. **GENERAL:** Readout: 5 digits plus overrange. Temperature Range: Storage; —55 to 80 degrees C. Operating; 0 to 50 degrees C. Power Requirements: 105-125 or 210-250 V AC, 50/60 Hz, 8 watts. Cabinet Dimensions: 8 1/4" W x 3 1/2" H x 9" D not including handle. Net Weight: 4 1/2 lbs.

HEATH COMPANY, Dept. 25-12  
Benton Harbor, Michigan 49022



a Schlumberger company

Enclosed is \$ \_\_\_\_\_, plus shipping.

Please send model (s) \_\_\_\_\_

Please send FREE Heathkit Catalog.  Please send Credit Application.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

\*Mail order prices; F.O.B. factory. Prices & specifications subject to change without notice. TE-232

Circle 32 on literature card

## productreport

for further information on any of the following items, circle the associated number on the reader service card.

### "The Noise Eliminator"

Omega-t Systems, Inc. has announced "the noise eliminator", a noise blanker for use with CB and business-band radios.

For use on mobile or base stations, the noise eliminator, is placed between the antenna and receiver, and reportedly extinguishes external impulse noise, generated by automobile ignition systems, power lines, general electrostatic and radio hash, without interrupting the desired signal.



"The noise eliminator" increases side-channel rejection, which reduces splatter and bleed-over from adjacent channels, according to the manufacturer.

The unit's preselector control enhances the channel selection so the desired channel is amplified while others are attenuated. There also is a blanking threshold sensitivity control with a numbered log scale; this control includes an on/off switch.

The unit features 29 solid-state components, and operates on standard 12-volt DC power at 0.175 amps. The unit sells for \$69.95.


Circle 65 on literature card

### Hand Cleaner

A new hand cleaner which reportedly does not effect the dielectric strength of insulating materials and leaves no corrosive residue on hands to damage sensitive electronic components has been announced by CRC Chemicals.


(Continued on page 74)

Model 5410  
30db Gain  
VHF Amplifier

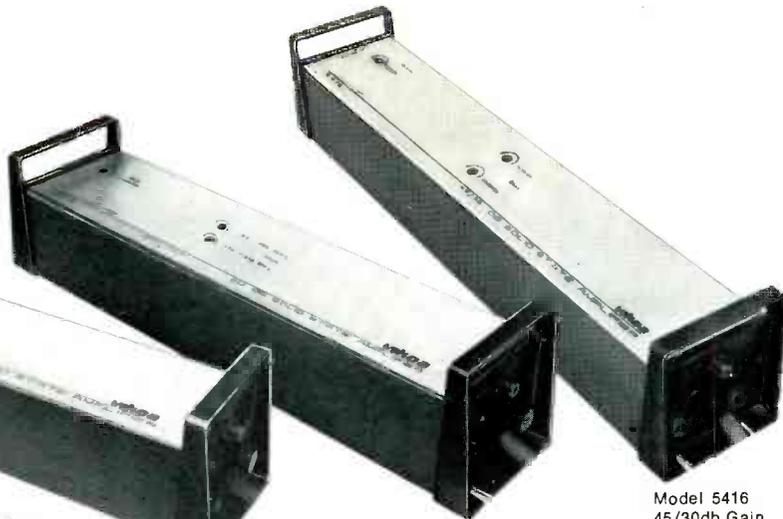

Model 5415  
30db Gain  
UHF/VHF Amplifier

Model 5416  
45/30db Gain  
UHF/VHF Amplifier

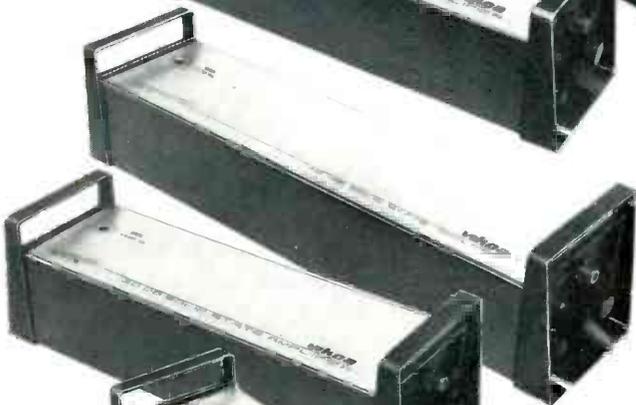


Model 5414  
45db Gain  
UHF Amplifier

Model 5411  
45db Gain  
VHF Amplifier

Model 5413  
30db Gain  
UHF Amplifier

# **vikoa** CUSTOMIZED MATV POWER

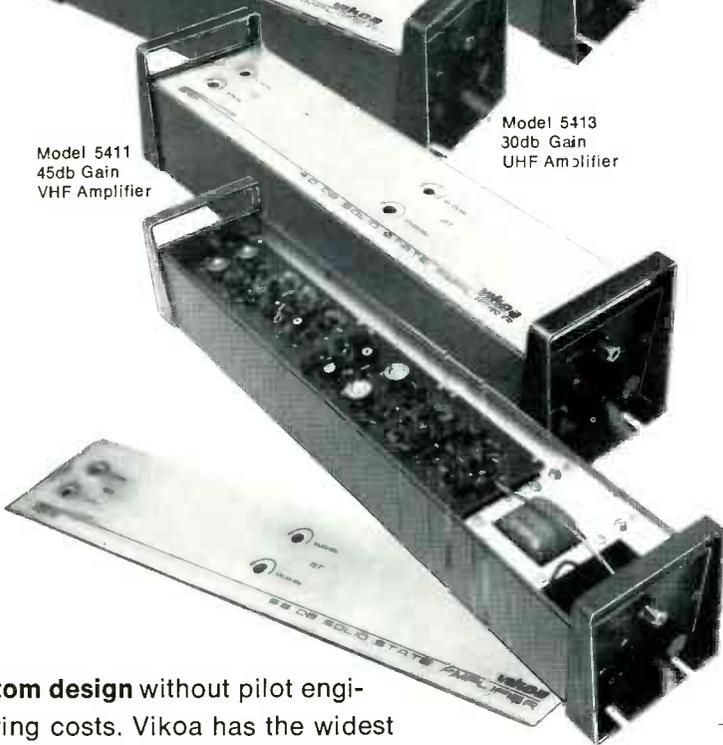


Model 5412  
55db Gain  
1 Volt  
VHF Amplifier

**Custom design** without pilot engineering costs. Viko has the widest range of options available in the industry, fit the amplifier to your system, rather than fitting your system to an amplifier. 30 to 55db gain available, VHF and/or UHF, and

+47dbmv to +60dbmv (one full volt) output capability. These completely modular amplifiers feature low noise figure, flat response, and the dependability of silicon solid-state devices

mounted on military grade glass substrates. With attractive aluminum housing and cast end bells for rail type mounting, these low profile units can be mounted in the most inaccessible locations. For your next project get the best.

**vikoa**  
technically the one.

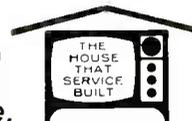

COMMUNICATIONS DIVISION: New York, N. Y. (212) 943-5793 • Hoboken, N. J. (201) 656-2020 • San Francisco, Calif. (415) 342-5239 • Dallas, Tex. (214) 276-1181 • Viko of Canada, Limited (514) 341-7440

Circle 33 on literature card

Division of Loral Corporation



# Fix it. Forget it.

We wind our tv-replacement capacitors with computer-grade aluminum foil for your protection. They last longer in your customer's set and they won't deteriorate even at high tv operating temperatures. Yet, they're priced for tv service.

**Elmenco & Arcolytic Capacitors—mica, Mylar, electrolytic, ceramic.**

Free: Replacement Guide, Cross Reference, Catalog. Call or write today.

LORAL DISTRIBUTOR PRODUCTS  
Pondhill Industrial Park  
Great Neck, New York 11022  
516 466-5500

Circle 34 on literature card

SOLID STATE

## ONE GUN BOOSTER

FOR COLOR TV

**EXTENDS COLOR GUN LIFE**      **RESTORES RED, BLUE OR GREEN BRILLIANCE**

**EASY TO INSTALL**  
(INSTRUCTIONS ON BACK)

WORKMAN *Electronic* PRODUCTS, INC.  
SARASOTA FLORIDA

WEAK

SERVICE LINE

BEFORE

BOOSTED

SERVICE LINE

AFTER

installation of  
**ONE GUN BOOSTER**  
Boosts the one weak color needed for a **BALANCED** color picture.

MANUFACTURED BY  
**WORKMAN** *Electronic* PRODUCTS, INC.  
SARASOTA FLORIDA

Circle 35 on literature card



ELECTRICAL  
**ANTISEPTIC  
HAND  
CLEANER**

No. 2065

RUB ON  
WIPE OFF  
CLEANS WITH OR  
WITHOUT WATER

NET WT. 5 OZ.

Electrical Antiseptic Hand Cleaner will effectively remove creosyl, insulating varnish, wire-drawing lubricant, ink, grease, oil adhesives and most other types of grime encountered by electronic technicians, according to the manufacturer, yet contains no harsh solvents or abrasives that irritate the skin. Skin conditioning lanolin and chloroxylenol, an antiseptic agent that inhibits bacterial growth, are included in the hand cleaner formula. Price is 55 cents per tube, or \$6.00 per dozen tubes.

Circle 66 on literature card

### Speaker Muting Relay

The new speaker muting relay, available from the Antenna Development Co., is designed for use in areas where two radio receivers each are tuned to different stations carrying unrelated information.

This device provides an automatic tuning system, to avoid background pick-up of one receiver while transmitting the source of the second receiver. According to the manufacturer, this device is connected to each of the two receivers and to the microphone. When the operator is speaking to one station, the receiver tuned to the second source is muted to allow conversation free of background crosstalk and to prevent feedback of power during transmission.

All components reportedly are en-



capsulated in the case to prevent malfunctioning from transmitted vibration. Also, the unit is hermetically sealed in a cadmium-finished case to prevent moisture seepage internally, rust externally. Maximum power is 5 watts continuous, and load resistance is 4 ohms.

The unit measures 2 inches X 2 inches X 1 1/4 inches, weighs 5 oz. and sells for \$18.95.

Circle 67 on literature card

### VHF Radiotelephone

Pearce-Simpson, Inc. has introduced the new BIMINI VHF, a VHF radiotelephone which transmits 25 watts of power.

The 8 1/2-lb., 6-channel unit uses plug-in sockets and integrated circuits to facilitate on-board servic-



ing. A plug-in power lead is provided for easy removal and safe-keeping. Also incorporated in the unit is a press-to-talk telephone handset and low-power switch.

The unit is priced at under \$300.00. ▲

Circle 68 on literature card

## ANTENNAS

100. *Jerrold Electronics Corp.*—has released a 56-page full-line general distributor catalog which includes a guide to MATV systems and nearly 300 Jerrold products. The catalog price is \$1.00.
101. *Jerrold Electronics Corp.*—Catalog S, titled "Systems and Products for TV Distribution," lists specifications of this manufacturer's complete line of antenna distribution products, including antennas and accessories, head-end equipment distribution equipment and components, and installation aids.

## AUDIO

102. *Jensen Manufacturing Div.*—has issued an 8-page, catalog, No. 1090-E, which describes application of 167 individual speaker models. Special automotive, communications, intercom and weathermaster speakers, plus a complete line of electronic musical instrument loudspeakers are featured.
103. *Shure Brother, Inc.*—has published a 4-page brochure, "Professional Sound Systems in High Schools, Colleges, and Universities," No. AL 398, describing the company's Vocal Master Sound System and how it helps solve public-address problems.
104. *Telex Communications Div.*—has issued a new catalog, No. BI-2166-2, covering over 30 general communication and dictation headphones and other private-listening devices plus accessories. The 8-page, 2-color catalog includes production information, photographs and price.

## COMMUNICATIONS

105. *Sonar Radio Corp.*—Catalog titled "Sonar Business Radio, FM Monitor Recivers and CB Equipment" lists specifications and prices of this manufacturer's line of transceivers, receivers and communications accessories.

## COMPONENTS

106. *Loral Distributor Products*—has made available a 24-page electrolytic capacitor replacement guide. The catalog features replacement products by the original manufacturer part number.\*
107. *General Electric Tube Department*—has released a new 52-page Entertainment Semiconductor Almanac, No. ETRM-4311F. The almanac contains approximately 20,000 cross references from JEDEC, or OEM part number to GE part numbers for universal replacement semiconductors, selenium rectifiers for color TV, dual diodes, and quartz crystals.\*
108. *International Electronics Corp.*—has announced a 4-page folder featuring axial lead (TAD series) and upright radial lead (PCD series) low-voltage 85-degree C miniature aluminum electrolytic capacitors. Capacitance, voltage and size specifications are clearly shown for easy reference.
109. *Microtran Co., Inc.*—is offering a 32-page catalog which lists transformers, inductors, and torroids for both commercial and MIL construction. All transformers are shown with detailed ratings and outline drawings. Full pricing and quantity discount is also available.
110. *Motorola, Inc.*—has made available a HEP cross reference guide catalog No. HMA07 which lists replacements for over 27,000 different semiconductor device type numbers available through authorized HEP suppliers.

111. *Semitronics Corp.*—has a new, revised "Transistor, Rectifier, and Diode Interchangeability Guide" containing a list of over 100 basic types of semiconductors that can be used as substitutes for over 12,000 types. Include 25 cents to cover handling and postage.
112. *Stancor Products*—pocket-size, 108-page "Stancor Color and Monochrome Television Parts Replacement Guide" provides the TV technician with transformer and deflection component part-to-part cross reference replacement data for over 14,000 original parts.
113. *Sylvania Electric Products Inc.*—a 73-page guide which provides replacement considerations, specifications and drawings of Sylvania semiconductor devices plus a listing of over 35,000 JEDEC types and manufacturers' parts numbers. Copies are \$1.00.\*
114. *General Electric*—a 12-page, 4-color, illustrated "Picture Tube Guidebook", brochure No. ETRO-5372, provides a reference source for information about GE color picture tube replacements and tube interchangeability.\*
115. *Workman Electronic Products, Inc.*—has released a 32-page, pocket-size cross reference listing for color TV controls. 105 Workman part numbers are listed in numerical order with specifications and illustrations of the part.\*

## TECHNICAL PUBLICATIONS

116. *Howard W. Sams & Co., Inc.*—literature describes popular and informative publications on radio and television servicing, communications, audio, hi-fi and industrial electronics, including their 1970 catalog of technical books on every phase of electronics.\*
117. *Sylvania Electric Products Inc., Sylvania Electronic*

(Continued on page 76)

*Components Div.*—has published the 14th edition of its technical manual, which includes mechanical and electrical ratings for receiving tubes, television picture tubes and solid-state devices. The price of this manual is \$1.90.\*

**TEST EQUIPMENT**

- 118. *B & K Mfg. Div., Dynascan Corp.*—is making available an illustrated, 24-page, 2-color Catalog BK-71, featuring B&K test equipment, with charts, patterns and full descriptive details and specifications included.\*
- 119. *Eico*—has released a 32-page, 1970 catalog which features 12 new products in their test equipment line, plus a 7-page listing of authorized Eico dealers.\*
- 120. *Mercury Electronics Corp.*—14-page catalog provides technical specifications and prices of this manufacturer's line of Mercury and Jackson test equipment, self-service tube testers

testers, test equipment kits and indoor TV antennas.

- 121. *Sencore, Inc.*—has issued its 12-page, 1970 catalog, Form No. 517, which describes the company's complete line of test instruments, and features 5 new instruments, with performance data and prices included.\*
- 122. *Triplett Corp.*—Bulletin No. 51570, a two-page technical bulletin which provides the specifications and price of Triplett's new Model 602 VOM.

**TOOLS**

- 123. *General Electric*—has issued 2-page brochure No. GEA-8927, describing the features of GE's new soldering iron.\*
- 124. *Jensen Tools and Alloys*—has announced a new catalog No. 470, "Tools for Electronic Assembly and Precision Mechanics." The 72-page handbook-size catalog contains over 1,700 individually available items.

125. *Xcelite, Inc.*—has published a 2-page illustrated Bulletin N670, which introduces two new reversible ratcheting handles for use with more than 60 of the company's available Series "99" nut-driver, screwdriver and special purpose blades.\*

126. *Xcelite Inc.*—Bulletin N770 describes this company's three new socket wrench and ratchet screwdriver sets.\*

\*Check "Index to Advertisers" for additional information. ▲



"WHAT DO YOU MEAN YOU GUESS YOU MADE A LITTLE MISTAKE?"

no other  
heat gun...  
**offers  
all these  
attachments!**

Attachments to speed your job... attachments that tailor Master heat gun airflow precisely to your needs... attachments that fit any existing Master flameless heat gun. No other line offers so many choices... including the exclusive patented cone for 1/4" concentrated heat, optional adjustable base, convenient carrying case, and the only U.L. listed gun available. Send for free 12 page catalog.



for shrinking thermoplastic tubing and film, curing, forming, melting, drying, soldering.

**MASTER HEAT GUNS**

Racine, WI 53403

Circle 36 on literature card

# 10 million reasons why it pays to promote matrix, the brightest, sharpest color picture tube in RCA history!


Reasons 1 to 10,000,000. Large-screen MATRIX can upgrade the performance of at least 10 million color TV sets now in use. The RCA 25BCP22 is a direct replacement for the 25XP22, 25AP22A, 25BGP22, 25BAP22 (Chromacolor), and 20 other industry types! Giant-screen sales potential for the RCA MATRIX—practically unlimited!

More RCA Color Picture Tubes are stocked and

sold by distributors than any other color picture tubes in the industry. So, MATRIX is more readily available to you no matter where you are, to give your customers faster service and ring up more profitable sales.

MATRIX is the brightest and sharpest color picture tube in RCA history!

Here's why:

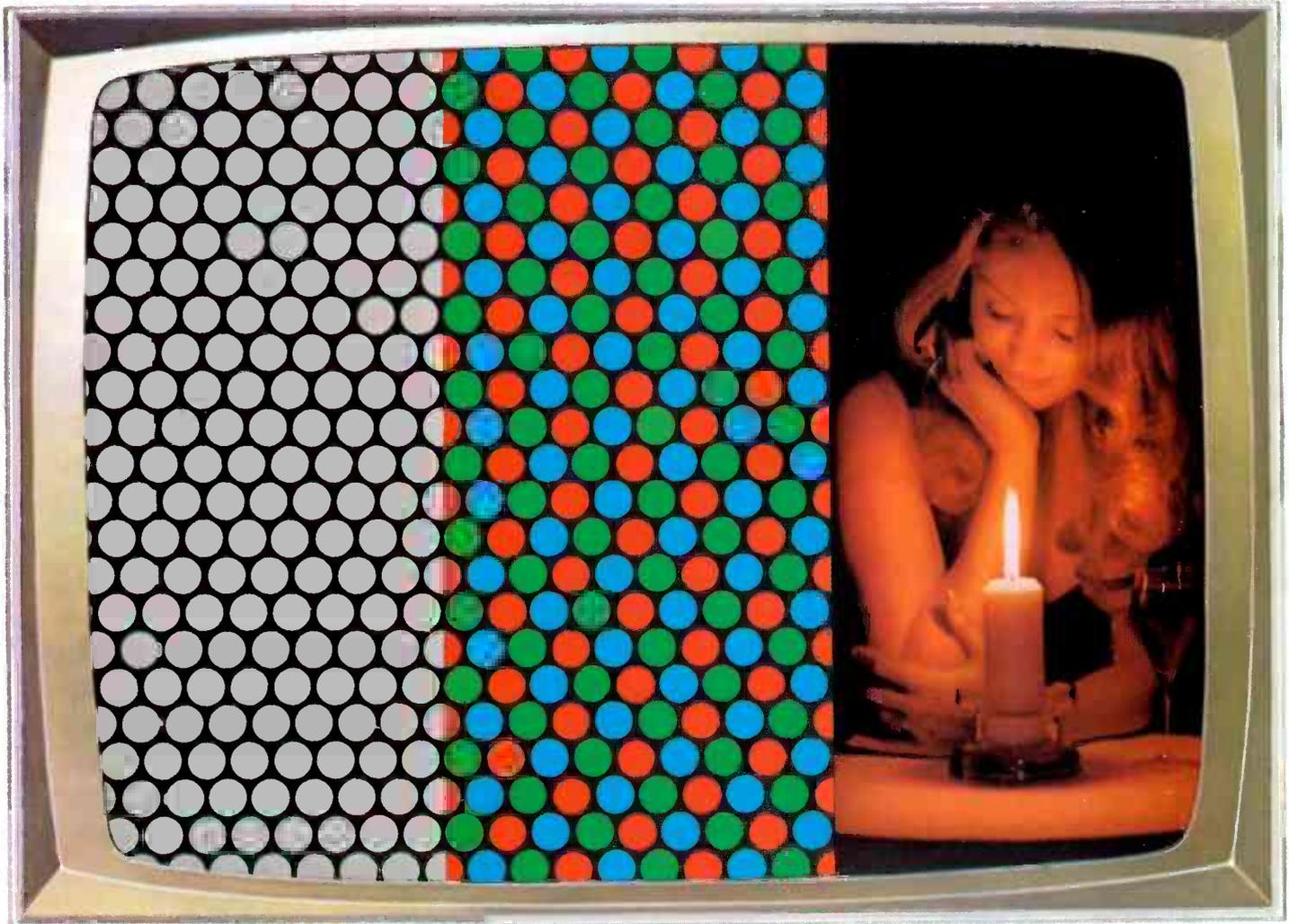

#### The RCA jet-black matrix\*

It soaks up room-light normally reflected back at the viewer from the face of the tube. Result: brighter pictures because now there's no need to "filter out" brightness to maintain contrast under strong room-light conditions.

#### The RCA MATRIX phosphor-dot process\*

First, we developed brilliant new phosphors and a unique screening process incorporating a jet-black matrix. Then we deposited the 1,200,000 red, green, and blue high-intensity phosphor dots precisely within the black matrix. Result: brightness doubled with dramatic improvement in contrast and clarity.

#### The RCA MATRIX picture\*\*

Spectacular! In operation, a new, unique high-resolution gun "shoots" the phosphors with more energy than any other gun previously available. Result: black matrix + phosphors + high-resolution gun = maximum sharpness over the entire brightness range, truer colors under all viewing conditions.



New 4-color consumer flyer on MATRIX is available from your RCA Distributor.  
RCA | Electronic Components | Harrison, N. J. 07029

\*Magnified drawing \*\*Simulated

# THE SAFEST SETS YOU'LL EVER SERVICE HAVE LITTELFUSE CIRCUIT BREAKERS.



Standard Catalog Part No.	Hold Rating (Amps.)	Standard Catalog Part No.	Hold Rating (Amps.)
815.650	.490	8152.75	1.92
815.800	.600	815003	2.1
815001	.650	8153.25	2.2
8151.25	.930	815004	2.5
81501.5	1	81504.5	3
8151.75	1.2	815005	3.25
815002	1.4	815006	3.9
8152.25	1.5	815007	4.14
81502.5	1.65		

Littelfuse TV set circuit breakers are the safe, reliable, money saving short-circuit-problem-solvers . . . 17 available models—exact replacements—cover the entire range of domestic television sets.

Littelfuse circuit breakers are available from your distributor—singly or in bulk.

Super-simple in operation—the sensitive breaker flips open under current overloads protecting the circuitry. Reset by merely pressing the red reset plunger. A built-in “trip free” feature of Littelfuse breakers prevents forced closing when dangerous overload currents are present.

Nothing's more reliable than a Littelfuse circuit breaker. Thermal-responsive Littelfuse breakers are dual operated bi-metallic devices providing temperature compensation over a wide range of ambient temperature variation. Molded phenolic construction eliminates warping and distortion of the base, maintaining exact factory set calibrations. The unit is completely enclosed to protect critical moving parts from dirt and other foreign matter.

Any TV set you're likely to service will take Littelfuse circuit breakers.

They'll flip for safety.

You'll flip for satisfaction.

# LITTELFUSE

DES PLAINES, ILLINOIS 60016

SUBSIDIARY OF TRACOR, INC.  
Circle 2 on literature card