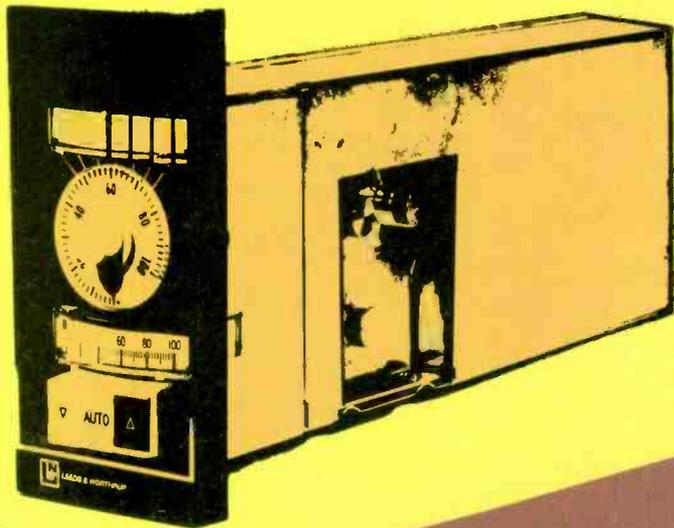


# Electronic Servicing

**Industrial electronic controllers:**  
• where they're used  
• how they work



Measuring standing waves

---

RCA power supplies





*As 1979 draws to a close, we pause and reflect with appreciation on the support and patronage received again this year from the friends of PTS.*

*On behalf of PTS employees nationwide, may I wish you the happiest of holidays and a prosperous New Year.*

Roland F. Nobis  
President, PTS Electronics, Inc.



**PTS ELECTRONICS, INC.**  
The Only Name You Need To Know

For the location nearest you, see the servicer center guide on the next page.  
Circle (1) on Reply Card

# Holiday Greetings From PTS

## MIDWEST

**BLOOMINGTON, IN**  
Jack Craig, General Manager  
**CLEVELAND, OH**  
Tom Young, Regional Manager  
**KANSAS CITY, KS**  
George Rice, General Manager  
**MINNEAPOLIS, MN**  
Alan Westerman, General Manager  
**ST. LOUIS, MO**  
John Tucker, General Manager  
**DETROIT, MI**  
David Fuhrmann, General Manager  
**GRAND RAPIDS, MI**  
Bruce Nelson, General Manager  
**CINCINNATI, OH**  
Bill Terrell, Regional Manager  
**MILWAUKEE, WI**  
Robert L. Clevenger, General Manager  
**INDIANAPOLIS, IN**  
Terry Banks, General Manager  
**DAVENPORT, IA**  
Douglas Arthur, General Manager  
**OMAHA, NE**  
Donald Reusch, General Manager  
**CHICAGO, IL**  
Pini Nannar, General Manager  
**COLUMBUS, OH**  
Ron Fraudenburg, General Manager

## SOUTH

**CHARLESTON, SC**  
(Roger) Steve Weaver, General Manager  
**JACKSONVILLE, FL**  
Robert Gidcumb, Regional Manager  
**WASHINGTON, D.C.**  
Randy McNaught, General Manager  
**CHARLOTTE, NC**  
Max Smith, General Manager  
**BIRMINGHAM, AL**  
Kenneth Hair, General Manager  
**MEMPHIS, TN**  
John Postlewaite, General Manager  
**NORFOLK, VA**  
Duane Seger, General Manager  
**NEW ORLEANS, LA**  
Richard A. Hammer, General Manager  
**TAMPA, FL**  
Michael Jones, General Manager  
**NASHVILLE, TN**  
Roger Floyd, Regional Manager

## PACIFIC

**SACRAMENTO, CA**  
J.M. Rollison, Regional Vice President  
**SAN DIEGO, CA**  
Ernie Clark, General Manager  
**LOS ANGELES, CA**  
Steven D. Cooper, General Manager  
**PORTLAND, OR**  
Art Uhlmeyer, General Manager  
**SEATTLE, WA**  
Paul Jones, General Manager

## NORTHEAST

**SPRINGFIELD, MA**  
Murl Reeves, Regional Vice President  
**PHILADELPHIA, PA**  
Eduardo Arroyo, General Manager  
**PITTSBURGH, PA**  
Cliff Weigand, Regional Manager  
**ELMWOOD PARK, NJ**  
Charles Risner, General Manager  
**BOSTON, MA**  
James Cornwell, General Manager  
**BUFFALO, NY**  
Steve Cohen, General Manager  
**BALTIMORE, MD**  
Jack (Jay) Jacobs, General Manager

## MOUNTAIN

**DENVER, CO**  
Carlen DeJong, Regional Vice President  
**SALT LAKE CITY, UT**  
James Hopp, General Manager  
**PHOENIX, AZ**  
Larry Smith, General Manager  
**TUCSON, AZ**  
Don Bovey, General Manager

## SOUTHWEST

**LONGVIEW, TX**  
Louis Stangle, Regional Manager  
**OKLAHOMA CITY, OK**  
David Hoehner, General Manager  
**HOUSTON, TX**  
Hadley Postlewaite, General Manager



PTS ELECTRONICS, INC.

## Electronic Servicing

Editorial, advertising and circulation correspondence should be addressed to P.O. Box 12901, Overland Park, KS 66212 (a suburb of Kansas City, MO); (913) 888-4664.

### EDITORIAL

Bill Rhodes, *Editorial Director*  
Carl Babcoke, *Editor*  
Mary Thornbrugh, *Associate Editor*

### ART

Dudley Rose, *Art Director*  
Linda Franzblau, *Graphic Designer*

### CIRCULATION

John C. Arnst, *Director*  
Evelyn Rogers, *Manager*

### ADMINISTRATION

George H. Seferovich, *President*  
George Laughead, *Publisher*

### ADVERTISING

Cameron Bishop, *Marketing Director*  
Pam Morris, *Production*

Regional advertising sales offices listed near Advertiser's Index.



Member,  
American Business Press



Member,  
Audit Bureau  
of Circulation

**ELECTRONIC SERVICING** (USPS 462-050) (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, Overland Park, KS 66212. Controlled Circulation Postage paid at Shawnee Mission, KS 66201. Send Form 3579 to P.O. Box 12901, Overland Park, KS 66212.

**ELECTRONIC SERVICING** is edited for technicians who repair home-entertainment electronic equipment (such as TV, radio, tape, stereo and record players) and for industrial technicians who repair defective production-line merchandise, test equipment, or industrial controls in factories.

Subscription prices to qualified subscribers: 1 year—\$10, 2 years—\$16, 3 years—\$20, in the USA and its possessions. All other foreign countries: 1 year—\$13, 2 years—\$22. Subscription prices to all others: 1 year—\$25, 2 years—\$50, in the USA and its possessions. All other foreign countries: 1 year—\$34, 2 years—\$68. Single copy price \$2.25; back copies \$3.00. Adjustment necessitated by subscription termination to single copy rate. Allow 6 to 8 weeks delivery for change of address. Allow 6 to 8 weeks for new subscriptions.



INTERTEC PUBLISHING CORP.

## Creative Electronics

ESR METER checks electrolytics IN-CIRCUIT and is TV shop FIELD-TESTED:

Used it 3 months; it only missed once—Marinette, Wis. (Typical) It's fantastic—St. Joseph, Mo. The most fantastic instrument I've ever bought—Billings, Mt. Please ship another; very satisfied—Glen Rock, Pa. Squeal & no sync: 3 bad caps in B+ & AGC; Many Thanks—Taos, N.M. Please rush; heard good reports—Hicksville, N.Y. One tremendous meter—Alexandria, Minn. Send your Super meter; heard about it—N. Olmsted, Ohio. Love that ESR Meter—Acton, Mass. Used it intensively for 30 days; it's been 100% effective—Pittsburgh, Pa. I understand that if I'm not completely flabbergasted, you will refund my money—Sanford, Fla. (Refund not requested)

60-day Satisfaction Guarantee.

Send check or M.O. or call  
(313) 435-8916 for COD

Or write for free brochure to:

## Creative Electronics

ESR Brochure ES 11-79 \$88.00  
1417 N. Selfridge postpaid  
Clawson, Mich. 48017 in USA

Circle (4) on Reply Card

## APPLIANCE REPAIR BOOKS



Thirteen Handbooks written in easy-to-understand language by experts in the service field with illustrations and diagrams! Acclaimed by instructors and professionals alike! How to diagnose and repair air conditioners, refrigerators, washers, dryers, ranges, microwave ovens, dishwashers, vacuum cleaners, electrostatic air cleaners, RV gas appliances, hair dryers, motors, water heaters, coffeemakers, can openers, floor polishers, steam irons, food mixers, lawn care appliances, electric knives, electric and digital clocks and many others. Also fundamentals of solid state, setting up a shop, using test instruments and more. Only \$2.65 to \$4.90 ea.

SEND FOR FREE PRICE LIST

Gamit, Dept. ES

110 W. St. Charles Road,  
Lombard, Illinois 60148

Circle (5) on Reply Card

---

---

## Maintenance

### 11 Electronic controllers in industry

*By Dale R. Patrick*

Functions and circuit operation of several electronic controllers are described.

### 20 Reports from the Test Lab

*By Carl Babcock*

Hitachi model V-302 30MHz dual-trace scope proved to have the features and excellent performance needed for present-day servicing.

---

---

## Servicing

### 22 RCAs unique scan rectification

*By Gill Grieshaber*

Two sets of Siamese Twin rectifiers are in the CTC99 low-voltage power supplies. Duty cycle of SCR conduction regulates the 123V supply.

### 28 Technical Notebook

*By J. A. "Sam" Wilson*

In this final article, Sam presents the prize-winning counter design, explains the j-operator and corrects an exam answer.

### 31 Measuring standing-wave ratio

*By Joseph J. Carr*

The origin of standing waves is discussed, and precautions are given for obtaining accurate SWR readings with certain meter types.

---

---

## Departments

- |                      |                          |
|----------------------|--------------------------|
| 4 Electronic Scanner | 39 Catalogs & Literature |
| 5 Symcure            | 40 New Products          |
| 6 People in the News | 42 Test Equipment        |
| 7 Readers Exchange   | 43 Photofacts            |

---

---

## About the cover

Graphic design by Linda Franzblau

© Copyright, 1979, by Intertec Publishing Corporation. All rights reserved. Material may not be reproduced or photocopied in any form without written permission of publisher.

# ELECTRONICS UPGRADING Seminars

**EASTERN Sessions - PITTSBURGH PA**

**WESTERN Sessions - LOS ANGELES CA**

CONSUMER/DEALER TECHNICIANS  
Pittsburgh - March 13-15, 1980  
Los Angeles - April 14-16, 1980

INDUSTRIAL MAINTENANCE TECHNICIANS  
Pittsburgh - March 19-21, 1980  
Los Angeles - April 8-10, 1980

SPECIAL OPTION - VTR Servomechanism Servicing  
Pittsburgh - March 16 or 22 / Los Angeles 11 or 13

Consumer or industrial electronics upgrading made easy.  
Unique, concise tell-and-show methods, plus hands-on experience,  
place new electronics technology at your fingertips.

## So VITAL no electronics servicer should miss it!

### SUMMARY OF THREE-DAY SEMINAR

**DAY 1 - TRIGGERED SCOPES**  
Hands-On Workshop

Learn to manipulate modern scopes wisely and knowledgeably. Speed up troubleshooting of even the most complex equipment. This familiarization program explains controls for CRT, vertical input, time base, and triggering...plus advanced scope techniques. Scope displays become easy to analyze after this day-long session, with Forest Belt instructing.

**DAY 2 - SOLID-STATE UPGRADING and Updating**

Gain unexpected insight into new and established solid-state devices and technology. Practical, entertaining tips on solid-state circuitry teach you how to troubleshoot quickly. Industrial maintenance session covers higher-power solid-state devices and applications. Wayne Lemons instructs.

**DAY 3 - DIGITAL ELECTRONICS**  
for Home or Industry

Clear up mysteries of digital electronics: gates, flip-flops, R-S stages, truth tables, and more. Practical help in troubleshooting digital circuits. Instruments that make servicing clear and direct. An information-packed day that puts you on top of digital technology, whether for consumer or industrial electronics. James R. Manery and Forest Belt instruct.

VTR Servomechanisms - OPTIONAL (Separate Fee of \$150)

Take the uncertainty and frustration out of VTR servicing. Forest Belt guides you step-by-step through the electronic heart of motor control in Beta and VHS video recorders. Truly understand the unusual three-phase, electronically commutated, direct-drive DC motor that spins the helical-recording heads drum. On the day industrial technicians attend, U-Matic will be treated too.

**FEES:**

Consumer/Dealer Tech Session  
Pittsburgh or Los Angeles \$ 795 \*  
  
Industrial Tech Session  
Pittsburgh or Los Angeles \$ 850 \*  
  
VTR Servomechanisms Session  
Pittsburgh or Los Angeles \$ 150 †

**FEES INCLUDE:**

† \* Timely training  
† \* Best teachers  
† \* Carry-home manual  
\* Hands-on experience  
† \* Certificate of training  
\* All workshop materials and functions  
\* Hotel room (double-occupancy)  
\* Meals † Lunch only

### Here's my enrollment.

NAME \_\_\_\_\_ AGE \_\_\_\_\_  
COMPANY \_\_\_\_\_ TITLE \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_  
PHONE ( ) \_\_\_\_\_

### I want to attend:

- Consumer/Dealer Technician Session  
 Pittsburgh  Los Angeles \$ 795
- Industrial Maintenance Technician Session  
 Pittsburgh  Los Angeles \$ 850
- VTR Servomechanisms Session - Consumer  
 Pittsburgh  Los Angeles \$ 150
- VTR Servomechanisms Session - Commercial  
 Pittsburgh  Los Angeles \$ 150

TOTAL Enclosed \$ \_\_\_\_\_

Check number \_\_\_\_\_ Money Order \_\_\_\_\_



Mail to: **Liaison**  
P. O. Box 40821  
Indianapolis IN 46240

**Stereo sound for television will receive a theoretical analysis in January**, with field testing of four different systems expected to begin in the spring. The analysis and field tests are arranged by the Broadcast Television System Committee of the EIA. Several 1980 model color TVs have more powerful speakers and amplifiers, and some include *simulated* stereo. Japan now has a choice of bilingual or true stereo sound with TV broadcasts, and interest in similar systems is growing rapidly in the United States.

**PTS Electronics has moved its Memphis branch** to 1289 Madison Avenue, P.O. Box 41043, Memphis, TN 38104. The move provides space for a larger inventory and improved service along with sufficient off-street parking.

**The Institute of High Fidelity (IHF) has been merged into the EIA**, becoming an operating subdivision of the Audio Division of the Consumer Electronics Group of EIA.


**Maurice R. Valente becomes president and chief operating officer of RCA** on January 1, 1980. Edgar Griffiths formerly was president. He will continue as chief executive officer and also assume the chairmanship. Herbert S. Schlosser, executive vice-president of RCA, has predicted that between 25 and 40 million videodisc players will be sold during the first 10 years. About 300 titles for the RCA SelectaVision videodiscs should be available when RCA introduces its players. License to use 75 Paramount Pictures feature films was obtained recently, and RCA also has agreements with MGM, 20th Century Fox, ITC Entertainment and United Features Syndicate.

**No license now is required for receive-only satellite TV terminals.** Previously, before licensing a terminal, the FCC asked for a local survey to prove that the new system could have good reception without interference from other microwave signals. Nothing now prevents anyone owning a direct satellite terminal except the high cost of special antenna, down converter and amplifiers.

**John J. Nevin resigned recently as chairman of Zenith**, and Joseph S. Wright was appointed as interim chairman and chief executive officer. Zenith also has announced a new five-hour microprocessor-controlled videocassette recorder that can be programmed to record up to four TV channels at four different times during a 14-day period. Other features include automatic indexing, triple-speed play and remote control.


**A new lie detector is said to identify deception by analyzing inaudible microtremors in the human voice.** It is the Telestar Voice Stress Analyzer which is small and sells for \$149.

Chassis—RCA CTC85  
PHOTOFACT—1800-1

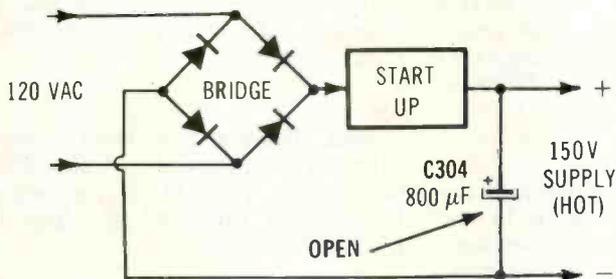


**Symptom**—No sound, no picture, no start-up  
**Cure**—Check filter capacitor C304, and replace it if open

Chassis—RCA CTC88  
PHOTOFACT—1787-1

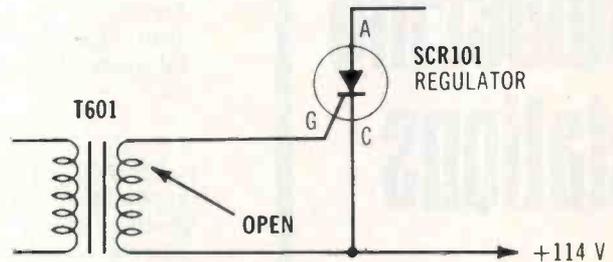


**Symptom**—No sound, no picture, and no start-up  
**Cure**—Check triggering transformer T601, and replace it if open

Chassis—RCA CTC88  
PHOTOFACT—1787-1

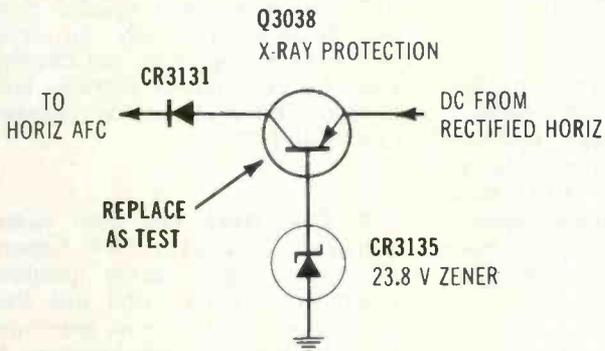


**Symptom**—No sound, no raster, and horiz osc is dead  
**Cure**—Check shut-down transistor Q3038, and replace it if bad

Chassis—RCA CTC87  
PHOTOFACT—1778-2

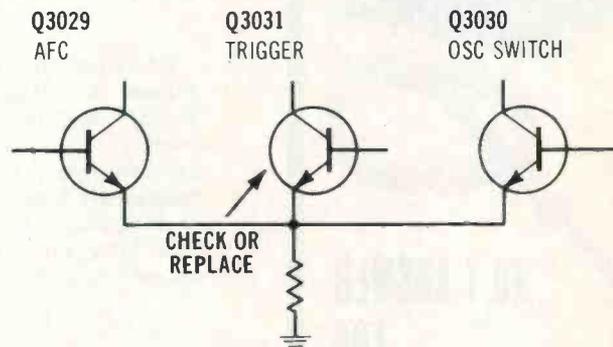


**Symptom**—Erratic start-up or intermittent raster  
**Cure**—Check or replace trigger transistor Q3031, and replace if bad

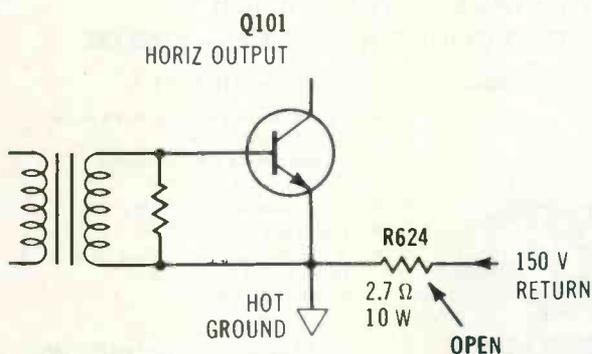Chassis—RCA CTC97  
PHOTOFACT—No Photofact




**Symptom**—No picture, no sound and no start-up  
**Cure**—Check R624, and replace it if open

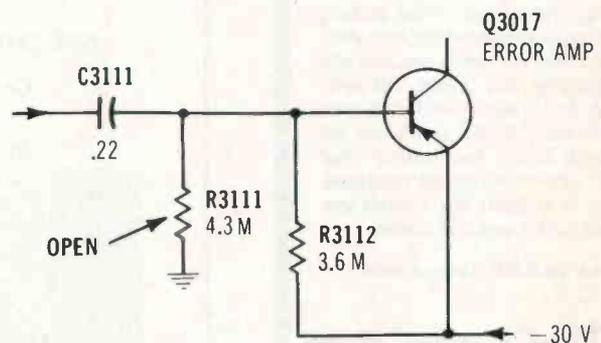Chassis—RCA CTC97  
PHOTOFACT—No Photofact



**Symptom**—No height, or insufficient height  
**Cure**—Check R3111, and replace it if open

# miniature soldering stations

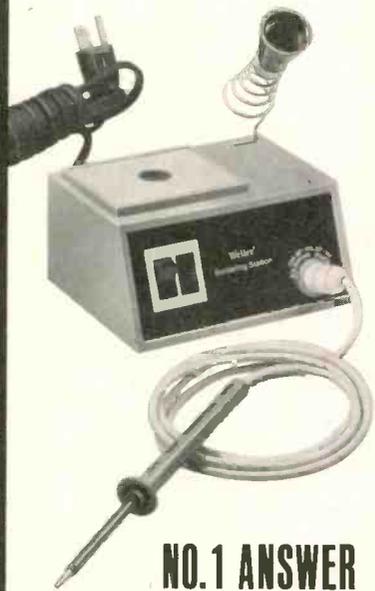

**NO.1 ANSWER  
FOR  
PRINTED CIRCUITS  
BY Weller®**

MP Series. Two models, 650°F or 750°F output, designed especially for today's printed circuit electronics. Famous closed loop control protects sensitive components from heat damage. Comfortable pencil-grip iron with non-burnable cord. Power unit operates from line-voltage with step-down transformer. ON/OFF switch and red indicator light. "Non-sinking" tool stand. Tip-cleaning sponge receptacle. Variety of available tips multiply usefulness of this versatile station.

Ask your local distributor or write...



**The Cooper Group**  
**Electronics Division**

WELLER® • WISS® • XCELITE®

P.O. BOX 728, APEX, NORTH CAROLINA 27502, 919/362-7511

Circle (6) on Reply Card

## people in the news

The Electronics Industries Association recently awarded **William E. Boss** the 1979 Distinguished Service Award. Boss is division vice president, distributor and commercial relations, RCA Consumer Electronics.

US JVC recently announced the appointment of **N. Sakoda** to the position of director and president. Sakoda was formerly general manager of the export administrative division of Victor Company of Japan.

The appointment of **Seth M. Willenson** as staff vice president of SelectaVision videodisc programs was announced by RCA. Willenson joined RCA in April. Previously, he was vice president, feature distribution, with Films Incorporated.

GC Electronics has appointed **Wayne G. Timpe** vice president-general manager. Timpe was previously vice president-manufacturing and research. Also at GC, **James Highway**, former national manager of distributor and consumer sales, has been promoted to director, special marketing.

**Terry McCarthy**, former Western region manager of marketing communications for the electronic components group, TRW, has been named manager, advertising, ITT Cannon Electronic. McCarthy is a director and past president of the

Los Angeles chapter, Business/Professional Advertising Association. Previously, he was advertising manager, Turco products division, Purex.

**Ellen Beebee** has been named sales representative for Alpha Wire Corporation. Prior to her promotion, Beebee was employed at Alpha in technical service.

ITT Blackburn has elected **Peter E. Fuerst** president. Fuerst succeeds **William E. Wilton**, who has been named chairman of ITT Blackburn's executive committee.


**Richard C. Tyrrell** has been named director of AutoSound sales, RCA distributor and special products division. Previously, he served as manager, planning and development for government services marketing, in the RCA service company, Cherry Hill, NJ.

**R. Fred Webb** has been named manager, marketing, for General Electric's semiconductor products department. Webb, who has been with GE since 1960, was previously regional manager, Southeastern region, for the electronic component sales department. Webb replaces **John C. Garrett**, who was named president and managing director of ECCO Ltd., GE's semiconductor manufacturing subsidiary in Dundalk, Ireland.

### MICROWAVE SURVEY METER SPECIAL U.S. INTRODUCTORY PRICE — \$169.00

Compact "Little Brother" of the popular HI-1501

Model HI-1800

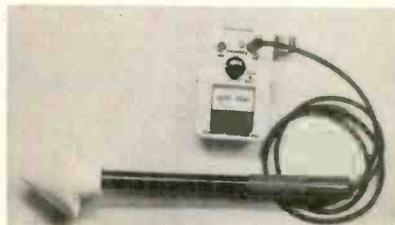

- Operates on two 9 volt alkaline batteries, included
- Temperature Compensated
- Range: 0-10 mw/cm<sup>2</sup>
- Calibrated at 2450 MHz
- Accuracy: ± 1 db
- Attractive Carrying Case with foam insert, beaker and instruction manual

Immediate Delivery - 90 Day Warranty

Order from  
**HOLADAY INDUSTRIES, INC.**  
7509B Washington Ave. South  
Edina, MN 55435 (612) 941-5100  
Telex: 290922

Circle (13) on Reply Card

# reader's exchange

There is no charge for a listing in *Reader's Exchange*, but we reserve the right to edit all copy. Due to the limited amount of space for this department, ads must show no more than five items. If you can help with a request, write directly to the reader, not to **Electronic Servicing**.

**For Sale:** 100 octal tubes (mostly unboxed) with 1V, 7V, 14V, 35V and 50V heaters, \$35 plus shipping, or trade for test equipment; Millivac model MV-27 micro-millivoltmeter (250 $\mu$ V to 1000V in 14 ranges), with manual, in good condition and calibration, \$45; McMurdo-Silver model 900 Vomax VTVM, with manual but needs selector switch rewired, \$25 or trade. Howard Adams, 209 West Shadywood Drive, Midwest City, OK 73110.

**Needed:** Magnavox volumes 5-12 service manuals. Will buy complete set or single volumes. Gerwig's TV, Rt 1, Box 194, Round Hill, VA 22141.

**For Sale:** Complete set of Rider's TV manuals with indexes; Rider's radio manuals 6 and 8-to-22 inclusive; Rider's PA manual 1. \$15 each in sets, or \$25 singly. R. N. Douglas, 1020 Fitzallen Road, Glen Burnie, MD 21061.

**For Sale:** Overstock of transistor, tubes and other TV and stereo parts and merchandise. A. Tucker, P.O. Box 2636, Macon, GA 31203.

**For Sale:** EICO 495 voltage calibrator, \$10; Sprague TO-6 capacitor tester, \$100; Hickok 470 VTVM with probes, \$50; B&K-Precision 970 radio Analyst, \$100; also, 5AXP4 and 8YP4 test tubes, \$15 each. L. E. Stokes, 2316 Fontaine Drive, Alton, IL 62002.

**For Sale:** Leader model LS-5 electronic switch, never used, \$65; Rider's volume 12 Perpetual Troubleshooter's manual, \$15; Photofacts 330 to 800, \$2.75 each. Richard Sanderford, 6400 Andy Drive, Raleigh, NC 27610.


**For Sale:** Precision E-200 RF generator, \$15; Heathkit LG-1 RF generator, \$15; Heathkit IO-30 5-inch scope, \$30; Kirby 98 flyback tester, \$10; Simpson 479 FM/TV signal generator, \$30; Supreme 589A tube tester, \$10. Paul Ellis, 419 Bellevue, Santa Cruz, CA 95060.

**For Sale:** Antenna lead wire and installation materials, tubes, speakers and many other components at below cost. Send for list. H. C. L., 20 Etna Lane, Dix Hills, NY 11746.

**For Sale:** Army BC-221-T frequency meter with ac supply, \$20; Navy LM-14 frequency meter, \$10; Hickok 203 VTVM, \$15; B&K-Precision 350 CRT tester, \$10; and Supreme servicing data, volumes TV-8 to TV-29, \$30. Paul Ellis, 419 Bellevue, Santa Cruz, CA 95060.

**Needed:** Convergence assembly for Sylvania D12 or D13 chassis. State price and condition. John DeLuco, 435 Ocean Boulevard, Cliffwood Beach, NJ 07735.
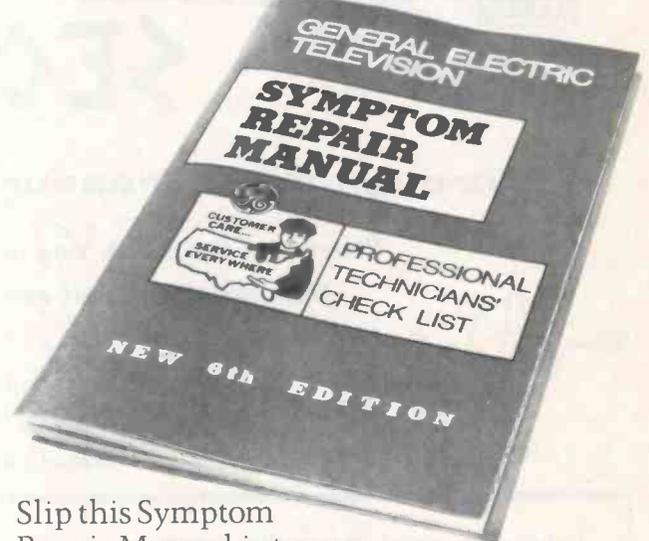
## The one tool that pays for itself first time out.



Slip this Symptom Repair Manual into your tool caddy. It lists all sorts of symptoms for individual GE TV chassis and tells you what to check and in what order. You can save hours of frustrating (and unprofitable) diagnostic time.

The new Sixth Edition manual packs the combined experience of hundreds of service technicians into a 5½" by 8½", 104 page package. It's free to subscribers of GE Technical Data, but non-subscribing technicians may obtain a copy by paying a \$2.00 handling fee. You can make that back in the first few minutes it saves.

"DUTCH" MEYER  
GENERAL ELECTRIC COMPANY  
PORTSMOUTH, VA 23704

Please check items desired:

- One Symptom Repair Manual (\$2.00 Enclosed)  
 Two Symptom Repair Manuals (\$3.00 Enclosed)

Enclosed is  Check  Cash or  
 Money Order (No C.O.D. Please)

Name \_\_\_\_\_


Service Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

IT'S OUR BUSINESS TO MAKE YOUR BUSINESS EASIER.

GENERAL  ELECTRIC

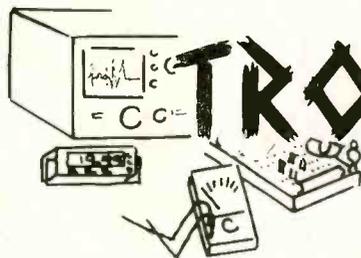


# UNLOCK TROUBLESHOOTING SECRETS



Through this Treasure of servicing Know-How!

Chart your path with this introductory collection of REPRINTS from among the best servicing articles ever published.

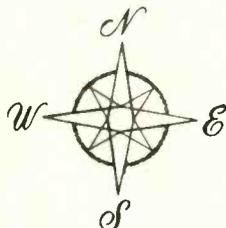

Employ today's TOP Authors as your Guides:

FOREST BELT, JACK DARR, WAYNE LEMONS, CARL BABCOKE  
...and other popular writers.



Valuable bargains in specific, timely, easy-to-remember, profitable training ...at less than \$2 a page.



### Service Training REPRINTS

Each \$ 5.50 postpaid  
15 - 24 5.25 each  
25 or more 5.00 each  
(Add 20% outside U.S.)

- |  |   |
|--|---|
| <input type="checkbox"/> AD-0001 Digital Principles for Communications - 1       | <input type="checkbox"/> AC-0001 Understand CB Transmitters the Easi-Way  |
| <input type="checkbox"/> AD-0002 " " " " - 2                                     | <input type="checkbox"/> AC-0002 Understand CB Circuits the Easi-Way      |
| <input type="checkbox"/> AD-0003 " " " " - 3                                     | <input type="checkbox"/> AC-0003 Understand Oscillators the Easi-Way      |
| <input type="checkbox"/> AD-0004 " " " " - 4                                     | <input type="checkbox"/> AC-0004 Troubleshoot Citizens Band Receivers     |
| <input type="checkbox"/> AD-0005 Digital Electronics in Video Cassette Recorders | <input type="checkbox"/> AC-0005 Modulation Limiting in CB                |
| <input type="checkbox"/> AD-0006 Replacement Transistors—Do They Work?           | <input type="checkbox"/> AC-0006 Mobile Installations in Custom Vans      |
| <input type="checkbox"/> AV-0001 Troubleshoot Video IFs with Sweep - 1           | <input type="checkbox"/> AC-0007 How To Fix Small Transceivers - 1        |
| <input type="checkbox"/> AV-0002 " " " " " - 2                                   | <input type="checkbox"/> AC-0008 " " " " " - 2                            |
| <input type="checkbox"/> AV-0003 Find Chroma Troubles with Sweep Generator       | <input type="checkbox"/> AC-0009 " " " " " - 3                            |
| <input type="checkbox"/> AV-0004 Really Understand Television Alignment          | <input type="checkbox"/> AC-0010 Switching From CB to FM Two-Way          |
| <input type="checkbox"/> AV-0005 Television Alignment Techniques - 1             | <input type="checkbox"/> AO-0001 Hints for Better Troubleshooting         |
| <input type="checkbox"/> AV-0006 " " " " - 2                                     | <input type="checkbox"/> AO-0002 Installing Security Systems              |
| <input type="checkbox"/> AV-0007 Television Chroma Alignment                     | <input type="checkbox"/> AO-0003 Testing Transistor Automobile Ignition   |
| <input type="checkbox"/> AV-0008 Servicing Pulse-Derived B-Plus Supplies         | <input type="checkbox"/> AO-0004 Creative Electronic Servicing            |
| <input type="checkbox"/> AA-0001 Troubleshoot Direct-Coupled Audio Stages        | <input type="checkbox"/> AT-0001 Which Scope—Recurrent or Triggered?      |
| <input type="checkbox"/> AA-0002 Cassette Recorder Workshop - 1                  | <input type="checkbox"/> AT-0002 Triggered Scopes Simplified              |
| <input type="checkbox"/> AA-0003 " " " " - 2                                     | <input type="checkbox"/> AT-0003 Triggered Oscilloscopes for Color        |
| <input type="checkbox"/> AA-0004 " " " " - 3                                     | <input type="checkbox"/> AT-0004 How To Use Triggered Scopes (programmed) |
| <input type="checkbox"/> AA-0005 " " " " - 4                                     | <input type="checkbox"/> AT-0005 Why Vectorscopes are Popular             |
| <input type="checkbox"/> AA-0006 How Eight-Track Car Stereos Work                | <input type="checkbox"/> AT-0006 Introduction to Vectorscopes - 1 and 2   |

**X** HERE! ES  
I have selected \_\_\_\_\_ Service Training REPRINTS, for which I enclose \$ \_\_\_\_\_ check or money order.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Phone \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

**FREE...**  
Binder and Index Guides  
with order of  
\$200 or more

MAIL TO: **Service Training GROUP**, Post Office Box 47, West Newton, IN 46183

# Electronic controllers in industry

By Dale R. Patrick, Professor Eastern Kentucky University

Automation in industrial systems is possible principally because of *electronic controllers*. Typical applications of controllers range from simple on/off operations to huge totally automated systems that respond to signals from a digital computer. Control might be applied to only one variable (such as temperature, pressure, fluid flow or electrical conductivity), or controls might correct hundreds of variables simultaneously in a large process.

Functions and circuitry of several representative electronic controllers will be analyzed in this article.

These controllers have gone through several generations. When first introduced in the early 1940s, they were equipped with vacuum tubes and mounted in large metal cabinets. With the development of solid-state devices in the late 1950s, the outward appearance of controllers was significantly changed.

The transition to all-solid-state controllers, however, has been rather slow. Initially, most companies were reluctant to give up their popular-selling vacuum-tube controllers. There was then a period when controllers employed both vacuum tubes and solid-state devices. These "hybrid" controllers and many of the vacuum-tube devices are still in operation today.

Some manufacturers still have vacuum-tube controllers available because the demand for them continues to be surprisingly good.

All major controller manufacturers today produce a wide variety of solid-state instruments. These units, in general, are small in size and usually employ hundreds of discrete components. Figure 1 shows a typical solid-state controller of this type. It has unusually precise control capabilities with exceptional stability.

The advent of solid-state controllers has brought about some innovative design features that have had a decided impact on controller maintenance. Components, for example, are mounted on removable printed-circuit cards or boards for easy replacement. Figure 2 shows an example of an indicating controller that has been partially removed from its metal housing. The printed-circuit modules of this controller can be easily removed by pulling the wire rings near the center of the controller. This controller has a great deal of versatility through this type of construction. Figure 3 shows a functional diagram of the potential location of alternate modules that can be utilized in this unit.

The next trend in controller technology found large numbers of discrete solid-state components replaced by integrated circuits. These controllers are somewhat smaller than their discrete component solid-state counterparts. Maintenance, in this case, is based on faulty IC determination and PC board replacement.

Microprocessors are now finding



Figure 1. A typical solid-state controller. Photograph courtesy Lees & Northrup Company.

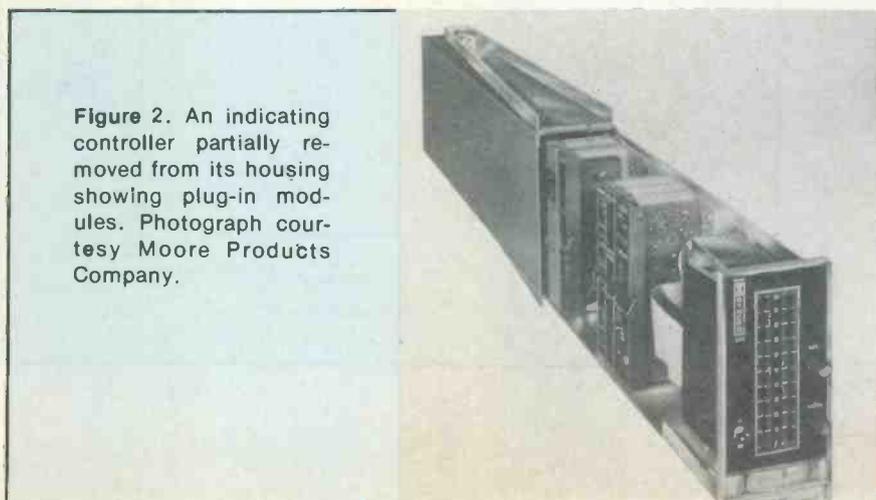


Figure 2. An indicating controller partially removed from its housing showing plug-in modules. Photograph courtesy Moore Products Company.

Material in this article has been adapted from Chapter 12 of *Instrumentation Training Course, Volume 2*, which is book number 21580 by Howard W. Sams [\$11.95].

Circle (15) on Reply Card

# Controllers

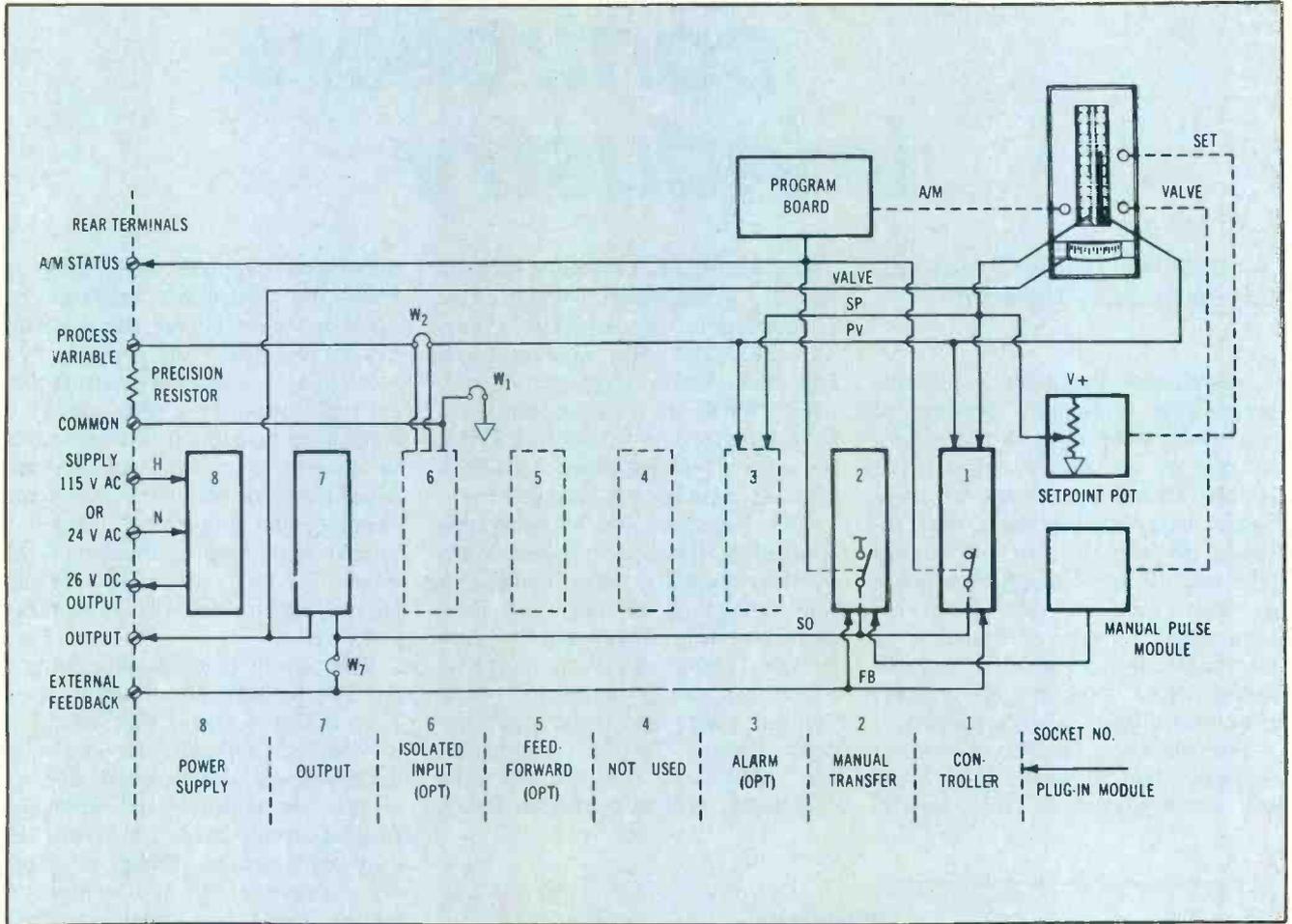


Figure 3. Functional diagram of alternate module locations for the controller of Figure 2.

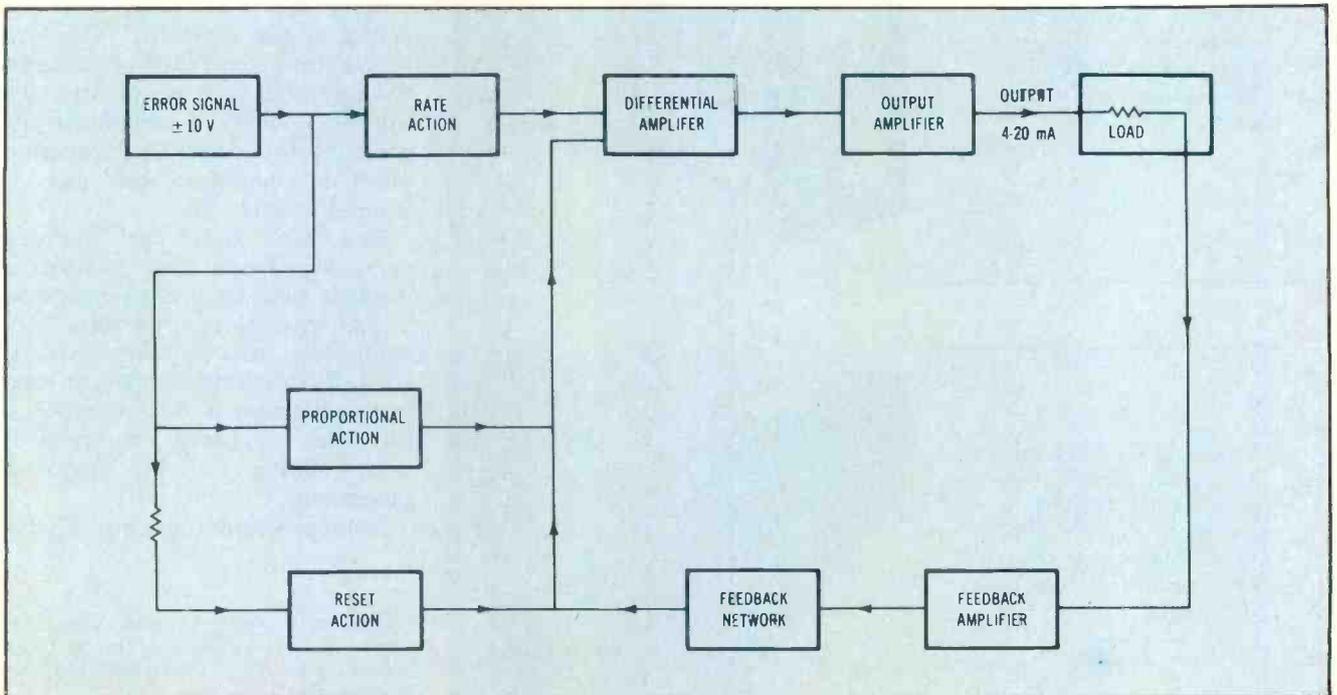


Figure 4. Block diagram of a typical controller.

their way into the process controller field. A microprocessor has a large number of discrete ICs on a single chip. In many situations the entire controller may be built on a single chip. This will obviously change the controller size again, and in many cases eliminate most maintenance problems.

With the wide range of diversity that exists today in controller technology, it is difficult to single out a particular controller that is representative of the field. In this regard, we will first discuss some common solid-state controller circuitry, then show some typical IC applications using op amps. Through this approach you will be able to pick out the information that is particularly applicable to your controller needs.

### Controller functions

#### General information

Figure 4 is a block diagram of a typical controller. Three modes of operation are incorporated in this instrument: (1) proportional action, (2) reset action, and (3) rate action. They will be discussed in connection with the input circuits of the controller.

Sections will be devoted to the rate action, differential, output, and feedback amplifiers. The controller power supply will not be covered separately because it is so similar to

power supplies previously discussed.

#### Controller input circuits

Figure 5 is a simplified schematic diagram of the controller input circuits. Each of the three previously mentioned modes of controller operation are described here.

1. **Proportional action.** This action determines the ratio between the controller output signal and the input signal. If the proportional-band control is set at 100%, the controller output will result in a change that is directly proportional to the error signal. For insensitive transmitters, the proportional-band control will be set for less than 100%. The error signal will, therefore, produce an output that is proportionally greater. This is called narrow-band control. A narrow range in error signal can produce a full range of controller outputs. For settings of the proportional-band control of greater than 100%, the error signal range will be greater than the controller output. This is called wide-band operation.

2. **Reset action.** This action is constantly driving the final control mechanisms to zero-out any error signal. Any time the controller position differs from the set point, reset action moves the controlling device in such a

direction as to agree with the set point. The amount of action depends on the amount and the length of time of the deviation.

3. **Rate (derivative) action.** This action determines the rate of controller action. Its effect on controller output is twofold: If the controller output rate were dependent on proportional-band control only, it is possible for the error signal to become so great that the controller could not possibly zero itself. On the other hand, if the rate action were too fast, the controller would oscillate or hunt. The error signal input to the controller is differentiated so that its rate of change can be detected and the proper rate action provided.

Figure 5 shows that the error signal is applied to a voltage divider made of  $R_{25}$  and  $R_{26}$ . This signal is a dc voltage with a magnitude of 10V or less. The plug into the controller can be positioned in either the direct or reverse position. In the direct position, a positive input produces an increase in controller current. In the reverse position, a positive input produces a decrease in controller current. This input is fed directly to the rate-action amplifier, which will be discussed later. Its output is one of the inputs to the differential amplifier.

The first input to the differential amplifier is a signal that combines reset and proportional action. One-half of the error signal is developed across  $R_{20}$ . This voltage is fed to the reset control circuit. The reset control circuit is made up primarily of  $R_{28}$  and  $C_{12}$ ,  $R_{27}$ ,  $R_{39}$ , and a portion of  $R_{31}$  are also in the circuit. Since  $R_{28}$ , calibrated in repeats per minute, is so much larger than the others combined, it largely determines the time constant of the circuit. This time constant determines how often the proportional response is repeated. In other words,  $C_{12}$  charges to the change in the error-signal voltage;  $R_{28}$  determines the length of time it takes  $C_{12}$  to charge. The voltage across  $C_{12}$  is the second input to the differential amplifier. The amplifier is stabilized by a feedback voltage that is equal and opposite to the

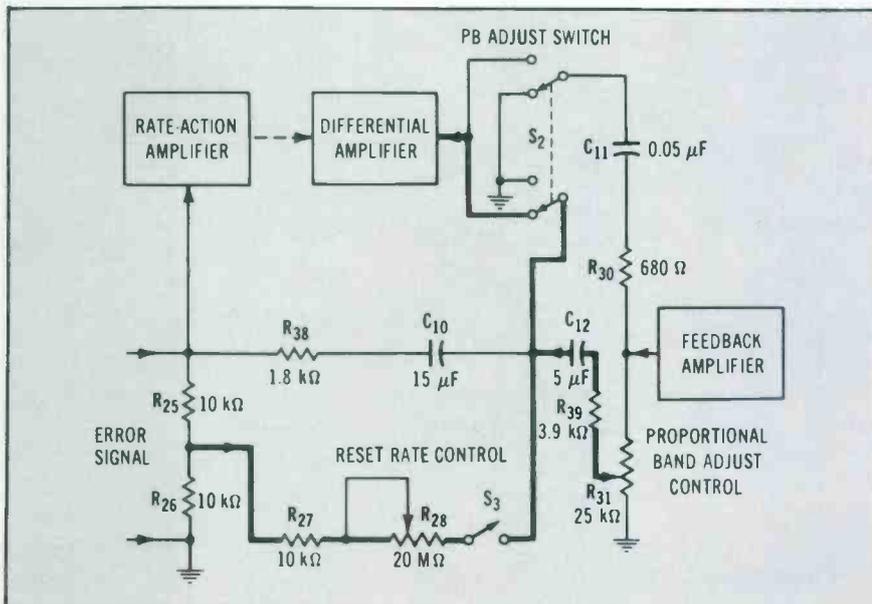


Figure 5. Simplified schematic diagram of controller input circuits.

# Controllers

input. How this signal is produced will be discussed in the section covering the feedback amplifier.

Proportional action is determined by the percentage of feedback-amplifier output that is applied to the differential-amplifier input. The percentage of feedback is determined by the setting of the proportional-band control,  $R_{31}$ . The voltage at the wiper arm of  $R_{31}$  determines proportional action as well as a reference voltage for  $C_{12}$ . The reset action voltage, the charge across  $C_{12}$ , adds to this voltage. The sum of these two voltages makes up the input to the differential amplifier. A few words need to be said about the proportional-band adjust switch,  $S$ . This switch is incorporated in the proportional-band adjust ( $R_{31}$ ) procedure by being a push-and-turn type of adjustment.

When the switch is pushed, the normal differential-amplifier input is grounded. The other pole of  $S_2$  feeds an input into the amplifier that is the charge across  $C_{11}$ . During normal operation,  $C_{11}$  maintains a charge that is equal to the voltage across  $R_{31}$ . When  $S_2$  is thrown, the ground is removed from one side of  $C_{11}$  and applied to the input of the amplifier. Since this voltage is the same as that maintained previously, no change in output is assumed until after the adjustment has been made. The result is a smooth transfer from one proportional band setting to another.

## Solid-state controllers

Discrete component solid-state controllers have obviously not been around as long as their older

vacuum-tube counterparts. Nearly all controllers sold in recent years are, however, predominantly solid-state. Figure 6 shows a representative schematic diagram of a discrete component solid-state controller.

As can be seen in Figure 6, the power supply provides two dc -outputs. They are +36V and +46V, respectively. Each power supply uses silicon diodes to provide full-wave rectification.

Filtering of the power supply voltage is not quite as obvious in this circuit as is generally displayed in other schematics. The +36V source, for example, is filtered by a pi-section filter near the center of the diagram. (See printed-circuit points 32, 33 and 10.) The +46V supply, by comparison, employs an LCR filter composed of  $L_2$ ,  $C_{12}$  and  $R_{31}$ . These components are located

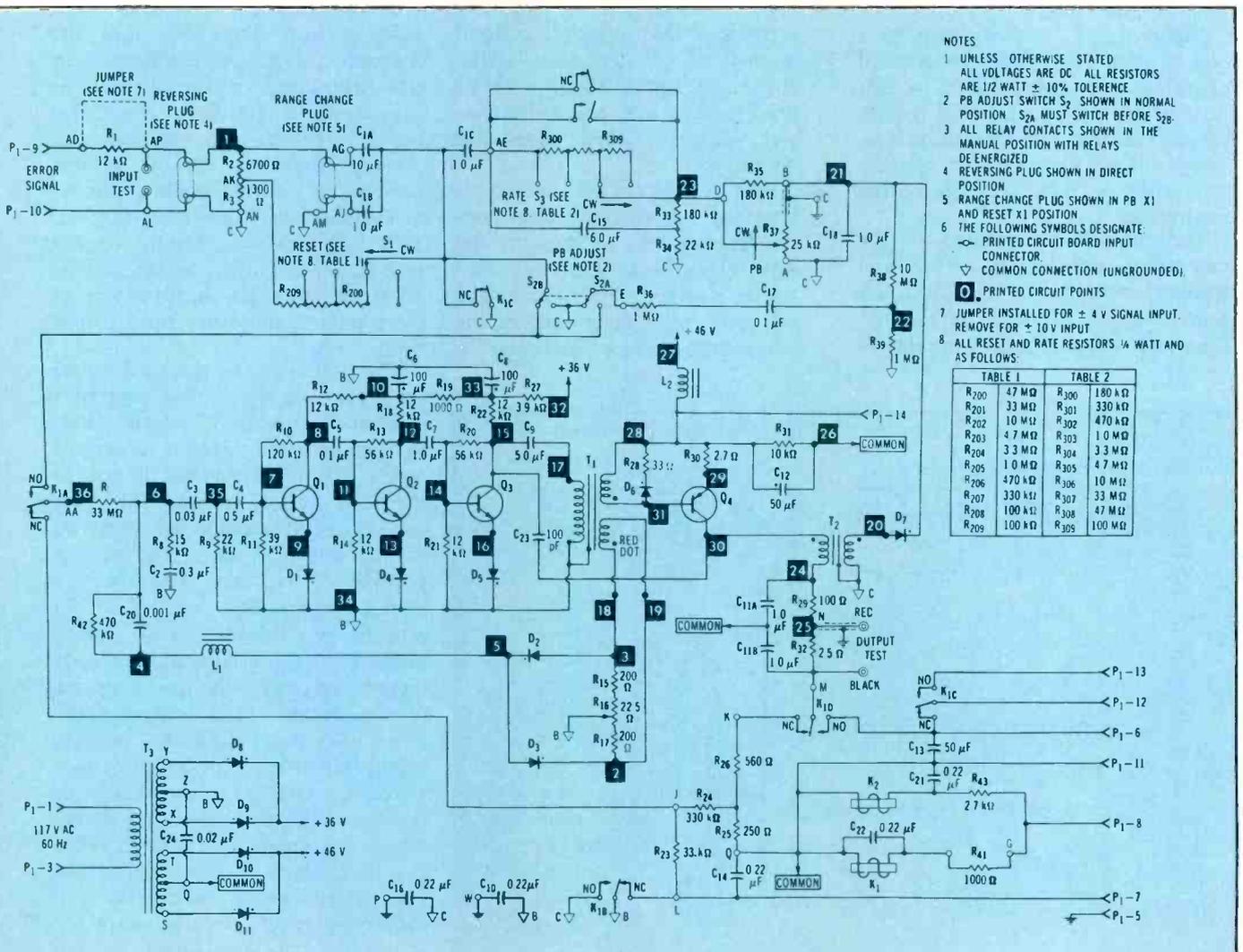


Figure 6. Schematic diagram of a typical discrete component solid-state controller.

between printed-circuit points 27 and 26.

In the discussion that follows, we will single out specific solid-state controller circuits for explanation. In some cases operational amplifiers will be used in circuits where this type of component finds acceptance today. Through this approach you will see how the IC simplifies the circuit and the explanation of its operation.

The controller input is the error voltage developed by the recorder.

This input signal is negative or positive, depending on whether the process variable signal is above or below the set point. When the process variable signal is the same as the set point, the input to the controller is zero. The operational amplifier circuit shown in Figure 7 is the basis for amplifier action. It consists of an input network and a feedback network in which the current is equalized by an amplifier. If the input current is constant,  $C_{in}$  charges to that voltage. The

feedback current, produced by this input voltage, charges the feedback capacitor,  $C_f$ . Once the two capacitors are equally charged, no current will conduct. The slight excess of input current necessary to sustain amplifier output is insignificant.

An input signal causes an input current to conduct, charging  $C_{in}$ . This amplifier input immediately produces an output, or feedback current. Feedback current charges  $C_f$  to a value that equals the charge on  $C_{in}$ . Since the reaction of the amplifier is practically instantaneous, the feedback current is constantly tracking or following the input signal. As these two equal currents vary, adding to and subtracting from the charge of the capacitors, these charges always remain the same. As a result of this action, the junction of the two capacitors (summing junction) is always essentially at a ground potential.

#### Proportional action

The effective ratio of the value of the input capacitance and the feedback capacitance determines the proportional band. The effective value depends not only on capacitor size, but on the voltage gain of the amplifier. If the effective ratio is 1:1, then the proportional band is 100%. Under these conditions, a full-scale input change produces a full-scale output change. A change in the ratio of the capacitances changes the proportional band. A range of proportional bands can be provided by 1—100% or 10—1000% by changing the ratio. In addition to a variation in range of the proportional band, a change within the range is provided by a potentiometer. The potentiometer is the proportional-band adjust control shown in Figure 8. By adjusting this control, the amount of the output that is used in the feedback circuit can be varied. With a decreasing feedback signal, a larger output must be produced to fully charge  $C_f$ . An increased output for a given input is merely a narrowing of the proportional band. A full range of output signals can, therefore, be produced by small input signals. The range of input in percent that produces a full range

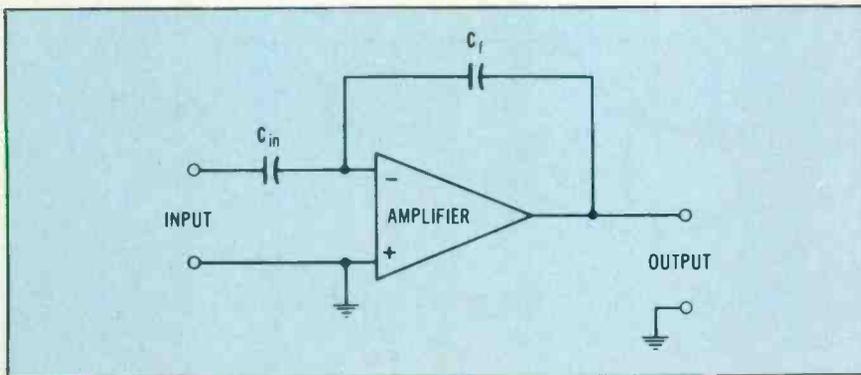


Figure 7. Operational-amplifier equivalent of transistorized controller.

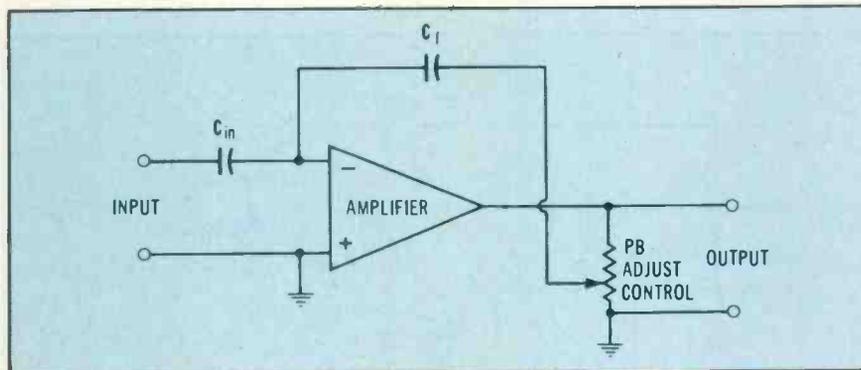


Figure 8. Proportional-band circuit.

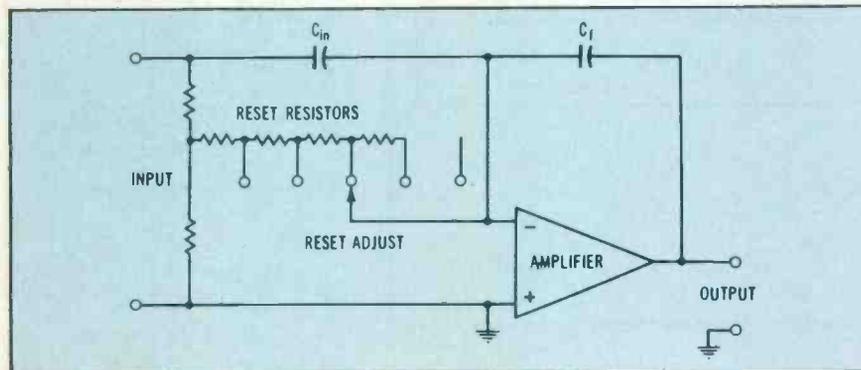


Figure 9. Reset circuit.

## Controllers

of output signals is the proportional band.

### Reset action

A voltage divider is placed across the controller input and a variable resistor is placed in parallel with  $C_{in}$  for reset action (Figure 9). The voltage divider and variable resistor provide a path for current whenever an error signal exists. This current provides a continuous amplifier input whenever the process variable signal differs from the set point. Feedback current, therefore, continues to charge, or discharge, the feedback capacitor as long as there is an input. The amplifier then produces a continuous change in output as long as an input signal exists. This, by definition, is reset action, since the controlled device is seeking the null position. In discussing the proportional circuit, it was evident that there was current only when there was a change in the input signal. In the reset circuit, the only time that input current stops is when the error voltage is zero. By decreasing the value of the reset resistors, input

current is increased for a given input signal. The output current must increase at a faster rate in order to produce a matching charge across the feedback capacitor. The result is a faster reset rate. Increasing the size of the reset resistors results in a slower reset rate. To produce a very low reset rate, the voltage divider has been incorporated in the input circuits. The voltage divider causes the reset resistors and the amplifier to see a smaller portion of the input signal,

resulting in a smaller charging current. The input capacitor, however, still sees the full input voltage. The value of the reset resistor determines the number of times that proportional action is repeated per minute.

### Rate action

Rate (derivative) action is accomplished by the addition of a voltage divider, a variable resistor, and a capacitor in the feedback circuit (Figure 10).

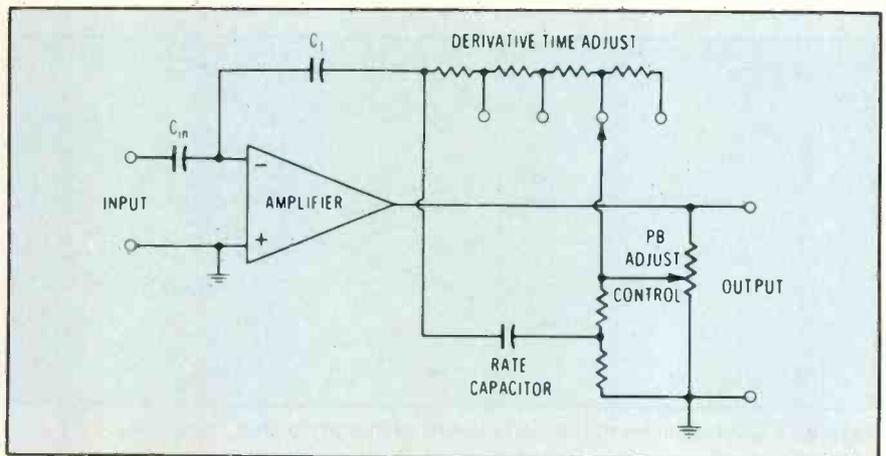


Figure 10. Derivative (rate) circuit.

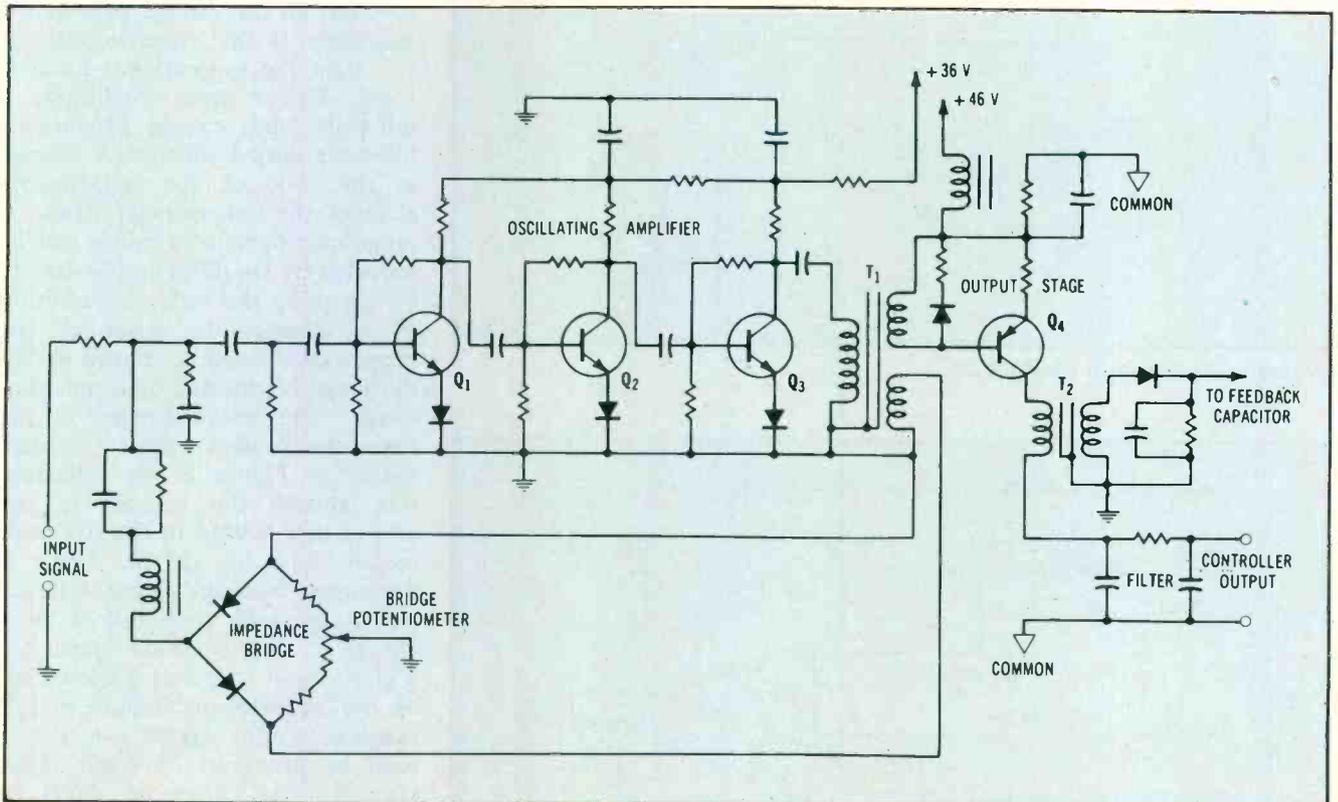


Figure 11. Oscillating amplifier and output circuit.

An input signal change produces an output change that is easily passed by the rate capacitor. Since this change is taken from across the voltage divider, the result is that the feedback capacitor sees only a portion of the output. The effect is the same as a decrease in the proportional-band control. That is, the instantaneous effect is a narrowing of the proportional band. This results in a greater output change for a given input until the rate capacitor charges. The time it takes the rate capacitor to charge depends on its time constant. This can be changed by the variable resistor, the rate time adjustment. As soon as the rate capacitor charges, the effect of the voltage divider disappears. The proportional band is then restored to its original value. Rate amplitude will be determined by the voltage divider. This, of course, determines the amount of the instantaneous change in signal fed through the rate capacitor.

Rate action has an anticipatory function that acts only when the output is changing. It then provides a braking or damping action. In general, rate action is used to reduce cycling and overshoot and to permit the use of narrower proportional bands.

### Amplifier

The amplifier used in the transistorized controller can be divided into three basic sections: the impedance bridge and internal feedback loop, the three-stage oscillating amplifier, and the output stage. The schematic for the amplifier is shown in Figure 11.

A Wheatstone or impedance bridge forms an important part of the feedback loop that makes oscillation within the amplifier possible. This bridge is made up of two fixed resistors, a potentiometer, and two diodes. Two legs of the bridge are resistive, while the two remaining legs are formed by the diodes. The diodes provide rectifying action and also function as variable resistances. The amplifier output is applied across the bridge. A portion of this voltage developed across the bridge is fed to the amplifier input. The amount of feedback is determined by the position of the bridge potentiometer. The polarity of output coupled to the feedback loop is determined by the feedback winding of the output transformer. The polarity is such as to provide positive feedback (regeneration) at the operating frequency. The amount of feedback is determined by the bridge as mentioned previ-

ously. The frequency of oscillation, about 20kHz, is determined by the coil and capacitors located in the amplifier input circuit.

The input signal comes from the recorder. This voltage is fed to the base of  $Q_1$  along with the feedback signal. If this error signal has the same polarity as the feedback signal, the output of the three-stage amplifier will increase. On the other hand, if the polarity is reversed, the output voltage across transformer  $T_1$  will decrease. The amplitude of the signal across the primary of  $T_1$  depends on the error signal. The three-stage amplifier is composed of three npn transistors connected as common-emitter amplifiers. The three stages are RC-coupled, and a voltage divider determines the forward bias of each.

The base signal is taken from a secondary winding of  $T_2$ , which is associated with  $Q_4$ , a pnp transistor that is the output amplifier. Transistor collector current passes through the load for controller output. Since this current is a changing or pulsating dc, it must be filtered to give a dc current range of 4 to 20mA. Collector current also passes through the primary of transformer  $T_2$ . The secondary voltage, rectified and filtered, charges the feedback capacitor as discussed in the preliminary paragraphs of this section.

### Vacuum-tube controllers

Using the previous controller block diagram (Figure 4) as a general reference, vacuum tubes can be used to achieve the same basic modes of controller operation as those of the transistor circuits. In general, these circuits are considered obsolete today. A large number of vacuum-tube controllers are, however, still being used in many applications.

### Rate-action amplifier

Figure 12 is a simplified schematic of a vacuum-tube rate-action amplifier. This is a two-stage dc amplifier. The first stage is a normal voltage amplifier and the second stage is a cathode follower. A dc plate voltage for both stages is provided by 100V ac, which is

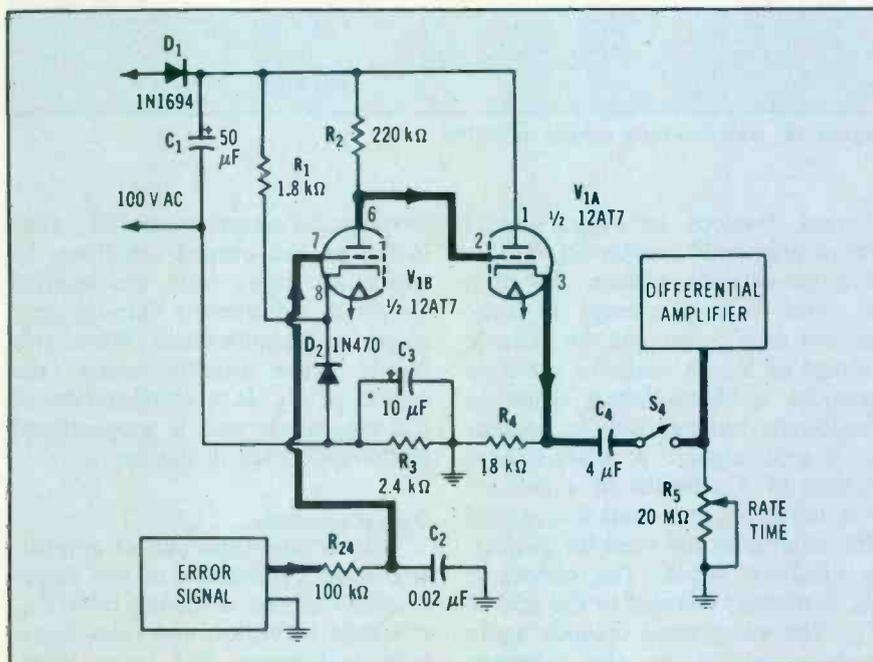


Figure 12. Vacuum-tube rate-action amplifier.

## Controllers

rectified by  $D_1$  and filtered by  $C_1$ . A negative voltage is developed across  $R_3$  by rectifier action and is maintained at the cathode of  $V_{1B}$  by the action of  $C_3$  and  $D_2$ . This develops the proper plate voltage so that direct coupling can be used with the proper bias on  $V_{1A}$ .  $V_{1B}$  amplifies and inverts the input error signal. The error signal input is integrated by the action of  $R_{24}$  and  $C_2$ . By integration, we mean that the rate of change in error signal voltage is averaged out by the rate of charge (time constant) of the input circuit. If the position of  $C_2$  and  $R_{24}$  were reversed, the input signal would be differentiated. In both cases, the amount of integration, or differentiation, is dependent on the size of the resistor or capacitor involved.

This changing signal is fed to the grid of  $V_{1A}$ . Static tube current maintains a constant positive voltage at the cathode of  $V_{1A}$ .  $C_4$  assumes a charge equal to the voltage drop across  $R_4$  (the cathode voltage). During static operation (no signal input) there is no current through  $R_5$ . The input to the differential amplifier is then zero volts during this period of time. When a change of voltage occurs at the grid of this cathode follower, the cathode voltage changes. Since the charge across  $C_4$  does not change immediately (notice the long time constant of  $C_4$  and  $R_5$ ), the change appears across  $R_5$ . Notice that only the change, or rate of variation in voltage, appears as an output of the rate amplifier.  $R_5$  and  $C_4$  make up a differentiating circuit.

### Differential amplifier

Figure 13 is a simplified schematic diagram of a vacuum-tube differential amplifier circuit. Two stages of amplification are provided for the rate-action signal. Two stages also amplify the combined proportional-band and reset-action signal. These two outputs are mixed by common cathode coupling; a single output is developed that is the difference of these two input signals.

The output of the rate-action amplifier is directly coupled to the grid of  $V_{2B}$ . Any change in tube

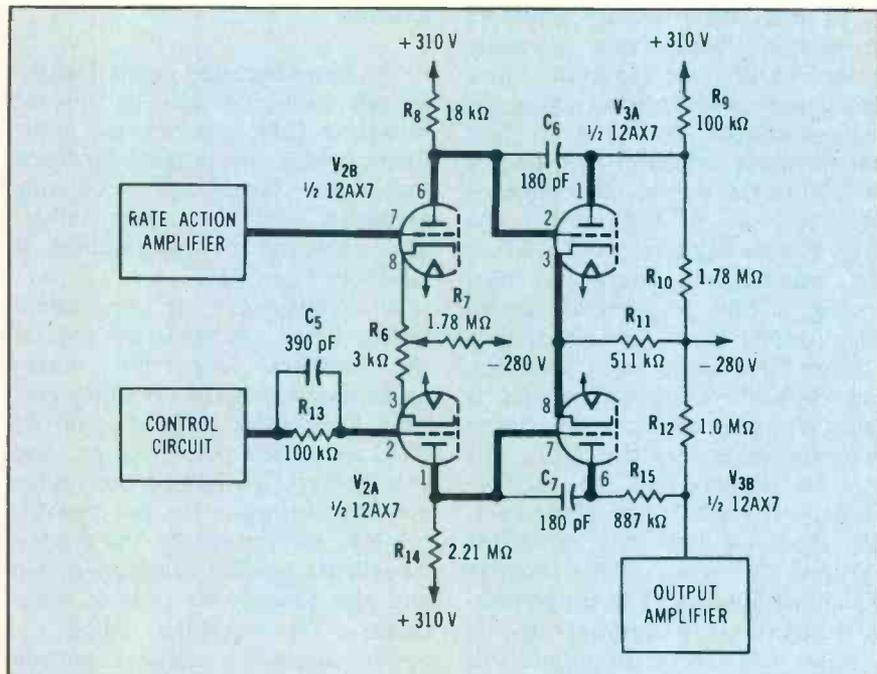


Figure 13. Vacuum-tube differential amplifier.

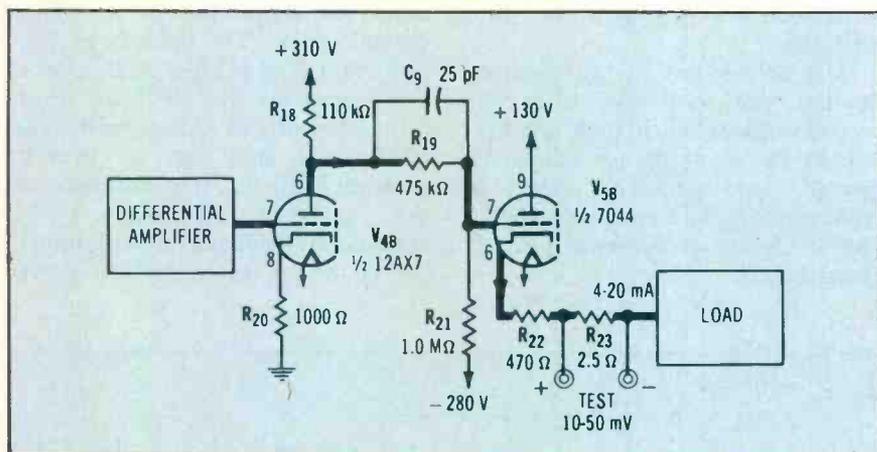


Figure 14. Vacuum-tube output amplifier.

current develops an output signal across plate-load resistor  $R_8$ .  $R_7$  is a common-cathode resistor for both  $V_{2A}$  and  $V_{2B}$ . A change in tube current of  $V_{2B}$  changes the cathode voltage of  $V_{2A}$ . A cathode variation provides a signal input equal in amplitude, but opposite in polarity to a grid signal. A plate-voltage change of  $V_{2A}$  results in a rate-action input.  $R_6$  is a balance control that eliminates the need for perfectly balanced tubes. The output is  $V_{2B}$  is directly coupled to the grid of  $V_{3A}$ . The unbypassed cathode again feeds a signal to the common cathode of  $V_{3B}$ . This cathode signal

develops an output across  $R_{15}$  that is fed to the output amplifier, to which an input from the control circuit is fed directly through two stages of amplification. When two inputs occur simultaneously, the output of  $V_3$  is a combination of the two inputs and is proportional to the difference in the two.

### Output amplifier

The vacuum-tube output amplifier (Figure 14) consists of two stages of amplification involving tube  $V_{4B}$ , a voltage amplifier, and tube  $V_{5B}$ , a cathode follower. The input signal from the differential amplifier is

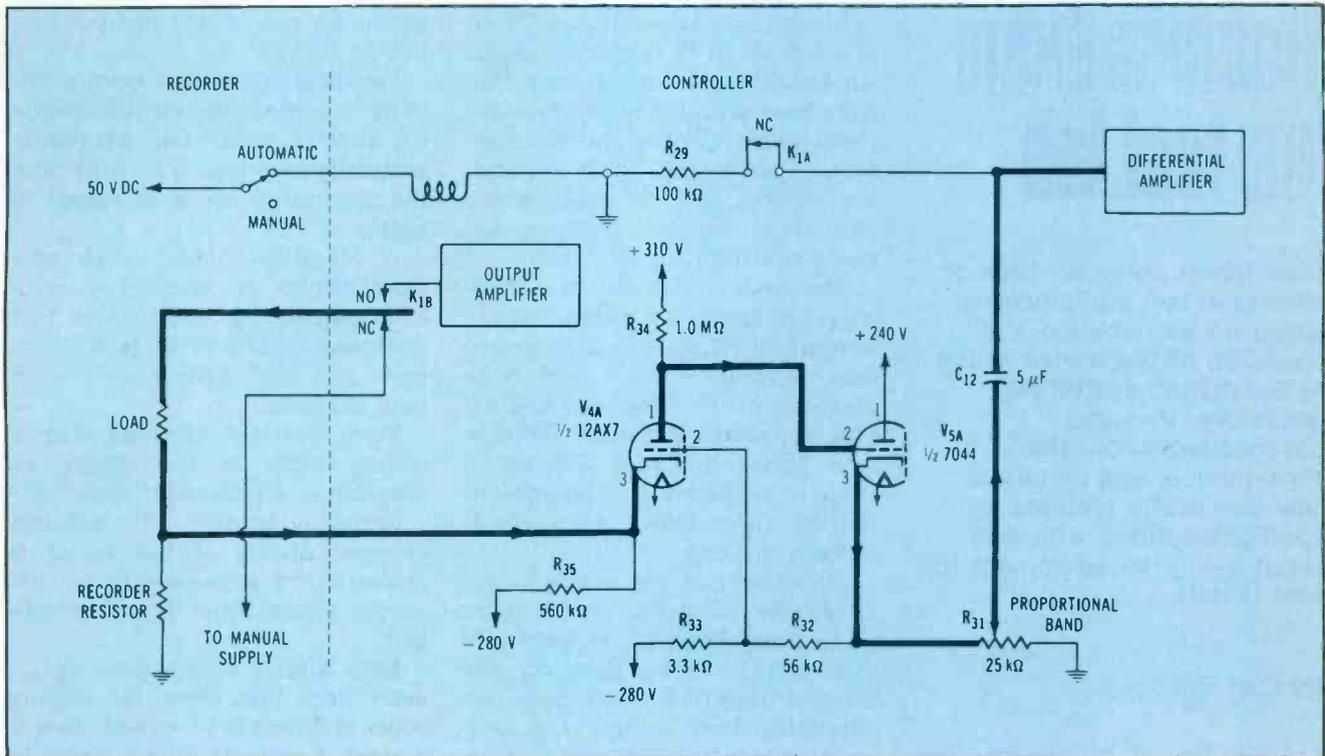


Figure 15. Vacuum-tube feedback amplifier.

fed to the grid of  $V_{4A}$ , which amplifies and inverts it. The output of  $V_{4A}$  is dc-coupled to the grid of the cathode-follower stage. Capacitor  $C_{12}$ , by shunting  $R_{31}$ , helps prevent parasitic oscillation.

The cathode-follower stage takes the high-impedance voltage input from  $V_{4A}$  and changes it into a high-current, low-impedance output. The current output lies within the range of 4 to 20mA dc. A 2.5 resistor ( $R_{23}$ ) is inserted in series with the current output to provide a convenient test point to measure the output current in equivalent millivolts.

#### Feedback amplifier

Figure 15 is a simplified schematic diagram of a vacuum-tube feedback amplifier. The output-amplifier current passes through the load ( $0.1150 \Omega$ ) and a recorder resistor. This recorder resistor ensures a constant current output from the controller, regardless of load impedance. It also develops the input voltage for the feedback amplifier. The feedback amplifier involves two stages of amplification. The first stage ( $V_{4A}$ ) is a normal voltage amplifier that is

dc-coupled to the second stage, cathode follower  $V_{5A}$ . The voltage developed across the recorder resistor is fed to the cathode of  $V_{4A}$ . A cathode input affects tube current in exactly the same manner as if fed to the grid with an opposite polarity. A change in cathode voltage produces a plate voltage change in phase with the input signal. The plate-load resistor,  $R_{34}$ , is connected to the +310V plate supply, while the cathode resistor is connected to the -280V is maintained at about 0V so that dc coupling can be used.

The output of  $V_{4A}$  is fed to the grid of  $V_{5A}$ . Any change of grid voltage produces an in-phase change in cathode voltage. Tube current develops this voltage across  $R_{31}$  (the proportional-band control) and the parallel voltage divider,  $R_{32}$  and  $R_{33}$ . The portion of the output voltage developed across  $R_{33}$  is fed back to the grid of  $V_{4A}$ . This voltage is out of phase with the input to  $V_{4A}$  and is, therefore, a negative feedback. The amount of negative feedback determines the gain of the feedback amplifier and stabilizes the dc amplifier. The amount of feedback at the input of

the differential amplifier is determined by the setting of the proportional-band control. The less the feedback voltage, the greater the sensitivity of the entire system. This, of course, is the purpose of the proportional-band action.

As described previously, when the recorder is in the manual position, the load current is determined by the set position of the manual control. The controlled output is open-circuited. Manual load current is still detected by the voltage drop across the recorder resistor. This voltage is still fed to the input of the feedback amplifier. Feedback amplifier output maintains a charge across  $C_{12}$ .  $C_{12}$ , therefore, remembers the load current (the charge of  $C_{12}$  is proportional to load current) so that smooth, continuous operation can be maintained when switching to automatic operation.

#### Summary

Present-day electronic controllers usually employ discrete transistors and integrated circuits, while older models have vacuum tubes.

The three major modes of operation are proportional action, reset action and rate action. □

# Reports from the test lab

Each report about an item of electronic test equipment is based on examination and operation of the device in the **ELECTRONIC SERVICING** laboratory. Personal observations about the performance, and details of new and useful features are spotlighted along with tips about using the equipment for best results.


By Carl Babcoke

A new line of four oscilloscopes has been released by Hitachi Denshi America. These models are virtually identical. Therefore, the top-of-the-line model V-302 is described here as typical of all four, except for the stated exceptions.
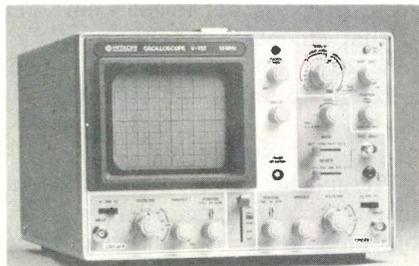
## General features

Wide bandwidth, high sensitivity and several advanced features qualify these versatile scopes for adjustments and analysis of radios, audio systems, TVs, videocassette recorders, industrial systems, computers and other products.

One unusual feature is the choice of two bandwidths. When the 5MHz bandwidth is selected, the maximum vertical gain is 1mV.



All four models of the new Hitachi line of scopes have similar appearance and features. This is the 15MHz model V-152.

## Horizontal sweep


Sweep times extend from 0.2S/div to 0.2 $\mu$ S/div in 19 calibrated ranges. An uncalibrated variable-time control allows selection of slower-in-between values. Pulling out the horizontal positioning knob expands the sweep width to 10 times normal (X10 mag), which provides a fast sweep equivalent to 100nS/div.

The *mode* switch selects normal triggering (no sweep unless locked), automatic triggering (has sweep even without signal) and both polarities of TV sync. An internal sync separator provides TV-type sync pulses for solid locking of video waveforms (an important feature since video otherwise is difficult to lock).

Adjustment of the *source* switch allows the triggering signal to be taken from channel 1, channel 2 (if dual-tract), 60Hz line or the external-triggering input jack. An adjustable level control also provides triggering on positive or negative slopes.
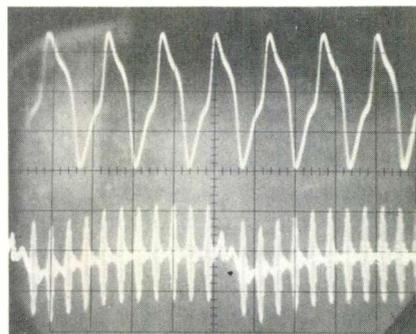
## Vertical channels

Vertical frequency response of model V-302 is rated within -3dB from dc to 30MHz. Sensitivity between 5mV/div and 5V/div is available in 10 fixed steps. Also, continuous height variation is possible by an uncalibrated control. The 0.005V (5mV/div) maximum sensitivity is higher than that of older models, and it can be increased at the expense of reduced bandwidth. With an X10 probe and



Top trace shows a 3.58MHz color carrier at 0.2 $\mu$ S sweep on the Hitachi model V-302 30MHz scope. Bottom trace has two horizontal lines of color-bar chroma waveforms viewed at 10 $\mu$ S sweep.

the graticule of eight divisions, the maximum measurable input is limited to 400VPP.

For those times when extra sensitivity is needed, the vertical centering knob is pulled out. Maximum sensitivity increases to 1mV/div and the upper response is decreased to 5MHz.

A 5-position *mode* switch provides display of: channel 1 waveform; channel 2; both channels in dual-trace; addition of both channels; and the difference between both channels.

Each vertical channel has a sliding switch for ac coupling, dc coupling or a grounded input.


Switching between alternate and chopped display of two traces is accomplished automatically by the setting of the *time/div* sweep control.

Both 30MHz models have signal-delay lines that allow the leading edges of pulses to be viewed. This is a good feature that is imperative for digital waveforms.
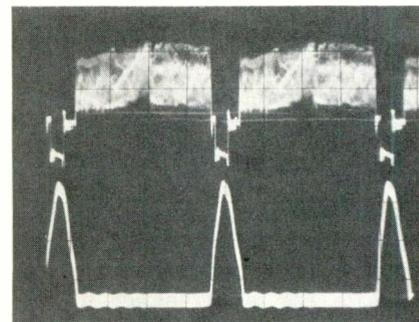
## CRT and calibration


Each 5-inch CRT has blue traces, black lines for graticule calibration and no provision for illumination. Ordinary room light is usually adequate for taking readings from the screen.

In addition to the customary *trace intensity* and *focus* controls, a screwdriver-adjustable *trace rotation* control is provided. This control can tilt the horizontal traces as needed. If a local magnetic field moves the traces so they no longer are parallel with the graticule lines, a simple adjustment will level the traces.



Excellent detail without ringing or overshoot is shown by this dual-trace view of composite video and horizontal-sweep pulses.

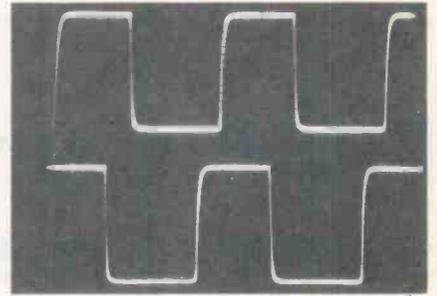These waveforms show the effect of signal delay lines in Hitachi scope models V-302 and V301. Top waveform shows a 200kHz series of square waves with the initial leading edge displayed. When the signal-delay line was bypassed by locking from the same signal applied to the external-trigger input jack, the leading edge and part of the first peak are missing.



### Probes

Probes supplied with these Hitachi scopes provide only an X10 function that reduces the input amplitude by a factor of 10 while it provides low-capacitance operation. Elimination of the direct (or X1) function is not a disadvantage because it is offset by the high vertical sensitivity. And without the X1 function, the probes are smaller and less prone to problems. The cable has a small diameter and is very flexible.

For frequency compensation, the hook probe is attached to the calibration waveform terminal at the panel upper-right corner, then a

trimmer (inside the cable's BNC plug) is adjusted for flat-top square waves.

### Comments

Model V-151 is the single-trace 15MHz version. Model V-152 is similar except for the dual-trace feature. Both have about 2kV acceleration voltage.

Model V-301 is identical to the V-302 just described except it has one vertical channel for single-trace operation. Both are rated at 30MHz vertical response, have about 4kV acceleration voltage and feature a vertical-signal-delay line.


Each year the need increases for better scopes and other items of test equipment. Therefore, it is recommended for the purchase of any scope that the model selected have more features and better specifications than those required at the present time. This will prevent early obsolescence.

The sample model V-302 performed very well in the Test Lab where it produced sharp stable waveforms of color-TV signals. It is recommended for troubleshooting of home-entertainment, industrial, radio-communication and digital equipment. □

Circle (16) on Reply Card

## Electronic Servicing is Available in MICROFORM

FOR INFORMATION  
WRITE:

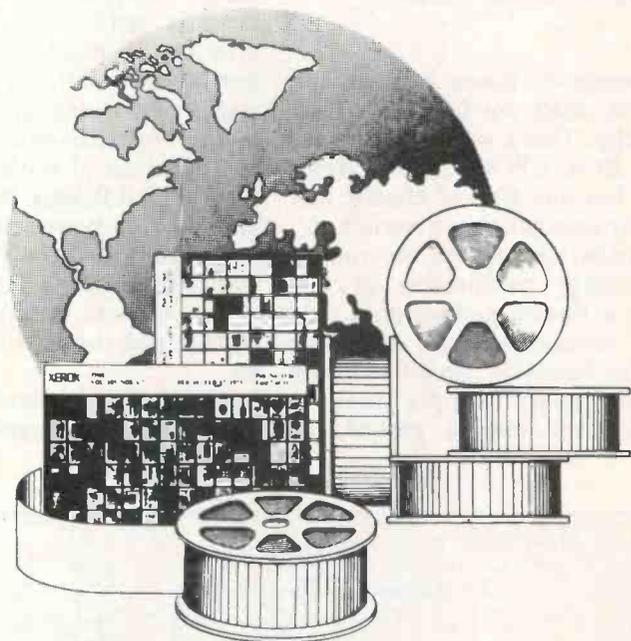

## University Microfilms International

300 North Zeeb Road  
Ann Arbor, Mich. 48106  
U.S.A.

18 Bedford Row  
London, WC1R 4EJ  
England

# RCA's unique scan rectification

## CTC99 & CTC101

In an unusual upside-down circuit, two diodes are the Siamese-twin connection between the +23V and +10.5V power supplies. Regulation of the +123V supply is accomplished by switching-on an SCR for an adjustable period of time. These sweep-rectification and regulation circuits are more difficult to understand than most, so they should be studied carefully.

By Gill Grieshaber, CET

Although dc power supplies are essential, most are boring in their simplicity. That's not true of those in the RCA CTC99 chassis. Never before has one type of chassis had so many unusual circuit variations.

As stated last month, dc voltage from bridge rectification of line voltage is filtered and supplied only to the horizontal-output transistor and the regulator circuit. This is the hot power supply that is isolated from chassis ground for

safety. A special dc supply (that operates only for a split second after the TV is turned on) starts the horizontal oscillator and driver stages. After start-up applies drive to the horizontal-output transistor, rectification of horizontal sweep from several flyback pulses provides all other dc power (including that for oscillator and driver after start-up). Isolation for these other voltage sources is furnished by the flyback and the start-up transformer.

An interesting mixture of unorthodox and conventional engineering

is found in the power supplies that are described here.

### 210V supply

Most uncomplicated of all dc supplies is the 210V source shown in Figure 1. Positive-going 250VPP pulses (without any dc component) are rectified by CR403. Hash remaining after filtering by peak-reading capacitor C409 was only 1.5VPP, and the measured dc was +208V (which supplies the color output transistors). CR403 is the smallest diode of the three in Figure 2. (The others are CR401


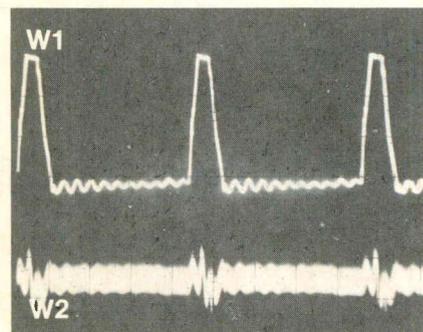
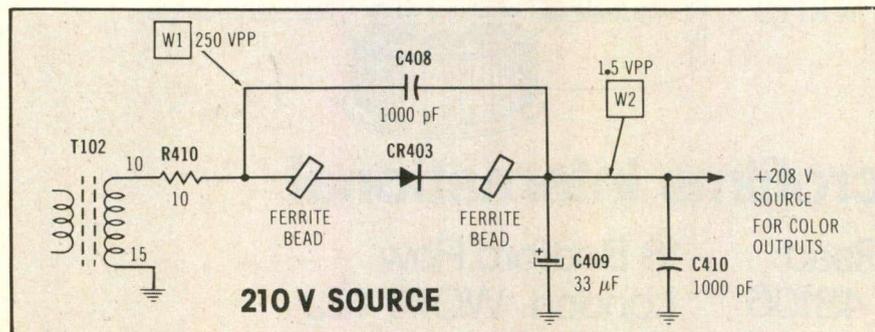


Figure 1 CR403 rectifies the positive-going horizontal-sweep pulses to produce a measured +208V for the color-output transistors. T102 is the flyback (HV transformer).

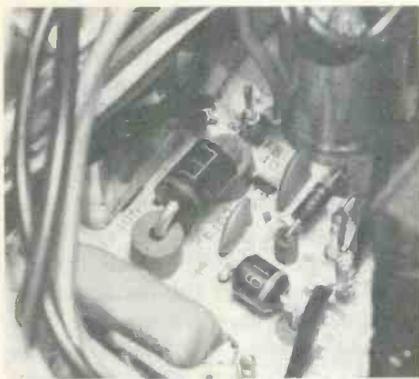

**Figure 2** Three diodes of different sizes are almost hidden in the wires between the pincushion-transistor heat sink and the flyback (at right). The smallest diode is CR403 which rectifies the +210V supply. Below it is the medium-sized CR401, and the large CR402 is shown at the left.



and CR402 that are discussed later.) These diodes are located to the left of the flyback.

The next "simple" voltage supply gave the first surprise.

### 60V supply

Both the -10V and the +60V sources appeared to be somewhat conventional. It certainly is *possible* to obtain a high B+ and a lower B- (or vice versa) by rectification of a pulse waveform's two peaks (see Figure 3). And it is unusual but not impossible for both polarities to come from two series rectifier circuits fed through a common coupling capacitor, as is true with CR405 and CR404 in Figure 4. A single series rectifier circuit fed through a coupling capacitor is not efficient because the capacitor side of the diode develops a reverse voltage that subtracts from the desired dc voltage at the other end of the diode. (This is compatible with a "law" proposed by ES editor Carl Babcoke which states: *A dc voltage produced by rectification will be positive at the cathode end of the diode or negative when at the cathode end.* So, a single diode can develop opposite polarities of dc voltage at cathode and anode in certain cases.)

When both positive and negative peaks of a sine wave are rectified by two circuits that have about the same load, and differ only in polarity, the undesired dc voltages at the coupling capacitor cancel each other. Those specific conditions allow two series rectifiers to be operated efficiently through a

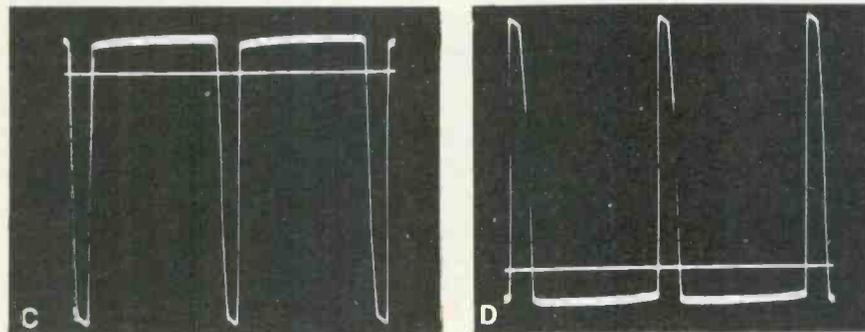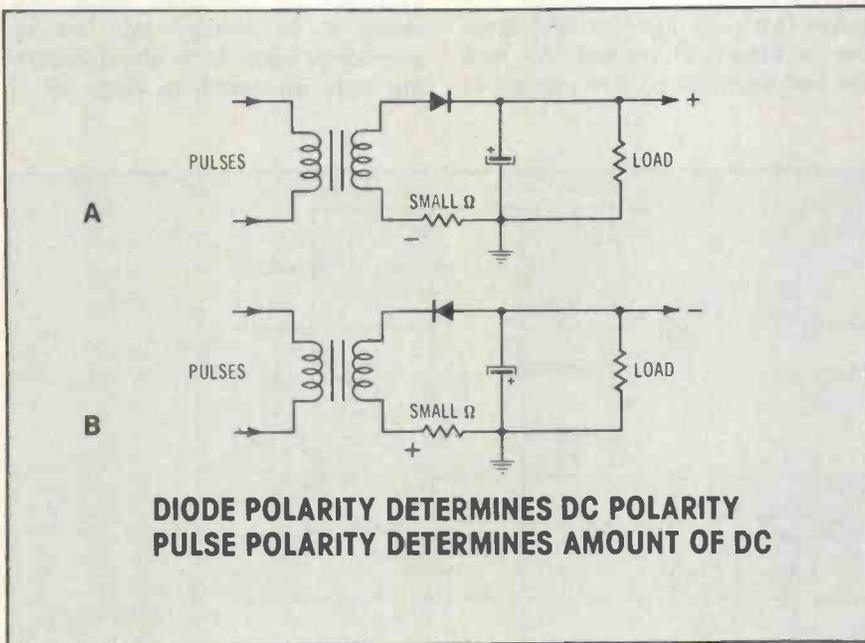

**Figure 3** The amount of dc voltage obtained from series rectification depends on the voltage between the zero-voltage line and the tip of whichever peak is forward bias for the diode. Therefore, inverting the pulse polarity changes the dc voltage reading, since the zero line always is nearer the baseline of waveforms without dc. For example, the pulses of C applied to schematic A allow only a *low positive* voltage. If the C pulses are supplied to the B schematic, about six times as much *negative* voltage is produced. Also, the D pulses with the A schematic generates a high positive voltage, but the D pulses with the B schematic produces a low negative voltage (which is equal to the low positive voltage from C pulses and A schematic). As the caption says: The diode polarity alone determines the rectified dc polarity, but the pulse polarity determines the amount of rectified dc voltage.



Diode CR405 of the 60V supply and the -10V supply CR404 diode are located near the flyback and the 123V regulator circuit.

common coupling capacitor.

Therefore, your writer at first deceived himself by believing that CR405 (+60V supply) and CR404 (-10V supply) were operated within the limits given in the last paragraph. That delusion was dispelled when it was noticed the pulse waveform was negative-going; therefore, the positive dc voltage should have been smaller than the negative dc voltage (the positive peak has less amplitude than the negative peak). Perhaps the wrong point had been scoped, and the pulses actually were positive-going.

A quick recheck proved the 74VPP pulses were negative-going,

as shown in the Figure 4 waveforms. Until a digital multimeter was used to check the dc voltages, it seemed the paradox had no logical explanation. The DMM measured +55.9Vdc at the anode of CR405 and the cathode of CR404. This dc was aiding the pulses for the positive supply and subtracting from the negative supply. But that did not explain where the positive voltage originated.

Additional dc tests answered some questions, but others appeared. A dc waveform of the pulses (with average-line and zero-line in Figure 5) showed the zero line had been moved down to about

10V above the negative tips. If the waveform had no dc, the zero line would have provided 8VPP or positive rectification and 66VPP for negative rectification. But with the zero line moved down because of the positive voltage present, the positive peak had 64VPP and the negative peak 10VPP. This corresponds closely with the measured dc voltages from rectification.

Unfortunately, the source of the positive voltage still was not known.

Two partial explanations are available. A clamping diode can insert a dc voltage into an ac waveform. Some facts about clamping were discussed on page 26 of


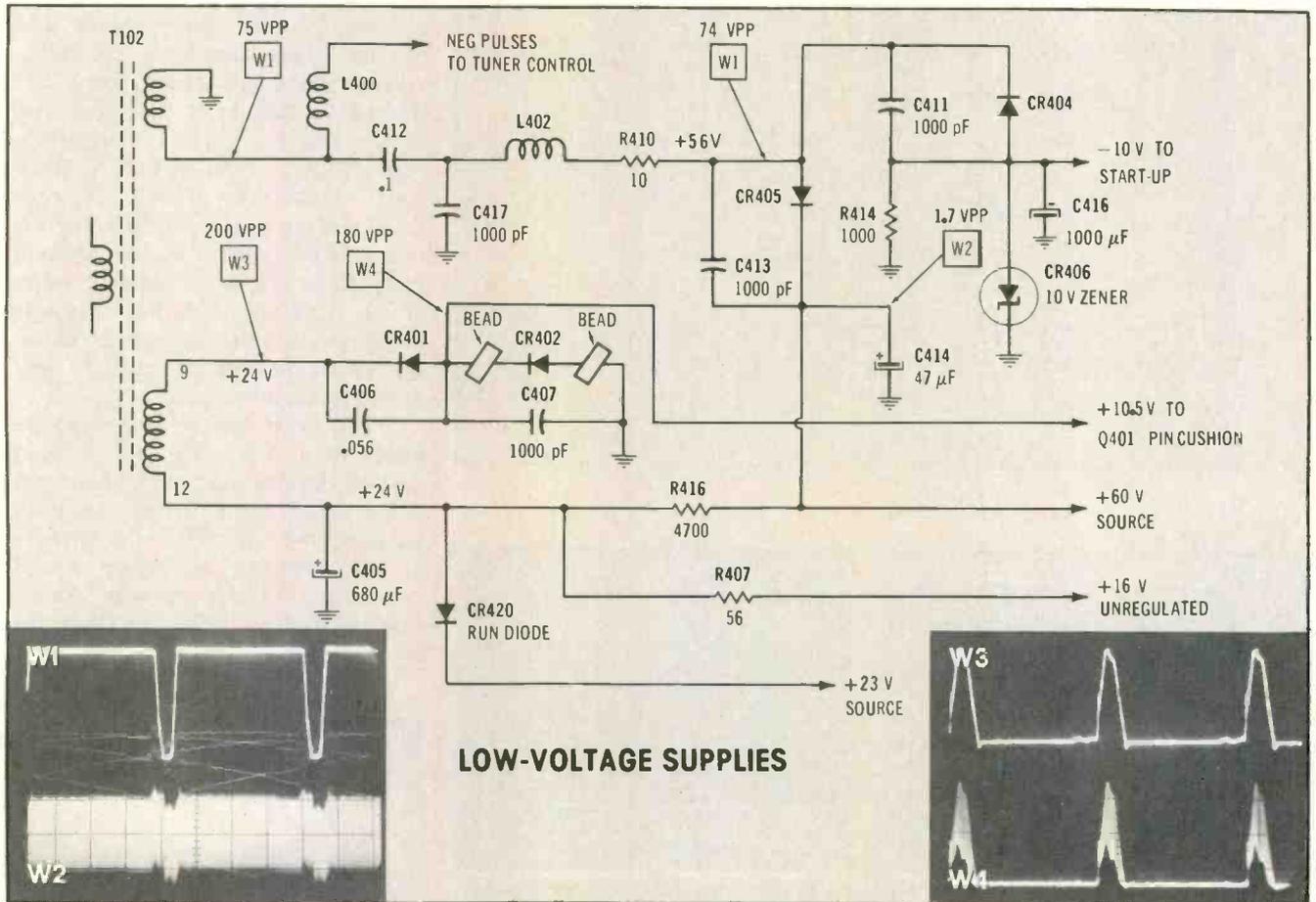


Figure 4 Both CR405 and CR404 receive input from C412. In the other Siamese-twin supply, CR405 rectifies the +23V source and CR402 rectifies +10.5V for the pincushion transistor. C406 eliminates vertical-rate variations of the flyback pulses.

Figure 5 Clamping of CR404's anode voltage forces the remainder of the rectification dc to appear at the cathode (input) of CR404. This +55V remainder is added to the input waveform, moving the original zero line (near top of waveform) down near the pulse tips (bottom line). This has the effect of increasing the voltage of the positive peak. So, the CR405 output is +63V rather than the usual +8V.

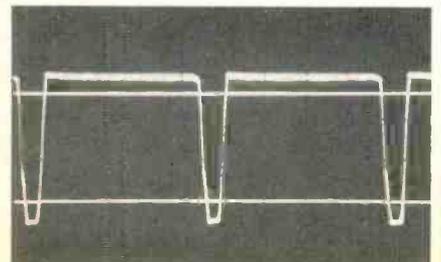

**Electronic Servicing, June 1979.** Also, one type of voltage doubler operates by adding the dc from shunt rectification to the ac input of a series rectifier (Figure 6A). As shown in the simplified schematic in Figure 6B, the CR404 rectification of the pulse negative peaks must produce 66V. But, the -10V

supply has heavy current plus a zener diode for regulation. Therefore, the -10V supply is dominant, and the remaining +55V must appear at the CR404 cathode where they add to the 10VPP waveform to produce +63V at the cathode output of CR405. (Voltage drops across the diodes and small errors


between scope and voltmeter readings account for the minor discrepancies in the figures.)

### 23V inverted circuit


Although the 23V supply is basically a series peak-reading rectifier circuit, it appears to be all wrong. The diode (CR401) is grounded through an extra CR402 diode, and the positive voltage is taken from the transformer winding. Figure 7 gives a progression from basic circuit to the same one with the flyback winding moved, and then to the same circuit redrawn as it is in Figure 4. So far, the conventional wiring has been juggled and drawn differently. But no reason for the CR402 diode has been given.

### The pincushion connection

Diode CR402 produces a dc voltage that powers the pincushion output transistor (Q401), as shown in Figure 7D. Conventional schematics do not make clear that two "siamese" power supplies are at work here. CR401 rectifies flyback

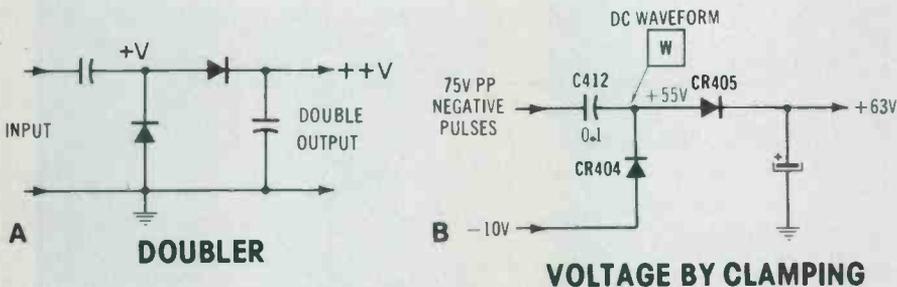

**Figure 6** (A) The conventional voltage doubler has a peak-reading shunt rectifier feeding a series peak-reading rectifier. Thus, the output is twice the dc voltage of either. A more accurate explanation is that the shunt rectifier actually is a clamp which shorts the negative peak tip to ground leaving a positive waveform. Therefore, it is possible to control the dc voltage coming from clamping (shunt rectification) by applying a reverse (negative) voltage to the anode (-10V, in this case), as shown by the (B) schematic redrawn from the CTC99.

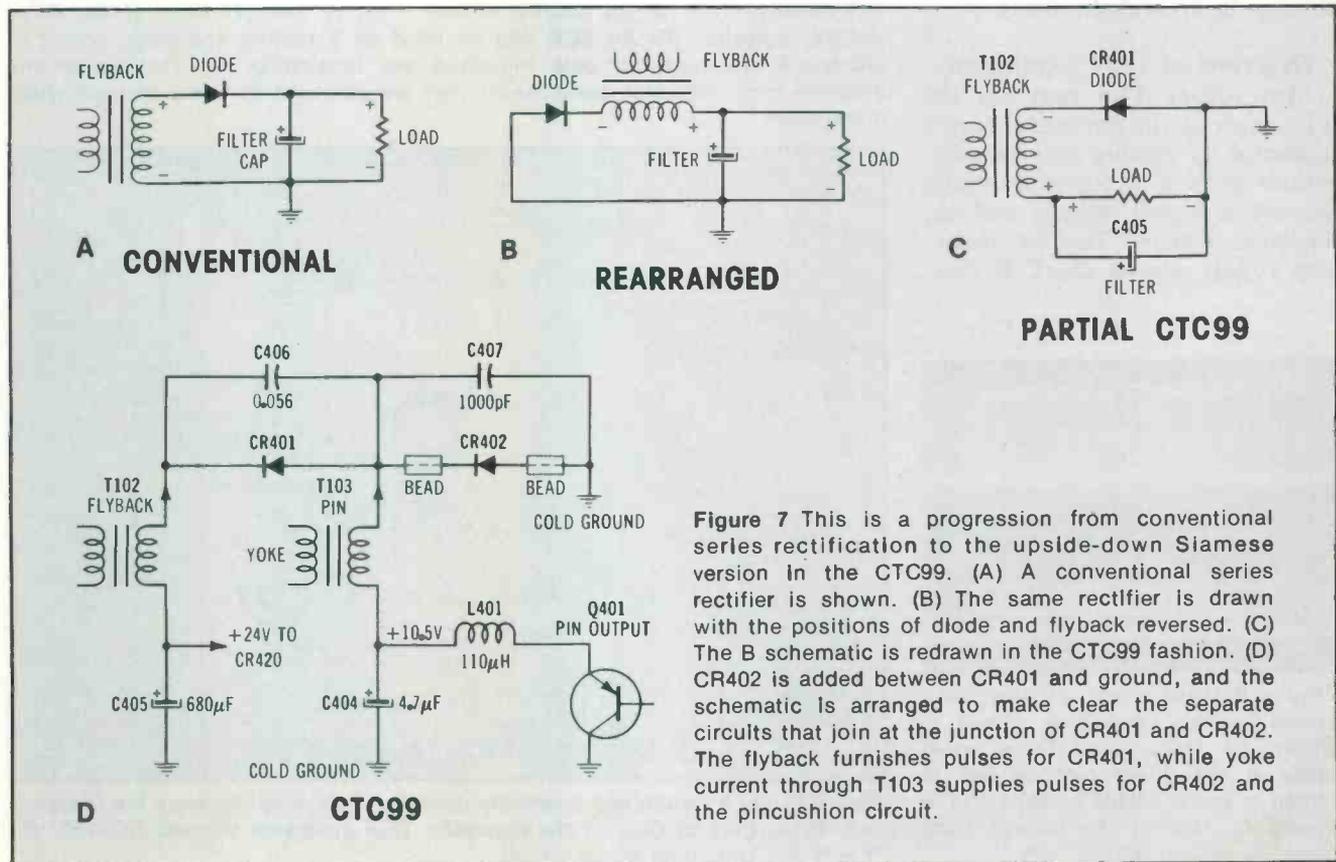

**Figure 7** This is a progression from conventional series rectification to the upside-down Siamese version in the CTC99. (A) A conventional series rectifier is shown. (B) The same rectifier is drawn with the positions of diode and flyback reversed. (C) The B schematic is redrawn in the CTC99 fashion. (D) CR402 is added between CR401 and ground, and the schematic is arranged to make clear the separate circuits that join at the junction of CR401 and CR402. The flyback furnishes pulses for CR401, while yoke current through T103 supplies pulses for CR402 and the pincushion circuit.



tance (and voltage drop) to whatever value is required to maintain the regulated supply at the desired voltage. This resistance variation is gradual and stepless. It seldom approaches either an open circuit or zero ohms. Therefore, the power transistor dissipates considerable wasted heat.

Although the RCA SCR system obtains an input dc voltage from a higher (+155V) source, the power to maintain the regulated voltage comes in on-or-off pulses, not continuously.

As shown in Figure 9A, these dc pulses are averaged by the filter capacitor. The filtered output voltage varies directly with the S1 on duty cycle. In other words, if S1 is on for 90% of the time and off for 10%, the output voltage will be 90% of the battery voltage. If the switch is turned on for 20% of the time, the voltage at the load will be 20% of the battery voltage. The RCA system operates this way, but an electronic switch replaces the mechanical switch.

**SCR switching**—An SCR has many desirable qualities of a good switch. Because of internal regenerative action, both switching on and turning off occur very rapidly. Such fast switching minimizes the heat that is dissipated, and allows a high repetitive frequency to be used.

But SCRs have a peculiarity. When the anode has positive voltage, and the gate is made positive, conduction occurs. After conduction starts, removal of the base voltage (or applying negative) does not stop the A/C conduction. Nothing except reduction of the anode current below the latching point will stop the conduction. Usually, the unlatching is accomplished by reducing the anode voltage to zero or reversing it to negative.

In Figure 9B, the control circuit between gate and cathode produces a positive-going pulse at the gate to start anode/cathode conduction *sometime* during each horizontal scanning line. SCR current continues until another part of the control circuit applies a large negative-going flyback pulse to the anode, thus stopping all SCR conduction. Those components are shown in Figure 9C.

The control circuit (covered next month) senses how much the +123V has dropped during each horizontal scan. If more than average power is needed to restore the supply, the circuit triggers-on the SCR earlier in the horizontal scanning time. During darker scenes when less replenishing voltage is needed, the SCR is triggered later in each horizontal scan. Thus the SCR is forced to conduct for longer or shorter periods of time as required to maintain the regulated voltage near the designated +123V. In all cases, SCR current is stopped during horizontal-retrace time and is not resumed until the SCR is triggered later.

**SCR pulse rectification**—An important action not mentioned in any RCA books or service data is that a portion of the +123V supply comes from rectification of the negative pulses that are applied to the SCR anode to unlatch it. This operation was discovered first in the anode current-versus-voltage waveforms, and then proved by more tests.

Voltage from rectification of the unlatching pulses greatly helps the voltage regulation at low line voltage. Otherwise, the regulation would cease when the +155V hot supply dropped to less than +123V.

#### **Regulator oscillator and control**

Remember that the so-called multivibrator oscillator (including Q104 and Q105) must reset C132 to a discharged condition during each horizontal pulse from the flyback. That allows good accuracy when Q102 and Q103 charge C132 at a rate that varies in step with the precise voltage of the +123V regulated supply. Then when the C132 voltage reaches a certain level, the oscillator fires, triggering the SCR (Figure 10). Any voltage above +123 in the regulated supply causes C132 to be charged at a slower rate. Therefore, the SCR is triggered later and contributes less voltage to the regulated supply.

A lower regulated voltage reverses that action. C132 is charged more rapidly, thus reaching the oscillation point (and triggering the SCR) earlier in the horizontal scanning time. Then the SCR conducts for a longer time, which restores the

regulated supply to the required +123V.

Q104 and Q105 are opposite-polarity transistors. Therefore, both conduct at the same time, not alternately. Q105 collector current discharges C132 through the primary winding of transformer T104, and the secondary pulse triggers SCR100 into full conduction. It latches there until turned off by the next negative anode pulse.

Actually, Q105 conducts twice during each horizontal scan. The first is when the C132 voltage charge starts an oscillation. However, C132 is not discharged completely this time. In addition, it begins to charge again following the oscillation. The second discharge conduction is produced by a retrace flyback pulse at the Q105 base, and C132 is discharged totally (as required for accurate SCR firing).

**Not a multivibrator**—Although the collectors of Q104 and Q105 are connected through resistors to the other's bases, the oscillator is **not** a multivibrator. A multivibrator must have one or both bases fed through a coupling capacitor that sets the repetition rate according to the time required for the capacitor charge to leak away. None of these bases or collectors has a coupling capacitor.

Actually, C132 is the time-constant capacitor which is connected through diode CR113 to the Q104 emitter. Even so, this oscillator is not an upside-down multivibrator, for the Q104 emitter current plays no part in the C132 charging or discharging. Instead, the C132 voltage controls the Q104 bias through this emitter connection.

#### **Next month**

Detailed circuit operation of the regulator system will be discussed first next month. This includes the oscillator, control circuit, SCR regulator and an explanation about how the regulated voltage can be higher than the source voltage at low line voltages.

Troubleshooting methods for the various power supplies and the +123V regulator will be presented after coverage of the horizontal-sweep circuit, which begins next month. □



correct, for when it is multiplied again by  $\sqrt{-1}$  it moves to the -1 position.

$$\sqrt{-1} \times \sqrt{-1} = -1$$

In this case, the operator  $j$  commands you to rotate the designated vector by  $90^\circ$ .

### Relating operator $j$ to electricity

Ac current in a purely inductive circuit lags behind the voltage by  $90^\circ$ . It would be proper to say the current vector is operated on by a  $j$ .

Ac current in a purely capacitive circuit leads the voltage by  $90^\circ$ . If  $j$  rotates a vector  $90^\circ$  for a lag, then  $-j$  should operate on it for a  $90^\circ$  lead.

The expression  $R+jX_L$  means that  $X_L$  is at an angle of  $90^\circ$  relative to  $R$ . A  $+j$  causes a counterclockwise rotation. So the expression  $R-jX_C$  indicates that  $X_C$  is clockwise by  $90^\circ$  from  $R$ .

To summarize,  $j$  simply is an

operator that rotates a vector away from the standard position. A  $+j$  rotates it  $90^\circ$  counterclockwise, while a  $-j$  rotates it  $90^\circ$  clockwise.

The term *vector* indicates a magnitude and a direction. In electrical circuits, the arrows of vectors represent magnitude and phase *differences*. Therefore, they properly should be called *phasors* rather than vectors.

### Repetition makes it true

Lewis Carroll said in *The Hunting of the Snark*, "What I tell you three times is true." Repetition does enhance credibility.

I have heard the following story more than three times. Therefore, it *must* be true. There was an intense but friendly rivalry between engineers of Swiss and American watch factories. Finally, the Swiss engineers made a spring so delicate that observation of it required a microscope. They sent it to the American engineers with the challenge,

"Match this." Before the Americans sent the spring back, they drilled a tiny hole in the end of it.

The story took on special significance for me last spring when one of my brighter students placed a circuit board on my desk. It was a breadboarded digital counter that first counted all odd numbers between zero and 20, then the even numbers were counted, and finally it counted zero to 20 by ones. "Match this," he said in an arrogant manner. I drilled a hole in the counter.

### Last charge for the wire capacitor

Letters came in for several months following previous descriptions of the marvelous infinite capacitance made from a short length of solid wire.

A few readers suggested that the wire really was made up of an infinite number of capacitors in series, thus making the final value equal to zero. Others said the circuit equivalent is an infinite capacitance paralleled by a zero-resistance leakage path, as shown in Figure 4. However, no one has argued successfully against the wire capacitor having a very thin air space for a dielectric.

### Two correct answers

Richard Colby of Honolulu, HI, doubts the completeness of my answer to a question from Allen Daubendiek (Beatrice, NE) about a question in one of my CET Practice Tests. The schematic and original question are printed in Figure 5.

The corrected answer given on page 42 of the September 1978 issue of *Electronic Servicing* was number four. Colby replied that although answer four is correct, answer three is also equally correct. In fact, answer four precedes answer three in the circuit analysis.

Good tests should not have two correct answers to any question. So, Colby wondered if the jumper could be moved to other points that would make answer two the correct condition.

Quoting from his letter: "If the short is changed to the Q1 collector and the Q2 emitter, the situation is

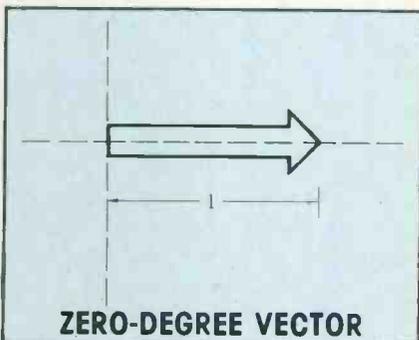


Figure 2 The value of this vector is +1. It lies in the standard or zero-degree position.

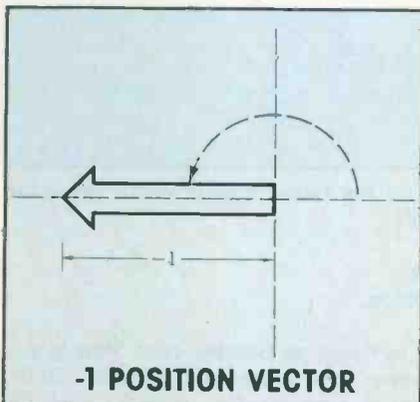


Figure 3 Rotation of the vector by  $180^\circ$  brings it to the -1 position.

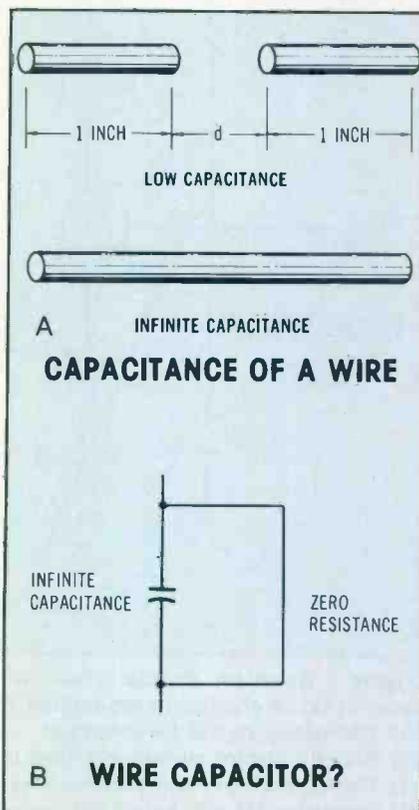


Figure 4 (A) This is the original drawing of the wire capacitance. (B) Some readers believe the wire has infinite capacitance but is paralleled by zero resistance.

# Give and Take.

Give a little today.  
Take a lot tomorrow.

That's what makes United States Savings Bonds a great way to secure your future. And why over nine million people like you have already joined the Payroll Savings Plan.

You see, once you sign up, a small part of each paycheck is set aside to buy Bonds. Saving is so automatic, you'll soon forget about it.

So buy United States Savings Bonds. Automatically, through the Payroll Savings Plan.

You won't even feel like you're giving, until all those Bonds are yours for the taking.

Take stock in America.



A public service of this publication and The Advertising Council.

## Technical notebook


similar to Q1 saturation. The emitter is made more positive by voltage from R3. This is lower forward bias for Q2, so its reduced conduction increases the collector voltage. This increases the forward bias at the Q3 base and causes heavy current to flow through Q3."

**The corrector is corrected**—One of the difficulties faced by those who make up tests is that a lack of vigilance and crosschecking can allow several answers to be correct rather than just one. It is interesting to note that Colby also fell into the same trap he tried to correct.

His suggestion of moving the jumper *does* make answer two correct. Unfortunately, it also makes answer four correct. (Answer four stated: Transistor Q1 would be cut off.) Perhaps one could argue that

the new short does not affect the R1/R2 base voltage divider, so it could not have decreased the base voltage. That's true. (In fact, the reversed bias increases the base-to-ground voltage.) However, the emitter voltage rises *above* the base voltage because of voltage from R3 (usually a low-value resistor). Remember, the emitters of Q1 and Q2 are connected together; therefore, Q1 is biased to cut off, and answer four is correct.

Because the Q1 and Q2 emitters are connected together, the new jumper position gives the same symptoms and voltage readings as a collector-to-emitter short in Q1. Check for such a short immediately after a voltage reading shows the transistor bias is reversed but collector-emitter current is flowing. □

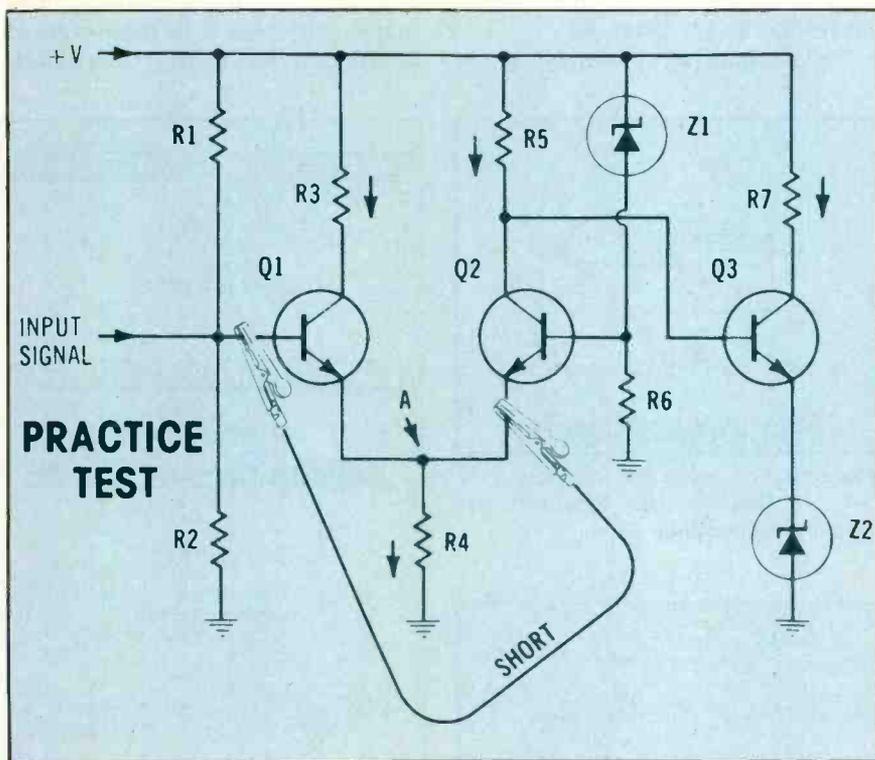

**Figure 5 Question:** In this circuit, which of the following will occur when the base of Q1 is shorted to the emitter of Q2?

- (1) Transistor Q2 will be destroyed.
- (2) Heavy collector current will flow in Q3.
- (3) The Q2 collector will become less positive.
- (4) Transistor Q1 will be cut off.

In the practice test, the correct answer is listed as number two. That is not true. Instead, both answer three and answer four are correct. Reader Colby suggested the jumper should be connected between Q1 collector and Q2 emitter, which would make answer two correct. Is anything wrong with such reasoning?



# Measuring standing-wave ratio

By Joseph J. Carr, CET

The terms *standing waves*, *standing wave ratio* (SWR) and *voltage standing-wave ratio* (VSWR) are used constantly regarding antennas, coaxial cable and radio/TV transmitters. Unfortunately, there is much confusion about the importance and measurement of standing waves. Even the name is not informative. Does it imply that other waves sit, lie down or run?

A lack of basic understanding about standing waves can lead to misuse of excellent VSWR meters so they might produce wrong readings under some conditions. The material in this article is intended to help technicians avoid such pitfalls.

## Standing-wave model

Complex subjects can be understood more rapidly when they are compared to other already-known concepts. Hydraulic water flow is used often to illustrate electron current in basic circuits.

A model of standing waves can be the undulations in a length of rope. The rope is fastened at one end to a solid wall while the other end is moved up and down in various ways. It's easy to see the waves travel smoothly down the

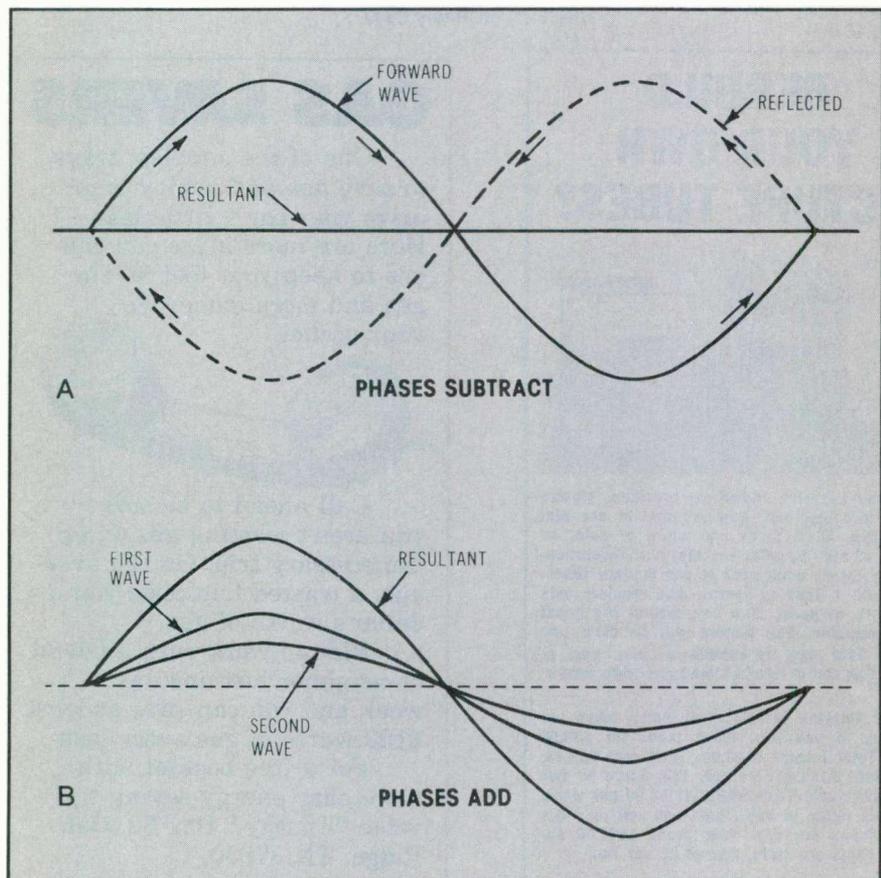


Figure 1 (A) When the forward wave and the reflected wave happen to be at 180° relative phase, subtraction occurs. If both have the same amplitude, cancellation takes place. (B) At antinodal points, both signals have the same phase, so the amplitudes add.

**ORIGINAL JAPANESE SEMICONDUCTORS & IC**

**CALL TOLL FREE**  
NATIONWIDE 800-421-2841  
OHIO 800-421-2877

TYPE	25UP10-24	1-9	TYPE	25UP10-24	1-9	TYPE	25UP10-24	1-9	TYPE	25UP10-24	1-9
2SA 234	45	53	59	2SC 756	1.50	1.80	2.00	2SC 1975	1.30	1.70	1.90
2SA 473	45	53	59	2SC 757	1.50	1.80	2.00	2SC 2026	50	54	70
2SA 484	1.80	2.10	2.40	2SC 758	1.50	1.80	2.00	2SC 2029	1.50	1.80	2.00
2SA 485	1.80	2.10	2.40	2SC 775	2.00	2.20	2.50	2SC 2076	50	64	70
2SA 493	1.10	1.25	1.40	2SC 777	3.00	3.25	3.50	2SC 2091	90	110	120
2SA 495	25	35	40	2SC 778	2.90	3.20	3.40	2SC 2092	1.80	2.00	2.25
2SA 497	1.00	1.20	1.40	2SC 779	3.00	3.20	3.40	2SC 2098	3.20	3.40	3.70
2SA 509	30	35	40	2SC 784	35	40	45	2SD 72	50	64	70
2SA 517A	1.50	1.80	2.00	2SC 785	2.00	2.20	2.50	2SD 92	1.30	1.45	1.60
2SA 561	30	35	40	2SC 793	2.00	2.20	2.50	2SD 91	1.30	1.45	1.60
2SA 562	30	35	40	2SC 799	90	80	45	2SD 187	1.60	1.80	2.00
2SA 634	40	45	50	2SC 828	20	27	30	2SD 188	1.80	2.10	2.40
2SA 635	30	35	40	2SC 829	20	27	30	2SD 225A	1.30	1.45	1.60
2SA 684	40	45	50	2SC 839	30	40	45	2SD 234	60	70	80
2SA 685	40	45	50	2SC 838	35	40	45	2SD 235	60	70	80
2SA 693	40	45	50	2SC 897	2.00	2.20	2.50	2SD 287	1.30	1.45	1.60
2SA 694	40	45	50	2SC 900	20	27	30	2SD 291	2.10	2.50	2.80
2SA 706	85	100	110	2SC 930	20	27	30	2SD 315	80	70	80
2SA 719	25	35	40	2SC 945	20	27	30	2SD 325	60	70	80
2SA 720	25	35	40	2SC 959	1.00	1.20	1.30	2SD 358D	70	80	90
2SA 733	25	35	40	2SC 1000	35	40	45	2SD 357D	70	80	90
2SA 744	4.20	4.90	4.90	2SC 1013	50	64	70	2SD 359	90	100	110
2SA 745A	3.80	4.00	4.40	2SC 1014	50	64	70	2SD 427	1.80	2.00	2.25
2SA 747	4.20	4.90	4.90	2SC 1015	50	64	70	2SD 428	1.80	2.00	2.25
2SA 847	40	53	59	2SC 1030	1.80	2.10	2.40	2SD 429	1.80	2.00	2.25
2SB 54	30	40	45	2SC 1061	70	80	90	2SD 435	90	110	120
2SB 55	40	53	59	2SC 1081	70	80	90	2SK 23	85	100	110
2SB 56	30	40	45	2SC 1082	3.40	3.55	3.90	2SK 33	60	70	80
2SB 57	30	40	45	2SC 1096	45	55	60	2SK 34	50	64	70
2SB 186	20	27	30	2SC 1122	50	64	70	2SK 40	50	64	70
2SB 187	20	27	30	2SC 1096	45	55	60	2SK 41	50	64	70
2SB 324	25	35	40	2SC 1111	2.10	2.50	2.80	2SK 49	60	70	80
2SB 325	25	35	40	2SC 1114	4.20	4.40	4.90	2SK 55	60	70	80
2SB 405	25	35	40	2SC 1115	2.50	2.70	3.00	2SK 68	40	45	50
2SB 407	70	90	1.00	2SC 1116	3.40	3.55	3.90	2SK 86	40	45	50
2SB 434	80	90	1.00	2SC 1124	80	90	90	2SK 22Y	1.40	1.60	1.80
2SB 473	70	80	90	2SC 1128	80	90	90	2SK 35	1.30	1.45	1.60
2SB 474	70	80	90	2SC 1129	3.20	3.60	3.95	2SK 37	1.80	2.10	2.40
2SB 507	70	90	1.00	2SC 1162	70	80	90	2SK 38	90	110	120
2SB 511	70	80	90	2SC 1166	50	64	70	2SK 39	1.80	2.10	2.40
2SB 516	1.00	1.20	1.30	2SC 1172B	3.20	3.60	3.95	2SK 41	1.30	1.45	1.60
2SB 517	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 42	1.30	1.45	1.60
2SB 518	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 43	1.30	1.45	1.60
2SB 519	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 44	1.30	1.45	1.60
2SB 520	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 45	1.30	1.45	1.60
2SB 521	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 46	1.30	1.45	1.60
2SB 522	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 47	1.30	1.45	1.60
2SB 523	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 48	1.30	1.45	1.60
2SB 524	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 49	1.30	1.45	1.60
2SB 525	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 50	1.30	1.45	1.60
2SB 526	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 51	1.10	1.25	1.40
2SB 527	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 52	1.10	1.25	1.40
2SB 528	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 53	1.10	1.25	1.40
2SB 529	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 54	1.10	1.25	1.40
2SB 530	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 55	1.10	1.25	1.40
2SB 531	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 56	1.10	1.25	1.40
2SB 532	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 57	1.10	1.25	1.40
2SB 533	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 58	1.10	1.25	1.40
2SB 534	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 59	1.10	1.25	1.40
2SB 535	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 60	1.10	1.25	1.40
2SB 536	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 61	1.10	1.25	1.40
2SB 537	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 62	1.10	1.25	1.40
2SB 538	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 63	1.10	1.25	1.40
2SB 539	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 64	1.10	1.25	1.40
2SB 540	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 65	1.10	1.25	1.40
2SB 541	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 66	1.10	1.25	1.40
2SB 542	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 67	1.10	1.25	1.40
2SB 543	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 68	1.10	1.25	1.40
2SB 544	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 69	1.10	1.25	1.40
2SB 545	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 70	1.10	1.25	1.40
2SB 546	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 71	1.10	1.25	1.40
2SB 547	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 72	1.10	1.25	1.40
2SB 548	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 73	1.10	1.25	1.40
2SB 549	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 74	1.10	1.25	1.40
2SB 550	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 75	1.10	1.25	1.40
2SB 551	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 76	1.10	1.25	1.40
2SB 552	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 77	1.10	1.25	1.40
2SB 553	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 78	1.10	1.25	1.40
2SB 554	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 79	1.10	1.25	1.40
2SB 555	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 80	1.10	1.25	1.40
2SB 556	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 81	1.10	1.25	1.40
2SB 557	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 82	1.10	1.25	1.40
2SB 558	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 83	1.10	1.25	1.40
2SB 559	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 84	1.10	1.25	1.40
2SB 560	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 85	1.10	1.25	1.40
2SB 561	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 86	1.10	1.25	1.40
2SB 562	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 87	1.10	1.25	1.40
2SB 563	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 88	1.10	1.25	1.40
2SB 564	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 89	1.10	1.25	1.40
2SB 565	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 90	1.10	1.25	1.40
2SB 566	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 91	1.10	1.25	1.40
2SB 567	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 92	1.10	1.25	1.40
2SB 568	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 93	1.10	1.25	1.40
2SB 569	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 94	1.10	1.25	1.40
2SB 570	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 95	1.10	1.25	1.40
2SB 571	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 96	1.10	1.25	1.40
2SB 572	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 97	1.10	1.25	1.40
2SB 573	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 98	1.10	1.25	1.40
2SB 574	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 99	1.10	1.25	1.40
2SB 575	1.10	1.20	1.30	2SC 1200	25	35	40	2SK 100	1.10	1.25	1.40

**Minimum Order \$5.00**

Ask for our 48 page catalog containing 800 Japanese transistors, IC, FET, diodes and test equipment and parts for service.

**FUJI-SVEA ENTERPRISE**

a Division of Fuji-Svea Incorporated

P. O. Box 40325 Cincinnati, Ohio 45240  
Hours: Mon-Fri 10-7 Sat 11-5 (EST)

Circle (7) on Reply Card

**REBUILD YOUR OWN PICTURE TUBES?**



With the Lakeside Industries precision picture tube rebuilding unit, you can rebuild any picture tube, be it black and white or color or 20mm or etc. We offer you the most revolutionized precision equipment of our modern times. This unit is easy to operate and requires only 4 x 8 ft. of space. You can rebuild the finest tube available. The picture will be clear and sharp. Your cost to rebuild a color tube is \$5.50. Your cost to rebuild a black and white tube is \$2.15.

Profit? Imagine building four color tubes per day and if you sold these tubes for \$60.00 each. Total income \$240.00. Total cost \$26.40. Net profit \$213.60. Multiply this figure by five days per week. Your profit \$1,068.00 per week. Cut this figure in half! Build and sell only two color tubes per day. Your profit \$534.00 per week. Facts are facts, figures do not lie.

For further information, please send your name and address to Lakeside Industries, 4071 N. Elston Ave., Chicago, Illinois 60618. Phone: (312) 583-6565.

P.S. No salesman will call.

Circle (10) on Reply Card

**G**

short or an open load. However, the phase is different by a quarter wavelength for the two conditions.

### Measuring SWR

SWR can be measured with different degrees of accuracy at some point in the transmission line by comparing one of these conditions: forward versus reflected voltage; forward versus reflected current; or forward versus reflected power.

VSWR tests by RMS power provide consistently accurate readings, but they are not fast or convenient. For example, if a Bird model 43 Thru-line RF wattmeter is used to measure the forward and reversed powers, the VSWR must be calculated from the following formula:

$$VSWR = \frac{1 + \sqrt{\frac{P_r}{P_f}}}{1 - \sqrt{\frac{P_r}{P_f}}}$$

Of course, radio technicians soon learn the range of forward versus reversed power readings that indicate acceptable VSWR ratios, and therefore do not calculate each one.

The advantage of power SWR measurements is that testing at the transmitter, the antenna base or any other point in the coaxial cable gives the same dependable reading.

Most service-shop SWR meters compare forward and reversed voltage or current. However, these tests are sensitive to the location of the measuring equipment. In fact, they might mislead a technician into believing erroneously that VSWR can be reduced to 1:1 by trimming the length of the coaxial cable.

These voltage or current VSWR meters do indicate relative VSWR, and so are useful for trimming the antenna length or tuning the matching circuit for minimum VSWR reading. But the 1.3:1 or 2.2:1 VSWR numbers obtained are not valid unless the measurement is made either at the base of the antenna or through a section of coaxial cable that is a multiple of the signal half wavelength.

For 27MHz, a half-wavelength

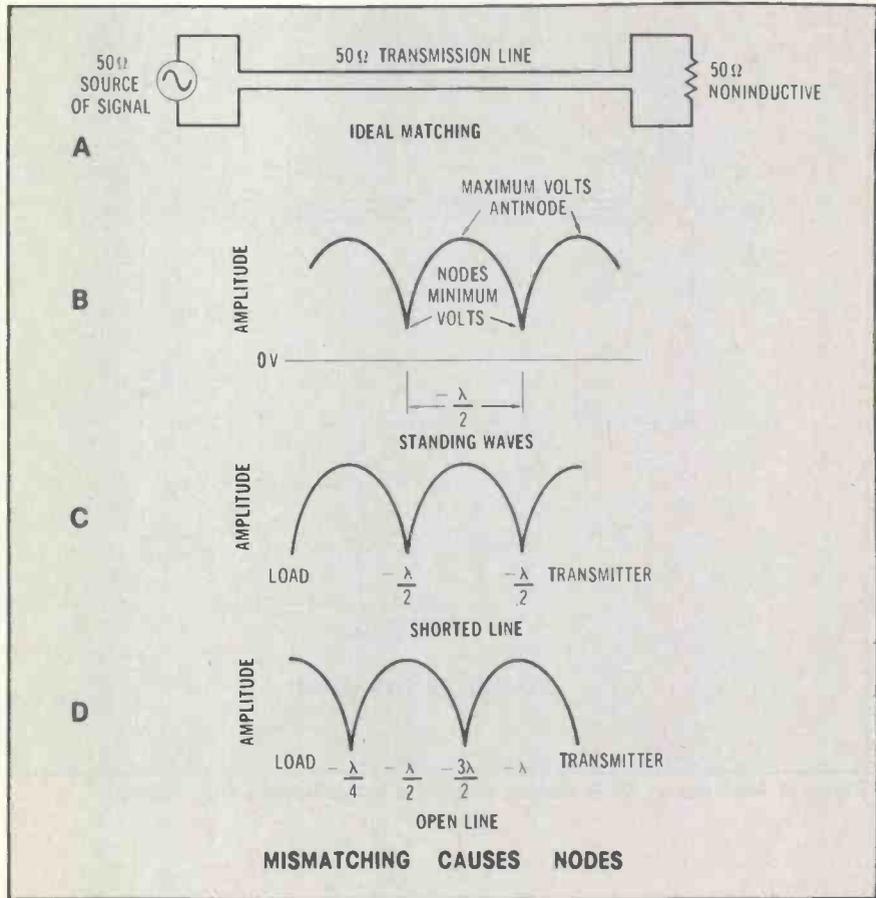


Figure 2 Mismatching of impedances produces the nodes and antinodes of standing waves. (A) Perfect impedance matching eliminates all standing waves. (B) The nodes are a half wavelength (of signal) apart. (C) and (D) Although the standing waves have identical high amplitudes, a short or an open at the antenna end of coax changes only the relative phase of the antinodes (or nodes).

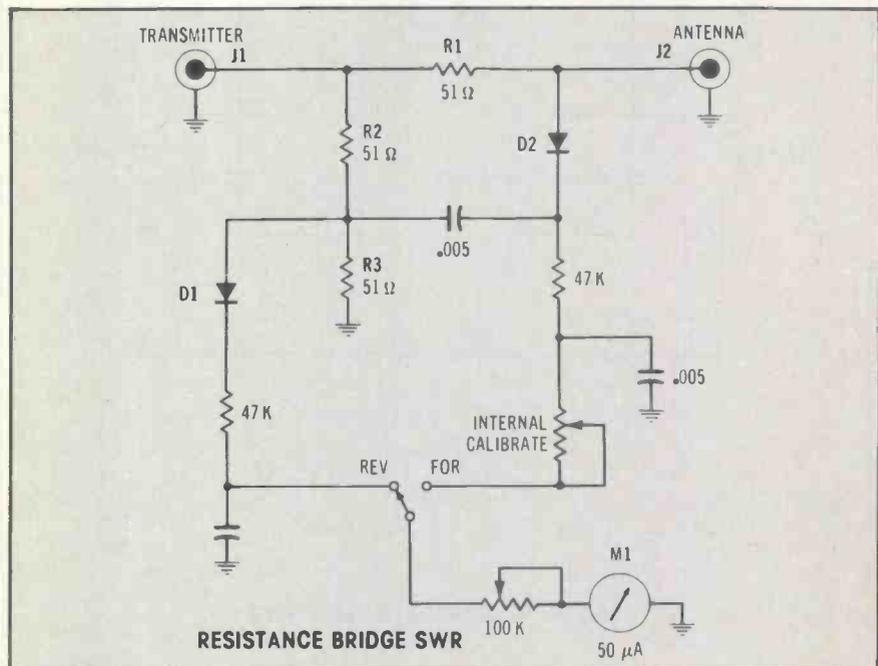


Figure 3 The voltage drops of forward and reversed signals are measured in a resistance-bridge SWR tester.

## Standing waves

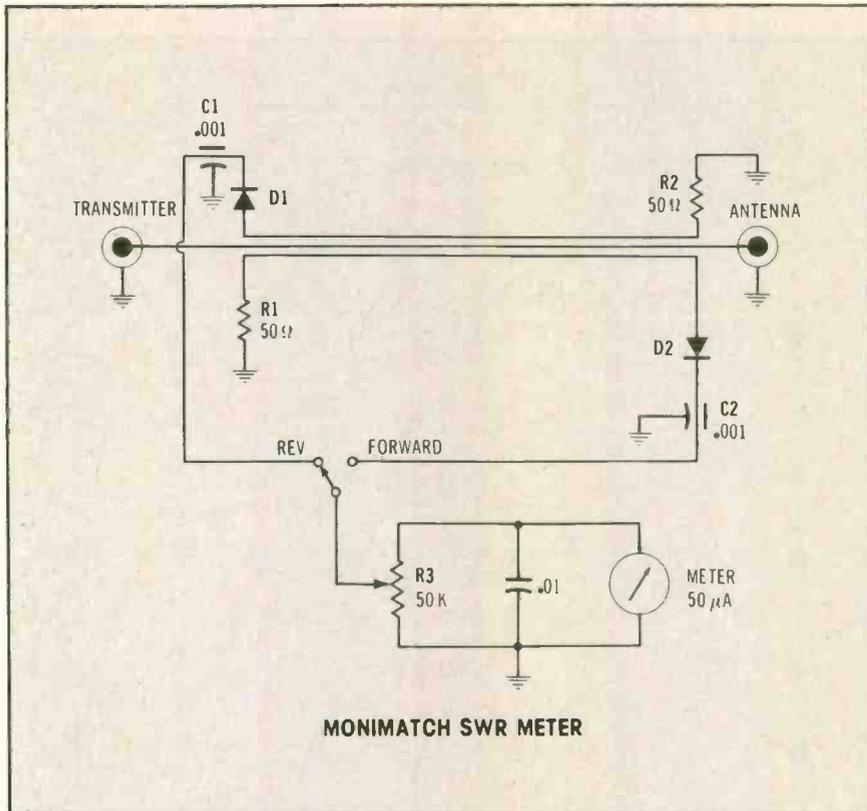


Figure 4 Monimatch SWR meters employ a transmission-line bridge.

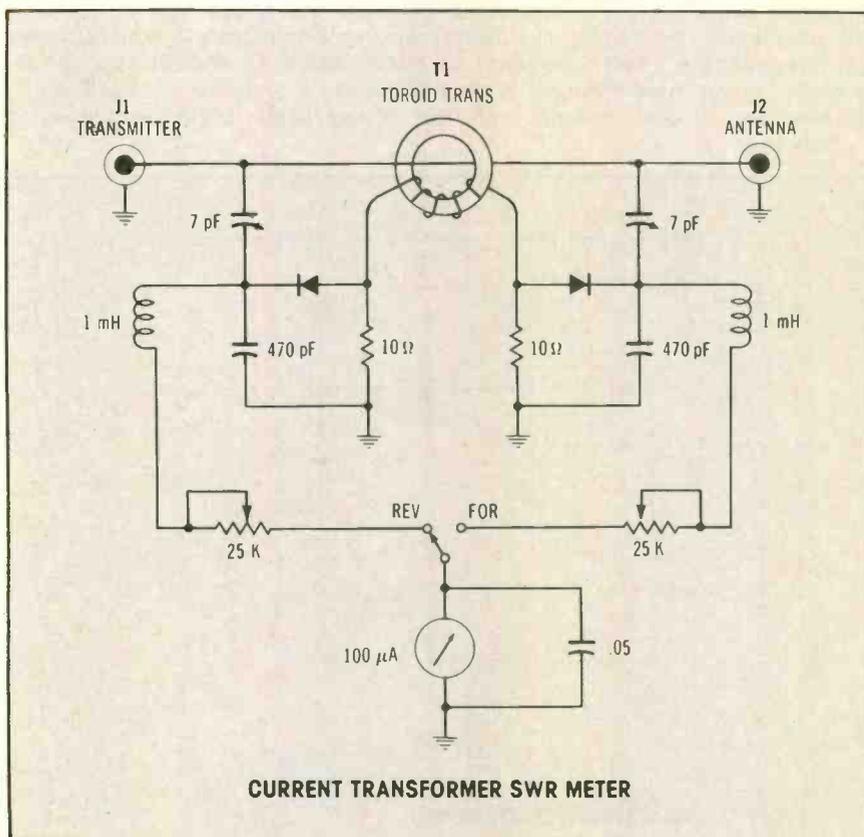


Figure 5 A toroid-type current transformer tests forward and reversed current to measure the SWR.

cable should be 14.6 feet long for foam type or 12 feet for regular.

### Bridge VSWR meter

Figure 3 shows the schematic of a typical resistance-bridge type of VSWR meter. Two of the bridge arms are R1 and R3, and the bridge is balanced when the antenna impedance is exactly 51 Ω.

The switch is set to forward, the meter control is adjusted for full-scale reading, then the switch is turned to reverse for the SWR reading from a special meter scale.

### Monimatch meter

Two identical pick-up conductors are spaced the same distance from the center conductor of the internal transmission line in the monimatch type of SWR meter (Figure 4). RF current in the center conductor induces current in the pick-up wires and the signals are rectified by matched diodes to form dc voltages which are in proportion to the amplitudes of forward and reflected signals. With the switch set for forward, the calibrate control is adjusted for a full-scale reading. After the switch is turned to reverse, the SWR is read from the calibrated meter scale.

### Toroidal type

Basically, a toroidal-transformer VSWR indicator (Figure 5) operates similarly to the previous monimatch type. However, the doughnut-shaped current transformer is used instead of a pick-up assembly.

RF wattmeters often employ a toroidal transformer, using the Ohms Law formula of wattage equals current squared divided by resistance. Capacitor values are chosen to provide accurate readings between 3MHz and 30MHz. This frequency compensation is not required for SWR readings because the meter is calibrated before each measurement.

### Other antenna instruments

Although many CB-radio technicians use only a SWR meter and perhaps an RF wattmeter, there are other antenna-testing instruments that can provide valuable information.

An antenna-impedance meter measures the resistive component of

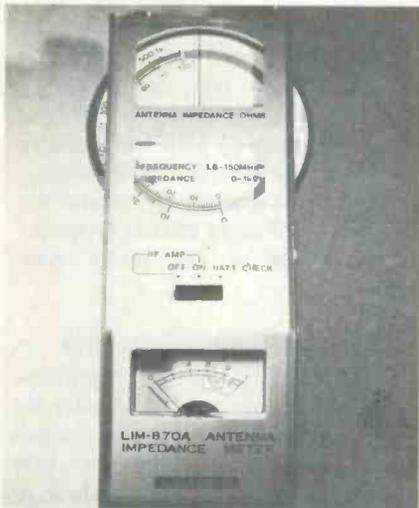


Figure 6 Leader model LIM-870A tests antenna impedances between zero and 1000  $\Omega$ .

the antenna-feedpoint impedance. One commercial model (Leader LIM-870A) is pictured in Figure 6. It employs a variation of the standard ac Wheatstone bridge to measure between zero and 1000  $\Omega$ .

Another method of measuring antenna impedance is found in noise bridges of several brands (pictures and schematic in Figure 7). A noise bridge also is a type of Wheatstone bridge, but a wide-bandwidth noise signal is used instead of a sine wave. The noise is produced by a reverse-biased diode inside the meter, and is amplified before it is fed to the bridge. This is *white* noise, containing all frequencies (theoretically).

Operation of the noise bridge is simple, although it requires a receiver (preferably with an "S" meter) for the test-frequency band. First, the bridge control is set for the coaxial-cable impedance (50  $\Omega$  in most cases), and then the receiver is tuned slowly around the desired frequency until a dip or null of the noise level is noticed. This is the resonant frequency of the antenna.

Some models have an additional control to show whether the resonant frequency is upband ( $X_L$ ) or downband ( $X_C$ ) from the desired one.

Approximate measurements of resonant frequency can be made with a dip meter (formerly a grid-dip meter, when tubes were

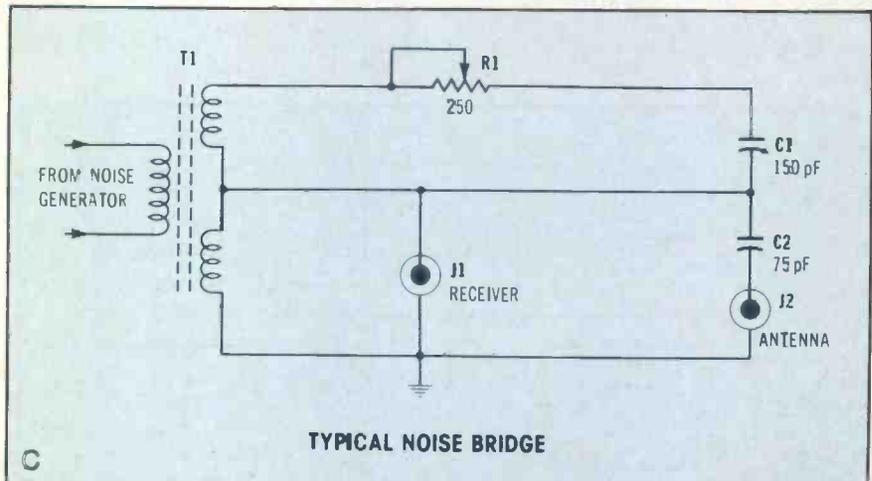


Figure 7 (A) The Omega-T noise bridge tests antenna resonance. (B) Palomar also markets a noise bridge with an extra control that can indicate whether the antenna has a high or low resonant frequency. (C) This is a typical noise-bridge circuit.



Figure 8 The Heath Solid-State Dip Meter can measure the approximate tuned frequency of coils.

## Standing waves

used), which is an RF L/C variable-frequency oscillator having a plug-in tank coil mounted externally, as shown in Figure 8. When the dip meter coil is placed near (and in line with) the coil that is being tested for resonant frequency, energy is transferred from one coil to the other. If both coils have the same resonant frequency, the test coil loads down the dip signal and reduces the meter reading.

### Sweep tests with scope

Sweep tests can reveal the exact physical length of coax needed for

any specific frequency. For example, the author used the equipment of Figure 9 to cut a coaxial cable for a certain 27MHz frequency.

A short at the load end of coax reflects a similar short to the input end when the cable length is precisely a half wavelength of the signal. Therefore, a dip in the sweep response curve shows the location of the half wavelength.

The coax was cut too long in the beginning. Next, the load end was shorted from shield to center wire, and the sweep/marker test was made to be sure the dip of the

response curve was beyond the marker. One inch was clipped off and the sweep test made again. This was continued until the response dip merged with the marker. Therefore, the coaxial cable electrical length was correct for producing accurate SWR tests at that frequency, regardless of the meter type used.

### Summary and comments

Total elimination of standing waves can be accomplished only by perfect matching of source impedance, cable or transmission line impedance, and the non-inductive load impedance. Any less-than-perfect matching allows the signal to bounce from the load (or the source) and travel back through the cable in the wrong direction.

Relative phase between these forward and reversed signals produces stationary points of maximum amplitude (nodes from addition) and minimum amplitude (antinodes from subtraction). These maximum and minimum areas are called standing waves.

Notice that standing waves do *not* cause any reverse signal; instead, the direct and reversed signals produce standing waves. However, standing waves in SWR units can be measured either directly according to the node and anti-node amplitudes or indirectly by the amount of forward and reversed signals. Measurements by RMS power are accurate when made *anywhere* in the coaxial/antenna system, while SWR measurements by voltage or current vary according to where the meter is connected.

**TV ghosts**—Excessive reversed signals (high VSWR ratio) reduce the total power radiated by the antenna in radio systems. Also, the reverse signal might be absorbed partially by the output stage, thus increasing the dissipation. But the bouncing signals cause other problems.

At the frequencies used by MATV and CATV systems, these reversed signals can cause an effect similar to location ghosts. So, correct matching of all such systems is much more important for obtaining sharp video pictures than for reducing transmission losses. □

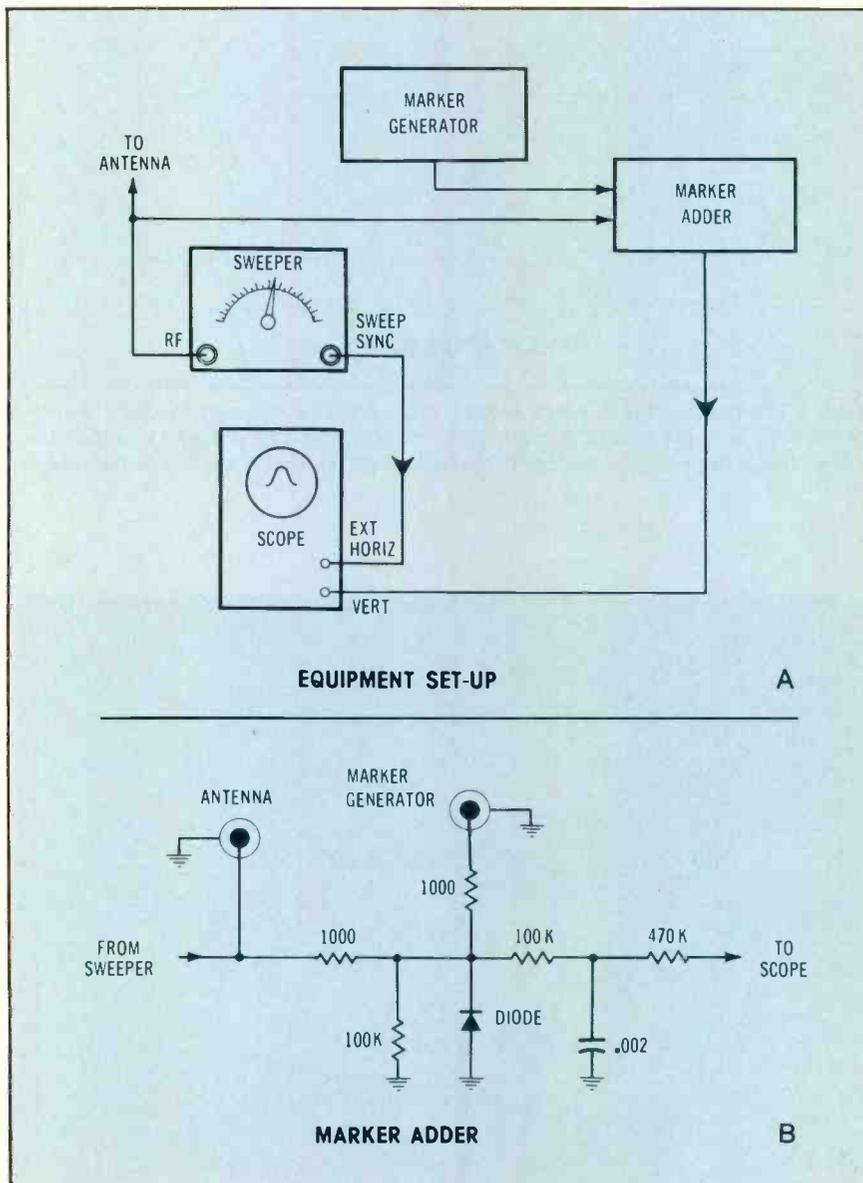


Figure 9 (A) This interconnection of equipment can show when coax is a half wavelength. (B) A marker adder for post-injected markers is easy to construct.

# catalogs literature

A six page brochure illustrating the Intervox line of custom auto speaker products is available from **International Components**. The brochure contains sections describing speakers, acoustically transparent wire mesh grilles, custom metal and plastic grilles, speaker controls and accessories.

Circle (17) on Reply Card

The **Sprague** short-form catalog WR-167B lists the complete line of Sprague semiconductor products. The catalog contains 65 pages of integrated circuits, transistors and diodes, with new products listed in every category.

Circle (18) on Reply Card

The **ETCO Electronics** catalog, issue H, contains 80 pages of unusual and hard-to-find parts, factory termination material and hundreds of bargain-priced items.

Circle (19) on Reply Card

A 60-page catalog from **Sprague** contains information on capacitors, resistors, interference filters, switches and optoelectronic devices. Also included are pulse transformers, miniature lamps, wiring components, both entertainment and MRO, as well as for electronic experimenters, schools and laboratories.

Circle (20) on Reply Card

A handbook called **Mold Design Guide** for the designer discussing injection molding of Noryl thermoplastic resins is available from **General Electric Company's Plastics Division**. The pocket-sized pamphlet is designed for on-the-job use.

Circle (21) on Reply Card

A short form catalog is available from **Ailtech Division Cutler-Hammer**. Photographs and specifications of such items as frequency synthesizers, spectrum analyzers and EM/RFI test instrumentation are included.

Circle (22) on Reply Card

**Radio Shack** has issued a 24-page catalog, *The Expanding World of TRS-80*. It includes information on the model I and model II TRS-80 microcomputer systems. Also listed are peripherals and accessories

such as five line printers, disc expansion units, a voice synthesizer, system desk, dust covers, carrying cases and software including more than 50 ready-to-run programs. □

Circle (38) on Reply Card




## Shopping

*At Profit Saving Prices*


For Belts, Chemicals & Solid State Devices - Phono Cartridges & soldering needs

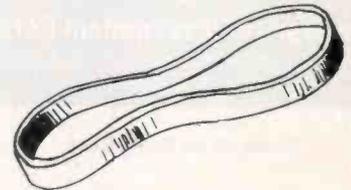**BELTS** Quality PRB exact replacement belts for Video Tape machines, Cassettes, 8-tracks, & Turntables - in stock & ready for immediate shipment . . . . .  
AT PROFIT SAVING PRICES


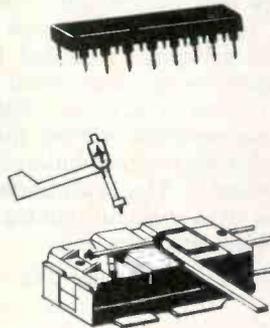
### SOLID STATE DEVICES

Original Japanese Replacement Transistors & Integrated Circuits. ECG Replacements from Raytheon . . . . .  
AT PROFIT SAVING PRICES



### PHONO NEEDLES & CARTRIDGES

**Pfanstiehl**

Thousands of quality needles in stock for for Immediate delivery . . . . .  
AT PROFIT SAVING PRICES

### CB & AUDIO ACCESSORIES

Patchcords, cables, record & tape care products - in stock for immediate shipment . . . . .  
AT PROFIT SAVING PRICES



**SERVICE AIDS** Aerosol Degreasers & Tuner Cleaners, lubricants, adhesives, solvents . . . . .  
AT PROFIT SAVING PRICES



**PROJECTOR  
RECORDER  
Belt Corporation**

200 Clay Street, P.O. Box 176  
Whitewater, WI 53190

**Toll Free 1-800-558-9572**

Ask for our  
New Products Catalog  
& your Free Belt Bible  
Complete Belt Cross-reference Chart

Circle (8) on Reply Card



## endeco soldering & desoldering equipment

### SOLDERING IRONS

Pencil style. Safety light. Two heats — 20w and 40w. 6 tips. Unbreakable handle, 2 and 3 wire neoprene cords.

### DESOLDERING IRONS

Pencil style. Safety light. Some operate at 40w, idle at 20w. 8 tip sizes. 2 and 3 wire neoprene cords.

### SOLDERING & DESOLDERING KITS

Everything needed to solder or desolder or both. All in a handy lifetime metal box with hasp.

See your distributor or write...

## Enterprise Development Corp.

5127 E. 65th St. • Indianapolis, IN 46220  
PHONE (317) 251-1231

Circle (9) on Reply Card

# You Are Not ALONE!



If you think that being in business makes you INDEPENDENT, think again! Consumerists and government agencies are your silent — but greedy — partners; AND THEIR SHARE COMES FIRST; even if you don't make a profit.

**WELL, YOU DON'T HAVE TO  
FACE THEM BY YOURSELF**

**JOIN NESDA  
AND YOUR LOCAL &  
STATE ASSOCIATIONS**

Send for more information to:  
NESDA, 2708 W. Berry St.  
Fort Worth, Texas 76109



# productreport


### 800MHz mobile antenna

An 800MHz low-silhouette radome-enclosed antenna, model ASP-930, has been designed by **The Antenna Specialists**. The unit has a maximum power rating of 100W and a VSWR of less than 1.5:1 over a 60MHz bandwidth. Frequency range is 806-866MHz.

Circle (23) on Reply Card
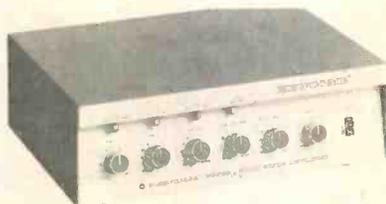
### P. A. amplifier

The new Pathfinder line of all-solid-state public address amplifiers is being manufactured by **Newcomb Audio Products**. Six models in the line range from 25 to 100 watts. Most of the amplifiers have microphone-precedence music muting,



Circle (24) on Reply Card

### Distribution amplifiers

Three Eagle series MATV distribution amplifiers are available from



**Trans USA**. All models are 75  $\Omega$  units with gains of 8dB (DA-7508), 16dB (DA-7516) and 24dB (DA-7524). Maximum output is 52dBmV and noise figure is 7dB on all models.

Circle (25) on Reply Card

### Power inverters

Two Micronta power inverters for converting 12Vdc/120Vac to power ac appliances from a car, boat or recreational vehicle battery are new from **Radio Shack**. The 300W (25 amps) and 100W (12 amps) inverters



feature a normal/boost switch and automatic overload protection.

The 300W inverter is priced at \$79.95. The 100W unit, with cigarette lighter plug, is \$39.95.

Circle (26) on Reply Card

### Industrial sound transducer

The MS-1 electronic sound transducer, by **Floyd Bell Associates**, is a piezoelectric audio warning device that provides size and current



advantages over buzzers or speakers. The unit is a medium impedance device of a few thousand ohms. Operating voltage for the MS-1 ranges up to 150VPP maximum.


Circle (27) on Reply Card

### Microwave survey meter

**Holiday Industries** has developed a microwave survey meter, the HI-1800. It has a single range of 0-10 mw/cm<sup>2</sup>, push-to-use switch

and low-battery indicator. Two 9V batteries are included.

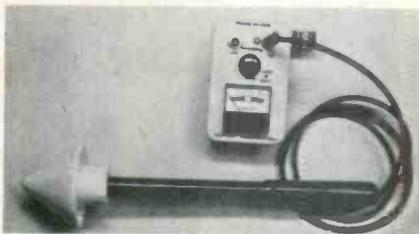The HI-1800 comes complete with carrying case, beaker and operating instructions for \$169.



Circle (28) on Reply Card

#### Industrial electrical tapes

Tesa offers 16 different electrical tapes in a range of base materials, dielectric strengths and insulation class ratings. The line features tesa-film tapes which are either polyester or kapton film tapes with dielectric strengths ranging from 2100 to 4200 V/mil.

Circle (29) on Reply Card

#### Receiving tubes

Sylvania has added nine receiving tubes to their electronic tube line. The new line includes: Tube EY500A16E4, designed primarily for damper service in color television receivers; PCL805/18GV8 contains a double triode/pentode for




vertical multivibrators; PCL86/14GW8 and ECL86/6GW8 contain high amplification triodes and pentodes for audio power applications; PL504/27GB5 and EL504/6GB5, beamed pentodes with Magnaval construction and a special anode for better dissipation.

Circle (30) on Reply Card

## When you price by "The Book"... everyone benefits!

tv & radio  
tech's guide  
to pricing

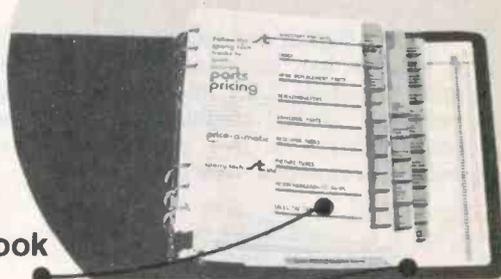

Eliminates undercharging... controls overpricing... treats both customer and shop owner fairly!

### The Parts Pricing Book

Lists over 160 pages of current parts prices for instant reference. Computerized with automatic up-dating... \$24.50 + up-dating.

### The Labor Pricing Book

The new 4th Edition will expand your business mind as never before! Greatly simplified while being expanded to include all the new products, as well as the traditional.

**CALL TOLL FREE: 800-228-4338**

8/5 C.S.T. MONDAY/FRIDAY

Each book is a great time saver!  
Pricing parts and labor from **ONE BOOK**... together they're fantastic!

**sperry tech inc.** P.O. Box 5234 Lincoln, Nebraska 68505

Circle (11) on Reply Card

IT'S NO PUZZLE

TO ORDER

### OELRICH SERVICE FORMS

FOR TV-RADIO & 2 WAY RADIO SERVICE LEGAL FORMS FOR CALIF. FLA. UTAH NOW AT YOUR PARTS JOBBER OR WRITE FOR CATALOG B64  
**OELRICH PUBLICATIONS**

4040 N. NASHVILLE AVE. CHICAGO, ILLINOIS 60634

Circle (12) on Reply Card

**Heart disease and stroke will cause half of all deaths this year.**



**American Heart Association**

WE'RE FIGHTING FOR YOUR LIFE

NATESA  
5908 S.  
Troy  
Chicago  
IL 60629



### ARE YOU A PRO?

...the not for profit association championing independents' right to compete, and delivering valuable benefits continuously since 1950.

- LEADING SPOKESMAN
- TRADE INFORMATION DISPENSER
- WATCHDOG
- LOBBYIST
- YARDSTICK OF STANDARDS
- CONSUMER RELATIONS
- COUNSELOR
- PROBLEM SOLVER

We are not freeloaders. So our check for \$60.00 dues is attached. As our special premium, please ship the indicated \$15.00 Manual.

- Practical Business Manual  
- OR -  
 Service Contract Manual

# test equipment report

## Digital multimeter

Weston has designed the model 6100 3½-digit LCD display audio response digital multimeter. The unit features a five range audio response function which allows go-



no-go testing to be performed without paying attention to the display and has instantaneous response. The unit also features five functions: ac/dc volts, ac/dc current and resistance.

The 1600 is priced at \$139.

Circle (31) on Reply Card

## 15MHz dual-trace scopes

Telequipment's two new 15MHz scopes, the D1015 and D1016, feature 8 x 10 cm CRTs and color-coded front panels, 5mV to 20V/div vertical sensitivity, and triggering capa-




bilities including TV mode. The D1016 also features full sensitivity X-Y, differential, X5 vertical magnification and a variable time base.

Circle (32) on Reply Card
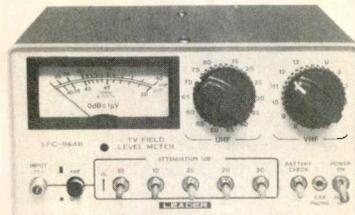
## Strength meter

The model LFC-944B VHF/UHF field strength meter from Leader

measures levels of 20 to 120dBµV on VHF channels. A built-in attenuator up to 80dB of attenuation in 10dB steps. The unit features VHF channel selection with accurate detuned



The unit features VHF channel selection with accurate detuned tuning and continuous UHF tuning, and is battery powered.

The suggested price is \$512 complete.

Circle (33) on Reply Card

## Scope probes

Model SP100, replacement 1X/10X scope probe, is available now from Test Probes. A ground reference switch position enables the scope input to be grounded at the probe tip. This feature serves as a positive means of trace identification, and allows a zero voltage to be selected from the probe. The cable has a flexible and rugged center conductor, strain relief at connector and probe head fittings, and a BNC-pin-diameter tip. For the 10X function, a 10-60pF trimmer range is provided.

The SP100 comes complete with sprung hook, trimmer tool, BNC adaptor, IC tip, and insulating tip for \$36.

Circle (34) on Reply Card

## 30MHz scope

The B&K-Precision model 1479 features an internal 160nS signal-delay line, minimum visible delay of 12nS. Rise time is 11.7nS or less. Other features include a 10-position vertical attenuator which covers 5mV to 5V per cm at an accuracy of +3%, 20 calibrated sweep positions from 0.2µsec/cm to 0.5 sec/cm (X5 magnification increases sweep speed to 40 ns/cm), and TTL-compatible intensity modulation. The 1479 has fully regulated power supplies and

is designed to maintain accuracy over a 105-130VAC range. Optional accessories include a rack mounting kit and protective cover.


The unit lists at \$1099.



Circle (35) on Reply Card
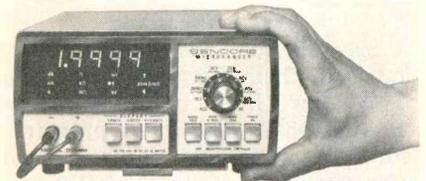
## Microprocessor-controlled DVM

Sencore is now marketing a microprocessor-controlled auto-ranged DVM. Basically a 4½-digit instrument, the DVM-56 Microranger can be changed to a 3½ or 2½-digit DVM with the push of a button. The DVM-56 features a dc voltage accuracy of .075%, plus or



minus five counts, with 15M Ω input impedance. Three automatic peak-to-peak ac voltage ranges to 2KV at 100KHz, also are featured. Three automatic dB ranges to 1KV at 20KHz from -43 to +62dB, 1mV into 600 Ω, extends the use of the DVM to audio frequencies.

The DVM-56 is priced at \$695.

Circle (36) on Reply Card

## VHF signal generator

The Leader LCG-138 VHF signal generator is a calibrated source of test signals for CATV and MATV systems. The unit provides calibrated outputs on two high and two low VHF channels at accurate levels from 60 to 10dBµV in 10dB steps. It is battery powered.


The LCG-138 sells for \$244. □

Circle (37) on Reply Card

<b>HITACHI</b>	
Chassis SU .....	1848-1
<b>QUASAR</b>	
Chassis TS-967, VTS-967 .....	1848-2
Chassis AEDTS-961N (Run A01) .....	1849-2
<b>SAMPO</b>	
7619 .....	1850-1
<b>ZENITH</b>	
Chassis 19KC52	
Remote Control Receiver 130-9	
Remote Control Transmitter 124-11 .....	1850-2
<b>GENERAL ELECTRIC</b>	
Chassis 10AA-E/-F .....	1869-1
<b>GOLD STAR</b>	
Chassis NF7X .....	1870-1
<b>HITACHI</b>	
Chassis SK-A4 .....	1871-1
<b>MAGNAVOX</b>	
Chassis T809-01-AA/02-AA/03-AA/04-AA/05-AA ...	1865-1

<b>QUASAR</b>	
Chassis AGTS-965N, ETS-965N, LTS-965N, TS-965N .....	1866-1
Chassis 12TS-969 .....	1868-1
Chassis AGTS-973N, GTS-973N, LTS-973N, TS-973N .....	1871-2
<b>RCA</b>	
Chassis CTC96A .....	1870-2
<b>SAMPO</b>	
Chassis CS-13A, C .....	1868-2
<b>SANYO</b>	
21T50 .....	1869-2
<b>SHARP</b>	
19B86 .....	1866-2
KMC-970, 9B12B .....	1868-3
<b>TOSHIBA</b>	
Chassis TAC720 .....	1869-3
<b>TRUETONE</b>	
GCJ3011A-08, GCJ3911B-97 .....	1867-2
SCJ3904C-97 .....	1870-3

**NEW!**

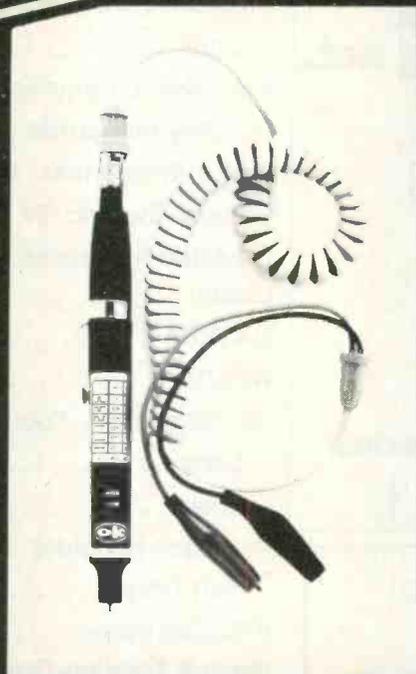

## PRB-1 DIGITAL LOGIC PROBE

Compatible with DTL, TTL, CMOS, MOS and Microprocessors using a 4 to 15V power supply. Thresholds automatically programmed. Automatic resetting memory. No adjustment required. Visual indication of logic levels, using LED's to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt pocket portable (protective tip cap and removable coil cord).

**\$36<sup>95</sup>\***

- DC to > 50 MHz
- 10 Nsec. pulse response
- 120 K  $\Omega$  Impedance
- Automatic pulse stretching to 50 Msec.
- Automatic resetting memory
- Open circuit detection
- Automatic threshold resetting
- Compatible with all logic families 4-15 VDC
- Range extended to 15-25 VDC with optional PA-1 adapter
- Supply O.V.P. to  $\pm 70$  VDC
- No switches/no calibration

\* ADD \$2.00 FOR SHIPPING  
(N. Y. CITY AND STATE RESIDENTS ADD TAX)

**OK MACHINE & TOOL CORPORATION**

3455 Conner St., Bronx, N.Y. 10475 (212) 994-6600 / Telex 125091

Circle (14) on Reply Card

# the marketplace

Advertising rates in the Classified Section are 35 cents per word, each Insertion, and must be accompanied by cash to insure publication.

Each initial or abbreviation counts a full word. Minimum classified charge \$3.00.

For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$3.00 per insertion to cover department number, processing of replies, and mailing costs.

Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or a distributor.

## Advertising Services

**PROJECTION TV:** Fact sheet prepared by an optical expert. Directions, sources for lens, screen, and kit hardware for quality installations. Send \$1 to Bernard Lee, Box 211, Little Silver, N.J. 07739 11-79-3t

**SOLVE COMPLEX VERBAL EQUATIONS** in minutes. \$2.00. Stamped envelope. Gardner, 110 Epworth, Chester, SC 29706 12-79-1t

## Business Opportunity

**MEN/WOMEN FOR FUN!** Shaklee Independent Wholesale Distributors earn \$200-\$5,000 monthly, Bonus, New Car, Etc. Details, Golden, RT2, Box 392ES, Fair Grove, MO 65648 Phone (1-417) 759-2738. 3-79-12t

**ESTABLISHED T.V. and Antenna Service** Business available in small city location on beautiful Lake Michigan. Easily expandable to county wide operation, residence included. Schools and shopping near by. Interested? Call Stevensville T.V. 616-429-7349. 10-79-3t

## For Sale

**REPLACEMENT COLOR YOKES—DEALER ONLY.** Zenith 95-2501-2532-2638-2667-S-89633 etc. \$19.94, Magnavox 361380-1 \$21.95, Sylvania, GE etc. \$17.95 to \$22.95. Request for price list on your letterhead. David Sims Enterprises, Inc., 665 Jericho Turnpike, Huntington Station, N.Y. 11746, (516) 549-3925. 5-79-tf

**AUTOMOBILE RADIO** and tape replacement parts: Delco, Chrysler, Philco-Ford, Motorola, Panasonic and many others. Large inventory. Laran Electronics, Inc., 3768 Boston Road, Bronx, NY 10469, (212) 881-9600, out of New York State, (800) 223-8314. 5-79-tf

**TV & RADIO TUBES**, 36 cents EA!! Free color catalog. Cornell, 4221 University, San Diego, California 92104. 8-76-tf

**ELECTRONIC SURPLUS: CLOSEOUTS, LIQUIDATIONS!** Parts, equipment stereo, industrial, educational. Amazing values! Fascinating items unavailable in stores or catalogs anywhere. Unusual FREE catalog. ETCO-011, Box 762, Plattsburgh, N.Y. 12901. 6-78-tf

**FOR SALE:** Television sales and service shop in Wilton N.D. For more information, write or call Vera Gorden, phone 701-734-6684, Box 57, Wilton, N.D. 58579 12-79-1t

**HELP WANTED:** TV Technician-experienced, paid vacations, fringe benefits, excellent opportunity with secure future, start March 1980, Delman TV, 651 E. Park Ave., Long Beach, N.Y. 11561, 516/432-7373 12-79-2t

**VHS VIDEO CASSETTES:** 4 hr, name brands, \$17.50, pay for 12, we ship 13, Dotty's Buying Service 651 E. Park Ave., Long Beach, N.Y. 11561 Shipping \$3.50. Pre-pay or Master Charge or Visa. 12-79-1t

**TV SHOP—GOING OUT OF BUSINESS.** B&K 177 VTVM \$55 (Price New-\$100). REM CRU-1 Cathode recovery unit and CRT tester \$95 (Price New-\$240). Sylvania CK1500X test jig and adapters \$145 (Price New-\$440). All excellent working condition, over 340 popular TV tubes \$225 (New list price \$2500) Free tube caddy with tubes, over 150 Sams photofacts (between 557 and 1452) \$35. New and used Quasar panels and free caddy \$175 (Dealer cost new over \$800). Misc. TV parts 25 cents per pound. All items F.O.B. Write for details, Dennis Staley, 220 Woodland Drive, Hartford City, IN. 47348. Call evenings (317) 348-4952. 12-79-1t

**COLOR PICTURE TUBE REBUILDING EQUIPMENT. SEMIAUTOMATIC ELECTRONICALLY CONTROLLED PROCESS. COMPLETE TRAINING.** Call or write Atoll Television, 6425 W. Irving Park, Chicago, IL 60634. Phone 312-545-6667. 12-79-2t

**FOR SALE:** All G.E. 5" Scope ST-2A \$50.00; Marker generator ST-5A \$100.00; Sweep generator ST-4A \$100.00 cables and manuals. Heatkit electronic switch 1D-101 \$35.00; Precision VTVM EV-10 scale 4"x6" \$50.00; Sencore 5" scope wide band PS-148 \$50.00; Sencore sweep and marker generator SM-152 \$75.00; Sencore ringer YF-33 \$35.00 (New). Varivolt Master 500W N-202 \$25; B&K VTVM Model 175 \$50.00, all with cables. Paul TV 7548 West Belmont Ave., Chicago, IL. 60634, 312/889-1245 12-79-1t

**300 NEW**, original box, Octal TV tubes, lot \$100.00 plus shipping. James Fred, Cutler, IN 46920. 12-79-1t

**SAMS PHOTO FACTS:** Numbers 1 through 800, sent postpaid, \$4.00 each, Hy's Television, 911 East 15th St. Brooklyn, N.Y. 11230 12-79-1t


**RADIO & TV. SERVICE FOR SALE:** Established 5 years, new equipment & parts, low overhead, inventory included, Jake Share, 16 N. Water, Greenwich, Conn. 06830 12-79-2t

**SATELLITE TELEVISION—Movies, sports, etc.** Build or buy your own earth station. Send \$3.00 for information. Satellite TV, RD 3, Box 140, Oxford, N.Y. 13830. 10-79-3t

## Wanted

**WANTED:** RCA and ZENITH color TV modules, Ed Herbert, 410 N. Third, Minersville, PA 17954. 12-79-1t

**Perform a death-defying act.**

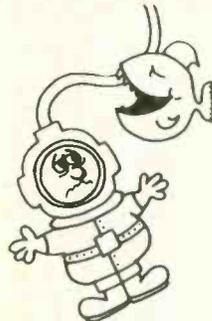

**Have your blood pressure checked.**

Give Heart Fund  
American Heart Association

**To get more information...**

on items advertised or described in this publication, use the Reader Service Card.

## Electronic Servicing

Advertising Sales Offices

**NEW YORK, NEW YORK**  
Joe Concert, 4 West 58th St.,  
New York, NY 10019;  
Phone: (212) 888-1977

**KANSAS CITY, MISSOURI**  
Helen Hull, P.O. Box 12901,  
Overland Park, KS 66212;  
Phone: (913) 888-4664

**LOS ANGELES, CALIFORNIA**

3055 Wilshire Blvd.,  
Los Angeles, CA 90010  
Phone: (213) 387-0639

**LONDON, ENGLAND**

John Ashcraft & Co., 12 Bear St.,  
Leicester Square, London, WC2H 7AS,  
England;  
Phone: 930-0525

**AMSTERDAM, HOLLAND**

John Ashcraft & Co., John J. Lucassen,  
Akerdijk 150A, 1171 PV-Badhoevedorp  
Holland;  
Phone: 2968-6226


**TOKYO, JAPAN**

International Media Representatives, Ltd.,  
2-29, Toranomon 1-chome, Minato-ku,  
Tokyo 105, Japan;  
Phone: 502-0656

## advertisers' index

Channel Master .....	IBC
The Cooper Group .....	6
Creative Electronics .....	1
Enterprise Development Corp .....	40
Fuji-Svea Enterprises .....	32
Holiday Industries .....	6
Gamit Enterprises, Inc. ....	1
General Electric/TV .....	7
Lakeside Industries .....	32
Liason .....	3
NATESA .....	41
NESDA .....	40
OK Machine & Tool Corp .....	43
Oelrich .....	41
Projector-Recorder Belt Corp .....	39
PTS Electronics .....	IFC, 1
Service Training Group .....	8
Sperry Tech .....	41
Zenith Radio Corp .....	BC
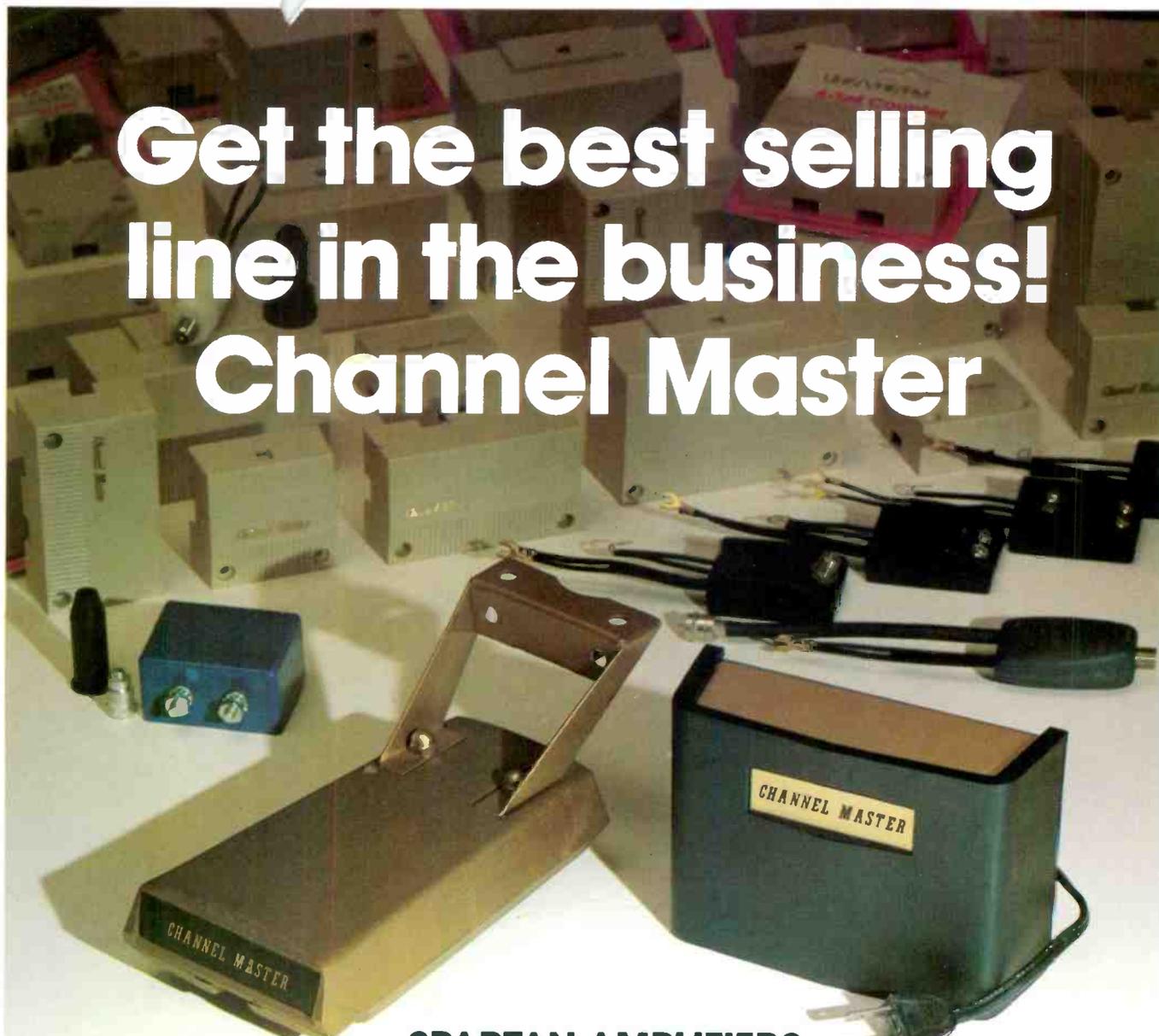
# Get the best selling line in the business! Channel Master



## **SPARTAN AMPLIFIERS and the broadest selection of home ANTENNA SYSTEMS EQUIPMENT in the industry!**

Channel Master's Spartan Amplifiers are a complete line of outdoor signal boosters, designed to meet the entire spectrum of TV and FM reception needs. They cover everything from 300 ohm Deep Fringe VHF/FM to 75 ohm High Input UHF, and they all display the same superior engineering and technology that has made Channel Master famous. Backed by Channel Master's Antenna Systems Equipment, Spartan amplifiers represent the ultimate in performance and dependability.

Different areas, different stations and different sets all add up to customers with different reception needs. That's why Channel Master has developed ASE, Antenna Systems Equipment, a versatile group of reception components that

will let you match your customer's needs exactly. The ASE system gives you all the pieces, both actives and passives, every piece quality-engineered and feature-oriented for superior performance and trouble-free installation.

Channel Master Spartan and ASE—get the competitive edge!

NEW! Couplers, Joiners, Separators and Rejection Filters with newly designed housings and packaging. Ask your Channel Master distributor for them today.

## ***Channel Master***

Division of Avnet, Inc., ES1279, Ellenville, New York 12428

# 150,000 REASONS WHY YOU SHOULD SWITCH NOW TO THE BIGGEST, BROADEST-EVER LINE OF ZENITH UNIVERSAL SEMICONDUCTORS covering Zenith exact replacements plus the most popular types in the industry—all in a new catalog!

**RCA TO ZENITH CROSS REFERENCE**

**SYLVANIA TO ZENITH CROSS REFERENCE**

**GE TO ZENITH CROSS REFERENCE**

**ECG®**


DEVICE	CRSP
ECG109	103-Z9001
ECG123A	121-Z9000-A
ECG125	903-334
ECG154	121-777-01
ECG156	212-Z9000
ECG159	121-Z9003
ECG196	121-987-03
ECG506	103-287
ECG712	221-48
ECG5081	103-Z9000

**SK**

DEVICE	CRSP
SK3004/102A	121-Z9004
SK3051/156	212-Z9000
SK3066/118	212-85
SK3083/197	121-985-03
SK3100/519	103-131
SK3115/165	121-1029
SK3119/113	103-101
SK3313/116	212-76-02
SK3444/123A	121-Z9000-A
SK3452/108	121-522

**GE**

DEVICE	CRSP
GE-20	121-Z9000-A
GE-53	121-Z9007
GE-86	121-925
GE-217	121-Z9036
GE-504A	212-76-02
GE-512	212-Z9000
GE-514	103-131
GECR-1	212-85
GEIC-13	221-45
GEIC-33	221-69

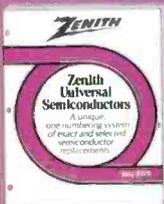

It's all under one numbering system that saves you time and adds value to any Zenith semiconductor you may already have in stock!

Switch now to Zenith Universal Semiconductor replacements and see how well your shop shapes up... your bottom line, too.

Check with your Zenith distributor for your copy of Zenith's Universal Semiconductor cross-reference guide... and ask how you can enjoy the convenience of our special Tube Caddy/Benchtop Organizer.

ECG is a registered trademark of GTE SYLVANIA

Shown here are just a few of the more than 150,000 cross-references in the July, 1979 edition of the Zenith Universal Semiconductor cross-reference guide.



The quality goes in before the name goes on®

Zenith Radio Corporation / Service, Parts & Accessories Division / 11000 Seymour Avenue / Franklin Park, Illinois 60131

Circle (3) on Reply Card