

SOLVES YOUR TV PROBLEMS

PRACTICAL TELEVISION

AND TELEVISION TIMES


A NEWNES PUBLICATION

Vol. 5 No. 51

AUGUST, 1954

1/-

EDITED
F. J. CAMM

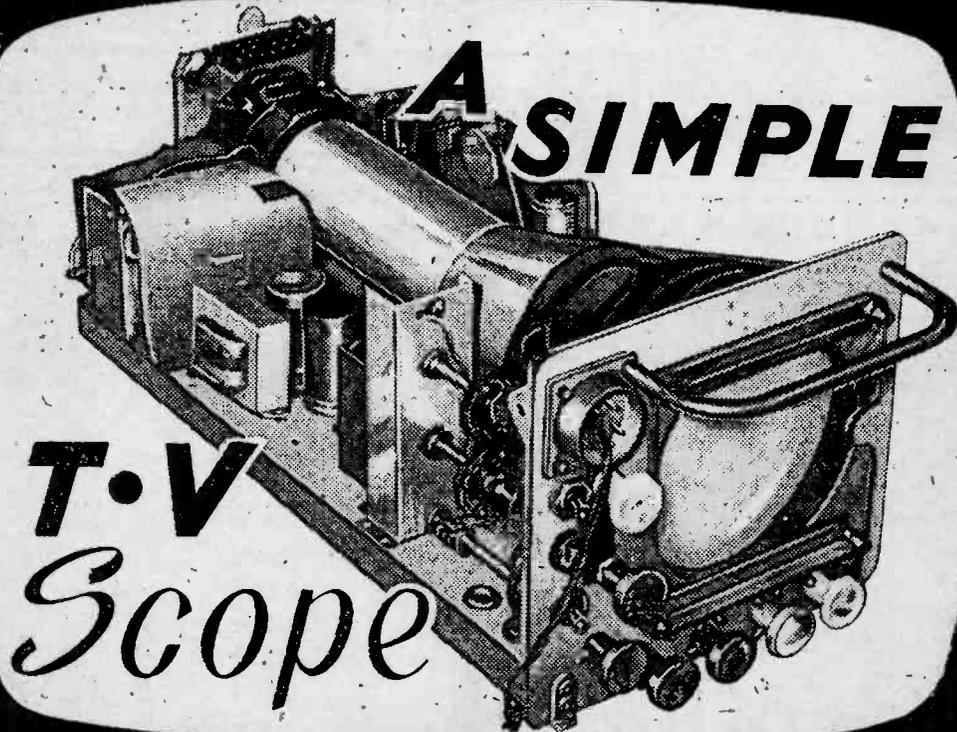

FEATURED IN THIS ISSUE

A New Magnetic Receiver
Line Linearity
TV in The Channel Islands

Aerials for the Simplex
Valves at U.H.F.
Fault Symptoms

Prices slashed at Clydesdale

INDICATOR UNIT "AS.B." SERIES (U.S.A.)

Contains 5BP1 C.R.T. with mu-metal screen 3 6H6's, 2/5SH7's, 6AC7, 6AC7, plus H.V. conds., etc. metal case, 18 1/2 in. x 8 1/2 in. x 8 in. All controls brought to front panel beside viewing screen.
ASK FOR **£3.19.6** each CARRIAGE PAID D/H573

INDICATOR UNIT TYPE 62
With VCR-97 tube and valves 16-VR85-CV118 (SP61), 2-VR74 (EB34), 2-VR92 (EA50), etc. Dim.: 18 in. x 18 1/2 in. x 11 in. Wgt. 42 lbs. In original wood case.
ASK FOR **79/6** each CARRIAGE PAID D/H523

INDICATOR UNIT TYPE 62
As above, but in Used, good-condition, loose stored.
ASK FOR **49/6** each CARRIAGE PAID D/E774

INDICATOR UNIT TYPE 305
BRAND NEW. REF. 10QB 6504 With Tubes VCR-324A, VCR525, and valves 7-VR91 (EF50), 2-VR34 (EB34), 6-VR92 (EA50). Dim.: 12 in. x 7 in. x 16 in. Wgt. 30 lbs.
ASK FOR **79/6** each CARRIAGE PAID D/H493

POWER UNIT TYPE 285
Ready made for T.V.
A.C. Mains. Input 230 v. 50 c.p.s. Outputs E.H.T. 2 Kv. 5 m/a., H.T. 250 v. 150 ma., L.T. 6.3 v. 10 a. and 6.3 v. 5 a. Fully smoothed and rectified with valves VU120, 5U4G, VR91 (EF50), plus cond., resistors, etc.
ASK FOR **£4.19.6** each CARRIAGE PAID D/H947

THE BEGINNER'S TIMEBASE
Mains Transformer 20/- each
E.H.T. Transformer 50/- & 45/- each
Smoothing Choke 15/6 each

REPRINTS FROM "PRACTICAL TELEVISION"

Components Price List Free on Request.
The "Beginner's Receiver," modifying the R3170A 1/6
The "Beginner's Timebase" 1/6
Economy Television, modifying the Ind. 62 1/6
Argus Television, data and blueprint D/H524 2/6

INDICATOR UNIT TYPE 6
With VCR-97 Tube and valves 4-VR91 (EF50), VR34 (EB34), 3-VR92 (EA50), VR76 (D1), etc. Dim.: 18 in. x 8 1/2 in. x 7 1/2 in. Wgt. 21 lbs. In original wood case.
ASK FOR **59/6** each CARRIAGE PAID D/H524

BEGINNER'S T.V.
Mains Transformer 32/6 each
Smoothing Choke 15/6 each
Output Transformer 9/9 each
Crystal Diodes 5/3 each

INDICATOR UNIT TYPE 6H
With VCR-97 Tube and valves 4-VR91 (EF50), 3-VR54 (EB34). Dim.: 18 in. x 8 1/2 in. x 7 1/2 in. Wgt. 22 lbs. In original wood case.
ASK FOR **89/6** each CARRIAGE PAID D/E777

ION TRAP MAGNET ASSEMBLY
Mfg. Surplus
Type IT/6 by Elac for 35 mm. tube neck. ASK FOR **2/6** each POST 3d D/H919 EXTRA

IF/AF AMPLIFIER UNIT R1355
With Valves 8-VR65 (SP61), 5U4G, VU120A (SU150A) I.F. 7 mc/s., etc. Dim.: 18 in. x 8 1/2 in. x 7 1/2 in. Wgt. 31 lbs. Used, good condition. In Transit Case.
ASK FOR **32/6** each CARRIAGE PAID D/E770A

R.F. UNIT TYPE 24
In original Carton.
With valves 3-VR65 (SP61), etc. Range 20-30 mc/s. switched tuning. Dim.: 9 in. x 7 1/2 in. x 4 1/2 in. Wgt. 7 lbs.
ASK FOR **15/-** each POST 1/6 EXTRA D/H850

R.F. UNIT TYPE 25
In Original Carton.
Range 40-50 mc/s., otherwise as R.F. 24.
ASK FOR **19/6** each POST 1/6 EXTRA D/H847

R.F. UNIT TYPE 27
With Broken Dial.
Range 65-85 mc/s. Valves 2-VR135 (EF54), VR137 (EC52), etc. Dim. and Wgt. as R.F. 24.
ASK FOR **29/6** each POST 1/6 EXTRA D/E771

RECEIVER UNIT R3601
Ref. 10DB 6937
With valves 2-VR136 (EF54), VR137 (EC52), 5-VR65 (SP61), 4-VR92 (EA50), VR91 (EF50), 6V6G, VU39A (R3), etc. I.F. 13 mc/s. Dim.: 18 in. x 9 in. x 6 in. Wgt. 38 lbs.
ASK FOR **39/6** each CARRIAGE PAID D/H493

CIRCUITS AVAILABLE AT 1/3
ASB3/5/7 or 8, type 62, R1355, R.F. 24, 25, 27 and R3601.

PLEASE NOTE—Carriage and Postal Charges refer to the U.K. only. Overseas freight, etc., Extra.

Order direct from:

CLYDESDALE SUPPLY CO. LTD.

2, BRIDGE ST., GLASGOW, C.S. Phone: SOUTH 2706/9

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES AND C.R.T.s.

AVO METERS IN STOCK					
Avo Model 7	—	—	—	—	£19 10 0
Avo Model 8	—	—	—	—	23 10 0
Electronic Test Unit	—	—	—	—	27 10 0
Electronic Test Meter	—	—	—	—	40 0 0
Valve Characteristics Meter	—	—	—	—	60 0 0
* Cossor Oscilloscopes Models 1052	—	—	—	—	104 0 0
1049	—	—	—	—	132 0 0

Full range Taylors Meters. List on request.
Leak—TL/10 Amplifier and "Point One" Pre-amplifier Complete 28 7 0
Specification on request.
Leak Tuning Unit 35 6 3
Chapman Tuning Units 17 6 8

LATEST VALVE MANUALS
MULLARD, OSRAM, & BRIMAR No. 5, 5/- each, MAZDA 2/- each.
ART AND SCIENCE IN SOUND REPRODUCTION.
By F. H. BRITTAI, D.F.H., 2/6 each.
Postage 6d. each extra.
Terms C.O.D. OR CASH with order and subject to price alterations and being unsold.

Arthur's

Est. 1919
PROPS: ARTHUR GRAY, LTD.
OUR ONLY ADDRESS: Gray House,
150-152 Charing Cross Road, London, W.C.2
TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."
CABLES—"TELEGRAY, LONDON."

U.S.A. SURPLUS

R. 9/APN4 Receiver Brand
New in Maker's Case

£5

Carriage Paid United Kingdom Mainland.

16 U.S.A. VALVES

- | | |
|---------|-----------|
| 1.—5U4G | 1.—6SL7 |
| 3.—6B4 | 1.—6H6 |
| 2.—2X2 | 4.—6SK7 |
| 1.—6SA7 | 1.—6SJ7 |
| 1.—6SN7 | 1.—105/30 |

VINER'S (Middlesbrough)
RADIO Government Surplus **ELECTRICAL**
26, EAST STREET, MIDDLESBROUGH
Telephone: MID 3418

Positively the 2 BEST T/Vs yet built for the Home Constructor!

The STERN'S "TELE-VIEWERS"

5 CHANNEL SUPERHET RECEIVERS


Suitable for any transmitting channel and for which commercial adaptors will be available.



PERFECT PICTURE QUALITY
SIMPLE DIAGRAMS MAKE CONSTRUCTION EASY



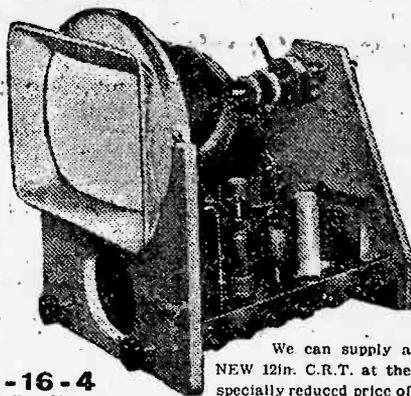PERFECT FRINGE AREA RECEPTION
BETTER RECEPTION AT HALF COMMERCIAL COST



The "WIDE-ANGLE" TELE-VIEWER


★ This is the most efficient large screen TV yet offered to constructors.

★ Excellent Time Base efficiency producing 15 to 16 Kv with ample scanning power for C.R.T.'s up to 17 inch.

CAN BE COMPLETELY BUILT FOR

£33 - 0 - 0

(Plus cost of C.R.T.)

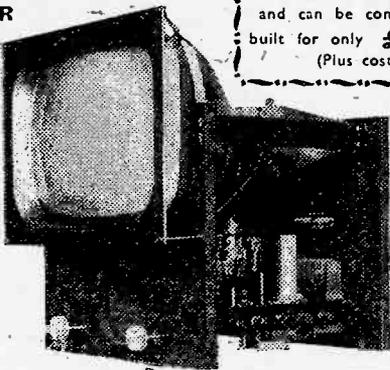

This is the 12" TELE-VIEWER and can be completely built for only **£28 - 16 - 4** (Plus cost of C.R.T.)

We can supply a NEW 12in. C.R.T. at the specially reduced price of **£12.19.6.** (Carr. & Ins., 15/- extra.)

The complete set of ASSEMBLY INSTRUCTIONS for these T/Vs are available for 5/- each. They include really detailed PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. AN ATTRACTIVE TABLE MODEL CABINET FOR THE 12in. Model IS AVAILABLE FOR £8.19.6.

STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4.

TEL.: CENTRAL 5812-3-4.

HENRY'S

(RADIO LTD.)

We have over 20,000 American and B.V.A. valves in stock.

ALL VALVES NEW AND GUARANTEED.

SETS OF VALVES

- Ten EF50 (Ex-Brand New Units), 5/- each 45/- Set
- 6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G (or KT11) ... 37/6 ..
- 1R5, 1S5, 1T4, 1S4 (or 3S4 or 3V4) ... 27/6 ..
- TP25, HL23/DD, VP23, PEN25, (or QP25) ... 25/- ..
- 6K8G, 6K7G, 6Q7G, 25A6G, 25Z3 or 25Z6G ... 37/6 ..
- 12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 25L6GT or 50L6GT 37/6 ..
- 12A7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35S6LGT or 50L6GT 37/6 ..

CRYSTAL MICROPHONE INSERTS

8/6

8/6

POST FREE

POST FREE



Ideal for tape recording and amplifiers. No matching transformer required.

T.C.C.: 1 5/7,000 v. wkg. Type CP53Q, Bakelite Case, 7/6 each.

Q24A	7/1-6AG7	12/8	12SR7	7/6	EL32	7/6	S130	7/6
1C3	6/8 6K8G	9/-	25Z6GT	8/6	EF50	7/6	7475 (VS70)	
1R5	7/6 6K8GT	9/-	25Z5	8/6	Red. Sr.	10/-		7/6
1S4	7/6 6L6G	10/-	35Z4GT	8/6	EF50	5/-	CV86	6/-
1S5	7/6 6U5	7/6	35Z5GT	8/6	SP2	8/6	VR150/30	8/6
1T4	7/6 6U5C	7/6	25A6	8/6	VP2	8/6	CK510AX	5/-
1C5	8/- 6V1GT	7/6	35L6	8/6	TTDD2A	8/6	DI	9/-
1LN5	8/- 6Q7GT	8/6	50L6GT	8/6	DK40	9/-	AC3/PEND	6/6
2X2	5/- 6S7GT	8/6	42	8/6	UL41	9/-		12/6
3A4	9/- 6R7	8/6	43	8/6	UY41	9/-	PEN23	6/6
3V4	7/6 6X5G	8/6	75	8/6	4D1	4/-	PEN46	7/6
3S4	7/6 6S47GT	8/6	80	8/6	8D2	4/-	QP25	6/6
5Z3G	8/6 6S7GT	8/6	866A	15/-	9D2	4/-	SP61	4/-
5U4G	8/6 6SG7	7/6	9001	6/-	R3	8/6	SP41	4/-
5Z4G	8/6 6SK7GT	7/6	9002	6/-	D41	5/-	HL23/DD	6/6
6A7G	8/6 6SL7GT	9/-	9003	6/-	D42	5/-	VP23	6/6
6AC7	6/6 6SN7GT	8/-	9004	6/-	DP3	5/-	VP41	7/6
6AG5	7/6 6SC7	10/-	9006	6/-	U2	5/-	U22	8/6
6A8C	8/6 6V6GT	7/6	951	6/-	U52	8/6	ATP4	4/-
CAM6	9/- 7C5	8/6	955	6/-	U19	10/-	TP22	8/6
6B8	7/6 7A7	8/6	953	37/6	Y83	8/6	HT23	10/-
6C4	8/6 7C7	8/6	T240	50/-	MU11	8/6	41MP	7/6
6C5GT	5/- 7B7	8/6	931A	2/-	PL81	11/-	25SP	6/-
6C3	6/6 7S7	10/-	EA59	12/-	PL82	10/-	25SSG	4/-
6D6	6/6 12A6	7/6	ECH35	12/-	PX23	12/6	MS/PEN	7/6
6F8C	8/6 12C4	7/6	EF54	6/-	PY81	10/-	MS/PEN	7/6
6CG6	6/6 12K7GT	8/6	EB31	3/6	PY82	8/6		
6H9GT	8/6 12K8GT	8/6	EB33	8/6	KT83C	10/-	VT501	7/6
6H9M	8/6 12Q7GT	8/6	EP36	6/6	KT83	12/6	AC/PEN(7)	10/-
6J5CT	6/- 12S4GT	8/6	EP39	6/6	GU50	12/6	PENDD4020	
6J6	9/- 12S7GT	8/6	EX51	12/-	XP2V	4/-		
6AK5	9/- 12SQ7GT	8/6	EX51	12/-	XH (1.5)	4/-		
6J7G	6/6 12SG7	7/6	EK32	6/6	VU111	10/-	FC13C	10/-
6J7M	8/6 12SH7	7/6	EK32	6/6	VU111	10/-	VU111	12/6
6K6	9/- 12S7	8/6	EP91	9/-	VU133	4/-	VP47	8/6
6K7G	6/6 12SK7	8/6	EL33	10/-	VU120A	4/-	ID5	8/6

MORSE PRACTICE BUZZERS

Morse tapper and 4 volt buzzer complete on baseboard, with battery and headphones. Brand New complete 15/- p.p. or less Headphones and Battery, 6/- post paid.

22-page Catalogue, 3/4.

Open Mon.-Sat. 9-6. Thurs., 1 p.m.

5, HARROW ROAD, PADDINGTON, LONDON, W.2

TEL: PADDINGTON 1008/9, 0401.

Brand New R.F. UNITS

- RF24 20-30 mc/s 15/- post free
- RF23 40-50 mc/s 18/6 post free
- RF23 50-65 mc/s 45/- post free.

"428" CONTROL UNIT

Containing 4-REDEF50, 2-SP61, 2-EA59, 1-EB34, 2-Single-gang .0005 Condensers, W/W, Vol/controls and Switches, etc. Size: 12in. x 9in. x 5in.. 35/- Carr., 3/-

"182A" INDICATOR

UNIT. - Complete with VCR517 and Screen, 3-EP50, 4-SP61 and 1-5U4G W/W V/controls. Ideal for TV or Scope. Brand New (less relay). Circuit Free. In original cases, 67/6 plus 7/6 carr.

CATHODE RAY TUBES

- VCR97, Guaranteed full TV picture (carr. 2/-) ... £2 0 0
- VCR517C, full TV picture ... £1 15 0
- VCR517, full TV picture ... £1 15 0
- M-u-M-e-t-a-l Screens for above ... 10 0
- 6in. Finerizer Lenses for above ... 17 6
- VCR139A (ACR10) For TV or scope, brand new and boxed £1 15 0

A GOOD SET deserves a Mullard long life picture tube

Technical Service Department will be pleased to send you Data Sheets describing any of the following Mullard Long Life Picture Tubes:—

12" MW31-74 14" MW36-24 17" MW43-64



MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVE., LONDON W.C.2

MVM 262

NOW . . . AVAILABLE TO THE CONSTRUCTOR ! THE CHANNEL T.I. TELEVISION WAVEFORM GENERATOR

The only professional fully-synchronised pattern Generator available to the amateur constructor.

This versatile instrument provides :

- ★ Adjustable composite test pattern, with line and frame sync pulses.
- ★ Blank video raster, fully synchronised.
- ★ Unmodulated R.F. video or sound carrier.
- ★ R.F. sound carrier, with variable tone modulation.
- ★ Direct video pattern modulation, fully synchronised.
- ★ Direct audio modulation, for post-detector sound checking.



SPECIFICATION :

Covers complete TV. Band 40-70 mc/s, directly calibrated. Additional scale indicates each sound and vision channel. Attractive two-colour finish. Robust construction. Three-level output attenuator. Guaranteed 12 months. Fully portable. Weight 10 lbs. Dimensions 12 x 9 x 5 in. Employs 6 valves. For A.C. operation 200-250 v. Complete with operating instructions and guarantee.

PRICE **£20** CARRIAGE PAID.

ORDER TO-DAY, DIRECT FROM :

CASH WITH ORDER. IMMEDIATE DELIVERY.

CHANNEL ELECTRONIC INDUSTRIES, BURNHAM - ON - SEA, SOMERSET.

THE T.I. GENERATOR CHECKS

- Line and frame linearity.
- Picture height, width and aspect ratio.
- Weak, excessive, or faulty sync pulses.
- Brilliance, contrast and focusing.
- Picture shape distortion.
- Video, audio and pulse response.
- Bandwidth and circuit alignment.
- Receiver smoothing faults.

PRACTICAL TELEVISION

& "TELEVISION TIMES"

Editor: F. J. CAMM

Editorial and Advertisement Offices: "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363.
Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 5 No. 51

EVERY MONTH

AUGUST, 1954

Televiews

EUROVISION—A CRITICISM

THE linkage of several countries by what has come to be known as Eurovision is one of the greatest technical achievements since the inception of television. The technical problems which had to be anticipated and overcome, apart from the known difficulties, were enormous. Every viewer has now had an opportunity of examining the results of many months of diligent work on the part of the BBC engineers and their foreign collaborators. It marks a new era in television, and it may pave the way eventually for world-wide standardisation of television transmission systems. The problem was made unnecessarily complicated by the fact that most of the continental systems which took part in the experiment transmit vision on 625 lines, whereas our system is 405 lines. The problem was solved by photographing the pictures to be transmitted from the end of a receiving tube. Whilst that is a solution it is not the best solution. It is indeed tele-cine. Great praise is due to the British television engineers for their part, and we have no criticisms to make of their work.

From the point of view of the material selected for this broadcast, we have some critical comments to make. We do not think it should have been made the occasion for a broadcast by the Pope, thus giving undue prominence and publicity to a particular religion. It must not be construed from this that we are expressing any disfavour of Roman Catholicism.

Our criticism would have been made irrespective of the denominational chief selected for such a broadcast. The public does not like religion mixed with what was intended to be entertainment, a fact of which the BBC is well aware from the criticisms of those mournful Sunday programmes for which Reith was responsible. It was a snub to the dozens of other religions also having world-wide adherents. Religion and politics do not mix with science. We hope those responsible will heed these remarks. The programmes, whilst we cannot expect them to please everybody, should endeavour to please the greatest number. A large number were offended by this particular part of the broadcast,

a point which they could have anticipated and avoided.


TV IN THE CHANNEL ISLANDS

ALTHOUGH the BBC decided five years ago that Jersey, Guernsey, Alderney and Sark were beyond the range of even fringe area TV reception it has recently been demonstrated that it is possible. A relay company who serve about 3,000,000 listeners and viewers throughout the world by wired network direct into their homes has solved the problem, one of great magnitude, for the very-high-frequencies used by television are a straight line emission and do not follow the curvature of the earth's surface and normally cannot be received except under freak conditions by any set or station which is out of "sight" of the transmitter. The islands, therefore, by virtue of their distance from English transmitting stations and the curvature of the earth were well beyond the fringe area. Seventy miles is considered the average distance over which television can be received. The company concerned made use of tropospheric propagation, a condition which reflects the V.H.F. waves, and these were "caught" when they came to earth at a spot considerably beyond seventy miles. It is upon this fact that the new Channel Islands stations have been able to operate. The BBC admits the success of this effort on the part of private enterprise and they have built a pilot unit in Guernsey to pick up transmissions from Wenvoe and later from the transmitter which is to be erected at North Hessary Tor in Devon. The company will monitor these transmissions from Jersey for the BBC. Fuller details of the installation will be found on page 117. Other developments will follow.

CAREERS IN RADIO

THE Radio Industry Council has recently issued an illustrated booklet entitled: "Careers in Radio and Electronics," copies are being circulated by the Ministry of Labour to public schools and grammar and technical schools. It is available from the Secretary of the R.I.C., at 59, Russell Square, London, W.C.1.
—F. J. C.

A NEW MAGNETIC RECEIVER

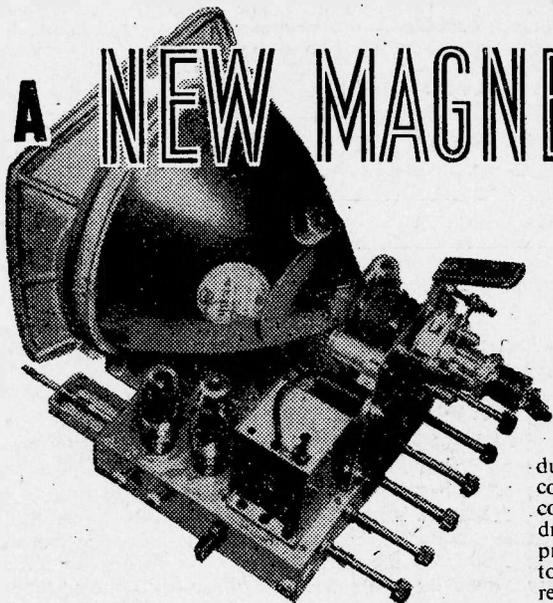

CONSTRUCTIONAL DETAILS OF AN
ECONOMICAL RECEIVER UTILISING
SURPLUS COMMERCIAL RECEIVER
COMPONENTS

By J. Cook

(Concluded from page 58, July issue)

THE difficulty of using a Tetrode tube has been surmounted by rectifying direct from the 300 volt tap of the auto-transformer with a small pencil rectifier and supplying the resulting 350 volts through a smoothing circuit to the first anode. The smoothing resistor (R32) may seem unduly high, but it should be remembered that the current consumed by the first anode is so extremely low as to be insignificant. The condensers C33 and C34 are good quality condensers placed across the mains input to the earth terminal (insulated from chassis) to filter out mains-borne interference. The earth connection is not essential, but it improves the general screening of the equipment. Direct connection of the earth terminal is, of course, precluded by the mains connection to the chassis, but R.F. coupling is effected by C35 which, like the filter condensers above, should possess reliable insulation. Two fuses in the mains supply input and one in the rectifier circuit protect the equipment—the latter fuse is especially valuable in protecting the rectifier and transformer if there is any trouble with the electrolytic condensers. This is always a distinct possibility when condensers have been in stock for some time and require "reforming." In this connection it is probably good practice to break in a new electrolytic on a low voltage source, such as a small H.T. battery, before putting the normal working voltage across it.

Decoupling of the sound and vision strips is effected by R9 and C4, which keeps the voltages down below the maximum ratings of the valves concerned. The sound output stage is the exception and has a separate decoupling arrangement R50 and C36 to avoid, as far as possible, voltage fluctuations of the H.T. supply caused by any overload in the sound output valve. Focus is effected by a permanent magnet rather than by the focus coil (which is supplied with the line transformer set) because of the unavoidable loss of H.T. volts which would occur by using the coil, and also there is some difficulty in obtaining comparable focus stability

due to the T and R heat changes which occur in the coil. Nevertheless, if it is decided to use the focus coil, compensation can be applied to counter focus drift. Since the coil is not specially designed, probably the simplest method of doing this would be to use a series thermistor resistance with an ordinary resistance in parallel with the thermistor. The value of this resistance is carefully chosen to compensate exactly for the increase in resistance of the coil over the temperature required.

Construction


Although it is not the intention of this article to give precise stage-by-stage details for construction, it may, nevertheless, be helpful to make some general remarks on recommended layout and construction. Once beyond the R.F. and video side of the receiver, the length of wiring and layout become much less critical and the requirements are similar to those applying in audio amplifier design. But it is wise not to take undue liberties, and the line oscillator and output components should be kept to one side of the chassis with the frame components on the opposite side. The line transformer, being in a heavy screening box, is mounted near the edge to relieve stress on the chassis. The sync separator could be in the middle of the chassis together with video output and vision limiter valve and components, the latter being mounted beneath the chassis. Three eight-way tag boards are located near each valve socket and carry the principal components as illustrated at Fig. 3. As there is only one valve on the line timebase side, the sound output stage with associated volume/on/off control is arranged on this side. Cables connect this chassis to the power pack and, in particular, care should be taken to ensure that the 6.3 volt heater supply cables are of sufficiently heavy gauge to carry the 4½ amps. without any significant drop.

The 10in. by 14in. aluminium chassis, which is the largest recommended in this material in the interests of rigidity, has a quarter hoop cradle affixed to a 3in. outrigger extension. The front of the 12in. picture tube rests in this cradle and a thin brass band from ¼in. to 1in. wide clamps the tube down by the rubber mask which cushions the tube against shock. If a 9in. tube is used, the outrigger extension is unnecessary and the cradle is mounted on the edges of the chassis. In both cases the rear mounting

bracket is an aluminium plate parallel with the edge of the chassis. The tube neck, which passes through it, rests on one of the special 35 mm. grommets made for the purpose; this grommet should bear up against the rear of the deflector coils and is thus interposed between coils and magnet. This gap should be about 1in. for optimum results with the tube used; a smaller distance may produce interaction between the two components whilst a greater distance will produce a slightly more even focus, but with a larger spot. It is profitable to experiment, because the position for best results is critical. The deflector coils are slipped on the tube with the lettering facing the tube, i.e., with the lettering

centring controls. The characteristics of the multivibrator frame timebase may cause alarm and dependency to those unfamiliar with it. Without the presence of a sync. pulse, due to no signal being received or extreme lack of gain (contrast), the raster, if such it can be called, comprises a series of haphazardly spaced lines building up to a closely spaced section in the middle of the picture which shows up as a bright band. This all sorts itself out as soon as the sync. pulses are present, except for the adjustment of linearity, which may stretch the top of the picture out considerably. In the first instance Lin. 1 should be adjusted. It will be found that this mainly influences the central portion of the

picture and is adjusted for the even spacing of the lines. Lastly Lin. 2 is adjusted and this will correct any deformity at the top of the picture. There is only one linearity control in the line circuit and it will be found that adjustment of this will have some influence on the synchronisation of the line oscillator, and the picture which will probably no longer hold towards the extremes of adjustment and the setting up is thereby a little more complicated. The coarse line hold may seem a little sensitive to adjust, but in actual fact it is normally capable of holding its adjustment indefinitely once set to the mid-position. The frame hold is very definite and should hold throughout most of its range, but some occasional readjustment will pay dividends in improved interlace. A final adjustment of the contrast, brilliance and vision limiter (adjusted so

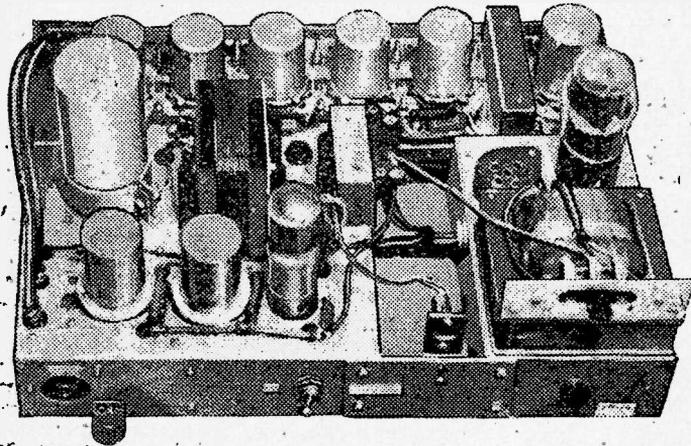

Vision/sound strips and power pack. Front left: Sound receiver with main H.T. smoothing components. Front right: Power pack. Rear: Pye vision strip.

upside down when viewed from the rear. F2 and E are joined and should be at about two o'clock. In soldering particular care is advised with the line transformer, and any connections which will have high voltages present should have nicely rounded blobs of solder without any roughness in order to avoid corona troubles. Condenser and resistor types are not specified, so something should be said about them. Whilst war surplus resistors are generally quite usable, if in good condition, it can only be said that war surplus condensers of the paper variety are most ill-advised things to use, especially in the all-important timebase circuits. In the writer's experience more often than not these condensers qualify better as resistors! Paper condensers of the ex-manufacturer category generally seem to be all right, and oil filled, mica and ceramic of all types can usually be relied upon. In any case, trouble taken in testing all parts before assembly will be well repaid. With the complexity of a TV circuit it is no easy matter to trace faulty components in a newly built set which may well have wiring faults in addition.

Operation

The contrast and brilliance controls should be advanced until some sort of modulation pattern is seen on the screen when it should be easily locked with the appropriate hold controls and, after focusing the lines, the height and width controls can be adjusted to fill the screen in conjunction with picture

that it limits just before peak white level), to obtain the best gradation of whites through greys to blacks, as observed on the test card, should complete the adjustment.

If an ion-trap tube such as the MW31/16 is used, the appropriate magnet must, of course, be fitted. Instructions on the adjustment of ion-traps have already appeared in this magazine, so they are not repeated here.

Modifications

Since the publication of the first part of this article Messrs. Lasky have disposed of the specified frame transformer. They have, however, stocks of an alternative type which we have tested and find suitable with slight modification to three of the components which form part of the linearity arrangements. These new values are: R40 100k Ω , C27 .1 μ F and C26 .01 μ F. These two condensers should be of the 250 v.w. type. A further change is required in R40 in the case of the original transformer. In the list of parts in the June issue this was given as 470k Ω but this has been found rather high and a reduction to 270k Ω is recommended.

NEWNES SHORT-WAVE MANUAL

6/- or 6/5 by post from

GEORGE NEWNES, LTD.

Tower

House, Southampton Street, London, W.C.2.

Making an Aerial for the **SIMPLEX** RECEIVER

SOME DETAILS FOR THE HOME CONSTRUCTION OF INEXPENSIVE AERIALS

SINCE the publication of the blue print of our £16 television receiver we have had many requests for details of the construction of an inexpensive aerial to accompany it.

Before dealing with the constructional work it would be useful for the newcomer to be given some idea of the type of aerial required. It is not possible for us to specify exactly what type of aerial is suitable for any particular locality; local conditions affect the signal and it is quite possible to get poor results at points well within the service area of the transmitter. Our advice then, must be of a general nature; the best guide is to be governed by the type in general use in the locality.

In order to simplify construction we have compiled details for three types of aerial—a dipole, double-vee and a yagi.

The dipole is for use within the service area up to a radius of about 20 miles in the case of the high-powered transmitters; this distance will vary according to the actual local conditions in the immediate vicinity, but if the aerial should prove too weak then it can be easily converted into a double-vee type.

The double-vee aerial is for use in localities up to about 45 miles from the transmitter. Normally, it should be mounted at as great a height as is practical, though under favourable conditions it can be fitted in the loft. It is about equivalent to an "H" aerial, but is more convenient, mechanically.

The yagi is composed of two directors with dipole and reflector and can be used up to 80 miles from the transmitter. It must be understood that reception cannot be guaranteed at any distance; a lot depends upon local conditions. It should be remembered that a straight receiver has not the "pulling" power of a superhet and a further pre-amplifier may be necessary.


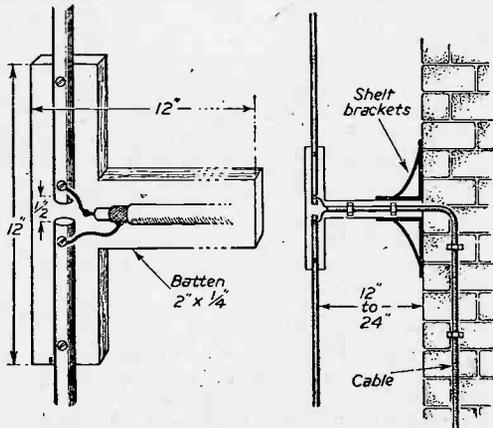


Fig. 1 (left).—Suggested mounting for the dipole. Fig. 2 (right).—A method of wall-fixing.

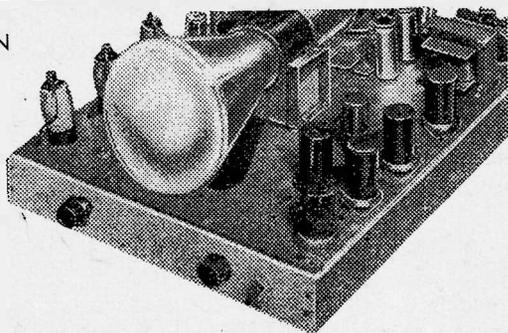

The Dipole

The key point of a television dipole is the insulator; the commercial type used by manufacturers is rather difficult to construct without the aid of a lathe. The insulator is rather important because it not only performs the mechanical function of holding the aerial to the mast or cross-boom, and the electrical function of shielding the connections from the weather, but it also has a material effect on the characteristics of the dipole itself.

The centre impedance of a dipole cut to half a wavelength and in free space is about 70 to 80 ohms. However the aerial must be supported and the introduction of the support alters the characteristics of the aerial. It is possible to counteract the alteration by "tuning" the dipole which, in practice, amounts to shortening it by five per cent. When this is done the aerial will be tuned to the desired frequency and the centre impedance will be back to between 70 and 80 ohms when the insulator is fitted.

It will be seen, therefore, that the insulator must be kept as small as possible and although the method of mounting the dipole given in this article means that the "insulator" is longer than that used commercially, there will be no deleterious effect if the measurements given in the table are adhered to.

The main purpose of the insulator is to provide a fixture for the rods and to preserve the terminations from the weather. When copper wire (such as is used in coaxial cable) is connected to the rods the action of the damp atmosphere on the dissimilar metals is to cause corrosion; this would result in creating a high resistance joint between the two and, in the secondary stage, cause the copper wire to corrode and eventually to fracture.

Where the aerial is mounted in a dry position, such as a loft, then the simple termination shown in Fig. 1 can be used. It consists of a "T" shaped piece of batten 2in. by 1/4in. to which the rods are bolted, each rod having two bolts. The bolts can go right through the rods and the wood. The coaxial cable is brought along the main member of the "T" and is cleated to it, and the inner conductor is connected to the upper rod under the supporting bolt, while the outer braiding of the coaxial cable is connected to the bottom rod.

The lengths of the rod are given in Table I for the different channels. Where horizontal polarisation is

used the rod must be mounted horizontally and turned so as to receive the best signal. With vertical polarisation the rod must be kept in the vertical direction.

Note that if the rod is mounted in the attic or loft it may be beneficial to erect it at an angle to the plane of reception, and it is often worthwhile tilting it in order to pick up the best signal. A further point to note is that pick-up conditions are liable to vary within the roof-space and if satisfactory results are not obtained then a search should be made for a better position—an alteration of only a few feet often makes an appreciable difference in the strength of the received signal.

The aerial should be kept clear of electrical wiring circuits in order to keep mains-borne interference at a minimum.

A simple dipole as described can be used out of doors. All that is necessary is to plug the ends of the rods with wooden plugs and to fit some sort of cover over the central connections. A small wooden box can be built where the cross member of the "T" joins the main member, or an electric junction box of the round plastic type can be employed.

In order to prevent corrosion due to moisture, Chattertons compound can be applied to cover the terminals and the end of the coaxial cable.

Works, Marlborough, Wilts, who both are advertisers in PRACTICAL TELEVISION.

Fringevision, Ltd., will supply insulators and chimney lashings if required.

It is an easy matter to mount the dipole on a wall

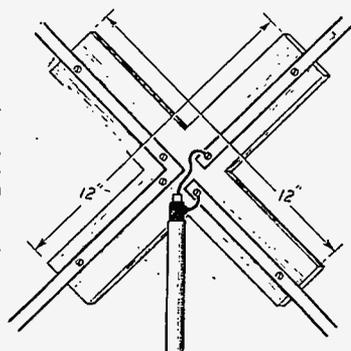


Fig. 5.—Mounting of the double-vee aerial shown in Fig. 3.

or chimney. Simply extend the main member of the "T" piece so that it is between 18-24 in. long and then, by the use of shelf brackets, it can be fitted directly at right-angles to the brickwork (Fig. 2). The coaxial cable is run along the main member of the "T" and down the wall.

The aerial should be erected as high as is feasible and care should be taken to keep it clear of metal guttering and down pipes.

The Double-vee Aerial

This aerial has quite a good pick-up having a gain of more than 3 db over a normal dipole. It is light yet mechanically strong and requires no special matching devices.

The "circuit" of the aerial is given in Fig. 3 and element lengths in Table II. It consists of a dipole which is bent into the form of a "V" lying on its side and a director also formed like a "V". The director is not connected to the dipole in any way. It is pointed at the station being received while the dipole points away from the station. This is the reverse of the conditions of an "H" aerial which should have the dipole pointed towards the transmitter.

It is possible to mount the aerial in the roof but it is preferable to mount it outside, well clear of walls, etc. If it is mounted in the attic some trouble from mismatch may be experienced; it can usually be tuned out by the following method: connect a length of stiff wire (or an additional rod) to a sliding connection on the lower member of the director. A metal clothes-peg can be used for the slide. The wire should equal the length of this section; it should hang vertically and be slid along the director rod until the best picture is obtained on the screen. It can be finally bolted in that position.

This method of tuning out mismatch due to nearby objects is much simpler than the cut-and-try method with quarter-wave stubs.

Mounting

A method similar to that employed with the dipole can be used for mounting the rods. Two pieces of batten 12in. long are formed into an "X"; they should be jointed in the centre so that the back and front faces are flush. The rods are bolted on to the "X," two bolts being used for each rod, and the

TABLE I				
Dipole Lengths				
Channel	Length
1	10ft. 10in.
2	9ft. 4in.
3	8ft. 6in.
4	7ft. 9in.
5	7ft. 3in.

The diameter of the rods used is governed partly by the insulator. By using the method described in the foregoing paragraphs the diameter should be 3/8in. Rod which is smaller than this is inclined to whip and thereby cause picture flutter.

It is not strictly necessary to use 3/8in. diameter rod; in the attic 1/2in. diameter can be employed, while for an outside aerial up to 1in. is practicable.

Duralumin or similar tubing is the best kind as it is light in weight yet mechanically strong and has good electrical characteristics. If difficulty is experienced in obtaining it locally, then it can be got from H. Rollet and Co., 6, Chesham Place, London, S.W.1, or from Fringevision, Ltd., Angel Yard

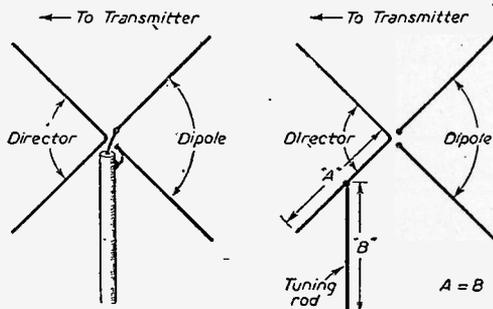


Fig. 3 (left).—Double-vee circuit. Fig. 4 (right).—A reactance tuner for double-vee aerial.

dipole rods should be separated at the centre by $\frac{1}{2}$ in. The director rods should be continuous, though bent at an angle of 90 deg., but if separate rods are used then they should be electrically bonded together.

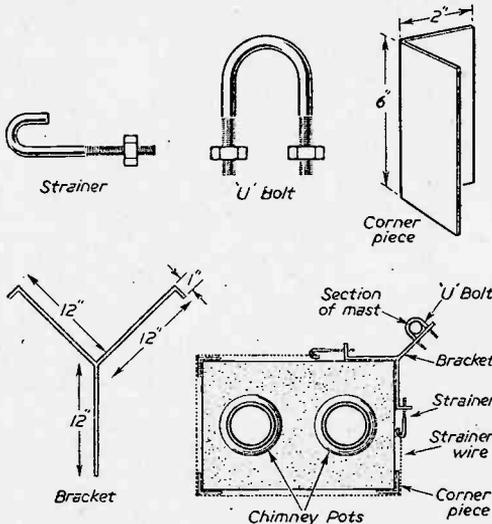


Fig. 6.—Details of chimney-lashing.

The arrangement can be mounted in the attic as it is and the bottom rods stood on the floor. The aerial should be aligned approximately on the transmitter; there is very little difference in signal strength received over an arch of plus or minus 20 deg.

Where the transmitter is horizontally polarised then the aerial will, of course, have to be mounted horizontally.

External Fixture

If the aerial is to be fitted externally then the ends of the dipole with their connections to the cable must be boxed in and a method similar to that explained for the normal dipole can be used.

For mast fitting the wooden "X" portion can be bolted to a metal or wooden mast. In the case of a metal mast the coaxial cable should be bound to the mast with adhesive tape. A generous supply of tape should be used at intervals down the mast.

It is not recommended that the cable be brought down inside the hollow metal mast. If the mast is of any length the cable will vibrate against the inside and cause a noise which can be a real nuisance at night.

Fixing to the Chimney

The home construction of chimney mountings is dependent on the facilities and material available and many constructors will prefer to buy these. For those who wish to construct their own the details in the following paragraphs are given.

Two sections of wrought iron or mild steel 1 in. wide and $\frac{1}{4}$ in. thick are required to be shaped into a "Y." The angle between the upper arms of the "Y" should be 90 deg. An inch of the end of each short arm should be turned over to form an angle of 90 deg. and should be drilled to take a strainer bolt. It is preferable to use the "U" ended strainers with a diameter of about $\frac{3}{8}$ in.

Six corner pieces will be required to prevent the straining wire from cutting into the chimney and they can be made from sheet iron of about 14 gauge.

Two "U" bolts are required made of about $\frac{3}{8}$ in. diameter mild steel whose overall diameter is the same as the external diameter of the mast.

Two holes should be drilled in the long arm of the "Y" to take the "U" bolt.

TABLE II
Double-v ee

Channel	Director	Dipole
1	5ft. 4in.	5ft. 10in.
2	4ft. 9in.	5ft. 3in.
3	4ft. 4in.	4ft. 9in.
4	4ft. 0in.	4ft. 4in.
5	3ft. 8in.	3ft. 11in.

Note that the above are the lengths of the individual elements. For example, Channel 1 has a director consisting of two arms, each of which is 5ft. 4in. in length and a dipole, each arm of which is 5ft. 10in.

Straining wire of about 7/14 strands will be required.

Fig. 6 shows the various items and gives a plan view of the fixing.

For a short mast up to 6ft. the mast can be made of duralumin tubing 1 in. in diameter. For a mast up to 16ft. in length the tubing should be 2 in. It is possible to use iron or steel tubing but is not recommended because of the increased weight.

Suitable tubing can be obtained from the advertisers mentioned previously.

When mounting the aerial externally it is not necessary to get it strictly in line with the transmitter. There will be no noticeable fall off in gain over an arc of plus or minus 20 deg. It is better to

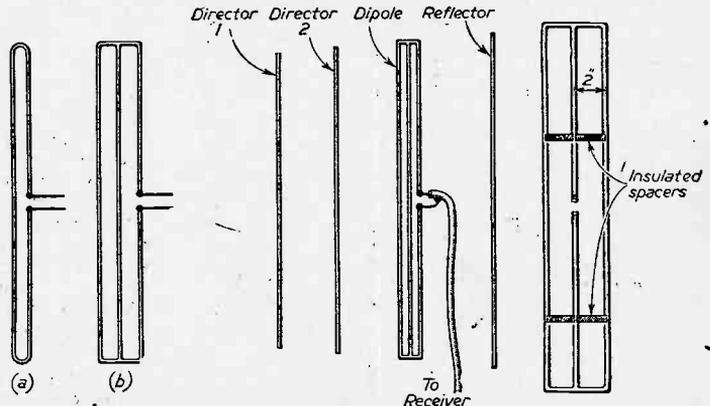


Fig. 7 (left).—Folded dipole aeriels. Fig. 8 (centre).—Folded dipole with directors. Fig. 9 (right).—A triple-folded dipole.

try the aerial for a week or so before deciding its final orientation so that it can be rotated away from any source of interference.

Yagi Array

The yagi array described here has two directors, a dipole and a reflector. It does not give the highest gain possible with such a combination but makes a

One of the difficulties associated with high gain arrays is in matching the aerial to standard 80Ω cable. The addition of the other elements causes the centre impedance of the dipole to fall to about 8Ω with the close spacing recommended and some form of matching device is essential. There are various forms of matching methods such as the Delta, "T" match, transformer and the use of folded dipoles; we have chosen the latter as being the simplest and offering no difficulties in cut-and-try methods.

The centre impedance of a dipole increases by folding the dipole. Fig. 7a shows a double-folded dipole. The centre impedance is the square of the number of elements used, so that the dipole in Fig. 7a has an impedance of four times the dipole without the fold. In Fig. 7b we have a triple-folded dipole and the centre impedance is therefore $3^2=9$ times.

We have seen that the centre impedance of our yagi array is in the region of 8Ω , therefore if the dipole is triple folded the impedance will become $8 \times 9 = 72\Omega$, which is a good match to 80Ω cable.

A further advantage gained is that folding the dipole widens the bandwidth. When directors are used to increase the gain not only is there an increase in the signal picked up by the aerial, but the array becomes more directive (the signal rapidly falls off as the angle between the direction in which the aerial is facing and the direction of the transmitter is increased), but the bandwidth of the aerial is reduced.

Fig. 8 shows the "circuit" of the yagi and Table III gives lengths of elements. It will be noted that neither the directors nor the reflectors are connected to the aerial electrically. They are "parasitic" elements, and it is unnecessary to make direct connection.

The folds in the dipole should have a centre-to-centre measurement of 2in. Direct metallic connection is made at each end and bonding bars can be used for this purpose. It is as well to insert strengthening insulators halfway between the end and centre of the dipole (top and bottom half) to strengthen it and to maintain correct spacing. Paxolin blocks or Tufnol rod suitably shaped can be used, or even well-painted hardwood.

The dipole can be mounted at right angles to, or in line with, the other elements but care must be taken to ensure that the metal boom (if used) does not short-circuit the dipole elements.

TABLE III
Yagi

Channel	Director 1	Director 2	Dipole	Reflector
1	10ft. 0in.	10ft. 5in.	10ft. 10in.	11ft. 2in.
2	8ft. 8in.	9ft. 0in.	9ft. 4in.	9ft. 8in.
3	7ft. 11in.	8ft. 2in.	8ft. 6in.	8ft. 10in.
4	7ft. 2½in.	7ft. 5½in.	7ft. 9in.	8ft. 0in.
5	6ft. 9in.	6ft. 11½in.	7ft. 3in.	7ft. 5½in.

The spacing between directors and reflectors for each channel is given below.

Channel	Directors	Reflector
1	2ft. 2½in.	3ft. 0in.
2	1ft. 11in.	2ft. 10in.
3	1ft. 9in.	2ft. 8in.
4	1ft. 7in.	2ft. 5in.
5	1ft. 5in.	2ft. 1½in.

near approach to the problem. The highest gain obtainable with two directors and a reflector is when all elements are spaced at 0.2 wavelength. In this array we are using a spacing of 0.1 wavelength for the directors and 0.15 wavelength for the reflector, which gives a gain of about 1db less than that with 0.2 spacing, but the array is much lighter and more compact.

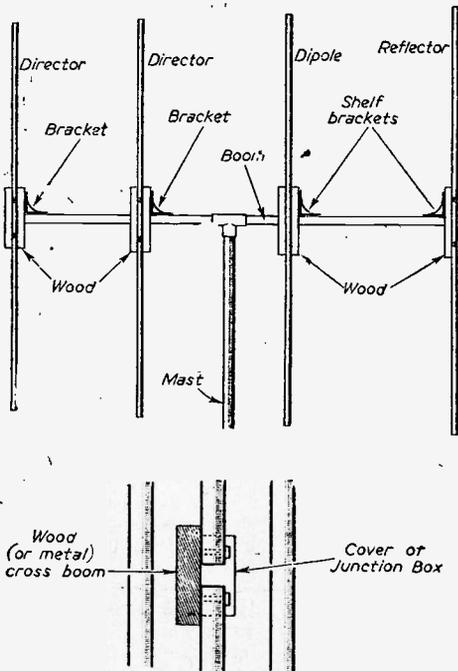


Fig. 10.—"Yagi" array and details of gap in dipole.

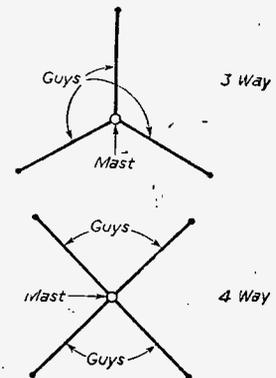


Fig. 11.—Method of guy in a heavy mast type aerial.

The method shown for the ordinary dipole can be used to fix and house the centre dipole rod, but account must be taken of the extra weight of the dipole.

The cross-boom should be of hardwood or aluminium alloy, and for strength coupled with lightness a material of 1in. diameter would be suitable.

Specially made reflector and director rod holders can be employed or the rods can be bolted to strips of 2in. batten, which is, in turn, bolted to the cross-boom and kept in position by shelf brackets.

Fig. 10 shows the scheme.

The mast, if fitted on the chimney, should not exceed 18ft. in length, and in windy localities guy wires should be used. The guys can be either three or four in number set at 60 deg. or 45 deg. angles respectively (Fig. 11).

It is important that the guy wires have no direct relationship in length to the aerial rods, and insulators must be inserted to break up the wires into elements which are neither one quarter nor one half of a wavelength. If one third wavelength sections are used then there should be no trouble.

Avoiding Humming

Yagi arrays (and even the simpler types of aerial) are inclined to vibrate when the wind is in a certain direction. The humming is communicated through the mast to the chimney and can thus be mechanically amplified and sound throughout the house.

To mitigate this nuisance the rods should be filled with dry sand or fine granulated cork and the ends thoroughly corked and sealed. If the mast is first wrapped with a layer of sheet lead or thick rubber, which, in turn, is surrounded by a hardwood block before being bolted to the mast, no trouble from this source should be experienced.

Extreme Ranges

Where signal conditions are difficult the yagi array should be used, and it should be erected as high as possible. If the distance from the dipole to the receiver is likely to exceed 60ft., then the use of low-loss fringe-type coaxial cable should be considered.

Under such conditions the use of a mast-head type of pre-amplifier is often worthwhile.

BBC TELEVISION CENTRE (WHITE CITY)

THE first concept of the proposal involved the planning of just over half the 13-acre site for the needs of the television service, the remainder of the site being left unplanned in any detail until the BBC was in a position to judge how it should be developed to meet the demands of the service in the light of later experience.

The architectural conception of the half-site scheme had, however, to take into account the development of the site as a whole. The curvilinear "tail-piece" seen in the plans illustrating the scheme provided that measure of flexibility necessary for the planning of the second half of the site when requirements had been decided.

It is now envisaged that the "tail-piece" shall provide, in addition to further studios, a large garage, a block of rehearsal-rooms, and possibly a roof "heliport."

Scenery Block

This building, which covers approximately one acre, is the first part of the project to be completed. It has been designed to take its place as a unit in the general architectural conception. Extensive workshops are provided for carpenters, property-makers, scenic-artists and others engaged in the making of scenery for studio productions. There is also a high (26ft.) setting-space where scenery is assembled together with large areas in which scenery and properties, suitable for re-use, can be stored.

The scenery block building contains in addition 200 offices for the use of administrative staff, producers, designers, etc., also, temporarily, a canteen for use of occupants of the block until such time as the main block is built.

Main Block

This block will consist of a multi-storey "ring" providing accommodation for dressing-rooms, wardrobe-service, engineering and offices, around a garden of 150ft. diameter. Radiating from the "ring" will be television production studios and their ancillaries,

together with two "presentation" studios (where announcements, captions, etc., are inserted), telecine and telerecording areas and a central control-room.

The outer periphery of the studios will be enclosed by a continuous runway, along which units of scenery, properties, etc., can be conveyed from the scenery block direct to the studios, these services being thereby segregated from areas allocated to artists, etc.

Canteen Block

Work has just commenced on this block. Initially, it will be divided and used for rehearsal purposes, but when the main block is occupied this block will be equipped as a canteen to serve 750 diners at a sitting. It will later be connected with the main block by a tunnel and by a bridge across the road outside the scenery runway.

Works Block

The works block will house the workshops for the maintenance and repair of technical equipment and an experimental laboratory where lighting and optical effects can be tried out. It will also provide accommodation for staff engaged on building maintenance.

Road Traffic

The centre will have its main entrances on Wood Lane and a secondary entrance on Frithville Gardens—which leads to the BBC Television Studios in Lime Grove. Parking space will be provided within the curtilage of the site for all cars using the centre.

WIRELESS COILS, CHOKES & TRANSFORMERS

8th Edition

6/- or 6/4 by Post from

GEORGE NEWNES, LTD.,

Tower House, Southampton Street, Strand, London, W.C.2



Pages from a TELEVISION ENGINEERS Notebook

19.—HEATER WIRING IN A.C.-D.C. RECEIVERS

IT has become general practice to operate television receivers from an auto-transformer which also carries a heater winding or windings for the valves and tube after the fashion shown in Fig. 1. This system has much to recommend it, for not only does the auto connection do away with the necessity for an expensive transformer having a separate primary and double (centre-tapped) secondary for the receiver H.T. supply, but the valve heaters can still be conveniently wired in the usual A.C. parallel arrangement. Further, a separate heater winding for the tube itself is readily provided.

The rectifier can, of course, be either metal or valve, the former being in general more common. If a valve is used, a further heater winding is necessary, but this is no serious drawback in the general simplicity and cheapness, to say nothing of physical size, of the system. It has only one disadvantage, if it may be called that, and that is in the design of a D.C. or A.C.-D.C. receiver, where obviously any sort of transformer is ruled out. The set must then be built to run directly from the mains without step-up, and the valve heaters must be run in series. The loss of any actual voltage step-up is of small consequence in modern techniques where booster diode circuits, R.F. or fly-back E.H.T. and other special valve systems can be brought into play; in fact, even with the auto-transformer circuits just mentioned, the step-up seldom exceeds some 250 volts A.C. It is in the necessity for series heater connections that some thought and care is necessary, and this will be the subject of the present discussion.

The Series Circuit

In any series circuit (assuming resistive components) the voltages are additive, but the current is the same throughout each element. Consequently, for the series valve circuit, all the valves must normally take the same heater current. If, for example, a 0.3 amp. heater line is decided on all the valves used in the set must take (or be made to take) 0.3 amp. The voltage ratings of the valves is not particularly important provided that the total voltage required by them does not exceed the voltage supply available. Let us look at this by means of a simple example.

Suppose a receiver is to use six EF91's in the vision and sound strips, a UB41 limiter and detector, an ECC81 as line and frame oscillator, a PL33 and PL38 as frame and line amplifiers, a PY80 as booster, an EL42 as sound output, and a MW31/74 tube. Fig. 2

shows these valves wired in a series system, with their respective voltage and current ratings marked off beside each of them. It will be noted at once that, though all current ratings are not the same, the bulk of the valves require 0.3 amp., and that the others are rated lower than this value. We are not concerned at the moment with the order of the valves, although this is quite important, as we shall see later on.

Adding up the voltages of the valves we find this to be 143.7 volts; therefore, assuming a mains voltage of 220 volts, a total of $(220 - 143.7) = 76.3$ volts must be lost in the resistance R . The value of this dropper is now easily found to be 254.3 ohms, say, 250 ohms, and it must consequently dissipate 22.5 watts, which is quite a lot of heat. Now, two of the valves are rated

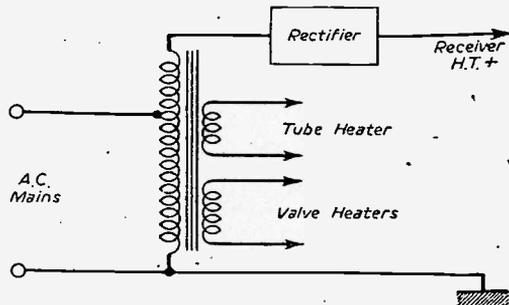


Fig. 1.—The familiar auto-transformer system of H.T. and heater supplies used on modern A.C. receivers.

lower than 0.3 amp. heater current; the EL42 takes 0.2 amp. and the UB41 takes 0.1 amp. In order that these valves will work without damage, the excess currents of 0.1 amp. and 0.2 amp. respectively, must be bypassed in suitable parallel resistances shown in the diagram as R_1 and R_2 . The calculation of such resistance values is quite simple; for the EL42 the voltage across R_1 (and the heater) is 6.3 and the current through R_1 has to be 0.1 amp., making its value 63 ohms at a wattage rating of 0.63 watts; and for the UB41, a current of 0.2 amp. at 19 volts gives 95 ohms at a rating of 3.8 watts for R_2 . In practice, a 1 watt 68 ohms resistance would be used for the EL42 shunt, with a 91 ohms 4-watt type for the UB41 shunt.

It is very important when making up a series valve

line in this way to check from the valve manufacturer's lists all heater ratings and ensure that no ratings lower than the main line current (0.3 amp. in the example above) are left unbypassed by a proper shunt. Failure to do this will result in the heater being considerably overrun, and actual damage may well result. Shunt values are not usually critical, and the

a component would have to be of a generous size and well spaced away from other parts; in addition, good ventilation would be necessary. If a series circuit can be made to do away with such a large resistance as dropper, or if several resistances of much lower rating can be used, the design of the set becomes easier, and ventilation problems are eased.

This can be done if valves having high voltage and low current heaters are used. Such valves come under the 0.1 amp. ranges of the various manufacturers and some examples are the Mullard UF42 high slope R.F. pentode, with a 21-volt heater, the UB41 double diode with a 19-volt heater, the UL41 output pentode with a 45-volt heater, and the UL44 line output pentode also with a 45-volt heater. If such valves are used in a series chain of the average television receiver, the total voltage chain can be made to come very close to that of the mains supply figure, with the result that very little voltage has to be lost in a dropping resistance such as R. In addition, the low current of 0.1 amp. reduces the wattage rating considerably, and problems of heat dissipation are easily overcome.

Fig. 3 shows the heater system used in the Baird P167 and similar models. This is a series-parallel arrangement, with a common mains dropper tapped at points to permit of various mains inputs, and then each valve chain has a separate dropper, of 10 watts rating, these components being easily obtained and quite small in physical size. Notice how the 12AT7 is made to carry the currents of both parallel lines of the other valves, so making its rating of 0.3 amps. correct.

The constructor intending to design his own A.C.-D.C. receiver should bear these points of series heater connections in mind, and select his valves accordingly.

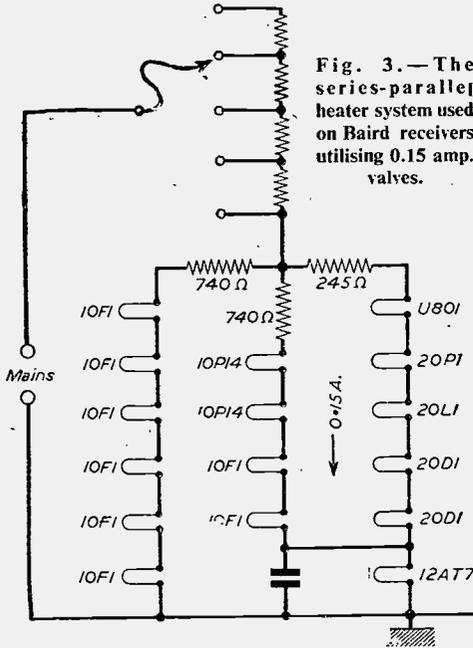


Fig. 3.—The series-parallel heater system used on Baird receivers utilising 0.15 amp. valves.

nearest preferred resistance value of adequate wattage rating will serve.

It must be noted also that valves with heater currents greater than 0.3 amp. cannot be used in a circuit such as that above; shunts cannot be used in such a case, and if wired up a valve will be under-run, which is often as bad as over-running. Further, as the total valve voltage chain adds up to 143.7 volts, the supply cannot be less than this, the greater the excess, the greater being the value of R to drop it.

Other Methods of Connection

We have seen that the wattage dissipation of R in the example above is 22.5 watts. Now such a dissipation means great heat, and in practical design such

Order of Wiring

In wiring valves in a series line, the valve nearest the dropper resistance has its heater at a fairly high potential (perhaps some 200 volts) above chassis or cathode, while the valve at the other extremity of the chain is earthed. Obviously, it is important to ensure that the valve heater-cathode potential rating will withstand such voltage differences, and a valve with a rating of, say, 50 volts, will not be used at the dropper end.

The order shown in Fig. 2 is a fairly typical one, the line output valve, booster diode and other "insensitive" types being wired at the high voltage end of the chain, while the R.F. pentodes of the vision and sound strips, the tube and the detector

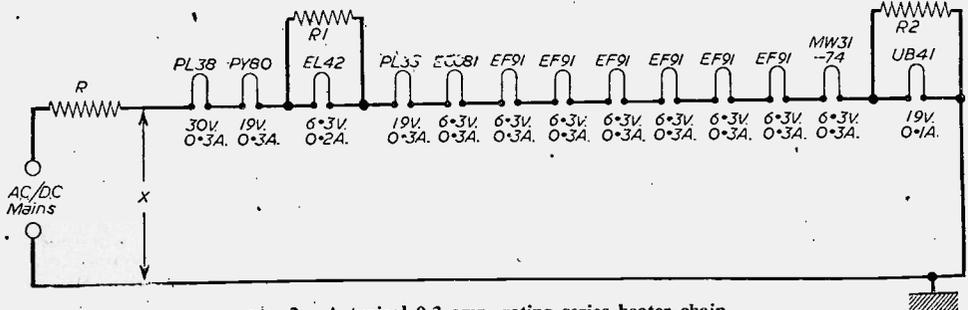


fig. 2.—A typical 0.3 amp. rating series heater chain.

are kept towards the earthy end. The valve manufacturer's lists should be studied in respect of the maximum permissible heater-cathode potential, and the valves arranged accordingly. One other point, however, is the matter of keeping valves such as detectors, low-level R.F. amplifiers, etc., somewhere near earth on their heaters as the possibility of hum induction into the cathode or grid is eliminated. The heater circuit of the A.C.-D.C. receiver described in the May, 1952, issue and the Lynx (which uses a series heater line although a transformed H.T. and tube heater supply is arranged), described in the July, 1953, issue, where all the above points will be illustrated, should be studied.

It is important that a valve in a series chain is never unplugged when the set is switched on. Suppose, for example, that one of the EF91's in the circuit of Fig. 2 is removed when the supply is on; all the valves go out, of course, but the heaters of those on the left of the removed valve immediately rise to the level of potential of the point X, perhaps 200 volts and more. The danger of a breakdown in the heater-cathode insulation of those of lower rating than this is, therefore, evident.

When a valve heater fails in such a chain, of course, all the valves are extinguished, and when such a fault is suspected, it is absolutely essential to switch off at once and then test each valve heater for continuity out of the set.

The Brimistor

The Brimistor, or thermistor element, is used in series chains to prevent heavy surges when first switching the current on to cold valves. It is usually wired in series with the main dropper R and is usually shunted with a resistance (about 5 watts rating) of some 250-300 ohms, to reduce the warming-up period. The resistance of the thermistor is very high to begin with, but falls as its temperature rises, finally reaching a steady state of some 40 ohms. This resistance must be allowed for in calculating the total dropping resistance required in any particular case.

There are several types of such thermistors, each designed for a particular current chain, 0.1 to 0.3 amp. and the proper type should be used.

Queries from readers sometimes show that a thermistor is often confused with a burned 1-watt resistance. The physical resemblance is very close, but the thermistor is unpainted and is normally black. It runs very hot in practice, and when cold will give a high ohmmeter reading. When such a component is noted in a heater line it is almost certainly a thermistor; a 1-watt resistance would not be a very likely component in such a position.

An Improved TV Aerial

By J. W. Hobley (G2VU)

THIS aerial marks a radical departure in design and theory, and is the result of much experimenting to provide an aerial which is compact, more efficient, and which can be made for a quarter of the cost of a metal rod aerial. It weighs only 4½ lbs., does not moan or whistle, renders chimney bands, wires, etc., unnecessary and has a long life.


It is based on the theory that a straight half-wave dipole aerial is fundamentally efficient and correct, and that aerials are merely collectors or radiators of energy, and I have, therefore, abandoned the use of such terms as "gain" in favour of "pick-up." Reflectors, etc., are not required.

The larger, within certain limits, the metallic surface presented to the transmitter the greater the "pick-up." In my opinion what little increased "pick-up" is obtained by adding rods to a dipole is due mainly to the additional metal surface obtained thereby.

By using wire netting of suitable length and mesh and rolling it into cylindrical form, I have found that by using two such cylinders as a dipole, the "pick-up" is increased by at least 50 per cent. as compared with a rod aerial, and that no advantage is gained by using gauze, perforated or expanded metal. These results relate to tests, etc., at 51 miles from Sutton Coldfield.

As will be seen from the drawing, the two cylinders are supported by a central wooden rod A, the lower end of which is extended to fit into an iron bracket B for attaching to the bottom of a chimney or under the eaves at which height, in the majority of cases, the "pick-up" equals that of a rod aerial mounted on a chimney.

Each cylinder is fitted with ends C of treated wood or the like and the inner ends are spaced and insulated at E as in an ordinary dipole. The inner wire of the co-axial cable D is soldered to the top section and the braiding to the bottom section. Twin feeder can also be used. Both vertical and horizontal forms are covered by patent applications. The latter type is not fitted with a central wooden rod, the cylinders being self supporting.

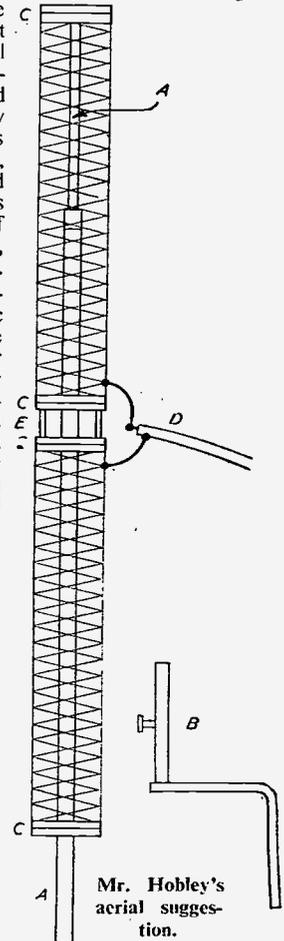

JOIN THE PRACTICAL GROUP
 Edited by F. J. CAMM

PRACTICAL WIRELESS	1/-
Every Month.	
PRACTICAL MECHANICS	1/-
Every Month.	
Devoted to Mechanics, Science and Invention.	
PRACTICAL ENGINEERING	6d.
Every Friday.	
For Engineers, Mechanics, Designers and Works Managers.	
PRACTICAL MOTORIST & MOTOR CYCLIST	1/-
Every Month.	

FAULT SYMPTOMS

THE CAUSES OF COMMON FAULTS, AND METHODS OF CORRECTION

By Gordon J. King, A.M.I.P.R.E.

(Continued from page 76, July issue.)

IN some Ferguson's a Metrosil resistor functions as a rectifier on the line flyback pulses taken from a tapping on the primary of the line output transformer, and produces across C1 about 200 volts above the H.T. line potential.

If all voltages on the tube appear normal, and the setting of the ion-trap magnet has been checked, the fault may lie in the scanning circuits. It is frequent practice to couple the frame deflecting coils to the output valve by means of a resistor capacitor network (see Fig. 55). Should C1 develop a short-circuit a very heavy current would be permitted to flow through the scanning coils, and since the coils used in this type of circuit are of high impedance the resulting magnetic field may be of sufficient magnitude to deflect the electron beam right off the fluorescent screen. To determine whether such a fault is responsible for our blank screen we can momentarily open-circuit the frame deflecting coils, when a single horizontal line should appear across the screen.

Very rarely are the line deflecting coils coupled in this way. Invariably, a transformer is employed, the insulation of which has not been known by the writer to break down in such a way as to cause a heavy current to flow through the line coils.

Having arrived at this latter check with still no sign of screen illumination we can assume with reasonable safety that the tube has died in some way.

A Blank Screen (Mainly Projection Receivers)

In all types of projection receivers, and in certain sets of the directly-viewed type, facilities are embodied to cut off tube beam current should one of the timebases cease to function. The symptom of a blank screen on such a receiver might, therefore, be due to one of the faults we have already considered, while, on the other hand, a timebase failure may be responsible.

Projection television receivers demand the formation of an intensely bright picture on the small 2½-inch diameter tube face, and for this reason very high final anode potentials are essential. Standard Mullard projection units use 25,000 volts, obtained from a "ringing" choke E.H.T. generator and a three-stage voltage multiplier, and in some directly-viewed sets final anode potentials in excess of half this figure are now commonplace.

Such high potentials subject the screen phosphors to damage by local heating should either of the timebases stop working, and as this is a contingency that might arise in any receiver, so-called tube protection circuits are introduced to eliminate the possibility of tube damage from this cause.

Most directly-viewed receivers employ a flyback E.H.T. system. With this type of circuit an automatic tube protection feature is provided so far as line timebase failure is concerned for, obviously, if this section fails no E.H.T. is generated. Even so, in certain circuits of this type the occurrence of an open circuit in the line deflecting coils may have but little affect on the generation of E.H.T. It is, therefore,

advisable to bear this point in mind when making adjustments to the picture-width tapping—which allows the selection of a suitable tapping on the line output transformer secondary to the deflecting coils—found in certain sets instead of the more conventional control. Moving the link from one socket to another while the set is working may render the deflecting function of the timebase inoperative—whilst still providing perhaps an even enlarged E.H.T. potential—for sufficient time to burn a vertical line on the screen.

From the frame timebase point of view, this danger from burning exists in most directly-viewed sets. Turning the brightness control down as low as it will go may only appear to cut off screen illumination, while the beam is being deflected normally, though it must not always be assumed that under this condition beam current is non-existent, for with a stationary

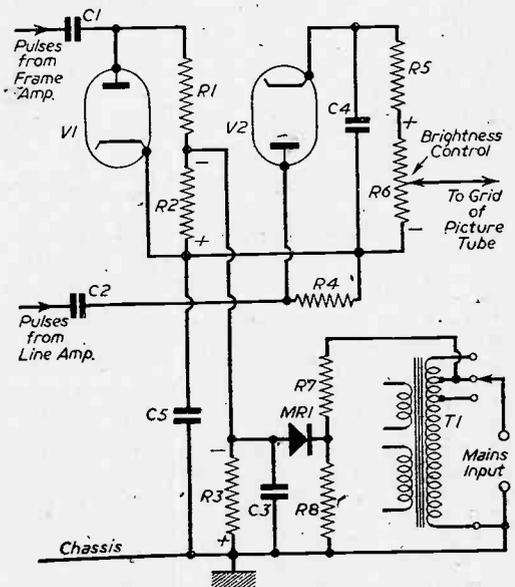


Fig. 56.—Picture-tube protection circuit used in the directly-viewed Ekco Model TC165.

beam, or with one which is being deflected in one plane only, the bombardment of the screen by very high velocity electrons in the resulting small area may, in certain cases, be sufficient to warrant concern.

To a large extent, of course, this reasoning depends upon the style of tube biasing arrangements adopted, and somewhat upon the characteristics of the tube; certain tubes possess a lower beam cut-off potential than others, and, as we have already seen, the resistive element of the brightness control is not always returned to chassis.

The directly-viewed Ekco TC165 is one receiver

that may fail to give a raster due to a timebase defect. This set uses a mains derived E.H.T. system, and the tube protection section under discussion is shown in Fig. 56.

Referring to the circuit we can see that the mains voltage across the primary winding of the mains transformer T1 is applied across a potential divider, consisting of R7 and R8. The resulting potential across R7 is rectified by MR1, and bled by R3; C3 being the reservoir capacitor, across which a potential in the region of 120 volts negative with respect to chassis is developed. This potential is applied through R2 and R6 to the grid of the picture-tube, making this electrode much more negative than the cathode, and, therefore, holding the tube well into cut-off.

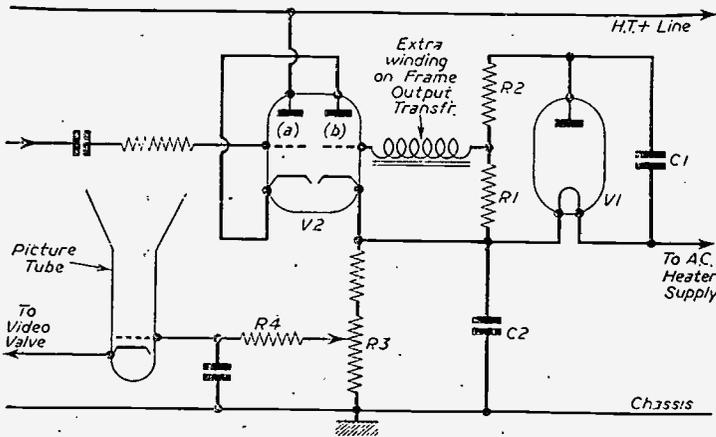


Fig. 57.—Protection circuit used in Philips' projection receiver, Model 799A.

Frame and line pulses, taken from across the appropriate deflecting coils, are applied to the anodes of diodes V1 and V2, via C1 and C2, respectively. Under these conditions both diodes conduct and a D.C. potential corresponding to the line pulses is set-up across R5 and R6, making the cathode of V2 positive. Similarly, the frame pulses are rectified and correspond to a D.C. potential across R1 and R2, and again the cathode of the valve V1 goes positive.

It can be seen, therefore, that the sum of the potentials developed across R2 and R6 is applied in positive sense, via the brightness control R6 slider, to the grid of the picture-tube.

The positive potential so derived tends to outweigh the cut-off potential across C3, and the component values are so arranged that with the cathode of the tube connected to the anode of the video amplifying valve in the usual way, R6 has the normal potential range for a brightness control.

Clearly, then, if both timebases fail, no positive potential exists across R2 or R6, and the full negative bias across C3 is applied to the tube grid to hold it well within the cut-off region. If the line timebase fails only, the resulting loss of positive potential across R6 is sufficient to upset the normal biasing arrangements, and the tube is held within beam current cut-off, although not quite to the extent of the full potential across C3. Similarly, if the frame timebase fails the potential at the tube grid falls less positive. In this case, however, the potential loss is less severe,

and the tube is not cut-off completely, nevertheless beam current is limited to a safe value.

A Circuit by Philips

Another tube protection circuit evolved by Philips, Ltd., and in use in the Philips Model 799A projection receiver, is shown in Fig. 57. Here the alternating voltage present across the valve heater supply line is taken to the cathode of the diode V1. A D.C. potential is thus developed across the reservoir capacitor, C1 and the potential divider R1 R2. The potential existing across R1 is negative with respect to V1 cathode, and is applied to the grid of triode V2(b) through an extra winding on the frame output transformer.

Since the cathode of this valve is in direct contact with the cathode of the diode, V2(b) is, therefore, held at anode current cut-off.

Because triode (a) of the V2 is connected in series with triode (b), triode (a) is also held at cut-off. As a result of this no potential is developed across the brightness control R3. Under such a condition the grid of the small type picture-tube is heavily negative, for the cathode is maintained positive from the anode of the video amplifier valve in the usual way.

This, then, is representative for conditions of no line or frame drive, and only when both triodes are fed from their respective sawtooth generators do they conduct and cause a current flow through R3, and a resulting volts drop which then

allows the potentiometer to function as a brightness control as is standard practice.

It should be mentioned that there are a few variants of this system, though in most cases the basic function is similar, and once the general principle of the artifice has been established, its mode of function can be readily assimilated.

A legion of faults—in addition to those intended—can cause protection circuits to operate and give rise to a blank screen. This can prove rather bewildering for the experimenter, but, nevertheless, systematic and judicial circuit analysis should soon reveal the defective section. In the first place it is desirable to ascertain that operation of the protection circuit is definitely responsible for the blank screen, and if it is, then extreme care must be taken to ensure that the produced paralysing bias is not inadvertently taken from the picture-tube due to a short-circuit or component by-pass during the process of analysing.

It is almost a certain fact that operation of the tube protection circuit is the cause of the blank screen if—after allowing a few minutes for the set to warm up properly—the receiver is switched off, when, provided E.H.T. is reaching the tube anode, a patch of diffused light appears in the centre of the screen. This is a simple and, in most cases, a rapid and reliable test.

Assuming the E.H.T. to be correct, a check for tube cathode potential is signified, for fault conditions may be indicative in this connection, when checking procedure as described previously in this series should

be adopted. If the potential at the cathode is not abnormally high a check for grid potential will, without much doubt, reveal it lacking.

Arriving at this point we can be fairly certain that a fault in either the line or frame generator—or maybe in the protection circuit itself!—is responsible.

The most likely cause will be a failure of one of the timebases. These can be checked by employing a pair of headphones as an indicating device. If, on the other hand, it is found that the timebases are working satisfactorily, it now remains to check meticulously all components in the protection circuit proper, unless it is possible to isolate the faulty section by potential checks.

Other Faults Associated with Protection Circuits

Although tube protection circuits yield nearly one hundred per cent. safeguard they are not entirely fool-proof. For instance, it has probably been observed from the circuits described that a deflecting coil going open-circuit would affect very little the action of the protection system, and that a fault of this nature would give rise to a damaging brilliant horizontal or vertical line on the screen of the tube.

Should this symptom suddenly appear, and if one is quick switching the set off, it may be possible to save the tube, though, generally, the damaging feature of this symptom is not readily recognised by the less technically minded members of the family, and many minutes may elapse in bewildered gaze before it is decided that the transmitter is not to blame and the set is eventually switched off. Unfortunately, by this time, apart from the open-circuited deflecting coil, the picture-tube also is in need of replacement.

Certain line output valves, such as the PL81 type, when employed in a self-oscillating line timebase circuit, continue to oscillate at a much reduced amplitude should the screen grid H.T. feed resistor (generally a wire-wound component) become open-circuit. This sometimes prevents satisfactory operation of the protection circuit, and allows the display of a very bright vertical band of light on the tube face which, within a few seconds, can easily ruin the fluorescent phosphors.

To eliminate this possibility a 100,000-ohm 1-watt resistor should be connected in parallel with the existing screen feed resistor. This ensures that sufficient line amplitude will be available under such a fault condition to prevent damage to the tube face. In particular, this protective modification applies to the Ferranti projection receiver, Model T1625.

Faults in the timebases which may have little effect on the general performance of a set not embodying a tube protection circuit tend to provoke a secondary disturbance in projection receivers, via the protection circuit, and thus on to the picture-tube grid.

An interesting symptom to illustrate this point is shown in Fig. 58. Although normal in all other respects, the raster depicted (modulated or unmodulated) resolved with a gradual fall-off in brilliance in the vertical direction; the projection receiver

concerned was a Decca Model 131. The symptom was eventually found to be caused by a ripple voltage at the grid electrode of the picture-tube. A further test revealed that the ripple was superimposed on the D.C. potential across the brightness control and was, in fact, originating from the frame generator (using a T41 valve) and gaining admittance to the brightness



Fig. 58.—A raster of uneven brilliance on the picture-tube of a Decca projection receiver, Model 131, caused by a fault in the frame timebase.

control circuit through the protection network. Replacing the relevant T41 solved the problem without any further trouble.

A Dim Picture

Unlike a definite symptom, such as complete lack of raster or picture, the actual cause of a dim picture can sometimes be a little tedious to establish, since numerous factors may contribute to the general effect. In the main, however, a dim picture is caused either by (a) insufficient video drive or (b) a defect preventing the picture-tube from emitting its maximum intensity of light, even when unmodulated.

In case (a), low sensitivity of the video chain as a whole is essentially responsible. This may be due to either deterioration of one or more of the valves associated with the vision section or an alteration in the overall response (alignment) of the vision section as a result of an alteration in the value of a capacitor or a shift of tuned-circuit adjustment; vibration from the loudspeaker may, for instance, quite easily disturb the setting of an iron-dust tuning core.

Furthermore, an alteration in valve characteristics, which often accompanies a reduction in emission, frequently upsets or modifies the loading of an associated tuned circuit. This is why it is generally considered advisable to check tuned circuit alignment after replacing a valve in the more critical section of the vision amplifier.

Apart from defects arising in direct connection with the tuned circuits proper, as above, the tuned frequency is also controlled to a large extent by shunt capacitances formed by the circuit wiring and the input and output capacitances of the valves.

(To be continued.)

VALVES AT U.H.F.

THIS ARTICLE DEALS WITH VARIOUS TYPES OF KLYSTRON, RESNATRON
AND THE TRAVELLING-WAVE GUIDE

By S. Simpson

IN the March issue of this magazine the trend of development of valves for use at U.H.F. was reviewed, and the position was dealt with up to the Klystron. The present article completes the review and deals with the various types of Klystron and the Resnatron. The article ends with some notes on the new travelling-wave tube.

In the "straight" Klystron tuning is quite a difficult procedure and the tube has the disadvantage of rather a narrow frequency pass-band before the power drops to half the value at the working frequency. This mitigates against the use of the tube on television links and multi-channel communication systems. To overcome this difficulty the "Reflex" Klystron was produced in which a much wider control over tuning and improved bandwidth characteristics are available.

The Reflex Klystron

In this tube, a typical version of which is seen in Fig. 1, the electron stream is acted upon in much the same manner as in the straight Klystron, but the tube differs in having only one resonator which has an exit gap opposite to the entry gap. Bunching occurs between the gaps, and the electrons emerge from the resonator only to find a negatively charged electrode opposing their further progress. They are returned to the resonator by this "repeller" and pass back into the gap in pulses which are timed to assist the oscillations in the resonator.

The advantages of the Reflex over the Klystron are twofold, apart from the need for only one resonator, and are brought about by the inclusion of the repeller. Rough tuning, as in the Klystron, is effected by altering the cavity dimensions, but transit time of the electron also has a great deal to do with the development of reasonable power at very high frequencies. The transit time in the Reflex depends mainly on three things: the gap between repeller and anode, the velocity of the forward current to the repeller, and the velocity of the returning current to the resonator or anode. The latter depends largely on the potential of the repeller, and herein lies one answer to the problem of easier fine tuning and of extended tuning range. Electronic tuning is now added to the mechanical tuning outlined above by variation of the standing potential on the repeller.

A second advantage of the repeller is its facility for providing a means of frequency modulation by application of the modulation voltage to that electrode. This type of modulation is fast becoming the recognised method in the communications applications of U.H.F., and it will readily be appreciated that the advent of the Reflex Klystron has opened a new line of approach to the subject.

Frequencies available from the Reflex are extremely high, even for U.H.F., experimental results having been obtained at ranges around 30,000 Mc/s. The output, however, is low and the tube finds its greatest use as a low-power oscillator or in test equipment designed for use on centimetric projects. In an attempt to keep the valuable properties of the Reflex

as an amplifier, another version of the Klystron has been developed, known as the three-cavity Klystron.

The Three-cavity Klystron

In this version, which again may be magnetically focused, there is a buncher resonator and a catcher resonator. Mid-way between them lies a third resonator, which can be regarded as replacing the drift-tube. Its action is to accentuate the bunching before passing the stream to the catcher, with a resulting increase in the power delivered because of the higher peaking of the stream. This version of the Klystron is used as a power amplifier with efficiencies ranging from 30 per cent. to 40 per cent. The possible gain is approximately 25 db.

F-M Drift-tube Klystron

Possibly the latest development in Klystron technique is that in which the drift-tube of the early Klystron reappears in a new form, isolated from the walls of the resonator and therefore capable of having a voltage applied to it which will vary the transit time of the electron. In effect, it replaces the frequency modulation action of the repeller, which, in some circles, has fallen into disfavour because of the defocusing effect of the repeller on the returned electron stream and the resulting inaccuracy of transit back through the gap of the resonator. There is also a belief that the repelled stream may be returned so violently as to reach the vicinity of the cathode and interfere with the

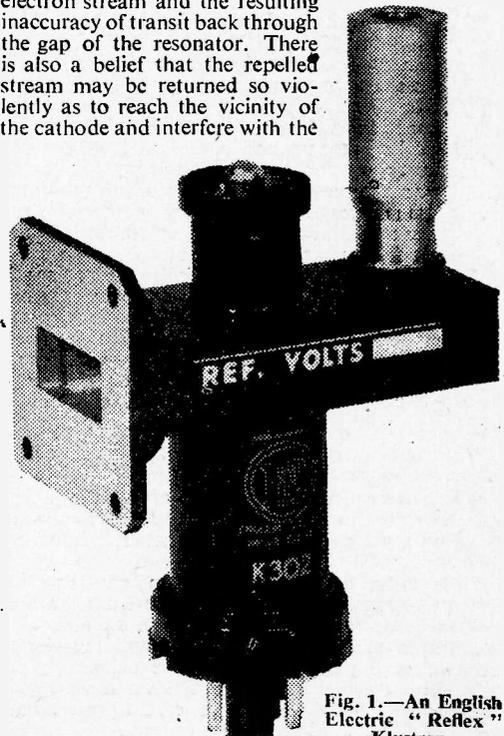


Fig. 1.—An English Electric "Reflex" Klystron.

normal bunching occurring near that electrode. On these points it is claimed that the isolated-tube Klystron has the advantage, and there is a better phasing of the repelled electrons which serves to increase still further the efficiency obtainable in this type of Klystron tube.

The Resnatron

All the above tubes work on the principle of "velocity modulation," i.e., the velocity of the travelling electron is varied due to "modulation" by the R.F. oscillations.

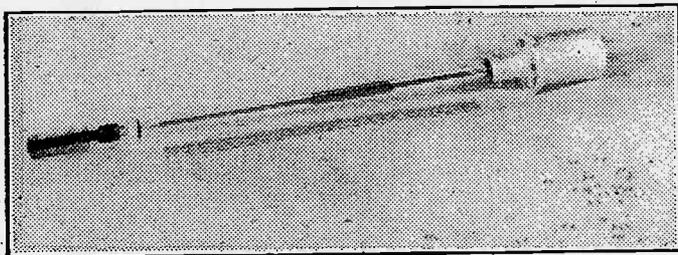


Fig. 2.—A travelling-wave tube such as is now in use in the Manchester-Edinburgh TV link.

A second method is that of "density modulation," in which the electron stream is acted upon in such a way as to produce variations in the mass, or quantity, of electrons passing through the electrodes at any instant. Chief among these is the new Resnatron, also produced in a "straight" or a "reflex" version.

In form it comprises a cathode surrounded by a shield formed by part of the input cavity resonator, in which the density modulation occurs. The electrons then pass through a grid in the cavity and enter an output cavity by means of a similar grid. From this point the electrons pass on to meet the repeller, as in the Reflex Klystron, and are returned to the output resonator to sustain the oscillations existing there. In much of its make-up and operation the Resnatron seems very similar to the Klystron, but in the Resnatron the repeller is introduced into the output cavity and increases the efficiency of the tube as a frequency modulator. A second difference is the use of two tuned resonators instead of one.

The tube was produced in an effort to increase the available power from the reflex action, and typical figures—30 kW pulsed power at 420 Mc/s with 75 per cent. efficiency—would indicate that the efforts of the development engineers have been reasonably successful. The valve is capable of 60 kW output power, is water cooled and has a continuously operating pump to maintain the vacuum while in action.

Travelling-wave Tube

Perhaps the most promising of all the U.H.F. tubes so far produced is the T-W tube, now in use with so great success in the Manchester/Edinburgh TV Link.

This tube differs greatly from any described hitherto. The tube derives its name from the interaction between a helix, clearly seen running along the length of the tube in Fig. 2, and the electron stream passing axially through the helix.

An input signal at R.F. is fed via a wave-guide and coupled to the helix, so creating an electromagnetic field within it.

The electric field, which is axial to the helix, causes bunching of the electron stream. This bunching, in turn, creates a second wave on the helix, which then reacts on the stream, and in this manner the R.F. cycle is maintained in progressive steps along the helix.

Three types of wave exist on the helix. The required wave is partly determined by the diameter of the helix, and the developed wave is then picked up by the output wave-guide located at the end of the helix remote from the cathode assembly.

Because of the length of the electron path the technique of electron stream production is largely akin to that of the cathode-ray tube. Focusing and accelerating anodes are placed near the cathode, and magnetic fields are applied throughout the length of the flow within the helix, apart from the vicinity of the wave-guides. Accurate alignment of cathode and helix is essential, and cooling of the collector at the "target" end is also provided.

The tube is sensitive to variation of beam current and helix voltage; the gain alteration is rapid for any change in these figures, and a stabilised circuit has been found desirable. Approximate helix voltage is around 3,000 volts.

On the question of bulk perhaps the T-W tube may be criticised. It is larger than most tubes, requires a power supply for magnetic focusing, and a source of E.H.T.

On the other hand, one tube will give a gain over input which cannot be met by less than three or four stages using other types of tube. The pass-band of the tube is wide at high-gain levels, a point very much in its favour in multi-channel communication systems.

Development work is still proceeding on the T-W tube with the object of reducing the bulk of auxiliary apparatus, the E.H.T. voltages required, and of increasing still further the output power available at the frequency range around the 4,000 Mc/s mark.

Apart from the tubes already mentioned, others are still in process of development, and there seems little reason to doubt that the little glass valves we know so well, and which have served so faithfully at the lower frequencies, will soon have little or no resemblance to their new and highly efficient successors.

As useful as a Tool Kit—

8th (Fully Revised) Edition of the
PRACTICAL MOTORIST'S ENCYCLOPEDIA
By F. J. CAMM

With full section on Car Radio

400 pages, 493 Illustrations

17/6 or 18/- by post from :

**GEORGE NEWNES, LTD., Tower House,
Southampton Street, Strand, W.C.2**




Pointers for Designers

AND CONSTRUCTORS NUMBER ELEVEN

VALVES FOR TAPE RECORDERS

INPUT STAGE Z729


[low noise pentode]

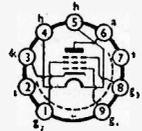

- V_h 6.3V
- I_h 0.2A
- V_a 250V
- V_{g2} 140V
- g_m 1.85mA/V
- V_{hum} 1.5μV
- R_{g1-k} = 470Ω
- Base B9A

Tone correction and intermediate stages B309


[double triode]

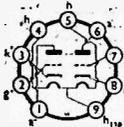

- V_h 6.3V
- I_h 0.6A
- V_a 250V
- g_m 5.5 mA/V
- r_a 10 kΩ
- Base B9A

Output and bias oscillator

N727/6AQ5 or N78

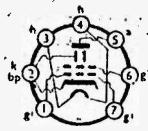


- V_h 6.3V
- I_h 0.45A
- V_a 250V
- V_{g2} 250V
- I_k 50 mA
- V_{g1} -12.5V
- P_{out} 4.5W
- Base B7G

Rectifier

U709

[full-wave rectifier]

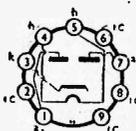

- V_h 6.3V
- I_h 0.95A
- V_{h-k} 450V (max.)
- V_{in} 350 rms (max.)
- I_{out} 150 mA
- Base B9A

The heater-cathode operation of the U709 permits operation from a common 6.3V heater winding

For further information and full technical data write to: The Osram Valve and Electronics Dept., THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2

Volume Controls

Midget Edison type. Long spindles. Guaranteed 1 year.

No. Sw. S. P. Sw. 3/- 4/-

D.P. Sw. 4/8

ALL VALUES—10,000 ohms to 2 Megohms.

BALANCED TWIN FEEDER per yd. 1/6

TWIN SCREENED COAX FEEDER per yd. 1/3

50 OHM COAX CABLE, 8d. per yd.

TRIMMERS, Ceramic, 50, 70 pf., 9d.; 100 pf. 1/3

Ditto Carbon Track 50K, 1/8; 600 pf., 1/8

RESISTORS—All values: 1 w., 40; 1/2 w., 6d.; 1 w., 8d.; 2 w., 1s. 4; 1/2 w., 2/6

WIRE-WOUND RESISTORS—Best Makes, Miniature Ceramic Type—1 w., 15 ohm to 4 K.; 1/2 w., 10 w., 20 ohms to 6 K., 2/3; 15 w., 30 ohm to 10 K., 2/6; 6 w., Vitreous, 15 K. to 25 K., 3/-

WIRE-WOUND POTS, 3 WATT, FAMOUS MAKES

Pre-Set Min. Turn Type Standard Size Pots, 21in. Knurled Slotted Knob. Spindle, High Grade. All values 25 ohms to 30 K., 3/- ea. 50 K., 4/-

Ditto Carbon Track 50K, 1/8; 600 pf., 1/8

2 to 2 Meg., 3/-

O/P TRANSFORMERS—Tapped final pentode, 3/8. Heavy duty 70 ma., 4/8. Ditto, tapped, 4/8

L.F. COILS 10 h. 60 ma., 5/2; 20 h., 150 ma., 12/8; 1 h., 100 ma., 10/8; LYNX, 3 h., 250 ma., 13/8

SIMPLEX 10 h., 150 ma., 10/8

MAINS TRANS.—Made in our own workshops to high grade specification. Fully inter-lead and impregnated. Heater Trans., tapped min., 0.200 v./250 v., 6.3 v., 11 amp., 7/8; 12 v., 75 amp., 7/8; 6.3 v., 2 a., 10/8; 350-600 ma., 6.3 v., 4 a., 3 v., 2 a., ditto 200-0-200 ditto 250-0-250, 21/-

Viewmaster, auto type, 35/-; Teloking, 30/-; Lynx, 30/-; Coronet, 30/-; Simplex (modified with 4 v. tap), 35/-

TV. AERIALS—Aerialite etc. full range all channels in stock. Indoor loft type Inv. T., 12/8 etc. etc.

80 ohm COAX

STANDARD lin. diam. Polythene insulated. Grade "A" Not Ex Govt., 8d. yd.

COAX PLUGS, 1/2 each.

SOCKETS, 1/2 each.

LINE CONNECTOR, 1/2

OUTLET BOXES, 4/8

30 ohm COAX CABLE, 8d. per yd.

TRIMMERS, Ceramic, 50, 70 pf., 9d.; 100 pf. 1/3

Ditto Carbon Track 50K, 1/8; 600 pf., 1/8

RESISTORS—All values: 1 w., 40; 1/2 w., 6d.; 1 w., 8d.; 2 w., 1s. 4; 1/2 w., 2/6

WIRE-WOUND RESISTORS—Best Makes, Miniature Ceramic Type—1 w., 15 ohm to 4 K.; 1/2 w., 10 w., 20 ohms to 6 K., 2/3; 15 w., 30 ohm to 10 K., 2/6; 6 w., Vitreous, 15 K. to 25 K., 3/-

WIRE-WOUND POTS, 3 WATT, FAMOUS MAKES

Pre-Set Min. Turn Type Standard Size Pots, 21in. Knurled Slotted Knob. Spindle, High Grade. All values 25 ohms to 30 K., 3/- ea. 50 K., 4/-

Ditto Carbon Track 50K, 1/8; 600 pf., 1/8

2 to 2 Meg., 3/-

O/P TRANSFORMERS—Tapped final pentode, 3/8. Heavy duty 70 ma., 4/8. Ditto, tapped, 4/8

L.F. COILS 10 h. 60 ma., 5/2; 20 h., 150 ma., 12/8; 1 h., 100 ma., 10/8; LYNX, 3 h., 250 ma., 13/8

SIMPLEX 10 h., 150 ma., 10/8

MAINS TRANS.—Made in our own workshops to high grade specification. Fully inter-lead and impregnated. Heater Trans., tapped min., 0.200 v./250 v., 6.3 v., 11 amp., 7/8; 12 v., 75 amp., 7/8; 6.3 v., 2 a., 10/8; 350-600 ma., 6.3 v., 4 a., 3 v., 2 a., ditto 200-0-200 ditto 250-0-250, 21/-

Viewmaster, auto type, 35/-; Teloking, 30/-; Lynx, 30/-; Coronet, 30/-; Simplex (modified with 4 v. tap), 35/-

TV. AERIALS—Aerialite etc. full range all channels in stock. Indoor loft type Inv. T., 12/8 etc. etc.

TYANA—Midget Soldering Iron, 200/250v., or 250/250 v., 14/11. Triple three mod. with detachable bench stand, 19/8. Stono Midget Iron, 18/8. TAG STRIPS—2- or 4-way, 2d.; 4- or 5-way, 3d.; 6-way, 4d.; 9- or 10-way, 6d.; 25-way, 1/8

SIMPLEX TELEVISION

Detailed price list available.

STAGE 1. VISION AND SOUND.

- 7 Valves ... 50/-
- 12 Resistors ... 3/-
- 18 Condensers ... 8/-
- 2 Potentiometers ... 10/8
- 7 Coil formers with cores ... 4/8
- 7 Valveholders ... 8/8
- Sundries (with undrilled chassis) 22/8

STAGE 2.—TIME BASE.

- 8 Valves ... 29/-
- 20 Resistors ... 8/8
- 15 Condensers ... 15/8
- 5 Potentiometers ... 12/8
- 8 Valveholders ... 2/8
- Sundries ... 1/8

etc., 17/8, or 10/- extra with Kit or Sundries (Stage 1).

VCR97 TUBE TESTED & GUAR., £2 (P. & P., 2/-)

NEW BOXED VALVES GUARANTEED ALL

- | | | | | | | |
|------|------|-------|------|-------------|------------|---------------|
| 1R5 | 8/- | 6K8 | 9/- | 12K7 | 10/8 | Syl. Red 10/8 |
| 1R5 | 8/- | EF80 | 10/8 | 10K8 | 10/8 | EP91 9/- |
| 1T4 | 8/- | 6BQ6 | 12/8 | 12Q6 | 10/8 | EV51 12/8 |
| 1S4 | 8/- | 6P5 | 15/- | 31L6 | 10/8 | HVR2a 7/8 |
| 3S4 | 8/- | 6B7 | 8/- | 32Z4 | 10/8 | NY80 11/8 |
| 2X4 | 8/- | 6B17 | 8/- | 807 | 10/8 | PY82 10/8 |
| 2X2 | 5/8 | 68N7 | 11/- | EA50 | 2/- | RP61 8/8 |
| 6Y4 | 10/8 | 613 | 10/8 | VC638 | 10/8 | UD22 9/8 |
| 5Z4 | 8/- | 6V6 | 8/- | 6BC33 | 9/8 | DC150 12/8 |
| 6AM6 | 9/- | 6X3 | 8/- | 6F50 | 9/- | 25L5 10/8 |
| 6AT6 | 10/8 | VT127 | 10/8 | 6F50 | 9/- | 25L5 10/8 |
| GAM6 | 3/8 | 46 | 9/- | Equip 5/8 | EC142 12/8 | |
| 6J5 | 7/8 | 12A7 | 10/8 | British 7/8 | M14 9/8 | |

Huge Stock B.V.A. Valves at 1951 low tax prices.

TV. PRE-AMP.—Channel 1, easily modified to other channels or converter use. Midget chassis 6in. x 5in. x 1 1/2in. Complete with roax, lead, plug and EF42 valve. Brand new boxed. Listed £3/15/- Special clearance, 27/8, pp. 116.

P. and P., Gd. £1 orders post free. Lists 3d. ALL TRANS. P. & P. 1/- extra please.

T.R.S. RADIO COMPONENTS SPECIALISTS

307, Whitetors Road, West Croydon.

C.R.T. HEATER ISOLATION TRANSFORMER

Low leakage winding with 25% sec. boost, 2 v., 10/6; 4 v., 10/6; 6.3 v., 10/6; 12 v., 10/6

BRIMISTONS.—CZ1 3 a., 3/8. CZ2 15 p., 2/8

CONDENSERS.—New stock. 500 mfd. 6 K.V. T.M.C., 5/8; 1000, 12.5 K.V., 9/8; 2 pf. to 500 pf. Mica, 6d.; 500 Mica or T.M.C. 500 v., 1/1

Sprague 500 v., .02 N.R.P., 6/8 v. 1 mfd. 350 v. Micamould Tub. 9d.; Hunts Moldseal 500 v. .005, .01, 9d.; 35 mfd. and 1 mfd., 1/-; 25 mfd., 1/8

10 mfd. 350 mfd., 350 v., 1/8

SILVER MICA CONDENSERS.—10% 1.5 pf. to 500 pf., 1/-; 600 pf., to 3,000 pf., 1/3. DITTO 1% ex Stock.

1.5 pf. to 500 pf., 1/8; 515 pf. to 1,000 pf., 2/6

ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends (Can Type, Clips, 3d. ea. 2450 v. B.E.C. 2/3

16/450 v. T.C.C. 3/8

4500 v. Hunts 2/-

600/50 v. T.C.C. 9/8

8/450 v. B.E.C. 2/3

250/350 v. B.E.C. 9/8

8/450 v. T.C.C. 2/8

8/1650 v. B.E.C. 5/-

8/1650 v. Dublier 2/8

16/500 v. Dublier 4/-

16/1650 v. B.E.C. 5/8

8/450 v. Dublier 4/8

32/350 v. Dub. 5/8

32/350 v. B.E.C. 5/8

32/350 v. Dub. 5/8

100/100/350 v. Hunts, 11/8

500/5 v. B.E.C. 1/8

500/25 v. Plessey 1/8

60/50 v. Plessey 2/8

6/000 6 v. B.E.C. 5/8

16 mfd. 700 v. B.E.C. 12/8

SENTERCEL RECTIFIERS.—EMT Type. Fly-back Voltage.—K2/25 2 Kv., 4/3; K3/40 3.2 Kv., 6/8; K3/45 3.6 Kv., 6/8; K3/50 4 Kv., 7/8; K3/100 8 Kv., 12/8; K3/150 14 Kv., 18/-; MAINS TYPE.—RM1 125 v., 50 ma., 4/-; RM2, 100 ma., 4/8; RM3, 120 ma., 5/8; RM4, 250 v., 275 ma., 16/-

KNOBS, GUD ENGRAVED.—Walnut or Ivory, 1 in. diam., 1/8 each. Not engraved, 1/4 each.

LOUDSPEAKERS P.M. 3 OHM.—2in. Plessey, 12/8; Goodmans, 4in., 15/8; 5in., 14/8; 6in., 16/8; 8in. T. & A., 17/8; 10in. Plessey, 25/-

SLEEVING.—Various colours, 1/2 mm., 2d.; 3 mm., 5d.; 5d. yd., 5d. yd. TOGGLE SWITCHES EX-60VT.—On-On, 9d. Exin M-core solder, 60/40, 16 g. or 15 g., 4d. yd., 5/8 lb. h. PVC Connecting wire, 10 colours. Single or Stranded 2d. yd.

WELDERS.—Fax 10, 4d.; EP30, 15/60, 6d.; 15/24 CRT, 1/8, Moulded, 10, 6d.; B7G, 9d.; with screening can, 1/8; BSA, 35/8; B9A, 1/2; VCR97, 2/8. Ceramic; EP30, 17/8, 1/4; All English, 5, 7, 9 pin and U.S.A. UX types, 1/4; VCR97 moulded holders, 2/8. ALADDIN FORMERS and core, 1in., 8d.; 1/2in., 10d.



OFFER THESE VALVES

GUARANTEED NEW AND BOXED

024	6/ 6P14	11/6 807	3/3 1E148	2/ - P22	8/ -
1A5GT	6/6 6GG6	6/6 8D2	2/6 2BC41	11/ - U35	13/6
1A7	11/6 6H6	4/6 954	2/ - LC42	11/6 U81	10/ -
1CBGT	8/ 635G	5/ 855	4/9 8E42	10/6 UAF42	12/6
1L4	7/6 645GT	5/6 956	3/6 6CH35	13/ - UB41	9/6
1R5	7/6 635M	6/6 9D2	3/ - 6BP80	11/6 UBC41	11/6
1R4	7/6 637G	6/6 9001	6/ - 6B41	11/ - UCH42	12/6
1R5	7/6 6K7G	6/ - 9002	6/ - 6PCL30	11/6 UP41	12/ -
1T4	7/6 6K7M	6/6 9004	6/ - 6E36	6/6 UY41	10/ -
1U5	10/ 6K7GT	6/6 9006	6/ - 6E41	10/ - 6F39	6/6
220VSG	6/6 6K8G	8/6 10P9	11/ - 6F50	11/6 6B34	2/6
2X2	5/ 6K6GT	6/6 10LD11	11/ - 6Z40	11/ - 6BC33	7/6
3A4	9/ 6K8GT	9/ - 12A6	6/6 6M31	9/ - 6C52	5/9
3Q4 (N18)	9/ 6376	8/6 12AU7	6/ 6Y91	9/ - 6C61	5/9
3Q5	10/6 6L6G	9/ - 12AT7	9/6 6Y61	13/6 6F36	6/6
3D6	5/ 64L7M	7/6 12BA6	11/6 6Z41	11/ - 6P61	3/9
384	6/6 6N7	7/6 12C8	8/ - 6H14	10/ - 6K32	8/9
3V4	8/ - 6P26	10/ - 12H6	5/ - 6H63	7/6 6P41	3/6
4D1	3/ - 6Q7G	9/ - 12J5	6/ - 6H30	8/ - 6E50	3/6
4E	8/ - 6Q7GT	9/ - 12K7	9/ - 6H23DD	8/ - 6E50 Spt	8/ -
5U4G	6/6 6S67	7/6 12K8GT	9/ - 6K22	5/ - 6R30	2/ -
5V3G	8/ 6SH7	6/ 12S67	5/6 6K74	8/ - 6R116	4/ -
5Z3	6/6 6S7GT	8/6 12S7H	5/6 6X23	15/ - 6LD14	4/ -
5Z4G	8/6 6S87	8/6 12S7	8/6 6K76	10/ - 6E8	6/6
6A7	9/6 6S17	8/ - 12S67	7/6 6R81	10/6 6F54	7/ -
6A8G	9/6 6SNTGT	8/ 12S87	6/6 6KWS1	7/6 6R105/30	9/ -
6U4500	8/6 6S97	9/ 12S87	7/6 6KZ41	6/ - 6R150/30	9/ -
6AC7	6/6 6S87	8/ 12S87	6/6 6KZ63	6/6 6L32	8/ -
6AG5	7/6 6U5G	8/6 12Q7	9/ - 6L39	11/6 6T11	6/ -
6AK5	9/ 6V6G	7/6 20D1	10/6 6M4	5/6 6V23	8/6
6AL5	7/ - 6V6GT	7/6 20P3	11/6 6MS/PEEN	5/ - 6V39	8/6
6AM6	7/6 6X4	8/ - 20J1	11/6 6N5	11/6 6U11	3/6
6AT6	10/ - 6X3GT	7/6 20P1	12/6 6PEN25	8/ - 6U120A	3/6
6AM5	9/ - 6X5G	7/6 22A6G	9/ - 6PEN46	8/6 6U133	3/6
6B8G	4/ - 7B7	8/6 25L6GT	8/6 6PEN220A	4/8 6W77	8/6
6B6E	9/ - 7C5	8/6 25Z40	9/ - 6P33	9/8 6W81	16/ -
6C4	8/ - 7C6	8/6 25Z6GT	8/6 6P81	13/6 6X65	10/ -
6C5GT	7/6 7H7	8/6 27B1	13/ - 6P82	11/6 6X66	11/6
6C6	6/6 7R7	8/6 30L6GT	8/6 6P83	13/ - 6X79	11/6
6C9	8/ - 7T	8/ 35A5	8/6 6P82	11/6 6Y63	9/ -
6D3	7/6 787	8/6 35Z4GT	8/6 6P89	11/6 6BARETTES	9/ -
6D6	7/6 7Q7	8/6 56L6GT	8/6 6P81	11/6 Type 150A	4/6
6P1	13/6 7Y4	8/ 6ATP4	8/6 6P22	7/6 Atlas	4/6
6P6G	7/6 7S	10/ - 6ACPEEN	4/6 6P21	7/6	9/ -
6E8G	17/ - 80	8/6 6C133	11/6 6D73M	9/ -	9/ -
6P13	11/6 85A1	12/6 6CV71	1/ - 6P22	9/ -	9/ -

A SPECIAL PURCHASE OF TUNGSRAM VALVES ENABLES US TO OFFER THE FOLLOWING:


25Z5	9/ 6V6G	9/ - AS4125	11/6 25Y5	9/ - LD210	6/ -
HP4101	11/6 6V6GT	9/ - 6BP11	6/6 6U7G	8/6 6P220	6/ -
637G	8/6 80	9/ - 6V30	1/ - 6P220	8/ - 6P220	5/9
				8/6 6P220	6/ -
				HRK10	5/9

LOUDSPEAKER UNITS

PLESSEY	8in.	Round type for personal portables, 2 to 3 ohm	12/9
ELAC	3 1/2in.	Square type 3/02, 2 to 3 ohm	13/6
ELAC	4in.	Square type 4/02, 2 to 3 ohm	13/9
ELAC	5in.	Round type 5/04, 2 to 3 ohm	13/6
GOODMANS	5in.	Round type	14/9
PLESSEY	5in.	Latest type	14/9
GOODMANS	5in.	Round type	15/11
ELECTRONA	6in.	With transformer	18/ -
PLESSEY	6in.	Round type, 2 to 3 ohm	14/11
ELAC	6in.	Type 6/19, 2 to 3 ohm	15/6
TRUVOX	6in.	Water, only 1 1/2 in. deep, 2 to 3 ohm	18/ -
R. & A.	8in.	Lightweight, 2 to 3 ohm	22/6
PLESSEY	8in.	Mains Energised	17/6
PLESSEY	8in.	Mains Energised	21/ -
ELECTRONA	8in.	PM 2 to 3 ohms	18/6
ELAC	8in.	PM 2 to 3 ohms	17/6
ELAC	10in.	Units, 2 to 3 ohms	22/6
PLESSEY	10in.	Lightweight	18/6
TRUVOX BX11	12in.	Lightweight	49/6

TERMS: Cash with order or C.O.D. Postage to be added to orders as follows: 9d. up to 10/-; 1/- up to 20/-; 1/6 up to 40/-; 2/- up to £5. MAIL ORDER ONLY: Send 6d. in stamps for illus. catalogue.

WHEN ORDERING PLEASE QUOTE "DEPT. P.T."

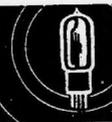

ALPHA RADIO SUPPLY CO.

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

MAINS TRANSFORMERS

3-way mounting type
 MT1.—Primary 0-210-250 v.
 Secondary 250-0-250 v. 80 mA. 6.3 v.
 4 amps, 5 v. 2 amps with taps at
 4 v. on filament winding. Price,
 17/6 each.
 MT2.—Primary 0-210-250-250 v.
 Secondary 250-0-250 v. 80
 mA. 6.3 v. 4 amps, 5 v. 2 amps. Both
 filament windings tapped 4 v.
 Price 17/6 each.
 MT3.—30 volt 2 amp. tappings as
 follows: 3.4, 5, 6, 8, 9, 10, 12, 15, 18,
 20, 24 v. 17/6 each.

CONDENSERS

The following is a selection from our
 stocks of manufacturers' surplus
 condensers, all by well-known makers,
 DUBLIEE, B.I., BEC (EDISWAN),
 SPRAGUE, etc.

Aluminium Can Types, Clip Fixing	
8 x 8 mfd. 450 v.	4/-
8 x 16 mfd. 450 v.	4/-
8 x 24 mfd. 350 v.	3/-
8 x 32 mfd. 475 v.	3/9
12 x 4 mfd. 450 v.	2/-
16 mfd. 450 v.	3/-
16 x 8 mfd. 350 v.	4/-
16 x 16 mfd. 350 v.	3/6
20 x 20 mfd. 500 v.	4/6
24 mfd. 450 v.	2/8
25 x 16 mfd. 350 v.	3/6
32 x 16 mfd. 350 v.	3/6
32 x 32 mfd. 350 v.	6/11
32 x 32 mfd. 500 v. 350 v.	5/6
32 x 32 mfd. 350 v. 25 mA. 25 v.	5/9
64 mfd. 350 v.	2/-

(B.R. Range)

BR.850 8 mfd. 500 v.	2/9 ea.
BR.1650 16 mfd. 500 v.	3/3 ea.
BR.2050 20 mfd. 500 v.	3/8 ea.
BR.501 50 mfd. 12 v.	4/- ea.
BR.501 50 mfd. 12 v.	1/6 ea.

Midget Metal Types

2 mfd. 350 v.	1/9
8 mfd. 350 v.	1/1
8 x 8 mfd. 350 v.	3/-
8 x 8 mfd. 450 v.	4/-
16 mfd. 350 v.	2/9
16 x 8 mfd. 450 v.	4/-
16 x 16 mfd. 450 v.	4/8
16 x 24 mfd. 350 v.	4/9
24 mfd. 350 v.	2/9
32 mfd. 350 v.	1/9
32 x 32 mfd. 350 v.	4/8
250 mfd. 12 v.	1/9

Wire Ended Types

8 mfd. 450 v. Cariboard covered	1/11
30 mfd. 450 v.	3/9

Bias Condensers

Tag ended metal types	
12 mfd. 50 v.	1/-
25 mfd. 25 v.	1/3
50 mfd. 12 v.	1/-
50 mfd. 50 v.	2/6
100 mfd. 12 v.	1/9
100 mfd. 25 v.	1/9

Wire Ended Types Cariboard Covered

25 mfd. 25 v.	1/9
50 mfd. 12 v.	1/9
50 mfd. 50 v.	2/3

42in. EXPONENTIAL HORNS. 1 1/2 in. fitting. These horns have a 28in. square base, weigh approx. 25 lbs. and measure 44in. from top to bottom, 42 1/2 in. carriage 7 1/2 in.

FLEX CONNECTORS. 5 amp. size 2 pin, 1/- ea.

VITAVOX PRESSURE UNITS. Heavy Duty P.M. 20 watts. To fit the above horns. Brand new. £4/9/6, carriage 5/-.

ELECTRIC LIGHT CHECK METERS. 200-250 v. A.C. at 10 amps. Bakelite case, in very good condition. 15/-, p.p. 2/6.

CRYSTAL DIODES, 2 for 2/1.

CHARGER TRANSFORMERS. High Grade Wax Dipped 220/240 v. input. 6 and 12 v. 2 amp. output. 10/6 each.

NYLON DRIVE CORD. 25 yds. on Wooden Reel. Best quality. Special Price, 2/9 each.

RADIO CRYSTALS, 1/6 doz.

ELAC 4in x 7in. ELLIPTICAL TYPE SPEAKER complete with output transformer, 10/6 ea.

LINE CORD

3 amp 3 core, 1/8 yd.
 2 amp 3 core, 1/8 yd.

ION TRAPS, Type 1T6, 2/6 ea.

OUTPUT TRANSFORMER, Jantard Pentode, 2/9 ea.

I.F. TRANSFORMERS, 465 kc/s., 6/3 pair.

SUMMER VALVE OFFER

EF6, 6/-, EL2, 6/-, S130, 5/-, 250 IPT, 6/-, HL13C, 2/6, MHL4, 5/-, 6A6, 3/9, 7D6, 6/9, 6C8, 5/-, 6F13C, 6/9, 6P33, 5/-, KIL32, 6/-, KT32, 8/-, UR3C, 7/-.

TV PRE-AMPLIFIER LONDON FREQUENCY.

Manufacturer's surplus stock. Brand new on chassis size 6. Valve type 6F42 included, standard co-axial input and output. Price, 21/- each; post, 1/6 each.

THE "COMPACT" TELEVISION AERIAL by Antiference, Ltd.

Cat. No. CD4. List price, 50/-, Our price, 19/6; post, etc., 2/6.

CO-AXIAL CABLES. 1/036, semi air spaced, 1 1/2 yd.; 1/022, solid type, 7 1/2 yd.; 7/076, stranded, 8 1/2 yd.

1lb. REELS SOLDER by well-known maker 7/6 lb.; post and packing, 1/-.

COLLARO AC37 GRAMOPHONE MOTOR

with 16in Turntable, governor controlled to run at 78 RPM. Suitable for 100/125 v. 200/250 v. 46/- each, plus 2/6 P. & P.

Just arrived: a few more VCR97 complete with screen and base. Price 29/6 each, plus 2/6 post.

SURPLUS UNIT containing 12 Mazda valves and 1 VCR138 tube and a host of condensers, resistors, etc. 40/- each; 5/6 carriage and packing.

METAL RECTIFIERS, etc.

12 v. 1 amp., 1/6; 2 v. 1 amp., 3/-; 250 v. 45 mA., 0/9; 390 v. 60 mA., 7/8.
 12 v. 1 amp. FW, 4/8; 12 v. 2 amp. FW, 5/8; 12 v. 3 amp. FW, 13/8.
 RM1, 4/8; RM2, 4/8; RM3, 5/8; RM4, 16/-; K3/25, 5/8; K3/40, 7/-; K3/45, 8/2; K3/50, 8/8; K3/90, 9/8; K3/100, 14/8.

HAVE YOU GOT YOUR CATALOGUE?

For the latest edition showing hundreds of bargains send 6d. only in stamps.

TV in The Channel Islands

HOW PRIVATE ENTERPRISE ATTACKED AND SOLVED THE PROBLEM OF RECEPTION
BEYOND THE NORMAL RANGE

THE British Broadcasting Corporation decided five years ago that Jersey, Guernsey, Alderney and Sark were beyond the range of even "fringe" TV reception. The challenge was taken up by Broadcast Relay Service, Ltd., the parent company of the Rediffusion group of companies—who serve about 3,000,000 listeners and viewers throughout the world with daily sound or television programmes by wired network direct into their homes, and either broadcast or relay in over 20 foreign languages or dialects.

It was a problem of the greatest magnitude, for the Very High Frequencies used by television are a "straight line" emission. They do not follow the curvature of the earth's surface and therefore cannot be received—except under freak conditions—by any set or station which is out of what we might term the line-of-sight of the transmitter. The Channel Islands, by virtue of their distance from the English transmitting stations and the natural curvature of the earth, were well beyond the ultimate point at which BBC transmissions could be normally received.

Seventy miles—cited as the average distance over which television could be received, had hitherto decided who would or would not receive TV transmissions anywhere in the world.

Fortunately, Rediffusion have on their staff a number of peculiarly unconventional engineers. On the principle that physical laws, at any rate, are made to be broken, they set out to find the loophole in this one.

And they succeeded. No one can say who was responsible for the first idea that the freak broadcast could be resolved to normalcy, but it was decided that atmospheric conditions which had hitherto caused solely annoying interference could be disciplined to give service.

Tropospheric propagation, which arises where the layer of warm and cool air meets at a height of from one to three miles, is a condition which reflects the Very High Frequency waves used by TV. Rediffusion's technicians endeavoured to "catch" the reflected waves where they come to earth at a spot considerably beyond the "line-of-sight" distance.

Aerial Billiards!

The success of the attempts caused these experts to indulge in a rare form of celestial billiards—and their preliminary work was done in so unlikely a place as the files of the old Channel Island newspapers. If TV signals from England were to be caught in their "freak" form against the tropospheric cushion and neatly pocketed in Jersey, it was necessary to make sure that the "cushion" would be a stable one—and only meteorological information could determine the question.

Fortunately, such conditions between England and Jersey were excellent—and the great experiment bore its first fruit on June 2nd, 1953, when all the pageantry of the Coronation was brilliantly received in Jersey on the 110 sets specially installed in the Island by Rediffusion.

New and very special aerials, together with other

equipment, had been designed, partly by Rediffusion's engineers at the London laboratories and partly by the technicians of the associated company in Jersey, Television Research, Ltd.

Work began on the construction of Rediffusion's Jersey Station—including the setting up of the biggest receiving unit in Britain—and the station was formally opened on June 24th, 1954. The special aerials play a key part in the working of the station, and one of them is set up to pick up the TV programmes radiated from Paris, 200 miles away!

What have been the BBC's reactions to this private pioneering in a field where the Corporation has a monopoly? It has been quite objective. There has been no question of reluctance on the part of the Corporation in acknowledging that Rediffusion's "first there" in the Channel Islands has done what might not otherwise have been done for a long time, if at all.

Senior BBC officials have seen for themselves the quality of reception on the Rediffusion screens in Jersey; one of them said "We are extremely interested, particularly in the standard of picture obtained from such weak and variable signals."

Now the Corporation has made concrete acknowledgment of Rediffusion's success by asking the Company for co-operation in the establishment of the BBC's own direct Channel Islands Service.

A pilot BBC unit has been set up in Guernsey to pick up all transmissions from Wenvoe and later from the newest transmitter which it is proposed to erect at North Hessary Tor in Devon. At the same time, Rediffusion will monitor these transmissions on Jersey for the BBC. On the result of these co-operative experiments by Rediffusion and BBC engineers will rest the development of the Corporation's service.

Meanwhile, the Rediffusion Group of Companies are not standing still. As soon as the new French TV transmitters—now being built near the French coast—are—in operation, Rediffusion will give its Jersey viewers the first-ever alternative programmes. By turning a knob the subscriber will be able to select either the British or the French programmes—and the Commercial broadcasts as well when they come into being!

The choice will be available every day and is a notable step forward from the present rare and complicated "Eurovision" programmes.

Just how good is Jersey's Rediffusion service?

A Jersey hotelier who subscribes to the Rediffusion TV service complained that the reception was not as good as he thought it ought to be... but a visiting holidaymaker from Britain silenced his complaints for ever.

"Why," said the visitor, "it is much clearer than we get at home—and we are only 15 miles from the Sutton Coldfield transmitter!"

Technical Data

The first cable laid used for TV signals was 12 gauge unscreened quad in sections with two 22 gauge

quads for the sound (four programmes). On test the 22 gauge cable failed completely owing to mechanical damage.

For subsequent demonstration purposes the television signals were fed to Bouley Bay over a two quad (16 gauge) cable unscreened for a distance of $1\frac{1}{2}$ miles. Carrier frequency was 45 Mc/s and four Baird amplifiers were employed with long time constant automatic gain control fitted to these amplifiers. The same method is still used, not the synchronised pulse scheme, and has been found quite satisfactory, and it is understood that the Development Department are now using the same method for some repeaters.

The variation of attenuation with weather was too great at 45 Mc/s, and one cable was replaced with 18 gauge aluminium quad and this is still working. The signals were fed at the carrier frequency at 45 Mc/s for a period of 12 months. Carrier frequency was then changed to 9.72 Mc/s and this frequency was used for the Coronation demonstrations.

Vision signals were fed on one-pair of the screened cable and the mains supply for four repeaters working at 45 Mc/s phantomed over the quad. These repeaters operated at a 30db gain. Each pair of each cable carries an A.F. programme at 45 volts, one programme being TV sound.

Vision signals are now fed at 9.72 Mc/s with only one three valve repeater with the mains supply phantomed.

With regard to the tilted wire aerial arrays, these were in two sets, one for Sutton Coldfield Station and one for Alexandra Palace Station, and automatic diversity reception was employed. Interference was so strong, however, from continental transmitters, that the scheme of automatic diversity reception proved unsatisfactory and the switching was then done manually. The present installation comprises three sets of tilted wire arrays beamed on Alexandra Palace, Wenvoe and Paris.

Diversity was originally at 45 Mc/s with a converter to change the 61.5 to 45 Mc/s.

Repeaters

For feeding the signals to St. Helier, repeaters were designed and used similar to the scheme employed at Thanet where the carrier frequency is now 9.72 Mc/s.

The repeaters for the seven mile link were designed with negative feedback in the output stages and not only gave a bandwidth of at least 7 Mc/s but enabled the output stage to function at its optimum load and be independent of quite wide variations of the 12 gauge unscreened cable characteristics. This cable is buried in ground which is literally lying in water at certain times of the year and at others in completely dry earth.

The variations in the magnitude of characteristics impedance are from 53 to 90 ohms with a considerable variation in the phase angle.

At the aerial there are two A154 low-noise amplifiers in cascade for each signal followed by an RG109 frequency changer. A power output stage made in Jersey design provides 16 volts into the link. There are seven repeaters, the last of which is in Colomberie Close.

The link is built up as follows:—

To first repeater—2,000 yds. underground 12 gauge aluminium.

To second repeater—1,600 yds. underground 12 gauge aluminium.

To third repeater—600 yds. 12 gauge unscreened joined to 900 yds. of 18 gauge screened.

To fourth repeater—1,200 yds. of 12 gauge unscreened:

To fifth repeater—1,200 yds. of 12 gauge unscreened.

To sixth repeater—1,760 yds. of 18 gauge screened.

To seventh repeater—1,760 yds. of 18 gauge screened.

This link was used throughout for the Coronation demonstration. The penultimate 1,760 yds. was laid in a sewer, and the last 1,760 yds. partly in a brook and partly under the street in a duct.

Since the Coronation, mechanical faults have developed on 1,200 yds. of the first 12 gauge section, and since Rediffusion was not allowed to dig up the road it has been replaced with a catenary supported overhead 18 gauge copper squad mounted on the Electricity Company's poles.

The overhead cable allows for feeders to other parts of the island also for subscribers' connections *en route* to Colomberie Close. The Carrier scheme had been abandoned. A 22 s.w.g. quad will be added to the squad for country areas, and the four A.F. programmes amplified in the subscribers' units.

For distribution in St. Helier it was eventually decided to use unscreened squad for the drop-ins, and also for sections of the network, while for other parts copper screened quad would be used.

The feeder repeaters are TV31s—a 3 valve small repeater in a housing giving 4-watts output. These cost £36 including power pack, housing and sound by-pass units.

For unscreened drop-ins the signal has to be 100 millivolts, and for screened drop-ins 20-40 millivolts at the subscribers unit. All the terminal units have only one I.F. valve. In St. Helier the sound distribution is at audio.

A four programme unscreened network was in existence so a squad was added to the quad. At the ends of spurs lengths of up to 200 yds. of existing unscreened squad were used for the TV feed. Chokes were not put in for the non-TV subscribers, who just had the "D" programme drop-in disconnected. By using this method there was a considerable saving in cost of blocking chokes.

All the inserts were designed and made locally. The terminal units are made by Felgate Radio modified to the Jersey design on 9.7 Mc/s, 100 of these with 12in. tubes were used for the Coronation, while 14in. and 17in. diameter tubes also from Felgate will be used in the future.

Outside St. Helier, all the cabling is to be run on the Electricity Company's poles using an amplified audio system. The network consists of one 22 s.w.g. quad and one squad. As feeders of up to 12 miles length are needed, audio is amplified in the subscribers' unit.

It is anticipated that there will be three Rediffusion programmes and two TV sound programmes. Four of these will be at audio, and one either phantomed or using a 50 Kc/s carrier. The terminal units for this scheme are now being designed, and a high gain vision repeater has been designed for pole mounting with A.G.C.

A SIMPLE T.V. "Scope"

DETAILS FOR THE CONSTRUCTION OF AN INEXPENSIVE OSCILLOSCOPE FOR TV

By B. L. Morley

An oscilloscope is one of the most useful test instruments which the TV constructor can possess, indeed for the experimenter—a first-class multimeter and an oscilloscope can be regarded as essential.

It is not necessary to have an elaborate instrument; provided the linearity is good, amplification is sufficient to cater for the voltage waveforms usually found in TV, and the range of frequencies covered extends from below the frame frequency to above that of the line, nothing more is required.

The instrument described here possesses all these features and has the added advantage of being quite inexpensive. If every item has to be bought, then the total cost should not be much more than £7 and by use of the spares box and ex-Government equipment it can be lower than this.

Factors Governing the Design

When designing the instrument the points mentioned previously were considered and it was decided to keep the cost as low as possible, so that the instrument would become available to as many as possible. This feature has not been achieved by sacrificing efficiency and the constructor will find that it is quite capable of doing all that is required. Linearity is good and also the amplification, yet only two valves are employed with a 6in. C.R.T.!

The prototype employed a VCR97, but a VCR517 could be used equally successfully. There are available a number of 3in. C.R.T.s on the ex-Government market, but it was decided to use the 6in., first because there are many constructors

who have started TV work with this type of tube and now, having changed over to magnetic working, have a spare tube, and secondly because there are quantities of VCR97 tubes which suffer from cut-off and which cannot therefore be used for TV but can be used in a 'scope.

The prototype was constructed from an Indicator unit type 6H simply because it was available. The Indicator is not strictly necessary and, provided the general layout scheme is adhered to, any form of chassis can be employed.

The use of the Indicator can reduce the cost because they can often be purchased, less valves and C.R.T., very cheaply; the prototype was bought for 2s. 6d., but this was, of course, exceptional. As only two EF50 valves are required and a cut-off type of tube can be used, it is clear that a very cheap instrument can be built.

So much for the economic considerations; another important factor ruling the design was simplicity of circuitry and construction. Every effort has been made to cut out superfluities; the result is what one might term a basic oscilloscope; it performs its functions adequately but is devoid of frills. Each component pulls its full weight and nothing has been left in which can possibly be left out.

The beginner has not been forgotten. Quite often it is he who requires an oscilloscope most, and in order to assist him wiring diagrams have been given.

In order to simplify the printing of wiring diagrams in a small space, the various sections have been separated and each can be built as a complete section in its own right.

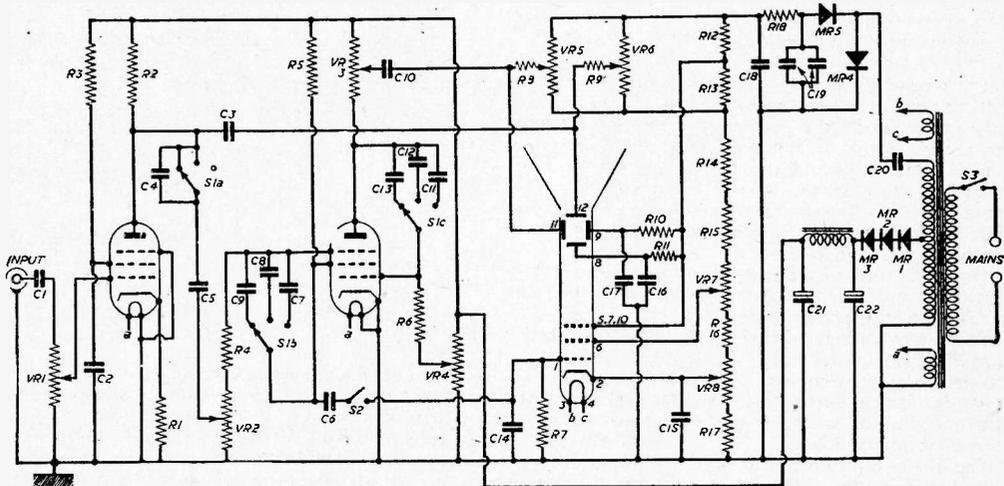


Fig. 1.—Complete theoretical circuit of the TV 'scope.


The Circuit

Fig. 1 shows the circuit diagram.

It can be analysed into four sections—the amplifier, the oscillator, the C.R.T. network and the power supply, and they will be dealt with in that order.

The input to the 'scope is made via a Pye socket feeding into a potentiometer via the coupling condenser C1. The condenser will be found suitable for the three ranges covered by the 'scope, but other values can be added in series with the lead, if desired.

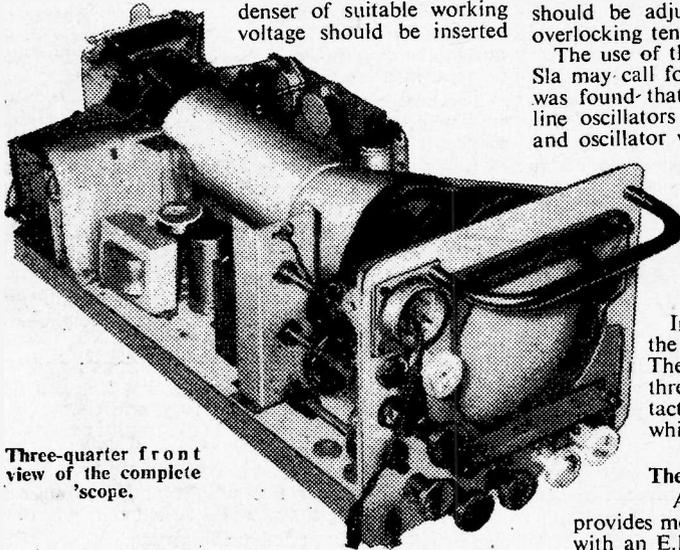An important point to note is that when testing high voltage circuits (such as examining the ripple of the E.H.T. supply) a condenser of suitable working voltage should be inserted



Three-quarter front view of the complete 'scope.

in series with the input lead. C1 has been given a working voltage rating of 450 volts and this should be suitable for most requirements.

VR1 is the amplitude control and the signal input to the amplifier valve V1 is fed through it. The control will cater for most inputs found in the TV receiver, but if it is found that the control is crowded at one end, then suitable attenuators can be applied prior to the input.

V1 is an EF50 and is used because it was available. The constructor is advised to use one of the British type as an expensive red Sylvania is not really necessary here.

The bias resistor R1 is left undecoupled and provides an improvement in the linearity by reason of negative feed-back. It will be found that the linearity is very good.

Note that screened cable (a short section of coaxial will do) is used

to couple C1 to the control, and the control to the grid of the valve. This should not be omitted.

The coupling condenser to the deflector plate C3 has a working voltage of 1.5 Kv. and this is the minimum working voltage allowable.

V2 is the oscillator which provides the horizontal sweep; in order to effect synchronisation between the circuit being examined and the oscillator, a sync control has been fitted. It is accomplished by taking a portion of the output from the amplifier valve V1 and injecting it into the suppressor of V2 via the variable control VR2.

The latter control serves to lock the sync and it should be adjusted so that the trace just locks; overlocking tends to distort the trace.

The use of the condenser C4 in conjunction with S1a may call for comment. As the circuit stands, it was found that on the higher frequencies covering line oscillators the coupling between the amplifier and oscillator was too great, resulting in distortion of the trace. The coupling is, therefore, reduced by C4 which comes into series with C5 when the coarse frequency control is in its highest frequency position. As S1 is the coarse frequency control, the operation becomes automatic.

In the prototype (using the indicator) the existing switch provides this facility. The switch in these units is a two-pole, three-position type of Yaxley and the contacts above the chassis were used for S1a while those below were used for S1b and c.

The Oscillator

A standard Miller oscillator is used and provides more than adequate scan in this circuit with an E.H.T. of over 1,500 volts. In order to obtain full width it is important to adhere to the component values given.

The frequency is controlled by the coarse control which may be referred to as a band selector, dividing

COMPLETE LIST

Condensers

C1—0.1 μ F 450 v.
C2—0.1 μ F
C3—0.1 μ F 1.5 kV.
C4—100 pF
C5—0.001 μ F
C6—50 pF
C7—300 pF
C8—3,000 pF
C9—0.05 μ F
C10—0.1 μ F 1.5 kV.
C11—100 pF
C12—0.001 μ F
C13—0.01 μ F
C14—0.001 μ F
C15—0.01 μ F
C16—0.01 μ F 1.5 kV. (or 2.5 kV.)
C17—0.01 μ F 1.5 kV. (or 2.5 kV.)
C18—0.01 μ F 2.5 kV. (or 3 of 0.03)
C19—(2) 0.03 μ F, 2.5 kV. (or 1 of 0.1)
C20—0.1 μ F, 750 v. minimum.
C21 }
C22 } 32+32 μ F 450 v. wkg.

All condensers 350 v. wkg. unless stated otherwise.

Resistors

R1—180 Ω	VR
R2—10 k. 1 w.	VR
R3—10 k.	VR
R4—27 k.	VR
R5—47 k.	VR
R6—470 k.	
R7—220 k.	VR
R8—2.2 m. 1 w.	
R9—2.2 m. 1 w.	VR
R10—2.2 m. 1 w.	
R11—2.2 m. 1 w.	
R12—100 k.	
R13—100 k.	
R14—470 k.	
R15—2.2 m. 1 w.	
R16—220 k.	
R17—100 k.	
R18—470 k. 1 w.	

All resistors $\frac{1}{2}$ w. rating unless stated otherwise.

the frequency range covered by the instrument into three bands. The control operates on the forward stroke by C11, 12 and 13, and on the flyback by C7, 8 and 9. A fine control over the selected frequency is effected by VR4.

The operation is to select the frequency band by S1 and to use VR4 to select the actual frequency within that band.

Frequencies covered in each band will depend to some extent on the tolerances of the components used, but the range will be approximately: Position (1), 10-60 cycles per second; Position (2), 50-2,500 cycles per second; Position (3), 2,250-12,000 cycles per second.

Overlapping takes place in each band, therefore both line and frame frequencies of the TV receiver are covered.

One disadvantage of the circuit is that the simplification has introduced a little non-linearity on the bottom of each band covered; however, as overlapping takes place the top portion of the preceding band should be used and this will be found to be perfectly linear. As an example, the top of Band (1) will give one complete cycle of the frame oscillator and a true representation of the waveform is obtained; the bottom of Band (2) will also give the same conditions but the trace is a little distorted. No distortion takes place beyond the overlapping portion of each band.

Coupling from the oscillator to the deflector plate is made via C10; as in the case of C3 the working voltage quoted is the minimum and a higher-rated component can be used.

The signal to the deflector plate is taken from the slider of VR3 which is the anode load resistor of V2. This alters the amplitude applied to the plate and, therefore, becomes the width control.


Note that under no circumstances must R6 be omitted or full H.T. may be placed on the grid of the valve.

A small coupling condenser C6 has been fitted to

the suppressor grid of the oscillator and the grid of the C.R.T., the connection between the two points being made via a switch S2. This provides an additional negative pulse to the C.R.T. during the flyback period and has a useful cleaning up effect on the trace when using the highest band.

It would have been possible to provide the facility for each band covered by arranging further condensers to be switched by an extra section on the coarse frequency control, but this was not considered necessary as no trouble was experienced on the lower bands.

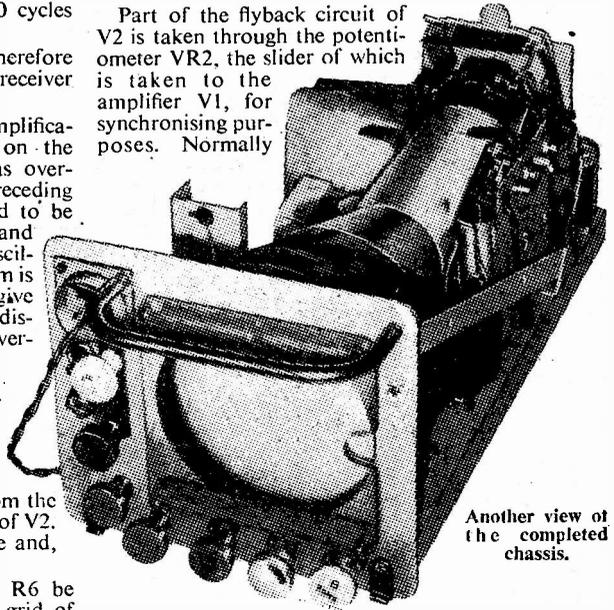Part of the flyback circuit of V2 is taken through the potentiometer VR2, the slider of which is taken to the amplifier V1, for synchronising purposes. Normally



Another view of the completed chassis.

the control should be kept at the minimum position and only used to lock the trace.

OF COMPONENTS

Potentiometers

- 1—Amplitude, 1 M. carbon
- 2—Sync, 25 k. ww. or carbon
- 3—Width, 100 k. carbon
- 4—Fine freq., 2 m. carbon
- 5—Shift U/D, 100 k. carbon, pre-set
- 6—Shift L/R, 100 k. carbon, pre-set
- 7—Focus, 500 k. carbon
- 8—Brilliance, 100 k. carbon

Valves and Rectifiers

- V1—EF50
 V2—EF50
 MR1—SenTerCel K3/40
 MR2—SenTerCel K3/40
 MR3—SenTerCel RM1
 MR4—SenTerCel RM1
 MR5—SenTerCel RM1.

Miscellaneous

- Mains Transformer: 350-0-350 v. 30±80 mA, 6.3 v. 1-4 A.
 Lasky MBA/3—5 v. tapped 4 v. 1.5-3 A.
 (Minimum and maximum current ratings)
 Smoothing Choke—10 Henry, 30 mA. minimum
 Cathode Ray Tube—VCR97, VCR517 (can be types with cut-off)
 Yaxley Switch—3-way, 3-pole, 3-bank
 Two on/off toggle switches
 One Pye socket and plug
 7 Knobs.
 2 B9G valveholders
 One C.R.T. holder
 10-Way resistance panel
 One 3-way tag strip
 Two 2-way tag strip
 Two yards twin flex for mains, 2 yards coax cable, wire bolts, etc.

C.R.T. Network

The network follows standard principles and employs E.H.T. with negative earthing. Some oscilloscopes employ a positively earthed system so that the deflector plates are available for external connection. It was decided that such a facility was not necessary in this instrument and the simplification obtainable with negative earthing was the more important factor.

Centralising of the trace on the screen is accomplished by the two shift controls VR5 (up/down) and VR6 (left/right). Some oscilloscopes bring these controls out to the front panel but it was not

considered necessary in this model, so pre-set controls were used.

The constructor may, if he desires, bring the controls out to the front panel but care must be taken thoroughly to insulate the wire.

C16 and 17 balance the vertical and horizontal scans and greatly assist in preventing the trace from creeping with the operation of the brilliance control.

The Power Supply

The power supply has been so arranged that standard components can be used.

The key-piece is naturally the transformer and while the current requirements are small the voltage is high. The minimum requirements are 350-0-350 at 30 mA, 6.3 volt 0.6 amp and 4 volt 1.5 amp. A transformer meeting these requirements exactly is not available so a near substitute must be employed.

There is H.T. current and heater current which is above the requirements but this makes no difference to the operation of the circuit.

Other makes of transformers can be used provided that current outputs are at about these figures and the voltages are as specified.

The 5-volt winding is tapped at 4 volts and is normally used for the rectifier; and in this circuit we use it for the C.R.T. heater. The 350-0-350 volt winding is used for H.T. and E.H.T. in the same manner as the "Simplex" television, using half-wave rectification for the normal H.T. and a Cockroft-Walton multiplier section for E.H.T.

The H.T. is rectified by three SenTerCel RM1 rectifiers in series and the current is smoothed by the 10 Henry choke and C21/22. The choke must be rated at 30 mA minimum and the one specified for the "Simplex" can be used.

C21/22 can be a combined condenser, although separate condensers can be used if desired. A working voltage of 450 volts is recommended so as to ensure that they will absorb the surge voltage when the instrument is first switched on.

There are available some 350-volt metal rectifiers on the ex-Government market and these can be used if desired.

It is also possible to use a valve rectifier and this method was employed in the prototype, a transformer from the junk box being modified to provide the extra heater winding.

E.H.T. is obtained from the multiplier circuit using two rectifiers, SenTerCel K3/40.

The smoothing condensers in this part of the circuit may call for some explanation. There is a shortage of the popular 0.1 μ F 2.5 kV condensers which are usually employed in this class of circuit, and so the use of alternatives was considered. The condenser C19 was made up of two 0.03 μ F 2.5 kV condensers in parallel, while C18 was a metal-cased 0.1 μ F 2.5 kV. Three 0.03 μ F 2.5 kV can be used in parallel if desired.

Construction

Construction is not at all difficult, and although an Indicator Type 6 was used in the prototype, the scope can be built up on a new chassis.

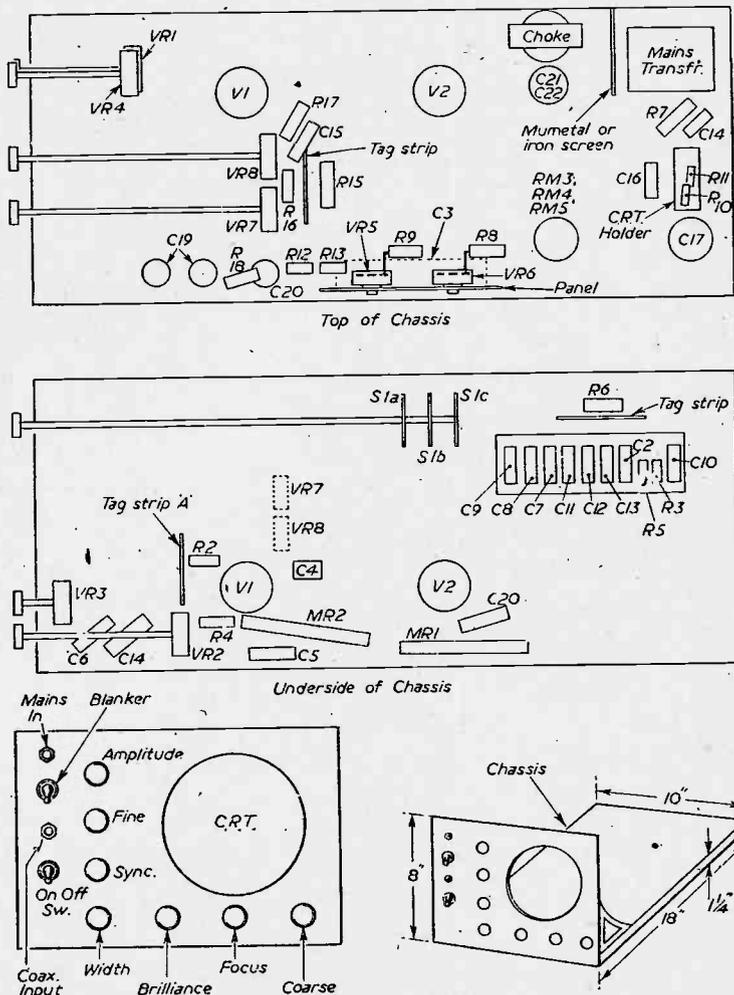


Fig. 2.—Details of the layout and positions of the main components.

THE NATIONAL

August 24th to
September 4th

RADIO SHOW

List of Principal Exhibitors
in Alphabetical Order,
with Stand Numbers

Name	Address	Stand No.	Name	Address	Stand No.
Aerialite, Ltd. ...	Castle Wks., Stalybridge, Cheshire	64	English Elec. Co., Ltd.	Marconi Hse., Strand, W.C.2	85
Antiference, Ltd.	Southern Rd., Bicester Rd., Aylesbury, Bucks.	34	Ever Ready (G.B.), Ltd.	Hercules Place, Holloway, N.7	66
Argosy Radio-vision, Ltd.	Argosy Wks., Hertford Rd., Barking, Essex	8	Ferguson Radio Corp., Ltd.	105, Judd St., London, W.C.1	14
Associated Technical Mfg., Ltd.	Vincent Wks., New Islington, Manchester, 4	25	Ferranti, Ltd. ...	Hollinwood, Lancs.	58 & 76
Automatic Coil Winder & Elec. Equip. Co., Ltd.	Winder House, Douglas St., S.W.1	61	Fitton, Ltd., R. N. (Ambassador Radio)	Princess Wks., Brighouse, Yorks.	41
Bakombé, Ltd., A. J.	52, Tabernacle St., London, E.C.2	35	Garrard Eng. & Mfg. Co., Ltd.	Newcastle St., Swindon, Wilts.	71
Belling & Lee, Ltd.	Cambridge Arterial Rd., Enfield, Middx.	67	General Elec. Co., Ltd.	Magnet Hse., Kingsway, W.C.2	68
Bowmaker, Ltd. ...	Bowmaker Hse., Lansdowne, Bournemouth	47	Gibbs, Ltd., Herbert E.	First Ave., Montague Rd., Edmonton, N.18	20
British Broadcasting Corporation	Broadcasting Hse., London, W.1	200	Goodmans Industries, Ltd.	Axiom Wks., Wembley, Middx.	63
Brown Bros., Ltd.	Browns Bldgs., Gt. Eastern St., E.C.2	91	Gramophone Co., Ltd.	Head Office, Hayes, Middx.	10
Bulgin & Co., Ltd., A. F.	Bye Pass Rd., Barking, Essex	99	Hartley Baird, Ltd.	Lancelot Rd., Wembley, Middx.	88
Bush Radio, Ltd.	Power Rd., Chiswick, W.4	86 & 89	Hobday Bros., Ltd.	21, Great Eastern St., E.C.2	78
Chald Products, Ltd.	184, Low Rd., Leeds, 10	26	Hunt (Capacitors), Ltd., A. H.	Bendon Valley, Garratt Lane, S.W.18	90
Champion Elec. Corp.	Champion Wks., Drove Rd., Newhaven, Sussex	33	Iliffe & Sons, Ltd.	Dorset Hse., Stamford Street, S.E.1	45
Cole, Ltd., E. K.	Ekco Wks., Southend-on-Sea, Essex	22 & 92	Invicta Radio, Ltd.	Radio Wks., 79, Parkhurst Rd., Holloway, N.7	94
Collaro, Ltd. ...	Ripple Wks., Bye Pass Rd., Barking, Essex	11	J. B. Mfg. Co. (Cabinets), Ltd.	86, Palmerston Rd., London, E.17	18
Co-operative Wholesale Society, Ltd.	Exhibition Section, 99, Leman St., E.1	106	J. Beam Aerials, Ltd.	Cleveland Wks., Weedon Rd., Northampton	31
Cosmocord, Ltd.	700, Gt. Cambridge Rd., Enfield, Middx.	44	Keith Prowse & Co., Ltd.	159, New Bond St., London, W.1	1
Cossor, Ltd., A. C.	Cossor Hse., Highbury Grove, N.5	57	Kolster - Brandes, Ltd.	Footseray, Sidcup, Kent	70
Decca Record Co., Ltd.	1-3, Brixton Rd., London, S.W.9	39	McMichael Radio, Ltd.	190, Strand, London, W.C.2	72
Dubilier Condenser Co. (1925), Ltd.	Ducon Wks., Victoria Rd., North Acton, W.3	83	Marconiphone Co., Ltd.	Head Office, Hayes, Middx.	13
Dynatron Radio, Ltd.	The Firs, Castle Hill, Maidenhead, Berks.	103	Masteradio, Ltd.	10/20, Fitzroy Place, N.W.1	62
E.M.I. Sales & Service, Ltd.	Head Office, Hayes, Middx.	9 & 73	Mullard, Ltd. ...	Century Hse., Shaftesbury Ave., W.C.2	56
Econasign, Ltd. ...	92, Victoria St., London, S.W.1	23	Multicore Solders, Ltd.	Multicore Wks., Maylands Ave., Hemel Hempstead, Herts.	100
Edison Swan Elec. Co., Ltd.	155, Charing Cross Rd., W.C.2	37	Murphy Radio, Ltd.	Welwyn Garden City, Herts.	40
Electric Audio Reproducers, Ltd.	17, Little St. Leonards, Mortlake, S.W.14	49			

Name	Address	Stand No.	Name	Address	Stand No.
Nera of England, Ltd.	Jefferies Passage, St., Guildford	High 208	Standard Tel. & Cables, Ltd., (BRIMAR)	Footscray, Sidcup, Kent	6
NEWNES, LTD., GEORGE	Tower House, Southampton St., W.C.2	51	Standard Tel. & Cables, Ltd., (SenTerCel)	10, Essex St., London, W.C.2	82
Pam Radio & T/V, Ltd.	295, Regent St., London, W.1	84	Stella Radio & T/V Co., Ltd.	Oxford Hse., 9/15, Oxford St., W.1	55
Peto Scott Elec. Insts., Ltd.	Addlestone Rd., Weybridge, Surrey	60	Taylor Elec. Insts., Ltd.	419, Montrose Ave., Slough, Bucks.	54
Philco (Overseas), Ltd.	Romford Rd., Chigwell, Essex	36	Telegraph Condenser Co., Ltd.	Wales Farm Rd., North Acton, W.3	101
Philips Elec., Ltd.	Century Hse., Shaftesbury Avenue, W.C.2	96 & 97	Telemechanics, Ltd.	3, Newman Yard, Newman St., W.1	81
Pilot Radio, Ltd.	31/37, Park Royal Rd., N.W.10	59	Tequipment, Ltd.	1319A, High Rd., Whetstone, N.20	80
Plessey Co., Ltd.	Vicarage Lane, Ilford, Essex	28	Telerection, Ltd....	Antenna Wks., St. Pauls, Cheltenham	5
" PRACTICAL WIRELESS " & " PRACTICAL TELEVISION "		51	Trix Electrical, Ltd.	1/5, Maple Place, Tottenham Court Rd., W.1	65
Pye, Ltd.	... Radio Wks., Cambridge	4 & 95	Ultra Electric, Ltd.	Ultra Works, Western Ave., Acton, W.3	69
Radio Gramophone Dev. Co., Ltd.	Eastern Avenue West, Mawneys, Romford, Essex	93	Valradio, Ltd. ...	New Chapel St., Feltham, Middx.	29
Regentone Radio & T/V, Ltd.	Eastern Avenue West, Mawneys, Romford, Essex	38	Vidor, Ltd. ...	West St., Erith, Kent	87
Roberts' Radio, Ltd.	35/37, Creek Rd., East Molesey, Surrey	102	Waveforms, Ltd.	Radar Wks., Truro Rd., N.22	75
Rola / Celestion, Ltd.	Ferry Wks., Summer Rd., Thames Ditton, Surrey	3	Westinghouse Brake & Signal Co., Ltd.	82, York Way, King's Cross, N.1	2
Rudman, Darlington (Electronics), Ltd.	Wednesfield, Staffs	207	White - Ibbotson, Ltd.	52A, Goldhawk Rd., Shepherd's Bush, W.12	98
Simon Equipment, Ltd.	48/50, George St., Portman Square, W.1	104	Whiteley Elec. Radio Co., Ltd.	109, Kingsway, London, W.C.2	105
Sky-Masts	... Beadon Garage, Beadon Road, W.6	30	Wolsey Television, Ltd.	43/5, Knight's Hill, West Norwood, S.E.27	16
Sobell Industries, Ltd.	Langley Park, nr. Slough, Bucks.	12	Wright & Weaire, Ltd.	131, Sloane St., London, S.W.1	74

The G.E.C. Micro-wave Radio Television Link

ONE of the most outstanding technical achievements in the recently inaugurated European television tie-up is the micro-wave radio link spanning the Alps. This link, 125 miles long, runs from Chasseral in northern Switzerland, through a relay station located high up the 15,000ft. Jungfrau, to Monte Generoso in southern Switzerland, and it is the only link between the Italian and German television networks.

The equipment used was supplied throughout by the Coventry Telephone Works of The General Electric Co., Ltd. The order was placed in January by the Swiss firm, Hasler S.A., acting on behalf of the Swiss Post Telegraph and Telephone Administration, and the equipment was installed jointly by the G.E.C. and Hasler S.A. in time for the preliminary Eurovision tests at the end of May.


For the extension of the television network in Switzerland, Hasler S.A. has received an additional order for identical equipment to provide a radio link between Uetliberg, Chasseral, Romont and Dôle,

and the equipment for this project will be made by Hasler S.A. on behalf of the G.E.C.

The link provides a one-way reversible television channel handling television signals with a bandwidth extending to 5.5 Mc/s so that it is suitable for 625-line pictures. It comprises a terminal transmitter and receiver at Chasseral, a relay station on the Jungfrauoch, and a terminal transmitter and receiver at Monte Generoso. The relay station situated 12,000ft. above sea level on the Jungfrauoch is 60 miles from Chasseral and 65 miles from Monte Generoso. The stations are so high that towers are not required.

The system is frequency modulated and operates in the 1,700-2,300 Mc/s band, the two frequencies used in this instance being 1,776 Mc/s and 1,848 Mc/s. Two frequencies are necessary because reception and transmission at the relay station have to take place on different frequencies in order to prevent feedback from the transmitter to the receiver. The link, which is a permanent installation, has been designed so that it requires the minimum of maintenance.

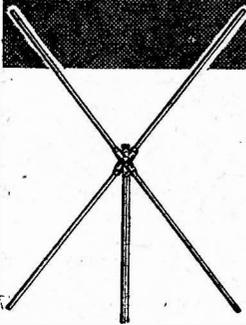The Famous UNEX TELEVISION AERIAL IS NOW ONLY 74'6



The popularity of the Unex has resulted in increased production which has enabled us to reduce the prices substantially. The outstanding features of the Unex are:—

- Easy fitting.
- Robust construction.
- 100% waterproofing.
- 3 dB forward gain.
- Light weight.

Unex 83S. Complete with 6ft. alloy mast, chimney bracket, etc.. £3/14/6.

Unex 83X array only, £2.

Unex 83T complete with 10ft. x 2in. alloy mast, brackets, etc.. £8/15/0.

Unex 83F complete with 14ft. x 2in. alloy mast, brackets, etc.. £7/12/6.

Unex 83C with cranked arm, chimney brackets, etc.. £3/14/6.

Above prices are for all vertical channels and 2/6 extra for horizontal channels.


BAND III

Aerial and downloads will be equally important for Band III reception—we design and manufacture both aerials and cables, so order Aerialite when the time comes.

The DUBLEX High Grade Aerial

The Dublex has the highest gain (6dB) of any aerial in the same price bracket. It has particularly strong mechanical construction with special resilient mountings to prevent element breakage. The Dublex is available with cranked, 7ft., 10ft. or 14ft. chimney mounting masts and brackets.

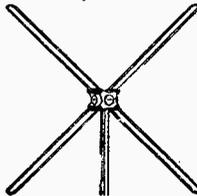Dublex 77S (complete with 7ft. mast, brackets, etc.), £4/8/6.



Aerialite LTD.


CASTLE WORKS STALYBRIDGE CHESHIRE.

NEW! ENLARGED! EXTENDED!

NEWNES

ELECTRICAL ENGINEER'S REFERENCE BOOK

JUST OUT! This rich store of electrical knowledge, written and compiled by 68 specialists, provides authoritative information on new developments and latest practice in all branches of electrical engineering. It gives you wanted information and data immediately—there is no time-wasting or searching through a number of books for facts you must have. Judge the value of the work for yourself, *now*, without cost or obligation.

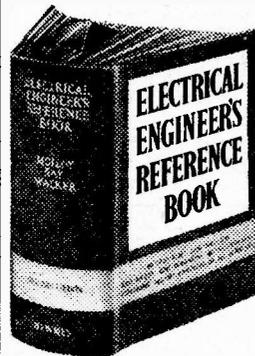

32 Fact-filled Sections including: Theory . Calculations . Power Station Practice . Materials . Transformers . Distribution Motors . Wiring and Installation . Illumination . Measurement . Heating, Ventilation and Air Conditioning . Welding . Electronics . Lifting and Conveying . Electricity in Mines, Agriculture, Horticulture, Aircraft and Automobiles . Progress and Education and Training . Literature . Rules, Regulations.

Many New Sub-sections including: Generators for Hydro-electric Plant . Surge Protection and Testing of E.H.T. Transformers (special reference to 275-kV Super-grid) . Testing Induction and Synchronous Motors.

YOURS for 7 DAYS FREE EXAMINATION

2,184 pages and 32 sections on modern standard practice and latest information on new developments. 2,065 Diagrams prepared by expert draughtsmen. 280 Special Photographs. Strongly Bound in Hard-Wearing Blue Moroquette. Size 7½" x 5". Weight 3½lb.

Do not miss this opportunity of Free Examination in the quiet of your own home. Post the coupon TO-DAY. No cost. No obligation to purchase.

George Newnes, Ltd., 66/69, Great Queen St., London, W.C.2

Please send me ELECTRICAL ENGINEER'S REFERENCE BOOK. It is understood that I may return the work within eight days. If I keep it I will send a first payment of 7s. 6d. eight days after delivery, and 10s. 0d. monthly thereafter, until the sum of £3 17s. 6d. has been paid. Cash price within eight days is £3 12s. 0d.

Name.....

Address.....

Place X where it applies

Occupation.....	<input type="checkbox"/> Houseowner
Your Signature.....	<input type="checkbox"/> Tenant
(Or your Parent's Signature if under 21)	<input type="checkbox"/> Living with Parents
EERB 27	<input type="checkbox"/> Lodging Address

THIS TV. CONSOLE CAN BE YOURS

for **£8.13.0** deposit



THE TELEVISOR CHASSIS

The Televisor is the Practical T.V. Simplex, all components for which we will supply for only £15. The Simplex does not entail converting or adapting ex-Government units and has been designed for construction by the novice. For £15 (carriage 7/6) you would receive all the parts, including 14 valves and VCR517 6in. cathode-ray tube. The metal chassis would be supplied but undrilled. Alternatively these can be drilled for a small extra charge, supplied and prepared.

THE CABINET

The cabinet is our standard Regina which would be supplied with a smaller cutout. This can, of course, be bought separately at £7.17.6, carriage 10/-.

THE INTERNAL ENLARGER system is our special line. It comprises a veneered and polished wooden surround with a specially shaped mask, oil-filled enlarger and four chromed-headed secret fixing screws; it is suitable for any cabinet. Price 39/6, plus postage and packing, 2/6.

The three items above and an 8in. Speaker will be supplied for £25.12.0, or **£8.13.0** deposit, balance over 12 months plus 15/- carriage.

FREE THIS MONTH


Customers spending one pound or more this month will receive, free of charge, a copy of our constructional booklet entitled "The Stroller" (see last month for full details of this fine battery portable which converts into a picnic record player). Alternatively, the booklet is available, price 2/6, which will be refunded if parts purchased.

GRAMOPHONE AUTO CHANGER

COLLARO 3/521

£9.19.6 carriage 7/5

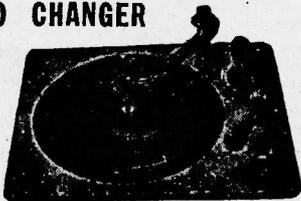The latest three-speed type with the famous "Studio" turn-over pick-up.




SUMMER SALE

Many special bargains will be available at our Branches during July and August. For instance, console cabinets suitable for tape recorders, radiograms, etc., will be available from £7.15.0. It will really pay you to call. If you cannot call, however, send a long stamped-addressed envelope for "Summer Sale List."

19/6

Post 2/-

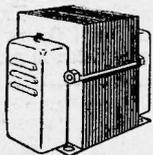


MAINS

TRANSFORMER

Fully shrouded—standard 200-250 v. primary. Sec. 300-0-300, 120 m.a., 6.3-0-6.3 at 4 amps., 2-0-2 at 2 amps.

39/6

Carr. 3/6

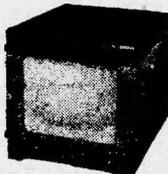

12" TELE-CABINET

Veneered and polished—with glass or perspex front.

THE SUPERIOR 15in.


up to the minute big picture TV. for only £37.10.0. A 20-valve televisor for the amateur constructor, all components, valves and 15in. Cossor Cathode Ray Tube costs £37.10.0, plus £1 carriage and insurance or £12.10.0 deposit and 12 monthly payments of £2.11.6. Constructor's envelope giving full details and blueprint, 7/6. Returnable within 14 days if you think you cannot make the set.



THIS MONTH'S SNIP

THE

"WOLSEY 54"

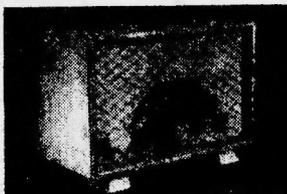

This month you have an opportunity to purchase a really fine ready built modern Superhet at the remarkable price of

£7.19.6 or £3. deposit,

balance over twelve months.

The Wolsey 54 is an A.C. mains Superhet employing latest circuitry covering long- and medium-wavebands in an ultra-modern case with illuminated dial—overall size approximately 11 1/4 x 7 x 8—complete ready to work. Twelve months' guarantee. **THIS OFFER WILL NOT BE REPEATED.**

MULTI-METER KIT

The Multi-meter illustrated measures D.C. volts, D.C. m amps and ohms. It has a sensitivity of 200 ohms per volt and is equally suitable for the keen experimenter, service engineer or student. All the essential parts including 2in. moving coil meter, selected resistors, wire for shunts, 8-point range selector, calibrated scale, stick-on range indicator and full instructions for making are available as a kit, price 15/-, plus 9d. post and packing.




DANCE AMPLIFIER



Powerful three-valve mains amplifier in portable case—10in. speaker in detachable lid, bass and treble controls. £7.10.0 complete, ready to work. Microphone, 12/6 extra.

MINIATURE PORTABLE TV.

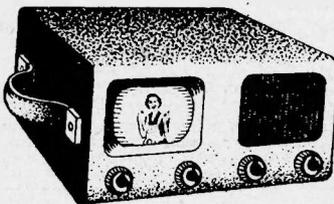

You can probably think of many other reasons when you may need a midget televisor, but it will certainly be useful when—

- (a) Someone is ill, or confined to another room.
- (b) Your big TV fails.
- (c) You want to alter or adjust your big TV.
- (d) The commercial programmes start.
- (e) Servicing an aerial installation.

The Elprez Miniature Televisor uses standard conventional circuitry, employing a total of 13 valves and 2 crystal diodes. The cathode-ray tube used is a 2in. crystal type VCR13-9A, which has a standard equivalent and will therefore always be obtainable. The layout is extremely clean, straightforward and professional. The wiring, whilst naturally being a little more intricate due to miniaturisation, is nevertheless completely accessible, and very good results have been obtained. The

total cost, if you have to buy every part, would come to £16-£17, but you may have many of the components already in stock as only standard conventional components are used. A carrying case, similar to the artist's illustration above, will be available shortly. Its size will be approximately 9in. x 8in. x 6in. (internally). Full construction data, layout, diagrams, templates, etc., running into some 50 sheets, is available, price 5/-, post free.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 5, RUISLIP.

Personal shoppers, however, can call at:

42-48, Windmill Hill, Ruislip, Middx.
Phone: RUISLIP 5780
Half day, Wednesday.

152-3, Fleet Street, E.C.4.
Phone: CENTRAL 2983
Half day, Saturday.

29, Stroud Green Road, Finchbury Park, N.4.
Phone: A.R.C. Way 1919
Half day, Thursday.

TELENEWS



Television Licences

THE following statement shows the approximate number of television licences issued during the year ended May, 1954. The grand total of sound and television licences was 13,479,308.

Region	Number
London Postal	963,754
Home Counties	363,461
Midland	650,729
North Eastern...	449,406
North Western	472,726
South Western	146,006
Wales and Border	166,512
Total Eng. and Wales	3,212,594
Scotland	154,346
Northern Ireland	12,426
Grand Total	3,379,366

Sets From Shrewsbury

HARTLEY-BAIRD LTD., the new company formed by the merging of the Shrewsbury firm of Hartley Electromotives Ltd. and Baird Television Ltd., have started production of television sets in one of the recently built factories in Shrewsbury.

Radar Spots Waterspout

AN unusual report has been received by The Marconi International Marine Communication Co. Ltd., concerning the "Radiolocator IV" radar installed on board the 12,340-ton tanker *Caltex Tanganyika*.

On a recent Atlantic crossing an echo resembling that given by a squall was observed on the radar screen at a distance of seven miles, although the weather was fine and clear with no cloud in the area to warrant any squalls. The explanation was seen about half an hour later when a waterspout was observed to be forming in the position where the supposed squall had originally been plotted.

That Extra Pound

THOUSANDS of licence holders received a shock when they tried to renew their licences on the last day in May.

G.P.O. counter clerks informed them that new licences could only be taken out on the day following expiration, so that licences expiring on May 30th could be renewed on May 31st at the old rate of £2, but those expiring on May 31st were not due for renewal until June 1st, when the additional £1 was charged. Hundreds of complaints were received at the Post Office headquarters about the manner in which the scheme had been handled.

Brazil Buys Equipment

BRITISH progress in the South American television market has taken another important step forward with a recent shipment to


Brazil of a complete set of sound and vision equipment for a large television studio.

The equipment, which includes four television camera channels, a vision mixer and associated equipment, was consigned by Marconi's Wireless Telegraph Co. Ltd., to Radio Televisao Difusora in Sao Paulo, the main industrial centre of Brazil.

"Stars at Blackpool"

THE second programme to be televised this summer under the above title will be on September 15th under the production of Barney Colehan.

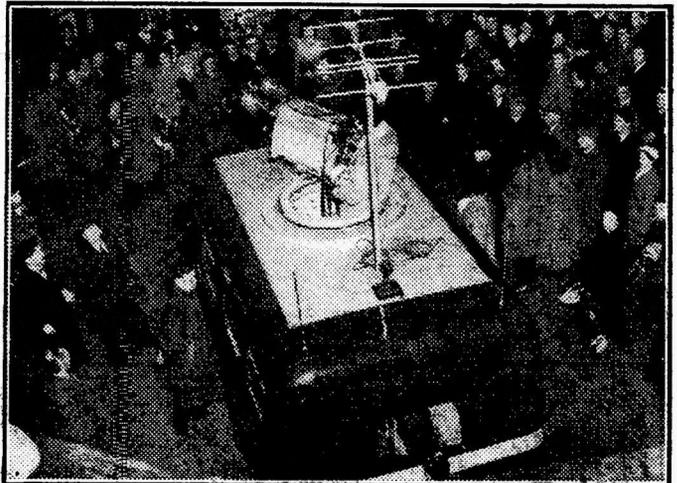The broadcast offers many hazards because when the TV programme is being presented between 8.25 and 9.25, all the artists taking part are appearing in one of the 14 current shows in Blackpool. It is necessary, therefore, to juggle with the running order to put the artists on when they have a free period from their



The BBC television "roving-eye" camera unit is seen on another of its journeys round London, bringing pictures of crowded streets and bright shop window displays to the viewer at home by the fireside.

own theatre. It is not unusual for one artist to be appearing in the television show while another is arriving and a third still performing at his or her own theatre.

Band III Reception

R.E.C.M.F. and B.R.E.M.A. have jointly agreed to recommend the standardised use of a single input of 75 ohms for both

problem for the G.P.O. technicians; they find that it's hardly practicable to fit a suppressor to every single bell.

Manchester Studios

WE learn that the BBC intends to adapt premises in Dickenson Road, Manchester, to serve as television studios for the North Region.

The studios are the first to be situated outside London and will be used until new headquarters are built. All cameras and control equipment will be of the mobile type until permanent equipment becomes available.

Isle of Wight Station

THE Rowridge television transmitter on the Isle of Wight is expected to come into operation some time in November. As soon as the mobile transmitter and cameras become available it is hoped that outside events on the island can be televised including many of the yachting fixtures at Cowes.

Big Screen at Luncheon


LARGE-SCREEN TV was used at a recent big Harrogate luncheon to enable guests at one end of the large banquetting hall to see and hear speakers at the top table as if they were seated but a few yards away.

The luncheon was held at the Majestic Hotel for over 700 people. The closed circuit transmission projected a picture on to a 12ft. by 9ft. screen by arrangement with Cintel, Ltd.

"Coin-in-the-slot" Receivers

IT is possible that "coin-in-the-slot" television receivers will arrive on the British market this year.

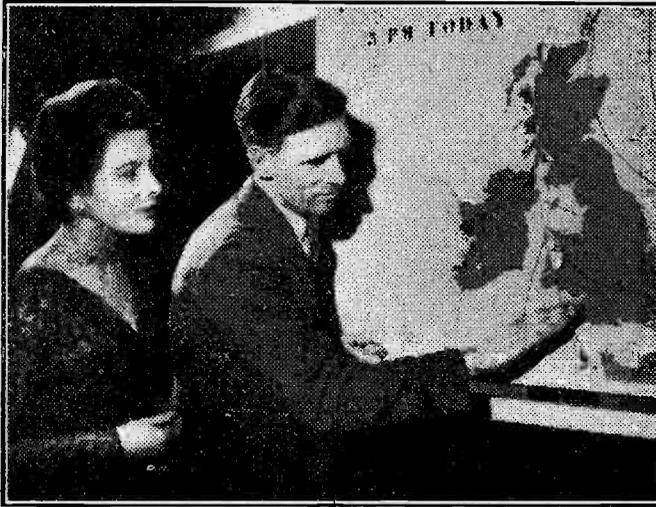The first of this type of set has been installed in a California home. It offers the viewer a list of films together with the charge that is being made to view them. The customer selects the film he wishes to see and inserts the necessary money in a slot on the side of the set.



Forecast Officer T. H. Clifton, of the Air Ministry Meteorological Office, one of the forecasters who appear each evening and, with the aid of maps, show the current weather trends. With him is Noëlle Middleton, television announcer.

Television's Hollywood

MR. D. GAMMANS, Assistant Postmaster-General, told the House of Commons recently that he foresaw "tremendous developments" in the field of television and had visions of Britain becoming the "Hollywood of the television world."

"There is so much talent in this country," he continued, "that if we do not adopt a too restrictive attitude and do not try to protect British films because they are British films, we have our opportunity."

Transatlantic Agreement

THE British Broadcasting Corporation and the National Broadcasting Company have concluded an exclusive exchange agreement concerning Television News film. The agreement will come into operation on December 1st next.

Band I and Band III. This follows technical discussions between the two associations.

It is recognised that this single input is a long-term standard to which both receiver and aerial manufacturers will work, but that in the interim period there will be some installations for which two inputs will be necessary.

Bells Cause Interference

LUTON buses have all had television suppressors fitted to their windscreen-wipers following three years of experiments by Post Office engineers.

A new problem has been brought to their attention, however, by television viewers living along bus routes in the town who complain that every time a bell is rung on a bus, their TV sets emit a buzzing noise and a flash appears on the screen. This is certainly a real

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

RADIO SUPPLY CO. (LEEDS) LTD. Dept. N., 32, THE CALLS, LEEDS, 2.

Post Terms C.W.O. or C.O.D. No. C.O.D. under £1. Postage 1/1 charged on orders up to £1: from £1 to £3 add 1/9; over £3 post free. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 5d.; Trade List 5d.

R.S.C. MAINS TRANSFORMERS (GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v 50 c/s Screened.

TOP SHROUDED, DROP THROUGH

250-0-250 v 70 ma. 6.3 v 2.5 a	12/11
250-0-250 v 70 ma. 6.3 v 2 a, 5 v 2 a	15/11
350-0-350 v 80 ma. 6.3 v 3 a, 4 v 2.5 a	15/11
350-0-350 v 80 ma. 6.3 v 2 a, 5 v 2 a	17/6
250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a	23/11
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a	23/11
350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a	29/11

FULLY SHROUDED UPRIGHT

250-0-250 v 60 ma. 6.3 v 2 a, 5 v 2 a. Midget type. 2 1/2-3 in.	16/9
250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a	25/9
250-0-250 v 100 ma. 6.3 v 6 a, 5 v 3 a, for R135 Conversion	29/9
300-0-300 v 100 ma. 6.3 v 4 a, 5 v 3 a	25/9
350-0-350 v 70 ma. 6.3 v 2 a, 5 v 2 a	18/9
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a	23/9
350-0-350 v 150 ma. 6.3 v 4 a, 0-4-5 v 3 a	33/9
350-0-350 v 250 ma. 6.3 v 6 a, 4 v 8 a, 0-2-6 v 2 a, 4 v 3 a, for Electronic Engineering Television	69/6
425-0-425 v 200 ma. 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a, suitable Argus Television, etc.	49/9
450-0-450 v 250 ma. 6.3 v 6 a, 6.3 v 6 a, 5 v 3 a	69/6

FILAMENT TRANSFORMERS

All with 200-250 v 50 c/s Primaries: 6.3 v 1.5 a, 5/9; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 9/11; 6.3 v 6 a, 17/9; 230-250 v Input 4 v 2 a, 5/11.	
---	--

CHARGER TRANSFORMERS

200-250 v 0-9-15 v 3 a, 16/9; 0-9-15 v 6 a, 22/9	
--	--

OUTPUT TRANSFORMERS

Standard Pentode 5000 to 3 ohms	4/9
Standard Pentode 7000 to 3 ohms	4/9
Standard Pentode 10,000 to 3 ohms	2/11
Small Pentode 5000 to 3 ohms	3/9

E.H.T. TRANSFORMERS 200-230-250 v

2,500 v 5 ma, 2-0-2 v 1.1 a, 2-0-2 v 1.1 a, for VCR97, VCR517, ACRX	39/6
5,000 v 5 ma, 2 v 2 a	39/6

SMOOTHING CHOKES

250 ma 3 h 100 ohms	11/9
100 ma 10 h 200 ohms Potted	9/6
100 ma 10 h 350 ohms	9/6
60 ma 10 h 400 ohms	4/11

CO-AXIAL CABLE 1/4 in.

75 ohm 14/36	101 yd
Twin Screened Feeder	70 yd

TV. PREAMPLIFIER. For Fringed Screens

Brand New. Complete with 6F13 valve. Only 22/6.

SELENIUM METAL RECTIFIERS.

RM2 125 v 100 ma, 4/9; RM4 250 v 250 ma, 11/9; RM3 125 v 120 ma, 5/9; G.E.C. 300 v 250 ma, 12/9; 120 v 40 ma, 3/9; 6/12 v 1 a, F.W. 5/9; 250 v 50 ma, 5/9; 6/12 v 2 a, F.W. 9/9; 250 v 80 ma, 7/9; 6/12 v 4 a, F.W. 14/9.	
---	--

BATTERY SET CONVERTER KIT

All parts for converting any type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplied 120 v 93 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 v at 0.4 a to 1 a. Price including circuit 49/9. Or ready for use 8/9 extra.

ALL DRY RECEIVER BATTERY SUPERSEDER KIT

All parts for the construction of a unit (housed in metal case 5-4-4 1/4 in.) to supply 90 v 10 ma, and 1.5 v 250 ma. Fully smoothed. From 200-250 v 50 c/s mains. For 4-valve receivers. Price inc. point-to-point wiring diagrams, 35/9. Supplied assembled and tested at 49/9.

SILVER MICA CONDENSERS. Most values 5d. ea., 3/9 doz. one type.

VOL. CONTROLS (standard long spindles).

All values, less switch: 2/9; with S.P. switch, 3/9; with D.P. switch, 4/6.

TELEPHONIC ATTENUATORS

12.5 db. 16 mfd 450 v, 2/11; Can 8-8 mfd 450 v, 3/11; 8-16 mfd 450 v, 3/11; 16-16 mfd 450 v, 4/11; 32 mfd 350 v, 5/6; 32-32 mfd 450 v, 5/11; 64 mfd 450 v, 4/9; 69-100 mfd 350 v, 7/6.	
--	--

EX-GOVT. BLOCK PAPER CONDENSERS.—4 mfd 500 v, 2/9; 4 mfd 1,500 v, 5/9; 8 mfd 200 v, 7/9; 11.7 mfd 500 v, 7/9; 0.1 mfd plus 0.1 mfd 8,000 v common negative isolated, 11/9; 0.5 mfd 2500 v, 2/11; 1.5 mfd 4000 v, 5/9.

EX-GOVT. SMOOTHING CHOKES.

50 ma 5-10 h	2/9
100 ma 10 h 150 ohms Tropicalised	6/9
150 ma 10 h 150 ohms	9/6
250 ma 3 h 50 ohms Potted	11/9
250 ma 10 h 150 ohms	16/9
250 ma 10 h 50 ohms	14/9

EX-GOVT. MAINS TRANSFORMERS

Primaries 230/250 v 50 c/s 4 v 2.5 a, 4/9; 4 v 6 a (High Ins.), 7/9; 48 v 1 a, 9/9; 175 v 150 ma, 9/9; 300 v 200 ma, 9/11; 250-0-250 v 40 ma 6.3 v 2 a, 5 v 2 a, 9/11; 2800 v C.T. 5 ma, 22/9; 2200 v C.T. 120 ma, 21/6; 400 v C.T. 150 ma 4 v 6 a, 6.3 v 6 a, 6.3 v 0.6 a, 4 v 6 a, 4 v 3 a, 4 v 3 a, 4 v 3 a, 5 v 2 a, 22/9; 300-0-300 v 120 ma 4 v 1 a, 17/6; 665-775-690-620-775-665 v 500 ma, 29/6; 610-0-610 v 150 ma, 200-0-300 150 ma, 15/9; 150 350 ma, 29/6; 460 v 200 ma, 6.3 v 5 a, 29/6.	
---	--

EX-GOVT. AUTO TRANSFORMERS

200 watts 0-195-200-210-215-220-225-230-240-245-250 v 25/9.

5000 watts 0-57.5 v and tapped every 11 volts up to 230 v (carr. 10/- extra on this item), only 89/6.

EX-GOVT. E.H.T. SMOOTHERS

4/2 mfd 8000 v, 1/11; 25 mfd 4000 v (Block), 9/9; .5 mfd 3500 v, 3/3.	
---	--

"SIMPLEX" PARTS

7 valves for Vision and Sound Section	29/6
7 valveholders for above	4/-
2 Electrolytic Condensers H.T.	9/-

Smoothing Choke 150 ma 10 h

6 Valves for Time Base	25/-
6 Valveholders for above	1/10
50 mfd 1000 v	22/6

Mains Transformer 350-0-350 v 150 ma


6.3 v 4 a, 0-4-5 v 3 a	29/11
------------------------	-------

Most other components available at low prices.

R.F. UNITS TYPE 26.—Brand new. Cartoned, 39/6, plus carr., 2/6.

ADCOLA

(Regd. Trade Mark)

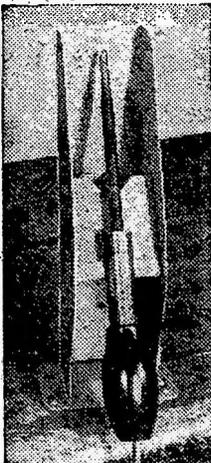

Shields as illustrated 10/6 extra.

SOLDERING INSTRUMENTS

FOR

SUCCESSFUL HOME CONSTRUCTION AND ALL SOUND EQUIPMENT SOLDER JOINING

"STANDARD MODEL," as ILLUSTRATED, 25/6

Any volt range supplied. 6/7 to 230/250.

3/16" dia. bit Standard Model

Equally suited to daily or intermittent use

Made in England

Registered Design

(British, U.S.A., Foreign Patents)

Export Enquiries Invited

WRITE DIRECT TO

ADCOLA PRODUCTS LTD.

Sales, Offices & Works: CRANMER COURT, CLAPHAM HIGH ST., LONDON, S.W.4. M.A.Caulay 4272

CYLDON 5-CHANNEL SWITCHED TELEVISIONS



Instant and positive selection of any one of the 5 E.B.C. channels by a single control knob. Uses EF.80 R.F. pentode and ECC81 or 12AT7 Double Diode Triode as frequency changer. Tuning is obtained by switching incremental inductances. Size: 4 1/2 x 2 1/4 in. Spindle 2 1/4 in. long. 4 in. diameter. I.F. Output 9.5-14 Mc/s, noise figure on all channels better than 10.5 db. I.F. rejection better than 45 db on all channels. Power gain 24db.

LASKY'S PRICE..... 12/6
Postage 2/6 extra

AERIAL ROD SECTIONS

Steel, copper plated. Any number may be fitted together. 12 in. long. 1/4 in. diam. 2/6 per doz.

TABLE TELEVISION

For 12 in. and 14 in. C.R. tubes. Beautifully finished in polished medium walnut veneer. Complete with mask glass, speaker, frot. Internal dimensions: 15 in. wide, 16 in. deep, 14 in. high. LASKY'S PRICE..... 39/11

Carriage 7/6 extra. Also available in unpolished veneer. LASKY'S PRICE..... 19/11

Carriage 7/6 extra.

LASKY'S RADIO

LASKY'S (NARROW ROAD), LTD.

370, HARROW ROAD, BADDINGTON, LONDON, W.9.

Telephone: CUNNINGHAM 1974-75

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m.; Thurs. half day 1 p.m.

Postage and packing charges (unless otherwise stated); on orders value £1—1s. 0d. extra; £5—2s. 0d. extra; £10—3s. 6d. extra; over £10 carriage free. All goods fully insured in transit.

MANUFACTURERS' SURPLUS TV. COMPONENTS

Wide Angle Scanning Coils, Low Imp. line and frame.....	19/6
Scanning Coils, 35 mm. Low Imp. line and frame	12/6
Frame output trans.	10/6
Focus Coil, 35 mm. electro magnetic	12/6
Line or Frame B.O. transformer A.724	4/6
Wide Angle Frame B.O. trans.	10/6
P.M. Focus Magnets. With vernier 35 mm. Triode	15/-
Triode	17/6
Wide Angle P.M. Focus Unit. For all 38 mm. tubes. With vernier and picture shift. Ferruxure	25/-

PLESSEY

Scan coils per pair	25/-
Width Control	6/8
P.M. Focus Magnet. Less vernier. 35 mm.	12/6

CRYSTAL DIODES

Wire ends. Glass. 1/6

WAX-GHOSB RECTIFIERS

Type WX.6. Wire ends..... 1/6

TELESCOPIC PORTABLE AERIAL MASTS

Made of lightweight but extremely strong alloy. Extends to 15ft. Guyed at top and centre. Supplied complete with all guy lines. LASKY'S PRICE..... 32/6

Carriage 2/6 extra.

BRIMISTORS

Type CZ.1, 1/6 each. CZ.3 10/6 each or 9/- doz.

SOLDERING - SAFE - SIMPLE - SPEEDY

with the sensational

new

70/-

post free,
less trade
discounts



PRIMAX—★
BALANCED GRIP SOLDERING GUN

The PRIMAX-SOLDERER is the ideal tool for any RADIO-TV-TELEPHONE mechanic or amateur. Just the tool for service calls and small jobs on the bench. The Primax-Solderer works on a different principle from that of commonly known soldering irons. A current of high amperage produced in the transformer will heat the soldering tip within 6 seconds. Available for 110, 200/220 and 220/250v. A.C., 50/60 cycles (60w.). One year guarantee.

Specially designed for easy soldering on hard-to-reach jobs.

TRIGGER CONTROL.

- ★ EXCLUSIVE ALLOY TIP—never needs re-tinning, lasts indefinitely under normal use.
- ★ INSTANT HEATING—Ready for soldering in 6 seconds.
- ★ COMPACT LIGHTWEIGHT—slips into your pocket or tool-kit, weighs only 23 ounces.

Sole Distributors:—

S. KEMPNER, 19 Ebury Street, London, S.W.1
Tel. SLOANE 3586 Through wholesalers and retailers

SIMPLEX
VALVE SET

(13) **39/-** VALVES

ALL GUARANTEED. EX.-GOVT.

EF50	4/-	EF50(Sy)18/3	3	SP61	2/6	SP41	2/6
EB34	2/-	EA50	2/-	6J5	5/-	GSN7	9/-
6J5(M)	6/-	6H6(M)	4/6	6SH7(M)	5/-	GSK7	5/-
EF36	4/6	EF8	7/6	EF54	5/-	EF39	7/-
EC52	5/-	EC34	4/6	EL32	7/-	EL33	12/-
EB33	7/6	EK32	7/-	6AM6	7/6	6AL5	7/-
6BW6	8/6	6BW7	8/6	9BW6	8/6	6R5	13/-
1T4	7/-	1R5	7/-	1A4	7/-	1S5	7/6
3S4	7/6	3V4	8/6	3A4	7/6	CV63	5/6
VU39	8/6	5Z3	8/6	5Z4	8/6	5C4G	9/-
6X5	7/6	FW430J	8/6	807	8/-	HL2	2/6
Pen22)	3/-	CV183	6/-	CV173	9/6	VU111	3/-
VU133	3/-	U22	7/6	6K8	11/-	6K7	8/-
6Q7	8/6	6V6	8/6	VR115	4/-	3L5	8/6
50L6	8/6	35Z4	8/6	12A5	7/-	123A	6/-

Condensers.—Electrolytic, 450 volt working: 8 mfd., 2/3; 8+8 mfd., 3/9. 16+16 mfd., 4/6. Dabiller 500 volt working, 20 mfd., 3/-, 32 mfd., 5/-. Bias, 25 mfd. 25 volt, 50 mfd. 50 volt, 2/- each.

Resistors.—Our Selection, 12/8 per 100. 1, 1, 1, 2 w.

Co-axial Cable.—1in. dia., 80ft. Brand new. 8d. per yard.

Potentiometers.—All values to 2 meg., less switch, 2/6 each. With switch, 100 k. 1 meg., 1 meg., 1 meg., 2 meg., 4/- each.

VINER'S (Middlesbrough)
Radio Government Surplus Electrical

26, EAST STREET, MIDDLESBROUGH
Telephone: MID 3418

NEW!

EXPERIMENTAL OUTFITS

LEARN THE PRACTICAL WAY

Specially prepared sets of television parts (which you receive upon enrolment) with which we teach you, in your own home, the working of circuits and bring you easily to the point when you can construct and service a television set. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business—this Practical Course is intended for YOU—and may be yours at very moderate cost.

EASY TERMS FROM £1 A MONTH

A tutor is available to give individual help and guidance throughout the Course.



EXPERIMENTAL OUTFITS:

TELEVISION—Instruction and equipment for building a Television Receiver.

RADIO 1—A course in basic principles.

RADIO 2—Instruction and equipment from which you build a Radio Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.

E.M.I. INSTITUTES The only Postal College which is part of a world-wide Industrial organisation.

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:

I am interested in.....


To: E.M.I. INSTITUTES, Dept. 138X, 43 Grove Park Road, Chiswick, London, W.4.

NAME.....

ADDRESS.....

AUGUST..... IC.30

UNDERNEATH THE DIPOLE

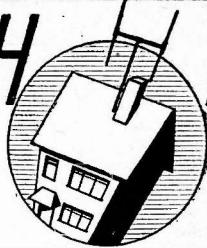

By Iconos

MULTIPLE TRACK RECORDINGS

MULTIPLE sound track recordings are the order of the day for all kinds of purposes, using both photographic or magnetic recording, and though much of the detail equipment design is quite unsuitable for picture recording, the pioneer work has been valuable. Triple magnetic track recording on film has been used in Hollywood for some years for re-recording dialogue, music and effects tracks on to a final photographic track for theatre release. The same equipment has been used for television films production, which also occasionally make use of $\frac{1}{4}$ in. magnetic tape using twin tracks. One track is used for recording the sound for the television picture and the second track is used for a time-base recording. When reproducing or transferring to another track (such as a 30ft. per second magnetic TV picture tape) the original timebase is scanned on a C.R. tube against a 50 or 60 cycle reference to ensure that synchronisation is maintained. Multiple track recordings are also used for all kinds of other purposes, from prospecting for oil to research on atom bombs. But that is another story altogether!

THE MANCHESTER STUDIO

TV follows the film! At any rate, the siting of the BBC's "new" television studios seem to follow the trails, blazed by film pioneers. Alexandra Palace and Lime Grove were both sites of early British cinema studios, the homes of Big Ben and Gaumont films respectively. And now, the acquisition of the first provincial TV studio is announced — at Manchester. Following what seems to be the usual precedent, the studios where "Mancunian" films were made have been taken over by the BBC for its Manchester TV studio.

This is situated in Dickinson Road, Rusholme, and has been operated for about eight years by Film Studios (Manchester) Ltd., which is closely associated with the Mancunian Film Corporation, a producing and distributing

organisation which has been in existence for over twenty years. John E. Blakeley, the managing director, has carried out a policy of "what Lancashire thinks to-day — London will think to-morrow," and it must be admitted that in many ways he has been right. Aiming at the tastes of the cinema audiences of Lancashire and Yorkshire, which account for about one-third of the cinema seating capacity of the British Isles, he has ignored the jaded tastes of the London film critics. Finding that the British and American films he was handling did not quite meet the regional requirements of these counties, he started making films on broad comedy lines, featuring comedians well known locally and at Blackpool, Morecambe, Scarborough and other seaside resorts. He put George Formby, Jr., into his first film, a modest effort called "Boots! Boots!" which broke records all over the two counties and was well received elsewhere. Enlisting the services of Arthur Mertz, the most prolific music hall "gag" writer in the northern counties, he launched upon a series of broad slapstick comedies of the Crazy Gang type, featuring Duggie Wakefield, Frank Randle, Norman Evans, Nat Jackley, Tommy Fields, Betty Jumel and others. Blakeley's earlier films were made at studios in London, but after the war he acquired a disused chapel with buildings adjacent in Manchester. He spent a great deal of money fitting them out and equipping them with lights, cameras and sound apparatus, not to mention all the other necessities such as workshops, scene docks, a theatre, property rooms, dressing rooms and offices. There are two nice stages, No. 1 being 100 ft. x 55 ft. widening to 80 ft. and No. 2 measuring 50 ft. x 40 ft. Power supplies are from the local mains, cameras are by Newall, lights by

Multiple H.D. Industries and Mole-Richardson with sound by Visatone and G.B.-Kalee. In other words, the BBC have acquired in one piece something which would have taken them quite a long time to assemble. John Blakeley, who directed most of the films made by Mancunian, plans to continue making his films especially for Lancashire and Yorkshire—but they will be once more made in London studios.

FUTURE TV CENTRES ?

WHERE else will the BBC look for provincial studios? If they follow precedent and acquire studios or premises already established in the provinces, there are a surprising number of possible sites. Close to Torquay, old film studios, now disused, are situated at Watcombe Hall, Babbacombe and at Oldway, Paignton. The latter studio was established just as the British film studios faced a slump. The only film wholly made at the Oldway Studio was one intended for American Television! The equipment, by Western Electric, Mitchell, Mole-Richardson and others, was first-class and there were excellent and well-fitted cutting-rooms. The equipment has gone, but the premises and, I believe, the sound proofing are still there. Perhaps this ill-fated local enterprise will yet revive in the interest either of BBC or sponsored television. Other early film studios existed in Sheffield, Hove, Brighton, St. Annes (near Blackpool); Lancaster, Holmfirth (Yorks), Bradford; Macclesfield, Liverpool, Rochester, Shoreham and Hastings. Some of the "studios" were of the early glass-house or open air type. Bamforth comedies were made by a Yorkshire firm which also specialised in religious lantern slides and seaside post cards! Their studio at Holmfirth was quite a centre of local activity in the heyday of the silent film. The St. Annes Studios was a huge plant, converted from an old aeroplane hangar. Brighton and Hove had several well-equipped studios. Indeed, there is a modern and very active studio there now in St. Nicholas Road, Brighton,

with two stages and a full schedule of film productions ahead. Most of these places are far better and more commodious than the BBC's original studios at the Alexandra Palace.

TV COMPETITION

THE passage of the Television Bill through the House of Commons has been stormy, but at last it is through and goes on to "the other place," the Lords. Activity in sponsored television enterprises will now be intensified, particularly by those companies engaged in the making of films for television. Norman Collins' High Definition Films at Highbury and Douglas Fairbanks' Company at Elstree are particularly active and many other companies will now enter the field. Already there are said to be at least six hundred technicians engaged upon making films for television. Some of these have been working on films for American television for some time, of course, but now the demand will be for local I.T.A. programmes in addition. There will be competition for staff, too, and it is possible that quite a few BBC TV producers and engineers will change over to sponsored TV or to the film companies specialising in this work. The Highbury Studios of High Definition are fully fitted up for electronic shooting, using television cameras and recording the pictures on specially designed tele-cine cameras made by Moy to High Definition's specification. The TV method of shooting does enable a large footage of finished product to be achieved in a remarkably short time. Pictures viewed on the TV monitor, are of wonderful quality and give one an idea of the quality and definition it is possible to achieve under ideal circumstances.

VISTAVISION

TO meet the competition of improved quality TV, both from BBC and sponsored sources, the film industry have produced yet another gimmick to improve presentation at theatres. Under the name "Vistavision," special motion-picture cameras photograph the negative horizontally along the film, as with a Leica "still" camera, one frame of picture covering the space formerly occupied by two. This means that the picture area of negative is over two-and-a-half times as large as the standard type of negative, and the

inherent grain size and other blemishes on the negative are correspondingly reduced. The negative film travels at twice normal speed, but the wide negative is exposed at the usual 24 frames per second. Prints are made by optically reducing this large negative and at the same time twisting the picture 90 deg. into its normal size on a standard print. Quality and definition are improved to an extraordinary degree, especially on the enormous screens now in use. This is another effort—and a most impressive one—to draw viewers back from their armchairs to the plushy tip-ups of the cinemas.

16mm. TV RECORDING

OF course, the consumption of film stock and the amount of processing required for the negative will be doubled when Vistavision type negatives are photographed.

This rules it out as a method of recording large photographic negatives of TV material along the lines of the High Definition or other tele-film systems. For TV recording, the tendency is towards smaller negatives which are quite capable of giving sufficient resolution for most purposes. 16mm. film is being used experimentally both by the BBC and High Definition and is in general use in the U.S.A. Good quality results are achieved with much less cost. Accuracy—or, rather, insufficient accuracy of perforations of standard commercial 16mm. film—is one of the main problems. Research departments engaged upon development in this field are unperturbed by the report of successful magnetic recording of pictures on tape. "An interesting laboratory experiment," they comment, and turn back to their flying-spot scanners.

New TV Tower at Crystal Palace

IT is now possible to give some details of the aerial tower which British Insulated Callender's Construction Co. Ltd. are to design and erect for the BBC to their detailed specifications of structural requirements, wind loadings, etc., at their new London Television Station at Crystal Palace. This station will eventually replace the existing transmitting station at Alexandra Palace.

The new tower is to be a self-supporting lattice-steel structure, 640ft. in height, and will have a base width of 120ft. For the first 440ft. it will taper after the manner of the Eiffel Tower and from this point until it reaches the height of 600ft. will be of square construction with parallel sides of 9ft. 6in. square section. The top 40ft. of the tower, which is also to be of square section, will have parallel sides of 2ft. 6in. face width.

The structure will be designed to resist wind pressures varying from 27 pounds per square foot at the base to 55 pounds per square foot at the top. Allowance has been made for icing in bad weather and the tower will resist these wind pressures even when all its members are coated with a half-inch thickness of ice.

Between the 440ft. and 660ft. levels, eight stacks of four dipole aerials will be mounted and at 440ft.

provision will be made for the installation of dish-type receiving aerials for picking up outside broadcast transmissions.

The foundations of the tower are being specially designed to provide for the possibility of future underground extensions of the transmitter buildings beneath the structure. The tower itself will be provided with an electrically-operated hoist to carry two passengers or a goods load of five cwt. to a height of 440ft.

The whole structure will be of bolted construction and will weigh approximately 370 tons. All structural members and connections will be hot dipped galvanised at the works of Messrs. Painter Bros., at Hereford, who will fabricate the steel work.

British Insulated Callender's Construction Co. Ltd. were responsible for the supply and erection of the existing 750ft. high masts at the BBC's high power television stations at Sutton Coldfield, Holme Moss, Kirk O'Shotts and Wenvoe, and are to provide masts for three of the medium power television stations now to be built. These are at North Hessary Tor (Devon), where a 750ft. mast is to be erected, and at Pontop Pike (Newcastle) and Rowridge (Isle of Wight), where 500ft. masts are to be installed.

BUILDING THE "SIMPLEX"?

Thousands of enthusiasts are building the "Simplex" Television, now being featured in "Practical Television." WHY NOT YOU? CONSTRUCTOR'S ENVELOPE containing full constructional details and Blue Print, additional notes and suggestions, and Query Service form, sent for only 5/- . All components available ex stock as follows:

ALUMINIUM CHASSIS—18 s.w.g. DRILLED, with screens and tube holder bracket, 27/6. PLAIN, with screens and tube holder bracket, 20/-

TRANSFORMER—250-0-350 v., 150 m.a. 6.3 v. 5 a., 5 v. 3 a. tapped at 4 v. ONLY 32/6. (Postage 2/-)

CHOKE—10 h. 120 ma. 10/6. (Post 1/-)

RECEIVERS—RM3 5/- ea., K3/40 6/- ea. VALVES—EF50 6/6. SP1 4/-. 6SN7 9/- . 6J5 5/6. EB34 3/6. EA50 3/6.

VALVE HOLDERS—B9C(EF50) 10d., I.O. and M.O. 6d., Diode (EA50) 6d., VCR97 2/6.

VCR97 TUBE—Tested full screen, 42/6. CONDENSERS—Electrolytics 25 mfd. 25 v. 1/10. 18 x 8 mfd. 450 v. 5/6. 32 x 32 mfd. 450 v. 6/- . 1 mfd. 2,500 v. 4/6. Mica, silver mica, and tubulars, 350 v. 6d. each.

POTENTIOMETERS—All values, pre-set 1/9 each, long spindle 3/-, with switch, 4/6.

RESISTORS—1 watt 4d., 1/2 watt 5d., 1 watt 6d., 1.5 K. 5 watt, 1/6.

COIL FORMERS—1 in. 8d., 1 in. 10d. **SPEAKER**—4 in. ROLA P.M. with trans. 17/6 (postage 2/-).

All Components Brand New and Unused. Full Price List available on request.

VALVES					
1G6	6/6	7A7	8/6	5Z4	10/-
1E7	6/6	7C5	8/6	5U4	10/-
1LH4	8/6	7F7	8/6	6AC7	6/6
1LN5	8/6	7W7	8/6	6K7GT	5/6
1L4	7/6	12H6	8/6	807	7/6
2B7	8/6	12J5	6/6	ECH35	12/6
3A4	9/6	12AH7	12/6	EA50	3/6
3B7	8/6	12SG7	7/6	EBC33	8/6
6AG5	7/6	12SK7	8/6	EB34	3/6
6AK7	9/6	12SR7	7/6	EF36	6/6
6B4	7/6	28D7	7/6	EF39	6/6
6C3	7/6	32	7/6	EF50	6/6
6C3	8/6	38	7/6	.. Red	
6G6	6/6	50Y6	8/6	Sylvania 8/6	
6H6	5/6	58	8/6	EF91	12/6
6K6	9/6	1622	11/-	EY51	15/-
6L7	7/6	1626	4/-	EK32	6/6
6N7	7/6	1289A	7/6	EL32	7/6
6R3	8/6	VR150/30	8/6	SP61	4/-
CU5	8/6	VR137	5/9	MU14	10/6
6V6	8/6	VR137	5/9	RL37	6/-
6V6GT	7/6	KT44	8/6	V570	7/6
6L7	7/6	KT2	5/-	954	6/6
6SG7	7/6	VP23	6/6	955	6/6
6SH7	7/6	HL23DD	6/6	9003	6/6
6SJ7	8/6	TP25	8/6	9004	6/6
6SK7	7/6	155	3/-	931A	50/-
6SL7	9/6	174	8/6		
6SS7	7/6	1R5	8/6		

R.F. UNIT'S TYPE 26 and 27. For use with the R.1355 or any receiver with a 6.8 v. supply. These are the variable tuning units which use 2 valves EF54 and 1 of EC52. Type 26 covers 65-50 Mc/s (6-5 metres) and Type 27 covers 65-45 Mc/s (3.5-5.0 metres). Complete with coils, and BRAND NEW IN MAKER'S CARTONS. ONLY 45/- each.

R.F. UNIT TYPE 24. Complete with 3 valves SP61 and full details of modification required to cover all TV. Stations. ONLY 15/-

TRANSFORMERS—Manufactured to our specifications and fully guaranteed

Normal Primaries, 425-0-425 v., 200 ma. 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., ONLY 50/- . 350 v.-0-350 v., 160 ma., 6.3 v. 5 a., 6.3 v. 3 a., 5 v. 3 a., ONLY 42/6 . 250 v.-0-250 v., 100 ma., 6.3 v. 6 a., 5 v. 3 a., ONLY 32/6 . 350 v.-0-350 v., 150 m.a., 6.3 v. 5 a., 5 v. 3 a., ONLY 32/6. The above are fully shrouded, upright mounting, 5.5 kV. E.H.T. with 2 windings of 2 v. 1 a., ONLY 72/6 . 7 kV. E.H.T. with 4 v. 1 a., ONLY 82/6. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

E.H.T. TRANSFORMER FOR VCR97 TUBE—250 v. 5 ma. 2-0-2 v. 1.1 a. 2-0-2 v. 2 a. 37/6 (postage 2/-)

AMERICAN ROTARY TRANSFORMERS—12 v. D.C. input, output 255 v. 65 ma. Useful for car radio, or running electric shaver from car battery, etc. ONLY 22/6.

INDICATOR UNITS, TYPE 6—Contain VCR97 Tube with mu-metal screen, 4 valves, EF50 and EF54. NEW CONDITION. ONLY 59/6 (carriage, etc., 7/6).

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station), 5 mins by bus from King's Cross
Cash with order, please, and print name and address clearly. Include postage as specified and on Component Orders under £2.

U.E.I. CORPN. THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.1.
(Phone TERMINUS 7937.)

IT'S 60% CHEAPER!!

To Construct Your Own Television Aerial
SUMMER TIME IS THE RIGHT TIME TO CONSTRUCT AND ERECT AN AERIAL
WE SHALL BE PLEASED TO SUPPLY INFORMATION, IF REQUIRED, ON ELEMENT LENGTHS AND SPACINGS, WITH FULL ASSEMBLY INSTRUCTIONS. ALL WE NEED IS THE CHANNEL NO. AND TYPE OF AERIAL TO BE CONSTRUCTED

All fittings are die-cast, using high quality aluminium and are fully guaranteed.

- 14ft. 16 s.w.g. 2in. Aluminium Masts Inc. Carr. 50/- (Transit Board 15/- extra. Returnable.)
 - 1in. 18 s.w.g. D/H Alloy Tubing Per ft. 10d.
 - 1in. 18 s.w.g. D/H Alloy Tubing Per ft. 1/4d.
 - INSULATORS. Unbreakable, waterproof (standard 1in. x 1in. fitting). Each 6/9
 - INSULATORS. Unbreakable. For "In-line" Aerials. 1in. x 2in. fitting. Each 8/9
 - MASTHEAD MOUNTINGS, 2in. Pole fitting, 1 in. Cross Boom. Each 8/6
 - MASTHEAD MOUNTINGS, 1in. Pole fitting, 1in. Cross Boom. Each 6/-
 - REFLECTOR AND DIRECTOR ROD HOLDERS, for 1in. Elements, 1in. Cross Boom. Each 3/9
 - BRACKETS. Heavy Duty, 2in. Pole fitting, double lashing. Set 40/- & 35/-
 - BRACKETS. Lightweight, 1in. Pole fitting, single lashing. Set 30/- 25/- £1 & 15/-
- 2d. stamp for illustrated Price List. C.W.O. Package and Postage 1/6 extra for castings or 2/3 extra where orders include tubing.
Address in block letters please.

Fringevision Ltd.
MARLBOROUGH, WILTS. Phone 605.

VIEWMASTER

LONDON — MIDLAND — HOLME MOSS — KIRK O'SHOTT'S — WENVOE — PONTOP PIKE — TRULIEGH HILL — ISLE OF MAN — ROWDRIDGE (ISLE OF WIGHT).

Constructional envelope with fully illustrated manual, full size diagrams and operating instructions for building on dished chassis with simple tools in 7 easy stages from guaranteed new, as specified, components—a first-class 9in. or 12in. tube television in table or console form. 7/6. Constructional envelope for modifying to 16in. or 17in. big-picture tube, 3/6.

W.B. COMPONENTS—WB200 Sound and Vision drilled chassis with all valveholders and grommets mounted, 18/6 ; WB101 Chassis Support, 6/- ; WB102 Power Pack drilled chassis with all valveholders mounted, 13/6 ; WB103 Heater Transformer, 42/- ; or WB103A Heater-auto Transformer, 52/6 ; WB104 Smoothing Choke, 15/6 ; WB105 Special T.V. type Loudspeaker, 43/6 ; WB106 Frame Transformer, 23/6 ; WB107 Line Output Transformer, 32/6 ; WB108 Scanning Coil, 53/3 ; WB109/1 Focus Ring for C.R. Tubes, except Mullard and Mazda, 22/6 ; WB109/2 Focus Ring for Mullard Tubes, 22/6 ; WB109/3 Focus Ring for Mazda Tubes, 22/6 ; WB110 Width Control, 7/6 ; WB111 Boost Choke, 5/9 ; WB112 C.R. Tube supports, 21/6 ; WB300 Pre-amp chassis, 17/6 ; 12in. Console Conversion kit, 35/- . **Wide Angle Components**—WB113 Line Transformer, 48/6 ; WB114 Frame Transformer, 23/6 ; WB115 Scanning Coil, 42/- ; WB116 Width Control, 7/6 ; WB117 Linearity Control, 7/6 ; WB118 Focus Ring, 22/6 ; WB119 Heater Transformer, 18/6.

WEARITE COMPONENTS—Complete set of coils and type L9 choke ; Model "A," 22/- ; Model "B," 30/- ; Model "C," 30/- ; Model "D," 30/- ; Model "E," 28/- . Pre-amp coils, all models, 4/- pair.

WESTINGHOUSE RECTIFIERS—14A86, 20/4 ; 14D36, 11/7 ; 36EHT100, 29/5 ; 36EHT30, 17/6 ; WX3, 3/9 ; WX6, 3/9.

ALL OTHER PARTS AVAILABLE. VIEWMASTER LIST FREE ON APPLICATION.

Postage and packing extra on orders under £2. 54-page illustrated Catalogue No. 2, post free.

Southern Radio & Electrical Supplies
SORAD WORKS
REDLYNCH : SALISBURY : WILTSHIRE
Telephone : Downton 207

A REMINDER



Deflector Coils type DC300/C. As specified for the "Teiking," "Supervisor" and "Magnaview." Conversion circuits for 14in. and 17in. C.R. Tubes now available.

Since we pioneered wide-angle scanning for the Home-Constructor several years ago, we have become so well known as manufacturers of reliable television components that some of our standard lines are liable to be forgotten.

Typical examples of these are :

465 kc/s I.F. Transformers type 160 (Miniature), size 1in. x 1in. x 2in. Price 7/6 each.

465 kc/s I.F. Transformers type 158 (Standard), size 1 1/2in. x 1 1/2in. x 3 1/2in. Price 9/6 each.

Tape-Deck Oscillator Coils, type 31. High impedance, screened, each coil adjusted to 9 mH. Price 9/3 each.

From all Leading Stockists.

ALLEN COMPONENTS LIMITED

Crown Works, Lower Richmond Rd., Richmond, Surrey
Telephone : Prospect 9013

Send 9d and S.A.E. for Wide-Angle Circuit Diagrams.

TALLON CABINETS

for television, radio and grams, polished, ready for assembly in packed flat kits or factory assembled.

TELE-KING cabinets with space for radio or tape recorder with or without doors, for 12", 15", 16" or 17"

VIEW MASTER cabinets, console, or table, 12 and 17in.

P.W. 3-SPEED AUTO-GRAM CABINET.
LYNX CABINET.
ARGUS CABINET.

RADIOGRAM, RADIO AND SPECIAL CABINETS TO CUSTOMERS' DESIGNS.
SUPER CABINETS FOR SOUNDMASTER.
MINI-FOUR AND CRYSTAL DIODE cases at 14/6 each, including postage.

Consult your local dealer or write to :
(DEPT. P.T.L.)

JAMES TALLON & SONS LTD.
MANOR WORKS, MANOR ROAD
RUGBY Telephone : RUGBY 2070

Unrepeatable VALVE BARGAINS

6K7G	5/-	EF36	6/-	MSPEN	5/-	R19	8/8
6BE6	6/6	VU111	5/-	EP50	6/-	6AM6	6/6
6SN7	8/6	12SC7	5/-	EL32	6/-	EP54	4/6
12AT7	8/-	6AQ5	6/9	AC6PEN	5/-	VP23	5/-
12BE6	6/9	6BW6	6/-	6B4	5/6	7S7	8/-
8D3	6/6	6U5	5/9	6V6G	7/-	12A6	5/6
KTZ41	4/6	12AU7	9/-	6BA6	6/6	U78	7/-
6SH7	5/-	1T4	6/3	6X4	6/6	6K6GT	6/8
R3	8/6	6AT6	7/6	9BW6	6/-		

TWIN GANGS. 0005, 6/-.
SOLID DIELECTRIC. 0001, 0002, 0003, 3/10.
8p. 4-way YAXLEY FOUR BANK, 3/6 ; 6 BANK YAXLEY, 2/3.

ELECTROLYTICS—NEW SURPLUS: 8 mfd., 350 v., 1/8 ; 8 mfd., 500 v., 1/11 ; 16 mfd., 350 v., 2/6 ; 16 mfd., 450 v., 3/6 ; 8-8, 350 v., 3/9 ; 16-16, 275 v., 4/- ; 8-16, 450 v., 4/3 ; 25 mfd., 50 v., 1/9.
POTS.—25 K., less, 1/9 ; 100 Kv. Midget (Short Spindle), 9d. ; All others, 2/3, less ; 4/- with Switch ; Wirewound Pre-set 100, 2 to 30 K., 3/2.

6-9 kv. EHT OSCILLATOR COILS, 15/-.
Few Only. GARRARD MAGNETIC PICK-UPS. High Impedance, 24/-.

COILS STOCKED : R.E.P., Osorn, Denco, Wearite, Weymouth TIRE MIDGET MATCHED PAIR with Reaction, including Diagram Battery and Mains Receiver, 8/- pair.

CHARGING TRANSFORMERS, Tapped 4 v., 9 v., 18 v. for 2 v., 4 v., 12 v. Charging, 19/6 ; 1 v., 2 v., 4 v., 6 v., 10 v., 15 v., 20 v., 30 v., 4 amp. type, price 22/6.

CO-AXIAL CABLE, 9d. yd., 1/4in. diam. Stranded, 17/6 for 25 yds.
NEW BOXED GOODMAN'S, 5in. Spkrs., 15/-.
5in. M.E. 1,000 ohm FIELD + TRANS., 15/-.

SILVER MICA'S., 6d. ; TUBULARS, 6d.
T.C.C. .001, 6 kv., 6/- ; .001 12 kv., 7/6 ; .001 15 kv., 10/-.

75 pf. and 25 pf. CERAMIC SHORT WAVE VARIABLES (Long Spindle.) 2/6.
TYANA SOLDERING IRON, 14/11 ; ADCOLA, 25/6 ; HENLEY, 19/8 ; ADCOLA DETACHABLE BIT, 33/6.

Quotes, S.A.E. Surplus Booklet, 6d.
Post 6d. up to 5/-, 1/- up to 21, 1/6 to 22. C.O.D. (over 21).

RADIO SERVICING CO. 82, SOUTH EALING ROAD, EALING 5737. Next to South Ealing Tube Station.

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

NORTHERN POLY CLASSES

SIR,—Our new classes commence on September 27th, 1954, and will be of interest to your readers, and I should be most grateful if you could spare some editorial space to announce them.

I have received the most generous material assistance from all the manufacturers of Band III and F.M. equipment, and the governing body of the Northern Polytechnic are spending a considerable sum on new test gear.

There is no doubt that the future of Band III television and F.M. broadcasting principally lies in the hands of the installation and servicing engineers, and it is with this in mind that we are trying to encourage as many people as possible to study the problems associated therewith.—**JOHN GILBERT** (Head of Departments of Telecom. Engineering, Northern Polytechnic, N.7).

"H" VERSUS THE MULTI-ELEMENT ARRAY

SIR,—I am, of course, aware of the published figures of galactic noise in relation to wavelength, but I disagree with Mr. Harknett's interpretation of this data.

To give a readily appreciated example, Mr. Harknett would have us believe, if I understand him, that the signal/noise ratio is determined entirely by the magnitude of galactic noise. Thus by implication it appears that a television receiver having, say, as a first stage a mixer (i.e., no R.F. stage) connected to a conventional "H" aerial, will give the same performance, so far as noise is concerned, as one possessing an effective R.F. stage connected to an efficient directional aerial. That this is not the case is readily demonstrable both practically and theoretically.

If I may venture a personal opinion, I feel that Mr. Harknett has over-generalised his arguments in pursuit of support for what was an original false premise, namely the superiority of an "H" aerial over a more elaborate array.—**SPENCER-WEST** (Gt. Yarmouth).

ARE M/cs NECESSARY?

SIR,—In the July issue of your magazine there appeared an article entitled "Are the 3 Mc/s Bars Necessary?" I do not agree with the author's result of approximately 2.4 Mc/s bandwidth for equal horizontal and vertical definition. Similar results have been obtained by authors in other technical publications.

The author has obtained the figure of 96,700 cycles of black and white elements in each complete picture, but in multiplying this by 25 to obtain the frequency in cycles per second he has overlooked the fact that these 96,700 cycles must be resolved in less than 1/25th second. The frequency will be greater the lower proportion of the total frame time the active line elements occupy. For instance, if half the frame time was occupied in transmitting pulses and black levels, then the 96,700 cycles would have to be transmitted in 1/50th second and the maximum bandwidth would be 96,700 × 50, or 4.835 Mc/s.

The correct bandwidth required in our 405-line system to give equal horizontal and vertical definition will therefore be:

$$97,700 \times 25 \times \frac{\text{Total frame lines}}{\text{No. of actual lines}} \times \frac{\text{Total line acrial}}{\text{Actual line acrial}}$$

$$= 97,700 \times 25 \times \frac{405}{377} \times \frac{99 \text{ (approx.)}}{84 \text{ (approx.)}} \quad 3,061,000/\text{s}$$

or just over 3 Mc/s.

This may be checked from an accurate photograph of Test Card C by measuring the active time rate and comparing with the frequency gratings. It will be seen that the closest comparison is given by the 3 Mc/s grating.—**W. RUSSELL** (Coventry).

INTERLACING

SIR,—I have followed recent articles on interlacing etc., and have listened to a number of club members discussing this point; but I fail to see just what all the fuss is about. I do not make receivers, being content with a commercial model, and I do not know whether this interlaces or not. What does it matter? The picture looks good, and when I have been shown sets with a so-called bad interlace, they look just as good—unless of course, the lines are paired. After all, it was recently stated in the article on 3 Mc/s definition that the correct distance for viewing is where the lines just merge. Surely, then, at such a distance the picture will look good with all but the most atrocious interlacing. Another point is this 3 Mc/s business. Surely, at the normal viewing distance anything above 2 Mc/s looks all right, as there are few details in the average "telecast" which are fine enough to be produced by 3 Mc/s and then, as the article mentioned pointed out, you can't see them if you are not sitting right on top of the set. Aren't we all getting too critical about the last detail in various aspects of TV? Surely, it is on a par with sound broadcasting where the "experts" tell us that the ordinary set is no good—you must have a Hi-Fi with twin speakers in acoustic cabinets and suchlike. That is all very well for the real fans, but over 90 per cent. of the listeners are satisfied with commercial sets with 5in. speakers, superhet circuits and other aids to poor quality, and I think that a similar proportion are satisfied with non-interlaced, 1½ to 2 Mc/s tele sets.—**G. BORDON** (N.W.9).

SOUND QUALITY

SIR,—I should like heartily to endorse the remarks made by K. S. Barr, in last month's correspondence column.

He pointed out that the sound track of a televised film was of a poorer quality to that of the sound system of a cinema or the normal sound reception of a television broadcast. I could not agree more with him. I have just returned from a business trip to the States and had many opportunities to view the American programmes. A large percentage of these are of course "canned" or, as we say, filmed and the continuous use of these films meant continuous bad sound reception. So much so, that I eventually refused to watch any kind of TV programme but the "live" kind. Not only is the sound "crackly" but it is also very faint compared with the background noise that goes with it.

TV and the cinema must both keep their respective places and play their own parts. Films for the cinema and live transmissions for TV.—**J. BARWELL** (Haywards Heath).

Line Linearity

HOW LINEARITY IS CONTROLLED ON THE HORIZONTAL SCAN AND
COMMON FAULTS EXPLAINED

By W. J. Delaney

LAST month we dealt with the problems of frame linearity, as in our experience this is one of the most troublesome faults in receivers. On the line or horizontal side, however, the trouble is not quite so serious, occurring less or being less noticeable. On the frame side any non-linearity results in figures being made grotesque—with either big heads or small heads and big bodies. On the horizontal side, however, any distortion results only in figures on one side of the screen being disproportionate to those on the other. In "panning" shots this may be noticed by a figure suddenly growing stouter or thinner as it passes off the screen, or in lettering changing in size, but it is not nearly so troublesome and, in fact, in many cases almost passes unnoticed. In other words it is possible to use a screen and obtain worth-while enjoyment from it with distortion in the horizontal direction, whereas it is not possible to tolerate it in a vertical direction. Owing to the much higher frequency at which the line or horizontal scanning section operates it is possible to obtain a much better waveform, but many of the previous remarks on the frame section still hold good. For instance, the load resistor for the oscillator will still affect the output from the oscillator and the line output valve will still have to be adjusted to obtain a correction of any distorted output.

One of the most common of linearity controls met with in older circuits consists of an R/C combination across the scanning coils, and adjustment of either R or C or both results in a correction of the waveform.

It should be borne in mind at this stage that at the high frequency of the horizontal scan there is generated a back E.M.F. or surge from the scanning coils and this is, in fact, employed in modern receivers for the E.H.T. supply. This back E.M.F. exercises a correcting influence on the waveform of the line circuits and simplifies to some extent the problems arising from a non-linear scan.


Saw-tooth Waveform

It will be remembered from last month's description of the combined oscillator and output valve that the oscillator delivers a distorted form of saw-tooth and the output valve is made to deliver an output so distorted that it acts as a corrective to the input wave and thus delivers a straightened form of saw-tooth. One way of effecting this in the modern horizontal timebase is not to employ all of the saw-tooth output from the oscillator, but to use only one half of it, and to arrange for the output stage plus the recovery diode to add the second half. The second half of the oscillator output is usually "bent" whilst the first half of the recovery circuit is bent, and thus by combining the good portions of each a tolerable saw-tooth is delivered to the scanning coils. It should again be emphasised that in order to avoid complications and make it easier for the beginner to follow these explanations certain liberties are being taken, but the broad principles are covered for the purposes of following the general arrangement.

Auto-transformer

Most modern line timebases make use of an auto-transformer in which losses have been reduced by using one of the latest types of iron core. These are much smaller than older types of transformer and actually give greater efficiency, with the added advantage that linearity and width adjustments may be made easily by varying the values of certain parts of the transformer winding. This is usually accomplished by shunting a part of the winding by another coil with adjustable core or using a series arrangement of the same type of circuit. For the linearity control a very common arrangement, and one which is used in both the View Master and the Supervisor, is shown in the accompanying illustration. A diode is connected between the anode of the output valve and the H.T. line, and this is also included across part of the winding of the auto-transformer. To some

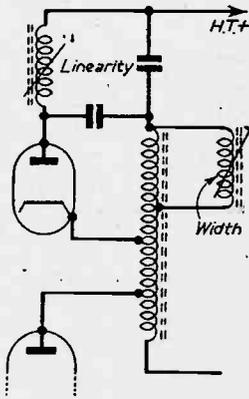Typical line linearity circuit as used in the View Master and Supervisor.



it may appear that this prevents H.T. from being applied to the output valve as there is no apparent direct connection to the anode. Actually, of course, H.T. passes through the diode at certain periods, and this diode fulfils another function. From the diagram it will be seen that an iron-cored inductance is included between the diode anode and the H.T. line and on each side of this choke is a small condenser. This will be recognised by most readers as a filter circuit such as is found in a normal H.T. supply and in fact it functions in a very similar manner. The circuit is rendered conducting over the major portion of the saw-tooth and during this period the condensers charge up. When the diode is non-conducting they discharge, and thus the anode of the output valve is provided with H.T. when the diode is not conducting.

The surge or back E.M.F. from the scanning coils is also fed to this part of the circuit and the additional 50 or so volts produced is added to the normal H.T. line. The linearity adjustment operates in the following manner: during the first half of the trace period the voltage across one of the condensers rises due to the rectified E.M.F. from the coils. During the second half of the trace the voltage falls due to the drain of the line output valve. From this it will be seen that the rise and fall across the filter will be in the form of a ripple voltage at the same frequency as the saw-tooth. This ripple voltage will be present on the H.T. supply to the line output valve, and by adjusting the phase of the ripple (by varying the value of the inductance) the linearity may be modified.

SAFEGUARD YOUR SET ECONOMICALLY

55' FOR 5/-

AND NOT AN INCH WASTED

**ERSIN
Multicore
SOLDER**



ERSIN MULTICORE SOLDER makes every electrical connection in your equipment a sound, permanent joint. Countless jobs—construction, repair—can be done with one 5/- carton. And, because ERSIN MULTICORE contains 3 cores of extra-active, non-corrosive Ersin Flux to prevent oxidation, 'dry' and H.R. joints, it solders instantly, without trouble, waste or extra flux. Get a carton today.

MULTICORE SOLDERS LTD.

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS • BOXMOOR 3635.

HANNEY of BATH offers:—

P.W. SIX-VALVE A.C. SUPERHET. Osmor 3-Band R.F. coilpack, 69/-; Osmor pre-aligned T.F.'s, 16/- pr.; Elstone mains trans. to specification, 32/-; Denco 16 x 8 x 2 1/2 in. chassis, 11/-, etc., etc. Priced parts list available on application.

FREQUENCY MODULATION. For Wrotham high fidelity Transmissions. Denco technical bulletin giving circuit and point to point wiring diagram for building an F.M. Feeder unit, 1/6. We have all components available. Priced parts list on application.

W.B. STENTORIAN High Fidelity Speakers. HF610, 50/6; HF810 60/6; HF912 67/-; HF1012 (3 or 15.2), 73/6.

ACOS Hi-g Pick-ups. HGP 20-1 std. or LP 68/8. Heads only std. or LP 42/3.

COILPACKS. Denco CP 4/1L and CP 4/1M, 33/4; CP 3/370 pf. and CP 3/500 pf., 42/8. OSMOR "Q" HO 48/-; LM, 40/-; Bats., 50/-; TRF, 40/-; HF stage for HO pack, 20/-; ETA 4-Station pack, 43/8. We stock COILS by Weymouth, Osmor, Wearite, Denco, Teletron and R.E.P.

ELSTONE Mains Trans. for the SIMPLEX TV, 48/-.

VIEWMASTER. WIDE ANGLE VIEWMASTER CONVERSION. Complete set of parts for converting existing Viewmaster to W.A., less valves, tube and mask £14/18/6. W.A. Conversion instructions, 3/6; WB13, 48/6; WB14, 23/6; WB15, 42/-; WB16 and WB17, 7/6 each; WB18, 22/6; WB19, 28/6; WB21, 3/6; WB24, 10/6; Westinghouse 38/EHT/33, 17/-. Plus condensers and resistors as per our general list.

MULLARD "UNIVERSAL" LARGE SCREEN A.C./D.C TELEVISOR. Denco drilled chassis with all mechanical parts, 53/6; FD12/4 duomag focaliser, 37/6; 14A/342 rectifiers, 37/2; Goldsman droppers DK37/6, 8/9; DK35/6, 7/6. VA1008 varite res., 4/6. Other Denco parts please see below.

WIDE ANGLE COMPONENTS. ALLEN. Telexing Chassis, 50/-; Collsets (TK & Super-Visor), 44/6; L.O.308, 40/-; FO.305, 21/-; DC.300c, 39/6; FC.302, 31/-; GL.16 & 18, 7/6 each; SC.312, 21/-; AT.310, 30/-; OP.117, 9/-; BT.314, 15/-; Denco Chassis Magnaview, 37/6; Chassis, Super-Visor, 51/6; Collsets, Magnaview, 41/2; WA/DCA1, 43/-; WA/PCA1, 31/-; WA/LC1 and WC1, 7/6 each; WA/FMA1, 21/-; WA/LC1, 42/-; WA/FBT1, 16/-.

Send 6d stamps for our General List of components for Viewmaster, Soundmaster, Williamson Amplifier, Telexing, Magnaview (Brimar & English Electric large screen TV), Super-visor, Mullard Universal, Close tolerance Silver Miccas, etc., etc. Please add 1/- postage to orders under 1/-.

L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

Used Mazda C.R.M. 123 cathode heater short aluminized. Complete with rubber mask Elac P.M. focus unit, scan coils, low line, low frame and frame o.p. trans., £5.10.0. P. & P. 7/6.

Used Mazda 12in. C.R. Tube 121. 121A heater cathode short. £3.7.6 P. & P. 7/6 Guaranteed 3 months.

Used Mazda 9in. C.R. Tube, heater cathode short. C.R.M. 91, 92 & 92A. Guaranteed 3 months, 37/6. P. & P. 7/6. Most of the above 9in with ion burn 27/6. P. & P. 7/6.


USED Mullard 12in. with ion burn 50/-, P. & P. 7/6.

Line and E.H.T. Transformer, 9KVA using ferrocart core complete with built-in line and width control. Mounted on All-chassis. Overall size 4 1/2 in. x 1 1/2 in.. EY51 Rec. winding. P. & P. 2/6, 27/6.

Scan coils, low line, low frame, complete with frame o.p. trans. to match above line and E.H.T., 27/6. P. & P. 2/6.

Heater Transformer, Pri. 220-250 v. 6 v. 1 1/2 amp. 6/-; 2 v. 2 1/2 amp. 5/-; P. & P. each 1/-.

Completely built. Signal Generator. Coverage 120 Kc/s-320 Kc/s. 300 Kc/s-900 Kc/s-2.75 Mc/s. 2.75 Mc/s-8.5 Mc/s. 8.5 Mc/s-25 Mc/s. 17 Mc/s-50 Mc/s. 25.5 Mc/s-75 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c/s. to depth of 30 per cent., modulated or unmodulated. R.F. output continuously variable 100 milli volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black

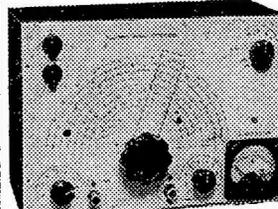

crackle finished case and white panel. £4.18.6, or 34/- deposit and 3 monthly payments 25/-. P. & P. 4/- extra.

Pattern Generator, 40-70 Mc/s. direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits, and vision channel, band width. Silver plated coils, black crackle finished case, 10 x 6 1/2 x 4 1/2 in. and white front panel. A.C. mains 230/250 volts. This instrument will align any T.V. receiver. Cash price £3.18.6 or 29/- deposit and 3 monthly payments of £1. P. & P. 4/- extra.

T.V. Converter for the new commercial stations complete with 2 valves. Frequency: can be set to any channel within the 186-196 Mc/s. band. I.B.: will work into any existing T.V. receiver designed to work between 42-68 Mc/s. Sensitivity 10 Mu/v with any normal T.V. set. Input: arranged for 300 ohm feeder. 60 ohm feeder can be used with slight reduction in R.F. gain. Circuit EP80 as local oscillator, ECC81 as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. amplifier 10 db. Required power supply of 200 v. D.C. at 25 mA., 6.3 v. A.C. at 0.6 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2.10.0. P. & P. 2/6.

Line & E.H.T. transformer, 9KV, ferrocart core, EY 51 heater winding, complete with scan coils and frame output transformer, and line and width control. P. & P. 3/-, £2.5.0.

T.V. Filter in lightly tinted perspex size 13 1/2 x 11 x 3 1/2 in., 4/6.

Metal rectifier, 250 v. 250 mA., 12/6. Used metal rectifier 250 v. 150 mA., 6/6.

R. and A.T.V. energised 6in. Speaker, field coil 175 ohms. Requires minimum 150 mA to energise maximum current 250 mA P. & P. 8/6.

Valve Holders, moulded octal Mazda, and octal, 7d. each. Pinxolin octal, Mazda and octal, 4d. each. Moulded B7G, B8A and B9A, 7d. each. B79 moulded with screening can, 1/6 each.

Combined 12in. Mask and Esectheon in lightly tinted perspex. New aspect, edged in brown. Fits on front of cabinet, 12/6. As above for 15in. tube, 17/6.

Frame Oscillator Blocking Trans., 4/6.

Smoothing Choke, 250 mA. 5 henry, 8/6; 250 mA., 10 henry, 10/6; 250 mA., 8 henry, 8/6.

P.M. Focus Unit for any 9 or 12in. tube except Mazda 12in., with Vernier adjustment, 15/6. P.M. Focus Unit for Mazda, 12in. with Vernier adjustment, 17/6. Wide Angle P.M. Focus Units Vernier adj., state tube, 25/-.

Energised Focal Coil, low resistance mounting bracket, 17/6.

Ion Trans for Mullard or English Electric tubes, 5/- post paid.

T.V. Coils, moulded former, iron cored, wound for rewinding purposes only. All-can 1 1/2 in. x 1 1/2 in. 1/- each; 2 iron-cores All-can, 2 1/2 in. x 1 1/2 in. 1/6 each.

Dubitler .011 10kV. working 3/6.

Clydon 5 channel T.V. tuner 12/6 post paid.

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.

D. COHEN

RADIO AND TELEVISION COMPONENTS

23, HIGH STREET, ACTON, W.3.

(Opposite Granada Cinema)

MONEY BACK GUARANTEE **DUKE & Co** **3 MONTHS GUARANTEE**
 Tel: GRA 6677 **CWO OF COD**
 621 ROMFORD RD. LONDON, E.12. **3**

12" £5 TV TUBES
 MAZDA CRM181-A-B, and a few other types and makes. Picture shown to callers. Not Ex-W.D. Carriage and insurance 15/6 extra. No catch. Special offer of tubes with burns for testing and spares at 30/- each.

SALVAGE VALVE CLEARANCE SALE

10/9	8/9	6/9	5/9	3/9
PL81	EF91	EF92	DL84	6A37
PY31	Z77	1S4	3V4	37
EBF80	6BE6	1S5	KTW61	UM4(M.ave)
12AT7	6BW6	6K7	OZ4A	SP2(5 pin)
ECC81	6BA6	EL91	E1436	4D1
PL83	6V6C	6AM5	77	CV6
PY82	6BR7	UF1	21OVPT	1LN5
			12Y4	1LD5

Postage on Valves 1/- up to 6.

SPOTLIGHTS.—3/9 Butlers, new but ex-W.D. 7in. dia. 6in. deep. These lights are similar to those sold for £3—£5, but finished Black. The lamp fitting is of the pre-focus type. Post 1/3.

BULBS.—For above now in stock, 6 volt, 36 watt, 12 volt, 48 watt, 4/6 each.

SIDELIGHTS.—1/9. Infra-red glass. Ideal tail lamps. New ex-W.D. Post 9d.

INTERFERENCE & NOISE SUPPRESSOR.—5/9. Cuts out frig., hair drier, etc., interference. Post 1/3.

RECTIFIERS

Selenium type, 180 volt at 40 m.A., 3/9. Metal recs., 200 v. 200 m.A. Also 200 v. 80 m.A.; either at 8/9. TV. type, new, 300 v. 200 m.A., 12/9. P. & P. on rec. 1/-.


P.M. 12" 10" SPEAKERS 8" 6".

12in. Truvox, 47/6; 10in., 25/9; 8in., 18/8; 6in., 14/9; 5in., 13/9. All 3 ohms. Best makes. P. & P. 1/9.

TV. COLOUR FILTERS. for outdoor sports viewing, 6/9. 9in., 12in. and 15in., post 1/-.

STAMP ONLY FOR 1954 CATALOGUE.

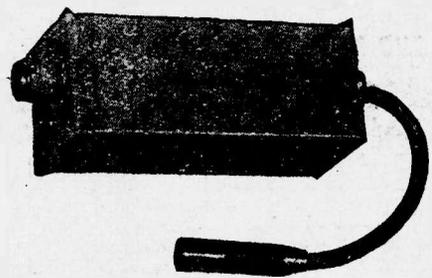— — — — — **at long last!**
TV INTERFERENCE ELIMINATED IN SECONDS!
 Announcing the latest **PLUG-IN HIGH-PASS FILTER** for TV Receivers



Removes interference from nearby Transmitting Stations (on 30 Mc/s or lower).


NO SOLDERING—ATTACHED IN SECONDS.

Does not even require back to be removed from set. Suitable for any set using co-axial aerial input.

PRICE **30/-** Retail from your local stockist.

In case of difficulty write to :

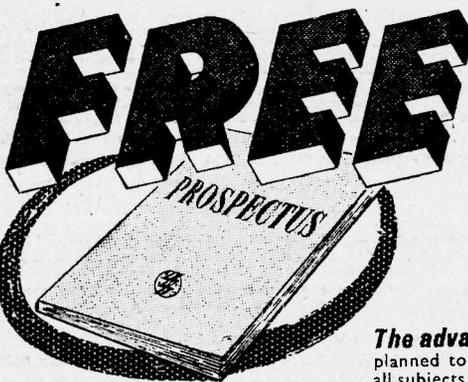Labgear (Cambridge) Ltd.
 WILLOW PLACE, CAMBRIDGE Tel. 2494—2 lines



POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES.

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME
 City and Guilds Grouped Certificates in Telecommunications; A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates. General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY.
 With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses from £1 per month

POST THIS COUPON TODAY

Send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 138K
 43 Grove Park Road, London, W.4.
 Phone: Chiswick 4417/8.

NAME.....
 ADDRESS.....
 SUBJECT(S) OF INTEREST.....
 AUGUST

EMI INSTITUTES
 The only Postal College which is part of a world-wide Industrial Organisation.

YOUR Problems SOLVED

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 143 must be attached to all queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

TUNING CIRCUIT ALIGNMENT

I have a Vidor TV CN369A, four years old. My trouble first started with sound on vision 18 months ago. The set has been out for repair twice since then with the same trouble. The last time it had not been on 10 minutes when both sound and vision cut out. On inspection I found it was the aerial trimmer faulty. I managed to get a new one with the same capacity (3/30 pF) and fixed it in. Now all is well if I could get a little more volume. I think the service engineer must have cut down the sound to minimum in one of the cores to stop sound on vision when the faulty trimmer was in. Could you please give me instructions to identify same?—J. D. Staniland (Gillingham).

The only real solution to this problem lies in having the receiver realigned. It is not possible for us to advise on the adjustment of a tuned circuit, which will provide an increase in sound sensitivity without upsetting the balance of the circuit generally.

BOOST FOR TUBE

Recently I fitted a 25 per cent. boost transformer to the C.R.T. (CRM92A) of my Baird portable. The resulting picture is definitely an improvement, and I told my friends.

As one of them has a similar tube in his set (an Ekco TS105) and which is giving a rather dim picture, he was interested in making the same improvement, so I got him one of these little transformers.

He complained that in his case his picture was worse with the boost, and was emphatic that he had made the right connections. Thinking there might have been something wrong with the transformer, I took it home and replaced my own with it. I can find nothing wrong with it.

I suggested a bad soldered joint or the use of too long leads of thin gauge wire was the reason of my friend's disappointment, so he had another try, mounting the transformer as close as he could (he said) to the tube base and using stout flexes. The result was again a dull picture which was slightly improved only when the transformer was discarded in disgust.

Can you give us some idea why this boost transformer should have such opposite effects on two similar tubes?—J. W. Day (N.1).

The success of the treatment described depends upon a number of factors which the experimenter cannot check, and it is a hit-and-miss operation from the practical aspect. In the case cited we feel that the tube emission might well be up to standard, but that the dim picture may be caused by deterioration of

the screen phosphors, and in this case, of course, nothing at all can be done to enhance the brightness.

FAULTY TUBE ?

My Baird television receiver portable T164 has developed a fault, and I hope you can help me.

If I advance the contrast control to obtain a good picture the whites tail off to the right, giving a fuzzy appearance; this happens also when brightness control is advanced. It seems very much like flaring, but I am not quite certain. I have a circuit diagram of this set.—G. Taylor (E.6).

Since you mention that the symptom can be provoked by advancing the brightness control as well as by advancing the contrast control, we feel that a fault may exist either in the E.H.T. section or in the tube itself. Your remarks indicate, of course, that a form of instability occurs when the tube bears current increases beyond a certain figure. This may originate in the E.H.T. circuit when called upon to provide more power; suspect the E.H.T. transformer and E.H.T. rectifier. On the other hand, an illusive tube defect sometimes gives rise to a similar symptom.

INTERACTION OR HUM ?

I am building the Beginner's Timebase as described in "Practical Television" at the end of last year. I am having trouble with the frame circuit, and I would be much obliged if you could help me.

With V6 and V7 inserted and the frame hold at almost maximum value I get on the screen two vertical lines that are straight at one end and appear to come together and then move about 1½ in. apart. In the middle they cross and then take the form of an "S" at the other end. At most other settings of the frame hold there appears a mass of similar lines moving rapidly, the "S" part moving down the screen. At nearly minimum setting of the frame hold three lines appear reasonably steady and similar to those mentioned before.

If I change the frame coupling to the tube from C11 and C10 to C8 and C9 (disconnecting the line) and obtain a horizontal line from the frame, I get exactly the same effect as before.

I do not think the proximity of the transformers and the choke can be the cause, because turning the tube round slightly makes no difference to the distortion of the lines.—J. Cartwright (Horley).

It is possible for the fault to be in the paraphase valve V7 or the oscillator itself. This point can be checked by working with V6 while V7 is out of circuit. If the wavy line persists, then the trouble is likely to be in the flyback circuit, and may not affect the raster when the picture is received. Check C14, 12, 15 for leakage and the components around this part of the circuit.

Some VCR97 tubes are more sensitive to external influence than others and you may be picking up some hum. If you find the edge of the raster is curved like an elongated "S," then hum is getting into the timebase from the E.H.T. network. Try the effect of connecting an 0.3 μF 2.5 Kv between the cathode of the C.R.T. and chassis.

If the edge is like a double "S" (one on top of the other), then hum is getting through from the main power supply and the smoothing arrangements must be checked.

INTERMITTENT C.-H. SHORT

I have an Echo television set Model T141.

For two and a half years I have had excellent results, until recently.

The picture now becomes slightly misty and flickers to an extent that it hurts the eyes to view it even for a short time.

I can obviate this by turning the contrast control: the picture then appears to be perfect; this lasts for a short time until I get double lines. I again adjust the contrast control.

I have also noticed that the changing of cameras at the studio affects my picture, or this is a coincidence? —Thomas Gibbs (E.16).

From the clues you have given to us we feel that the trouble may be due to an intermittent heater to cathode shoji in the picture-tube itself. In the first place, therefore, you should have the tube tested in this respect. Should a short prove to be the case, and if the emission of the tube warrants it, a low-loss tube heater isolating transformer could be employed to obtain a further lease of life from the defective tube. See "Operating With a Heater to Cathode Short," PRACTICAL TELEVISION, May, 1953.

SOUND REJECTOR CIRCUIT, CHANNEL 3

Would you please let me know the correct values for C1 and C2, also the number of turns of wire, as enclosed, for "L," on former 1 in. outside diameter tuned by 0 B.A. either brass or iron dust core slug (whichever you prefer)? —O. W. Kingsley (Hove).

You desire the circuit illustrated to resonate at 53.25 Mc/s—assuming, of course, that the receiver to which it is to be included is of the T.R.F. type. It would be a simple matter for us to compute an inductance value in the form of so many turns, and then work out the value of capacitance needed to produce a circuit that would tune to 53.25 Mc/s. This would be of little assistance to you, though, for it is essential to take into consideration the capacitive elements of the general circuit in order to discover the precise C.R. values of the rejector circuit.

These, of course, depend on the total value of valve, wiring, and circuit capacitances existing at the point at which the rejector circuit is to be installed. The way the associated valves are operating, and thus the Miller effect, will also have a governing factor on the precise values.

Generally speaking, a high "Q" circuit is desirable for the sound rejector. With this in mind, therefore, it may be desirable to form the inductor with six turns of 18 S.W.G. tinned copper wire—making it self supporting, and bringing it into resonance with a 30 picofarad air-dielectric trimmer. So far as the experimenter is concerned, this method of rejector circuit design is to be preferred. See "Sound Rejection," PRACTICAL TELEVISION, June, 1952, and "TV For the Beginner—Coil Winding," PRACTICAL TELEVISION, December, 1953.

TUBE FLASHOVER

I would be pleased if you could assist me in locating a fault which has developed in my home-constructed television set. The model in question is the one advertised by the Electronic Precision Equipment Co. in your journal, using the Cossor 85K 15in. tube. I enclose circuit diagram for your guidance.

The set has given reasonable reproduction for several

months, but has now developed the following fault:—

On switching on, after the usual warming-up period a sharp crack is heard, similar to that heard on the discharge of a large condenser, at the same time a spark can be seen inside the tube, but not apparently on the tube face. The discharge (?) can be brought about at will by advancing brilliance control and also occurs on switching off when the raster collapses. The flash seen is of a pinkish hue and is sometimes accompanied by faint fluorescence of the screen.—R. Dodson (Mexborough).

We feel that this symptom is caused by a fault inside the picture-tube itself. Sometimes the inner aquadag coating flakes, a section of which reduces the flashover distance between the final anode and a lower potential electrode.

FAULTY OSCILLATOR WAVEFORM

Could you please help me with a fault I have in my View Master?

The trouble is almost non-existent E.H.T. with the consequence that the tube doesn't light up. The voltage at the anode of V10 is only approximately 240 v. I have nil volts at anodes of V9 and V11. Also no boost volts across C51 and neon lamp doesn't light up.

Voltage at the mains choke is O.K. Also all valves have been checked. C51, C53, C54, all O.K. C55 was found to be dud and was renewed with no results.

MR4 was also changed but without success.

Sound is quite O.K.—W. J. Banner (Bromsgrove).

You have not given sufficient information to enable us to advise you with any accuracy, but from your description it is quite evident that thyatron V9 is not producing a sawtooth voltage for driving V10 and we suggest that you closely examine the wiring and components of the V9 stage and the input to V10.

E.H.T. RECTIFIER FAULTY

I would welcome your advice regarding trouble I am having with my Vidor model 391, 9in. receiver. The trouble is in the E.H.T. section and causes the E.H.T. rectifier (EY51) to arc as soon as the line whistle is audible.

I have had the EL38 checked and have replaced odd resistors and electrolytics in this section also the EY51 itself.

Outward appearance of the line transformer appears quite good with no signs of melted wax, etc. As a reader of your commendable journal since number one, I referred to issue No. 16, where you give the circuit of Vidor CN4207, which is very similar to my set, except for the E.H.T. section. However, are the values quoted (resistance) for the scanning coils, etc., the same as in the CN391? Hoping you will be able to assist me in this direction. Thanking you in anticipation.—D. G. Mathew (Birmingham).

This system is almost certainly caused by a deterioration of insulation in the heater circuit—E.H.T. line—of the EY51 valve. Disconnect the E.H.T. feed wire from the valve and switch on the set. If the flashover continues, suspect a short-circuit between the heater winding in the line output transformer. If, on the other hand, the flashover ceases, check the E.H.T. smoothing capacitor and picture-tube anode for a short to chassis. Check by removing from circuit each component in turn.

There are slight deviations of the resistance values of inductive elements between the different Vidor models.

BOOKLETS: "How to use ex-Gov. Lenses and Prisms." Nos. 1 and 2, price 2/6. Ex-Gov. Optical lists free for s.a.c. H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

R.F. UNITS, Types 26 at 37/6, 25 at 17/6, 24 at 12/6; brand new in original cartons. E.W.S. CO., 69, Church Rd., Moseley, Birmingham.

AMERICAN MAGAZINES.—One-year "Audio Engineering," 28/6, specimen copy. 3/-; "High Fidelity," 50/-, specimen copy. 4/6; "Popular Science," 28/6. Free booklet quoting others. WILLEN LTD. (Dept. 23), 101, Fleet Street, London, E.C.4.

ALL YOUR T.V. COMPONENTS, Valves, Books and Transformer Rewinds can now be obtained from one source. Send 9d. stamps for new "Replacement and Rewind Manual." "DIRECT T.V. REPLACEMENTS." 134-136, Lewisham Way, New Cross, S.E.14. (Tideway 3696. 2330.)

ELECTRONIC COMPONENTS. Send stamp for interesting comprehensive bargain list. A. J. S. McMILLAN, 5, Oakfield Rd., Bristol, 8.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

STORAGE BATTERIES, 12v. 75AH heavy duty, 19 plates, separate cells in hardwood cases; finest possible specification. £5/17/6, 9/6 delivery; 12v. 22AH, almost similar specification, surprisingly powerful. £2/14/-, delivery 5/6; 6v. 90 AH. 15 plates, hard rubber Cells, also suitable for cars, tractors, lorries, etc., £3/7/6, delivery 7/6; 6v. 150 AH, extra heavy duty, 25 plates, separate cells in hardwood cases, £5/7/6, delivery 8/6. TEDDINGTON ENGINEERING CO., LTD., Dept. "C," High St., Teddington, Middx. (KINGSTON 1193-4.)

SERVICE SHEETS for Radio and Television, over 2,000 models. S.A.E. enquiries. W. GILBERT, 24, Frithville Gardens, London, W.12.

VIEWMASTER Sound/Vision Chassis, assembled, aligned and tested, with specified parts, £7/15/6; with alternatives, £5/17/6; and a still cheaper version, £4/12/6; amazing value, fully guaranteed; send for details. Complete Viewmaster Kit, less speaker, only £23/17/6, with free alignment service for sound/vision chassis. MASSEY, 58, Wakefield Ave., Hull.

TELEVISION: Coilsets for all PT Television; Argus Simplex 21/-, Supervisor Lynx, AC/DC, 63/-; 4in. IP cans, tagged, with cores, 1/3 ea.; unwound Lynx Coil Kit, 11 pieces, 16/8; 4in x 4in. Paxolin Tube, 4in. 1/2; 4in. Poly Formers 8/- doz., 4in. 6/-. BEL, Marlborough Yard, Archway, London, N.19.

MAKE YOUR OWN TV Pre-Amplifier. Kit of all parts, 32/6. Sprayed Metal box, 9in. x 4in. x 3in. punched all holes, transformer, condenser, rectifier, mains lead, sub-chassis (wired) with wound coils and new EF80 valve; wiring diagram included. Building your own Aluminium Alloy Aerial? Wall mounting single dipole with 18in. stand-off, 12/6; "H" Aerial, complete set parts, 22/6; 3-element folded Dipole Kit, basically as Mr. Symonds' design in June, 1953, issue, comprising boom drilled all holes, element holders, elements, junction box screws, bolts, cast mounting bracket, 10ft. pole (2in.) and chimney lashings; £5 the lot, carr. pd. GLADSTONE RADIO, Gladstone Place, Newton, Abbot, Devon.

ARGUS TV, Holme Moss, Enlarger; good reception. Offers over £16. Box No. 171.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

EHT TRANSFORMERS for VCR97; brand new; made to specification; 2.5kV, 2v-0-2v, 2v-0-2v, 39/6, post paid per return post. Selector Unit type 10K/13045, relay operated on 6 or 12 volts, with rotary wheel action with twin-contacts; ideal for model enthusiasts. 3/9, post paid, W. B. SUPPLIES, 100, Oldham St., Manchester, 4.

PREMIER Console T.V., Complete, Less Vision unit, Doncaster District. Box No. 172.

BARGAINS. Transformers, all standard mains input 50c. (i) EHT 2.0kV, 5ma. 2v. 2a. 25/-; (ii) 350-0-350v. 150ma. 5v. 3a. 25/-; (iii) 6.3v. 5a & 6.3v. 10a. 20/-; (iv) 250-0-250v. 70ma. 6.3v. 3a. 4v. 2a. 10/6; (v) 350-0-350v. 120ma. 6.3v. 4a. 4v. 2a. 16/-; (vi) 600v. HW. 6.3v. 4a. 4v. 2a. 12/-; (vii) 345-0-345v. 200ma. 6.3v. 5a. 5v. 2a. 30/-; (viii) 14 or 20v. 15-20a. 30/-; (ix) Intervalve, 240v. input gives 1200v. output, 7/6; (x) 240v. input gives 75-0-15v, 15mA; 7/6; Chokes: 9H 100ma; 7/6; 9H 200ma; 8/6; 8H 50ma; 6/6; EHT Condensers: 0.1mfd 2.5kV, met. tub. 3/6; 0.1 1.5kV, small block 3/-; 0.25 2.5kV, larger block 3/6; 0.02 4.5kV, met. tub. 2/-; Mica resistance strips, 800µ .3a. with 2 taps 1/6. IFTs, new, canned, 10/13mcs. 1/-; R1355 (7mcs) Diode box, 2/-. Postage extra; on large transformers 2/-; smaller & chokes, 1/-. 1d. S.A.E. for list/enquiries. Immediate despatch. Cash with order. W. A. BENSON, 308 Rathbone Rd., Liverpool, 13.

12in. ELECTROSTATIC TUBES Type VCR.511. Tried and tested on T.V. Gives Blue-Yellow picture very similar to a commercial tube. Change your 6in. VCR.97 for a 12in. and enjoy large pictures without even changing the tube base. Price £4/17/6; carriage 10/6 extra. If you are not on our mailing list send stamp for new list to-day. "SERVIO RADIO 156/8 Merton Rd., Wimbledon, S.W.19. LIBERTY 6525.

SIMPLEX T.V. 18 swg. Chassis with screens and valve punched 17/6, post 1/6; fully-wound Coil Sets 15/-, post 1/-; Lynx-wound Coil Sets, 35/-, post 1/-; Super-Vision and Tele-King Coil Sets, 37/6, post 1/-; 4in. square Cans. Former, Side Wires, etc., 1/9 each; Simplex Mains Transformers, 27/6, post 1/6. C. O. PRESTON & SON, Healey Lane, Batley, Yorks.

WINWOOD FOR VALUE.—Valves: 9D2, 8D2, 4D1, EF36, CV54, 954, CV136, 6F33, 6K7, all at 3/6 each; Red, EF50, 6/6; 807, 7/-; G/mans 4in. P.M. 14/6; Fil/trans. 200/240v. 6.3v at 1.5a. 5/6; Coilpacks, 3-wave band, 23/6; T.R.F. Coils, M. and L., 5/6 pr.; Twin-gang, 0005 4/6; C/diodes, 1/6; Wey-Rad 465Ks I.F.S. 9/- pr.; Rev. Counters, ex-GPO 9999, 3/9. Full list, stamp. WINWOOD, 12, Carnarvon Road, Leyton, E.10. (Mail only.)

H.M.V. 9in. Radio/Television Console, not working, £13, 3, Park Ave. Barnet. (Tel.: 1934.)

TELEKING c/w new tube; R1355 c/w R.F. unit 24, built in P.P. audio stage R.F. unit 26, I.F. unit 35 in working order; various oddments: owner going abroad; offers? MELLORS, Woodland, Upper Colwall, nr. Ma'vern.

"VIEWMASTER" Valves, exact to specification; guaranteed new and boxed, set of 12, £5/15/-; "Tele-King" 17in. Receiver, complete set of 17 valves exact to specification, £28/19/6; 6AM6, EF91, 6F12, 27F, EB91, 6AL5, 6AM5, EL91 any 8 for 50/-, post 1/6; 1.4v. miniatures, 1S5, 1R5, 1T4, 3V4, 3Q4, N18, 3S4, 1S4, DK92, any 4 for 27/6, post 1/-; all guaranteed new and boxed. For individual prices and other types see displayed advert., p. 144. READERS RADIO, 24, Colberg Place, Stamford Hill, London, N.16. (STA 4587.)

PREMIER (S.C.) 9in. CRT, pre-amp, modified vision Strip; all data; suit beginner. Offers? WATSON, 68, Lansdown Rd., Gloucester.

"RADIO UNLIMITED" offer: Coilpacks, L., M., and Short with circuit, 24/6; V/master Coils, cplete, set, incl. choke, 17/6; Iso Trans. 25% boost for 2v. 4v. or 6v. 6/9; Heater Trans., 230/240v, O/pout 2v-3v in 4v steps at 2 amps, 16/-; Pre-set W. W. Contrl. 2/9; 5K and 25K 3-watt W. W. Contrl. 3/6; Metal Recs., RML1, 3/6; RML2, 4/3; RML3, 5/-; RML4, 15/-; Dubilier, 8 or 8-5000v, 3/6; 16 x 16-5000v, 4/6; 32-5000v, 4/3. Carbon Contrl. all values, 2/9; SP/sw, 4/-; Xtal Diodes, 1/6. Valves: 6AM6, 6/-; ECL80, 9/-; EF66, 10/-; 6V6, EL32, 6/9; 6L6G, 8/9. Over 13,000 valves in stock. Free list. RADIO UNLIMITED, Elm Road, London, E.17. (KEY. 4813.)

WANTED

NEW VALVES WANTED, small or large quantities. PL81, EY51, KT61, 524G, 5R4, 5U4, 3Q5, all television; prompt cash. WM. CARVIS LTD., 103, North St., Leeds, 7.

EDUCATIONAL

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast, or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the college operated by Britain's largest electronic organization; moderate fees. Write to E.M.I. INSTITUTES, Postal Division, Dept. PT28, 43, Grove Park Road, London, W.4. (Associated with H.M.V.)

I.P.R.E. Data for constructing TV Aerial-stretcher Meter, 7/6; 5,500 Alignment Peaks for superhets, 5/9; sample copy "Practical Radio Engineer," 2/-. Membership-examination particulars, 1/-. Syllabus of seven postal courses free and post free. SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

SITUATIONS VACANT

THE ENGLISH ELECTRIC VALVE CO., LTD. CHELMSFORD, requires the following technical staff for their Camera Tube Division: (a) Test Room Supervisor. (b) Test Camera Operator. Applicants should have H.N.C. in Radio Engineering or its equivalent, and some experience would be desirable. (c) INSPECTOR. Experience of Valve Assembly and process detail is necessary and a science degree would be a considerable advantage. (d) TECHNICAL ASSISTANT. H.N.C. is necessary for this vacancy, together with some knowledge of Vacuum/Chemical processing. (e) CIRCUIT MAINTENANCE ENGINEER. Some experience in this field is highly desirable together with suitable technical qualifications. IN CERTAIN CASES HOUSING ASSISTANCE MAY BE PROVIDED. Write with full details of qualifications and experience and quoting relevant vacancy and ref. SA52, to Dept. C.P.S., 336/7, Strand, W.C.2.

FOR YOUR SIMPLEX TV

1 MFD. 2.5 KV. CONDENSERS, OIL FILLED. 3 1/2 in. x 1 1/4 in. BRAND NEW. PRICE 4/5 EACH. 5 FOR £1. Hunts .025 + .025 mfd., 7 Kv. wkg. Condensers. Block type. 3/8 each. 3 for 10/- .05 mfd., 2.5 Kv. wkg. at 2/6 each. .25 mfd., 1,500 v. at 2/6 each. .1 mfd., 1,200 v. wkg. at 1/9 each.

INDICATOR UNIT, TYPE 233. Complete with VCR97 C.R.T., 3-VR91 (EP50), 3-VR65 (SP61), 2-VR92 (EA30) Valves, Resistors, Condensers, (including .1 mfd., 2.5 Kv.), Pots., etc. Price 49/6 plus 5/- carr. in transit cases.

INDICATOR UNIT, TYPE 157. Has same line-up as INDICATOR UNIT, TYPE 62, viz.: VCR97 C.R.T., Mask and Mu Screen, 10-SP61, 2-EB94, 4-EA30 Valves, 15 Potentiometers, Resistors, Condensers, Muirhead S.M. Dial, etc. BRAND NEW, IN TRANSIT CASE. Price £37/7 1/2 plus 7/6 carr.

R.F. UNITS, TYPE 28. Covering 50 to 65 Mc/s. Complete with all valves. Brand New in Carbons. Price 35/- plus 2/6 post. Also R.F. UNITS, TYPE 24. Complete with all valves. Slightly soiled on outside. Price 14/6 each, plus 2/6 post.

194 I.F. STRIP. The well-known I.F. Strip for TV conversion. Complete with 6-VR65, 2-VR92 (EA30), EF39 Valves. A few on hand available at 35/- each, plus 2/6 post.

RUBBER MASKS for 12in. C.R. TUBES. Modern type which fixes to cabinet. 3/6 each, plus 1/- post.

TRANSLUCENT PROJECTION SCREENS. (Size 15 1/2 in. x 12 in.) as used in Projection Television and Epidiascopes. Price 7/6 each.

MU METAL SCREENS for VCR97, VCR517 C.R. Tubes, etc. Price 6/6 each, plus post.

COIL FORMERS. Manufacturing type. 1in. with Iron Dust Cores. Wound to TV frequencies. 2/6 doz.

VALVES. VR55 (SP61), EA50, all at 2/6 each. EF50 at 5/- each.

GERMANIUM CRYSTAL DIODES. Wire-ended 1/8 each. 13/6 doz.

ION TRAPS. Type IT6 for 35mm. Tubes. 2/6 each, post paid.

SPEAKER TRANSFORMERS. Multi-ratio. 80:1, 32:1, 65:1, 60 mA max. Brand New at 3/9 each plus 9d. post.

L.F. CHOKES. 16 Henries, 60 mA. 2 1/2 in. x 1 1/2 in. x 2 in. Ideal for small receivers, etc. 4/6 each, plus 9d. post.

C. MARKS AND CO.,

90, COMMERCIAL ST., NEWPORT, MON.

Telephone: Newport 4711.

Also at 25, WYNDHAM ARCADE, CARDIFF.

ALL MAIL ORDERS AND ENQUIRIES TO NEWPORT BRANCH, PLEASE.



QUALITY TELEVISION COMPONENTS

SCANNING COILS

6/10 KV. R.F., E.H.T. UNITS

E.H.T. and OUTPUT TRANSFORMERS
LINE FLY-BACK E.H.T. UNITS

Write for illustrated list (Publication 75)

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

Here is "CONSTRUCTOR'S CORNER"

A Jy-return service for the amateur radio constructor. **GRAMOPHONE 3 SPEED INDICATORS.** Made in high grade Ivorine, stroboscopic for A.C. mains, will give an exact check of speed at 33, 45 and 78 r.p.m., 1/6.

RESISTOR COLOUR CODE CALCULATORS. All moving parts made of high-grade Ivorine and sized to slip into the pocket. Gives exact values and tolerances of all colour coded resistors. 1/6.

"BIB" THE NEW WIRE CUTTER AND STRIPPER. Cuts wire and strips insulation without nicking. Adjustable to different gauges. A fine little tool. 3/6.

"SOLO" INSUREMENT SOLDERING IRON No. 625. 220/240 v. 25 watts. Overall length, 9in. Detachable pencil bit. Ideal for all radio and TV work. Supplied complete with flex and only 19/8, post paid.

ALUMINIUM PANELS. 10in. x 8in., 3/-; 12in. x 9in., 4/2; 14in. x 10in., 5/3.

Cash with order or C.O.D. Please add postage under £1. Block letters please. Callers very welcome.

HOME RADIO OF MITCHAM 187, London Road, Mitcham, Surrey.

MIT 3282. Open Every Day Until 6.30 p.m. (Weds. 1.0 p.m.)

FIRST-CLASS TELEVISION and RADIO COURSES . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Science and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M. Brit. I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches),** etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER

150,000 SUCCESSSES

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

Just Published—

PRACTICAL TELEVISION CIRCUITS

by F. J. Camm

Photographs, Wiring Diagrams and Constructional Details for Cheap and Efficient Home-Built TV. Receivers, with additional chapters on Pre-Amplifiers, E.H.T. Generators, Pattern Generators, Test Gear, etc. 15s. 0d. Postage 6d.

The Oscilloscope at Work, by A. Haas and R. W. Hallows. 15s. 0d. Postage 6d.

Television Circuit Refinements, by C. H. Banthorpe. 5s. 0d. Postage 3d.

Television Engineers' Pocket Book, edited by E. Molloy and J. P. Hawker. 10s. 6d. Postage 6d.

Crystal Rectifiers and Transistors, edited by M. G. Say. 21s. 0d. Postage 6d.

"Practical Wireless" Circuits, by F. J. Camm. 10s. 6d. Postage 4d.

The Radio Amateur's Handbook, by the "A.R.R.L." 30s. 0d. Postage 1s. 0d.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS OF BRITISH AND AMERICAN TECHNICAL BOOKS

19-23 PRAED STREET

(Dept. T.8)

LONDON, W.2.


Please write or call for our catalogue.

Phone: PADdington 4185

Open all day Saturday.

MAST HEAD UNITS

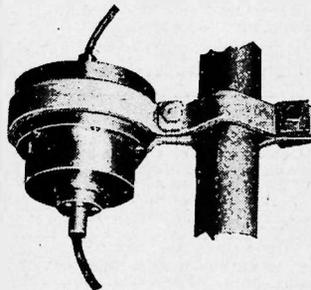(Gain approximately 15dBs. Noise factor approximately 2dBs.)



Beautifully designed and engineered. Incorporating a Cascade connected amplifier and suitable for use with all types of aerials. Supplied complete with power supply unit and mounting bracket as illustrated. Descriptive leaflet on request.

Price complete with 40ft. £19-0-0

(sent carriage and packing free or available from your Dealer).

SPENCER - WEST

Quay Works, Gt. Yarmouth

News from the Trade

T.C.C. CATALOGUE

AN impressive new catalogue has been produced by the makers of the well-known T.C.C. condensers, and this is finished in six colours each dealing with a separate type. Paper, Electrolytic, Mica, Ceramic, Plastic film and special purpose are separately colour-identified and the art paper pages give all the relative data concerning each type. Of the loose-leaf type this handsome 108-page production, in quarto size, is well worth study.—The Telegraph Condenser Co., Ltd., North Acton, London, W.3.

THE RADAR "405" DUAL-BAND SIGNAL GENERATOR

THE Radar Television Signal Generator Type 405 is a portable signal source intended mainly for use in the service department and by outside service engineers in the absence of transmissions. The instrument provides both sound and vision R.F. signals for injection into the aerial socket of a receiver and the complete Video signal is available for connection to the video stage. The generator covers all channels in Bands I and III and tuning is continuously variable over each band. Sound and vision carriers are independently tuned and may be used simultaneously. The output of the combined signals is continuously adjustable by a variable output attenuator over the range of 10 microvolts to 10 millivolts.

The Video modulation allows a choice of patterns affording facilities for the rapid checking and adjustment of line and frame hold, picture width and height, linearity and contrast gradation. Fine vertical rulings with a short rise-time allow "ringing" and overshoot to be checked. A plain raster with correct blanking is available at peak white or black level, enabling the interlace to be readily inspected. The raster may also be inspected for hum or sound-on-vision very easily.

The synchronising waveform is strictly to BBC standards with correctly interlaced frame sync. The half-line pulses and the correct front and back porches are included.

The sound R.F. carrier is internally modulated at 750 c.p.s. to a depth of 30 per cent. and the level is 10 dB below peak vision carrier at all settings of the attenuator.

The generator employs 16 double valves of the new "World Series" type apart from the rectifier, and the complete equipment is built into a case measuring only 12in. x 9in. x 6½in. and weighing only 18 lbs. A useful feature is the provision of internal storage of leads, etc. The instrument is for use on A.C. mains 200 to 250 volts, 50 cycles.

The price is £52 nett trade (not subject to P.T.) and delivery is through normal wholesalers or from the manufacturers, Waveforms, Ltd., Radar Works, Truro Road, London, N.22.

NERA MODELS CP48, CP40 AND CP30

THIS new large-screen receiver has been designed for accommodation in the smaller sized room. An ingenious folded beam arrangement reduces the

distance normally required between projector and screen by about 2ft. The small veneered cabinet of contemporary design presents an attractive appearance.

This model is intended for projecting the picture on to a wall screen, and in operation the lid is raised, automatically switching on the receiver and adjusted to position the picture at the height required.

A single 8-in. speaker, mounted below the lid of the cabinet, gives full-quality, non-directional sound reproduction. With this exception, the receiver embodies all the outstanding refinements of other Nera models, giving a picture of outstanding quality and definition. It employs interchangeable chassis



The Radar "405" signal generator.

for the R.F., time base, and power supply units, a method which facilitates rapid servicing, since a complete chassis may be changed in a matter of minutes should a fault occur. The standard Nera remote control panel is fitted, giving complete control over brilliance, contrast, focus and sound volume. This remote control is normally supplied to operate at any distance up to 20ft. from the receiver, but this distance may be extended to order, as required. Model CP48, picture size 4ft. x 3ft. Price, £146 10s., less screen, tax free. Model CP40 and CP30, picture sizes, 40in. x 30in., and 30in. x 22½in., respectively. Price, £197 15s. 6d., less screen, including tax. Dimensions, 28in. wide, 25in. high, 19in. deep.—Nera of England Ltd., Jefferies Passage, High Street, Guildford.

QUERIES COUPON

This coupon is available until August 21st, 1954, and must accompany all Queries.

PRACTICAL TELEVISION, August, 1954.

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.T. SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEPherds Bush 1729

H.V. CONDENSERS.—As specified for the "Simplex" May "P.T." 0.1 mfd. 1.5 Kv. working. PRICE 2/6 each, post free.

THIS MONTH'S VALVE SPECIALS.—CV138 equiv. EF01, 6AM6, 27T. PRICE 7/6 each. Type 866A. PRICE 12/8 each. VR65A (SP81, 4 v. Htr.). PRICE 2/6 each, post 6d.; 3 for 9/-; or 6 for 10/-. All as new and guaranteed.

ANOTHER SPECIAL BARGAIN THIS MONTH.—I.F.F. Units, less valves and relays, fitted with mica. metal case and variable condensers, resistors, valve holders, etc. Most important: a rotary converter for 12 v. D.C. input and having an output of 480 v. at 40 mA. A rear box is attached to the converter with 3 separate driving shafts reducing speed of rotation to approx. 21, 5 and 10 r.p.m. Overall size of complete unit 12 x 12 x 8 in. In good clean condition. A tip top buy for model maker and experimentalist. PRICE ONLY 9/6, carriage 5/-, 3 or more carriage free.

THERMOMETERS.—Consist of a circular glass fronted dial 2in. dia. with metal temperature detection stem protruding 5in. at right angles from back of dial. The temp. is clearly calibrated on the dial's face from -70 deg. C. to +50 deg. C. and is indicated by a rotating pointer. PRICE 10/6, post 9d.

AERIAL MASTS.—Consist of two sections of stout all-weather resisting paxolin tubing, each 7ft. long x 3/16in. wall and respective dials of 1 1/2 and 2in. The sections plug into each other by means of metal ferrules. Guy ropes, etc. are not provided. Total weight only 5lb. PRICE 14/6, carriage 2/6.

OPPORTUNITIES IN TELEVISION

144 pages
Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

We Guarantee "NO PASS—NO FEE"
If you are earning less than £15 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

WRITE TODAY!

British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane,
Kensington, W.8. **BIET**

Introducing the:—



TYANA TRIPLE THREE

MAKE SOLDERING A PLEASURE

SMALL SOLDERING IRON

Complete with detachable BENCH STAND 19/6
The smallest high-power soldering iron. Length only 8 1/2"; adjustable long bit dia. 3/16"; mains voltages 100/110, 200/220, 230/250.

The "STANDARD" Popular Soldering Iron now reduced to 14/11. Replacement Elements and Bits for both types always available.

KENROY LIMITED
152/297 UPPER ST., ISLINGTON, LONDON, N.1.

Reg. Design No. 867894

Telephone: Canonbury 4905-4663

HIGH GRADE TRANSFORMERS

FOR ALL PURPOSES
SINGLY OR IN QUANTITIES
TO YOUR SPECIFICATION

VARNISH IMPREGNATED
BAKED WINDINGS
WITH OR WITHOUT TAG PANELS
GOOD DELIVERIES
Our rewind dept. will handle your repairs promptly and efficiently.
S.A.E. with enquiries please.

P. HOWORTH
(Dept. P.T.)
51 POLLARD LANE - BRADFORD
Tel: 37030

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH
CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE

(DEPT. B)

72-76 Leather Lane,
Holborn, E.C.1
Phone: CHAncery 6791/2

When replying to advertisers' announcements please mention "Practical Television."

1954-5

CATALOGUE

JUST RELEASED

- ★ 60 PAGES
- ★ 2000 COMPONENT TYPES
- ★ 500 ILLUSTRATIONS
- PRICE 1/-

COVENTRY-RADIO

189, DUNSTABLE ROAD, LUTON

Tel: Luton 2677

COMPONENT SPEC'ALISTS SINCE 1925

GUARANTEED NEW BOXED VALVES

Same Day Service

1A7GT	15L	6LD20	9/8	3524GT	1EM34	11/-
1C3GT	7/8	6P25	15/-	3525GT	8/6	EY61 12/-
1H5GT	7/8	6Q7GT	9/-	3526GT	8/6	E240 9/-
		6SN7GT	9/-	50L6GT	8/6	E241 9/-
1N5GT	12/-	6U4GT	9/-	50L6GT	8/6	C232 15/-
		6U4GT	8/6	50L6GT	8/6	HVR2A
1R5	7/8	6V6G	17/-	80	8/6	6/9
1S4	7/8	6V6GT	7/8	807	8/6	KT33C 12/-
1S3	7/8	6X4	7/6	A231	10/-	KT63 7/6
1T4	7/8	6X5GT	6/8	CV31	12/-	MU14 8/6
3Q4	7/8	7B7	7/8	DAC32	12/-	N7R 15/-
3Q5GT		7C5	7/6			PL38 18/6
		7C5	7/6			PL81 11/-
		7C5	7/8	DF33	12/-	PL82 11/-
3V4	7/8	7H7	7/8	DH77	8/6	PY80 9/6
3V4	7/8	7S7	7/8	DK32	15/-	PY81 10/6
5Y3GT	7/8	7Y4	8/8	DK32	7/8	PY82 8/6
5Z4G	8/6	10C1	12/6	DL33	12/6	PZ30 17/-
6A7	10/6	10C2	12/6	DL35	7/8	R19 13/6
6AR6	9/-	10P1	10/8	EAC91	8/-	SP41 3/8
6AL5	6/8	10P9	10/6	EAF42	8/6	SP61 4/6
6AM5	7/8	10LD11			10/6	U22 7/6
6AN6	8/8		10/-	E891	6/8	U25 13/6
6AT8	8/6	10P13	10/6	EBC33	7/8	U50 7/8
6BA6	7/8	12A6	7/8	EBC41	10/-	U78 8/8
6BE6	7/8	12AT7	9/-	EBF60		U94 9/-
6B6B	7/8	12A7	10/6			UB41 8/6
6B36	7/8	12AX7	7/8	ECC81	9/-	UB41 8/6
6BW6	7/8	12K7GT	9/-	ECC91	12/-	
6CH6	8/6	12K8GT	9/-	ECH42	10/-	UBF80 10/-
6C1	7/8		10/6	ECL80		12/6
6C3	10/6	12Q7GT	9/-	EF39	7/8	UCH42
6F1	10/6		9/-	EF39	7/8	
6F6G	7/8	20D1	8/6	EF41	9/-	UF41 10/-
6F12	6/8	25L6GT	8/6	EF50	7/8	UF42 13/6
6F15	10/6		8/6	EF54	8/-	UL41 9/-
6J6	8/8	25Z4G	9/-	EF80	10/6	UL44 13/6
6J7GT	7/8	25Z5	8/6	EF91	6/8	U08 17/-
6K7C	6/-	25Z6GT	8/6	EF92	5/8	U08 9/-
6K7GT	6/-		8/6	EL38	22/6	UY41 9/-
6K8C	9/-	35L6GT		EL41	10/-	W77 5/6
6K8GT	9/-		8/6	EL91	7/8	Z77 6/8

Postage 4d. per valve extra.
See special offer in classified advert. page 14.

READERS RADIO 24, Colberg Place, Stamford Hill, London, N.16. STA 4587.

HOME BUILT TV

Full HP Facilities • Return Post Service

SIMPLEX

Stage 1, £5/3/- Stage 2, £4/4/- Stage 3, £6/-/-
Stage 4 (less C.R.T.), 14/6. Sundries Kit, 13/-.

All items available separately. Send for list.

VIEW MASTER

We have fully detailed lists available for all versions of the View Master. -Any of these will be sent free upon request.

INSTRUCTION MANUALS

Standard set. For 9in. or 12in. tube, 7/6. Wide Angle Conversion, 16in. and 17in. tube, 3/6.

WATTS RADIO (Weybridge) LTD.

8, Baker Street, Weybridge, Surrey

Phone : Weybridge 2542

LINE E. H. T TRANSFORMERS REWOUND PROMPTLY

Our 30 years' experience of winding and wave-winding enables us to provide the finest service in the Country for all types of TELEVISION COMPONENTS.

We repair or manufacture transformers singly or in quantity, and welcome your enquiries.

Catalogue on request.

H. W. FORREST,


349, HASLUCKS GREEN ROAD,
SHIRLEY. BIRMINGHAM.

COVENTRY TECHNICAL COLLEGE

Session 1954-55

ELECTRONIC ENGINEERING

Applications invited for entry to 3 year full-time course commencing September, 1954, from those requiring comprehensive training to advanced level in ELECTRONIC ENGINEERING, qualifying for technical posts in radio, telecommunications, television and industrial electronics. Syllabus will cover requirements of C. & G., Brit.I.R.E., and I.E.E. examinations. Entry age 16 or over. Application forms and further information from Principal, Technical College, The Butts, Coventry.

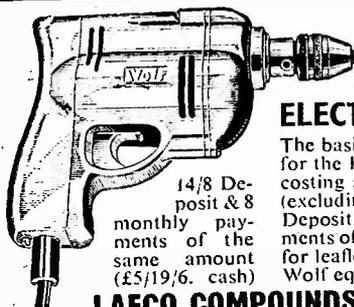

WOLF CUB

$\frac{1}{4}$

ELECTRIC DRILL

The basic item in an outfit for the Home Constructor costing £16.17.6 complete (excluding fretsaw) or 41/3 Deposit & 8 monthly payments of the same amount (£5/19/6. cash) for leaflet giving details of Wolf equipment.

LAFCO COMPOUNDS LTD. (DESK 19)

3 CORBETTS PASSAGE, ROTHERHITHE NEW RD. S.E.16. BERMONDSEY 4343.

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP,
WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
SLOane 3463

Works:

36, ROSEBERY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester,
Birmingham, Leeds.

"No Quantity too Small"

BENTLEY ACOUSTIC CORP. LTD.

38, Chateaufort Road, N.W.1.	PRImrose 9090.	
2D21 8/6	6J6 7/-	ACT23 10/6
5U4G 8/-	6K8 8/-	EB91 6/6
5Z4 8/6	10P1 10/6	EF39 6/6
6AMC 6/6	10P13 10/6	EF50 5/-
6BA6 7/-	12AT7 7/-	EF54 6/-
6BE6 7/-	12BE6 7/6	EF80 10/6
6BJ6 7/6	20F2 8/6	EL91 7/-
6BW6 7/6	20L1 12/6	EL91 11/6
6CH6 6/6	807 7/6	NT8 20/6
6F33 9/6	5763 9/-	PL33 20/6
		PZ30 12/6

Post 6d. extra. 24 hr. C.O.D. Service.
Refund Guarantee. S.A.E. for full List.

RADIO AND TELEVISION COMPONENTS

All parts in stock for:
VIEWMASTER, SOUNDMASTER,
TELEKING, ETC.

Easy Terms Available.
Stamp for list; NOT S.A.E.

JAMES H. MARTIN & CO.
Finthwaite, Newby Bridge.
Ulverston, Lancs.

TELEVISION COMPONENTS

always in stock for the
**P.T. LYNX, TELE-KING
P.T. SUPER-VISOR**

THE E.E. TELEVISOR AND VIEWMASTER

Viewmaster wide angle conversion
instructions 3/6d. List available.

**SOUND MASTER and
CORONET FOUR**
components also in stock

Separate price lists available on request.

J. T. FILMER,
Maypole Estate, Bexley, Kent
Tel: Bexleyheath 7267

National Radio Exhibition

Earls Court

August 25th—September 4th

'On Stand 85 the interests of the amateur set builder have not been overlooked. A section with expert personnel in attendance is devoted to showing the 'English Electric' Reconditionable Metal/Glass C.R. tube. The tubes, for which full line and frame scanning information and construction notes are supplied, together with examples of complete receivers built by amateurs, are presented for examination and discussion.'

Extract from the Official Catalogue.

Come along and see us on Stand 85 or write for information to

'ENGLISH ELECTRIC'

The ENGLISH ELECTRIC Company Ltd., Television Department, Queens House, Kingsway, London, W.C.2