

IMPROVED BAND III CONVERSION

Practical Television 1's

AUGUST 1956


AND TELEVISION TIMES

EDITOR: E.J. CAMM



NEW SERIES


*A Beginner's Guide
to Television.*

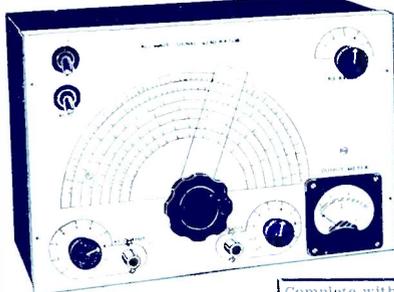

COMPLETELY BUILT SIGNAL GENERATOR

Completely built Signal Generator, coverage 120 Kc. s-320 Kc. s, 500 Kc. s-600 Kc. s, 900 Kc. s-2.75 Mc. s, 2.75 Mc. s-48.5 Mc. s, 8 Mc. s-29 Mc. s, 16 Mc. s-56 Mc. s, 24 Mc. s-84 Mc. s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated R.F. output continuously variable 100 milli-volts. C.W. and mod. witch, variable A.F. output and moving coil output meter. Black crackle-finished case and white panel. Accuracy plus or minus 2%. **£4.19.6** or **34/-** deposit and 3 monthly payments 25/- P. & P. 1/6 extra

COMMERCIAL TELEVISION CONVERTER

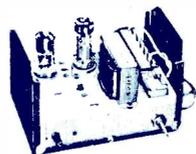


Illustrated a converter known as **SUITABLE ANY T.V.** No Alterations To Set **£3.19.6** Plus Post & Pk. 2/6

Complete with built-in power supply, 230-250 v. A.C. mains. Crackle finish case 5 1/2 in. long, 3 1/2 in. wide, 1 1/2 in. high incorporating gain control and band switch.

Less power supply **£2.19.6** P. & P. 2/6

BOTH GENERATORS GUARANTEED FOR 12 MONTHS

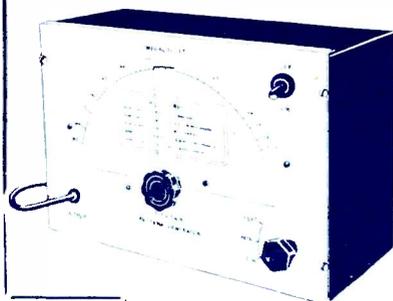

PATTERN GENERATOR

40-70 Mc. s direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits and vision channel band width. Silver plated coils, black crackle-finished case 10 x 6 1/2 x 4 1/2 in. and white front panel. A.C. mains 200-250 volts. This instrument will align any T.V. receiver, accurate v plus or minus 1%. Cash price **£3.19.6** or **29/-** deposit and 3 monthly payments of **£1. P. & P. 1/6** extra. Line or Frame oscillator Blocking Transformers, 4/6 each. Smoothing Choke, 250 mA, 5 henry, 8/6; 250 mA, 10 henry, 10/6

3-speed TRANSCRIPTION MOTOR BY FAMOUS MANUFACTURER

Complete Kit of parts comprising accurately balanced, precision made, heavy turntable with rubber mat, large constant speed condenser start motor, base plate. Can be assembled in half an hour. **£6.19.6** Parts sold separately Post Paid.

BAND III CONVERTER KIT

comprising 5 channel tuner, main transformer, metal rectifier, electrolytic, 2 valves, 12AT7 and EF80, and all necessary components for A.C. mains operation. Complete with conversion data.

£2.5.0 P. & P. 2/6.

Three-speed automatic changer by B.S.R. MONARCH, current model. Will take 7in., 10in., or 12in. records mixed. Turnover crystal head. Cream finish. BRAND NEW.

VERY LIMITED QUANTITY. A.C. Mains 200-250. **£7.15.0.** P. & P. 3/6.

Line and E.H.T. Transformer, 9kV. Ferronart core. EY31 heater winding, complete with scan coils and frame output transformer and line and width control. **35/-** P. & P. 3/-

As above but complete with line and frame blocking transformers, 4 henry 250 mA choke, 100 mid, and 150 mid, 350 wkr., 380 mA. A.C. ripple. **£2.9.6.** P. & P. 3/-

Standard wave-change switches, 4-pole 3-way; 5-pole 3-way; 3-pole 3-way, 1/9 each; 3-pole 3-way, 3/6; Miniature type, long spindle, 4-pole 3-way and 4-pole 2-way, 2/6 each. 2-pole 11-way twin water, 5/-; 1-pole 12-way, 5/- P. & P. 3/4

USED metal rectifier, 250 v. 150 mA., 6/6.

Combined 12in. Mask and E-scutcheon perspex. New aspect, edged in brown. Fits on front of cabinet. 12/6. As above for 15in. tubes, 17/6.

Polishing Attachment for electric drills. 1in. spindle, chromium plated 5in. brush, 3 polishing cloths and one sheepskin mop mounted on a 3in. rubber cup. Post & pkr. 1/6. 12/6. Spare sheepskin mops, 2/6 each

R. & T.V. COMPONENTS (ACTON) LTD.
23 HIGH STREET, ACTON, LONDON, W.3

16in. TUBE BY FAMOUS MANUFACTURER

Brand new E.H.T. 11 Kv. Heater, 6.3 volts, 0.5 amp., guaranteed 3 months, **£9.19.6.** Post, packing and insurance 2/6. H.P. terms available. E.H.T. and scanning components available.

Wide Angle P.M. Focus Unit, Vermer add., state tube, 15-P.M. Focus Unit for Mullard tubes with vermer adjustment, 15/-

Ion Traps for Mullard or English Electric tubes, 5/- Post paid. T.V. Coils, moulded former, iron cored, wound for rewinding purposes only. Also an 12in. 3 in., 1 - each, 2 iron-cores African, 2 1/2 in. x 3 in., 1/6 each. These coil formers are suitable for the 'Prac.' T.V. Converter.

Doublier .001 10kV, working 3/6
Primary, 200-250 v., P. & P. 2/-
100-0-300, 100 mA, 6 v, 3 amp., 5 v, 2 amp., 22/6.
Drop thro' 350-0-350 v, 70 mA, 6 v, 2.5 amp., 5 v, 2 amp., 14/6.
Drop thro' 250-0-250 v, 80 mA, 6 v, 3 amp., 5 v, 2 amp., 14/6.
290-0-290, drop through, 80 mA, 6 v, 3 amp., 5 v, 2 amp., 14/6.

GARRARD RC/110 3-SPEED AUTOMATIC CHANGER

10 Records, turnover crystal head. BRAND NEW. A.C. Mains, 100-250 v. **£8.19.6** P. & P. 1/6. LIST PRICE £14.10.0

Drop thro' 370-0-270 80 mA, 6 v, 3 amp., 11/6.
250 v. 350 mA, 6.3 v, 4 amp., twice 2 v, 2 a., 19/6.

Semi-shrouded drop-through 380-0-380 120 mA, 6.3 v, 3 amp., 5 v, 2 amp., 25/-

Auto Trans., Input 200-250 H.T. 500 v., 250 mA, 6 v, 4 a., twice 2 v, 2 a., 19/6.

Auto Trans., Input 200-250, H.T. 350 v., 350 mA. Separate L.T. 6.3 v, 7 a., 6.3 v, 11 amp., 5 v, 3 amp., 25/- P. & P. 3/-

Heater Transformer, Pri 230-250 v, 6 v, 11 amp., 6/-
350-0-350 75 mA, 6.3 v, 3 a. Tap, 4 v, 6.3 v, 1 a., 13/6.
500-0-500 125 mA, 4 v, C.T. 4 a., 4 v, C.T. 4 a., 4 v, C.T. 2.5 a., 27/6.
500-0-500 250 mA, 4 v, C.T. 5 a., 4 v, C.T. 5 a., 4 v, C.T. 4 a., 39/6.

Chassis mounting or drop-thro'. Pri 110-250 v. Sec. 350-0-350 250 mA, 6.3 v, 7 amp., 6.3 v, 0.5 amp., 5 v, C.T. 0.5 amp., 4 v, 4 amp., 32/6. P. & P. 3/6.


P.M. Speakers, closed field 3 ohm speech coil 12in., 25/-; 10in. 25/-; 8in., 20/6; 6in., 18/6; 5in., 18/6. P. & P. 2/- each extra. 1,200 Ft. High Impedance recording tape on aluminium spool, 12/6 post paid.

Valve Holders, moulded octal Mazda and loctal, 7d, each. Paxolin, octal Mazda and loctal, 4d, each. Moulded 167G, 8BA and 89A, 7d, each.

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to 11 and 2/6 up to 12. All enquiries S.A.E. Lists 5d, each.

LASKY'S RADIO

FAMOUS MAKE TURRET "TELETUNER"

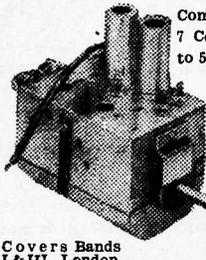

Complete with 7 Coil Sets, 1 to 5, 8 and 9.

99/6

Post 2/6, Knob, 3/6 extra.

Covers Bands I & III, London and Birmingham. Valves used: FCC94, R.F. double triode, cascade R.F. amplifier, PCF80 triode pentode i.c. and mixer. I.F. output 33-36 Mc/s easily modified to other I.F. outputs. Full instructions and circuit diagram supplied.

All Types Band III Aerials

All Channels, 3-, 4-, 5- and 6-element outdoor, also indoor and loft types. Aerialite, King Pin, Labgear, Belling Lee Wolsey, etc. Also Diplexes, Cross-over Boxes, Co-axial Plugs, Co-axial Sockets.

CO-AXIAL CABLE. 80 ohms semi-spaced, 8d. yd. 300 ohms Feeder, 9d. yd.

Biggest Bargain Ever Offered in TV Cathode Ray Tubes!



16" METAL CONE C.R.T.
6.3 v. heater, Ion trap, 14 Kv. E.H.T., wide angle 70°, standard 38 m.m. neck, duodecal base, magnetic focus and deflection.

Length 17 11/16in. Gives large black and white picture 11in. x 14in. Unused in original cartons. Guaranteed by us 3 months. Full data, connections and suggested time bases supplied with every Tube.

LISTED AT £23.9.10

LASKY'S PRICE £9.19.6

Carr. & Insur. 22/6 extra. Masks, Anti-Corona Rings, Bases and Ion Traps available.

12-CHANNEL TV TUNER

Famous make. Covers Bands I and III. Complete with valves EF80 and ECC81. Ceramic valveholders, finest quality components, Switch and fine tuning, I.F. output 20-22 Mc/s, Freq. coverage 50/87 Mc/s and 175-215 Mc/s. Supplied with full details and circuit diagram. Post 3/6. Knob, 2/9 extra. **79/6**

MAIL ORDERS TO HARROW ROAD PLEASE
LASKY'S (HARROW ROAD) LTD.

42, TOTTENHAM COURT ROAD, W.1.

Telephone: MUScum 2805.

370, HARROW ROAD, PADDINGTON, W.9.
LADbroke 4075 and CUNningham 1979.

Open all day SATURDAY. Half day Thursday.

WIDE ANGLE T.V. COMPONENTS

Will match our 16in., or any other wide angle C.R. Tube. Line Output E.H.T. Trans. Perroxcube, with EY51 winding, 9-14 kV, 25/-, Deflection Coils, Perroxcube, 25/-, Width and Linearity Controls, each 3/6.

SPECIAL OFFER. Line Output Trans., with width and linearity controls and deflection coils to match, pair, 50/-.

Ion Traps each, 3/-, Deodecal Bases, Paxolin, 9d.

Amphenon, 1/6,

Focus Magnets, with vernier, 17/6.

Frame Output Trans., 8/6.

Frame or Line blocking osc. Trans. each, 4/6.

All types of Masks, 14, 16, 17in., rubber or plastic.

BAND III CONVERTERS


2 valves and metal rectifier. Metal case, own power supplies, for A.C. 200/250 v. Listed at **£8.10.0**

LASKY'S PRICE 79/6.

COMPLETE 5-VALVE RADIO CHASSIS

Brand new and unused. A.C./D.C. 200/250 v. I.F. 465 kc/s. A.V.C., 4 watts output, 3-station pre-set, frame aerial, fully aligned, chassis 10 x 5 1/2 in., max. height 5 1/2 in. Completely wired and ready for use with the addition of a speaker and output transformer. Two controls, volume and station switch. Valves used: 10C1, 10F9 or UF41, 10LD11, 10P14, U404 or UY41. Ideally suitable as radio receiver for inclusion in a TV set.

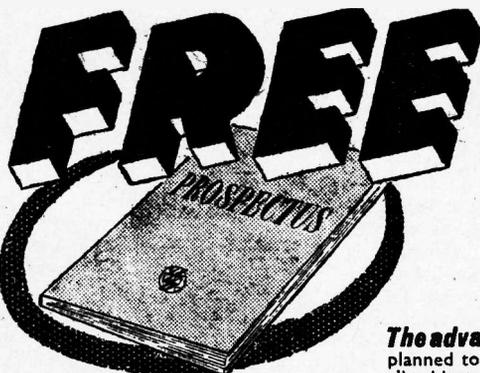NOW REDUCED TO 52/6 less valves. Post 3/6.



POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME
City and Guilds Grouped Certificates in Telecommunications: A.M.Brit.I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY. COURSES WITH EQUIPMENT
With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Equipment supplied upon enrolment and remains your property.
Courses from 15/- per month

POST THIS COUPON TODAY

Send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 138K, 43 Grove Park Road, London, W.4.

NAME _____

ADDRESS _____

8/56 SUBJECT(S) OF INTEREST _____


EMI INSTITUTES
The only Postal College which is part of a world-wide Industrial Organisation.

BRIMAR



Transistors

save space power & weight

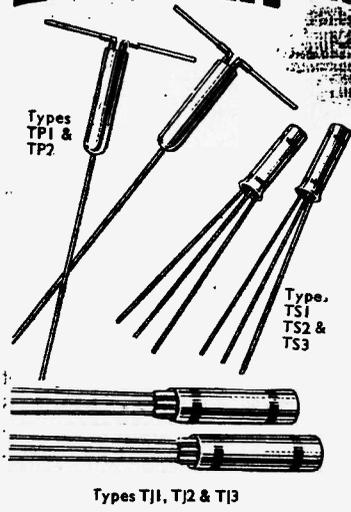

These long-life transistors in your circuits will save space and power and incidentally save weight. Exhaustive tests by our unique triple-test process have proved their reliability over a long period.

Their small size and low consumption permit the design of light, compact equipment and, since the cases are of metal, there is little danger of accidental fracture.


The BRIMAR TP1 and TP2 are point contact n type, germanium transistors. Type TP1 may be used in control and switching circuits at frequencies up to 100 Kc/s and will work consistently and reliably within this range. Type TP2 may be used as an amplifier or oscillator at frequencies up to 2 Mc/s. Collector dissipation 150 mW max. at 20° C. The BRIMAR TS1, TS2 and TS3 are p.n.p. alloyed junction transistors intended for use in low frequency applications up to 500 Kc/s. These transistors are fully hermetically sealed. They are thus immune from the effects of humidity and noxious atmospheric conditions. The collector dissipation of these types is 50 mW at 20° C. The TJ1, TJ2 and TJ3 are similar to the TS1, TS2 and TS3, but have a collector dissipation of 200 mW at 20° C. and are somewhat larger in size.

Send for data sheets of these transistors to

Standard Telephones and Cables Limited FOOTSCRAY, SIDCUP, KENT Footscray 3333

For super tropical service 'METALPACK' PAPER CONDENSERS

This range has been developed for operation in high humidities and high temperatures. Their ability to withstand variations from -40°C. to +100°C. makes them the obvious choice for the most stringent conditions. Internal construction follows the well-proved T.C.C. technique of winding non-inductively two or more layers of paper dielectric to each layer of solid aluminium foil, all impregnated under vacuum, and finally hermetically sealed in aluminium tubes.

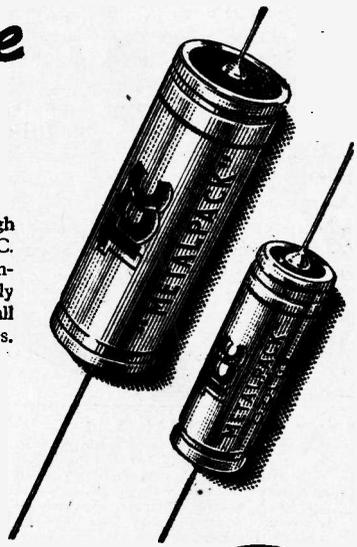

Cap. μ F	Wkg. Volts D.C.		Dimns. inches		Type No.	List Price Each
	At 70°C.	At 100°C.	L	D		
.005	1,000	750	1 1/2	1/8	CP45W	1/10
.01	1,000	750	1 1/2	1/8	CP45W	1/10
.02	750	600	1 1/2	1/8	CP45U	1/10
.05	500	350	1 1/2	1/8	CP45S	2/10
.1	500	350	2	1/8	CP46S	2/2
.1	1,000	650	2 1/2	1/8	CP47W	2/6
.25	350	175	2	1/8	CP48N	2/8
.5	350	175	2 1/2	1/8	CP47N	3/-
.5	500	350	2 1/2	1/8	CP91S	3/10
1.0	350	175	2 1/2	1/8	CP91N	4/-

DETAILS OF COMPLETE RANGES AVAILABLE ON REQUEST



THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION : NORTH ACTON · LONDON · W.3 · Telephone : ACOm 0061



Practical Television



& TELEVISION TIMES

Editor: F. J. CAMM

Editorial and Advertisement Offices: "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4383. Telegrams: Newnes, Rand, London. Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 7 No. 73

EVERY MONTH

AUGUST, 1956

TelevIEWS

COMMERCIAL TV ADVANCES

ACCORDING to Television Audience measurement the number of homes in the I.T.A. areas of London, Lancashire and the Midlands receiving commercial television is in excess of 1,500,000, and from the number of queries we receive asking for details of converters, it is apparent that the programmes are providing healthy competition for the BBC. No one, however, would suggest that the I.T.A. programmes are as yet comparable to those of the BBC in quality or in content. Every I.T.A. programme gives one the impression of an almost indecent haste to get the programme over, and bearing in mind the high cost of these advertising programmes it is understandable that the timing must be to the split second. This quite often destroys dramatic effect, and that is where the more leisurely style of the BBC scores.

It would equally be wrong to suggest that the quality of the I.T.A. transmissions have not improved during the past few months. Whether advertisers find the somewhat fleeting references to their product of value is not yet known. Some of the references indeed are so short that they could be completely obliterated during a few moments of interference caused by passing cars.

TV IN CARS

THE Minister of Transport, no doubt viewing the shape of things to come, proposes to incorporate in amendments to the Motor Vehicles (Construction and Use) Regulations a measure making it an offence to use or to install for use in a motor vehicle a television receiver, if the screen is partly or wholly, and whether directly or in a mirror, visible to the driver while in the driving seat. Furthermore the controls, apart from a main switch in the sound volume control, must not be within reach of the driver, and the set must not be so placed or used as to cause distraction to other drivers on the road.

Objections were raised to the installation of car radio in its early days because it was thought

that by listening to the radio the driver would not be concentrating upon the road. Experience has found, however, that these fears were unfounded. TV, it is admitted, is in a different category, for it would be impossible for a driver to watch a television programme and drive with safety at the same time.

THE RADIO SHOW

WILL readers please note that this and our associated journals together with our full range of technical books and blueprints will be exhibited at our Stand No. 111 on the ground floor where we shall be pleased to welcome all readers visiting the show. The technical staff will be available to deal with readers' queries.

DROP IN TV SALES

ACCORDING to the *Board of Trade Journal* the drop in the sale of TV receivers during the past few months cannot be attributed to the raising of the minimum deposit in February, and the drop must, therefore, be attributed to the usual seasonal decline. There can be no doubt, however, that the raising of the deposit must eventually affect sales, because that is what it was intended to do. If, however, it does not affect sales the minimum deposit should revert to its original figure to encourage sales.

NEW VOLUME

THIS issue commences Volume 7. Indexes for Volume 6 are in course of preparation and will cost 1s. 3d. by post. Orders should be sent to the publishers, address as above.


Previous volumes have commenced in May, but due to the printers' strike in the early part of the year, March and April issues were lost, and thus Volume 6 will cover from June, 1955, to July, 1956, although still consisting of 12 issues.—F. J. C.

A Beginner's Guide to Television

A NEW SERIES

5.—TRACING THE SIGNALS THROUGH THE RECEIVER

By F. J. Camm

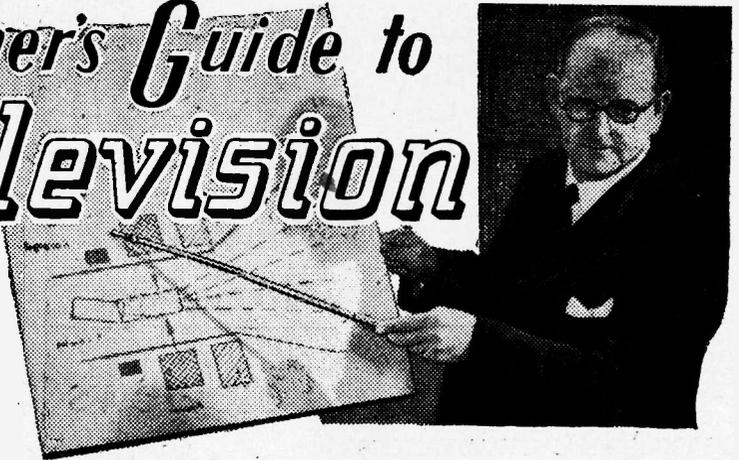

HAVING in the four preceding articles explained the function of each part of the television receiver and the system of transmission it would now be as well to recapitulate and make a connected theme. We have seen that a TV receiver consists of the aerial, which collects both sound and vision signals at the same time and passes them to the first stage of the television. From this stage the two signals are separated into the two channels—sound and vision—the sound signal passing to the audio section and the vision signal to the video section.

The sound signal is amplified and passed on to the loudspeaker. The vision signal, of course separated from the sound, is passed to the video section, where it is amplified and passed on to the cathode ray tube, which consists of a large glass envelope having on the front a fluorescent screen.

The sound signals are made audible by means of the cone of the loudspeaker, and the vision signals are made visible by a stream of electrons which are projected on to the end of the screen in the form of a spot, which is made to trace out the picture elements by means of the deflector coils.

The Aerial

There are many types of aerials as we have seen, but in all of them the principle is the same. It receives the modulated signal containing both sound and vision. The length of the aerial is decided so that it can receive a certain wavelength.

Sometimes the wavelength is expressed in terms of its frequency, and they are directly related to one another. We all know that the electro-magnetic wave radiated from a transmitter is said to have a certain wavelength. If, for example, a radio programme is being received on 350 metres, this means that the distance from the top or node of one wave to the top of the next is 350 metres.

Now the product of wavelength and frequency is the speed of light, and if we know the wavelength we have only to divide this into the speed of light, which is 186,282 miles per second. In other words the speed of wireless waves is exactly that of light. Similarly, if you know the frequency, in order to obtain the wavelength we divide the frequency into 186,282. From this it will be seen that as the frequency increases the wavelength decreases, although the product of the two will always be the same, viz., 186,282. Thus

we may say that a programme is being radiated on a wavelength of so many metres or we may also say that it is radiated on a frequency of so many cycles per second.

Whilst the wavelength is high the number of cycles per second will be low, but when we come to deal with the very low wavelengths on which television is broadcast definition of the accurate wavelength is difficult. The wavelength for Wenvoe, for example, is 4.63 metres. It is much easier to express this in terms of frequencies, which is 65 megacycles (1,000,000 cycles \times 65), which is abbreviated to 65 Mc/s.

Band Width

Now let us consider the question of band width, and in order to do so let us consider the transmission of sound. We know that when a high note on a piano is struck the string is vibrating at a very high rate, and a low note is due to a string vibrating comparatively slowly. In other words, the frequency of a high note is higher than that of a low note. Now when we hear a broadcast we must be able to hear all of the notes, the high, medium and low. Unfortunately it is not possible for us to hear all of the notes over the audible frequency range, and so we have to strike a compromise. In fact those between 5,000 and 8,000 cycles are transmitted.

It will be obvious from this that the wave transmitted from the aerial—that is, the electro-magnetic wave—must be 4,700 cycles wide so that all of the notes or frequencies we wish to hear are encompassed by it.

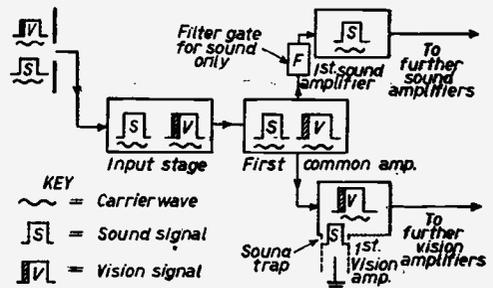


Fig. 19.—Block diagram in which the audio and video signals are traced through a "straight" receiver.

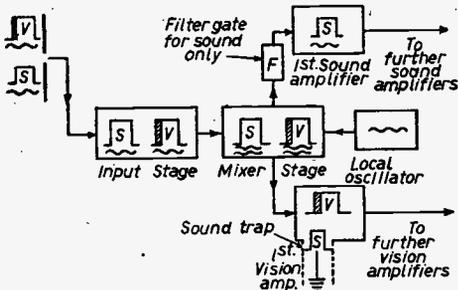


Fig. 20.—A block diagram similar to Fig. 19, but relating to a superhet receiver. See also Fig. 21.

It is because of this that we refer to the band width of the electro-magnetic wave (it is termed the carrier wave), and it is 4,700 cycles wide.

Now with vision a much greater range of frequency is dealt with, and it must encompass a dead black to the whitest white, and in this case a band width of 3,000,000 cycles (3 megacycles) is required. It will be clear from this that if the vision circuit will not permit this wide range of frequencies to pass through it picture quality will suffer. The designer has, however, attended to all this, and it is rare to find a receiver where the full range of frequencies is not covered. Of course, there are single and double side-band transmissions, but most of the TV channels work on a single side-band.

The input circuit of the receiver obviously has to be designed so that the band width is wide enough to include the sound channel as well as the vision. The first amplifying stage in most cases includes both signals, but from this point on the audio and video signals are separated by tuned circuits known as filters. In some cases the sound is separated at the input stage, but more often it is separated after the first amplifier. Occasionally, the signals are not separated until they reach the output of the second amplifying valve. One of the difficulties which occur in separation is that it is difficult to rid entirely the sound from the vision circuits, and filters are included in later stages to filter off any traces of sound signal.

In the case of a superhet the vision carrier frequency is "beaten" or heterodyned against a frequency generated by a local oscillator. This changes the frequency which carries the signal to one of a low figure, making it easier to handle. The sound signal is treated in a similar way.

This heterodyning or beating together occurs in the mixer valve. Unlike other valves, however, this one does not amplify. Indeed it is often the case that there is a loss.

The filter to which I have referred is, in reality, a coil or inductance and capacitates tuned to the sound channel. It acts as a vent, permitting sound only to pass through.

Similarly, in the video stage a coil and condenser comprise a trap or rejector and indeed it is termed a sound rejector or sound trap.

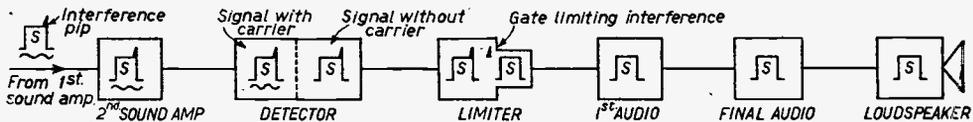


Fig. 21.—Block diagram of the path of the sound channel from the final stage of Fig. 20.

The sound signal proceeds through the filter and from thence its course is similar to that as in a radio receiver (see "The Beginner's Guide to Radio"). The only difference is that an interference limiter is nearly always included which filters away any interference caused by car ignition or other electrical apparatus. The carrier conveying the sound is amplified with the sound until it reaches that part of the circuit where it can take care of itself and it is here that vision and sound signals are separated; in other words, at a detector stage. At this point sound alone is amplified and passes to the loud-speaker.

The Video Section

We have seen that the first stage of a TV receiver is common to vision and sound in most cases, and where a straight receiver is concerned, that is, one which amplifies throughout at signal frequency, it is common practice to make the first amplifying stage common to vision and sound and after separation of the two signals has been effected by means of gate filters and traps referred to earlier the two signals are amplified in separate channels until sound reaches the speaker and the vision reaches the cathode-ray tube.

Three stages of vision amplification are commonly employed at signal frequency up to the detector stage at which, as already explained, the vision signal is separated from its carrier in a similar manner to that of the sound signal. It is passed on to the video amplifier.

Between the aerial and the detector four amplifying stages occur, for it would be almost impossible to design an amplifier to suit the wide range of frequencies encompassed by vision and sound. It is for this reason that a wide band amplifier using single-tuned couplings between stages which will provide the necessary degree of amplification is difficult to design, and to overcome the difficulty stagger tuning is used, and this is arranged so that each stage amplifies a certain proportion of the band. By tuning each stage to its particular band the total result will be a wide band amplified signal which is applied to the detector.

We have, of course, considered the vision signal as a simple band wave with a frequency extending from 0 to 3 Mc/s, but, in fact, it is a very complex affair. The main point is, however, that the video signal contains all the picture detail as well as the synchronising pulses which keeps the standing spot in the receiving tube in step with that of the camera.

These pulses are extracted from the video signal and fed to the timebases where triggering takes place.

We have already noted that this process takes place in the detector stage, which thus performs the double function of separating the video from its carrier and the sync pulses from the picture.

The timebase must trigger the oscillators and the pulses must be free from "picture intelligence," for if the pulses contain the latter any change in scene from light to dark would give rise to a spurious pulse and the timebase oscillators would not function correctly. With the result that the picture would be broken up.

The Video Valve

The purpose of the video valve is to amplify the entire frequency range from 0 to 3 Mc/s. To obtain the maximum gain from the stage it is possible to make the anode load resistor 20 per cent. higher than that called for in the design and also to increase the value of the coupling condenser. This, however, is always accompanied by an adverse effect on the quality of the picture, but in the fringe areas the extra gain is probably worth some sacrifice of picture quality.

The Television Camera

Although many different types of television camera are used today they differ in the matter of design and lens arrangement, and their differences are mechanical and optical rather than fundamental. Each of them is based upon the principles first laid down by Campbell Swinton more than 40 years ago. The Emitron camera and the Super-Emitron with their later improvements are chiefly in use in great Britain, whilst America uses the Iconoscope and the Orthiconoscope or Orthicon, and the Image Orthicon which perhaps is more used in America than any other type.

Before we can understand the television camera it is necessary to have a knowledge of certain fundamentals. We have seen earlier that in both sound and vision systems the received signal is made up of one or more periodic wave forms. They are waves of air pressure in the case of sound, and variations of strain in the ether in the case of vision. In both it is necessary to transmit amplitude (strength or intensity), frequency (pitch or colour), phase (the relationship in time between one component wave form and another), and spatial distribution. The latter is of great importance in television, but only of slight importance in sound. In television reproduction it would be purposeless to indicate the strength of a light impulse or even its colour unless it is related to the exact point where it fits into the picture as a whole. At any one instant the output from one photocell can only convey one single item of information, so to speak, and it will produce exactly the same current whether it is looking at a chequerboard of black and white or at a scene which is uniformly grey. The problem admits of two solutions. The system may consist of a number of separate channels each confined to one small section of the picture. That, however, is impracticable. The system, therefore, must confine itself to one section at any time covering the whole scene in an orderly sequence known as scanning, and then repeating the whole operation at a rate sufficiently

fast to deceive the eye into thinking that it is viewing a continuously present picture instead of only a spot.

A vital point is the number of sections into which the picture must be broken up for good reproduction, or what we now term definition. In the Baird 30-line system the number was approximately 1,000, which we now know to be totally inadequate. The optimum number of sections, which in turn determines the number of lines, is still a matter of conjecture, but it certainly cannot be less than 50,000, and it can be said that any increase above 1,000,000 is not justified by any improvement in definition which is perceptible to the human eye.

In the standard BBC system the picture is broken up into approximately 200,000 elements, and it is the duty of the television camera to scan the picture at every instant to produce an output current which is proportional to the intensity of the light falling upon the camera at that instant. The picture being televised is scanned in zig-zag lines from left to right. The start of each line is below that of its predecessor by a distance equal to twice its own thickness or depth. When $20\frac{1}{2}$ lines have been covered, the scanning spot returns to the top of the picture and scans the lines which have been missed out during the first half of the process, making 405 lines in all. The whole process is then repeated 25 times every second, which is fast enough to take full advantage of the well-known persistence of vision effect in the eye. As a parallel, it will be recalled that in film production a similar device is used; although only 24 frames pass through the projector every second, each frame is actually viewed twice, giving the same smoothness as if the frame frequency were 48. The equivalent television frequency is increased to 50 to take advantage of the controlled grid supply in this country.

With sequential scanning, one difficulty which immediately arises is that of getting adequate sensitivity, bearing in mind that each individual section is only viewed for roughly one two-hundred-thousandth part of the duration of each picture, which in any case only lasts for one twenty-fifth of a second itself. Camera-minded readers will appreciate the problem of exposure times in the order of 0.0000002 second! It is this problem of combining a sensitivity high enough to overcome the inevitable background noises with the demand for a high rate of scanning, and therefore a short duration of coverage on each individual section, that has determined the characteristics of the television camera as we know it today.

(To be continued.)

Smaller TV Sets

U.S. television set manufacturers are putting on a big competitive drive to sell smaller sets at the present time. This is part of the industry's general programme of selling its customers who already have large sets in the house a second receiver.

Radio Corp. of U.S.A. has on the market a set with an 8½-inch screen that sells for \$125. Admiral Corporation has begun production of a 10-inch set which is priced at from \$90 to \$120, according to model. General Electric has just

ODDS AND ENDS

brought out a 9-inch set that is priced at under \$100.

TV Receivers in Cars

IN the additions and amendments to the Motor Vehicles (Construction and Use) Regulations it is proposed to include a paragraph concerning the installation of television receivers in cars. This will make it compulsory that the

receiver be fitted in such a position that the screen cannot be seen wholly or partly by the driver, and that the only controls permitted within reach of the driver are a main switch and a sound control.

Danish TV

DENMARK'S third television station, which cost £130,000, was opened in May at Aarhus. The State Radio began its television broadcasts in 1953 and there are now over 25,000 viewers, with 60 per cent. of the country covered by transmissions.

RINGING CHOKE EHT

AN INEXPENSIVE EHT SUPPLY FOR THE EXPERIMENTER By "Erg"

ONE of the problems which faces the experimenter is that of a suitable supply of EHT. Where a small 6in. C.R.T. of the ex-Govt. type, such as the VCR97, is used, then the usual EHT source is from a 50-cycle mains supply with its attendant problems of too good a regulation, and the expensiveness of good quality EHT mains transformers.

Although the VCR97 and kindred tubes take a fair EHT current (comparatively!) other methods of supplying the necessary high voltages are available. A common method is by means of an R.F. circuit where an oscillator functions at very high frequencies, and the other is by the ringing choke.

The R.F. oscillator type of EHT supply is quite efficient for normal use, but is a rather difficult type of circuit for the novice to get going efficiently; moreover, where electrostatic tubes are employed with their necessary bleeder networks feeding the different tube elements, then quite often it is difficult to get the necessary current from the circuit.

The regulation of the R.F. supply is rather poor; it is too poor for many requirements.

poorly regulated supply the voltage falls rapidly with increase of current.

The variation of voltage with supply of current has some advantages and some disadvantages.

The main disadvantage of a poorly regulated supply is that peak whites tend to defocus. This is the case with most television receivers which employ the line flyback for supply of EHT. Such a source has poor regulation and it will be noticed that the white parts of the picture do not focus correctly; they come out of focus and cause two defects. First, the defocusing causes the lines to thicken with resultant distortion of the picture, and second the thickening process makes the lines appear to interlace incorrectly.

Close examination of the screen of practically any commercial television receiver which employs such methods of EHT provision will reveal these defects.

Another defect is that ignition interference which drives the tube beyond peak whites causes such defocusing that the interference which would normally appear as small white spots, is turned into large blobs spreading over several lines.

The employment of interference suppression circuits materially assists in cutting down this effect and it is not now such a nuisance as in the earlier days of television.

A major advantage of poor regulation is that as the voltage drops considerably as the load is increased, it becomes rather safer to handle such an EHT source. Where accidental contact is made with the hands, for instance, then the applied voltage drops immediately and beyond the initial "kick" no damage is done. A well-regulated 50-cycle supply,

EHT Regulation

When dealing with supply of EHT voltages the question of the regulation of the supply must come into the picture.

Without becoming too technical we can say that by regulation we mean the ability of the supply to maintain its normal voltage under varying conditions of load.

In a well-regulated supply the actual voltage remains constant over a fair range of current. In a

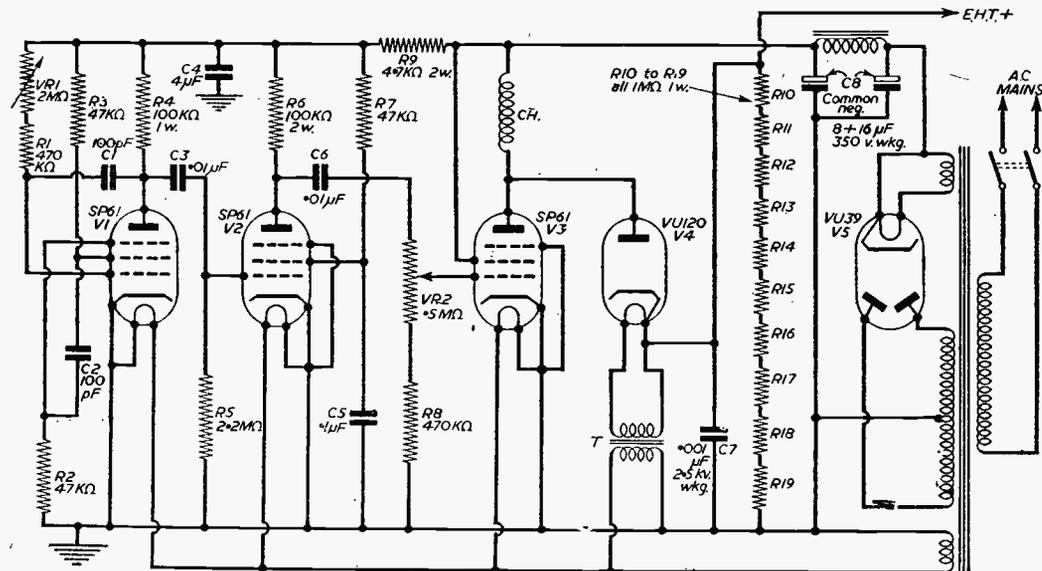


Fig. 4.—Complete circuit as referred to on page 9.

however, tends to retain the original applied voltage, and great care must be exercised when handling such supplies.

An EHT supply obtained from an R.F. oscillator can supply very high voltages, and this method is employed on most projection systems. For moderate EHT, such as the experimenters' VCR97 type of tube, the "ringing choke" method of supply will be found to effect a good compromise between a well-

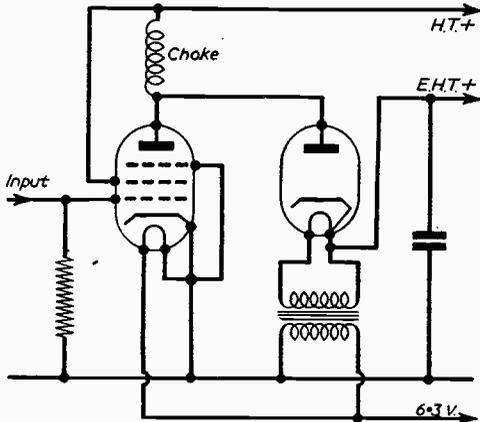


Fig. 1.—Ringing choke output circuit.

regulated, but expensive, mains supply and the not-so-well regulated R.F. supply.

The voltage obtained from this system can be classified as being of the "safe" type yet the regulation is quite good for normal purposes.

The Ringing Choke

It is well known that any rapid change of current through an inductance will cause a heavy voltage change across the inductance. The more rapid the current change, the greater is the voltage change. We have an example of this in the output of the line amplifier. On the flyback, voltages are generated in the anode circuit of the valve and can be as high as 2,000 volts—sometimes even more.

The sudden drop of current from a very high figure to zero causes the primary of the output transformer to "ring" and to produce these high voltages.

In the television arrangements are made for the output transformer to have some extra windings so that the voltage produced is stepped up still further and it is then rectified and used for EHT.

The same principle applies in the case of a ringing choke EHT. An amplifying valve is fed with an impulse type of waveform which produces shock excitation of the inductance in its anode circuit. The value of the inductance is chosen so that it tends to oscillate or "ring" at the frequency of the input. The resultant voltages can then be rectified and employed in the usual manner (Fig. 1).

When considering the use of ringing choke systems there are several important points which must not be overlooked.

First, to produce the best results the current must change very rapidly: for this reason excitation by means of a flyback pulse produces very good results.

Second, the inductance in the output circuit must be highly insulated or breakdown is liable between windings of adjacent turns.

Third, it is important that the pulse producing the high voltages at the anode is in the correct phase so that positive voltages are produced and not negative ones which would be liable to damage the valve. Therefore the input to the valve must be such that the flyback is in the negative direction at the grid, and therefore positive at the anode.

The Choke

The value of the choke should be in the region of 0.2 Henries. This need not cause any difficulty, as it is quite easy to make a choke approximately this value, at home.

The choke is wound on a piece of dowel rod $\frac{3}{8}$ in. diameter and about $1\frac{1}{2}$ in. long. Cheeks can be fitted at the ends so as to retain the windings, the cheeks being made of stiff cardboard or plywood (Fig. 2).

The wire to be used is 38 s.w.g. enamelled wire and about $\frac{1}{4}$ lb. will be required.

Each layer of windings should be separated by a layer of waxed paper, and that from an old paper condenser can be used.

The wire is wound on in as even layers as possible with a layer of waxed paper between each layer of wire. A total of 7,000 turns are necessary.

When completed the choke can be bolted to the chassis by running a bolt down through the centre of the dowelling. This makes a neater job than trying to use a wood screw from underneath the chassis.

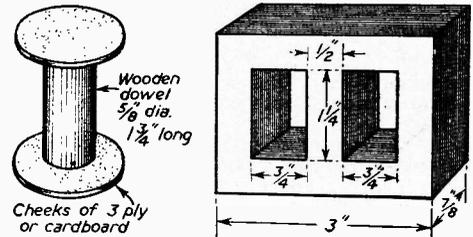


Fig. 2. (Left).—The choke former. Fig. 3. (Right).—Transformer core.

Heater Transformer

Having overcome the problem of the choke the next problem is that of the heater supply for the rectifier valve. If desired an EY51 can be used as a rectifier the heater being fed either from a transformer with highly insulated wiring, or from a separate winding on the choke. 18 turns of wire should be sufficient, but this winding must be well insulated from the remainder of the choke and, if waxed paper is used for insulation, then the choke must not be allowed to become heated.

A cheaper, though more laborious, method is to make a heater transformer and to use an ex-Govt. valve such as the VU120.

The transformer need not be at all difficult in construction and anybody could make a simple one of the type about to be described, as it is purely a heater to heater transformer and requires very few turns of wire.

The transformer requires an area of about $\frac{1}{2}$ sq. in. for the centre limb on to which is to be wound the windings. The window area should be about $\frac{1}{2}$ in. by $1\frac{1}{2}$ in. to accommodate the windings. (Fig. 3).

An old loudspeaker transformer can often be used for this job, or a transformer from an ex-Govt. unit with approximately the above dimensions.

If an old transformer is used the stampings should be unbolted then taken apart very carefully noting the "lay" of them so that they can be re-assembled in the same manner. Having removed the stampings, then the existing wire should be removed.

For the primary fresh wire is wound on and 22 s.w.g. enamelled wire should be used. Sixty-five turns are necessary and the wire should be wound so that each adjacent turn touches; this will mean that more than one layer is necessary and each layer should be insulated from the previous one with a layer of oiled silk, empire cloth, or good quality insulating tape.

Having wound on the primary, several layers of a good insulator should be wound on as the secondary will be at about 2-3 Kv. above the primary.

The best material is undoubtedly oiled silk but P.V.C. sheeting, several layers of empire tape, or similar high insulation material can be used. Waxed cardboard can often be employed. It is not wise to use P.V.C. sheeting alone as, if any heat is generated, the P.V.C. softens and this may be the cause of a flash-over.

The secondary uses the same type of wire as the primary but only 27 turns are required as the heater of the VU120 requires only 2 volt. (Note: If a 4-volt rectifier is to be used then double the number of turns given above).

Having wound the transformer the stampings are replaced and bolted together firmly. If the stampings are loose then they will vibrate to the mains hum.

The Complete EHT Supply

Having settled the problems of the choke and the heater supply we can now consider the complete circuit.

In Fig. 4 we show a complete unit which will provide an EHT of between 2 and 3 Kv. The whole unit is very inexpensive as it is made mostly from ex-Govt. materials.

The EHT is obtained from the rectifier valve V4, which is a VU120. The heater is fed from a transformer which is made as described previously. The output is smoothed by the condenser C7 which, due to the high frequency of the supply, can be of low value; this solves the problem of smoothing condensers for mains-supplied EHT, which are in rather short supply. A value of 0.001 μ F can be used, 2.5 Kv. working minimum.

The output is fed into the bleeder network which is composed of ten 1 megohm 1 watt resistors. These resistors should be mounted on a well-insulated paxolin panel in staggered formation to prevent flashover.

V3 is the amplifier which supplies the EHT. The valve type is not at all critical and one of the inexpensive SP61 valves (VR65) which can be obtained very cheaply can be used in this position.

The input to the valve, and hence the output of EHT is controlled by the potentiometer VR2.

The supply for the input to this valve can be obtained from an existing timebase provided that the supply is positive going. The output from the normal Miller oscillator as is used in many home constructors' receivers is negative going, and such a signal must be reversed in phase before being applied.

In the circuit given in Fig. 4, we have provided for

a suitable input source for the amplifier valve. This is obtained from V1 and V2. V1 is a standard form of Miller oscillator and uses an SP61 valve, while V2 is the paraphase amplifier. The two valves form a "see-saw" arrangement often found in electrostatic timebases, and could, with slight modifications, be used for this purpose. However at this point we are only concerned in getting a sawtooth voltage at line frequency and in correct phase, to the input of V3, and this circuit will provide that voltage.

The complete circuit has its own power supply with a valve rectifier V5; and here once again the use of an ex-Govt. valve provides for economy. The type of valve will depend upon the outputs of the mains transformer. In the prototype the mains transformer had 6.3 volt supplies for the valves with a 5 volt tapped 4 volt for the rectifier, and a 4-volt rectifier, a VU39, was used as it was to hand.

The 6.3-volt supply should be at about 2A and the H.T. should be about 350 volt at about 60 mA minimum.

Adjustment

The circuit should be switched on and after allowing time for warming up VR2 should be adjusted for minimum position (slider towards "earthy" end of potentiometer) and VR1 should be adjusted so that the well-known whistle is heard. The whistle can be adjusted so that it is just beyond normal hearing limits, if found objectionable.

Once set, VR1 should not be disturbed.

A milliammeter should be inserted in the cathode of V3, and VR2 is then adjusted until a maximum current of 15mA is obtained. The voltage obtained can be obtained by checking the current through the bleeder chain by insertion of a milliammeter in the earthy end. The current reading obtained multiplied by the total resistance of the chain will give the EHT voltage.


Once the circuit has been set up it is important to screen the entire unit to avoid interference. A simple perforated zinc or other metal screen should be used to enclose the whole unit.

PRACTICAL WIRELESS AUGUST ISSUE NOW ON SALE PRICE 1/3

The current issue of our companion paper, "Practical Wireless," has, as its main feature this month full constructional details of a small portable receiver, utilising a normal diode as detector with two transistors as L.F. amplifiers. This makes a compact receiver which requires only a 9-volt battery as the power source. The receiver will be found very useful as a bedside or outdoor model. Another constructional feature deals with the modification of a standard alarm clock movement for the switching of the mains supply to control either a radio or any other mains apparatus.

Details of a simplified mains-operated add on F.M. tuner also appear, and there is a constructional feature dealing with an Inexpensive Testmeter. Further details are given on the 3½ in. oscilloscope, and amongst the remaining features in this issue will be found servicing data for the Philco Model A3606; Replacing Test Meter Movements; Simple Adjustable Voltage Supplies; Transmitting Topics; Finding Transformer Connections; Building a Constant Voltage Transformer; Using Test Instruments and the usual features—Letters from Readers, Programme Pointers, etc.

Servicing TELEVISION RECEIVERS

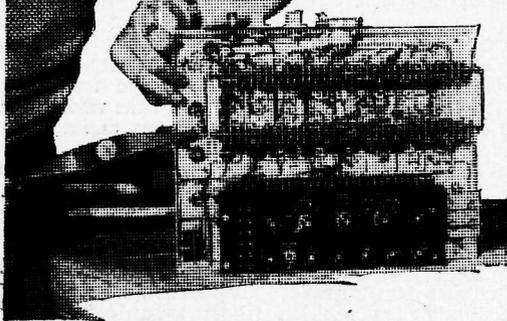

No. 21. THE EKCO TS46, TSC48 AND TSC91

By L. Lawry-Johns

P61 often becomes excessive causing the UU8 to become overloaded and the fuses to blow, provided that these are correctly rated at 500 mA. These fuses are not included in the mains supply leads, but complete the chassis return to each half of the H.T. secondary winding of the mains transformer. Fig. 1 shows the actual circuit. Therefore, in the event of frequent fuse failure, replace the UU8 rectifier, which is subject to internal shorts, and if the condition persists remove the cover from the left-hand screening box and replace the P61.

THE TS46 is a 9in. table model, the TSC91 the console version, and the TSC48 is a larger 12in. indirectly viewed (raised mirror in lid) with broadcast radio facilities. These notes are based mainly upon the TS46 as this is the more popular model.

Points of interest are the R.F. EHT unit mounted on the left side of the chassis, the method of wiring the circuit fuses and the fact that the C.R.T. is grid modulated.

The R.F. EHT unit contains a P61 oscillator and U22 EHT rectifier in addition to the transformer and EHT smoothing capacitors, etc. The P61 is a frequent cause of fuse failure and internal shorts in the UU8 rectifier valve. The current drawn by the

The disadvantage of providing fuses in the H.T. line only is that faults occurring in the heater circuit or mains transformer will not cause these fuses to blow and disconnect the receiver from the mains. As an instance of what is meant, one of these receivers was received with the complaint that smoke was issuing from the chassis, no sound or vision signals, and an objectionable smell! No H.T. shorts were detected and the mains transformer was suspected of having shorted turns. However, when the set was operated it was noticed that the rear R.F. sound and vision valves were not being heated, although the 4 volt valves, PEN45, PEN46, etc., were.

The fault was eventually located in the R.F. strip where a heater lead to a 6F13 valve was found fouled under the edge of one of the separate screening cases.

A new length of lead, properly routed, cured the rather ominous symptoms. The point remaining that under some circumstances a fault of this nature, where no mains fuses are included in the circuit, could have resulted in more serious damage.

Failing H.T.

A small picture, extreme setting of the focus control and variation in the setting of the line and frame hold controls indicate low H.T., probably due to one of the 500 mA fuses failing. If the replacement fuse fails, follow the previous notes in reference to the UU8 and P61 valves. Do not be tempted to increase the fuse rating.

A frequent cause of complaint is that of intermittent variation of picture size. This sometimes gives the impression that the picture is "breathing," the variation being regular rather than intermittent. In nearly all cases

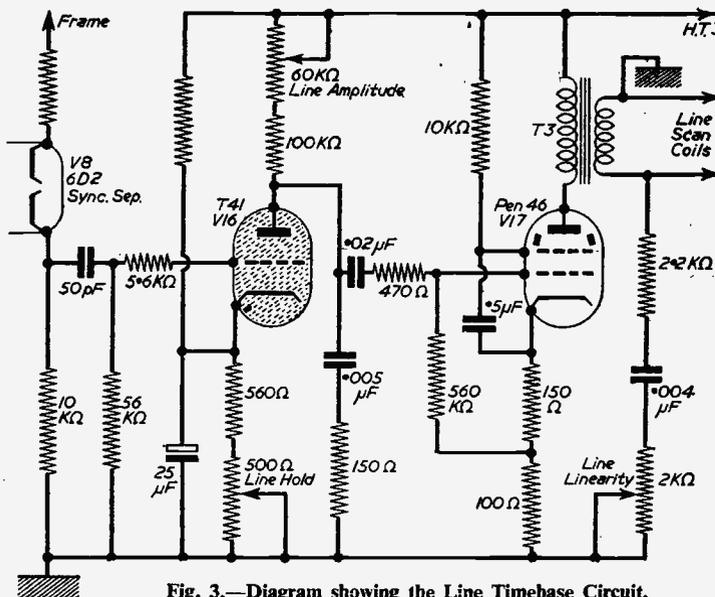


Fig. 3.—Diagram showing the Line Timebase Circuit.

this effect is due to the U22 valve, and a replacement will clear the fault. Intermittent flashing on the picture is often again due to the U22. In this case the envelope of the valve becomes charged and glows blue. This type of valve is prone to this fault. The replacement U24 is not so affected, but the valve base must be changed to international octal if a substitution is to be made.

In the 9in. models a Mazda CRM92 is employed, although a few chassis were fitted with Cintel tubes which involved some circuit alteration and different type scanning and focus assemblies.

The TSC48 uses a 12in. Mazda CRM121 and on this model the EHT is slightly increased, necessitating the voltage rating of the EHT smoothing capacitors C71 and C72 to be increased from 6 kV to 7 kV.

The tube circuit is shown in Fig. 2, and this covers all late models. The brilliance circuit of early models differed somewhat and V4 was supplied from the H.T. line via a 4.7 kΩ resistor rather than via the brilliance circuit as shown. The focus coil is in series with the H.T. line, with the focus control in series with a fixed resistor shunted across it. The fixed resistor (R79) is of 390 Ω and is mounted beneath the tube neck on top of the chassis. It is normal for this to appear rather burned or discoloured. Quite often the focus control develops a fault whereby the track (wire-wound) becomes open circuited. Depending upon the actual position of the break the control may be completely inoperative or may be operative over only part of its travel. This control is referred to as R80 and is a 2 kΩ wire-wound potentiometer. Note that as the track and wiper arm are at H.T. potential, it is possible to obtain some types of control where one, normally the centre, tag is joined to the metal case. Obviously, this type must not be used for replacement purposes.

As can be seen from the diagram, the control grid

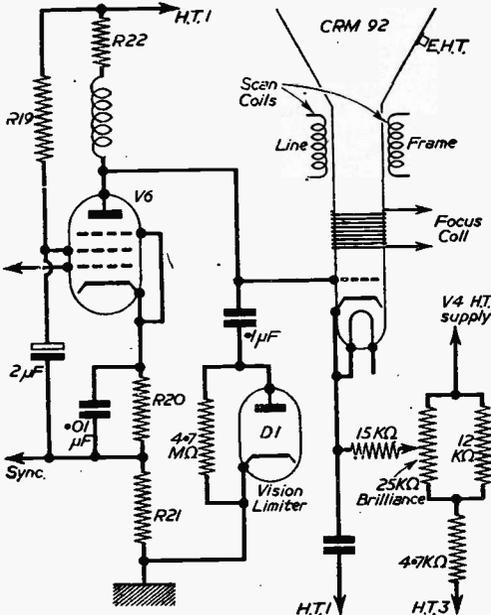


Fig. 2.—Video amplifier output, C.R.T. and brilliance circuit.

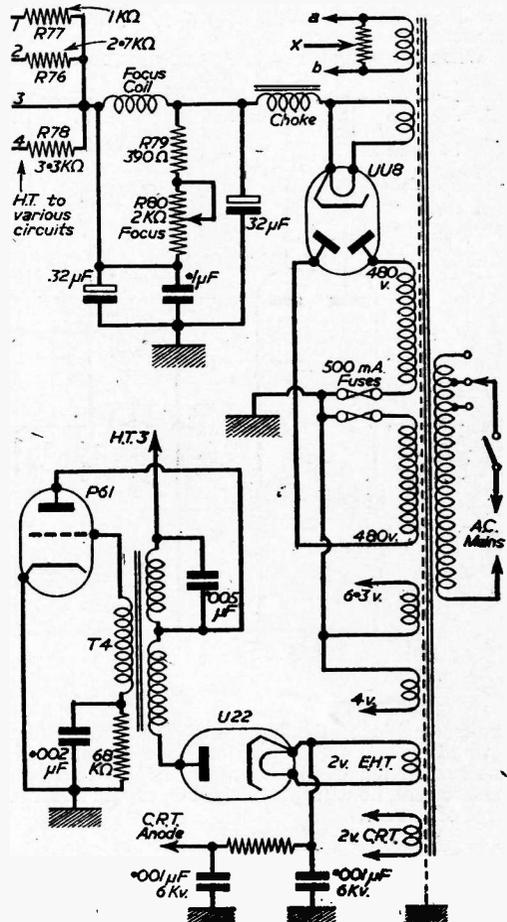


Fig. 1.—Diagram showing Mains supply H.T. wiring and E.H.T. circuit. Heater winding a-b supply sound valves V13 and V14 which are susceptible to hum.

of the tube is fed from the anode of the video amplifier. If a fault develops in V6, therefore, the anode voltage could rise to that of the H.T. line. The displayed condition would be that of no picture with excessive brilliance. Therefore excessive brilliance should direct attention to V6 and its associated circuit. If no fault is found in the video amplifier stage, as indicated by a correct anode voltage, attention should be directed to the brilliance circuit which controls the H.T. potential applied to the tube cathode. A fault in V4 stage could cause this voltage to fall as the H.T. applied to this valve is derived via the brilliance circuit.

R.F. Stages

These are very straightforward and are of the tuned radio frequency type (T.R.F.). The only troubles likely to be encountered are actual valve failure and lack of H.T. to any particular stage caused by a shorted decoupling capacitor. This often causes the H.T. feed resistor, associated with this capacitor, to burn out. In the event of an open-circuited resistor being discovered, the associated decoupling capacitor

should be checked and, if necessary, replaced before the resistor is replaced.

When removing the separate screening covers from

and the width is R66. The linearity, mainly on the left side of the picture, is controlled by R75 in series with R74 and C62. Any left side distortion which is

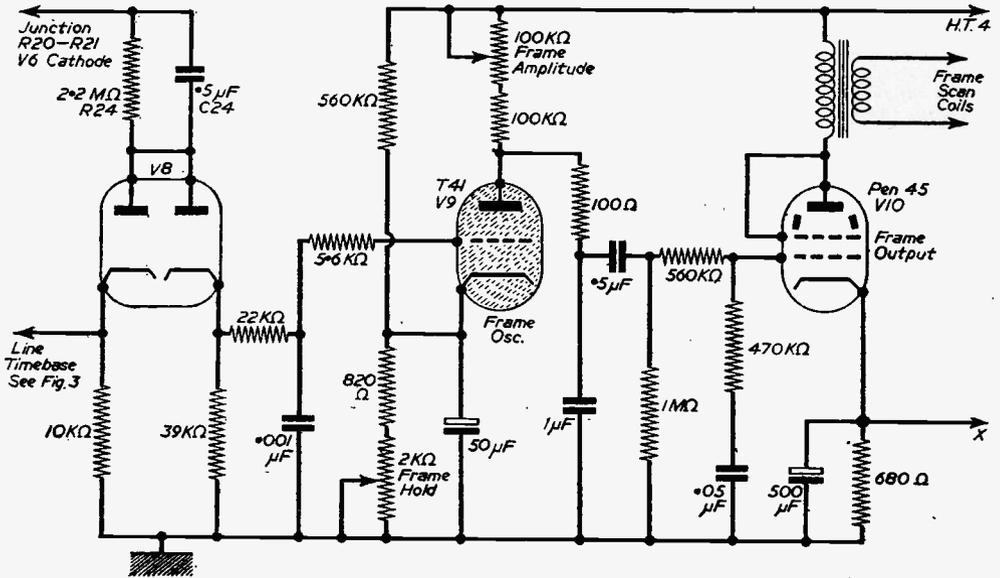


Fig. 4.—Frame Timebase and Sync Separator circuit.

the underside of the individual R.F. stages (each secured by two 4 BA nuts from above the chassis) ensure that the wiring is undisturbed so that upon replacement, no wiring is likely to be caught under the edge of screens.

Timebases

The line timebase consists of a T41 gas-filled thyratron oscillator and a PEN46 output beam tetrode. The circuit is very simple and does not require much explanation.

Most of the troubles which occur, such as unstable line hold, picture ragged in a horizontal direction, intermittent picture slip and sometimes poor width, may be cured by replacing V16 T41.

Insufficient width can be a trifle deceptive, however, since a failing PEN46 or low H.T. voltage (check fuses and UU8) applied to the anode and/or screen of this valve could equally be responsible. Extremely poor linearity and width should direct attention to the capacitors C60 (.02 μF) and C61 (.5 μF). A complete upset of the line timebase working which does not respond to valve replacement should direct attention to C58 (25 μF) which is the T41 cathode by-pass electrolytic.

The line hold control is R65

not corrected by the control should direct attention to the 2.2 kΩ resistor (R74), which may be open-circuited.

The frame timebase is extremely similar in operation, a T41 (V9) is the oscillator and a PEN45 (V10) is the frame output.

Normally, the PEN45 output stage is comparatively trouble free, picture jumping, intermittent frame hold, multiple images, etc., usually responding to a change of T41. The frame hold R31 (2 kΩ) varies the cathode potential of this valve, whilst the frame

Pre-amplifier fitted on models suffixed ... /

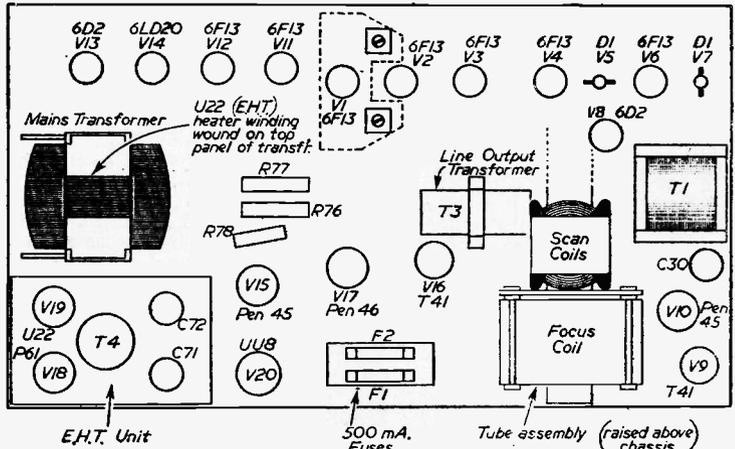


Fig. 5.—Top view of the chassis.

amplitude or height varies the H.T. applied to the anode. Poor, vertical linearity may be caused by a defective PEN45 (low emission) or a leaky .5 μ F coupling capacitor C28. Although the PEN45 could be responsible for loss of height, the T41 could equally be responsible. If both are in order check the 100 k Ω T41 load resistor and the electrolytic cathode capacitors.

On odd occasions R34 (100 Ω) or C27 (1 μ F) have been found responsible for complete loss of frame hold. These are the "charge" components which determine the repetition frequency.

Sync Separation

The sync pulses are derived from the cathode circuit of the V6 video amplifier. These are applied to the anodes of a double diode V8 (6D2) which are strapped. The line sync pulses are taken from one cathode and the frame from the other. The biasing of the valve removes the picture content (video signals) whilst the value of the components ensures that the frame and line pulses are adequately separated. See note on early models regarding poor sync.

The Video Amplifier

V6 is a 6F13 loaded "top and bottom," that is, it has an anode load resistor R22 (3.3 k Ω) in series with a correction choke from which the positive going picture signals are applied to the C.R.T. control grid, whilst the cathode is also loaded by two 4.7 k Ω resistors in parallel R21 (effective resistance 2,350 Ω) in addition to the normal cathode bias resistor of 47 Ω , R20. The sync pulses are derived (negative going) from the junction of the two. The screen of the valve is fed from the H.T. line by R19, 4.7 k Ω , and decoupled to the junction of R20 and R21 by a 2 μ F electrolytic capacitor.

The Sound Stages

V11 and V12 are two 6F13 R.F. amplifiers transformer coupled and tuned to 41.5 Mc/s. Detection is by one of the diodes of the 6LD20 V14 which functions as the detector (diode) and A.F. amplifier (triode). The other diode section is unused and is wired to chassis. V13 is a 6D2 double diode which functions as the noise limiter and V15 is the PEN45 sound output valve. Two high value resistors are used in the 6D2 circuit, both 4.7 M Ω , and sound distortion should direct attention to these resistors. If the distortion is not cured by substituting these resistors, check the insulation of the .1 μ F capacitor which couples the A.F. signals to the control grid of

V15. Low sound which does not respond to valve replacement may be caused by one of the several electrolytic capacitors associated with V14 or V15, becoming open circuited. The H.T. supply to these valves is derived from R76.

Early Models

Some considerable modification has been carried out from time to time and the extent of these is too lengthy to be included in this article. However, if the picture is inclined to lose sync, i.e., roll or slip on change of programme or picture content, R21 may be found to be 820 Ω , R24 1 M Ω and C24 .1 μ F. Changing R21 to 2,350 Ω , R24 to 2.2 M Ω and C24 to .5 μ F should enable more reliable hold to be maintained.

TSC48 Models

After the multi-pin connecting plugs have been removed and refitted several times, it often happens that one or more leads may become disconnected. This particularly applies to the screened A.F. cable where the inner and more fragile lead may become detached from its pin or soldering tag.

These voltage figures are intended as a guide and some small variation need not indicate a fault.

	Valve	Anode	Screen	Cathode
V1	6F13	212	212	1.8
V2	6F13	210	210	1.8
V3	6F13	215	215	1.7
V4	6F13	196	196	1.7
V5	D1	—	—	—
V6	6F13	220	245	42
V7	D1	—	—	—
V8	6D2	—	—	—
V9	T41	53	—	3.1
V10	PEN45	271	271	12.5
V11	6F13	217	217	1.7
V12	6F13	210	210	1.8
V13	6D2	—	—	—
V14	6LD20	58	—	1.3
V15	PEN45	244	152	5.3
V16	T41	55	—	4
V17	PEN46	345*	205	15
V18	P61	350	—	—
V20	UU8	480 each anode	—	382
CRT	CRM92	6kV	—	240

*High A.C. voltage at PEN46 anode makes testing inadvisable. This also applies to the P61 EHT generator.

Independent Television in Scotland

THE Independent Television Authority has now completed its negotiations in connection with the selection of a contractor to supply all the programmes from the Authority's station in Central Scotland, and has decided to accept, subject to contract, the application of Scottish Television, Ltd. This is a new company which will have as its chairman Mr. Roy Thomson, who is also the chairman of The Scotsman Publications, Ltd. It plans to include a number of other Scottish interests.

The I.T.A. is about to start the construction of a new television transmitting station at Black Hill between Airdrie and Bathgate, and the necessary planning and other permissions have already been

obtained. The site will be 900ft. above sea-level, and the transmitting mast will be 750ft. high. This means that the aerial array will be 1,650ft. above sea-level, and a very good coverage of the Central Scotland area should be possible. The transmitter will have an effective radiated power of at least 100 kilowatts, and it will serve approximately three-and-a-half million people. Those living in Glasgow and Edinburgh should receive very good signals, and most people living within the area bounded on the north by a line from Helensburgh to Dundee and on the south by a line from Prestwick through Biggar to Dunbar should be able to receive satisfactory signals. The Authority hopes to bring the transmitter into operation by August, 1957, in time for the beginning of the Festival of Music and Drama in Edinburgh.

COLOUR TELEVISION

THE LAST ARTICLE IN THE SERIES DEALING WITH THE PRINCIPLES AND PRACTICE OF MODERN TELEVISION IN COLOUR

4.—THE COLOUR CATHODE RAY TUBE

By C. Grant Dixon, M.A.

Colour Picture Display Tubes

THE three previous articles in this series have dealt with the various methods of producing a television signal which will satisfactorily represent a coloured image, but the weakest link in the whole chain from studio to viewer is undoubtedly the picture display tube at the receiving end. Much effort has gone into the design and production of standard monochrome cathode-ray tubes, and if this type of tube could be used in conjunction with a device to give colour to the white image a successful system would result. The frame sequential system with its rotating colour wheel is, in fact, a simple example of this method. Working along other lines, several patents have been taken out which describe crystal "sandwiches" which are stressed electrically to give a colour filter effect in conjunction with Polaroid film, but the loss of light in such a system is very great, and most work has been directed towards the production of a tube the screen of which can be made to fluoresce in the required colours. It will be recalled that any colour may be reproduced by the addition of the three primary colours in the proper proportions. Therefore, for any screen to be able to reproduce these colours it must either consist of a three-layer arrangement with the front two layers translucent; or be divided up into a large number of small areas, such areas being grouped in sets of three. An example of the first system was Baird's original two-colour tube on which he was experimenting just before his death. Fig. 1 shows the three-colour version of this tube which he called the "Telechrome." The screen of the tube is viewed from one side only (the picture is reversed on the other side) and a fully detailed picture is seen in green. The red and blue pictures appear through the transparent green screen and are limited in definition by the fact that the red or blue screen consists of a series of lines. This is no detriment provided these lines are small enough, because the

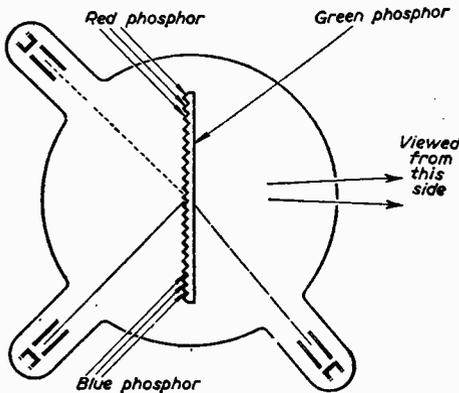


Fig. 1.—The Baird "Telechrome" tube.

eye does not see fine detail in red or blue as explained in the last article. The chief disadvantage of this tube is its bulk, but it is interesting to note that one of the new American experimental colour tubes uses this same transparent plate principle built into a flat glass bulb.

Colour Strips

The second method, that of dividing up the screen into a series of small colour areas is employed in almost

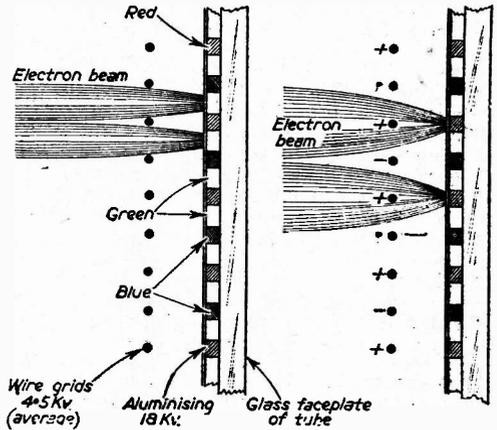


Fig. 2.—Showing the focus action of the wire grids.

Fig. 3.—Vertical section through "Chromatron" screen.

all colour tubes. There is a choice between dividing into small colour strips, or small colour dots, and the "Chromatron" invented by Prof. Lawrence uses a system of colour strips. The phosphors which glow in the three primary colours are deposited on the screen of the tube in the form of thin strips as shown in Fig. 2, and a short distance behind the screen is an accurately positioned double wire grid, alternate wires being brought out to a common connection. When the wire grids are at the same potential the electron beam is made to converge towards the green strips because there is a potential difference of 13.5 kV. between the screen and the wire grids, and this produces an electron lens effect. If the wires are given opposite polarities as shown in Fig. 3, then the stream of negative electrons is attracted towards the positively charged wires and the beam strikes the red strips. Reversal of polarity will cause the beam to strike the blue strips. One disadvantage of the tube is that the colour presentation must be sequential; owing to its novel method of construction it is impossible to excite all colour phosphor strips at the same time. Nevertheless, it is possible to use an R.F. switching voltage and a "dot sequential" display is produced. Another disadvantage is the fact that the strips are laid

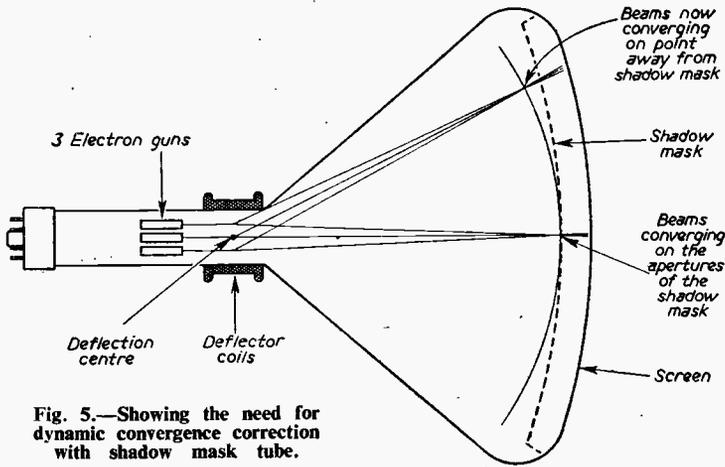


Fig. 5.—Showing the need for dynamic convergence correction with shadow mask tube.

These signals are of a parabolic wave form and are derived from the line and frame timebase generators. A further requirement is that the high voltage supply of 25,000 volts for the final anode shall be stabilised and special regulator valves have been developed for this particular service. All this adds considerably to the complexity of a colour TV receiver and may account for some of the increase in cost over a monochrome receiver. As mentioned in last month's article the Y, or brightness, signal is normally fed to the cathodes of all electron guns and the R-Y, B-Y, and G-Y signals are fed to the grids. In the latest

horizontally and are 720 in number, this limits the vertical definition, and can cause spurious patterning by a "beat" effect with the scanning lines. On the credit side there is the fact that it is a simple gun tube and requires much less setting up than the three-gun colour tubes; also it requires just the normal deflecting power as the wire grids are only at 4.5 kV. above the cathode, but despite this it can give a brilliant picture owing to the post deflection acceleration of 13.5 kV. referred to previously.

21-inch R.C.A. tube there are also separate screen electrodes which equalise the beam currents for all signal levels so that the three guns can be adjusted to give a true black-and-white picture when receiving non-colour transmissions. This type of phosphor dot tube seems to have stabilised itself in the American colour TV market and is now being produced by various firms, although there is still a lot of research being carried out to see if an even simpler receiving tube can be found.

Colour Dots

A screen of phosphor dots is used in the tube developed by R.C.A. The dots are arranged in groups of three, one for each primary colour, and these "dot triads" are distributed over the screen in a regular manner. A short distance behind the screen is a sheet of metal perforated with a large number of small holes, one hole for each group of phosphor dots, this is the shadow mask and in conjunction with the three electron guns in the neck of the tube it ensures that the screen may be caused to fluoresce in any desired colour. The dot screen is actually produced by using the shadow mask in a photographic printing process repeated three times, once for each colour phosphor. The electron guns are so situated in the neck of the tube that each gun, directing a stream of electrons at the shadow mask can only cause the dots of one colour to fluoresce (see Fig. 4). Thus the three electron guns are responsible for the images in each of the three primary colours. In practice the electron beam is wide enough to cover several holes and the spot on the screen is caused by the excitation of several dot triads, thus to the observer who is a reasonable distance from the screen the apparent colour spot depends on the relative intensity of the different colour dots. One of the disadvantages of this tube is the requirement that the three electron beams should all converge at a point on the shadow mask. This is easily arranged if the beams are stationary at the centre of the screen, but when they are deflected to one side of the picture the distance of the shadow mask from the centre of deflection is greater, and they must converge at a point farther away (Fig. 5). This means that the convergence depends on the position of the spot on the screen and thus dynamic convergence signals are fed to special convergence coils on the neck of the tube.

Discs Again ?

A method of receiving colour transmissions which will appeal to the amateur experimenter is that in which the simultaneous colour signal is turned into a frame sequential signal by gating the drive to the

(Continued on page 36)

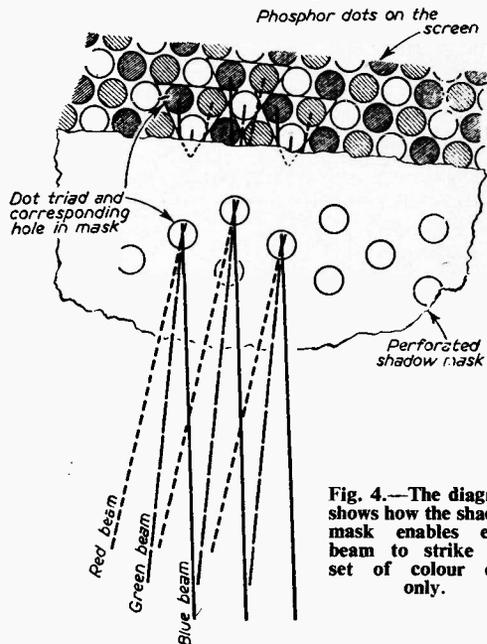


Fig. 4.—The diagram shows how the shadow mask enables each beam to strike one set of colour dots only.

THE I.T.A. NETWORK

SOME INTERESTING DETAILS OF THE COMPREHENSIVE RELAY SYSTEM

THE elaborate network of vision and sound circuits set up by the Post Office to enable the I.T.A. to operate the new independent television service has now been extended to Lancashire. Manchester and the new transmitter at Rivington Moor are now added to a network which has grown rapidly out of the local network of studio links provided for the first I.T.A. transmitter in London which opened as recently as 22nd September, 1955. The network is routed through the main Post Office repeater stations and links the I.T.A. transmitters at London, Lichfield and Rivington Moor to the various studios, theatres and master controls of the programme contractors.

Vision and sound circuits in the London network radiate from the Post Office Television Control at Museum Telephone Exchange near Tottenham Court Road. Television House in Kingsway, which accommodates the master control of Associated Rediffusion Ltd. and also the Independent Television News, is linked by two balanced cables to Museum yielding 10 vision circuits. The master control of Associated Television Ltd. at Foley Street is linked by two coaxial cables to Museum yielding eight vision circuits. Further vision circuits link Museum to the London I.T.A. transmitter and to a number of studios and theatres in London, some as far distant as Wembley. Vision circuits have also been

(Continued on page 26)


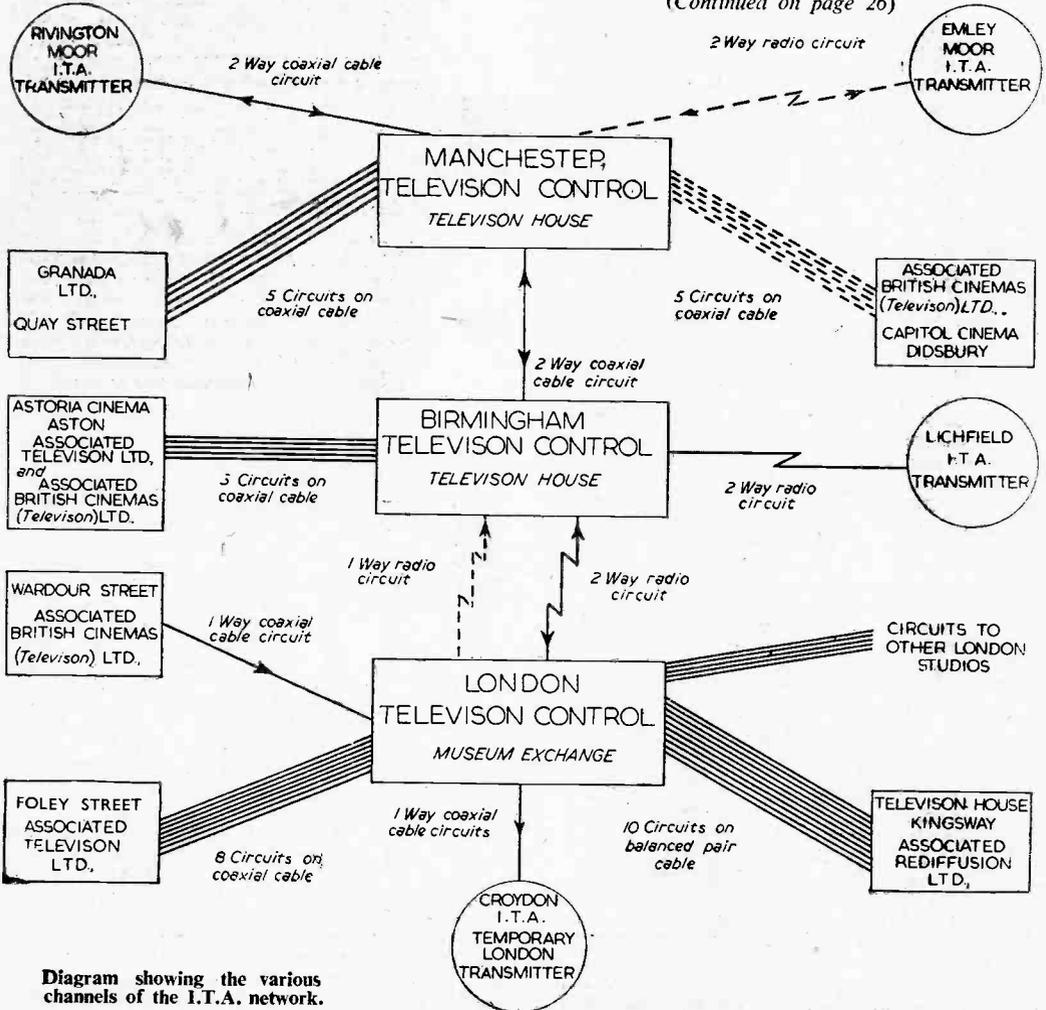


Diagram showing the various channels of the I.T.A. network.

BAND 1 pre-amplifier

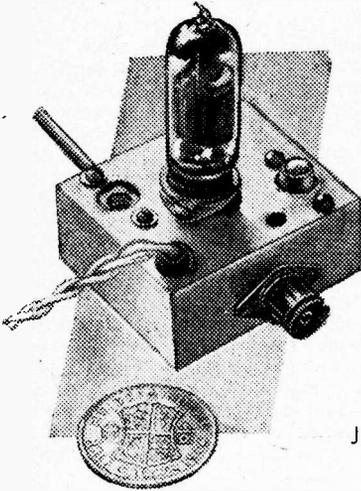

By
J. E. Tanner

THE writer was asked to try to improve the reception on a friend's TV. After checking the valves in the R.F. stages, it was decided that a pre-amp. was necessary, and the one shown here was built and is proving very successful; there are no special circuits and everything is quite straightforward. The main feature of it is its small size—only 2½ in. x 2 in. x 3½ in. with valve.

The Circuit

The circuit is built up round the well known EF91 valve. This is very common and is readily available on the surplus market at about 7s. 6d. There is a tuned circuit in the anode and grid, and the decoupling for the anode is provided by a 4.7k. resistor and a 500 pF capacitor. The cathode is by-passed with another 500 pF capacitor. The pre-amp. is very easy to line up and shows no sign of instability. The

AN INEXPENSIVE PRE-AMPLIFIER FOR IMPROVING RECEPTION

bandwidth is quite sufficient to give a really good improvement in both vision and sound.

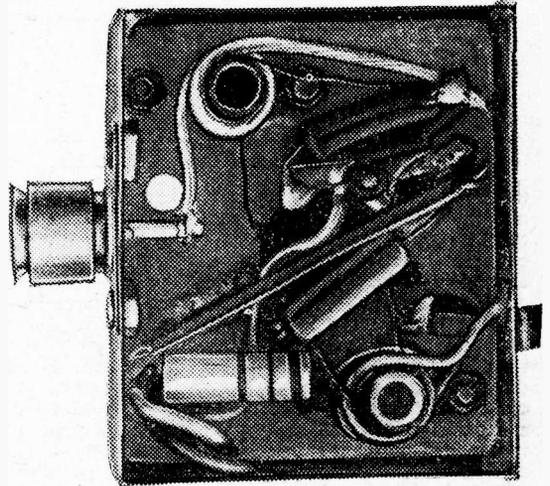


Fig. 3.—Under-view of chassis showing the layout.

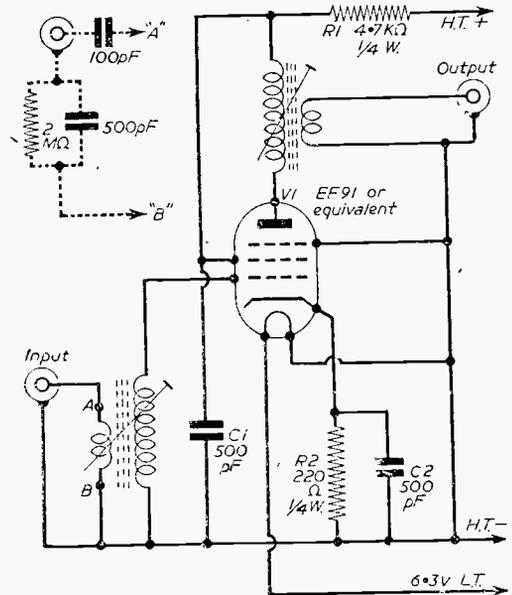


Fig. 1.—Circuit diagram of amplifier using EF91.

Building the Pre-amp.

First, the chassis should be cut out and bent up: the material used is not critical, but in the original ordinary tin-plate was used because the chassis is sufficiently small to hold itself rigid, and tin-plate is easy to solder at the corners. No special tools are necessary: a hammer, a file, a pair of metal shears, a drill and a soldering iron only were used in the original. The large hole may cause some difficulty, and if a chassis cutter is not available a ring of small holes should be drilled and the edges filed smooth afterwards, a large drill should not be used because it tends to tear and stick. All the holes for cables, core adjustments, etc., should be drilled after clamping the metal firmly between two pieces of wood. The hole for the power supplies should be provided with a grommet. The internal screen should be soldered in position after mounting the valveholder, and the screen soldered to pin 3 on it. This eliminates the need for any wires to pass from one compartment to the other. Any other details regarding the chassis should be self-explanatory from the drawing (Fig. 2). When the chassis is completed and the valveholder and the screen fixed, the coil formers and three-way tag strip should be fixed in their positions. All is now ready to wire up the input compartment: first, wind the coil (11 turns for Channel 1, London) according

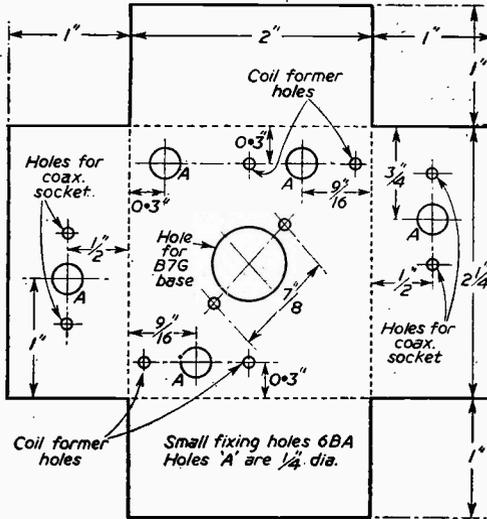


Fig. 2.—Showing drilling and fixing hole details.

to the table. Now solder in the cathode resistor and condenser after having previously twisted them together. Connect the "earth" ends of the coil and cathode circuit to a common point in the middle of the screen (no earthing tag provided—it is possible to solder directly to the screen). The aerial input coil is two turns of about 20 gauge P.V.C. insulated cable wound round the aerial coil as near to the centre of the coil as possible. It should be wound in the same direction, and the same end earthed as in the grid coil; the other end goes directly to the co-axial input socket. The other end of the grid coil is wired directly to the grid pin on the valholder (pin 1). This completes the input compartment. For the position of the bias resistor and capacitor see the drawing of the component layout (Fig. 3). Now proceed to the output compartment; first wire the heater lead from the tag board to pin 4, then wind the coil with the same number of turns as the aerial coil. Take one end to pin 5 and the other to pin 7. Earth pin 6 to

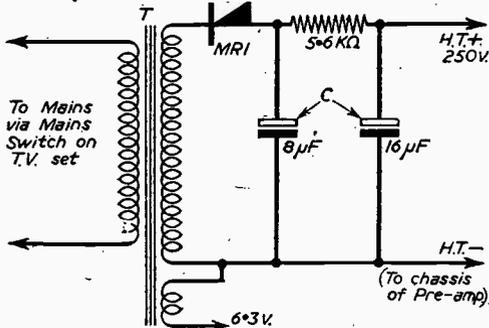


Fig. 4.—The circuit diagram of the power unit. MR1—Any metal rectifier or combination of rectifiers giving 250 volts at 15 mA. (2 RM1 in series.)

T—Mains transformer giving :

- (i) 250 volts at approximately 25 mA.
- (ii) 6.3 volts at approximately .3 amp.

C—Electrolytic condenser—8 and 16 mfd. 300 volts working.

the nearest point on the screen. From pin 7 take a 500 pF to the same point on the screen as pin 6, and take a 4.7 k. to the other spare tag on the tag board. The output coupling coil is wound in an exactly similar way to the input coil, with the same number of turns (two). Now connect the three power leads to the tag board, taking care to note which is which.

Testing and Lining-up

After checking connect aerial (70 ohm co-axial) to the input and a co-axial lead from the output to the aerial of the set. Connect up the power supplies and switch on. Allow the normal warming-up time to pass, set the contrast and volume controls for maximum gain, reducing them as the signals get stronger. Using a knitting needle filed to a screwdriver shape, or any other similar trimming tool, slowly adjust L1 for maximum vision, then adjust L2 in a similar manner. The sound signal should be strong enough, but if not a slight readjustment of the cores will solve the problem.

Power Supplies

The current consumption is small enough to permit both the H.T. and the L.T. being taken from the main set. This is permissible in sets with the chassis isolated from the mains, but in the A.C./D.C. type of set a separate power unit is necessary. This can be of standard design and a circuit is given (Fig. 4).

Coil Winding Table

Channel	Turns
1	11
2	10
3	9
4	8
5	8
Coupling coils have two turns for all channels.	

However, some sets use a transformer for L.T. only. In this case the pre-amp. may be used on the existing power supplies, if the aerial socket is mounted on a small paxolin sheet and wired up as shown in dotted lines.

GLASS PROCESS FOR TV EQUIPMENT

MULTIFORM glass, the result of a new method of fabrication, originally developed in the United States, is now being produced for the first time in Britain at the works of James A. Jobling & Co., Ltd., of Sunderland, world-famous manufacturers of heat-resisting glass.

In this process specially treated glass powders are compressed in moulds and subsequently fused to form a uniform opaque glass, destined in the main for the electronics industry, where high-precision glass parts are required for television tubes and mounting electrodes.

By the new method the existing difficulty of making small and accurately dimensioned articles on long production runs is eliminated, for Multiform glass can be controlled to one-thousandth of an inch.

Production is being initially confined to television gun-mount rods and to small beads which are being manufactured for glass-to-metal seals in order to speed up certain classes of production in the electronics field.

C.R.T. ISOLATION TRANSFORMER

Type A. Low leakage windings. Ratio 1:1.25 giving a 25% boost on secondary.
2 v. 10/6; 4 v. 10/6; 6.3 v. 10/6; 10.8 v. 10/6; 15.3 v. 10/6.
Type B. Mains Input 230/240 volts. Multi Output 2, 4, 6.3, 7.3, 10 and 13 volts. Input has two taps which increase output volts by 25% and 50% respectively. Low capacity, suitable for most Cathode Ray Tubes. With Tag Panel, 21/- each.
Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emission. Input 220/240 volts. Output 2-21-21-21-3 volts at 2 amps. With Tag Panel, 17/6 each.

NOTE—It is essential to use mains primary types with T.V. receivers having series-connected heaters.
TRIMMERS, Ceramite, 30, 50, 70 pf., 9d., 100 pf. 50 pf. 1/3; 250 pf. 1/6; 500 pf. 750 pf. 1/3.
RESISTORS. All values. 10 ohms to 10 meg., 1/4 w., 4d.; 1/2 w., 6d.; 1 w., 8d.; 2 w., 1/-.
HIGH STABILITY. 1/2 w., 1% 2/- Preferred values 100 ohms to 10 meg.
WIRE-WOUND RESISTORS { 1/3 5 watt 25 ohms—10,000 ohms 1/6
2-15,000 ohms—50,000 ohms, 5 w., 1/9; 10 w., 2/3.
KNOBBS, GOLD ENGRAVED.—Walnut or Ivory, 1 1/2 in. diam., 1/6 each. Not engraved, 1/- each.

PURETONE RECORDING TAPE

1,200 ft. on standard fitting 7" Plastic reels. Brand new, boxed, 17/6.
Spools 5" metal 1/6, 7" plastic 4/3.

O/P TRANSFORMERS. Heavy Duty 50 mA., 4/6. Multitrate, push-pull, 6/6. Tapped small pentode, 2/9. L.P. CHOKES 15/10 H. 60/65 mA., 5/-; 10 H. 120 mA., 15/6; 15 H. 150 mA., 12/6.

MAINS TRANS. 230-0-230, 80 mA., 6.3 v. tapped 1 v. 4 a., 5 v. tapped 4 v. 2 a., ditto 250-0-250, 21/-.
HEATER TRANS. Tapped prim., 200-250 v. 6.3 v. 1 1/2 amp., 7/6; tapped sec. 2, 4, 6.3 v., 1 1/2 amp., 8/6.
VC897 TESTED FULL PICTURE, 22.

COPPER PLATED AERIAL RODS. 1/2 x 12 in. push fitting, 3/4 doz. per p. 1/-.
ALADDIN FORMERS and core, 1 in., 8d.; 1 in., 10d. 1/2 in. FORMERS with Caps and Core, 1 in. sq. x 1 1/2 in. and 1 in. sq. x 2 1/2 in., 2/- ea.

TYANO. Midget Soldering Iron, 200/220 v. or 200/250 v., 14 1/2. Solder Midget Iron, 24/-.
MIXER TRANS. Ratio 50:1, 3/6 ea.
MAINS DROPPERS. 3 x 1 1/2 in. Ado. Sliders, 3 amp. 750 ohms, 4/3. 2 amp., 1,000 ohms, 4/3.

LINE COIL. 3 amp., 60 ohms per foot, 3 amp., 100 ohms per foot, 2 amp., 6d. per foot, 3-way, 7d. per foot.
LOUDSPEAKERS P.M. OR M.
5 in. Goodman's, 17/6. 7 in. x 4 in. Goodman's, 21/6. 3 1/2 in. square ELAC, 21/-.
8 in. ELAC, 25/6. 10 in. R. & A. 30/-.

4 in. ditto w/Trans., 18/-.
12 in. Plesey 30/-.
8 in. M.R. 2.5 k. or 2 k. field, tapped O.P. Trans., 24/6.
CRYSTAL DIODES. G.E.C., 2/- Crystal Book, 1/-.
GEX24, 4/-, 40 Circuits for Germanium Diodes, 8/6.
HIGH RESISTANCE PHONES. 4,000 ohms, 17/6 pr.

CRYSTAL MIKE INSERT by Acos, precision engineered. Size only 1 1/2 x 3/16 in. Bargain Price 6/8. No transformer required.


SWITCH CLEANER Fluid, squirt sprout, 4/3 tin.
TWIN GANG TUNING CONDENSERS. .0005 mfd. mid. with trimmer, 8/6; .375 pf. mid. get. less trimmers, 6/6; .0005 Standard size with trimmers and feet, 9/-; less trimmers, 8/-; ditto, soiled, 2/6.
SPEAKER FEET. Woven Plastic TYGAN. Walnut tone. 12 in. wide, 2/- per foot. Expanded metal, Gold 9 x 12 in., Silver, 15 in. x 9 in., 2/- each.

VALVES
A SMALL SELECTION FROM OUR STOCKS
All Boxed 1/6 New & Guaranteed

8/6	5/6	1/6	6/6	10/6
1R5	6B8	934	GAL7	5Z4
1T4	9Y2	2/6	GJ5	12AT7
185	Equip.	2X2	6K6	EF80
354	Equip.	EB33	6K7G	EBH35
3V4	Equip.	EB34	EB91	ECG40
5U4	SP41	3/6	HVR2	ELCH22
6AM6	EF92	3/6	EB41	(near)
6AT6		6HEM	EF90	
6J7	7/6		EL41	
6K5	6BE5	7/6	EL32	EZ40
6SL7	6BW6	6K4	HVR2A	KT385
6SN7	6P6	6K5	PE23	MT14
6V8CT	6K7G	807	U22	PY81
EB23	6K7M	EF30	VP23	EX51
EP50				607
SPV. Red	12K8, 12Q7, 12K7, 35L6, 35Z4			Special Price—37/6 Net.
EP91				X79

We have no connection with any other firm. Please address all Mail Orders correctly as below.

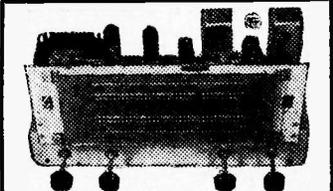RADIO COMPONENT SPECIALISTS 307 WHITENORSE RD., WEST CROYDON
OPEN ALL DAY—(Wed. 1 p.m.) 10 page list 1/6
Tel. THO 1665, Buses 133 or 63 pass door. 48-hour postal Service. P. & P., 1/- £2 orders post free. (Export Extra.) C.O.D. Service J/6



ALL WAVE RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES
S.W. 16 m.—50 m. LATEST MULLARD
M.W. 200 m.—550 m. ECH42, EF41, EB41,
L.W. 800 m.—2,000 m. EL41, EZ40.
12 month Guarantee.
A.C. 200/250 v. 4-way Switch; Short-Medium-Long-Gram. A.V.C. and Negative feedback.
4.2 watts. Chassis 13 1/2 x 5 1/2 x 2 1/2 in. Glass Dial 10 x 4 in. horizontal or vertical available.
2 Pilot Lamps, Four Knobs, Walnut or Ivory. Aligned and calibrated. Chassis isolated from mains.
10 gns. Carr. & Ins., 4/6.
MATCHED SPEAKERS FOR ABOVE CHASSIS
8 in., 19/6; 10 in., 25/-; 12 in., 30/-.

R.C.S. SCOOP

Collaro Auto-changer EC551 for 78 r.p.m. 10 in. and 12 in. records. Brand new in maker's boxes! High impedance lightweight Pick-up with sapphire needles, will match any Amplifier or Radio. Less than half price.
£5.19.6. carr. and ins., 5/6.



£7-19-6 Post Free.

Brand new Plesey 3-speed Autochanger Mixer Unit for 7, 10 and 12 in. Records. Twin Hi-Fi Xtal Head with Duopoint sapphire stylus. Plays 4,000 records. Spring mounting. Base-board required 15 1/2 x 12 in. Height 5 1/2 in. Depth 2 in. Super Quality, 200/250 v. A.C.

Walnut Veneered Playing Desk out ready for Plesey, only sold complete with Changer 10/6 extra.

AMPLION. 3-speed Single Record unit with Acos 37 Turnover Head, each Sapphire Stylus plays 2,000 records. Starting Switch Automatically places Pick-up on records, 7 in., 10 in. or 12 in. Auto Stop. Baseplate 12 x 6 in. Height 2 1/2 in. Depth 1 1/2 in. Price £7.15.6, post free.

B.S.R. MONARCH. 3-speed Motor and Turntable with selecting switch for 32, 45 and 78 r.p.m. records, 100-120 v. and 200-250 v. A.C. 50 cps. Also B.S.R. MONARCH Lightweight Pick-up with Acos Xtal turnover head, separate Sapphire stylus for L.P. and Standard records. SPECIAL OFFER, THE TWO! £4.15.6, post 2/6.

T.V. PRE-AMP. (McMICHAEL). Tunable Channel-1 to 5. (Will Amplify Output of your Brand 3 Converter.) Midsize size. High Gain Fringe Model, B.V.A. Valve, Full instructions. Ready for use. (H.T. 200 v., L.T. 8.3 v., 3 amp. required.) BRAND NEW, 25/- each. SPECIAL MAINS POWER PACK for above, 25/- extra.

F.M. TUNER COIL KIT, 22/6. I.F. coil, Aerial coil, Oscillator Coil, two H.F. Transformers 10.7 Mc/s. Detector transformer and heater choke. With circuit and component list, using four 6AM6. Chassis and Dial, 19/6.

TELETRON BAND III CONVERTER
For London, Midland and Northern Transmissions.

Suitable all T.V. makes. T.R.F. or Superhet. Ready wound coils, two EF90 valves, all components, punched and fitted circuit diagram, wiring plans. COMPLETE KIT for mains operation 200-250 v. A.C. £3.10.0.

As ABOVE less POWER PACK. Requires 200 v. 20 mA. H.T. 6.3 v., 5.6 A. L.T. £2.5.0.
Mains Transformer to above Spec. 10/6
Min. Westinghouse Rect. ditto 8/6
B.B.C./I.T.A. crossover unit 7/6
Punched and drilled chassis 3/9
Larger chassis for Mains Model 6/-
Teletron Coilset with plans 15/-
Full plans and circuit details 6d.

Volume Controls 80 ohm COAX CABLE

Long spindles. (Guaranteed 1 year.) All valves Semi-air spaced. Polyethylene insulated. 1 in. dia. 10,000 ohms to 2 Meg. Stranded core. 9d. yd. No Sw. S.P.S.W. D.P. Sw. Losses cut 50% 3/4 4-9 STANDARD 8d. yd. Ext. Spkr. Type, 3/- 1 in. Coax.

COAX PLUGS ... 1/- DOUBLE SOCKET ... 1/3
SOCKETS ... 1/- OUTLET BOXES ... 4/6
BALANCED TWIN FEEDER, yd. 6d. 80 or 300 ohms. **DITTO SCREENED yd. 1/-**, 80 ohms only.
WIRE-WOUND POTS, 3 WATT. Pre-Set Min. T.V. Type. All values 25 ohms to 30 K, 3/- ea. 50 K, 4/- (Carbon 50 K. to 2 m., 3/-).

WIRE-WOUND 4 WATT. Pots, 2 1/2 in. Spindle. Values, 100 ohms to 50 K, 5/6; 100 K, 6/6. **WERNERS.** New stock. 64-101 mfd., 7/6. T.C.C., 5/6. Ditto, 20 kV., 9/6; 100 pf. to 500 pf. Micas, 6d.; Tubular 50 v., 001 to 01 mfd., 9d.; .05, 1, 1/-; .25, 1/6; .5 1/9; 1/350 v., 9d.; 1/600 v., 1/3; 1 mfd. 2,500 volts 5/6.

CERAMIC COND. .500 x 3 pf. to .01 mfd., 10d. **ALUMINUM CONDENSERS.** 10%, 5% to 500 pf. 1/-; 600 pf. to 3,000 pf., 1/8. **DITTO 1%, 1.5 pf. to 500 pf., 1/9; 515 pf. to 1,000 pf., 2/-**

I.F. TRANSFORMERS 7/6 pair
405 Kcs Slog tuning Miniature Can, 2 1/2 in. x 1 1/2 in. Eight 4 and good bandwidth. By Eye Radio. Data sheet supplied.

NEW ELECTROLYTICS, FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES	5/6
1275 v. 2/-	100/25 v. 2/-	8+16/500 v. 5/6	
2/450 v. 2/6	16+16/500 v. 4/6	16+16/450 v. 5/6	
4/450 v. 2/6	16+16/500 v. 4/6	16+24/350 v. 4/6	
8/450 v. 2/3	6/-	32+32/350 v. 4/6	
8,500 v. 2/3	CAN TYPES	32+32/450 v. 5/6	
16/450 v. 3/6	Clips	64+120/275 v. 7/6	
32/450 v. 4/-	16/450 v. 3/6	64+120/350 v. 8/6	
32,500 v. 5/6	32/350 v. 4/6	100+200/275 v. 5/6	
25/25 v. 1/6	60/350 v. 5/6		12/6
30/25 v. 1/9	500/12 v. 3/-	1,000+1,000/6 v. 6/6	
50/50 v. 2/-	8+16/450 v. 5/6		6/6
1275 v. 2/6	512, 9/500 v. 4/6	16/500 v. 4/6	
SPECIAL KEYS	E.H.T. TYPE FLT. BACK VOLAGES, K3/25 2 kV., 4/3; K3/40 4 kV., 3/6; K3/45, 3.8 kV., 6/6; K3/50 4 kV., 7/6; K3/100 8 kV., 12/6; MAINS TYPE, RM1, 125 v., 60 mA., 4/-; RM2, 100 mA., 4/6; RM3, 120 mA., 6/6; RM4, 250 v., 275 mA., 12/6.		
G.E.C. Neon Ouglim, M.B.C. 180 v. 5 mA., 2/6.	COILS Wearite, "P" type, 3/- each. Osom Midget "Q" type adj. dust core, 4/- each. All ranges TELETRON, L & Med., with re-action, 3/6.		
H.F. CHOKES, iron cored, 14 M.H., 5/- each.			

ALUMINIUM CHASSIS. 18 s.w.g. un drilled. With 2 sides, riveted corners and lattice fixing holes, 2 1/2 in. sides, 7 x 4 in., 4/6; 9 x 6 in., 5/9; 11 x 7 in., 6/9; 13 x 6 in., 8/6; 14 x 1 1/2 in., 10/6; 15 x 14 in., 12/6; 18 x 16 x 3 in., 16/6.

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 2, 6 or 12 v. 1 1/2 amp. 6/9; 2 a., 11/6; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input, 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amp., 13/6; 4 amp., 21/-.

ALL BERNARDS books in stock.
VALVE MANUALS I & II, 5/- ea. part.
VALVE and TV Tube equivalent's book, 5/-.
ACID HYDROMETER. New Ex Good. Unusable. Packed in metal case 7 x 1 1/2 in. Dia., 4/6.

WAVELENGTH SWITCHES.
5 p. 4-way 2 water, long spindle ... 6/6
2 p. 2-way, 3 p. 2-way, short spindle ... 2/6
2 p. 2-way, 4 p. 2-way, 4 p. 2-way, long spindle 3/6
3 p. 4-way, 1 p. 12-way, long spindle, long spindle 3/6

VALVEHOLDERS. Fax. Int. Oct. 4d., EF50, EA50, 6d. B12A, CRT, 1/2 in. Eng. and Amer. 4, 5, 6, 7 and 9 pin, 1/-.
MOULDED Masda and Int. Oct. 6d.
B7G, B9A, B9G, B9A, 8d., B7G with can 1/6.
VC897 2/6, B9A with can 2/6.
CERAMIC, EF50, B7G, B9A, Int. Oct. 1/-, B7G with can 1/6.

BLACK CRACKLE PAINT, air drying, 3/- tin.

OSMOR VARIABLE Band I ATTENUATOR

Balance reception of ITA and BBC in all areas and avoids constant adjustment of controls. The Osmor is the only variable attenuator that will reduce the signal exactly to the required level. Easily Fitted—just plug in. Reduction ratios variable 2-1 to 10-1. An Essential with all types of Band III Converters. 15/- From your Dealer—or direct.

BAND I FILTER

Rejects BBC from ITA aerial and improves picture. Suitable for all makes. 10/- inc. instructions. Fitted in two minutes.

ITA CONVERTERS LONDON · LICHFIELD · MANCHESTER


A very efficient Band III Converter for all TV sets of any age (including TRF). Approximately one hour to build! Guaranteed no breakthrough of Band I. Will convert any Band III Channel to any Band I Channel. Station switching. A.C. or A.C./D.C. Size 4½ in. x 2½ in. x 3 in. Circuits, Wiring Diagrams and full constructional information, ready to fit inside your TV cabinet.

Complete Kit

65/-

Completely wired

80/-

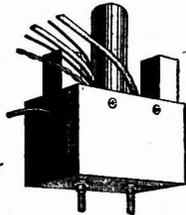

FREE We keep right up to date in building the latest circuits published in "Practical Wireless," "Wireless World" and "Radio Constructor" and we stock the components specified. Send 7½d. in stamps for circuits, fully descriptive literature together with coil and coilpack leaflets, component lists, chassis drawings and templates.

ITA Band III CONVERTER KIT

Complete with all components, including power unit, for construction of an efficient Band III converter. Nothing else to buy. Circuit, wiring diagram, chassis templates and complete instructions, £6.19.0.

OSMOR RADIO PRODUCTS LTD. 418 Brighton Road, South Croydon, Surrey. Croydon 5148-9

RADIO SUPPLY CO. (LEEDS) LTD.

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/- extra under 10/-; 1/6 extra under £1; 2/- under £3. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 6d.; Trade list 5d.

R.S.C. TRANSFORMERS

Fully Guaranteed. Interleaved and Impregnated.
TOP SHROUDED DROP THROUGH
 250-0-250 v 70 ma, 6.3 v 2 a, 5 v 2 a ... 16/9
 350-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a ... 18/9
 250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 29/9
FULLY SHROUDED UPRIGHT
 250-0-250 v 60 ma, 6.3 v 2 a, 5 v 2 a ... 17/6
 Midget type, 21-3-3in. ... 26/9
 250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 26/9
 for R135 Convension ... 31/-
 300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 26/9
 350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-350 v 150 ma, 6.3 v 4 a, 0-4-5 v 3 a ... 31/6
 425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a ... 49/9

FILAMENT TRANSFORMERS
 All with 200-250 v 50 c/s Primaries: 6.3 v 1.5 a, 5.0; 6.3 v 2 a, 7.6; 0-4-6.3 v 2 a, 7.9; 12 v 1 a, 7.11; 6.3 v 3 a, 8.11; 6.3 v 6 a, 17.9.
CHARGER TRANSFORMERS
 200-250-0-9-15 v 1 a, 11.9; 0-9-15 v 3 a, 16.9; 0-9-15 v 5 a, 19.9; 0-9-15 v 6 a, 22.9.

OUTPUT TRANSFORMERS
 Standard Pentode 5,000 to 30hms ... 4/9
 Small Pentode 5,000 to 30hms ... 3/9
F.I.L.T. TRANSFORMERS 200-250-250 v 2, 250 v 5 ma, 2-0-2 v 1.1 a, 2-0-2 v 1.1 a for VCR37, VCR517 ... 36/6

SMOOTHING CHOKES
 250 ma 5 h 50 ohms ... 11/9
 100 ma 10 h 250 ohms ... 8/9
 80 ma 10 h 350 ohms ... 5/9
 60 ma 10 h 400 ohms ... 4/11
SELENIUM METAL RECTIFIERS
 G.E.C. 300 v 250 ma, 12.9; 120 v 40 ma, 3/9; 6/12 v 1 a F.W., 5.9; 240 v 50 ma, 5.9; 6/12 v 2 a F.W., 8.9; 6/12 v 4 a, 16.9; 250 v 90 ma, 7.9; 6/12 v 6 a F.W., 19.9; 6/12 v 10 a, 29/6.

BATTERY SET CONVERTER KIT
 All parts for converting any normal type of Battery Receiver to A.C. mains 200-250 v 50 c.s. Supplies 120 v 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. 2.2 v and 0.4 a to 1 a. Price including circuit 49.9. Or ready for use, 9.9 extra.
ALL DRY RECEIVER BATTERY ELIMINATOR KIT.—All parts for the construction of a unit (metal-case 51-41-2in.) to supply Battery Portable receivers requiring 30 v and 1.5 v. Fully smoothed. From 200-250 v 50 c.s. mains. Price, inc. point-to-point wiring diagrams, 39.9. Or assembled and tested at 49.9.

R.S.C. TA1 HIGH QUALITY TAPE DECK AMPLIFIER. For ALL Tape Decks with High Impedance, Playback and Erase Heads, such as Lane, Truvox. Adjustment to type of deck. Ready for use by alteration of a resistor. For A.C. Mains 230-250 v. 50 c.s. Positive compensated identification of recording level given by Magic Eye. Recording facilities for 15, 7½ or 3½ in. per sec. Automatic equalisation at the turn of a knob. Linear frequency response of ± 3db, 50-11-000 c.p.s. Negative feed-back equalisation. Minimum microphony and hum. High output with completely effective, erasure and distortionless reproduction. Sensitivity is 15 millivolts so that any kind of crystal microphone is suitable. Provision is made for feeding a P.A. amplifier. Unit can also be used as a gram-amplifier requiring input of 0.75 v R.M.S. Carriage 7.6. Illustrated leaflet 6d.
EX-GOVT. UNIT RDE1.—Brand new, cartoned. Complete with 14 valves, including 5Z4G. Also mains trans. L.F. choke rectifier, etc., etc. Only 29.9. Carr. 7/8.

Dept., N. 32, THE CALLS, LEEDS 2.

SMALL POTTED MAINS TRANSF.
 Remove from New Ex-Govt. units.
 Primary 0-200-230-250 v Secs 250-0-250 v 60 ma, 6.3 v 2 a, 5 v 2 a. 11/9
 Size 3½ x 4½ x 3 in.

CO-AXIAL CABLE 1in.
 75 ohms 14.36 ... 8d. 3d.
 Twin-screened Feeder ... 11d. 3d.
EX-GOVT. SMOOTHING CHOKES.
 100 ma 10 h 250 ohms Tropicalised ... 3 11
 150 ma 6-10 h 150 ohms ... 6 9
 150 ma 10 h 150 ohms ... 11 9
 250 ma 10 h 50 ohms ... 14 9

E.H.T. SMOOTHERS
 .5 mid 2,500 v Blocks (ex-Govt.), 2 11.
BATTERY CHARGER KITS.—Consisting of attractive Green Crackle Case, Transformer, F.W. Rectifier, Fuse, Fuseholder, Tag strip, Grommets and Circuits. For mains input 200-230-250 v 50 c.s. 6 v 2 a, 25.9; 6 v or 12 v, 2 a, 31.6; 6 v or 12 v, 4 a, 49.9. Any type assembled and tested for 6/9 extra.

R.S.C. 6 v or 12 v BATTERY CHARGER
 For normal A.C. mains input 200-230-250 v 50 c.s. Selector panel for 6 v or 12 v charging. Variable Charge rate of up to 4 AMPs. Fused, and with meter. Well ventilated case with attractive hammer finish. Guaranteed for 12 months. 69/6. Carr. 2/6.



TV CABINETS
 Handsome well-constructed with walnut veneer finish. Size 18in. high, 20in. wide, 13in. deep. Size of aperture 17in. 13½in. Fitted Doors. For 15in. or 17in. Tube. Limited number at only 79/6 Plus 7/6 carr.
Table Model, 412in. Tube, 29/9, 5/- carr. BATTERY CHARGERS.—For mains 200-250 v 50 c.s. Output for charging 6 v or 12 v at 1 amp. In strong metal case. Only 25.9. Above can also be used for electric train power supply.

CIRCUIT EFFECTS AT HIGH FREQUENCIES

THE EFFECTS OF STRAY CAPACITANCES

By C. H. Banthorpe

Decoupling

It is not always appreciated by the experimenter how important are the effects of stray capacitance and inductance which inevitably become added to a circuit when it is made up from a circuit diagram. These "strays" explain many cases where circuits which appear to be good on paper are disappointing in practice, where wide differences occur between the performance of the same circuit made up by different constructors and, something which must have happened to us all at some time, the difference between the performance of a "breadboard" circuit and the cleaned-up edition.

One danger point is inductance which occurs in the leads of capacitors. For instance, it is important that decoupling capacitors should not only be of a suitable capacity but also of a suitable physical construction. At high frequencies the impedance of the inductance of the leads to a capacitor may be so great that the capacitor will be quite ineffective for decoupling purposes. If the value of a capacitor is chosen to form, with its lead inductance, a series resonant circuit at the operating frequency, then the decoupling effect can be actually improved. Fig. 1 shows two most interesting curves. It will be seen that the capacitor used as a stand-off and with a 0.5 cm. lead has a lower impedance over the band 10 mc/s to 75 mc/s, approximately, than that of a 1,500 pF. capacitor with no series inductance. Above 75 mc/s, however, the combination becomes much worse than the same capacitor used as a feed-through or than the theoretical 1,500 pF. If the lead cannot be reduced below 0.5 cm. then a smaller value capacitor would provide better decoupling or it should be feed-through connected.

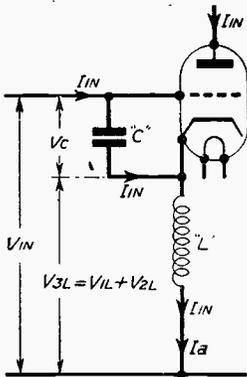


Fig. 2.—Grid-cathode capacity (C) and circuit constants.

Sometimes a decoupled point has two capacitors, e.g., a 0.1 μ F and a 0.001 μ F in parallel between it and the point to which it is coupled, chassis, cathode, etc. The object is to provide a low impedance at lower frequencies by means of the larger capacitor and a low impedance at high frequencies by the small capacitor, it being assumed that the inductance of the large capacitor prevents it being effective at high frequencies. What is not always remembered, however, is that the small capacitor may form a parallel resonant circuit with the effective inductance of the larger capacitor and at some frequency practically no decoupling at all will be present.

If the cathode circuit of a valve is not properly decoupled at high frequencies an effective resistor can appear between the grid of the valve and earth.

This resistor will damp the input circuit and this may be undesirable as too much damping may occur. A simplified explanation of how this resistance appears is as follows.

Assume that at the frequency considered the cathode circuit is effectively an inductance, "L." This is due to the actual length of leads from the real cathode of the valve to the external circuit and to the

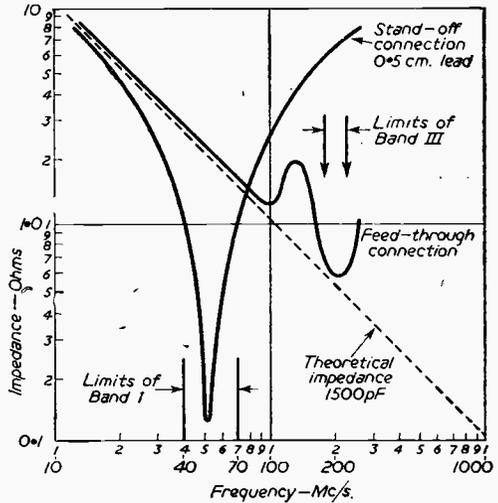


Fig. 1.—Set of curves for a Dubilier stand-off insulator, reproduced by courtesy of Messrs. Dubilier.

inductance of the leads of the decoupling capacitor, etc. This assumption is true up to some high frequency, the actual frequency depending upon the type of valve, components and length of wiring. Fig. 2 shows the circuit with the input capacity of the valve shown as "C."

To show that an effective resistor appears across the input, it is only necessary to prove that the input voltage is no longer lagging the input current by 90 deg., as it would be if there were no impedance between the cathode and earth, when "C" would be directly across the input which would, therefore, appear to be purely capacitive to the external circuit.

Fig. 3 shows the vectors of the circuit, the various current and voltages also being marked as on Fig. 2.

An input current I_{in} flows through "C" and "L" and causes a voltage V_C and V_L , respectively, to appear across each of them, the two voltages being 180 deg. out of phase because the current through a capacitor leads the voltage across it while the reverse is true in the case of an inductor. The voltage developed across "C" by I_{in} is the grid/cathode voltage of the valve, and this causes an anode and cathode current I_a in phase with V_C . There are thus two currents flowing through "L," one, I_{in} , produces a voltage V_L which leads I_{in} by 90 deg. and a

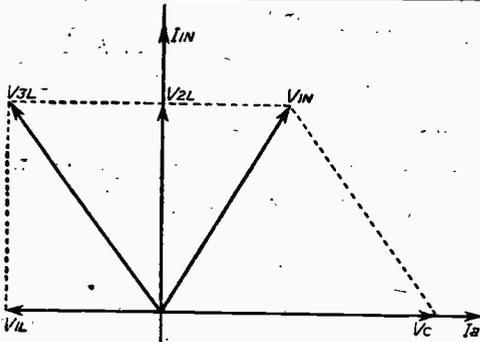


Fig. 3.—Circuit constants of Fig. 2 shown in vector form.

New Safety Aid in London Power Station

A NEW type of periscopic television unit, incorporating Marconi industrial TV equipment, has been installed at Barking "C" power station for the remote observation of the interior of a boiler furnace.

With furnaces of the latest type, such as are installed at Barking "C," it is essential that the jet-injected pulverised fuel remains ignited at all burners, otherwise a serious explosion might result. This has hitherto been ensured by constant observation through small inspection doors, but modern boilers have now become so tall that a complete tour of inspection could take half an hour and involve climbing more than 100ft. of galleries and ladders.

The new periscopic TV unit solves this problem by enabling all burners to be observed by one television camera, the resultant picture being displayed on a monitor screen, or screens, at any convenient points in the power station. The comprehensive view obtained is far greater than is possible by direct visual examination through any one inspection door.

Basically, the unit consists of two main assemblies, namely the panoramic periscope and the industrial TV camera.

The periscope is completely water-cooled, with an incorporated air-blast to keep fly ash from settling on the lens windows. Twin-entrance apertures are used, with lenses and prisms so arranged that the two fields of view are combined in panoramic form, with a dividing line at the centre of the picture. A field of 90 deg. in one plane and 45 deg. in the other can easily be resolved.

The camera, which forms part of the standard Marconi industrial equipment, measures only 5½ in. by 4 in. by 8½ in. and weighs only 4½ lb. The output from it is fed to a Control Unit and thence to the monitor screens, which may be up to 2,000ft. away from the camera itself.


second, I_A , which produces a voltage V_{2L} which leads I_A by 90 deg. When these two voltages are added together *vectorially* they produce V_{3L} . V_{3L} and V_C added together *vectorially* produce V_{IN} . It will be seen that V_{IN} is not lagging I_{IN} by 90 deg. as it would be if the input was purely capacitive (" L "=0) but is less than 90 deg.

This is the same so far as the input circuit is concerned, as if the input consisted of a pure capacitor and a pure resistor across V_{IN} . The magnitude of the resistance depends, among other things, upon the value of the inductor in the cathode circuit. It will be seen that extra damping occurs in the input circuit if the cathode circuit of the valve is inductive. Other somewhat unexpected effects which occur in circuits and valves at high frequencies will be discussed in later articles.


The complete unit is mounted on a carriage which is designed to project the nose of the periscope through a 4 in. diameter aperture in the furnace wall, or to retract the unit from the furnace when it is not required to view the interior. The carriage is power-operated by compressed air, and is remotely controlled. Specially-designed entrance mechanisms ensure that "blow-back" from the furnace cannot occur during the operation, while a full complement of safety interlocks guard against failure of the cooling water or blast air supplies.

The periscope unit is normally used only when lighting-up operations are in progress. When the furnace is operating under stable conditions, the unit is withdrawn and monitoring is taken over by a photo-electric cell. Should the overall brightness of the furnace decrease, the photo-electric cell operates an alarm on the control panel; at the same time the periscope nose is automatically advanced into the furnace, and a picture obtained to show which burner has been extinguished.

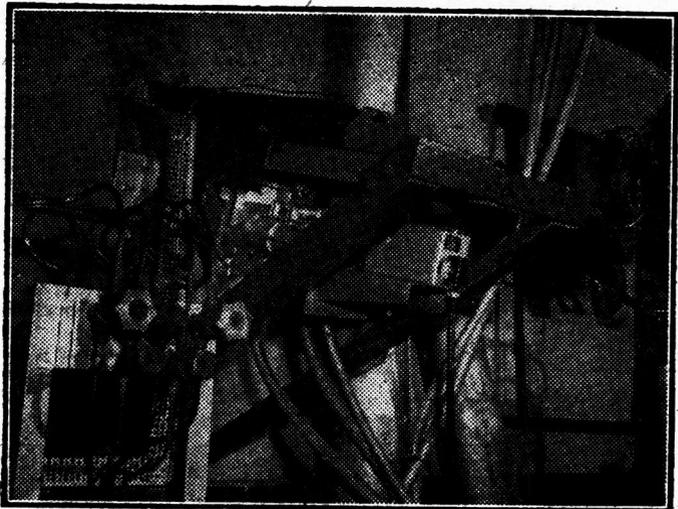The unit has been developed by Babcock and Wilcox Ltd., in conjunction with the British Iron and Steel Research Association, the Foster Instrument Co. Ltd., and Marconi's Wireless Telegraph Co. Ltd.



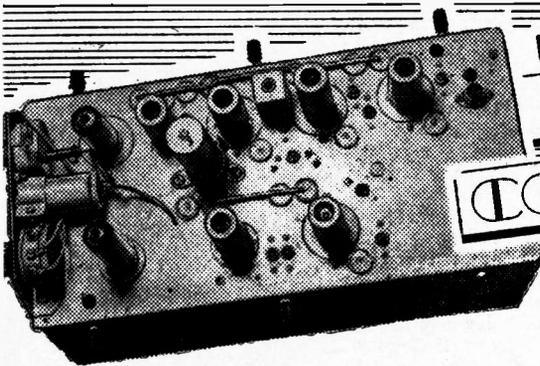The new Marconi camera installation at Barking Power Station.



IMPROVED BAND III CONVERSION

SOME PRACTICAL SUGGESTIONS

By G. T. Layton

WITH the commissioning of further ITA stations on Band III, the matter of converters for reception of this band is receiving the attention of amateurs in all districts, and from the articles in this journal and also the various pieces of commercial equipment available several methods of approaching this problem are possible. First with existing five-channel receivers such as the later commercial versions, the simplest addition is that of a superhet converter which changes the Band III signal into a Band I signal and feeds into the front end of the existing receiver.

This is not a particularly good method because there is always the danger of the signals being superimposed to a certain extent on each other from set pickup, and there are two oscillators that can drift, although with appropriate rejector coils the former trouble can be overcome. Alternatively with the same type of receiver a better method is to convert the Band III signal to the existing intermediate frequency of the receiver by removing the first valves and plugging into these valve bases. Although this is much improved it still suffers from the disadvantage that the I.F. has a rather low frequency as compared with the incoming frequency. If the existing receiver employs a T.R.F. circuit this form of converter using Band I frequency output will cause interference to others when the converter is in action.

The later type of commercial receiver with the 13-channel turret has a 38 Mc/s I.F. band, is a single superhet, and this particular I.F. band has been carefully chosen by the manufacturers because of its freedom from various troubles. Again this method has its disadvantages, and they are that it does not give a pre-set switchable receiver, in that on changing from one band to the other a fine trimmer on the oscillator always needs to be adjusted, and also the signal strength on each band will inevitably be different and thus the contrast and brilliance will need to be readjusted. In most cases the functioning of this trimmer is quite critical and can only be set right by an experienced

operator on test card C. It follows that in general due, to the difficulty of recording the true setting on all controls when changing from one band to the other, most of such receivers will not be set correctly by the average householder and only passable results will normally be obtained. Apart from this it must be remembered that these turret switches are operating a very high frequency and, as such, dirt and wear on these switches will in due course cause trouble, particularly when one considers that they may be switched to and fro several times in an evening. There are obvious reasons why this method is used commercially, but it does not follow that this is the best

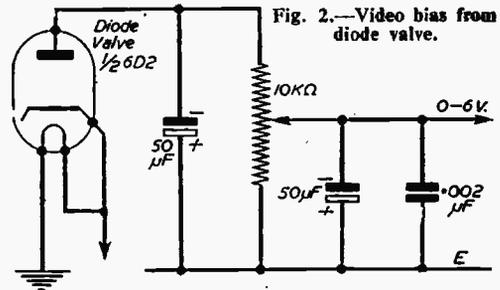


Fig. 2.—Video bias from diode valve.

method for an amateur to adopt. In the case of an amateur he is only interested at present in the reception of two stations, but they should be receivable in a perfectly adjusted state and the other members of the household should be able to change by the operation of one simple switch giving immediate results.

Preferable Arrangement

Given an existing set which is a T.R.F. of the type so popular amongst amateurs such as the Viewmaster, the obvious course is to convert the existing set to an I.F. strip on the 38 Mc/s band similar to the description in this journal some months ago. As a matter of interest there are one or two modifications incorporated in addition to those mentioned in this article. For example, the replacing of the coils as suggested makes a fairly extensive alteration and it is worth while to replace the EF50s by modern miniatures such as 6F12 as shown, 6CH6 as a video output valve and EL84 as a sound valve. At the same time provision of bias by a diode rectifying the heater current is a more convenient method of supplying the bias to the video output valve than the original Viewmaster (see Figs. 2 and 12). In inserting

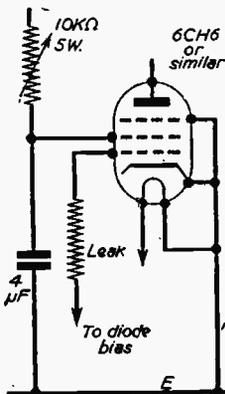


Fig. 12.—Video output with variable bias and variable screen volts.

the new modern miniature valves blanks need to be cut to fill the existing holes, with smaller holes cut for the miniature valves, and then a small anplate screen can be soldered in to make the necessary screen between anode and grid (which is the underside view of this chassis). Having completed the I.F. strip it is highly desirable to line this up as accurately as possible by feeding in signals in signals

perfectly as possible before proceeding to the next stage.

The Converters

On the market at the moment one can purchase simple sets of coils and chassis as supplied by Creton Radio, of Portsmouth, and one of the types is arranged for a cascode first valve followed by a frequency changer, the circuit being as conventionally used in most converters. The

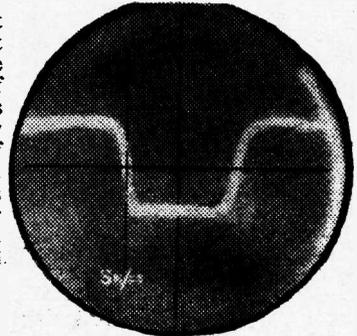


Fig. 5.—The overall response on Band III.

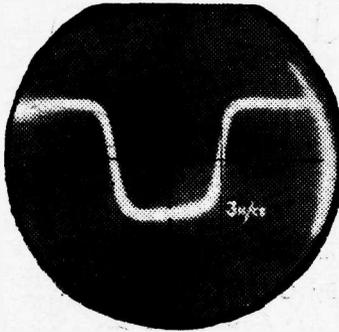


Fig. 3.—Shows the overall response of the I.F. unit.

around the 35-40 Mc/s band. The writer used a Televet instrument which very conveniently combines a signal generator and oscilloscope with which the output curve can be thrown up on the screen of the oscilloscope tube as in Fig. 3. In this figure the 3 Mc/s frequency has been marked on. The aligning can, however, be carried on with any good calibrated

signal generator. In this case signals of the various frequencies would need to be fed in and the A.C. voltmeter could be connected across the video load resistance so that the voltage could be read at each frequency and the characteristic curve could be drawn after this. It is, as previously mentioned, very desirable to be quite certain that the I.F. amplifier is functioning as near

The chassis is already punched and is quite small. The units are designed to be coupled in front of existing five-channel receivers for use when receiving Band III and to be disconnected when reverting to Band I. On building up one exactly as suggested to the circuit of Fig. 4, the signal could be fed into any existing receiver to check that this converter is

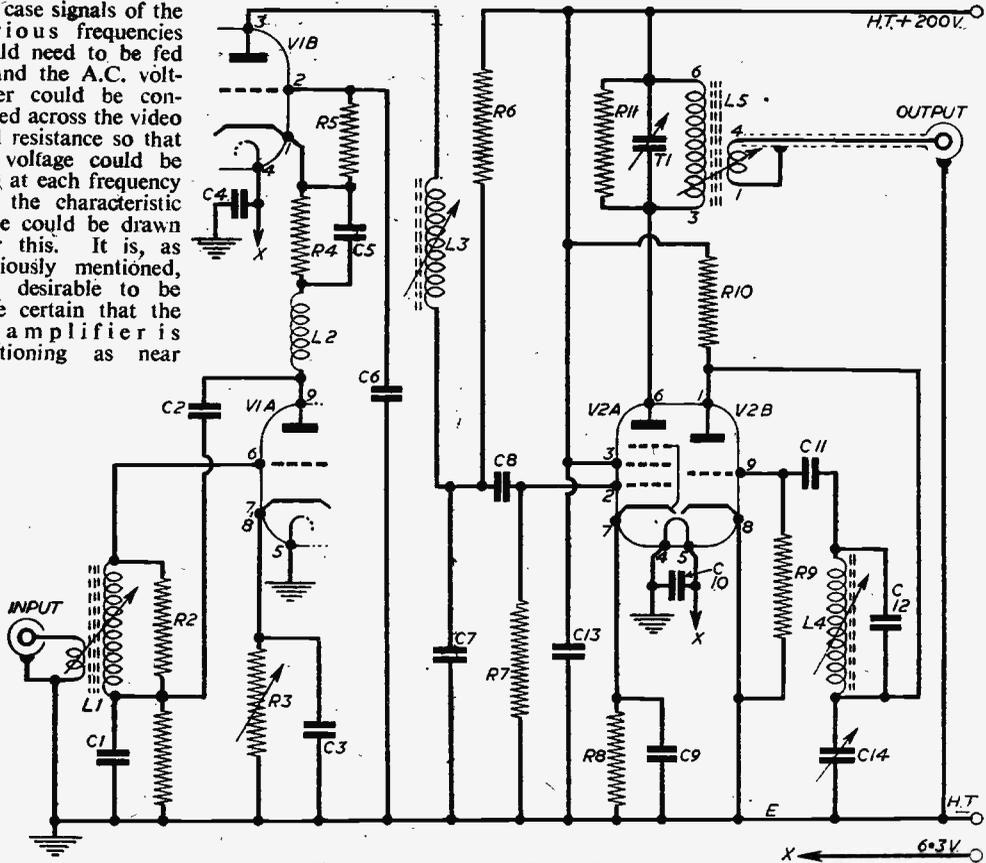


Fig. 4.—Circuit diagram of the Band III converter.

provided to sites on high ground at Kensington and Highgate which serve as radio reception points for the longer distance outside broadcasts. With the exception of the circuit to the London I.T.A. transmitter, all of the studio vision circuits have been provided on standard coaxial cables containing coaxial tubes of diameter $\frac{3}{8}$ in. The vision signals on the shorter circuits are transmitted directly in the video frequency spectrum 0.3 Mc/s; but, on the longer circuits, vestigial sideband carrier transmission is used, the vision signals being translated into the carrier spectrum 3-7 Mc/s. The circuit to the London transmitter also operates in this spectrum. The cable, however, is a low-loss type containing coaxial tubes of diameter 0.975 in. which enables the distance of approximately nine miles to be

spanned without the aid of intermediate amplifiers.

The opening of the Independent Television service on 17th February, in Birmingham, necessitated the provision of vision and sound circuits from Museum to the Post Office Television Control at Telephone House, Birmingham. This in turn was extended to the new transmitter at Lichfield, and to the master control of the two programme companies at the Astoria Cinema, Aston. Additional circuits in London were also provided for Associated British Cinemas (Television) Ltd.—week-end contractors for Birmingham. The London-Birmingham vision link consists of a two-way radio circuit operating at 900 Mc/s. Later this year, the link will be reinforced by the addition of a second vision circuit working in the north-going direction.

Experimental Closed Circuit TV System

SO far India has no television service, and perhaps the greatest attraction for many visitors to the recent Indian Industries Fair which concluded in New Delhi in December, 1955, was TV demonstrated by American, Dutch and Russian organisations. After witnessing radio and closed-circuit TV, also large-screen television for the first time, I decided to see what I could do to rig up quickly a simple low-cost experimental TV system using ex-radar equipment throughout. The results have been very promising.

A 5FP7 flying-spot C.R.T. in an AN/APS3 deflection and focus-coil housing (see front centre of illustration) scans a slide or film transparency, and the resulting light impulses are picked up by a 931A PM phototube as in wartime radar-video-mapping systems. A 6AC7 amplifier with cathode-coupled output followed by five stages of 6AC7 video amplification (3 Mc/s bandwidth) boosts the signals, which are then applied, via co-ax. cable, to the grid of a 5CP1 receiving C.R.T. unit (see respectively extreme left, and right rear of illustration). L.F. compensation is provided in the anode circuits of the amplifier, and there is an H.F. peaker in the third stage.

It was originally intended to use the 100 kc/s crystal-controlled step-down counter chain of a Loran indicator (AN/APN4) to trigger the line and

frame timebases, but satisfactory results were obtained from the 20 kc/s blocking oscillator for line-scan sync, and 50-cycle power-supply for frame sync, so several tubes were saved. A 2-valve 50-cycle frame timebase is incorporated in the Loran indicator (right-rear) and a similar 2-valve unit with modified R-C constants was built as a line timebase (see small box in centre of table). The TV raster can be adjusted for sequential scans up to 400 lines. The timebases are common to both transmitting and receiving C.R.T.s. The 5FP7 magnetic tube uses a 6SN7 (with both sections in parallel) as a frame-coil driver, and an 807 line-coil driver. In both cases low-power audio modulation-transformers were used for coupling to the deflection coils.

The power-supply portion of the Loran receiver (see illustration right front) is arranged to supply low, medium and high tension voltages to the whole equipment, with the exception of the video amplifier, which has an independent 50-cycle mains-operated power unit. As the 5FP7 C.R.T. requires an accelerating potential of 6 kv, a second Loran 3,000 volt high tension unit, in series, makes up the difference. This is housed in a safety wooden box (see rear centre of picture). An input power source of 115 volts 400 cycles is required for the Loran equipment so all unnecessary valves were removed from their sockets in order to conserve power, and to ensure that only a few minor wiring modifications are required in the Loran units.

Valve Complement


Power Supply: 1-5U4 for H.T. and 2-2X2 for EHT (also 2-2X2 for second EHT unit).

C.R.T. Indicator Unit: 1-6SN7 20 kc/s blocking oscillator, 1-6SJ7 frame sweep generator, 1-6SN7 frame sweep inverter and input sync, 1-6H6 C.R.T. D.C. restorer, 1-5CP1 C.R.T.

Line Timebase: 1-6SJ7 sweep generator, 1-6SN7 sweep inverter and input sync.

Flying-spot Scanner and Driver Unit: 1-6SN7 frame-scan driver, 1-807 line-scan driver, 1-5FP7 C.R.T.

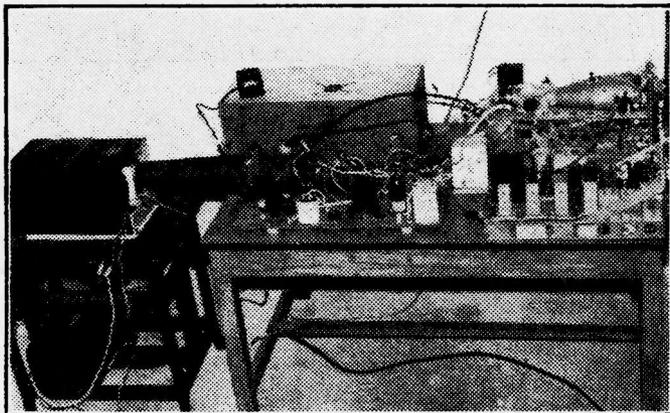Video Amplifier and Pick-up unit: 6-6AC7 TV pentodes, 1-931A photomultiplier.—C. M. SWEET.



The experimental layout referred to by Mr. Sweet.

Simplified Fault Finding

IMPROVISED METHODS FOR THE HOME CONSTRUCTOR

By B. L. Morley

(Continued from page 535 July Issue)

AN interesting point to note is that if there is a serious discrepancy in the components so that the frequency is above 50 c.p.s. then this will be revealed by the pitch of the tone produced.

The frame oscillation can be traced through the amplifier circuit to the scan coils or the deflector plates themselves but the precaution of disconnecting the EHT should always be taken.

As with the line circuit it is advisable to disconnect the aerial or to take out the sync separator valve.

Our simple test instrument can also be used for checking infiltration of line oscillations into the frame circuit by simply taking out the frame oscillator valve and listening for the line whistle. Similarly a check can be made for infiltration of the frame oscillations into the line circuit by taking out the line valve.

Note that in electromagnetic circuits some induction takes place between the two sets of scan coils and it is possible to detect infiltration in the outputs to a certain extent.

Sync Faults

A rough check on the operation of the sync circuits can be made and the sync pulse examined.

A typical sync separator as used in many receivers is shown in Fig. 8. This particular example is again taken from the PRACTICAL TELEVISION Simplex television.

Using the test instrument as before with the test lead on point "A" it should be possible to hear the composite video signal; this will indicate that the signals are actually reaching the sync valve.

The next step is to take out the line oscillator valve and the frame oscillator valve, it should then be possible to hear the line sync pulses at "B" and at "C," and the frame pulses at "D." The point "E" occurs before the integrator circuit and will not give a true representation of the frame sync pulses.

Note that the oscillator valves *must* be removed or the oscillations produced by them will mask the sounds produced by the sync pulses.

Note also that because of the small value of the condenser "C" the line sync pulses will sound rather on the faint side. In this case it is often helpful to connect the testing point to the pick-up sockets of a broadcast receiver.

Sound Receiver Faults

So far as the audio side of the sound receiver is concerned, normal audio technique can be employed. The earphone tester will, however, prove quite useful in enabling the sound to be traced.

The usual form of supplying sound is by tapping the R.F. or I.F. from the vision stages at some point, providing a further stage or stages of R.F. or I.F. amplification followed by detector, noise limiter, first sound amplifier and finally sound output.

With the phones tester, tests can be made from the loudspeaker back to the detector. A simple and rapid check of the audio stages is to tap the grid of the first audio valve with the finger and a "plop"

or howl should be heard in the loudspeaker if the stages are functioning.

It is a little more difficult to test the I.F. or R.F. stages, but a rough check can be made by connecting the phones across the L/S output and tapping the detector input with the blade of a screwdriver. A distinct click should be heard if all is well.

The screwdriver blade can be used to make a rough check of the R.F./I.F. stages working from the grid of the valve nearest to the detector to the grid of the valve nearest the aerial.

Finally a short-circuit tapped across the aerial should be heard in the phones.

As each stage amplifies then the clicks should become louder as the aerial circuit is approached. If, for example, a click is heard at the last I.F. or R.F. stage and a fainter click is received from the next stage nearest the aerial then weak amplification in the intervening stage is suspected.

The "click" test will prove that the circuit is "alive" and through, but no more; it will not prove that the coils are tuned correctly, for example, but nevertheless will provide a good method of making a check when the receiver seems dead.

Vision Receiver

The vision receiver can be roughly checked in a similar manner to the sound receiver. The phones can be connected between the anode of the video valve and chassis (including the condenser in the circuit to act as a D.C. block). A more sensitive arrangement is to insert the phones without the condenser directly between the anode of the video valve and the load resistor.

The video valve can be tested by tapping the grid and a click should be received if all is well. The test can then proceed by tapping the input of the

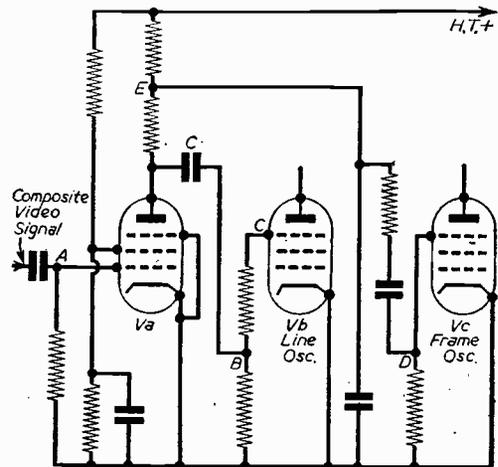


Fig. 8.—A typical sync circuit.

detector valve, then the grid of the last R.F. or I.F. valve and so on up to the aerial circuit.

In the case of a superhet tuned to a suitable intermediate frequency, such as 13 Mc/s, a useful check is to attach a length of wire to the grid of the first I.F. valve. If this is done, stations operating at the same frequency as the I.F. tuning should be heard in the phones.

If the EHT is disconnected the video signal can be traced right through to the grid or cathode of the C.R.T. and the circuit proved right through.

An important point to note is that the phones should be disconnected when attempting to receive the picture on the tube. At the worst condition the signal will be severely attenuated so far as the tube is concerned, so that it will not produce a picture; at the best the resultant picture will be of very poor quality and difficult to identify.

Checking the Video Signal

As we have indicated in the foregoing section, it is possible to check the video signal right through to the C.R.T. It is quite easy to identify as it sounds like a rather rough mains hum mixed up with motor-boating and which varies in pitch, up and down.

There are two points which should be observed about this signal. First, it sounds similar to the frame oscillator and can sometimes be mistaken for it. This is especially true where, due to lay-out or stray wiring, etc., induction exists between the receiving circuits and the timebases. If the frame oscillations get into the sound section it makes a noise like vision on sound which cannot be tuned out; if it gets into the vision stages it may be mistaken for the vision signal.

A second important point is that it is possible to receive the sound signal through the vision stages. This is often a useful check that the stages are working, but confusion is liable to arise when both signals, sound and vision, are received together.

This is particularly noticeable with wide-band straight receivers, especially where a VCR97 tube is employed. The VCR97 is much less sensitive than commercial magnetic tubes and quite a large volume of sound signal is allowable before the picture becomes affected. The main point is to keep the sound as low as possible by correct adjustment of rejector coils and it should be quite practicable to keep it low enough so as not to trip the sync or to produce bands on the screen.

Other Simple Checks

Our simple little tester in Fig. 1 can be used to make a rough check of the aerial system. If a folded dipole is used then a test across the ends will show that the cable is through to the aerial. The evidence of the tester is not wholly conclusive, however, for a short-circuit in the junction box, etc., would also light the lamp.

If the aerial is not one of the folded dipole types then a check with the tester across the cable ends would show if a short-circuit existed; it would not, however, show if one of the leads was disconnected.

The tester can be used to check the continuity of tuning coils and for short circuits to chassis, but it will not test the continuity of anything which has a resistance greater than a few ohms.

A method which can be used to check such items is to employ a good condenser of about 4 μ F or

more. If the article to be tested (say a loudspeaker transformer) is connected in series with the condenser, H.T. and chassis, then the condenser will charge up. If the condenser is disconnected and then short circuited a spark should be obtained if the item tested was continuous.

Fig. 9 shows the method to be employed.

A useful method of tuning in the signal in a weak area where it is thought that the coils may possibly be wrongly wound is to use the audio side of the sound section of the televisior.

All that is necessary is to disconnect the output of the sound detector from the audio input and to connect, in its place, the output of the video detector. A useful increase in amplification is obtained which will enable a weak signal to be detected.

In some cases, where picking up of the signal proves very difficult it is helpful to make use of the sound I.F. or R.F. stages. In this case the output from the last vision R.F. or I.F. valve is taken to the input of the first sound I.F. or R.F. stage, the existing coupling between the two stages being disconnected.

This method has some danger in it as the circuits are liable to break into oscillation. It can, however, prove very useful on many occasions.

One of the difficult things to check without instruments is the functioning of an oscillator. It is very useful to know if a valve is oscillating or not in the case of a superhet and it is possible, in some cases, to employ a simple bulb tester.

The basic tester is shown in Fig. 10 and is very simple to construct. A two-turn coil is made which should be of sufficient diameter to go over the oscillator coil without actually touching it. Ideally a $\frac{1}{2}$ in. gap should be between the two coils (the oscillator coil and the testing coil) all round.


The turns of the coil should be separated by about $\frac{1}{4}$ in. The wire should be of heavy gauge (preferably of about 10 s.w.g.) and should be insulated.

The two ends of the coil are taken directly to a low consumption bulb, a rear-lamp cycle bulb of about 0.04 amp. rating, or a peanut bulb should do the trick.

If the coil of the tester is closely coupled to an oscillating circuit the bulb will light up. If the oscillations are very weak the bulb will only light dimly or will not light at all.

Confirmation that the bulb is lighting due to the oscillator functioning can be verified easily by temporarily short-circuiting the oscillator grid to chassis, whereupon the bulb should go out.

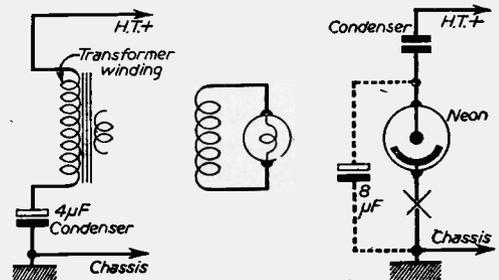Leaky condensers are one of the bugbears of the constructor who employs ex-Govt. parts and only careful testing will show the good ones.



Figs. 9, 10 and 11.—Testing for continuity; an oscillator tester, and (right) a condenser test.



FOR VALVES—GUARANTEED NEW AND BOXED

0Z4	8/6	6F14	12/0
1A3	6/-	6F15	14/-
1A5GT	8/6	6G6G	4/-
1C2	10/0	6H6	3/6
1A7GT	11/6	6J5G/GT 5/-	
1C5GT	9/6	6J5M	6/6
1H5GT	10/6	6J6	7/6
1U3	8/6	6J7G	8/6
1LD5	6/0	6K6GT 7/-	
1N5	10/6	6K7G/GT	
1R5	8/6		
1R5	7/6	6K7	6/0
1T4	7/6	6K7G	6/0
1U3	8/6	6K7GT	6/0
2X2	4/6	6K80	8/0
3A4	7/6	6K8GT	9/6
3Q4	9/6	6L6G	9/6
3Q5	10/-	6L7M	7/6
3R4	8/6	6N7	7/6
3V4	9/6	6E7	8/6
4D1	8/6	6S47GT 8/-	
J2	8/6	6S7	7/6
5R4Gy	8/6	6S7	7/6
5U4G	8/6	6S7GT 8/-	
5Y3GT	8/6	6S7	7/6
5Z4G	9/6	6S7	7/6
6A7	11/6	6S7	7/6
6A8GT	10/6	6S7	7/6
6AC7	6/6	6S7	7/6
6A95	6/6	6U4GT 15/-	
6AK5	6/6	6U5G	8/6
6AK7	8/6	6U7G	8/6
6AL5	7/-	6V6G/GT7/6	
6AM5	5/6	6X4	8/6
6AM6	7/6	6X5G/GT	
6AQ5	9/6		
6AT6	8/6	7B6	8/6
6B4	5/6	7B7	9/6
6B8	4/6	7C5	8/6
6BA6	8/6	7C6	9/6
6BR6	8/6	7Q7	8/6
6BW6	8/6	7E7	8/6
6C4	7/6	7S7	9/6
6CSGT	7/6	7Y4	8/6
6C6	6/6	75	10/6
6C9	10/6	77	8/6
6CF6	8/6	80	8/6
6D6	7/6	807	8/6
6F1	13/6	8D2	2/9
6F6G	7/6	9D2	3/9
6P6M	8/6	9001	5/6
6P11	13/-	9003	5/6
6P13	14/-	9004	5/6

9006	6/-	ECC31	3/6
954	2/-	ECC40	14/-
955	4/0	ECC84	14/6
956	3/6	ECC85	12/6
10C1	12/6	ECCF82	15/-
10C2	12/6	ECCF85	13/6
10F1	12/6	ECCF42	11/-
10F9	12/6	ECL30	10/6
10P13	11/6	EF37A	9/-
12A6	6/0	EF22	8/6
12A7	6/0	EF41	11/6
12A7T	9/6	EF42	13/6
12A7U	9/6	EF80	11/6
12A7K	10/-	EF86	13/6
12BA6	9/6	EF89	12/6
12BB6	10/-	EL2	12/6
12H6	5/-	EL35	7/6
12J5	6/6	EL41	11/6
12K7	9/6	EL54	12/6
12K7	9/6	EM31	11/6
12K8	11/-	EM34	11/6
12L6	9/6	EM80	11/6
12M7	6/6	EY31	12/6
12M7	7/6	EY86	14/6
12M7	8/6	EZ40	10/-
12M7	9/6	EZ41	10/6
12M7	10/6	EZ50	10/6
12M7	11/6	EZ50	10/6
12M7	12/6	EZ50	10/6
12M7	100/6	EZ50	10/6

A NEW ALPHA KIT FOR YOU TO BUILD

Modern Portable. A.C./D.C. Mains/Battery Receiver. Four valves (latest types), 2 Waveband Superhet. In an attractive Lizard Grey Case, size 8 1/2 in. x 8 1/2 in. x 4 1/2 in. Full Kit of Parts down to last nut and bolt.

£9.9.0

Or if you prefer you can build the battery version first for £7.17.6 and add the mains components later.

Post extra on Kit, 2/6. Full Circuit Diagram, Shopping List, and Point-to-Point Wiring Diagram, 3/-.



Aerialite Band III Aerials, 5-element, 702XU. An array with Universal lin-2in. masthead bracket, suitable Channels 8, 9, and 10. Price 41/- carriage 4/6.
Aerialite Coaxial Outlet Boxes at 4/6 each.
Aerialite Coaxial Plugs and Sockets at 1/1 each.

TRANSFORMER MTS
Small mains transformer suitable for T.V. converters, etc. Primary 230 v., Secondary 250 v., 40 M/A and 6.3 v. 1.5 amp. Price 15/6 each, postage 1/6.
Transformers T1154N, 25/- each; T1154H, 37/- each; T1154, in rough condition, 15/- each. Carriage and postage on these three is 12/6.
Meters 0-100 M/A, panel mounting, 7/6 each; 0-5 amp. R.F. panel mounting, 7/6 each.

MAINS TRANSFORMERS
3-way mounting type -

MT1
Primary: 200-220-240 v.
Secondaries: 250-0-250 v., 80 M/A 0-6.3 v. 4 amp., 0.4 v. 2 amp. Both tapped at 4 v. each 18/6

MT2
Primary: 200-220-240 v.
Secondaries: 350-0-350 v. 80 M/A 0-6.3 v. 4 amp., 0.5 v. 2 amp. Both tapped at 4 v. each 18/6

MT3
Primary: 200-220-240 v.
Secondary: 30 v. 2 amps. Taps at 3 v., 4 v., 6 v., 8 v., 9 v., 10 v., 15 v., 18 v., 20 v., 24 v., each 18/6

2/- Post and Packing on above transformers.

3-VALVE T.R.F. KIT

- Easy to Build.
- Valves 6J7, 6K7, 6V6G1 plus metal rectifier.
- Walnut cabinet.

Full instructions, point to point wiring diagram. Circuit diagram, and full shopping list 1/-. All components may be purchased separately.

£5.10.0

Post and Packing 3/-.

When ordering please quote "DEPT. P.T."



LOUDSPEAKER CABINETS
This attractive walnut finished cabinet is available for 8in. or 8in. speaker units. Metal speaker fret, complete with back and rubber feet.

8in. type:
Measures 8 1/2 in. x 8 1/2 in. x 4 1/2 in. at base. Price 20/6 each.

8in. type:
Measures 10 1/2 in. x 10 1/2 in. x 5in. at base. Price 20/6 each.

8in. type:
Measures 6 1/2 in. x 4 1/2 in. x 7 1/2 in., 16/6.

LOUDSPEAKER UNITS, ETC.

3 1/2 in. Types Each 17/6
8 in. Types by Elac, Lectrona, Celestion, etc. 17/6
6 1/2 in. Types by Goodmans, Rola, R. & A. 18/6
8 in. Types by Goodmans, Plessey, L. & A. 19/6
10 in. Types by R. & A., Celestion, etc. 25/6
6 1/2 in. Water Speaker by Traxxon, suitable for Car Radio, etc. ... 20/-
12 in. Plessey Lightweight ... 35/-
Elliptical Speakers, Goodmans 4 in. x 7 in. 19/6
All above are P.M. Speakers. Standard 2-4 ohms. Speech Coil.

HEATER TRANSFORMERS
230v. Input 2 volt 5 amp., each 5/-
230v. Input 2 volt 3.0 amp., each 8/3
230v. Input 4 volt 1.5 amp., each 5/6
230v. Input 4 volt 2.0 amp., each 10/6
230v. Input 5 volt 2.0 amp., each 10/6
230v. Input 6.3 volt, 5 amp., each 9/6
230v. Input 6.4 volt 1.5 amp., each 6/6
230v. Input 6.3 volt 3.0 amp., each 9/6
230v. Input 12 volt, 7.5 amp., ea. 5/6

ALPHA RADIO SUPPLY CO.

5/6 VINCES CHAMBERS VICTORIA SQUARE LEEDS 1.

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated. Minimum C.O.D. fee and postage 2/3.

MAIL ORDER ONLY.

Unfailingly fresh

Tobacco at its best. Player's Medium Navy Cut is once again supplied in the familiar pocket tin, vacuum sealed, which means that absolute freshness is retained and enjoyment assured whenever you buy it.

2 oz. tin 9/7d.

PLAYER'S MEDIUM NAVY CUT TOBACCO



To open, simply
remove small
rubber seal.

'The choice for a lifetime'

[NCT 94M]

BAND III CONVERTER.

Coil kit by TELETRON, with circuit and wiring details, etc. For use with TRF or Superhet TV Receivers. **ONLY 15/-**. Cascade coil kit 17/6. Drilled chassis 3/9, or slightly larger to hold power pack components, 6/- (postage on either 6d.). Instruction leaflet only, 6d.

INDICATOR UNIT TYPE 6.—Contains VCR 97 tube with mu-metal screen, 4 valves EF50 and 2 of EB34, valveholders, CRT holder, condensers, resistors, etc. **NEW CONDITION. ONLY 39/6** (carriage, etc., 7/6).

AMPLIFIER TYPE 223A or 202A.—As described in July, 1955, issue of *Practical Television*, for making a TV CONVERTER. Complete with 2 valves EF50. **ONLY 10/-** (post, etc., 2/-).

PYE 45 MC/S.I.F. STRIPS.—Ready-made for London Vision Channel. Complete with 6 valves EF50 and 1 of EA50, and details of very slight mods. required. **BRAND NEW. ONLY 49/6** (post, etc., 2/6).

I.F. STRIP 194.—Another easily modified strip for TV. Complete with 6 valves SP61, 1 of EA50, and 1 of EF36; also mod. data. **ONLY 29/6** (post, etc., 2/6).

RECEIVER UNIT 159.—Contains 4 valves, 1 each EF50, EA50, SP61, RL37 and 21 v. selector switch. **ONLY 7/6** (post, etc., 2/-).

R.F. UNITS TYPE 26.—Complete with 2 valves, EF54 and 1 of EC52, this is the variable tuning unit covering 65-50 Mc/s (5-6 metres). **BRAND NEW IN MAKER'S CARTONS. ONLY 27/6.**

POTENTIAL VOLTMETERS.—Read 0-15 and 0-200 v. A.C. or D.C. **BRAND NEW. ONLY 13/6.**

COMMAND RECEIVERS.—Huge purchase from the Air Ministry. These famous compact American receivers which can be used for a variety of purposes are offered at ridiculously low prices while stocks last. Complete with six metal tube valves, one each of 12K8, 12SR7, 12A6 and 3 of 12SJ7, in aluminium case, size 11in. x 5 1/2in. x 5in. Used, but in good condition. Choice of models, BC 455 (6-9 Mc/s), 25/-, BC 454 (3-6 Mc/s), 27/6, BC 453 (190-550 kc/s), 59/6, and a few of the 1.5-3 Mc/s model, 65/-. (Postage on all models 3/-). Circuits supplied.

COLLINS' TRANSMITTERS.—The renowned American TCS models covering 1.5-12 Mc/s in 3 bands. Complete with 7 valves, employing 2 of 1625 in P.A. stage, one of 1625 in each of buffer and modulator stages, and 3 of 12A6 in oscillator stage. Provision for V.F.O. or crystal control for 4 Xtal positions. Incorporates plate and aerial current meters. In Brand New Condition. **ONLY £12-10-0** (Carriage, etc., 15/-).

COLLINS' RECEIVERS.—Matches the above transmitter and is exactly the same size, 11in. x 13in. x 11in. Has same coverage, and is complete with 7 valves, 1 each of 12SA7, and 12SQ7, 2 of 12A6, and 3 of 12SK7. Also has provision for Xtal control. A really terrific receiver for the serious operator. In Brand New Condition. **ONLY £8-10-0.** (Carriage, etc., 15/-). **OR THE TRANSMITTER AND THE RECEIVER TOGETHER. £20-0-0.** (Plus Carriage, as above).

L.T. HEAVY DUTY TRANSFORMER.

—Ex Admiralty. Has 3 separate windings of 5v.-0.5v. at 5 amps, and by using combinations will give various voltages at high current. **BRAND NEW. ONLY 29/6** (post, etc., 2/8).

MODEL MAKERS MOTOR.—Reversible poles. Only 2in. long and 1 1/2in. diameter, with 1in. long spindle. Will operate on 4, 6, 12 or 24 volts D.C. **ONLY 10/6** (post, etc., 1/-).

TRANSFORMERS.—Manufactured to our specifications and fully guaranteed. Normal Primaries. 425-0-425 v. 200 ma. 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., **ONLY 65/-**. 350 v.-0-350 v. 100 ma., 6.3 v. 5 a., 6.3 v. 3 a., 5 v. 3 a., **ONLY 37/6**. 250 v.-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., **ONLY 37/6**. 350 v.-0-350 v., 150 ma., 6.3 v. 5 a., 5 v. 3 a., **ONLY 37/6**. 250-0-250 v. 60 ma., 6.3 v. 3 a., 5 v. 2 a., **ONLY 21/-**. The above are full shrouded, upright mounting, 5.5 kv. E.H.T. with 2 windings of 2 v. 1 a., **ONLY 79/6**; 7 kv. E.H.T. with 4 v. 1 a., **ONLY 89/6**. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.


E.H.T. TRANSFORMER FOR VCR57 TUBE.—2,500 v., 5 ma., 2-0-2 v. 1.1 a. 2-C-2 v. 2 a., 42/6 (postage 2/-).

SPEAKERS.—P.M. 6 1/2in. less trans., 19/6; 8in. less trans., 16/6; 10in. with trans., 27/6 (post 2/-).

CHOKES.—10H 60 mA., 4/-; 5H 200 mA., 7/6 (post 1/-).

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station) 5 mins. by bus from King's Cross. Cash with order, please, and print name and address clearly. Include postage and carriage on all items.

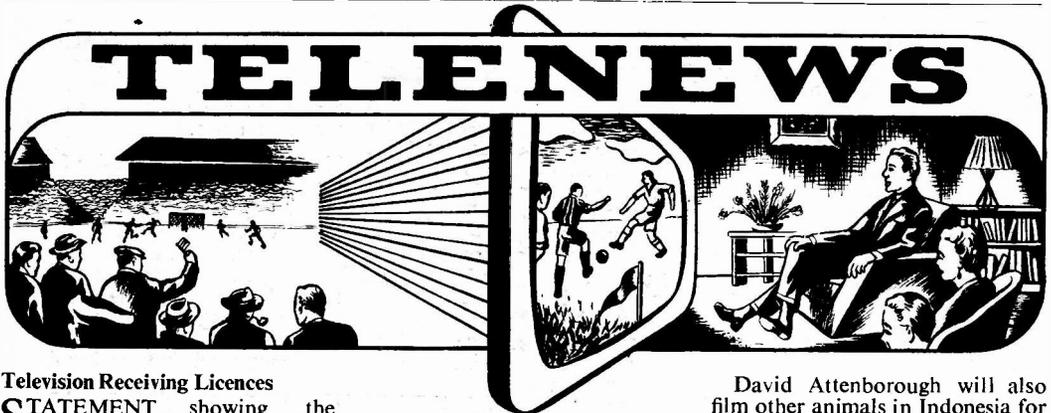U.E.I. CORPN. THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.1
(Phone TERminus 7937.)



Television Receiving Licences

STATEMENT showing the approximate number of Television Receiving Licences in force at the end of May, 1956, in respect of receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Totals
London Postal	1,315,921
Home Counties	671,431
Midland	1,011,743
North Eastern	893,346
North Western	845,413
South Western	393,369
Wales and Border Counties	326,999
Total England and Wales	5,458,222
Scotland	360,537
Northern Ireland	44,714
Grand Total	5,863,473

New BBC Station for Cumberland

THE BBC announces that a site has been chosen for the projected medium power television station in Cumberland at Sandale, 1,200ft. above sea level and some 14 miles south-west of Carlisle.

The new station is expected to be ready for service before the end of 1957 ; it will bring the BBC's television service to the greater part of Cumberland and Westmorland as well as to the coastal areas of south-west Scotland.

The site will also be suitable for V.H.F. (F.M.) transmissions of the Home, Light and Third programmes when it becomes possible to extend this system to this part of the country.

Radio Show Catalogue Features

A COLOURED plate of H.M. The Queen—a reproduction of the Annigoni portrait which caused so much interest in last year's Royal Academy exhibition—is to be included, by special permission, in the catalogue of the Radio Show, August 22 to September 1, 1956. The Queen, as

has already been announced, is again patron of the show.

A sale of 50,000 is expected and applications for advertising space, more than half of which is already booked, are asked for by the R.I.C. immediately.

Another Zoo Quest

ON Thursday, May 3, David Attenborough left London Airport for Djakarta via Singapore on the first state of another Zoo Quest. With cameraman Charles Lagus he will spend three months in Indonesia, visiting Sumatra, Bali and other parts of the islands. His main objective is to find and film the Komodo Dragon for the London Zoo.


David Attenborough will also film other animals in Indonesia for his third " Zoo Quest " which will consist of six programmes beginning probably in October.

Hungarian TV Plans

OPENING of a second television station in Hungary is scheduled in the Second Five Year Plan, details of which are now being discussed prior to submission to Parliament in a few weeks' time.

The new station will be at the industrial city of Miskolc, North-east Hungary. A five kilowatt transmitter is to open there in 1958.

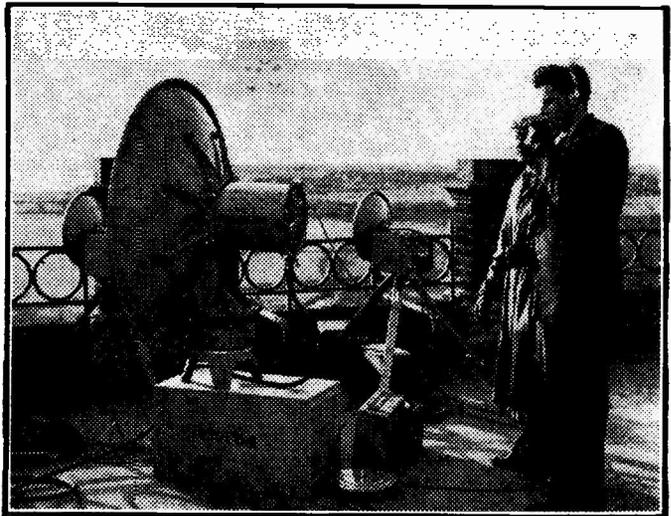The plan proposals add : " We must ensure connecting up with the international television network and introduction of colour television must be prepared."



RUSSIA BUYS BRITISH TV EQUIPMENT

The above picture shows Marconi centimetric link equipment undergoing field trials before being shipped to Russia. This apparatus represents part of a large quantity of television equipment which Marconi's are supplying to the U.S.S.R. Amongst the main items in this order are included two three-camera television outside broadcast vehicles, two mobile petrol-electric trailer power units and a comprehensive supply of spares.

The country's first TV station is already operating from Budapest on low power, but next year a 30 kw transmitter is being installed.

Domestic manufacture of TV receivers is now just getting under way. It is planned to turn out 110,000 in the next five years.

Channel Island TV

AS we go to Press it is announced that the first television programme from the Channel Islands will be transmitted in July. For the transmission the BBC will move 10 tons of equipment to the islands to set up a temporary link. The broadcasts will be fed into the Eurovision network at Cherbourg, thence to London.

Production of TV Screens

PRODUCTION of television filter screens at a Birmingham factory has now reached the 1½ million mark.

An official of the Triplex Safety Glass Co., Ltd., said that production started four years ago, since when the screens have been leaving the production line at a steady rate, on occasions reaching a peak of 14,000 a week.

I.T.A. Preferred

IN homes receiving both BBC television and I.T.A., it is estimated the commercial programmes attract "more than twice as many viewers as those of the BBC." This is claimed by the Television Audience Measurement organisation which recently issued a report on the first six months of I.T.A.

Colour Television in the United States

THE Director of Technical Services of the BBC, Sir Harold Bishop, spoke about colour television in the United States at a luncheon on his return from a visit to the United States.

He said that colour television had made a good start there, but he thought progress would be slow until the price of sets drops. The system which they had adopted—the National Television Standards

Committee system—was capable of excellent results, and intensive work on the development of television sets was continuing.

So far only about 25,000 colour television sets had been sold at a price of about 800 dollars (£300 approximately) each. The service on these sets averaged about 100 dollars (£35) a year. The R.C.A. company was now making about 30,000 sets a month at a cost of 700 dollars each. Sir Harold had been told that as manufacture developed it was hoped that the price would come down to about double the cost of an ordinary black and white television set.

Automation at the Opera!

WHEN the 1956 opera season opened at Glyndebourne in June, television was there for the first time in this country as an integral part of the production facilities.

A miniature Pye television camera, of the sort used in many parts of the country, was installed in the stage of the Glyndebourne Opera House beside the prompter's box to enable the chorus-master in the wings to follow the conductor of the orchestra.

In previous years, in opera houses all over the world, chorus masters have had to peer through holes in curtains or scenery in order to cue the chorus at the right moments. Now that television has made its debut, things are no longer left to chance. The chorus is grouped round a monitor in the wings and the chorus master has the conductor in full view.


Fall in TV Sales

THE Radio and Television Retailers' Association report that sales of TV sets in May averaged 5.38 per shop as compared with 5.74 a year ago.

New BBC Television Tuning Signal

THE BBC introduced, on Saturday, June 16th, a new television tuning signal to replace the old one. The new tuning signal retains all the essential features of the old one but the presentation and general appearance have been improved.

The purpose of the tuning signal

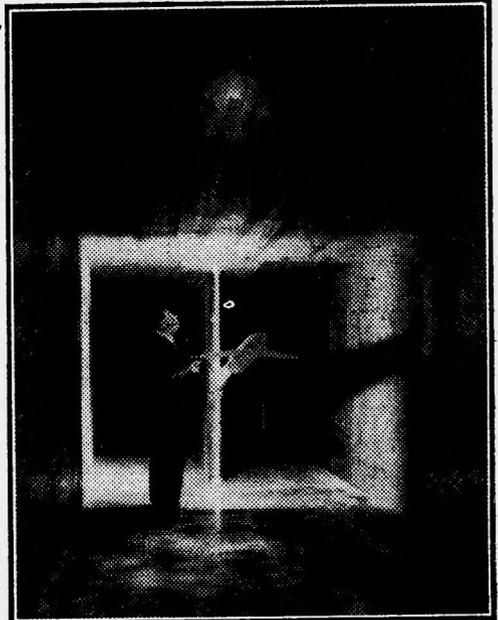

A technician seen checking the lights and position of the industrial television camera set up above a model to be tested inside the trans-sonic wind tunnel recently inaugurated by H.R.H. The Duke of Edinburgh at the Aircraft Research Association's establishment at Bedford.


is to assist viewers in making any necessary minor adjustments to their sets immediately before the start of the programme. It is not to be confused with Test Card "C" which is radiated at regular times for the benefit of the radio industry.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.


Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

HIGH VOLTAGE TESTER

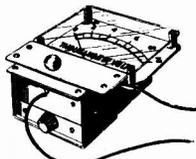

An instrument that will measure voltages up to 10,000 but which draws no current from the source, will probably be a valuable addition to your workshop equipment. It can be made entirely from odds and ends. Booklet giving full instructions, plans, etc., 2/6 post free.

14 in. T.V. CABINET

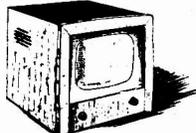

14in. T.V. cabinet of the latest styling made for one of our most famous firms—beautifully veneered and polished—limited quantity—19/6 each. Carriage and packing 3/6 extra.

F.M. TUNER




This tuner is based upon the very successful circuit published by Data Publications. We have made up models at all branches and will gladly demonstrate. Stability is extremely good and making and aligning most simple. Cost of all parts including valves, prepared metal chassis, wound coils and stove enamelled scale, slow-motion drive, pointer, tuning knob, in fact everything needed is £6/12/6. Data is included free with the parts or is available separately, price 2/-. Extra for fringe area model, 20/-.

CRT VCRI39A

New, unused and guaranteed, 32/6, plus 2/6 post.

Band III Aerial Kit

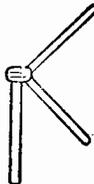


"The Folded V" was described in the July 1955 number of this magazine. We tried this and found it to be most efficient. The kit comprises alloy elements and connectors, neat plastic centre piece and saddle for mounting. 8/6, post 1/6.

BAND III PRE-AMP



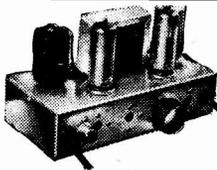In difficult areas it will be necessary to increase the signal level and this is the ideal unit for this purpose. It is A.C. mains operated and is fitted with input and output coils, plugs. Price £4, post and packing 3/6.



"The ESTRONIC" Band III Converter

To-day's best value in Band III converters suitable for your T.V. or money refunded. Complete ready to operate, 59/6 non mains or 85/- mains, post and insurance, 3/6.

RECORD PLAYER £4-10-0



3-Speed Gramophone Motor

Latest rim drive 3-speed motor with metal turntable and rubber mat. Small mod. makes speed

easily variable for special effects and dance work. Hi-Fi Pick-Up Using famous Cosmocord Hi-G turn-over crystal. Separate sapphire for each speed. Neat bakelite case with pressure adjustment. **Special Snip Offer This Month** The two units as illustrated £4 10/- or made up on board as illustrated £5 10/- plus post and insurance.


THE "CRISPIAN" BATTERY PORTABLE



A 4-valve truly portable battery set with very many good features as follows: Ferrite rod aerials. Low consumption valves. Superhet circuit with A.V.C. Ready built and aligned chassis if required. Beautiful two-tone cabinet covered with I.C.I. Rexhite and Tygan. Guaranteed results on long and medium waves anywhere.

All parts, including speaker and cabinet, are available separately or if all ordered together the price is £7 15 0, post & insurance 3/6, complete ready built chassis 30/- extra. Instruction booklet free with parts or available separately, price 1/6.

BAND III AERIALS

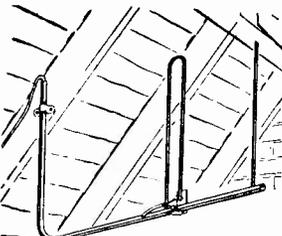


THE INDOOR


This is a 1 wave, 3 element array. Of all alloy construction, the aerial is completely assembled and ready for instant mounting in loft, bedroom cupboard, window frame, etc. Price 12/6, plus 2/6.

- 3 element array with swan-neck mast with "U" bolt clamp for fitting to existing masts from 1 1/2 in. to 2 in. dia. 41/6
- 3 element array with cranked mast and wall mounting bracket ... 42/6
- 3 element array with cranked mast and chimney lashing equipment ... 65/-
- 5 element array with swan-neck mast and "U" bolt clamp for fitting existing mast from 1 1/2 in. to 2 in. dia. 52/6
- 5 element array with cranked mast and chimney lashing equipment ... 67/-
- 8 element array with swan-neck mast and "U" bolt clamp for fitting to 1 1/2 in. to 2 in. dia. mast ... 69/-

The Eipreq E.H.T. Generator

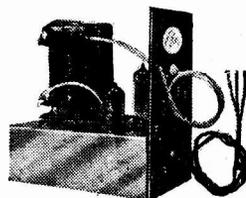

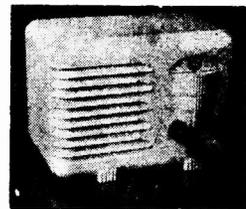This unit contains three BVA valves. Output from 6 kV to 9 kV rectified with normal H.T. rail input but somewhat higher outputs can be obtained with higher H.T. supply. Dimensions are 6 1/2 x 4 1/2 x 7 in. Price 69/6, post packing, etc., 5/-.



MAINS-MINI

Uses high-efficiency coils, covers long and medium wavebands and fits into the neat white or brown bakelite cabinet—limited quantity only. All the parts, including cabinet valves, in fact, everything. £4 10 0, plus 3/6 post. Constructional data free with the parts, or available separately 1/6.

MISCELLANEOUS BARGAINS

Valves.—Most types available, many at really bargain prices. Coaxial Cable.—Cellular polythene—super low loss for Band III—11d. per yard. 200 m Chokes, 8/6. Mu-Metal Screens for VCR97, etc., 8/6 per pair. Resistors.—1 and 1/2 watt, 5d.; 1 watt, 6d. American Microphone Inserts—4/6 each. Condensers.—3/- per dozen. 1,000 pf. Ceramic Condensers.—6/- per dozen. Extra High Voltage Testers.—001 mfd. 28,000 volt test (20,000 volt) working at 8/6 each. Silver Mica Condenser.—50 assorted containing (3 of each) values from 2 pf. to 2,000 pf., 10/-, 100 assorted containing (3 of each) values from 2 pf. to 2,000 pf., 17/6. Metal Rectifier, 250 volt, 250 milliamperes, 12/6 each; 300 volt 60 m.a., 5/6 each.

Gramophone Auto-Changers



The latest models by very famous manufacturers. 3-speed with crystal turn-over pick-up, brand new and perfect, in original cartons. Choice of four from £7/15/0, carriage, ins., etc., 7/6.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to E.P.E., LTD., Dept. 5, Sutton Road, Eastbourne Personal shoppers to one of these addresses please.

42-46, Windmill Hill, 152-3, Fleet Street, 29, Stroud Green Rd., 249, Kilburn High Road, Kilburn, E.C.4, Finsbury Park, N.4, Road, Kilburn. Phone: RUISLP 5780 Phone: FLEet 2833 Phone: ARCHway 1049 Half day, Wednesday. Half day, Saturday. Half day, Thursday. MAIda Vale 4921.

NEWNES
Radio and Television
Servicing

RADIO AND TELEVISION SERVICING

E. MOLLOY
W.F. POOLE

1955 1956
MODELS

320 POPULAR 1955-56 Models
IN ONE VOLUME

Free for 7 days

HERE is the latest volume in Newnes RADIO AND TELEVISION SERVICING Library. It adds 320 popular 1955-56 models to your servicing range. Servicemen who are profiting from these yearly volumes know their value in £ s. d. and snap them up as soon as they are published! If you have not yet started building a Newnes library of Radio and Television data, claim Free Examination and judge for yourself!

348 Pages of T.V. Servicing Data
198 Pages of Radio Servicing Data

596
PAGES
320
MODELS

TELEVISION

MODELS BY ...

Alba, Ambassador, Baird, Banner, Bush, Cossor, Decca, Defiant, Ekco, E.M.I., English Electric, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Murphy, Pees Scott, Philco, Philips, Pilot, Portadyna, Pye, Rainbow, Regentone, R.G.D., Sobell, Stella, Ultra, Valradio, Vidor.

RADIO

MODELS BY ...

Ace, Banner, Bush, Champion, Cossor, Decca, Defiant, Eddystone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Murphy, Philco, Philips, Pilot, Pye, Regentone, R.G.D., Roberts' Radio, Sobell, Strad, Ultra, Vidor.

CLAIM FREE EXAMINATION NOW

To: George Newnes Ltd., 66-69 Gt. Queen St., London, W.C.2.
Send me the 1955-1956 VOLUME of Newnes RADIO AND TELEVISION SERVICING. I will either return it in 8 days or send 10/- deposit 8 days after delivery, then 10/- monthly, paying 50/- in all. Cash Price in 8 days, 45/-.

Name.....

Address.....

Occupation.....

Signature.....
(Parent's Signature if under 21)


R.2G

	Place X where it applies
	HouseOWNER
	Householder
	Living with Parents
	Lodging Address

BAND III T.V. CONVERTER

12 months' guarantee all items.

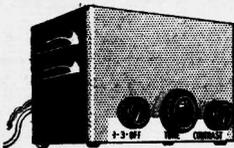FOR I.T.A. LONDON, BIRMINGHAM, MANCHESTER, YORKS, GLASGOW. For superb or T.R.F. State B.B.C. station. Fully wired with power pack, aerial switching, tested and ready for use.



£4-10-0

Post Free

C.O.D. fee 1/6 extra

Ditto in walnut cabinet, £5.
High gain; satisfaction or money back.
OR Complete kit of parts including two valves, wound coils, punched chassis 6in. x 4in. x 2in. metal rectifier, and all screws, solder, etc. As illus., but 1 knob. Price 62/6.
Without power pack, 42/6. Power required 200 v. 17 m.a. and 6.3 v. 1 A.
Print showing details exc. values, 1/6.
Outdoor Band III Dipoles with 4 yds. co-axial, 13/9. Co-axial cable 8d. yd. Plugs 1/- ea. "Gold" filled knobs, 10d.
Cross-over units, 8/-.
B.B.C. Filter to eliminate interference patterns, 8/-.

GLADSTONE RADIO
P.O. BOX 8, CAMBERLEY, SURREY

TECHNICAL TRADING CO.

SPECIAL BARGAIN 12 V. 4 AMP RECTS. 9/6 EA., 25 Doz. Iron Selenium, Full Wave, heavy, compact.

WIDE ANGLE TRANSFORMER KITS, boxed, consisting of: (a) Line Transformer 14 Kv., ceramic base, E351 mountings, ferricite core, 17/6 with instructions. (b) Frame Transformer, large efficient for ECL80, 9/6. (c) 250 ma 7 H Smoothing Chokes. 3 way mounting, 7/6.

COMPLETE KIT AS ABOVE. Snp Price for 3 items, 30/-.
Width Coils and Linearity Coils, to match above, 4/- ea.

ION TRAP MAGNETS.—Best quality 3/6. **ALLADIN FORMERS**, 1in. with slug, 4/- doz. **VISCOOL COILS.**—402 mf., 18 Kv., 4/9.

DEFLECTION COILS.—Standard 35 mm., iron core, 9/6.

5 CHANNEL TUNERS.—Complete chassis, famous make, for EF80 and EOC81 (less valves), 12/6. **BOWLER HATS**, 1/-. **FOCUS MAGNET HANDLES**, 6d. **MONITORS TYPE 33.** 200/250 v. A.C., 24 10/-.

INDICATORS Type 74A, 200/250 v. A.C., 24 10/-. **LOUDSPEAKERS.**—Top makes, 7 x 4 elliptical, 17/6. 8in. P.M., 12/6. Ditto, ex. EQPT. 7/6. **THEATRE MIKES.**—British, boxed, 2/6. Single LR earphones with headband, 2/6.

TV TABLE CABINETS.—Top makes, brand new, boxed, beautiful appearance, latest designs. 14in., 19/-; 17in., 22/6; ditto with mask and glass, 14in., 29/-; 17in., 29/-; all 7/6 each.

WIREWOUND PRE-SET POTS.—500Ω, 1 K, 2.5 K, 5 K, 10 K, 20 K, 25 K, 50 K, 2/- ea.

AMPHENOL HOLDERS.—Octal, Mazda, Noval, 27G, B9A, 6/- doz. B9G W/Screen, 1/6 ea. Tube Holders, Octal, 6d. Duodecal, 1/-.
1 MEG POTS D.P. SWITCH.—3in. spindle, small type, 3/6. Ditto, 1in. spindle, 2/6.

RESISTANCES, ASSORTED.—1/2 Ceramic, 4.7Ω —1mΩ, 2/- doz., 10/- 100.

MIDGET CERAMIC CONDENSERS.—10, 20, 50, 300, 1,000, 3,000, 6/- doz. Midget 16 + 16 350 v., 3/-; Midget 8 x 250 v., 1/-; Midget 100 mfd. x 6 v., 1/-; 60 + 100 350 v., 6/-.

F.M. CHASSIS.—Drilled 6 valve receiver, hammered finish, 1/6.

F.M. TUNERS.—A.C. Power Pack, EF84, EF80, EOC81, EZ80, Listed 19 pins, 27 10/-. Ditto, less valves, 25. Ditto, less mains transformer valves, 23 15/-.

CHASSIS.—6 x 4 x 1 1/2, 2/9. 6 x 4 x 2 1/2, 3/-. 8 x 5 x 2 1/2, 3/6. 8 x 6 x 2 1/2, 4/9. 8 x 10 x 2 1/2, 5/9. All best quality heavy aluminium sheet.

5H 250 mA CHOKES.—Compact type, special snip, 4/8 ea.

RADIO VALVES GUARANTEED PERFECT

6AK5 6/6	6EP3 6/6	12AX7 6/6	EF92 4/6	SP61 3/6
6AG5 5/6	6J6 6/6	813 5/6	EL91 5/6	SP210 3/6
6AL3 5/6	6J7G 4/6	EB54 2/-	B235 8/-	U22 3/6
6C4 6/6	6J5G 4/6	EB84 2/-	PEN25 5/6	VR150/30
6F6G 6/6	6K7M 6/6	EOC21 6/6	FY31 4/6	6/-

Postage 1/- in 21. (1/9 in 21 Speakers/Trans.), minimum 6d.

1,000 OTHER BARGAINS TO CALLERS AT

350/352, FRATER ROAD, PORTSMOUTH
PORTSMOUTH'S RADIO, TV AND TOOL SHOP

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

IMPROVING I.T.A. CONVERTERS

SIR,—I would like to thank you for publishing the article, "Improving I.T.A. Converters," in the June issue of PRACTICAL TELEVISION.

Newark is well inside the fringe area of the Lichfield transmitter, so an efficient converter is essential for good reception here.

I found my converter quite efficient on vision, but not so good on sound, so I made the necessary modifications, according to the article. The result was a 50 per cent. increase in sound and a "cleaner" picture.

Once again, many thanks.—J. H. TWYDELL (Newark).

ADDING A TURRET TUNER

SIR,—Having had requests from various people to add converters to television receivers, more particular the "Tele-King" and "Supervisor," I found many ways in which to do this and they have appeared in your journal and others.

The most convenient and quickest is merely to remove from the sockets, valves 1, 2 and the frequency changer No. 3. Disconnect the anode-load resistor (R13, also C10 and C11 in the "Supervisor") from V3.

Bring the grid output lead of the Valradio or Teleng tuners, etc., to the top end of L5, where we have just disconnected the resistor and condensers mentioned and of course, ground the shielding. A dropping resistor from the B+ (180 volts.) of about 2 K provides approximately 150 volts for the tuner connected at the point originally occupied by R13.

Where there has been difficulty with either tuner as to connection using the suggested circuitry provided by the manufacturer or a magazine the above has proved to be 100 per cent. perfect and much simpler.

In the latter tuner having pre-set position for sensitivity on both bands, it depends on the district, but at Ealing, using just a Band I "X" aerial a 50 K control fully extended on Band I and on Band III short circuited, gives equal gain. The aerial by the way, is in the loft and not outside, and does not face either station due to fitting position.

I make these points because I am quite certain that the many methods described in various journals have served to mislead and make the addition to a turret type tuner very complicated.—A. G. BOURNE (Ealing).

TV SOUND BREAK-THROUGH ON 80 M.

SIR,—I have just read the current edition of PRACTICAL TELEVISION, and would like to raise a few points. First, the TV sound break-through on the 80 metre band is probably caused as follows: The distance between the vision and sound transmissions is 3.5 Mc/s. It is possible for these to beat together in the TV receiver and produce a radiation of TV sound superimposed on a rough hum, which is the video signal. This will be a 3.5 Mc/s or 85.75 metres.

Secondly, Iconos complains of poor quality I.T.A. sound, and I would like to mention that the quality of sound of the I.T.A.'s Winter Hill transmitter far

surpasses that of Holme Moss. The frequency response is really amazing in both bass and treble registers, but I have often failed to hear the bass accompaniment of an organ or a double bass on the BBC. The I.T.A. sound has, however, less volume than the BBC's.

Thirdly, S. P. complains of BBC break-through on his converter. This can often be cured on the Mark I by altering it to a tuned input. This means replacing the 1 k Ω resistor in the grid of the first valve by a coil. This can be done by winding 4½ turns of 22 gauge wire on a ½ in. former (such as a radio screwdriver). This coil is then connected between the grid and chassis. The signal from L1 being tapped in one turn from the chassis. The coil can be tuned by altering the spacing between the turns with a knitting needle. As well as reducing break-through a useful increase of gain can be achieved by careful tuning. It might also be helpful for me to point out that the performance of a Band III converter can be completely spoilt by the use of four iron dust cores. If proper Band III ones are not available I have found Radiospares "A" type cores to be very good.—HARRY LEEMING (Blackburn).

A SCOPE FOR TV

SIR,—I am interested in making the oscilloscope described by Mr. J. Hillman in the last two issues. There are two points, however, regarding which I should like confirmation.

The theoretical circuit shows the control grid of V3 taken to the slider of a potentiometer which is strapped between the H.T. rail and chassis. Consequently, at one end of its traverse the grid of this valve will be at full H.T. potential.

Probably the control will never need taking to its extreme setting, but the arrangement still seems questionable. Will you please state if this particular provision is in order?

Two of the switches, as listed, would be more expensive than they need be. Only a five-way switch is required for S2, where a six-way is specified, and only a one-pole switch is required for S1, although there is no one-pole four-way switch listed among the components.—J. BROADBENT (Sale).

[The connections to R25 as shown in Fig. 1 are quite in order and follow normal procedure for a Miller integrator circuit. The action is as follows: When the slider of R25 is at the H.T.+ end with S2B in position 1 then C20 is charged to full H.T. voltage. The anode of V3 is -ve with respect to H.T.+ due to the anode current flowing in R19, 20, 21, 22 and because C20 is charged then the grid is -ve with respect to the anode by the full H.T. voltage. The grid is then -ve with respect to the cathode by the amount of the volts drop across the anode load resistors. The valve is thus working with a -ve grid and grid current does not flow in spite of the fact that the grid return of the valve is taken to H.T.+.

With regard to the switches used, the reason for quoting a six-way switch was that this particular switch is an ex-government type, and quite cheap, and the contacts are spaced radially equidistant and by using two of the two-P six-way types one three-P six-way can be made up.—ED.]

CAR RADIO—APPROPRIATE

SIR,—In view of recent reports that a television set has been manufactured for use in a car, I would like to register a strong protest. It is a well-known fact that the number of deaths on the road has increased tremendously since the war, until now the number killed and injured each year is becoming so high that one is afraid even to cross the most unfrequented lanes.

Surely it is about time we all woke up and started doing something about this dark patch that hangs over us all. But no, we seem to shrug our shoulders, and now, what is worse, we allow motorists to have television sets in their cars so that it will distract them even more. I am aware that the proposed law will forbid a motorist to look at a television set whilst driving, but the present law also forbids a motorist to drive a car whilst under the influence of drink. However, I notice that they still do drive in a state of intoxication. It is to be hoped that the dangers are realised before it is too late. Television has undisputedly a place in our homes today, so let it remain there.—**W. J. WILKINSON** (London).

[According to Sir Alker Tripp, the number of accidents caused by drunken motorists is so small as to be not worth considering. We do not think that car TV will be popular.—ED.]

COMMUNITY OF CRYSTAL GAZERS?

SIR,—I have for some time waited to hear on TV a programme that has any good music included in it, and it would appear so have others, judging from the speech given by Lord Lucas when addressing the 42nd anniversary of the Performing Rights Society in London recently. He said that "we are becoming a glassy-eyed community of crystal gazers" and that both the BBC and the I.T.A. had "failed utterly" to give the public any good music on television. He also went on to say that "Sound broadcasting did more to educate people in the appreciation of good music than any other single force. But with the advent of television I hold an entirely different view."

Lord Lucas continued, "I watch television with keen interest and I see arrogant and impertinent people pretending to produce and direct Beethoven, Chopin, or any of the great composers. Their ideas of production generally result in showing the artists performing in every posture except standing on their heads."

COLOUR TELEVISION

(Continued from page 15)

synchronous detector so that it delivers a different colour signal for each frame. (A phase shift is introduced by means of a tri-stable switch which is triggered from the frame timebase.) This means that if this signal is displayed on a normal tube which is then viewed through a disc of rotating colour filters a colour picture is seen. This picture will, however, suffer from a rather low repetition rate and colour fringing and flicker may be present. Obviously, this is not the method which will lead to a standard home colour television set but it is mentioned in passing to show that there is plenty of scope for interested amateurs once colour transmissions are commenced in this country.

British Colour TV

What of the future? The system which will

He went on to say that to tie up culture and commercialism is a great mistake. "What have we in place of good music? Alleged humour which starts as mediocrity, gets to vulgarity and on all too many occasions reaches the level of obscenity.

"I believe this is the result of a great mistake made in trying to tie up cultural education with the commercial considerations of advertising.

"I hope the day will come when we shall have a government with the common sense to give the BBC facilities for a second programme, which can give the cultural artistry of good music, and allow the other to compete with the squalid profanity which is at present the hallmark of commercial television"—**G. A. MANUEL** (Bromley).

I.T.A. CRITICISED

SIR,—Just lately I had my set converted so that it would receive the Band III programmes, but after looking at these I now wish that I had left it to receive Band I only. Some of the programmes put on by the I.T.A. are very interesting and one becomes absorbed in them; however, just when you relax, look at the show and enjoy yourself, what happens? A gaudy advertisement accompanied by a stupid song suddenly flashes on the screen and completely takes one's interest away. This type of advertising is doing a lot of harm to the I.T.A., for this half-hearted attempt to copy the American style of high pressure selling is not appreciated by British viewers.—**B. FILMER** (Kilburn).

A BOUQUET


SIR,—I have been a regular reader of PRACTICAL TELEVISION since the first and I would like to take this opportunity to thank you for the mine of information that is in each issue.—**F. MORGAN** (Australia).

PRAISE FOR OUR "SUPERVISOR"

SIR,—Whilst sorting through some old copies of PRACTICAL TELEVISION some time ago, I decided to build the "Supervisor" as described in your August, 1953, issue.

I was surprised to find that although the "Supervisor" is now three years old, and a lot of advances in electronics have taken place during those three years, it is still comparatively up-to-date in its design. I might add that I am more than satisfied with its performance.—**N. J. OHME** (Isle of Wight).

eventually be adopted in this country is a matter of guesswork at the present time. There is much to be said for the American system scaled down to our 405 line standards, and this has been demonstrated by the Marconi company last year and is currently the subject of experiments by the BBC. The chief disadvantage is the occurrence of patterning in areas of highly saturated colours when the transmission is being received in monochrome on the normal set. Many advantages would be gained by the use of a wider bandwidth, but overcrowding of the wave bands seem to preclude this solution. In the meantime, it is satisfying to note that a compatible system is considered essential and this means that if colour does come sooner than we now think, a 1956 TV set will not be out of date as it will still be able to reproduce the colour transmission, though only in black and white.

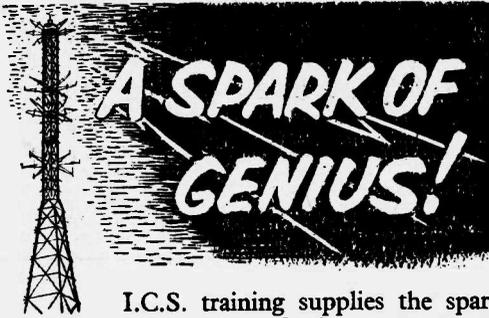

I.C.S. training supplies the spark you need to further your career. The Courses I.C.S. offer are practical and up to date, they recognise the present emphasis on Frequency Modulation, and can help you attain one of the many well-paid posts that exist today in the radio world. Prepare yourself now, at home and in your own time, with the expert help of I.C.S. tutors. The cost of an I.C.S. Course is moderate and includes all books.

Among the I.C.S. Courses available are:

- FREQUENCY MODULATION ENGINEERING
- T/V ENGINEERING
- RADIO SERVICING
- RADIO ENGINEERING
- RADAR ENGINEERING
- BASIC ELECTRONICS
- INDUSTRIAL ELECTRONICS
- ELECTRONIC ENGINEERING

Complete the coupon below and post it to us today for further details of the Course which interests you. Write to: Dept. 172B, I.C.S., Kingsway, W.C.2.

REDUCED TERMS FOR H.M. FORCES

INTERNATIONAL CORRESPONDENCE SCHOOLS
DEPT. 172B, INTERNATIONAL BUILDINGS KINGSWAY,
LONDON, W.C.2.

Please send FREE book on.....AGE.....

NAME.....
(Block letters please)


ADDRESS

OCCUPATION

INTERNATIONAL
CORRESPONDENCE SCHOOLS

THE STIRLING BAND III CONVERTER

FOR ONLY
6gns.

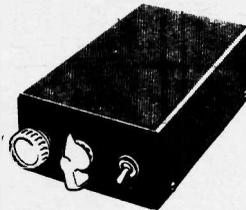

Self-contained power supply and aerial cross-over network. Simple to fit. No internal connections have to be

made to your receiver, the only connection is to the normal aerial socket.

Designed for reception of B.B.C. and I.T.V., the unit is fitted with FINE TUNING, PRE-SET GAIN CONTROL, CHANNEL CHANGE-OVER SWITCH, and ON-OFF Switch. In brown crackle case size 6½" x 3½" x 2". Fully guaranteed. S.A.E. for leaflet.

Obtainable from:

HOME RADIO OF MITCHAM

187, LONDON ROAD, MITCHAM, SURREY.

Telephone: MITcham 3282.


17" TV TUBES 14"

6 MONTHS GUARANTEE

17" £7.10.0 RECTANGULAR. Tetrode and Triodes. All popular makes and types. Ins. and carr. 15/6.
14" £5.10.0 RECTANGULAR. Latest types on all makes available. Ins. and carr. 15/6.
12" £5 ROUND. State make and type required. If possible state equivalent second choice. Due to very heavy demand for some makes Ins. and carr. 15/6.
6 months guarantee on Mullard. 3 months other types. As we have been selling tubes for the past 5 years. All enquiries welcomed. Please send cash with order.

39'6 RADIOGRAM CHASSIS

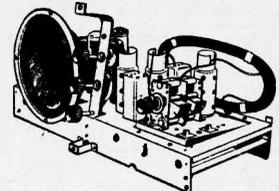3 w/band & gram. Extra speaker sockets, 5 valves international octal. Built-in portable aerial optional. 4 knob control. A.C. or universal. Less valves (see our cheap list). 8" P.M. speaker 7/9 with order. Set of knobs 2-. Chassis 19" x 7" x 9" (when speaker is fitted). Carr. 4/6.



POWER TRANSFORMERS, 15/9. 325-0-325 v. mains. 6 v. at 5 A., 4 v. at 5 A., 4 v. at 5 A. Extra isolated windings for 2 or 4 v. tubes. Also similar trans. with 6 v. at 5 A., 6 v. at 5 A., 22 v. at 14 A. Both are 250 mA. Plus post 2-.

MAINS TRANSFORMERS, 5/9. Heaters 6 v. and 5 v. 350-0-350 v. primary 200-250 v. Post 2-.

MAINS TRANSFORMERS, 3/9. 350-0-350 v. heaters 12 and 4 v. primary 100-250 v. Ideal auto-trans. Post 2-.

MAINS TRANSFORMERS, 5/9. 350-0-350 v. heaters 4 and 4 v. primary 200-250 v. Post 2-.


MONEY BACK
GUARANTEE

DUKE & CO

Tele: GRA 6677

CWO
ON
COD

621 ROMFORD RD. LONDON, E.12.

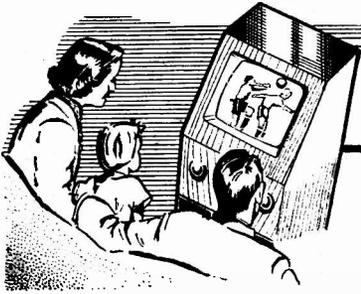

UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

NEWS PRESENTATION

THE BBC do not seem to be satisfied with the presentation of their TV news. At any rate, they still seem to be experimenting with various trick devices to give a more visual effect. The idea of projecting still photographs appropriate to each headline in the corner of the picture as they are read by the announcer is an ingenious one, but doesn't quite come off. This is possibly due to the BBC's restraint upon the announcers putting over their own personality; their policy is for the announcer to remain a kind of catalytic agent, quietly and factually reporting news items without a glimmer of emotion. This has the unintentional effect of making even the best of good news sound slightly depressing. I see no reason why the headline visuals should not be shown filling the screen, with no announcer in the picture. On the other hand, the I.T.A. News has more of a "tabloid" flavour, savouring of the four-million or so circulation newspapers of Fleet Street. The I.T.A. newsreaders have a little more scope for dramatising events on occasion and are often given amusing silly-season items to finish off the bulletin in a more cheerful vein, which brings the viewer more into contact with the newsreader. I.T.N.'s interviews with typical "men in the street" are not always successful, chiefly because the interviewer seems to ask the most obvious and rather feeble questions. This kind of thing requires a very strong personality to put it over. Still, I think it can be said that both of the TV News services are improving. If you read a staid, factual newspaper, then you'll probably prefer the BBC news. If you normally read a high-circulation pictorial newspaper (and its strip cartoons) then you will plump for the I.T.A. News. For amusing and vivid reporting, however, I put the BBC's Jacqueline Mackenzie

at the top. Her vivid descriptions of the Grace Kelly wedding and the Chelsea Flower Show were bright and chatty, interpolated with dainty, thumb-nail imitations which ranged from French taxis to tulips! Miss Mackenzie is definitely a personality-plus reporter, whose charm is putting her into the star class. The BBC cautiously keep her entirely separate from their factual TV news. She could not produce the correct depressing effect even if she tried.


DECLINE ?

PERHAPS the most depressing item put over by the BBC, for a long time, however, has been the half-hour series entitled, "We, the British—Are we in Decline?" Christopher Mayhew's carefully written and smoothly produced composite of live TV and film seemed to me to reek of unconstructive political propaganda. Fortunately, there was a silver lining to the series; that was the alternative I.T.A. programme. All of the viewers I questioned about it quickly switched over to the commercial channel, even those who would normally agree with Mr. Mayhew's political outlook. Mr. Mayhew is a skilled performer on TV, with first-class voice and appearance; he should devote himself to some other less contentious subject. Mr. Woodrow Wyatt is another politician who got himself into hot water by giving an account of the election procedure and possible extremist trends in a certain trade union. In this case, criti-

cism was stifled a few days later by the nation-wide anger over the Electrical Trade Union's support for the terrorists of Cyprus. It seems to me that Mr. Woodrow Wyatt had some of the answers to Mr. Mayhew's tale of woe. They should get together.

MORE PROVINCIAL I.T.A. STATIONS ?

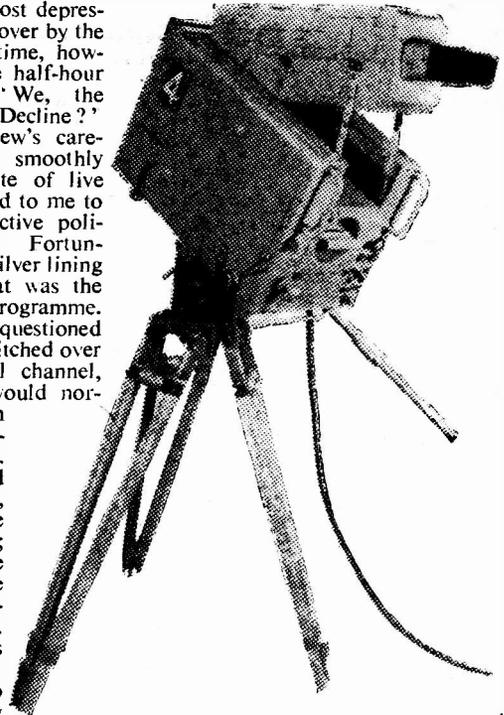ON account of the general hold-up of capital investment, there has been some delay in proceeding with the Scottish



The new Emitron TV camera, the first of 17 ordered by the BBC. Several new features making for easier operation are embodied. As this illustration shows, the electronic view-finder can be adjusted so that it remains level when the camera is tilted for high- or low-angle shots; the focus control is specially designed for accurate adjustment with minimum hand movement.

and Welsh areas of I.T.A. But I hear that two or three potential contractors are now ready with schemes to put before the executive of I.T.A. In the meantime, existing I.T.A. contractors are extending their outside commitments. Both the I.T.A. and BBC are going ahead with plans for live outside TV broadcasts from seaside resorts during the holiday season. The holiday visits will have a rousing start-off with the Jimmy James show, "Let's Have Fun" from the Central Pier, Blackpool, which will be on the BBC. This will be followed up with regular programmes from Blackpool, Morecambe and other Northern resorts by Granada and A.B.C.-TV. There are no difficulties in arranging with the town councils or entertainment managers for facilities; the difficulty is holding back the queue of "Public Relations Officers" awaiting the chance of gratis advertising. Blackpool has a special advantage with its famous tower—an ideal site for a micro-wave relay transmitter.

I.T.A. NETWORKING

It is no secret that the first few months of operation by the commercial TV contractors have been difficult, both from the financial and organisational points of view. Revenues have not reached the heights expected, in spite of strong evidence that a slight majority of viewers is in a position to receive both BBC and I.T.A. programmes prefer the latter. The provincial contractors, A.B.C.-TV and Granada, have benefited by watching the teething troubles of A.R.-TV and A.-TV in London, and have been much more cautious both in their planning of programmes and in their capital outlay on equipment and premises. A.B.C.-TV had the least time of all to prepare for their openings at Birmingham and Manchester, and in some respects they have been the most successful. In spite of apparent co-operation between the different operating companies, there has been considerable poaching of staff, manoeuvrings for position by executives, major and minor catastrophes in both production and engineering departments, resignations, dismissals and also, pleasant to report, a few meteoric promotions. Agreements to exchange programmes on a network basis will lead to economies all round. The I.T.A. contractors are achiev-

ing amazing results when one considers the limited facilities at their disposal. A.-TV have virtually no studio space compared with the BBC, and their Foley Street premises are little more than a telephone exchange for outside television set-ups, such as the Palladium Show and their other regular theatre set-ups at Wood Green and elsewhere.


A.R.-TV have a well-equipped studio at Wembley, but have had to reduce facilities (and operating costs) temporarily. Birmingham studios turn out to be the Astoria Cinema only (used by A.-TV and also A.R.-TV) and Manchester has A.B.C.-TV's converted Capitol Cinema at Didsbury and the Granada Studio in the centre of that city. However, out of chaos seems to come order, so far as the viewers are concerned. The

enormous rise in TV licences since commercial television started has benefited the BBC financially, and BBC executives are rather touchy on this point. Sooner or later, they expected the I.T.A. to ask for a "cut" in the increased revenue from licences. The thought seems to have had results. I hear that application is to be made for a subsidy for the more "cultural" items. If this means that we will see more shows of the Hallé Orchestra type on I.T.V., then I, for one, would be in favour of it.

CO-OPERATION

It is pleasing to note the increasing measure of co-operation which is growing between all the TV organisations and the music hall artistes. The show put on by their own special kind of masonic society, the Grand Order of Water Rats, last year, was such a big success that the variety folk are taking more kindly to the advancing "menace" of television. Both the Water Rats and the Variety Artistes are now willing to co-op-

erate *en masse* as well as accept individual engagements. Celebrations usually give the excuse for this, much to the enjoyment of viewers, and the Golden Jubilee of the Variety Artistes Federation is an admirable time for the presentation of a Variety Cavalcade. Of course, with this type of show, everybody wants to take part and Dave O'Gorman (of O'Gorman Brothers, the cross-talk comedians) has had quite a job fitting in a large number of acts in a limited time. You can't very well blame them for wanting to jump on the band wagon. They realise that the TV public must be encouraged to re-acquire a taste for the music hall. Streamlining of variety acts by TV producers who really know something about variety will accomplish this.

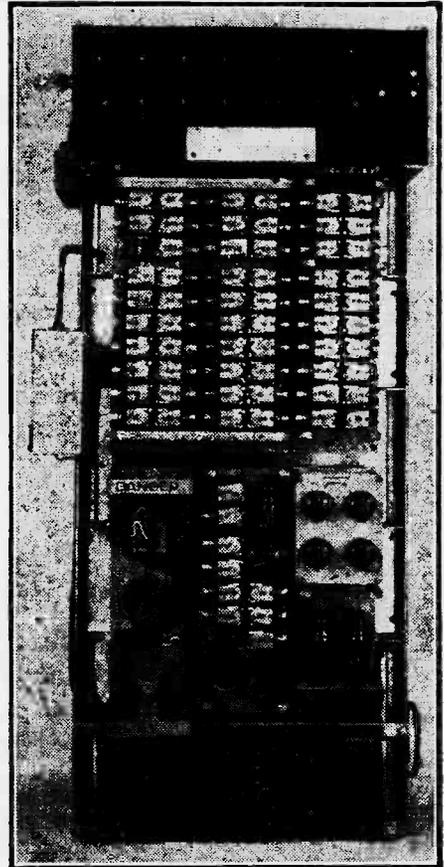

(Photo by courtesy of Siemens General Electric Co., Ltd.)

The automatic brain of our traffic light system, which sorts out pulses from the detector pad in the road and effects the changing of the lights.

NEW! EXPERIMENTAL KITS in Radio, T.V. etc.

LEARN THE PRACTICAL WAY


Specially prepared sets of radio parts from which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at a Very Moderate Cost.

EASY TERMS FROM 15/- A MONTH
With these outfits, which you receive upon enrolment, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to complete Radio and Television Receiver Testing and Servicing.



TELEVISION — With this equipment you are instructed in the design, construction, servicing and testing of a modern high quality Television Receiver.

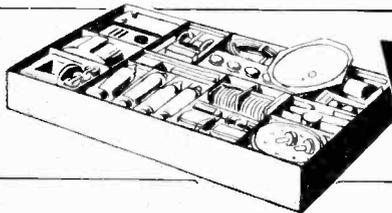ALL EQUIPMENT SUPPLIED IMMEDIATELY AND REMAINS YOUR PROPERTY




BEGINNER'S RADIO OUTFITS

— For carrying out basic practical work in Radio and Electronics, from first principles and leading to the design and building of simple Receivers.

ADVANCED RADIO OUTFITS

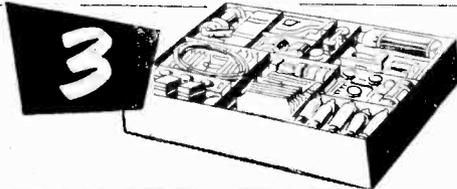— With this equipment, you are instructed in the design, construction, testing and servicing of a complete modern T.R.F. and Superhet Radio Receiver.



OTHER COURSES WITH OUTFITS INCLUDE:

**MECHANICS · ELECTRICITY
CHEMISTRY · PHOTOGRAPHY
CARPENTRY**

**ALSO DRAUGHTSMANSHIP · COMMERCIAL ART
AMATEUR S.W. RADIO · LANGUAGES · ETC.**

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses: I am interested in Television
Radio: Beginners , Advanced
Other subjects _____
(Please indicate Item(s) required)
To: E.M.I. INSTITUTES, Dept. 138X, Grove Park Road, London, W.4.



NAME _____

ADDRESS _____

AUG.

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation

HENRY'S

(RADIO LTD.)

TRANSISTORS

This Junction Transistor is designed for audio-frequency amplification, although its frequency response makes it suitable for intermediate frequency and switching applications, together with many other uses, e.g., Local Station Receiver, Transistor Voltmeter, Signal Tracer, Oscillators, Experimental Work, etc. (Circuit supplied).

DUE TO A LARGE PURCHASE, WE CAN OFFER THESE TRANSISTORS (A PRODUCT OF WELL-KNOWN MANUFACTURER) AT THE VERY LOW PRICE OF:— EACH

10/- Call and Hear Demonstration Models Working.

INDICATOR UNIT TYPE 182A

Unit contains VCR517 Cathode Ray 6in. tube, complete with Mu-metal screen, 3 EF50, 4 SP81 and 1 3U4G valves, 9 wire-wound volume controls and quantity of resistors and condensers. Offered **BRAND NEW** (less relay) at 67/6 plus 7/6 cart. Radio Constructor scope circuit included.

V981A The Selected EF50, Brand New Red Sylvania original cartons, 10/- each, 90/- for ten.

U.S.A. INDICATOR UNIT TYPE BC929A

In black crackled cabinet 14in. x 9in. x 9in. Complete with 3BP1 C/R Tube, shield and holder, 2 6SN7GT, 2 6HG7, 1 6X5GT, 1 2X2, 1 6G6, V/controls, condensers, etc. Ideal for 'scope. Brand new, 65/-, carriage paid.

MINIATURE I.F. STRIP TYPE "375" 6-72 MEG.

Brand new miniature I.F. Strip size 10in. x 2 1/2in. x 3in. high. Valve line-up: 2 EF92; 3 EF91 and EB91. With Circuit. Price (less valves), 7/6. P.F. 1/8.

SPECIAL REDUCTION FOR SETS OF VALVES

1A7GT, 1N5GT, 1H5GT, 1A5GT (or 1Q5GT or 3Q5GT)	37/6	Set
10 EF50 (Ex-Brand New Units), 5/- each	45/-	"
6K8G, 6K7G, 6Q7G, 5Z4C, 6V8G	35/-	"
1L5, 1L5, 1T4, 1S4 or 3S4 or 3V4	27/6	"
DK36, DF66, DA98, DL66	35/6	"

We have over 50,000 valves in Stock at more than 50% off. SEND 3d. for 28-PAGE ILLUSTRATED CATALOGUE.

CRYSTAL MICROPHONE INSERTS



Ideal for tape recording and amplifiers. No matching transformer required.

QUARTZ CRYSTALS

Type FT243 Fundamental Frequencies, 2-Pin lin. Spacing. 120 Types: 5675 Kc/s to 8650 Kc/s (Channel 270/389). (In steps of 25 Kc/s.) 80 Types: 5706.667 Kc/s to 8340 Kc/s (Channel 0/79). (In steps of 33.333 Kc/s.)

BRAND NEW AND GUARANTEED, 10/- each. Complete sets of 80 and 120 Crystals available.

Type FT241A '54th Harmonic

2-Pin lin. Spacing
80 TYPES: —
30 Mc/s.—27.9 Mc/s. (in steps of 100 Kc/s.)

BRAND NEW AND GUARANTEED, 7/6 each. Complete Sets of 80 Crystals Channel 0/79 available.

200 Kc/s, 10/- each. **CRYSTAL HOLDERS, 1/3 each.** 10% Discount on all orders of 25.

CATHODE RAY TUBES

(Brand New)

VCR97 (slight cut-off) 15/-
VCR97 guaranteed full T/V Picture ... 40/-
VCR517C guaranteed full T/V Picture ... 35/-
VCR139A, guaranteed T/V Picture ... 35/-
VCR139A (with Screen) ... 35/-
3BP1 guaranteed full T/V Picture ... 30/-
Carr. & Packing on all tubes, 2/-.

"88" WALKIE-TALKIE SETS

Special offer of above set. Complete with 5 valves. 4 ARF12 and ATP4 with circuit. Range 7.4 to 9 mc/s. These sets are not guaranteed but are serviceable. 25/-
Junction box 2/8 extra.

PYE 45 MC/S STRIP TYPE 3583 UNITS

Complete with 45 Mc/s Pye Strip, 12 valves: 10 EF50, EF34 and EA50, volume controls, 25 hosts of resistors and condensers. New condition. Modification data supplied. Price 69/6, carriage paid.

62A INDICATOR UNIT CONTAINING VCR97

with Mu-metal screen, 21 valves: 12-EF50, 4-SP61, 3-EA50, 2-EB34. Plus pots., switches, H.V. cond., resistors, MuIrhead S/Y dial, double deck chassis, anode crystal. **BRAND NEW ORIGINAL CASES, 67/6, carriage 7/6.**

5, HARROW ROAD, PADDINGTON, LONDON, W.2. TEL.: PADDINGTON 1085-9, 0401

HANNEY OF BATH offers:—

VIEWMASTER 3-STATION TV TUNER (P. Television).—Denco colliet with screens, can and screws, 30/-; Denco switch, Fine Tuner, Coil mounting plates and tag panel, 27/-; Kit of resistors, 7/6; TCC condensers kit with 2 printed circuits, valveholders, etc., 43/-; Gain controls, 3/3 each; Co-ax P/S kit, 2/6; Valve lines, 1/3 each. Complete kit of parts for the TUNER, with the 2 Genuine MULLARD Valves, nuts, bolts, wire co-ax., etc., 28/19/6. Denco Colliet for conversion of the V-Master S/V chassis to the I.F. amplifier, 20/-, OR Complete kit of S/V conversion components, 39/6. All Standard V-Master items in stock. Full list available.

MULLARD 3-VALVES 3-WATT AMPLIFIER.—Punched chassis 10/6; Gilson Trans. Mains, 35/-; Output, 25/6; Elstone Trans., Mains, 35/-; Output, 21/-; Condenser kit, 20/-; Resistor kit with 3 pots, 22/6. Complete kit with Genuine Mullard VALVES 28/19/6. Full list available.

MULLARD 510 AMPLIFIER.—Erie Resistors, 27/-; TCC Condensers, 45/-; Elstone Mains Trans., 38/- (100 m.a.); 42/6 (120 m.a.); Output Trans., 45/- (6K, or 8K); Gilson mains trans., 60/- (140 m.a.); Output trans., 47/6 (6K, or 8K.); Ultra linear type, 52/6; Partridge Mains trans., 65/6; Output trans., P.3677, 55/6; Partridge Ultra Linear type P.4014, 98/6; Denco punched chassis, 19/6, with base plate; Printed front panel, 8/6; Type "A" and "B" chassis (panel not printed), 8/6 and 12/6 respectively; condensers, "A", 15/6; "B", 24/6; Resistors, "A", 17/6; "B", 35/6 (with pots.). Full list available, giving details of complete kits.

OSRAM 912 PLUS AMPLIFIER.—Erie resistor kit, 17/4; Erie 1 meg. pots., 4/6 each; TCC condenser kit, 55/-; PARTI-RIDGE component with loose leads (terminations includes peaking charge), Mains trans. 85/6; choke, 34/6; output trans., 85/6; W.B. components, Choke, 18/9; output trans., 32/-; Denco drilled chassis, 14/6; Denco 912 Plus printed panel, 7/6; preamp or passive chassis, 6/-. Full list available.

COMPONENTS are still available for the following **F. M. TUNERS:** Wireless World, Mullard, Osram 912, Denco Maxi-Q. List available.

WIDE ANGLE COMPONENTS. ALLEN Telesing Chassis, 50/-; Collists (TK and Super-Visor), 44/6; LO.308, 40/-; FO.305, 21/-; DC.300c., 39/6; FC302, 31/-; GL.18 and 18, 7/6 each; SC.312, 21/-; AT.310, 30/-; OP.117, 9/-; BT.314, 15/-; DENO Chassis Magnaview, 37/6; Chassis, Super-Visor, 51/6; Coil sets Magnaview, 41/6; WAFMAL 43/-; WAFMAL 41/-; WAFMAL 41 and WCL, 7/6 each; WAFMAL 21/-; WAFLOT1, 42/-; WAFBTL, 16/-.

Send stamp for lists. Please add 2/- postage to all orders under 23 (excess refunded).

L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

TEL.: 3811

"You can rely on US" for ...

ALL RADIO and ELECTRONIC COMPONENTS

One of Britain's Largest Stockists of all Leading Makes: Hunts, T.C.C., Haynes, Allen, Denco, Osmor, Weymouth, Morganite, Bulgin, Belling Lee, Teltron, R.E.P., Scotch Boy, Ellison, Elstone, Partridge, Wynall, Westinghouse, S.T.C., AVO, Taylor, Goodmans, J.B., Wharfedale, Wearite, Acos, etc.

Suppliers to: Ministries, Development Laboratories, Education Authorities, etc.

Some of the more difficult parts you may not be able to acquire:

- Tapped Vol. Control, Linear C.T. 1/4 mg., 1/2 mg., 1 mg., 7/6. Linear 1/4 mg., 1/2 mg., 1 mg., 6/6. Post 6d.
- 2 High Stub 1/4 w. Resistors. 2% Range, 1000 to 2 meg., 1/6 each. 1% Silver Micas up to 100 pf., 1/, 280 pf., 1/2. 500 pf., 1/4. 1,000-5,000, 2/6. Post 6d.
- Telatron Band III Converter—Punched Chassis, 4/-, Post 6d. Set of Coils and Circuit, 15/-.
- Band III Loft Aerials, 30/- plus 2/- carriage.

Thousands of Valves, Condensers, Resistors—Can We Help You?

MULLARD 510 and GEC 912 all specified parts and lists available.


Catalogue, Book Lists, S.A.E.

RADIO SERVICING CO.,

82, SOUTH EALING ROAD, LONDON, W.5.

Tel.: EAL 5737. Next Sth. Ealing Tube, 65 Bus.

1 p.m. Wed.

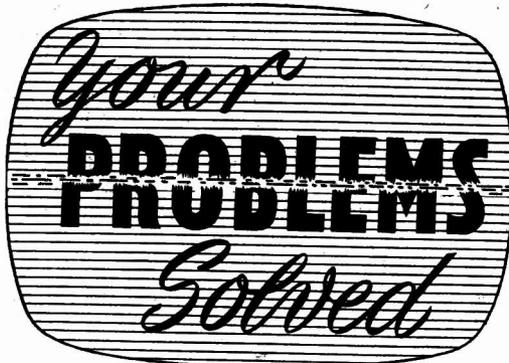

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 47 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

H.M.V. 1808

My trouble developed after fitting a 3.3 k Ω resistor in the noise-limiter circuit.

The picture seems to have lost all highlights and has dark streaks across it. I can get rid of the streaks if I turn up the brightness, but the picture is still rather dim. I have replaced some of the Z77 valves and also the X78, but with little difference.—A. W. Heywood (Rotherham).

It would seem that you have used the wrong value resistor. Our records do not show a 3.3 K resistor associated with either of the noise-suppression circuits.

MARCONIPHONE VT56DA

My trouble is that at times the picture disappears, and is replaced by black and white lines travelling down the screen.

To overcome this I have to turn the picture interference limiter fully anti-clockwise; if this does not bring back the picture, I have to turn the set off for a few minutes. On switching the set on the picture flashes and jumps for about half a minute. There is bad sound on vision all the time.—A. C. Perrin (S.W.6).

This trouble is probably caused either by a faulty valve or a short in the picture tube. Try gently tapping the valves and the neck of the tube while the set is working, taking care to avoid electric shock. If the fault can be provoked by this action, then the valve concerned should be replaced. You should also ensure that the valve pins are making good connection to the valveholders; if necessary, clean the pins with fine emery cloth.

Excessive sound on vision may indicate that the signal is now too strong due to the recent increase of power from Crystal Palace. Try a 12 db attenuator in the aerial lead.

DECCA DM146531

I am having difficulty in getting the I.T.V. Channel 9 on my set. The picture is not very bright and sometimes it is alive. I have an eight-element aerial on a 20ft. pole, but at the back of the house is a hill and

trees, and at front more trees. I get a perfect BBC picture with an "H" aerial.

Is there any way of getting a good picture on Channel 9 or improving it in any way?—R. F. Edwards (High Wycombe).

Yours is undoubtedly trouble as the result of a weak signal on Band III. The Decca series is generally extremely sensitive on Channel 9 and operates well in fringe districts. We can only suggest that you pay attention to the Band III aerial system, ensuring that the array is accurately oriented for optimum pick-up and that it is connected to the receiver through low-loss feeder. If you are using a combining filter, ensure that this is properly connected.

COSSOR 933

My set has developed a peculiar fault. After it has been on an hour or two, there is a distinct click from inside the set, like the discharge of a condenser; the picture dims considerably and slightly folds at the corners, then immediately starts to build itself up again to its original fullness and brightness. This may happen periodically for perhaps half-hour or less and then settles down again. It may happen the next night or for several nights running, or may not happen again for some considerable time. A friend of mine told me it was due to a weak signal. I have an indoor, under-the-roof H aerial, self installed. Would an outdoor one be better, do you think?—A. Moore (Coventry).

We do not think this trouble is the result of a weak signal. In our opinion, the "click" which is heard is due to an EHT flashover, thereby starving the tube of EHT a few seconds before it builds up again. Check the EHT rectifier and the associated wiring; make sure all soldered connections in this vicinity are formed of small blobs with no sharp edges. Suspect an E.H.T. flashover within the tube.

STELLA ST.8314U

I am at present using a Stella model which has given me good service until recently, but is now giving trouble with the horizontal hold. The setting of control is critical and has to be reset frequently during the programme. The valves ECL80 and PL81 have been tested and found up to standard. Can you please inform me where I may locate the trouble? I have a service sheet for the above model.—H. Philips (Stapleton).

Re maker's service sheet: check V8, R52 and C62. If these parts are in good condition, the trouble is sometimes caused by poor insulation in the line oscillator transformer (S30-S31-S37).

EKCOVISION 231

When first switched on the picture will fail to appear for perhaps 10 minutes; at other times it will appear after normal warming up period, but the screen will suddenly become blank after a few minutes, the picture reappearing just as suddenly after another few minutes. The set has given seven months' trouble-free service, and is normal in every other respect.—G. B. Spackman (Byfleet).

Check for EHT when the trouble next occurs. If this is missing during the time when the screen is blank suspect (a) the EHT rectifier, (b) the reclaim diode, (b) the line amplifier valve, (c) the line oscillator valve, in that order. If EHT is present check the tube feed circuits and the tube itself for an internal short.

EKCO T217

I am wanting to change my TV set from the Holm Moss frequency to which it is at present tuned to Pontop Pike frequency. Could you give me the necessary information on which controls to adjust? I assume there will be the aerial H.F. and osc. tuning to adjust.—A. Palfreeman (Hurworth).

Looking at the chassis from the rear of the cabinet, you will observe four adjustments coloured red, black, yellow and green on the top of four coils situated in the near right-hand corner of the chassis. These controls correspond to the R.F., mixer input, oscillator and aerial coils respectively. The oscillator should be adjusted for maximum sound and the other circuits followed up for maximum sound and vision. The oscillator should finally be re-set for maximum sound consistent with minimum sound on vision.

REGENTONE BIG 12

I should be glad if you would help me diagnose a fault to Regentone Big 12B. The set has been going well for a number of years but has just recently developed sound distortion, but does not lack volume.—G. Rogerson (Liverpool, 7).

Check the value of the 1 megohm resistor from the anode (pin 7) of the noise limiter diode (20D1) to the H.T. circuit. You will probably find that this is up in value.

MURPHY V150

I have a Murphy V150 which has been giving very inferior results since the change-over of the BBC London transmitter.

I have a circuit diagram and I shall be pleased to know:

Should I remove R10 33 K Ω shown across L8 and marked London only?

Which coils should be re-trimmed in the vision circuit?

What is the reason for L14?

This is shown completely disconnected in the diagram.—E. Metcalfe (W.9).

The disconnected coil is for use when the channel is changed for use in the Midlands (Channel 4). Your receiver is suitable for single sideband operation. To get best results from the new transmitter you may find it necessary to re-orient the aerial and possibly fit an attenuator in the aerial lead. The set cannot be aligned without the use of special test equipment.

AERIAL MOUNTING

On some TV aerial masts the I.T.A. aerial is secured to the BBC mast, whilst with others arms are used to throw the I.T.A. aerial away from the BBC aerial.

Is there any reason for fitting these arms, please?—P. Humphreys (Holyhead).

Interaction inevitably occurs between two aerials mounted in close proximity. It is best, where possible, to employ a "bent" mast to keep the Band III array away from the Band I array when the existing BBC mast is used to secure both arrays.

BAND I ATTENUATION

When receiving I.T.A. on my home-constructed converter, I am troubled with considerable patterning due to BBC break-through.

By removing the Band I aerial I can diminish this

somewhat. I can then receive a reasonably clear picture by suitably arranging and positioning the Band III aerial down lead.

This, not always being convenient, I wonder if you could describe a suitable wavetrapp for I.T.A. and perhaps an attenuator for BBC signals if you think this would cure the trouble.—L. A. Winnot (N.W.10).

Connect the converter to the receiver through a 66in. length of close-woven low-loss coaxial feeder. This will attenuate the BBC signal in relation to the I.T.A.

FERGUSON 988T

Could you please inform me of any modifications needed to the Ferguson 988T for Band III reception, using the October blueprint converter, as I have just completed this but cannot get any results.

The converter is using own power pack with approximately 160 volts. H.T.

No modifications have been made to the 988T.—G. W. Allinson (Manchester).

It is not necessary to alter the receiver in any way. Check the wiring of the converter, and ascertain that it is correctly aligned as detailed in the article to which you refer.

ENGLISH ELECTRIC 1550M

I am using an English Electric model 1550M TV and convert to I.T.A. with a Wolsey converter tuned to the Lichfield transmitter.

Reception has been quite good, but since the opening of the northern I.T.A. transmitter I am suffering from fairly heavy patterning.

It appears that the source of the interference is from the new transmitter as I have one or two friends who are experiencing the same trouble.

I would appreciate any help you may give to eliminate this trouble.—W. R. E. (Stoke-on-Trent).

The interference may indicate that the Channel 9 signal is stronger than the Channel 8, and by tuning the converter to Channel 9 and reorientating the aerial, complete freedom from interference may result. Even if the signal strength of the northern transmitter is not so high, it does not necessarily follow that interference from Channel 8 will be worse since it may be a matter of frequency beating which is causing the trouble.

FERRANTI T138M

Fault: Sound on vision (distortion of picture only). On turning up contrast control, this causes an increase of sound just the same as increasing the volume control.

—J. S. (Wigan).

Viewing the receiver from the rear; on the top (R.F.) chassis, on the left side, will be found two concentric trimmers of the "beehive" type. The lower one should remove the sound on vision upon rotating one way or the other. Hand capacity effects may be noted whilst adjustments are being made. If no amount of adjustment improves the situation, check the upper trimmer and then suspect an open-circuited capacitor beneath the power pack.

REFRESHER COURSE IN MATHEMATICS

8/6, by post 8/10. 4th Edition.

By F. J. CAMM

From: GEORGE NEWNES, LTD.

Tower House, Southampton Street, Strand, W.C.2

VIBRAPACKS, Mallory, 12 v, D.C., to 250v, 80ma, synch., reversible, new, 18/6; Jefferson/Travers, synch., 12v, D.C., to 150v, 40ma, smoothed, 18/- (post each 2/9). Dynamotors, D.C., 5v to 250v, 80ma output, 11/6; Filters, H.T./L.T. 2/6 (post. 2/9); T.C.S.-12, D.C., 12 or 24v to 225v, 100ma and 440v, 200ma, 52/6 delivered. RX161, 160/220 mc/s with 1/VR137, 2/VR136, 1/CV66, 17/6; I.F. Amplifier 178 (for this), 13/0 mc/s, with valves, 17/6 (postage 2/9 each). R1355, new improved type, 37/6 (carr. 7/6). Condensers, Bak. tubular, 0.1/1.2 kv, 5/800v, 25/800v, 9d. each; .032/5 kv, .05/3.5 kvw, .25/1.5 kvw, 1/- each; 1/2 kw Block, 2/6. Responder RDP1, new, 160/220 mc/s, 12 valves, 15/- (carr. 8/6) or ZC8931, 9 valves, 25/- (carr. 6/-). Relays, 6v, 2 break, 1/6. R1355 I.F. Strips only, complete, new, with valves, 25/-, less -valves, 12/6 (post 2/6). Brand new R.F. Units, Types 26 or 27, 27/6 (postage 2/9); R.F.24, R.F.25, soiled, 10/6. I.F.T.s 10/13 mc/s, canned, new, 1/3. Closed 29th July-6th Aug. List and enquiries. S.A.E. please! Terms: C.W.O., postage extra. Immediate despatch. W. A. BENSON (P.T.), 308, Rathbone Rd., Liverpool, 13.

SERVICE SHEETS, T.V. and Radio, over 2,000 models, sale or hire. Valves and Components, S.A.E. with enquiries. W. J. GILBERT, 24, Frithville Gardens, London, W.12.

B.S.R. MONARCH 3-speed auto-change units; new in maker's sealed carton; guarantee; complete with instructions, template, suspension springs, 29/15/1, carriage paid; immediate delivery. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

TELEVISION, 9in. models, 26/10/-; 12in. models, 25/15; all makes; working; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

GUARANTEED TELEVISION, 12in. models, first-class picture, 5-channel, 230 each, carriage paid. THE GRAMOPHONE SHOP, 19-21, Brockley Rise, Forest Hill, S.E.23.

DIRECT T/V REPLACEMENTS offer the most complete Handbook of T/V Components and Rewinds, price 1/-; T/V Components for all kit sets in stock. "Nuray" heater booster isolator for 2-volt C.R.T.s, just plugs in, 27/6, plus 2/- packing and postage. 134-136, Lewisham Way, S.E.14. (TIDeway 3696-2330.)

SUPER-TONIC SUN-RAY LAMPS. Ultra-violet Infra-red combined. Superb therapeutic quality, controlled output, automatic exposure. All mains. Listed 27/10/-, our price 80/-, S.A.E. illustrated brochure. Dept. 16, SCIENTIFIC PRODUCTS, Cleveleys, Lancs.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

SERVICE SHEETS and Manuals for sale or hire; several thousands in stock. Stamp with enquiries. M. FOY, 6, Wykebeck Gardens, Leeds, 9.

TELEVISION INTERFERENCE. Receiver Filters, High-Pass E.5037, 30/-; Low-Pass E.5031, 30/-; Composite Band I/III, 49/6; Transmitter Filter E.5043-80dB, 1kw, 26. LABGEAR (CAMBRIDGE) LTD., Willow Place, Cambridge.

MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or, in fact, anything that needs lenses. Then get our booklets "How to Use Ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive list of lenses, optical Radio and scientific gear free for s.a.e. H. W. ENGLISH, Rayleigh Road, Hutton, Brentwood, Essex.

EDISWAN 12H "static 12in. Tube, no burns; with mask, base and 4 kv. E.H.T. Trans., 23/10, o.n.o. "Colwyn," Gasden Lane, Witley, Surrey.

ALL TYPES OF VALVES REQUIRED for cash. State quantity and condition. RADIO FACILITIES LTD., 36, Chalcot Road, N.W.1. (PRIMrose 909.)

SURPLUS TO REQUIREMENTS, 20 only, London Service Area Band III Converters, B.B.C. and 3 Pre-set Band III Positions by leading manufacturer, 27/10/- each, carriage paid. D. J. CLARKE (BIGGLESWADE) LTD., 37, Hitchen Street, Biggleswade, Beds. (Phone: Biggleswade 2377.)

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

TELEVISION AND RADIO BARGAINS—12in. 5 Channel, 218/10/-; 12in. London Station, 212/10/-; 9in. London Station, 27/10/-, All guaranteed. Phone LAD 1734, call 1070, Harrow Rd., N.W.10.

FOR SALE, brand new 5-element Channel, 8 and 9 aeriels, with mast etc. to fix to existing aerial, 39/6. (List 52/6.) Indoor model, universal fixing, 39/-. Special price for doz. or over. Send P.O. 1/- for our illustrated lists of Aerial Parts, Data, etc. Amazing value. Full guarantee. SKYLINE WORKS, Burnshall Rd., Coventry. (Tel.: 60418.)

SEVERAL EARLY MODELS 9in. Television, complete, and mostly working, 25/5/- each; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

SITUATIONS VACANT

HEARING AID Service Mechanics reqd. at once. Knowledge of L.F. amplification and miniature circuits essential. Interesting work, good wages and conditions. Apply Box No. 186, c/o PRACTICAL TELEVISION, or phone W. J. S., Welbeck 8247.

WANTED, Valves 6F13, 6P15, 6U4, EY51, 5Z4, ECL80, KT61, 25A6, etc.; prompt cash. WM. CARVIS LTD., 103, North Street, Leeds, 7.

ALL TYPES of new radio valves wanted, small or large quantities; cash payment. R. H. S. LTD. (T), 155, Swan Arcade, Bradford, 1.

EDUCATIONAL

BUILD YOUR OWN TV and learn about its operation, maintenance and servicing. Qualified engineer-tutor available while you are learning and building. Free brochure from E.M.I. INSTITUTES, Dept. P.T.58, London, W.4. (Associated with H.M.V.)

I.P.R.E. Data for constructing TV Aerial-strength Meter, 7/6; 5,500 Alignment Peaks for superhets, 5/0; sample copy "Practical Radio Engineer," 2/-. Membership-examination particulars, 1/-. Syllabus of seven postal courses free and post free SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B. and other professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to E.M.I. INSTITUTES, Dept. P.T.28, London, W.4.

COVENTRY TECHNICAL COLLEGE. Session 1956-57. Electronic Engineering. Applications invited for entry to next 3-year full-time course commencing September, 1956, from those requiring comprehensive training to an advanced level in Electronic Engineering, qualifying for posts in Radio, Telecommunications, Television and Industrial Electronics. Syllabus will cover requirements of C and G, Brit.I.E.E., and I.E.E. examinations. Entry age 16 or over. Application forms and further information from Principal, Coventry Technical College. W. L. CHINN, Director of Education.

DISC CERAMIC CAPACITORS

The modern decoupling capacitor. Midget size, non-inductive with excellent dielectric insulation. Ideal for T.V., etc. 500 v, D.C. (300 v. A.C.) working: 470 pF., .001 μF., 5/16in. dia., .002 μF., .003 μF., 1/2 in. dia., .005 μF., 3/4 in. dia. Each 9d. Minimum postage 6d. on orders under £2.


SOUTHERN RADIO & ELECTRICAL SUPPLIES
SORAD WORKS, REDLYNCH SALISBURY
Telephone: Downton 207

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP, WIRE, ANGLE, CHANNEL, TEE
3000 STANDARD STOCK SIZES

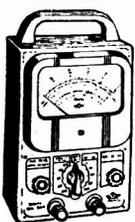H. ROLLET & CO., LTD.
6, CHESHAM PLACE, LONDON, S.W.1
SLOane 3463

Works:
36, ROSEBURY AVE., LONDON, E.C.1.
Branches at Liverpool, Manchester, Birmingham, Leeds.
"No Quantity too Small"



PULLIN
SERIES 100
TEST METER

AC/DC 10,000 n/v
21 RANGES
100μA to 1000V

COMPLETE IN DIE-CAST CASE WITH TEST LEADS CLIPS AND PRODS FULLY GUARANTEED

SENT POST FREE FOR £2.10s. DEPOSIT AND ELEVEN FURTHER MONTHLY PAYMENTS OF £1.4s. CASH PRICE £12.7s

FRITH RADIOCRAFT LTD

69-71 CHURCHGATE
LONDON E.C.4
PHONE 5927

28 HIGH STREET
NEWPORT PAVILLION
BUCKS. PHONE 237

THE VALVE SPECIALISTS

Bentley Acoustic Corp. Ltd.

38, CHALCOT ROAD N.W.1
PRImrose 9090

1st grade goods only. No seconds or rejects.

0Z4	6/-	68L7	8/-	1203	7/-	HL2	3/-
1A3	6/-	68N7	8/-	5783	12/6	HL13C	7/6
1A5	6/-	68P7	7/6	7493	2/6	HLS	10/6
1D6	8/6	6U7	8/6	7473	5/6	HL41	7/6
1H3	11/-	6V6G	7/-	9002	5/6	HL41DD	7/6
1L4	7/6	6V6GT	7/6	9005	5/6		12/6
1LD5	5/-	6X4	7/6	9006	7/6	HVR2A	7/-
1LN5	5/-	6X5	7/6	AC/BL		KBC32	8/6
1N5	11/-	6Z4/84	12/6	DD3	15/-	KC32	9/-
1R5	9/-	6Z5	12/6	AC/Pen	6/6	KL35	8/6
1R5	7/6	7A7	12/6	AC/P4	8/-	KT2	5/6
1T4	7/6	7B7	8/6	AC/VP112	6/6	KT33C	10/-
1U5	7/6	7C5	8/-	AP4	7/6	KTW61	7/-
2A3	12/6	7C5	8/-	ATP4	8/6	KTW62	7/-
2C26	4/-	7H7	8/-	AZ31	10/6	KTZ67	6/6
2D13C	7/6	7Q7	8/-	BS19	12/6	KTZ63	6/6
2X2	4/6	7T7	9/6	BL63	7/6	L43	6/-
3A4	7/6	7V7	8/6	CK523	6/6	LN309	12/6
3A5	8/6	7Y4	8/6	CK525	6/6	LZ319	12/6
3B7	8/6	8A8	8/6	CV85	12/6	MY4	5/6
3D6	2/6	8D2	2/6	D1	8/6	MHL4	7/6
3Q5	9/6	9D2	3/-	D43	5/-	M84B	15/-
3P4	7/6	10C2	10/6	DAF96	9/6	MU12	8/6
3V4	8/6	10D1	7/6	DCC90	8/6	OC3	9/-
5V4	10/-	10P1	11/-	DP96	9/6	OD3	9/-
6A3	10/-	12A3	10/6	ED2	8/6	PA	10/6
5Y3	8/-	12A8	15/-	DK96	9/6	PABC80	
5Y4	10/-	12AH7	12/6	DL2	15/-		15/-
5Z3	8/6	12AH8	12/6	DL33	11/-	PCC84	9/-
5Z4	8/6	12AT7	9/6	DL96	9/6	PCC85	12/6
6A8	9/6	12AU7	8/-	DL510	10/6	PCF90	9/6
6AB7	9/6	12AX7	10/6	E144	15/-	PCF92	11/6
6AB8	11/-	12BA6	9/-	EA50	2/6	PCL83	12/6
6AC7	6/6	12BE6	10/-	EABCO8	8/6	Pen25	6/6
6AG5	6/6	12E1	20/-	EAF42	12/6	Pen48	8/6
6AG7	12/6	12H6	6/-	EH34	2/-	PI81	12/6
6AJ9	10/-	12J5GT	6/6	EH3	8/6	PI82	10/6
6AK3	6/6	12J7	9/6	EB91	6/6	PI83	12/6
6AK8	10/-	12K7	9/6	EBC3	12/6	PM12	4/-
6AL5	6/6	12SA7	8/6	EBC33	7/6	PM12M	6/6
6AM5	4/6	12SC7	7/6	EBC41	10/-	PM2B	12/6
6AQ5	7/6	12SGT	7/6	EBF80	10/-	PM202	4/6
6AC8	6/6	12SH7	6/6	ECC3	8/6	PF30	10/6
6AT6	8/6	12S7	8/-	EC54	8/-	PY81	10/-
6B4	6/-	12SK7	6/6	ECC32	10/6	PY82	10/-
6B7	10/6	12SQT	8/6	ECC33	8/6	PY83	10/-
6BA6	7/6	12SR7	7/6	ECC35	8/6	QP21	7/-
6B8G	4/-	12U5G	7/6	ECC40	15/-	QP22B	12/6
6B9	4/6	12Y4	10/6	EC90	8/6	Q8150/15	9/6
6BE6	8/-	138PA	10/6	ECC82	10/6	Q8150/15	9/6
6BG6	12/6	13VPA	10/6	ECC88	10/6		10/6
6BJ6	8/-	14B7	10/6	ECC84	12/6	SD6	7/6
6BW6	8/6	16A5	10/-	ECC85	10/-	SP2(7)	8/6
6BW7	10/-	19B1	10/-	ECC91	6/-	SP4(7)	12/6
6C48	6/6	20P1	12/6	ECC90	14/6	SP8	15/6
6BY7	10/-	20P3	12/6	ECC82	15/-	TD2A	8/6
6C4	7/-	25Z4	9/-	ECH85	11/6	TE233	12/6
6C6	6/6	25Z5	8/6	ECH42	10/6	TP22	10/6
6C8	8/-	27	7/6	ECH81	9/-	U16	12/-
6CH6	9/6	25D7	7/6	ECL80	11/-	U17	12/6
6D8	6/6	30	7/6	EP8	10/6	U22	7/6
6F1	12/6	30C1	12/6	EP9	12/6	U25	15/-
6P6G	7/6	30L1	12/6	EP36	4/6	U30	8/-
6P7	10/6	31	7/6	EC37A	10/-	U32	8/-
6P8	10/6	35L6	8/-	EP39	6/-	U35	12/6
6P13	12/6	35Z4	8/6	EP40	17/-	U329	10/6
6P15	12/6	35Z5	8/6	EP41	9/6	UAF42	11/-
6P17	12/6	35/51	12/6	EP42	12/6	UBC41	10/6
6P32	12/6	41MP	12/6	EP30(A)	7/-	UCH42	11/-
6P33	12/6	41MTL	7/6	EP30(B)	8/-	UF41	10/6
6R6	6/6	40Z5	12/6	EP53	5/-	UF42	12/6
6R6G	2/6	50C3	10/-	EP30	10/6	UL1	11/6
6H6M	2/6	50L6	8/6	EP35	9/-	UL46	11/6
6J5G	5/-	57	8/6	EP36	12/6	UY41	10/6
6J5GT	5/6	58	8/6	EP39	10/-	VL607	5/6
6J6	6/-	61B7	12/6	EP91	9/-	VL8402A	25/-
6J7G	6/-	61BP	10/6	EZ80	8/6	VM545	15/-
6K5	7/6	61PT	7/6	EP32	12/6	VP2(7)	8/6
6K7G	6/-	72	6/6	EP41	10/6	VP4(7)	12/6
6K8G	8/-	76	7/-	EL42	13/-	VP23	8/6
6K8GT	8/6	77	8/-	EL81	12/6	VP41	7/6
6L6G	9/-	78	8/6	EL34	11/-	VP133	10/6
6L7	7/6	80	8/6	EM34	10/-	VS01	4/-
6N7	7/6	83	8/6	EV31	11/6	X66	10/6
6Q7	8/6	150B2	12/6	EY86	12/-	XFW10	6/6
6Q7GT	9/-	210LF	3/-	EZ40	8/-	XPY12	8/6
6R7	8/6	240QP	10/6	EZ41	11/-	XH(1.5)	4/-
6BA7	8/6	307	8/6	EZ80	8/6	XG1.5	4/-
6B6	6/6	308	8/6	EL13	12/6	Y33	10/6
6B7	6/-	366A	12/6	H30	5/-	Y65	10/6
6B7	8/-	385	10/6	H63	12/6	EZ77	9/-
6BK7	5/6	956	3/-	HK90	10/-	Z719	10/6

Closed for annual holidays July 30-August 11 inclusive.
All boxed. Full maker's guarantee. Post 6d. each. Insurance (optional) 6d. per order. Shop hours 8.30 to 5.30, Sats. 1 p.m. Why not 'phone or wire that urgent order for immediate despatch C.O.D.? List and conditions of sale S.A.E.

"VIEWMASTER"

T.V. TUNER COMPONENTS

- 6 wafer Switch assembly ... 20/-
- Fine Tuner ... 4/-
- 3 Coil platforms ... 1/-
- Set of three metal brackets... 7/6
- Screen complete ... 5/-

All prices include postage

Send for complete list of radio and T.V. components. POST FREE.

Components for the ARGONAUT A.M./F.M. RECEIVER available from stock.

AUDIO LTD.,
Tower Road, London, N.W.10.

OPPORTUNITIES IN TELEVISION

144 pages
Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M. Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

We Guarantee "NO PASS-NO FEE"

If you are earning less than £15 a week you must read this enlightening book.

Send for your copy NOW-FREE and without obligation.

WRITE TODAY!

British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane,
Kensington, W.8. **BIET**



THE SPENCER - WEST PATTERNING REMOVAL UNIT TYPE 54

works with any Band III convertor unit and completely removes patterning caused by Band I breakthrough. Results are guaranteed.

PRICE 25/- Complete

Full instructions for simple fitting supplied. We will send a unit on approval for 7 days against cash on receipt of order, or from your Dealer.

SPENCER - WEST LTD.
QUAY WORKS
GT. YARMOUTH

Phones : 4794 and 3009
Grams : Spencer-West, Great Yarmouth

WHY WASTE TIME

Give that set its best chance
FIT QUALITY COMPONENTS
Catalogue 1/-.

Parts for the following :-

- Manual
- Osram "912" plus Amplifier 4/-
- Mullard 10-watt Amplifier 3/6
- The Coventry
- 2-watt Amplifier ...
- 4-watt Amplifier ... 1/-
- 6-watt Quality Amplifier ...
- The Coventry A.M. Tuner
- Unit 1/-
- Denco F.M. Tuner Unit ... 1/6

Complete Component Price Lists will be supplied with each Manual.

COVENTRY RADIO
EST. 1925

189, DUNSTABLE ROAD,
LUTON, BEDS.
Phone : Luton 2677

News From the Trade

AERIALITE TWIN BAND AERIAL MODEL 805

IT has been found possible to reduce the price of this aerial by 7s. 6d., so that it is now £7 5s. 0d. retail. Model 805 incorporates a dipole and reflector for Band I reception, with a five-element Band III array placed in broadside. The Band III section can be rotated to give different directivity from that of the Band I section.—Aerialite, Ltd., Castle Works, Stalybridge, Cheshire.




frequency modulator or sweep generator, switchover from internal to external synchronisation being effected by inserting a plug in the appropriate socket.

The cathode ray tube has symmetrical deflection characteristics. Its diameter is 7 cms. (2½ in.), and a measuring lattice and shield to cut out incident light are provided. Measuring 4½ in. wide by 9½ in. high by 12½ in. deep (approximately), the GM5650 weighs only 17 lbs.

SPENCER-WEST ATTENUATOR

A NEW type of variable plug-in attenuator is now available from Spencer-West. It is designated type 60. The attenuator is continuously variable from 6dbs to at least 36dbs. Full matching is maintained at all settings and a lockable type control is fitted. This attenuator is based on a new circuit arrangement which ensures that no frequency selective circuits likely to spoil the picture quality are present. It is priced at 12s. 6d.—Spencer-West, Ltd., Quay Works, North Quay, Great Yarmouth, Norfolk.

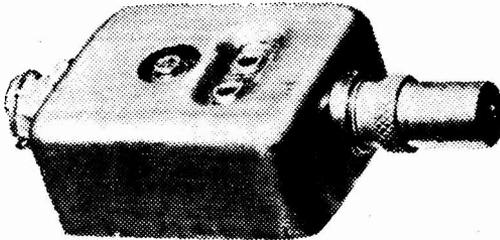

The new type 60 Spencer-West attenuator.

PHILIPS NEW OSCILLOSCOPE FOR TV SERVICING

SMALL and light, the type GM5650 D.C. coupled oscilloscope recently introduced by Philips Electrical, Ltd., has been designed primarily for the radio and television engineer.

The vertical amplifier provides a wide band width from D.C. up to approximately 10 Mc/s with normal sensitivity of 100 mV rms/cm. or a narrow band width from D.C. to 1 Mc/s with high sensitivity of 10 mV rms/cm.

The timebase generator can be used free-running or triggered, and covers eight ranges from 10 c/s to 300 kc/s. Pulses of short duration can be produced satisfactorily up to a maximum speed of 0.5 μsec/cm.

Input impedances are :

Via step attenuator, 1 MΩ and 50 pF.

Via fixed attenuator, 1 MΩ and 15 pF.

Via probe, 1 MΩ and 15 pF.

A saw tooth voltage is provided for connecting to a

NEW STELLA TELEVISION RECEIVER

A NEW 14in. table television receiver (Model ST8514U), selling at 63 gns. (list £47 2s. 1d., plus P.T. £19 0s. 11d.), is announced by Stella Radio and Television Co., Ltd.

Incorporating automatic gain control on sound and vision, this new receiver gives a picture size of 11½ in. by 8½ in. and is suitable for operation on 200 to 250 volts A.C. (50 c/s) or D.C. Power consumption is 150 watts. It is fitted with an all-programme turret tuner for BBC and I.T.A. (Band I and III Channels 1-5, 8-10.)

The cabinet is in natural walnut veneer with a Tygan covered loudspeaker baffle. Volume/on/off, brightness, station selector and fine tuning controls are mounted at the front of the cabinet, as is the loudspeaker. Dimensions : height, 19½ in. ; width, 17 in. ; depth, 15½ in. Valve line-up : PCC84, PCF80, EF80 (4), EBF80, ECL80 (3), EB91, PL81, PY81, PY32, EY51, OA70 (crystal diode). Cathode ray tube MW36/24.

POLYSTYRENE FOR TV AERIALS

TERMINAL boxes and dipole insulators for television aerials produced by Labgear (Cambridge), Ltd., are injection moulded in high-impact polystyrene.

Moulded for Labgear by the Plastics Division of the Mentmore Manufacturing Co., Ltd., the insulator has a screw-down panel for easy access to connections. Both the panel and the detachable polythene bushes are tight-locking to prevent moisture infiltration. Holes in the base allow the aerial lead to be fixed by a self-tapping screw.

The terminal box is moulded with a snap-fitting lid and depressed cavities in the base. These can be easily cut to allow for variations in fitting.

NATIONAL RADIO SHOW

Practical Television Stand No. 111

QUERIES COUPON

This coupon is available until AUGUST 21st, 1956, and must accompany all Queries.

PRACTICAL TELEVISION, AUGUST, 1956.

BAND III AERIALS OR FITTINGS

Whether you are contemplating the construction of a Band III aerial or purchasing one complete it will be well worth your while to write to us who, as manufacturers, can offer you real

VALUE FOR MONEY

THE FOLLOWING IS A CROSS SECTION OF ITEMS TAKEN FROM OUR NEW COMPREHENSIVE CATALOGUE.

- * 10 Element Band III Aerial, 77/6.
- * 8 Element Band III Aerial, 62/6.
- * 6 Element Band III Aerial, 47/6.

FITTINGS

- * Universal Band III Clamp-on Fitting.
- * Band III Insulator, complete with folded dipole.
- * Director and Reflector Rod Holders for Bands I, II, and III.
- * Straight and Cranked Masts (all sizes).
- * Chimney and Wall Brackets. Alloy Tubing, etc. etc.

Send I/- P.O. for the NEW MULTI-PAGE illustrated Catalogue (together with element and boom measurements (all Bands) to help the constructor) to:

FRINGEVISION LTD. MARLBOROUGH WILTS.
Phone 657/8

VIEW MASTER CONVERTER

All items for the View Master Converter as described in "Practical Television" can be supplied from stock. Full details are given in our special list which is available free upon request.

COIL SET AND METAL PARTS. Denco. Includes a ready wound set of coils, switch screens and metal cover, 30/-.

SWITCH ASSEMBLY. Denco. Complete switch with fine tuner, and coil platforms, 27/-.

CONDENSER AND PRINTED CIRCUIT KIT. T.C.C. Contains all the condensers, printed circuit and valve holders, 43/-.

RESISTOR KIT. We make up this kit with the specified LAB resistors. All labelled with value and position, 8/-.

GAIN CONTROLS. Colvern CLR901 5,000 ohms. Three required, 3/3 each. Panel for mounting three controls, 1/-.

VALVE SCREENS. Carr Fastner. Skirt and screen. Two required, 1/3 each.

CO-AXIAL PLUG AND SOCKET. Belling Lee. L604S Socket. 1/3. L734P Plug, 1/3.

SOLDER. Erskin Multicore. Special for printed circuits, 2/6.

VALVES. Mullard PCC84 24/4. Surplus 13/6.

Mullard PCF80 23/9. Surplus 13/6.

KNOB. Pointed knob for switch, 1/-.

SUNDRIES KIT. Contains all nuts and bolts, flex, wire co-axial cable, copper foil and spring wire, 8/-.

COMPLETE KITS. All above items supplied at one time.

KIT A. With new Mullard valves. £9.4.0. Credit Terms: Deposit £1.6.9 and seven monthly payments of £1.6.9.

KIT B. With surplus valves. £8.2.0. Credit Terms: Deposit £1.4.0 and seven monthly payments of £1.4.0.

PLEASE NOTE. These kits do not include the items needed for conversion of the View Master Sound/Vision Chassis. We can supply the chassis conversion kit for £2.0.0. Full details in our list.

SET OF TWIST DRILLS. Complete set of the correct size twist drill for drilling the Printed Circuit Panel, 10/-.

WATTS RADIO

8 Apple Market, Kingston-on-Thames, Surrey.
Telephone: KINGSTON 4099.

NEW-MAX ELECTRONICS LTD.

220, Edgware Rd., London, W.2
Tel. PAD. 5607

Come and visit us. The largest Electronic Bargains Store in London. We have 500 Repossessed T.V.'s, all sizes always in stock, also Radio Sets, Radiograms, Reclaimed and guaranteed C.R. Tubes, 12in. £5, 14in. £6 10/-, 15in. £7 10/-, 17in. £9 10/-, p. and p. 10/-; Tubes with Heater Cathode Short, 14in. £3 10/-, 15in. £4 10/-, 17in. £5/-, p. and p. 10/-; Surplus Valves, Components and Test Equipment, etc., etc. Also available all types and makes of new C.R. Tubes at list prices. Part exchanges welcomed!

SPECIAL OFFER

Projection T.V. Unit. Complete optical projection box with focus and frame coil, usual cost £30 our price £6 -- incl. p. and p. Any set can be converted to large screen T.V. with this unit by increasing E.H.T. (to approx. 15-20 kV).

TELEVISION COMPONENTS

in stock for the

P.T. SUPER-VISOR, TELE-KING, VIEWMASTER, E.E. TELEVISOR and BAND III and wide angle modifications

Price lists available on request to:

J. T. FILMER, Maypole Estate, Bexley, Kent.
Tel.: Bexleyheath 7267

VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

1.4v. midget, 1R5	1S5	1U5	1T4	3S4	DAF91
DF91	DK91	DL32	DL91	any 4 for 27/-	
1A7GT12/6	6U4GT15	DH77	8/6	EZ40	8/6
1CSGT11	6V6C	7/6	DK32	12/6	GZ32
1D5	11	6V6GT	7/6	DK92	7/6
1H5GT	6X4	7/6	DK96	9/6	7/-
1N5GT	11/6	6X5GT	6/9	DL33	11/6
		7B7	8/6	DL35	11/-
1R5	11/6	7C5	9/6	DL36	9/6
1S5	8/6	7C6	8/6	EB91	8/6
1T4	7/3	7H7	7/6	EB33	7/6
1U5	7/3	7S7	9/6	EB41	10/-
3A5	7/6	7Y4	8/6	EBF80	11/6
3Q9GT11/6	10C1	13/6		ECC40	13/6
3S4	7/6	10F1	10/-	ECC81	10/-
3V4	8/6	10LD11		ECC83	10/6
5U4G	8/6	10/6		ECC91	6/-
5Y3GT	7/9	12A7	8/9	ECF80	PL82
5Z4G	9/-	12AU7	8/6	EW13	PL83
6AK5	5/-	12J7GT		ECH35	PL89
6AL5	6/9		9/6	ECH42	PL82
6AM6	7/6	12K7GT	9/6		PL82
6AQ5	7/6	12K8GT			PL82
6AT6	8/6	12/6		ECH81	9/6
6BA6	7/9	12Q7GT		ECL80	10/-
6BE6	7/6	9/6		EP37A	U25
6BW6	7/9	14S7	15/6		U26
6C9	10/-	20L1	10/9	EF39	U50
6F6G	7/6	25L6GT	8/6	EF40	U78
6F13	13/6	25Z4G	9/6	EF41	UAF42
6F15	13/-	25L6GT	9/6	EF42	11/9
6J6	6/-	35Z4GT	8/6	EF50	UBC41
6J7G	7/6	35Z5GT	9/6	EF80	9/6
6K7C	6/-	60L6GT	8/9	EF85	9/6
6K7GT	6/-	AZ1	11/6	EP86	9/6
6K8G	8/6	CCH35	11/6	EP91	9/6
6K9CT	9/6	D15	7/-	EP92	7/6
6L18	10/6	DAC321	11/6	EL32	6/6
6LD20	9/6	DAF96	9/6	EL41	10/6
6Q7GT	9/6	DCC90	7/6	EL84	11/6
6SN7GT	9/6	DF33	11/6	EM34	10/6
		DF96	9/6	EX31	11/6
				Z77	7/6

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587



QUALITY TELEVISION COMPONENTS

SCANNING COILS, 6/10 kV. R.F., E.H.T. UNITS, E.H.T. and OUTPUT TRANSFORMERS, LINE FLY-BACK E.H.T. UNITS.

Write for illustrated list (Publication 75)

Coil Kit of two for Aug. "P.T." Band III Converter 5/-, Kit for 7/6, Kit of four for October Band III Converter 6/-.

HAYNES RADIO Ltd.,

Queensway, Enfield, Middlesex.

BAND III CONVERTORS OSMOR

LONDON and MIDLANDS. Simple, efficient. Guaranteed No Break Through or Re-Radiation. For any TV, including T.R.F. Complete Kit, £3.5.0. Ready wired, 24.

TELETRON
Mk. I Coil Sets, 15/- Complete Kit, £2.10.0. Mk. II Cascade Coil Sets, 17/6. Complete Kit, £3. All above post free.
THE ELECTRONIC SUPPLY CO.,
29, Leigh Rd., Highbury, London, N.5.

TELEVISION TUBES

MULLARD ...	12in. £6.10.0	14in. £7.10.0	17in. £10.0.0	} Ex Stock
COSSOR ...	12in. £6.10.0	14in. £7.10.0	17in. £10.0.0	
EMITRON ...	12in. £6.10.0	14in. £7.10.0	17in. £10.0.0	

MAZDA. 12in. only £6.10.0. 4 Weeks Delivery.

All Tubes plus 12'6 carriage and insurance.

SIX MONTHS' GUARANTEE

Converter M.1. Midlands area, high gain, own power supply, built in crossover unit	£9.9.0
Converter M.2. Midland fringe area, own power supply	£9.18.0
Crossover Box. Low loss	12 6

Finished in Stove Enamelled Steel Case.

Terms to the Trade.

RE-VIEW (LONDON) LTD.

81, HIGH STREET

MERTON, S.W.19

Telephone : CHERRYWOOD 3255

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES AND C.R.T.s.

AVO METERS IN STOCK

Avo Model 7	—	—	—	£19 10 0
Avo Model 8	—	—	—	23 10 0
Electronic Test Unit	—	—	—	27 10 0
Electronic Test Meter	—	—	—	40 0 0
AC DC Minor	—	—	—	10 10 0
* Cossor Oscilloscopes Model 1052	—	—	—	104 0 0
" " " 1035	—	—	—	120 0 0

Full range Taylors Meters. List on request.

LEAK Pick-up Arm	—	—	—	2 15 0
		P.T.	...	1 3 1
.. Long Play or Standard Heads	With			
Diamond Stylus	—	—	—	5 15 0
		P.T.	...	2 8 4
.. Matching Transformer	—	—	—	1 15 0

Leaflets on Request

JASON AF/FM Tuner, complete with valves and automatic frequency control, also cascade input — — — — £28 13 0

LATEST VALVE MANUALS

MULLARD, 10 6, OSRAM & BRIMAR No. 6, 5/- each.
OSRAM Part 2, 10/-, Post 9d. each extra.
TRANSFORMER for 200/230 v., 37/6.

Terms C.O.D. OR CASH with order and subject to price alterations and being unsold

Arthur's

Est. 1919

PROPS: ARTHUR GRAY, LTD.

OUR ONLY ADDRESS: Gray House
150-152 Charing Cross Road, London W.C.2

TELEGRAMS: TEMPLE BAR 5833/4 and 4765
TELEGRAMS: TELEGRAY, WESTCENT, LONDON.
CABLES: TELEGRAY, LONDON.

LINE E.I.T. TRANSFORMERS REWOUND PROMPTLY

Our 30 years' experience of winding and wave-winding enables us to provide the finest service in the Country for all types of TELEVISION COMPONENTS. We repair or manufacture all types of transformers singly or in quantity, and welcome your enquiries.

H. W. FORREST
(TRANSFORMERS) LTD.

349 HASLUCKS GREEN ROAD, SHIRLEY,
BIRMINGHAM.

Telephone : SH1 2483

PREMIER RADIO COMPANY


OPEN TILL
6 P.M. SATURDAYS

Regd.) B. H. MORRIS & CO. (RADIO) LTD

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone :
AMBASSADOR 4033
PADDINGTON 3271

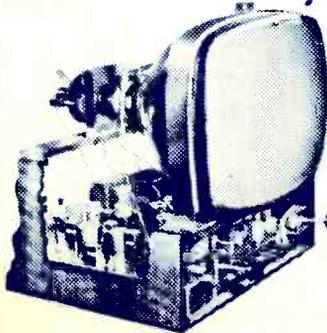★ **Band Three (Commercial)**
For the Home Constructor



Instruction Book 3/6. Post
F r e e. Includes details of
both designs.



The Televisor may be constructed in 5 easy stages : (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions. The Instruction Book also includes full details for converting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced.

THE NEW PREMIER TELEVISOR 13 CHANNEL DESIGN

SUITABLE FOR USE WITH ANY POPULAR WIDE ANGLE TUBE

DESIGN 1. Includes a Multi-Channel Tuner (Channels 1-13) continuously variable 40-100 Mc/s and 170-225 Mc/s. The Tuner is supplied wired and tested and is complete with Valves, all connecting leads and fixing brackets.

THIS DESIGN MAY BE BUILT FOR **£32. 7. 11** (plus cost of C.R.T.)

DESIGN 2. Channels 1-5, tunable from 40-68 Mc/s.

THIS DESIGN MAY BE BUILT FOR **£27. 9. 4** (plus cost of C.R.T.)

★ Constructors who have built Design 2 (5 Channels) may convert their Receivers to Design 1 for £6; this price includes Multi-Channel Tuner, New Vision Input Coil and full instructions.

★ All Coils supplied for these two Superhet Receivers are PRE-TUNED, ASSURING ACCURATE ALIGNMENT AND EXCELLENT BANDWIDTH.

★ Duomag permanent magnet focusing with simple picture centring adjustment.

★ Exceptionally good picture "hold" and interlace. ★ Noise suppression on both Sound and Vision

G.E.C. ALUMINISED C.R. TUBES



7203A. 14

The G.E.C. 14in. Cathode Ray Tube type 7203A has the following attractive features:—

- (1) Improved tube life and reliability.
- (2) A narrow beam angle triode gun giving:—
 - (a) Uniform focus over the entire screen area.
 - (b) Small spot size. (c) Freedom from astigmatism.
- (3) A high reflectance aluminium backing to the fluorescent screen giving:—
 - (a) 70% increase in picture brightness. (b) High contrast daylight viewing. (c) Complete elimination of ion burn from both positive and negative ions.

Price
£14. 15. 0
P.Tax £6. 18. 1

THE GENERAL ELECTRIC CO. LTD MAGNET HOUSE, KINGSWAY, LONDON W.C.2