

SUBSCRIPTION TV - PAY AS YOU VIEW

Practical Television 13

MARCH 1959

AND TELEVISION TIMES

EDITOR: F. J. GAMM



CONTENTS

A TV OSCILLOSCOPE
RELAXATION OSCILLATORS
REPLACING C.R. TUBES
SERVICING TV RECEIVERS
YOUR PROBLEMS SOLVED



Just Right for your pocket !

THE MULTIMINOR

19 Ranges

- D.C. Voltage:** 0-1,000V in 7 ranges
- A.C. Voltage:** 0-1,000V in 5 ranges
- D.C. Current :** 0-1A in 5 ranges
- Resistance :** 0-20,000 Ω , 0-2M Ω .

Pocket Size : 5 1/2 x 3 1/2 x 1 1/2 inches.
Weight : 1 lb. approx.

List Price **£9 : 10s.**

Complete with Test Leads and Clips.
Leather Case if required 32/6.

Sensitivity :
10,000 ohms per volt on D.C. voltage ranges.
1,000 ohms per volt on A.C. voltage ranges.

Accuracy :
On D.C. 3% of full scale value.
On A.C. 4% of full scale value.

To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge.

Telephone : VICTORIA 3404 (12 lines)

AVO LTD AVOCET HOUSE • 92-96 VAUXHALL BRIDGE RD. • LONDON • S.W.1

M.M.2

A NEW LEASE OF LIFE

FOR YOUR T.V. TUBE AND RESTORATION OF BRIGHTNESS

Pat. pending.
Reg. design.
B12A



PRICE **30/-**
Post, packing & ins. 2/6.

● NO SOLDERING ● NO WIRING ● JUST PLUG IN ● IT'S AUTOMATIC ● IT'S GUARANTEED!

Unlike valves, over 80% of T.V. tubes can be made to give extra useful life and service (for months and months or even years) with these amazing truly successful plug-in booster units. We can now offer these units for all makes of T.V. sets and tubes A.C. or A.C./D.C. when operating off A.C. mains.

Important. When ordering, please write name and address and make and model No. of set and tube in block capitals. Terms P.O. C.W.O. (C.O.D. charges 1/4 extra). Money refunded if returned in good condition within 7 days.

SINCLAIR ELECTRONICS,
Dept. PT.
18. NEWPORT COURT, CHARING CROSS ROAD, W.C.2.

TELEVISION TUBES REBUILT

12"	-	-	-	-	£6. 0.0
14"	-	-	-	-	£7. 0.0
17"	-	-	-	-	£7.10.0

Carriage and insurance 12/6 extra.

Customers are requested to send their old tubes for rebuilding. We offer 48 hr. service. All tubes are guaranteed for twelve months.

MARSHALLS for TELEVISION

131 St. Ann's Road, Tottenham, London, N.15.

Telephone: STAmford Hill 3267

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090.

EXPRESS SERVICE! C.O.D. ORDERS RECEIVED BY 3.30 P.M., EITHER BY LETTER, PHONE OR WIRE, DESPATCHED THE SAME AFTERNOON, ALL ORDERS RECEIVED BY FIRST POST DESPATCHED SAME DAY.

ANY ORDER UP TO £10 INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6d. EXTRA. ORDERS OVER £10 INSURED FREE.

0B2	17/6	5BX6	8/-	6V6G	7/-	19E6G6	7/45	7/6	DK92	10/6	EK32	8/6	KTZ41	8/-	PZ30	20/11	UCC85	10/6
0Z4	6/-	6C4	7/6	6V6GTG	8/-		9002	5/6	DK96	10/-	EL32	5/6	KTZ63	10/6	QP21	7/-	UCF80	23/-
IA3	3/-	6C5	6/6	6X4	7/-	19H11	10/9006	6/-	DL2	15/-	EL33	20/2	L63	6/-	QP25	15/-	UCH21	24/4
IA5	6/-	6C6	6/6	6X5GT	6/6	20E1	16/-	AC/PEN (5	DL33	9/6	EL34	17/6	LN152	14/-	QS150/15		UCH42	11/6
IA7GT	23/-	6C8	12/6	6Z4/84	12/6	20E2	27/10	or 7 pin) 24/4	DL66	15/-	EL38	27/10	LZ319	9/-			UCH81	11/6
ICS	12/6	6C9	12/6	6/30L2	10/-	20F2	27/10	AC2PEN	DL92	7/6	EL41	11/-	MH4	7/6	QV04/7	15/-	UCL82	15/6
ID5	17/5	6C10	12/6	7A7	12/6	20L1	27/10		DL94	9/-	EL42	11/6	MHD4	25/9	R2	10/-	UCL83	25/9
ID6	10/6	6CD6G	11/4	7B7	8/6	20P1	27/10	AC2PEN/	DL96	10/-	EL81	15/-	MHL4	7/6	R12	10/6	UF41	9/-
IH5GT	11/-	6CH6	32/5	7C5	8/-	20P3	24/4	DD 27/10	DL510	10/6	EL84	10/6	MHLD6	12/6	R18	17/6	UF42	19/6
IL4	6/6	6D3	20/11	7C6	8/-	20P4	27/10	AC4PEN	DM70	8/6	EL91	5/-	ML4	12/6	R19	25/11	UF80	10/6
ILD5	5/-	6D6	6/6	7D5	24/4	20P5	24/4		EA50	7/-	EL95	10/6	ML6	6/6	S6	12/7	UF85	10/6
ILN5	5/-	6E5	12/6	7H7	8/-	25A6G	20/2	AC5PEN	EA76	9/6	EM34	10/-	MPT4 (5 or		SP4(7)	15/-	UF86	24/4
INSGT	11/-	6F1	27/10	7R7	12/6	25L5GT	10/6		EAC80	9/6	EM71	24/4	7 pin) 24/4		SP41	3/6	UF89	10/6
IR5	8/-	6F6G	7/-	757	10/6	25Y5G	10/6	AC5PEN/	EAC91	7/6	EM80	10/6	MU14	10/6	SP42	12/6	UL41	10/6
IR5	8/-	6F6GTG	8/5	7Y7	8/6	25Y5G	10/6	DD 27/10	EAC92	10/6	EM81	10/6	MX40	27/10	SP61	3/6	UL44	27/10
IT4	6/6	6F8	12/5	7Y7	8/-	25Z5G	10/6	AC6PEN 7/5	EB34	2/6	EN31	34/9	N37	20/11	SU25	27/10	UL46	15/-
IU5	10/-	6F11	18/6	8D2	3/6	25Z4G	10/6	AC/HL/	EB41	8/6	EY51	10/6	N78	20/11	SU27	10/6	UL84	11/6
Z27	10/6	6F12	7/6	8D3	7/6	25Z5G	10/6	DDD 15/-	EB91	6/6	EY83	17/5	N108	19/6	T41	24/4	UM4	18/1
2C26	4/-	6F14	12/6	9D2	4/-	25Z5GT	17/5	AC/PA 8/-	EBC33	7/6	EY86	14/6	N108	27/10	TDD4	25/9	URIC	17/5
2D13C	7/6	6F14	27/10	10C1	15/-	27S1G	20/11	AC/TP 34/9	EBC41	10/-	EZ35	6/6	OA70	5/-	TDD13C		UU6	20/11
2P	2/6	3F15	16/-	10C2	27/10	28D7	7/-	AC/VP1	EBC81	14/8	EZ40	8/6	OA71	6/-	TH4B	27/10	UYIN	17/5
2X2	4/6	3F15	16/-	10F1	19/6	30C1	9/-		EBC81	14/8	EZ40	8/6	OA71	6/-	TH4B	27/10	UYIN	17/5
3A4	7/-	6F17	12/6	10F9	11/6	30F1	9/-	AC/VP2	EBC81	14/8	EZ40	8/6	OA71	6/-	TH4B	27/10	UYIN	17/5
3A5	12/6	6F17	12/6	10F18	12/6	30F1	9/-		EBC81	14/8	EZ40	8/6	OA71	6/-	TH4B	27/10	UYIN	17/5
3B7	12/5	6F23	7/6	10LD3	8/6	30L1	9/-		EBC81	14/8	EZ40	8/6	OA71	6/-	TH4B	27/10	UYIN	17/5
3D6	5/-	5G6	6/6	10LD11	16/9	30P2	12/6	AL60	10/-	EBC13	24/4	FC2A	25/9	TH2321	20/11	UY85	10/6	
3Q4	7/6	5HG6GT	3/-	10P13	17/5	30P16	10/6	ATP4 5/-	ECC52	5/6	FC4	27/10	PCC84	9/-	TP22	15/-	VMP4G	15/-
3Q5GT	9/6	5HG5GTG	3/6	10P14	20/2	30P16	10/6	AZ1	ECC54	6/6	FC13	27/10	PCC85	12/6	TP25	19/6	VMP(7)	12/6
3S4	7/6	6I5G	5/-	11D3	25/9	31	7/6	AZ31	ECC70	12/6	FC13C	27/10	PCC80	9/-	TP2620	34/9	VP4(7)	15/-
3V4	9/-	6I5GTG	5/5	11E3	15/6	33A, 158M		AZ41	ECC31	15/-	FW4/500		PCF82	12/6	TY86	20/11	VP4B	24/4
5R4G	17/5	6I5GTG	6/-	12A6	6/6	33B	25/9	ECC32	10/6		FW4/800	10/-	PCL82	12/6	UJ2/14	12/-	VP13C	7/-
5U4G	8/6	5I6	5/6	12AC6	16/-	35/5	12/6	ECC33	8/6				PCL83	14/6	U16	12/-	VP21	6/6
5V4G	11/6	6I7G	6/-	12AD6	16/-	35LGT	9/6	ECC34	25/9				PEN4DD		U18/20	10/-	VP41	6/6
5X4G	12/6	5I7GT	10/6	12AE6	14/8	35V4	8/6	ECC35	8/6	GZ30	10/6			U22	8/-	VR105/30		
5Y3G	8/6	6K6GT	5/-	12AH7	8/-	35Z	10/6	ECC36	8/6	GZ32	12/6	PEN25	20/11	U24	31/4		9/-	
5Y3GT	8/5	6K7G	5/-	12AH8	10/5	35Z	7/6	ECC37	7/6	GZ34	14/-	PEN36C		U25	24/4	VR150/30		
5Y4	12/6	6K7GT	6/-	12AT6	10/6	35Z1 GT	9/-	ECC38	10/6	H30	5/-			U26	12/6		9/-	
5Z3	12/6	6K8G	8/-	12AT7	8/-	41M1 L	8/-	ECC39	10/6	H63	12/6	PEN40DD		U31	10/-	VT61A	5/-	
5Z4G	13/6	6K8GTG	8/-	12AU6	24/4	42	24/4	ECC40	10/6	HAB80	25/-			U33	27/10	VT501	5/-	
5Z4GT	12/6		11/-	12AU7	7/6	43	24/4	ECC41	10/6			PEN44		U35	27/10	W6M	27/10	
6A7	27/10	5K25	20/11	12AX7	10/-	50C1	12/6	ECC42	10/6	HK90	13/6			U37	27/10	W76	7/6	
6A8	10/-	6L1	24/4	12BA6	9/-	50C1P6G		ECC43	10/6	HL133DD		PEN45	19/6	U43	10/6	W81M	6/-	
6A87	8/-	6L6G	9/6	12BE6	12/6		31/4	ECC44	10/6	HL23	10/6	PEN45DD		U45	10/6	W107	12/6	
6A88	14/-	5L7GT	12/6	12BH7	22/3	50L6 GT	9/6	ECC45	10/6	HL23DD		PEN46	7/6	U50	8/-	W729	19/6	
6AC7	6/5	6L13	13/-	12C9	15/-	53KLI	20/11	ECC46	9/6	HL31	18/6	PEN483	24/4	U52	8/6	X31	27/10	
6AG5	6/5	6L19	24/4	12E1	30/-	7	4/6	ECC47	9/6	HL41	12/6	PEN453DD		U76	7/6	X41	27/10	
6A18	9/-	5LD20	15/9	12I5GT	4/6	75	25/9	ECC48	9/6	HL41DD				U78	7/-	X42	27/10	
6AK5	8/-	5N7	3/-	12J7G	10/6	77	8/6	ECC49	10/6			PEN45DD		U107	17/5	X61	12/6	
6AK8	9/-	6P25	24/4	12K5	18/10	78	8/6	ECC50	10/6					U191	20/11	X61M	27/10	
6AL5	6/5	6P28	27/10	12K7GT	7/6	80	9/-	ECC51	10/6					U251	15/-	X63	10/-	
6AM6	7/6	5Q7G	19/-	12K8GT		83	12/6	ECC52	10/6					U282	23/8	X66	12/6	
6AQ5	8/6	5Q7GT	11/-		14/-	83V	15/6	ECC53	10/6					U301	24/4	X76M	14/-	
6AT6	8/5	6R7G	10/6	12Q7GT	7/6	85A2	15/-	ECC54	10/6					U329	15/-	X78	22/3	
6AU6	10/5	5SA7GT	3/6	12SA7	8/6	150B	15/-	ECC55	10/6					U339	20/11	X79	22/3	
6B4G	6/6	6S7	10/6	12SC7	8/6	185B T	34/9	ECC56	10/6					U404	10/6	X109	18/1	
6B7	10/6	6S9GT	8/-	12SG7	8/6	185B TA	34/9	ECC57	10/6					U480	31/4	XID(1.5)	6/6	
6B8G	4/6	6SH7	8/-	12SH7	8/6	203T 1A		ECC58	10/6					U4020	17/5	XFG1	18/-	
6B8GT	5/-	6S17	8/-	12S17	8/6		27/10	ECC59	10/6					U4080		XH(1.5)	6/6	
6BA6	7/6	6SK7GT	8/-	12SK7	8/6	220T H	25/9	ECC60	10/6						10/6			
6BE6	7/5	6SL7GT	8/-	12S7G	12/6	402P:NA		ECC61	10/6					UAF42	10/6		6/6	
6BG6G	24/4	6SN7GT	7/6	12SR7	8/6		24/4	ECC62	10/6					UB41	12/7	Y63	7/6	
6BH6	9/-	6S9GT	9/-	12Y4	10/6	807	7/6	ECC63	10/6					UBC41	10/7	Z63	10/6	
6B16	7/6	6S57	8/-	14S7	17/7	956	3/-	ECC64	10/6					UBC81	14/8	Z66	20/-	
6BR7	11/6	6U4GT	12/6	15D1	27/10	1921	17/5	ECC65	10/6					UBF80	9/6	Z77	7/6	
6BW6	9/5	6U5G	7/6	18	24/4	5763	12/6	ECC66	10/6					UBF89	10/6	Z719	8/-	
6BW7	8/5	6U7G	8/6	19AQ5	11/-	7193	5/-	ECC67	10/6					UBL21	24/4	Z729	14/-	

NEW METAL RECTIFIERS—FULLY GUARANTEED

DRM-1B	15/4	RM-3	9/6	1VX3	3/6	14A100	27/-	14RA 1-2-8-2	19/-	16RE 2-1-8-1	8/6
DRM-2B	16/2	RM-4	14/-	1VX4	3/6	14A124	28/-	14RA 1-2-8-3	23/6	16RA 1-1-8-1	4/6
DRM-3B	23/3	RM-5	24/-	1VX6	3/6	14A163	38/-	14RA 2-1-16-1	21/-	16RA 1-1-16-1	6/6
RM-0	7/11	W4	3/3	4A86	18/-	14B130	35/-	16RC 1-1-16-1	8/6	16RA 1-2-8-1	11/-
RM-1	7/11	W6	3/6	4A97	25/-	14B261	11/6	16RD 2-2-8-1	12/-	16RD 2-2-8-1	15/-

Technical leaflet on Metal Rectifiers or Hivac Miniature Valves free on receipt of S.A.E.

VOLUME CONTROLS

All with long spindle and double-pole switch, 4/6 each.
 10K. 25K. 50K. 100K.
 1/2 meg. 1 meg. 1 meg. 2 meg.

Standard Can

32 x 32 mfd., 450 v. 5/9
 64 x 120 mfd. 350 v. 8/3
 60 x 250 mfd., 275 v. 9/6

ELECTROLYTIC CONDENSERS

100 x 400 mfd., 275 v. 12/6
 100 mfd., 275 v. 2/6
 200 mfd., 275 v. 3/6
 100 x 200 mfd., 275 v. 9/6

Wire-ended Tubular

8 x 8 mfd., 450 v. 3/-
 16 mfd., 450 v. 1/9
 32 x 32 mfd., 350 v. 4/-
 32 mfd., 450 v. 3/9
 8 x 8 mfd., 450 v. 4/-

TERMS OF BUSINESS: CASH WITH ORDER OR C.O.D. ONLY. POST-PACKING CHARGES 6d. PER ITEM; ORDERS VALUE £3 OR MORE POST FREE. C.O.D. 26 EXTRA. WE ARE OPEN FOR PERSONAL SHOPPERS MONDAY TO FRIDAY 9.30-5.30. SATURDAY 9.30-1.30. ALL VALVES, NEW, BOXED, TAX PAID, AND SUBJECT TO MAKERS' GUARANTEE. FIRST GRADE GOODS ONLY. NO SECONDS OR REPAIRS. CATALOGUE OF OVER 1,000 DIFFERENT VALVES, WITH FULL TERMS OF BUSINESS, PRICE 6d. PLEASE ENQUIRE FOR ANY VALVE NOT LISTED. 3d. STAMP, PLEASE.

RECORD PLAYER CABINETS



(R.P.1)
49/6

A practical cabinet, nicely designed, cloth covered two-tone, brown and coffee. Size 15 x 17 x 8in. deep. Takes B.S.R. 4-speed Autochanger and 6½in. round or elliptical speaker. Carr. & Ins. 4/6.



(R.P.4)
79/6

Stylish cabinet by a famous manufacturer. Cloth covered in contrasting colours (red and grey). Grilled front controls panel. Size 15 x 19 x 8½in. deep. Beautifully made—a cabinet of which you can be really proud. Takes 4-speed B.S.R. Autochanger; 8½in. round or elliptical speaker. Room for any amplifier of your own choice. Carr. & Ins. 4/6.

(R.P.2)
69/6

A beautifully styled cabinet made by a famous manufacturer. In polka dot cloth with clipped lid with carrying handle. Size 16 x 14½ x 8½in. deep. Will take B.S.R. Monarch 4-speed Autochanger and 4 x 7in. elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6.



(R.P.6)
49/6

Elegant cabinet, cloth covered in grey or red, with sunken control panel and speaker fret. Size 13 x 17 x 8in. deep. Takes a B.S.R. Monarch 4-speed Autochanger; 7 x 4in. elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6.



(R.P.3)
79/6

A delightful-looking cabinet 14½ x 17½ x 8½in. in two-tone leatherette. Will take a B.S.R. Monarch 4-speed autochanger and 6½in. round speaker. Carr. & Ins. 4/6.



★
TERMS AVAILABLE
★
AMPLIFIERS

12 Months' Guarantee
PORTABLE AMPLIFIER MARK D.1, 59/6

Brand new. Latest design with printed circuit. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated; 2-3 watts output. Incorporating EL84 as high-gain output valve. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.




PORTABLE AMPLIFIER MARK D.2, 79/6

Printed circuit. Latest design. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated; 3-4 watts output. Incorporating the latest ECL82 triode-pentode output valve, giving higher undistorted output. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

PORTABLE AMPLIFIER MARK D.3, 89/6

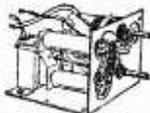De luxe model. Printed circuit. Latest design. Dimensions 7 x 2½ x 5in. A.C. only. Mains isolated; 3-4 watts output. Incorporating the latest ECL82 triode-pentode output valve, giving higher undistorted output. Volume, treble and bass control. Knobs 3/6 extra. P. & P. 3/6.



PORTABLE AMPLIFIER MARK D.4, 69/6

Brand new. By famous manufacturer. Especially built for portable record players. Dimensions 4½ x 3½ x 4in. A.C. only. 2 valves EL84 as high-gain output valve. EZ80 as rectifier. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

Collaro 4-Speed Autochangers £7.19.6

Incorporating auto and manual control complete with studio crystal p.u. and sapphire stylus. P.P. & Ins. 5/6.



B.S.R. Monarch 4-Speed Autochanger
£6.19.6

Incorporating auto and manual control complete with turnover crystals p.u. and sapphire stylus. P.P. & Ins. 5/6.

★ **EXTENSION 19/9 SPEAKERS,**



Polished wood cabinet of attractive appearance. Fitted with 8in. P.M. Speaker, W.B. or Goodmans, of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins. Carr. 3/6.

IDEAL FOR STEREPHONIC SOUND. 8in. P.M. Speakers, 8/9. With O.P. Transformer fitted, 10/-, 6½in. P.M. Speakers, 12/6; 4 x 7in. Elliptical Speakers, 19/6. Postage 2/9.

★ **STEREPHONIC AMPLIFIERS, £7.19.6**

Beautifully made for portable stereophonic record players. Latest design with printed circuit: 3 x 5½ x 9½in. A.C. only. Mains isolated Twin amplifiers each side giving 3-4 watts output. Incorporating ECL82 triode-pentode valve. Knobs 3/6 extra. P. & P. 4/6.


Televox Telephone Amplifier 89/6



Invaluable in a noisy office or workshop. 3 valves: UY41, UF41 UL41. 3in. speaker and a suction type vibration microphone. A.C./D.C. Size of amplifier 7 x 11 x 3in. Fits any type of G.P.O. telephone. P/P & Ins. 4/6.

DUKE & CO.

T/V TUBES • CHASSIS • SPEAKERS

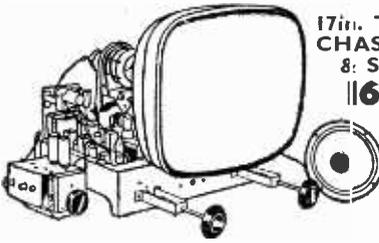

17in. T.V. CHASSIS, TUBE & SPEAKER
116 Gns.

17in. Rectangular Tube on modified chassis. Supplied as single channel chassis covering B.B.C. chan-

nels 1-5, or, incorporating Turret Tuner which can be added as an extra, at our special price to chassis purchasers of 50/- giving choice of any two channels (B.B.C. and I.T.A.). Extra channels can be supplied at 7/6 each. Chassis size 12 x 14½ x 11in. less valves. Similar chassis are used by well-known companies because of their stability and reliability. With Tube and speaker—less valves—16 guineas. Complete and working with valves and Turret Tuner. 24 guineas. 12 months' guarantee on the Tubes. 3 months' guarantee on the valves and chassis. Ins., carr. (incl. Tube), 25/-.

14in. T.V. CHASSIS, TUBE & SPEAKER
11 Gns.

As above, with 14in. Rectangular Tube. 12 months' guarantee on the chassis and valves. Chassis with Tube and Speaker (less valves), 11 guineas. Complete and working with valves and Turret Tuner 19 guineas. Ins., Carr. (incl. Tube), 25/-.

POPULAR 12in. PLESSEY T.V. CHASSIS
39/6

This is a real bargain for anyone wanting to make up their own T.V.

at a very low cost. I.F.'s 10.5-14 Mc/s. Simply adapted for a 12 Channel Turret Tuner and can be modified to take a larger Tube. A chassis in one unit. Untested. Less valves, tube, speaker and scanning coils. (All can be supplied as extras.) Circuit diagram available, 3/6, or FREE with order. Carr. & Ins., 10/6.

EXPRESS DESPATCH SERVICE

Please phone to confirm Tube in stock. Send Telegraph Money Order. Tube despatched Passenger Train same day. This service only available with remittance by a Telegraph Money Order.

REGETTERED IMPROVED VACUUM T.V. TUBES

17in. rect. ... **£7.10.0**
14in. rect. ... **£5.10.0**




12 MONTHS' GUARANTEE

Our 12 months' guarantee (6 months full replacement, 6 months progressive) illustrates our wholehearted confidence in the Tubes we offer. We sell many hundreds a week throughout the country and have done so for the past 7 years. Many of them go to the Trade, i.e., to Insurance Companies, Renters & Retailers who are thoroughly satisfied with our supplies. Remember, they also hold a 10 days' money back guarantee. 9in., 10in., 14in., 15in. and 16in. Round tubes. Our special offer of these sizes. £5. 12in. T.V. Tubes, £6. Three months' guarantee on round tubes. Ins., Carr., 15/6.

SUPER CHASSIS, 99/6

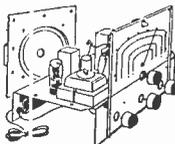5 valve superhet chassis including 8in. P.M. speaker and valves. Four control knobs (tone, volume, tuning, w/change switch). Four wavebands with position for gram. p.u. and extension speaker. A.C. Ins., carr., 5/6.



SOUND/VISION & I.F. STRIP, 25/6

Plessey. Tested. I.F.'s 10.5 Mc/s. sound. 14 Mc/s. vision. 8 valve holders. Less valves. Size 8½ x 5 x 4½in. Circuit incl. The tuner unit plugs directly into this chassis. P.P. 2/6.

SOUND/VISION & I.F. STRIP, 5/9

Salvaged. Complete sound and vision strip. 8 valve holders. Less valves. I.F.'s 16-19.5 Mc/s. Size 8½ x 4½ x 4½in. Drawings free with order. P. & P. 2/6.

TIMEBASE, 4/9

Containing scanning coils, focus unit, line transformer, etc. Less valves. Drawings free with order. P. & P. 2/6.

POWER PACK & AMPLIFIER, 19/6

Tested. Output stage 6V6 with O.P. trans. 3 ohms choke. Smoothed H.T. 350 v. at 250 m.a. 6.3 v. at 5 amp. 22 v. at 3 amp. 6.3 v. at 4 amp. and 4 v. centre tapped. Less valves. Ins. carr. 5/6.

MIDGET 5 VALVE SUPERHET, 49/6

5 valve superhet. Can be used on 110 volt-250 volt mains. A.C. or Universal. Compact little set using 12K8, 12K7, 12Q7, 35L6 and 35Z4 G.T. valves. 5in. speaker. Cabinet size 17 x 8 x 6in. Carr. & Ins., 3/6.

SOLO SOLDERING TOOL, 12/6

110 v., 6 v., or 12 v. (special adaptor for 200/240 v. 10/- extra). Automatic solder feed including a 20ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 2/9.



★ Mains Transformers ★

DROP THROUGH TYPE, 12/9

350-0-350 volts at 250 m.a., 6.3 volt at 4 amp., 6.3 volt at 4 amp., 4 volt at 3 amp., 22 volt at 3 amp., 4 volt centre tapped at 1.5 amp. Primary 200-250 volt. 50 cycles. P. & P. 3/9.

DROP THROUGH TYPE, 12/9

350-0-350 volts at 250 m.a. 6.3 volt at 5 amp., 4 volt at 4 amp. 4 volt at 7 amp. 4 volt centre tapped at 1 amp. Primary 200-250 volt. 50 cycles. P. & P. 3/9.

UPRIGHT TYPE, 3/9

350-0-350 volt at 80 m.a. 12 volt at 1.5 amp., 4 volt at 2 amp. Primary 100-120-200-250 volt. Fully shrouded. Ideal for mains auto transformers. P. & P. 2/9.

MAINS AUTO, 12/6

0-205-225-245 volts at 300 m.a. Isolated windings of 6.3 volt at 2-6 amp. 6.3 volt at 3-6 amp., 2 volt at 1-4 amp. P. & P. 3/9.

O.P. TRANS., 1/3

Standard size 2-5 ohms. Post 1/- 20 for £1. P. & P. 5/6.

HOME RADIO, 79/6

A.C./D.C. Universal mains 5 valve octal superhet. 3 waveband receiver can be adapted to gram. p.u. In attractive wooden cabinet 9½ x 18½ x 11½in. Ins. carr. 7/6.



DUKE & CO.

TERMS AVAILABLE. Send for FREE Catalogue. (Dept. E.3.)
621/3, Romford Road, Manor Park, E.12
Telephone: ILFORD 6001/3
Open all day Saturday. Closed 1 p.m. Thursday.



'CATHODRAY' VISCONOL CONDENSERS

for the most stringent conditions

The 'Visconol' Process — exclusive to T.C.C. — means greater dependability and a longer useful life than ever before. It is the answer by T.C.C. research engineers to the insistent demand for condensers which will stand up to higher and still higher voltages. A selection from the range is given below. Features include: low power factor; complete dielectric stability; resistant to voltage surges; ample rating at higher temperatures; proof against breakdown or flash-over. Full details on request.

Cap. in μ F.	Max. Wkg. at 60°C.	Dimens. (Overall)		T.C.C. Type No.	Price
		Length	Dia.		
.0005	25000	5 1/8	1 1/8	CP57H00	18/-
.001	6000	2 1/2	1 27/32	CP55Q00	6/-
.001	12500	3	1 3/8	CP56V00	10/-
0.001	20000	2 1/2	1 1/8	CP56G00	10/-
.002	18000	5 1/8	1 1/8	CP57X00	18/-
.01	6000	3	1 3/8	CP56Q00	10/-
.02	12500	6 1/8	2	CP58V00	20/-
.05	6000	5 1/8	1 1/8	CP57Q00	18/-
.1	7000	6 1/8	2	CP53Q00	20/-
.25	1000	3	1 3/8	CP56V	10/-

THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION : NORTH ACTON · LONDON · W.3 Tel: ACORN 0061

LASKY'S RADIO

MAKER'S SURPLUS COMPONENT BARGAINS

WIDE ANGLE 33 mm.

- Line E.H.T. Trans. Ferro-cube core, 9-18 kV. 19/6
- Scanning Coils. Low imp. line and frame 19/6
- Ferro-cube cored Scanning Coils and Line Output Trans., 10-15 kV. EY31 winding Line Trans. with width and linearity controls, circuit dia., pair... 50/-
- Frame Output Transformer 6/6
- Frame or line block osc. Transformer 4/6
- Focus Magnets Ferro-core P.M. Focus Magnets, Iron Cored 19/6
- Duomay Focallisers 22/6
- 303 m/a Smoothing Chokes 10/6

STANDARD 35 mm.

- Line Output Transformers 8.9 kV, E.H.T. and 6.3 v. winding, Ferro-cube..... 17/6
- Scanning Coils. Low imp. line and frame 7/6
- Frame or line blocking oscillator Transformer ... 4/6
- Frame Output Transformer 7/6
- Focus Magnets : Without Vernier 12/6
- With Vernier 17/6
- 203 m/a Smoothing Chokes 7/6

AMAZING BARGAIN IN BAND III CONVERTERS

LISTED AT 9 GNS.

LASKY'S PRICE

75/-

Post & Pkg. 5/-



By famous manufacturer in Pye group. Limited number only, in maker's cartons. 3 valves: ECF80, ECC84, EZ90 rectifier. 8 switched channels on Band III, converting to any Band I channel. Incorporates own power supply for 100-250 v., 50 cycles. A.C. Black crackle finish metal case, 8" x 5 1/2" x 4" high, with rubber feet. Send NOW!

TURRET TUNERS. All types in stock—Cylcon, Brayhead, Telenge, Valradio. Describe your set and we will quote you. Prices from 79/6.

C. R. TUBES, new and unused. 14", £14.19.6. 17", £16.19.6. 12", £8.19.6. Carr. & Ins. 22/6.

MAIL ORDERS TO HARROW ROAD, PLEASE **LASKY'S (HARROW RD.) LTD.** 42, TOTTEHAM COURT ROAD, W.1. Telephone: MUScum 2605

370, HARROW ROAD, PADDINGTON. W.9. LADbroke 4075 and CUNningham 1979. Open all day SATURDAY. Half day Thursday.

SPECIAL OFFER!

Standard 90° Deflection Coils (Ferro-cube core), Line Output E.H.T. Trans. and Frame Output Trans. with width and linear controls. Lasky's Price, the Set **59/6** Post 2/6.

MINIATURE INSTRUMENT SOLDERING IRONS

Famous make, 230/250 v. 25 watts, complete with pencil bit and 3-core flexible lead. Overall length 10". Tell-tale light in handle shows when current is on. LIST PRICE 22/6.

Lasky's Price **16/6** Post 1/3.

SPECIAL OFFER OF SOLDER

1-lb. reels of Er sine S-core "Savebit" Solder, LIST 15/-.

Lasky's Price **10/-** Post 1/6.

20,000 VALVES IN STOCK

Brand new surplus and imported, also full stocks of B.V.A. valves and C.R. Tubes. List post free.

C. R. TUBE BARGAIN

Special Offer of FERRANTI 9in. C.R. Tubes, type T9/3. 4 v. heater, triode, octal base, standard deflection. New and unused. LIST £12/19/-.

LASKY'S PRICE **59/6** Carr. & Ins. 12/6.



Practical Television



& TELEVISION TIMES

Editor : F. J. CAMM

Vol. 9 No. 104

EVERY MONTH

MARCH, 1959

Editorial and Advertisement Offices :
PRACTICAL TELEVISION
George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.
© George Newnes Ltd., 1959.

Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - 19s. per annum
Abroad - - 17s. 6d. per annum
Canada - - 16s. per annum

CONTENTS :

	Page
Editorial	381
Servicing Television Receivers ...	382
Replacing C.R. Tubes ...	385
Trans-oceanic TV ...	387
A TV Oscilloscope ...	388
Relaxation Oscillators—4 ...	391
Trans-Atlantic TV ...	392
Transistors in TV Receivers ...	393
Telenews ...	395
A Home-constructed Tele- vision Receiver ...	399
Subscription TV—Pay-As- You-View... ..	402
Television Troubles—7 ...	404
TV in Iran ...	406
Analysing and Servicing TV Receivers ...	409
Underneath the Dipole ...	413
Completion of I.T.A. Service ...	417
Correspondence ...	418
Your Problems Solved ...	421

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

TELEVISIONS

RECORD YEAR FOR THE INDUSTRY

AS a result of the change in the rental and hire purchase controls, introduced last autumn, the television and radio industry has had a brisk year. Manufacturers have been working at peak capacity and it seems feasible that they will reach an annual output of 2,000,000 sets this year, compared with 1,870,000 last year. The large stocks which were accumulating in the factories have all been cleared. As we go to press, the imminence of the Budget will cause manufacturers to limit their stocks in anticipation of any further changes, such as in purchase tax, which the Budget may introduce. It is somewhat surprising to learn that in spite of the competition of television, the sales of sound receivers have shown a marked increase. On the other hand, the sales of gramophone record playing equipment, and this includes radiograms, has not been very good. Stereo sound introduced at the Radio Show last year gave the trade a small filip, but nothing like what was expected. What was gained on the roundabouts has, to some extent, been lost on the swings, for the interest in stereo sound apparatus has had an adverse effect on the sales of radiograms and reproducers with only single amplifiers.

COLOUR TELEVISION

ALTHOUGH colour television was demonstrated by J. L. Baird in 1928, we are still far from having a colour television programme. Indeed, all interest in the subject seemed to have been lost between 1928 and 1946, when a somewhat luke-warm interest on a purely experimental basis was introduced. In America, however, considerable research was taking place to find a compatible system of colour television—that is to say a system which would serve existing receivers with a black-and-white picture and at the same time provide a colour picture to new receivers specially designed for the purpose. It was also necessary that the addition of colour signals could be accommodated in the existing radio frequency channels. As a result, the N.T.S.C. system (National Television Systems Committee) was introduced and provided a solution to both of these problems. The method is to use a three-colour camera to produce three signals which relate to the red, green and blue primary components of the coloured scene. These signals are combined in such a manner as to provide a standard black-and-white signal together with another signal which describes only colour. A conventional receiver will reproduce a standard black-and-white picture from the luminance signal in the normal way, but a colour receiver will reconstitute the red, green and blue primary signals and produce a colour picture on the screen of a tri-colour picture tube.—F. J. C.

Our next issue, dated April, will be published on March 20th



Serviceing TELEVISION RECEIVERS

No. 45.—THE PYE CW17 SERIES, WIRED VERSIONS; ALSO COVERING INVICTA T123 SERIES AND PAM 754

By L. Lawry-Johns

IN order to embrace as many receivers as possible, without being misleading, no detailed description of the circuits will be given, as there are so many variations that the whole of this article would be taken up in confusing descriptions—"ifs and buts," etc. On this broad outline, therefore, it is possible to include earlier models such as the VT17 series, the PAM 752 and others in the family which employ a similar chassis, including the 21in. variants. The system of numbering the Pye CW, CS and CT range has become so complex, with three or four variations of each, and to add to the confusion, printed circuit models (still with the same model No.) that no amount of various identification dots, stripes, etc., would enable the writer to be comfortably sure that his efforts are comprehensive and easily understood, notwithstanding the confusion that exists in his own mind.

Therefore the diagrams cannot be regarded as applicable to every model, and are provided to enable the general layout to be appreciated. On most Invicta models the tube is mounted on the chassis and is thus withdrawn with it. It is general Pye practice, however, to mount the tube separately and several Invicta models are so constructed. However, to get on to the more common faults which can almost certainly be expected; the symptom of *no vision, no sound*, all valves lighting up normally, is perhaps the most common and easiest to diagnose.

No trace of hum will be heard from the loud-speaker(s), no whistle from the line timebase, and the receiver except for the valve heaters is dead. This, of course, indicates that no H.T. is being supplied to any part of the circuit and in most cases it is unnecessary to look further than the contact cooled metal rectifier, bolted to the inside of one of the chassis side walls on the left side as viewed from the rear. The fault is that the conductive path from the discs to the connecting tag has become open circuited. The type of rectifier found fitted will be a 14RA1-2-8-3. This type has now been superseded by the type FC31

which has the same connections and fixing holes, but is of different internal construction. As always, however, one can be wrong in the diagnosis, the rectifier may be entirely innocent. The impulse to assume the rectifier to be at fault because it usually is, should be resisted. The A.C. voltage applied to the -tag should be checked. If a meter is not available, a test lamp (240 v.) may be connected from the -tag to chassis. If it lights up, or an A.C. reading is recorded on a meter, the rectifier is at fault and should be replaced. Incidentally, the test lamp may be touched to the + or H.T. tag to make absolutely sure. If the rectifier is at fault the lamp will not light up. Thus "juice" is going in but not coming out. However, it is often the case that A.C. is not being applied to the rectifier at all and a glance at the circuit will show that a surge limiting resistor is included in the circuit from the mains dropper to the rectifier. This is a

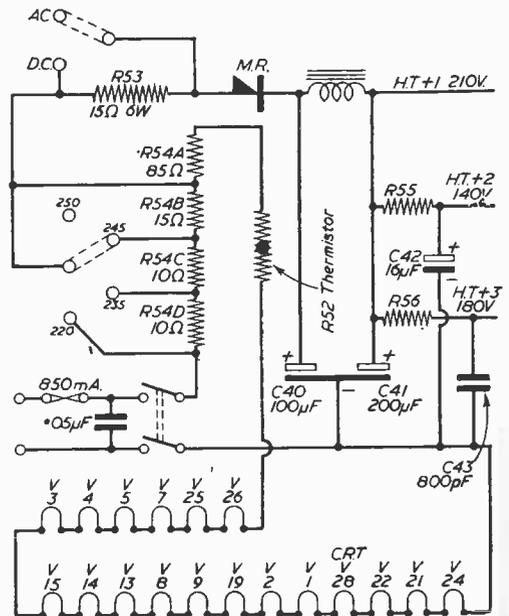


Fig. 1.—Mains supply, H.T. and tube heater chain.

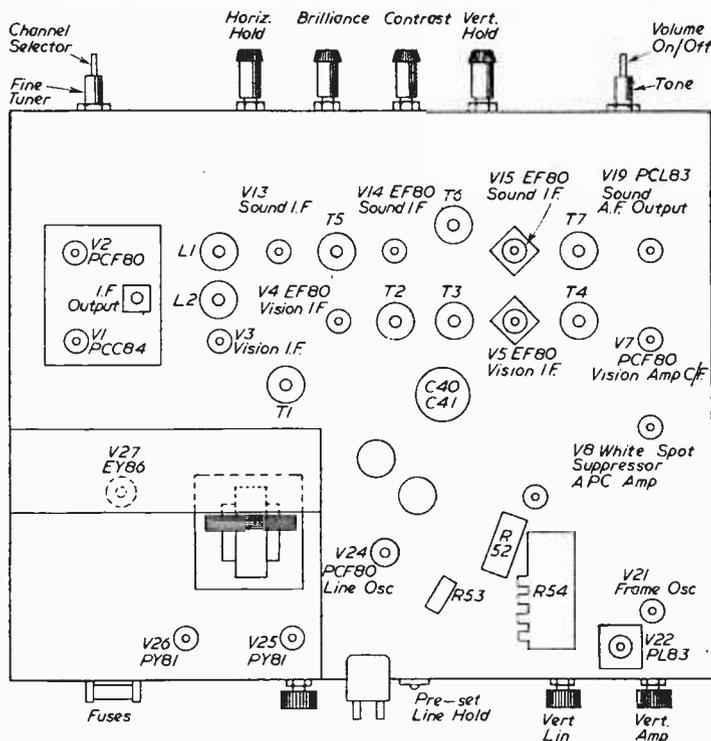


Fig. 3.—Top chassis view. Pye model CW17.

C.R.T. EHT clip removed as a short in the tube may be responsible.

Terms

To digress a moment, it may have been noticed that stress is laid upon the terms open circuit and short circuit. In all the articles in this series the writer attempts to introduce some basic principles for the benefit of the beginner. After dealing with electrical circuits for a period one becomes used to thinking electrically and complicated circuits then resolve themselves into a series of simple ones. It should always be borne in mind, however, that any circuit can exhibit only one of two faults. One is an open circuit (where the circuit is not completed) and the other a short circuit (where the circuit is completed prematurely). All faults are varying degrees of either.

Next month's article will give more servicing information on the Pye CW17 and will include the causes and cures of such faults as "Sound Without Picture," "Hum Bars" on the picture and "Hum on Sound," etc.

(To be continued)

rules. In one case the writer found the cause to be the screened cable which connects to the line scanning coils. It had developed a short between the inner core and outer screen. In another, the leads in the scanning-coils plug had become detached and were shorting together, possibly as a result of heat over a period aided by the owner's happy habit of persistently removing the plug to clean the chassis (he said). However, assuming the fuse is not blown, check the PL81 and the 3.9 kΩ 2-watt screen dropping resistor (to pin 8). If, however, the line timebase whistle is audible, check the EHT at the top cap of the EY86. If the circuit is in order up to this point, a heavy spark will jump to the blade of a screwdriver advanced to its immediate area. The presence of such activity should naturally cause one to suspect the EY86 itself, the heater of which may be open-circuited. If the timebase whistle is rough and sounds "overloaded," check the conditions with the

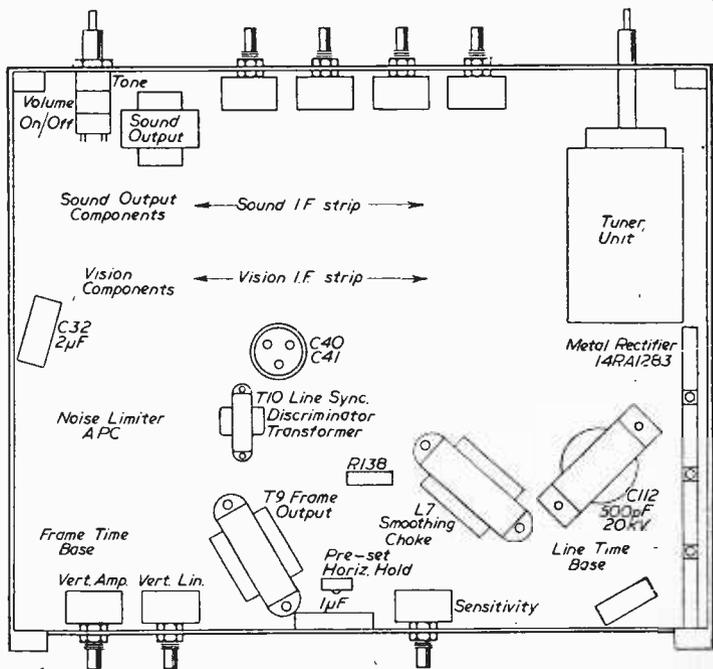


Fig. 4.—Simplified under-chassis view.

Replacing C.R. Tubes-3

MORE INFORMATION ON EKCO RECEIVERS

By H. Peters

(Continued from page 349 of the February issue)

TO clean the screen on these sets it is necessary to remove the chassis and tube cradle as outlined last month, and then remove the tube and cradle off the safety glass and mask.

Boosting the Tube (A.C. Mains Only)

Remove the existing heater wires from pins 1 and 12 of the tube base. Short the two wires together and tape them back, at the same time altering the voltage flyleads C and D on the adjustment panel to the setting correct for 10 volts higher (e.g., from 230 v. to 240 v.). This will compensate for the removal of the tube from the heater chain.

to the aluminium and lift the metal part of the cradle off leaving the rubber around the tube. This can then be removed by rolling back, grasped by a pair of long-nosed pliers in the manner of opening a sardine tin.

Models with V.H.F. need different treatment when boosting the tube as the boost transformer will need to have its "live" wire switched out when the set is switched to V.H.F. Early sets have a spare set of contact on the "trombone" switch, but later series with V.H.F. on a single channel need to have one provided. This can be done by using the set of contacts that switch the tube out and the pilot lamp in on V.H.F.

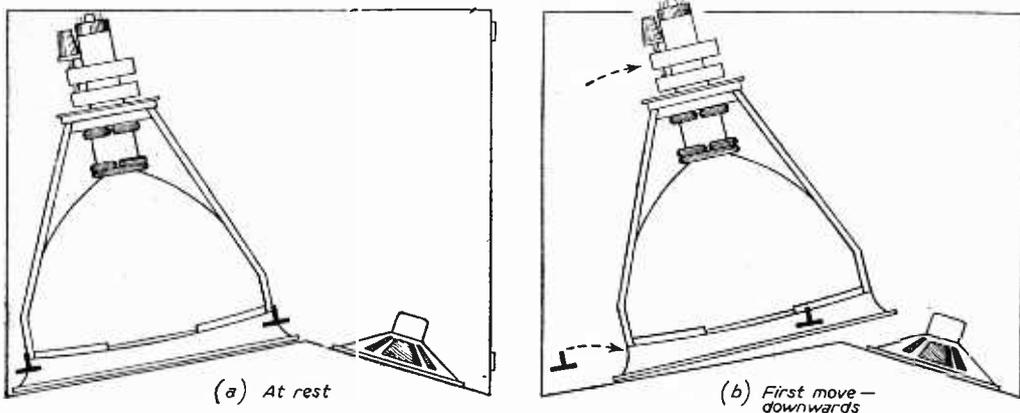


Fig. 5.—The stages in removing the tube cradle of the T231, as seen through the side of the cabinet.

The boost transformer secondary is then connected to the empty pins 1 and 12 of the C.R.T. base using short leads, whilst mains for the transformer primary can be picked up from between any convenient chassis point and the brown voltage adjustment flylead "A."

Variations and Notes

If a CRM172 is fitted in place of a CRM171 be sure to connect the graphite coating to chassis. This coating may be used instead of the EHT condenser.

On very early receivers a small resistor is fitted across the heater pins of the tube base and this should be removed when replacing the C.R.T. On 14in. models the tube is clamped around the bowl by an aluminium band bolted at the sides and cushioned with a rubber strip.

During the course of time this rubber strip becomes bonded to the tube face and then the safest way to remove the tube from the cradle is to cut the strips of tape holding the rubber

The wires are joined so as to disconnect the tube and leave the pilot lamp permanently "on."

Models T301, 311, 326, 327, 330, 331, 330F

These comprise the more recent range of Ekco sets and although similar to the preceding models are much easier to handle when changing tubes. Remove the chassis the same way as in the T231, but with the deflector coils, which do not unplug. These slide easily off the tube neck after the ion trap and focus magnets have been removed. The cabinet is then laid on its face and the four corner bolts holding the tube assembly are removed. There is no tube cradle as such and care must be taken when transferring the metal clamps which hold the tube bowl to ensure that they are sufficiently forward to prevent the front of the tube from touching the safety glass, thus making a small opaque spot in the middle of the tube. Screen cleaning on this range can be done without unboxing by laying the set on its side and removing the three brass


6 B.A. screws holding the gilt bar at the bottom of the safety glass.

Boosting the tube follows the general lines of the 231, with the addition of the switch rewiring as outlined under "variations" if the receiver incorporates V.H.F., but as the mains tapping arrangements are different it is necessary to alter flyleads "A" and "B" to the setting correct for 10 volts higher to allow for the removal of the tube from the heater chain. Mains for the boost transformer can be picked up between chassis and voltage flylead "B."


Early Ekco Receivers

The 12in. T161. (Also covering TU169, TU211, T216, TC196, and 196/1, T205, TC206, T207, T207/1, TC185, TC178, TC166, TC165, T164, TC162, TC155.)

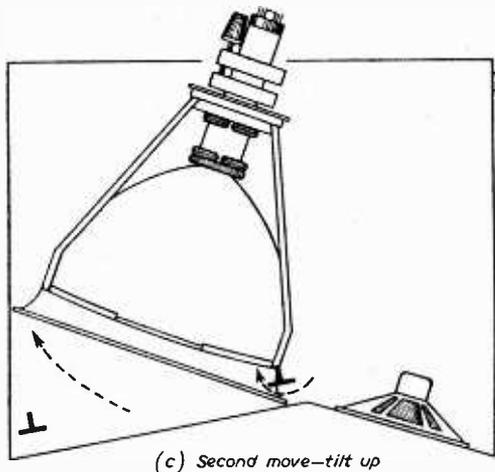To unbox the set remove the back and loosen the control panel. Unplug the scancoil lead, EHT connector, C.R.T. socket and loudspeaker plugs. Remove the two 4 B.A. bolts holding down the rear of the chassis and withdraw the



(c) Second move—tilt up

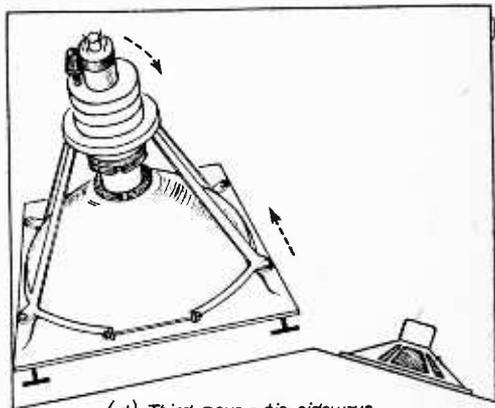

(d) Third move—tip sideways

Fig. 5.—(Cont.) The heavily printed T-shaped objects are the fixing brackets on the cabinet which constitute the major obstacle to pulling the assembly straight out.

chassis and control panel. Turn the cabinet upside down on to a soft cloth then remove the 2 B.A. nuts (four in all) holding the tube cradle to the top of the cabinet. Lift the cradle clear of the screws, taking care not to hit the loudspeaker, and draw backwards out of the cabinet. Remove the four screws that hold the mask and put this on one side with the dust excluder rubber. Place the tube and cradle face down on a soft cloth; mark the scancoils to ensure correct refitting; remove the focus magnet by unscrewing the two 2 B.A. screws holding the assembly to the tube cradle and slacken off the four 4 B.A. screws that are now revealed, releasing the rubber clamp ring around the tube neck. Slacken off the two bolts clamping the aluminium band around the tube bowl and lift the cradle off the tube, noting the relative position of the anode cap to the cradle. Thoroughly clean all parts and the inside of the cabinet before re-assembling in the reverse order.

The trickiest part is keeping the inside of the mask free from fluff and hair during reassembly and also the refitting of the rubber dust excluder. This is best done by stretching the rubber around the circular front clamp before refitting the mask, pulling it forward off the brass studs at each corner to which the mask is attached. Once the mask is in position the dust excluder can be slipped over the gap between the tube and the mask. Make sure that the mask is squarely on the tube at right angles to the line of the gun or else difficulty may be experienced in refitting the cradle to the cabinet.

This is the next step, and any small gap between the mask and the cabinet may be taken up by inserting slotted washers provided under the appropriate 2 B.A. bolts. When the tube cradle is snug, tighten all down, invert the cabinet and refit the chassis.

Setting Up

Picture tilt is accomplished by the lever on top of the deflector coils, and picture positioning by moving the entire focus assembly around in

the play provided by the two fixing screws. The focus lever should be vertical for correct focusing, and if this is not the correct setting the focus magnet should be slid up and down the tube neck, having slackened the four side screws, until good focus is obtained.

Corner Shadow

This may be experienced if the tube gun is not central and may not be corrected by the adjustments provided. It is then necessary to rotate the tube in the mask until a clear position is found, taking care not to hit the anode cap on the side supports, nor to leave it too close to one of them, causing flashover.

Fitting C.R.T. Transformers (A.C. Mains Only)

On models having CRM141 and 153 a 13 volt transformer will be required, on models with the CRM121B, 123, 151 and 152, a 2 volt transformer is required. The universal models TU169 and 211

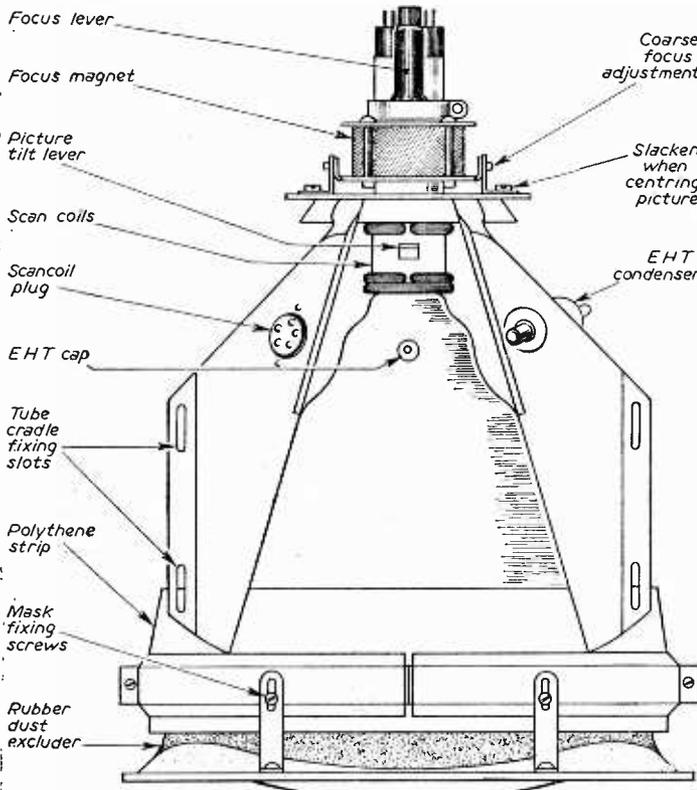


Fig. 6.—Detail of the T161 tube cradle assembly—top view.

fit the CRM122 which has a 7.5 volt heater in series with the heater chain and are treated similarly to the T231.

For the 13 v. and 2 v. types, remove the heater wires from the two pins on the tube adjacent to the keyway and tape them back. Do not short them together. Also remove all other components (particularly condensers) which are connected to the heater pins and connect the secondary of the C.R.T. transformer to the two empty pins by short freespaced leads. Mains for the primary may be obtained from between chassis and the copper bar behind the mains voltage adjuster.

If symptoms of heater-cathode breakdown cause intermittent bars of picture slip, a 1 K resistor can be fitted between heater and cathode. On models fitting the CRM122 the wires removed from the heater pins are taken across a 25 ohm 3 watt resistor to complete the heater chain. Mains for the transformer can be picked up between chassis and the green voltage adjusting lead.

Screen Cleaning

This involves removing the tube cradle as outlined above except the T205 and TC206 whose safety glass may be lifted up through the slot in the top of the cabinet after the metal fillet has been picked out.

Variations

On some consoles, such as the TC178, TC155, TC165, there is no need to remove the chassis before removing the tube cradle. This latter slides out complete on a wooden board which runs in a channel on the cabinet roof and is locked in position by two 2 B.A. bolts.

Earlier Models. T141 (Covering TU142, TC140, TRC139, TRC1124, 124, TC138, TS114, TS1114, TSC102, TSC1102)

In these models the tube is loosely mounted and is held firm by the mask, so care is needed in handling the chassis out of the cabinet. To unbox, remove the speaker leads and (on consoles) the control panel, remove the two 2 B.A. nuts and washers at the rear upper chassis corner flanges and withdraw the chassis complete with tube.

Remove the C.R.T. base and anode cap, slacken off the rubber clamp around the tube neck behind the focus bracket (which is all that holds the tube) and lift the tube out forwards. Replace in the reverse manner, adjusting the bowl support straps if necessary.

Boosting the tube is carried out as for the T161, with the exception of the TU142, which is treated as for the TU169. Console models with radio have an additional multiway plug connecting to the light behind the station names.

(To be continued)

Trans-oceanic TV

THROUGH the use of earth satellites as passive reflectors, trans-oceanic TV will be both economically and scientifically feasible, according to Dr. John R. Pierce, Bell Telephone Laboratories director of electrical communications research.

He told an IRE symposium in Washington that the best site for the relay system would be over the Atlantic between Newfoundland and Scotland. He proposed a series of 100lb. satellites 100ft. in diameter, with reflective metallised coating, revolving in a transpolar orbit 3,000 miles in space.

The satellites need have no electronic equipment in them. The signals would be bounced off them from 250ft. parabolic aerials on the ground, fed by 100 kW transmitters. He suggested frequencies of 1,500-2,000 or 8,000-10,000 Mc/s. A total of 24 such spheres would be sufficient for 99 per cent. continuity of contact, he added. He stressed the advantage of such passive reflectors: all of the electronic equipment is on the ground.

A TV OSCILLOSCOPE

THIS IS THE FIRST OF A SERIES OF ARTICLES DEALING WITH THE DESIGN OF A HIGH-GRADE OSCILLOSCOPE SUITABLE FOR TV EXPERIMENTERS

By R. Coates

THE oscilloscope is invaluable to the television experimenter, as he has to deal with repetitive circuits to a large extent. It is also particularly useful if it can be used to display the picture being received, without the use of the EHT supply and the magnetic deflection system, or even without the use of one of the timebases. The requirements of an oscilloscope designed specifically for television use are as follows:

1. The timebase should have a frequency range of at least 10 c/s to 15 kc/s, although an upper limit nearer 100 kc/s would be very useful on occasions.
2. The trace should be perfectly linear.
3. The fly-back should be suppressed.
4. The timebase should be capable of very accurate synchronisation.
5. The Y-amplifier should have a wide bandwidth, which is best accomplished by the use of negative feedback.
6. The gain of the Y-amplifier should be high, and a full trace should be obtainable from an input of three millivolts. The gain should also be variable.
7. Facilities should be provided for displaying the television picture on the screen.
8. The design should ensure maximum tube life consistent with adequate performance.
9. A refinement would be the provision of a valve voltmeter to measure the A.C. component of the signal being inspected.
10. The instrument should have a very high input impedance, so as to have a negligible effect on the circuit under observation.

The choice of tube colour, afterglow, etc., is a matter of individual preference, and will not be discussed.

The question of mechanical design will be discussed, but nothing will be specified, as these articles are not intended merely to set forth the details of one particular design for all to copy or leave alone, but rather to show the principles of design.

Mechanical Design

The majority of oscilloscopes built, both commercially and privately, consist simply of a box with the tube face vertical and flush with the front panel. This design is usually adopted because it is simple, but it suffers from some severe disadvantages. In the first place, it is rarely convenient to have the tube face vertical, as it should then be observed from its own plane, and the whole unit must then either be tilted back or raised to the level of the observer's eyes in order to allow the trace to be viewed with minimum strain. This can be overcome in several ways: one way is to make the box so shaped that the tube face is angled, but the top should still be horizontal, so as to allow other

equipment to be placed on top. Alternatively, the box may open at the centre, with a hinge at the back so that the top half may tip up when in use: this type is economical in storage space, but not in bench space, as the top is not level when in use. Another alternative is to build the tube into a completely separate box, which may be of very small dimensions, and which may be placed conveniently anywhere. This type, however, lacks portability.

The second disadvantage of the majority of instruments is that the tube face is flush with the front panel. A hood then has to be fitted to the front in order to reduce the distractions owing to the reflection of stray light from the surroundings by the tube face. The hood is inconvenient as it collects dust and protrudes from the face of the unit: the best remedy is to build the unit with the tube face recessed in a matt black painted cavity in the front of the panel which will exclude all unwanted light. Another alternative is that the tube may be mounted vertically, and viewed by means of a mirror mounted at 45°

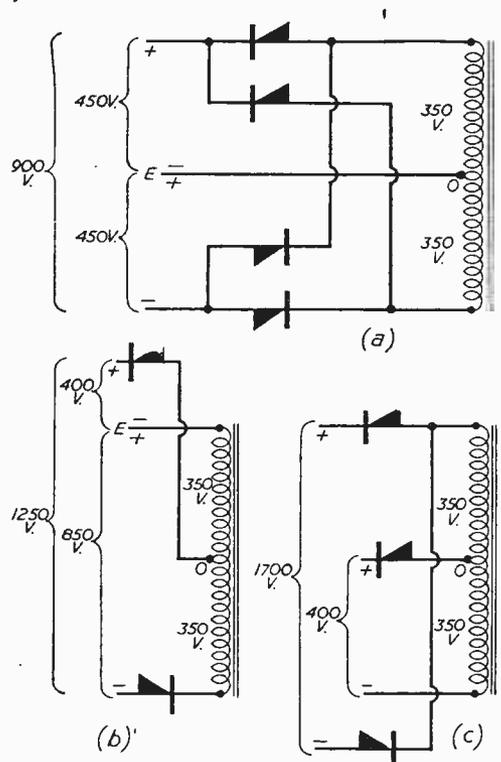


Fig. 1.—Power supply arrangements suitable for oscilloscopes: (a) full-wave rectifiers; (b) half-wave rectifiers; (c) voltage doubling.

deg. from the horizontal above it. The mirror should preferably be a metal one, in order, to avoid the possibility of multiple reflections.

The front panel should be clearly marked, the knobs of adequate size and well spaced. As regards the internal layout, the high-gain sections appropriate to the X and Y channels should be kept well apart, and certainly screened from each other. The case may be made of wood or metal, but if the former is used care should be taken to ensure adequate internal screening. One factor which should not be overlooked is the possibility of picking up 50 c/s magnetic hum on the tube deflection system. The best safeguard against this is the provision of a mu-metal screen around the tube. The mains transformer is best situated near the base of the tube.

Choosing the Tube

The choice of tube is a very important matter, as this governs the design of the rest of the instrument in almost every detail. It is not wise to be guided by size alone: the tube is intended for viewing by one person at a time, so a large size is not necessary. Furthermore, the larger the tube face, the higher the voltages required to operate it, so not only does the tube cost more, but so do the power supply components and the amplifier and timebase units. Accordingly, the best choice seems to lie in the range between a 3in. diameter screen and a 5in., although 2½in. screens are very useful and are becoming popular for general purposes.

Power Supplies

The tube selected, data sheets can be consulted to determine what supply voltages are needed. Note that the highest voltages recommended should not necessarily be chosen. The higher the final anode voltage, the higher is the voltage required to deflect the spot the same amount. A typical deflection sensitivity, for instance, is 400V/mm. per volt, where V is the final anode voltage on the tube, so that if V is increased, then the outputs required from the amplifier and timebase units are also increased. Another point to bear in mind is that the tube life decreases with excessive final anode voltage, so it is better to use, not the highest value of EHT recommended, but rather the lowest.

The EHT voltage thus selected, the mains transformer may be specified. Remember that the D.C. rectified voltage will be higher than the A.C. voltage from which it is obtained: for instance, a 700 volt R.M.S. winding will probably give an EHT of about 900 volts after smoothing. This supply will be adequate for the operation of most small tubes, and it may easily be obtained by using the full winding of a 350-0-350 volt H.T. transformer. Higher voltages may be obtained with larger secondaries, or by voltage doubling. For economy, the same mains transformer should be used to supply the H.T. to the amplifiers and timebase circuits, and the value of the H.T. voltage is commonly about half that of the tube circuit. A number of suitable power supply arrangements are shown in Fig. 1. If higher or intermediate voltages are required, the secondary voltage of the transformer should be altered

proportionately: the output voltages marked are those which may be reasonably expected, but will vary with the load and smoothing arrangements. The ratings of the rectifiers in cases (a) and (b) will be obvious, and the smoothing capacitors should all be connected to earth.

Valve rectifiers may be used if preferred, but care should be taken over the heater supplies: in (a) the top pair of rectifiers may be a conventional double diode, with its own heater supply, but the other two should be separate valves each with a separate heater supply. Similarly in (b), the two valves should each have their own heater supply. In (c), the H.T. rectifier is normal, and the capacitor should be connected in the normal way between + and -, but the other two rectifiers should each be of 700 volts R.M.S. rating, and two sets of smoothing capacitors should be used, one from each rectifier to the negative side of the H.T. supply.

These capacitors should each be 1,000 volts working, that is, half the EHT voltage. Circuit (a) is recommended, as it provides full-wave rectification of both H.T. and EHT, and 900 volts will meet most needs. A valve rectifier is very suitable for the H.T. supply, but

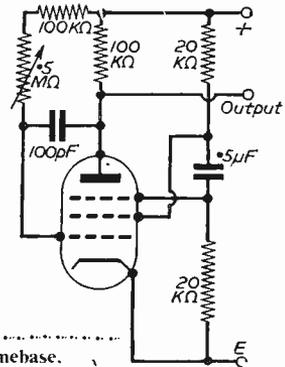


Fig. 2.—The Miller timebase.

metal rectifiers are recommended in the other cases, owing to the additional heater supplies which would be required if valves were used. Circuit (b) should be used if the EHT obtainable from circuit (a) is insufficient, but suffers from being only a half-wave rectifier. Circuit (c) is not recommended except in exceptional circumstances, and two mains transformers are better.

In the tube data, will be found values given for the voltages on all the tube electrodes: these are normally supplied from a potential divider. We must therefore connect a bleeder chain across the EHT supply, and, for convenience, assume that this chain takes 1 mA and that the tube takes a negligible current. In the first place, the anode should be connected to the positive terminal of the supply, and we then look up the voltage required on the focusing anode: this will be variable, as this constitutes the focusing control, and may be from, say, 650 to 800 volts negative relative to the final anode. Thus, we require to drop 650 volts in the resistor to be connected as a part of the bleeder chain from the focusing anode to the final anode, and, as the chain current is 1 mA, we see that this resistor should be 650 kΩ. The focusing anode, voltage must be variable, so the next resistor must be a potentiometer with the focusing anode connected to the slider: the voltage is required to vary by 150 volts, so 150 volts must be dropped in the potentiometer, whose value is thus 150 kΩ.

Similarly, if the cathode is to be at 75 volts negative with respect to the focusing anode, then 75 k Ω is connected between these electrodes. If the grid is to be variable (brightness control) from cathode potential to -25 volts from the cathode, then it is connected to the slider of another potentiometer of 25 k Ω this time, this being connected between cathode and EHT negative. We can now check our calculations, as the total resistance in k Ω between the positive supply and the negative should be equal to the expected voltage in volts. In the above example, we see that $650 + 150 + 75 + 25 = 900$. Alternatively, the bleed chain current may be taken as $\frac{1}{2}$ mA, when all the resistance values will be doubled. There is no need to adhere rigidly to the calculated values, as the nearest preferred value will be good enough. Don't forget to connect the cathode to one side of the heater. When testing the tube circuit, do not allow the deflector plates to "float": they should be connected to the anode, each through a resistor.

Timebase Selection

So far as the amateur is concerned, linearity of the timebase is of supreme importance to him. There are a number of very good designs of timebase available, and one which was used very extensively at one time is the Puckle. Nowadays, however, it is being replaced by the Miller timebase, so called because it operates by virtue of a large capacity between anode and grid. The thyratron timebase, which many people still use, is now well out-dated by both these types. We will consider primarily the Miller, as it is well known that this circuit gives an output which can virtually be guaranteed to be linear without any investigation. Also, the Miller is economical, as it requires only one pentode, compared with the Puckle's requirement of two pentodes and a triode.

The circuit is given in Fig. 2 together with suggested values for the components. No attempt will be made to explain the circuit action, as this subject is well covered in the series "Relaxation Oscillators." The fine frequency control has a limiting resistor in series with it to prevent the grid from being connected directly to H.T. The value of the Miller capacitor shown will give a fairly high frequency output, and 0.001 μ F or even 0.01 μ F may be used here. The values shown for the screen-suppressor chain will give a fairly fast fly-back, and the only value which should need alteration to any great extent is that of the anode load: there is an optimum value for this resistor, which is easily found, as it corresponds with minimum frequency. If the value of this resistor is too large, the Miller capacitor will not charge adequately between strokes; if it is too small, the suppressor will tend to cut off the anode current too soon: each of these faults raise the frequency, so the resistor should be adjusted for minimum frequency.

Looking back at the original specification, we see that this circuit is capable of fulfilling all the requirements: the frequency range can easily be adjusted over a wide range, the trace is as linear as one can reasonably expect; fly-back suppression signal is available at screen,

and synchronisation may be injected at the screen in the form of negative pulses. The valve may be any high-gain pentode, such as the 6AM6, or EF91, and the output voltage may well be as much as 200 volts peak-to-peak. For a deflection sensitivity of 400/V mm./volt. and an EHT of 900 volts, this will give a trace of about 9 cm., which should be adequate for most applications. If it is too great, it may be reduced best by taking the output from a tap on the anode load: this tap may be variable, i.e., a potentiometer, if desired.


If the power supply arrangement is as Fig. 1 (a), i.e., the H.T. positive terminal is common with the EHT positive, also in Fig. 1 (b), then there is no need for a coupling capacitor between the timebase and X-plate: the anode of the pentode should be connected directly to the left-hand deflection plate. As the deflection plate will then have a mean voltage below that of the H.T. supply voltage, a shift voltage must be applied to the other plate in order to make the mean voltage between the plates equal to zero in order that the trace may be central. This D.C. voltage may conveniently be made variable, by connecting the X-plate to the slider of a potentiometer connected between H.T.+ and a point about 200 volts below H.T., this may be accomplished most easily by making the potentiometer, say, 1 M Ω and connecting a 1 M Ω fixed resistor between the lower end of this potentiometer and earth. The detailed adjustments of these values is not of importance.

Other Timebases

The circuit described above is the main member of a large family of timebases; many modifications have been put forward for its improvement, but it is quite adequate for our purposes in its original form. Other forms have appeared, some of them using more than one valve, but all depending on the negative feedback by the Miller effect for the linearity.

Practically all other timebase circuits depend for their action on the direct charging or discharging of a

Fig. 3.—The "long-tailed" pair.

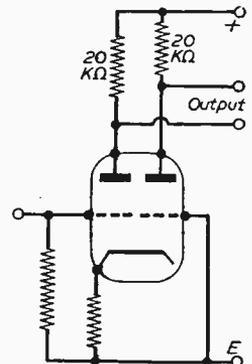

capacitor: this may certainly be made far more linear in output if the charging is done through a pentode connected so as to feed a constant current

through the capacitor. This pentode often has a potentiometer fitted to control the voltage of one of the grids, which forms a control of the current in the capacitor circuit and hence a control of the rate of charge, which controls frequency. Coarse frequency is controlled by switching in various values of capacity, between anode and grid (see Fig. 2). The 0.5 M Ω potentiometer then forms a fine frequency control on each range.

(To be continued)

Relaxation Oscillators—4

THE MILLER TIMEBASE OR SCREEN-COUPLED PHANTASTRON

By R. Couvela

(Continued from page 349 of the February issue)

THE Miller sweep generator is in a class of its own so far as operating principles are concerned, but it comes under the general heading with which we are concerned here, which is the reason for its inclusion. No attempt will be made to show the derivation of the circuit, we will merely deal with its operation.

A glance at the circuit of Fig. 1 will show why it is called the Miller circuit. The capacitor C is seen to be connected directly in parallel with the anode-grid capacitance, the cause of the Miller effect, which was so much of a stumbling-block in the early days of electronics. Since those days, several circuits have been published making use of the effect, or even, as in this case, increasing it.

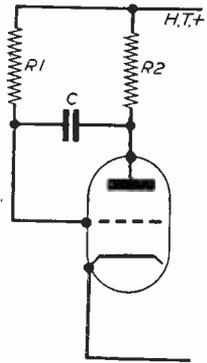


Fig. 1.—The Miller sweep generator.

The effect is that, by virtue of the anode-grid capacitance, any signal which is applied to the grid will, after being amplified, appear at the anode, and return through this stray capacity in the form of severe negative feedback. This effect naturally increases with frequency, and renders the triode useless at high frequencies, and led to the invention of the pentode.

Consider now the effect of applying H.T. to the circuit of Fig. 1. Current will flow in two paths: firstly, it will flow through R1 to the grid, and so to the cathode, using these electrodes as a diode. As the grid-cathode path is of very low resistance, the current will be approximately $I_g = H.T./R1$. If R1 is made sufficiently high, this current will be very small.

Let us assume, temporarily, that the valve will not conduct, in which case, the second current path will be rapidly charging C exponentially through R2 towards H.T. value. The lower end of C will be held at a potential very little above that of earth by the grid-cathode diode effect.

Now, suppose that Ia suddenly starts to flow. Immediately, Va will drop, and, as C is charged, Vg will drop by the same amount. But if Vg drops by more than a few volts, the valve will be cut off, so the circuit will find a point where balance is obtained somewhere between cut-off and full current, in fact, nearer to the former. Note the Miller effect of negative feedback, by which the change in anode voltage is immediately fed to the grid, opposing the change.

Now, observe that the bottom end of R1 has been taken below earth potential, while the top end remains at H.T. level. Current must flow in this resistor, but, since the grid is negative

with respect to the cathode, grid current cannot flow as before. In fact, this resistor attempts to discharge the capacitor, and current flows from H.T. through R1 into C. Accordingly, current must flow from the other plate of C to the anode, and thence via the cathode to earth.

Thus, C discharges, but only very slowly, as R1 has already been stated to be of a high value. Notice that the bottom end of C is held just below zero, so the current in R1 will be for all practical purposes a constant value. As C discharges, its voltage reduces, and, as the discharge current is constant, the rate of reduction of voltage will be constant. Thus, the anode will reduce in voltage at a perfectly linear rate, and all the time the negative feedback Miller effect is holding the grid below zero in order to retain equilibrium, this fact causing the current through R1 to remain constant, thus preserving the linearity.

As the anode voltage of the valve falls to a very low value, so the current must increase in order to take up the additional voltage on R2. As the current increases, so the grid voltage must rise slightly. This rise will only slightly affect the current in R1 as the voltage across this resistor is given by $V_{R1} = H.T. - V_{g-k}$

As an example, if the H.T. is 300 volts, and V_{g-k} is, say, (-6) at the start of the discharge, the total voltage on R1 is $300 - (-6) = 306$ volts. If V_{g-k} falls to, say, -3 volts

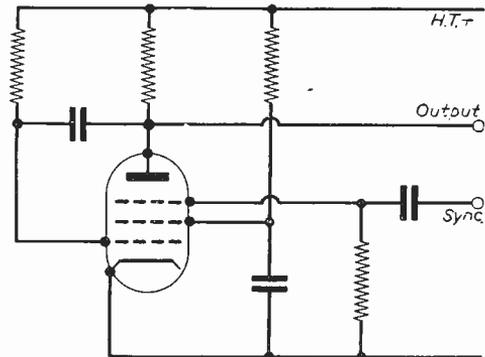


Fig. 2.—The practical version of the Miller sweep generator.

towards the end of the discharge, then the total voltage on R1 will become $300 - (-3) = 303$ volts. Thus, the total change in the voltage on R1 is less than one per cent., so the total change in current will be less than one per cent., and can be ignored. Thus we can say, with all confidence, that the run-down section of the waveform is a straight line.

There remains one point to be cleared up. You will recall that at the start we assumed that Ia was cut off, although grid current was

flowing. How is that to be brought about? In Fig. 2 we have changed the valve to a pentode, and the required anode current cut-off can now be brought about quite simply, by applying a high negative potential to the suppressor grid. All the cathode current will then flow to the screen.

Thus, we see that we have the makings of a triggered sweep generator. The action is controlled by the reception of negative pulses at regular intervals on the suppressor. During one such pulse, the anode current is cut off, and the capacitor charges to full H.T. At the end of the pulse, we commence the linear run-down, which continues until the next pulse, when the anode is again cut off, and the action is repeated.

We now have to find a convenient source of large negative pulses, which we can obtain from the transitron relaxation oscillator. Readers will remember the transitron oscillator as described in Part 2 of this series, and the circuit is

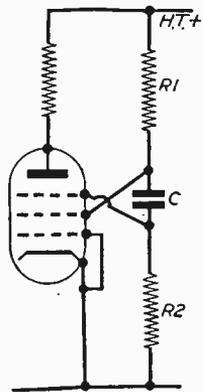


Fig. 3.—The transitron oscillator.

shown in Fig. 3.

This circuit, you will remember, gave a square wave output at the anode. In fact, the anode and screen currents alternated with equal time durations. Notice that in this circuit the anode and control grid, which are required for use in Fig. 2, are not used, thus making the arrangement eminently suitable in the present application. Thus, we can couple the two circuits together to produce the circuit which goes by the amazing name of the Screen-coupled Phantastron, shown in Fig. 4. The circuit components are so adjusted as to give an oscillation frequency in the transitron very considerably greater than that of the required timebase.

Now, if we consider the moment when the

screen is conducting, the Miller capacitor is charging, and the anode is cut off, we find that the suppressor voltage is rising from a negative value towards zero. On reaching a suitable value, anode current is permitted to start, and the transitron action cuts off the screen current, and raises the suppressor voltage to a high value.

The anode current thus permitted is limited by the Miller action, and the run-down commences. Meanwhile the suppressor returns towards zero. On reaching zero, a landslide would normally take place, but this is effectively prevented by the fact that the control grid is now holding the cathode current to a low level, preventing any rise in screen current, thus preventing a landslide, and the valve operates under conventional pentode conditions.

Ultimately the voltage on the anode drops to a low level in the region of that of the screen grid, and the Miller action fails to function effectively when the curved portion of the characteristic is reached. Thus, the control grid potential rises, allowing cathode current to flow freely and the screen conducts, which results in a landslide. The screen goes into full conduction, the suppressor is well below zero, the anode is cut off, and the Miller capacitor charges. As the suppressor voltage rises to a suitable value, the return landslide occurs, and the action is repeated.

Note that the screen conducts heavily during the flyback. This permits the use of the pulse signal on this electrode as a means of flyback suppression, if required. The screen grid is then connected via a capacitor to the grid of the cathode-ray tube.

(To be continued)

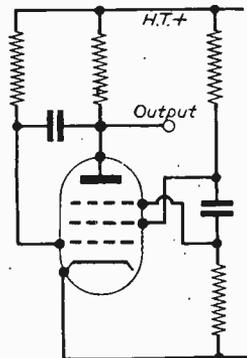


Fig. 4.—The Miller time-base generator (Screen-coupled Phantastron).

Trans-Atlantic TV

THE possibility of transmitting satisfactory television signals across the Atlantic Ocean has occupied the attention of engineers for some time. A multiple cable would meet the case, but in view of the video signal bandwidth, it is commercially uneconomic. One suggestion which seemed quite feasible was to make use of existing aircraft which make regular trans-Atlantic crossings, by having low-powered radio transmitters installed in the aircraft. These machines would receive a television signal at a great height and relay it through the medium of the transmitter to another aircraft in flight, this process being repeated until the expanse of the ocean was covered in hops. The signals received finally at the other side of the Atlantic would be suitable for rebroadcasting.

Space Satellites

Now that space satellites have become a possibility, the latest suggestion is to use one or more of these man-made devices to relay or reflect television signals so that they can cover the required distance. Scientists have worked out the size of the satellite and the distance from the earth for this to happen when using a low-powered transmitter and with a number of these satellites in orbit round the earth, there would always be one in the correct position to relay the signals. Very high frequency carrier signals would be required and special dish aerials employed for final ground reception, but even so this nebulous idea has not been dismissed as impracticable. Indeed, some such scheme has undoubtedly been used both by Russia and the U.S.A. H. J. B. C.

Transistors in TV Receivers

THE THIRD ARTICLE OF A SHORT SERIES DEALING WITH THE USE OF TRANSISTORS IN MODERN TELEVISION EQUIPMENT

(Continued from page 357 of the February issue)

THE circuit used for the Beanstalk amplifier is shown in Fig. 8. The basic idea behind the operation is best understood by considering two transistors only, Tr18 and Tr19, and visualising the circuit above the point A as replaced by a resistive load of small value. Considering a fixed output current swing, the potential swing at point A will depend entirely on the resistance load owing to the high-impedance characteristics of the transistor. The potential swing at point B will depend entirely on the effective resistance in the base circuit of the transistor Tr19. If the resistance is low then the potential swing at point B will be small; all the swing will appear across the second transistor Tr19. If the resistance is high then the potential swing at point B will be large.

In the Beanstalk video amplifier, the effective base resistance is made relatively high in a controlled manner by feedback via a low impedance potentiometer chain fed from the collector of the upper transistor (R88, R87). Thus, in the case we have been considering, the potential swings are shared equally.

In the television receiver being discussed five experimental transistors are used in series in the video stage. The potential swings are equalised across the five transistors by potentiometer chains R94, R93, R92, R90, R91, R89, R88, R87. To minimise the effects of the current taken in these potentiometer chains the lower resistances are appropriately valued and returned to convenient points up the chain rather than to ground.

The overall gain of the amplifier will depend primarily on the load resistance, the a^1/r in the lower transistor Tr18 and the emitter resistance, R86. If, at this stage in the description, it is assumed that the transistors will not limit the frequency response then we may consider the load network (R95, L34, etc.) chosen in the usual manner for an anode-compensated video stage. There will be some reductions in shunt capacitance of which advantage may be taken (e.g., collector capacitance lower than usual anode capacitance, no valve holder, no noise limiter, lower synchronising pulse separator loading, and possibility of less wiring-capacitance as the small video amplifier may be mounted close to the tube base).

With the load resistance (4.2 K Ω) and the emitter resistance chosen for this stage and the experimental transistor (Tr18) used at the bottom of the Beanstalk the overall voltage gain is approximately 50 times. Thus as the same potential swing occurs at the collector of each transi-

tor the individual voltage gains will be: Tr18, 10 times; Tr19, 2 times; Tr20, 1.5 times; Tr21, 1.33 times; and Tr22, 1.25 times. From this distribution of the voltage gain a number of things follow.

First, the Miller capacitance effect for the first transistor Tr18 is considerable, and a low impedance signal source is essential. In order that the detector load impedance may be kept sufficiently high to achieve good efficiency a grounded collector stage (Tr17) is, therefore, used as a buffer. The presence of this buffer in turn means that the fl of the lowest transistor is not so

The information given in this short series is taken, with permission, from a Paper read to the Television Society by B. R. Overton, B.Sc.(Eng.), A.M.I.E.E., and published in the Journal of that Society.

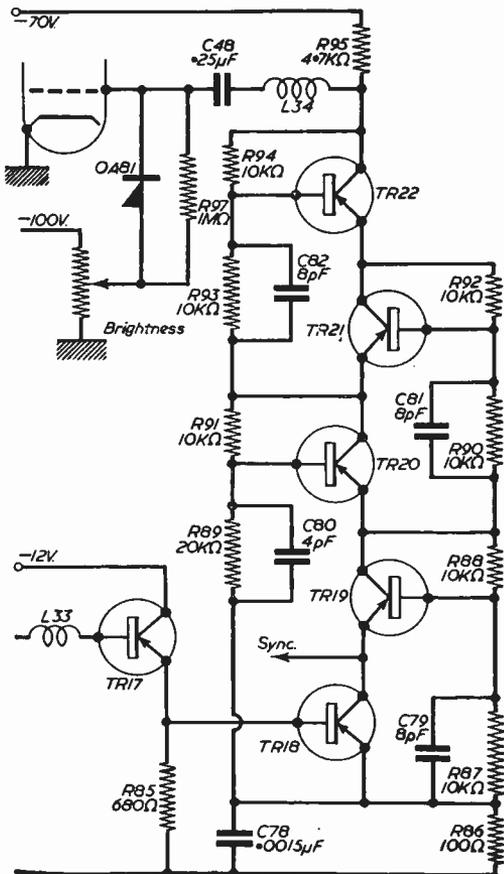


Fig. 8.—Beanstalk video amplifier.

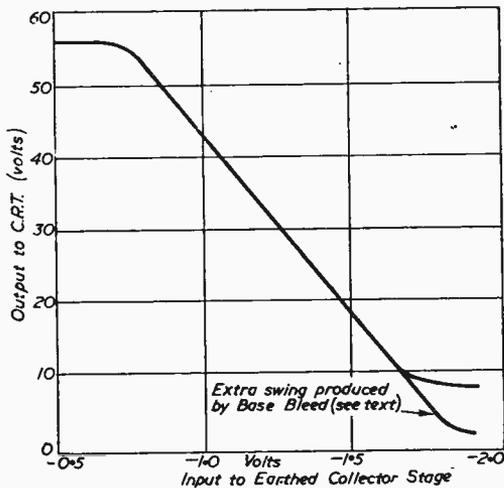


Fig. 9.—Transfer characteristic of video amplifier.

important. In fact, the driving impedance is so low that even with an f_l of 30 Mc/s and a gain of 10 times the transistor Tr18 does not influence the high frequency response of the amplifier.

Second, the upper transistors (Tr19, Tr20, Tr21, Tr22) are relatively non-critical so far as such properties as a' and f_l are concerned. This can be seen, of course, very readily by considering the top four transistors as subject to heavy negative feedback. In fact some compensation for poor high frequency performance of these transistors can be made by increasing the value of the capacitors, C82, C81, C80 and C79, which otherwise balance the effect of the transistor collector-to-base capacitance in the feedback potentiometers. High frequency compensation (R86, C78) is included in the emitter of the transistor Tr18. This compensation may be used to make up for deficiencies in the high frequency performance of the transistor Tr18 or, of course, the video output load network, or the I.F. amplifier. Also the emitter resistance R86 (being large in comparison with r_e) linearises the transfer characteristic.

The output from a video amplifier may be limited by the dissipation or the voltage rating of the transistors. In the example under consideration the dissipation limit of 50 mW per transistor was the limiting factor. Thus the total dissipation (250 mW) and the load resistor (4.2 K Ω) can be used to determine the maximum voltage (60 v. approximately) across the beanstalk by settling the position of the load line on the collector characteristic. The load line also shows the maximum current (15 mA approximately) which should flow for maximum output potential swing.

However, the theoretical swing is not achieved at the low collector potential for the following reason. At full collector current the base current is considerable. This must flow through the base bias network and the lowest collector potential will be set by the necessity to provide the base current. As an example take a base current of 0.1 mA corresponding to a collector

current of 13 mA for transistor Tr19. A current of 0.1 mA flowing in resistor R88 (10 k) means that point A (the collector of Tr12) must be 1 volt more negative than the base. The excess potential at the collector of Tr20 includes that of the previous transistor (Tr19) but must, besides providing its own base current, take account of the current flowing in the potentiometer resistor R89. Thus the effect is cumulative. Of course, the potentiometer resistors can be reduced in value, but as they shunt the load resistor its value must be increased and also the H.T. potential must be increased to restore the voltage conditions for the transistors cut-off. Alternatively, resistors may be connected from each base to the video stage H.T. line valued (say, about 700 K Ω) to provide the base current for bottoming. The lower potentiometer resistor may be adjusted to restore the cut-off conditions. To be completely successful this method involves choosing the extra bleed resistors to suit the a' of the individual transistors.

The transfer characteristic of the complete video amplifier is shown in Fig. 9. The sharp limiting of the transfer characteristic means that a noise limiter is superfluous, at least at present, when the limited drive is likely to be used to its fullest extent.

The D.C. restorer is used to eliminate any D.C. drift in the video amplifier with temperature. Quite clearly this question of D.C. drift will be a very important problem if cathode drive has to be used and a conventional D.C. restorer could not be used conveniently. Furthermore, a direct coupled cathode drive arrangement requires a further negative bias supply for the cathode ray tube grid.


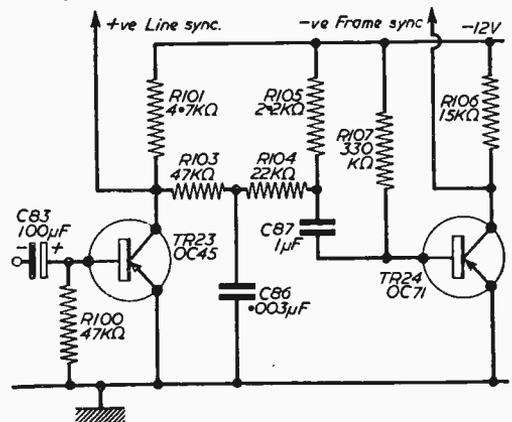


Fig. 10.—Synchronising pulse separator.

As has already been indicated the first really practical and cheap solution to the problem of video drive may be a compromise—the transistor designer contributing something and the tube designer something. Perhaps the transistor designer will make his contribution first and then the two or three stage Beanstalk may enjoy a temporary popularity. Here is a field in which there is plenty of room for ingenuity and invention.

(To be continued)

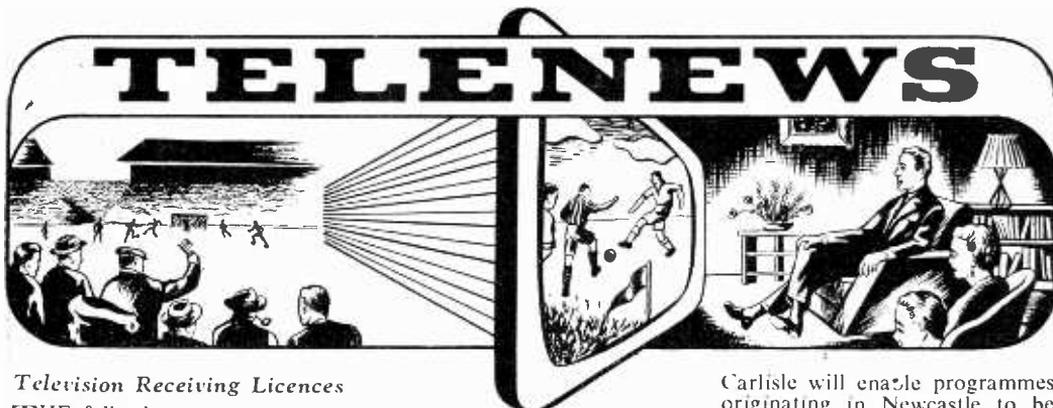

Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of December, 1958, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,654,716
Home Counties	1,135,782
Midland	1,394,921
North Eastern	1,440,666
North Western	1,230,017
South Western	720,061
Wales and Border Counties	520,778
Total England and Wales	8,096,941
Scotland	703,697
Northern Ireland	98,429
Grand Total	8,899,067

Training Young Scientists

TO help meet the national shortage of scientists and to assist Science teachers, the BBC is prepared to expand its present TV schools programmes. The Director General of the BBC, Sir Ian Jacob, told the School Broadcasting Council "If there is a national need, we are a national institution, with a duty of filling it." Sir Ian said that the Presidents of certain associations had called on him recently to urge that the BBC should do its best to interest people in science. The BBC, he said, proposed to put all the resources it could behind this job. As the world pioneer of schools programmes in sound radio, the BBC was well placed to expand its present experimental television service to schools. But TV costs six times as much as sound. Given the money, channel space and support from the educational authorities, the BBC was ready

to increase its already great effort for education.

Post Office Links for I.T.A. Transmitter at Burnhope

NOW that I.T.A. has opened its new transmitter at Burnhope a variety of vision links have been provided by the Post Office. The station is joined by a single-way link to the Newcastle Studios of Tynes Tees Television. Programmes from the main I.T.A. network are received over a single-way

link from Telephone House, Manchester. The routing involves both land line and radio links, radio being used on the section between Carlisle and the Post Office radio station at Pontop Pike. A new Post Office network switching centre at Telephone House, Newcastle, has been set up to handle both network and local programmes.

Some eight miles of additional coaxial cable has been laid to provide the land lines and many new sections have been added to existing ductways. Later in the year the radio link will provide a two-way service and this with other new work at

Carlisle will enable programmes originating in Newcastle to be radiated northward and southward to cover the whole I.T.A. national network.

New Soviet TV Installation

N. KUPREVICH, senior scientific worker at the Pulkovo Astronomical Observatory, designed a TV installation for astronomical observations and is perfecting it now. He has introduced new more sensitive transmitting tubes and reception tubes with increased brightness. He can take snapshots of the moon, Mars and Jupiter, etc.,



N. Kuprevich adjusts the reflector telescope to watch the moon.

with the aid of the reflector telescopes having a mirror with a diameter of 300 mm. and a focal length of 18 metres, and scores of photographs of the moon and Mars have already been taken.

BBC Appointment

THE BBC announces the appointment of Mr. J. S. Clemo as Engineer-in-Charge of the Rosemarkie Television and V.H.F. Sound Broadcasting Station in succession to Mr. M. Clough who recently became Assistant Engineer-in-Charge at the BBC's high-power station at Holme Moss.

Mr. Clemo joined the BBC at the Redruth Transmitting Station in 1944. After serving at a number of the Corporation's transmitting stations, first as a technical assistant and later as an engineer, he was transferred in 1954 to the BBC's television and V.H.F. sound broadcasting station at North Hessay Tor in Devon, from where he takes up his present post.

Southern ITV Increase

A MID-NOVEMBER survey of the Southern ITV area—the fourth carried out in that area by Television Audience Measurement Limited (TAM) since Southern Television Limited began operations on August 30th—reveals that 260,000 homes were then receiving ITV transmissions from Chillerton Down, an increase of 79,000 over the opening night total of 181,000.

An encouraging feature of ITV progress in the area was that after only two and a half months of ITV transmissions, 30 per cent. of all private households were receiving ITV programmes compared with 22 per cent. and 26 per cent. recorded in the Scottish and South Wales and the West of England ITV areas respectively, after a similar period.

Independent Television in Northern Ireland

THE INDEPENDENT TELEVISION AUTHORITY has decided to accept, subject to contract, the application of a group under the chairmanship of the Earl of Antrim to provide the programmes for transmission from its Northern Ireland sta-

tion to be built at Black Mountain, near Belfast. It is planned to begin programme transmissions from this station at the end of 1959.

The group will be controlled by residents of Northern Ireland and will have its headquarters and studios in Belfast.

It represents a wide diversity of professions and industries in Northern Ireland, together with varied educational, journalistic, social and cultural interests.

The Black Mountain station will bring independent television programmes within reach of over one million people and the service area will include practically the whole of Northern Ireland with the exception of Fermanagh, the western parts of the counties of Tyrone and Londonderry, a small part of County Down in the Warrenpoint and Kilkeel area and the Antrim coast from Larne to Portrush.


Giant Tokyo Tower

SIX-YEAR-OLD Yoshiko Maeda, daughter of the President of the Tokyo Tower Corporation, performed the ceremony of opening the 1,090ft. high TV tower in Tokyo, the world's tallest independent tower, recently. She took the place of Crown Prince Akihito who could not perform the ceremony because of prior engagements.

"Town and Around"

LONDON and south-east England, embracing over ten counties and a population larger than several European countries, now has its own news magazine on BBC television.

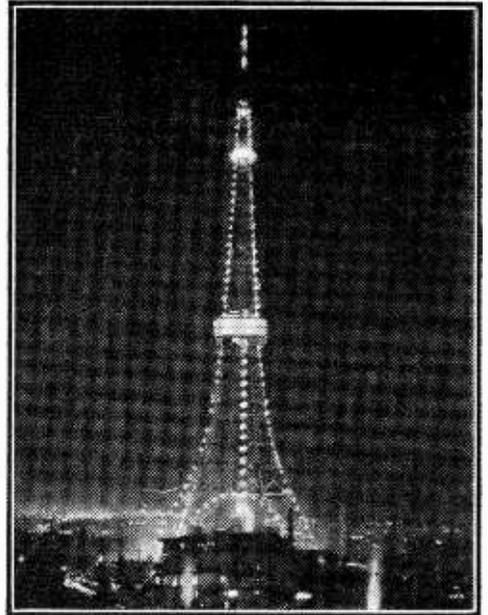The programme goes under the title "Town and Around," and it has its own special team of presenters, distinct from the three National newsreaders, and



The giant Tokyo Tower illuminated after the opening ceremony had been performed by a six-year-old girl.

a woman is among those selected after a series of camera tests in the news studio at Alexandra Palace. The initial panel consists of John Ellison, Nan Winton, Robert Gladwell and John Tidmarsh.

Two Million London ITV Homes

THE number of ITV homes in the London ITV area now exceeds the two million mark. It means that 44 per cent. of all London's 4,490,000 private households can now view ITV programmes, reports Television Audience Measurement Limited (TAM). This compares with a homes viewing audience of only 190,000 (5 per cent. of all homes) when ITV first began operations in the London ITV area slightly more than three years ago. As to individuals within these homes, the number of ITV viewers has multiplied almost ten times—from the opening night figure of 670,000 to the current total of some 6,680,000.

The number of ITV homes viewing both weekday and weekend programmes now regularly exceeds 1,400,000 at peak viewing periods.

Radar or Radio -



TRAIN WITH THE ROYAL AIR FORCE



There are immediate vacancies today for Radar and Wireless Mechanics in the Royal Air Force. This is an increasingly important job in the R.A.F. and a responsible one, because there is a constantly growing range of vital equipment to be maintained and serviced—including that used for bombing and for the navigation, detection, interception and control of aircraft and the latest guided missiles.

A life of opportunity!

You get a full training in servicing many types of radar or radio. Your work is full of interest—particularly if you are keen on television or radio. Promotion is rapid for the right man. Pay and allowances are better than ever before; for example, a married Corporal can earn £14. 12s. 10d. a week including full allowances. There's a month's leave a year, the chance to travel and see something of the world and all the wider interests of life in the modern Service. This is not just a job but a *career*—with good prospects. Post the coupon for details now!

TO *The Officer Commanding, R.A.F. Central Recruiting Office (PTN.56), Victory House, Kingsway, London, W.C.2.*

Please send me

R.A.F. Ground Trade leaflets A.M.P. 347 and Inf. 263. I understand that this puts me under **NO OBLIGATION.**

NAME _____

ADDRESS _____

_____ Date of Birth _____

Applicants from British Isles only.

Suffolk Tubes Ltd. offer you the finest service there is for the complete rebuilding of your Cathode Ray Tube. Using the very latest equipment, each tube is rebuilt to manufacturers' specification.

HAVE THAT TV TUBE REBUILT

Consider these points : 72 hour delivery Service ; free delivery by our own fleet of vans in the London area ; plus a 7 MONTHS' GUARANTEE from the INVOICE DATE. With prices that are only a fraction of the cost of a new tube.

As an extra service we can supply 12in., 14in., 17in. and 21in. rebuilt tubes off-the-shelf with complete new Gun Units, write now for full details and prices (trade terms available) to :

SUFFOLK TUBES LTD.

SUFFOLK HALL,
1-3, UPPER RICHMOND
ROAD, LONDON, S.W.15.
Telephone : VAN 4304, 5267.



SILICONE COATED MAINS DROPPER RESISTORS

Available in the following types :
 Midget Type .1 amp. 2,000 ohms 5/3
 .15 amp. 1,500 ohms 5/3
 Standard Type .2 amp. 1,000 ohms 6/-
 .3 amp. 1,000 ohms 6/-
 Long Type .2 amp. 1,000 ohms 6/-
 .3 amp. 1,000 ohms 6/-
 The above droppers have a fixed clip at each end and 2 slider clips.

CARBON TRACK DUAL GANG POTENTIOMETERS

Type SP5—3 K. linear Front Section.
 1 M. log Rear Section D.F.S. Used in English Elec. T40-T41-C42. 13/6 each.
 Type SP32—20 K. linear Front Section.
 1 meg. log Rear Section D.F.S. Used in Bush T.V. 53, T.V. 56, T.V. 57 and TUH 58. 13/6 each.
 Clarostat 37. Dimensions : 1 1/2 in. diameter, depth of case without switch 19/32 in., spindle diameter 1/4 in., length 2 1/2 in., with full length flat. Type 37 Less Switch, available in 5 K., 10 K., 25 K., 50 K., 100 K., 1 meg., 1 meg., 1 meg., 2 meg., 2/10 each.
 37S. As above but with Double Pole Switch. 4/6 each.
 100 Brand New Resistors. 1, 1, 1 and 2 watt, our selection. 12/6.

DOUBLE POTENTIOMETERS FOR STEREO

1 meg. + 1 meg. linear.
 500 K. + 500 K. linear.
 250 K. + 250 K. log. All 6/6 each.

CABLE T.R.S. FLEXIBLE

23/36 3-core flexible cable suitable for all portable tools, etc.. 25 yard coil. £1. Shorter lengths at 1/- yard.

ALPHA RADIO SUPPLY CO.

VALVES

GUARANTEED ALL TESTED BEFORE DISPATCH

CL33	20/2	KT66	15/-	5Y3GT	8/-
CY31	12/6	KTW61	6/6	5Z4G	10/-
DAF96	10/6	N78	12/6	6A7	13/-
DF96	10/6	OZ4	5/8	6AL5	9/6
DK96	10/6	PCC94	10/-	6AM6	7/6
DL86	10/6	PCF80	13/6	6PF6	7/8
EBC33	7/6	PL81	16/-	6F1	14/-
EBC41	10/-	PL82	9/6	6F13	14/-
EBF80	10/6	PX25	12/6	6F15	14/-
ECC84	10/3	PY80	9/-	6KT6	5/-
ECC85	9/6	PY81	10/-	6K9G	8/6
ECH35	10/6	PY82	9/-	6L6G	9/-
ECH42	10/6	PEN4VA	15/-	6L18	13/6
ECH81	11/-	PEN25	5/-	6Q7G	9/-
ECL80	13/6	PEN4A	15/-	6Q7GT	9/-
EF39	6/6	SP41	3/-	6SN7	7/6
EF40	14/6	SP61	3/-	6SL7	8/-
EF41	8/9	TP25	27/10	6U4	20/-
EF42	11/-	U25	15/-	6V6G	7/-
EF50	4/-	U50	8/6	6V6GT	7/6
EF80	8/6	UCH42	10/6	6X5G	7/-
EF86	14/6	UL43	10/6	12AT7	9/-
EL41	11/-	VU39	9/9	12AU7	8/-
EL42	12/-	X78	22/3	12AX7	9/-
EL84	10/6	1C5	12/6	12CX	9/-
EM80	10/6	1H5	10/6	12K8	13/6
EY51	13/6	1N5	10/6	25A6	11/6
EY86	13/6	1R5	8/6	25L6	10/-
EZ40	9/-	1S5	7/6	25Y5G	9/9
EZ80	8/9	1T4	7/-	3L6	9/6
GZ32	12/-	3S4	8/-	35Z4	8/-
HL3DD	8/6	3V4	9/-	42	8/-
KT33C	10/-	5U4	8/-	80	8/6

RECORDING TAPE

Paper base, plastic reel, 1,200ft., 12.6. Empty spools. 3in., 3.5, 5in., 3.6. 5 1/2in., 3/8, 7in., 4.3.

HEATER TRANSFORMERS

6.3 v. 1 1/2 amps., 6/9. 6.3 v. 3 amps., 10/- tubes, 7/6 each.

ESCUTCHEONS. For 12in. and 17in. tubes, 7/6 each.

LOUDSPEAKER UNITS

ALL BRAND NEW
 2 1/2in. units by Celestion. 19/6.
 3 1/2in. units by Celestion. 19/6.
 5in. units by Plessey, Goodmans.
 Lectrona. 17/6.
 6 1/2in. units by Plessey. 18/6.
 8in. units by Goodmans. 19/6.
 10in. units by Elac, Plessey. 25/6.

PERMANENT MAGNET 3 ohms IMPEDENCE

6in. x 4in. units by Plessey. 19/6.
 7in. x 4in. units by Goodmans. 19/6.
 7in. x 5in. units by Goodmans. 19/6.
 8in. x 5in. units by Goodmans. 25/6.
 10in. x 6in. units by Plessey. 25/6.

CHARGER RECTIFIERS (FULL WAVE)

12 volt 1 amp. 4/3
 12 volt 2 amp. 7/-
 12 volt 3 amp. 10/-
 12 volt 4 amp. 12/6
 12 volt 6 amp. 15/9

OUR 1958-59 FULLY ILLUSTRATED CATALOGUE

of components and accessories— invaluable for enthusiasts and engineers—is now available. Send 1/- in stamps for your copy.

TERMS : Cash with order or C.O.D. Postage and Packing charges extra, as follows : Order value 10/- add 1/3 : 20/- add 1/9 : 40/- add 2/6 ; £5 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

103 LEEDS TERRACE, WINTOUN STREET, LEEDS, 7.


A Home Constructed TV

Receiver

ADDITIONAL INFORMATION ON THE RECEIVER DESCRIBED IN THE FOUR RECENT ARTICLES

By P. Green

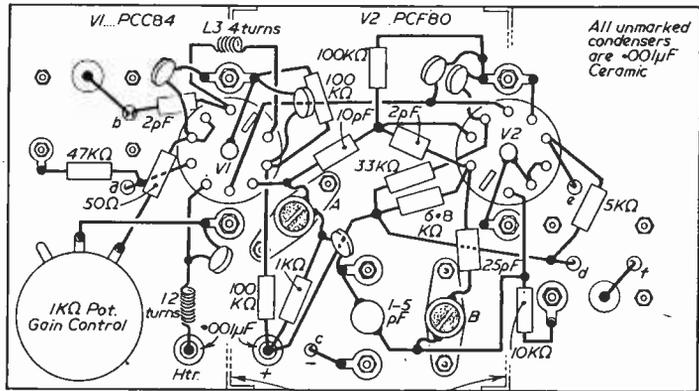ALTHOUGH the article on this set is now complete, there are many readers who have difficulty in reading and working from a circuit diagram. The author, therefore, has prepared a set of five drawings, showing point to point wiring connections. Undoubtedly, these will be welcomed by many readers.




Coil details A...2turns B...4½ turns Screens

The ITV converter (with the screen removed).


Connections for ITV and BBC Converters

Three drawings show the connections for the ITV and BBC converters, with a top view of them bolted together. The screens are not shown, for clearness. All resistors are half watt, and the condensers close tolerance except the .001 μ F ceramics. The top view shows the D.P. changeover switch, which switches off the heaters and the output coils of the converter not in use. Three leads from the power pack supply the chassis, and the heater lead is connected to the centre of one side of the D.P. switch. In the heater connection of the BBC converter a further 2 ohms coil is connected, as the voltage drop of

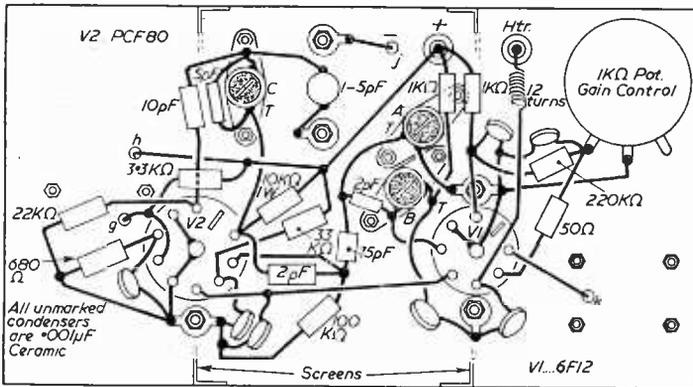

Coil details A...12turns B...10 turns C...6turns T-top of coil

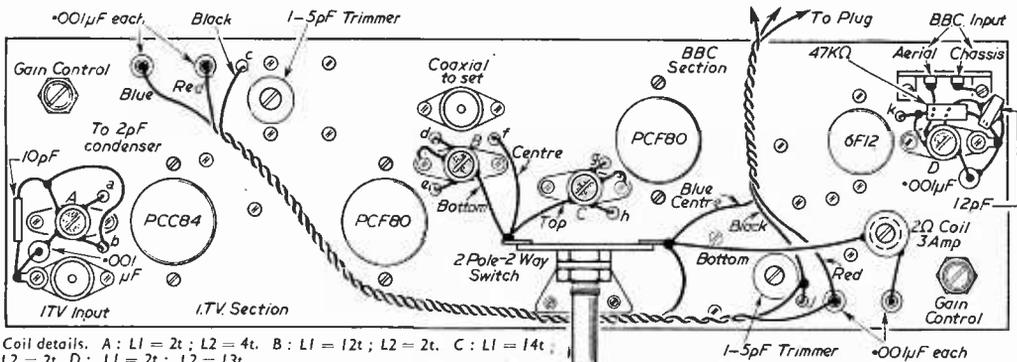The BBC converter (with the screen removed).



Coil details: A: L1 = 2t; L2 = 4t. B: L1 = 12t; L2 = 2t. C: L1 = 14t; L2 = 2t. D: L1 = 2t; L2 = 13t.


View of the two converters from above. (Top, Bottom and Centre refer to positions on switch.)

the two valves is less than those on the ITV converter. To prevent drift the chassis should be kept cool, and it is advisable to mount them clear of the cabinet sides to allow plenty of ventilation. In use the converters are easy to align, and the gain controls are an asset. Both pictures can be adjusted similarly, without further use of the brilliance control.

Power Pack

The power pack and timebase chassis is shown completely wired with all the modifications that have appeared from time to time in these pages.

POWER PACK AND TIMEBASE CHASSIS COMPONENTS LIST	
R42—22 k.	R54—33 k.
R43—2.2 k.	R55—10 k.
R44—1 k.	R56—270 k.
R45—2.5 k.	R57—330 Ω
R46—47 k.	R58—6.8 k.
R47—330 Ω	R59—10 k.
R48—220 k.	R62—470 k.
R49—330 Ω	R63—1 k.
R50—2.2 k.	R64—250 Ω
R51—90 Ω	R65—5 k.
R53—47 k.	R66—330 Ω
C37—47 pF.	C41—.5 μF.
C38—.005 μF.	C46—.002 μF.
C39—.01 μF.	C47—.01 μF.
C40—.1 μF.	C48—.25 μF.

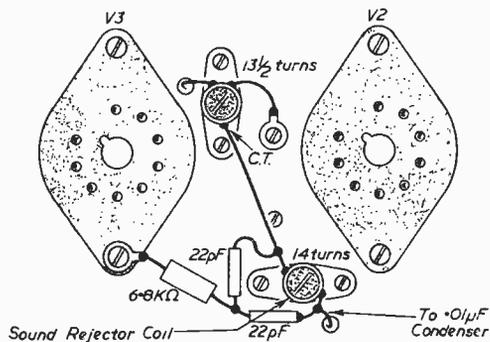


Location of the sound rejector coil.


These have greatly increased its efficiency, with more latitude to the height and width controls. The mains transformer with rectifier supply gives more output and more voltage, with the addition of adjustments to the taps for a failing mains supply.

Sound and Vision

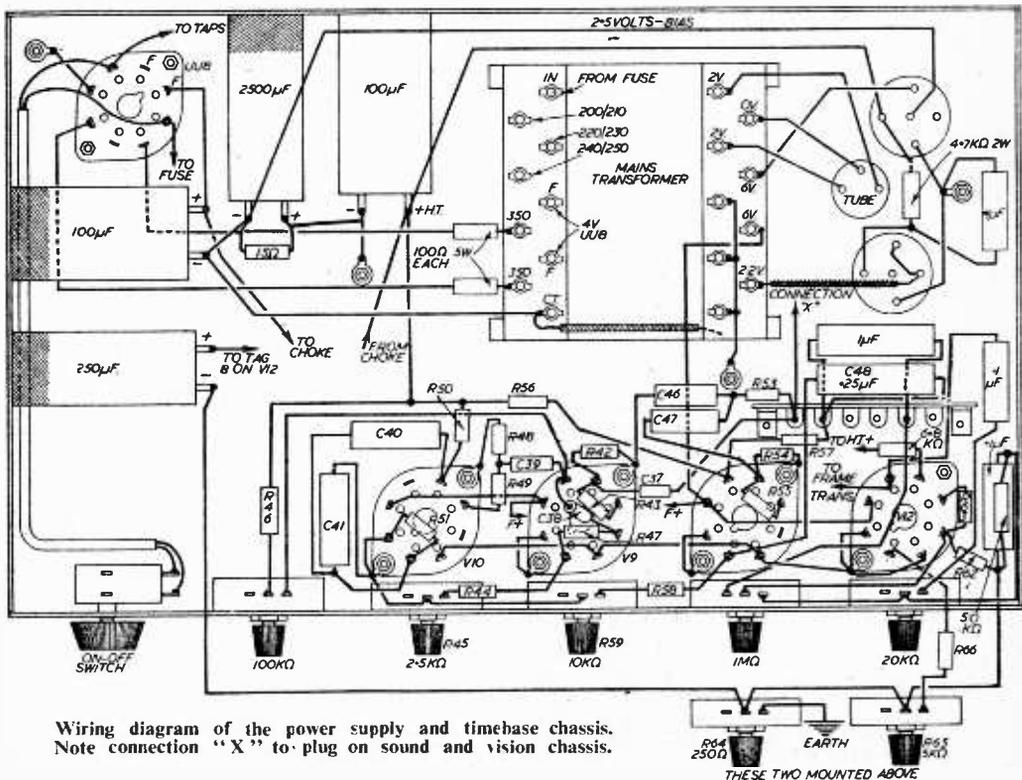On the sound and vision chassis, modifications are only shown for use as an I.F. amplifier; the original rejector coils are now removed. The coils can be rewound, or additional turns added,



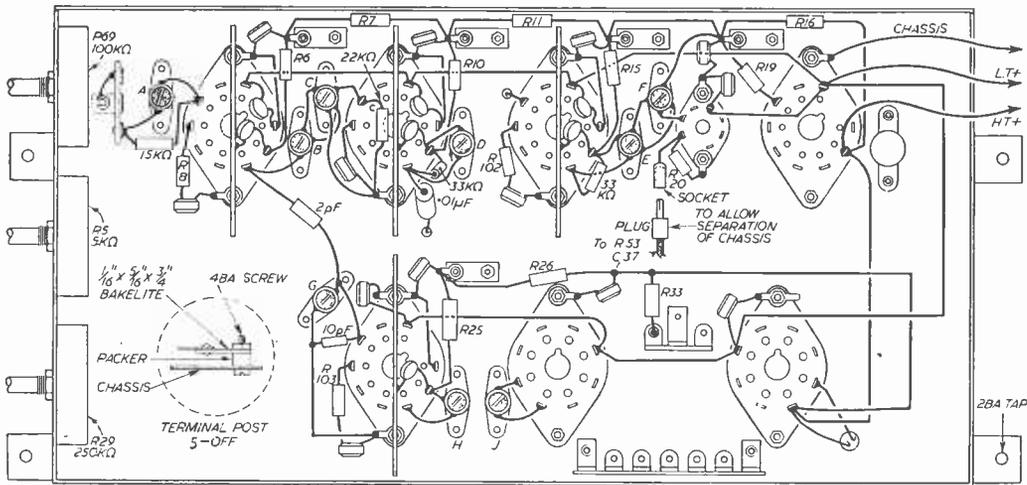Wiring diagram of the power supply and timebase chassis. Note connection "X" to plug on sound and vision chassis.




COIL DETAILS A 1 1/2 TURNS B 1 1/2 TURNS C 1 1/2 TURNS D 1 1/2 TURNS E 1 1/2 TURNS F 2 TURNS G 0 1/2 TURNS H 1 1/2 TURNS J 1 1/2 TURNS
 ALL UNMARKED CONDENSERS ARE .001 μF CERAMIC

Modifications to "Viewmaster" chassis for conversion to I.F. amplifier. (All "Micadiscs" replaced with 0.001 μF ceramics.)

as given in the table on page 177 of the November issue. The new "T" sound rejector coil may be wound on one of the removed formers, and fitted on the chassis as shown on the drawing. In place of the mica discs, a small terminal post is used, to secure positions for the .001 μF ceramics and resistors. On the existing chassis only the decoupling mica discs should be shunted with .001 μF condensers to prevent instability on the

lower frequencies. Other modifications to the sound side consist of a 2 pF condenser from the anode of V1 to grid of V6. The grid coil is shunted with a 10 pF condenser. All other connections are as given for the "Viewmaster."

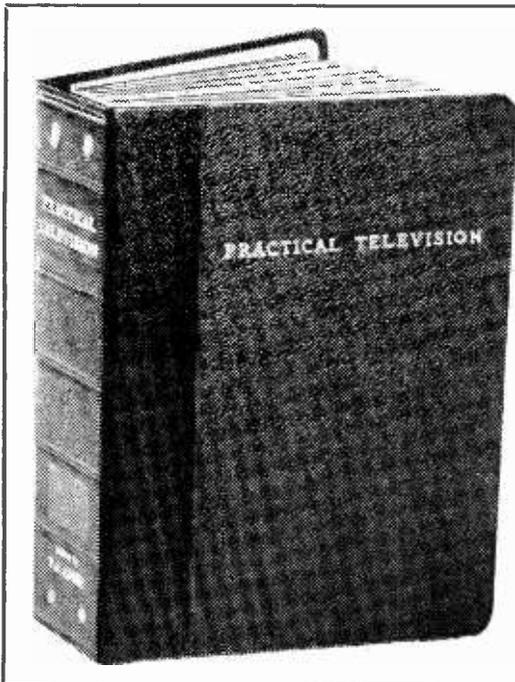As stated in the December issue the alignment of this receiver should be carried out with the aid of a signal generator, although the author aligned his on a transmission.




Self-Binders FOR "PRACTICAL TELEVISION"

AS a service to our readers we have arranged for self-binders to be supplied in which they may preserve the copies of this journal. Copies can be inserted as received, and you do not, therefore, have to wait for the completion of the volume. You secure the same all-time protection as with ordinary binding. The self-binders are in black, waterproof and greaseproof cloth, attractively lettered in gold. This system avoids copies becoming damaged or mislaid. The Easibinder opens flat at any page of any separate edition and gives quick reference facilities. When the volume is complete our annual index published at 1s. 3d. should be inserted.

Please state the volume number when ordering.

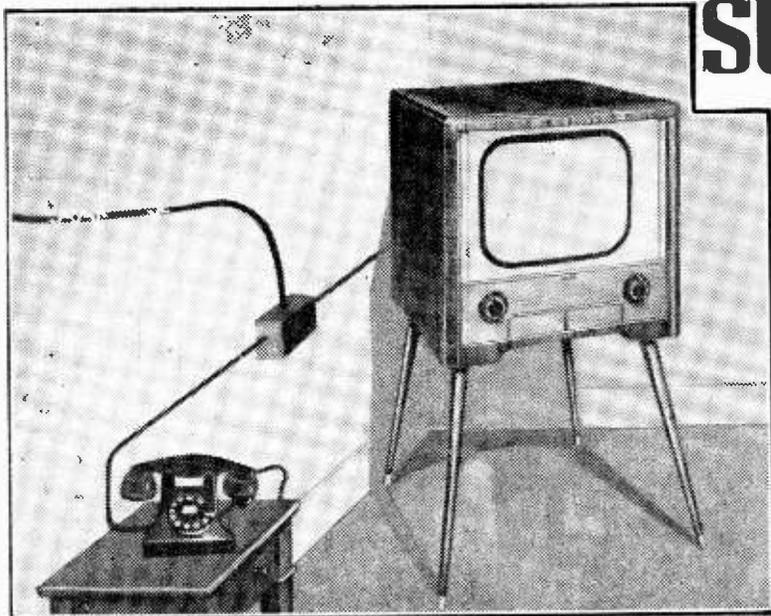Binders cost 10s. 6d. post free. Orders should be sent to "Practical Television" (Binding Dept.), George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.



SUBSCRIB

WITH THIS SYSTEM THE
THAT HE WISHES TO SEI

was called Phonevision and several demonstrations were undertaken to prove that the idea was a workable one. Details of the method will serve to show how this subscription television could collect the fees to provide for the special costly programmes.

Synchronising and Video Signals

The idea formulated and tried by Phonevision to ensure privacy for the transmissions was to bring about a change in the

FOR nearly ten years there have been many discussions and several demonstrations given in the United States of America of schemes which will enable those responsible for producing an expensive television entertainment to collect payment from those viewing the transmission. This is not to be confused with the normal television broadcasts which are financed by private capital and the sale of advertising time on the air. The collection of a fee based on the type and duration of the programme from each set owner viewing it would, in effect, move the box office into the home, for the owner of the set is really paying an admission fee to go to the theatre or cinema in his own lounge.

"Pirate" Viewing

To prevent any form of "pirate" viewing, it is therefore necessary to devise methods for applying secrecy to the signals which are broadcast so that clear pictures may only be received on those sets incorporating a decoder which applies a correcting signal to the received broadcast. At the moment, Congress in the U.S.A. has imposed a temporary ban on some of the schemes proposed so that a full investigation of their implications can be undertaken.

The Coding Signal

The coding signal can be sent over the air or applied via a cable linked up with the potential viewer. There are several methods whereby this can be accomplished and one of the most interesting was that which intended to make use of the ordinary telephone line. Almost every home in the U.S.A. seems to possess a telephone, so the lines linking the house or flat provide a ready-made link which could be adapted for this purpose. Because of the nature of the scheme, it

phase relationship between the synchronising and video signals. The shift was introduced deliberately, but at random intervals between the video or picture signal. The shift was only a small percentage of the horizontal synchronising period, but this did not persist all the time, the balance being that of a normal picture.

This random changing of the phase relationship produced a picture on the receiver which was in no way distorted but the image moved to the left and to the right at an irregular slow rate to give an exasperating blurring effect. Any ordinary television receiving set tuned into this transmission was therefore incapable of showing a locked picture and the only way to restore the picture to normality was to inject a key signal to neutralise the shift.

Secondary Control Line Link

The change from one mode to the other was undertaken during the vertical blanking period and in this way the circuits involved have sufficient time to reach stability. To enable the secondary control line link to be employed for its original legitimate purpose—in this case a telephone service—a special filter was incorporated in the telephone line and the band width of the key signal was limited to 120 cycles, the keying rate varying between 10 and 30 per second. In this particular system, the coded horizontal synchronising pulse causing the time displacement of the viewed picture was also fed into the shading generator at the transmitter to limit any possible flicker.

Coded Picture

In the television receiver employed to view the

TELEVISION TV-PAY AS YOU VIEW

SUBSCRIBER PAYS ONLY FOR THOSE PROGRAMMES

By H. J. Barton Chapple, B.Sc.

coded picture, the horizontal synchronising pulse was fed into the small decoder unit after it had been separated from the main transmitted signal. The key signal sent over the line link activates the unit so as to apply the required amount of correction to the pulse triggering the horizontal sweep circuit.

The distribution of the key or decoding signal to the potential subscriber to the service is carried out by superimposing it on the customer's telephone line outside the normal aural band for voice circuits.

Fees


Looked at from the business or economic standpoint, the important question is the collection of the fees or payment demanded by the specialised service which is providing the television programmes. A flat rate monthly charge could be imposed, but this would be unfair to the subscriber who only desired to use the service on those occasions that the type of programme appealed to his taste. The idea was to make the programmes range over films, outstanding sporting events, plays with a star cast, etc., and a "box office season ticket" was not the best way to meet this.

In effect there are three principal problems to be dealt with:

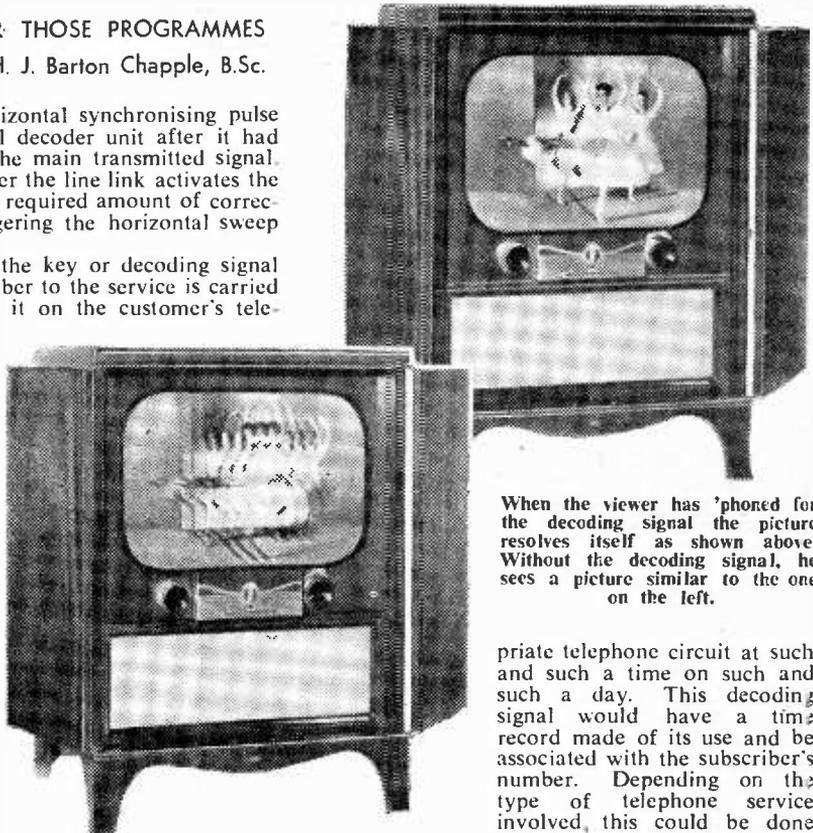- (a) The subscriber intending to use the service must be able to make known his desire for the decoding signal for the programme or programmes of his choice.
- (b) The correct type of decoding signal must be fed to this subscriber during the one or more programmes selected and not at any other time as otherwise the latter would be a free service.
- (c) An exact record of all the transactions—date, time, duration, etc.—must be made so that a true account can be rendered to the customer.

The Decoding Signal

To preserve the right of selection by the customer, the idea proposed was for a call to be put through to the telephone exchange requesting that the decoding signal be applied to the appro-



When the viewer has 'phoned for the decoding signal the picture resolves itself as shown above. Without the decoding signal, he sees a picture similar to the one on the left.

appropriate telephone circuit at such and such a time on such and such a day. This decoding signal would have a time record made of its use and be associated with the subscriber's number. Depending on the type of telephone service involved, this could be done verbally or by digit codes, and

although it was naturally hoped that subscribers would book the service ahead there would always be cases of viewers watching the coded picture at the beginning of a transmission and suddenly being intrigued by the nature of the programme and hastily telephoning for the key signal to be applied to the line.

Payment to the Company

Reimbursement to the programme company would be provided by quarterly or half-yearly collection of the sum of money calculated on the basis of the number of hours the viewer looked in, the time record being obtained from the telephone service. The idea is a novel one capable of adaptation in many different directions where secrecy in television transmission is required, but these coded schemes must now await the decision of Congress in the U.S.A. as to future developments.

It is difficult at this juncture to forecast whether or not such a viewing system will ever be used in this country. No doubt this will depend in some measure on further progress in this direction in the U.S.A.

Poor Frame Hold

So as to provide an improvement of frame hold in poor reception areas, later versions of the T161 series feature a special frame oscillator transformer with a tertiary winding for the application of the sync pulses. The circuit is shown in Fig. 2. There may also be found a small metal rectifier in the frame sync circuit, which should be checked in persistent cases of poor hold.

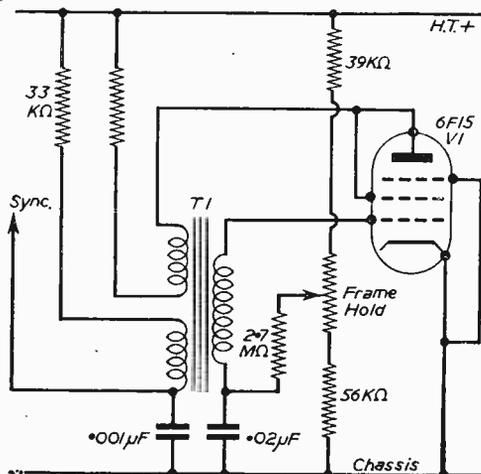


Fig. 2.—The modified frame oscillator.

A leak across the $2\ \mu\text{F}$ electrolytic capacitor connected to the screen of the 20F2 sync separator valve (pin 5) is another frequent cause of the trouble, though does not appear to affect the line hold unduly. However, if a serious leak develops, the sync fails completely, and there have been cases of the capacitor shorting, sometimes aggravated by excessive pressure of the capacitor retaining clip, this pressing into the body of the component.

If poor frame hold is accompanied by a slightly reduced frame scan, and the smaller components appear to be in good condition, there is a possibility that the frame oscillator transformer is responsible. This would appear to develop a slight leak between the windings or the winding resistance may rise for some reason or other. The only conclusive test lies in transformer substitution.

Frame Jitter

This can be caused by a faulty oscillator valve (V1), trouble in the oscillator transformer or a leak in C1 or $0.02\ \mu\text{F}$ capacitor connected to the slider of the frame-hold control. Where the frame components check normal, however, and substitution tests do not reveal the trouble, it often pays to check the condition of the $120 + 250\ \mu\text{F}$ electrolytic, even though symptoms of hum are not in evidence.

Hold Control at End of Range

In receivers using the circuit as in Fig. 2, it may be found that the optimum position for the frame hold control is becoming progressively near one end of its travel. The cure lies in the

replacement of the $2.7\ \text{M}$ resistor connected between the centre tap of the frame-hold control and the frame oscillator transformer.

Line Oscillator Failure

Fig. 3 shows the circuit of the line oscillator/output sections along with the complementary reclaim and EHT networks. When these sections are working correctly, the 10 kc/s line whistle will be heard from the line output transformer (T2), the pitch of which can be altered by adjusting the line-hold control.

If lack of EHT is coincidental with lack of whistle, a possible cause is shorting turns in the line output transformer, but several tests should be made before transformer replacement is contemplated. In the first place, it should be established that H.T. is present at the cathode of V2 (part of U801) and that section A of the transformer possesses continuity (the correct resistance is 79 ohms, subject to slight deviation).

Next, a check should be made of the voltage on the screen of V1 (20P1). This should normally be in the region of 125 v., but if zero voltage, section A of T1 (normally 10 ohms) should be checked for continuity and the voltage at the junction of this winding and the $2.2\ \text{k.}$ resistor should also be checked. Zero voltage should then lead to a check of the $3.3\ \text{k.}$ resistor, which will probably be found to be open-circuit.

If the line whistle occurs and EHT becomes available when the deflector coils are unplugged from the chassis, the $50\ \mu\text{F}$ electrolytic capacitor connected to the line coils should be replaced.

Also, before the transformer is replaced, V1 and V2 should be checked, preferably by substitution, as also should the smaller components associated with the circuits.

Low EHT

The frame timebase circuits are energised from the boosted H.T. line (from the cathode of V2—see Fig. 3) and it has been known for a fault in the frame circuits to load the boost circuit to such an extent that operation of the line timebase is considerably impaired. A heater-to-cathode short in the 6L18 is one cause of the trouble.

A similar symptom, also showing as poor focus and sub-standard performance generally is caused by open-circuit of one of the surge-limiting resistors in the anode circuit of the H.T. section of the U801. Two 50-ohm wire-wound components are employed, one to each anode, and open-circuit of one considerably reduces the H.T. voltage, while also putting an abnormal load on the resistor left in circuit. It is, therefore, best to change both resistors when one fails.

Lack of EHT

If the line whistle is present, even though weak, and the anode of the U25 EHT rectifier is glowing red hot, the cause is shorting EHT as the result of insulation failure between the U25 heater winding and the line output transformer core. Transformer replacement represents the only sure cure.

It should be mentioned, however, that the same effect would result from a short across the $0.001\ \mu\text{F}$ EHT filter capacitor, though this happens less frequently than the transformer short.

Non-linear Line Scan

This symptom should lead to a check of H.T. voltage (see Low EHT) and a substitution test of the two 50 μ F electrolytics in the line circuit, one connected to V2 cathode and the other to the line coils (Fig. 3).

No Line Hold

If there is no trace of line lock, though the line hold control serves to adjust the oscillator frequency to steady the picture within its range of adjustment, attention should be directed to the 5 pF line sync coupling capacitor which is connected to the control grid of the 20P1. In areas of weak signal, enhanced line lock can be secured by increasing the value of this capacitor to 10 pF.

If it is found that the operating point of the line hold control falls to the end of the core adjustment, or if the correct locking point is outside the range of the adjustment, balance of the control can sometimes be achieved by either connecting or disconnecting the line hold control shunt winding on T1 to chassis, as indicated by the lead marked "X" on the circuit.

If this does not effect a complete cure, the trouble may be caused by an alteration in the characteristics of the

20P1. A substitution test proves this possibility without trouble. Attention should also be given to the 2 μ F electrolytic coupled to the end of winding A on T1 in the event of line trouble.

(To be continued)

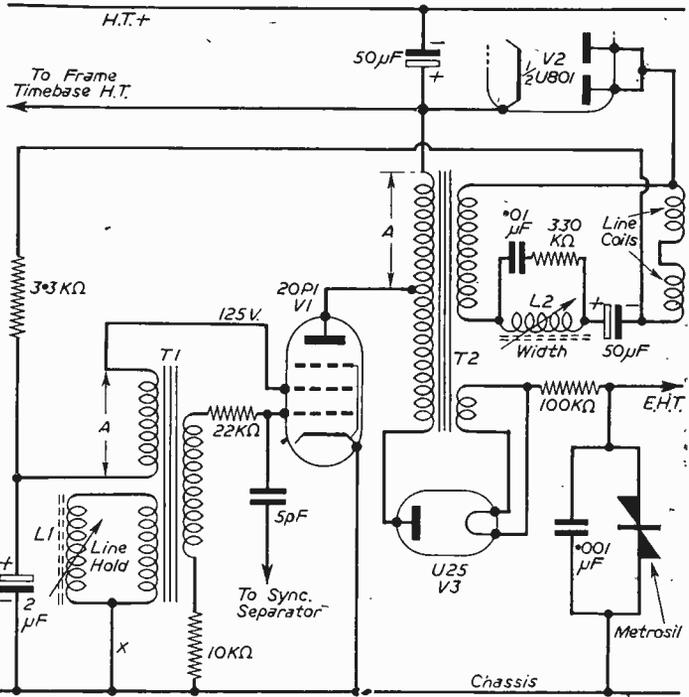


Fig. 3.—The line oscillator amplifier circuit.

Television in Iran

TELEVISION in Iran has made rapid progress during the three short months it has been on the air. Opened by His Majesty The Shah-in-Shah last October as the first commercial television station in the Middle East, Television of Iran has already built a large audience. Now on the air four hours a day seven days a week, over 80 per cent. of Television of Iran's programming is live. This in itself is most unusual and especially so in an area where none of the 60-odd employees had ever seen television prior to its opening three months ago.

One of its most popular programmes is the teaching of English, as developed in co-operation with the British Council in Tehran. This programme has generated a wide appeal among all income groups. It is now a common sight to see clustered around the receivers in the showrooms of the stores people from all walks of life not only watching the show intently but with pencil and notebook in hand taking down the words of the language as it is presented by this particular programme.

Television of Iran is unique in that this newest means of communication is given over to private enterprise. The owners of the station, the Habib

Sabet family, are prominent business leaders in Iran.


The station manager of Television of Iran is Mr. A. Vance Hallack, who came to Tehran from Baghdad where he organised and managed Television of Baghdad.

Television of Iran is equipped with two major studios, the larger one being 75ft. \times 45ft. and the smaller being 60ft. \times 36ft. It has a complete complement of studio equipment plus a mobile unit for outside activities. To quote Mr. Hallack: "Television of Iran is another example of the ability of the Iranian people to master an instrument as delicate as television and through this, help develop Iran by presenting a medium that will not only further cultural and educational possibilities but build a new large commercial market in the field of television advertising."

Mr. Hallack was a pioneer in television in the United States and has also been a pioneer in television overseas.

The receiver sales are higher than expected. The commercial sales of the station are expected to hit 50 per cent. by the middle of January—three months ahead of the established goal for this figure. A step forward in the advertising industry has been made as some international agencies have already set up divisions in Tehran.

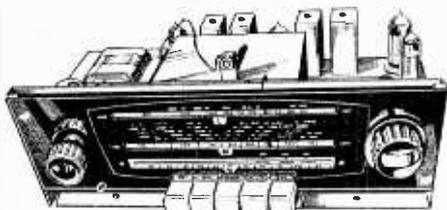WONDERFUL OFFER OF A.M.-F.M. CHASSIS AT £14 (P. & P. 10/-)



Payments of 38/-, or with Cabinet and Speaker £6 down + carr. and 5 Monthly TERMS:—(Chassis) £5 down + carr. and 6 Monthly Payments of £2.

Why buy a F.M. Tuner at the same price?
Tapped input 200-225 v. and 226-250 v. A.C. ONLY.
Chassis size 15" x 6 3/4" x 5 1/2" high. New manufacture.
Dial 14 1/2" x 4" in gold, red and deep brown.
Pick-up, Extension speaker, Ae., E. and Dipole sockets.
Five "piano" push buttons—OFF, I.W., M.W., F.M. and Gram. Aligned and tested. With all valves.
Covers 1,000-1,900 M.; 200-500 M.; 88-99 Mc/s.
Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85.
Speaker & Cabinet to fit, polished, with back, 70/-.
8" x 5" ELLIPTICAL SPEAKER 20/-.

HIGH GAIN I.T.A. CONVERTER ONLY £47.6

All areas, all sets except Philips' with only twin feeder input. Internal power pack; direct switching I.T.A. to B.B.C.; no alteration to your set; fitted in 10 mins. Valves ECC81, metal rectifier; fine tuner; grey hammer finish; walnut finish wood cabinet 10/- extra.

(3/- p. & p.)




EX-ADMIRALTY HEAVY DUTY TRANSFORMER. Unused, in original transit cases, 230 v. 50 c.p.s. input, 500-0-500 v. at 1/2 amp. output. 60/- (7/6 carriage). Worth double.

EX-ADMIRALTY TRANSFORMER, 230 v. 50 c.p.s. input, 1,000 v. 2 mA., and 2 v. 2 A. output. Size 4 1/2" x 3" x 2 1/2". Unused, 13/- (2/- post).

ANOTHER 230 v. 50 c.p.s. input, 63 v. 66 v. 69 v. out at 1 1/2 A. Unused. 3,000 v. test—14/6 (2/6 post).


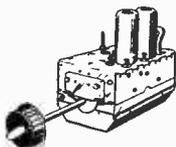
LOUDSPEAKERS—VERY SPECIAL OFFER !— Rola (10,000 line) (2-3 ohm), 3 1/2" square 15/- (1/-); 8" x 5" Celestion elliptical 20/- (1/6); 6 1/2" circ. 14/6 (1/6); 5" circ. 13/- (1/6); 5" with trans. 15/- (1/6); all 2-3 ohm (p. & p. in brackets).



CYLDON 16 Mc/s and 19 Mc/s TURRET TUNER with two sets coils (state B.B.C. & I.T.A. channels). Extra pairs of coils, 5/- pr. With knobs. ONLY 77/6 (2/6 post). Valves PCC84 and PCF80 included, or valves UCC84 and UCF80.

THE BRAYHEAD TURRET TUNER, £7.7.0, post free.

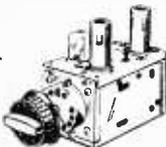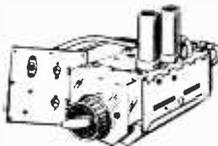Complete with booklet and fitting instructions. State set and model no. when ordering.



INCREMENTAL TURRET TUNER by famous manufacturer for 35 Mc/s only; with knobs. Valves PCC84 and PCF80. ONLY 77/6, post free, or without valves, 60/-, or valves UCC84 and UCF80.

Posted Orders to Worthing, please. Delivery by return. Terms:—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment. (C.O.D. 2/- extra.)

These terms are applicable to all items except A.M.-F.M. chassis.

All goods are new unless otherwise stated.

GLADSTONE RADIO, 25 WORDSWORTH ROAD, WORTHING. Tel.: 235
58a High Street, Camberley, Surrey. Tel.: 2633; and 3 Church Road, Redfield, Bristol. Tel.: 51207

GRAMOPHONE AMPLIFIER with 5in. SPEAKER

WHY PAY MORE? ONLY 60/- (POST 3/-)

On Fabric-covered Baffle 12 1/2" x 5". Mains and Output Transformers. Metal Rectifier. ECL82 Valve. Tone and Volume Controls. On-off switch. Plenty of volume. Fully Guaranteed. Two Knobs supplied. Ready to play.

BATTERY ELIMINATOR. Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK96 range). 90 v. 15 mA. and 1.4 v. 250 mA., 42/6 (2/6 post). 200-250 v. A.C. Size 5 3/4" x 3 3/4" x 2".

I.T.A. AERIALS clipping to existing mast 1-2" dia. 3-element, 27/-; 5-el., 35/-; 9-el., 55/-; Loft mount, 3-el., 20/-; 5-el., 27/6; Combined single B.B.C. and 5-el. I.T.A., 75/- with chimney lashings; Co-axial cable semi-air-spaced, 8d. yd. or 20 yds., 12/6; aerial and cable prices carr. pd.

SEND 6d. FOR CATALOGUE

ANOTHER "READY TO USE" I.T.A. CONVERTER

I.T.A. high gain converter. ALL CHANNELS—ALL AREAS—ALL SETS. Direct switching (I.T.A. to B.B.C.); internal power pack; valves PCF80 and PCC84; moulded cabinet 8 1/2" x 4" x 6". No alteration to your set; fitted in 10 mins. 12 months' guarantee.



£55.50 P. & P. 3/-

ARMOUR PLATED GLASS, 16" x 14" x 3/16". 10/-, p. pd.

Mixed 4 B.A., 6 B.A. screws, mostly round and C.H. but some C.S. 500 for 3/6 (post 1/-). Mixed rivets, alum. and copper, 500 for 3/6 (post 1/-). 4 B.A. Simmonds nuts, 500 for 5/- (post 1/-).

PERSPEX UNSCRATCHED, post 2/- each size, 6 post free; sizes in ins. 14 1/2 x 11 x 3/16 clear, 5/-; 12 x 9 1/2 x 1/2 clear, 4/-; 16 x 14 x 3/16 clear, 7/-; 15 x 12 x 1/2 tinted or clear, 6/-.

ELECTROLYTICS 200-200-200 mf. 275 v., 7/6 (post 1/6). 200-100 mf. 275 v., 4/6 (post 1/-).

PRE-SET WIRE WOUND POTS, 3 K. 5 K. 10 K., 2/6 ea. (post 6d.), or 20/- doz. mixed (your choice), post free.

NEW SILVERED MICA CONDENSERS. 50 different values, 10/-, post paid.

RESISTORS. 50 different values. 1/2 watt to 1 watt. 5/-, post paid.

BATTERY CHARGER. 1 amp. 6 v. and 12 v., £2, post paid.

ADVISORY SERVICE

We offer a complete before and after sales service. Our advice is ALWAYS available and freely given, BUYING or NOT!
Whether expert or novice, let our extensive experience ensure your success.

AERIALS

An even wider range. We select the ever popular I.T.V. add-ons to illustrate our bargains.
5 ELEMENT. Complete with universal clamp and stand-off arm. Still unbeatable, 39/6. Also at 45/-.
8 ELEMENT. As above. 51/6. Also at 62/6.
Easifix. All aerials pre-assembled and collapsed for transit. Easimod. All single aerials can be modified to "double" arrays if desired.
Takitessi! DO be careful on the roof. DON'T wear crêpe soles in wet weather. (Better still wait for good weather).
NOTE.—Efficiency and gain of aerials depends on number of elements, spacing, siting, etc., and hardly varies with PRICE which concerns finish, long-term durability and patent assembly methods. DO write us for aerial advice if in doubt.

CABLE & ACCESSORIES

CO-AXIAL. Hi-grade, low loss, suitable all normal purposes. Expanded polythene type. 8d. per yd. any length.
SEMI-AIRSPACED. A "must" for long runs in fringe areas. ("Don't spoil the ship," etc.) 1/6 per yd. any length.
DIPLEXERS (junction boxes). Indoor type, 10/3. Outdoor type, 13/-.
IF-IN-DOUBT. Use a separate download for I.T.V. with a skirting board "diplexer" if necessary.

TURRET TUNERS

Still available. The famous "Brayhead" at £6.19.6.
Easifix. Over 600 models convertible to I.T.V. by simple "plug-in" technique.
SUCCESSFUL! We have received very many appreciative letters. Our supplementary advice ensures success.

CONVERTERS (external)

£6.19.6. Accessories, 7/6.
Our external converter gives the very simplest conversion to I.T.V.
Handsome appearance.
Easifix (in fact, dead easifix!) Place on top of T.V. and connect up as per our instructions.
Efficient. 2 valve circuit. Best on the market at the price. Definitely superior to the cheap 1 valve efforts.

AMPLIFIER KITS

Our DO-IT-YOURSELF amplifier. After exhaustive tests we have selected the famous Cossor 562KX.
Definitely the job for novice or expert. Not a "lash-up," but the real thing. OUR SUPPLEMENTARY ADVICE ensures success.
Printed circuit technique giving Hi-Fi 3 watts output.
Twin Loudspeakers. Suitable all inputs.
Illustrated step-by-step advice. Everything except the cabinet! £9.15.0 tax paid.

RADIO KITS (F.M./V.H.F.)

Our DO-IT-YOURSELF radio. Again, after many tests, we have selected the famous Cossor 701K.
Everything except the cabinet for a 6 valve V.H.F./F.M. radio. Pre-aligned R.F. and I.F. stages. (Expensive test gear not required).
10in. Elliptical loudspeaker.
Illustrated construction manual plus our Supplementary Advice. £15.15.0 tax paid.

AUTOCHANGERS

The famous and reliable MONARCH UAB.
Multi-speed, multi-play. Hi-Fi turnover cartridge.
Note our price. £6.19.6. (List £9.15.0).
Convert your old "gram" or build your own "player."

TERMS OF BUSINESS

Cash with order or C.O.D. (2/6 extra.)
Extended credit on expensive items. Write us in confidence.
Carriage free above £5 except aerials and autochangers.
Packing and carriage Aerials: 5 EL. (2/6); 8 EL. (3/6); Others (5/-); Autochangers (7/6).
If in doubt about carriage, terms, etc., or if needing advice, WRITE US FIRST.

WILSON

48, CATHAY, BRISTOL, I.

TEL. 57819 or 26242.

CATHODE RAY TUBES

- * RE-BUILT
- * RE-GUNNED &
- * RETURNED

WITHIN 72 HOURS WITH A SEVEN MONTHS' GUARANTEE!

For peak quality workmanship and unfailing service contact:

MIDLAND TUBES LTD.

37, George Street, Manchester 1.

TELEPHONE CEN 0432.



VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

1.4 v. midget. 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL52, DL94; ANY 4 for 27/6.

1A7GT	16/6	6X4	8/9	DF91	6/3	EP91	6/9	PY90	8/-
1D5	9/6	6X5GT	6/-	DF96	8/6	EP92	5/-	PY81	8/6
1H5GT	10/-	7B7	8/-	DH76	7/3	EL33	16/9	PY82	8/6
1N5GT	10/-	7C5	8/-	DH77	7/3	EL38	22/6	PY83	8/6
1R5	8/-	7C5	8/-	DK32	16/6	EL41	9/6	PZ30	18/-
1S4	10/-	7H7	8/-	DK40	16/-	EL42	10/6	SP31	3/6
1S5	7/6	7S7	9/9	DK91	8/6	EL84	8/9	U25	15/-
1T4	6/3	7Y4	8/-	DK92	8/6	EM80	9/6	U50	7/6
1U5	6/6	10F9	10/6	DK96	8/6	EM81	9/6	U52	6/6
3A5	10/6	12AH8	9/-	DL33	9/-	EM84	13/6	U76	7/6
3Q4	8/6	12AT7	9/-	DL35	14/6	EY51	11/6	U78	8/9
3S4	7/6	12AU7	7/6	DL92	7/6	EY86	12/6	UABC90	9/-
3V4	8/6	12AX7	8/-	DL94	8/6	EZ40	7/9	UAF42	9/6
5U4G	8/6	12K7GT	7/-	DL96	8/6	EZ41	10/-	UBC41	8/6
5V4G	11/-	12K8GT	12/6	EABC80	7/9	EZ80	7/9	UBF80	9/6
5Z3GT	7/6	12K7GT	7/-	EAF42	9/6	EZ81	8/6	UBF89	18/6
6Z4G	9/6	14S7	15/9	EB91	5/6	EY500	10/6	UCC84	18/-
6AL5	5/6	19AQ5	7/6	EBC33	7/-	G232	11/-	UCC85	9/6
6AM5	5/-	25A8G	11/-	EBC41	9/6	K73C3	8/6	UCF80	19/6
6AM6	6/9	25Z4G	9/-	EBF80	8/9	KT41	14/6	UCH42	9/9
6AQ5	7/-	25Z6GT	12/6	ECC81	8/-	K763	6/6	UCH81	9/6
6AT3	7/3	35L6GT	10/6	ECC82	7/6	K771	12/6	UCL42	13/-
6BA6	7/6	35Z4GT	7/6	ECC83	8/-	MH4	6/-	UCL83	14/3
6BE6	7/-	35Z5GT	8/6	ECC84	9/6	MU14	9/-	UF41	9/6
6BH6	8/-	43	12/6	ECC85	9/6	N18	8/6	UF42	15/-
6BJ6	7/-	50CDBG	28/9	ECCF80	11/6	PCF84	9/-	UF89	9/-
6BW7	7/6	50L6GT	9/9	ECCF82	11/6	PCF89	17/6	UL41	9/6
6CD6G	26/9	AC/VP1	13/6	ECH35	10/-	PCF80	9/-	UL44	22/6
6F6G	6/6	AZ1	12/6	ECH42	9/6	PCF82	12/-	UL84	8/6
6K7G	4/6	B36	15/6	ECH81	8/6	PCL82	11/6	URIC	9/6
6K7GT	6/-	CL33	16/9	ECL90	11/9	PCL83	14/6	UY1N	12/6
6K8G	7/-	CY31	12/6	ECL82	12/6	PEN44	11/-	UY21	14/-
6L18	12/3	D77	5/6	EF99	5/6	PEN36C	9/6	UY41	7/-
6Q7GT	8/6	DAC32	10/-	EF41	9/6	PEN46	6/-	UY85	7/6
6SL7GT	7/-	DAF91	7/6	EF42	11/6	PL38	22/6	VP4B	9/6
6SN7GT	6/6	DAF96	8/6	EF80	7/6	PL81	15/-	VP41	6/-
6U4GT	11/-	DACC90	10/6	EF86	13/6	PL82	8/6	W75	7/-
6V6G	6/6	DF33	10/-	EF89	9/-	PL83	10/6	W77	5/-
6V6GT	7/6							Z77	6/9

Any Parcel Insured Against Damage in Transit 6d. extra.

READERS RADIO


24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA 4587

A NEW SERIES

Analysing and Servicing TV Receivers

No. 5—The Line Timebase

By "Diadem"

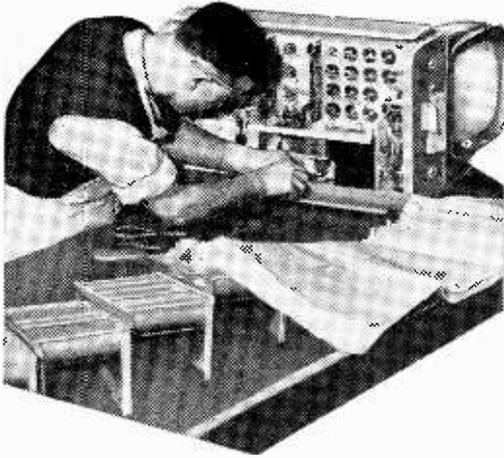

A SELF-OSCILLATING line timebase is shown in Fig. 22. The oscillator feedback capacitor is C1 and the line hold control is R1. A leakage across C2 will prevent the line from locking to the correct frequency. The booster diode V2 rectifies the line flyback energy developed across the scan coil winding giving an increase of 250 v. over the H.T. line voltage. This increased voltage is fed to the line oscillator

anode V1 with the H.T. voltage. The voltage from the diode when smoothed also feeds the tube's first anode. The EHT overwind between points A and B provides a step up in voltage to 9 kV. This is then rectified by V3 and fed to the tube anode. The brilliance control, R3, in conjunction with R2 forms a potential divider across the H.T. line. The variable trimmer, C6, is a "striation" control for the removal of vertical bars (line ringing). The scan coil D.C. isolating capacitor is C9. The last two components are the ones referred to in the faults section. A fuller description of line timebase working will be found in the EHT section. To prevent confusion a "booster," "efficiency," "economy" or "reclaim" diode are all the same thing, a damping diode does just what the name suggests and is connected in place of the resistor/capacity combination across the scan coils in Fig. 24. In the case of the damping diode the flyback energy is not fed back to boost the line transformer primary voltage to V1 anode.

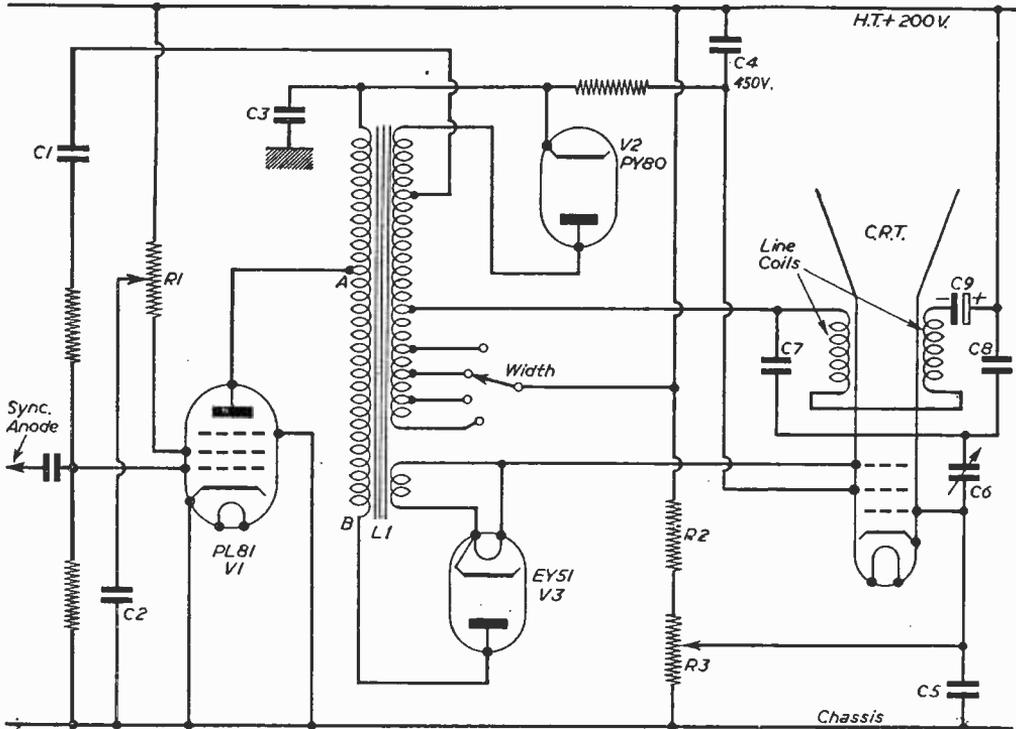


Fig. 22.—Circuit of a self-oscillating line timebase.

NEW
UP-TO-DATE
EDITION

FOR
READERS OF
"PRACTICAL
TELEVISION"
AT REMARKABLY
LOW COST!

RADIO, TELEVISION & ELECTRICAL REPAIRS


SAVES YOU POUNDS!

Here is just the practical, at-a-glance guidance YOU need, whether you wish to know how to service radio and TV sets, install an extra lighting point, or repair any domestic electrical appliance—from a bell or an iron to a vacuum cleaner or washing machine. Explains, in simple language, basic principles and working of modern radio and TV sets and electrical appliances. Shows how to test for faults and carry out maintenance and repair work by the most modern methods. Special section on the operation and servicing of frequency modulated receivers. 480 pages. Over 400 illustrations. Amazing value—Standard Edition, 18/- inc. postage, packing, etc.

ESSENTIAL TO EVERY SERVICE ENGINEER, ENTHUSIAST AND HANDYMAN!

GETTING THE BEST FROM RADIO AND TV SETS

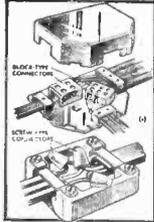
Here is expert advice that will enable you to make the necessary adjustments or repairs in order to get the best possible performance from any radio or TV set. **All you need to know about DOMESTIC WIRING**



Learn from these helpful pages how to carry out all kinds of installations and extensions — with efficiency and safety! Complete guidance on conductors, insulation, safety regulations, conduits, cables, earthing, practical work, fuses, flexible cords, etc.

BASIC RADIO CIRCUITS

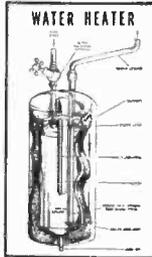All you want to know about circuits. so that you can find your way around modern sets without hesitation. How components form various types of set; gives circuits for one-valve receiver, 3-valve receiver, battery TRF receiver, 4-valve superhet, Universal sets, etc.



FIRES & SPACE HEATERS


Full, easy-to-follow instructions for servicing small domestic fires—whether of the radiant, reflector or convector type.

WATER HEATING

All you should know about the various types of electric water-heaters and how to install them and keep them in perfect working order. Advice that will save you POUNDS!

TRACKING DOWN TROUBLE

This grand book is invaluable for tracing faults in radio and TV sets. Tells you all you want to know—from how to carry out Preliminary Tests to how to align R.F. and I.F. circuits. Shows how to carry out Dynamic Testing. Also shows how to trace the cause of Noises, Distortion and Instability and deal with the trouble. Gives detailed information on Components and Loudspeakers and how to deal with any faults that may develop.

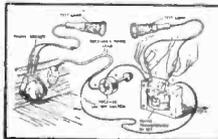

DO THIS NOW!

Simply fill in form and post in 2d. stamped, unsealed envelope to Dept. H.F.35, People's Home Library, Basted, Sevenoaks Kent. Offer applies in U.K. and Eire only, closes Mar. 31.

FULL SATISFACTION or No Charge GUARANTEE



ALL THIS—AND MORE—IN ONE GREAT VOLUME

Comprehensive Contents include:

Current, Voltage, and Resistance. Coils, Capacitors and Valves. Basic Radio-receiver Circuits. Preliminary Tests. Instruments for Set Testing. Locating Faults. Dynamic Testing. Tuned Circuit Alignment. Noises, Interference, Distortion and Instability. Components. Loudspeakers. Pick-ups. Gramophone Motors. Frequency Modulation. Television Circuits and Test Gear. Television Faults, Symptoms and Cures. Aerials and Pre-amplifiers. Maintenance of Domestic Electric Wiring. Small Appliances. Fires and Space Heaters. Vacuum Cleaners and Polishers. Rewinding Small Motors. Cookers and Boiling Plates. Washing Machines. Refrigerators. Electric Water Heaters. Battery Charging, Testing and Repair, etc.

The book that cuts out guess-work! **TV FAULTS—their SYMPTOMS AND CURES**

POST FORM NOW!

Dept. H.F.35, People's Home Library, Basted, Sevenoaks, Kent.

WITHOUT OBLIGATION reserve me "Radio, Television and Electrical Repairs" and send Invoice with "100% Satisfaction or No Charge" Guarantee.

BLOCK LETTERS

NAME

Full Postal ADDRESS

.....

.....

.....

H.F.35, March '59.....


Firmly affix 2d. stamp in margin

See how to maintain Vacuum Cleaners and Floor Polishers, Refrigerators, Cookers and Boiling Plates, Washing Machines, etc.



Disconnecting Boiling Plate on Cooker

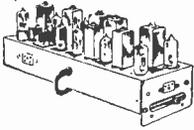Do your own BATTERY CHARGING
Here are clear, complete instructions.



P. P. COMPONENTS LTD.

Dept. T 3

S./Vision STRIP. 5/6. S/het, takes 6-EF91, 1-6D2, 1-6F14. Valves not included. Please state channel. Post 2/6.
TIME BASE. 4/9. Complete with scanning coil, focus unit line transformer, etc.; less valves. Free drawing. Post 3/6.

ELAC FOCUS MAGNET. 5/9. 35-38 mm. Permanent magnet. Salvage. P. & P. 1/9.
ELAC FOCUS MAGNET. 12/6. Brand new. 35-38 mm. P. & P. 1/9.
PLESSEY FOCUS MAGNET. 3/9. 35 mm. Permanent magnet. Salvage. P. & P. 1/9.
SLIDER CONTROLS. 5/- . 5 on a panel. 1K, 5K, 10K, 42 at 50K. Complete with knobs. P. & P. 1/6.
17in. T.V. MASKS. 9/9. Brand new. Good quality. Grey or white plastic. Post 2/-.

T.V. AERIALS. 25/6. For I.T.A. channels. Outdoor or Loft. 3 element. P. & P. 2/6.
T.V. AERIALS. 7/9. Fitted with 9 ft. co-ax cable. Suitable for door-roof or loft. Post 1/3. Extra co-ax. 6d. yard.
CAR AERIALS. 6/9. Plated. Whip antennae. 50 in. long. Collapsing to 11 in. One hole fixing. P. & P. 1/-.



8in. P.M. SPEAKERS. 5/9. A bargain offer, but limited quantity of these modern type speakers. All tested and carry "Money Back Guarantee". They have a slight cone fault which is repaired not affecting the quality. P. & P. on 1 2/6, on 2 3/6. Also 8in. P. M. Speakers 8/9. An ideal gift if fitted in small cabinet. Complete. With O.P. Transformer fitted. 10/- . P. & P. 2/9.



TRANSFORMERS
MAINS POWER TRANS. 12/6. 350-0-350 v. @ 250 m/a. 6.3 v. @ 4 amp., 6.3 v. @ 4 amp., 4 v. @ 3 amp., 22 v. @ 3 amp., 4 volt centre tapped @ 1.5 amp. Primary 200-250 volt. 50 cycles. P. & P. 3/9. Drop through type.

MAINS POWER TRANS. 12/6. 350-0-350 v. @ 250 m/a. 6.3 v. @ 5 amp., 4 v. @ 4 amp., 4 v. @ 7 amp., 4 v. centre tapped @ 1 amp. Primary 200-250 volt. 50 cycles. P. & P. 3/9. Drop through type.

MAINS TRANS. 3/9. 350-0-350 v. @ 80 m/a. 12 v. 4 v. heaters. P. & P. 2/9.

MAINS TRANS. 5/9. 280-0-280 v. @ 80 m/a. 6 v. @ 3 amp., 5 v. @ 2 amp., 4 v. @ 2 amp. Drop through type. Half shrouded. Primary 200-240. P. & P. 2/9.

O.P. TRANS. 1/3. Standard size. 2-5 ohms. P. & P. 1/- . 20 for £1. P. & P. 5/6.

EXTENSION SPEAKERS. 19/9. In attractive cabinet. Complete with 8 in. P.M. speaker, flex and switch. Standard matching to any receiver. 2-5 ohms. Size 11 in. x 13 1/2 in. x 6 1/2 in. A nice present and a real bargain. P. & P. 3/6.
VISCONAL CONDENSERS. 5/9. 0.001 µF, 12.5 Kv working, and 0.1 7 Kv working. P. & P. 6d.

COIL PACK SETS. 3/9. Bargain including 3 w./band coil pack. 2 gang condenser. Pair 455 I.F.s. P. & P. 2/3.

INSULATING TAPE. 1/6 Roll. Finest quality tape. 75 ft. x 1 1/2 in. wide. In sealed metal container. BARGAIN. Post on 1 tin 9d. On six tins 2/-.

SOLDER REELS. 1/6. 20 ft. 3 core ERSIN solder. 60/40. P. & P. 4d.

GANGED CONDENSERS. 1/9. Standard size .0005. 2 and 3 gang. Salvage. Guaranteed. P. & P. 1/3.

Stamp for Catalogue.

U.K. only.

219 ILFORD LANE, ILFORD, ESSEX.

Phone: ILFord 0295.

RST

MAIL ORDER DEPARTMENT

211 Streatham Road, Mitcham, Surrey.

ALL VALVES LISTED ARE NEW STOCK

• Terms C.W.O. or C.O.D. Postage 3d. per valve.

MITCHAM 6201.

AZ31 10/8	EF93 7/6	N153 11/3	UCL33	6K7 4/6
B65 8/8	EF93 12/-	N154 11/3	19/6	6K7GT 10/-
DAF91 9/-	EF91 10/-	N727 9/6	UF41 8/-	6K8GT
DAF93 9/6	EF91 8/6	PCC84 11/6	UF39 10/-	
DD320 10/6	EF95 14/-	PCF80	UL41 9/6	6L1 12/3
DF31 8/8	EL42 10/-		UL44 9/-	6L6G 7/6
DH71 9/8	EL84 9/-	PCF82	UY41 7/6	6L8 12/6
DK41 9/-	EL90 8/6	PCL82 11/6	UY95 8/-	6L9 21/-
EABC30	EM80 10/-	PCL83 12/6	VF43 17/6	6N7G/GT
EAF42 10/-	EM81 11/6		W181 8/6	6SL7GT 8/-
EB31 5/9	EY81 10/-	PEN41 15/6	W192 8/6	6SN7GT 7/6
EBCH1 9/3	EY84 13/-		W727 8/6	
EBF81 9/8	EY86 14/6	PEN44 11/6	X78 19/-	6X5GT 8/6
EBF83 9/8	EY91 9/-	PEN4VA 11/6	X79 17/-	6X5GT 8/6
EBF83 9/8	EZ35 8/6		Z21 10/6	7Y4 12/8
EC31 8/9	EZ40 8/-	PL33 15/-	Z77 10/8	7Y4 7/6
ECC33 8/6	EZ41 10/6	PL31 17/6	Z152 8/6	8D3 8/6
ECC31 8/8	EZ83 8/-	PL32 10/-	Z719 8/6	10L1D 14/9
ECC33 9/-	EZ81 8/-	PL33 14/-	1R5 9/-	12AH8 10/-
ECC84 10/-	FC2 14/6	PY30 8/3	5Y3GT 8/6	12AT6 8/9
ECC85 10/6	FC4 23/8	PY81 9/6	5Z4C 10/-	12AT7 8/9
ECF30	FC13 14/6	PY82 8/6	6A9GT	12AU7 9/-
	FC13C 19/6	PY83 8/6		12AX7 9/-
ECF32	GZ32 13/6	R10 22/-	6AL5 5/9	12BA6 8/9
ECH33 12/8	H30 4/9	R19 19/-	6AM5 9/-	12BE6 9/3
	H63 10/-	TDD4 15/-	6AQ5 7/8	12BH7 10/-
ECH42 9/6	HBC30 8/-	TP22 12/6	6BAS 8/6	12J7G/GT
ECH81 9/3	HL92 11/6	U142 8/6	6BE6 8/3	10/-
ECL80	HL133D 11/6	U147 9/9	6B76 12/6	12K7GT 8/6
	KT33C 12/6	U153 9/6	6B76 12/6	12K8GT 10/6
ECL32 13/6	KT33 16/8	UABC8 10/-	6BW6 8/6	12K8GT 12/3
EF37A	LZ319 12/6	UAF42 10/-	6BW7 9/6	12Q7 8/6
	MKT4(G) 15/-	UBC41 8/6	6BX5 8/6	12Q7GT 8/6
EF41 15/-	(or 7) 21/-	UBF80 9/6	6D2 5/9	12Q7GT 8/6
EF41 9/6	ML1 12/3	UBF81 9/6	6F1 19/3	35Z4GT 8/6
EF42 12/-	MSP4 15/-	UCH12 10/-	6F12 8/8	35Z4GT 8/6
EF50 (A)	MU14 10/-	UCH31 10/8	6F13 13/6	30L6GT 8/6
EF50 4/6	MX4 15/-		6J3G 8/6	
EF80 8/-	N113 9/8		6J7G T 10/-	

Quotations given for any types not listed. Obsolete and old types a speciality.

TV PICTURE TUBES

QUALITY REBUILT

AND FULLY GUARANTEED SIX MONTHS

TRADE & RETAIL ENQUIRIES S.A.E., PLEASE

LINE OUTPUT TRANSFORMERS AND DEFLECTOR COILS

Most types can be supplied. State set, make, model number and part required. S.A.E., please.


Terms : C.W.O. or PRO-FORMA INVOICE

PRIME ELECTRICS (Dept. W/2)

36, QUEENSDALE ROAD, LONDON, W.11

(Nr. Shepherds Bush Central Line.) Phone PARK 4131

Callers : 10.30-3 Mon.-Sat. Closed Wed.

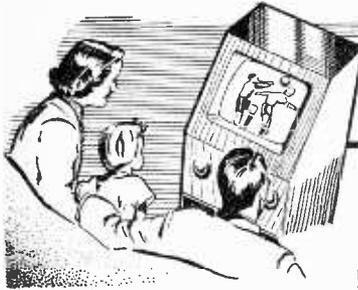

UNDERNEATH THE DIPOLE

A MONTHLY COMMENTARY

By Icons

Mutual Aid

THE healthy and prosperous state of the British television industry is reflected in the thirst that has developed amongst its technicians for technical education.

The Television Society and the British Kinematograph Society, independent of one another and yet co-operating amicably in the arrangements for their meetings, are receiving strong support from both BBC and I.T.A. engineers. The programme companies are supporting these societies financially by becoming patrons or providing facilities for lectures and studio visits. Special "refresher" courses are being fully attended, which are followed by lively discussions in which many a new idea is put forward—and noted by the equipment manufacturers present. The London Polytech-

nic is now considering the establishment of a British School of Cinematography, which will organise a two-three year course on film production, this term to cover film production for television, including photography and sound recording. There has long been a need for such an educational centre, but it has required the impetus of television to get things going. Schools of this type already exist in Paris, Warsaw, Moscow and Hollywood, and these are already tending to take the television aspects into their curriculum. At the moment, 35 mm. and 16 mm. film is the basis of all of these educational schemes, but it cannot be long before magnetically recorded pictures come under the terms of reference.


Provincial Centres

THE lecture activities of these societies are mainly confined to the London area, but in

the case of the B.K.S., there are active branches at Manchester and Leeds. The Granada Television Network, Manchester, has given great encouragement to these branches by providing a preview theatre for lectures and conducted studio visits. The Television Society has not yet penetrated the provincial cities, but will sooner or later have to consider this step. In a curious way, these societies do not appear to overlap. Broadly speaking, the Television Society deals with problems of design and the B.K.S. with problems of operation. The former covers research development and maintenance, while the latter includes production techniques, art work and set design, telerecording of all kinds (including video-tape), lighting and camerawork.

Video Tape Problems

THE Ampex magnetic video tape system is rapidly becoming a world standard for internal use in television studios. I say "internal use" because the magnetic recording of pictures at British television studios is naturally on the 405 line standard, whereas the Americans use 525 lines and most other countries use 625 lines. However, as a delayed programme storage, more uses are being found for Ampex equipment every day. The lecture by W. H. Cheevers to the B.K.S. on "Practical Experience with Video Tape Recording" at the Royal Society of Arts attracted much attention, and the demonstration and paper were followed by a lively discussion, which revealed many of the operational advantages—and difficulties—of picture recording on tape. One interesting disclosure was the possibility—and difficulty—of editing the recorded material. Mr. Cheevers stated that joints in the video tape could be made, but required great skill and took about 45

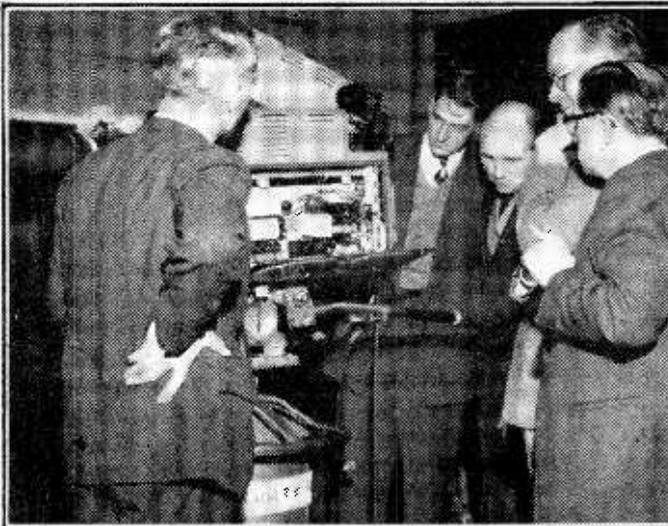

The inner workings of an image orthicon camera being explained to an interested party, following a lecture by Mr. R. Hammonds, the Chief Engineer at Granada, Manchester.

minutes to do! Every effort was being made to reduce this, but so far, it was only achieved at the risk of picture disturbances, rolling, breakage of tape and similar faults.

Paramount Films, Hollywood, were said to have evolved a splicing device that was reasonably reliable, but this was not yet available. Part of this lecture was given by playing back from the Ampex recorder at Associated Rediffusion's Studio in Kingsway, a recording made earlier of Mr. Cheevers talking into a television camera. This was sent by line to the Royal Society of Arts and reproduced on two large monitor sets. Various possible faults in recording and drop-outs on the tape were simulated, as well as normal first-class reproduction of recordings made of live television and films that had actually been transmitted to the public. Though video recording was now quite reliable, Mr. Cheevers said that telerecording on photographic film would be with us for many years, especially for exporting recorded programmes abroad.

Repertory Companies

MY recent remarks in this column about the aid that commercial television contractors are giving caught the eye of the theatrical newspaper, *The Stage*. Whilst supporting my theory that the repertory movement needed audiences as well as money, the repertory editor doubted the effectiveness of a "what's on" list of theatres appearing in a free TV advertising slot. I agree that a long list of theatres such as appear in the London and national newspapers, would not mean very much. But in some of the new smaller I.T.A. areas, such as T.W.W., Southern, Tyne-Fees and Anglia, the number of live theatres is regrettably low and patrons often travel many miles to see a play, musical comedy or music hall. An announcement covering the few remaining theatres would be a service to the playgoers who are also television viewers. After all, plenty of free space has been given to films in one way or another in such items as *Picture Parade*, *Picture Profiles* and *Close Up*.

Everlasting Series

FOR some reason that I have been unable to fathom, television series, whether live or on film, seem to aim at a total number of 39 episodes. Of course, some of them fall by the wayside before reaching this figure and a few—very few—seem to go on for ever. Both the BBC and I.T.A. wisely rest the popular ones for a few months, before they outstay their welcome. *Waggon Train*, *I Love Lucy*, *Robin Hood*, *Burns and Allen* and *The Army Game* have all had phenomenal successes, and one cannot help admiring the ingenuity of the producers in keeping the ball rolling. *Emergency-Ward Ten* (A-R) has proved very popular, but the other medical serial *Mary Britten M.D.* (Southern) has not stayed the course on the commercial networks.

It was most praiseworthy and ambitious of Southern to enter the highly competitive field of the network so early in their operations. I hope it will be followed up with a rather more active serial, with less throw-away lines and padding. This serial suffered from poor acting in the smaller parts—all the principals were first class. *Emergency-Ward Ten*, on the other hand, is excellently cast in all the parts, even the smallest. However, some of the pretty nurses are inclined to be a little inaudible at times.

Vidicon Cameras

THE BBC studios in London are at present more or less standardised on Marconi 4½in. image orthicon cameras and C.P.S. Emitron cameras of the new sensitive type. Each type of camera has its special advantages. The C.P.S. Emitron has a very good grey-scale and photographic quality, which flatters the "victim." The 4½in. image orthicon gives a very sharp picture indeed and is slightly more sensitive. BBC engineers are divided on which is the better camera, but each has advantages for particular fields. When a play calls for delicate lighting effects and many close-ups, the C.P.S. is preferred. For other shows, with quick action and detail required in long shots, the image orthicon wins. But there is now another type of camera which is steadily improving—the vidicon. Originally used for industrial purposes, clock dials and telecine, this type of camera has been improved rapidly in the last few months and is found in many BBC and I.T.A. presentation or interview studios. Main improvement has been in the camera tube, which rivals the C.P.S. camera in its photographic qualities when a specially selected tube is carefully lined up. Naturally, as the camera is less than half the price of the big ones and very nearly half the weight, it is having a big appeal to television engineers.


PRACTICAL WIRELESS

CHIEF CONTENTS OF MARCH ISSUE

NOW ON SALE, 1/3.

A STEREOPHONIC AMPLIFIER
A SIX-VALVE CAR RADIO
A PUSH-BUTTON MULTI-RANGE TESTMETER
PRINTED CIRCUITS
A.V.C. WITH "STRAIGHT" VALVES
SERVICING RADIO RECEIVERS
STEREO BY RADIO
THE THERMISTOR IN PRACTICE
A WIDE RANGE AUDIO SIGNAL GENERATOR
AN ECONOMY MAINS TRANSPORTABLE
BASIC THEORY FOR CONSTRUCTORS

Complete Walkie-Talkie 25/-

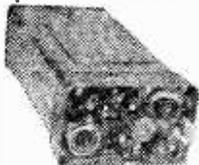

This is the 46 Walkie-Talkie. It has a range of approx. 5 miles—just right for search parties, fire brigades, etc. Operates from dry batteries. Complete with six valves and in metal case. Size approx. 12in. x 6in. x 3 1/2in. Complete but best crystal, not tested nor guaranteed. 25/- plus 2/6 carriage.

Band III Converter

Suitable Wales London, Midlands, North, Scotland, etc. All the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers, and resistors. (Metal case available as an extra.) Price only 19/6 plus 2/6 post and insurance. Data free with parts or available separately. 1/6.

Please send two more kits, the one you sent last week is performing magnificently.

We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

Battery Charger

High output car battery charger, gives quick (car start charge) or trickle charge. Input standard A.C. mains, output 6 or 12 volt at 1-2i or 4 amps. With meter and variable charge selector. Complete in hammer finish louvered case. Only 75/-, plus 4/6 carriage, or 10/- deposit and 8 fortnightly payments of 9/-. New and unused, guaranteed for 2 years.


FREE GIFT

All purchasing this month, will receive as a free gift, a pair of heavy duty charging clips.

Cathode Ray Bargain

VCR517C 6 1/2in. (medium persistence) plug in replacement for VCR97 offered at the bargain price of 8/6 each, plus 3/6 carriage.

The Fluorescent Lighting Kit

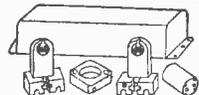

For customers wishing to use fluorescent lighting without metal work, for shop window lighting, etc. We offer complete kits of parts. Five items as illustrated comprising best quality choke ballast, canister starter and white bakelite holders. 40 watt kit 22/6, 80 watt kit 26/6 plus 2/- post and insurance.

If ordering by post, address your order to the Company nearest to you and please include postage.

Electronics (Eastbourne), Ltd.
66, Grove Rd., Eastbourne, 6565.
Phone: Eastbourne 6565.
Half day Wednesday.

Electronics (Ruislip) Ltd.
42-46, Windmill Hill, Ruislip, Middx.
Phone: RUISLIP 5780.
Half day, Wednesday.

Electronics (Croydon) Ltd.
266, London Road, Croydon.
Phone: CRO 6559.
Half day: Wednesday.

Electronics (Finsbury Park, Ltd.).
29, Stroud Green Rd., Finsbury Park, N.4.
Phone: ARCHWAY 1049.
Half day, Thursday.


Pullin Series 100 Test Set

Undoubtedly a most useful instrument by a firm long famous for fine instruments, entirely redesigned, it has a square movement with diacon plastic cover. This makes for a brighter more readable scale, extra scale length and wide range of vision. With the test set, is included a pair of combined test prods and crocodile clips also a stand for inclining the meter at the best reading positions. Ranges A.C. Volts: 0-10, 0-25, 0-100, 0-250, 0-500, 0-1,000, ditto D.C. A.C. Current 0-100 mA, D.C. Current 0-2.5, 0-10, 0-100, 0-500 mA. Resistance: 0-1M and 0-10K. All at 10,000 ohms per volt.—Price £12.7.6 or £1 deposit and 24 fortnightly payments of 10/-, non callers add 5/- carr. & ins.




FREE GIFT.—All purchasers of the above item this month will receive Range Extender scale and data which add: capacity 2pF.—1mFd., in two ranges. Inductance 0-100 henrys, etc., etc.

Gram into Tape Recorder

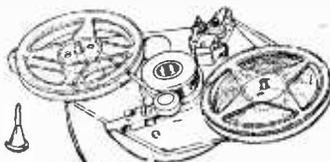

Convert your Record Player or Radiogram into a Tape Recorder. Can be fitted (or removed) in a few seconds and then you have all the facilities afforded by a normal Tape Recorder, record, playback, erase, rewind, etc. As top part of illustration with circuit of suitable Pre-Amp. Price only £7.10.0 or 10/- down and 16 fortnightly payments of 10/- or as per illustration that is with Pre-Amp., £13.2.6, or £1 down and 26 fortnightly payments of 10/-.

Famous Transmitter Virtually Given Away

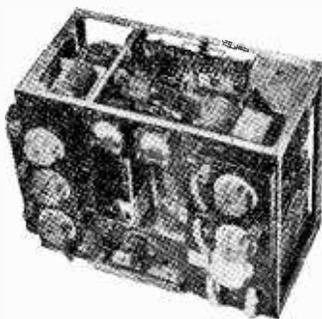

The famous RU154—unused but slightly soiled and not tested. Covers 200-500 kc/s., 3-5.5 Mc/s and 5.5-10 Mc/s. Has unique "click stop" mechanism (7 stops) and permits selected frequency to be held, returned to, etc. Harley oscillator, power amplifier, keying and speech. Wonderful breakdown value meters, relays, switches. Complete with valves—real bargain at 29/6, plus 10/- carriage.


**Hi-Fi Snip
Infinite Wall Baffle**

Nicely veneered and polished. Corner fitting (a t t aches to picture rail). Takes up no floor space. Gives really fantastic results with only low-priced 8in. speaker. Fitting for tweeter. Only 45/- each. Carriage and insurance 3/6.



14in. T.V. Cabinet

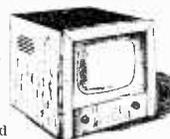14in. T.V. cabinet of latest styling made for one of our most famous firms—beautifully veneered and polished. Limited quantity—15/- each. Carriage and packing 3/6 extra.



MULTI-SPEED MOTOR

Works on A.C./D.C. mains; fitted with gear-box gives any speed from 1 r.p.m. 22/6 post and packing 1/6.




Break-up Bargain

The unit 3515 less valves and I.F. strip. This contains components valued at least £10 as follows:
20—Paper tubular condensers up to 1 mfd.
60—Carbon Resistors many high stability.
40—Silver Mica Condensers.
30—R.F. Chokes.
13—Octal Valve Holders.
1—Yaxley Switch.
1—A.F. Choke.
2—Miniature Variable Condensers.
1—Transformer.
2—Mansbridge Condensers.
1—Useful chassis size 18in. x 11 1/2in. x 7 1/2in. with outer case. Plus hundreds of miscellaneous items, nuts, bolts, washers, tag trips, I.F. sockets, etc. All for 6/6, plus 5/- carriage up to 250 miles.

A.C./D.C. Multimeter Kit

Ranges: D.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. D.C. milliamps 0-5, 0-100, 0-500, 0-50,000 with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions. Price 19.6, plus 2/6 post and ins.

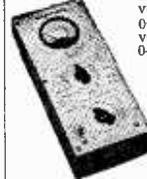

Absolutely No Pre-Cleaning with the VICTOR

Soldering Tool



Covered by British & World Patents

The VICTOR is *revolutionary*—it heats the work direct by gripping it with the twin arms of the tool. Simply press the button, the work instantly heats up and the solder runs. *No pre-cleaning—even of oil—is required except where the metal has been oxidised previously.* Operation is from a 6 VOLT supply.

For heavier materials and work the 6-12 volt VENUM Soldering Tool is available. Price £4 4s.

TRADE ENQUIRIES INVITED.

Price
£2. 2s.

- * Speed in operation
- * Versatility
- * Low-voltage safety and economy

Please supply VICTOR/VENUM (quantity.....) NAME I enclose P.O./cheque value £.....

soldering tool/s or send me free illustrated literature. ADDRESS P.T.202

ALLIED DISTRIBUTING CORPORATION LTD. 13/17 Rathbone St., London, W.1. MUSeum 5411

OPPORTUNITIES IN TELEVISION

148 pages
Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit., I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 148-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

We Guarantee "NO PASS—NO FEE"

If you are earning less than £20 a week you must read this enlightening book.

Send for your copy **NOW—FREE** and without obligation.

WRITE TO-DAY!

British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane, **BIET**
Kensington, W.8.

TELEVISION ENGINEERS' POCKET BOOK

The new and enlarged edition of this pocket manual and data book has been extensively revised. Many pages of essential reference data on cathode-ray tubes, valves, also special sections on servicing equipment, dealing with printed-circuit models and projection receivers, aerials and interference problems.

Ed. by J. P. Hawker.

12/6. Postage 6d.

THE RADIO AMATEUR'S HANDBOOK, by A.R.R.L., 1959 Ed., 32/6. Postage 1/9.

TELEVISION SERVICING HANDBOOK, by G. J. King, 30/- Postage 1/3.

SERVICING TRANSISTOR RADIOS, by L. D'Airo, 23/- Postage 1/-.

WORLD RADIO HANDBOOK FOR LISTENERS, 1959 Ed., 14/6. Postage 1/-.

IMPROVE YOUR RECEPTION, by J. Cura & L. Stanley, 5/- Postage 4d.
RADIO VALVE DATA, by "V.V.V.", 6th Ed., 5/- Postage 9d.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET, LONDON, W.2.

Complete catalogue 6d.
Phone: PADdington 4185.
Open 6 days 9-6 p.m.

Amplifiers, 3-4 watts, ECL82 triode-pentode two-stage with tone and volume control; size 7in. x 2 1/2in. x 5 1/2in., 72/6. Ion Trap Magnets, 5-. 0.1 mid., 500v. Stragic Conds., 8 - doz. Pre-set Pots., all values, 3-. T.R.F. Coils, 7- pair. Balanced B.M. Twin Feeder Cable, 6d. per yd. Air-spaced Coaxial Cable, 9d. per yd., 65- per 100 yds. Television Aerials, Band III 3-element, 24/6; 5-element, 37/6; 8-element, 57/6; Single Dipole Band I, 32/6; "H," 70-. We carry large stocks of good aerials. Send S.A.E. with your requirements and we will reply by return.

Television Tables, 20in. x 20in. x 2 1/2in. high, walnut finish, 67/6.

Guaranteed Valves

AZ1	12/6	PY31	15/-	UL46	18/6	6BW6	8/6
AZ31	12/6	PY32	15/6	UL84	10/6	6BA6	8/6
CBL1	22/6	PZ30	15/6	UY41	7/-	6AT6	7/6
CBL3	22/6	PCF80	UY85	7/6	6BG6G		
CL3	15/-	PY81	12/6	IA7	16/6	6U4	17/6
CY31	12/6	PY82	8/6	IA5	4/6	6F6	9/6
EBL31	19/6	PY83	8/6	IN5	13/6	6V6G	8/6
		PL81	18/6	IH5	13/6	6Q7	9/6
EBL1	19/6	PL36	17/6	IC5	12/6	6SN7	5/6
EBC33	16/6	PC84	ILN5	3/6	25Z4	9/6	
EF39	14/6	15-	1R5	7/6	35Z4	9/6	
EF80	10/6	16/6	1T4	7/6	25U4	15/-	
EF85	9/6	UABC90	2X2	3/6	50L6	15/-	
EF88	11/6	11/6	2A5	16/6	807	5/-	
EL33	15/6	UAF42	3C4	12/6	1825	6/6	
EBF80	11/6	5Y3	10/6	6CH16	6/6		
	11/6	UBC41	7/6	5U4	10/6	6SL7	5/6
ECL82	11/6	UBF80	9/6	5V4	10/6	6F8	5/6
	15/6	UCH42	8/6	5Z4	10/6	U404	7/-
GZ32	14/6	UCL83	6AT	15/6	PEN46	8/6	
PT33	15/6	16/6	6K7	2/6	6L6G	9/6	
PL38	22/6	UL44	22/6	6K8	9/-	3D1	3/6

MAIL ORDER ONLY—NO CALLERS. Terms: C.W.O. or C.O.D. Minimum C.O.D. charge 3/6. Postage and packing per valve, 6d. Other items under £2 1/6; £5, 2/-. Aerials 2/6 carriage.

ELECTRO-SERVICES & Co.
221 BATTERSEA PARK ROAD,
LONDON, S.W.11. #IAC 8155

Completion of I.T.A. Service

PLANS for the practical completion of its present television service by 1960 have now been provisionally approved by the Independent Television Authority.

According to these plans, the last programme companies will be appointed this year and the last major service areas will be provided with programmes in 1960, four years before the end of the ten-year life of the Television Act of 1954.

The Authority has so far appointed ten independent programme companies:

Programme Company	Service Area	Air Date
Associated-Rediffusion	London (weekdays)	September, 1955
Associated TeleVision	London (weekends)	September, 1955
Associated TeleVision	Midlands (weekdays)	February, 1956
A.B.C.	Midlands (weekends)	February, 1956
A.B.C.	North (weekends)	May, 1956
Granada	North (weekdays)	May, 1956
Scottish Television	Central Scotland	August, 1957
T.W.W.	South Wales and West	January, 1958
Southern Television	Central South	August, 1958
Tyne Tees Television	North East	January, 1959
Anglia Television	East Anglia	Late, 1959
Ulster Television	Northern Ireland	Late, 1959

Of these ten companies, seven are already supplying programmes for the Authority's service, while programme transmissions in the service areas of the last three begin this year: the north-east coast in January, and East Anglia and Northern Ireland towards the end of the year. (The name of the recently appointed Northern Ireland company is not yet final.) More than 91 per cent. of the population will then have been brought within the Authority's service areas.

The completion of the Authority's first service will then require:

1. Three New Service Areas

Three new service areas are still to be created, making a total of thirteen within the first service. The Authority hopes to begin transmissions in all of them in 1960 or at the latest in the winter of 1960-61. They are:

(a) South-west England

This service area will include about one million people living in Devon and Cornwall. This area cannot be covered by one Band III transmitter, and the Authority hopes to build two stations, one in Devon and one in Cornwall, to come into simultaneous operation and to radiate the same programmes. Various sites have been examined, but none has been finally selected and submitted for Post Office approval. The extension of the I.T.A. service to the South-west has been approved in principle by the Postmaster-General.

(b) North-east Scotland

This service area will serve the population of some 600-700,000 people living broadly within the large triangular area of which the points are Fraserburgh, the Moray Firth, and Forfar. As a

result of the capital expenditure restrictions still imposed upon the Authority, it has not yet been possible for the Postmaster-General to give formal approval for transmissions by the Authority in this area, but preliminary work has already been undertaken. The transmitting station will almost certainly be built in Aberdeenshire.

(c) The Solway

This service area includes about 450,000 people living on both sides of the Border around the Solway Firth in Cumberland, Dumfries, Kirkcudbright and Wigton. This station, which has the Postmaster-General's approval, will be placed on the English side of the Border, but the site is not yet determined.

2. Four to Six Satellite Stations

Beyond these 13 main service areas, the Authority sees the need for four to six satellite stations to serve areas not reached by its transmissions but too small to require or make financially possible the operation of independent companies. The first of these, which has been approved, will be opened near Dover in the winter of 1959-60. Further satellites are being considered for the Berwick area, West Wales, Inverness, and the Channel Islands and the Isle of Man. Consideration is also being given to the possibility of building some small satellite stations along the west coast of Scotland, but this is not an immediate prospect.

3. Improvement of Two Existing Stations

In two important cases the Authority is transmitting from stations which fall short of what is technically possible. In the time available, it was necessary to begin transmissions in London from the present temporary station at Croydon and from a tower of only medium height at Lichfield. The Authority intends to radiate its London signal from a higher and more powerful aerial and to substitute a tall mast for the present tower at Lichfield. These improvements are expected to add about 800,000 people to the London service area and about the same to the Midlands.

The completion of this programme should give the Authority's first service something like 99 per cent. coverage. This will have been broadly achieved by the use of only four of the eight Band III channels, leaving the remaining four available for a new television service. If by the time of its completion in 1960-61 there is still no decision about a third television service, the Authority's programme of construction will be finished except for keeping pace with technical change and giving consideration to the possibility of filling in such small gaps as remain in isolated towns or remote regions.

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

UNIT "161"

SIR.—I used the "161" unit, which was the subject of an article in the December, 1958, issue, to receive the early test transmissions and later the programmes from ITV. At that time it was advertised as 160/220 Mc/s with an I.F. output of 16.5 Mc/s and the 178A I.F. amplifier was offered as the complementary unit. I also, like your contributor, used the unit as a front end converter but replaced the I.F. transformer L4, L5, L6, L7, with a single Aladdin coil wound to 45 Mc/s as has since become common practice in this type of circuit.

By removing the switch mechanism it is possible to use any pair of the eight turret coils thereby obtaining a varied selection of I.F. outputs.

Fitting the appropriate I.F. transformer renders the unit suitable for use as a front end converter for any channel or for injection into the I.F. section of any receiver. The versatility can be further increased by re-winding the turret coils as required, which is by no means difficult if one first removes the two screws holding the brass cores which can then be used to size the coil diameter.—W. HIGGINS (Beckenham).

SERVICING DATA

SIR.—Your correspondents who complain of unwillingness on the part of certain manufacturers to supply technical information have my sympathy.

I purchased a television set and within a fortnight it had broken down. The set sent in replacement started giving trouble within three months.

Complaints and requests for information have produced a lack of interest on the part of the manufacturer that I would not have thought possible had I not experienced it. Even a solicitor's letter produced the same result. Apparently it is merely my misfortune to have acquired two pieces of inefficient apparatus.

Your correspondent in the January issue who has given up and contemplates purchasing another receiver is merely playing into the manufacturers' hands. The industry will have sold two receivers.

There must surely be some remedy for those who are dissatisfied with the standard of the equipment they buy or the service, or lack of service, they obtain.—D. MAINSTONE (Goring).

[In certain cases the purchaser can sue for breach of implied warranty.—ED.]

LINE TIMEBASE

SIR.—In my experiences as a service engineer I have found quite a few faults which occur in the line timebase circuit that can be quite puzzling. One example that caused a considerable amount of search was where the line slipped

after a short period and needed continual resetting. Sync was at first suspected but sync pulses were arriving O.K. The trouble turned out to be two condensers in the feedback circuit, altering their capacity with change of temperature. A change to silver mica condensers effected a cure.

A further interesting line fault was where the line output transformer was overheating. The horizontal drive control was checked and was apparently incorrectly set. However, this was due to the anode resistor of the line oscillator valve going high in value, causing incorrect line drive. By the way, an indication of incorrect horizontal drive is often a white vertical bar down the centre or slightly to the left of picture.—F. E. A. (London, W.6).

SPECIAL NOTE

Will readers please note that we are unable to supply Service Sheets or Circuits of ex-government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

9in. PYE MODIFICATION


SIR.—I have heard that it is possible to dispense with the heavy mains and EHT transformer in the early 9in.

Pye and similar TV sets. Apparently the method was a heater transformer for the valves and tube, and H.T. from rectified mains current. The EHT of some 3,000 v. is obtained by two high voltage ex-Government rectifying valves on the line flyback.

Could any reader give details of this modification, especially a circuit with component values given.—C. W. BROOKS (Oxshott).

ITV AERIAL

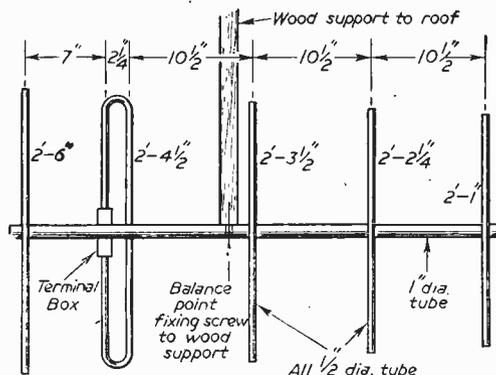SIR.—I have recently constructed a five-element, Channel 9, ITV aerial which gives excellent results. It is installed in the loft space of my house, and is supported by a single piece of wood which is fastened to a roof member. The sketch below shows the dimensions and construction of the aerial.—P. G. (Manchester).



The home constructed ITV aerial.

...another TRS Winner




Latest 4-tube BSR Player Unit and P.U. ... £4.12.6 carr. 3/6
 2 v. Amplifier wired complete with speaker, etc., on Mounting Board ... £3. 5.0 carr. 2/6
 Contemporary styled lightweight case in Maroon and Grey. 14 1/2 in. x 11 1/2 in. x 6 in. ... £1. 7.6 carr. 2/6

SPECIAL OFFER

all 3 units
 only £9 carr. 4/6



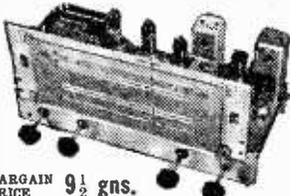ALL-WAVE RADIOGRAM CHASSIS 3 WAVEBANDS 5 VALVES



BARGAIN PRICE 9 1/2 gns.
 or 10 in. speakers to match. 20/- and 25/- P. & P. 1/6

CONVERTER ACCESSORIES

Band 1-Band 3 Cross-over Unit, 7/6. Var. Attenuators 6db-36db., 7/6. BBC Pattern Filter, 8/6. Band 3 Aerials—outside Single Dipole with 4 yds. co-ax., etc., 13/9. 3 Element Beam, 25/-, 5 Element, 32/6.

VOLUME CONTROLS

10,000 ohms—2 Megohms. All long spindles. Morganite Midget type, 1 in. diameter. Guar. 1 year. Log. or Lin. Ratios. Less Sw. 3/-, D.P. 5/-, 4/9.

RECORD PLAYER CABINETS

Contemporary Cabinet style, rexine Price covered cabinet £3.3.0. in fawn and brown with cream interior. Size 18 1/2 x 13 1/2 x 8 1/2 in., fitted with all accessories, including baffle board and anodised metal fret. Space available for all modern amplifiers and auto changers, etc. Uncut record player mounting board 14 x 13 in. supplied.



2-valve AMPLIFIER Mk. 2

Latest developed circuit giving a higher fidelity response and greater output (2.3 watt) using twin stage valve ECL82 and neg. feedback Tone Control. Complete with knob wired and tested with 6in. Speaker, etc., ready to fit in above cabinet. Only £3.19.6. Carr. 2.6.

RECORD PLAYER BARGAINS

New Reduced Prices!

SINGLE PLAYERS 4-speed BSR (TU9), 92/6; 4-speed COLLARO JUNIOR, 90/-; 4-speed GARRARD (4 S.P.), £7.15.0. GARRARD (TA Mk. 11), £9.5.0. Carr. and Ins. 3/6.
AUTOCHANGERS 4-speed BSR (UA8), £8.19.6; 4-speed COLLARO, £7.19.6; GARRARD (RC12 D Mk. 11) Plug-in head, stereo adapted, 10 gns. BSR UA12 latest stereo model, 10 gns. Carr. and Ins. 4/6. All above units are latest 4-speed models, fitted lightweight crystal pick-up and twin sapphire styl. Complete and ready to use.
FINEST SELECTION AVAILABLE—ALL BRAND NEW AND GUAR.

S.W. 16 m.—50 m. LATEST MIDGET B V A SERIES
 M.W. 200 m.—500 m. B V A SERIES
 L.W. 800 m.—2,000 m. B V A SERIES

Brand new and guar. A.C. 200-250 v., 4 pos. W/C sw. Short-Medium-Long-Gran. P.U. socket. High Q dust core coils. Latest circuit technique, delayed AVC and neg. feedback O/P 4 watts. Chassis size 13 1/2 x 5 1/2 x 2 1/2 in. 13al 10in. x 4 1/2 in. Hor. or Vert. station names. Walnut or Ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost. Carr. and ins., 4/6.

7 Valve De Luxe, push-pull EL41 version, 7 watt output, with H.T. Output Transformer, £12.10.0. Carr. & ins. 5/-.

C.R.T. Heater Isolation Transformers

New Improved types—mains prim. 200/250 v. tapped.

All isolation Transformers now supplied with alternative no boost plus 25%, and plus 50% boost taps, at no extra charge.

2V.	2A type	12/6 (P. & P. 1/6)
6.3V.	.6A	12/6
10.5V.	.3A	12/6
13V.	.3A	12/6

Other voltages in course of production. Small size and tag terminated for easy fitting.

JASON F.M. TUNER UNIT 87-106 Mc/s.

Factory Approved Kit of parts to build this modern highly successful unit, drilled chassis and superior type dial, coils, cans, and all quality components, etc., for only 5 gns., post free. Set of 4 spec. EF85 or equiv. valves, 30/-, post free. Illustrated handbook with full details, 2/- post free. FREE WITH KIT, 48 hr. alignment service, 7/6 plus 2/- P. & P.

NEW BOXED VALVES

ALL	GUARANTEED
1R5, 1T4, 7, 6	DF96 9/- EF41 10/6 PCF82 12/6
1R5, 1R4, 7, 6	DK96 9/- EF80 10/6 PCL83 12/6
3A4, 3V4, 8, 1	DL96 9/- EF86 14/6 PL81 14/6
5Z4	8, 6 35L6 10/6 EF91 8/6 PL82 10/-
6AT6	8, 6 2AB6 9/6 EL41 10/6 PL83 11/6
6K7	8, 6 EB91 10/6 EL84 11/6 PY40 9/6
6K8	8, 6 EDC41 10/6 EM85 11/6 PV81 9/6
6Q7	8, 6 ECC83 9/6 EY51 12/6 PY82 8/6
6SN7	8, 6 ECX48 12/6 EY86 14/6 PV83 10/6
6X6	7, 6 EC980 12/6 EZ40 8/6 U22 8/6
6X4	7, 6 EC982 12/6 EZ80 9/6 U25 15/6
6X3	7, 6 EC142 10/6 EZ81 8/6 UCH42 10/6
7C5	8, 6 EC181 10/6 MU14 9/6 UP41 10/-
7Y4	8, 6 1CL89 12/6 PCC84 10/6 UL41 10/6
DAF96	8, 6 ECL82 12/6 PCF80 10/6 UY41 8/6

SPECIAL PRICE PER SET

1R5, 1T4, 1R5, 1R4 or 3A4, or 3V4	27/6
1R5, 6, 6, 7, 6, DA F96, 11, 50	27/6
6K8, 6K7, 6Q7, 6V4, 5Z4 or 6X3	35/-

RE-GUNNED TV TUBES

GENUINE OFFER

New Heater, Cathode and Gun Assembly can now be fitted to your old Tube—Reconditioned virtually as new. Fully guaranteed to highest standards—as used by our own Service Dept.
 12in. £8. 14in. £8.10.0. 17in. £10.
 Regret only Mullard and Mazda types at present. Delivery approx. 7 days. Carr. & ins. 12/6.

ELECTROLYTICS ALL TYPES NEW STOCK

25/25 v., 50 12 v. 1 1/2 Can Types, Clips 3d. ea.	3/-
25/50 v. T.T.C.	2/- 3/500 v. Dub.
50/50 v., 4,500 v.	2/- 8+8/450 v. T.C.C.
100/25 v., 2,400 v.	2/- 8+16/450 v. Hunts
8/450 v. T.C.C.	2 3 16+16/450 v. T.C.C.
8+8/450 v. B.E.C.	4 E 32/350 v. B.E.C.
8+16/450 v. T.C.C.	5 32+32/275 v. Hunts
16/450 v. B.E.C.	3 16+2+32/450 v. T.C.C.
16/500 v. Dub.	4/- 250/350 v. B.E.C.
10+16/450 v. T.C.C.	5/600/350 v. T.C.C.
32/350 v. B.E.C.	4/- 60+100/350 v. B.E.C.
32/500 v. Dub.	5/- 80+250/275 v. B.E.C.
50+50, 550 v. B.E.C.	6/- 100+200/275 v. B.E.C.

MULLARD 3-3 QUALITY AMPLIFIER.—A

First-class Hi-Fi Companion Unit to the Jason Tuner. Hi-Duty Mains Transformer allows for H.T. and L.T. Power supply. Mullard's latest circuit, 3 valve, 3 watt. Freq. response 40 c/s-25 Kc/s + or -1db with special sectionalised O/P/T Trans., Punched chassis, all components, valves, etc. Only £6.19.6. Ready wired and tested. 8 gns. Carr. and ins. 4/6.

SEMPERCEL RECTIFIERS. E.H.T. Type Fly-back

Rectifier Voltages. K3.25 2 kV., 5/-; K3/40 3.2 kV., 8/9; K3/45 3.6 kV., 7/8; K3/50 4 kV., 7/9; K3.100 8 kV., 13/8. MAINS TYPES.—RM1, 125 v. 60 mA., 4/8; RM2 125 v. 100 mA., 5/8; RM3 125 v. 120 mA., 7/8; RM4 250 v. 250 mA., 16/-; RM4B type 270 mA., 17/6; RM5, 250 v. 500 mA., £1.-

SPEAKER FRET.—Expanded Bronze anodised

metal 8 x 8 in., 2/3; 12 x 8 in., 3/-; 12 x 12 in., 4/6; 12 x 15 in., 6/-; 24 x 12 in., 9/-, etc.

TYGAN FRET (Munby pattern) 12 x 12 in., 2/-;

12 x 18 in., 3/-; 12 x 24 in., 4/-, etc.

EMITAPE Recording Tape ALL NEW & BOXED!

1/2 in. Type 98 (Stand). Type 99 (Long Play), 500ft., 9/-
 3/4 in. ... 750ft., 7/-
 5/8 in. ... 600ft., 10/-
 5/8 in. ... 850ft., 24/6
 7 in. ... 1,200ft., 30/-
 Spare Reels (Unboxed) 7 in. metal, 1/6; 7 in. plastic £EM1, 8/6.

RECORDING TAPE.—1,200 ft. on 7 in. Plastic reel

85 Type. Hi Quality Product. Each boxed, 22/6.

NEW REDUCED PRICES!

80 OHM CO-AX CABLE

Semi-arsenical, low-loss, high quality 80 ohm co-axial. Stranded conductor, standard 2 in. dia. Famous make. ONLY 8d. per yard. See what you save by ordering:
 20 yds. ... 12/6 40 yds. ... 20/-
 Carr. 1/6 Carr. 2/-

TRANSFORMER & COIL WINDING CAPACITY AVAILABLE FOR PROTOTYPES & SMALL RUNS

Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 1lb 7d., 1lb. 1/11, 3lb. 1/6, 5lb. 2/-, 10lb. 2/9. Hours: 9 a.m.-6 p.m. 1 p.m. Wed. Open all day Saturday.



RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Special Cuts: 130A. 133. 159. 166 and 190

"373" MINIATURE I.F. STRIP 9.72 Mc/s



The ideal F.M. conversion unit as described in "P.W." April/May, 1957. Complete with 6 valves, three EF91's, two EF92's and one EB91, I.F.T.'s, etc., in absolutely new condition. With circuit and conversion data.

12/6 (less valves) **NOW 37/6** (with valves)
Postage and packing 2/6 (either type)

VIBRATOR PACKS. Input 6v. D.C. Output approx. 100v. D.C. at 30 m/amps., fully smoothed and R.F. filtered. Size 6 1/2 x 5 x 2 in. Fitted with Mallory 629C vibrator. **12/6**
BRAND NEW. Boxed.

RF UNITS TYPE 25 Switched **10/-**
Tuning 30 to 40 Mc/s. Includes three SP61's. Carriage 2/6.
TYPE 26. Variable tuning, 50 to 65 Mc/s. Including two EF54's and one EC52. Carriage 2/6. **25/-**
(Circuits in stock for both types, 9d. ea.)

STROBE UNIT
Complete with : 6—EF50 ; 5—EA50 ; SP61. Relays, etc. **35/-** P. & P. 2/6.

MIXER UNIT TYPE 79
Frequency range 172 to 190 Mc/s. Comprising : VCR139A Cath. ray tube ; 7-EF50 ; EF55 ; 4-EA50 ; 2-EB91 ; 5U4 ; VU120 and EC52. Standard main input 200-250 volts 50 c/s. Ideal Scope Basis. **£5.10.0.** Carriage 5/-.

CRYSTAL CALIBRATOR For No. 19 Set
10 kc/s. ; 100 kc/s. ; 1 Mc/s. ; spot frequencies : Crystal controlled oscillators ; includes 5-12SC7 valves, neon modulator handbook, etc. **£4.19.6.** Post free.
BRAND NEW and BOXED.

PACKARD BELL PRE-AMP.
Complete with screened case with 6SL7GT ; 28D7 ; relay ; leads, jack plugs ; handbook, etc. Sealed in carton.
ONLY 12/6 P.P. 2/-.

RADAR TX UNIT TYPE 1683
Complete with the following valves : 2-6C4 ; 832A ; 829B ; 2-5R4G ; 3-6AC7 ; 6V6GT ; 931A photo multiplier with associated network. Also 2-blower motors. Input 80-115 volt 400 to 2,600 c/s. 26v. D.C. **£6.10.0.** P.P. 5/-.
BRAND NEW.

PYE 45 Mc's STRIP TYPE 3583
Complete with 12 valves. 10-EF50 ; EB35 ; EA50 ; with modification data.
ABSOLUTE BARGAIN **ONLY 39/6** Carriage 5/6.

SYNCHRONIZER UNIT
Includes : 3-6L6M ; 12-6AC7 ; 1-65Q7 ; 5-717A ; 6-65N7GT ; 1-65Q7 ; 1-6H6 ; slow motion drive ; transformers ; chokes, etc.
£4.19.6. P. P. 5/-.
BRAND NEW.

CRYSTAL MIC. INSERTS

1/4-inch Square.....	3/6
Acos 1/4-inch Round.....	5/-
Acos 1 1/2-inch Round.....	7/6
Acos 2-inch Round.....	12/6
Lightweight moulded hand microphone case, suitable for any of the above inserts.	P. & P. 9d. per item.

ONLY 2/6

SEND FOR NEW FREE LISTS OF VALVES ; QUARTZ CRYSTALS ; TRANSISTOR COMPONENTS AND CIRCUITS.

See "PRACTICAL WIRELESS" for more Bargains.
* OPEN MONDAY TO SAT. 9-6—THURS. 1 o'clock.

HENRY'S RADIO LTD.
(DEPT. PTM)
5, HARROW ROAD, EDGWARE ROAD, LONDON, W.2
TEL. : PAD 1008-9

T.V. TUBE TROUBLE ?

DON'T HAVE IT REPLACED . . . HAVE IT REBUILT !

For a fraction of the cost of a new tube your old Cathode Ray Tube can be rebuilt completely to manufacturer's specification and returned to you in 72 hours.

GUARANTEED for 7 months from the invoice date

We can also supply 12", 14", 17" and 21" rebuilt tubes from stock, fitted with completely new Gun Units. For full details and price lists (Trade Terms available) contact :

VIDIO REPLACEMENT CO.

Hales Street, Deptford High Street, London, S.E.8.
Telephone : TID 4506.



SUPER-VISION LIMITED

Every Item Brand New and Guaranteed at Low Prices
ENAMELLED COPPER WIRE
12 to 45 S.W.G. from 11/6 lb. Also available in smaller quantities.

VALVE HOLDERS
Int. Octal. 4d. each. B7G, 4d. each. B9A, 6d. each. CER. B9A with screen, 1/9 each.

CONDENSERS
2 to 100 pF., 5d. each. 220-5,000 pF., 7d. each. .01 to .1, 8d. each.

RESISTANCES
Variable T/V type pots. 3K, 5K, 25K and 1M, 2/6 each.

EGEN SLIDER TYPE
3K, 5K and 25K, 1/9 each.

VOLUME CONTROLS
.5M, 2/9 each. .5M with DPS switch, 4/3 each.


ELECTROLYTICS
60/100 mfd., 5/6 each. 32+32+16 mfd., 350 v., 3/6 each.
Clips, 3d. each. 50 mfd., 12 v., 8d. each.

AUTO TRANSFORMERS
50 w. to 1,000 w., from £1.10.0 to £9.0.0.

PLEASE INCLUDE SUFFICIENT TO COVER POSTAGE
13 CHANNEL TURRET TUNED projection T/V chassis, also suitable for driving 17in., 21in. or 24in. tube. 3 gns. Packing and carriage, 10/-.
OPTICAL UNIT for above, complete with tube, deflector coils, focus assembly and connecting cable and plug. Suitable for picture sizes of 24in. to 48in. 33 gns. Packing and carriage, 10/-.

25KV. E.H.T. CANS containing 3 EY51's and components. Manufacturers' rejects. 15/- Post and packing, 2/-.

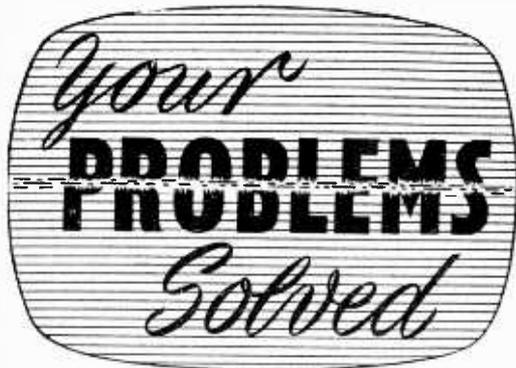SUPER-VISION LIMITED
136 High Street, Teddington, Middlesex. KINGSTON 4393



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** The coupon from p. 425 must be attached to all Queries, and if a post reply is required a stamped and addressed envelope must be enclosed.

PYE CONTINENTAL

My trouble is that when the set is switched on the picture height is insufficient, and leaves at least an inch at the top and bottom of the screen. As the set warms up the picture height increases, but stops about a quarter of an inch from the edge of the screen. The picture height controls only distort the picture if used to remedy the fault.

The dealer who supplied the set suggested that stepping up the voltage would probably cure the trouble. I tried this as an experiment, but although there was some improvement it did not completely rectify the fault. In any case I am not prepared to over-run the valves in this way.

My limited experience of television suggests that the trouble is due to loss of emission of the frame timebase. I would have tried changing this valve but have no circuit data to show which valve it is.—A. Steventon (Pinner).

The frame timebase valve is the PCL82 near the back of the chassis adjacent to the voltage selector panel. We agree that this is the most likely cause of your trouble, but if replacement is ineffective, check the H.T. rectifier.

COSSOR 938

The picture is shimmering. If viewed on test card C all the uprights are ragged, but the horizontals are O.K. The set only resolves 2.0 Mc/s, the corner wedges are ragged or stepped. If you displace the picture about 1½ in. to the left with the line hold the set clears itself, but as soon as you lock it, it becomes ragged.

I have changed V10, V11, V14, V16, V12. This set uses the sync circuit 4 pF with 150 KΩ and I have changed both. I have a service sheet and I would be grateful for any modification or help in clearing the fault.—S. W. Topping (Tredegar).

Your set is displaying the symptoms associated with low gain. We suggest you check the 7AN7 (PCC84) R.F. amplifier in the turret tuner as this is the usual cause of the symptoms.

FERGUSON 992T

I have had repeated trouble with the line timebase. The PL81 overheats and emission drops. This has happened three times in four months. I have checked voltages in the line timebase and everything seems to be in order. PY81 and EY51 have been checked and are O.K.

This set is a Sch.D. using an ECL80 as line generator, but I have no circuit for this section.—W. Wilson (Co. Durham).

We note that you have not changed the ECL80. This you should do since the PL81 depends upon the drive from this valve for its bias, and scanning efficiency. If the valve is not at fault, check associated resistors and the preset drive capacitor which could have an intermittent leak to chassis.

FERRANTI 14T3

From a perfect picture to a blank screen overnight. Shorting EY51 to chassis shows spark ¼ in. long. All valves EF80s, ECL80, EB91 exchanged. No result. I earthed cathode of tube with a wire and got a raster and dim picture quite clear and in shape, but it faded away slowly to blank. Switching off shows ¼ in. square, centre of screen, which fades away to fine pin point in five seconds. Only valves not checked by replacement are EY51 and PY81, but appear to be O.K. No resistors or condensers appear burnt or boiled. Can you please give me a clue to fault.—C. Sharp (Hull).

Check position of ion trap magnet on tube neck which may have been displaced. Then check tube base voltages if possible. Pin 11—cathode—100-150 v. Pin 2—grid—0-150 v., depending upon brilliance control. Pin 10—first anode—low reading on average meter owing to 4.7 MΩ resistor wired in series (this and the 1 μF to chassis should be checked). Check heater voltage across pins 1 and 12—6.3 v. approximately. If voltage at pin 11 is high, check 8.2 KΩ load resistor at video amplifier—trace lead from pin 11.

FERGUSON 988T

Sound O.K. but vision nil. Just thin line across screen.

There appears to be a leakage of oily appearance on the chassis in the centre. There appears to be overheating in the set as the wax has run on most condensers.

Set was working O.K. Can you give details of necessary replacements?—C. R. Hill (E.17).

The waxy appearance of the resistors, etc., may be ignored. Check the ECL80 valves on the left centre of the chassis and the components associated with their bases. Check height control and .1 μF coupling capacitor in particular and H.T. to pins 1 and 6 on ECL80 valve bases.

PHILIPS 2337A-15

When I increase brightness, the picture enlarges and fades out. I have also tried to get ITV with a converter but it does not seem to make any difference. The sound from the BBC comes on as clear as ever with a poor picture BBC.—D. McNeil (Motherwell).

The symptoms denote a failing EY51 in the voltage tripler unit (EHT sealed can), or a defective

valve in the EHT section (check ECL80, PL38 and PZ30, etc.), or a faulty resistor under the unit or a faulty EHT blocking oscillator transformer. Check in order given.

Conversion should be by means of a turret tuner such as the Brayhead 10s or Cyldon P10L. If an add-on converter is tuned, use coaxial socket and make connections as direct as possible.

H.M.V. 1826

The picture only goes down to just below half way on the screen, the lower part remaining blank and unlit. There are two rows of everything on the picture and these are in triplicate and elongated horizontally.

For instance, the circle on the test card is oval and there are about three of them in one row about a quarter of the way down and then underneath this there is a similar row.

I have also noticed that there is a small blank space in the top right-hand corner of the screen, and the picture is rather weak.

When I move the horizontal hold control to another position I can get the test card to appear almost its proper size and single, but it is distorted, wavy, and I can't straighten it out. The lower part of the screen remains blank at all times.

I have changed the valve V15 which is an ECL80, but there was absolutely no difference and I have tried a new RM4 rectifier also without result.—D. Fitzgerald (Chepstow).

You should check the 100 μ F electrolytic connected pin 3 of LN152 (ECL80) to chassis and the .1 μ F capacitor connecting to pin 9. Also check 2.2 M Ω resistor to pin 9 and components in the linearity network. We will advise you further if necessary.

ULTRA TV MODEL V817

Originally the picture closed up to about 6in. On replacing the 6K25 frame generator valve I cured this fault for about a week, then it occurred again. I again replaced this valve and it was all right for about another week when the fault developed again. This time the replacement of this valve did not cure the fault. I had all the valves associated with the frame circuit tested and found to be O.K. I replaced the 3.3 M resistor which was suspect, but still the fault persisted. On switching on the following night there was a flash from under the chassis near valves 13A and B. I traced this fault to R51 and R53 which had gone open circuit. I replaced this with two 5 watt, 50 ohm resistors in series as I could not get a direct replacement of the component. I replaced the fuses and switched on again, this time only half the valves were lit up. I again traced the fault to an open circuit heater on V7 10F1. I replaced this valve only to find that the same thing happened again, the heater went o.c.—C. Chadwick (Leeds).

It would appear that V9 or V8 has developed a heater-cathode short, resulting in a heavy flow of current. We could be mistaken in the valves suggested as it is possible for the fault to be caused by a number of heater circuit faults, check V6. Regarding the lack of height, check the

47 K Ω in series with height control, also .5 μ F in series with 3.3 M Ω .

MURPHY VU150

I wish to convert this set, preferably by turret tuning. However, I find some difficulty in finding data of I.F.s used on this model.

Should the Murphy VU150 use I.F.s requiring the oscillator to be on the other side of signal frequency. Do you consider it would be economical to attempt to readjust this tuner?—E. J. Russell (Sandiacre).

The Murphy V150 I.F.s are 15.5 Mc/s sound, 19.0 Mc/s vision local oscillator beating low. Thus the Cyldon tuner you would require is type U/16/L, which is a plug-in type and has the local oscillator on the correct side.

EKCO 14in. T205

Since fitting another tube (re-vacuumed) the following faults have appeared.

After switching on, and adjusting the contrast or brightness, for a fairly bright picture, I get a black band on either side of any highlights in the picture called black after white I think.

Also the definition of the picture appears to be very soft and gives the appearance as if the vision interference limiter is screwed in for maximum limiting.

If I turn contrast or brightness down, the symptoms I have described disappear and the picture seems quite normal except, of course, for the low level of brightness.—J. Lepley (Ebbw Vale).

We suggest that you fit a 2 watt carbon resistor for your video amplifier anode load. We do not think that this is your fault, however, as your symptoms describe a faulty C.R. tube, and if there is a guarantee on your new tube we suggest you have it tested.

EKCOVISION T221

I get a very good picture with this set, but am troubled by five thin white horizontal lines, unevenly spaced, across the picture's full width. Please could you advise me?—R. F. Brain (Swindon).

Your fault may well be due to parasitic oscillations in the frame output valve which is a type 20P5 and is situated in the centre of the chassis beneath the scan coils.

PHILIPS 1800 A/15

This set suddenly burst into a loud harsh roar, which at first blotted out sound and picture, picture being blacked out by a patch of black wicker-work of interference across the middle.

I tried the various controls and gradually picture interference disappeared leaving a pale raster of light which could be adjusted to a full width lin. deep white line. Once or twice I obtained a black cross full size which was torn and stretched beyond recognition, adjusting controls made it worse.

Frame is only a few inches deep in centre of screen, but full width there appears to be hardly any control over width which seems to be filtering all the time. I have tried a new UCH42 and

(Continued on page 425)

**TAKE THE PROBLEMS
OUT OF SOLDERING**



**HENLEY
SOLO**
TRADE MARK

**FOR 25 YEARS THE BEST
ELECTRIC SOLDERING IRON**

Leaflets on request from:
**W. T. HENLEY'S
TELEGRAPH
WORKS CO. LTD.**
Engineering
Sales Department,
59-62 High Holborn,
London, W.C.1
Telephone: CHAncery 4364

*25 watt instrument
model (Illustrated)*

TELEVISION TUBES

RE-ACTIVATED & RE-GETTERED, 50/-. PROVIDED YOUR OLD TUBE HAS NO ELECTRODE FAULTS AND HAS NOT BEEN SEVERELY ROOSTED THERE IS A 70% CHANCE OF RE-ACTIVATION LASTING UP TO 12 MONTHS. NO RESULT, NO CHARGE. SPECIAL PRICE TO TRADE.

T.V. TUBES IN STOCK. ALL MAKES, MOST SIZES. 9" £3. 10" £3.10.0. OTHERS £5 EACH plus POSTAGE AND INSURANCE 12/6. GUARANTEED 3 MONTHS.

GERMANIUM CRYSTAL DIODES. 1/-, 10/- per doz.

TORCH BULBS. Ever Ready 2.5 v. and 3.5 v.. 16/- per 100, 9/- per 50.

HEADPHONES. Moving iron, low impedance. 6/-, high, 9/-. Balanced armature, low, 10/-, high, 15/-. Moving coil, low only, 10/- per pair.

GLASS FUSES. 1", 2 and 10 amp. only. 5 for 1/-.

MAINS POWER PACKS. 250 v. 80 m.amp. or stabilised 150 v. 80 m.amp. with 6.3 v. winding, 30/-.

RELAYS. High speed, 1,000+1,000 ohms, plat. cont., 7/6.

VALVES. All valves tested before despatch on MULLARDS latest ELECTRONIC TESTER.

1L4	5/-	6C4	6/-	6V8	6/6	50C5	10/-	EF92	8/-
1T4	6/6	6D2	6/-	6X4	7/-	807	6/-	EL32	5/-
1U4	6/-	6F6	7/-	6X5	7/-	EAS5	1/6	EL91	5/6
3A4	6/-	6P13	7/6	8D2	4/6	EABC80		EY51	6/-
5Z4	9/6	6J5	6/-	9D2	5/-	EB41	7/6	EY51	9/-
4D1	4/-	6J8	6/-	10F1	7/6	EB91	5/6	F61	4/-
6AG5	5/-	6J7	6/-	12A6	7/6	ECH42	9/-	Pen46	7/-
6AL5	5/6	6K7	4/6	12AH8	8/-	ECL30	10/-	SP61	4/-
6AM5	5/-	6L6	6/6	12AT7	7/6	ECL30	10/-	VR150/30	
6AM6	7/6	6SA7	7/-	12AU7	7/-	EF36	6/6	UL94	9/-
6AG6	7/6	6S7	4/6	12AX7	8/6	EF50	3/6	VR138	25/-
6AU6	8/-	6S7J	6/-	12BH7	10/-	EF50	5/-	VR139A	
6BA6	8/-	6SK7	5/-	12SH7	6/-	EF37A	9/-		
6BE6	7/-	6SL7	7/-	12SK7	7/6	EF39	5/6		
6BH6	5/-	6SN7	7/6	12SX7	8/6	EF90	8/6	VCR97	25/-
6BW6	6/6	6U5	7/6	15D2	6/-	EF91	7/-		15/-

HUGGETT'S LIMITED
24 PAWSONS ROAD, WEST CROYDON

COMPLETELY BUILT 8 WATT PUSH PULL AMPLIFIER




Complete with Crystal Mike and 8" Loudspeaker A.C. Mains 110/250 v. Size 10 1/2 in. x 8 1/2 in. x 2 1/2 in. Incorporating 6 valves. H.F. pen., 2 triodes, 2 output pens., and rectifier. For use with all makes and types of pick-up and mike. Negative feedback. Two inputs, mike and gram, and controls for same. Separate controls for Bass and Treble lift. For use with Std. or L.P. records, musical instruments such as Guitars, etc.

Or 35/- deposit plus P. & P. 7/6 & 3 monthly payments of 25/-.

£4.19.6
Plus P. & P. 7/6

SIGNAL GENERATOR

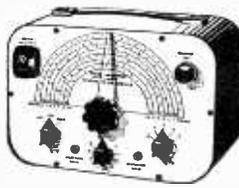

£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10 1/2 in. x 6 1/2 in. x 5 1/2 in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier A.C. Mains 200/250. Internal Modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F., output continuously variable, 100 milli-volts. C.W. and mod. switch, variable magic-eye as output indicator. Accuracy plus or minus 2%.


FAMOUS MAKE "TELETUNER"



Covers all Channels, Bands I and III. Valves used: PC84, R.F. double triode, cascade R.F. amplifier, PCF80, triode pentode f.c. and mixer, 1.F. output 33-38 Mc/s.


Post 2/6 **59/6** Knobs 3/6 per set extra.

SIGNAL & PATTERN GENERATOR

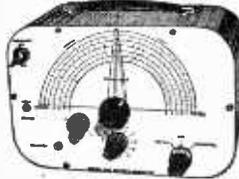

25/- deposit plus P. & P. 5/- and 6 monthly payments of 21/6. Cash £6.19.6 plus P. & P. 5/-. Coverage 7.6 Mc/s-210 Mc/s in five bands, all on fundamentals, slow-motion tuning, audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ± 1%. A.C. mains 200-250 v.

AC/DC POCKET MULTI-METER KIT

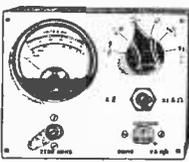

Comprising 2 1/2 in. moving coil meter scale calibrated in AC/DC volts, ohms and milli-amps. Voltage range AC DC 0-50, 0-100, 0-250, 0-500, milli-amps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), toggle switch, resistors and rectifier. Basic movement 2 mA. In grey hammer finished case.

19/6 Plus P. & P. 1/6. Built and tested 7/6 extra.

Point to point wiring diagram 1/-, free with kit.

13 CHANNEL TUNER

34-36 Mc/s. Complete with PCF80 & PCC84. These have been removed from chassis.

19/6 Plus P. & P. 2.6. Knobs 3/6 per set extra.

RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

RADIO SUPPLY CO. (LEEDS) LTD., Dept. N, 5/7 COUNTY ARCADE, BRIGGATE, LEEDS, 1

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/9 extra under £2. 2/3 under £5. Open to callers 9 a.m. to 6 p.m. Wednesdays until 1 p.m. S.A.E. with enquiries, please. Full list 6d. Trade supplied.

R.S.C. TRANSFORMERS

Fully Guaranteed Interleaved and Impregnated. Primaries 200-230-250 v 50 c/s screened TOP SHROUDED DROP THROUGH
 231-0-250 v 70 ma. 6.3 v 2 a. 5 v 2 a... 16/9
 331-0-331 v 80 ma. 6.3 v 2 a. 5 v 2 a... 18/9
 251-0-250 v 100 ma. 6.3 v 4 a. 5 v 3 a... 23/9
 351-0-351 v 100 ma. 6.3 v 4 a. 5 v 3 a... 23/9
 351-0-351 v 150 ma. 6.3 v 4 a. 5 v 3 a... 23/9
FULLY SHROUDED UPRIGHT
 251-0-250 v 60 ma. 6.3 v 2 a. 5 v 2 a
 Midget type 24-3-in. ... 17/9
 251-0-250 v 100 ma. 6.3 v 4 a. 5 v 3 a... 23/9
 311-0-310 v 100 ma. 6.3 v 4 a. 5 v 3 a... 23/9
 351-0-350 v 100 ma. 6.3 v 4 a. 5 v 3 a... 23/9
 351-0-350 v 150 ma. 6.3 v 4 a. 5 v 3 a... 33/9
 131-0-121 v 231 ma. 6.3 v 4 a. C.T. 6.3 v 4 a. C.T. 5 v 3 a... 49/9

FILAMENT TRANSFORMERS
 All with 200-250 v 50 c/s Primaries : 6.3 v 1.5 a. 5/9 : 6.3 v 2 a. 7/6 : 0-1.6-3 v 2 a. 7/9 : 12 v 1 a. 7/11 : 6.3 v 3 a. 8/11 : 6.3 v 6 a. 17/9.
CHARGER TRANSFORMERS
 211-211 v 0-9-15 v 11 a. 11/9 : 0-9-15 v 3 a. 16/9 : 1-15 v 5 a. 19/3 : 0-9-15 v 6 a. 22/9.

OUTPUT TRANSFORMERS
 Standard Pentode 5,000 to 3 ohms ... 4/9
 Small Pentode 5,000 to 3 ohms ... 3/9
SMOOTHING CHOKES
 103 ma 10 h 250 ohms ... 8/9
 33 ma 10 h 350 ohms ... 5/9
 33 ma 10 h 400 ohms ... 4/11

NILHELIUM METAL RECTIFIERS
 25 v 250 ma. 11/9 : 250 v 80 ma. 7/9 : 25 v 50 ma. 4/11 : 120 v 40 ma. 3/9 : 21 v 2 a. 14/9 : 6/12 v 1 a F.W. 3/11 : 6/12 v 2 a F.W. 7/3 : 6/12 v 3 a. 9/9 : 6/12 v 4 a. 13/11 : 6/12 v 5 a. 14/6 : 6/12 v 6 a F.W. 14/11 : 6/12 v 10 a. 25/9 : 6/12 v 15 a. 35/9.

COAXIAL CABLE 1in. ... 8d. yd.
 75 ohms 14/36 ... 8d. yd.
 Twin-screened Feeder ... 11d. yd.

BATTERY SET CONVERTER KIT
 All parts for converting any normal type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplies 120 v. 30 v or 60 v at 40 ma. fully smoothed and fully smoothed L.T. of 2 v at 0.4 a to 1 a. Price including circuit 49/9. Or ready for use, 9/9 extra.

ALL DIY RECIEVER BATTERY ELIMINATOR KIT—All parts for the construction of a unit (metal-case 5 1/4-1 1/2 in.) to supply Battery Portable receivers requiring 90 v and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 39/9. Or ready for use, 46/9.

D.C. SUPPLY KIT—Suitable for Electric Trains. Consists of mains trans. 200-250 v 50 c.p.s. A.C. 12 v 1 a Selenium F.W. Bridge Rectifier. 2 Fuseholders. 2 Fuses. Change Direction Switch. Variable Speed Regulator. 29/9
 drilled Steel Case, and Circuit.

EX-GOVT. CASES. Well ventilated, black crackle finished, undrilled cover. Size 14 x 10 x 8 1/2 in. high. **IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE. OR COVER COULD BE USED FOR AMPLIFIER.** Only 9/9, plus 2/9 postage.

TELEVISION RECTIFIERS
 250 v 200 ma. Size 3 x 1 1/2 in. Brand New, 6/9.

EX-GOVT. VALVES (NEW)					
1R5	7/9	6J6	4/9	MH4	4/9
174	7/9	6K7G	3/9	6AT6	7/9
185	7/9	6C7G	9/11	DF96	8/9
354	8/9	6X4	6/9	EBC33	6/9
5Y3G	7/9	6X5GT	7/9	EB91	8/9
524G	9/9	6SN7GT	8/9	ECC91	4/6
5U4G	8/9	6L6G	11/9	EF91	8/9
635G	4/9	807	7/9	EL32	3/9
6BC6	9/9	808	7/9	EL91	5/9
6S7GT	8/9	12A6	7/9	FW4/500	8/9
6V6G	7/9	3524	9/9	SP61	2/9
6U5G	3/9	3524	6/9		

EX-GOVT. MAINS TRANSFORMERS

All 200-250 v 50 c/s input. Removed from New ex-Govt. units. 22/9
 275-0-275 v 100 ma. 6.3 v 7 a. 5 v 3 a
 230-0-230 v 80 ma. 12.6 v 1.5 a. 5 v 2 a... 11/9
 250-0-250 v 150 ma. 5 v 3 a ... 18/9
 350-0-350 v 160 ma. 6.3 v 5 a. 5 v 3 a ... 27/9
 400-0-400 v 250 ma. 5 v 2 a. 5 v 2 a ... 18/9
 450-0-450 v 250 ma. 6.3 v 3 a. 6.3 v 1 a. 5 v 6 a ... 49/9
 12.5 v 3 a. 5 v 3 a ... 12/9

EX-GOVT. SMOOTHING CHOKES

60 ma 5-10 h 250 ohms ... 2/11
 80 ma 10 h 150 ohms ... 6/9
 100 ma 5 h 100 ohms Trop. called ... 3/11
 100 ma 10 h 100 ohms Parmeko ... 6/9
 120 ma 12 h 100 ohms ... 9/9
 150 ma 6-10 h 150 ohms Trop. ... 6/9
 150 ma 10 h 150 ohms ... 11/9
 200 ma 8-5 h 100 ohms Parmeko ... 9/9
 250 ma 20 h 200 ohms ... 19/9

ELECTROLYTICS (NEW)

Tubular	Can Type		
8 mfd 450 v	1/9	8-8 mfd 450 v	2/11
16 mfd 450 v	2/9	8-16 mfd 450 v	3/11
8-16 mfd 500 v	4/11	16-16 mfd 450 v	4/11
25 mfd 25 v	1/3	32-32 mfd 350 v	4/9
50 mfd 12 v	1/3	32-32 mfd 450 v	5/9
90 mfd 50 v	1/9	150 mfd 450 v	5/9
100 mfd 25 v	2/3	100-100 mfd 350v	5/9
3,000 mfd 6 v	3/9	100-200 mfd 275 v	6/11
6,000 mfd 6 v	3/11		

BATTERY CHARGERS

For 200/250 v 50 c/s A.C. mains. 12 months guarantee. Attractive, well ventilated, hammer finished cases. 6 v or 12 v 4 amp, with meter and variable charge rate selector, as illustrated. 75/-
 carr. 4/6.
 6 v or 12 v 1 amp type. Also suitable for electric train power supply. Only 27/9, post 2/9.



LINE OUTPUT TRANSFORMERS

Most types available. State Make and Model Number of Receiver when ordering.

S.A.E. please with all enquiries.

HOWORTH

51 POLLARD LANE, BRADFORD, 2, YORKS

Tel. 37030

NEW-MAX ELECTRONICS

220 Edgware Road, London, W.2. PAD 5607

For London's Finest Bargains in electronics, television and radio equipment.

LARGE SELECTION OF TAPE RECORDERS ALL GUARANTEED. FOR EXAMPLE FRUSTRATED EXPORT ORDER. 3-speed tape recorders, brand new in maker's cartons, fitted with latest Mark IV Collare tape deck. 4 watt output, plays all pre-recorded tapes. Instantaneous track change over. With microphone and tape. Current list price 55 gns. Our Price 41 gns. Leaflet available on request. Also smaller version of the above machine, current list price 44 gns. Our Price 35 gns. complete with tape and mike. Fully guaranteed.

T.V. TUBES

BRAND NEW FULLY GUARANTEED
 14in. M.W. 36-24 tubes, £16.10.0
 17in. M.W. 43-64 tubes, £17.10.0
 21in. M.W. 53-80 tubes, £20.0.0
 P.P. & Insurance on all tubes. 15/-
 T9-39in. Ferranti Tube. 4 volt filament with the use of a filament transformer. This tube will replace Brimar, Mazda, G.E.C. 9in. tube, price £5.0.0 inclusive. REVACUUMED & GUARANTEED
 10in. and 12in. 26 : 14in. 25 : 15in. and 17in. 27.10.0
 A full range of F.M. and A.M. Tuners. Hi-Fi and stereophonic amplifiers, record players, record changers, A.M. and F.M. Radiogram chassis. All types and makes of test instruments, shavers, typewriters, radios (battery and transistors).

B.B.C.-I.T.V.-F.M. AERIALS

B.B.C. (BRAND 1). Telescopic loft. 19/6. External, S/D. 26/3.
 I.T.V. (BRAND 3). 3 Element loft array. 24/- 5 Element. 32/6. Wall mounting. 3 Element, 33/9. 5 Element. 41/3.
 COMBINED B.B.C. + I.T.V. Loft. 1+3 Element. 41/3. 1+5 Element. 46/9. Wall mounting. 1+3 Element. 56/3. 1+5 Element. 63/9. Chimney and mast mounting units also available.
 F.M. (BRAND 2). Loft "H" 28/- 3 Element loft. 52/6. S/D loft. 12/6. External S/D. 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable. 8d. yd. Coaxial plugs. 1/3. Send 6d. stamps for illustrated lists.
NOW—BY RETURN OF POST Complete stocks of all B.V.A. valves, metal rectifiers, condensers, resistors, etc. V/Cs with or without switch (all valves). O/P transformers, etc. Many more items available. Send 3d. stamps for lists.
K.V.A. ELECTRONICS (Dept. T.P.)
 3B, GODSTONE ROAD, KENLEY, SURREY

RADIO AND TELEVISION COMPONENTS

We operate a prompt and efficient MAIL-ORDER Service. 3d. stamp (only) for Catalogue.

JAMES H. MARTIN & CO.
 FINSTHWAITE, NEWBY BRIDGE, ULVERSTON, LANCs.

RECORDING TAPES

— famous makes. 850ft. 5in. reel. 18/- : usual price 28/- : 850ft. 5in. reel L.P., 23/- : Brand New 1,700ft. tape on 7in. reels 35/- : usual price 50/- : 1,800ft. 7in. reel L.P., 22. 1,200ft. on 7in. reels, 21/- : usual price 35/-.

RES/CAP. BRIDGE 35/-

p. & p. 2/-
 Checks all types of resistors, condensers 6 RANGES
 Built in 1 hour. Direct reading
READY CALIBRATED
 Stamp for details of this and other kits.
RADIO MAIL (Dept. VL)
 Raleigh Mews, Raleigh Street, Nottingham

UL41 in frame timebase and changed UCH42 and UL44 in line, with no difference.

Sound was obtained clear and reasonably loud, but to get this contrast and volume, controls were both at their limits, the roar is constant with or without aerial, but changes pitch on change of scene (I presume).—T. W. Carr (Hull).

The symptoms indicate an open circuited smoothing capacitor. One of those standing (tags uppermost) along the chassis is likely to be at fault. For test purposes only, use a wire ended 450 v. working 32 μ F capacitor and shunt this across each tag in turn (+ or Pos. to tag, —or Neg. to chassis). When a position is found where the roar stops, check that capacitor and replace with one of the correct type.

PYE VT4

Firstly there is no picture, owing to the fact that the EY51 valve does not light up.

I assume, therefore, the fault is in the Line O.P. transformer. I think the heater winding is at fault.

Can you tell me if I can get another similar transformer, what is the make and where can I get one?

Or is it possible to rewind the heater winding or to have it new?—C. P. Charlton (Leicester).

You order an exact replacement line output transformer from your Pye dealer. It will cost about £2 10s. Before doing so check the three line timebase valves ECL80, PL81, PY81, the 47 ohm resistor in the PL81 anode, the top H.T. fuse, and the scan coils. This is done by disconnecting the line feed (green and pink wires) beneath the scan coils. If this restores EHT, the scan coils are faulty.

EKCOVISION TC162N

On switching on sound O.K., tube lights up, 2in. to 3in. band across screen, no amount of adjustment of controls makes difference. All valves been tested and found good.—G. Brookes (Monkwood).

We advise you to check the 500 μ F cathode bias condenser which decouples the 6L18 frame output valve. If this fails to cure your fault check the 4,700 pF feedback condenser between the frame output transformer and frame linearity control.

PYE FV1

Recently I have moved from a district supplied with 230 volts to one supplied with 200 volts which appears to be mostly overloaded. In the previous district the picture was good. In the latter, foggy, dark and under screen size, varying according apparently to the load. This improves at the week-end, but still not up to standard.

Owing to age of set (six years), would some improvement be made if the metal H.T. rectifier was replaced?—F. W. Johnson (Cardiff).

We certainly agree that the metal rectifier should be replaced, especially if it is the original one. The type you require is a 14A86 or its equivalent and we assume that you have already altered the

voltage selector tapings to agree with your new voltage.

MURPHY V160

The line oscillator screen grid feed is from the cathode of the audio output valve, this being used as a constant current generator. The fault in this receiver is that "sync" pulses(?) are fed into the audio output from the line oscillator drowning the signal. The audio circuit behaves normally if its base end is earthed. The line oscillator valve 20P1 has been tested.—A. L. Humphreys (W.11).

The cathode of the sound output valve is heavily decoupled by two 40 μ F electrolytics, one at the cathode itself, and the other at the lower end of the horizontal hold control. We suggest you replace these condensers which are the most likely cause of your fault.

INTERFERENCE

I am having trouble with interference to M.W. and L.W. from my parents' television set. As my vertical rod aerial is only about 10 yards from the television aerial, a whistle is picked up. This is audible on Home and Light Programme wavelengths, but as I have an F.M. tuner I am not worried about them. The real trouble starts if I am listening during the afternoon to Berlin or Hilversum and other distant M.W. stations, which do not come in with very great strength. Is it possible to incorporate in the television aerial lead some form of filter which will remove this radiation?—J. Webster (Stroud).

We advise you initially to check that it is in fact the TV aerial which is radiating the signal. This is simply done by running the set with the aerial unplugged. If the interference persists radiation is either direct or via the mains supply. The latter can be reduced by fitting a filter at the TV end, but the first two conditions can only be improved by removal of both sets and aerials as far away from each other as practicable.

MURPHY V120C

My trouble is loss of power. If the set is connected to the 220-240 v. tags, the highest reading I can get is 80 v. If I connect to the 200-210 tag, I get a reading of 110 v. I have lost EHT. Before this happened, the fuse kept blowing and I suspected the UU8. I have had this valve tested, and it seems to be O.K.

The fuse went as soon as I switched on, but at times it lasted quite a few minutes. When this happened, I could see the UU8 very slowly going blue.

We would say that you have a faulty 200 μ F smoothing condenser, faulty UU8, or both. We would not recommend setting your mains voltage tapping to a lower figure in an attempt to increase your A.C. voltage.

QUERIES COUPON

This coupon is available until MARCH 21st, 1959, and must accompany all Queries sent in accord with the notice on page 421.

PRACTICAL TELEVISION, MARCH, 1959.

EDUCATIONAL

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation I.C.S. Courses for the enthusiast and for those seeking examination qualification. Brit.I.R.E., City and Guilds, R.T.E.B., etc. Build your own equipment with Practical Radio Course. Write to-day for free book. **INTERNATIONAL CORRESPONDENCE SCHOOLS**, 71, Kingsway (Dept. 516), London, W.C.2.

II+ EXAMINATION

In your child's interest write NOW for **FREE 24-page GUIDE** and Test stating age of child to The Registrar (Dept. M.7), **MERCER'S CORRESPONDENCE COLLEGE** 69 Wimpole Street, London, W.1

INCORPORATED Practical Radio Engineers home study courses of radio and T.V. engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text free; "The Practical Radio Engineer" journal, sample copy 2/-, 6,000 Alignment Peaks and Superhets, 5/9. Membership and Entry Conditions booklet 1/-, all post free from the **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

SETS & COMPONENTS

SATISFACTION OR MONEY BACK GUARANTEE on all goods if returned unused within 14 days. **4-SPEED RECORD PLAYER**. Consisting of latest B.S.R. Turntable and separate light weight Galaxy dual sapphire pick-up. Repeatable **£3.15.0**.

TV SETS

5-CHANNEL T.V.s. Table models, tested pictures before dispatch, good tubes, tuneable all B.B.C. stations, all top makes, **£8**. Carr., etc., 10/-. **13-CHANNEL T.V.s.** Consisting of a 5-channel B.B.C. T.V. with separate mains-driven Band III converter (new, listed £7). **£11**. Carr., etc., 10/-. **STARR GALAXY SPARES**, 1,000's available, low prices. S.A.E. list.

TV TUBES

FACTORY REVACUUMED ALL GUARANTEED 6 MONTHS. Carriage and insurance 12/6. Nearly all types of Mullard, Mazda, Brinar, Cossor, Emiscope, Emitron, Ferranti, Cathodion, C.T.C., available ex-stock. All 9in. **£2/15/-**. All 12in., 14in., **£3/19/-** and 16in. **£4/15/-**. 15in., 16in.

Except those listed under: **CRM 123**, MW3116, MW3174, 3/31, 3/32, CRM143, MW41 I, CRM152. All Mullard 14in., **£4/10/-**. All 17in. **£4/15/-**. 21in., **£7/10/-** types.

TRANSISTORS, Red Spot, L.F. 6/8 White Spot, R.F. 12/6. Latest "Top Hat" Ediswan XB104, 12/6. S.A.E. details.

GUARANTEED P.M. SPEAKERS. Standard 3 ohms, ex-equipment, tested, top makes, per-imp. price guaranteed. 5in., 9", 6 1/2in., 9", 7" x 4in., 12" x 9in., 9": 10" x 6in., 14", 10in., 14".

RECTIFIERS, Selenium, 12V. 1A., 5/-; 12V. 2A., 7/6; 12V. 3A., 9/6; 250V. 80mA., 5/-; 250V. 250 mA., 12/6; contact cooled, 250V. 50mA., 7/6; 250V., 250mA., 19/-; 250V. 300mA., 23/-.

All items test 5% and post free for a decet. Post 1,3 in cl. Mfrs. Ltd. No.C.O.D. 10,600 STNPS FOR CALLERS.

TECHNICAL TRADING CO.
350/352, FRATTON ROAD,
PORTSMOUTH

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

LINE OUTPUT TRANSFORMERS

DIRECT REPLACEMENTS for 500 sets. State make and model No. (3d. stamp).

BRAYHEAD TURRET TUNER for ANY AREA. The best converter! State Channels, set make, model No. **£6.15.0**, post/ins. 2/6.

WESTWAY RADIO

5 Westward Way, Harrow, Middx.

I.F. STRIP 373, new, with valves. 37/6. Vibrators, Mallory, G634C 12v. 4-pin, 7/6. R.F.27, good cond., 18/- (p.p. 3/6). Metal Rectifiers: 240v. 100mA., 4/-; 240v. 30 mA., 3/6; 1,000v. 30 mA., 7/6. Chokes. L.F., 10H. 120 mA., screened, 7/6; 5H. 200 mA., 4/6. R1155B, new condition, tested, with handbook, **£7/10/-** (rail 10/-). Indicators with C.R.T.'s VCR339 and VCR139A. 10 valves, etc., 50/- (rail 8/6). Single 6 1/2in. C.R.T., 10 valves, 30/- (rail 7/6). Converters (Rotary), 24v. D.C. to 50v. A.C. 4 A., 40/- (rail 7/6). Mic Inserts, G.P.O. carbon, 2/6. Drives: slow-motion, Admiralty 200:1 ratio, scaled 0-100, 5/6; R1155 S.M. "N" type, new, 10/6. Meters, contain 2 separate micro-amp. movements and 2 neons, new, 8/6; Cross-over needle, 1 mA. x 2, 8/6. Resistors, vitreous, 4 1/2 watt., most values from 1 k. to 100 k., each 9d. Amplifiers (Turbo) with 2/7C5, 1/7F7 and 7Y4. 25/-, Meters, 2in. round flush, Mc/s 100, 200, 300, 500 mA., each 8/6; 1 mA., 17/6; 8 A., T.C., 6/-; 3 1/2in., 1 mA. (40 ohm), scaled 0/5, 0/10, 0/15, 0/30, 55/-. Valveholders, U.S.A., Octal, doz., 4/-. Potentiometers, 100 k. or 500 k., new, doz., 5/-, Aerial Mast Stays, 40ft. multi-strand toughened copper, cleared, 4/-. List and enquiries; s.a.e. please! Terms, c.w.o. Postage extra. Immediate despatch. W. A. BENSON (P.T.), 136, Rathbone Road, Liverpool, 15. (SEP 6853.)

C. EDWARDS

1070 HARROW ROAD
LONDON, N.W.10
LADBROKE 1734

Offers
S/H T.V. in
First-class
Condition
12in. **£10.10.0**.
14in. **£14.0.0**.
17in. **£20.0.0**.
(all 5 channel)
+ 10/- carriage
Guaranteed
tubes, all sizes,
12" 14" 17", 45 ea.



in stock : **PYE, FERGUSON, EKO**
CASH ONLY. 10/- Carriage.
Trade Enquiries Welcome.

SETS & COMPONENTS continued

REBUILT T.V. TUBES

MULLARD	MAZDA
12", £6.0.0	CRM141, £6.10.0
14", £6.10.0	CRM142, £6.10.0
17", £8.0.0	CRM153, £7.0.0
21", £10.10.0	CRM171, £8.0.0

Carriage and insurance 10/- Customers' own Tubes rebuilt.

MIDLAND TUBES LIMITED
37, George St., Manchester, 1. Central 0432

COMPONENTS, Valves, Tubes, etc. Write or phone for free list. **ARION TELEVISION**, 4, Maxted Rd., Peckham, S.E.15. (New Cross 7152.)

T.V. TUBES

14in. types, **£4.0.0**.
17in. types, **£5.0.0**.
12in. MW 31/74, **£4.10.0**.

All carriage paid. Picture tested and guaranteed 3 months.

14in. and 17in. for testing or boosting at 25/- each, Carriage Paid.

S. BRADLEY

6, Beadon Avenue, Waterloo, Huddersfield.

TELEVISIONS, 9in. models, **£7/10/-**; 12in. models, **£13/10/-**; 12in. 5-Channel models, **£19/10/-** each; all working; carriage paid. Send for list. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.28. (FOR 5497.)

TELEVISION

CATHODE RAY TUBES

Reconditioned and Guaranteed 6 months.
14" round Mazdas—**£5.0.0**.
15" round Mazdas—**£6.0.0**.
17" rect. Mazdas—**£6.0.0**.
Carriage and Insurance, 10/-.

Cash with orders to **L.E.T. SERVICES**, Dept. P/T, 1, 41, Station Street West, Coventry. Telephone: 89564.

Save 30% on all outdoor aerials and fittings. Example: Double Five Array costs only 70/- Self-contained Band III Pre-amplifiers only 60/- Converters 100/- complete. Turret Tuners 94/- complete. Fringe Area Super Low-loss Co-axial, 1 1/4 yard. Reconditioned T.V. Tubes, 6 months' guarantee, 12" 120/-, 14" 110/-, 17" 150/-, 21" 210/-. C.W.O., carriage 10/- extra. Tubes delivered in 24 hours all parts U.K. S.A.E. FOR FULL LISTS.

G. A. STRANGE

North Wrexhall, Nr. Chippenham, Wilts. Tel.: Marshfield 236.

TUBES FOR SALE

Seconds, 12 in.	£5
14 in.	£6
17 in.	£7

	From
L.O.P.T. For any set	17/6
F.O.P.T. " " " " " " " " " "	7/6
S.O.P.T. " " " " " " " " " "	5/-
Focus Magns. " " " " " " " " " "	7/6
Scan. Coils " " " " " " " " " "	15/-

Any make! Any part! For any television. Also any valve in stock. All seconds. All perfect, from 5/-. Cash refunded if not satisfied.

C.W.O. or C.O.D. Despatched immediately. Write or telephone:

SPARES DEPT. 2400,
33, Merton High Street, Merton, S.W.19
LIB 4559.

SETS & COMPONENTS (continued)

MAKE YOUR OWN AERIALS with our fully machined parts. Example: full kit of ready to assemble parts for 5-element array, plus 3ft. mast and universal clip, 35/-, post paid. Get our full lists and Aerial Data Chart for 1/- postal order. SKYLINE WORKS, Burnshall Rd., Coventry.

TELEVISION BARGAINS. 12in. from £9, 14in. from £18, 17in. from £25. TYLER TELEVISION, 63, Lee High Rd., Lewisham, S.E.13. (Lee 5979.)

SERVICE SHEETS

SERVICE SHEETS for sale and hire. Radio/T.V.; s.a.e. enquiries. J. PALMER, 32, Neasden Lane, N.W.10.

SERVICE SHEETS. Radio. T.V. 5,000 models. Lists 1/-. S.A.E. enquiries. TELRAY, 11, Maudland Bk., Preston.

SERVICE SHEETS.—We have the largest stock of Radio and T.V. Service Sheets in the country for sale at 4/- each. Why tolerate delay in obtaining Service Sheets when we will despatch by return? S.A.E. with enquiries, please. S.P. DISTRIBUTORS, 11, Old Bond St., London, W.1.

SERVICE SHEETS for sale.—T.V., 4/-; Radio, 3/-; immediate delivery; s.a.e. with inquiry. SULTAN RADIO, 23b, Albert St., Tunbridge Wells, Kent.

TELEVISION SERVICE SHEETS, over 100 sheets covering 330 popular models, 18/6, post free. Send for full details. All types of Service Sheets for sale and hire. Radio, Television, Electronics Books, Television Servicing, 5/-; Radio Servicing, 4/-. List free. HAMILTON RADIO, BCM7/DATA3, London, W.C.1.

WANTED

ALL TYPES OF VALVES WANTED. PL81 ECL80, EY51, U25, PCF80, PZ30, U801, etc. etc. Best cash price by return. STAN WILLETTS, 43, Spon Lane West Bromwich, Staffs. (Tel.: WES 2392.)

NEW VALVES WANTED. EY51, PL81, ECL80 and similar types. R.H.S. 155, Swan Arcade, Bradford, 1, Yorks

QUANTITY RM4 and New Valves wanted. Offers with price to: Box 16, c/o PRACTICAL TELEVISION.

IMPORTANT! New Valves and Metal Rectifiers wanted, state price. Same day payment. ROBERT, 414, Whitefoot Lane, Bromley, Kent.

WANTED. Service Sheets and Manuals, highest prices paid, no quantity too large or small. SULTAN RADIO, 23b, Albert St., Tunbridge Wells, Kent.

WE BUY FOR CASH new and second-hand Televisions, Radios, Radiograms, Fridges, Spin Dryers, Washing Machines, Tape Recorders, Valves and Components. (Phone: LJB 4559.)

FOR SALE

SERVICE SHEETS; also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20, Extension, Shepherds Bush Market, London, W.12. (Phone: SHE 3052.)

FOR SALE (continued)

TELEVISION SETS.—Learn to service on the genuine articles—part exchange Receivers, complete with tube, valves and cabinet, £4 each, postage and packing 15/- extra. Order now whilst stocks last. Send P.O. or c.o.d. to: DEWAR'S RADIO, 102, Grove Lane, Birmingham, 21.

AMAZING OFFER.—Originally £40/£100 each. Ekco, Pye, H.M.V., Marconi, Philips, Murphy, etc., 9/10in. Televisions, complete, not working, 50/- each; carriage paid; immediate dispatch. 12in., £5/5/-; 15in., £9; Philips 17in. Projection Televisions, £9/15/-.. TOMLINS, 127, Brockley Rise, London, S.E.23.

TELEVISION BARGAINS. 12in., O.K., £10; 14in. and 17in. cheap for cash. New sets at bargain price. T.V. SUPPLIES, 1 High St., Chalvey (Tel.: Slough 21860).

FOCUS MAGNET, 9/9. Brand new. 38 mm. Incorporating picture shift control. P. & P. 1/3.

SCANNING COILS, 10/6. Low impedance. 38 mm. Brand new. P. & P. 1/3.

COLVERN PRESET POTENTIOMETER, 2/9. Brand new. 200 ohms. 10 k. and 20 k. P. & P. 6d.

DUKE & CO.

(Dept. E.3), 621/3, Romford Road, Manor Park, E.12. Tel.: ILF 6001/3

TELEVISIONS.—12in. £7/10/-; 5 chan., £10; 13 chan., £16. 14in.: 5 chan., £15; 13 chan., £20. 17in. from £22. Non-workers, etc., cheap. Callers only. TELEGRAM ELECTRONIC, 68, Kings Ave., Clapham, S.W.4 (Phone: TUL 6971.)

VALVE CARTONS at kept prices. Send 1/- for samples and list. J. A. BOXMAKERS, 75a, Godwin St., Bradford, 1.

100 BAYS of brand new adjustable steel Shelving, 72in. high x 34in. wide x 12in. deep, stove enamelled dark green; sent unassembled, 6-shelf bay, £3/15/-; sample delivered free; quantity discounts. N. C. BROWN LTD., Eagle Steetworks, Heywood, Lancs (Tel.: 69018.)

AVO SIG. GEN., Type III, 150 kc/s to 220 Mc/s, as new, £20. A. SHARP, 25, Ariel Rd., Fratton, Portsmouth.

1,000 TELEVISIONS, all makes, from £23 working, 10/- not. Callers only. 9 till 6, including Sats. 39, Whitehorse Lane, Stepney, London.

VALVES, 6F1, 10F1, 6F13, 6L18/19, UF44/46, 10/- each; EF80, UL41, UF42, etc., 7/- each; EF50, 2/6 each, postage paid. Many obsolete types in stock. Recording Tape, high-quality plastic on standard spools. 1,200ft., 19/6. R.V.P.F., 24, Avon Rd., Chelmsford, Essex.

VIEWMASTER, complete set, little used, parts incl. 12in. tube, £12/10/-.. WELLS, 6, Nevill St., Abergyeny.

MAKING YOUR OWN TELESCOPES, Enlargers, Projectors, Viewers, Microscopes, Episcopes, etc., then our booklets "How to Use Ex-Gov. Lenses and Prisms," Nos. 1 and 2, 2/6 ea., will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

VALVES

GUARANTEED 3 MONTHS. 24 HOUR SERVICE Free Transit Insurance. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days

Table listing various vacuum tube valves with their types, prices, and stock status. Includes models like LA7, 6X4, 6Y5, etc.

Post per valve, 6d.; 2-6 9d.; 7-11 12d. 12-PAGE LIST OF 75 TYPES FOR 6d. All items less 5% and post free for a dozen. TECHNICAL TRADING CO. 350/352, Fratton Road, Portsmouth

EDDY'S (Nottm.) LTD.

DEPT. P.T.

172, ALFRETON ROAD,
NOTTINGHAM.

ACOS CRYSTAL TURNOVER PICK-UPS, 2 sapphire stylii, 29/11. Post 2/6.

TRANSISTORS. Yellow/Green Spot, 6/11.

TRANSISTORS. R.F. Yellow/Red Spot, 13/11. Post 4d.

SUB-MINIATURE TRANSISTOR CONDENSERS. 1.6 mfd., 5 mfd., 10 mfd., 16 mfd., 32 mfd., 2/6 each. Post 4d.

JACK PLUGS. Standard type, 1/11. Post 4d.

MORSE TAPPERS. Placed contacts, adjustable gaps, heavy duty, good quality. Special Price, 3/6. Post, etc. 4d.

ACOS CRYSTAL MIKE INSERTS, 4/11. High quality. Can be used for Tape Recorders, Baby Alarms, etc. Post 6d.

MIDGET BATTERY ELIMINATORS. To convert most types portables to mains operation, 57/6. Post 2/6. Size 3.7in. x 2.5in. x 1.8in. Smaller than H.T. battery alone (please state make and model No.).

SINGLE PIECE THROAT MIKES. 1/- each. Post 6d. Can be used for electrifying musical instruments, etc.

NEON MAINS TESTER/SCREW-DRIVER, 4/6 each. Post 6d.

GERMANIUM DIODES, 1/- each, 10/- dozen. Post 4d.

CONDENSERS, TUBULAR WIRE END (Not ex-Govt.). 8 mfd. 450 v. 1/9. 8-8 mfd. 450 v. 2/6. 16 mfd. 450 v. 2/9. 16-16 mfd. 450 v. 4/3. 32-32 mfd. 350 v. 4/9. 32 mfd. 450 v. 3/9. 16-8 mfd. 450 v. 3/9. 25 x 25 mfd. Midget 1/3. 50-50 mfd. 400 v. 6/11. Post 6d.

B.S.R. MONARCH 4-SPEED AUTOMATIC RECORD CHANGER. Type UA8. Complete with high fidelity turnover head type HGP 37-1. Capacity of 10 records, plays 12in., 10in., 7in. intermixed in any order. 78, 45, 33 and 16 r.p.m. For A.C. mains 100-250 volts. £6/19/6. Post, etc., 5/-.

RECORDING TAPE. 1,200ft. plastic reels, 10/11. Post, etc., 9d.

All above are new and guaranteed.

NEW AND SURPLUS GUARANTEED VALVES

1D5	10/-	6L6G	6/11	AZ31	10/-
1R5	7/6	6SN7GT	5/9	DAF96	8/6
1S5	7/-	6V6G	5/11	DF96	8/6
1T4	5/6	6V6GT	6/6	DK96	8/6
3D6	4/9	6X5GT	6/6	DL96	8/6
5U4G	6/6	25A6G	11/6	DM70	7/6
6AG5	5/-	807(B)	3/9	EF80	7/11
6BB8	2/11	807(USA)		L63	6/-
6BJ6	8/6			PCC84	8/6
6C4	3/11		5/6	PCF80	9/-
6F1	12/6	954	1/6	PCL82	12/6
6F13	12/6	955	3/11	PY81	8/11
6K7G	2/11	956	2/11	TDD4	12/5
6K8G	7/6	AZ1	12/5		

All tested before despatch.


C.W.O. or C.O.D. only. Postage and Packing 6d. per valve extra. Over £3 Free. S.A.E. with all enquiries.

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk.

Send 1/- for 56 page Illustrated Catalogue.

TRADE ENQUIRIES INVITED.

59 Gns.—'17'

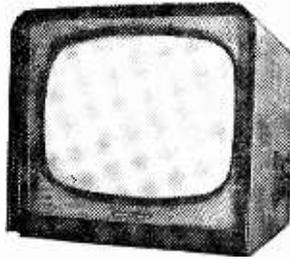

A full specification 17in. Television Receiver to Spencer-West standards now available at your Dealers. Remarkable performance and priced at 59 Gns. only, complete.

For Leaflet apply to:—

SPENCER-WEST LTD.
Quay Works, Great Yarmouth
Norfolk

Phones: Works 4794; Sales 3009
Grams: Spencer-West, Great Yarmouth

COVENTRY RADIO LTD.

189/191, Dunstable Road,
Luton

If you are unable to visit us at Luton, why not send for one of our

"HI-FI" CATALOGUES?

Price 1/-, plus 6d. postage. 70 pages and listing over 300 items.

Also now on sale: "THE GRUNDIG BOOK."

Price 12/6, plus 1/- postage.

The owner of any make of tape recorder will find this book an essential for successful recording.

LUTON'S HI-FI CENTRE

Telephone: Luton 7388/9.

LINE OUTPUT TRANSFORMERS


replacement or rewind. Send us your faulty one and we will be pleased to quote and save you money.

For Quotation S.A.E. Please.

AUDIO LTD.

Tower Road, London, N.W.10

Build your own Aerials...

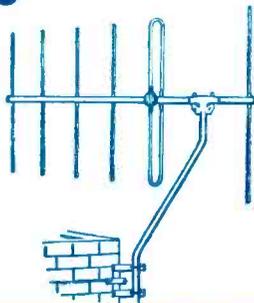

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.
 Useful formulæ and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above to :-

*Fringe*vision Ltd.

MARLBOROUGH, WILTS. Phone : 657/8

YOUR OWN TELEVISION TUBE RE-BUILT

THE FOLLOWING TYPES AND SIZES ONLY

MULLARD . .	12in. £7-10-0.	14in. £8-10-0.
OR EQUIVALENTS		
COSSOR-EMITRON-CATHODEON	17in. £10-10-0.	21in. £12-10-0.

48 Hr. SERVICE

All Tubes plus 10/- carriage and insurance.

SIX MONTHS' GUARANTEE

Terms to the Trade.

OWING TO PURCHASE TAX REGULATIONS WE CAN ONLY RE-BUILD YOUR OWN TUBE. THESE CAN BE SENT TO US BY BRITISH ROAD SERVICES (Parcels) LTD., CARRIAGE FORWARD.

TERMS, CASH WITH ORDER or C.O.D.

RE-VIEW (LONDON) LTD.

81, HIGH STREET . . . MERTON S.W.19

Telephone : CHERRYWOOD 3255

C.R.T. ISOLATION TRANSFORMER

Type A. Low leakage windings. Optional 25% and 50% boost on secondary. 2 v. or 4 v. or 6.3 v. or 10.8 v. or 13.3 v. with mains primaries ... 12/6.

TRIMMERS, Ceramic, 30, 50, 70 pf., 9d.; 100 pf., 150 pf., 1/3; 250 pf., 1/6; 500 pf., 750 pf., 1/9. RESISTORS, Preferred values, 10 ohms to 10 meg., 1 w., 4d.; 1 w., 4d.; 1 w., 8d., 14 w., 8d., 2 w., 11/4.

12/6 PURETONE RECORDING TAPE

1,200 ft. on standard 7" Metal reels. Spare Reels 7" plastic, 4; 7" metal, 2/3. SUPERIOR 1,200 ft. Plastic Tape on 7" Plastic Reels, Quality Guaranteed, 21/-.

O.P. TRANSFORMERS, Heavy Duty 50 m.A., 4/6. Multiratio, push-pull, 7/6. Miniature, 38/1, etc., 4/6. L.F. CHOKES 1510 H, 60/65 m.A., 5; 10 H, 8/5 m.A., 10/6; 10 H, 150 m.A., 14/6.

MAINS TRANSFORMERS 200 250 v. A.C.

STANDARD, 250/0-250, 30 m.A., 6/3 v. 35/3 v. tapped 4 v., 4 v., 2.4, ditto, 350/0-350 ... 2/6. MINIATURE, 200 v. 20 m.A., 6/3 v. 1.4, 10/6.

ALADDIN FORMERS and core, 1in., 8d.; 1in., 10d. 0.5in. FORMERS 4937/8 and Cans TV1 2, 1in. sq. x 2in. and 1in. sq. x 1 1/2in., 2/- ea., with cores.

TYANA.—Midget Soldering Iron, 200/220 v. or 250/250 v. 16/9. Famous Instrument Iron, 17/6. MAINS DROPPERS, 3in. x 1 1/2in., Adis, 5/6d.

All Boxed VALVES 90-day Guarantee.

Table listing various vacuum tubes and their prices, including 1R5, 1R5G, 1T1, 2N2, 2N4, 2N7, 2N8, 2N9, 2Y3, 2Y4, 2Y5, 2Y99, 2Y100.



1959 RADIOGRAM CHASSIS THREE WAVEBANDS FIVE VALVES S.W. 16 m.—50 m. LATEST MULLARD M.W. 200 m.—500 m. I.F. 442 EP41, EB41, L.W. 800 m.—2,000 m. EL11, EZ10, 12-month 300 guarantee.

£9.10 Carr. & Ins. 4/- TERMS: Dep. £5.0.0 and five monthly of £1. MATCH SPEAKERS FOR ABOVE CHASSIS. 8in. 17/6; 12in. 21/6.



UAS World's Finest 4-Speed Autochanger OUR PRICE £6.19.6 TERMS: Dep. £3.10.0 and four monthly of £1. Stereo Model UA12 £11.17.6

COLLARO LATEST MODEL HIGH-FIDELITY AUTOCHANGER 4-SPEEDS—10 RECORDS With Studio "O" pick-up BRAND NEW MAKER'S BOXES OUR PRICE £7.19.6 post free.

BUILD THIS REPRODUCER BARGAIN SINGLE PLAYER KIT Ready for immediate assembly. 4-speed Collaro 'Junior' that ... £12 6 Hand-some case, 17 1/2 x 13 1/2 x 7 1/2 in., with room to play 12 in. records ... £2 5 0 Ready-built 3-watt amplifier with two valves and loudspeaker ... £12 6 or £9.15.0 complete kit post free.

ALUMINIUM CHASSIS, 18 swg. drilled, with 4 sides, riveted corners and lattice fitting, 2 1/2 in. sides, 7 x 4 in., 4/6; 3 x 7 in., 5/8; 1 1/2 x 7 in., 6/9; 1 1/2 x 9 in., 8/6; 1 1/2 x 1 1/2 in., 10/6; 1 1/2 x 1 1/2 in., 12/6; 1 1/2 x 1 1/2 x 1 1/2 in., 16/6.

TRANSISTORS, GENUINE PYE GOLTOP, Audio, 10/-, R.P.F. 13 Mc/s. average, 18/- Power, 20/-, Complete data sheets supplied.

HANDY VOLT METERS, 0-25 v. and 0-250 v., D.C., with leads and leather case, 9/6.

CRYSTAL MIKE INSERT by Acos, precision engineering. Size only 1in. x 3/16in., 6/6.

HI-GAIN BAND 3 I.T.A. PRE-AMP KIT. Cassette circuit with coils EP41. Price 29/6 With Power Pack, 49/6. Plans only 6d. Band 1 B.B.C. version same prices.

TELETRON "TRANSIDYNE" 6" x 4" x 1 1/2" 6 transistors, printed circuit, Ferrite aerial, All parts and cabinet, £11.19.6. We include 6 Pye Goltop Transistors for maximum performance. Plans 9/6.

GARRARD 45P. SINGLE PLAYER

AUDIO PERFECTION Designed to play 16, 33, 45, 78 r.p.m. Records 7in., 10in., 12in. Lightweight Xtal pick-up. GC2 turnover head, two separate amplifier stl's. OUR PRICE £8.0.0 each. Post Free. De luxe cabinet, quality amplifier and 64 in. speaker, £8.15.0 or complete kit, £14.10.0.

Volume Controls 80 OHM COAX

Long spindles. Guaranteed 1 year. 5K ohms to Meg. No wax. 3. Linear or Log Track. COAX PLUGS—1. DOUBLE SOCKET ... 1.3 SOCKETS—1. OUTLET BOXES ... 4.6 BALANCED TWIN FEEDER ... 6d. 80 or 300 ohms. DITTO SCREENED per yd., 12/- 50 ohms only. WIRE-WOUND POTS, 3-WATT. Pre-set, Min. 1/4, 1/2, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 15, 20, 30, 40, 50, 60, 70, 80, 90, 100, 150, 200, 300, 400, 500, 600, 700, 800, 900, 1000, 1500, 2000, 3000, 4000, 5000, 6000, 7000, 8000, 9000, 10000, 15000, 20000, 30000, 40000, 50000, 60000, 70000, 80000, 90000, 100000, 150000, 200000, 300000, 400000, 500000, 600000, 700000, 800000, 900000, 1000000, 1500000, 2000000, 3000000, 4000000, 5000000, 6000000, 7000000, 8000000, 9000000, 10000000, 15000000, 20000000, 30000000, 40000000, 50000000, 60000000, 70000000, 80000000, 90000000, 100000000, 150000000, 200000000, 300000000, 400000000, 500000000, 600000000, 700000000, 800000000, 900000000, 1000000000, 1500000000, 2000000000, 3000000000, 4000000000, 5000000000, 6000000000, 7000000000, 8000000000, 9000000000, 10000000000, 15000000000, 20000000000, 30000000000, 40000000000, 50000000000, 60000000000, 70000000000, 80000000000, 90000000000, 100000000000, 150000000000, 200000000000, 300000000000, 400000000000, 500000000000, 600000000000, 700000000000, 800000000000, 900000000000, 1000000000000, 1500000000000, 2000000000000, 3000000000000, 4000000000000, 5000000000000, 6000000000000, 7000000000000, 8000000000000, 9000000000000, 10000000000000, 15000000000000, 20000000000000, 30000000000000, 40000000000000, 50000000000000, 60000000000000, 70000000000000, 80000000000000, 90000000000000, 100000000000000, 150000000000000, 200000000000000, 300000000000000, 400000000000000, 500000000000000, 600000000000000, 700000000000000, 800000000000000, 900000000000000, 1000000000000000, 1500000000000000, 2000000000000000, 3000000000000000, 4000000000000000, 5000000000000000, 6000000000000000, 7000000000000000, 8000000000000000, 9000000000000000, 10000000000000000, 15000000000000000, 20000000000000000, 30000000000000000, 40000000000000000, 50000000000000000, 60000000000000000, 70000000000000000, 80000000000000000, 90000000000000000, 100000000000000000, 150000000000000000, 200000000000000000, 300000000000000000, 400000000000000000, 500000000000000000, 600000000000000000, 700000000000000000, 800000000000000000, 900000000000000000, 1000000000000000000, 1500000000000000000, 2000000000000000000, 3000000000000000000, 4000000000000000000, 5000000000000000000, 6000000000000000000, 7000000000000000000, 8000000000000000000, 9000000000000000000, 10000000000000000000, 15000000000000000000, 20000000000000000000, 30000000000000000000, 40000000000000000000, 50000000000000000000, 60000000000000000000, 70000000000000000000, 80000000000000000000, 90000000000000000000, 100000000000000000000, 150000000000000000000, 200000000000000000000, 300000000000000000000, 400000000000000000000, 500000000000000000000, 600000000000000000000, 700000000000000000000, 800000000000000000000, 900000000000000000000, 1000000000000000000000, 1500000000000000000000, 2000000000000000000000, 3000000000000000000000, 4000000000000000000000, 5000000000000000000000, 6000000000000000000000, 7000000000000000000000, 8000000000000000000000, 9000000000000000000000, 10000000000000000000000, 15000000000000000000000, 20000000000000000000000, 30000000000000000000000, 40000000000000000000000, 50000000000000000000000, 60000000000000000000000, 70000000000000000000000, 80000000000000000000000, 90000000000000000000000, 100000000000000000000000, 150000000000000000000000, 200000000000000000000000, 300000000000000000000000, 400000000000000000000000, 500000000000000000000000, 600000000000000000000000, 700000000000000000000000, 800000000000000000000000, 900000000000000000000000, 1000000000000000000000000, 1500000000000000000000000, 2000000000000000000000000, 3000000000000000000000000, 4000000000000000000000000, 5000000000000000000000000, 6000000000000000000000000, 7000000000000000000000000, 8000000000000000000000000, 9000000000000000000000000, 10000000000000000000000000, 15000000000000000000000000, 20000000000000000000000000, 30000000000000000000000000, 40000000000000000000000000, 50000000000000000000000000, 60000000000000000000000000, 70000000000000000000000000, 80000000000000000000000000, 90000000000000000000000000, 100000000000000000000000000, 150000000000000000000000000, 200000000000000000000000000, 300000000000000000000000000, 400000000000000000000000000, 500000000000000000000000000, 600000000000000000000000000, 700000000000000000000000000, 800000000000000000000000000, 900000000000000000000000000, 1000000000000000000000000000, 1500000000000000000000000000, 2000000000000000000000000000, 3000000000000000000000000000, 4000000000000000000000000000, 5000000000000000000000000000, 6000000000000000000000000000, 7000000000000000000000000000, 8000000000000000000000000000, 9000000000000000000000000000, 10000000000000000000000000000, 15000000000000000000000000000, 20000000000000000000000000000, 30000000000000000000000000000, 40000000000000000000000000000, 50000000000000000000000000000, 60000000000000000000000000000, 70000000000000000000000000000, 80000000000000000000000000000, 90000000000000000000000000000, 100000000000000000000000000000, 150000000000000000000000000000, 200000000000000000000000000000, 300000000000000000000000000000, 400000000000000000000000000000, 500000000000000000000000000000, 600000000000000000000000000000, 700000000000000000000000000000, 800000000000000000000000000000, 900000000000000000000000000000, 1000000000000000000000000000000, 1500000000000000000000000000000, 2000000000000000000000000000000, 3000000000000000000000000000000, 4000000000000000000000000000000, 5000000000000000000000000000000, 6000000000000000000000000000000, 7000000000000000000000000000000, 8000000000000000000000000000000, 9000000000000000000000000000000, 10000000000000000000000000000000, 15000000000000000000000000000000, 20000000000000000000000000000000, 30000000000000000000000000000000, 40000000000000000000000000000000, 50000000000000000000000000000000, 60000000000000000000000000000000, 70000000000000000000000000000000, 80000000000000000000000000000000, 90000000000000000000000000000000, 100000000000000000000000000000000, 150000000000000000000000000000000, 200000000000000000000000000000000, 300000000000000000000000000000000, 400000000000000000000000000000000, 500000000000000000000000000000000, 600000000000000000000000000000000, 700000000000000000000000000000000, 800000000000000000000000000000000, 900000000000000000000000000000000, 1000000000000000000000000000000000, 1500000000000000000000000000000000, 2000000000000000000000000000000000, 3000000000000000000000000000000000, 4000000000000000000000000000000000, 5000000000000000000000000000000000, 6000000000000000000000000000000000, 7000000000000000000000000000000000, 8000000000000000000000000000000000, 9000000000000000000000000000000000, 10000000000000000000000000000000000, 15000000000000000000000000000000000, 20000000000000000000000000000000000, 30000000000000000000000000000000000, 40000000000000000000000000000000000, 50000000000000000000000000000000000, 60000000000000000000000000000000000, 70000000000000000000000000000000000, 80000000000000000000000000000000000, 90000000000000000000000000000000000, 100000000000000000000000000000000000, 150000000000000000000000000000000000, 200000000000000000000000000000000000, 300000000000000000000000000000000000, 400000000000000000000000000000000000, 500000000000000000000000000000000000, 600000000000000000000000000000000000, 700000000000000000000000000000000000, 800000000000000000000000000000000000, 900000000000000000000000000000000000, 1000000000000000000000000000000000000, 1500000000000000000000000000000000000, 2000000000000000000000000000000000000, 3000000000000000000000000000000000000, 4000000000000000000000000000000000000, 5000000000000000000000000000000000000, 6000000000000000000000000000000000000, 7000000000000000000000000000000000000, 8000000000000000000000000000000000000, 9000000000000000000000000000000000000, 10000000000000000000000000000000000000, 15000000000000000000000000000000000000, 20000000000000000000000000000000000000, 30000000000000000000000000000000000000, 40000000000000000000000000000000000000, 50000000000000000000000000000000000000, 60000000000000000000000000000000000000, 70000000000000000000000000000000000000, 80000000000000000000000000000000000000, 90000000000000000000000000000000000000, 100000000000000000000000000000000000000, 150000000000000000000000000000000000000, 200000000000000000000000000000000000000, 300000000000000000000000000000000000000, 400000000000000000000000000000000000000, 500000000000000000000000000000000000000, 600000000000000000000000000000000000000, 700000000000000000000000000000000000000, 800000000000000000000000000000000000000, 900000000000000000000000000000000000000, 1000000000000000000000000000000000000000, 1500000000000000000000000000000000000000, 2000000000000000000000000000000000000000, 3000000000000000000000000000000000000000, 4000000000000000000000000000000000000000, 5000000000000000000000000000000000000000, 6000000000000000000000000000000000000000, 7000000000000000000000000000000000000000, 8000000000000