

PRACTICAL TELEVISION

3/6

MAY
1970

AERIALS FOR THE

70^S



**also
inside:-**

**FOCUS ON CHROMA CIRCUITS
SURPLUS TV IF PANEL
TRANSISTOR FIELD OSCILLATORS**

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W. 1
THE VALVE SPECIALISTS Telephone 01-722 9090

SAVE POSTAL COSTS! CASH AND CARRY BY CALLERS WELCOME

0A2	5 9	6B8G	2 6	6P25	12-	12AUV	4 6	30L15	13 9	AC2PEN	DL35	4 9	ECC38	31 6	EFP60	10-	K78	34 6	PCL84	7 6	R16	34 11	U1R/20	10-
0B2	6	6RA6	4 6	6P26	12-	12AV6	5 0	30L17	15 6	19 6	DL92	6 9	ECC44	29 6	EH90	7 6	KT11	19 6	PCL85	9-	R17	17 6	U10	34 6
0Z4	4 6	6RE6	4 9	6P28	25-	12AX7	4 6	30P4	17-	AC2PEN/	DL94	5 9	ECC40	9 6	EL35	12-	KT61	20-	PCL86	8 6	R18	9 6	U22	7 6
1A3	4 6	6RH6	7 6	6Q7	8 6	12AX7	9 3	30P4M	17-	AC2PEN/	DL96	6 6	ECC82	4 6	EL34	10 6	KT61	12-	PCL88	15-	R19	6 6	U23	13 6
1A3	5	6BF6	8 6	6Q7G	6-	12BA6	6-			AC2PEN/	DL98	10 6	ECC83	4 6	EL37	17 3	KT66	17 3			R20	17 6	U24	11 6
1A7GT	7 2	6BQ5	4 9	6R7	11-	12BB6	5 9	30P12	13 9	AC2PEN/	DM70	6-	ECC84	6 3	EL41	10 3	KT74	12 6	PEN 43	7-	RK34	7 6	U33	29 6
1C5	4 9	6BQ7A	7-	6R7G	7-	12BH6	6-	30P19	12-	19 6	DM71	7 6	ECC85	5 6	EL42	9 9	KT76	12 6	PEN 45	DD	SP42	12 6	U35	16 6
1D5	6 9	6BR7	15 6	6SA7GT	7-	12E1	17-	30P11	15-	AC2PEN/	DM73	6 6	ECC86	8-	EL81	8-	KT88	29 6			SP61	3 3	U37	34 11
1D5	9 6	6BR8	3 6	6SA7M	7-	12F7GT	6 6	30P13	15 6	19 6	DM74	6 6	ECC87	7-	EL83	6 9	KT89	8 6	PEN 46	4 9	TH48	10 6	U43	15 6
1FD1	6 6	6BS7	18 6	6SC7GT	6 3	12K5	10-	30P14	15-	AC2TH1	DY86	5 9	ECC88	7-	EL84	4 9	KTW62	10-	PEN 45	DD	U49	7 6	U47	13 6
1FD9	4 3	6BW7	11-	6BS7	6-	12K7GT	5 9	30P15	15-		DY87	5 9	ECC89	5 9	EM84	6 6	LN330	15-	PEN 47	19 6	U50	10 6	U49	11 6
1G6	6-	6BZ6	6-	6BS7	3-	12Q7GT	4 6	35A3	9-	AC2TP	E80F	24-	ECC90	5 9	EM85	11-	LZ329	6 6	PEN 48	19 6	U51	10 6	U51	12 6
1HG7	7-	6C6	3 9	6B7	6 6	12SA7GT	4 6	35A3	15-	AC2VP	E80F	24-	ECC91	5 9	EM87	7 6	ME140014	9-	PEN 49	19 6	U52	10 6	U52	14 6
1L4	2 6	6C6	14 6	6SK7GT	4 6		6 9	35D5	12-	AL60	15 6	E88C0C	12-	EM87	6 6	N78	27 10	PL81A	10 6	U53	10 6	U53	14 6	
1LD5	5-	6CD6G	19 6	6SN7GT	4 6	12M7	4-	35L6GT	8 6	AR73	7-	E180F	17 6	EM88	7 6	MHL2	7 6	PL82	6 6	U54	10 6	U54	14 6	
1LN5	8-	6CH6	6-	6G4GT	7 6	12M7	4-	35W4	4 6	ATP4	2 3	E180C	22 6	EY81	7-	N339	25-	PL83	6 6	U55	10 6	U55	14 6	
1NAGT	7 9	6CL8	8 6	6U3GT	12-	12M7	3-	35Z3	3-	AZ1	8 6	E1148	10 6	EY82	8 6	MX40	12 6	PL84	6 6	U56	10 6	U56	14 6	
1R3	5 6	6CW4	12-	6UT6	7-	12M7	4 6	35Z4GT	4 9	AZ1	9 6	E150	1 6	EY83	8 6	MX40	12 6	PL85	6 6	U57	10 6	U57	14 6	
1R4	4 9	6D3	7 6	6V6G	3 6	12M7	4 9	35Z5GT	6-	AZ1	7 6	E176	13-	EY84	7 6	MX40	12 6	PL86	6 6	U58	10 6	U58	14 6	
1R5	4 3	6D6	3-	6X3	4 3	12M7GT	7 6	35Z5	6 3	B36	6 6	E180C	6 6	EY85	6 6	N78	27 10	PL87	6 6	U59	10 6	U59	14 6	
1U4	5 9	6E6	5 9	6XGT	5-	14H7	9 6	59Z5	5 3	BL33	10 6	E180C	22 6	EY86	8 6	MX40	12 6	PL88	6 6	U60	10 6	U60	14 6	
2D21	5 6	6F6	12 6	6Y7G	12 6	14H7	19 6	59Z6GT	4 3	CL33	18 6	E180C	22 6	EY87	8 6	MX40	12 6	PL89	6 6	U61	10 6	U61	14 6	
3A5	10-	6F6G	4-	7B6	10 9	18 6	12 6	59Z6GT	9-	CV6	10 6	E180C	22 6	EY88	8 6	MX40	12 6	PL90	6 6	U62	10 6	U62	14 6	
3B7	5-	6F12	3 3	7B7	7-	19AQ5	4 9	72	6 6	CY10	10 6	E180C	22 6	EY89	8 6	MX40	12 6	PL91	6 6	U63	10 6	U63	14 6	
3D4	3 9	6F13	3 9	7C6	6-	10H1	4 6	55A2	8 6	CY31	7 6	E180C	22 6	EY90	8 6	MX40	12 6	PL92	6 6	U64	10 6	U64	14 6	
3Q1	6 6	6F15	10-	7F5	12 6	20D1	13 6	55A3	8 6	D63	5 6	E180C	22 6	EY91	8 6	MX40	12 6	PL93	6 6	U65	10 6	U65	14 6	
3Q3GT	6-	6F15	6 6	6F15	5 6	20D1	20 6	59A2	8 6	D77	10 6	E180C	22 6	EY92	8 6	MX40	12 6	PL94	6 6	U66	10 6	U66	14 6	
3R4	5 9	6F23	13 3	7R7	12-	20F2	14-	98AV	8 6	DAC32	7 6	E180C	22 6	EY93	8 6	MX40	12 6	PL95	6 6	U67	10 6	U67	14 6	
3V4	5 9	6P24	11 9	7V7	5-	20L1	13 6	90CG	34-	DAF91	4 3	E180C	22 6	EY94	8 6	MX40	12 6	PL96	6 6	U68	10 6	U68	14 6	
5R4G	5 9	6P25	13-	9BW6	7-	20P1	17 6	90CV	33 6	DAF96	6 6	E180C	22 6	EY95	8 6	MX40	12 6	PL97	6 6	U69	10 6	U69	14 6	
5U4G	5 9	6P28	14-	9D7	9-	20P3	18 6	90C1	10-	DAC90	6 6	E180C	22 6	EY96	8 6	MX40	12 6	PL98	6 6	U70	10 6	U70	14 6	
5V4G	7 6	6P29	15-	10C1	12 6	20P4	18 6	130B2	14 6	DD4	10 6	E180C	22 6	EY97	8 6	MX40	12 6	PL99	6 6	U71	10 6	U71	14 6	
5V3GT	5 6	6G6G	15-	10C2	10-	20P5	18-	130C3	5 9	DE33	7 9	E180C	22 6	EY98	8 6	MX40	12 6	PL100	6 6	U72	10 6	U72	14 6	
5Z3	8-	6H6GT	1 9	10D1	8-	25LGT	5 6	301	20-	DF91	2 9	E180C	22 6	EY99	8 6	MX40	12 6	PL101	6 6	U73	10 6	U73	14 6	
6Z4G	7-	6J5G	3 9	10D2	14 7	25Y3	6 6	302	18 6	DF96	6 6	E180C	22 6	EY100	8 6	MX40	12 6	PL102	6 6	U74	10 6	U74	14 6	
6J30L2	12 6	6J6	3-	10P1	15-	35Y3G	8 6	303	15-	DF97	10-	E180C	22 6	EY101	8 6	MX40	12 6	PL103	6 6	U75	10 6	U75	14 6	
6A80	5 6	6J7G	4 9	10P9	9-	35Z40	6 6	303	16 6	DH63	6 6	E180C	22 6	EY102	8 6	MX40	12 6	PL104	6 6	U76	10 6	U76	14 6	
6A67	3-	6J7GT	6 6	10P18	7-	35Z5	7-	303	13-	DH76	4 6	E180C	22 6	EY103	8 6	MX40	12 6	PL105	6 6	U77	10 6	U77	14 6	
6A65	3 6	6K7G	2-	10LD110		25Z6G	8 6	307	11 9	DH77	4-	E180C	22 6	EY104	8 6	MX40	12 6	PL106	6 6	U78	10 6	U78	14 6	
6AK5	5-	6K7GT	4 6	10P13	13-	30C1	8 6	306	2-	DH81	10 9	E180C	22 6	EY105	8 6	MX40	12 6	PL107	6 6	U79	10 6	U79	14 6	
6AK6	6-	RL1	10 4	10P14	12 6	30C15	13 6	18 21	10 6	DH101	25-	E180C	22 6	EY106	8 6	MX40	12 6	PL108	6 6	U80	10 6	U80	14 6	
6AL5	2 3	6LGT	7 9	12A6	3 6	30C17	16-	5763	10-	DH107	17 11	11 11	11 11	EY107	8 6	MX40	12 6	PL109	6 6	U81	10 6	U81	14 6	
6AM3	3 3	6LGT	12 6	12A36	7 6	30C18	11 6	6060	5 6	DK32	7 3	E180C	22 6	EY108	8 6	MX40	12 6	PL110	6 6	U82	10 6	U82	14 6	
6AQ3	5 6	6LGT	8 6	12A36	8 6	30C19	16-	7193	10 6	DK40	10-	E180C	22 6	EY109	8 6	MX40	12 6	PL111	6 6	U83	10 6	U83	14 6	
6AB6	20-	6L19	19-	12A36	7 6	30P11	13-	7473	4-	DL31	5 6	E180C	22 6	EY110	8 6	MX40	12 6	PL112	6 6	U84	10 6	U84	14 6	
6AT6	4-	6LD20	9 6	12A78	4 6	30P14	13 6	A1534	20-	DK92	9-	E180C	22 6	EY111	8 6	MX40	12 6	PL113	6 6	U85	10 6	U85	14 6	
6AU6	5 6	6N7G	6 6	12A77	3 9	30P14	13 6	A2134	10-	DK96	7-	E180C	22 6	EY112	8 6	MX40	12 6	PL114	6 6	U86	10 6	U86	14 6	
6AV6	5 6	6P1	12-	12AUG	4 9	30L1	6 6	A3042	15-	DL33	6-	E180C	22 6	EY113	8 6	MX40	12 6	PL115	6 6	U87	10 6	U87	14 6	


All goods are new and subject to the makers' guarantee. We do not handle manufacturers' seconds, nor rejects, which are often described as "new and tested" but have a limited and unreliable life. Business hours Mon.-Fri. 9.30-5.30 p.m. Sat. 9-1 p.m.
Terms of business: Cash with order only. Post/packing 6d. per item. Orders over £5 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 6d. extra. Complete catalogue of valves, transformers and components with conditions of sale, price list, post free. No enquiries answered unless S.A.E. enclosed for reply.

EX-RENTAL TELEVISIONS TWO-YEAR GUARANTEES

FREE ILLUSTRATED LIST OF TELEVISIONS
17" SLIMLINE 405 only £11 10 0
19" SLIMLINE 405/625 39 gns.

17"-19"-21"-23"
WIDE RANGE OF MODELS, SIZES AND PRICES

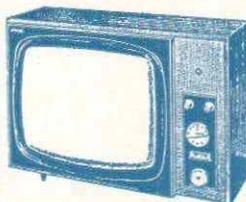DEMONSTRATIONS DAILY
Carriage and Insurance 30/-



TWO-YEAR GUARANTEED TUBES 100% REGUNNED
Slim Line Tubes 110° 17" and 19" 109/6, 21" and 23" 129/6.
Normal Tubes 70° and 90° 17" 99/6, 21" 119/6, 14" and other sizes 79/6.

SPEAKERS 10-, 2 1/2" 8Ω, 3 1/2" 25Ω, 4" 10Ω, 3" x 5" 8Ω, 7" x 4" 3Ω, 8" x 3" 3Ω. BRAND NEW. P. & P. 2/-

Transistors: Mullard matched output kit 7/6, OC81D—2 OC81's. P. & P. FREE. AF 117, AF114, OC44, OC45, OC71; 2/6 each

Ferrite Rods 3/6: 6" and 8" complete with LW/MW Coils. P. & P. FREE.

Transistor Cases 4 for £1.
SIZE: 9 1/2 x 6 1/2 x 3 1/2 P & P 9/6.

STRIP LIGHT TUBES 3/9 each, 11" (284 mm.) 230/240 volts, 30 watts. Ideal for cocktail cabinets, illuminating pictures, diffused lighting, etc. 6 for £1. P. & P. free.

RECORD PLAYER CABINET 49/6.



Cloth covered. Size 16 1/2" x 14 1/2" x 7 1/2". Takes any modern auto-changer. P. & P. 7/6.


DUKE & CO. (LONDON) LTD.

621/3 Remford Road, London, E12

Tel. 01-478 6001/2/3

T.V. TUBES "VIDEOCHROME" T.V. TUBES

FOR BRILLIANCE & DEFINITION

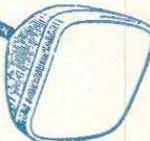

CASH OR CHEQUE WITH ORDER

COMPARE OUR PRICES

17"—£4-15-0
19"—£5-5-0
21"—£6-10-0
23"—£7-10-0

TRADE SUPPLIED

ALL TUBES PRECISION REBUILT AT OUR OWN FACTORY BY SKILLED CRAFTSMEN WHO HAVE BEEN REBUILDING TUBES FOR OVER 10 YEARS ● EACH TUBE BENCH AND SET TESTED TO A VERY HIGH STANDARD BEFORE DISPATCH

PRICES FOR TWIN PANEL TUBES AVAILABLE ON REQUEST
2 YEARS GUARANTEE ● FREE DELIVERY ANYWHERE IN THE U.K.

VIDEOCHROME TUBES LTD.

25 BELLEVUE AVENUE, RAMSGATE, KENT. Tel. THANET 52914

NEW LINE OUTPUT TRANSFORMERS

ALBA 655, 656, 717, 721e 75/-
BUSH TV53 to TUG69 40/-
DECCA DMI, DM3C, DM4C (70°) 78/-
DYNATRON TV30, TV35 50/-, TV36, TV37, TV38, TV40, TV46, TV49F 70/-
EKCO T231, T284, TC267, T283, T293, T311, T326, T327, T330 50/-, TMB272 68/6, T344, T344F, T345, TP347, T348, T348F, TC347, TC349, TC356, T368, T370, TC369, T371, T372, TP373, TC374, T377A, T393, T394, 433, 434, 435, 436, 437 all at 70/-, 503, 504, 505, 506 95/-
FERGUSON 306T, 308T 55/6 each, 406T, 408T, 416, 436, 438, 506, 508, 516, 518, 536, 546, 604, 606, 608, 616, 619, 636, 646, 648, 725, 726, 727, 3600, 3601, 3602, 3604, 3611, 3612, 3614, 3617, 3618, 3619, 3620, 3621, 3622, 3623, 3624, 3625, 3626, 3627, 3629 65/-
FERRANTI T1001, T1002, T1002/1, T1004, T1005 50/-, T1023, T1024, T1027, T1027F, TP1026, T1071, T1072, T1121, TC1122, TC1124, T1125, TC1126 70/-, 1154, 1155 95/-
G.E.C. BT302, BT304 62/6, BT454DST-456DST, 2010, 2013, 2014, 2012, 2000DS, 2001DS, 2002DS 85/-
H.M.V. 1865, 1869 55/-, 1870, 1872, 1874, 1876, 1890, 1892, 1894, 1896 65/-
KB OV30, NF70, NV40, PV40, QV10, QV30, PVP20 90/-, Featherlight 90/-
PILOT PT450, 452, 455, 650, PT651 70/-
PHILCO 1019, 1020, 2021 82/6, 1029, 1030, 1035, 1036, 1040, 1050, 1060 82/6
PYE V200, V400, 200LB, 210, 220, 300F, 300S, 310, 210S, 410 70/-, **PYE** 11U P/No. AL21003 70/-
REGENTONE TV403 90/-
R.G.D. RV203 90/-
ULTRA 1770, 2170, 1772, 1782, 2172, 1771, 2171, 1775, 2175, 1774, 2174, 1773, 2137, 1980c, 1984c, 100c, 200c, 2380, 2384, 1984, 1985, 1986, 1980, 1980a, 1780, 2180, 2181, 2183, 2182, 1871, 1783 80/-

LINE OUTPUT TRANSFORMER INSERTS

BUSH TV92, TV93, TV94, TV95, TV96, TV97, TV98, TV99, TV100, TV101, TV103, TV104, TV105, TV106, TV108, TV109, TV110, TV113, TV115, TV115R, TV115c 55/- Complete with heater windings.
DECCA DR95, DR100, DR101, DR202, DR303, DR404, DR505, DR606 55/-
EMERSON E700, E701, E704, E707, E708, E709, E710, E711, Portarama 32/6
FERGUSON 204T, 205T, 206T, 214T, 235T, 236T, 244T, 245T, 246T 30/-
FERRANTI 14T2, 14TC, 14T3F, 14T4, 14T4F, 14T5, 14T6, 17K3, 17K3F, 17T3, 17T3F, 17K4F, 17K6, 17SK6, 17T4, 17T4F, 17T5, 17T6, 21K6, 21K6V 32/6
INVICTA T118, T119, T120 40/-
K.B. PV40, MV100, OF100, PV100, NV40, NF70, OV30, QV10, QV30 32/6; VV80, VV30, VV20, VV10, WV05, WV20, RV30, RV70, QUP20, KT001, KT405A 55/- pair.
PETO SCOTT 1416, 1418, 1419, 1422, 1423, 1716, 1719, 1720, 1922, 1723, 1724, 1725 29/6
PYE V4, V7, CTM4, TCM7 40/-
REGENTONE 10-4, 10-6, 1021, 17-18, 10-12 30/-, T176, T77, 191, 192 32/6
R.G.D. Deep 17, The 17, 590, 600, 606, 611, 710, 723 32/6
Guarantee. Post and Package 4/6. C.O.D. 6/- **CALLERS WELCOME.**

THIS LIST CANCELS ALL PREVIOUS LISTS

All new components inserts are guaranteed for three months from the date of invoice subject to the breakdown being due to faulty manufacture or materials. S.A.E. all enquiries.

RETURN OF POST SERVICE

Dept. "R" D. & B. TELEVISION (Wimbledon) LTD

80 MERTON HIGH STREET, S.W.19

01-540 3513 01-540 3955

NEW RANGE U.H.F. - TV - AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays, 7 element, 40/-; 11 element, 47/6; 14 element, 55/-; 18 element, 62/6. **Wall Mounting with Cranked Arm,** 7 element, 60/-; 11 element, 67/6; 14 element, 75/-; 18 element, 82/6. **Mast Mounting with 2in. clamp,** 7 element, 42/6; 11 element, 55/-; 14 element, 62/-; 18 element, 70/- **Chimney Mounting Arrays,** Complete 7 element, 72/6; 11 element, 80/-; 14 element, 87/6; 18 element, 95/- **Complete assembly instructions** with every unit. **Low Loss Cable,** 1/6 yd. **U.H.F. Pre-amps** from 75/-. State clearly channel number required on all orders.

BBC - ITV AERIALS



BBC (Band 1), Loft 25/-, External S D, 30/-, "H", £2.15.0.
ITV (Band 3), 3 element loft array, 30/-, 5 element, 40/-, 7 element, 50/-, Wall mounting, 3 element, 50/-, 5 element, 55/-, Combined BBC/ITV, Loft 1+3, 40/-; 1+5, 50/-; 1+7, 60/-; Wall mounting 1+3, 60/-; 1+5, 70/-; Chimney 1+3, 70/-; 1+5, 80/-; VHF transistor pre-amps, 75/-

COMBINED BBC 1-ITV-BBC2 AERIALS 1+3+9, 70/-, 1+5+9, 80/-, 1+5+14, 90/-, 1+7+14, 100/- **Loft mounting only.** **F.M. (Band 2),** Loft S D, 17/6, "H", 35/-, 3 element, 57/6. External units available. Co-ax. cable, 8d. yd. Co-ax. plugs, 1/6. Outlet boxes, 5/-, Diplexer Crossover Boxes, 17/6. C.W.O. or C.O.D. P. & P. 6/6. Send 6d. stamps for illustrated lists.

CALLERS WELCOME
OPEN ALL DAY SATURDAY
K.V.A. ELECTRONICS (Dept.P.T.)
 40-41 Monarch Parade
 London Road, Mitcham, Surrey
 01-648 4884

Learn at home... First Class Radio and TV Courses

get a
certificate

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.I.E.R.E. Guide also gives details of range of certificate courses in Radio/TV Servicing, Electronics and other branches of engineering, together with particulars of our remarkable terms of

Satisfaction or refund of fee

Write now for your copy of this valuable publication. It may well prove to be the turning point in your career.

Founded 1885 Over 150,000 successes

CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)
 (Dept. 844V) 148 Holborn, London, E.C.1.

YOUR PERSONAL INTRODUCTION to the wonderful world of LASKY'S. Send at once for our AUDIO-TRONICS '70 catalogue—available FREE on request. Everything for the Hi-Fi and Radio enthusiast, electronics hobbyist, serviceman, communications ham, etc. ALL at Lasky's unbeatable prices PLUS our fantastic MONEY VOUCHERS worth over £25. 1,000's of items comprehensively arranged for you to select in the comfort of your own home. Just send your name, address and 2/- to cover post only, and the inclusion on our regular mailing list, to Lasky's Radio Ltd., Dept. PT., 3-15 Cavell Street, London E1 2BN.

REBUILT TUBES !

YOU'RE SAFE WHEN YOU BUY FROM RE-VIEW !

HERE IS WHAT YOU PAY:

12in. ...	£4.15.0	19in. ...	£5.15.0
14in. ...	£5. 0.0	21in. ...	£6. 5.0
15in. ...	£5. 5.0	23in. ...	£8.10.0
17in. ...	£5. 5.0	19in. Twin Panel	£7.10.0
	23in. Twin Panel		£10.0.0

Cash or cheque with order, or cash on delivery

Discount for Trade

- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater
- ★ Each tube comes to you with a guarantee card covering it for two years against all but breakage
- ★ Each tube is delivered free anywhere in the U.K. and insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

RE-VIEW ELECTRONIC TUBES

237 London Road, West Croydon, Surrey. Tel. 01-689 7735


Available now!

The new Mullard data book for 1970

Quick! get up-to-date with the latest information about Mullard semiconductors, valves, television picture tubes and components.

For easy flick-through location, each section of this pocket-sized data book is colour-coded.

just 4/-
(20p)

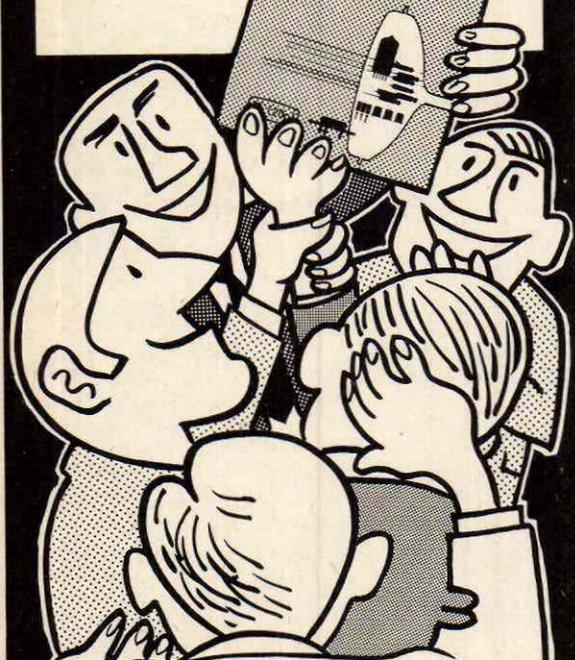

Get your copy from your local TV retailer, Bookshop or cash with order, including p.p. 4/9 (24p), direct from Mullard Limited.

Mullard

Mullard Limited, Mullard House,
Torrington Place, London, WC1

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1R5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94.
Set of 4 for 18/6, DAF96, DF96, DK96, DL96, 4 for 27/-.

0Z4	4/8	19BG6G17/8	DK92	8/6	EH80	6/8	PCL82	7/8	UBF80	5/9	
1A7GT	7/8	20F2	13/6	DK96	7/3	EL33	9/9	PCL83	12/-	UBF89	6/9
1H5GT	7/3	20P3	11/9	DL35	5/-	EL34	9/6	PCL84	7/6	UC84	7/6
1N6GT	7/9	20P4	18/6	DL92	5/9	EL41	11/-	PCL85	8/-	UC85	7/8
1R5	5/9	25L6GT	5/-	DL94	6/3	EL54	4/9	PCL86	3/9	UCF80	7/8
1R5	4/3	25A9T11	8/6	EL90	7/8	EL90	4/6	PEN44	12/6	UCH42	12/6
1T4	2/9	30C1	8/6	DY86	5/9	EL500	12/6	PFL200	11/9	UCH81	6/6
3S4	5/9	30C15	13/-	EY87	5/9	EM80	7/6	PL36	9/9	UCL84	11/9
3V4	6/3	30C17	16/-	EAB080	6/6	EM81	7/6	PL81	8/9	UCL83	11/9
5Y3GT	5/9	30C18	14/-	EAF42	10/-	EM84	6/9	PL81A	10/6	UF41	10/8
8Z4G	7/6	30F6	19/-	EB91	2/3	EM87	7/6	PL82	6/6	UF80	7/-
6/30L2	12/-	30FL1	14/-	EB033	8/-	EY61	7/3	PL83	6/6	UF85	6/9
6AL5	2/8	30FL12	14/8	EB041	9/6	EY86	6/6	PL84	6/6	UF89	6/9
6AM6	2/9	30FL14	14/9	EBF80	6/9	EZ40	8/-	PL600	13/-	UL41	11/9
6AQ5	4/6	30L1	6/6	EBF89	6/3	EZ41	8/-	PL604	13/6	UL44	20/-
6AT6	4/-	30L15	14/-	ECC81	3/9	EZ80	4/8	PL608	23/8	UL84	7/-
6AU6	4/6	30L17	15/6	ECC82	4/9	EZ81	4/9	PM84	7/6	UM84	6/6
6BA6	4/6	30P4	12/-	ECC83	7/-	EZ82	3/9	PX25	12/-	UY41	7/6
6BE6	4/9	30P12	13/6	ECC85	5/-	GZ34	9/9	PY32	10/-	UY85	5/9
6BJ6	8/6	30P19	12/-	ECC91	3/-	KT61	9/9	PY33	10/-	VP4B	10/9
6BW6	13/-	30PL1	14/9	ECC80	12/-	KT66	16/9	PY81	5/3	WL19	7/-
6F13	3/6	30PL13	17/6	ECCF80	6/8	N78	17/6	PY82	5/3	Z77	2/9
6F14	9/-	30PL14	18/6	ECCF81	6/6	PALC80	7/-	PY83	5/9		
6F23	14/3	35L6GT	8/6	ECH45	6/-	PC86	10/3	PY88	6/9	Transistors	
6F25	13/-	35W4	4/6	ECH42	13/6	PC88	10/3	PY800	7/6	AC107	3/6
6J6	3/-	35Z4GT	5/-	ECH81	5/9	PC96	8/6	PY801	7/6	AC127	2/6
6K7G	2/6	807	9/-	ECH83	3/3	PC97	8/6	R19	6/6	AD140	2/6
6K8G	2/9	6063	12/6	ECH84	7/6	PC900	7/6	R20	2/6	AR115	3/6
6L18	8/-	ACVP2	10/-	ECL80	7/-	PC84	6/6	U25	13/-	AF116	4/-
6N7GT	4/3	AZ31	9/6	ECL82	6/9	PC85	6/-	U26	12/-	AF117	4/-
6V6G	3/3	B729	12/6	ECL83	8/6	PC88	9/-	U47	13/6	AF125	3/6
6V6GT	6/6	CCH35	13/6	ECL86	8/-	PC88	10/6	U49	13/6	AF127	3/6
6X4	4/3	CL33	18/6	EF37A	6/6	PC189	11/6	U78	4/3	OC26	5/-
6X5GT	5/9	CF31	6/9	EF39	4/9	PCF80	6/6	U11	15/6	OC44	5/6
10F1	14/-	DAC32	7/3	EF41	10/9	PCF82	6/6	U193	5/6	OC45	2/3
10F18	7/-	DAF91	4/3	EF80	4/6	PCF86	10/6	U251	14/6	OC71	2/6
10P13	12/-	DAF96	7/3	EF85	6/8	PCF200	13/6	U301	10/6	OC72	2/6
12AT7	3/9	DF33	7/9	EF86	6/2	PCF800	13/6	U329	14/6	OC75	2/6
12AU6	4/9	DF91	2/9	EF89	5/3	PCF801	6/9	U801	19/6	OC81	2/3
12AU7	4/9	DF96	7/6	EF90	5/9	PCF802	6/-	U13C	6/6	OC81D	3/6
12AX7	4/9	DH77	4/9	EP94	4/6	PCF805	14/-	UAF42	10/3	OC82	2/3
12K8GT	7/3	DK32	7/3	EF183	5/9	PCF806	12/9	UB41	6/6	OC82D	2/3
12SN7GT	6/6	DK91	5/9	EF184	5/6	PCF808	14/9	UBC41	9/-	OC170	4/6

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDE, YORKS

Tel. Heckmondwike 4285

AW48-80 TV Tubes good picture—no guarantee £1 plus 12/- carriage.

Aircraft Sighting Head with Gyro Unit. Condition Fair 18/6, carriage B.R.S. 12/-.

Small 12-way Plug and Socket, 1/6 each, p.p. 1/-, 15/- doz., p.p. 3/6 Ex unit.

Panel of 19 mixed pots, 5/- post paid. Ex unit.

Panel of Resistors and Condensers 8/- per doz., post paid. Ex unit.

Bombsight—Computers containing a large selection of gears. A delight for the Model Maker. 55/- carriage paid.

Complete untested 17 inch TV Sets 12 channel 50/-, 15/- carriage. Small Sub Chassis containing small 12-way Plug and Socket.

Few Resistors and Condensers, 5/-, p.p. 1/6.

Speakers removed from T.V. Sets. All PM and 3 ohm. 6in. round 3/-, p. & p. 3/-; 6 for 24/-, post paid, 5in. round 3/-, p. & p. 3/-; 6 for 24/- post paid, 7+4in. 5/-, p. & p. 3/-; 6 for 34/- post paid. Slot Speakers 8x2 1/2in. 5/-, p. & p. 3/-; 6 for 30/- post paid.

Reclaimed T.V. Tubes, with 6 months' guarantee 17in. Type AW43/80, AW43/88 40/-, MW43/69 30/-, 14in. Type 17/-, All Tubes 12/- carriage.

Silicon Rectifier 500mA 800 PIV, 2/6 post paid 24/- per dozen, post paid.

Jap Earpiece. Magnetic 8 ohm. Small and Large Plug 1/11 post paid.

G.P. Diodes 3/6 per dozen, post paid.

Top Grade Mylar Tapes, 7in. Standard 11/6, 7in. Long Play 14/-, 5in. Standard 7/9, 5in. Long Play 10/-, plus post on any tape 1/9.

VALVE LIST—Ex Equipment, 3 month's guarantee. Single Valves Post 7d., over 3 Valves p. & p. paid.

ARP12	1/6	PCL82	4/-	6B8	1/8
EB91	9d	PCL83	5/-	6BW7	2/6
EF85	3/-	PL38	6/-	6K7	1/9
EBF80	3/-	PL81	4/-	6U4	5/-
EC081	3/-	PY31	5/-	6P28	5/-
ECC82	3/-	PY81	1/6	10P13	2/6
ECC83	4/-	PY32	1/6	185BT	3/6
ECL80	1/6	PZ30	5/-	20D1	3/6
EF50	1/-	U191	5/-	20P1	5/-
EF80	1/6	U281	5/-	20P3	2/6
EF91	9d	U282	5/-	30PL1	5/-
EY86	5/-	U301	5/-	30P12	2/6
PC084	2/-	U329	5/-	30F6	5/6
PCF80	2/-	U351	5/-	30FL1	5/-
				6/30L2	5/-

PRACTICAL TELEVISION

VOL 20 No 8
ISSUE 236

MAY 1970

CONSTRUCTIONAL PROBLEMS

READERS of Practical Television are a pretty loyal bunch; so are the staff of the magazine. And there are times when in the common effort it behoves both staff and readers to bear with each other. The cause of this heart call is the single-standard TV receiver we launched in the March issue, with three motives in mind: (1) as an academic exercise for readers who like to investigate circuits and their applications, (2) as an ideas source for the experimenter who may wish to develop his own ideas around sections of the P.T.V. design, and (3) as a complete constructional project for those wanting to build a first-class modern receiver.

We have quite frankly been overwhelmed by the number of readers falling into the third category! And the suppliers of the i.f. panel have likewise been taken by surprise by the demand. Consequently supplies have run short (large quantities of these i.f. panels have already been shifted). To add to the trouble the suppliers (Manor Supplies) are now in the process of moving premises. Some readers will therefore be subject to delay and for this everyone concerned offers their apologies. New supplies will become available, although these may not necessarily be exact replicas of the units used in the prototype. We will keep readers informed of the situation.

The manufacturer and supplier of the special mains transformer was inadvertently given as Olympic Electronics Ltd. This should have read Olympic Transformers Ltd. (at the address given correctly in the March issue). We apologise to readers and to the two companies concerned for any inconvenience this slip has caused.

We have also been asked to mention that the line output transformer is in stock at D. & B. Television (Wimbledon) Ltd., 80 Merton High Street, London, S.W.19. Finally we would like to mention that the complete chassis metalwork is now priced at £6 17s. 6d. including postage and packing (from the supplier mentioned).

Most of the trouble has been due to our aim to make construction of the receiver as easy and inexpensive as possible, which means using surplus units (such as the tuner and i.f. strip). Unfortunately these items not being catalogue pieces are liable to become in short supply. We are doing our best to remedy the situation and hope that readers will understand the difficulties.


W. N. STEVENS, *Editor*

THIS MONTH

Teletopics	340
Surplus I.F. Panel for the Constructor <i>by David Robinson</i>	342
Fault-Finding Focus—A Detailed Look at Colour Receiver Chrominance Circuits <i>by S. George</i>	346
Strobe-Trigger Timebase Unit— Part 2 <i>by Martin L. Michaelis, M.A.</i>	350
DX-TV <i>by Charles Rafarel</i>	356
Servicing Television Receivers— Bush-Murphy TV161U-V1910U series continued <i>by L. Lawry-Johns</i>	357
Aerials for the 70s <i>by K. Royal</i>	360
Single-Standard 625-Line Receiver for the Constructor—Part 3 <i>by Keith Cummins</i>	366
Regular Long-Distance TV Reception—Part 2 <i>by K. E. G. Pitt, B.Sc.</i>	370
Underneath the Dipole <i>by Iconos</i>	372
Transistors in Timebases—Part 7— Field Oscillators <i>by H. W. Hellyer</i>	374
Your Problems Solved	378
Test Case 90	379

THE NEXT ISSUE DATED JUNE WILL
BE PUBLISHED MAY 21

TELETOPICS

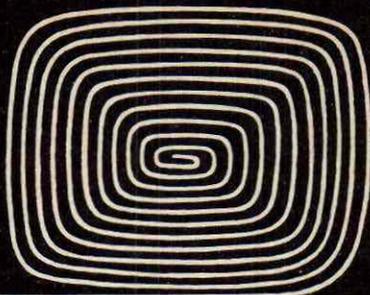

RESULTS FOR 1969

With colour television set deliveries at 25,000 for December the total for 1969 rose to 154,000, an increase of 27 per cent over 1968. Monochrome set deliveries for December were 143,000, bringing the total for 1969 to 1,673,000, a fall of 5 per cent.

On the radio side 1969 was a poor year with radio set deliveries down by 28 per cent, car radio deliveries down 12 per cent and radiogram deliveries down 11 per cent.

PLASMA DISPLAY SYSTEM

Fujitsu Ltd. of Japan in conjunction with the University of Illinois have recently developed a thin, bright and cheap plasma (ionised gas) display system which may be the forerunner of a new generation of display devices for computers, television sets and other electronic applications. The arrangement consists of a combination of three sheets of glass panels with two internal gaps filled with a mixture of 95 per cent argon and 5 per cent nitrogen gas and is about a centimetre thick. Plus and minus electrodes are attached to the outer panels to ionise the gas and a small hole in the middle panel is thus illuminated to produce an image which is claimed to be twice as bright as the average c.r.t. display.

GEC-SOBELL SERVICE PHONE

The GEC-Sobell radio and television service department at East Lane, Wembley, Middx. has been given a new telephone number—01-904 0171.

FRINGE UHF AERIAL FROM AERIALITE

The SP50 Golden Gain Supreme, a fringe u.h.f. array, is the latest addition to the Aerialite range of aerials and features a very distinctive design. A pair of folded dipoles mounted in the same plane and carefully spaced and dimensioned is used for increased gain in combination with a precisely calculated director structure consisting of sixteen directors of S configuration. The aerial can be seen illustrated on page 360. The S form of the directors when incorporated into a scientifically designed director chain not only ensures the correct phasing to increase the gain and capture area but also increases the total bandwidth percentage. The mesh-type reflector is aperiodic—non-resonant—across the bandwidth to improve the bandwidth characteristic, the placing and dimensions of the holes and slots playing an important part in these anti-resonance characteristics. The recommended retail price is £6. Aerialite Ltd. are at West Heath, Congleton, Cheshire.

US SATELLITE TV

Details of domestic satellite television transmission experiments being carried out in the US have been announced by the US Corporation for Public Broadcasting. NASA have agreed to the use of satellite ATS3 for these tests which involve transcontinental programme transmissions. The aim is to investigate the technical problems and costs involved.

BATC 1970 CONVENTION

The two-day British Amateur Television Club convention to celebrate the Club's 21st Anniversary is being held at Churchill College, Cambridge, on July 25th-26th. The convention is primarily intended for BATC members but a warm welcome will be extended to anyone interested in amateur television. Those interested should write to D. S. Reid, 71A Rose Valley, Brentwood, Essex.

SENSITIVE PLUMBICON TUBE

A new, sensitive 1in. Plumbicon tube for industrial CCTV use is announced by Mullard. The type XQ1071 tube gives acceptable pictures under normal lighting conditions, avoiding the need for the flood-lighting often required with vidicon tubes. The XQ1071's rapid response greatly reduces smear when the camera is focused on moving objects. Resolution is 600 lines, focusing and deflection magnetic, maximum operating voltage 1,100V, heater supply 6.3V at 95mA and capacitance between target and other electrodes only 4.5pF. The XQ1071 is intended for monochrome cameras but other versions suitable for use with red, green and blue light are available.

STEPS AGAINST PIRATE TV

W. European countries have been preparing plans to curb the intentions of pirate TV broadcasters to transmit from a plane circling over the North Sea. John Stonehouse, Minister of Posts and Telecommunications, has stated that concerted action would include withdrawal of aircraft registration, denial of airport facilities and legal measures against the individuals involved. Assurances of cooperation have been received from every W. European country within practicable flying distance of the North Sea.

TV LINK TO AUSTRALIA

A permanent live TV picture link to Australia has now been opened via satellite to a station at Ceduna, South Australia. The signal path is via the Goonhilly station to the Indian Ocean Intelsat III satellite.

SURPLUS IF PANEL

for the constructor

DAVID ROBINSON

THE receiver described in my article *A Constructor's 625-line Receiver* in the January issue was built about two years ago. Since then the Thorn conversion panel used in the set has become difficult to obtain. However another excellent conversion panel, made by GEC, is now available from Manor Supplies, price 32/6 (plus 4/6d post and packing). The panel was originally used on the Sobell ST282DS/GEC BT452DS series. This article describes how to use this panel and also how to improve it considerably in two respects, namely sound quality and d.c. restoration.

Since the constructor will no doubt already have a 405-line receiver, if this is still required for BBC-1 and ITV in his area it will be assumed that the unit is to be used on 625 only (although its circuits are dual-standard).

TUNERS

The use of a valve u.h.f. tuner is not recommended since not only are they much less reliable than transistor types but as they have a much higher noise level than transistor types the money saved on a valve tuner will have to be spent on the aerial.

There have been at least three types of transistor tuner available. Manor Supplies had two types, an integrated tuner complete with push-button mechanism at £4 10s 0d or the same tuner less the mechanism at £2 10s 0d. The former type is recom-

mended for ease of operation by non-technical families. Radio and TV Components (Acton) Ltd. had a two-transistor u.h.f.-only tuner at £2 10s 0d. This is also continuously tuned but is considerably easier to link to a drive mechanism than the second tuner mentioned. On the other hand unlike the integrated tuners it has no i.f. gain.

You will also need a set of valves for the i.f. strip and an old set to convert. Methods of timebase conversion have been described in previous issues of PRACTICAL TELEVISION.

IF STRIP CONNECTIONS

Figure 1 shows the layout of the various tags on the chassis. These are connected up to the parent receiver as listed under Fig. 2. Also link the chassis to the main receiver by a short, thick cable.

The EH90 heater should be placed near the lower potential end of the heater chain.

The tuner output should be connected to the two-pin socket on the side of the chassis, but be sure to remove the large 5.6kΩ resistor R18 (assuming that a transistor tuner is used). The volume control is connected to the three-pin socket provided—bottom to the braiding and top to the inner of the screened wire and slider to the 47kΩ resistor R96.

TESTING

Having adjusted the main dropper in the receiver to the correct value (easily found by Ohm's Law) the unit may be tested. If the integrated tuner is used

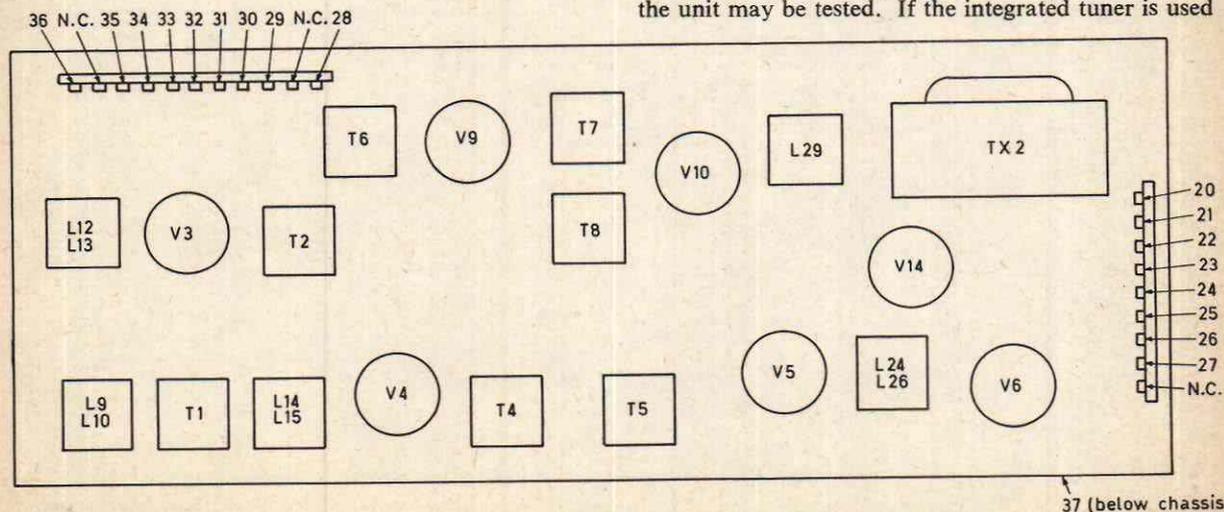


Fig. 1: Top layout of the panel, showing the tag connections.

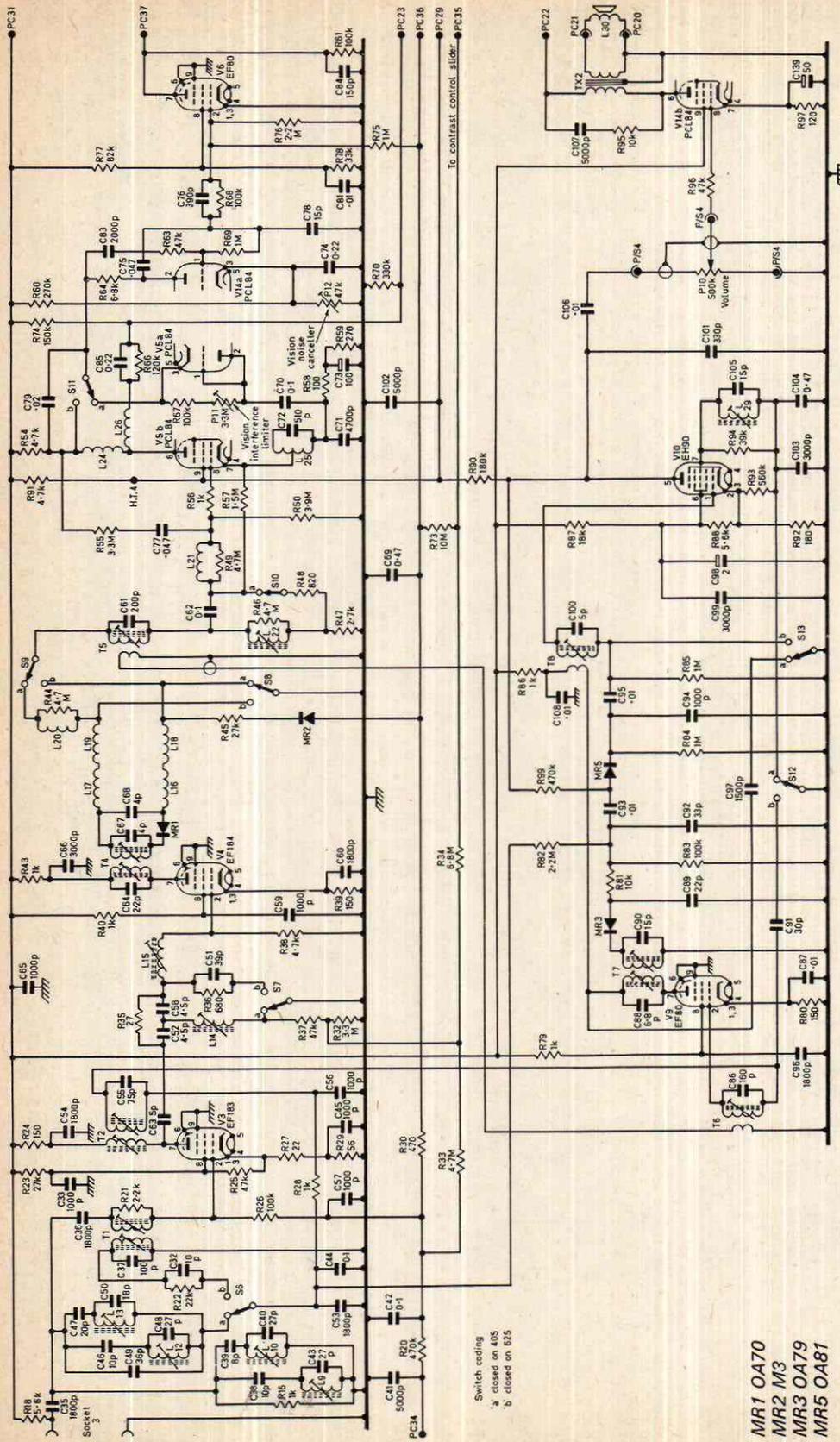


Fig. 2: Complete circuit of the panel before modification. Note that P10 is not supplied with the panel.

- MR1 OA70
- MR2 M3
- MR3 OA79
- MR5 OA81

- Tag number
- 20, 21
 - 22
 - 23
 - 24
 - 25-27

- Connection
- Loudspeaker
 - H.T. (not more than 200V)
 - C.R.T. cathode
 - With 32, EH90 heater (see below)
 - Other heaters (low potential end)

- 28 Not used
- 29 To 50µF 250V smoothing capacitor
- 30 Not used
- 31 H.T.
- 32 See 24
- 33 Heaters (high potential end)
- 34 Not used

- 35 To slider of contrast control (500kΩ)
- 36 To 35 via 3-3MΩ
- 37 To H.T. via 100kΩ and to time-bases (sync feed) via isolating capacitors

Switch coding
 'a' closed on 605
 'b' closed on 625

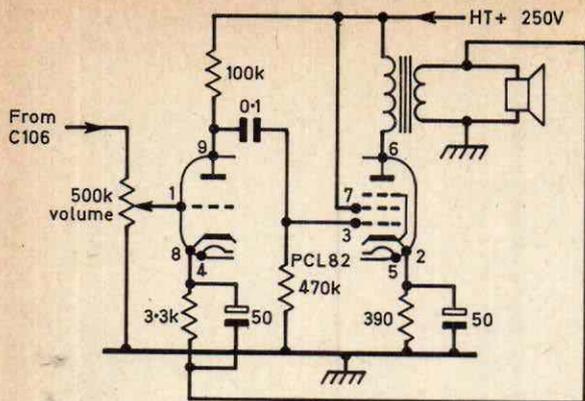


Fig. 3: Suggested audio amplifier circuit.

the connections are shown in Fig. 7. For u.h.f. the rounded end of the band switch bar should be pushed in as far as it will go. With this type of tuner the set will also work on 405.

The paxolin switch on the i.f. strip should be set towards the input end for 625, but not too far or it will short to its mountings. It is convenient to remove the metal operating bar and fasten the switch in the 625 position with adhesive tape.

It should be stressed that due to the use of band-pass couplings the alignment of this unit is very critical (in comparison to the Thorn unit, unduly so) and no adjustment should be attempted.

MODIFICATIONS

The unit gives a very good overall performance as it stands but at the expense of losing the 405-line facility—which will not usually be required anyway—the performance can be considerably improved as mentioned at the beginning of this article. The space and valve sections necessary for this are made available by dismantling the original interference limiter circuits (V5a and V14a) which I have not found to be necessary even though I live on a main road with my attic-mounted aerial directly facing the road. The entire circuitry from C79 through to C76-R68 inclusive should be removed and pins 1, 2 and 3 of V5 and V14 completely cleared of leads. The video amplifier V5b is then reconnected to the sync separator V6 by means of an $0.1\mu\text{F}$ capacitor and $10\text{k}\Omega$

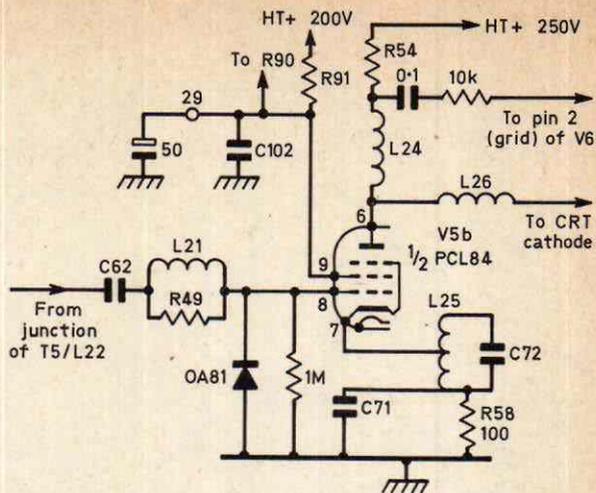


Fig. 5: Modified video amplifier circuit.

resistor in series from the junction of L24 and R54 to V6 pin 2.

The unit should then be retested.

DC RESTORATION

This is best done in two stages, first the replacement of the mean-level a.g.c. system with a true signal-level a.g.c. circuit and secondly the necessary changes in the video amplifier.

AGC

The circuit of my a.g.c. system is shown in Fig. 4 together with the necessary changes to the vision detector circuit. Layout is fairly non-critical except that the connections to the 1kpF decoupling capacitor and the OA81 gating diode must be as short as possible or the i.f. strip may go unstable. Although the circuit is quite simple it will provide more than enough control for all reception conditions.

The operation of the circuit is as follows. The required peak level of detector output is set by the contrast control which provides via the detector network a positive bias on the cathode of the OA81 gating diode. When the signal strength is such that the detector output is greater than the preset level

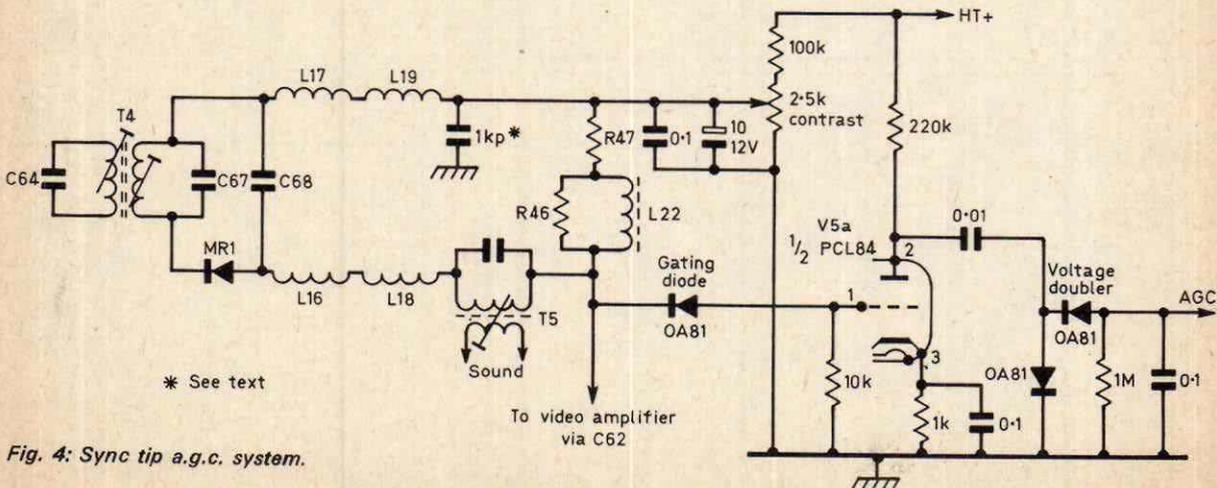


Fig. 4: Sync tip a.g.c. system.

fault finding

S. GEORGE

FOCUS

A DETAILED LOOK AT COLOUR RECEIVER CHROMINANCE CIRCUITS

THE chrominance amplifier section of a colour receiver consists of a two-stage amplifier centred on 4.43MHz, the chrominance subcarrier frequency. There is however probably greater divergence from one make to another in this part of the receiver than in any other section of a colour set. The stages may be tuned or untuned and use valves or transistors while the arrangements made for colour-burst blanking and the manner of the feed to the colour-burst amplifier all differ widely.

The chrominance stages must fulfil five main functions. These are: (1) To amplify the tapped off chroma signal to the level required for subsequent application along with the locally generated 4.43MHz subcarrier to the B-Y and R-Y synchronous detectors. (2) To incorporate a.c.c. (automatic chrominance control) to maintain a constant output level and to compensate for variations in fine tuning which could greatly affect colour intensity. (3) To remove or "blank out" the colour-burst signal to permit correct operation of the colour-difference output clamps and avoid putting a colour cast on scenes of low colour content. (4) To incorporate a means for manually varying the colour intensity or saturation. This is sometimes electrically or mechanically linked to the contrast control so that optimum luminance/chrominance balance is maintained throughout the contrast range. (5) To provide a suitable feed for the burst-signal channel.

Chroma Take-off Point

The take-off point for the chroma signal is commonly a video preamplifier stage in which case the chroma signal is taken via a high-pass filter so that the lower frequency (luminance) component of the composite waveform will be attenuated. Such filters are usually simple RC or LC series combinations with the chroma signal developed across the resistor or inductor.

Although the system just outlined is widely used it is not universal practice. In Philips receivers fitted with the G6 chassis the signal is derived from the collector of the second vision i.f. amplifier. To extract the chroma information from an i.f. signal it is necessary to employ a separate detector and in these Philips models the tapped-off i.f. signal is first applied to a separate transistor amplifier with the output being applied to a diode demodulator to develop the required chroma content. The signal is then fed to a two-stage valve chrominance amplifier comprising a variable- μ EF183 and straight EF184 with an interstage coupling blanked off

during colour-bursts by a switching diode. The idea is to detune the coupling and the arrangement is shown in Fig. 1. A positive-going pulse from the line output stage switches D1 on during the burst-signal period each line so that increased damping is applied to the primary.

A third method of deriving the chroma signal from the composite luminance-chroma signal is to use a separate sound-chroma detector. BRC and certain single-standard models use this technique. In both the dual- and single-standard BRC chassis the demodulated chroma signal is applied via a tuned acceptor circuit to an emitter-follower stage which feeds the untuned chroma amplifier stage(s) (only one chroma amplifier proper is used in the single-standard 3000 chassis). A complex filter with 1.57MHz (sound-chroma beat) and 6MHz (inter-carrier sound) rejectors and an acceptor circuit tuned to 4.2MHz is interposed between the emitter-follower and first chroma stage in the 2000 dual-standard chassis. The emitter-follower stage is on the i.f. board and the chroma stages of course on the decoder board.

GEC Circuit

However, to get down to detail, Fig. 2 shows the circuits used in the GEC dual-standard colour TV range. The composite video signal—luminance and

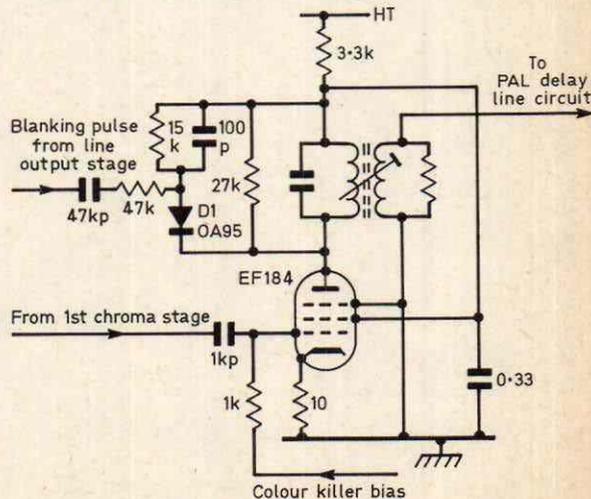


Fig. 1: Second chroma stage in the Philips G6 colour chassis, showing the burst-blanking system.

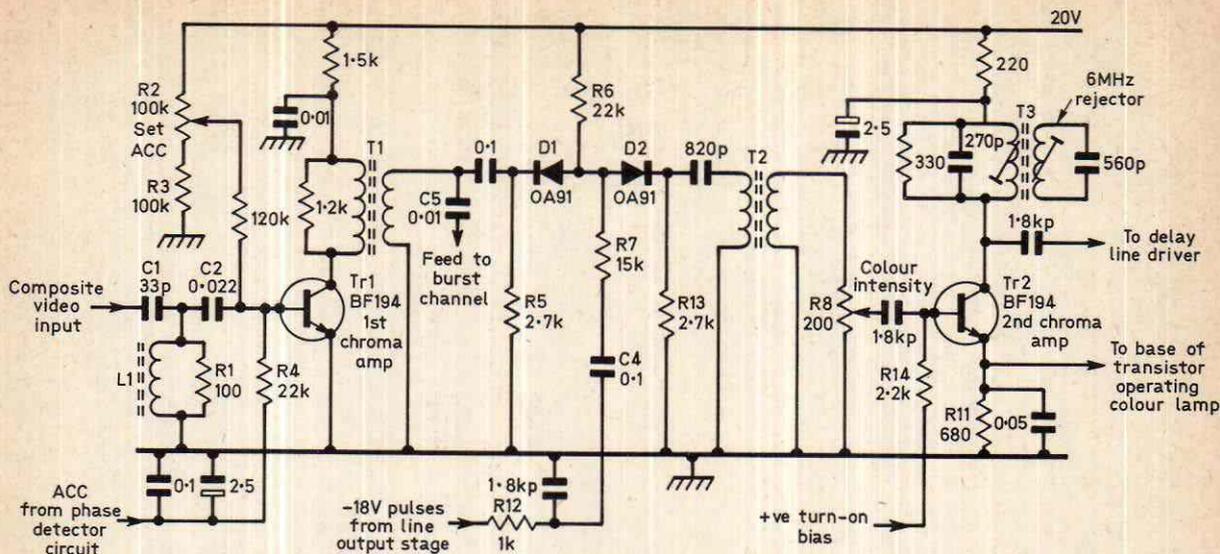


Fig. 2: Chroma amplifier stages in the GEC dual-standard colour chassis.

chrominance—is tapped from the emitter of a video phase-splitter stage. C1, R1 and L1 form a high-pass filter since the increasing reactance of L1 and the decreasing reactance of C1 to the higher frequency chroma content greatly attenuates the lower luminance frequencies. Tr1 bias is dependent on two factors, (a) the setting of R2 which determines the no-signal fixed bias and (b) the positive a.c.c. bias derived from the colour-burst amplifier. Since the amplitude of the colour-burst signal is directly proportional to signal strength a rectified sample provides a d.c. potential accurately related to sub-carrier amplitude—unlike mean-level monochrome a.g.c. systems which produce a control potential related to *average* video content.

Burst Blanking

Amplified signals are developed across the primary of T1 with the secondary signal fed two different ways, (a) via the burst-blanking diodes D1 and D2 to the primary of T2 and (b) via C5 to a separate burst amplifier which in turn feeds a second burst amplifier also via blanking diodes. The diodes in the chroma circuit are conductive during the line scan period and non-conductive during the bursts, so allowing only the chroma signal through, while in the colour-burst circuit the opposite applies, only the burst signal ending up at the burst detector (the a.p.c. detector in the subcarrier regenerator circuit).

Confining our attention to the chroma circuitry, however, the positive current drain through R6, D1 and D2 and through R5 and R13 to chassis keeps the diodes conductive throughout the line scan period. During the blanking period at line termination a $-18V$ pulse from the line output stage is timed to reverse bias the diodes—being applied to both anodes via R12, C4 and R7—and thus prevents transmission of the burst signal to the second chroma amplifier Tr2. Colour intensity is manually adjustable by means of the 200Ω potentiometer R8 shunted across T2 secondary.

Following general practice the second chroma

amplifier Tr2 has no fixed positive bias and is rendered operative only by the rectified ident signal which is applied to its base via R14 as a turn-on bias when a colour transmission is being received. This is the colour-killer action: it ensures that on monochrome reception the chroma channel is cut off to avoid spurious colour patterning due to noise.

Colour Beacon

An interesting point of detail in this circuit is the colour "beacon" light. On monochrome there is no voltage drop across Tr2 emitter resistor R11. On colour reception, however, when Tr2 is conducting its emitter voltage rises to between 3 and 8V. This voltage forward biases a BC107 transistor in series with a "colour on" indicator lamp which glows to indicate colour signal reception. This can be a valuable clue when there is complete colour loss since if glowing it indicates that all the circuitry necessary for the production of the turn-on bias—i.e., the burst channel and ident circuits—is in order and that the complete loss of colour is therefore due to loss of local oscillator signal or a defect associated with the chrominance output circuitry since the first chroma stage must be operative to produce the feed for the burst channel which subsequently provides the input for the ident circuits.


The output from the collector of the second stage Tr2 is capacitively fed to a PAL delay line driver stage.

Decca CTV25

Figure 3 shows another example of transistor chroma circuitry, as used in the Decca Model CTV25. This differs from the previous example in that colour-burst blanking is achieved at the second chroma stage instead of in the interstage coupling while the turn-on bias for this stage is clamped at optimum value by an additional diode D1.

C1 and L1 form a high-pass input filter designed to attenuate the luminance component of the composite input signal in similar fashion to C1, R1 and L1 in the GEC circuit. A 6MHz intercarrier rejector

Fig. 4: Pye-Ekco chroma circuits with electrical link between the saturation and contrast controls for optimum colour-luminance balance.

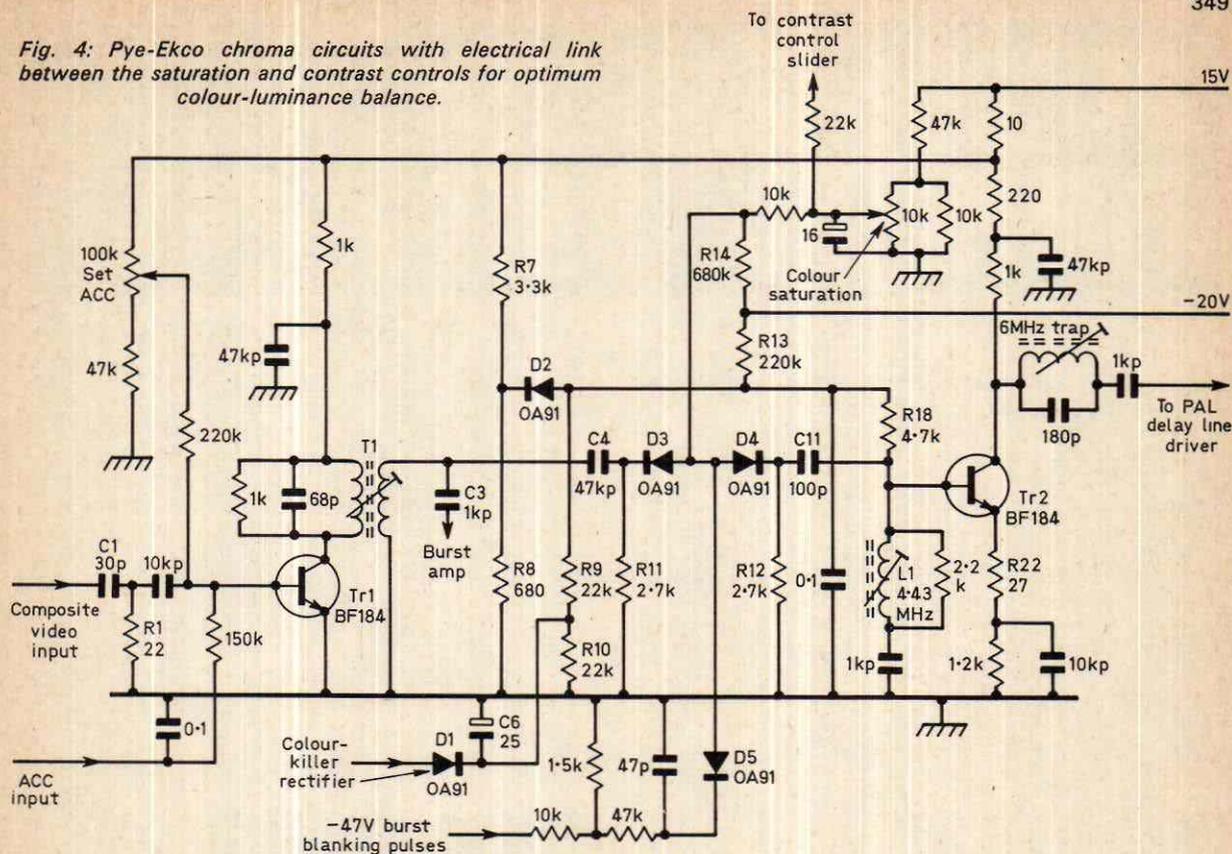

potentiometer with R12 as the lower section. Being arranged back-to-back in this manner the non-linearity of the diodes, which would otherwise be especially evident at low-signal levels, is cancelled out.

Colour-killer Action

As in other receivers the second chroma stage is turned on by application of a bias derived from the ident stage during colour reception, but the method is rather more involved in this instance. The base of Tr2 is returned via R18 to the junction of R9 and R13 and although the top of R14 takes a small positive potential from the saturation control this is outweighed on monochrome by the -20V feed to the junction of R13 and R14. The positive potential at the junction of R7 and R8 applied to D2 cathode cannot bias Tr2 on since it reverse biases D2. On colour reception however D1 produces a d.c. output of about 7V across smoothing capacitor C6 by rectifying the ident signal and this turns Tr2 on. It also makes D2 conduct by making its anode more positive than its cathode. Tr2 bias is then clamped to the constant value of about 3V produced at D2 cathode by the fixed potential divider R7 and R8.

As well as providing a means for electronically controlling the degree of interstage coupling, the junction of D3 and D4 also provides a convenient injection point for a negative-going pulse train from the line output transformer via D5 to bias D3 and D4 off during burst periods to provide burst blanking.

L1 is tuned with the base circuit capacitance of Tr2 to 4.43MHz and the stage gain is stabilised by the inclusion of an undecoupled resistor R22 in the emitter lead. The output at Tr2 collector is then applied to a delay line driver via a 6MHz rejector which prevents any intercarrier sound signal being passed to later stages.

Servicing


Chrominance amplifiers give little trouble in practice and the faults that do arise are mostly due to high-resistance or open-circuit diodes or a circuit disconnection.

When complete colour loss develops so that the possibility of a chroma amplifier failure is present undoubtedly the first move must be to over-ride the colour-killer action to ensure that the second stage, whether valve or transistor, is not biased off. If this action restores normal reception clearly the colour-killer circuitry is at fault but if there is no change in results there could be zero output from the local 4.43MHz oscillator or buffer stage or a fault in the chrominance output circuitry. First stage failure can be discounted since its operation is necessary to provide a feed to the colour-burst circuitry which in turn gives an output to the ident stage which develops the turn-on bias for the second stage.

As with most colour-receiver faults, scope testing will quickly locate a defective stage after which conventional voltage and resistance checks should soon identify the faulty component.

SERIES TO BE CONTINUED

STROBE-TRIGGER TIMEBASE UNIT

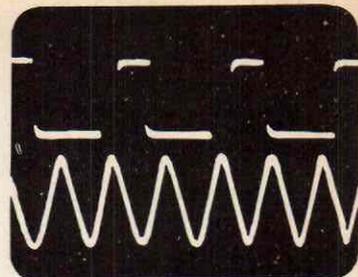

PART 2

THE master multivibrator circuit module employs a conventional free-running multivibrator with capacitive cross-coupling from the collector of each transistor to the base of the other one (Tr1 and Tr4). This produces a squarewave at each collector and a ramp at each base. The coarse frequency control is a switch (S1) selecting various cross-coupling capacitors while fine frequency control is provided by a variable base bias resistor (VR1) in one of the transistor base circuits. The squarewave pulse and ramp durations for this transistor are roughly equal to those of the other transistor when the fine frequency control is at its maximum setting, or about three times as long when the fine frequency control is at its minimum setting. This is shown by the respective top traces of oscillograms D(a) and C(b).

The ramp at the base of the transistor (Tr4) whose base bias resistor—and thus the pulse and ramp durations—are varied is applied as variable bias (VR2) to the transistor (Tr5) producing the delayed strobe trigger. The duration of this ramp is always from the end of one positive pulse of the master pulse waveform—oscillogram C—to the start of the next positive pulse. Depending on the bias for the threshold discriminator selected with the manual gate delay control VR2 the strobe trigger pulse may be produced at any desired point on the base ramp.

Oscillograms C show the relative timing of the master pulse and the final strobe ramp produced by the delayed strobe gate. By adjusting the manual gate delay control the start of the strobe ramp may be brought to lie at any desired point between almost immediately after the termination of the master pulse—oscillogram C(a)—and just before the start of the next master pulse—oscillogram C(c). Oscillogram C(b) shows the midway setting of the strobe gate delay control.

Note that the adjustments are independent of the signal frequency. The master multivibrator is tuned and synchronised to the signal to be displayed in the same manner as used for any ordinary timebase, and quite independently of the strobe gate delay and strobe gate width controls. This greatly simplifies operation as has already been mentioned. Any given setting of the strobe gate delay control represents a constant phase position of the start of the strobe ramp independent of the signal frequency.

The strobe gate width and thus the strobe ramp duration can be selected quite independently as shown by the set of oscillograms B(a-c). Here the strobe gate delay control has been set about midway so that the strobe gate and ramp always commence midway between the end of one master pulse and the start of the next one (any other phase setting would serve just as well for this demonstration).

Martin L. Michaelis M.A.


The duration of the strobe ramp is determined solely by the gate width setting which has been varied progressively in the oscillograms B(a-c).

Note that whereas the *start* of the strobe gate and strobe ramp must lie between two master pulses the ramp *run* can always be made to coincide partly or entirely with a master pulse by moving its start close to the start of the next master pulse. This is demonstrated most clearly in oscillogram C(c). It is important for slaved transient studies discussed later.

SYNCHRONISATION

We have seen that the function of any timebase synchronising circuit is to speed-up the timebase

A EFFECT OF GATE WIDTH CONTROL S5

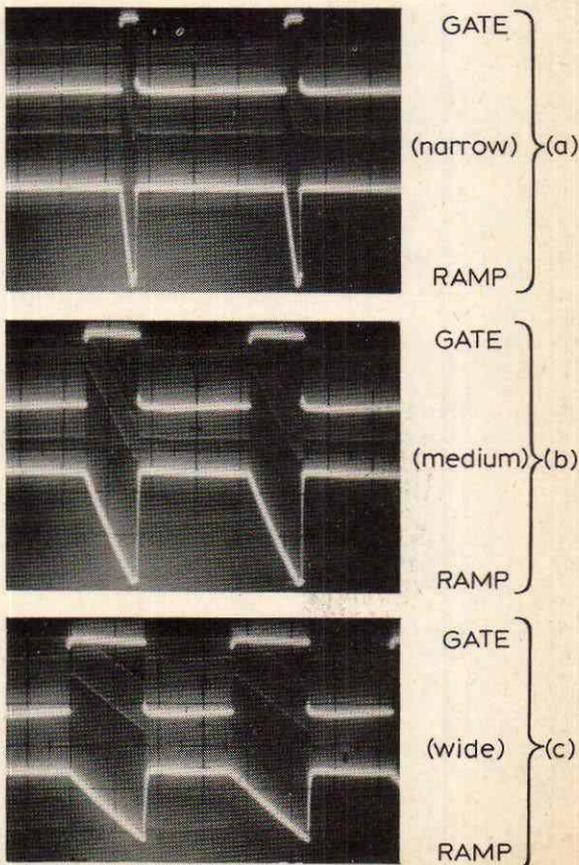

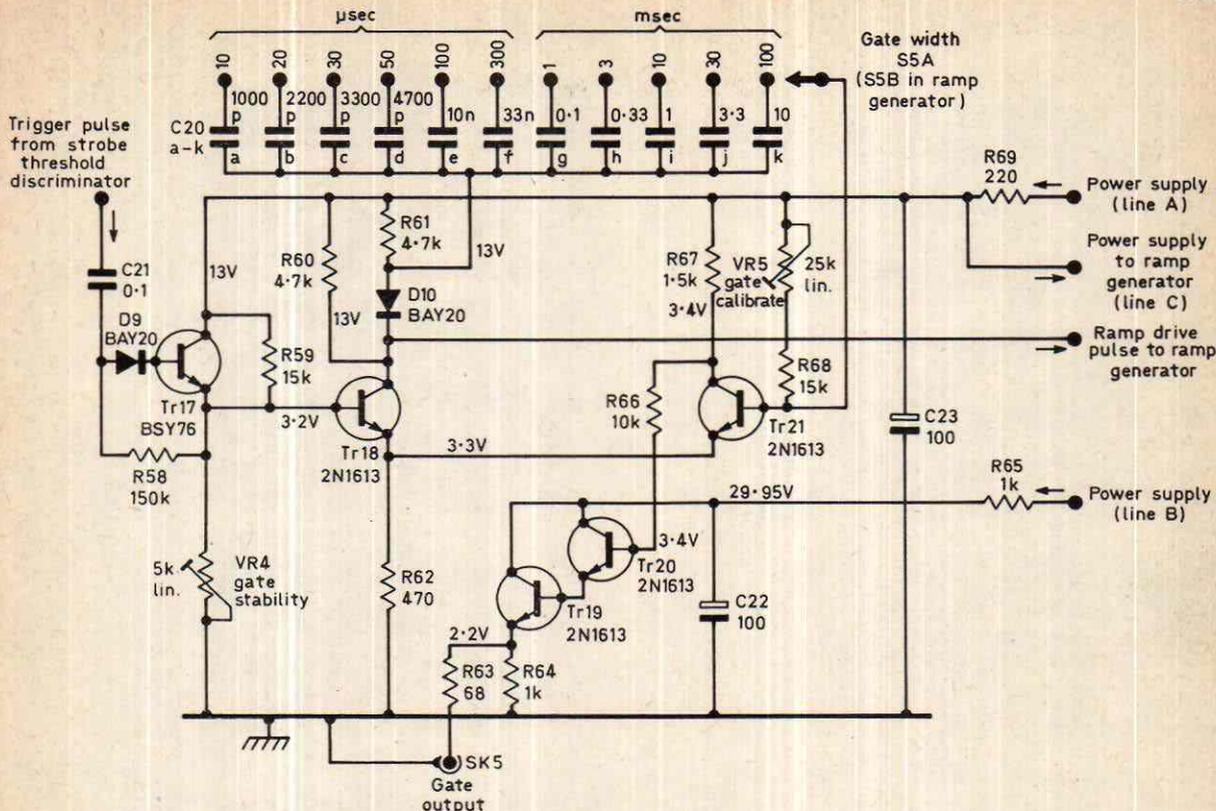


Fig. 5: Circuit diagram of the strobe gate generator. Voltages were measured with the master multivibrator off, gate width 100mS, gate delay maximum, zero sync and in the trigger setting, using a valve voltmeter.

oscillator which is otherwise, when running free, slightly too slow in relation to a whole number of cycles of the signal waveform. The type of synchronisation adopted for the master multivibrator in this circuit is gated so that the multivibrator is sensitive to applied sync only during the master pulses, i.e. only when the delay ramp is *not* running. This means that sync action and strobe trigger can never take place at the same moment. Sync action is possible only during the master pulse, and its effect is always to terminate the master pulse prematurely by the right amount. This means that the width of the unsynchronised master pulse is also the sync lock range.

Synchronisation takes place at the moment of a positive-going or a negative-going zero transition of the signal waveform, according to the respective setting of the sync polarity switch S4. The action is largely independent of signal waveform in other respects so that synchronisation is equally rigid with sinewave signals and with pulse signals. The oscillograms E(a) and (b) show a typical example with a sinewave signal. In E(a) the sync amplitude control VR3 is at zero so that the signal waveform (bottom trace) is running wild. The sync polarity switch was set to negative and the sync amplitude control turned up very slightly to give signal lock shown in E(b). We see that the master pulse is now slightly narrower than in E(a) because sync action has terminated it prematurely by just the right amount to make the end of the master pulse coincide with the negative-going zero transition of the signal sinewave. If the


sync polarity switch is changed over to positive the phasing would jump through half a cycle of the signal waveform so that the positive-going zero transition coincides with the end of the master pulse.

The depicted settings represent a point close to one end of the sync lock range because the negative-going zero transition of the signal occurs only *just* before the master pulse would terminate anyway of its own accord. Thus if the master multivibrator frequency is increased very slightly, or the signal frequency decreased very slightly, sync is lost. On the other hand if the master multivibrator frequency is decreased progressively, or the signal frequency is increased progressively, the synchronising point arrives earlier in relation to the free-running termination of the master pulse so that the latter is terminated prematurely to an ever increasing extent. In other words the master pulse becomes narrower and narrower until the other end of the sync-lock range has been reached where the master pulse is on the point of vanishing entirely. This large effective sync-lock range gives extremely stable synchronisation and the inherent gating which prevents sync response at all times when a delay ramp is running rules out all sync breakthrough into the strobe section so that the sync action is not only rigid but also very smooth.

NUMBER OF CYCLES

The interval between two master pulses is variable from one to three times the master pulse width with the fine frequency control, and this interval is always

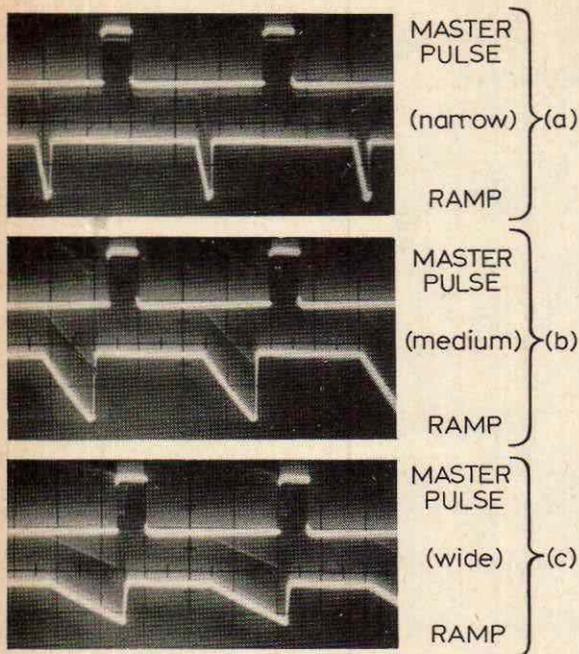B EFFECT OF GATE WIDTH CONTROL S5 (Medium delay, i.e. VR2 mid-way)




the full range within which the strobe trigger point may lie.

The aim of a strobe timebase is to permit selection of the strobe trigger point at any desired phase point on the signal waveform. In other words the interval between two master pulses, which is the strobe trigger shift range, must contain at least one complete cycle of the signal waveform in the synchronised state. This condition is satisfied under all possible circumstances if the master multivibrator is synchronised to one half of the signal frequency so that two cycles of the signal appear between two corresponding master pulse flanks. This is the normal synchronised state shown in oscillogram E(b).

As far as strobe resolution is concerned there is nothing to be gained by synchronising to give only one or more than two signal cycles per master multivibrator cycle. The phase angle of the signal waveform displayed on the strobe trace is determined solely by the strobe gate width. Jitter is a function of the master multivibrator phase angle occupied by the strobe gate so that we merely aggravate jitter if many signal cycles are synchronised on to a single multivibrator cycle. Furthermore the strobe gate delay control then becomes critical because its range covers not just one signal but several, so that phase positioning in one signal cycle becomes very cramped.

Master multivibrator frequencies up to 60kHz are available so that it is necessary to synchronise more than two signal cycles on to a master multivibrator cycle only if the repetition frequency of the signal exceeds 120kHz which is rarely the case in television work. Rigidity and smoothness of sync action improve rather than deteriorate however at higher frequencies. If four or more signal cycles are synchronised to one multivibrator cycle the succes-

C EFFECT OF GATE DELAY CONTROL VR2

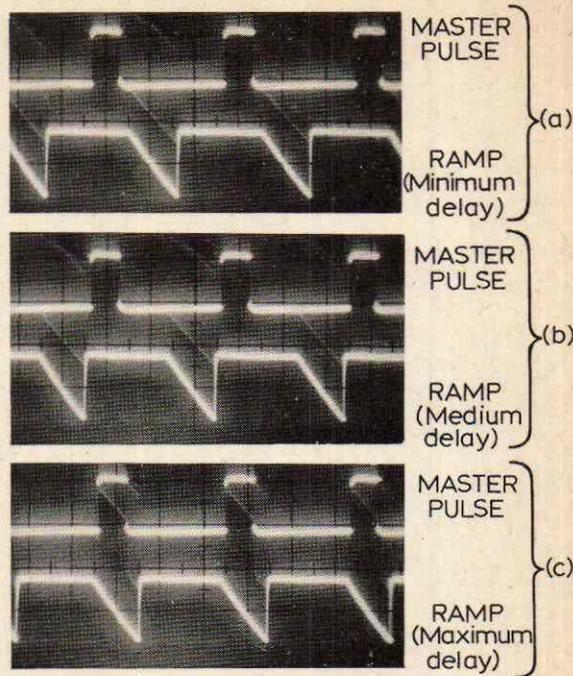


sive sync lock ranges overlap and an unlocked state is no longer possible. As the relative frequencies are changed cycles add or subtract abruptly without lock ever being lost. This automatic synchronisation persists up to signal repetition frequencies in the MHz range.

AUTOMATIC SYNC


The transition to automatic sync, as distinct from a sync range with loss of sync at either end, takes place as soon as the master multivibrator frequency is switched down or the signal frequency is increased to such an extent that the free-running master pulse is longer than one signal cycle. By virtue of the gated sync action this condition totally captures the master pulse so that it is always terminated prematurely and has a duration of exactly one signal cycle as soon as the sync control is advanced from zero. The interval between successive master pulses is quite undisturbed and the strobe delay and strobe gate width controls continue to function normally

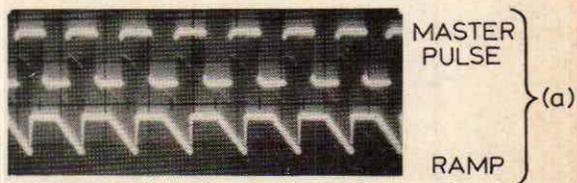D EFFECT OF FINE REPETITION FREQUENCY CONTROL, VR1



D(a) = MAX. } frequency setting with VR1
C(b) = MIN. }

E SYNCHRONISATION TO MASTER PULSE

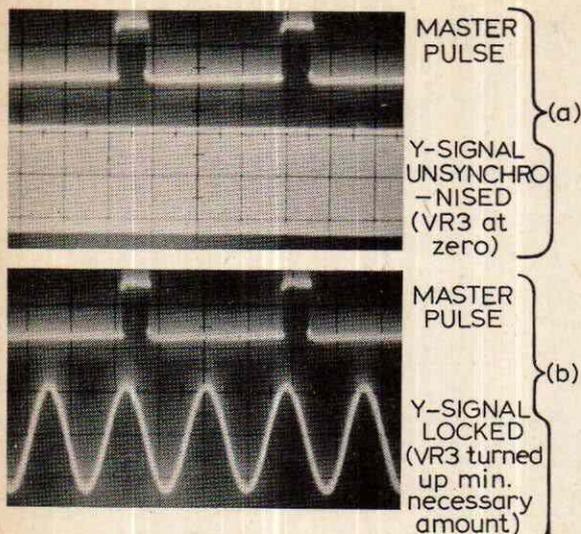

Note that master pulse here shortened to terminate with negative going zero transition of signal (S4 to negative sync polarity)

because the sync applied to the master multivibrator is effective only during a master pulse.

SINGLE CYCLE SYNCHRONISATION

We have seen that synchronising more than two signal cycles on to a single multivibrator cycle aggravates jitter. Conversely single cycle synchronisation with the signal and multivibrator frequencies equal gives improved jitter rejection because the strobe gate then occupies the largest possible phase angle of the multivibrator waveform. However the strobe gate trigger point cannot now be shifted over a complete signal waveform cycle. Nevertheless, half a cycle can always be covered and it is possible to shift the relative phasing by half a cycle with the sync polarity switch (provided the signal waveform is reasonably time-symmetrical) so that in many cases all points of the signal waveform cycle can be reached by the strobe after all. A strobe ratio of 40 is now usable, because the standard figure of 20 is valid for the normal two-cycle synchronised condition. The intensity available with the DG7-32 c.r.t. is adequate for exploiting a strobe factor of 40 if the ambient illumination is subdued.

Thus typical examples of the performance limit are the selection of groups of 10 to 15 lines of a television field on to the strobe trace, magnified display of the colour burst, or a display of a single cycle of a 100kHz transient sitting on a waveform with 2.5kHz repetition frequency. Transient ringing trains with frequencies up to several MHz are readily observable on TV line frequency pulse waveforms.

STROBE GATE AND STROBE RAMP

It is important to ensure that the strobe gate and strobe ramp are of the same duration and accurately

coincident in time because the external function of the strobe gate is to switch on the electron beam in the c.r.t. at the start of the strobe ramp and to blank it again at the end of the strobe ramp. Only if this timing is sufficiently accurate will the strobe trace be clean and free from all aberrations due to signal excursions made during the long waiting periods.

The simplest method of producing accurately coincident strobe gates and ramps is to derive the latter directly from the former. Thus in the absence of a strobe gate a transistor is held conducting heavily thus placing a short-circuit across the timebase capacitor used to produce the ramp. The strobe gate cuts off this transistor for its own duration so that the short-circuit is then removed from the ramp capacitor and it can commence at once to charge towards a large aiming voltage. Only a very small portion of this voltage has been reached by the time the strobe gate terminates, so that the charge waveform is confined to the early portion of an exponential and is thus a substantially linear sawtooth stroke. As soon as the strobe gate terminates the short-circuit is once again placed across the ramp capacitor so that flyback follows at once.

Oscillograms A(a-c) show the accuracy of this action for various strobe gate widths. It is seen that the strobe gate and strobe ramp are in all cases exactly coincident. The ramp commences with the leading flank of the strobe gate, runs very linear for the duration of the gate, and finishes with an abrupt flyback commencing with the terminating flank of the gate. Oscillogram A(c) shows the proper condition. In oscillograms A(a) and A(b) there is some fold-over present at the end of the ramp, before the gate has terminated. This is due to a deliberate displacement of the corresponding internal alignment control, to illustrate the alignment procedure discussed later in conjunction with the detailed circuit description. When properly aligned, all gate widths produce ramps as accurate as the one shown in A(c).

PRACTICAL APPLICATIONS

The majority of practical applications of a stroboscopic timebase in television work are concerned with studies of transients, overshoot and ringing. This is a very important method for assessing and devising methods to improve the response and bandwidths of all manner of pulse circuits, amplifiers and video cable networks. In the majority of practical cases a clean step function waveform is applied to the circuit on test from a suitable signal generator. The leading flank of a squarewave is the most commonly used signal for this purpose. The form in which this flank emerges again out of the test circuit gives valuable information regarding the performance of that circuit.


ASSESSING PHASE AND FREQUENCY RESPONSE

A few common examples will illustrate this point. If an accurate squarewave of duration t is applied to the input of an amplifier it will emerge without significant distortion only if the phase and frequency response of the amplifier are level in the frequency range from $1/t$ to $10/t$. The flanks are rounded if


F STROBE ACTION

Signal locked to master pulse according to E (b)

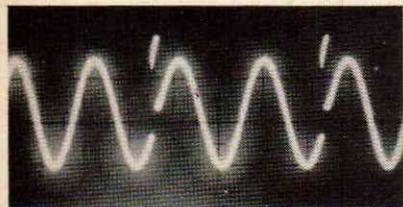
Gate and signal added in operational amplifier for demonstration



(a)

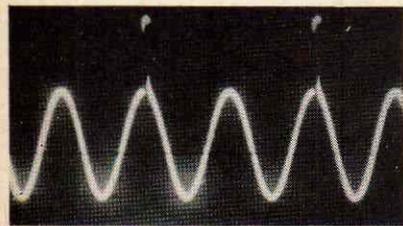

(b)

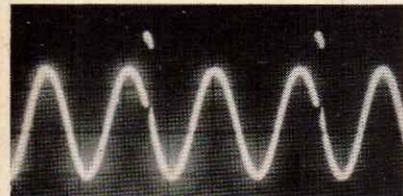

(c)

Increasing gate delay (a) → (c)

In each case the chunk chopped out of signal by gate is magnified alone over full screen in strobe operation as typically shown in G (b)

gain falls with increasing frequency. The flanks overshoot and then return exponentially to the level roof if gain rises with frequency. In either case the cut-off frequency can be determined from the time-constant of the rounded or overshooting flanks, provided the display can be expanded to permit read-off of the time-constant. This is possible with the stroboscopic timebase since it gives a large expansion and an unambiguous time scale because the calibrated setting of the gate width control states the total time value of the strobe trace, which can be brought to any convenient correlation with the screen graticule by adjusting the X-gain control of the oscilloscope accordingly.

If the squarewave roof emerges sagging, arched or regularly undulated, the phase response is not level in the frequency range concerned.

STUDYING TRANSIENT EFFECTS

The master pulse output provides squarewave pulses with logarithmically graded widths from about 0.1sec to about 10μsec, permitting amplifier phase and frequency response assessments throughout the range from 10Hz to 1MHz with ease, and with some practice up to several MHz.

A separate signal generator is not required. The master pulse output is taken to the circuit to be tested, the output from this circuit is taken straight

to the oscilloscope (looping through the stroboscopic timebase unit is required only when using the internal sync function), and the strobe gate delay is set close to maximum so that the strobe ramp commences just before the leading flank of the next master pulse—see oscillogram C (c). The strobe gate width is now set to correspond approximately to the duration of any transient effects expected or observed. No synchronisation of any kind is required since the system is obviously self-slaved. Thus the sync amplitude control is left at zero. The fine frequency control is set to minimum and the coarse frequency control set to range f1-f2. The amplifier or other test circuit is then being assessed for performance roughly in the frequency range from 2f2 to 20f2.

Note that this arrangement displays the entire flank as it comes out of the test circuit because the strobe ramp can be made to commence the appropriate amount earlier. Conventional trigger display of flanks and transients invariably misses the often all-important start.

If the flank distortion is not a simple rounded or overshoot exponential but consists of several cycles, ringing or instability in the test circuit is indicated. If the cause is ringing the cycles rapidly decrease in amplitude. If a train of cycles of constant amplitude is followed by a more or less abrupt decay, or if the amplitude first rises and then decays with a considerable train of nearly constant amplitude in between, the cause is feedback instability in the circuit being tested. This form of parasitic instability in an amplifier often does not produce self-oscillation with no input signal but appears only in the presence of a sharp transient such as the test squarewave or high-frequency components in an applied audio or video waveform. The effect in an audio amplifier is usually lack of clarity and maybe quite heavy distortion, without any indication to the uninitiated person as to what the real cause is.

CABLE RINGING

Ringing is not normally a sign of instability but rather of the presence of oscillatory circuits which may be intentional or may be combinations of stray inductance and capacitance distributed in the test circuit. Very valuable information is obtainable when a ringing transient can be blown up to full screen size so that its exact form may be observed. This is readily possible with the stroboscopic timebase unit.

Oscillograms G(a) and (b) show a typical practical example. Here the shielding lead of the coaxial CCTV distribution cable in the author's home was disconnected at one of the outlet junction boxes about midway on the cable run and the d.c. continuity maintained only via the equipment connected at each end. A clean 7kHz squarewave was fed in at one end and the waveform was observed as it emerged at the other end. Oscillogram G(a) is the normal display obtained with the ordinary built-in timebase of the videoscope. The presence of a ringing transient is clearly evident but its form cannot be scrutinised. Oscillogram G(b) shows the corresponding strobe timebase display of this transient.

We see at once that the ringing frequency is about 1MHz and that in addition to the exponential decay

of amplitude there is a pulsation component—the third cycle is smaller than the fourth. This form of ringing is always an indication of two or more over critically coupled tuned circuits, i.e. a bandpass filter characteristic. If a single tuned circuit is excited with a step function the ringing transient always shows a direct exponential decay.

To the engineer familiar with these facts a cable transient of the kind shown in G(b) reveals at a glance that there is a break in the outer conductor somewhere near the mid-point of the cable run. The nearly equal lengths of intact cable either side of the fault constitute the twin tuned circuit bandpass filter with their distributed inductance and capacitance. If the fault is well removed from the centre point of the cable run its position can still be determined reasonably well from the transient frequency and the listed cable characteristics. In this manner it is possible to test extensive cable runs in communal aerial or CCTV distribution systems.

The ringing transient vanishes entirely as soon as the proper connection is restored in the outlet junction box.

ADJUSTING TUNED CIRCUITS

Slaved ringing with the internal multivibrator as signal generator is also useful for adjusting tuned circuits which are inaccessible to a grid dip oscillator, e.g. because the coil is in a completely enclosed ferrite pot core. In such cases apply the master pulse to the tuned circuit in series with a carbon resistor of value 2 to 47k Ω (to be determined by trial and error) and at the same time connect the tuned circuit via the signal probe directly to the oscilloscope. Use the strobe unit to display the resulting transient whose frequency can thus be determined and is the resonant frequency of the tuned circuit being tested.

OTHER APPLICATIONS


Ringing transients or transients due to instability need not be coincident with a step function. For example if a faulty amplifier is driven with a large sine wave signal, bursts of parasitic oscillation may appear with any phase relationship to this sine wave. Even step function ringing or parasitics may be the result of other drive waveforms produced inside the equipment in question. For all these cases the general strobe function with free choice of strobe ramp phase position, usually with internal sync of the master multivibrator, will be required. It is necessary to loop the signal through the strobe timebase unit only if internal sync is used.

External sync must be used if certain phase relationships with respect to a reference waveform are of interest or if the signal waveform is not truly periodic. This is the case for a composite video waveform which is strictly periodic only with respect to the sync pulses. The picture content is aperiodic with a mean repetition frequency. This is unacceptable for any normal sync circuit which is also the reason why a television receiver must employ a sync separator to isolate the truly periodic sync pulses from the quasi-periodic picture content.


Similarly, synchronisation is possible but strongly dependent on picture content if taken directly from a television waveform in the strobe timebase unit. When working on CCTV and broadcast television

G PRACTICAL EXAMPLE OF STROBE USE

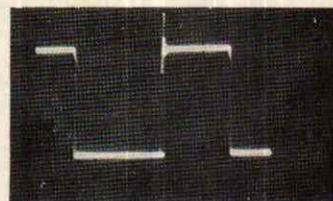7kHz squarewave with 1MHz damped ringing on leading flank



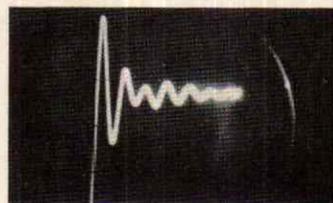(a)
NORMAL DISPLAY
With ordinary
synchronised
timebase



(b)
GATED STROBE
DISPLAY
Showing transient
over full screen

equipment it is preferable to switch to external sync and feed in a clean line or field waveform from some suitable point of the equipment, such as the scan coils or an early stage of the line or field timebase. The display signal then need not be looped through the strobe timebase unit but can be taken via the signal probe straight to the oscilloscope Y-input in the normal manner, the probe being moved in succession to all test points of interest without ever losing sync. External sync is thus desirable whenever numerous waveforms having the same repetition frequency but widely differing shapes and amplitudes are to be observed in succession, as is usually the case when checking through a television receiver.

Once the master multivibrator has been synchronised to half the line or field frequency—using an external sync signal taken via a separate sync cable from any convenient point in the TV receiver—it is merely necessary to use the vertical gain control on the oscilloscope and the gate delay and gate width controls on the strobe timebase unit whilst checking through the TV receiver. These three controls are all independent of each other so that operation is extremely simple and straightforward. If the vertical amplitude of the display is too small or too large when the signal probe is moved to a new test point in the TV receiver, adjust the vertical gain control on the oscilloscope. The gate delay control is adjusted to select the phase position at which the signal waveform is to be observed and the gate width control is set independently to the desired phase angle of the waveform which is to be included in the strobe display.

One complete cycle can always be accommodated in the strobe trace simply by switching the gate width to 100 μ sec (line) or 30msec (field). Each new waveform is first observed in this full cycle setting. If transient detail is seen to be present, move it with the gate delay control so that it is close to the start of the full cycle trace and then switch down the gate width so that the transient detail expands progressively across the screen.

TO BE CONTINUED

DX-TV

A MONTHLY FEATURE FOR DX ENTHUSIASTS CHARLES RAFAREL

THERE has been just no change so far in the disastrous SpE DX conditions we reported last month, and what openings there were did not seem to be as good. I hope this time I can safely say that things have been so bad they just cannot get worse. This has been an all time low for winter SpE and the generally bad weather with snow etc. has ruined any chances of compensation in the form of usable tropospheric reception. The only bright spot this time has been a further increase in F2 activity which was even better than in January.

I suspect that in due course when we get more

RANDOM METEOR TABLE FOR ANY YEAR, SHOWING FREQUENCY AT ANY DATE

Date	Jan.	Feb.	March	April	May	June	July	Aug.	Sept.	Oct.	Nov.	Dec.
1	19	24	12	10	13	14	9	37	10	10	15	22
2	33	3	8	9	14	6	16	32	18	12	16	18
3	30	21	5	12	19	8	21	22	15	18	23	30
4	20	16	13	5	19	10	15	32	10	19	17	19
5	17	16	5	7	18	4	26	14	23	17	11	18
6	16	16	14	4	19	9	14	20	22	15	12	19
7	16	4	11	9	18	8	21	21	19	18	17	36
8	17	10	10	5	15	13	19	35	16	20	10	18
9	25	11	14	12	18	16	32	33	14	17	15	12
10	20	12	11	21	12	21	18	42	14	12	11	29
11	14	12	11	8	25	17	22	66	34	23	19	25
12	26	11	12	11	26	13	13	39	22	18	15	83
13	19	19	13	20	21	20	20	32	10	20	14	44
14	12	13	26	8	9	7	35	29	13	17	21	30
15	11	13	11	10	10	19	9	17	13	21	25	18
16	20	9	5	9	13	17	24	16	28	20	20	23
17	16	3	11	7	12	16	22	26	13	20	15	18
18	20	17	17	18	12	15	11	18	8	21	21	18
19	12	20	8	7	11	14	13	19	19	24	13	22
20	16	15	8	10	12	31	23	24	18	25	13	17
21	19	15	10	14	13	13	14	22	25	41	31	16
22	17	15	12	14	13	23	33	32	25	25	28	7
23	12	15	6	9	14	40	17	24	21	25	19	27
24	12	15	2	6	20	5	36	11	20	19	15	16
25	14	9	8	14	14	9	31	21	19	17	17	23
26	12	12	6	8	21	12	34	22	17	22	19	16
27	10	16	8	11	9	22	24	24	27	28	21	28
28	14	8	5	14	20	20	28	23	15	22	16	15
29	16	15	1	13	7	14	23	17	10	10	30	19
30	20	—	12	10	28	18	29	20	11	22	15	25
31	14	—	11	—	21	—	30	15	—	22	—	11

reports from our US DX-TV friends we shall be hearing of their reception of BBC-ORFT in Band I complete with images, which is alas rather unlikely for us over here. Just to recapitulate, the lowest US channel is A2 (vision 55.25MHz, sound 59.75MHz), both "high" frequencies unless F2 conditions are superb, whereas our American friends have BBC-1 available on 45MHz vision, 41.50MHz sound, and ORFT Ch.F2 on 52.40MHz vision and 41.25MHz sound, which must help quite a lot at this period of the 10-11 year cycle.

Now to the SpE log here for the period 1-28/2/70:

3/2/70 Sweden E4.
8/2/70 USSR R1.
9/2/70 USSR R1 and Poland R1.
12/2/70 Sweden E2.
19/2/70 Poland R1.
21/2/70 Poland R1.

As noted above F2 was better with the USSR 38-41MHz forward-scatter network very good on the 9th, 15th, 20th, 21st, 22nd, 23rd, 24th, 25th, 26th and 27th. Even better was the reception of the US paging stations, often at good strength, on the 23rd to 25th inclusive.

The Trops were just terrible. The only day here showing some promise was the 19th when the "local" French came in at reasonable strength. By the 20th they had dropped back again into the background "hash". As I write however the plants are in bud so spring with better conditions cannot be long delayed now.


As promised we continue with the possibilities of meteor reflections in Band III, including the promised meteor table. To use this table simply pick the date that you wish to know about in the extreme left column then under the month involved read down until the date and month lines cross. For example the count on the 10th of October is 12.

This table is "brand new" to DX-TV work and opens up the possibility of predicting the chances of getting meteor-reflected signals (in Bands I/II and also in Band III) on any given date. Your reports will be of great interest to us and to Bob Cooper, as mentioned last month. I will be pleased to forward your reports to him as a measure of repayment for furnishing this most interesting information about this new DX-TV system.

Bob Cooper goes on to say: "It has been my own experience that dates with counts of under 20 are seldom worth losing sleep over, 20-30 are above average and 31 plus are in the meteor shower category. The peak dates shown of course reflect the occurrence dates of all major night-time meteor showers. You may find it useful to make up a calendar for each month in advance, listing the dates with different coloured pens. My working one has dates in blue for counts of 20 or under, green for 21-29 and red for 30 and over. In this way I can easily spot when I should be active with my gear (a red date is a "must", a green is worthwhile and a blue is "forget it")."

Now for some comment from Bob Cooper, Roger Bunney and myself as to the reception techniques that must be employed—I must stress that the requirements noted are really important. (1) A really high-gain receiver. (2) A good aerial preamplifier, 20dB gain or better. (3) A good aerial array for

—continued on page 365

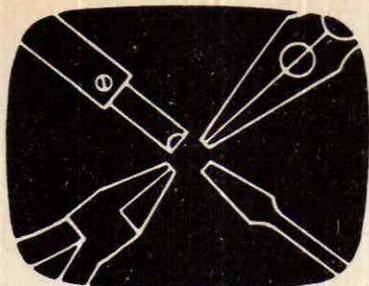

SERVICING television receivers

L. LAWRY-JOHNS

BUSH-MURPHY TV161U/VI910U—continued

The Video Stage

A PFL200 valve functions as the video amplifier and sync separator. This valve can give trouble resulting in a variety of effects from straightforward loss of contrast or sync to a more disastrous cook up of components and damage to the printed panel which may necessitate stripping back one or more tracks and replacing with wiring. This sort of thing is pretty well self-evident and is irritating rather than mystifying.

A little more subtle is the habit of 2C44 ($10\mu\text{F}$) drying up or becoming otherwise open-circuit. This affects u.h.f. reception more than v.h.f. The effect is one of very weak sync where the field tends to roll up or down. A similar effect, attended by more marked loss of contrast, is caused by 2C45 ($320\mu\text{F}$) becoming open-circuit. When the loss of sync also affects v.h.f. it is well to check the heater current as this may be the only indication that the heater circuit diode has shorted. No accurate measurements are required; a look is all that is

needed to see if the valve heaters are glowing more brightly than normal. To make certain a check can be made for 75V d.c. at the junction of 3R58 and P/S8.

Line Timebase

It is the writer's own experience that the line oscillator and output valves do not give a lot of trouble. The main defects seem to centre around the discriminator diodes (3MR1, 2) the boost line capacitor 3C18 $0.1\mu\text{F}$ which is at chassis potential at one end, and the PL504 screen feed resistor 3R22 ($2\text{k}\Omega$).

Discriminator diodes 3MR1 and 3MR2 cause loss of line hold etc. and being combined with 3MR3 can be replaced with a direct replacement block or by three separate diodes which is not difficult if the correct polarity is observed.

The boost capacitor causes more trouble since it can trigger off a chain reaction and the best thing which can happen (and does) is that the

4R3 may be
18k Ω and
4C17 120pF.


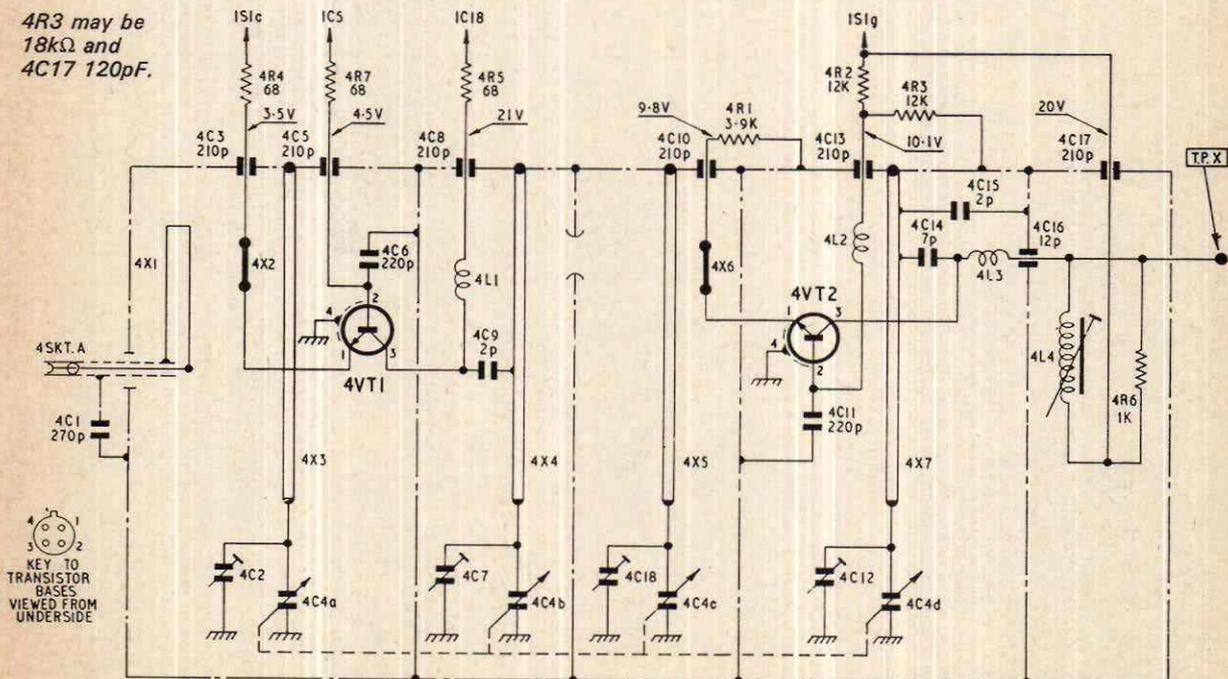


Fig. 5: U.H.F. section of tuner unit type A633. 4VT1 BF180, 4VT2 BF181.

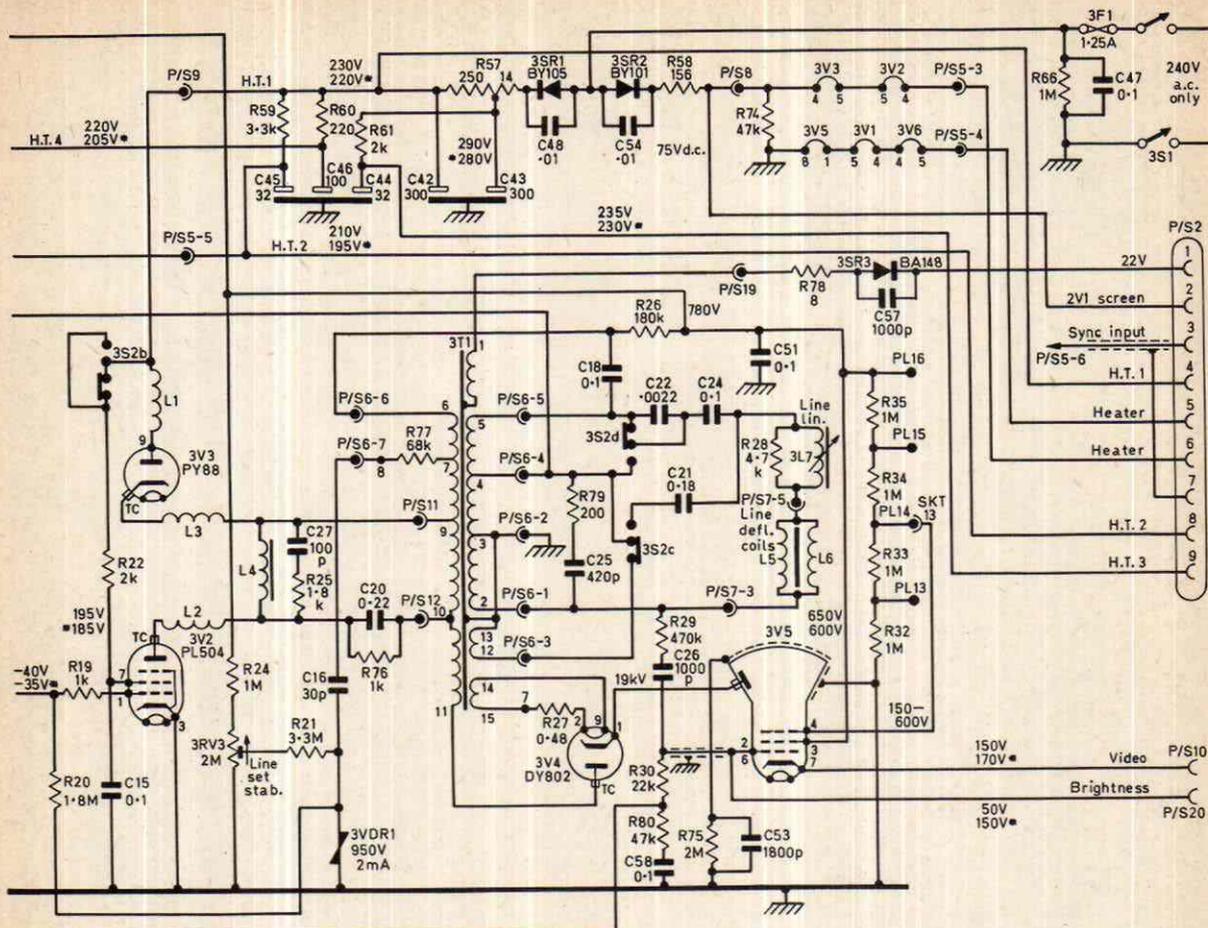

unit A634 and line output unit A581/A585.

previously mentioned dropper section of 14Ω goes open-circuit. The alternative is that the fuse fails (nice) or that the PY88 develops a heater-cathode short (nasty) with the risk of damage to one of the rectifiers before the fuse fails. This risk was doubled in earlier models (TV145U etc.) since the boost capacitor was made up of two $0.1\mu\text{F}$ capacitors connected in parallel.

The screen feed resistor 3R22 may fail of its own account in which case the print will not be damaged, but where there are obvious signs of over-heating, melted solder etc. it is well to check both the PL504 and 3C15.

Check the $4.7\text{k}\Omega$ resistor (3R28) across the line linearity coil 3L7 if striations are present.

Lack of Width

This follows the usual pattern of either a low emission PL504 or a faulty resistor (3R20, 3R21)—possibly 3VDR1—in the width circuit and should not cause any trouble.

IF Stages

One of the annoying things about transistorised receivers is the tendency for one or more transistors to fail in the event of an arc-over or spark at some other part of the receiver, e.g. the tube base, line

or field output stages. Whilst the inclusion of resistors in the collector circuit reduces the failure rate, it still occurs. Hence a sharp disturbance in a valved stage can cause the failure of a transistor in another.

A faulty stage or transistor can quickly be located by signal injection and then voltage readings at the collector, base and emitter of the suspect. The transistors are npn types with a positive collector rail. The voltages to be expected are given in the circuit diagrams and no difficulty should be experienced.


The contrast and a.g.c. controls tend to have a sharp cut-off so the settings should be checked before suspecting a fault in the tuner or i.f. stages.

Tuner Unit

This is in two sections as shown. Trouble is usually confined to faulty switching or a faulty transistor.

Do not disturb the layout in any way and ensure that replacements are exact and occupy the same position as the original. Weak u.h.f. signals where the aerial is known to be good should direct attention to 4VT1 (BF180) and wrong readings at 4R4

—continued on page 365

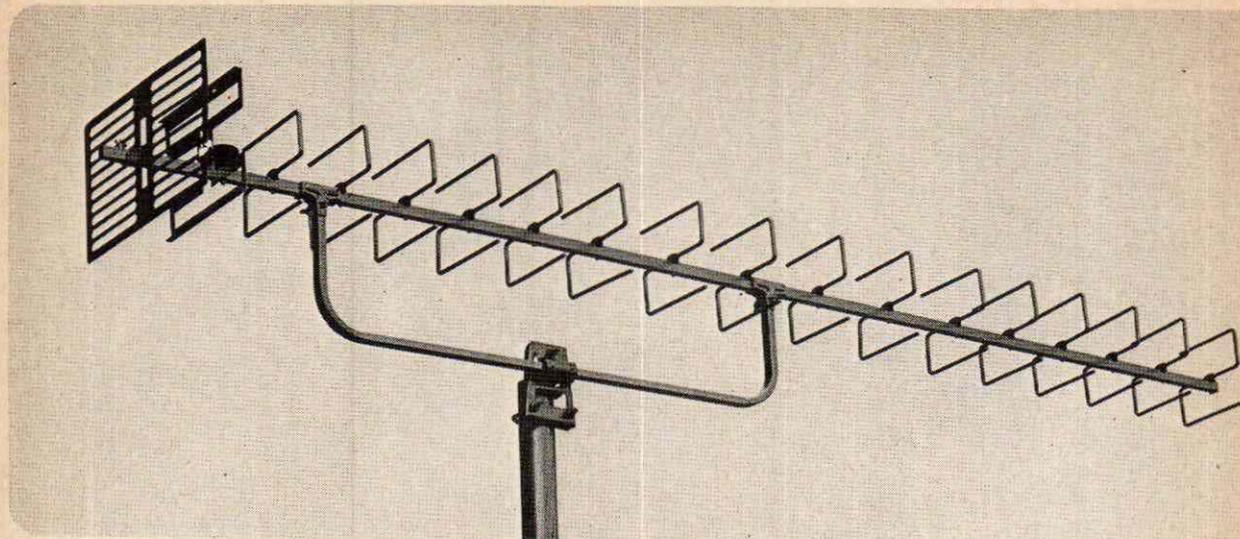

QUITE a few old hands will recall the days of Band I only aerials. It seemed wonderful then that domestic-quality signals could be transmitted, propagated and received at such high frequencies on channel 1. A lot was written about the problems that would almost certainly be involved when the top end of Band I (channel 5) was made active. Not only did we overcome the problems of rising noise with increasing frequency in the front-ends and those associated with propagation but we then entered even higher frequency realms and gallantly opened up Band III for a second TV programme and activated lots of channels to provide a country-wide service. Apart from the intrinsically insoluble co- and adjacent-channel shortcomings of covering the whole country with two programmes within a somewhat restricted v.h.f. spectrum (v.h.f. in reality extends from 30 to 300MHz or from 10 metres to 1 metre) we progressively overcame the new problems of Band III working at transmitter, aerial and set and ended up with a remarkably efficient two-programme TV service that could neither be improved in terms of picture definition nor in terms of programme multiplication. We were stuck.

We then followed America, explored the u.h.f. spectrum and eventually introduced a third programme within this spectrum (u.h.f. extends from 300 to 3,000MHz or from 1 to 0.1 metre). This time we gave ourselves much more elbow room, so to speak, for a significantly greater number of TV channels can be accommodated in the overall 2,700MHz spectrum of u.h.f. than in the 270MHz spectrum of

v.h.f. Although this may appear to be an excessive amount of additional TV spectrum it was necessary for three prime reasons. One because we decided early in the game that we would ultimately abandon the v.h.f. spectrum for the major part of domestic television and concentrate on up to a total of four programmes, country-wide, in the u.h.f. spectrum; two because we decided to enhance the display definition by changing from the early 405-line system to the better 625-line system which demands greater channel width than the former; and three because the effective area over which consistently good u.h.f. reception is possible from any given transmitter is less than in the v.h.f. spectrum, calling for many more u.h.f. transmitters than v.h.f. ones for country-wide coverage.

Co-channel Interference

Thus although the u.h.f. spectrum may appear unduly wide the number of 625-line TV channels that it provides is still below that required for four programmes in all parts of the country on separate channels. This means that we still have to go in for channel sharing but as in the v.h.f. spectrum this is very carefully engineered so that the transmitters sharing channels are as far as practicable away from each other. Moreover the directivity of the transmitting aerials and their orientation are arranged so that the smallest possible signal field is radiated towards the area in which the nearest u.h.f. transmitter is using the same channel. In this way it is hoped to avoid co-channel interference problems; *but just how well this arrangement will work in practice when each area is provided with three (BBC-1, BBC-2 and ITV) and subsequently four lots of programme signals will significantly depend on the efficiency of the receiving aerials as we shall see.* And since it is assumed that we know a bit more about television than the chap in the street, it is our duty at least to ensure that our own installations are perfectly in order and operating as efficiently as possible. It is indeed noteworthy that about half the complaints received by the BBC (and this is only one of a number of authorities) about adverse

Table 1: Standard u.h.f. aerial groups.

Group	Colour Code	Channels	Frequencies MHz	Range MHz
A	Red	21-34	470-582	112
B	Yellow	39-51	614-718	104
C	Green	50-66	702-838	136
D	Blue	49-68	694-854	160
E	Brown	39-68	614-854	240

Reproduced from "The Practical Aerial Handbook," 2nd Edition, by Gordon J. King, published by Butterworths.

Our heading photograph shows the Aerialite Golden Gain Supreme fringe u.h.f. array.

u.h.f. reception are eventually traced to badly erected, wrong type or inadequate aerials.

In addition to reducing the possibility of co-channel interference, the u.h.f. receiving aerial is also a highly critical link to good colour reception, to correct balance of the received signals of a local group and to optimum signal-to-noise performance (i.e. least grain on the picture and hiss on sound) of the receiving system as a whole.

Each area has been assigned a group of four u.h.f. channels. Quite a few are currently using one of the assigned channels for BBC-2 and some are also using two more channels for BBC-1 and ITV, both in monochrome and colour. At the time of writing about half Britain's television viewers could if they

is the dipole or radiator terminal resistance, for we have to ensure that this holds sensibly constant at the matching feeder impedance (typically 75 ohms) over the entire bandwidth without deep changes into reactance— C or L . Two is the overall response itself, for steps in this—especially at frequencies corresponding to the required u.h.f. channels—could impair the luminance-chroma ratio of a colour signal and thus disturb the colour displays at the set or at least put the set into some difficulty, while excessive end-of-response roll-off could diminish the array's efficiency at the group's terminal channels, again affecting colour reception. Three is the polar response, for this too should remain essentially constant over the entire spectrum and the design

AERIALS FOR THE 70s

K. ROYAL

wanted to receive all three programmes in monochrome and often in colour on u.h.f. This means that they could abandon their old v.h.f. aerials and instead employ a solitary, neat u.h.f. wideband array for the existing three programmes with the knowledge that this single array will be suitable for the fourth programme when it becomes available (there is nothing definite about this fourth programme yet).

One Aerial All Programmes

The aerial of the seventies is therefore a compact u.h.f. array which will satisfy all foreseeable developments in domestic entertainment television. It is important fully to realise that this one aerial will cater for all the channels of a local group, but—very important—it will only do this when it is very accurately designed, erected and orientated. There is a great deal more to the design of wideband u.h.f. aerials than many readers seem to realise. In the good old v.h.f. days we used an aerial "peaked" to a single channel and if we wanted to make one of these ourselves the problems were relatively small provided we used the well-known formulae for element dimensions, spacings and so on. A peaked aerial like this can be designed so that it "looks" pretty well resistive to the feeder through which the signal is conveyed to the set. Moreover when it is so peaked the directivity of a yagi type automatically maximises in the forward direction and so both prime parameters—frequency and directivity—are reasonably well satisfied and we can also be fairly sure that the dipole terminals will appear resistive to the feeder.

When however an aerial is designed for wideband working over a spectrum of up to 100MHz or more for four-channel operation trouble really starts. There are three main factors that we have to control. One

must avoid lobes appearing at the sides and at the rear of an array at the different frequencies over the group of channels as these lobes would defeat the requirement of maximum co-channel discrimination previously referred to.

Poor or Incorrect Design

These are no mean tasks and the majority of home-made aerials are unlikely to satisfy them all. A lab-full of specialised equipment and a well tailored test site are necessary for proper test plottings of new designs, such plottings then revealing how the polar response, impedance, bandwidth and so on are collectively or separately affected when a change is made, for example to the length or spacing of an element.

This is *not* to imply that home-made aerials will not work at all. Indeed it is possible that an array of given complexity when home-made and constructed in accordance with the old-established rules will exhibit better gain on one specific channel than a very carefully designed wideband commercial aerial. This is all very well at the moment in those areas where only BBC-2 is being transmitted. But where the three channels are active, users of such aerials will almost certainly find that some channels—if receivable at all—will carry more noise (i.e. background grain) than the one to which the aerial is peaked.

Sadly this effect is not confined only to home-made arrays, for some early commercial u.h.f. aerials appear to have been made in a hurry to satisfy the initial demand for a BBC-2 aerial and as a consequence are peaked to BBC-2. Thus their owners are having difficulty in obtaining good reception from the recently introduced BBC-1 and ITV pro-

grammes, especially when these are in colour.

If you have an aerial like this the only thing to do is to replace it with one of the latest wideband models and cut your losses! It is pointless to tolerate noisy pictures and excessive interference on a potentially high-definition TV system for the sake of a few pounds, particularly if you are running a new single-standard set or a colour set costing several hundred pounds. The same applies to u.h.f. aerial preamplifiers. Some of the early ones were purposely designed to peak BBC-2; but those made now are (or should) be wideband models.

Minimum Standards

Some years ago the major aerial manufacturers worked out certain minimum standards for u.h.f. aerials in terms of response, directivity and so forth and have since kept rigidly to these. So even an early aerial originating from such reputable manufacturers should not be plagued with the above-mentioned shortcomings. Regarding bandwidth versus gain the standard dictates a variation not exceeding 1dB over a channel and 3dB over the entire bandwidth. For directivity a minimum front-to-back ratio of 16dB for arrays of five or more elements is specified. Such parameters are very difficult for the amateur aerial constructor to control.

The latter aspect might seem relatively unimportant right now in some areas, but it must be remembered that there will be ultimately in excess of 1,000 u.h.f. transmitters sharing about 44 channels! Thus an aerial with a poor front-to-back ratio installed now would certainly be likely to respond later to unwanted signals arriving at the rear and sharing the same channel as the wanted signal arriving at the front. Front-to-back ratio expresses the "pickup efficiency" at the front of the aerial relative to that at the rear. As I have already pointed out, similar trouble can result from co-channel signals arriving at the sides of an aerial or at various angles relative to its axis if its overall design is poor with side lobes or pickup.

It is of course well known that the distance over which u.h.f. signals travel is limited. Nevertheless under certain reception conditions such signals can produce quite a strong field at distances of several hundred miles from the transmitter, so one can imagine the magnitude of interference that could

result from 1,000 transmitters sharing 40-odd channels under such reception conditions if the receiving aerial has spurious responses at the rear and sides.

Technicalities

Now let us look a little more technically at some of the points so far discussed. Fig. 1 shows the horizontal polar response (or "diagram" as it is often called) of an eighteen-element yagi. The major elongated pattern indicates the angles, relative to 0 degrees (the on-beam orientation), over which the aerial picks up signal. This indicates that if the array is about 10 degrees off-beam either side the response falls by about 2 points from maximum, given as 10, while if it is 20 degrees off there is virtually no pick-up at all. The importance of accurately beaming a yagi to the station is thus clearly shown. The minor patterns (or lobes as they are called) are not uncommon with high-gain arrays and it is the job of the designer to keep these as small as possible. Sometimes the lobes tend to expand and/or multiply by mounting two aerials broadside or one above the other, but such stacking can improve the main lobe directivity and increase the gain. Two in-line (yagi) arrays properly connected together can give a gain increase of up to 3dB and four up to 6dB. Fig. 2 shows how the minor lobes increase with stacking.

Pick-up efficiency is expressed in dB gain relative to a single dipole tuned to the same frequency. Thus an array with a gain of 3dB means that on-beam the signal extracted from a given field intensity is twice that of the dipole alone.

One thing about u.h.f. arrays is that we can use many more elements than on v.h.f. without making the system unduly bulky. This is just as well because the shorter the aerial the less signal it extracts from the passing radio wave. TV aerials are tuned devices and the efficiency of a dipole for instance is maximum when its length is almost *half* the wavelength of the signal it is required to receive. We say almost half because the wave velocity is reduced by about 5% owing to the wave passing into the aerial from free space: this means that the tuned length of the aerial is about 5% shorter than the in-space signal half wavelength. No significant improvement in pick-up efficiency results by increasing the length of the aerial since this will merely detune it and possibly detract from its efficiency. Thus a u.h.f. half-wave dipole working in say the C group of channels (Band V) is only about 7in. long as compared with about 127in. for a Band I, channel 1 dipole. This is the reason why u.h.f. aerials, even those working close to a transmitter, generally have more parasitic elements (i.e. directors and a reflector system) than their v.h.f. counterparts whose elements are longer when tuned.

The strength of the signal delivered by a tuned dipole is equal to the product of the dipole's *effective length* in metres and the signal field in volts/metre divided by two. The effective length of a tuned dipole is given by λ/π . However the signal actually received by the set is less than this owing to the attenuation of the coaxial cable and the losses at u.h.f. in plugs, sockets, filters and so forth. In weak signal areas therefore only the best low-loss u.h.f. coaxial cable should be used; plugs and sockets should be very carefully fitted and filters should be avoided.

Fortunately the fall in the effective efficiency of a

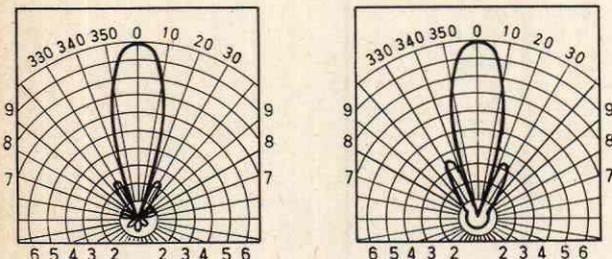


Fig. 1 (left): Horizontal polar diagram of 18-element yagi (including reflector system). This has a front-to-back ratio of about 26dB.

Fig. 2 (right): Horizontal polar diagram of four 12-element yagi arrays in side-by-side and stacked formation. While this has a front-to-back ratio of about 26dB, as in Fig. 1, the overall gain is some 3dB better than the single 18-element yagi. Note the development of the minor side lobes which is sometimes a tendency with stacking.

dipole as the signal frequency is increased (excluding the extra "gain" provided by parasitic elements) is countered by the stronger signal field evoked by transmitters at increasing frequency, even though the power remains constant, coupled with the relatively high gain provided by u.h.f. transmitting aeri-als of feasible size, the design laws of which are similar to those of receiving aeri-als. A transmitting aerial with say a gain of 10 times would give an effective radiated power of 1kW from a 100W transmitter, but generally this power would be concentrated in a specific direction.

The signal field in volts/metre can be expressed as

$$2.58 \sqrt{W} \frac{h_t \times h_r}{\lambda \times d^2}$$

where h_t and h_r are the heights of the transmitting and receiving aeri-als in metres, W is the power of the aerial signal in kilowatts, λ the signal wavelength in metres and d the distance from the transmitter. This clearly shows that the signal field is proportional to the height of the aeri-als and inversely proportional to the wavelength. Thus as the wavelength is made smaller (frequency increased) the signal field increases. The expression also reveals that the signal field falls off in accordance with the well-known inverse square law (i.e. $1/d^2$). The power at the aerial of course also affects the strength of the signal field, but less than generally realised. The height of the aeri-als is more important, especially towards the edge of the service area and into the fringe. Remember therefore that one of the most important factors involved in good u.h.f. reception is that of receiving aerial height. The transmitting people make sure they satisfy this factor adequately at their end!

Aerial Design

The majority of u.h.f. aeri-als are based on the yagi principle where the tuned dipole (about 5% shorter than the in-space signal half wavelength) has a reflector or reflector system behind it and a number of spaced directors in front of it. The centre impedance of a tuned dipole is about 75 ohms which

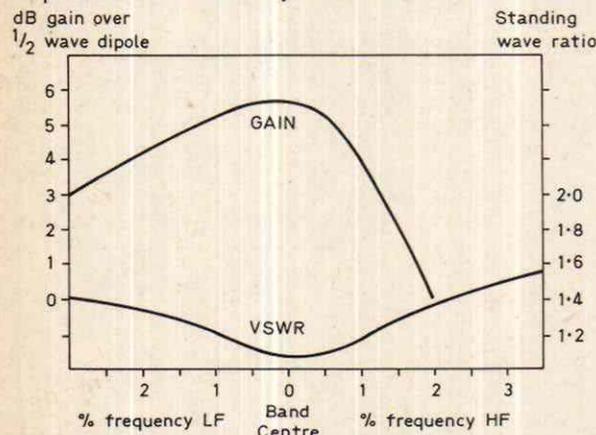


Fig. 3: The degree of mismatch over the bandwidth can be expressed as volts-standing-wave-ratio (VSWR in the diagram). The smaller the ratio the better the matching. The diagram shows that at band-centre the matching is almost perfect while either side of resonance it falls. A wideband aerial is designed to minimize the increase in VSWR over the entire channel group.

makes a very good match to 75-ohm coaxial cable. However when directors and a reflector system are added the impedance falls significantly and to bring it back to about 75 ohms again the artifice of folding the dipole is adopted. This allows the signal current to divide between two parallel paths and because of this the centre or feed impedance is stepped up by a factor of four. This factor of four arises because the power is proportional to the square of the current.

To keep the centre impedance essentially resistive and at a constant value over the aerial's bandwidth one fold of the dipole may be of a greater metal mass than the other, or it may be differently shaped. A simple half-wave dipole is akin to a tuned circuit and because of this it exhibits an increasing inductive reactance and a decreasing capacitive reactance across its terminals when the length is in excess of the signal wavelength, and vice versa (see Fig. 3). Thus to maintain an essentially constant resistive "impedance" over the aerial's bandwidth the designer has to work one electrical parameter against another and compromise to some extent. However the wide-band design is influenced by the presence of the parasitic elements which work something like tuned and coupled circuits which when they are all resonated to the same frequency tends to increase the effective Q and reduce the bandwidth, just the opposite to requirements.

However by staggering the tuning so to speak, by "phasing" the elements and by carefully adjusting their coupling, the bandwidth can be increased just as it can in radio circuits. Tuning is achieved by adjusting the length of the parasitic elements while the spacing between them determines the coupling coefficient and phasing. Even when an array has been optimised in this way there is still the possibility of the dipole impedance swinging reactive or away from the nominal 75 ohms unless precautions against this have been engineered into the design. Conditions like these can seriously reduce the signal transfer to the receiver by giving rise to standing waves on the feeder and by impairing the power coupling to the first r.f. amplifier, especially when this is a u.h.f. transistor.

Commercial Ideas

Schemes for maintaining a resistive load over the required bandwidth have resulted in the diverse u.h.f. aerial designs of recent years. Belling and Lee for example employed dipoles of special shape (now continued by Antiference) while Antiference have used a pair of coupled dipoles working "differentially" to counter mismatching arising from reactive swings over the bandwidth. J-Beam have used special balun transformers and continue to do so on their latest Multibeam and earlier Parabeam arrays. The radiator of these arrays is based on the skeleton slot principle rather than the dipole and since the terminal impedance is high on the slot compared with 75 ohms the balun, which is patented, serves both as an impedance transformer and as a wideband matching device. Fig. 4 shows how the J-Beam balun is formed.

All the major aerial manufacturers have their own pet ideas for securing a resistive feed over the required wide spectrum of the channel groups (listed in Table 1) but in addition to taming this area of the overall design the polar response must hold fairly accurately over the bandwidth. Indeed if the designer

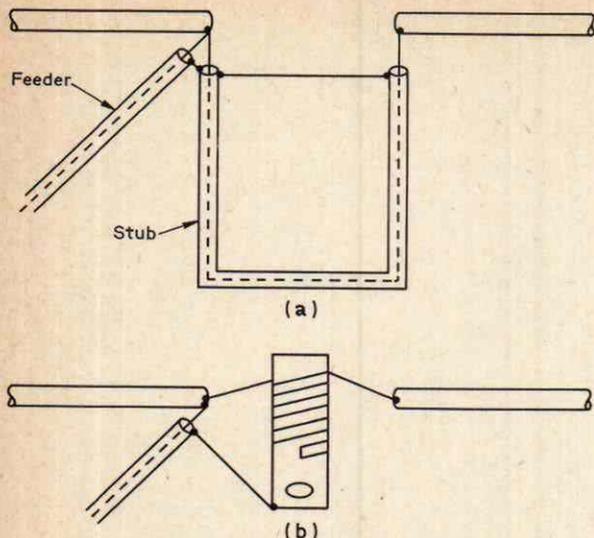


Fig. 4: Development of the J-Beam inverse balun: (a) shows the basic matching stub principle which gives a 75-ohm coax feed from the relatively higher terminal impedance of a skeleton slot radiator while (b) shows how J-Beam simulate the principle by means of a wound component.

fails to do his sums correctly it is possible for the array to "back-fire" at certain frequencies within the bandwidth with obvious impairment to the front-to-back ratio as shown in Fig. 5.

A technique that has recently been applied to domestic television aerials by Antiference, first in Band III and later in Bands IV and V, has given birth to the so-called log-periodic aerial. Although it looks like the conventional yagi its principle of working differs considerably. The array is composed of a series of in-line *dipoles* correctly matched to a special transmission line forming the boom which takes the normal feeder (see Fig. 6). The tuned frequency of successive dipoles is tapered so that as the signal frequency is varied over the bandwidth the resonance swings smoothly from one dipole to the next and so on over the series. Length and spacing of the dipoles are based on a logarithmic law (hence the aerial's name) and the system will only work when the dipoles are alternately phased along the boom. This is where the special boom-type transmission line comes in. At any frequency within the bandwidth the dipoles which are inactive tend to

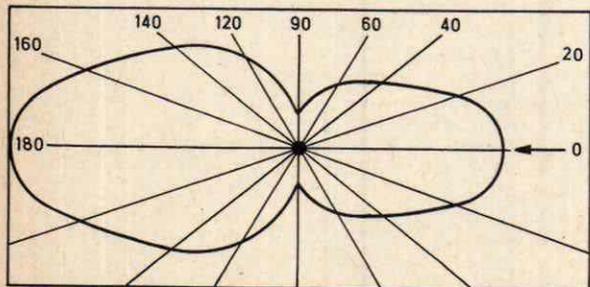


Fig. 5: Wrong design can cause a yagi to "back-fire" at certain frequencies within the bandwidth with a resulting impairment to the front-to-back ratio.

act something like parasitic elements, and in this way a very smooth bandwidth with consistency of polar diagram and loading is achieved. The gain is intrinsically less than that of a comparable yagi

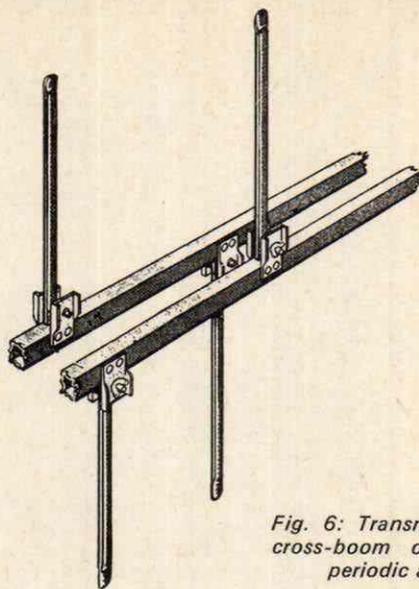


Fig. 6: Transmission-line cross-boom of the log-periodic aerial.

array but in areas of fair signals its other attributes can be very desirable.

Another idea, promoted by J-Beam, involves the use of special director elements. Those of the J-Beam Multibeam range for example are four-pronged devices and a considerable amount of basic research undertaken by J-Beam Aerials revealed that a single array employing this kind of "pronged" director throughout in conjunction with the J-Beam skeleton-slot radiator and inverse balun already described yielded almost the same high gain as a far more complicated stack of ordinary yagi arrays. Fig. 7 gives some idea of the gain versus bandwidth characteristics of a Multibeam aerial.

Basic Design Material

We have seen that there is a great deal to the design of efficient wideband u.h.f. aerials, possibly more than may have been realised. Bearing in mind the relatively low cost of guaranteed commercial arrays one wonders whether it is worthwhile to go to the trouble of making one's own, especially taking into account the "gamble" involved—when designing

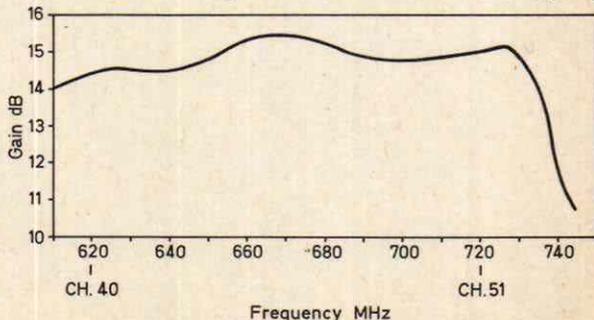


Fig. 7: Gain-bandwidth characteristic of the J-Beam Multibeam MBM38 array.

without specialised equipment—in obtaining an overall optimised design. Nevertheless quite successful u.h.f. aerials have been made at home and for enthusiasts wishing to have a go the following formulae will be of interest:

- (1) Length of dipole in inches = $5,616/\text{frequency in MHz}$.
- (2) Length of reflector in inches = $5,976/\text{frequency in MHz}$.
- (3) Length of first director in inches = $5,400/\text{frequency in MHz}$.
- (4) Spacing (0.25λ) reflector to dipole in inches = $3,052/\text{frequency in MHz}$.
- (5) Spacing (0.13λ) director to dipole in inches = $1,546/\text{frequency in MHz}$.
- (6) Spacing (0.13λ) director to director as (5).
- (7) Directors after the first can reduce progressively in length by $2\frac{1}{2}\%$.

These parameters will result essentially in a "channelised" response and adjustments along the lines examined in this article will be required to obtain wideband characteristics. Table 1 lists the five standard channel groups, the identification letters and colours, the channels and frequencies involved and the range of the groups in MHz. It will be seen that the frequency range is not the same for all groups, becoming wider with ascending group letter. Groups D and E cater for those areas which for some reason cannot use the basic 88 MHz bandwidth. ■

SERVICING TV RECEIVERS

—continued from page 359

and 4R7 will normally show whether this transistor is in fact the cause of the trouble.

System Switching

The method of switching on both panels is somewhat less than ideal and should be checked several times as the throw can vary. The left side is adjusted by moving the panel up or down and tightening the top and bottom screws in the correct positions. The right side is adjusted by opening or closing the V-shaped wire at the top.

Voltage Conditions

The readings given on the circuit diagrams were measured with 240V a.c. mains input, small signal input, contrast set for normal picture and normal width and height using an Avo Model 8 ($20,000\Omega/V$). Voltages followed by an asterisk were taken on 625 lines.

Picture Tube

19in. models are fitted with an A47-11W or CME1905 picture tube, 23in. models with an A59-11W or CME2305 tube.

Associated Models

Many Defiant models marketed by the C.W.S., for example the 903 and 303, employ this as well as earlier and later Bush chassis.

NEXT MONTH: GEC-SOBELL 2010-1010 SERIES

DX-TV

—continued from page 356

the appropriate Band/Channel, in excess of 13dB forward gain if possible. (4) It is very important that your receiver is (a) accurately calibrated for each channel you wish to investigate and that (b) your line and field lock controls are correctly set for 625 lines, 50 fields.

The set must lock-in on any picture received immediately. You will appreciate that one second or so signal bursts allow no time for readjustment of the controls. So get your receiver set up correctly, position the aerial towards the area of hoped for reception—for the British Isles I would suggest towards the North East, midway between the USSR and Scandinavia—then keep your attention riveted on the screen, and the best of good luck to you all!

Bob Cooper says that so far his reactions have been too slow to get any off-screen photos, so you know what we are up against! This new type of reception is I feel strictly for the established DXer and not for beginners until they have had a lot of SpE experience. It is however a very worthwhile project and can open up further DX fields for us that are independent of SpE and/or Trop conditions. Reception has already been achieved at the l.f. end of Band III and further investigation could show that it applies throughout the band.

IN NEXT MONTH'S ISSUE . . .

TV IN THE DARK

Most TV camera tubes are relatively insensitive, requiring high studio light levels. Techniques used in some specialised modern tubes have however led to remarkable advances, with clear TV pictures produced under starlight conditions, i.e. illumination levels millions of times less than those used in broadcasting studios. These new techniques are fully described.

THE 625-LINE RECEIVER

Next month we shall be publishing full underchassis wiring details for the constructor's single-standard 625-line receiver.

POWER SUPPLY CIRCUITS

A detailed account of the power supply arrangements used in TV receivers—including hybrid and colour sets—with fault summary.

R-Y PHASE ALTERNATION

The heart of a PAL colour receiver is the circuitry needed to process the line-by-line phase alternation of the R-Y chroma signal in the PAL system. The principles involved and circuits used are explained.

SERVICING TV RECEIVERS

A large number of models are fitted with the basic GEC-Sobell 2010-1010 chassis, the subject of our next servicing feature.

PLUS ALL THE REGULAR FEATURES

JUNE ISSUE ON SALE MAY 21

SINGLE-STANDARD PART 3 625-LINE RECEIVER FOR THE CONSTRUCTOR KEITH CUMMINS

We have now reached the stage when the line timebase arrangements can be examined in detail. Four of the eight valves used in the receiver are employed in the line timebase section so it will be realised that this part represents a large proportion of the circuit the constructor is required to build.

As the majority of readers will be well aware the line timebase besides providing the line scanning for the picture tube also supplies the e.h.t. needed by the tube final anode and a boosted h.t. rail. The boost rail feeds the charging circuit of the field timebase and the first anode of the picture tube. Therefore we can think of the line timebase in relation to the remainder of the receiver as a "black box" with synchronising pulses and power fed in and the boosted h.t., e.h.t. and line scanning coming out. Since it is possible to regard the line timebase section as a unit we will first discuss the circuit as a whole and then deal with its detailed internal functions.

Basic Considerations

The timebase is supplied with a positive h.t. rail of 230V and synchronising pulses from the sync separator stage V2a. While the noise-cancelling sync separator described in last month's issue reduces extraneous pulses to a minimum, it is still possible for noise occurring during a sync pulse period to operate the cancelling circuit so that the output pulse is removed. Considering the rate of line scanning, there is a high probability that sustained interference will bring about the deletion of line pulses. Lower-level interference below the cancellation threshold can produce additional incorrect line sync pulses. It will be appreciated therefore that the timebase should be designed to minimise the effects of sync pulse disturbance.

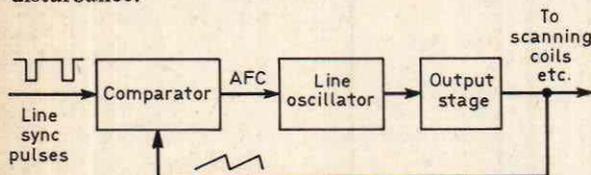


Fig. 5: Block diagram showing the basic operation of a flywheel line timebase.

The type of circuit employed controls the line timebase speed by comparing the mean incoming pulse rate with a sample of the timebase output, rather than having every line triggered by an incoming pulse. Experienced readers will recognise this as the flywheel timebase technique. Random interference with the regular chain of sync pulses has little effect since the timebase responds only to the aggregate comparison of a large number of pulses.

The basic system is shown in block form in Fig. 5.

The line oscillator drives the output stage and a sample of the output waveform is taken to the comparator where it is compared with the incoming line sync pulses. Depending upon whether the repetition rate of the incoming pulses is greater or less than the repetition rate of the timebase, the output from the discriminator will be a d.c. potential above or below earth. When the natural repetition rate of the timebase is the same as that of the sync pulses the discriminator output is zero.

Between the discriminator and the line oscillator is interposed a circuit with a time-constant equivalent to several picture lines, so that a significant error-control voltage cannot build up as a result of individual line pulse disturbances. Also the effect of noise on the sync pulses is significantly reduced. In effect this automatic frequency control system gives the timebase a running effect similar to mechanical inertia, hence the term "flywheel timebase".

Some readers will have recognised the foregoing description as that of a servo system, which brings us to two further design considerations, pull-in range and timebase stability. The pull-in range simply means the maximum frequency difference between input signal and oscillator that the system can correct before manipulation of the line hold control is necessary. It is important to note that while a wide pull-in range would superficially appear to be worthwhile it also involves a deterioration in noise immunity, tending to defeat the whole object of the exercise! This deterioration results from the necessary choice of time-constant in the filter circuit between the comparator and oscillator. From the noise point of view a narrow pull-in range is best. This however requires good oscillator stability since if the oscillator drifts badly the control circuit will not be able to apply sufficient correction.

The reader will now realise that here, as in the majority of design work, a suitable compromise has to be made between two conflicting requirements. The best oscillator circuit from the stability point of view is one using a tuned circuit. LC oscillators are in fact used in the majority of colour receiver line timebase designs. The stability of such an oscillator is determined by the capacitance and inductance and depends little on such factors as ageing valves etc.

From the constructor's point of view however an LC oscillator has one daunting disadvantage—the need for a special inductor with a large number of turns. It was decided therefore to adopt a compromise solution, using a multivibrator circuit with as good stability as possible. This course of action appears to have been completely satisfactory and the circuit as shown (Fig. 6) represents the result of a rigorous period of evaluation and test. The

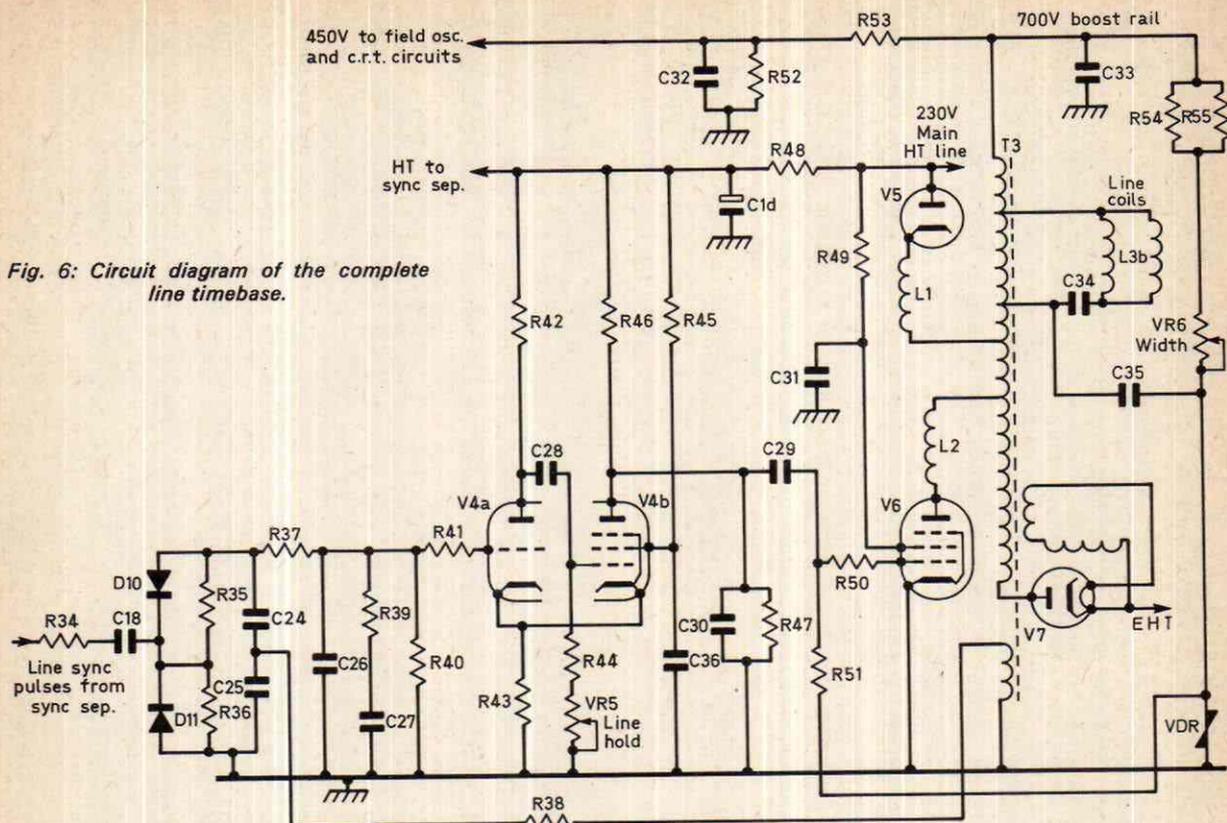


Fig. 6: Circuit diagram of the complete line timebase.

pull-in range has to be wider than would have been necessary had an LC oscillator been employed, but the noise immunity has proved to be completely adequate on test.

Flywheel Sync Circuit

We will next look at the circuit (Fig. 6) in detail. The line sync pulses from the sync separator are applied to the cathodes of D10 and D11 via the current-limiting resistor R34 and coupling capacitor C18. The diodes are shunted individually by resistors R35 and R36. The anode of D11 is earthed while the anode of D10 connects to the output line. From the output line to earth are connected capacitors C24 and C25 in series and the junction of these capacitors is fed with the sample of the timebase output via R38.

It will be realised on inspection of the circuit that if no signal is applied to the junction of C24 and C25, while the sync pulses are applied to the junction of D10 and D11, there will be no d.c. signal output from the circuit via R37. This occurs since D10 and D11 are in opposition to one another and while the negative-going sync pulses cause D11 to conduct and the junction of the diodes moves positively, D10 cannot conduct. Similarly if the sync pulses are removed and only the comparison signal from the timebase is applied there is again no output.

When both signals are applied however an output from the discriminator appears, its sense depending upon which signal has the faster repetition. The signal from the timebase is a sawtooth with a large overshoot. The overshoot is effectively removed by

the integrating effect of R38 and C25, so that only a sawtooth waveform is left for application to the discriminator. The arrival of both sync pulses and sawtooth waveform brings about conditions of unequal conduction in D10 and D11 if the two signals are not coincident, so producing an out-of-balance voltage which is taken off via R37.

R37 and C26 form the elements of the filter circuit mentioned earlier. In addition R39 and C27 are included. These form an anti-hunt network which stabilises the a.f.c. action. Without these components the correction signal would overshoot its optimum point cyclically, positively and negatively, so that the timebase would never find its correct operating point. By introducing critical damping, R39 and C27 effectively render the system "dead beat". Finally R40 besides restricting the pull-in range also reduces the d.c. impedance presented to the triode grid of V4.

Line Oscillator

V4a and b form a cathode-coupled multivibrator oscillator. This type of oscillator is useful for applications where a free electrode, namely V4a grid, is needed for the application of a control signal.

The action of the timebase is as follows. We start at a point when V4b control grid is negative and the valve is cut off. V4a is conducting. C30 commences charging exponentially via R46 from the positive h.t. supply. C28 is holding a charge which is decaying at a rate determined by the value of R44 and VR5, the line hold control. Eventually the negative grid potential on V4b has decayed

sufficiently to allow the valve to conduct. Anode and screen grid currents start to flow in V4b and pass through the common cathode resistor R43. The cathode potential of both V4b and V4a rises. So far as V4a is concerned this positive drive on its cathode is the same as a negative drive to its grid. Its anode current falls so causing its anode voltage to rise. This positive rise is conveyed via C28 to the grid of V4b, which in turn produces a further rise of the cathode voltage. The effect is cumulative and very rapid. The positive output (anode voltage) of V4a charges C28 via grid current in V4b. When C28 has charged grid current in V4b ceases and the cathode potentials fall, so turning on V4a. V4a anode potential reverts to normal and V4b is cut-off.

During the period of V4b conduction C30 discharges. It commences recharging when V4b cuts-off. So the output of the circuit is an exponential charging waveform with rapid flyback.

It will be noticed that the cut-on time of V4b is not only a function of its grid time-constant but also depends upon its cathode bias, which during the scan time is determined by the current flowing in V4a. This current is controlled by the grid potential of V4a, so it can be seen that the d.c. potential applied to this grid from the a.f.c. circuit will control the cut-on point of V4b and hence the frequency of the oscillator. Note that R45 and C36 have a time-constant chosen to improve the overall frequency stability of the oscillator.

Line Output Stage

The output circuit of the line oscillator consists of R46, R47 and C30. C30 is the charging capacitor and R46 the charging resistor. R47 is included to control the maximum drive amplitude so that it is less dependent upon valve characteristics. The output waveform is coupled to the grid circuit of the PL36 line output valve via C29. The remainder of the grid circuit consists of the stopper resistor R50 to inhibit parasitic oscillations and R51 the grid d.c. return resistor. The timebase is amplitude stabilised, so R51 is returned to the stabilisation circuit instead of to chassis.

As the line output valve does not saturate when operated in a stabilised circuit it can be regarded as an amplifier, the mean working point of which is controlled by a negative bias derived from the stabilisation circuit. To prevent screen grid feedback, the screen grid is decoupled to chassis by C31. Such a capacitor is not incorporated in line output stages which are used as simple switches, keying power into the line transformer.

The line transformer is an autotransformer with two small auxiliary windings, one for the heater of the e.h.t. rectifier V7 and the other for the comparator pulse output to the horizontal discriminator.

While the line output stage follows what has come to be accepted as conventional design it is useful at this point to consider its method of operation.

We shall start at the end of scan period as this is the most convenient point to begin a description of the line scanning cycle. At this point the current in the scan coils, reflected by the line transformer into the line output valve, is at a maximum. During the scan period it has been increasing with time at a rate determined by the inductance of the circuit

and the applied voltage. V6 is turned on to an extent dependent upon the stabilisation circuit bias (more of this later). The next event is the initiation of the flyback period, when V6 is suddenly turned off by the drive from V4.

The flow of current in V6 ceases abruptly but energy is still contained in the magnetic flux within the scan coils. This because of the cessation of current flow starts to collapse. The collapse of the flux produces in the scanning coils a voltage peak which tries to maintain the original condition, i.e. the anode potential of V6 moves in a positive direction in an effort to maintain the current flow. As V6 however is completely cut off it will not conduct even with a high anode voltage. The circuit would then ring at a frequency determined by the inductances and capacitances present—were it not for V5.

The second half-cycle of the attempted "ring" just referred to causes the cathode of V5 to move negatively with respect to its anode so that it conducts.

As V6 remains cut off the energy in the circuit is transferred to C33 which becomes charged. The efficiency diode V5 effectively damps the circuit and the initial heavy current decreases at a rate again determined by the voltage and inductance.

The reader will probably have observed that the direction of current flow as a result of the damper diode's action is in the opposite direction to that of V6, the line output valve. Also the current is decreasing through V5 whereas it increases with time through V6. This is of course just what we need since the initial high current in V5 places the scan at the extreme left of the screen while the linear decrease moves the spot towards the centre. Thus it will be seen that the damper diode circuit provides the first part of the line scan. The recovered energy stored in C33 is also utilised to provide an increased h.t. rail (the boost rail) which reduces the current demand on V6 so that the efficiency is even further improved.

It will be noticed that the lower end of C33 is connected to earth instead of the h.t. rail as is more usual. This method of connection was adopted in order to reduce the line frequency ripple present on the h.t. rail.

In order to provide e.h.t. for the cathode-ray tube the high voltage positive pulse appearing at V6 anode at the flyback time is stepped up by an overwind on the autotransformer and rectified by V7 the e.h.t. diode. The heater of this valve is supplied by a small winding on the e.h.t. transformer.

The line scanning coils are connected to the line output transformer via capacitor C34. This is an S-correction capacitor. Since 110° scanning is used the c.r.t. is short and its gun is significantly closer to the centre of the screen than to the edges. If the tube is scanned linearly there would thus be more

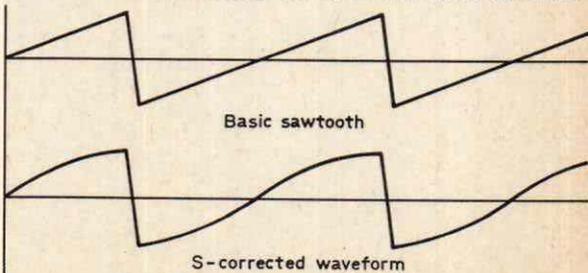


Fig. 7: Illustrating S-correction of line scanning.

movement of the beam near the edge of the screen, where the beam length is greater, than at the centre. Consequently some means has to be devised to increase the scanning speed at the centre of the screen and reduce it at the sides. This means that the scanning current waveform instead of being a saw-tooth must be more S-shaped, as shown in Fig. 7.

The required effect is obtained by placing C34 in series with the scanning coils. The scheme operates by resonance between the inductance of the coils and the correction capacitor. The circuit is pulsed into a damped oscillation by the flyback pulse. It will be seen from Fig. 7 that the correction waveform should be part of a sine wave and by choosing the resonant frequency so that it is around one half of the line frequency or a little less the position of a sine wave initiated by the flyback will modify the scanning waveform to that required.

Stabilisation Circuit

The width stabilisation circuit consists of C35, the v.d.r. E298ZZ/06, VR6 the width control, R54 and R55. The action of the circuit depends upon the characteristics of the varistor—otherwise known as a voltage-dependent resistor. The characteristic is such that when logarithmic applied voltage is plotted graphically against logarithmic internal resistance an approximately straight line results. It will be seen therefore that when presented with unidirectional pulses the v.d.r. behaves as a rectifier conducting significantly on pulses only.

In the circuit shown positive pulses from the scanning coils are applied via C35 to the varistor. Because of the rectification, a mean negative voltage appears at the top end of the varistor. This voltage is coupled to the grid of V6 via R51. Irregularity is effectively smoothed out by C29 and C30 so that the feedback is d.c. only. The negative voltage tends to cut V6 off. It is offset by applying a variable positive current via R54, R55 and VR6 to the varistor. VR6 forms the width control since it sets the operating point of the line output valve. As a result of the action of this circuit any decrease in the output from the timebase will result in the negative bias to V6 becoming less. Thus a greater current will flow, offsetting the decrease in output and stabilising the scan amplitude.

Miscellaneous Details

The heater supply for the line oscillator V4 is taken from the low-voltage 16V winding on the mains transformer. V4 heater is connected in series with that of V2 to make up the 16V. The centre point is decoupled by C42 which serves to shunt transients appearing on the heater line. V5 and V6 heaters are connected in series as part of the 75V heater chain. The heater of V6 is connected to chassis on one side, thus minimising the possibility of a heater-cathode short. In series with the top cap leads of V5 and V6 are small chokes L1 and L2. These chokes may be 1A suppressor types and serve to prevent parasitic oscillations, particularly the Barkhausen-Kurz type, which produce a vertical line on the screen.

The line transformer itself is bolted to the side plate of the receiver by its core securing bolts. In order to mount it this way its mounting lugs as supplied have to be carefully cut off, using tin shears. V7 and its mounting form an integral part

of the assembly, the valve being mounted vertically which helps prevent cathode sag, a problem with horizontally-mounted e.h.t. rectifiers.

When the line transformer is mounted in this position it is surrounded by objects which help to screen it without the need for a specially constructed can. There is the vertical side plate of course (also acting as a heat sink) and the main chassis. The c.r.t. has its outer aquadag coating earthed, which also assists since the c.r.t. is in close proximity to the transformer. Ventilation and cooling of the line timebase are thus very efficient.

The layout diagram (next month) shows the disposition of the components in the line timebase. Note that the lead from the sync separator to the horizontal discriminator is screened.

The h.t. supply for the line oscillator valve V4 is filtered by R48 and C1d which ensure that the supply is completely free from mains ripple. This is essential since the oscillator can be phase modulated by ripple, causing bent verticals. And since the transmissions are asynchronous any bending will move up or down the picture. The well-smoothed h.t. supply for the line oscillator is also used to feed the anode of the sync separator stage, via R56, ensuring that a.c. ripple is not superimposed upon the sync pulses. Such ripple could again produce phase modulation of the line timebase and also disrupt the field synchronisation.

Note that the numbers shown against the connections to the line transformer correspond to those marked on the tag connection layout diagram (Fig. 4). The constructor will find some small components attached to the line transformer. These are not used in this design and may be left *in situ* or removed; it makes no difference.

Remember that all the leads associated with the line timebase carry high voltages, d.c. or pulses or both. Therefore the leads should be spaced away from the chassis and sleeved where they pass through holes. Sufficient insulation is provided on the e.h.t. lead to enable it to touch the chassis however where it emerges from the bottom of the line transformer. When fitting the c.r.t. ensure that the e.h.t. cap connection is adjacent to the line timebase.

Audio Stages

The a.f. amplifier and output circuits are shown in Fig. 8. A conventional triode-pentode valve type PCL82 is used with its heater fed directly from the 16V winding on the mains transformer. The constructor may wonder why a valve as opposed to a transistor amplifier has been used. The main reason is simplicity. A transistor amplifier is rather more complicated than its valve counterpart. If it is to be fed from the existing transistor power supply its varying load, associated with normal class B working, could produce fluctuation of the supply voltage. Such fluctuations could disturb the action of the other transistor circuits so that either a separate power supply or a regulated supply would be needed. In the event of a transformerless output stage being used a high-impedance speaker would be necessary, another difficulty. While if a transformer were to be used it would need to be a special component.

In view of the foregoing considerations a valve circuit has been used with a conventional output

—continued on page 371

REGULAR LONG-RANGE TV RECEPTION

K.E.G. PITT, B.Sc.

PART 2

LAST month we described how it is possible to forecast which television transmissions may be received at a given site, including those normally considered out of range. The aim of these articles is twofold: to help viewers to decide whether or not they are using the best set of transmissions for their location, and to obtain additional ITV or BBC regional programmes to the ones normally used. It may not be generally realised that while the majority of ITV programmes are networked and eventually appear on most of the regional programme companies' schedules, the exact time may vary widely, giving a choice of programmes between adjacent regions. It should be noted however that although a distant transmitter may well give excellent results for most of the time there will be periods in which reception may be marred by interference from much more distant stations sharing the same channel. These freak transmissions often arise as a result of settled weather conditions. During these periods the extra programme may be below entertainment value due to patterning and line pairing effects.

Set Sensitivity

Having first decided which channels may be worth examining by means of transmitter maps as described previously, the set must next be critically examined to see whether it is capable of receiving them. A number of general points are worth considering. The ability of a set to give a reasonable picture on any given channel is governed by its overall sensitivity. If the set is very modern it is probably of high gain with automatic gain control enabling it to peak to its maximum sensitivity without control adjustment. It is also likely to be very much more sensitive than older sets. As a result, if a relatively new set fails to give a picture on a given channel once an aerial for that station is plugged in then probably there is little value in further study.

On an older set a local/distant control or a sensitivity control may preset the gain. Advancing these may bring in a picture. In addition in some earlier sets the contrast control itself acts partially as a gain control and advancing this may help.

The above of course assumes that there is present a set of coils for the required channel. Many modern sets carry coils for all channels or have continuous push-button tuning for Bands I or III. Earlier sets often only had coils for the local BBC/ITA channels, e.g. in the London area 1 and 9 only.

Selectivity

A third factor which may affect the usability of a weak signal is the presence of a strong signal on an adjacent channel which tends to swamp its weaker neighbours. Some recent sets have greater selectivity than earlier ones and are designed to accept adjacent channels without interference. If this is not

the case then it is quite possible that reception of an adjacent weak station will not be practicable.

Aerial System

Having decided that the set is suitable it is necessary to install an aerial system for the extra channels. In really favourable cases adequate pictures can be received on the existing aerial but this is an exceptional condition. It is often the case that the distant transmission is of a different polarisation from the local one. It will almost certainly be in a different direction and often on a channel some way away from the local one.

To get adequate reception of a weak signal the correct channel aerial is necessary. Use of an aerial cut for another channel gives poor results. For example a channel 10 aerial gave adequate results on channel 11 but poor results on 12 and 6 whereas a lower gain commercial broadband aerial gave results on channel 6 as good as the other aerial gave on channel 10 and a little better than previously on channel 12.

Possible Arrangements

The ideal system is to mount a correct channel aerial outside on the existing mast and line up accurately for the desired station. If possible use low-loss coaxial cable to improve the results. To change over aerials one can either use a rotary switch with a common coaxial lead to the set or to avoid losses plug over when required. The rotary switch should not be a paxolin type at 200MHz. A p.t.f.e. or ceramic type is necessary and it should be housed near the set in a plastic box with an insulated knob. This avoids risk of live parts if the aerial socket becomes live due to failure of insulation.

An aerial in the loft may in practice be adequate and is easier and cheaper to install. If the two or more signals desired are of the same polarisation then a rotary mast system and an aerial of sufficient bandwidth to cover all the channels is a possible solution. In the author's own case it was necessary to use three separate aerials and cables with a change-over switch. This was because the three stations required were Croydon (channel 9 vertical) south, Dover (channel 10 vertical) south east, and either Mendlesham (channel 11 horizontal) north east or Sandy Heath (channel 6 horizontal) north. As mentioned above the use of the wrong channel aerial gave poor results.

UHF Reception

Duplication of ITA stations on u.h.f. is also giving an opportunity for long-range reception but here the use of outside aerials is very much more beneficial because of the very great attenuation of these frequencies by roofing materials. Good long-range

colour results are unlikely with loft aerials. For best results in Bands IV and V a separate outside aerial of the correct channel group, direction and polarisation is generally essential. It is preferable to use separate aerials and to plug over to avoid mismatch trouble with a rotary switch.

Installing a Loft Aerial

In general when installing a loft aerial on any Band it is better for the operator to move well away from the aerial while his partner examines the results on the screen because body capacitance can give very misleading results. When installing in the loft it may often be found that some locations are vastly better than others and a little patience can be very well rewarded in the shape of unexpectedly good results.

Preamplifiers

A further increase in gain can sometimes be obtained by the use of a preamplifier. If however the picture is already noisy there may be little benefit in doing so. Best results are obtained by installing the preamplifier at the aerial end of the cable. Some commercial models are regularly advertised in PRACTICAL TELEVISION.

Experimental Investigations

Although a great deal of useful information on aerial installation is available in books and magazines there is much scope for experimental investigation and improvisation and non-conventional techniques often give surprisingly good results. The one area where improvisation must be avoided is electrical safety. Always ensure that an aerial is isolated from the mains, either by deliberately added capacitors or by capacitors present in the set itself.

Overseas Reception

In general one may well be able to receive results from foreign stations regularly, particularly on the south and south east coasts. However the system standards are all different from the British v.h.f. system. The French u.h.f. and v.h.f. systems both use positive modulation on vision with a.m. sound. This means that on v.h.f. pictures and sound can be received on a normal set but not together due to the different bandwidth. The number of lines on v.h.f. is 819 and this is again non-compatible. The French u.h.f. system is equally incompatible due to the positive vision and a.m. sound. Belgian transmissions are 625 lines and may use either positive or negative modulation and a.m. or f.m. sound depending on whether they are to the French- or Flemish-speaking areas.

Other Continental v.h.f. and u.h.f. systems are virtually compatible with the British u.h.f. system. The only country using the British 405-line system, and that only from one main transmitter, is the Republic of Ireland which still transmits R.T.E. from Mt. Kippure, Dublin on 405 lines as well as using the CCIR 625-line system. The latter system is in use exclusively in the rest of the Republic.

It is thus really necessary to have a set specially adapted to receive any regularly available foreign transmissions. It is not practicable to do this with one's normal domestic set. ■

625-LINE RECEIVER

—continued from page 369

transformer and speaker arrangement. The power supply presents little problem since the output stage naturally operates under class A conditions. Separate decoupling and smoothing for the audio section is provided by R3 and C1b.

Audio from the f.m. discriminator is applied to the volume control VR9. The audio signal from the wiper of the control is coupled to the grid of V8a by C37. Grid current biasing is developed across R57. The main sound h.t. supply is further decoupled by R60 and C38 before feeding V8a anode via its load resistor R59 and the screen grid of V8b. The triode V8a amplifier raises the audio signal to a level to drive the output section of V8b. The signal is coupled by capacitor C39 to the grid end of resistor R61. V8b uses conventional cathode biasing (a wire-wound resistor is used here since cathode resistors have the unhappy habit of becoming low-resistance after a while). The cathode resistor is bypassed by C40.

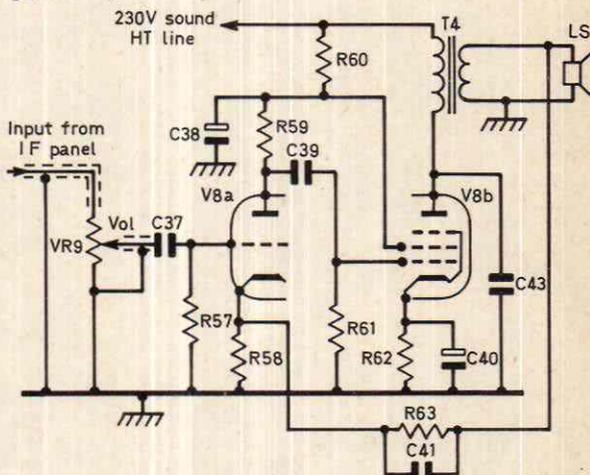


Fig. 8: The audio amplifier and output stages.

Negative feedback from the secondary of the audio output transformer T4 is applied via the network C41, R63 and R58 to the cathode of V8a. This feedback improves the audio quality at the expense of overall gain. To prevent possible h.f. instability the anode of V8b is decoupled to chassis by C43 (0.0047 μ F not 0.047 μ F as shown in the components list).

The audio output will match a 3 Ω loudspeaker and an extension speaker socket can be fitted if desired to the secondary of the output transformer. Also earphones or a deaf-aid earpiece may be connected with complete safety provided the chassis is earthed as recommended.

Note that the leads to and from the volume control should be screened. The audio output transformer is mounted between the speaker and the mains transformer, the leads passing through the hole in the chassis which also carries leads from the mains transformer and r.f. sections.

We shall deal with the i.f. and tuner sections of the receiver next month.

TO BE CONTINUED

UNDERNEATH THE DIPOLE

"IF winter comes, can spring be far behind?" was an optimistic question often quoted fifty years ago. Winter gloom, leafless trees, concrete structural horrors, strikes, taxation, concentrated protein pills (in lieu of juicy steaks) all make up the modern world. Thank goodness that colour television features shot in summer about the countryside, animals, history, beautiful architecture and similar refreshing presentations are kept in deep freeze for winter viewing, particularly by the BBC. Subjects like *Civilisation*, acclaimed all round the world, are antidotes as are also some much smaller (almost insignificant by comparison) colour features from regional ITV stations. Icons (and I'm sure all viewers) asks the BBC and all the ITV major and regionals to preserve some of the 1970 summer on film and tape for serving up in the gloomy days of winter.

FINE ARTS

Will radio and television ever be regarded as "fine arts", in the way the arts of painting, sculpture, engraving and music were considered a couple of centuries ago? These were esteemed as the products of "good taste, elegance, refinement and delicacy" the aesthetic appreciation of which was a matter of understanding the classic rules of the particular fine art concerned.

"Rules are made to be broken" is a commonplace (but inaccurate) saying. But rules are as essential in broadcasting communication as is the punctuation of the written word. In music hall terms, the comedian hopes his act will end with the audience wanting more. The stage actor, playwright and producer crave for applause. But what reaction does the television producer want or for that matter the organisation that employs him?

It is indeed difficult to find a logical reason for televising to the public material which they find offensive and which they can (and frequently do) switch off. After seeing about ten minutes of BBC-1's *The Dance of the Seven Veils* I switched off and resolved not to mention that nasty presentation in this column until I spoke to ten regular television viewers on the following day. Nine of them had switched their sets off or turned over to ITV. The tenth (who was a film director) held on to the end because he said he "couldn't believe such rubbish possible". The newspaper TV critics usually applaud avant-garde rule-breaking trends; but they didn't think much of it either. The only people who benefit from this kind of product from the BBC

are the ITV companies to whose programmes the offended viewers flee.

COMMERCIALS


There is no doubt that colour has put a new dimension into TV commercials—excepting when they are made with videotape. This is usually because videotaping is the only way to make a commercial quickly—because of a rush, because of topicality or because it is cheaper. Tape editing can involve transfers from one videotape machine to another; A and B roll transfers to a third machine; sequential overlaying; guillotining or simple skilled use of a pair of non-magnetic scissors in precisely the right place (when it can be located!). Though the long-established use of 35mm. film with its optically introduced dissolves, wipes and superimpositions will always continue, especially for commercials, the sophisticated use of new technical tricks in video is gaining ground. The extremely high capital outlay of such equipment leads to very high charges per hour for its use. The high speed with which such complicated operations can be carried out could justify the "high cost to low utilisation time" ratio—if the human element, the editor, could do it.

2 EMMA TOC WRITTLE TUESDAY EVEN!

Curiosity always gets the better of me when I see bundles of dusty books in dimly lit junk shops or at jumble sales. Recently I found an almost mint copy of *Broadcasting from Within* by C. A. Lewis ("Caractacus") and published in 1925(?) by George Newnes. It is an unofficial history of the British Broadcasting Company's first year of operations but it also talks of the pre-2LO days—of Captain P. P. Eckersley's tiny 250W transmitting station at Writtle with its call sign 2 EMMA TOC. This station sent out a half-hour programme every Tuesday to the growing number of wireless "hams", beginning operations in February 1921 and discontinuing early in 1923. 2 EMMA TOC transmitted the first wireless play in the United Kingdom—a scene from *Cyrano de Bergerac*—so the Tuesday play came before the Wednesday Play or Saturday Night Theatre!

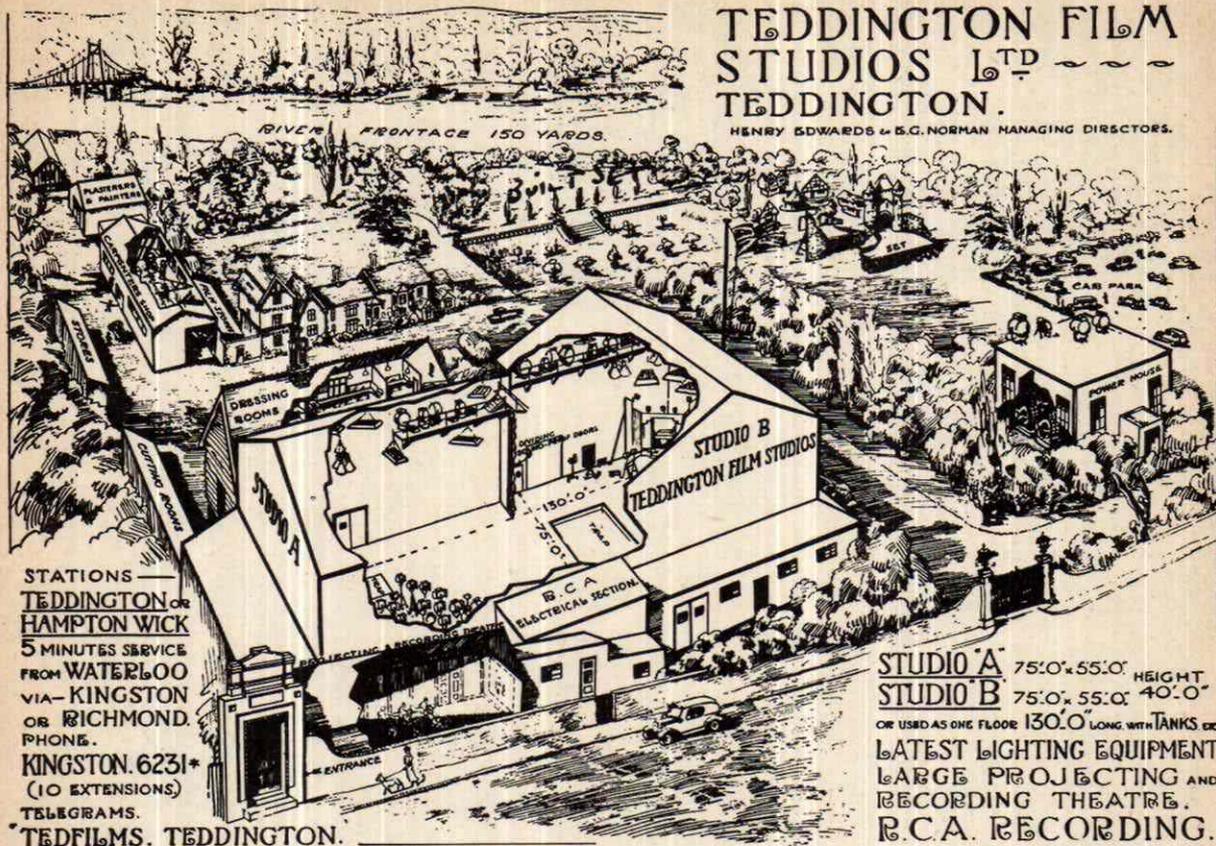C. A. Lewis, or "Uncle Caractacus" as he was known to thousands of children via the early Children's Hour programme, wrote a fascinating book—and the "B.O.P." and "Harry Wharton" atmosphere of those pioneer days comes out in such passages as this about the engineer at a concert broadcast: "... a crackle begins to develop. The concert becomes hopelessly distorted. The engineer leaps to the telephone and asks them to hold the concert up. He then looks quickly over the set... the insulation has broken down in one of the condensers. Off goes the current while a spare condenser seized from the store is quickly connected in place of the dud one. In goes the switch, the generators hum up to their load and the engineer telephones through to the studio 'Carry on, quite O.K.' The station was out of action for perhaps three minutes. Indeed during the total transmission time of the last year the breakdown period was $\frac{1}{4}\%$!" That was the time when BBC HQ were at Savoy Hill, when every programme was broadcast from one studio and one microphone.

Broadcasting from Within told us that "the cost of a transmission station complete is estimated at £8,000" and suggested to aspiring singers that "It's



TEDDINGTON FILM STUDIOS LTD

HENRY EDWARDS & S.G. NORMAN MANAGING DIRECTORS.

STATIONS —
TEDDINGTON OR
HAMPTON WICK
 5 MINUTES SERVICE
 FROM **WATERLOO**
 VIA — **RICHMOND**
 OR **RICHMOND**.
 PHONE.
KINGSTON. 6231*
 (10 EXTENSIONS)
 TELEGRAMS.
***TEDFILMS. TEDDINGTON.**

STUDIO A 75'0" x 55'0" HEIGHT
STUDIO B 75'0" x 55'0" 40'0"
 OR USED AS ONE FLOOR 130'0" LONG WITH TANKS ETC.
LATEST LIGHTING EQUIPMENT
LARGE PROJECTING AND
RECORDING THEATRE.
R.C.A. RECORDING.

worthwhile to be singing for the BBC. Think it over." A few years later the writer of this column designed a new-fangled "dramatic control panel" which controlled the outputs from several studio sources, with artificial echo and group mixing from five volume controls on each side of a central knob. It was unused for nearly a year before a producer summoned up courage to use it. The producer was "Uncle Caractacus".

In a chapter entitled *A Glance Ahead* Mr. Lewis wrote of "stereoscopic broadcasting" and Captain Round's (the Independent Research Department Chief of the Marconi Company) idea that "two transmitters would be kept working on their respective wavelengths, each connected to a microphone in the same studio . . . the listener fortunate enough to have two sets (two crystal sets don't cost so much) would tune to each of the two wavelengths respectively and get the stereoscopic effect."

THAMES TELEVISION STUDIO'S ORIGIN

Teddington is a pleasant riverside suburb of London famous for its lock, footbridge and weir. Close to the weir on the Middlesex side was the secluded mansion Weir House, with stables, coach house, well laid out gardens and river banks ideal for anglers. Except for the noise of the water cascading down the weir and the occasional husky hoot of a passing steamer all was peace and quiet—that was until 1915 when a film company moved in, producing "Ecko" comedies with the inevitable chases and ultimate splashing watery endings.

Interior settings were erected in the grounds on a revolving platform to face the sun. Later a glass-house studio was built, shown in our illustration as Studio A, to which Studio B was later added.

At this time, in 1932, it was soundproofed for talking pictures, using the RCA Phonophone system, under the direction of Henry Edwards. Warner Brothers of the USA leased it for two years and then bought it, adding a new large stage, two theatres, cutting rooms etc. It was bombed in the last war but afterwards restored. It was an ideal site for a studio for big-scale television productions and ABC Television, then with the weekend Birmingham and Manchester ITV franchises, took it over. This was a courageous step, taken when commercial television was losing millions during its first two-three years.

It has now become the main production centre for Thames Television, formed from ABC and Associated Rediffusion, with a second smaller studio complex near Euston. The perspective sketch was kindly lent by Mrs. Henry Edwards (formerly known as Chrissie White the British silent-screen film star). From the earliest days of silent comic policemen—played by Charles Austin, Lupino Lane, Billy Merson and other early crazy-gangers—it was locally referred to as "Weird House". Still in show business it retains that nickname.

Icons

TRANSISTORS IN TIMEBASES



PART 7 FIELD OSCILLATORS

H. W. HELLYER

FIELD timebases develop a lot of power. We can expect the deflection circuits to dissipate some 8W, even for a black-and-white receiver, while for colour reception it may be necessary to allow for half as much again. This has caused the development of fully transistorised field timebases to lag and in the hybrid set we usually find that the field output stage at least is designed around a well-ried valve. In the early days of transistorised television receivers there was a lot of talk about the impossibility of getting rid of the output inductor, and the oscillator-driver part of the circuit was largely taken for granted. Nowadays design concepts take the field timebase as a whole, regarding the oscillator as a switching device and part of a flyback switch.

BASIC DIRECT-COUPLED CIRCUIT

Figure 1 shows in simplified form the basic arrangement commonly used. This is a direct-coupled sawtooth generator using three transistors, the first being shown as a switch. The main action of the circuit is to discharge capacitor C through

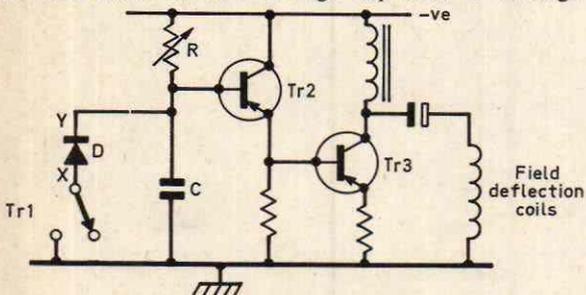


Fig. 1: Basic direct-coupled sawtooth-generator field timebase circuit with oscillator stage Tr1 shown as a switch.

diode D at regular intervals. C charges exponentially depending on the values of C, the variable control R and the supply voltage to provide the sawtooth waveform. When "Tr1" conducts point X will be at nearly ground potential, D will conduct and when C has discharged via D and "Tr1" point Y will be at near ground potential as well. When "Tr1" is cut off again C charges and the sawtooth signal is fed via the emitter-follower Tr2 to the base of the output transistor Tr3. In most practical circuits to date the switching action provided by "Tr1" is achieved by the use of a blocking oscillator circuit.

This basic arrangement provides a good waveform but because of the inductive loading caused by

the presence of the choke in the collector circuit of the output transistor the sawtooth waveform requires modification. This is generally done by adding a

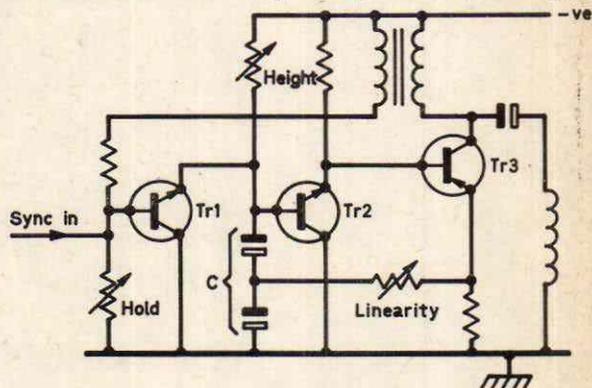


Fig. 2: Self-oscillating timebase circuit in which the flyback pulse caused by the collapse of the field around the deflection coils at the end of the scan is applied to the oscillator via a winding linked to the output inductor and drives the oscillator Tr1 hard on to discharge the scan charging capacitors. Note the introduction of a linearity feedback loop.

parabolic waveform to the sawtooth. A widely used method is shown in Fig. 2 where the charging capacitor C consists of two series-connected capacitors to the junction of which a parabolic waveform is applied from the emitter circuit of the output transistor. This is a self-oscillating circuit in which feedback from the output transformer drives Tr1 hard on so that C is rapidly discharged. The circuit is however for several reasons not a practical proposition. A practical circuit devised by B. E. Attwood, a Mullard engineer, is shown in Fig. 3. This uses an OC81 transistor in a blocking oscillator circuit to provide the switching action.

BLOCKING OSCILLATOR CIRCUITS

We mentioned earlier that points X and Y (Fig. 1) are taken *nearly* to ground. The reason for this is that small leakage currents prevent full bottoming of the switching transistor. The circuit in Fig. 3 allows for this: an overwinding is provided on the collector winding of the blocking oscillator transformer T1 and the positive voltage produced across this winding backs off the voltage drop across the transistor and OA10 diode. This reduces the standing current in the output transistor. By adjusting the

LAWSON BRAND NEW TELEVISION TUBES



SPECIFICATION: The Lawson range of new television tubes are designed to give superb performance, coupled with maximum reliability and very long life. All tubes are the products of Britain's major C.R.T. manufacturers, and each tube is an exact replacement. Tubes are produced to the original specifications but incorporate the very latest design improvements such as: High Brightness Maximum Contrast Silver Activated Screens, Micro-Fine Aluminising, Precision Aligned Gun Jigging, together with Ultra Hard R.F. High Vacuum Techniques.

DIRECT REPLACEMENTS FOR MULLARD-MAZDA BRIMAR GEC, ETC.

A47-11W (P)	MW53/20	T914	CME1901	21C2P4
A47-13W (T)	MW53/80	C19/10A	CME1902	21DKP4
A47-14W	AW-47-97	C19/10AP (T)	CME1903	23SP4
A47-17W (P)	AW-53-80	C19/AK	CME1905	171K
A47/18W (P)	AW53-88	C21/1A	CME1906 (T)	172K
A59-11W (P)	AW53-89	C21/7A	CME1908	173K
A59-12W (P)	AW59-90	C21/AA	CME2101	212K
A59-13W (T)	AW59-91	C21/AF	CME2104	7205A
A59-14W (T)	C17/1A	C21/KM	CME2301	7405A
A59-15W	C17/4A	C21/SM	CME2302	7406A
A59-16W (T)	C17/5A	C21/TM	CME2303	7502A
AW36-80	C17/7A	C23/7A	CME2305 (P)	7503A
AW43-80	C17/AA	C23/10A	CME2306 (T)	7504A
AW43-88	C17/AF	C23/AK	CME2308	7601A
AW43-89	C17/EM	C23/AKT (T)	CRM173	7701A
AW47-90	C17/HM	CME1402	CRM212	CRM121
AW47-91	C17/SM	CME1702	CRM211	MW31-74
MW43-69	MW/53-80	CME1703	I7ARP4	
MW43-64	T908	CME1705	I7ASP4	
MW43-80	T911	CME1706	I7AYP4	

FOR YOUR INFORMATION

Experience of supplying CRTs over many years has shown us that when a customer requires a new CRT he means **Immediately**. We at Lawson's are geared to give a by-return service. Tubes are sent fully insured by passenger train. Goods or Road Services are not used, delivery taking far too long for customer satisfaction.

		Carr.
		Insur.
12-14" Types	£4.10.0	10/-
16-17" "	£5.19.0	12/6
19" "	£6.19.0	12/6
21" "	£7.19.0	12/6
19" Panorama (P)	£8.10.0	12/6
23" Mono	£9.10.0	15/-
23" Panorama (P)	£11.10.0	15/-
19" Twin panel (T)	£9.17.6	15/-
23" Twin panel (T)	£12.10.0	15/-

LAWSON TUBES STATION ESTATE, MALVERN


Offices
18 CHURCHDOWN ROAD,
MALVERN, WORCS. MALVERN 2100

2 YEARS' FULL REPLACEMENT GUARANTEE

Complete tube fitting instructions are supplied with each tube.

Are people being stubborn by insisting on the Minitest?

No. Just choosy!

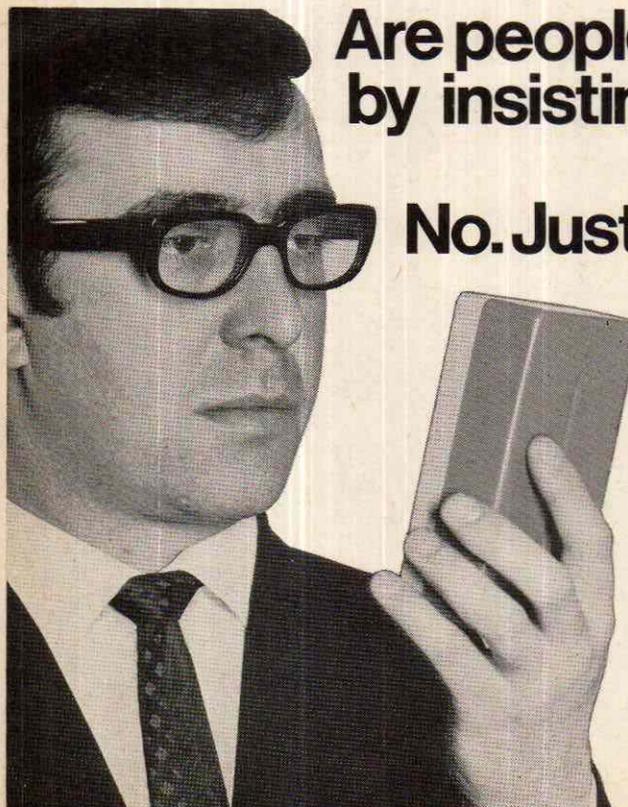

Diminutive, sensitive, neat, tough. These are the adjectives that describe the S.E.I. Minitest. You will never be provoked into using any other for years, hence this pocket size, multi-range test set will be serving you accurately. The Minitest measures a.c. and d.c. voltages, d.c. current, and resistance over 20 ranges to a sensitivity of 20,000 and 2,000 ohms per volt d.c. and a.c. respectively. Readings are instantaneous and the minutest is clearly discernible. A steel case shields the movement from external magnetic fields and shocks. This has a robust, wipe-clean, melamine cover. All controls are handily disposed. High voltage probes are available to extend the range of the Minitest to 25 or 30kV d.c. for testing electronic equipment with high source impedance. They can be used with any other meter of similar sensitivity. Wisdom suggests Minitest and S.E.I. probes together, right from the start. Act now: Send for the catalogue.

We manufacture a wide range of portable instruments... write today for full information.



SEI

S&C

SALFORD ELECTRICAL INSTRUMENTS LIMITED
Peel Works, Barton Lane, Eccles, Manchester M30 0HL.
Telephone: 061-789 5081 Telex: 66711
A Member Company of G.E.C. Electrical Components Ltd.

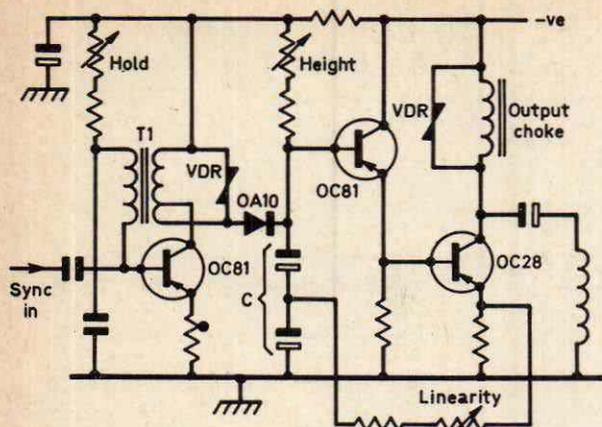


Fig. 3: Practical field timebase circuit using a blocking oscillator stage. Note the tapping on T1 primary, explained in the text.

height control the rate of charge of the C pair of capacitors is varied whilst in the feedback loop a linearity control gives parabolic waveform correction. This basic field generator scheme has been widely used and is to be found for example in the early Pye Model TT1, the Perdio Portarama and the BRC 2000 and Pye group dual-standard colour chassis.

PHILIPS T-Vette CIRCUIT

An example of "the same thing with a difference" is the circuit used in the Philips T-Vette and shown in Fig. 4. Here Tr1 is the blocking oscillator transistor and the sync pulses are applied to a tertiary winding on the blocking oscillator transformer T1. The speed is set by C1, R1 (the hold control) and R2. Tr1 is again used to discharge the charging capacitors C2 and C3 and since the discharge current flows through Tr1 and the collector winding on T1 in series we again get the problem that the potential across the collector circuit prevents the full discharge of C2 and C3 during the flyback period. In this circuit this problem is overcome by the feedback winding on T2 which provides the necessary backing-off voltage.

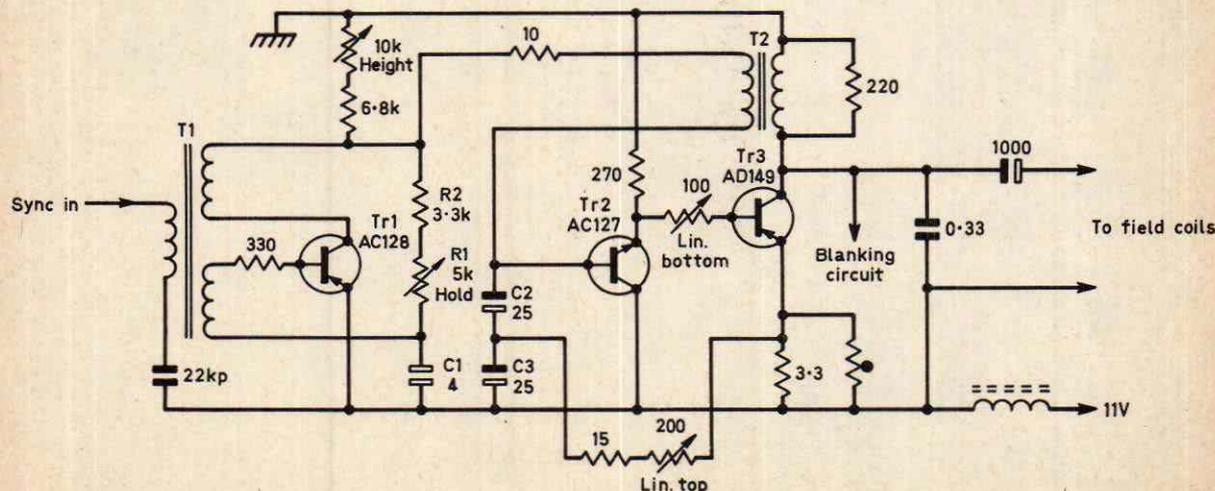



Fig. 4: A further practical blocking oscillator example, as used in the Philips portable T-Vette.

TRANSISTOR MULTIVIBRATOR

Until recently the blocking oscillator has reigned supreme in transistorised field oscillator circuits. However with the recently introduced BRC 3000 single-standard colour chassis we come upon the first use of a multivibrator circuit in this position—and a somewhat unusual one at that, as Fig. 5 shows. At first sight this looks like a triggered monostable circuit, since we have an RC time-constant network as one cross-coupling whilst the other cross-coupling is resistive. However it is free-running, which is in fact necessary if the field is not to collapse every time we change channels or pull the aerial lead out. Let's look at the circuit operation in detail. The operation is of course controlled by the time-constant network R2, C1, R3, R4 and R5. Suppose that Tr1 is cut off. Its collector voltage will be at almost h.t. potential and C1 will charge rapidly to almost h.t. The positive potential at Tr2 base will drive it hard on, but as C1 charges negatively with respect to Tr2 base Tr2 will be rapidly cut off. With Tr2 off its collector voltage will rise to the rail voltage and because of the resistive cross-coupling via R6 Tr1 will be turned on and its collector voltage will fall. When this occurs C1 will begin to discharge so that the voltage at the base of Tr2 is positive-going. Eventually Tr2 base will be sufficiently positive for it to conduct and the sequence of operations will be repeated, the fall in Tr2 collector voltage driving Tr1 towards cut off and C1 rapidly charging to the h.t. potential. The negative-going sync pulses applied to Tr1 base assist the action in driving Tr1 off. Tr2 conducts for only a brief period each cycle so that the output from it is as shown a series of negative-going pulses at field frequency. These pulses are in fact the discharge current of the charging capacitors C2 and C3 as they discharge via D2 and Tr2. The resistance in series with the charging capacitors trims the start of the scan (top of the picture) and the term "sit-up" adjustment is applied to this.

SILICON CONTROLLED SWITCH CIRCUIT

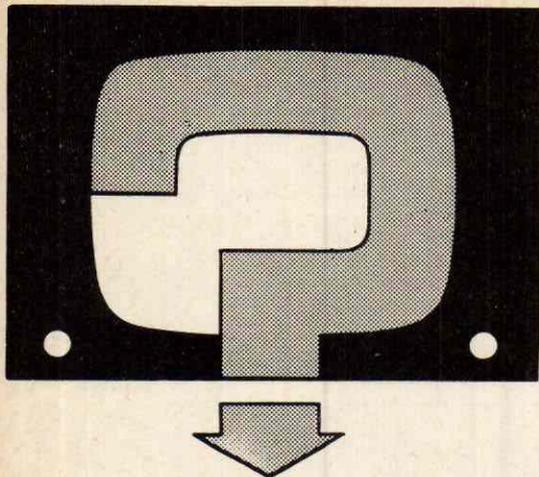For something quite new in timebases we return to Mullard who have developed (B. E. Attwood again and B. J. Simpson) a field generator circuit



EKCO T344

After about half-an-hour the lower part of the picture becomes inverted to a depth of 3-4in. The rest of the picture is OK. The inverted band can only be removed by switching off and giving the set a considerable while to cool down.—A. Corbett (Oldham).

Try changing the field output valve—testing it won't show up a heat-induced fault. This is the most probable trouble. If the valve proves to be OK check the following components: 50 μ F cathode decoupler; 22k Ω resistor in series with an 0.05 μ F capacitor across the primary of the field output transformer; 150k Ω feedback resistor; VA1033 thermistor in series with the field scan coils.

HMV 2700 COLOUR RECEIVER

After ten months' operation two of the convergence controls (R27 blue amplitude and R23 blue tilt—625) became ineffective due to overheating. They were replaced with identical components but after a similar interval there are again signs of breakdown.—A. S. Ball (London SW2).

Component overheating is certainly not general with the BRC colour chassis. The two controls are driven by a d.c. signal from the line timebase circuit to control the horizontal position of the blue raster. If the raster is badly out-of-centre there would be a higher than usual voltage across these controls. If this is not the case component failure must be assumed. The things to check would be the static clamp transistor W2 (AC153), C6 (0.22 μ F), the flying lead from PL16/2 to the timebase panel and on the timebase panel itself diodes W6 and W7 (BA148), electrolytics C26, C27, C28 and C29 and resistors R23 and R24. Also ensure that the winding these components are fed from is not open-circuit on one side.

PYE V200

After approximately 15 minutes a white line appears at the bottom of the screen and slowly widens to 2in., developing into a foldover leaving two inches under the picture black. I have replaced the PCL82, also C74, C60 and C58.—J. Dennis (Yorkshire).

We advise you to check the PCL82 cathode com-

YOUR PROBLEMS SOLVED

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply service data or provide instructions for modifying equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from page 379 must be attached to all Queries, and a stamped and addressed envelope must be enclosed.

ponents C62, R81 and also the screen grid feed resistor R85. Make sure that the boost volts at the upper end of R70 are correct.

MURPHY 625 VIDICON CAMERA

I have two Murphy 625-line cameras—one behaves perfectly but the other in addition to having spots on the screen produces a moving background. This is a shading effect more apparent in poor illumination and also seems to affect the camera line scan. Interlace is non-existent.—D. Bridger (Kent).

The spots on the screen of your faulty Murphy vidicon camera are caused by particles of dust which fall on to the photoconductive material inside the tube and make the particular spots on which they fall non-conductive to the electron beam. The dust sticks to the layer and so the only solution is replacement of the tube itself. For this reason it is a rule with all types of camera tube that they are not carried face-down and that they are not operated with a declination angle of more than about 60 degrees.

We feel that the second fault is almost certainly due to the lack of interlace causing target redistribution effects and causing the video clamps to give incorrect reference levels. This lack of interlace could be a fault almost anywhere in the pulse generation circuitry and should not be difficult to find using a scope and the waveforms given in the manufacturers' handbook. What to look for is the point where the field train loses a pulse timing, either by having insufficient number or too many broad pulses or equalising pulses.

FERGUSON 546T

This receiver has lines expanded from the middle of the screen to the top but crushed in to the bottom. The problem does not seem to be curable by the height control or by centring the picture. I have replaced several valves but the fault persists.—J. Campbell (N. Ireland).

The trouble is associated with the lower PCL82 valve (near the PY32). Check this valve, the electrolytic capacitor and bias resistor associated with pin 2 and the 0.01 μ F feedback capacitor from the linearity control.

EKCO T433

The set works OK most times but if knocked the sound is distorted with a high-pitched whistle appearing. I have cleaned the push-button switch but the results are still the same. The whistle sometimes comes on when the set has not been knocked.—J. Alvey (Bordon, Hants).

The way in which the fault appears suggests a mechanical error rather than a component fault. Check connections in the receiver for dry-joints, broken resistors, poor earth connections etc. To cause a whistle, the fault is most likely to be in the r.f./oscillator section.

PHILIPS 23TG152A

For about one-third of the picture at the top of the screen the lines are more widely spread apart, giving the impression of double lines. This is on ITV and BBC-1. The field hold and line hold have been troublesome and I have changed valves ECL80 and PCL85. I switched over the two ECC82s and this put things right for one night's viewing.—E. Brooks (Eccles).

Check the PCL85 valve and the two cathode "drop-off" resistors (ensure that there are two). Also check the cathode electrolytic (100 μ F), then check the smaller field output stage capacitors. Check the resistors on pins 6 and 8 of the ECL80, and the video stage PL83 and its associated components.

BUSH TV76

The fault with this receiver is lack of width. Recently I replaced all the valves except the e.h.t. rectifier and the ECC83 in the timebase unit. At the same time the height control inside the set was adjusted to give full picture height with the preset control for external setting at its fullest. The width control is at maximum but there is still a margin on either side of the screen, measuring approximately 1in. All valves are giving full emission and there is a good fat spark on the e.h.t. connector to the tube. There is also an annoying hum present which can be temporarily removed by adjusting the fine tuner control—this returns after a few minutes though.—T. Griffin-Thomas (Glamorgan).

We suggest you replace the h.t. rectifier on the lower-right side. Use an exact replacement or a silicon diode (BY100) in series with a surge resistor of about 25 Ω (wire-wound 10W).

QUERIES COUPON

This coupon is available until May 21, 1970, and must accompany all Queries sent in accordance with the notice on page 378.

PRACTICAL TELEVISION, MAY 1970

TEST CASE



90

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

? No brightness could be obtained on a Ferguson Model 3639 so the first check made was for tube bias. This was found to be reasonably correct (cathode and grid relative to chassis) and the effective grid-cathode bias was normally adjustable over the range of the brightness control.

With the aerial removed a very weak line whistle could be heard as the line hold control was rotated, but lack of line drive was discounted because the line output valve showed no signs of overload. The valve remained at a fairly normal (hot) temperature even during protracted periods of testing. If there is no line drive this valve generally gets very hot, its anode glowing red.

Voltage tests revealed abnormally low voltage at the screen grid of the line output valve (PL81A) and at the two anodes of the oscillator valve (6/30L2),

but subsequent tests of the feed resistors showed these to be of the correct values.

What important component was overlooked? See next month's PRACTICAL TELEVISION for the answer to this problem and for a further Test Case item.

SOLUTION TO TEST CASE 89 Page 331 (last month)

After correcting the low width and low boost voltage symptoms the technician should have investigated the cause of the overbright heaters. Had a service sheet or manual been available it would have been seen that in the KB VC11 chassis a BY100 rectifier is employed in series with the heater circuit as a mains dropper. This works by rectifying the a.c. which reduces its effective "heating power" so far as the valve heaters are concerned. In this way the heater current is cut to a value equal to the heater requirements, and because this type of silicon rectifier is very efficient hardly any heat is generated in the voltage-dropping process.

The voltage at the junction of the heater chain and a series VA1015 varistor should have been 89V but instead the technician read a value of a little over 200V. Removing the BY100 and checking the current through it both ways (this can be done with an ordinary ohmmeter) indicated clearly that the junction was shorting. There should be a very high resistance one way and a virtual short-circuit the other way. Rectifier replacement solved the problem.

WILLOW VALE ELECTRONICS

LIMITED

The Service Department Wholesalers

4 THE BROADWAY, HANWELL, LONDON, W.7

Telephones: 01-567 5400 01-567 2971 01-579 3582

Compare our prices

e.g. NEW 19" C.R.T's . . . OUR PRICE £5-19-0 Plus 10/6 carriage

Normal trade £7-13-4 SAVE £1-3-8 per tube

All 14, 16, 17, 19, 21, 23 and 25 inch C.R.T's in stock at really good discounts to you as the above example shows.

TUBULAR CAPACITORS (3's)		BIAS ELECTROLYTICS (3's)		SUB-MINIATURE ELECTROLYTICS (3's)		RADIO/TV GLASS FUSES	
Please note: Components are sold in packs, quantities per pack are shown under each heading. Prices are per piece of each value.							
TUBULAR CAPACITORS (3's)		BIAS ELECTROLYTICS (3's)		SUB-MINIATURE ELECTROLYTICS (3's)		RADIO/TV GLASS FUSES	
·001 400v. 9d.	25mfd 25v. 1/6d.	1mfd 18v. 1/8d.	50mfd 25v. 1/8d.	2mfd 18v. 1/8d.	1 amp, 1.5 amp, 2 amp, 3 amp. Per dozen 3/0d.		
·0022 600v. 9d.	100mfd 25v. 1/11d.	4mfd 18v. 1/8d.	100mfd 25v. 1/8d.	5mfd 18v. 1/8d.			
·0033 600/1500v. 9d.	250mfd 25v. 3/0d.	8mfd 18v. 1/8d.	250mfd 25v. 3/0d.	10mfd 18v. 1/8d.			
·0047 600/1500v. 9d.	500mfd 25v. 3/8d.	16mfd 18v. 1/8d.	500mfd 25v. 3/8d.	16mfd 18v. 1/8d.			
·01 400v. 10d.	1000mfd 12v. 6/0d.	32mfd 18v. 1/10d.	1000mfd 12v. 6/0d.	25mfd 18v. 1/8d.			
·022 600v. 11d.	2000mfd 30v. 5/9d.	50mfd 18v. 1/10d.	2000mfd 30v. 5/9d.	32mfd 18v. 1/10d.			
·033 600v. 11d.	2500mfd 30v. 9/0d.	100mfd 18v. 1/10d.	2500mfd 30v. 9/0d.	50mfd 18v. 1/10d.			
·047 600v. 11d.	3000mfd 30v. 9/6d.	200mfd 18v. 2/3d.	3000mfd 30v. 9/6d.	100mfd 18v. 1/10d.			
·1 600v. 1/-d.	5000mfd 30v. 10/0d.			200mfd 18v. 2/3d.			
·22 600v. 2/-d.	25mfd 50v. 1/8d.			THI 1/6d.			
·47 600v. 2/10d.	50mfd 50v. 2/0d.			2/4d.			
·01 1000v. 1/1d.	100mfd 50v. 2/6d.						
·022 1000v. 1/1d.	250mfd 50v. 3/8d.						
·047 1000v. 1/8d.	500mfd 50v. 4/6d.						
·1 1000v. 1/8d.	2000mfd 50v. 9/0d.						
·22 1000v. 2/8d.	2500mfd 50v. 10/6d.						
·47 1000v. 3/8d.							
·001 1500v. 1/6d.							
WIRE-WOUND RESISTORS (3's)		SMOOTHING ELECTROLYTICS		RECTIFIERS		CARBON FILM RESISTORS	
10 watt rating, suitable for mains dropper sections.		Wire ended, 450v. working.		Silicon Mains (3's)		½ watt and 1 watt.	
1 Ohm 1/9d.	1mfd 1/6d.			Westinghouse S10AR2 6/6d.		The following values are packed in cartons of six of each value. Price 2/6d. per carton.	
10 Ohms 1/9d.	2mfd 1/6d.			BY127 Mullard 5/3d.			
13 " 1/9d.	4mfd 2/3d.			BY105 Mazda 7/0d.			
25 " 1/9d.	8mfd 2/6d.			BY327 5/6d.			
33 " 1/9d.	16mfd 3/0d.			CONTACT COOLED FULL WAVE			
50 " 1/9d.	32mfd 4/6d.			75ma 12/8d.			
87 " 1/9d.	50mfd 5/0d.			100ma 13/8d.			
100 " 1/9d.	8/8mfd 4/0d.			150ma 16/8d.			
150 " 1/9d.	8/16mfd 5/0d.			CO-AXIAL PLUGS			
220 " 1/9d.	16/16mfd 5/0d.			Bakelite top 10d.			
330 " 1/9d.	16/32mfd 5/0d.			Egen metal 1/4d.			
1K " 1/9d.	32/32mfd 5/0d.			Single point (car radio) 2/0d.			
2.2K " 1/9d.	50/50mfd 8/0d.			SLIDER PRE-SETS (3's)			
3.3K " 1/9d.	50/50/50mfd 10/0d.			100K 1/6d.			
4.7K " 1/9d.				1 Meg 1/6d.			
				2.2 Meg 1/6d.			
PULSE CERAMICS (3's) 12KV		CANNED ELECTROLYTICS		JACK PLUGS		DIN PLUGS (3's)	
100pf 22pf 1/1d.	100/200mfd 12/6d.			Chrome standard 4/0d.		3-pin 1/10d.	
120pf 47pf 1/1d.	100/400mfd 16/6d.			Standard 3/0d.		5-pin 2/2d.	
180pf 68pf 1/1d.	200/200mfd 16/0d.			3.5mm. metal 3/0d.		Sockets 1/0d.	
250pf 1/1d.	200/400/100mfd 18/6d.						
Tubular type for use in Scan correction circuits and Line Outputs.	100/300/100/16 18/6d.						
	100/400/32mfd 18/6d.						
	100/400/64/16 21/0d.						
CERAMICS (6's)		SKELETON PRE-SETS (3's)		DOUBLE DIODE RECTIFIERS (3's)		VOLUME CONTROLS	
500pf 22pf 8d.	25K Vertical 1/4d.			Bush/Murphy/BRC etc. 6/3d.		Standard spindle with flat. 4/7d.	
690pf 47pf 8d.	50K " 1/4d.			Line/frame timebases etc. 6/3d.		Double pole switch 3/6d.	
820pf 68pf 8d.	100K " 1/4d.			3 leg 6/3d.		Without switch (One per pack) 3/6d.	
1000pf 100pf 8d.	250K " 1/4d.			4 leg 6/3d.		5K, 10K, 25K, 50K, 100K, 250K, 500K, 1 meg, 2 meg.	
1500pf 120pf 8d.	500K " 1/4d.			5 leg 6/3d.			
3000pf 180pf 8d.	1 meg Horizontal 1/4d.						
5000pf 8d.	680K " 1/4d.						
	1 meg " 1/4d.						

RECORD PLAYER CARTRIDGES

ACOS: GP67/2g. High gain general purpose Mono
 GP91/3SC. Stereo-compatible replacement
 GP91/3SC. High gain version of above
 GP94/1SS. Stereo cartridge

16/8d.
 22/0d.
 22/0d.
 37/9d.

GENERAL PURPOSE REPLACEMENT FOR TC8 s etc.
 High gain, plenty of output (Jap.)
 Stereo version

19/10d.
 37/9d.

SERVISOL AND ELECTROLUBE PRODUCTS (Nett trade)

Servisol aerosol can
 Electrolube 2AX aerosol
 Servisol Freezit
 Electrolube No. 1 Snorkel
 Electrolube 2GX Grease
 Servisol Aero-Clene for tape heads
 Servisol Aero-Duster

12/6d. nett
 14/0d. nett
 9/6d. nett
 18/0d. nett
 8/4d. nett
 10/6d. nett
 10/6d. nett

REPLACEMENT STYLI

TC8 4/6d.
 GC8 4/6d.

REBUILT AND NEW TUBES—TWO YEARS GUARANTEE

RE-BUILT	BRAND NEW	A FEW SAMPLE TYPES, REMEMBER WE STOCK EVERY TUBE
17" @ £4 14 6	£5 10 0	CME1702, AW43-80, CRM173, MW43-80, MW43-69*, CRM172*, AW43-88, AW43-89, CME1705, CME1703, C17AF, C17SM etc.
19" @ £4 17 6	£5 19 0	CME1903, CME1902, CME1901, AW47-90, AW47-91, A47-14W C19AH, C19AF, C19A.
21" @ £6 5 0	£8 10 0	CME2101, AW53-88, AW53-89, CRM211*, CRM212*, MW53-20*, MW53-80*.
23" @ £6 5 0	£8 19 0	CME2303, CME2301, AW59-90, AW59-91.
ALL PRICES ARE NETT.		* NEW ONLY. NO REBUILDS
TWIN PANELS 19" CME1906 A47-13W } £10 1 0		23" CME2306 A59/13W } £14 1 0

EVERY TUBE IN STOCK INCLUDING 11", 12", 16" PORTABLES, PANORAMA & RM GUARDS + Philips Tvette and KB Featherlight etc. TERMS: CASH WITH ORDER. CARRIAGE ANYWHERE IN GT. BRITAIN 10/6 per Tube

HOT-LINE ORDERS
 Tel: 01-567 5400/2971
 TRADE ONLY

e.g. New VALVES . . . 33 $\frac{1}{3}$ plus 13% plus quantity discounts 6%

RADIO AND TELEVISION VALVES SMALL SELECTION

British made valves normally supplied. EVERY TYPE IN STOCK

DY86/7	10/-	EY86/7	10/-	PCL86	11/4
DY802	9/1	EZ80	10/10	PD500	31/7
EABC80	12/8	EZ81	8/2	PFL200	15/9
EB91	8/2	EZ90	9/3	PL36	16/4
EBC90	10/10	GZ34	13/7	PL81	13/7
EBF80	10/10	GY501	15/9	PL81A	14/6
EBF89	10/10	PC86	14/6	PL82	10/10
ECC81	10/0	PC88	14/6	PL83	13/8
ECC82	10/0	PC97	10/10	PL84	12/8
ECC83	10/0	PC900	12/8	PL302	13/7
ECC804	15/4	PCC84	10/0	PL504	20/-
ECH81	14/6	PCC88	16/8	PL508	20/4
ECH84	12/8	PCC89	13/7	PL509	31/7
ECL80	9/6	PCC189	13/7	PY33	12/2
ECL82	12/8	PCC806	15/9	PY81	10/10
ECL83	13/4	PCF80	11/4	PY800	10/10
ECL84	11/4	PCF86	13/7	PY801	10/10
ECL86	12/8	PCF87	18/1	PY82	8/4
EF80	9/6	PCF801	13/7	PY83	13/7
EF85	12/8	PCF802	13/7	PY500	20/4
EF86	16/4	PCF805	14/11	UABC80	13/7
EF89	10/10	PCF806	13/7	UCH81	13/7
EF183	12/8	PCF808	14/11	UCL82	12/8
EF184	12/8	PCL82	11/4	UCL83	14/6
EH90	13/7	PCL83	13/4	UL41	14/6
EL34	10/0	PCL84	13/7	UL84	12/8
EY51	13/7	PCL85	13/7	UY85	9/0

ALL MAZDA/BRIMAR TYPES IN STOCK.

TRADE & SERVICE ENGINEERS ONLY SUPPLIED

Cash with order. 10% MAY BE DEDUCTED FROM THE ADVERTISED PRICES EXCEPT FOR NETT ITEMS, C.O.D., OR TUBES

All orders must exceed 50/0d. in value otherwise postage and packing will be charged at 5/0d. per invoice. Components must be ordered in multiples as packed.

SEE WHAT YOU SAVE AT WILLOW VALE, THE SERVICE DEPT. WHOLESALE, 4 THE BROADWAY, HANWELL, LONDON, W.7. 01-567/5400-2971, 01-579 3582.

Send 2/6d in loose stamps for our comprehensive catalogues listing valves, components, tubes, transistors, mikes, aerials, Line output transformers. BY RETURN SERVICE ANYWHERE.

L.O.P.T.'s

LINE OUTPUT
 TRANSFORMERS

ALL MAKES SUPPLIED

EXCHANGE UNITS AND
 NEW REPLACEMENTS

EVERY MAKE SUPPLIED
 (EXCEPT MURPHY OIL-FILLED)

REWIND SERVICE FOR
 OBSOLETE MODELS

FRAME OUTPUT, SOUND OUTPUT AND
 MAINS TRANSFORMERS REWOUND



REMEMBER . . . We are the Service department Wholesalers and supply only the Service Engineers requirements and can therefore carry large stocks, and also we know and understand your problems regarding getting the right spares QUICKLY and the RIGHT PRICE. HOT-LINE Orders: 01|567 5400-2971. 01|579-3582.

Practical Television Classified Advertisements

The pre-paid rate for classified advertisements is 4/- per line (minimum order 12/-), box number 1/- extra. Semi-display setting £2 10s. 0d. per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL TELEVISION and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, PRACTICAL TELEVISION IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4, for insertion in the next available issue.

SITUATIONS VACANT

ENGINEERS. A TECHNICAL CERTIFICATE or qualification will bring you security and much better pay. Elem. and adv. private postal courses for C. Eng., A.M.I.E.R.E., A.M.S.E. (Mech. & Elec.), City & Guilds, A.M.I.M.I., A.I.O.B., and G.C.E. Exams. Diploma courses in all branches of Engineering—Mech., Elec., Auto., Electronics, Radio, Computers, Draughts, Buildings, etc. For full details write for FREE 132 page guide: BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, (Dept. 171K), Aldermaston Court, Aldermaston, Berks.

RADIO AND TV Exams and Courses by Britain's finest home study School, Coaching for Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Certificate etc. Free brochure from British National Radio School, Russel Street, Reading.

TECHNICAL TRAINING

CITY & GUILDS (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, TV, automation, etc., send for 132-page handbook—FREE. B.I.E.T. (Dept. 173K), Aldermaston Court, Aldermaston, Berks.

EDUCATIONAL

BECOME "Technically Qualified" in your spare time guaranteed diploma and exam. Home-study courses in radio TV servicing and maintenance. T.T.E.B. City and Guilds, etc., highly informative 120-page Guide—FREE. CHAMBERS COLLEGE Dept. 858K, 148 Holborn, London, E.C.1.

TV and RADIO, A.M.I.E.R.E., City & Guilds, R.T.E.B., Certs., etc. on "Satisfaction or Refund of Fee" terms. Thousands of passes. For full details of exams and home training courses (including practical equipment) in all branches of Radio, TV, Electronics, etc., write for 132-page Handbook—FREE. Please state subject. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 172K), Aldermaston Court, Aldermaston, Berks.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Closed circuit TV, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for FREE prospectus and find out how ICS can help you in your career.

ICS, DEPT. 560, INTERTEXT HOUSE, STEWARTS ROAD, LONDON S.W.8.

MISCELLANEOUS

TELEKINESIS, hyperspace, time-reversal, fingervision (U.S.S.R.). Send S.A.E.: Paraphysical Laboratory, Downton, Wilts.

T.V. CAMERA on 405 line system. In working order. Changing to 625 system. £75 o.n.o. VISION SCREEN SERVICES, NORTH FAMBURGE, ESSEX.

Be well-equipped

You need not worry about the painful and lingering minor burns that occur from time to time in leisure pursuits if you keep BURNEZE close to hand. This unique new scientific aerosol cools and anaesthetizes. BURNEZE takes the heat out of a burn in just 8 seconds, then controls the blistering and pain that steal skill from nimble fingers. Be well-equipped - buy BURNEZE, from chemists.

Potter & Clarke Ltd Croydon CR9 3LP



REACTIVATE THAT TUBE, send 15/6d. for circuit and constructional details to VARNE, 10, Marine Parade, Folkestone, Kent.

SERVICE SHEETS

LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

FREE. Fault Tracing Guide or TV list on request with order. 10/- each, plus large S.A.E.

(Uncrossed P.O.s please, original returned if service sheets not available.)

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number/alternative.

Mail order only.

SERVICE SHEETS (continued)

TRADER SERVICE SHEETS

5/- each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

OAKFIELD ENTERPRISES

LIMITED
30 CRAVEN STREET, STRAND
LONDON WC2

Make	Model	Radio/TV

1970 List now available at 2/- plus postage

If list is required indicate with X

From

Address

enclose remittance of
(and a stamped addressed envelope)
s.a.e. with enquiries please
MAIL ORDER ONLY (May PT)

SERVICE SHEETS (1925-1970) for Televisions, Radios, Transistors, Tape Recorders, Record Players etc., by return post, with free Fault-finding Guide. Prices from 1/-. Over 8,000 models available. Catalogue 2/6. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex.

SERVICE SHEETS. Radio, TV etc. 8,000 models. List 2/-. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS with Free Fault Finding Chart, 4/6. S.A.E. Lesmar, 15 Conholt Rd., Andover, Hants. (Mail only).

RADIO, TELEVISION over 3,000 models—JOHN GILBERT TELEVISION, 1b Shepherds Bush Road, London, W.6. SHE 8441.

FOR SALE

VALVE CARTONS at keen prices. Send 1/- for sample and list. J. & A. BOX-MAKERS, 75a Godwin Street, Bradford 1.

WANTED

SERVICE SHEETS AND MANUALS PURCHASED. Highest prices paid. Sultan Radio, 29 Church Road, Tunbridge Wells, Kent. Phone: T.W. 22093.

CASH PAID for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

SERVICE SHEETS purchased, HAMILTON RADIO 54 London Road, Bexhill.

WANTED new valves, television, radio-grams, transistors, etc. STAN WILLETTS 37 High Street, West Bromwich, Staffs. Tel: WES 0186.

WANTED! New valves especially TV types. Cash waiting. Bearman, 6 Potters Road, New Barnet, Herts. Tel. 449/1934.

AERIALS

BAKER & BAINES

BBC dipole 30/-, H 42/-, 3 ele 89/-, ITA 3 ele 26/-, 5 ele 34/-, 8 ele 47/5, 11 ele 57/6, 159/-, Combined BBC/ITA D+5 45/-, D+8 52/-, H+5 69/-, X+5 75/-. Combined Loft Special D+5 with loft pole and fixings 37/-, UHF Aerials BBC-ITA 14 ele 37/-, 18 ele 54/-, 22 ele 63/-, Double 22 ele 142/-, CO-AX low loss at 1/3 and 2/3. Co-Ax plugs 1/4.

Diplexers—Triplexers—Matched UHF/VHF Diplexers. UHF/VHF Preamps. Poles, Lashings, Clamps, Couplers, etc. Postage paid on all aerials. Extra on accessories. Please state channels when ordering.

11 Dale Cres., Tupton, Chesterfield.

TELEVISION AERIALS BBC 2 LOFT AERIALS including fittings, 7-element 33/6, 11-element 39/6, 18-element 49/6. Chimney Lashing Kit, BBC 2 Array and Mast 7-element 65/6, 11-element 72/6, 18-element 82/-. BBC 1 EXTERNAL BBC/ITV 1+3 element 45/-. Combined BBC/ITV 1+3 61/6, 1+5 69/6, H+5 79/6, including Mast and Lashing. Low Loss Coax Cable 1/5 yd. Coax Plugs 1/4, 6 ft. 1 in. Masts 12/6, 12 ft. 2 in. masts 47/6. Chimney Mounting Brackets 14/6 and 22/6 Heavy Duty. Mark channels required. C.W.O. P. & P. 4/-. C. K. Aerial Erections, 1A Brook Street, Driffield, E. Yorks.

SETS & COMPONENTS

R & R RADIO

51 Burnley Road, Rawtenstall
Rossendale, Lancs.

Tel.: Rossendale 3152

VALVES BOXED, TESTED &
GUARANTEED

EF80	3/-	PCC84	3/-	PY81	3/6
EBF89	3/6	PCF80	3/-	PY82	3/-
ECC82	3/6	PCF82	3/6	U191	4/6
ECL80	3/-	PCL82	4/-	6F23	5/-
EF80	1/6	PCL83	4/-	30F5	2/6
EF85	3/-	PL36	5/-	30L15	5/-
EY85	4/-	PL81	4/-	30P12	4/6
EZ40	4/6	PL83	4/-	30C15	5/-
EBC41	4/6	PY33	5/-		

POST: ONE VALVE 9d. TWO TO SIX 6d.
OVER SIX POST PAID.

BARGAINS any 1-2/-, 5-8/-, 100-£5/- boxed, tested, your choice ECC82/3 ECL80, EF80, EF85, EBF80, EB91, PCC84, PCC89, PCF80, PCF801, PC86/8 PCL82/3, PCL84/5, PL81, PL36, PL500 PL504, PY81/2, etc. L.O.P.T. also obsolete types F/O.P.T., Scan Coils, Tuner Units and many others at lower prices, S.A.E. for lists J. S. Sondhis, 94/A, Netherwood Road, London W.14 (Mail Orders).

SETS & COMPONENTS (continued)

NEW BVA VALVES! Huge range by return postal service well known to the trade. Brief list of television types herewith, full list S.A.E. All types ex stock!

DY86/7	8/-	PCF86	12/3	PY82	7/-	20L1	19/6
EB91	5/-	PCF801/2	12/3	PY800/1	8/3	20P4	20/-
ECC82	8/6	PCF805	13/-	R19	13/-	30C15	13/9
ECL80	8/-	PCF808	13/6	U25	15/-	30C17	15/9
EF80	8/-	PCL82	10/3	U26	15/-	30F5	16/6
EF85	8/3	PCL83	12/3	U37	15/-	30FL1	12/9
EF183/4	11/3	PCL84	10/3	U191	14/6	30L15	15/3
EH90	10/3	PCL85	10/6	U193	8/3	30L17	14/6
EY51	7/6	PCL86	10/3	U251	17/3	30P12	15/6
EY86/7	7/9	PL36/8	12/9	U301	17/-	30PL1	12/9
PC86/8	10/3	PL81	10/3	U801	24/-	30P4MR	20/-
PC97	8/3	PL83	10/3	6/30L2	15/6	30P19	12/9
PC900	10/3	PL84	8/3	6AT6	9/9	30PL13	18/6
PCC84	9/3	PL500	16/6	6BW7	13/9	30PL14	18/6
PCC89	12/3	PL504	17/-	6CD6G	28/-		
PCF80	10/3	PY81	8/3	6F23	15/6	etc., etc.	

POST FREE OVER £3—LATEST ENCAPSULATED BY 100 & 33 ohm res, 4/-!

PAY BY GIRO. Our No. 34.361.4006.

SEE SEPARATE
TUBE LIST etc.

PHILIP H. BEARMAN

CALLERS
WELCOME

Tel. 449/1934 & 7873
(Robophone)

(Suppliers to HM Govt. etc.)

Closed Thursday &
Saturday afternoons

6 Potters Road, New Barnet, Herts.

AERIAL BOOSTERS 59/- EACH

Three types of high gain transistorized pre-amplifiers to work off PP3 battery or 210-250 D.C.

1. U.H.F. 625 Type L45 this will tune the complete U.H.F. band.
2. V.H.F. 405 Type L12 with separate tuning for band I and III. Please state band I Channel No. required.
3. F.M. V.H.F. Radio Type L11 with bandwidth for the complete band. All pre-amplifiers are complete and ready to use. Size 3½ x 3½ colour Ivory.
The 210-240 DC unit is 7/- extra.

VALVE BARGAINS

Any 1-2/-, 5-9/-, 10-14/-, 100-£5.10.0.

EB91, EBF80, EBF89, ECC82, EY86, EF80, EF85, EF183, EF184, PCC84, PCC89, PCF80, PCF86, PCL82, PCL83, PCL84, PL36, PL81, PY32, PY33, PY800, PY801, 30PL1, 30FL1, 30F5, 6F23, 6-30L2, 10F1.

Many other types in stock. BY100 Type Rectifiers 2/6 each

Guaranteed values 4/- each. Any from the list above (except valves in bold type) selected, tested, boxed and with three month written guarantee. S.a.e. for leaflets.

P. & P. on all goods 1/6.

Money refunded if not satisfied, if returned within 7 days.

VELCO ELECTRONICS

62 Bridge Street, Ramsbottom, Bury, Lancs. Tel. 3036

LOOK! Nearly every type in stock now!!

NEW TELEVISION TUBES!

TWO YEAR FULL REPLACEMENT GUARANTEE

SEE THE DIFFERENCE A NEW TUBE CAN MAKE TO YOUR VIEWING—LATEST SCREENING TECHNIQUES INCLUDING TINTED SCREENS ON MOST 19" & 23" TYPES

Large stocks by Cathodeon & other leading manufacturers so why buy ordinary rebuilds? Colour 25" £60!

Special offer! 19" rebuilds, 2 year guarantee £5 10s. 1 23" £7 10 0.

12" £3 0 0 (not 110°) 14" to 16" (not 110°) £4 15 0

17" £5 17 6 19" C19AH £7 10 0

Other 19" mono tubes—all £6 17 6. Carriage all 12/- All 21" mono tubes—£7 17 6, 23" mono tubes £9 10 0. Carriage 15/-

RIMBANDS, 19" £8 10 0; 23" £11 10 0 20" £10 17 0 Carriage

TWIN PANELS, 19" £9 17 6; 23" £14 0 0 (A50/120W) 20/-

Bulk enquiries welcomed, special terms.

PAY BY GIRO. Our No. 34.361.4006.

PHILIP H. BEARMAN

(Suppliers to H.M. Govt. etc.)

6 POTTERS ROAD, NEW BARNET, HERTS.

Closed Thurs & Sat afternoons TEL. 449/1934 (Robophone) & 7873

TELEVISION TUBE SHOP

ALL THE LATEST NEW TUBES
AT REDUCED PRICES

A28-14W	£11. 0.0
A31-18W	£12.10.0
A47-11W	£9.19.6
A47-13W	£11.15.0
A47-14W	£7.12.6
A47-26W	£10.15.0
A50-120WR	£12.10.0
A59-11W	£12.19.6
A59-13W	£15.10.0
A59-15W	£9.19.6
A59-16W	£14.15.0
A59-23W	£14.15.0
AW21-11	£10.10.0
AW36-20, 21	£5.12.6
AW36-80	£5. 7.6
AW43-80	£6.17.6
AW43-88, 43-89	£6.12.6
AW47-90, 91	£7.10.0
AW53-80	£8.17.6
AW53-88, 53-89	£8. 5.0
AW59-90, 59-91	£9.10.0
C17LM, PM, SM	£6.12.6
CME1201	£12.10.0
CME1101	£11.19.6
CME1601	£10. 5.0
CME1602	£12. 0.0
CME1702, 1703	£6.12.6
CME1705	£7.12.6
CME1901, 1903	£7.10.0
CME2013	£12.10.0
CME2101, 2104	£8. 5.0
CME2301, 2302	£8.15.0
CME2306	£15.10.0
CRM93	£5.10.0
CRM124	£5.10.0
CRM141, 2, 3, 4	£5.12.6
CRM171, 2, 3	£6. 7.6
CRM211, 212	£8.17.6
MW36-24, 44	£5. 2.6
MW43-64, 69	£6. 7.6
MW43-80	£6.17.6
MW53-20	£8.17.6
MW53-80	£8.17.6
7405A	£6.12.6
TSD217, 282	£14. 0.0

All tubes tested before despatch and guaranteed for 12 months.

Fully rebuilt tubes available—prices on request.

CARRIAGE 10/-, via B.R.S. or 15/- via Passenger train. Add 2/6 for Comprehensive insurance.

COLOUR TUBES

(Carriage & Insurance 40/-)

A49-11X	£66. 0.0
A56-120X	£72. 0.0
A63-11X	£77. 0.0

TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD
LONDON, S.W.11. BAT 6859

WE GIVE GREEN SHIELD
STAMPS

TOWERBY LTD

For Line Outputs and Deflector Coils

We have the Country's largest stock of Manufacturer's Original (or Authorised Replacement) Line Output Transformers for many "difficult" makes, including Ambassador, Baird, Cossor, Decca, Dynatron, Ekco, Ferguson, G.E.C., H.M.V., K.B., Masteradio, Peto-Scott, Philips, Regentone, RGD, Sobell, Ultra, etc. Also deflector coils output and oscillator transformers, inc. Alba, Bush, Murphy, Examples, L.O.P.T. Murphy 350/410/540/659/759, 147/-; Bush TV80, TV95, TV96, 147/-; Cossor 950, 77/6; Ferguson 306/308, 79/6; Philips 1768U L.O.P.T. assembly, 135/-; Ultra 1984-200c, 101/3.

Rewind most L.O.P.T., 90/-.

SPECIAL OFFER

Ekco improved type for Models T221, 231, 310, all at 45/-; Ferranti 1474 series inserts, 25/-; Philco 1019/1021, 52/6. Terms: C.W.O. or C.O.D. (3/6) post/packing 6/-; 2 or more L.O.P.T.s post/packing free.

All enquiries answered but regret no lists available. Same day delivery on most types.

TOWERBY LTD

MAIL ORDER DIVISION OF T.C.S. LTD.
70 STREATHAM HILL, LONDON, SW2.
Tel: 01-674 2185.

CONSISTENT LARGE QUANTITIES OF EX-RENTAL T/V's

Ideal for Slot or Re-sale

DELIVERY CAN BE ARRANGED

Ring: 061-872 3709 and 061-445 9091

VALVES, VALVES, VALVES

Any ten of your choice 14/6d., post 1/-.
100 £5 10s. Od., post paid.

EF85, EF80, EB91, EBF89, ECL80, EF183, EY86, PCF80, PCC84, PL36, PY81, PCL82, PCL83, PCC89, PY33, PY82, PY800, PY801, PY88, PCL84, 30F5, 6BW7, YR801.

BOB'S,

2 St. James Street, Rawtenstall
Rossendale, Lancs.
Mail order ONLY.

NEW! All-range (40-860 MHz) pre Amplifier. High gain T/V all channels, inc UHF, colour, FM/VHF Radio, Stereo, etc., built-in power unit. Precision job, superb value at £7 12s. 6d. p.p. and ins. paid to any address in U.K. or s.a.e. for literature. Johnsons (Radio) St. Martins Gate, Worcester, (Est. 1943).

150 NEW ASSORTED Capacitors, Resistors, Silvered Mica, Ceramic, etc. Carbon, Hystab, Vitreous 1/20 watt, 15/-, Post Free. WHITSAM ELECTRICAL, 33 Drayton Green Road, West Ealing, London, W.13.

TO HELP THE HOME CONSTRUCTOR Heathkit now make available our surplus Resistors, Capacitors, etc., at Bargain Prices. Send for lists. E. Moyle, Daystrom Ltd., Gloucester.

TELEVISION SALES, 1 Smallbrook Lane, Warmminster, Wilts., Phone Warmminster 8156. Valves, boxed, tested and guaranteed. PCF80, PCC84, PL81, PY81, EY86, EF80, 30F5, EB91, ECC82, PCL83, 30FL1, ECL80, PCL82, PY82, PCL84, 6-30-L2, you select 8 for 20/-, p. & p. 2/- S.A.E., other types, several CRTs cheap, tested, for callers only.

Free and illustrated lists of all types of Hi-Fi equipment; Tuners, Amps, etc. Electronic equipment, components and Gadgets at lowest prices

from:
ALBION ELECTRONICS SUPPLIES
D/5,
16 Albion Road, Birchington, Kent.

WITWORTH TRANSFORMERS LTD.

Dept. P.T., 26 All Saints Road,
North Kensington, W.11
Telephone: 01-229 9071. 9 a.m. till 5 p.m.

TELEVISION LINE OUTPUT TRANSFORMERS

PRACTICALLY ANY MAKE OR MODEL
SUPPLIED OR REWOUND

EKCO, FERRANTI, DYNATRON
Replacement cases 16/- each, please state model.

S.A.E. for return of post quotation.
TERMS: Cash with order or C.O.D., please add 4s. for postage.

C.O.D. orders will be charged 6s.
Transformers fully guaranteed. (98)

TOP PRICES PAID

for new valves and components

Write:

KENSINGTON SUPPLIES,

(A), 367 Kensington Street,
Bradford 8, Yorks.

EX N.E.V. C.C.T.V. Camera and Monitor
Circuits, S.A.E. for list. LOWE, 35 Henson
Point, Hackney, London, E.9.

NEW VALVES

Guaranteed and Tested

24 HOUR SERVICE

1R5	5/6	ECC81	3/6	PCL84	7/-
1R5	4/3	ECC82	4/-	PCL85	8/6
1T4	2/9	ECC85	4/9	PCL89	8/-
384	5/9	ECC85	5/-	PFL200	11/-
3V4	5/9	ECH35	5/6	PL86	9/3
6/30L2	11/6	ECH81	5/9	PL81	8/6
6AQ5	4/3	ECL80	6/6	PL82	5/9
6AT6	3/10	ECL82	6/3	PL83	6/3
6SN7GT	4/-	ECL83	8/-	PL84	6/-
6V6G	3/-	ECL86	7/6	PL500	12/9
25L6GT	4/6	EF37A	6/-	PL504	13/3
30FL1	13/9	EF39	4/6	PY82	10/-
30FL12	14/3	EF80	4/6	PY85	10/-
30P4	11/6	EF86	5/9	PY81	5/-
30P19	11/6	EF86	6/3	PY82	5/-
30P11	14/6	EF89	4/9	PY83	5/6
30PL13	16/9	EF183	5/6	PY88	8/6
CCH35	13/-	EF184	5/3	PY800	7/-
CL33	17/6	EH90	6/-	PY801	6/9
DAC32	6/9	EL33	9/3	R19	6/3
DAF91	4/3	EL84	4/9	U25	12/9
DAF96	6/9	EY61	7/-	U26	11/6
DF33	7/6	EY86	6/3	U191	12/-
DF91	2/9	EZ20	4/9	U193	8/6
DF96	6/9	EZ61	4/6	UB31	14/-
DHT	3/10	KT61	9/3	U801	10/-
DK32	6/9	KT66	16/6	U829	14/-
DK91	5/6	N78	17/-	UABC80	6/-
DK92	8/2	PABC80	6/9	UBC41	8/3
DK96	7/3	PC86	10/3	UBF89	6/3
DL92	5/9	PC88	10/3	UCB85	7/3
DL84	5/9	PC900	7/-	UCH81	6/6
DL96	7/-	PCC84	6/3	UCL82	6/9
EY86	4/9	PCO89	8/11	UF41	10/6
EY87	4/9	PCF80	5/11	UF89	6/-
EABC80	5/9	PCF801	6/6	UL41	11/9
EB33	7/9	PCF802	8/9	UL84	6/3
EB41	9/3	PCL82	6/9	UY41	7/-
EBF89	5/9	PCL83	11/9	UY85	5/3

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any parcel insured against damage in transit 6d. extra.

Office address, no callers.

GERALD BERNARD

83 OSBALDESTON ROAD
STOKE NEWINGTON
LONDON, N.16

A NEW "KING TELEBOOSTER"



THE M4 DUAL BAND V.H.F. UNIT KING . . .

the name you
can depend on.

- * Boosts all Band III and any specified Band I Channel simultaneously.
- * Still higher gain . . . nominally 17-18 d.B. both Bands.
- * Very low noise third generation passivated transistor.
- * Fitted fly lead . . . installed in seconds.
- * Quality Case 3 1/4" x 3 1/4" x 1 1/2" Cork base.

Specify Band I channel when ordering.

THE NEW UMF "COLOURBOOSTER"
Channels:-Group "A" Red Spot. "B" Yellow Spot,
"C" Green Spot. Prices: Both types:-75/- Battery
Model OR £5.17.6 Self Contained Mains Model.
P/P 2/6d.

TRANSISTOR DEVICES LIMITED

Bridge House, Newton Abbot, South Devon
Literature on request.

HERE'S A MARVELLOUS ANNUAL FOR YOUR CAR!

Just like the children, your car will appreciate being treated to its very own annual! It will enjoy your new-found confidence in putting right any minor troubles, keeping it all tricked out in the best accessories, and your ability to keep both the bodywork and machinery in mint condition!

ROUTINE MAINTENANCE

Advice on the cooling system, de-coking, brakes, etc.

TROUBLE-SHOOTING SECTION

A peculiar noise? Here's how to diagnose and correct typical faults.

FAULT-DIAGNOSING CHART

A 'family tree' of the working parts of your car.

50 GET-YOU-HOME TIPS

Could save you a lot of trouble and embarrassment!

OVERHAUL

The complete A-Z of all that needs to be done and how to do it including starter, dynamos, suspension.

RENOVATION

Repairing bodywork, tidying interior and exterior trims, 'touching up' with crude equipment.

PRESERVATION

Cleaning your car, anti-rust precautions, sorting out water leaks.

ALSO: A-Z Car Electrics, Motoring Holidays (9 pages), Workshop Hints, Accessories.

Surely your
car
deserves
this good
book?
Get it
today,
price 3/6

PRACTICAL MOTORIST ANNUAL

CS 382

maintenance • trouble-shooting • overhauls
renovation • preservation • electrical
accessories reviewed • camping

UHF, COLOUR AND TELEVISION SPARES

COLOUR Leading Brit. makers surplus time base units incl. frame o/p, line o/p and EHT trans. £6.0.0, p.p. 10/-, Scan coils £3.10, p.p. 6/-.
UHF/625 conversion kits and tuners at reduced prices. Lists available.
UHF integrated transist. 6 position push button tuners, leading Brit. maker surplus. £4.10.0, p.p. 4/6.
MURPHY 600/700 series UHF conversion kits in cabinet plinth assy, can be used as separate UHF receiver £8.10.0, p.p. 10/-, 925 IF amplifier incl. 5 valves and circuit 58.6, p.p. 6/-.
SOBELL/GEC dual 405/625 IF amp. and o/p chassis incl. circuit 32-6 **ULTRA** 1350C to 2384 925 IF amp. chassis and switch incl. circuits 30/-, p.p. 4/6.
UHF TUNERS transist. incl. s/m drive £5.5.0, valve type 58.6, p.p. 4/6.
TV SIGNAL BOOSTER UNITS Sens. gain all stations. **PYE/LABGEAR** transist. BBL/ITA or UHF Battery 'plug in', 75/- UHF Masthead £5.5.0.
FIREBALL TUNERS Perg., HMV, Marconi new 37/6, other types salvaged 18/6, p.p. 4/6. **PUSH BUTTON**, Plessey, Ekco incl. valves 58.6, p.p. 4/6.
TURBOT TUNERS Peto Scott 960, **COSSOR** 1964, **DECCA** DR 95, 101/606 50/- **CILDON** C 20/- **EKCO** 288/330 25/- **KB** Featherlight, Philips 19TG170 Series, Sobell 1010 35/-, p.p. 4/6. Large selection ch. coils.
LINE OUTPUT TRANSFS. Popular types available, brand new replacements fully guar. A selection which can be supplied, p.p. 4/6, C.O.D. 3/6.

PHILIPS 17TG100 range, STELLA 1011/1029	70/-	LOPT Inserts p.p. 2/-	35/-
BUSH TV53 to 69	32/6	Alba 655, 656	25/-
EKCO 221 to 331 (U25 or U26 types)	42/6	Bush TV32, 46, 43	45/-
FE IRANI 1001 to 1019 (U25 or U26 types)	42/6	Coscor 933 to 950	35/-
E..OD 342 to 394, FERRANTI 1021 to 1065	75/-	Ekco TP30S	38/6
EKCO/FERRANTI 418, 1093, etc.	62/6	Emerson 700 range	35/-
DECCA DM17, 3, 4 (70°) DR95, 101/606	78/6	Ferguson 203 to 246	35/-
FERG 305 to 436, 42/6; 505 to 727	55/-	Ferranti 1475 to 21KG	35/-
FERG HMV MARCONI ULTRA PHILCO	75/-	KB NF70, OV30, PV40	35/-
3560, 2500, 4590, 6600, 1100 ranges, Jelly pot	55/-	PVP20 , QV10, 29, 30	35/-
KB QV20, QV20/1 to 5V20	55/-	KB RGD Featherlight	50/-
KB VCI to VCI1	78/6	KB RGD VCI, 2, 3, 4	35/-
MARCONI VT157 to 172	55/-	PETO SCOTT 733, 738	35/-
GEC 302 to 346, 45/-; 448, 2000 series	89/6	Philco 1961 series	35/-
HMV 1355/9, 1570, 49/8; 1500 to 1924	55/-	Philips 17TG100 range	35/-
PYE VT17, CS, CDM, CW17, 17/21, 17/8,	62/6	Pye VT4, VT7	42/6
110 to 510, 700, 830, 11U to 40F	62/6	RGD D17, 590 to 619	35/-
PAM INVICTA equiv. LOPTS to above Peto	62/6	REG , 10-4, 10-17 to 192	35/-
PETO SCOTT 1419 to 1725, 35/-; 733 to 738	78/6	Ultra 1770 1780 range	35/-
SOBELL MeHIGH TPS173, 180, T23, 24, 178	45/-		
278, SC34, 270, MP17, 18, M72, 74	89/6		
TPS 781, T279, SC34, 370, MP27, M76, 76, 93	89/6		
195, 282, 1090, 762, 809 series	55/-		
PHILCO 1010 to 1021, 45/-; 1029 to 1060	55/-		
ULTRA 1770 to 2384, PILOT PT450 to 630	72/6		

SCAN COILS. Frame O/P, mains droppers, etc. C.O.D. despatch available.
NEW SCAN COILS 110° types surplus special offer, **PYE**, **EKCO**, **ULTRA**, **PILOT**, **MURPHY**, 30/-, FRAME O/P TRANS, **SOBELL** 17/6, p.p. 4/6.

MANOR SUPPLIES

64 GOLDERS MANOR DRIVE, LONDON, N.W.11
Callers: 5898 HIGH ROAD (nr. Granville Road) N. Finchley N.12
HIL 9118 (01-445 9118)

VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

**On 'SATISFACTION or
REFUND of FEE' terms**

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

WHICH OF THESE IS YOUR PET SUBJECT?

TELEVISION ENG.

Advanced Television Eng.—
Gen. Television Eng.—Tele-
vision Servicing and Main-
tenance.

ELECTRONIC ENG.

Advanced Electronic Eng.—
Gen. Electronic Eng.—
Applied Electronics—
Practical Electronics—
Radar Tech.—Frequency
Modulation—Transistors.

MECHANICAL ENG.

Advanced Mechanical Eng.—
Gen. Mechanical Eng.—
Maintenance Eng.—Diesel
Eng.—Press Tool Design—
Sheet Metal Work—
Welding—Eng. Pattern
Making—Inspection—
Draughtsmanship—
Metallurgy—
Production Eng.

RADIO ENG.

Advanced Radio—Gen.
Radio—Radio Servicing—
Telecommunications—
Sound Recording—Auto-
mation—Practical Radio—
Radio Amateurs' Exam.

ELECTRICAL ENG.

Advanced Electrical Eng.—
Gen. Electrical Eng.—
Installations—Draughts-
manship—Illuminating
Eng.—Refrigeration—
Elem. Electrical Science—
Electrical Supply—Mining
Electrical Eng.

CIVIL ENG.

Advanced Civil Eng.—
Municipal Eng.—Structural
Eng.—Sanitary Eng.—
Road Eng.—Hydraulics—
Mining—Water Supply—
Petrol Tech.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?
B.Sc. (Eng.), A.M.S.E., C.Eng., A.M.I.E.R.E., R.T.E.B., A.M.I.P.E.,
A.M.I.M.I., A.M.I.E.D., A.R.I.B.A., A.I.O.B., P.M.G., A.R.I.C.S., M.R.S.H.,
A.M.I.Mun.E., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

British Institute of Engineering Technology

445A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointment Dept.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

164 PAGES OF EXPERT
CAREER-GUIDANCE

PRACTICAL
EQUIPMENT

INCLUDING
TOOLS

Basic Practical and Theoretic Course for beginners in TV, Radio, Electronics etc. A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Television & Radio Servicing Practical Electronics Electronics Engineering Automation

The specialist Electronics Division of B.I.E.T.

NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", and you should send for your copy now—FREE and without obligation.



POST COUPON

TO B.I.E.T., 445A ALDERMASTON COURT,
ALDERMASTON, BERKSHIRE

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME

ADDRESS

WRITE IF YOU PREFER NOT-TO CUT THIS PAGE

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD