

JULY 1977

Australia 75c
New Zealand 75c

South Africa 70c
Malaysia \$2.25

45p

TELEVISION

SERVICING · VIDEO · CONSTRUCTION · COLOUR · DEVELOPMENTS

tv games in colour



also:
**SWITCH-MODE
POWER SUPPLIES
SERVICING FEATURES
ON THE RANK A774 & TANDBERG CTV1 CHASSIS**


FANTASTIC OFFER

**SERVICE PACK OF
100 MIXED ELECTROLYTICS 1000MFD to 4MFD £2.50**

**BELLING & LEE
STAR AMPLIFIER AND POWER UNIT £4.00**

**BAND B
CHANNEL B MAST-HEAD AMPLIFIER LESS POWER SUPPLY £1.00**

25Kv 2-5MA Silicone	£1.50	.044 MFD 1000v } .1 MFD 1000v } 8p .047 MFD 1000v } EACH .0047MFD 1000v } .01 MFD 1000v } 15p .47 MFD 1000v }	BF127 BF178 } BF264 BC350 } 15p BF180 BF121 } EACH BF181 BF257 } BF182 BF137 } BC300 BC161 }	
25Kv Selenium	£1.30			
3500 Thorn Triple	£3.50			
1730 Decca	£1.00			
TS11TAZ	£3.50			
TS2511TBH	£3.00	E.H.T. Rectifiers used in triplers (G770/HU37) 3 off 15p	BU105 ex panel 50p	
TS2511TCE	£3.00		BU105 new £1.00	
TS2511TCF	£3.00		BU105/04 new £1.50	
TS2511TBS	£3.00	E.H.T. Rectifier Sticks X80/150 12p CSD118XPA 15p CSD118XMH 15p	BU126 ex panel 50p	
TS2511TBQ	£1.50		BU205 new £1.90	
			BU208 new £2.00	
30 Pre Sets 50p	ISOLATING SOCKET VHF 40p UHF 40p MJE2021 15p EACH SJE5451 90V 80W 5A BY127 10p IN4007 20 for £1.00 1200 Piv 1 amp Diode PYX94 15 for £1.00 18Kv and 20Kv Rectifier Sticks and Base and Anode Lead 40p 18Kv 50p 20Kv BB105 Varicap Diodes BA182 12 for £1.00 Each Pack 5A - 300 TIC 106 Thyristors 25p Thyristors RZ427 300V 5A 27p Thyristors RCA 40506 50p 300M 350v } 50p 200M 325v } 600M 300V £1.20	Thorn Mains on/off Switch 15p	2N3055 new 45p	
100 W/W Resistors £1.50			200+150+50M 300V 50p	BD116 new 30p
300 Mixed Resistors £1.50			1000+2000M 35V 20p	BT106 95p
300 Mixed Condensers £1.50			100+200M 325V 30p	BT116 new £1.00
40 Mixed Pots £1.50			200+200+100 325V 40p	BY206 new 15p
20 Slider Pots £1.50			200+100+50+100 325V 40p	BY210/400 new 5p
TRIPLERS			150+200+200M 300V 70p	BYX55/350 new 10p
TK25KC1 5BL ex panel £1.50		200+100+100M 350V 70p	BD138 25p	
LP1193/61 Mullard £2.50		200+200+100+32 350V 70p	R2030 new 75p	
Bridge Rectifier 1 amp 100V 20p		400+400 200V 40p	AE Isolating Socket UHF lead 30p	
Bridge Rectifier 2 amp 100V 25p		800M 250V 40p	Sparkgap 5p	
Bridge Rectifier W005M 20p		200+100+100+50 300V 40p	12Kv Diodes 2M/A 30p	
D.P. Audio Switch push on/off 7½p		200+200+150+50 300V £1	18Kv BYF3123 2M/A 40p	
Mains Droppers 69 161R 20p		180PF 8Kv 10M 350v	TAA550 30p	
147 260R 25w 20p		1000PF 10Kv 100M 50v	TBA510 £1.00	
4 Push Button Tuner Unit U.H.F. Thorn £3.50		1200PF 10Kv 330M 10v	TBA480Q £1.00	
4 Push Button Unit £1.00		1000PF 12Kv 330M 25v	TBA550Q £1.50	
7 Push Button Unit for Varicap £1.50		160M 25v 330M 35v	TBA720A £1.50	
Thorn 2000 & 3000 series Hearing Aid External Loudspeaker Unit £2.00		220M 25v 330M 50v	TBA790B131 £1.00	
		1000M 16v 330M 63v	TBA800 95p	
		220M 35v 470M 25v	TBA920 £2.00	
		220M 40v 470M 35v	TAA700 £2.00	
		220M 50v 470M 40v	TBA530Q £1.00	
		470M 25v 10p	TBA550 £2.00	
		22M 315v EACH	SN76544N 50p	
			SN76640N £1.00	
			SAA570 50p	
			TBA120A 50p	
			TCA270Q £2.00	
			TCA270SQ £2.00	
			IN4005 5p	
100M 100V 4M 350V 1000M 35V } 12½p		SENDZ COMPONENTS 2 WOOD GRANGE CLOSE, THORPE BAY, ESSEX. Reg. Office only - No personal callers. Thank you. Post paid U.K. only. PLEASE ADD 12½% VAT		
470M 100V 470M 50V 1000M 40V } EACH				
32 + 32M 350V 250M 64V 1000M 50V } 25p				
470+470M 250V 75p 4700M 30V				
120 MIXED PACK OF ELECTROLYTICS & PAPER CONDENSERS £1.50				
100 Green Polyester Condensers. Mixed Values. £2.00 per 100.				
R1Z243619	UHF VARICAP TUNER UNIT, £2.50 NEW	ELC1043		

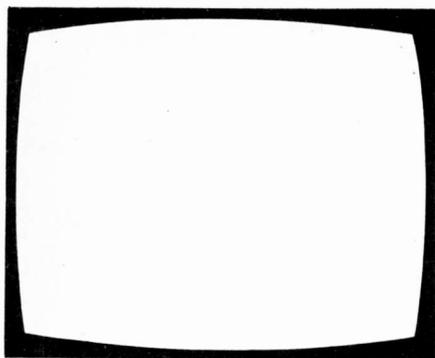

TELEVISION

July
1977

Vol. 27, No. 9
Issue 321

COPYRIGHT

© IPC Magazines Limited, 1977. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", Fleetway House, Farringdon Street, London EC4A 4AD. All other correspondence should be addressed to the Editor, "Television", Fleetway House, Farringdon Street, London EC4A 4AD.

BINDERS AND INDEXES

Binders (£2.10) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include inland postage and VAT. Overseas orders: add 60p to cover despatch and postage.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service.

this month

- 455 **Follow That Circuit!**
- 456 **In Puffed a Couple of Chaps . . .** *by Les Lawry-Johns*
Mainly this month on some of the problems that can arise with the Thorn 3000/3500 chassis.
- 458 **A Simple Soldering Iron Stand** *by Malcolm Burrell*
Hot soldering irons can be dangerous things. A simple way of taming them is described.
- 461 **TV Games in Colour, Part 1** *by Steve A. Money T.Eng.(C.E.I.)*
First of a two part article on a TV games unit designed to provide a full colour display.
- 464 **Servicing the Tandberg CTV1 Chassis** *by W. S. J. Brice, B.Sc.(Eng.)*
Circuit notes and stock faults on this interesting 90° colour chassis.
- 468 **Picture Sharpener for the Philips VCR** *by John de Rivaz, B.Sc.(Eng.)*
An add-on board which improves the definition of tapes replayed on these machines.
- 469 **More on the ITT CVC20 Chassis** *by Dewi James*
Report on a recent visit to ITT's Kersley plant, with notes on some early troubles on this chassis.
- 470 **Test Report: Eagle Transistor Testers** *by Vivian Capel*
Conclusions on the Eagle TT144 and TT145 transistor testers.
- 472 **Circuit Notes** *by H. K. Hills*
Spotlight on some less common circuit arrangements found in TV sets.
- 474 **Servicing the Rank A774 Chassis** *by John Coombes*
A thorough fault run down on this widely distributed single-standard monochrome chassis.
- 478 **Book Notices**
- 479 **Developments in Switch-Mode Power Supplies, Part 1** *by E. Trundle*
TV receiver designers are increasingly adopting switch-mode power supplies because of their various advantages. A description of some recent circuits, particularly those found in Sony colour sets.
- 485 **Next Month in Television**
- 486 **Long-Distance Television** *by Roger Bunney*
Reports on DX reception and conditions, and news from abroad. Also guidance on aerial preamplifier performance.
- 489 **Service Notebook** *by G. R. Wilding*
Notes on faults and how to tackle them.
- 489 **Readers' Printed Board Service**
- 490 **The "TV" Teletext Decoder, Part 5** *by Steve A. Money, T.Eng.(C.E.I.)*
Starting on the display logic board.
- 494 **Your Problems Solved**
- 497 **Test Case 175**

OUR NEXT ISSUE DATED AUGUST WILL BE
PUBLISHED ON JULY 18

IN RESPONSE TO POPULAR DEMAND



The proven reliability, small size, easy operation and stability of this truly famed instrument has obliged us to continue supplying it in order to meet unflagging demand. With improvements incorporated — plug-in I.Cs for example — it is going to be wanted more than ever. Many thousands are in regular use by TV renters and suppliers etc. Can be used overseas as it stands, if required. Operates from its own self-contained standard batteries.

NO EXTRA FOR POSTAGE AND V.A.T. Postage costs allowed to personal shoppers.

In kit form with instructions. Inc. p/p and V.A.T. **£10.50**

Ready built and tested (less batts) inc. p/p and V.A.T. **£12.75**

TV SIGNAL STRENGTH METER

Based on the original design in this journal, complete reprint of which is included with the kit. Gives direct reading from any domestic UHF aerial and as such makes an indispensable aid in obtaining better pictures. *Prices inc. p/p and V.A.T.*

£22.00

Make Cheques and Money Orders crossed and payable to Bi-Pak Ltd

STIRLING SOUND OFFER ONCE MORE BI-PRE-PAK'S FAMOUS

CROSS HATCH GENERATOR MK.2

AVAILABLE IN KIT FORM OR READY BUILT. GUARANTEED.

- ★ FOUR STANDARD PATTERN SELECTOR SWITCH
- ★ TOUGH FIBRE GLASS CASE 5 1/4" x 3" x 3"
- ★ OPERATES FROM SELF-CONTAINED BATTERIES
- ★ PLUG-IN I.Cs AND MORE SENSITIVE SYNC PICK-UP CIRCUIT
- ★ FUNCTIONS TO FULL PROFESSIONAL AND COMMERCIAL REQUIREMENTS

3 SPECIAL BARGAIN OFFERS

UHF TUNER by world famous manufacturer. BRAND NEW. Covers 625 lines, channels 21 to 65. Standard TV. I.F. frequency output.

Ideal for making a TV sound receiver. *Price inc. p/p and V.A.T.* **£1.95**

PUSH-BUTTON TUNING ASSEMBLIES for varicap TV tuning. 4 button **£1.95**; 7 button **£2.80** Both inc. p/p and V.A.T.

10 RECTIFIER STICKS for colour TV triplets. 12 KV working. Type CSD118XPA *Inc. p/p and V.A.T.* **65p.**

STIRLING SOUND

220-224 WEST RD, WESTCLIFF-ON-SEA, ESSEX S50 9DF

Telephone Southend (0702) 46344

● PERSONAL CALLERS WELCOME.

For those who appreciate Quality...

a complete electronic kit
The Forgestone 400

high quality
colour television receiver

SUPERB PICTURE QUALITY TOGETHER WITH PROVEN RELIABILITY

- 9 integrated circuits
- Thick film resistor units
- Ready-built and aligned IF module
- Glass epoxy printed circuit panels
- High quality components
- Fully isolated power supply
- Plugs and sockets for easy panel removal
- Each module kit available separately
- Full technical construction manual
- LT supply regulator

The isolated chassis makes the receiver ideal for the addition of Teletext decoders, remote controls etc. Please send stamp for further details of these quality products.

Forgestone Colour Developments Limited

Ketteringham, Wymondham, Norfolk, NR18 9RY, U.K.


Telephone: Norwich 810453 (STD 0603)

MAIL ORDER — Barclaycard & Access accepted



COMPONENTS FOR THE TELEVISION TELETEXT DECODER

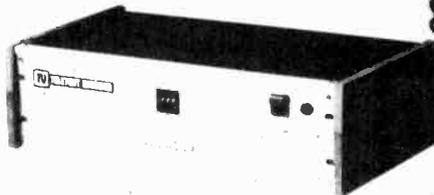The first kits are now available from CATRONICS LTD. for this project, all backed by CATRONICS exclusive Four Star Service (see page 394, June issue).



POWER SUPPLY UNIT (inc. PCB) — £26.75 + £1.00 p&p.
INPUT LOGIC CARD (inc. PCB) — £25.85 + 30p p&p.
MEMORY CARD KIT (Less PCB) — £22.90 + 20p p&p.
DISPLAY CARD KIT (Less PCB) — £26.65 + 20p p&p.

These kits contain all components required for the specific unit, including a reprint of the original article, plus the PCB when available.

I.F. Card, Modulator, Switches, Cabinet & all other parts also available. Send for full price list.

The following components are also available separately:

BYZ13 — 70p. BYZ88 zeners — 13p. 1A Bridge Rectifier — 40p. 10,000mfd 16V capacitor — £2.75. Heatsink — 30p. Illuminated Mains Switch — £1.40. Fuse and holder — 52p. Mains Transformer — £6.25 (+ £1.00 p&p). 2102 — £2.65. 7805 — £1.50. 7812 — £1.50.

7400 SERIES ICs FROM NATIONAL/TEXAS etc.

SN74 S262N Char. Gen.	£17.00	7400	19p	7402	19p
7403	19p	7404	24p	7406	44p
7410	22p	7411	22p	7412	27p
7421	28p	7427	34p	7428	47p
7432	38p	7442	84p	7474	36p
7483	£1.00	7485	£1.33	7486	35p
7492	60p	7493	65p	74107	52p
74123	£1.05	74150	£2.49	74153	90p
74164	£1.38	74165	£1.70	74174	£1.19
74177	£1.40	74180	£1.30	74196	£1.62
				74221	£1.55
				7408	26p
				7420	19p
				7430	21p
				7475	56p
				7490	58p
				74121	43p
				74157	90p
				74175	£1.30

Quantity discount on 7400 series only: 25 — 99 less 10%; 100 + less 20%. All prices INCLUDE VAT. Please add minimum of 20p P&P.

Catronics

(Dept 767), COMMUNICATIONS HOUSE
20 WALLINGTON SQ., WALLINGTON
SURREY SM6 8RG. Tel. 01-669 6700

BRIARWOOD TELEVISION LTD.

LEGRAMS MILLS, SUMMERVILLE ROAD, BRADFORD,
WEST YORKSHIRE BD7 1NS. TEL (0274) 22046.

**NOW AVAILABLE
EX-RENTAL MONO AND
COLOUR TV's
FOR SALE**

Type Price (£)

VALVES

DYB7	0.40
DY802	0.48
ECC82	0.42
EFB0	0.40
EF183	0.50
EF184	0.50
EH90	0.60
PC86	0.70
PC88	0.70
PCC89	0.55
PCC189	0.60
PCF80	0.50
PCFB6	0.58
PCF801	0.60
PCF802	0.70
PCL82	0.60
PCL84	0.55
PCL86	0.60
PCL805	0.60
PFL200	0.70
PL36	0.85
PL84	0.52
PL504	0.90
PL509	1.50
PY88	0.52
PY500A	1.00
PY801	0.50

Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
AC107	0.20	AF106	0.42	BC138	0.17	BC213L	0.13	BDY60	0.80	BF222	0.12	OC24	1.30
AC113	0.17	AF114	0.22	BC139	0.23	BC214L	0.13	BF115	0.23	BF221	0.21	OC25	0.45
AC115	0.17	AF115	0.22	BC140	0.25	BC249	0.31	BF121	0.30	BF256	0.37	OC26	0.40
AC117	0.24	AF116	0.22	BC141	0.24	BC281	0.17	BF154	0.14	BF258	0.42	OC28	0.60
AC125	0.20	AF117	0.22	BC142	0.24	BC262	0.20	BF158	0.20	BF259	0.47	OC35	0.45
AC126	0.20	AF118	0.43	BC143	0.23	BC263B	0.20	BF159	0.20	BF260	0.24	OC36	0.58
AC127	0.22	AF121	0.43	BC147	0.10	BC267	0.19	BF160	0.19	BF262	0.32	OC38	0.43
AC128	0.20	AF124	0.23	BC148	0.10	BC30T	0.30	BF163	0.30	BF263	0.25	OC42	0.45
AC131	0.13	AF125	0.25	BC149	0.10	BC302	0.30	BF164	0.20	BF271	0.18	OC44	0.18
AC141	0.22	AF126	0.25	BC153	0.15	BC307A	0.12	BF167	0.21	BF273	0.17	OC45	0.18
AC141K	0.27	AF127	0.27	BC154	0.15	BC308A	0.12	BF173	0.23	BFX84	0.27	OC46	0.35
AC142K	0.27	AF139	0.35	BC157	0.15	BC309	0.14	BF177	0.26	BFX85	0.26	OC70	0.22
AC151	0.17	AF151	0.24	BC158	0.14	BC547	0.11	BF178	0.33	BFX88	0.26	OC71	0.22
AC165	0.16	AF170	0.29	BC159	0.14	BC548	0.11	BF179	0.29	BFY37	0.22	OC72	0.30
AC166	0.16	AF172	0.20	BC160	0.24	BC549	0.11	BF180	0.31	BFY51	0.25	OC74	0.35
AC168	0.17	AF178	0.55	BC161	0.24	BC557	0.11	BF181	0.29	BFY52	0.25	OC75	0.35
AC176	0.20	AF180	0.60	BC167	0.13	BD112	0.50	BF182	0.35	BFY53	0.27	OC76	0.35
AC186	0.16	AF181	0.44	BC168	0.13	BD113	0.65	BF183	0.33	BFY55	0.27	OC77	0.50
AC187	0.24	AF239	0.40	BC169C	0.14	BD124	1.00	BF184	0.23	BHA0002		OC78	0.13
AC187K	0.28	BC107	0.14	BC171	0.13	BD131	0.39	BF185	0.23		1.90	OC81	0.20
AC188	0.21	BC108	0.14	BC172	0.13	BD132	0.39	BF186	0.30	BR100	0.32	OC810	0.14
AC188K	0.28	BC109	0.14	BC173	0.15	BD133	0.39	BF194	0.11	BSX20	0.23	OC82	0.20
AD130	0.50	BC113	0.12	BC177	0.16	BD135	0.35	BF195	0.11	BSX20	0.23	OC820	0.13
AD140	0.60	BC114	0.12	BC178	0.17	BD136	0.35	BF196	0.13	BSX76	0.23	OC83	0.22
AD142	0.60	BC115	0.12	BC179	0.17	BD137	0.35	BF197	0.13	BSY84	0.36	OC84	0.28
AD143	0.60	BC116	0.14	BC182L	0.11	BD138	0.40	BF199	0.17	BT106	1.10	OC85	0.13
AD145	0.50	BC117	0.14	BC183L	1.11	BD139	0.40	BF200	0.28	BU105/04		OC123	0.20
AD149	0.60	BC119	0.27	BC184L	1.11	BD140	0.40	BF216	0.12		2.00	OC169	0.20
AD161	0.50	BC125	0.15	BC186	0.25	BD222	0.40	BF217	0.12	BU126	1.65	OC170	0.22
AD162	0.50	BC126	0.15	BC187	0.25	BDX22	0.73	BF218	0.12	BU208	2.45	OC171	0.27
AD161	1.30	BC136	0.17	BC209	0.13	BDX32	1.90	BF219	0.12	OC22	1.10		
AD162	1.30	BC137	0.17	BC212	0.13	BDY18	0.75	BF220	0.12	OC23	1.30		

E.H.T. TRAYS

MONOCHROME

950 MK2 1400	2.26
1500 18" 19" stick	2.37
1500 24" 5 stick	2.48
Single stick Thorn T.V.	
11.16K 70V	0.75

E.H.T. TRAYS COLOUR

Pye 691,693	4.41
Decca (Large screen)	5.67
GEC C2110	5.77
GEC Hybrid C.T.V.	5.57
Thorn 3000/2500	5.77
Thorn 8000	2.42
Thorn 8500	4.73
GEC TVM25	2.50
ITT/KB CVC5	5.96
Philips 5B 520 Series	5.96
RR1 (RBM) A823	6.09

ALL TRANSISTORS, I.C.'s OFFERED ARE NEW AND BRANDED.
MANUFACTURED BY MULLARD, I.T.T., TEXAS, MOTOROLA, ETC.

Please add 12½%
VAT to all items and
overseas at cost.

P & P U.K. 20p PER ORDER. OVERSEAS ALLOW FOR
PACKAGE AND POSTAGE. CASH WITH ALL ORDERS.

All prices subject to
alteration without
notice.

EX-EQUIPMENT SPARES

MONO TUBES	MONO TUNERS	MONO LOPTS	MONO PANELS	COLOUR TUBES
(tested)	6-button integrated all at £6.50	All D/Standard Lopts at £4.00 + £1 p.p.	i.e. Philips, Bush etc £3.50 + £1 p.p.	(tested)
19" Rimguard £4.50	U.H.F. P/Button D/S £4.50	All S/Standard at £4.00 + £1 p.p.	QUOTATIONS for complete S/hand chassis if required.	19" £18.00
23" Rimguard £6.00	U.H.F. P/Button S/S £6.50		(different prices)	20" £20.00
20" Rimguard £7.50	Rotary £3.00			22" £25.00
24" Rimguard £7.50 + £3.00 p.p.	£1.00 p.p. on all tuners.			26" £32.00
				+ p.p. £3.50
				State tube number

★ MONO AND COLOUR SETS SUPPLIED TO THE TRADE

★ MONO AND COLOUR T.V.'s ALWAYS AVAILABLE FOR EXPORT TO ANY COUNTRY

★ COLOUR TUNERS, COLOUR LOPTS AND COLOUR PANELS AVAILABLE MOST OF THE TIME

All Mono valves supplied at 10p each + 20p p.p.
Many colour valves supplied. Please enquire for prices.
Self addressed envelope appreciated.
Many other spares i.e. Scancoils, Frame output, Transformers etc.
All miscellaneous spares available in large or small quantities.

WHY NOT TRY OUR EXPRESS MAIL ORDER SERVICE ON ANY OF THE ITEMS LISTED.

Please add 12½% VAT to all items and overseas at cost. Cash with all orders.

BRIARWOOD TELEVISION LTD.

Legrams Mills, Summerville Road, Bradford, West Yorkshire BD7 1NS. Tel (0274) 22046.

TV

LINE OUTPUT TRANSFORMERS

All items new and guaranteed

MONO TRANSFORMER £6.75ea
(No Extra for Carriage)

DISCOUNT FOR TRADE.

VAT @ 12½% . **84p**
TOTAL £7.59

BUSH

TV102C	TV128	TV183 or D
TV103 or D	TV134	TV183S
TV105 or D	TV135 or R	TV183SS
TV105R	TV138 or R	TV185S
TV106	TV139	TV186 or D
TV107	TV141	TV186S
TV108	TV145	TV186SS
TV109	TV148	TV191D
TV112C	TV161	TV191S
TV113	TV165	TV193D
TV115 or C	TV166	TV193S
TV115R	TV171	TV198
TV118	TV175	TV307
TV123	TV176	TV312
TV124	TV178	TV313
TV125 or U	TV181 or S	TV315

DECCA

DR1	DM35	DR123
DR2	DM36	DR202
DM3	DM39	DR303
DR3	DR41	DR404
DR20	DM45	DR505
DR21	DR49	DR606
DR23	DM55	666TV-SRG
DR24	DM56	777TV-SRG
DR29	DR61	MS1700
DR30	DR71	MS2000
DR31	DR95	MS2001
DR32	DR100	MS2400
DR33	DR101	MS2401
DR34	DR121	MS2404
	DR122	MS2420

MURPHY

V843 ...
all models to
V979
V153
V159
V173
V179
V1910
V1913
V1914
V2014 or S
V2015D
V2015S
V2015SS
V2016S
V2017S
V2019
V2023
V2027
V2310
V2311C
V2414D
V2415D
V2415S
V2415SS
V2416D
V2416S
V2417S
V2419
V2423

PHILIPS

17TG100u	19TG170a...	21TG106u
17TG102u	all models to	21TG107u
17TG106u	19TG179a	21TG109u
17TG200u	G19T210a	
17TG300u	G19T211a	23TG111a...
17TG320u	G19T212a	all models to
	G19T214a	23TG164a
	G19T215a	
19TG108u...		23TG170a...
all models to		all models to
19TG164a	G20T230a...	23TG176a
	all models to	
	G20T328	
		G24T230a...
	21TG100u	all models to
	21TG102u	G24T329

PYE

11u	40F	58	64	81	93	161
31F	43F	59	68	83	94	150 170
32F	48	60	75	84	95/4	151 170/1
36	49	61	76	85	96	155 171
37	50	62	77	86	97	156 171/1
39F	53	63	80	92	98	160

SOBELL

ST196 or DS
ST197
ST290
ST297

1000DS...
all models to
1102

THORN GROUP

Ferguson, H.M.V. Marconi, Ultra

By Chassis:-
800, 850, 900, 950/1, 950/2,
950/3, 960, 970, 980, 981,
1400, 1500, 1500 (24"),
1580, 1590, 1591.

Or quote model No.

PLEASE QUOTE PART NO.
NORMALLY FOUND ON TX. BASE
PLATE: 4121, 4123, 4140 OR 4142.

BAIRD

600	628	662	674
602	630	663	675
604	632	664	676
606	640	665	677
608	642	666	681
610	644	667	682
612	646	668	683
622	648	669	685
624	652	671	687
625	653	672	688
626	661	673	

GEC

BT454
BT455
BT455DST
2000DST...
all models to
2044
2047...
all models to
2084
2104 or /1
2105 or /1

KB-ITT

By Chassis:
VC1 VC52
VC2 VC52/1
VC3 VC100
VC4 VC100/2
VC11 VC200
VC51 VC300
Or quote model No.

INDESIT

20EGB
24EGB

Tidman Mail Order Ltd.,
236 Sandycombe Road,
Richmond, Surrey.

MON - FRI 9 am to 12.30 pm
1.30 pm to 4.30 pm
SAT 10 am to 12 noon

Approx. 1 mile from Kew Bridge.
Phone: 01-948 3702

Contact your nearest depot for service by-return.

Hamond Components (Midland) Ltd.,

416, Moseley Road,
Birmingham B12 9AX.


MON - FRI 9 am to 1 pm
2 pm to 5.30 pm

Phone: 021-440 6144

Callers welcome. Please phone before calling.

COLOUR TV LINE OUTPUT TRANSFORMERS E.H.T. RECTIFIER TRAYS (Prices on application)

TV Crosshatch & Pattern Generator

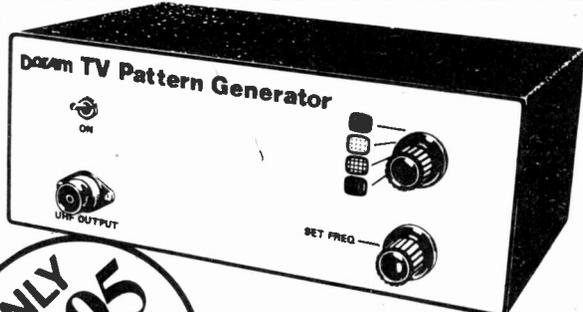

ONLY £29.95
+8% VAT
ORDER CODE
997-162

Built Tested and Guaranteed

or in D.I.Y. Kit form £19.77
ORDER CODE 997-033 + 8% VAT

Only requires connection to UHF aerial socket and to the mains. The generator has its own pulse generator and UHF modulator producing fully interlaced scan, 625 lines. Frequency is adjusted using visual display on TV screen to lock line and frame sync. Select Blank raster, dots, greyscale or crosshatch to set static and dynamic convergence, geometry, focus, beam limiting, black level clamp etc. etc.

DORAM

Allow 28 days delivery

Overseas orders—add 15% for p. & p. All items offered for sale subject to the Terms of Business as appears in Doram Edition 3 catalogue, price 60p. The Doram Kit brochure is also available, price 25p. Combined price only 70p which also entitles you to 2 x 25p vouchers each one usable on an order placed to the value of £5.00 or more (ex VAT).

DORAM ELECTRONICS LTD., P.O. BOX TR8,
WELLINGTON RD. IND. EST., LEEDS LS12 2UF
An Electrocomponents Group Company

TV'S! TV'S! TV'S!

'A' Price is good working order

'B' Price is complete but unserviced with tested tube

Philips 25" G6 D/STD	£48.00	£32.00
GEC 19/25" D/STD	£56.00	£40.00
GEC 19" S/STD	£64.00	£48.00
GEC 22" S/STD	£80.00	£64.00
Thorn 3000 25" S/STD	£88.00	£72.00

ALL ABOVE PLUS £8 DELIVERY AND PLUS VAT.

100% OF COLOUR TV'S OFF THE PILE FROM £20.00.

Always a good selection of modern and older C.T.V. panels and scrap chassis cabinets, mono tubes etc. etc.

AGENT FOR TOP QUALITY MERCURY UHF SET TOP MULTIBAND AERIALS, BOXES OF 25 FOR £45. DEL. & VAT INC., OR SEND £2.75 FOR SAMPLE.

SQUARE SCREEN MONO

MOST MODELS AVAILABLE i.e., GEC, DECCA FROM £10.00
PHILIPS, PYE, THORN, BUSH FROM £12.00.

HUNDREDS OF 19"/23" MONO TV'S

to pick from at giveaway prices
i.e. Pye, Olympic, Philips 210, Thorn 1400 £8.00
All prices plus VAT

EXTRA SPECIAL OFFERS!

Philips 22" Single STD Colour TV's. Models 511, 512, 513. Good working order with repolished cabinets. Singles at £64.00. Threes at £60.00 each. (Singles delivery and VAT inc. at £81.00 C.W.O.)
20"/24" GEC or Decca Mono TV's. Good working order. Singles at £20.00. Threes at £16.00 each. Singles delivery and VAT inc. at £27.00.

Please write for quotation on any set or spares.
Quantity discounts. Callers Welcome. Deliveries arranged.



SOUTHERN
Watling Street,
Hockliffe (3 miles
north of Dunstable
on A5). Tel. Hock-
liffe (05251) 768

NORTHERN
Thornbury
Roundabout,
Leeds Road,
Bradford 3.
Tel. (0274) 665670

SCOTLAND
Peacock Cross
Industrial Estate,
Burnbank Road,
Hamilton.
Tel. (06982) 29511

TRANSISTORS, ETC.		Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)		
AC107	0.48	AF149	0.45	BC159*	0.14	BC301	0.35	BD136	0.46	BDY20	1.07	BF259	0.61	8RY55	10.48	OC42	0.65	2N1893	0.40
AC117	0.38	AF178	0.75	BC160	0.78	BC303	0.60	BD137	0.48	BF115	0.30	BF262	0.64	8RY56	10.44	OC44	0.34	2N2102	0.51
AC126	0.36	AF179	0.78	BC161	0.80	BC307A & B		BD138	0.52	BF117	0.45	BF263	0.62	BT106	1.50	DC45	0.32	2N2221A	0.50
AC127	0.40	AF180	0.75	BC168B	0.14	BC308 & A10.17		BD139	0.56	BF120	0.55	BF270	0.47	BT109	1.99	OC71	0.73	2N2222A	0.52
AC128	0.35	AF181	0.72	BC169C	0.15	BC309*	0.17	BD140	0.59	BF121	0.85	BF271	0.52	BT116	1.45	OC72	0.73	2N2369A*	0.44
AC128K	0.35	AF186	0.99	BC170*	0.15	BC317*	0.22	BD144	2.24	BF123	0.58	BF273	10.33	BT119	1.18	OC81	0.53	2N2484	0.55
AC141	0.35	AF202	0.27	BC171*	0.15	BC318*	0.23	BD145	0.75	BF125	0.65	BF274	10.34	BU102	2.85	OC81D	0.57	2N2646	0.75
AC141K	0.40	AF239	0.60	BC172*	0.14	BC319C	0.26	BD157	0.51	BF127	0.68	BF333	0.67	BU105	1.95	OC139	0.76	2N2696	1.30
AC142	0.34	AF240	1.40	BC173*	0.22	BC320	0.28	BD160	1.65	BF137F	0.78	BF336	0.43	BU105/02	1.95	OC140	0.80	2N2904*	0.42
AC142K	0.39	AF279S	0.91	BC174A & B		BC322	0.24	BD163	0.67	BF152	10.19	BF337	0.46	BU108	3.15	OC170	0.34	2N2905*	0.33
AC151	0.31	AL100	1.10	BC176	0.22	BC323	0.68	BD177	0.58	BF157	0.32	BF338	0.58	BU126	2.18	OC171	0.34	2N2926G	10.15
AC152	0.34	AL103	1.13	BC177*	0.20	BC327	0.23	BD178	0.59	BF158	0.25	BF355	0.52	BU133	1.77	ON236A	0.72	2N2926G	10.14
AC153	0.42	AU103	2.10	BC178*	0.22	BC328	0.23	BD181	1.04	BF160	10.27	BF362	10.62	BU204	2.02	R2008B	2.25	2N2926G	10.14
AC153K	0.43	AU107	1.90	BC179*	0.22	BC337	0.24	BD182	0.90	BF160	10.27	BF363	10.62	BU205	2.24	R2108B	2.65	2N2955	1.12
AC154	0.41	AU110	1.90	BC182*	0.14	BC338	0.19	BD183	1.18	BF161	0.45	BF457	0.68	BU206	2.97	TIC44	10.29	2N3053	0.26
AC176	0.42	AU113	2.40	BC182*	0.14	BC347A*	0.17	BD184	1.43	BF162	10.65	BF458	0.84	BU208	3.15	TIC46	10.44	2N3054	0.62
AC178	0.42	BC107*	0.16	BC183*	0.14	BC348A & B		BD187	0.61	BF163	10.65	BF459	0.91	BU208	3.15	TIC46	10.44	2N3054	0.62
AC179	0.48	BC108*	0.15	BC183*	0.14	BC349A & B		BD188	0.65	BF164	10.65	BF459	0.91	BU208	3.15	TIC46	10.44	2N3054	0.62
AC187	0.42	BC109*	0.17	BC183*	0.14	BC350A*	0.20	BD189	0.71	BF165	10.65	BF459	0.91	BU208	3.15	TIC46	10.44	2N3054	0.62
AC187K	0.45	BC113	0.16	BC184*	0.14	BC351A*	0.18	BD201	1.15	BF167	0.52	BF597	10.17	BU208	3.15	TIC46	10.44	2N3054	0.62
AC188	0.42	BC114	0.20	BC184*	0.14	BC352A*	0.18	BD202	1.50	BF173	0.30	BF639	0.33	BU208	3.15	TIC46	10.44	2N3054	0.62
AC188K	0.42	BC115	0.21	BC186	0.26	BC355A*	0.18	BD225	0.91	BF177	0.36	BF640	0.29	BU208	3.15	TIC46	10.44	2N3054	0.62
AC193K	0.48	BC116*	0.21	BC187	0.27	BC355A*	0.18	BD232	2.20	BF179	0.42	BF660	0.35	BU208	3.15	TIC46	10.44	2N3054	0.62
AC194K	0.52	BC117	0.20	BC192	0.56	BC360	0.24	BD233	0.52	BF180	0.36	BF661	0.29	BU208	3.15	TIC46	10.44	2N3054	0.62
ACY17	0.50	BC118	0.17	BC207*	0.14	BC377	0.22	BD234	0.75	BF181	0.35	BF662	0.28	BU208	3.15	TIC46	10.44	2N3054	0.62
ACY19	0.40	BC119	0.32	BC208	0.12	BC441	0.59	BD235	0.69	BF182	0.44	BF679	0.36	BU208	3.15	TIC46	10.44	2N3054	0.62
ACY28	0.35	BC125*	0.22	BC212*	0.17	BC461	0.78	BD236	0.62	BF183	0.52	BF680	0.32	BU208	3.15	TIC46	10.44	2N3054	0.62
ACY39	0.78	BC126	0.24	BC212*	0.17	BC477	0.20	BD237	0.69	BF184	0.31	BF681	0.28	BU208	3.15	TIC46	10.44	2N3054	0.62
AD140	0.68	BC132	0.17	BC213*	0.16	BC478	0.19	BD238	0.70	BF185	0.28	BFT41	0.48	BU208	3.15	TIC46	10.44	2N3054	0.62
AD142	0.69	BC134	0.20	BC213*	0.16	BC479	0.19	BD253	2.58	BF194*	10.12	BFT43	0.55	BU208	3.15	TIC46	10.44	2N3054	0.62
AD143	0.71	BC135	0.19	BC214*	0.17	BC547*	0.13	BD410	1.65	BF195*	10.11	BFW11	0.66	BU208	3.15	TIC46	10.44	2N3054	0.62
AD149	0.86	BC136	0.20	BC214*	0.17	BC548*	0.12	BD437	0.98	BF196	10.14	BFW30	2.17	BU208	3.15	TIC46	10.44	2N3054	0.62
AD161	0.65	BC137	0.20	BC214*	0.17	BC549*	0.15	BD438	1.17	BF197	10.15	BFW59	10.10	BU208	3.15	TIC46	10.44	2N3054	0.62
AD162	0.70	BC138	0.30	BC238*	0.15	BC550	0.15	BD517	0.41	BF198	10.29	BFW60	10.20	BU208	3.15	TIC46	10.44	2N3054	0.62
AF114	0.35	BC140	0.90	BC239C	0.23	BC556	0.18	BD518	0.43	BF199	10.29	BFW90	0.28	BU208	3.15	TIC46	10.44	2N3054	0.62
AF115	0.35	BC141	0.95	BC251A & B		BC557*	0.14	BD519	0.88	BF200	0.65	BFX29	0.33	BU208	3.15	TIC46	10.44	2N3054	0.62
AF116	0.41	BC142	0.29	BC252A*	0.25	BC559*	0.15	BD520	0.88	BF218	0.42	BFX84	0.30	BU208	3.15	TIC46	10.44	2N3054	0.62
AF117	0.32	BC143	0.33	BC252A*	0.25	BC559*	0.15	BD599	0.87	BF224J	10.20	BFY18	0.53	BU208	3.15	TIC46	10.44	2N3054	0.62
AF118	0.98	BC147*	0.12	BC253*	0.17	BD115	0.93	BD600	0.92	BF240	10.32	BFY50	0.33	BU208	3.15	TIC46	10.44	2N3054	0.62
AF121	0.50	BC148*	0.11	BC261A	0.28	BD123	0.98	BDX14	1.02	BF241	10.31	BFY51	0.31	BU208	3.15	TIC46	10.44	2N3054	0.62
AF124	0.38	BC149*	0.13	BC262A*	0.26	BD124	0.88	BDX18	1.55	BF244	10.37	BFY52	0.30	BU208	3.15	TIC46	10.44	2N3054	0.62
AF125	0.38	BC152	0.25	BC263B	0.27	BD130Y	1.56	BDX32	2.76	BF245	10.68	BFY90	1.37	BU208	3.15	TIC46	10.44	2N3054	0.62
AF126	0.36	BC153	0.20	BC266	0.16	BD131	0.49	BDX64A	1.89	BF255	10.58	BLY15A	1.09	BU208	3.15	TIC46	10.44	2N3054	0.62
AF127	0.45	BC154	0.20	BC268C	0.14	BD132	0.54	BDX65A	1.69	BF256*	10.49	BR101	0.47	BU208	3.15	TIC46	10.44	2N3054	0.62
AF139	0.48	BC157*	0.13	BC294	10.37	BD133	0.51	BDY16A	0.83	BF257	0.49	BRC4443	0.76	BU208	3.15	TIC46	10.44	2N3054	0.62
AF147	0.52	BC158*	0.12	BC300	0.60	BD135	0.42	BDY18	1.55	BF258	0.53	BRY39	0.48	BU208	3.15	TIC46	10.44	2N3054	0.62

LINEAR IC's		Type	Price (£)	Type	Price (£)	DIODES		Type	Price (£)	ZENER DIODES		Type	Price (£)	RESISTORS		Alternative gain versions available on items marked *	
BRC1330	10.93	SC9503P	0.95	TAA960	11.35	AA113	0.17	8Y206	0.31	400mW plastic 3.0-33V	12p each	COLOUR BAR					
CA3005	1.80	SC9504P	0.97	TAD110	12.66	AA119	0.13	8Y238	0.25	1/1.3W plastic 3.3-180V	20p each	GENERATORS					
CA3012	1.32	SL414A	1.91	TBA120A	0.90	AA123	0.30	8Y238	0.25	1.5W flange 4.7-75V	85p each	Labgear CM6052/CB: VHF/					
CA3014	1.80	SL432A	2.52	TBA120S	0.99	AA123	0.30	FSY11A	0.58	2.5W plastic 7.5-75V	48p each	UHF gives standard 8 band					
CA3018	1.06	SL450	5.10	TBA240A	13.98	AY102	1.85	FSY41A	0.51	20W stud 7.5-75V	74p each	colour bars + variable					
CA3018	1.06	SL901B	14.10	TBA281*	12.07	BA100	0.24	IT44	0.08	75W stud 7.5-75V	£5.60 each	tuning + front panel on/off					
CA3020	1.86	SN72440N	10.46	TBA295	12.58	BA102	0.25	ITT210	0.63			switch + sync trigger					
CA3028A	1.06	SN72440N	10.46	TBA296	12.58	BA104	0.19	ITT210	0.63			output + blank raster + red					
CA3028B	1.26	SN76001N	11.95	TBA480U	11.84	BA110	0.80	ITT921	0.12			raster + crosshatch + grey					
CA3045	1.35	SN76003N	2.24	TBA500	11.99	BA111	0.70	ITT922	0.12			scale step wedge + colour					
CA3046	1.02	SN76013N	1.50	TBA500Q	12.00	BA115	0.85	ITT923	0.18			bar + centre cross + dot					
LM309K	1.98	SN76013ND1.25		TBA500Q	12.00	BA121	0.15	ITT1075	0.15			pattern + centre dot.					
MC1307P	11.32	SN76023N	1.50	TBA500Q	12.00	BA129	0.39	ITT2001	0.12			£148.05					
MC1310P	12.94	SN76023ND1.25		TBA500Q	12.00	BA145	0.19	ITT2002	0.13								
MC1312P	2.20			TBA530Q	12.50	BA148	0.19	ITT2003	0.25								
MC1314P	3.85	SN76033N	2.24	TBA540	13.21	BA154	0.19	OA10	0.37								
MC1315P	4.15	SN76110N	10.32	TBA540Q	13.20	BA155	0.19	OA47	0.15								
MC1327P	11.86	SN76226N	13.15	TBA550Q	14.10	BA155	0.19	OA81	0.17								
MC1327PQ		SN76227N	11.85	TBA560C	13.13	BA156	0.15	OA90	0.10								
MC1330P	11.86	SN76502N	10.92	TBA560CQ	13.22	BA157	0.25	OA91	0.12								
MC1350P	10.85	SN76530P	11.85	TBA570	11.29	BA158	0.28	OA200	0.10								
MC1351P	10.90	SN76544N	11.85	TBA641AX12		BA201	0.13	OA202	0.13								
MC1352P	10.90	SN76660N	10.90	TBA673	12.19	BAK13	0.08	S2M1	0.38								
MC1353P	0.92	SN76666N	10.90	TBA700	12.90	BAK16	0.10	S6M1	0.49								
MC1355P	1.15	TA7073P	13.51	TBA720Q	12.39	BB10											

COLOUR, UHF & TELEVISION SPARES

TELETEXT 77, MANOR SUPPLIES NEW ASSEMBLY KIT. AERIAL INPUT COLOUR, MIXED 'OFF AIR' & TELETEXT, NEWSFLASH, ETC. DEMONSTRATION MODEL IN OPERATION.

NEW! COMBINED COLOUR BAR GENERATOR AND CROSS HATCH UNIT KIT, MK. 4 AERIAL INPUT, ALSO GIVES R-Y, B-Y AND OTHER FUNCTIONS £35.00 p.p. 85p.*

NEW! COLOUR BAR GENERATOR KIT, MK. 3 (FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS) AERIAL INPUT, ALSO GIVES R-Y, B-Y AND OTHER FUNCTIONS £25.00 p.p. 85p.*

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR, BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £11.00 + 45p. pp.* COMPLETE TESTED UNITS, READY FOR USE (DE-LUXE CASE) £18.00 p.p. 75p.*

NEW GREY SCALE KIT, ADDS ON TO ABOVE CROSS HATCH KITS AND UNITS £2.90 p.p. 25p.*

"NEW TYPE" SIGNAL STRENGTH METER, ONE CONTROL, P.C. BOARD FULL KIT £18.00 p.p. 75p.*

CRT REACTIVATOR PROJECT FULL KIT £18.80 p.p. £1.00*

"TELEVISION" COLOUR SET PROJECT. MARK II DEMONSTRATION MODEL WITH LATEST IMPROVEMENTS. WORKING AND ON VIEW, LISTS AVAILABLE.

"TELEVISION" PROJECT CROSS HATCH KIT £3.60 p.p. 20p.*

VIDEO PRE-AMP MOD. KIT (Oct. '75 Article) £1.20 p.p. 20p.

SPECIAL OFFER I.F. Panel, leading British maker, similar design to "Television" panel. Now in use as alternative inc. circuit and connection data. checked and tested on colour £12.80 p.p. 80p. Also DECODER panel checked and tested on colour, full details, £16.80 p.p. 85p.

"FIVE in ONE" PANEL replaces Tuner IF, Decoder, RGB, and sound boards of original project. Tested on colour, with all data. £30.00 p.p. 90p.

MAINS TRANSFORMER 280W for "T.V." Colour Set £11.50 p.p. £1.20.

TRIPLER £6.00 p.p. 75p. ERIE FOCUS £2.20, p.p. 30p. NEW AUDIO UNIT £2.60 p.p. 30p. Original packs still available. List on Request.

STABILISER UNITS, "add on" kit for either 40V or 20V, £2.80 p.p. 35p.

DECCA Colour T.V. Thyristor Power Supply. HT, LT etc. £3.80 p.p. 95p.

BUSH CTV25 Power Supply Unit £3.20 p.p. £1.20.

PYE 697 Line T.B. P.C.B. for spares, £1.50 p.p. 85p.

MULLARD AT1023/5 convergence yoke. New £2.50 p.p. 60p.

DLIE delay line. New 90p p.p. 40p. AT1025/06 blue lat. 75p p.p. 30p.

PHILIPS G6 single standard convergence panel, incl. 16 controls, switches etc., and circuits £3.75 p.p. 75p, or incl. yoke, £5.00. PHILIPS G8 panels for spares, decoder £2.50 p.p. 75p. Field/line osc. 75p p.p. 35p.

VARICAP, Mullard ELC1043 UHF tuner £4.20, ELC1043/05 £5.50, G.I. type (equiv. 1043/05) £3.50 p.p. 30p. UHF & VHF salvaged varicap tuners £1.50. Control units, 3PSN £1.25, 4PSN £1.80, 5PSN £2.30. Special offer 6PSN £1.00, 7PSN £1.80 p.p. 25p. TAA 550 30p p.p. 15p.

VARICAP VHF PHILIPS £1.80, ELC1042 £4.80, p.p. 30p, ELC1042 on PYE P.C.B. £5.40, Plug in 6 posn. control unit £2.50 p.p. 65p.

VARICAP UHF/VHF ELC 2000S £12.50 p.p. 65p.

UHF/625 Tuners, many different types in stock. Lists available. UHF tuners transistd. incl. s/m drive, indicator £3.85; 6 posn. or 4 posn. push-button £4.20 p.p. 85p. Integrated tuners BUSH, DECCA, PYE 40 6 posn. £4.50 p.p. 90p. AE ISOL 30p p.p. 20p.

TRANSISTORISED 625 IF for T.V., sound tested (as featured in Practical Wireless, Nov. '75). £6.80 p.p. 65p.

PHILIPS 625 I.F. Panel incl. cct 50p p.p. 50p.

TURRET TUNERS, KB "Featherlight" VC11, Philips 170 series, GEC 2010 £2.50, GEC 2018, 2019, 2038, 2039 5 position £4.20 p.p. 75p.

TBA "Q" I.C.s. 480, 530, 540, £2.20, 550, 560C, 920 £3.20 p.p. 15p.

HELICAL POTS, 100K. 4 for £1.20 p.p. 20p.

BRC 1500 Mains Droppers, two for 90p p.p. 40p.

LINE OUTPUT TRANSFORMERS. New guar. p.p. 75p.

BUSH 105 to 186SS, etc..... £6.40

DECCA DR1, 2, 3, 121/123, 20/24, etc..... £6.40

DECCA MS2000, 2400..... £5.80

FERG., HMV, MARCONI, ULTRA 850, 900, 950I..... £7.30

950II, 1400, 1500, 1590..... £5.90

GEC 2000, 2047 series, etc..... £6.20

ITT/KB VC2 to 53, 100, 200, 300 £6.20

MURPHY 849 to 2417, etc..... £6.40

PHILIPS 19TG121 to 19TG156. £3.80

PHILIPS 19TG170, 210, 300..... £6.20

PYE 11U, 368, 169, 769 series..... £6.20

PYE 40, 67 series (36 to 55)..... £3.80

PAM, INVICTA, EKCO, FERRANTI equivalents as above.

SOBELL 1000 series..... £6.20

STELLA 1043/2149..... £6.20

THORN 850 Time Base Panel, Dual Standard 50p p.p. 75p.

MULLARD Scan Coils Type AT1030 for all standard mono 110° models, Philips, Stella, Pye, Ekco, Ferranti, Invicta £2.00 p.p. 75p.

PHILIPS G8 Tripler (1174) £6.00 p.p. 75p. Others available.

6.3V CRT Boost Transformers £2.90 p.p. 75p., Auto type £1.80 p.p. 45p.

CALLERS WELCOME AT SHOP PREMISES

THOUSANDS OF ADDITIONAL ITEMS AVAILABLE NOT NORMALLY ADVERTISED

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

(Near W. Hampstead tube stn: 28, 59 159 Bus Routes) 01-794 8751


Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

PLEASE ADD 12½% VAT TO PRICES (EXCEPT * 8%)

MANOR SUPPLIES

COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)

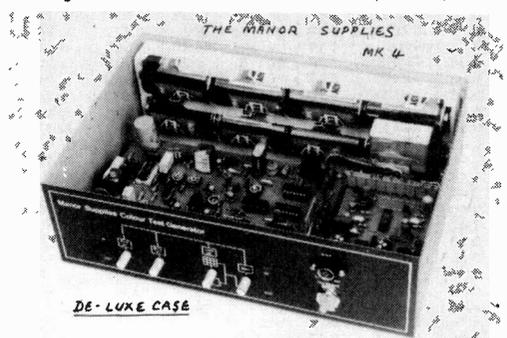

DE-LUXE CASE

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars, all R-Y, B-Y and Lum. Combinations.
- ★ Plus cross hatch grey scale, peak white and black levels.
- ★ Push button controls, small, compact battery operated.
- ★ Simple design, only five i.c.s. On colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £35.00 + 8% VAT + 85p P/Packing.

CASES, ALUMINIUM £1.80, DE-LUXE £4.80, BATT. HOLDERS 78p + 8% VAT.

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS.

- ★ Output at UHF, applied to receiver aerial socket.
- ★ All MK4 colour functions added to cross hatch, grey scale, peak white & black levels of original units.
- ★ Push button controls, small, compact, battery operated.

PRICE OF MK3 COLOUR BAR KIT £25.00 + 8% VAT + 85p P/Packing.

CASE EXTRA £1.40, BATT. HOLDERS 78p + 8% VAT

- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, N.W.6.
- ★★ Every kit fully guaranteed.

ALSO NOW AVAILABLE

ALTERNATIVE MAINS SUPPLY KIT £5.78 + 8% VAT + 50p P/Packing.

ALTERNATIVE VHF MODULATOR (CH1 to 4) FOR OVERSEAS. INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V. APPLICATION.

CALLERS WELCOME AT SHOP PREMISES.

MANOR SUPPLIES


172 WEST END LANE, LONDON, N.W.6.

(Near W. Hampstead Tube Station (Bakerloo Line).)

Tel: 01-794 8751.

Mail Order:-

64, GOLDERS MANOR DRIVE, London, N.W.11.

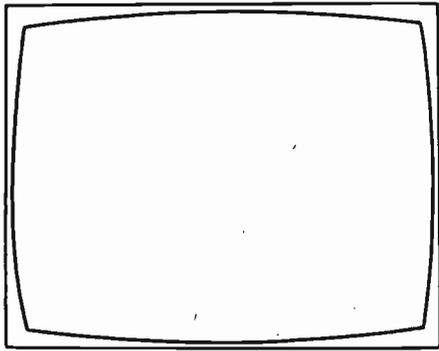

TELEVISION

FOLLOW THAT CIRCUIT!

ASSISTANT EDITOR

John A. Reddihough

TECHNICAL EDITOR

Luke Theodossiou

ART EDITOR

Peter Metalli

ADVERTS MANAGER

Roy Smith 01-634 4383

CLASSIFIED ADVERTS

Colin R. Brown 01-261 5762

Lionel Howes

We regret that due to his continuing ill health Lionel Howes, editor since October 1974, has had to relinquish the position. We are sure that readers and his many friends will join us in wishing him a speedy recovery to good health. It is hoped that he will be able to continue his involvement with the magazine at a later date.

A well known technical publisher used to use the slogan "books are tools". If you think that this is maybe far-fetched, just consider how often you have to refer to data of one sort or another, or a service manual when the fault you're dealing with won't respond to the normal checks and you've gone as far as you can with visual examination and prodding around. Practical works of reference are indeed tools in that they contribute to the process of successfully carrying out a repair.

The most useful tool of this sort is of course the service manual, and here above all else the circuit diagram is the item that contributes most in guiding you to a successful conclusion. There are many times when even the most experienced engineer can't get any farther without a study of the relevant circuit. This is much more likely to be the case if the set he's dealing with is one that he hasn't encountered all that often before – or perhaps not at all. With sets of foreign origin the problem is even greater. Take the back off one of those reliable Japanese sets that has at last succumbed to some sort of ailment and you're likely to be confronted with a mass of printed circuit boards of various shapes and sizes, interlinked by a labyrinth of multi-coloured wires. In this situation it's advisable to consult the circuit diagram first, to ascertain just what sort of circuit you're going to have to poke around in.

So we're back to circuit diagrams being tools. And the point we'd like to make here is that there are always good tools and bad tools and that this is nowhere less so than in the case of circuit diagrams. Considering that they all show how the same basic sorts of components are connected together it's quite extraordinary the degree of variation one finds. Some circuits are so logically and clearly laid out that one can see almost instantly where the power supplies come from and go to and the progress of the signals from the input to the output. Good tools! At the other extreme one comes across circuits that are so obscure that one is never quite sure without a lot of chasing along lines with a fine tipped instrument – the writer uses a small scapel – whether one is following a power supply or a signal path, let alone a feedback path, pulse path or something like a blanking or beam limiting arrangement. Indeed there is one oriental setmaker who issues circuits where even the main power supply paths can take an age to trace, whether you're going from the power supply panel to the fault area or vice versa. The supply wanders from board to board, splitting up to go hither and thither, sometimes going off a board and then going back in again at another point, and so on. A very bad tool, even if the voltages are clearly shown!

Is there anything that can be done about this? Perhaps it's getting too late in the day, since TV circuits are getting simpler all the time and if the concentration on i.c.s goes much further they'll soon consist of a very few items whose purpose is quite clear. But for some reason or another a resurgence of complexity always seems to occur. Your colour TV circuits may suddenly start to look like glorified crystal sets: but what about the VCRs and Teletext decoders you're going to have to deal with next? No, it's not too late to air the matter once more.

The fact is that most circuits are built up from basic "building bricks" which require standard inputs and outputs and the normal power supply connections. Transistor amplifiers may be of the common-emitter, common-base or emitter-follower configuration, may use pnp or npn transistors and may be powered from positive or negative rails. But there still has to be an input, a power supply, biasing and a load. And these can be drawn in standard ways. The same point can be made about most other discrete circuitry, oscillators, switches and so on. And however complex they are, it is possible to draw feedback paths, pulse shaping networks and so on quite clearly. The problem is greater with i.c.s, since you can't see what is lurking behind a particular pin. A block diagram within the i.c. block is the answer, but is not always practicable. But even without it, the links to the following and preceding i.c.s, the power supply feeds and external controls and time-constant or tuning circuits can be drawn clearly. All too often however they're not.

To get any order – and that's what's required – into all this some general and internationally accepted guidance is necessary. There have been attempts in the past – rather distant past now unfortunately – to lay down basic guide-lines. Simple potential divider, bias networks, load circuits, cross-couplings and so on can and should be drawn in a standard manner. Is it the training of draftsmen, or the engineers who brief them, or what that results in simple circuitry being drawn in unnecessarily confusing ways? Some basic guide-lines could at least be hammered home – though probably no one would agree as to what exactly they should be! What's certain is that we do need this improvement to one of our most essential tools.

COVER PHOTOGRAPH

Our thanks to Thorn Consumer Electronics Ltd. for the loan of the Ferguson Model 3738 colour set shown on the cover displaying the TV Games project featured in this issue.

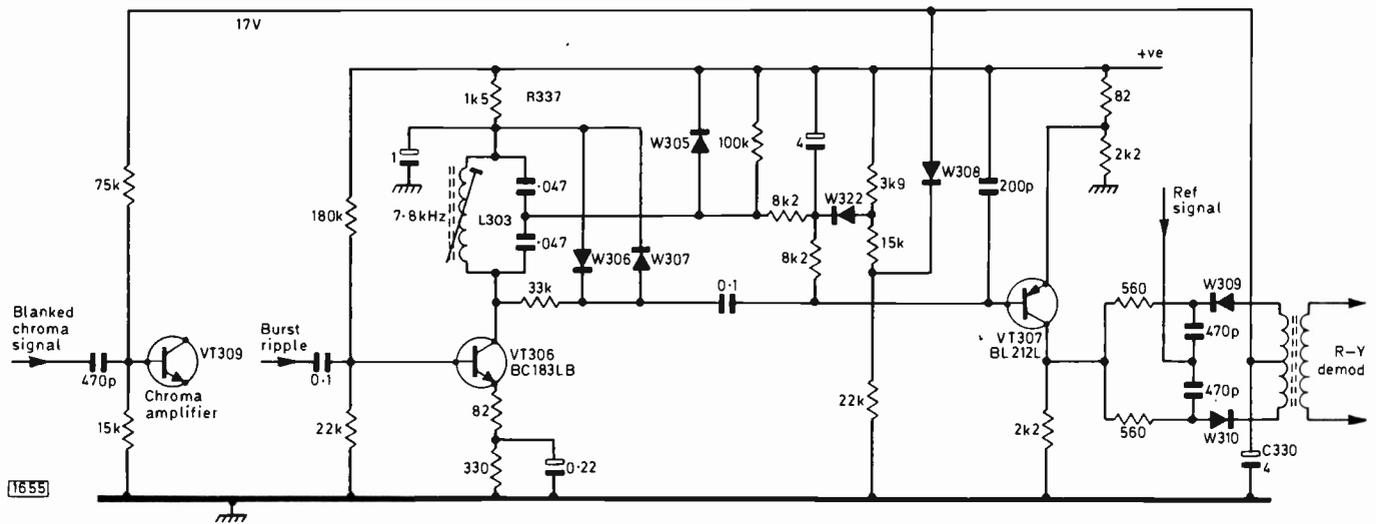


Fig. 3: The chroma turn-on bias is derived from the PAL switch circuit, which is driven by the ident amplifier VT306.

signal disappeared as it should have done in the first place (oh the complexity of it all).

Getting the Colour Back

We now had a clear picture in what should have been black and white with no trace of colour. Taking the opportunity, we set up the gray scale with the first anode potentiometers and the drive controls until the monochrome picture looked respectable, and then turned our attention to the decoder board. Most voltages were, well, not too far out, but there was a complete absence of turn-on voltage at the base of the chroma amplifier VT309 (Fig. 3). Ah ha, we said. Nipping smartly over to the PAL switch driver/chroma bias generator transistor VT307 we found no voltage at its emitter. The network of diodes connected in its base circuit caused us to have a momentary mental blackout, so we broke off for a cup of coffee.

Refreshed, we returned to the fray and found that there was now no voltage at the collector of the ident amplifier VT306, whereas this voltage had been about right earlier. A niggling doubt crept in. If the collector voltage had been there earlier, the chances were that the turn-on voltage for the chroma amplifier had also been there. If so, why had there been no colour? Dismissing these dismal thoughts, we investigated the supply to VT306. R337 had its 30V at one end but there was a dead short to chassis at the other. Looking at the circuit showed this to be unlikely from a component point of view, so we took the plastic cover off L303 and there was a thin sliver of solder which had somehow got under the cover during the manhandling process, having laid dormant and harmless for many moons after having dropped down from the previously mentioned clumsy soldering of the line output transistor. Being under cover, it had escaped our eagle eye. With the short removed however there was still no colour and the voltages, although much nearer, were still not right.

It was obvious that the trouble was now leading us back to the burst detector, and much time was spent checking and rechecking as the colour burst came in all right but petered out at the emitter of the burst detector driver VT302. Just at that moment my good friend Ray came on the scene. We poured out our troubles. "Can't say I've had much trouble with decoder boards on this chassis", said Ray helpfully. He suggested that since the detector coil L301 didn't tune there may be some solder under that one too. We shook our head. Couldn't get in there.

I went to see if the coffee pot was still going, and left Ray playing. A shout of triumph brought me hurrying helter skelter. Ray had taken the cover off L301 and there it was: a spot of green on one of the wires, which parted when touched. Again disturbed by the manhandling? Red faced and ashamed, I muttered that I had been about to investigate the condition of L301 when he came in but that nevertheless he was a fine fellow and a valued friend.

Having reset L301 after repairing it, glorious colour was displayed. "OK now?" Ray asked irritatingly. "I'll just borrow an indoor aerial and be on my way".

The Picture and Sound Vanish

When the smirking idiot had gone, we subjected the set to a simulated manhandling process – just in case. The picture and sound vanished. No chopper output, no 30V line, all fuses intact. Warily we returned to the fray. We spent some time looking for dry-joints etc. The 30V stabiliser transistor VT601 was OK (Fig. 4), with voltage at its collector. But there was nothing at its base to turn it on. Check C609, but this normally causes ragged verticals when defective, and it wasn't shorted. Check the zener W605. No shorts. Come back Ray, you're not an idiot, I don't mind if you do smirk.

Wait a minute though, have another look at the supply to VT601. Not quite right is it? Check C607. Open-circuit. Replace. All's well. I'm rather glad he didn't come back.

We delivered the set ourselves, and very carefully too.

Effects of Age

As these 3000 and 3500 chassis begin to feel their age,

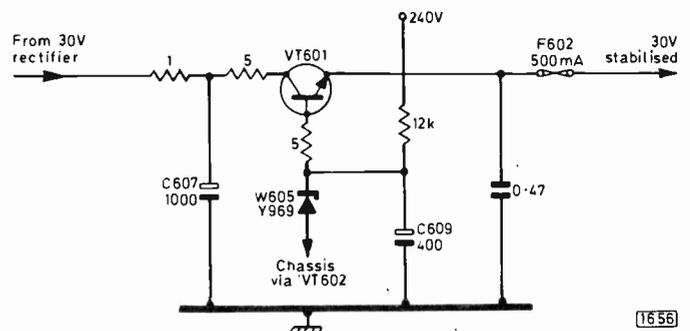


Fig. 4: The 30V stabiliser circuit.

the previous well known list of stock faults apply a little less and one now encounters the effects of heat over an extended period, corroding contacts etc. — as indeed we mentioned in the case of R907 on the beam limiter board. It's also worth while having a look at the timebase board, which is revealed in part when the beam limiter board is lifted. Particularly in older models, there is often quite a bit of corrosion around L502 and R528, whether W507 is fitted or not — these components are in the power supply feed to the line driver and output stages. A clean up job here can save trouble later.

Similar remarks apply to the power supply board, where the wirewound resistors are now tending to part company with the print — and it must be admitted that it's not easy to work on the underside of this panel. Our experience shows that the items likely to require replacement on the power supply panel are the chopper transistor itself (VT604) — remember to check its insulating washer, which can be punctured, and clear away any corrosion — the wirewound resistors (check all for continuity), the electrolytic capacitors (particularly C607), the 30V zener W605, and transistors VT601 (30V stabiliser) and VT605 (chopper driver). Smaller components likely to escape attention but which we've found troublesome include C631 (0.01 μ F) in the driver's collector circuit and C622 (0.022 μ F) and W618 in the feedback amplifier circuit.

Whilst line output stage failure due to faulty line output transistor(s) or the tripler is pretty obvious and easily checked (for example by merely pulling off the tripler lead from the transformer) there are other and more obscure line timebase troubles. For example, intermittent loss of line hold is often due to the small electrolytics C506 and C511 playing about. The two can be replaced in moments and there is no point in holding a conference about whether they are faulty or not or which. Oh yes, when soldering the line output transistor(s) make sure that no solder falls on the decoder panel . . .

The convergence panel has been subjected to consider-

able alteration as far as the layout is concerned, but the same basic comments apply. A little scorching here and there, shorted diodes or electrolytics, defective potentiometers and of course our old friends the first anode switches which tend to leak, thereby robbing the relevant c.r.t. first anode of its voltage and resulting in the absence of that colour (usually green, remember . . . ?).

We have said that the sudden drop out of a certain colour is often due to low first anode voltage on the c.r.t. gun concerned. The trouble is quite often that one colour comes up far too bright however, so that all that can be seen is an almost blank screen of that colour, making it difficult to see picture information contributed by the other two colours. A quick check at the tube cathodes will often reveal that although there may be about 160V on two of them there is precious little at all on the other. This immediately throws suspicion on the collector load resistor of the output transistor concerned. Earlier models used separate wirewound resistors (R250, R264 and R277). Later versions use a pack with four lead-out wires, enabling the unit to be stood off the panel. It appears that this thick-film unit is not as reliable as was at first hoped, and we fit separate resistors as required.

Intermittent Colour Drop Out

This is not a servicing article on the 3000 chassis however, so we had better not carry 'on too much about these sets. We have a 9000 series set which suffers from intermittent colour drop out. The slightest vibration restores colour (you've only got to blow on the cabinet and the colour comes back) and you can't make it go off no matter what. All plugs, sockets, leads and soldered connections have been checked, probed and prodded. No result. The colour stays for hours after intensive searching and then drops out. Can you hear me Ray? Rayyyy . . .

A Simple Soldering-Iron Stand

Malcolm Burrell

ACCIDENTS with hot soldering irons can be annoying at the least and both expensive and embarrassing at the most! In the home workshop, on the kitchen table or in the field some form of stand is desirable. The one shown here is just as efficient as many commercial models and was devised and built in half an hour.

It consists of a length of tubing, for example $\frac{7}{8}$ in. aerial mast, hammered flat at one end which then has two holes drilled in it so that the tubing can be mounted on a stout block of wood or screwed directly on to the bench. All sorts

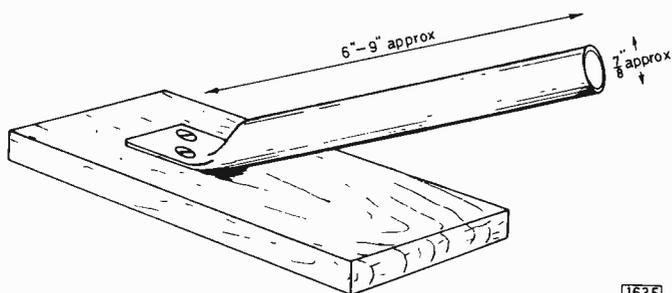


Fig. 1: The soldering-iron stand.

of variations are possible. A double unit to accommodate both a standard and a small low-wattage iron can be constructed for example, while a length of tubing mounted in the tool box provides a convenient stand which will protect other tools — and customers' carpets!

A hardboard cheek can be mounted on the lid of the tool box so that a long lead can be stored on the outside, giving more space for tools and essential spares inside. If the electrical installations in your area are not too diverse, fit a plug to the lead: a useful arrangement is a two-pin 5A plug with a 13A type razor adaptor.

If your soldering iron's bit is not of the fixed type it's a useful habit to give it a twist every time you plug the iron in: this ensures that the fixing does not seize and facilitates replacement of defective bits without having to scrap the element as well. ■

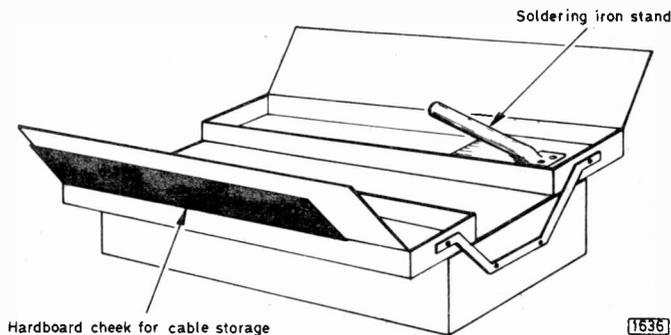


Fig. 2: Metal tool box adaptations.

Get a great deal from Marshall's

A. Marshall (London) Ltd Dept: TV
40-42 Cricklewood Broadway, London NW2 3ET
Tel: 01-452 0161/2 Telex: 21492
85 West Regent St, Glasgow G2 2QD Tel: 041-332 4133
1 Straits Parade, Fishponds, Bristol BS16 2LX Tel: 0272 654201/2
Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat
Trade and export enquiries welcome. Please enquire for types not listed.
NEW 168 PAGE CATALOGUE WITH 500 NEW LINES
55p POST PAID (40p to callers)

Our range covers over 7,000 items. The largest selection in Britain.

TOP 200 IC's TTL LINEARS

CA3018	0.81	LM380N-8	0.80	LM1845N	1.35	SN78008KE	2.50	TAA320A	1.15
CA3018A	1.08	LM380N14	0.88	LM1848N	1.80	SN78013N	1.70	TAA350A	2.48
CA3020	1.78	LM381AN	2.45	LM3900N	0.75	SN78013ND	1.57	TAA521	1.00
CA3020A	2.29	LM381N	1.60	LM3909N	0.68	SN78018KE	2.50	TAA522	1.00
CA3021	2.18	LM382N	1.25	MCI303L	1.47	SN78023N	1.50	TAA550	0.80
CA3022	1.83	LM384N	1.45	MCI304P	1.85	SN78023ND	1.57	TAA560	1.00
CA3023	1.78	LM386N	0.80	MCI305P	1.85	SN78033N	2.55	TAA570	2.30
CA3036	0.87	LM387N	1.05	MCI308P	1.00	SN78110N	1.46	TAA821	1.15
CA3041	1.49	LM388N	1.00	MCI310P	1.91	SN78115N	1.87	TAA851A	1.32
CA3042	1.49	LM389N	1.00	MCI312P	1.98	SN78118N	2.08	TAA818	1.32
CA3043	2.01	LM555CH	0.48	MCI327P	1.54	SN78131N	1.30	TAA700	3.91
CA3044	1.84	LM565CN	1.30	MCI350P	0.75	SN78226N	1.94	TAA930A	1.00
CA3046	0.88	LM701C	2.80	MCI351P	1.20	SN78227N	1.51	TAA930B	1.05
CA3048	2.23	LM702A	2.80	MCI352P	0.87	SN78228N	1.75	TAD100	1.95
CA3052	1.82	LM702C	0.75	MCI357P	1.45	SN78530N	0.81	TBA231	1.20
CA3064	1.64	LM703LN	1.05	MCI414L	1.20	SN78532N	1.50	TBA400	1.50
CA3065	1.74	LM709	0.65	MCI430P	2.20	SN78533N	1.30	TBA500	2.21
CA3066	3.02	LM709-8	0.45	MCI431P	3.00	SN78544N	1.44	TBA500D	2.30
CA3067	3.13	LM709-14	0.45	MCI433B	3.00	SN78545N	2.09	TBA510	2.21
CA3068	3.48	LM711CN	0.55	MCI435B	1.80	SN78546N	1.44	TBA5100	2.30
CA3070	2.49	LM726	5.38	MCI437L	1.80	SN78552-2	0.85	TBA520	2.21
CA3071	2.31	LM733CN	1.45	MCI438R	7.48	SN78552N	2.08	TBA5200	2.30
CA3072	2.37	LM741C	0.65	MCI439G	1.65	SN78550N	1.10	TBA530	1.98
CA3075	1.88	LM741C-8	0.40	MCI455G	1.55	SN78622AN	1.10	TBA5300	2.07
CA3078	1.83	LM741C-14	0.50	MCI458G	2.20	SN78550N	1.10	TBA540	2.21
CA3087	1.93	LM747CN	0.90	MCI495L	4.78	SN78668N	0.80	TBA550	3.13
CA3088	0.51	LM748-8	0.50	MCI498G	1.10	SN78668N	0.92	TBA5600	3.22
CA3088F	1.59	LM748-14	0.50	MCI529G	6.50	SL414A	2.35	TBA570	1.29
CA3089E	2.52	LM1303N	1.47	MCI530G	6.50	SL415	2.50	TBA641B	2.50
CA30900	3.80	LM1304AH	1.85	MCI531G	6.50	SL610C	2.35	TBA700	1.52
LM301AH	0.87	LM1305N	1.85	MCI553G	6.50	SL611C	2.35	TBA720AQ	2.30
LM301-8	0.44	LM1307N	1.10	MCI545L	8.75	SL620C	3.50	TBA750	1.98
LM308H	1.82	LM1351N	1.20	MCI550G	0.80	SL623C	5.75	TBA800	1.20
LM308N	1.17	LM1310N	0.91	MCI552G	6.40	SL630C	2.35	TBA820	1.03
LM370N	3.00	LM1458N	0.91	MCI553G	6.40	SL840C	4.00	TBA940	1.82
LM371H	2.25	LM1498N	0.91	MCI590G	3.75	SL841C	4.00	TCA180B	1.81
LM372N	2.15	LM1800N	1.78	SAS560	2.50	SL701C	2.00	TCA290A	1.30
LM373N	2.25	LM1808N	1.92	SAS570	2.50	TAA263	1.25	TCA290A	3.13
LM374N	2.25	LM1820N	1.10	SN78001N	1.57	TAA300	1.89	TCA740	2.76
LM377N	1.75	LM1841N	1.75	SN78003N	2.55			TCA800	3.13
LM378N	2.25	LM1828N	1.75						
LM379S	3.95								

THIS IS JUST A SMALL SELECTION FROM OUR RANGE - PLEASE ENQUIRE FOR TYPES NOT LISTED

TELEVISION TELETEXT DECODER

WE CAN SUPPLY FROM STOCK
COMPLETE KITS OF
INPUT LOGIC CARD PARTS

@£15.50p Excluding P.C. Board
plus 50p postage & packing + 8% VAT

SN7400	0.21	SN7438	0.55	SN7485	1.85	SN74153	1.11	SN74197	1.17
SN7401	0.21	SN7440	0.21	SN7488	0.41	SN74153	1.85	SN74198	2.93
SN7402	0.21	SN7441AN	1.03	SN7490AN	0.81	SN74155	1.11	SN74199	2.93
SN7403	0.21	SN7442	0.78	SN7491AN	0.88	SN74157	0.88	SN74221	1.80
SN7404	0.28	SN7445	1.35	SN7492	0.81	SN74180	1.41		
SN7405	0.28	SN7446AN	1.23	SN7493	0.81	SN74181	1.41		
SN7406	0.74	SN7447AN	1.17	SN7494	0.74	SN74182	1.41		
SN7407	0.74	SN7448	1.17	SN7495	0.78	SN74183	1.41		
SN7408	0.29	SN7450	0.27	SN7496	1.03	SN74184	1.23		
SN7409	0.29	SN7451	0.21	SN7497	4.85	SN74195	1.23		
SN7410	0.21	SN7453	0.21	SN74100	1.15	SN74187	3.70		
SN7411	0.29	SN7454	0.21	SN74107	0.43	SN74174	1.53		
SN7412	0.21	SN7460	0.21	SN74118	0.80	SN74175	1.35		
SN7413	0.54	SN7472	0.38	SN74119	1.80	SN74176	1.23		
SN7414	1.80	SN7473	0.43	SN74121	0.49	SN74177	1.23		
SN7417	0.81	SN7474	0.43	SN74122	0.85	SN74180	1.77		
SN7420	0.21	SN7475	0.58	SN74123	0.58	SN74181	3.70		
SN7423	0.38	SN7476	0.51	SN74124	0.80	SN74180	1.81		
SN7425	0.38	SN7480	0.45	SN74141	1.03	SN74191	1.91		
SN7427	0.38	SN7482	1.10	SN74145	1.08	SN74192	1.82		
SN7430	0.21	SN7483	0.87	SN74150	1.86	SN74193	1.82		
SN7432	0.28	SN7484	0.85	SN74151	1.11	SN74198	1.17		

"Full range of Thyristors, Triacs, Diacs & Zeners - always in stock"
Prices correct at 6 April 1977, but please add VAT,
postage & packing 30p.

We also carry a comprehensive range of transistors, diodes, bridges, thyristors, diacs, opto components all kinds of integrated circuits, resistors, capacitors, sockets ALL MANUFACTURERS BRANDED PRODUCTS OVER 8500 LINES.

TELEVISION ELECTRONIC DISTRIBUTION (SPARES) LTD.

412a Hanworth Road, Hounslow, Middlesex
Telephone: 01-572 4668

PANEL REPAIR/EXCHANGE SERVICE

THORN 2000 Series, 3000/3500 Series,
8000/8500 Series.

GEC Solid State 2110 Series.

PHILIPS G8

RBM A802/823

VERY COMPETITIVE PRICES. 3 MONTHS' WARRANTY FROM DATE OF OUR INVOICE. SINGLE AND BULK PRICES ON APPLICATION. 48 HOUR SERVICE WHEREVER POSSIBLE. ALSO VERY COMPREHENSIVE RANGE OF MULLARD TV COMPONENTS, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, THYRISTORS, TRIPLERS. CATALOGUE AVAILABLE ON REQUEST.

LOOK! Phone: LUTON, BEDS. 38716

OPPORTUNITIES TRADE SALES

START AT £25 INC. VAT!!

FOR D/S COLOUR TV's
G.E.C., Philips, Murphy, Decca, Ferguson

S/S COLOUR TV's
Philips, G.E.C., Telefunken, Decca, Ferguson

FROM £40 INC. VAT!!

MONO TV's, all makes from
£5 INC. VAT

SQUARE SCREEN, all models
£12 INC. VAT!!

Deliveries arranged if necessary.

HUNDREDS OF SETS EACH WEEK TO BE
DISPOSED OF AT GIVE-AWAY PRICES.

LUTON 38716

9.30-6.00 p.m. Weekdays
10.30-1.00 p.m. Sundays

TV Games In Colour

Steve A. Money T.Eng. (CEI)

Part 1

THIS seems to be the year of the TV game. Take a look in the radio and television department of any large store and you are likely to find various television games units on sale. Most readers, being electronically inclined, would probably prefer to be able to build their own TV games unit however. *Television* has therefore developed a constructional project which provides a TV games centre having a number of advanced features which are not available on most other TV games units.

TV games are not new of course, but until this year the construction of a suitable unit would have involved the use of a large amount of complex logic and even then would provide only a simple game such as television tennis. Most TV games were to be found in amusement arcades. Realising that there was a potential market in TV games, some of the big semiconductor manufacturers developed special integrated circuits which could provide the complex logic required on a single chip. At first these were aimed at the amusement arcade and commercial games market but the devices are now at last becoming available to the home constructor so that the TV game becomes a reasonable proposition for a home construction project.

Most of the TV games units on sale in stores, and the few construction kits that have appeared recently, make use of the General Instrument type AY-3-8500 device. This will produce a selection of up to six different games, although most games units provide only four of these since the two rifle shooting games require extra equipment. The display on the screen is in black and white and includes an automatic display of the score each time a point is scored. The sound effects are usually reproduced on a speaker mounted in the TV game control unit rather than coming from the TV set.

For the *Television* games centre a newer and rather more sophisticated integrated circuit, from National Semiconductor, has been used. This is the MM57105 which, when used with the LM1889 video modulator chip, provides a full colour display on the screen, assuming of course that you have a colour receiver. Sound effects when the ball hits the bat or the boundary fence are reproduced on the sound channel of the television receiver, giving a more realistic result. Three basic games are provided, with practice versions of each. There are thus six games options to choose from. Other features, such as automatic on-screen scoring, ball control and automatic service, are included.

Before going on to deal with construction let us take a closer look at the games and features offered in this TV games unit.

Ice Hockey

Because the National Semiconductor games chip was originally developed for the North American market it is

not surprising that the first game provided is ice hockey. This is played on a blue field, representing the ice, and the wall around the playing area is marked out by a yellow line on the screen. At each end of the field the gap in the wall forms the goal. Each team consists of a goalie and three forwards which are displayed as yellow rectangles and squares respectively. Each player can move his goalie up and down the screen in front of his goal line by operating the player control. The forwards in each team are controlled by the internal logic of the game however and move up and down in a more or less random fashion.

The hockey puck appears on the screen as a small blue square and moves around inside the playing area, bouncing off the walls or players whenever it hits them. In fact the players will deflect the puck only when it's travelling in the direction of their goal line – otherwise the puck passes right through the player as if he was not there. The object of the game is to get the puck through your opponent's goal, thus scoring a point. Whenever the puck passes through either goal the current score is displayed for about a second before play automatically resumes. When one team has scored 15 points the game is won and play stops until a new game is initiated.

Tennis

The second of the games is tennis which, as one might expect, is played on a green court with blue borders at the top and bottom of the screen. In this game the rackets for the two players are shown as vertical orange lines whilst the net and scores are yellow.

The ball, which is pale green, bounces off the upper and lower borders of the court in much the same way as the puck does in the ice hockey game. In tennis the object of the game is to try to make your opponent miss the ball so that you score a point. The game is won when either of the players reaches a score of 15, and the score is displayed automatically each time one of the players fails to hit the ball with his bat.

Squash

The third basic game is squash which is played on a three sided magenta coloured court with both players at the same end. Only one of the bats is displayed at a time and will be that for the player whose turn it is to hit the ball. The two bats are displayed in different colours, one blue and the other orange. The scores are displayed in the same two colours. The pink ball can bounce off all three walls of the court, and points are scored whenever a player fails to intercept the ball on his turn. As in the other games the first player to get 15 points is the winner and play ceases at that point.

Practice

Each of the three basic games can be set up for single player practice operation. One of the player controllers then moves both bats or goalies together. This is a useful feature which allows beginners to get the feel of each game before playing in earnest.

Handicapping

One player will often be a lot more experienced than the other. To deal with this a system of handicapping can be used. There are three sizes of bat which can be selected for each player. The normal bat size is a line about $1\frac{1}{2}$ inches high on a 22 inch TV screen. An intermediate $\frac{3}{4}$ inch high bat or a small $\frac{3}{8}$ inch bat can also be selected for either player so that if the better player is given a smaller bat he will compete on more even terms with his less experienced opponent. Bat size is selected by moving the bat to be changed to the top of the court and pressing the player's reset button either once or twice until the desired bat size is produced.

Using this facility it is possible to play against the machine in the ice hockey game. One goalie is set to full size and positioned in front of the goal. The player's goalie is set to the medium size to give the machine a fair chance and the game is played by one player using the small goalie.

Ball Control

When the ball or puck hits one of the side walls it will rebound at an angle which depends upon the angle at which it actually hit the wall. This follows the same rules that apply when a ball hits a wall in real life. When the ball hits a bat however it has been arranged that the new direction of travel depends upon the positioning of the bat relative to the ball. This allows the player to direct the ball to the part of the court that he wants to send it to.

To achieve ball control the bat consists of eight segments, though it does not appear like this on the screen. If the ball hits one of the two central parts of the bat it will travel horizontally across the screen. When the ball hits one of the upper three segments it will travel at an angle towards the top of the screen. Each of the three segments produces a different angle, with the top segment giving the steepest angle and the one near the middle the shallowest angle. A similar action occurs for the lower three segments, except that the ball travels at an angle towards the bottom of the screen. Thus by placing the bat so that the ball hits it at the proper point the ball can be sent off at any one of seven different angles. The segments still operate on the smaller bat sizes but directing the ball becomes rather more difficult.

To simulate the conditions of a real match the ball is arranged so that it travels relatively slowly when play is resumed after a point has been scored. This simulates a service stroke in tennis. After the ball has been hit four times the ball speed automatically increases to make play rather more exciting.

The Circuit

Now let's us get down to the hardware side of the games unit. Fig. 1 shows the complete circuit diagram of the *Television* games centre.

Since the complex logic of the system is contained in three integrated circuits there is not a lot of other circuitry to be added, apart from a power supply and the u.h.f. modulator.

The game itself and the generation of the TV display are controlled by the MM57105 (IC1) which produces at its outputs the composite video/sync signal, with sound and chroma control signals, needed to generate the TV display. Inputs from the two player control units are used to determine the positions of the two bats and control the reset action. The actual game displayed is selected by switch S4 on the front panel of the games control unit.

Bat position is determined by the time-constant of the player control resistor (RV1 or RV2) and the timing capacitor (C1 or C2).

Network R3, C3 operates a power on reset circuit in the MM57105 so that when power is first applied all the internal logic is correctly reset and the ice hockey game is set up ready to start play.

The games circuit requires two non-overlapping clock inputs for proper operation. These are generated by the MM53114 clock generator (IC3). The input to this device is a 4.43MHz colour reference frequency, and from this all the timing and video output generation is derived.

The third special integrated circuit is the LM1889 (IC4). This is a special video modulator circuit designed to operate with video games. It produces full colour PAL signals modulated on to one of the two v.h.f. signal channels or can be used to produce just the required modulation signal.

One part of the LM1889 consists of a 4.43MHz colour reference oscillator controlled by the external crystal X1. Lead and lag networks producing 45° phase shifts are used to drive a chrominance modulator in the LM1889 which when fed with chroma control signals from the games chip will produce the required PAL chrominance subcarrier at its output.

Because we need a u.h.f. signal for use with a British television receiver the v.h.f. modulators in the LM1889 are not used.

A sound oscillator within the LM1889 uses the tank circuit L1, C12 to produce a 6MHz sound subcarrier which is frequency modulated by a control signal from the games chip to give the desired sound effects.

Video, sound and chrominance signals are all mixed together at pins 12 and 13 of the LM1889 and passed on to the u.h.f. modulator section.

The Modulator

A simple transistor oscillator using a BFY90 produces the u.h.f. carrier signal which, with the layout used, will give a signal at around channel 40. Increasing the value of C19 will enable the circuit to be tuned to a lower u.h.f. channel if desired.

Composite video is applied to the base of Tr1, which acts as an inverting, unity-gain amplifier. The signal is then tapped from the $1k\Omega$ preset RV3 and injected at the emitter of the u.h.f. oscillator transistor. In this way the carrier is modulated by the video signal, the depth of modulation being varied by RV3 - adjust for optimum results. Because it is difficult to get full modulation, it may help to advance the setting of the receiver's contrast control.

Power Supply

Two power supply lines, at $-9V$ and $-15V$, are needed for the MM57105 games chip. A simple full-wave rectifier gives the $-15V$ supply which is stabilised by the 7815 fixed voltage regulator (IC2). For the $-9V$ supply a 5.6 volt zener is used in series with the $-15V$ rail to provide the necessary voltage drop.

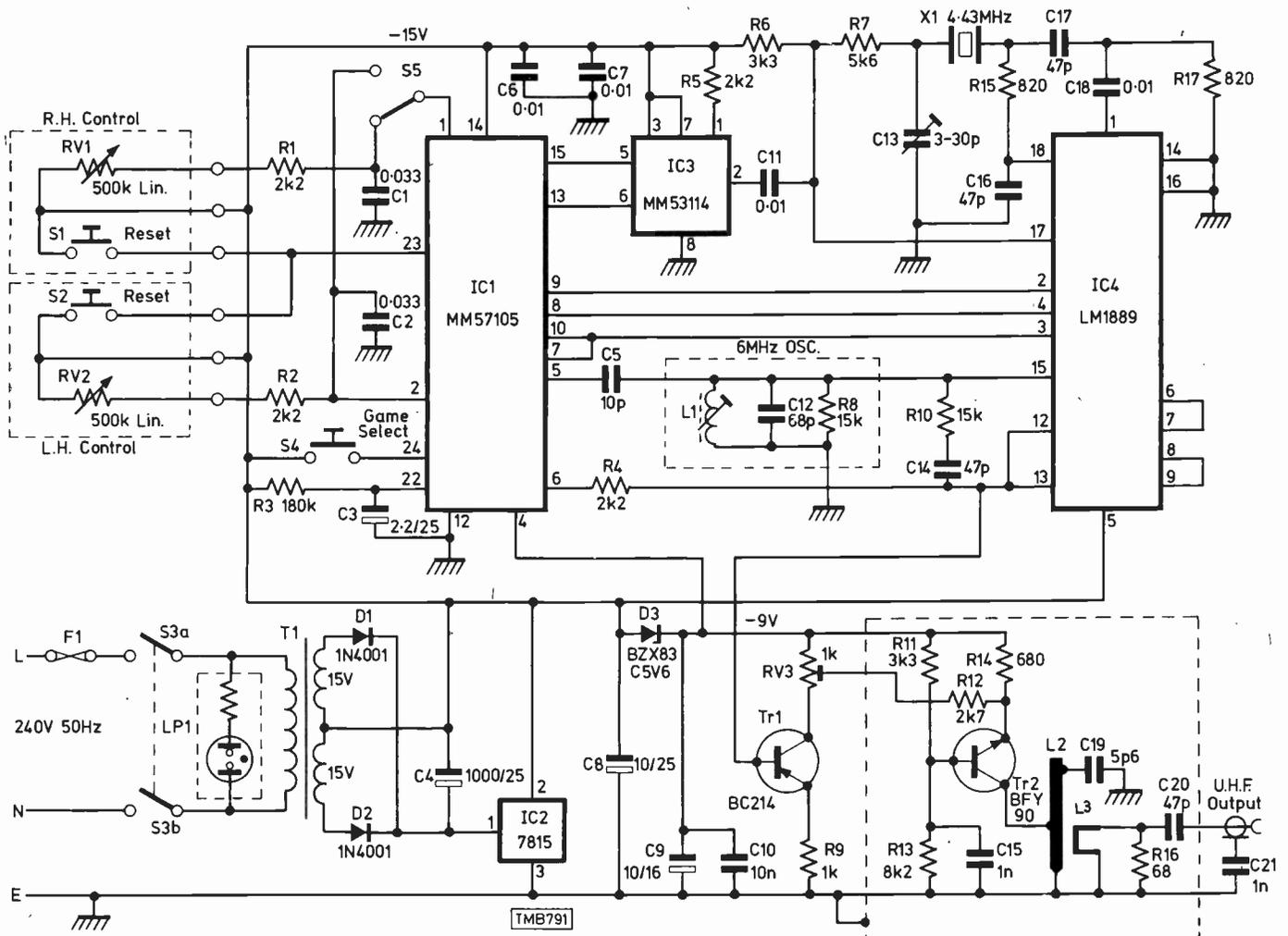


Fig. 1: Complete circuit diagram of the games unit.

★ Components list

Resistors: (all $\frac{1}{4}$ W, 5%)

R1 2.2k Ω	R7 5.6k Ω	R13 8.2k Ω
R2 2.2k Ω	R8 15k Ω	R14 680 Ω
R3 180k Ω	R9 1k Ω	R15 820 Ω
R4 2.2k Ω	R10 15k Ω	R16 68 Ω
R5 2.2k Ω	R11 3.3k Ω	R17 820 Ω
R6 3.3k Ω	R12 2.7k Ω	

RV1 500k Ω linear
 RV2 500k Ω linear
 RV3 1k Ω subminiature horizontal preset

Capacitors:

C1, 2	0.033 μ F polyester
C3	2.2 μ F tantalum bead
C4	1000 μ F 25V electrolytic
C5	10pF ceramic plate
C6, 7, 10, 11, 18	0.01 μ F ceramic disc
C8	10 μ F 25V tantalum bead
C9	10 μ F 16V tantalum bead
C12	68pF ceramic plate
C13	3-30pF ceramic trimmer
C14, 16, 17, 20	47pF ceramic plate
C15	1000pF ceramic plate
C19	5.6pF ceramic plate
C21	1000pF 1000V ceramic

Transistors and diodes:

TR1	BC214	D2	1N4001
TR2	BFY90	D3	BZX83 C5V6
D1	1N4001		

Integrated circuits:

IC1 MM57105
 IC2 7815 15V regulator
 IC3 MM53114
 IC4 LM1889
 IC1, IC3 and IC4 available as a set from A. Marshall (London) Ltd., 42 Cricklewood Broadway, London, NW2 3ET, price £17.00 including postage, packing and VAT.

Miscellaneous:

L1 50 turns 38s.w.g. enamelled close wound on standard 4mm TV coil former with can and tuning slug
 L2, L3 Part of PCB
 T1 Primary 240V
 Secondary 15V-0-15V 200mA
 X1 Standard 4.43MHz PAL colour reference crystal
 Case Vero case type 1411
 Hand controller boxes (Vero)
 Knobs for hand controllers
 S1 Min. Push button push to make
 S2 Min. Push button push to make
 S3 2 pole PC mount Push switch
 S4 2 pole PC mount Push switch (Action link removed)
 S5 2 pole PC mount Push switch
 IC sockets 24 pin DIL, 18 pin DIL and 8 pin DIL (or Soldercon sockets)
 PCB Reference no. DO34

Servicing the Tandberg CTV1 Chassis

W. S. J. Brice, B.Sc.(Eng.)

THE subject of this article, the Tandberg CTV1 chassis, is the predecessor to the company's current range of 110° solid-state colour TV receivers. In contrast to the latter it employs a 90° deflection c.r.t. and a hybrid chassis. At first glance it looks similar to many other hybrid designs, but on close scrutiny some unusual and interesting features are to be found. Correctly set up, the chassis is capable of producing excellent pictures. It helped Tandberg to establish a reputation as manufacturers of quality TV receivers.

Line Output Stage

The set is designed around a straightforward PL509/PY500A line output stage (see Fig. 1) with a tripler e.h.t. supply, but the protection of this stage is unusual and interesting. The protection device consists of two springs arranged vertically between the two line output stage valves and joined at the top by a low melting point alloy, thus forming a temperature sensitive switch which opens when either or both valves overheat, isolating the h.t. supply to the line output stage. To make the switch more sensitive to the overheating of the valves the springs have a matt black finish in order to absorb the infra-red radiation from tortured anodes more effectively. A short length of the special alloy in wire form is thoughtfully supplied with each receiver, twisted around a tag close to the bottom of the switch. Very early receivers had a fuse in place of the thermal switch.

Line Oscillator

In this hybrid receiver there is nothing quite so hybrid as the line oscillator, which uses a BC157 and an ECH84 (see Fig. 2). The BC157 is the oscillator stage, with the heptode section of the ECH84 as a reactance stage and the triode section as a voltage amplifier to give sufficient voltage swing to drive the PL509. Some earlier receivers do not have the transistor oscillator stage however, the triode section of the valve being both oscillator and driver. This is a point to watch as only one version is shown in the service information.

Field Timebase

The field timebase circuitry (see Fig. 3) is completely solid-state, using a silicon controlled switch as the field oscillator and a single transistor amplifier with linearity feedback, followed by two transistors connected as a Darlington pair to drive the rather unusual output stage. This uses a single transistor biased in class A and choke-

coupled to the scan coils. The choke is in fact an autotransformer with a step up winding providing pulses which after suitable shaping are fed to the c.r.t. cathodes for field fly-back blanking.

Power Supplies

Unlike many current designs in which the various l.t. rails required are conveniently derived from the line output stage, all the power supply rails are mains derived (see Fig. 4). The result is that the l.t. supplies are fairly complicated. The mains transformer has two l.t. windings, apart from the 6.3V winding for the c.r.t. heaters, and these feed two bridge rectifiers followed by regulator circuits. One gives a regulated +22V rail and an unregulated +29V rail, the other regulated -18V and +6V rails (set R422 for -18V).

The h.t. supply is straightforward, consisting of a half-wave rectifier with a choke filter.

Tuners

There are separate u.h.f. and v.h.f. tuners mounted at the back of the chassis. The latter is for continental 625-line transmissions on Bands I and III, but is useful in this country for operation on v.h.f. relay systems. The set is also unusual in having a solenoid operated mechanical band-switch for Band I/Band III in contrast to the usual switching diodes.

The IF Strip

The i.f. strip is built into a plug-in, screened module and among the five active devices three are dual-gate MOSFETS, no doubt used because of the advantages of low cross modulation and the easy design of the a.g.c. circuitry. There are three separate video detectors in the i.f. module. One (D1) is for the luminance and chrominance, another (D51) detects the 6MHz sound intercarrier beat, while the third (D220) detects the video signal for the noise-blanking, a.g.c., and sync. separator stages. This detector is fed from a point before the second 33.5MHz trap in order to produce the wide bandwidth video signal necessary for effective noise blanking.

Access

Access to the main chassis at first sight looks to be a problem - apart from the plug-in modules - but the whole

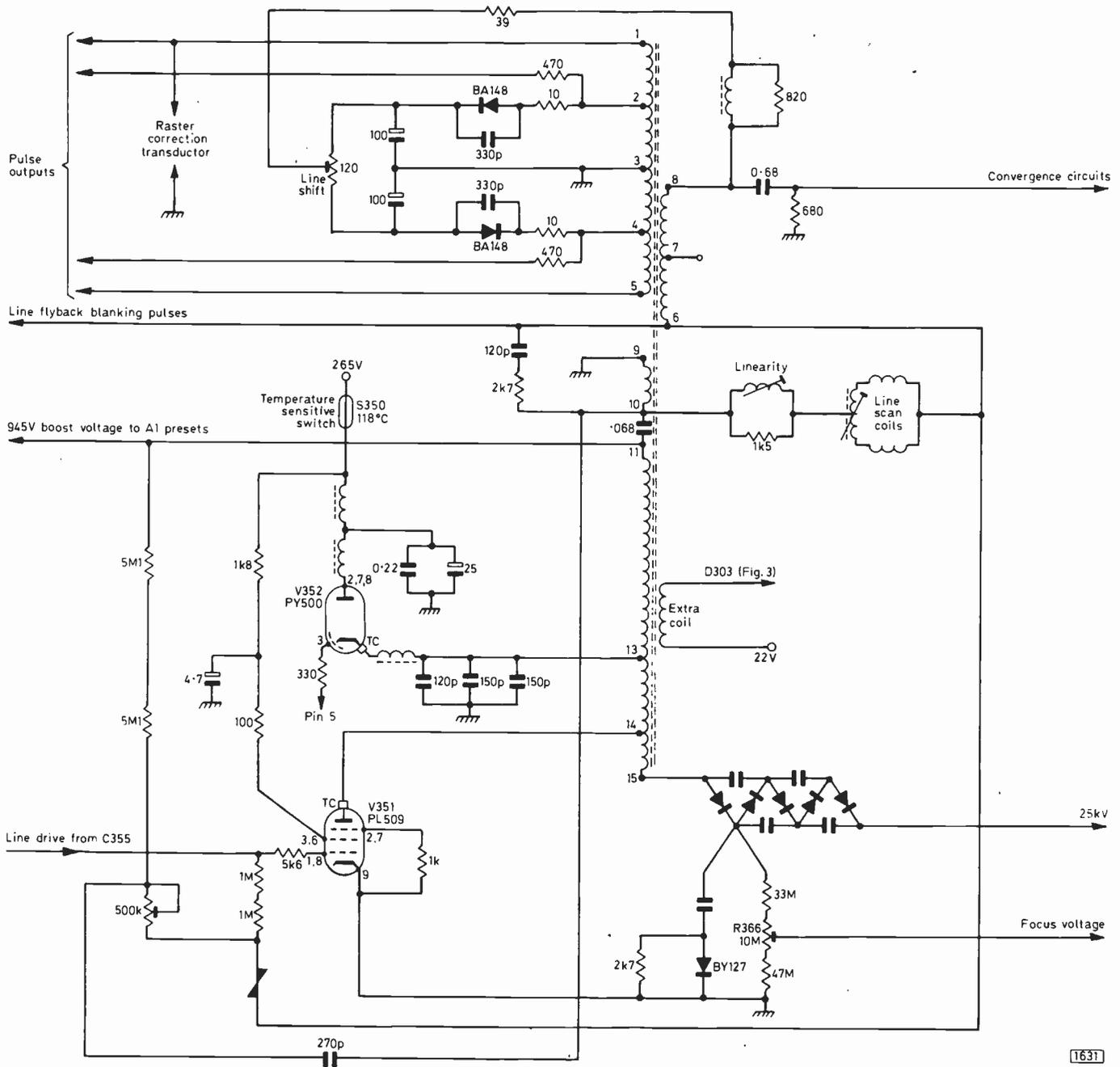


Fig. 1: Circuit of the line output stage. EW raster correction is carried out in the line oscillator circuit.

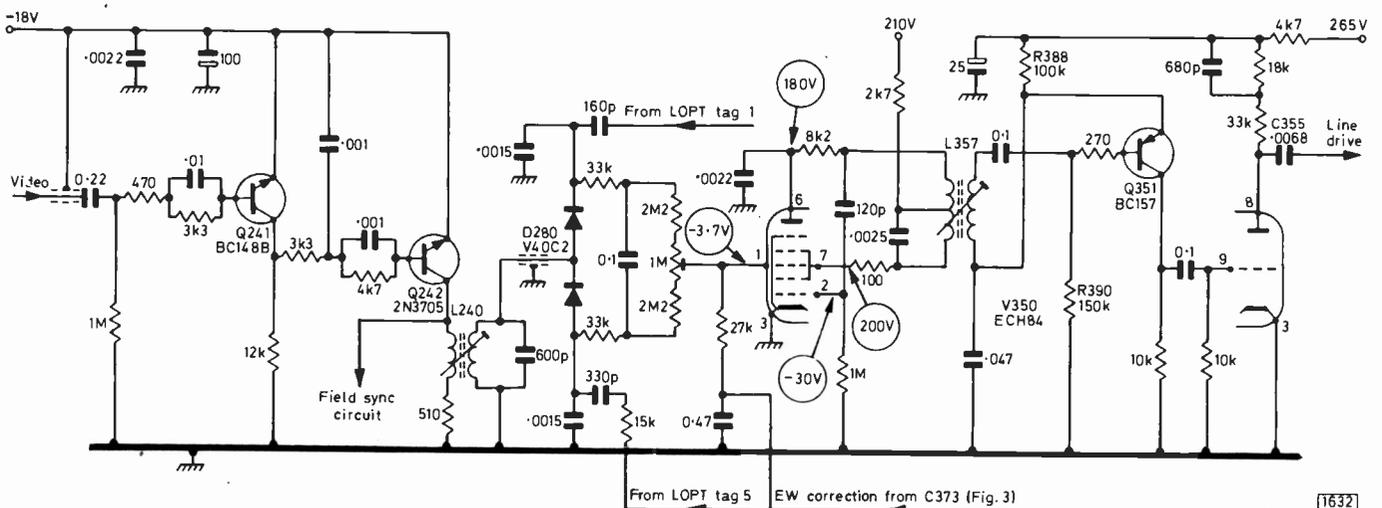


Fig. 2: The sync separator and line generator circuits. In some sets the ECH84 acts as oscillator and reactance valve, with Q351 omitted.

chassis is mounted on rails and can be slid backwards for service after two springs have been released. Access to the underside of the chassis is obtained by releasing the same two springs and pulling the chassis back farther and lifting it – it's hinged at the front – until the top of the line output chassis engages a hook at the top of the cabinet, holding it at a convenient 45°. When new, the sets were fitted with a peg on each side of the chassis secured by screws holding the chassis to the rails. This was a transit precaution. If the chassis is reluctant to slide backwards however these may still be in place.

The control panel, which also carries the audio amplifier and output stages, can be taken out as a unit by moving out of the way the three clips which hold it in place.

Stock Faults

These receivers seem to be inherently reliable but are let down by a number of stock faults which are soon recognised, making for easy servicing but doing nothing for customer satisfaction.

LT Troubles

The l.t. power supplies seem to be one of these "weak links" on the chassis. The usual trouble is that the l.t. supply goes on and off intermittently, sometimes for only a few seconds in an hour. This is usually due to a faulty 2N5296 regulator output transistor, but the BC147s which drive them are not always without blame, so it's a good policy to change both the BC147s and the 2N5296 when a fault like this occurs.

It's easy to identify which of the two l.t. regulators is causing trouble. Failure of either gives the no sound or vision symptoms whilst failure of the 22V regulator gives field collapse as well. So if the symptoms are no sound or picture with a blank raster transistors Q404, Q405 and Q406 are suspect, but if no sound or picture with field collapse go for Q401, Q402 and Q403.

Field Collapse

Field collapse by itself, again at times intermittent, is usually the 2N5496 field output transistor Q305 or occasionally the field oscillator Q301, a BR101. If the correct replacement for the field output transistor is not to hand a 2N3055 can be fitted in an emergency since the heatsink and printed board are drilled to take its TO3 case as well as the 2N5496.

Line Timebase Faults

The usual indication of trouble in the line output stage is the opening of the temperature sensitive switch between the two valves. Replacement of the valves and resetting the switch with the alloy provided is usually a permanent cure. On some occasions the switch seems to open for no good reason, probably due to higher than normal ambient temperature, high mains voltage etc., as the melting point of the alloy is only 118°C. The temptation to reset the switch with ordinary solder (with a melting point of 220°C) should be resisted: this would not melt until the worst possible fault conditions occurred, and could be the cause of severe damage or even a fire.

Other possible causes of no e.h.t. are the tripler – easily diagnosed by disconnection – or a line oscillator which is

reluctant to start. If the condition is not cured by a new ECH84 valve and the circuit is of the later type with a transistor oscillator the cause of the trouble may well be R388 or R390 being high in value.

In my own experience at least this chassis seems to suffer more than the average from arcing around the inter-connecting leads from the line output stage valves to the line output transformer, and the connections from the line output transformer to the printed circuit board. In the odd case this has even damaged the line output board beyond repair.

The moral of this is that when changing line output stage valves or working on the line output stage one should check that any leads carrying line power run clear of each other and of nearby components, and also watch out for dry-joints and loose connections. By doing this you may save the customer the cost of a new line output panel.

Focus trouble is nearly always the 10MΩ control, but in some cases the spark gap goes leaky in spite of the fact that a high quality glass encapsulated unit is used. When replacing the gap install it with some clearance between it and the c.r.t. base panel in order to prevent leakage due to dirt trapped between the two.

Intermittent Sound

A common and annoying fault which seems to occur sooner or later on most TV sets using this chassis is intermittent sound. In a few cases this is because the sound output transistor Q74, a 2N3055, is faulty, but in the majority of cases the source of this trouble is dry-joints on the emitter and base pins of this transistor and on its securing screws which also serve as the collector connections. The cure is to resolder the joints with a generous dose of solder, taking care that there is no strain on the soldered joints.

Tuning Troubles

Troubles with the tuner seem to be similar to those experienced in other TV receivers with varicap tuners – noisy switch contacts, tuning potentiometers and the like. Remedies are cleaning plus a dash of contact lubricant or replacement, depending on the severity of the case. After several years the most commonly used buttons refuse to work or become intermittent, operating only if the button is held in as far as possible. The cause is wear on the part of the push button which operates the bandswitch – this is located on the top of the push button assembly – and a quick cure is to slacken the screw holding the switch and to move the switch to take up the wear, finally retightening the screw. A more permanent cure where the receiver is used on u.h.f. only is to rewire the switch so that the u.h.f. tuner is permanently in operation.

IF Unit

The i.f. strip is a reliable unit. Since it's a plug-in module it can easily be returned to the manufacturer for service should the thought of working with MOSFETS prove daunting.

Colour Circuits

The decoder and the RGB drive circuits have proved trouble free, with nothing of the nature of a stock fault. It's

Picture Sharpener for the Philips VCR

John de Rivaz, B.Sc.(Eng.)

THE writer discovered that the circuit to be described had been added to a second-hand VCR he purchased. Its function is to increase the horizontal resolution of replayed material. It has no function in the record mode. The circuit is shown in Fig. 1, with waveforms in Fig. 2 to assist with the theoretical description – they are not sketches of actual oscillograms.

Circuit Description

The new circuit board is driven by the luminance emitter-follower TS429 on board B (panel 45). This has a 1kΩ emitter load resistor. Tr1 is also an emitter-follower, and drives the d.c. restorer D1 to set the d.c. level of the video to the correct point to bias Tr2.

The signal from Tr2's emitter is directly coupled to Tr3's base. Tr3, together with the choke in its collector lead, form the picture sharpener. The choke, together with stray capacitance, comprise a highly damped tuned circuit which is shock-excited by a step input waveform. D2 and D3 clip the top and bottom of the output. This has the effect of removing the subsequent oscillations of the damped tuned

coaxial cable coming from board B was unsoldered at point 622 on board C. This is coded "B281" on the circuit diagram for the machine. A further length of screened cable was soldered to the lead from board B and connected to the input of the new board, and a length of screened cable was connected from the new board to board C. A separate earth had been provided from the earthing point on the new board to the earthing point on board C, and the 12V required was taken from point 628 on board C (coded "B241" on the circuit).

Installation

After installation the 1kΩ potentiometer is adjusted so that the picture is sharper without any extra interference becoming apparent.

Scope for Experiments

The choke used is marked with the word "Cambion". There is room for experiment with the natural frequency

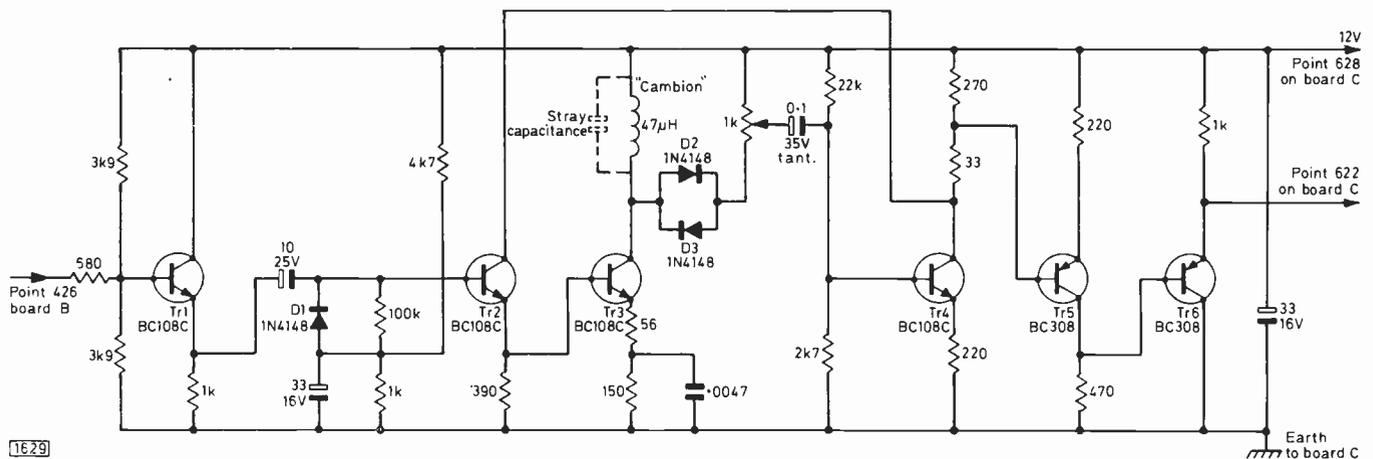


Fig. 1: Circuit diagram of the picture sharpener.

circuit and also any amplified noise that may appear there. The effect is to leave just the peaks and in practice the remaining ripple does not show on the resulting picture. The pulse produced in this way is further amplified by Tr4 and is mixed with the original signal in the resistors common to Tr2 and Tr4. Tr5 inverts the processed signal and corrects its level to that required by the overall VCR system, and Tr6 presents the correct output impedance to drive the luminance delay line on board C.

Construction

The circuit had been constructed on a piece of veroboard and fitted to the VCR at the front, perpendicular to board C. It was fixed to the hinged frame by two soldering tags. Connections were made to board C as shown in Fig. 1. The

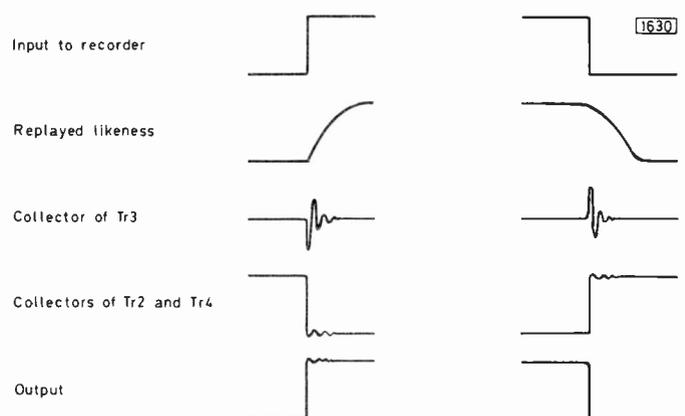


Fig. 2: Theoretical waveforms showing the sharpening action.

and damping factor of the choke to get optimum results. Also there is the possibility of building much more complex circuits to enhance the picture sharpness, using integrated circuit logic. Even some way of "flagging" sharp edges in the recording process could selectively activate a pulse generator on replay to give a much larger effective bandwidth. It's felt however that the modification shown gives a visible improvement in replay quality and is worth adopting. Some later models incorporate circuitry to improve picture quality. A device called the "Video Quality Recoverer" is marketed by Scientronics (40, High Street, Somersham, Huntingdon, Cambridge) at £10. This is probably similar, although I have not seen one.

Modulator Fault

Finally, a VCR fault that I encountered recently. There was no output from the VCR to the receiver, although a

picture was available at the monitor and sound was available at the receiver. Naturally the machine was tried with both a tape and an off-air signal, and the fault was the same in each case. This suggested a fault in the U505 modulator module, and probing with an oscilloscope soon revealed that the video was entering the module with the correct d.c. level at point P. By this time thought was being given to the possible cost and the delivery time required to get a replacement U505 module, but I decided to open it up in case IC401 was the cause of the trouble and was a type that could be readily replaced. The signal is fed to pin 2 of the i.c. through a 3pF feedthrough capacitor, a 100Ω resistor and a small choke. This consists of a few turns of self-supported "solderable" enamel covered wire. It was clear that one end of the choke was dry-jointed, and application of the soldering iron completely cleared the fault. Incidentally it would not have been possible to replace IC401 – it's an obscure flat-pack type, and had the fault been within it the whole module would have had to go. ■

More on the CVC20 Chassis

Dewi James visits ITT's Kersley plant

THE development of the new ITT CVC20 chassis, with its PIL tube, was described in *Television* last December. It's currently in production in at least a couple of ITT plants in the UK, and I recently visited the one at Kersley, Lancashire – originally built by Telefusion for the production of their Telpro colour sets. ITT aim to make the CVC20 the UK's most reliable colour TV chassis, and I was impressed by the care taken in its design and construction and the quality control exercised at all stages in its manufacture. Nevertheless there were a few initial problems, as with any new chassis: these are listed later.

Another aim of ITT is to strengthen the links between the manufacturing and servicing sides. One aspect of this will be regular training courses for dealers' engineers. During my visit I was able to discuss the circuitry and servicing with ITT's engineers, but the most useful result – to a practising TV engineer – was the information obtained on faults encountered with early production sets. For the benefit of others, these are as follows.

Early Troubles

The switch-mode power supply transistor T12 (BU126) sometimes goes short-circuit at switch on for no apparent reason, although this fault can also be caused by R80 (150kΩ) in the base circuit of the driver transistor T11 going open-circuit.

A peculiar symptom best described as a "pulsating field collapse" is usually caused by either the field linearity stage transistor T6 (BC183LC) or diode D5 (1N4148) between the field charging network and the field oscillator. Complete field collapse has been caused by failure of diode D5A (1N4148) in the coupling network between the TBA920 i.c. and the field oscillator, while reduced field scan can be due to a dry-joint at the junction of L7A (NS phase coil) and L3 (one of the NS raster correction transductor windings).

In the line timebase there were some early tripler failures but the more usual faults have been due to the diodes in the EW modulator circuit. When D24 (BYX71/350) – the one

with its anode connected to chassis – goes short-circuit the effect is excessive width; when the other diode D23 (MR854) goes short-circuit the effect is lack of width. Another cause of excessive width is when the EW modulator driver transistor T903 (BC213L) goes short-circuit – when it goes open-circuit the effect is lack of width.

Very weak contrast has been due to defective transistors in the beam limiter circuit. These are T1 (BC172B) and T2 (BC252B). Similar symptoms can be caused by the associated diode D3 (1N4148).

Should the chroma disappear during channel change, leaving vague green/white bars, fit a 150pF capacitor between pins 14 and 16 of the TCA800 chroma demodulator/PAL switch/RGB matrix i.c. IC503 to prevent instability.

If the electrolytic C39 (22μF, 400V) associated with rectifier D14 goes short-circuit it blows the plug fuse (if there is one) but not the set's fuses. This supply feeds the base of the driver transistor in the switched-mode power supply.

Finally, for the sake of completeness, we add the point made recently in *Your Problems Solved* (April) – intermittent colour drop-out due to dry-joints on the print side of the decoder panel, particularly at the transverse screening strut which runs across the print adjacent to the service switch S501/2.

New Reliability

ITT comment that the initial bugs on the chassis have now been ironed out, and we wish them every success in their quest for reliability.

20AX Screen Burn

Incidentally, it has been found during production of the newer CVC30 chassis, which uses the 20AX c.r.t., that this tube is susceptible to screen burn if the set is left in the field collapse condition for even a very short time. So beware. ■

Test Report

Eagle Transistor Testers

Vivian Capel

SOME sort of transistor tester is nowadays a must for the service department. A variety of such instruments is available and the types on offer fall into three classes: those that analyse the various characteristics of the transistor in detail, enabling curves to be plotted; testers which provide basic leakage and gain measurements; and the in-circuit go/no go tester. The first of these is really an instrument for the design laboratory and is not necessary for service work. There are examples of both the other types in the Eagle range, the TT145 and the TT144 respectively.

Model TT145

The TT145 is a basic characteristic meter. It has a 2½ in. meter scale which is calibrated for gain and leakage current. Both the alpha and beta modes are indicated on the gain scale. Alpha, the common-base configuration where the gain is less than unity, is calibrated from 0.7 to 0.9967. Beta, or to use the more common term h_{FE} , is calibrated from 0-300 but is easily extended to give readings up to 600 for high-gain transistors.

There are two leakage current ranges, one up to 50 μ A for small transistors and the other up to 1 mA for power types. There is also a resistance range for checking diodes — this reads up to 1 M Ω . In spite of these five different calibrations the scale is uncluttered and very easy to read.

The main control is a three-position switch selecting either npn or pnp tests with a centre-off position. It's also inscribed "forward" and "reverse" for diode testing. Selection of the gain or leakage tests is by means of a press key which is biased to a centre-off position. There's a selector knob for switching to general or high-power transistors or meter adjustment. Alongside is the potentiometer for adjusting the meter.

A pair of terminals is provided for diode connection. They're inscribed with the diode symbol. There are two methods of transistor connection, by three short colour-coded leads terminated by crocodile clips, or by means of a four-in-line transistor socket. I had some doubts as to whether the latter would stand up to continual workshop use in view of the small contact area. It has done so over many months without any sign of trouble however. The crocodile clips are rather less successful, being somewhat large and not inclined to make a firm grip on the transistor lead-out wires. It seems that these are really intended for the larger power transistors and that wire-ended transistors should be fitted to the socket.

Test Procedure

The test procedure is as follows. After connecting the transistor and switching to the correct polarity, the selector is set to the adjust position and the potentiometer adjusted to give a full-scale reading. The selector is then switched to

"general" and the test key pulled back. The gain can be read off directly on the scale. If the needle goes beyond the limit the gain is above 300 and the meter must be readjusted, this time to give a half-scale reading instead of a full one. This doubles the gain range to 600. Pushing the test key forward gives the leakage reading, of up to 50 μ A. If the scale is exceeded when testing power types switch the selector to "high-power". This extends the range to 1 mA.

For diode testing, the diode is connected as indicated to the terminals. The control is then switched from forward to reverse. Resistance is indicated on the scale in ohms and the forward reading should be much lower than the reverse one. If you are unsure of the diode polarity connect it at random: the forward and reverse readings will indicate whether it is connected correctly or is reversed.

Conclusions

This instrument has been used in the workshop for a considerable time and has always given positive, unambiguous readings. It has showed up many a suspected faulty transistor when a replacement has not been available to try in circuit. One is always happier ordering an expensive transistor of an uncommon type if one is *sure* that the original is faulty!


Model TT144

Now to the TT144. This is quite an ingenious device which tests transistors dynamically, that is under signal conditions and not just with d.c. currents flowing. Furthermore it does this without the need to remove the transistor from its circuit. Obviously if this is 100% reliable and successful it will be a boon to the busy service engineer.

The tester incorporates an oscillatory circuit which operates independently of the circuit into which the transistor under test is wired and its power supply. This circuit consists of a transformer which couples the base and collector of the transistor. An additional high-ratio winding supplies a neon lamp, thus giving an indication as to whether the circuit is oscillating.

The main control on this instrument is a potentiometer which varies both the feedback and the base bias. When the feedback and bias are at maximum a good transistor should oscillate strongly and light the neon. This it does when the control, which is arbitrarily calibrated from 0-100, is fully anti-clockwise, i.e. at the 0 marking. As the control is turned clockwise the feedback and bias are reduced and the neon fades until it goes out. The control's position at this point gives an indication of the dynamic gain and enables transistors to be dynamically matched. Any transistor fault, such as a short or open-circuit or high leakage, will prevent oscillation. "Goodness" is determined by just one test therefore.

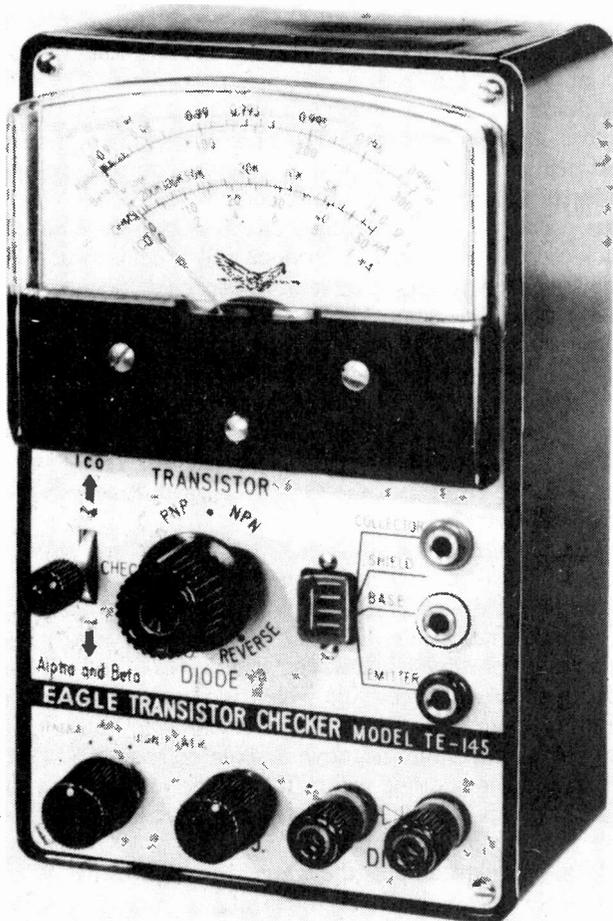If more accurate matching is required the neon can be



The Eagle Model TT145 transistor tester.

disconnected by means of a switch on the control panel. This eliminates its loading on the circuit, and a measurement of the oscillation amplitude can then be made by means of a scope or valve voltmeter – output sockets are provided for the connection of such an instrument. The only other control is the on/off and polarity selector switch. As the internal battery is only 1.5V and current is limited by the transformer primary no damage will be done if the wrong polarity is selected. A transistor of unknown polarity can be identified by switching from one polarity to the other to see which gives an indication.

Two sockets are provided for transistor connection, one a small triangular configuration for taking lockfit as well as wire-ended transistors, and the other a much larger one with a tapered moulding to guide the wires easily into their holders. This however prevents transistors with short wires being used with it. Three leads with crocodile clips are provided for in-circuit tests. These medium-sized clips are much too big for the cramped layouts of most printed boards encountered these days. They can be replaced by miniature instrument-type clips however and these are certainly more suitable.

Performance

How does the instrument perform? In most cases quite well. An indication is not always obtainable from the neon when testing sound output transistors in situ, but the oscillation produces a buzz from the loudspeaker. Most audio stages gave results, but it is in the i.f. circuits, both sound and vision, as well as radio i.f. and mixer stages that results were more uncertain. This is probably due to the

low-impedance paths presented by the i.f. coils – these shunt the i.f. oscillation and prevent it from getting going.


If no indication is forthcoming the handbook recommends disconnecting the emitter lead of the transistor from the circuit and connecting it directly to the tester. In the case of low-current transistors additional battery cells can be tried in series with the collector.

It was found that the neon would sometimes not light in the maximum position of the feedback/base bias control but at some other point. So if the neon doesn't light at first the control should be rotated slowly over its range. Why there should be no oscillations at the maximum bias and feedback settings while oscillations start at a lower level is obscure but may well be due to some peculiarity in the transistor characteristic.

Verdict

It can be seen that there is an element of uncertainty about in-circuit testing. If the neon lights, fair enough, we know we have an operational transistor. But if the neon doesn't light it could be because the transistor is faulty, or there are low-impedance circuit shunts, or the emitter needs isolating, or extra battery cells are required, or the control needs adjusting to find a favourable point! All this rather nullifies the advantage of in-circuit testing. Unless a piece of test equipment gives positive results it's of little value in a professional workshop. So ingenious though the TT145 is, I find myself going to the TT145 every time I have doubts about a transistor even though this means removing it from the circuit. The cost of the TT145 is £22.50 and of the TT144 £11.90, plus VAT. ■

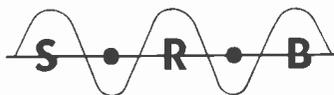18 watts of power at 240 v. straight to the bit



MINIATURE SOLDERING IRON

Probably the smallest 18 watt soldering iron to comply with Consumer Protection Regulations BS No. 3456 2/14.

The **S-R-B** has a new method of bit-securing (pat. pending) and a built-in suspension hook. All parts are very easily replaced.

Insulation tested at 1500 V. ac at maximum temperature.


BIT SIZES:

19 (1.5 mm)	20 (3.0 mm)
21 (4.5 mm)	22 (6.0 mm)

(Bit type 20 fitted as standard)

S. & R. BREWSTER Ltd
86-88 UNION ST · PLYMOUTH Tel 0752-65011

Manufacturers and Distributors

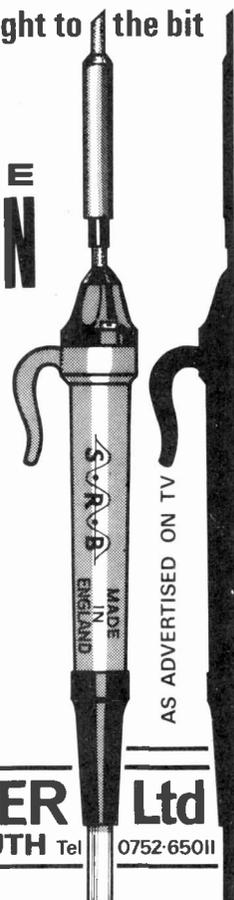


Circuit Notes

H. K. HILLS

Magic Green Line Tuning

We have received several letters from readers asking about the "magic green tuning line" featured in National Panasonic (Matsushita) colour receivers. On pressing a button a vertical green line appears down the centre of the screen. The set is then tuned for minimum width of the green line, this condition corresponding to correct tuning. The way in which the circuitry is arranged differs in different models, but the basic principle remains the same. We will take as our example the portable Model TC42G.

The idea is shown in block diagram form in Fig. 1, while Fig. 2 shows the circuit in simplified form. Basically, a sample of the signal appearing at the final i.f. stage is applied to an amplifier tuned to the vision carrier frequency (39.5MHz). This stage will obviously provide maximum output when the vision carrier is at maximum, i.e. the tuning is correct. This output is detected and fed to an i.c. to which a line frequency sawtooth signal is also fed. When the supplies to these stages are connected by pressing the green line tuning button, this i.c. produces an output pulse which is timed to coincide with the centre of the line scan. Its width depends on the input from the detector. The pulse is used to saturate the R-Y output stage and to cut off the G-Y output stage.

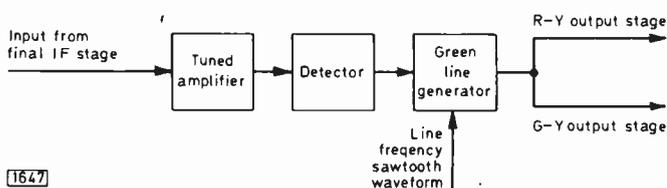

1647

Fig. 1: Block diagram showing the principle of the National Panasonic "magic green line" tuning system.


Turning now to Fig. 2, the signal at the collector of the final i.f. transistor is coupled by the small (1pF) capacitor C154 to the base of the 39.5MHz tuned amplifier Tr151. Power is applied to this stage and sections of the following i.c. only when the "magic line switch" is closed. The detector diode D151 is arranged to give a negative-going output across its load resistor R158. This is smoothed by C157 and reduces the small positive voltage tapped from the slider of the magic line width control R155. The voltage thus produced is fed to pins 5 and 6 of the i.c. A line fly-back pulse is integrated to produce a 30V peak-to-peak line frequency sawtooth waveform whose peak occurs at the centre of the line scan. This is fed in at pin 13 of the i.c., its exact position being determined by the setting of R170. The i.c. produces a rectangular pulse of 4V peak-to-peak amplitude at pin 3, the width of the pulse depending on the voltage at pin 5. This pulse is fed via D901 to the base of the R-Y colour-difference output transistor Tr901 and via D902 to the emitter of the G-Y colour-difference output transistor Tr902.

The set uses colour-difference c.r.t. drive, and since the output transistors are npn types the positive-going pulse from the i.c. drives Tr901 fully on while cutting Tr902 off. In consequence while the pulse is present the tube's green grid moves positively and its red grid moves negatively, producing a vertical green line which is superimposed on the picture. Optimum tuning gives maximum output from Tr151 and maximum negative d.c. output from D151, with a minimum magic line width. If the received signal is such that the line is completely killed, it can be restored to a suitable width by adjusting R155.

In subsequent models the whole operation is carried out in a single i.c. which also provides a.f.c.

Switched Subcarrier Trap

An unusual circuit in the TC42G is the method used to render the 4.43MHz trap in the luminance channel inoperative on monochrome, so that the full video bandwidth is used. Associated with the trap (see Fig. 3) are a diode (D303) and a pair of transistors which are connected in the basic differential-amplifier configuration though actually operating as a switch. The control voltage is derived from the colour-killer circuit in the chroma i.c. Pin 4 of this i.c. is at 12V on monochrome. In consequence Tr305 is turned hard on and the voltage developed across R375 cuts Tr304 off. With Tr304 cut off, no current can flow through D303 which consequently acts as an open-circuit switch. The

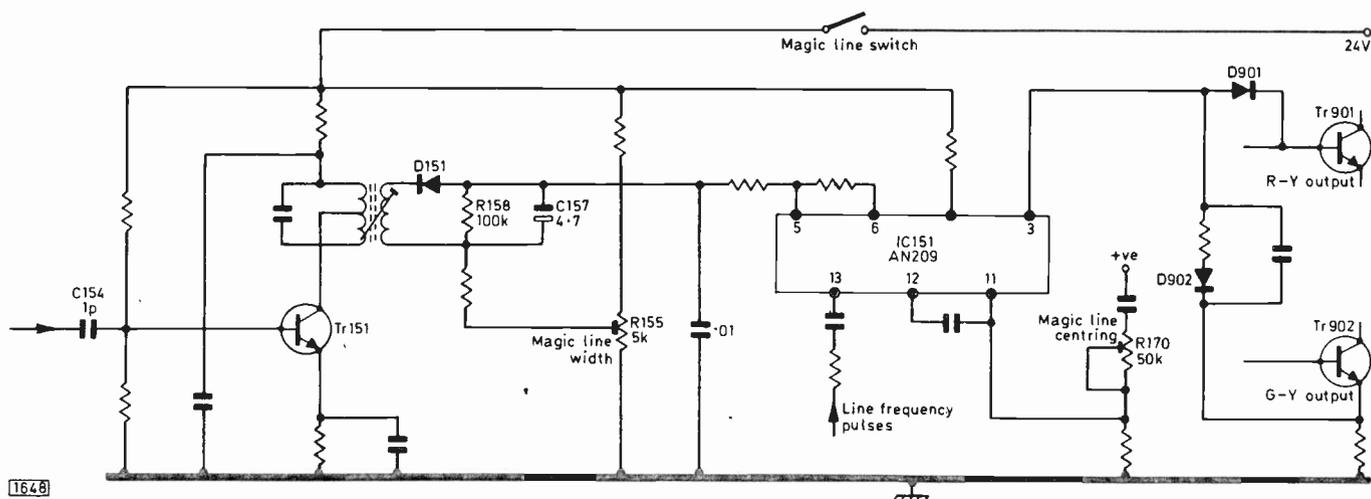

1648

Fig. 2: Simplified circuit of the "magic green line" tuning system used in Model TC42G.

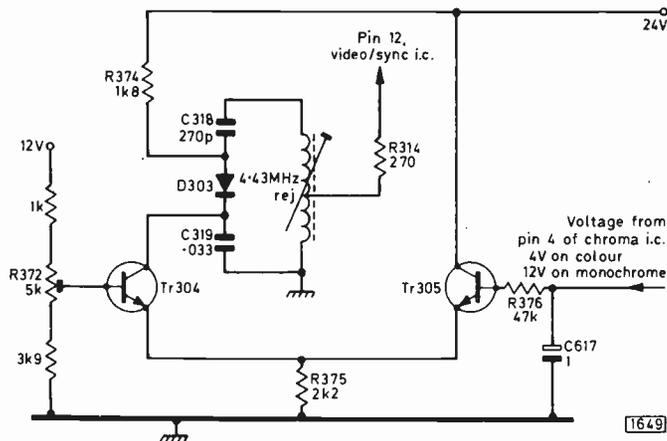


Fig. 3: The unusual switched 4.43MHz subcarrier trap used in the National Panasonic Model TC42G.

result is that C318 can no longer tune the associated 4.43MHz rejector coil. On colour the voltage at pin 4 of the chroma i.c. falls to 4V. In this condition Tr305 no longer conducts. The bias applied to the base of Tr304 from R372 switches it on, and the voltage across R375 this time holds Tr305 cut off. D303 is now conducting, and the 4.43MHz rejector circuit comes into operation.

Electronic Smoothing Filter

The smoothing arrangement following the h.t. rectifier is conventionally an LC or RC filter. Chokes are bulky and expensive however and their magnetic fields impose mounting restrictions; resistors on the other hand dissipate considerable wattage. An alternative approach used in several W. German chassis is to use an electronic filter. That used in the Nordmende FIV chassis is shown in Fig. 4. At switch on C557 charges rapidly via the zener diode D559 and R558, the voltage across the zener bringing the two transistors T505 and T506 into conduction. Once C557 has fully charged there is insufficient voltage across D559 for it to maintain conduction. It switches off therefore. T505 is now biased by the voltage at the junction of R556/R557, smoothed by C557. As a result the emitter current of T505 is highly smoothed and by further emitter-follower action T506 provides a highly smoothed output. The input from the thyristor regulated power supply has a 15V peak-to-peak ripple content. The output of the electronic filter has a hum voltage of approximately 300mV peak-to-peak. R539 provides current limiting in the event of an h.t. short-circuit, while D560 protects T506 by conducting and operating the protection circuit in the event of T506's reverse collector-emitter voltage being exceeded.

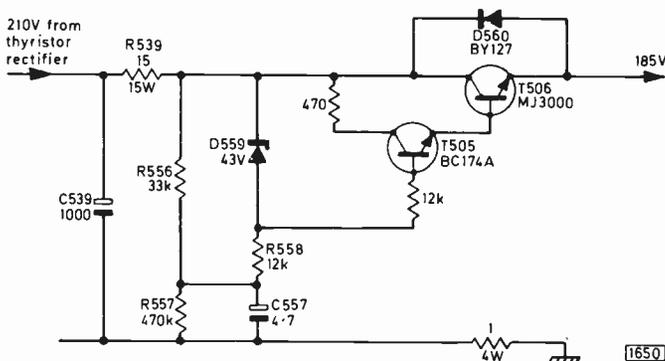


Fig. 4: The electronic smoothing filter used in the Nordmende FIV chassis.

Noise-free Field Sync Pulse Feed

Noise pulses occurring towards the end of the vertical scan can often trip the field timebase. A simple method of removing the effect of such noise is used in Decca hybrid colour receivers and also in the earlier Baird 620/640/660 series of monochrome receivers. The circuit as used in the Decca 10/30 series chassis is shown in Fig. 5. D400 is held conductive during the forward scan, thus clamping to

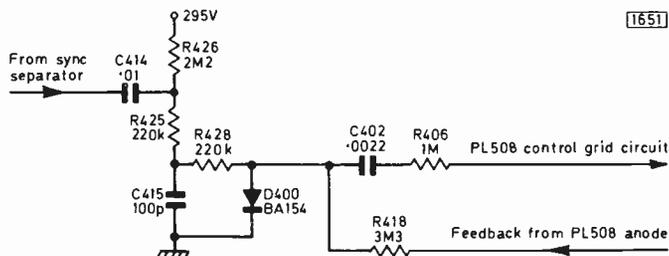


Fig. 5: Field sync pulse integrating/feed circuit used in the Decca series 10 and 30 colour chassis.

chassis the sync pulse feed to the field timebase. The field sync pulses are integrated by R425 and C415, reverse biasing D400 and passing via C402 and R406 to the control grid of the PL508 field output pentode to cut it off and thus initiate the field flyback. In the absence of the field sync pulse D400 is held forward biased by the voltage from R426/R425/R428 and in addition by the field scan waveform applied to its anode via R418. This waveform is taken from the PL508's anode circuit.

Transductor EHT Stabiliser

An unusual feature of many Hitachi colour receivers is the use of a transductor to stabilise the operation of the line output stage and thus the e.h.t. The circuit, simplified, as used in Model CNP192 is shown in Fig. 6. The transductor has three windings, two of which are connected in series

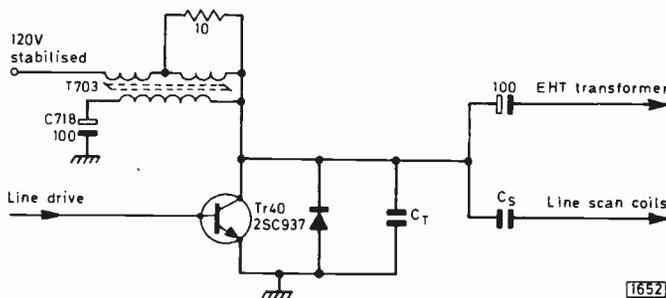


Fig. 6: Simplified circuit showing the use of a transductor in many Hitachi colour receivers to stabilise the e.h.t. voltage.

with the supply to collector of the line output transistor while the third, the control winding, is connected between the collector of the line output transistor and chassis via the d.c. blocking capacitor C718. Now the reactance presented by the series windings on the transductor depends on the a.c. flowing through the control winding. As this current increases, so the core increasingly saturates and the impedance presented by the series windings decreases. With increased demand on the line output stage, due to increased beam current, so the loading effect of the transductor decreases. The net loading on the line output stage thus remains substantially constant, and the e.h.t. voltage is stabilised. Since the transductor's dissipation is low the circuit is reliable.

Servicing the Rank A774 Monochrome Chassis

John Coombes

THE Rank A774 single-standard monochrome chassis was introduced in 1970 and remained in production for many years. Models using it include the Bush TV181S, TV183SS, TV185S, TV186SS, TV313 and TV315, and the Murphy V2015SS, V2016, V2415SS and V2417S. It's a hybrid chassis, using valves in the audio section and the field and line timebases, and transistors elsewhere. One distinguishing feature is the use of an EF184 as sinewave line oscillator. Many of the troubles relate to dry-joints and to capacitors in the line timebase. The latter part of the chassis is a good point at which to start off therefore. See Fig. 2 for the complete circuit of the main chassis.

Lack of Width

A common fault is lack of width. If a new PL504 line output valve doesn't restore full width check the line stabilisation control 3RV8 (2M Ω), which can also be responsible for intermittent lack of width or loss of raster altogether. If a new c.r.t. has been fitted, lack of width can be due to a faulty line linearity sleeve – it's under the deflection coils. If the sleeve is incorrectly positioned there will be cramping at one side of the screen. The adjustment simply consists of sliding the sleeve along the tube neck beneath the scan coils. Other causes of lack of width are a short-circuit scan-correction capacitor (3C49, 0.1 μ F) and the line output transformer 3T2. If necessary, check the high-value resistors in the line stabilisation/width circuit – 3R58 etc. If the line output transformer is responsible for the lack of width the line stabilisation control will have no effect, the picture will take a long time to appear and unless the brightness is turned well down the picture will balloon and disappear.

No EHT

No e.h.t. means no raster – and usually no sound signals either since the 20V supply for the transistor stages is obtained from the line output stage. The rectifier which provides the 20V supply is 3D8, with filtering by 3C45/3R69/3C48. If this rectifier is defective it can kill the line output stage. This however is not one of the more common causes of no e.h.t.

If a new PL504 doesn't restore the e.h.t. and the valve is running cool check its screen grid feed resistor 3R56 which sometimes goes open-circuit. Alternatively, the associated decoupler 3C37 may be short-circuit. This in fact may be the reason for 3R56 being open-circuit, so if 3R56 has to be replaced check 3C37 as well.

No e.h.t. and an overheated PY88 boost diode probably means that the boost capacitor 3C44 is short-circuit. All too often however loss of e.h.t. is due to the line output transformer. Very often there is a visual sign – a burn up through the e.h.t. overwinding lead, with insulation breakdown to the transformer's core.

On a few occasions I've come across loss of e.h.t. due to 3L6 being open-circuit. This coil is on the line output

transformer and feeds the top cap of the PY88. On another occasion the cause of no e.h.t. was traced to shorting turns on the scan coils. This was the only time I've had trouble with the deflection coils.

No e.h.t. and the PL504 line output valve glowing a very bright red probably means no drive from the EF184 line oscillator. A quick check is to see whether there is a negative voltage of about 25-35V at the control grid (pin 1) of the line output valve. If this voltage is absent the most obvious move is to replace the EF184. If this fails to cure the PL504's overheating check the tuning capacitor (3C32, 4700pF) in the line oscillator circuit: it tends to go leaky. If the PL504 is overheating but not too badly the line oscillator may be operating at the wrong frequency. The main suspects here are 3C32 and 3C34: check by substitution. Other causes of no drive to the PL504 are a faulty coupling capacitor (3C39, 0.01 μ F), the line oscillator's anode load resistor (3R55, 56k Ω) being open-circuit, and the line oscillator's supply decoupling electrolytic 3C31 (10 μ F) being short-circuit. As already mentioned, make sure that 3RV8 is operating correctly.

Sound but no e.h.t. is the symptom when the DY802 e.h.t. rectifier's heater winding shorts to the frame of the line output transformer.

Line Sync Problems

Loss of line sync is a frequent problem on this chassis and the most common cause is one or both of the flywheel sync discriminator diodes 3D6/3D7 going open-circuit – it is rare to find one short-circuit. Note that 3C60 across the c.r.t. heater was not present on early production sets. It was added to protect the flywheel sync discriminator diodes in the event of c.r.t. flashover. Another cause of loss of line sync is 3C29.

There is a fault which occurs quite often and is very misleading to anyone not familiar with this chassis. The customer might say that when the set is switched on the

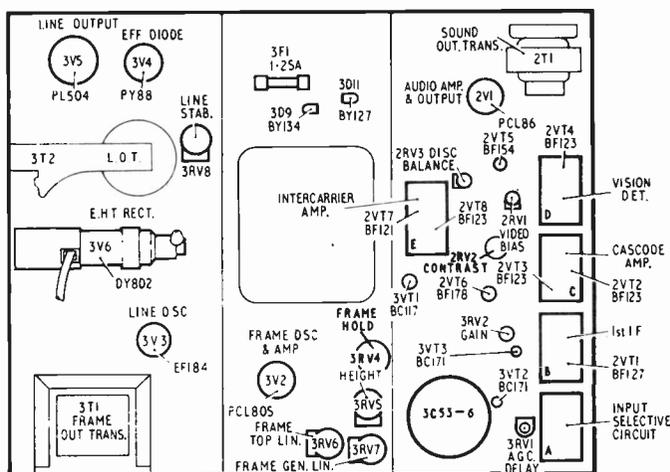


Fig. 1: Chassis layout, viewed from the front.

picture breaks up. If you haven't seen this you may make the mistake of thinking that there is a component failure. The fault may in a poor signal area be described as bad ghosting which occurs periodically. The trouble is due to the bonding around the chassis on the side of the line timebase circuitry. Quite a number of connections here are made to a metal runner around the outside of the line timebase. It has lugs which pass through the printed board and are soldered to the print. It is important to use a large soldering iron to ensure that proper connections are made to the printed board.

Line tearing and intermittent loss of line sync should lead to a check on the flywheel line sync discriminator diodes, the EF184 and 3C31 which can also cause intermittent troubles. Frequency drift is 3C31 again, and line jitter 3C32, 3C34, and 3C36 is also worth trying.

Poor Sync

Quite a common cause of loss of sync, poor sync or even intermittent loss of sync is the sync separator transistor 3VT1 (BC117). 3R3 also causes trouble, giving loss of line and field sync: when it goes open-circuit lock can be achieved for short periods but becomes uncontrollable when the scene changes. The input coupling capacitor to the sync separator transistor, 3C1, was changed from 0.22 μ F to 0.47 μ F in later production to give improved sync separator operation.

Field Timebase Faults

In the field timebase the most common offender is the PCL805 valve. Common complaints due to the PCL805 are: field roll, possibly for the first two-three minutes after the set has been switched on; lack of height; bottom cramping; and field collapse – a horizontal white line across the screen. When dealing with field collapse turn the brightness down in order to prevent a burn mark across the centre of the screen.

A common cause of field collapse is simply the wirewound resistor 3R74 going open-circuit – this resistor supplies the field output stage. An occasional cause of field collapse is 3C11 in the cross-coupling network between the pentode and triode sections of the valve going short-circuit.

If bottom cramping is not due to the valve, check its pentode cathode decoupling electrolytic 3C18 (220 μ F). Also check the bias resistor 3R37 (360 Ω). If it has a charred appearance it may have changed value as a result of overheating.

Lack of height, sometimes intermittent, can be due to the height control 3RV5 which very often has a dirty carbon track. Replacement of this skeleton preset is the best course: cleaning will still necessitate its replacement at a later date for sure.

The same fault, a dirty track, also applies to the top linearity control 3RV6 and the overall linearity control 3RV7. The usual result is intermittent faults such as bottom cramping or the top of the picture flicking in and out of linearity.

A rare fault I've come across on a few occasions is intermittent field bounce. Since it doesn't occur at regular intervals the cause is difficult to trace. In each case changing the thermistor 3TH1 in series with the field coils cured the trouble.

Power Supplies

In the power supply, the mains filter capacitor 3C59

(0.1 μ F) commonly goes short-circuit, blowing the mains fuse (3F1). If the fuse is found blown but no obvious cause can be traced suspect 3C59 of being intermittently faulty.

The most common cause of no supply to the valve and tube heaters is that the dropper resistor 3R72 is open-circuit. This resistor is at the top of the chassis. When the heater protection diode 3D12 goes short-circuit it blows the mains fuse 3F1. A BY127 is a suitable replacement. The heater dropper-diode 3D9 going short-circuit also blows the mains fuse.

The h.t. rectifier is 3D11 and again if this goes short-circuit 3F1 blows. The filter capacitors 3C57 and 3C58 across the heater dropper and h.t. rectifier diodes respectively can also go short-circuit to blow 3F1.

Another cause of 3F1 blowing is the on/off switch which is part of the volume control. It seems to short internally. This can usually be spotted due to a burn spot on the paxolin of the switch.

No results but the heaters alight generally means that 3R77 is open-circuit.

On several occasions I've come across the fault no results due to a break on the printed board – on the board side of the mains input plug P/S3.

Hum on sound can be due to an open-circuit h.t. electrolytic but very often it's just that the main electrolytic can (3C53/4/5/6) is not making proper contact to the solder on the printed board. This dry-joint situation can also cause intermittent rolling or poor line sync, with the picture being upset as the hum bar travels down the screen. Another result is line pulling. These troubles can be quickly detected by pushing the printed board near the electrolytic, thus briefly removing the faults.

Sound Faults

As in the field timebase, the valve is responsible for most troubles in the audio section. The PCL86 can be responsible for distorted sound, sound crackling, intermittent loss of sound and complete loss of sound. It can also be microphonic. Check its bias resistor 2R53 which may have been subjected to overheating.

No sound can also be due to the primary winding of the audio output transformer 2T1 being open-circuit. On a few occasions I have come across an open-circuit loudspeaker. This can usually be repaired because the pig-tail has broken, generally at the external lead connector on the speaker. If the speaker's internal coil has broken however a new speaker will be required. This will also be necessary if the trouble is sound distortion due to the cone rubbing.

Another cause of no sound is simply 3R76 going open-circuit, removing the HT2 supply.

2R47 which supplies the triode section of the valve and the screen grid of the pentode section can also go open-circuit to give the no sound symptom.

The intercarrier sound amplifier consists of the two transistors 2VT7 and 2VT8 in can E. One or other of these can also be faulty, removing the sound, but this is much less likely than the previously listed causes. Another rare cause of no sound is the sound detector diodes 2D2 and 2D3 in can E. Weak distorted sound can be due to 2C42 becoming ineffective.

A common complaint is hum on sound. The usual cause is the HT2 smoothing electrolytic 3C54 which is in the multi-section can. The whole can should be replaced. Check the connections first however in case the trouble is due to a dry-joint.

A modification in the sound output stage was the deletion of the output pentode's cathode decoupling


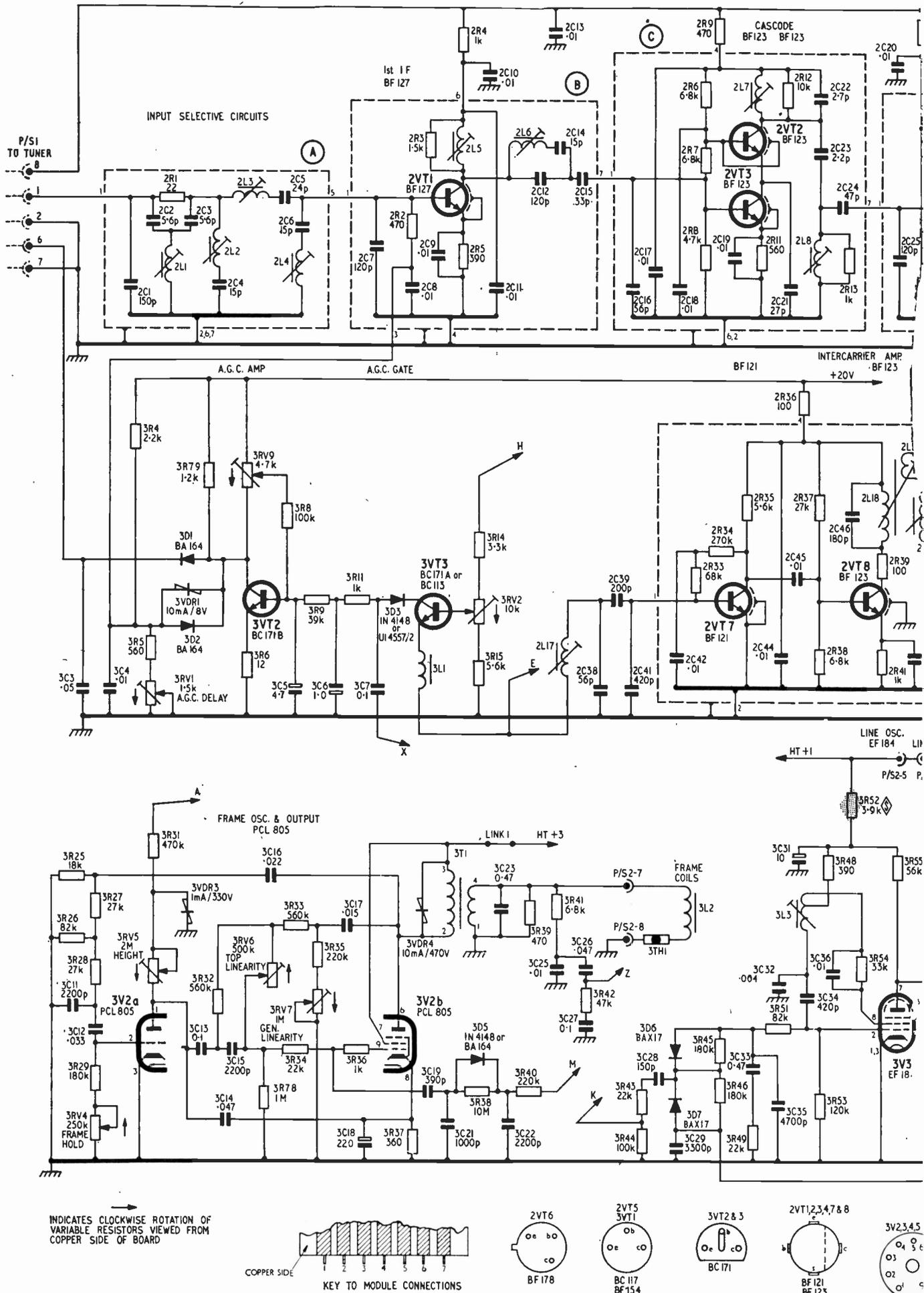
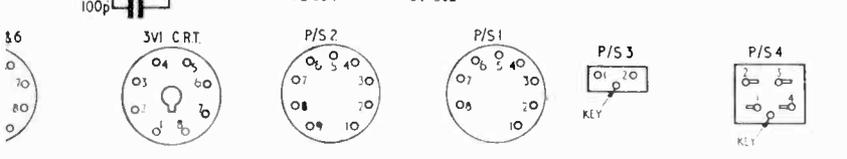
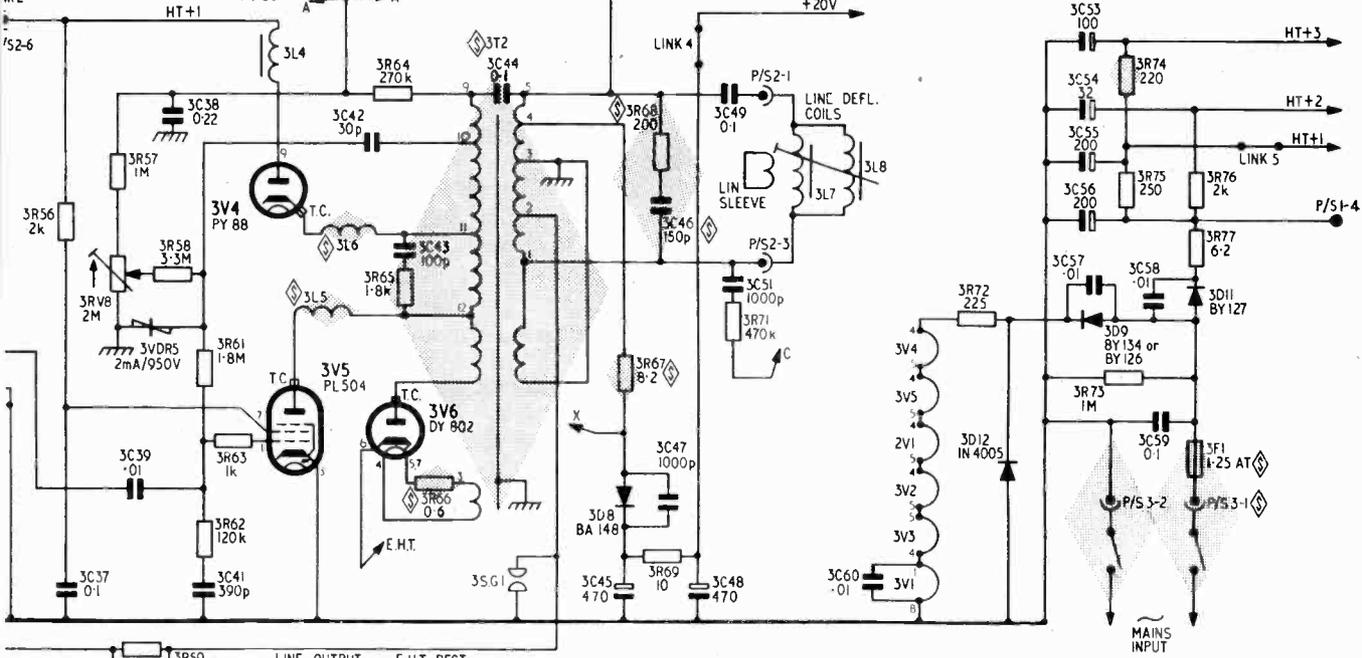
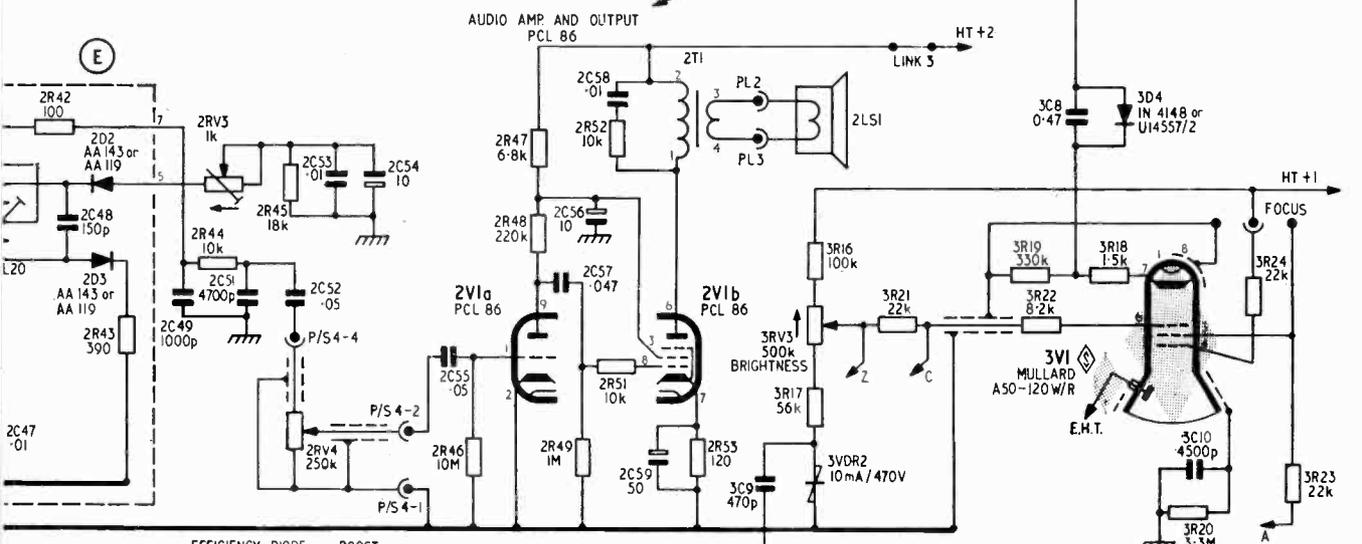


Fig. 2: Circuit diagram, RRI A774 chassis. Modifications include the deletion of 2C59 and the addition of an 0.1 μ F capacitor and a 2.2M resistor with 3R58 changed to 4.7M Ω to maintain the width adjustment.

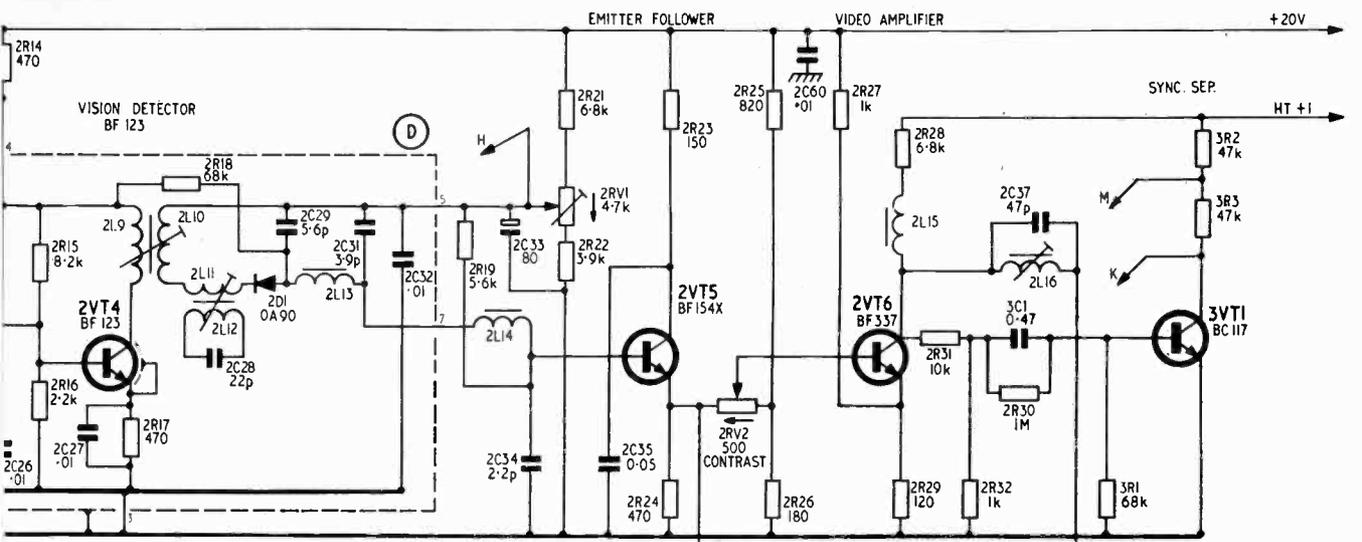

RESISTOR VALUES IN Ω & CAPACITOR VALUES IN μF UNLESS OTHERWISE STATED.

KEY TO PLUGS, SOCKETS, VALVES & TRANSISTOR BASES VIEWED FROM UNDERSIDE.

5763-24

27k Ω resistor in series between the collector and base of the a.g.c. amplifier 3V72. Later models use more sensitive deflection coils,

electrolytic (50 μ F). This was done to eliminate hum at low volume settings.

Another cause of hum on sound is incorrect earthing around the volume control. One end of the volume control is earthed to the case via the screened lead.

Signal Faults

Sound only with a blank raster seems to occur quite often. The usual cause is a defective video output transistor (2VT6, BF178, later BF337). This goes open-circuit or, less often, short-circuit. Caution is required here: the transistor sometimes doesn't read open- or short-circuit but a replacement restores the picture.

The video emitter-follower 2VT5 (BF154) and the video detector diode 2D1 (OA90) can be responsible for loss of signals. The diode, which is housed in can D, goes open-circuit. Removing the can from the mother board with the aid of a solder sucker is much easier than trying to replace the diode with the can in situ. Before undertaking this time consuming job make sure that the diode is at fault: the aid of an oscilloscope or even a signal generator will tell whether the video signal is being lost within can D.

Prominent flyback lines on the screen I traced to the 6MHz filter coil 2L16 in the video output transistor's output circuit.

An important check if there is line pulling on peak whites or a general bending of the picture is the setting of the video bias control 2RV1. First set the main contrast control fully

clockwise, then set the video bias control, using a suitably small trimming tool, fully anti-clockwise. Select a signal-free channel, then adjust 2RV1 until noise becomes just visible on the screen.

As in most modern sets the i.f. stages give very little trouble. If one of the four transistors goes open-circuit the usual result is either a grainy picture or complete loss of picture with grain on the screen.

Intermittent loss of vision along with weak, distorted sound I traced to the final i.f. transistor 2VT4 being intermittently faulty. A case of no sound or vision was found to be due to 2VT2 being open-circuit.

On the mechanical tuner the most common fault is the nylon lugs which travel along a screwed thread to tune in the channels. These break or split so that the channel cannot be selected. Spares are available from RRI and it's worth keeping them in stock since so many Rank tuners use them. Replacement is quite easy. The push-button knobs can also be the cause of inability to select channels or carry out fine tuning. They are made of nylon or plastic and turning or pressing them wears the linking cross.

The r.f. amplifier transistor in the tuner (4VT1, BF180) is sometimes responsible for a grainy picture which can be mistaken for an aerial fault. It can be replaced but care is necessary to avoid damaging or disturbing the surrounding components.

The aerial panel can also be responsible for a grainy picture due to poor soldered joints in the aerial connector. ■

Book Notices

Radio, TV and Audio Technical Reference Book, edited by S. W. Amos, published by Newnes-Butterworths, Borough Green, Sevenoaks, Kent, at £24.

It is not every day that a major work such as this one is published. It's a hefty price, but then it's a hefty book, well over 1,200 pages covering most aspects of radio, TV and audio from the studios to the equipment used at home.

How does one go about commenting on a book such as this? Obviously one can't go through it in detail. So the best thing is to plunge into those sections one is particularly interested in or knows something about. We had a good look at the audio and television sections, and found them up-to-date, well written, clearly illustrated and full of basic information. The sections on monochrome and colour receivers are written by A. G. Priestley, senior development engineer in the Philips' Television Design Laboratory, while E. Trundle, who will be well known to readers of this magazine, covers television receiver servicing.

Even a book of this size can't unfortunately give information on all the varied circuit techniques in use. Thus you won't find anything on the thyristor line timebase, the less usual transistor field timebase configurations, and little on switch-mode power supplies. The section on u.h.f. TV aerials was excellent so far as it went, but it only covered the basic Yagi and log-periodic aerials. There was little on closed-circuit TV and no mention of videocassette recorders, though the subject of amateur television techniques finds a place in the section on television transmitters. We carp however. The book must be regarded as a reference source to the basic components and techniques in use today rather than as a comprehensive guide to the vast multitude of circuits and techniques to be found in practical designs. The presentation makes the information easy to follow and absorb, and there is minimum reliance on mathe-

tics. Mr Amos, his contributors and the publishers are to be congratulated on producing a first class book.

Amateur Television, published by the British Amateur Television Club, 64 Showell Lane, Penn, Wolverhampton, Staffs. at £1.25 post paid to BATC members; £1.75 post paid to non-members. Edited by A. Hughes, T.Eng.(CEI), MITE.

The 112 pages of this book contain a great deal of information and should enable anyone interested in amateur television picture generation and transmission to get started. There are chapters on aerials and reception; transmitting; operating techniques; picture sources; monitors; video recording; slow-scan TV; and colour. The book is particularly helpful in giving practical designs as well as basic information. The presentation is a bit scruffy, but this doesn't detract once you get used to it. We strongly recommend it to anyone thinking of branching out into the world of cameras, transmitters and so on.

Solid State Colour Television Circuits, by G. R. Wilding, published by Newnes-Butterworths, Borough Green, Sevenoaks, Kent, at £5.75.

The change to solid-state colour receiver designs brought with it a vast increase in the circuit techniques the service engineer is likely to encounter. There is a need then for a book which charts a clear course through this wide and complex field. G. R. Wilding should be well known to readers as a regular contributor who concentrates on up-to-date circuit techniques and the servicing problems they bring with them. In this book he surveys and describes a large number of representative circuits used in UK, Japanese and continental colour receivers. It's thoroughly up-to-date, dealing amongst other things with diode modulators, switch-mode power supplies and the Syclops circuit. A useful reference book to have on your bookshelf to consult when next you find yourself short of an explanation of how some particular feature of a modern solid-state set works.

Developments in Switch-Mode Power Supplies

IN the October 1975 issue we described several switch-mode power supply circuits and their principles of operation. The prolific activity of setmakers since then has seen the introduction of a whole crop of switch-mode arrangements, and some of the more interesting circuits will be described in this sequel. If the author's grapevine is to be believed, activity in manufacturer's development laboratories is continuing at great pace on the power supplies front: perhaps in a year's time some of the up-to-the-minute stuff described below will have become obsolescent . . . oh, Syclops, where is thy sting!

Design Trends

The most significant trend is towards greater sophistication, especially in the overload trip circuits where more comprehensive protection tends to be provided without the off-or-bust system of crowbar thyristors or thermal cut-outs. Increasingly the receiver's pulse is being monitored at several different vulnerable points, each of which can initiate shut down of the power supply should things go amiss. The foremost examples of this are the ITT CVC20 circuit to be described next month and Thorn's Syclops (9000 chassis) system which was admirably covered by Barry Pamplin in the August 1975 and August 1976 issues.

Thyristor circuits require very large values of smoothing and reservoir capacitance with a high ripple-current rating, especially in circuits where overload protection on the sample-and-pulse system is incorporated. Electricity supply authorities do not look kindly on thyristors, and even where a bridge rectifier upstream of the control element prevents d.c. being drawn from the mains the system takes very large short duration bites from the supply line.

Line-frequency Switching

The solution to both these problems is to switch the control element at a rate much higher than 50Hz. The line frequency (15.625kHz) is convenient from three points of view. It is already available in the receiver and allows a degree of integration of the line scan and power supply functions; it is sufficiently high to enable small ferrite-cored power transformers and low-value ripple filter capacitors to be used; while any r.f. radiation due to switching transients is phase locked to the picture and can be more easily suppressed or hidden in the line blanking period, so that interference on the display is less troublesome than would be the case with a free-running oscillator driving the power switch.

Secondary Supplies

Hand in hand with this technique goes the idea of deriving most of the secondary supplies from the line output

transformer, either by the conventional method of scan or flyback rectification or, in 110° receivers, by making use of the diode modulator pincushion distortion-correction arrangement, in which the diodes are kept loaded so that they conduct throughout the line scan period, providing a useful source of l.t. power.

Starter Circuits

In many modern designs then, the power supply circuit supplies only the line output stage and the RGB output stages, with (typically) the field and sound departments, the line oscillator and signal stages being powered from the line output stage. This implies the need for some form of kick-start circuit to get the whole shooting-match off the ground: it usually takes the form of a bleed resistor to the line generator from the rectified mains supply, or a configuration whereby a capacitor charges towards h.t. potential, the charging current developing a potential to enable the oscillator (and in the case of the Rank Z718 chassis the line driver) to start up.

Design Requirements

The c.r.t. dictates the design of the line output stage because of its scan and e.h.t. requirements – these are closely defined by the tube manufacturer. The line output stage in turn governs the design parameters of the power supply unit. Most of the design philosophy of the new types of colour tube relates to wider deflection angles and simplification or elimination of the convergence adjustments required. So strong is the influence of the display tube on power supply design that the Sony Corporation currently use three different switch-mode power supply designs for three sizes of c.r.t. – more on this later.

Monochrome Portables

Colour sets do not have a monopoly on switch-mode power supply circuits; the technique has great advantages for portable small-screen monochrome sets in which power consumption is at a premium, even at mains voltage, and where generators or invertors may be used to power the set in certain situations. The other very relevant factor is the use of small-volume cabinets in which the components are fairly tightly packed; the more efficient the electrical circuits, the less the power dissipated in the form of heat – the greatest enemy of reliability, and the thin plastic cabinet shell in which these little sets are usually housed! The elimination of the mains transformer has the further advantage of reductions in cost and weight and the absence of leakage flux. On then to the Indesit 12in. portable receiver: this uses an ingenious pump circuit in which the

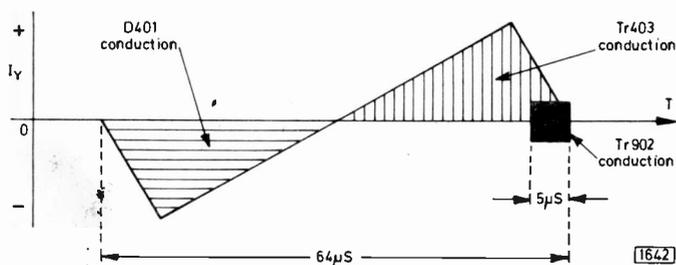


Fig. 3: Conduction duty-cycles of the line output transistor, the chopper transistor and the efficiency diode.

the l.t. voltage. If this is at all unclear, think back to the action of the PD500 in early colour set e.h.t. systems!

Kick-Start and Auxiliary Supplies

There remain one or two other points to clear up. The line oscillator, a TBA950 chip, is normally powered from the 12V line. Thus a start-up supply is necessary to power this – and the driver and output stages – at switch-on. Referring again to Fig. 2, the start voltage comes from the centre of the split reservoir capacitor C905/C906 and potential divider R905/6. At switch on, the mains-derived 6V or so at this point goes to the 12V line via D904 and to the 17V line via D905 so that the line output transformer is energised and the normal chopping action begins. As the 17V and 12V lines become established, D904 and D905 become reverse biased, isolating the start circuit. D903 is there to prevent the start up voltage being mopped up by the rest of the receiver, isolating the signal and sound stages during the kick-start process. This diode comes out of reverse bias and conducts when normal operation takes over.

The line timebase proper is conventional in this receiver, and is shown in Fig. 2. The square-wave oscillator output passes to the base of the line driver transistor Tr402 whose collector voltage source is the 17V line. There is a notable absence of frills around the line driver transformer T401 which feeds the line output transistor Tr403. The line output stage is tuned by C406, with D401 playing the dual roles of conventional efficiency diode and power-pump clamp, while C407 provides s-correction. Fig. 3 shows the conduction periods of D401 and Tr403. The flyback pulse at Tr403 collector is rectified by D910 to provide the supply for the video output stage and a control voltage source for the varicap tuner, while the c.r.t. first anode and e.h.t. voltages are provided by rectifiers operating from overwinds on the transformer.

When battery operation is selected, the chopper Tr902 takes no part, D907 now being reverse-biased. The set is then powered direct from the 12V line, with the 17V line provided by normal boost action from the line output stage.

SONY CAPACITANCE SWITCHER

Our next circuit is also used in a small-screen model, this time a colour set, the Sony KV1340UB. Basically, all Sony television sets are designed to run from a supply in the region of 130V, which is a convenient figure for continental and USA/Canada mains supplies: the basic chassis in each case is intended for a wide export market, and is tailored in the sound, tuner, decoder and power supply departments for the various areas of use. For the UK market, the 240V mains supply set Sony an interesting voltage-conversion problem. In tackling this they have used a different principle of operation in almost every model released, and in doing so

have run the gamut of virtually all possible techniques from a mains transformer to the unique circuit described here.

Before we can explain the operation of this power supply adequately we must delve for a moment into a little basic theory. Consider the circuit shown in Fig. 4, in which two capacitors in series are connected to a d.c. source via a switch and a resistor. When the switch is closed, charging current will flow through the capacitors, and since they are in series the same charging current must flow through them both. After a time determined by the relationship of the effective total capacitance and the resistor R, the voltage across R will have sunk to virtually zero, and the full d.c. voltage will appear between point A and earth. Now the charge on a capacitor is proportional to charging current and the time during which it flows. Because the charging current and time are the same for both of the series capacitors, the charge on each capacitor will be equal. Total charge in Coulombs is a function of voltage and capacitance, the relationship being that the larger the capacitance, the smaller the voltage for a given charge. If our equally-charged capacitors in Fig. 4 are of different values therefore, it follows that the voltage present across each is inversely proportional to its capacitance. To put it another way, ten volts across $1\mu\text{F}$ is worth five volts across $2\mu\text{F}$, which sounds fair enough! Thus if the upper capacitor in Fig. 4 was $2\mu\text{F}$ and the lower one $1\mu\text{F}$, one-third of the applied voltage would appear across the upper capacitor and two-thirds at point B with respect to earth.

Going off at a tangent for a moment, this charge = voltage \times capacitance idea suggests that if we charge a capacitor to a given voltage, then somehow reduce its capacitance (say by further separating its plates), the voltage across it will rise. This is so, and can be demonstrated with an electrostatic voltmeter and variable capacitor: this conjures up visions of mechanical voltage multipliers, which are quite feasible in theory, but of little practical use. Let's get back to the Sony power supply circuit though!

Circuit Operation

The skeleton circuit shown in Fig. 5 illustrates the principle. On the positive half-cycle of the mains input S2 is open while S1 is closed. C1 and C2 now charge in series from the mains, each becoming charged to almost half the peak mains voltage. Thus approximately 150V is developed across each capacitor. One half-cycle later the mains input drives point A negative with respect to ground, and S1 opens while S2 closes. This isolates the circuit from the mains, and connects the two capacitors in parallel: each is charged to about 150V, and the parallel pair discharge through the load which is thus provided with a 150V line.

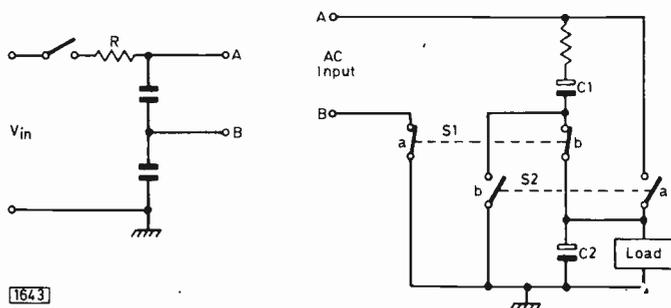


Fig. 4 (left): Series-connected capacitors charged from a d.c. source via a resistor.

Fig. 5 (right): Basic principle of the power supply used in the Sony Model KV1340U portable colour receiver.

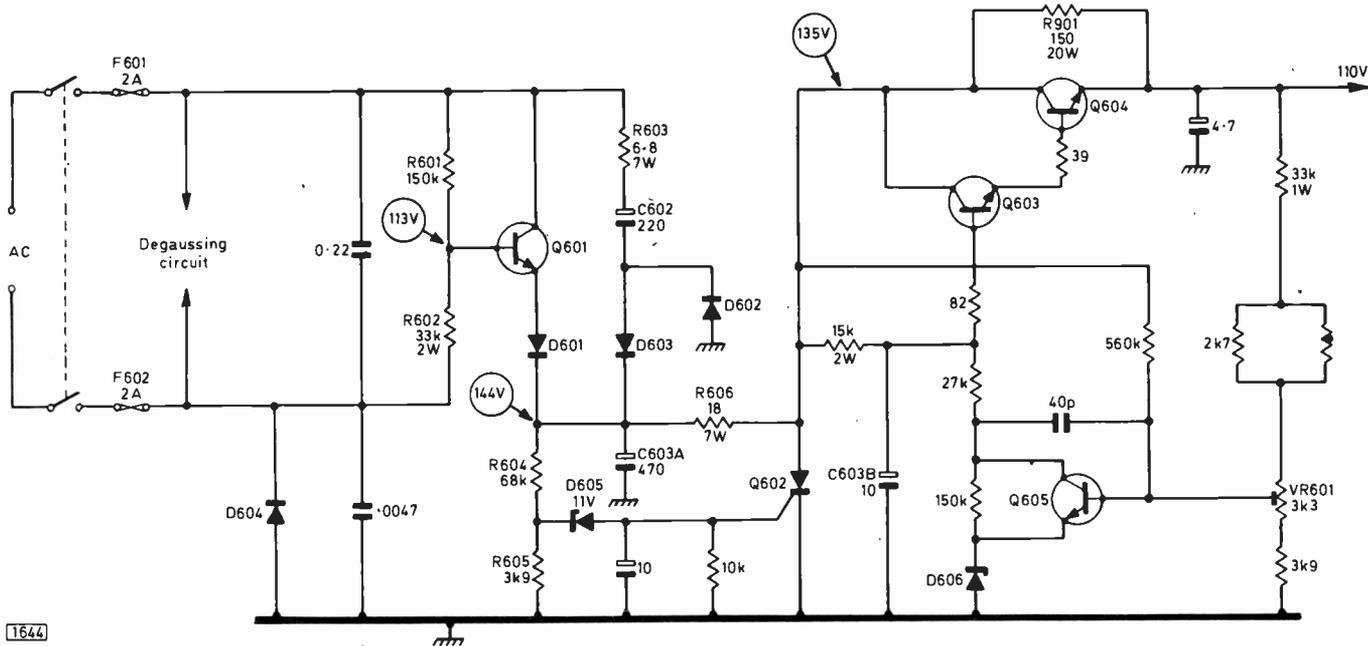


Fig. 6: The Sony KV1340U power supply circuit.

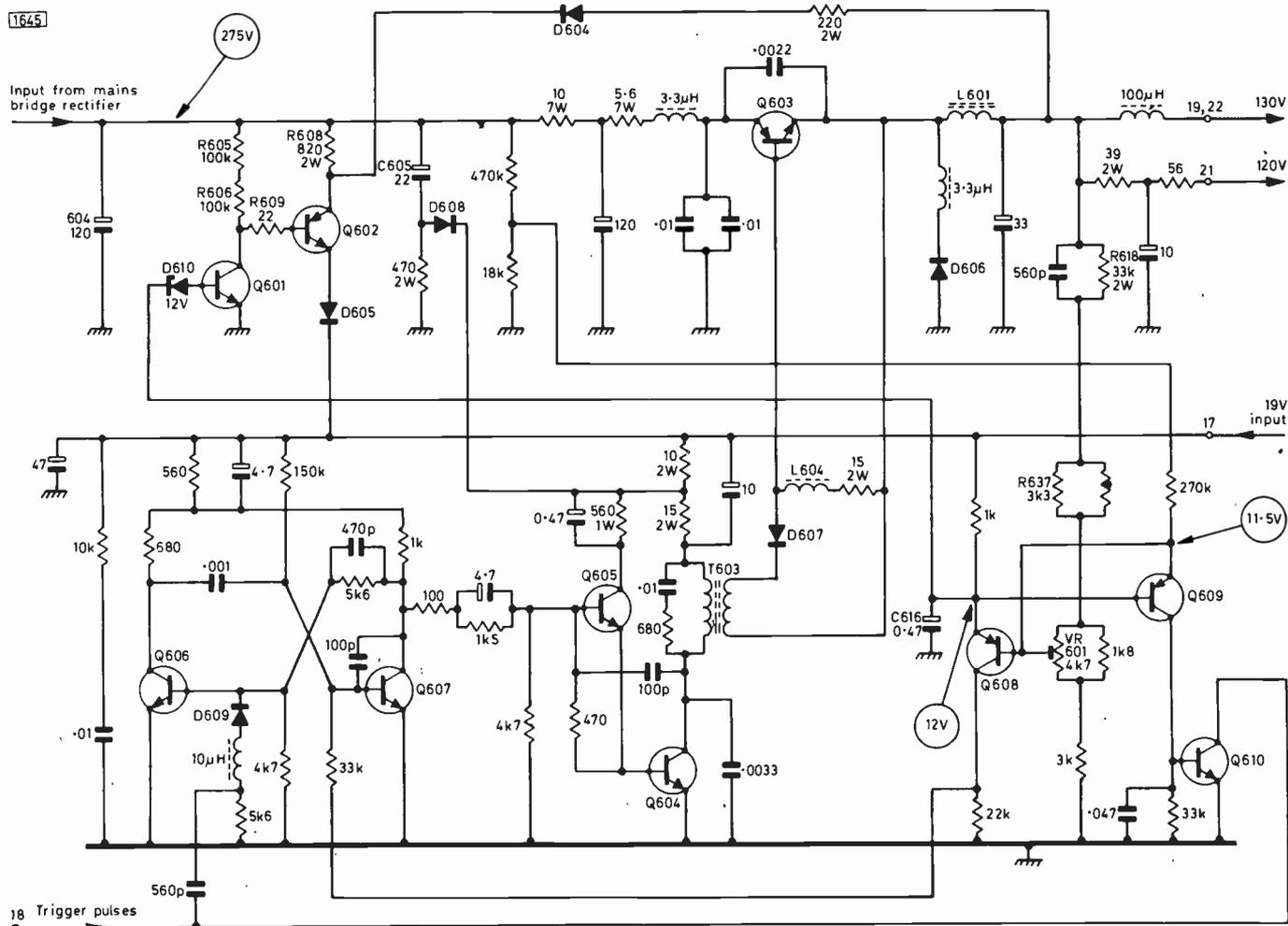


Fig. 7: The Sony Model KV1810U Mk. II power supply circuit.

Fig. 6 shows the actual circuit. C1 and C2 of Fig. 5 are C602 and C603A respectively, Q601 and D602 replace our S2a and b, while D603 and D604 act as S1a and b. On the positive mains excursion, Q601's base is held negative with respect to its emitter by R601/R602, so that the transistor

stays off. Charging current flows via R603 and C602, and via the forward-biased D603 and C603A. This is the first phase completed, and about 150V is established across C603A. Now the mains voltage swings through zero and F602 becomes more positive than F601. This reverse biases

D604, isolating the mains input, and turns on Q601 via its base resistor network. The conducting Q601 links together the positive plates of C602 and C603A. C602 cannot instantly discharge, so its negative plate follows in a downward direction, turning D603 off and D602 on, so that C602's negative plate becomes clamped to earth. Our capacitors are now in parallel, and make available on R606 about 140V. It will be noticed that the lower capacitor C603A is more than twice the value of the upper one, C602. This is because the load is still present across C603A (or C2 in Fig. 5) during the initial series-charging phase, and this shunts away some of the charging current for C603A. It's necessary therefore to increase its capacitance to retain the balance between the upper and lower halves of the circuit.

The load is of course the receiver, and interposed between the power supply and the load is the conventional d.c. regulator/filter circuit Q603/4/5. This reduces the h.t. voltage to 110V (adjustable by VR601) and removes the 50Hz ripple.

We have made no mention yet of D601, which plays no part in the switching action. It's included to protect Q601 from excessive reverse base-emitter voltage.

Overvoltage Protection

The potential divider R604, R605 monitors the voltage across C603A, and if this rises towards danger level the 11V zener threshold of D605 is exceeded. This component then passes a current into the gate of the crowbar thyristor Q602 which fires, shorting the 150V line to earth and blowing the mains fuses.

LT and CRT Supplies

The sound output and timebases are operated from the 110V line in this receiver, while supplies for the RGB output stages, the c.r.t. anode potentials, the tube heater and an l.t. line of 17.5V are all derived from the flyback transformer (this is not the line output transformer!). No start-up problems here, as the power unit works wholly at 50Hz mains rate.

This power supply circuit is certainly a neat and relatively simple design, but suffers from the disadvantages of drawing d.c. from the mains and a half-live chassis, an unusual combination. Heavy transient mains consumption, and the ripple-current requirements of the two capacitors involved, suggest that this circuit configuration will not be developed for larger-screen receivers.

A GCS CIRCUIT

For their 114° 18in. Trinitron Model KV1810UB MkII the Sony Corporation came up with another variation on the switch-mode theme. The circuit is shown in Fig.7. The bones of the circuit are the switch Q603, the chopper choke L601 and the recovery (clamp) diode D606. The basic energy store is L601, and the principle of the chopper circuit is the well-known one utilised in the Thorn 3000 chassis and its derivatives.

GCS Characteristics

The novel feature of the circuit is the use of a gate-controlled switch (a Sony special) instead of a conventional

transistor as the switch – it's also used as the line output device in this receiver. There is also the need for a start-up feed due to derivation of the secondary supplies from the line output transformer. The GCS is a cross between a transistor and a thyristor – a sort of Japanese Welsh Arab. If the gate is made positive with respect to the cathode, the device will conduct between its anode and cathode and stay latched on, even if the gate current is removed. These are the characteristics of a thyristor, and the similarity is maintained in that the GCS can be turned off by reducing the cathode current below a certain holding level. This property is not used for Q603 though, because the GCS, unlike a thyristor, can be turned off while in full cry if the gate is made sufficiently negative with respect to the cathode.

Circuit Description

Turning in our new-found wisdom to Fig.7 then, the similarity to the Thorn 3000 family will be seen in the line-triggered monostable Q606 and Q607 whose time-constant, and thus mark-space ratio, is governed by the d.c. amplifier Q608. The conduction of Q608 is dependent on the setting of VR601 (set h.t.) and the voltage of the 130V output line sensed via R637 and R618. The monostable's output at Q607 collector is buffered by the emitter-follower Q605 and passed to the chopper driver Q604. Thus we have a square-wave output at T603 secondary.

From this point on all similarity with other circuits ends, for the drive circuit to the chopper GCS must provide a turn-off pulse as well as a triggering pulse. Let's break into the cycle at the point where Q603 is conducting and we require to switch it off. The top end of T603 is so phased that it goes negative at this time, and D607 conducts to drive Q603's gate negative, thus turning it off. Energy is stored in L604 during this period, and at the end of the "space" section of the drive waveform along comes a "mark" and the polarity of the voltage across T603 secondary reverses, cutting off D607. The stored energy in L604 is now released to provide a positive spike to switch on Q603 at its gate, and the cycle is complete. This back-to-front explanation is valid after one half cycle of drive!

Kick-Start

There remains the problem of getting the line oscillator and the switch-mode control circuits off the ground at switch-on. Both are powered from the 19V rail, which is absent until the line output stage fires up. Thus Q601 and the GCS Q602 are provided to form a kick-start mechanism. At switch-on, current flows via R605, R606 and R609 into the gate of the GCS Q602 which conducts, connecting the 19V line via R608 to the 275V line from the mains rectifier bridge. As the 19V rail capacitors charge the voltage rises, until at about 15V (by which time the line oscillator and monostable are banging away) the zener D610 reaches its conduction threshold and passes current into the base of Q601. This npn device promptly turns on and grounds the gate of Q602. As Q602 cathode is at 15V or so, the negative-gate turn-off requirement is met, and with the h.t. and l.t. lines established Q601 stays on, and Q602 and D605 stay off. In fact when the receiver is switched off and the 19V rail falls to a level where D610 comes out of conduction, the kick-start GCS turns on again and conveniently discharges the reservoir capacitor C604 via R608 into the heavily-loaded 19V rail.

This brings us to D604. It spends most of its life reverse biased, but has a brief moment of glory at switch-off. As the

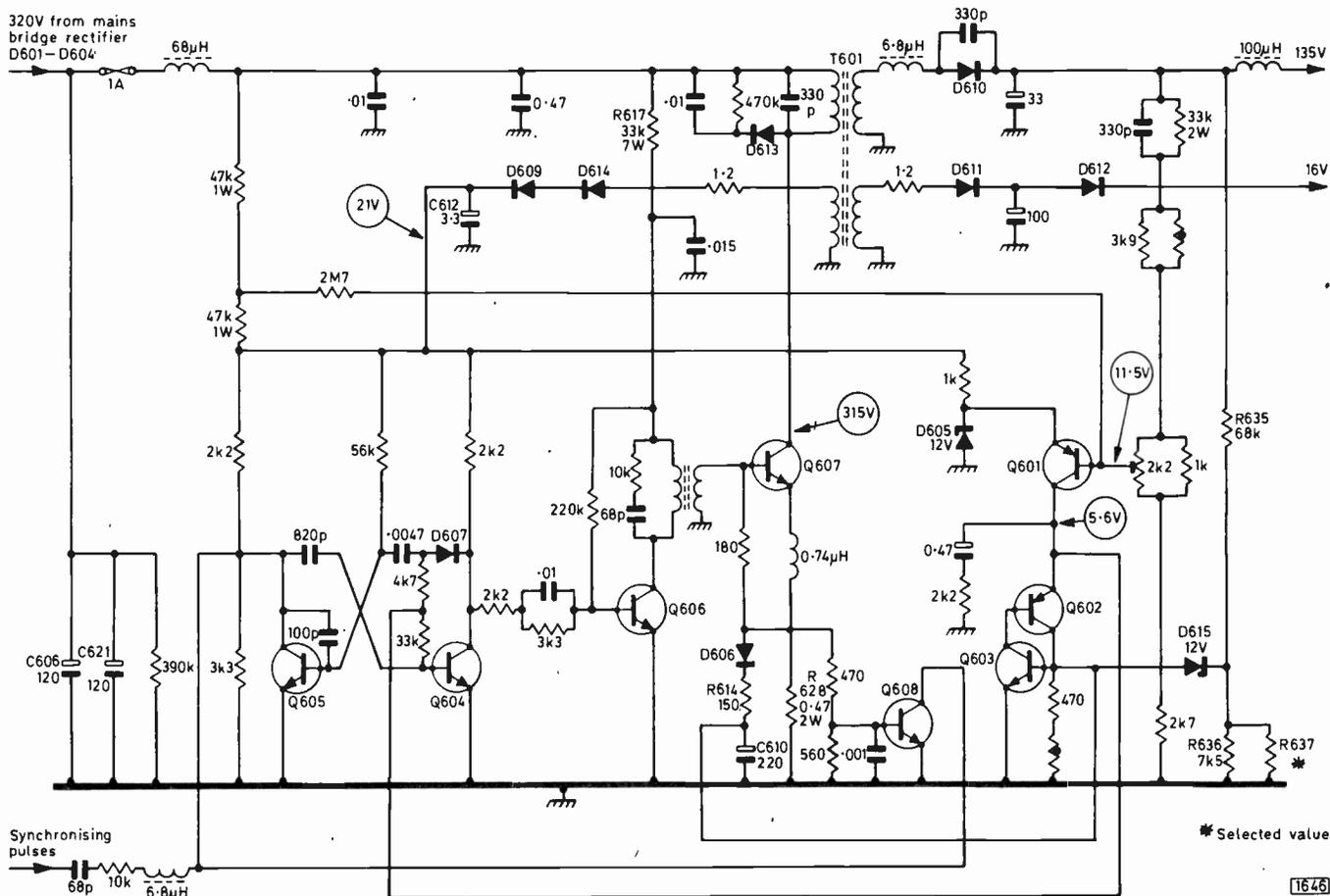


Fig. 8: The Sony Model KV2000U power supply circuit.

supply lines all decay it is important that the line oscillator continues until the bitter end – for reasons which we will explain in the next section. When the set is switched off then, the 275V line decays and Q602 comes into conduction. This connects the cathode of D604 to the 19V line, so that the last dregs of voltage on the 130V output drain into the line oscillator hanging on the 19V line. Thus the drives to the chopper and the line output stage are maintained until there is barely a volt to be had anywhere in the set.

There is an auxiliary start-up supply to the chopper driver department via D608, which furnishes a momentary voltage at switch-on by virtue of the charging current in C605.

line output GCS makes the supreme sacrifice. A puff of smoke and a blown mains fuse, with at best two dead short GCSs, bring down the curtain on the overload protection phase! Plainly this “protection” is something of a misnomer, and the same sequence of events can occur if the line oscillator stops. In fact the line oscillator i.c. is designed to continue in the face of a very low supply voltage. Our previous reference to D604 and its function can now be understood.

Not our favourite switch-mode circuit this one, but interesting nevertheless. We will offer some advice on dealing with this power supply in the servicing section next month.

Protection

It seems that excessive current consumption is such a remote possibility in this receiver that no over-current precautions are necessary – a very moot point after a year’s experience of this set, but that’s a different story!

Sony do provide an overvoltage trip however, in the form of Q609 and Q610. D610, whose anode is effectively earthed through the conducting Q601, sets up a stabilised potential of 12V on Q609’s base. Under normal circumstances the emitter of this transistor sits at 11.5V, and no base current flows. If the 130V rail rises however, Q609’s emitter comes up as well. Soon the base-emitter junction of Q609 becomes forward biased and Q609 conducts, turning on Q610 which grounds the squarewave triggering input and brings the monostable and chopper to a grinding halt. This usually leaves the chopper GCS hard on due to the absence of the switch off pulse from its drive department. The h.t. voltage goes “off the clock”, and the

SONY KV2000UB CIRCUIT

To round up our Sony collection, Fig. 8 shows the switch-mode power supply circuit used in the current Sony 20in. model. In many respects this set-up is conventional, but the protection circuitry is interesting. Basically it’s a shunt chopper circuit (the Thorn 3000 chassis uses a series chopper circuit). Let us first describe the operation of the main circuit, starting at the bridge D601-D604 which provides a 320V mains-derived supply across the reservoir capacitors C606 and C621. This voltage is switched across the primary winding of T601 by the chopper output transistor Q607, which operates at a mark-space ratio of almost 1:1. T601 has three secondaries, the main one providing a 135V line via D610. This powers the entire receiver including, indirectly, the scan-derived l.t. lines. The lower secondary provides a kick-start potential for the line generator i.c., while the “third secondary” winding provides 21V for use in the control circuits in the power supply itself.

The drive to the chopper transistor is from Q606, whose base waveform consists of a variable mark-space ratio line-rate squarewave derived from the line synchronised multivibrator Q604/Q605. Unlike the monostable in the 18in. receiver just described, this one is astable, free-running in the absence of synchronising pulses so that the power supply will operate if the line timebase in the receiver is not running. The mark-space ratio is controlled by the conduction of the error amplifier Q601, in similar fashion to the previous circuit.

Safety Circuits

There are three types of overload protection: excess current limiting, over-current cut-out and over-voltage cut-out. The first two depend on the voltage developed across R628 in the emitter return lead of the chopper transistor Q607. The voltage across this resistor is proportional to the current flowing in it, and this reflects the current drawn by the receiver and loading T601.

At normal beam currents, the h.t. current drawn from the 135V line is about 600mA. This corresponds to 200mV across R628. Such phenomena as c.r.t. flashovers cause transient current demands in excess of normal, and these momentarily increase the voltage across R628 to the point where Q608 turns on. This virtually grounds the collector of Q605 in the astable multivibrator, deleting the drive to the chopper. With no emitter current in Q607, the base current in Q608 drops back and it reverts to cut-off. Normal drive is then resumed. The threshold of operation for this circuit is about twice the normal h.t. current.

In the event of a short-circuit line output transistor or other sustained fault, the above action will take place but each time the chopper is reinstated a heavy current will flow through Q607. After about 700ms, C610 will have acquired enough charge via D606 and R614 to turn on Q603, whose collector current flows through the base-emitter junction of the pnp transistor Q602. The latter transistor thus conducts, and latches Q603 on by virtue of its collector current flowing through Q603's base. The pair are now locked in conduction regardless of the external conditions on Q603's base - this will be recognised as normal thyristor action, and in fact the pnp junctions of Q602 and Q603 form what might be called a discrete thyristor. Our D-I-Y thyristor is now hard on, and with the base of Q604 effectively grounded the astable multivibrator is muted, deleting the chopper drive so that the set cuts off and stays off.

The same transistors are used to shut down the set in the event of the 135V line rising unduly. When the h.t. voltage rises to about 146V, the potential developed by the divider R635/6/7 exceeds the 12V zener breakdown point of D615 and Q603 turns on. This shuts down the power supply as related above.

When the set has been latched off in this way, power can be restored only by switching off the set to allow the capacitors to discharge. At switch-on, conditions will again be sampled, and immediate shutdown will result if the fault remains.

Next Month's Circuits

So much then for the wonders of the Orient. We will return to these circuits when we discuss servicing. Before doing so next month we will be taking a look at an up-to-date switch-mode power supply used in a UK chassis - the ITT CVC20.

next month in Television

● INTRODUCING THE PHILIPS G11 CHASSIS

The first entirely new colour chassis from Philips since 1970 is a major event. This new chassis, designed around the 20AX tube, is intended to serve Philips well into the 80s. Great attention therefore has been paid to getting things right. The first of a two part article on the development of this chassis and the new techniques it uses.

● JAPANESE COLOUR SET FAULTS

Despite their reputation for fault-free service, Japanese colour sets must inevitably eventually fail as the effects of age appear. Peter Murchison reports on recent experiences with a selection of sets to show the sorts of troubles you can expect.

● THE TV LOGIC STATE CHECKER

The increasing use of digital i.c.s in TV circuitry and allied fields (e.g. our Teletext decoder) means that special fault-tracing techniques are required when problems develop. The construction of a simple instrument which indicates the "logical state" of every pin of a digital i.c. will be described. The device derives its power from the i.c. under test and uses l.e.d.s as indicators. It's housed in a small diecast box, with an external i.c. clip to hook up to the i.c. being investigated. Very useful for anyone dealing with logic circuits.

● TELEPRO COLOUR RECEIVERS

The Telepro range of colour receivers was made by a Telefunson subsidiary and used a chassis based on the Decca 30 series chassis. The sets have their own fault patterns however, and Barry Pamplin provides servicing hints on dealing with them.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the AUGUST issue of TELEVISION (45p), on sale JULY 18th, and continue every month until further notice.

NAME.....

ADDRESS.....

.....

.....

LONG-DISTANCE TELEVISION

ROGER BUNNEY

As May approaches there are increasing indications that the coming Sporadic E season will be a good one. Personally I feel that 1977 will provide us with an extremely active season. There have already been several SpE openings which have given quite strong signals from most parts of Europe. Meteor Shower reception has also had its moments. The most important recent MS reception was when Clive Athowe (Norwich) logged a two second burst from the Rumanian Ploesti ch. R6 transmitter (150kW e.r.p.) on March 24th at 1009 BST. The signal consisted of the monoscope test card and was accompanied by a Russian (TSS) signal on ch. R1. The distance travelled by the ch. R6 signal was over 1,200 miles and must constitute a new record for Band III reception. Our congratulations to Clive.

Report on the Month

Rather than list daily reception I'll give a summary of the more important signals received here during the month – yet again I'm short of space. There was something present most days. Some mornings produced virtually nothing, while other days were very active with MS bursts. The predominant signal seems to have been CST (Czechoslovakia) with the EZO pattern on ch. R1, often pinging with TSS (USSR) on programme material. There was an excellent SpE opening on the 19th – though personally I missed this – with excellent signals from RIA (Italy) on ch. IA, JRT (Yugoslavia) on chs. E3 and E4, MTV (Hungary) ch. R1, ORF (Austria) ch. E2a and West Germany ch. E2 during the late afternoon.

A Mystery Signal

The evening of the 24th produced a most unusual period of reception which I'm still uncertain about. Signals from a southerly direction were first noted at about 1845, with a characteristic multiple image effect and fading into the noise. A coloured announcer appeared at 1900, followed by a musical concert. Soon after, RTVE (Spain) was logged with football and commercials on ch. E3. The conclusion of the concert brought captions in English! Unfortunately the nature of the signal made exact identification impossible, and following a "Skippy" programme it faded out. Did anyone else see this mystery signal?

Belgium changes Systems

April 26th saw the start of Belgian operation on System B. The ch. E8 and E10 outlets were observed with the PM5544 test pattern during the early morning, the E8 transmission carrying the identification "WAV 8". It seems

that the ch. E2 outlet will continue using System C until the end of the year, when it will be dismantled.


The Annan Report

One topic in the Annan report is of interest to us. The 405-line service is due to end in the early 1980s. Annan suggests that there is a need for a fifth 625-line channel with a more regional flavour. This could use Band III, and Band I where necessary – finance allowing. I feel that the important words are: "It is difficult to foresee how much of v.h.f. Band I will be needed for the fifth off-air television service, but some frequencies in Band I might well be available for other services".

News from Abroad

Republic of Guinea: The Republic is to start TV transmissions late this summer, though it's planned to have a basic system in operation in the Conakry area (the capital) in time for the Independence Day Anniversary Celebrations on May 14th. Marconi supplied much of the studio equipment.

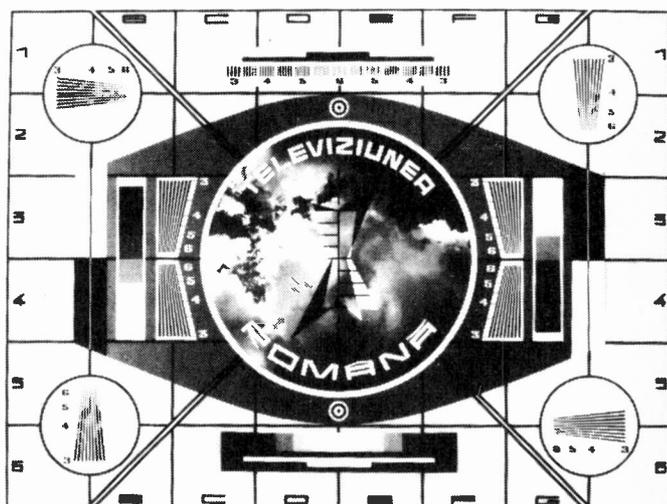Eastern Europe: A 500ft. tower has been completed for CST1 and CST2 (Czechoslovakia) on Mt. Klet near Cesky Krumlov (Southern Bohemia). Near Kosice the new Cizatic transmitter has come into operation – channels unknown. TVP2 (Poland) at Leborg is now operating. A new studio centre is being built at Riga hopefully improving reception in Latvia, USSR. *Broadcast* magazine has



The Televiziunea Romana (Rumania) monochrome test card. Photograph courtesy Brian Fitch.

pointed out that our caption on page 257, March issue is incorrect. The programme title "Vremya" is a weekly current affairs show produced at studio 5 of the Ostankino Centre, Moscow. Soviet TV's frequent news bulletins – at 1800 and 2000 local time on the first network – are identified by the word "Novosti" which on the screen looks like "Hobosti". The background graphic, a solarised animation of a satellite earth station, is the same as used for "Vremya".

Twenty-first Sunspot Cycle

Speculation continues as to whether the new sunspot cycle (the 21st) will provide a low or a high count. A high count is what we hope for since the m.u.f. (maximum useable frequency) of the F2 layer then rises sufficiently to reflect the lower v.h.f. signals over vast distances. The magazine *Nature* (February 1977) published a letter claiming that a formula which suggests that the new cycle will have an average high count (i.e. at peak time) of 195 – similar to cycle 19 which was at its peak in the late 1950s – has been derived. At its peak, cycle 19 produced v.h.f. propagation over paths of several thousand miles at up to 60MHz. We can but hope! The count is at present increasing and the maximum activity will be in 1981/2.

New EBU Listings

Finland: Kruunupyy YLE-2 ch. E30 200 kW e.r.p. (23E31 63N44); Pihitipudas YLE-2 ch. E32 1000kW e.r.p. (25E39 63N17). Both with horizontal polarisation.

Iceland: The ch. A2 AFRTS air base TV transmitter has closed (2mW).

Malta: Radio TV Indipendente (Tivumalta Ltd) ch. E21 10kW (horizontal).

Switzerland: La Dole ch. E4 reduction in e.r.p. from 150kW to 144kW.

Correspondents' Comments

Hugh Cocks has found that when making the Tru-Match type of wideband Band I array placing the smaller h.f. resonator some 3in. in front of the main dipole rather than 3in. below gives a noticeable increase in performance on ch. E4.

Earnie Earnshaw (Newcastle on Tyne) comments that he is astonished at the high prices quoted for set conversion and the supply of foreign receivers. He has obtained a Hitachi portable from West Germany fitted with both v.h.f. and u.h.f. tuners and with separate i.f. strips for systems B, G and I, the latter being selected via a single push button. It's similar to the model P20 sold in the UK but costs just £4.50 more than the UK price for the P20! The receiver can be obtained through Hitachi Sales (Europa) GmbH, Kleine Bahnstrasse 8, 2 Hamburg 54, West Germany – not from Hitachi UK.

Spectrum Analyser

Alan Latham in Abu Dhabi has constructed a spectrum analyser for TV use, using a 0-30V tuning line and a varactor v.h.f. tuner. He found that a suitable 30V sweep could easily be obtained by differentiating the voltage across the field scan coils. The tuner can thus be operated either normally, via a 30V tuning line, for single channel use, or be switched to analyse the full bandwidth. The spectrum appears as horizontal black bars and white spaces, the bars for transmissions and the white spaces for unused channels.

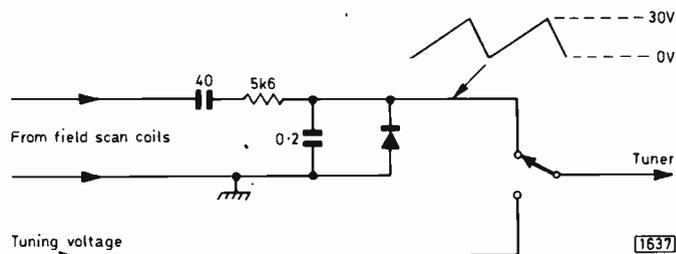


Fig. 1: Idea suggested by A. J. Latham for obtaining a 30V sawtooth to modulate the tuning voltage input to a varicap tuner, enabling it to be used in a spectrum analyser arrangement. The voltage across the field scan coils is integrated and clamped to give a field-frequency sawtooth of 0-30V.

We do not advise modifying TV sets for this purpose unless you are fully experienced in such work. See Fig. 1.

More on Satellites

Information has been coming in on the results of the recent conference in Geneva held under the auspices of the ITU. Much of this information is on future plans for an eventual satellite broadcasting service – still very much in the planning stage. The "Ariane Large Satellite" will be launched in October 1980 however and will carry high output equipment (450W) for TV/radio transmissions in the 12GHz band. Much of this information is detailed, giving considerable insight into the future of broadcasting in the forthcoming decades, but is best left to a separate article.

Philips have available (to order, price unknown) "direct to home" satellite TV reception equipment covering 860MHz (ATS), 2.6GHz and 12GHz. Head converters change down to 120MHz, though the 12GHz unit has an i.f. of 330-470MHz. The array consists of a 1.6m diameter dish with a gain of 44dB (isotropic) and with 60% efficiency. Philips initially designed for vertical polarisation but the conference decided on circular polarisation.

HOW TO DX – PART 3

Signal preamplifiers are basically used to lift the level of weak signals sufficiently to obtain pictures with the minimum noise (grain, snow). This is because noise in the first stage of a receiver is amplified throughout the succeeding stages: by adding at the input an amplifier designed for minimum noise the overall noise performance of the receiving installation is improved. In addition, in the case of long-distance television many of the signals are so weak that amplification at the aerial is essential if they are not to be lost in the feeder prior to arriving at the set's aerial input socket.

The noise performance of modern, transistor tuners can be very good, especially at u.h.f., and for this reason the addition of a preamplifier may make little difference to picture quality. With valve tuners however the addition of a low-noise preamplifier can give a dramatic improvement.

Performance Characteristics

In considering the purchase of a preamplifier thought has to be given to the noise figure as well as to the gain therefore. Another point is the ability of the amplifier to handle strong signals. Most of us live in areas served by at least one high-power u.h.f. transmitter, apart from the 405-line transmissions and a minimum of three v.h.f./f.m. radio trans-

missions present. The problem is what happens when the amplifier receives strong local signals in addition to the weak distant signals we're interested in. The characteristic of importance here is linearity. Any non-linearity will result in some mixing of the unwanted strong signals(s) and the wanted weak signal.

Gain

Amplifier gain is normally quoted in decibels (dBs), often related to a basic reference point, for ease say 1mV. If you look at a dB/voltage chart you will see that a gain of 6dB is twice, 12dB 3.98 times (say four) and 18dB 7.94 times (say eight). Giving the reference 1mV to these gains gives 6dBmV 2mV (twice 1mV), 12dBmV 4mV (four times 1mV) and so on.

Noise Figure

An amplifier's noise figure indicates how much noise it adds to the weak signal passing through: the lower the noise the less the grain on the picture – or the hiss on the sound channel. 75Ω input/output figures are normally used for aerials and amplifiers. Aerials are designed to maintain as nearly as possible a 75Ω output impedance over the bandwidth covered, so we use a low-loss coaxial feeder with a 75Ω characteristic impedance. The amplifier's input is designed to match this 75Ω impedance, and since the input at the receiver is 75Ω the amplifier's output is at the same figure. The aim is that with all the items matched there is maximum signal transfer through the system and minimum noise. Ideally then, the amplifier will see a 75Ω source at its input. If we connect a non-inductive 75Ω resistor here instead of an aerial we will be presenting to the amplifier a 1.25μV noise signal (a 75Ω resistor gives an *open-circuit* noise voltage of 2.5μV at 5MHz bandwidth). This, related to 1mV, is 800 times lower, which in decibel terms is -58dB (signal-to-noise figure).

Cross-modulation

Cross-modulation occurs when the signals entering the amplifier exceed its signal handling capability. Remember that the amplifier is a broadband device, so that strong local signals will be entering it in addition to the weak signal you're interested in. Thus the signal you're trying to receive may suffer from video buzz, excessive contrast etc. due to the other signals present, while these may also appear in weakened form – with all three u.h.f. transmissions in operation you may see all three pictures floating over each other on channels other than their own. Figures are often quoted for maximum output and mean output. The former usually indicates the amplifier's handling capability with a single input signal, and the latter its performance with a certain number of signals. Take for instance the Labgear CM6040/WB wideband masthead u.h.f. amplifier. The peak handling capability is quoted as 167mV (44.5dBmV) whereas with four signals present – as would be the case with the full local u.h.f. group on-air – the handling capability is derated to 94mV input (39.5dBmV). This amplifier is a two-stage unit. The single-stage CM6000 has lower ratings – 25mV (28dBmV) peak and 14mV (23dBmV) mean. Thus the CM6040 will not produce cross-modulation until the 90mV input signal level is reached while the CM6000 will start overloading at 14mV. The overall results obtained depend on the tuner's overload figures as well. These vary with different types of tuner. Despite its high noise figure, an old valve tuner will be less likely to over-

load than a bipolar transistor tuner. I have recently seen the specification of a Telefunken varicap tuner which uses f.e.t.s at v.h.f. and bipolar transistors at u.h.f. The cross-modulation figures given for an interfering signal two channels away from the wanted one are typically 100mV in Band I and Band III, dropping to 15mV at u.h.f. This is for 1% cross-modulation against a wanted signal of 1.5mV.

Choosing an Amplifier

In deciding on an amplifier therefore we have to consider gain, noise performance – remembering that with increasing bandwidth noise increases and gain falls – and cross-modulation performance also taking into account the tuner.

There is a large range of signal preamplifiers on the market. At u.h.f., and certainly where long coaxial feeder runs are involved, a masthead amplifier is essential. For Band III such an amplifier is helpful while for Band I it's unnecessary. The recommended approach therefore is to use a u.h.f. masthead unit – type depending on the aerial system – and for v.h.f. an indoor amplifier such as a wideband distribution type – this has the added bonus of a little extra amplification at u.h.f. if necessary. To avoid wear and possible intermittent contacts a separate aerial connection panel with the aerials, amplifier inputs and output and receiver input is recommended. Apart from operational ease this will avoid damaging the amplifier's sockets, particularly where these are soldered directly to the chassis.

If a single, wideband u.h.f. aerial such as the Antiference XG21W or Wolsey Colour King is used the obvious thing is to select a wideband amplifier, and unless you are unfortunate enough to live in the shadow of Crystal Palace or one of its brothers a two-stage unit will give higher gain with better noise and cross-modulation performance. Examples are the Wolsey Supa Nova u.h.f. amplifier or the Labgear amplifier previously mentioned. If you are some miles from your local transmitter and use separate aerials such as a local group A and a wideband group E, I suggest the Supa Nova type for wideband operation and a lower-gain, single-stage unit for group A. Supa Novas could be used with both aerials, but some form of attenuation and filtering/trapping may be necessary on channels adjacent to the local ones. Finance will dictate the eventual choice, and if only a single masthead amplifier can be afforded the two-stage Supa Nova approach should be adopted with signal tailoring as necessary indoors.

Reliability

Masthead amplifiers are reliable and do not nowadays suffer from the gain variations (i.e. falling during the cold Winter months) common years ago. Even close lightning strikes do not normally affect them. Two years ago the local brewery some ninety yards away was struck and this had no effect on the Wolsey Orbit amplifier I was at the time using atop the 50ft. mast!

Build or Buy?

It is easiest to buy a ready-made masthead unit with its custom made weatherproof housing, saving your constructional efforts for the indoor amplifiers and associated equipment. Most aerial manufacturers have a range of amplifiers. If you'd like me to go farther into the subject of decibels and noise, let me know and I'll put something extra in the concluding part. Those interested in construction will find a number of suitable designs in previous issues of the magazine.

Service Notebook

G. R. Wilding

Avo Repairs

Tens of thousands of big Avos are used in the TV service trade alone. Their Bakelite cases are extremely tough, but even so from time to time one will get dropped once too often from too great a height and, though the meter movement may be unaffected, the case may crack or break. It happened to me recently when I caught one of the leads in the car boot lid – the instrument was torn from my hand and hit the road with such force that both the case and the window glass were broken. The meter continued to work on all ranges however so replacement parts plus a new set of leads were obtained from the Avo spares and repairs division – the London Instrument Repair Centre, Archcliffe Road, Dover, Kent. The charges are very reasonable, so it's worth knowing about this service.

After fitting the new glass and case we decided to repaint the range markings etc. which had become faint and discoloured. The drill is to completely scrape out all the old lettering, swamp the indented printing with a quick drying hard enamel, then wipe off the surplus with a non-fluffy piece of material. The enamel sold in miniature tins for model makers is usually quite effective. Avo do not supply paint for marking in but suggest using a white crayon, one


proprietary make being Stanol, made by the Cosmic Crayon Co. Ltd. and available from most large stationers etc. This is suitable for temperate climates but not in the tropics – nor, probably, the rear window ledge of a car at the height of the summer!

Ragged Verticals

No line or field sync on a set fitted with the Thorn 1400 chassis was found to be due to absence of voltage at the screen grid of the sync separator section of the 30FL1, the feed resistor being open-circuit. On replacing it the line lock was solid but the verticals all had a ragged edge – particularly noticeable on the test card. In most sets this would place suspicion on the line oscillator and flywheel sync circuits, but in these sets the cause can be a faulty e.h.t. tripler which can be quite blameless in other respects – i.e. full e.h.t. and no ballooning on increasing the brightness to a high level. On fitting a new tripler the ragged edge to the verticals completely disappeared.

Weak Line Sync

A Pye hybrid colour receiver (697 chassis) had good field but weak line sync. Now this is very often due to the 47kΩ pulse feedback resistor R203 to the flywheel sync diodes. The resistor and diodes, on the vertical line timebase panel, can be easily checked but proved to be o.k. The PCF802 line oscillator valve was the next suspect, and a replacement cured the trouble. Why not, as is the usual procedure, check the valve first? Well it's possibly more difficult to get at it in this chassis than is any valve in any modern set, so it pays to check the components previously mentioned first.

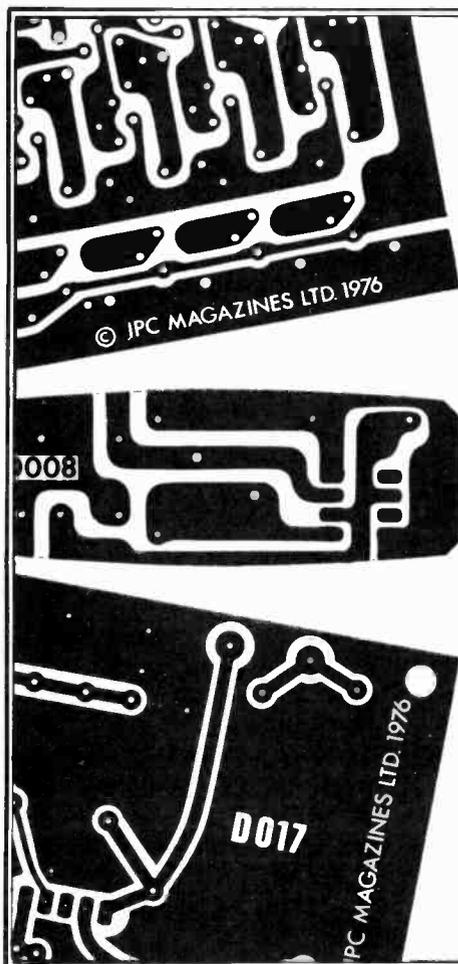

TELEVISION READERS PCB SERVICE

Issue	Project	Ref. no.	Price
April/May 1976	Video Effects Generator	DN0799A	£4.25
April/May 1976	Video Effects Generator-Fader only	DN0780A	£1.58
July 1976	Opto-coupled Audio Extractor	D001	£1.35
November 1976	Ultrasonic Remote Control	{ D007 } { D008 }	£2.95 per set
December 1976	IC Sound Circuits for the Constructor	{ D009 } { D017 } { D018 }	£1.25
Jan/Feb/March 1977	TV Pattern Generator	{ + u.h.f. } { mod. board }	£3.90 per set
March 1977	Teletext Decoder Power Supply	D022	£2.95
May 1977	Teletext Decoder Input logic	D011	£9.80
May 1977	Single chip SPG	D030	£3.00
June 1977	Wideband Signal Injector	D031	£0.65
June 1977	Teletext Decoder Memory	D012	£7.90

All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned. Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD. and not to the Editorial offices.

To:— Readers' PCB Services Ltd. (TV), P.O. Box 11, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:


Issue	Project	Ref.	Price
_____	_____	_____	_____
_____	_____	_____	_____
_____	_____	_____	_____

Prices include VAT and post and packing. Remittance with order please.

NAME _____

ADDRESS _____

Post Code _____

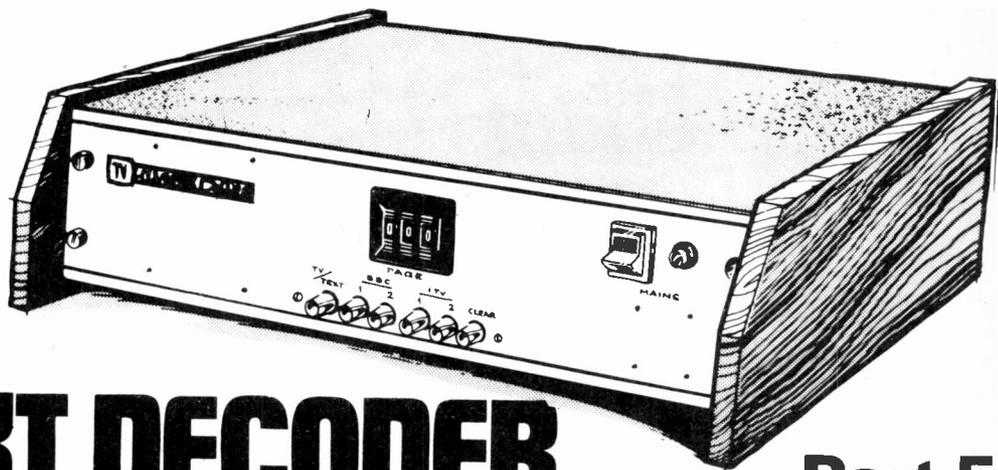

TELETEXT DECODER

Part 5

Steve A. MONEY T. Eng. (CEI)

HAVING selected the desired page of data from the incoming Teletext transmission and stored it in the memory card we now have to produce a display of the corresponding text on the television screen. This is the function of the third logic card.

Character Generation

The symbols displayed on the screen are made up from arrays of illuminated dots which are selected to give the shape of the desired symbol. In some Teletext decoders each character is displayed using an array of 35 dots arranged in seven horizontal rows of five dots each. When both upper and lower case letters are required however the array has to be made larger to cater for the descending tails of some of the lower case letters such as g and y. In addition, it's usual to leave one blank row of dots between successive rows of text in order to separate the rows and make them more readable. In the same way a single column of blank dots is usually included between adjacent characters to separate them. Allowing for these factors the total size of the dot array becomes six wide by ten rows high.

For convenience each horizontal row of dots in a row of text occupies one line scan. Thus a row of text uses ten lines and the whole page takes up 240 lines on the screen.

The complete set of characters used for Teletext, with the corresponding binary codes, are shown in Table 1. It will be seen that there are a total of 96 different letters, numbers and other signs.

To display a symbol the first thing we have to do is to convert the binary number obtained from the memory card into the corresponding pattern of dots needed to reproduce the required symbol on the screen. The most convenient way of achieving this is to have all the symbol dot patterns stored in a large memory array from which the desired dot pattern can be selected by applying the appropriate binary number to the memory address inputs. A large memory array such as this can be produced quite readily on a large scale integrated circuit. The dot patterns will be permanently built into the memory when it is made, i.e. the circuit is a Read Only memory or ROM. When this type of memory is used to store character dot patterns it is usually called a character generator ROM.

In the original prototype of the *Television* Teletext decoder the character generator used was a Signetics 2513. This produces only upper case letters plus the numbers and

signs. Some of the signs produced by the 2513 are different from those in the standard Teletext character set. The design of the display card has since been updated to use the Texas type X887 (SN74S262N) ROM which was designed for use with the Tifax Teletext module. This character generator provides all 96 Teletext characters, including the recently changed symbols, to exactly the Teletext specification.

A character generator device is arranged to give only one row of five dots at a time from the stored array. This fits conveniently with our television scan since we can display only one row of dots in the line of text during a line scan. On the next line scan the next lower row of dots in each of the character arrays will be traced out on the screen. The particular row of dots which has to be provided for each symbol array is determined by some form of counter operating from the line sync pulses.

Two sets of address signals are normally applied to the ROM. One selects the dot array and is controlled by the binary code of the character to be displayed. The second tells the ROM which row of dots in the character array is to be presented at the output, and is driven by the signal from the line scan counter as successive rows of dots for the line of text are scanned through on the screen.

Let us now look at the circuit operation and see how the character display is actually produced.

Circuit Operation

Fig. 1 shows the complete circuit of the display logic board.

To produce the dot patterns on the screen we start off with a dot clock generator which consists of the two monostable circuits of a 74123 (IC17) connected back-to-back to form a free-running oscillator.

One complete line scan period takes up $64\mu\text{s}$, but the part which is visible on the screen is usually only about $51\mu\text{s}$ or so (depending upon the setting of the width control). If we allow for margins at each side it is convenient to make the text display take up $40\mu\text{s}$ of the line scan. With 40 characters in a row of text this allows $1\mu\text{s}$ for each character space. If we assume six dots per character space, five for the symbol and one for spacing, the dot clock needs to be running at 6MHz. The frequency of oscillator IC17 is governed by RV2, R7, R8 and C8. Adjustment of RV2 will alter the frequency of the dot clock and can thus be used to alter the width of the text display.

To produce a centred display we need a blank margin at the top of the screen. Two 74177 counters, IC18 and IC19, control the size of this margin. When the field sync pulse occurs IC19 will be set at a count of five whilst the B, C and D sections of IC18 will all be set at 0. The A section of IC18 will be set at 1. Line sync pulses are applied to the input of IC19 so that the counters count off the line sync pulses. After 58 line pulses starting from the end of the field sync, stage D of IC18 goes to 1 whilst stage A goes to 0. The signal from A stops IC19 from any further counting action whilst the signal from stage D releases the dot clock circuits and allows the text display to start. This action produces the required blank margin at the top of the page display on the screen.

A second margin is needed at the left hand side of the screen to centre the display horizontally. This margin is produced by monostable IC16, which is triggered by every line sync pulse. When triggered, IC16 stops the dot clock generator for a period of about 17µs after the line sync pulse. This produces the blank margin at the left side of the screen. The width of this margin is controlled by RV1 which acts as a horizontal shift control for the text display.

To produce a clock pulse once for every character scanned on the screen, the dot clock is divided down by six in the 7492 counter IC12. This character clock is used to advance the memory card address circuits via output DCK, so that the next character to be displayed is selected from the memory ready for display.

The dot pattern from the character ROM IC2 is loaded in parallel into the eight bit shift register IC1 by the character clock pulse from the 7492. Once loaded, the dot pattern is shifted out of the register at the dot clock rate as a serial pattern of 1s and 0s which will form the video signal for the character display, producing the bright and dark dots on the screen. As the dot pattern for the symbol is clocked out of the register it is replaced by 0s and at the end

B4	B3	B2	B1	col row								
				B7	0	0	0	0	1	1	1	1
				B6	0	0	1	1	0	0	1	1
				B5	0	1	0	1	0	1	0	1
						1	2	3	4	5	6	7
0	0	0	0	0		sp	0	a	P	—	p	
0	0	0	1	1		!	1	A	Q	a	q	
0	0	1	0	2		.	2	B	R	b	r	
0	0	1	1	3		£	3	C	S	c	s	
0	1	0	0	4		\$	4	D	T	d	t	
0	1	0	1	5		%	5	E	U	e	u	
0	1	1	0	6		&	6	F	V	f	v	
0	1	1	1	7		,	7	G	W	g	w	
1	0	0	0	8		(8	H	X	h	x	
1	0	0	1	9)	9	I	Y	i	y	
1	0	1	0	10		*	:	J	Z	j	z	
1	0	1	1	11		+	;	K	←	k	1/4	
1	1	0	0	12		,	<	L	1/2	l	"	
1	1	0	1	13		-	=	M	→	m	3/4	
1	1	1	0	14		.	>	N	↑	n	÷	
1	1	1	1	15		/	?	O	#	o	■	

Table 1. Teletext text characters.

TMB643

of the character one of these is used to form the space between adjacent symbols.

Normally the page memory and the character ROM will take about 500 to 700µs to set up a new character dot pattern after the memory address has been changed. To allow for this delay the memory address is updated as soon as the pattern of dots for the current symbol has been loaded into the output shift register. By the time that character has been scanned on the screen the memory and ROM circuits will have the new dot pattern ready for the next character. The loading of the shift register is arranged to occur at the time it is providing the blank space between the characters, so that no part of the character pattern is lost during the loading operation.

To provide the row address for the character ROM the divide by ten counter IC15 is used. This counts off the line scans during the display of each row of text. The 7490 IC15 is set to zero during the upper margin period so that it always starts off from zero at the start of the first row of text in the page. At every tenth line scan a signal from the 7490 row counter is fed out via IC11d to produce a Row Clock (RCK) which updates the memory address circuits and selects the next row of text to be displayed.

After the 24th row of text has been scanned out on the screen an End of Page (EOP) pulse from the memory card resets IC18, which in turn stops the dot clock generator and blanks the rest of the field scan to produce the margin at the bottom of the page.

In order to ensure that the memory address circuits always start off from row 0 during a display scan a Row Address Clear signal is generated by IC18 and IC8d. This pulse occurs at line sync pulse number 42 after the field sync pulse and before the start of the text display. This makes sure that the header row (row 0) is always displayed at the top of the screen.

To ensure that the displayed text remains steady on the screen, the dot clock oscillator and character clock divider are both locked to the line sync pulses via the left margin generator IC16. If the dot clock generator is allowed to run free, the characters will have wavy edges as the dot frequency runs in and out of sync with the line scans.

The remainder of the display card logic is concerned with the generation of graphics and the blanking of the control codes, which must not be displayed on the screen. We shall examine these circuits next month and also deal with the construction of this card.

★ Display Card Components List

Resistors: All 1/4W 5%

R1	1kΩ
R2	4.7kΩ
R3	5.6kΩ
R4	5.6kΩ
R5	10kΩ
R6	10kΩ
R7	4.7kΩ
R8	4.7kΩ
RV1	10kΩ subminiature horizontal preset
RV2	1kΩ subminiature horizontal preset

Capacitors

C1	150pF polystyrene
C2	330pF polystyrene
C3	0.1µF ceramic disc
C4	0.1µF ceramic disc
C5	0.1µF ceramic disc
C6	2200pF polystyrene
C7	100µF 6V electrolytic
C8	10pF polystyrene

Integrated Circuits

IC1	74165
IC2	SN74S262N
IC3	74153
IC4	7474
IC5	7412
IC6	7402
IC7	7474
IC8	7400
IC9	7474
IC10	7408
IC11	7404
IC12	7492
IC13	7412
IC14	7473
IC15	7490
IC16	74121
IC17	74123
IC18	74177
IC19	74177

Miscellaneous

PCB type	DO13
Soldercon sockets.	

Diodes	
D1, 2, 3	0A91



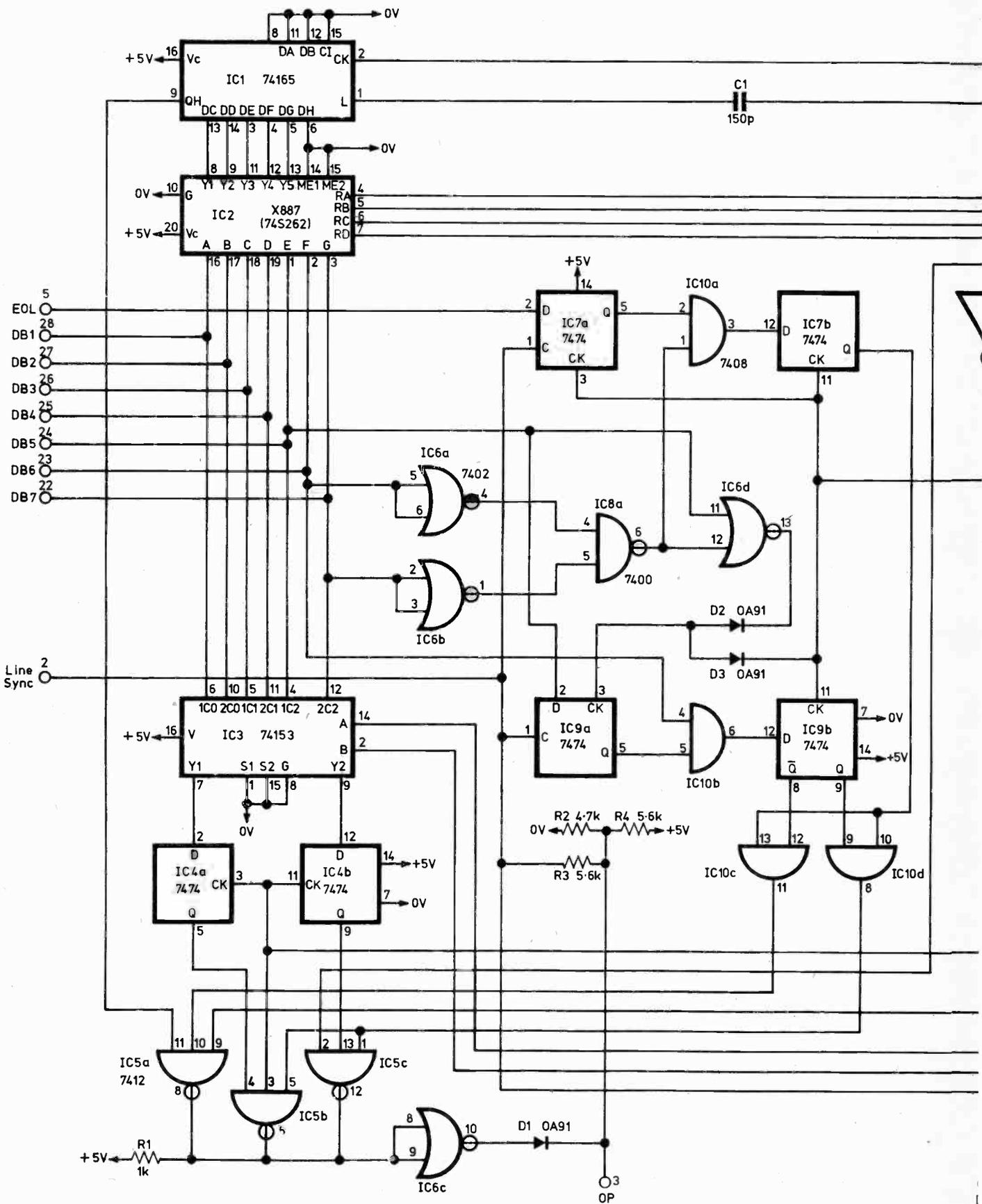


Fig. 1. Complete circuit diagram

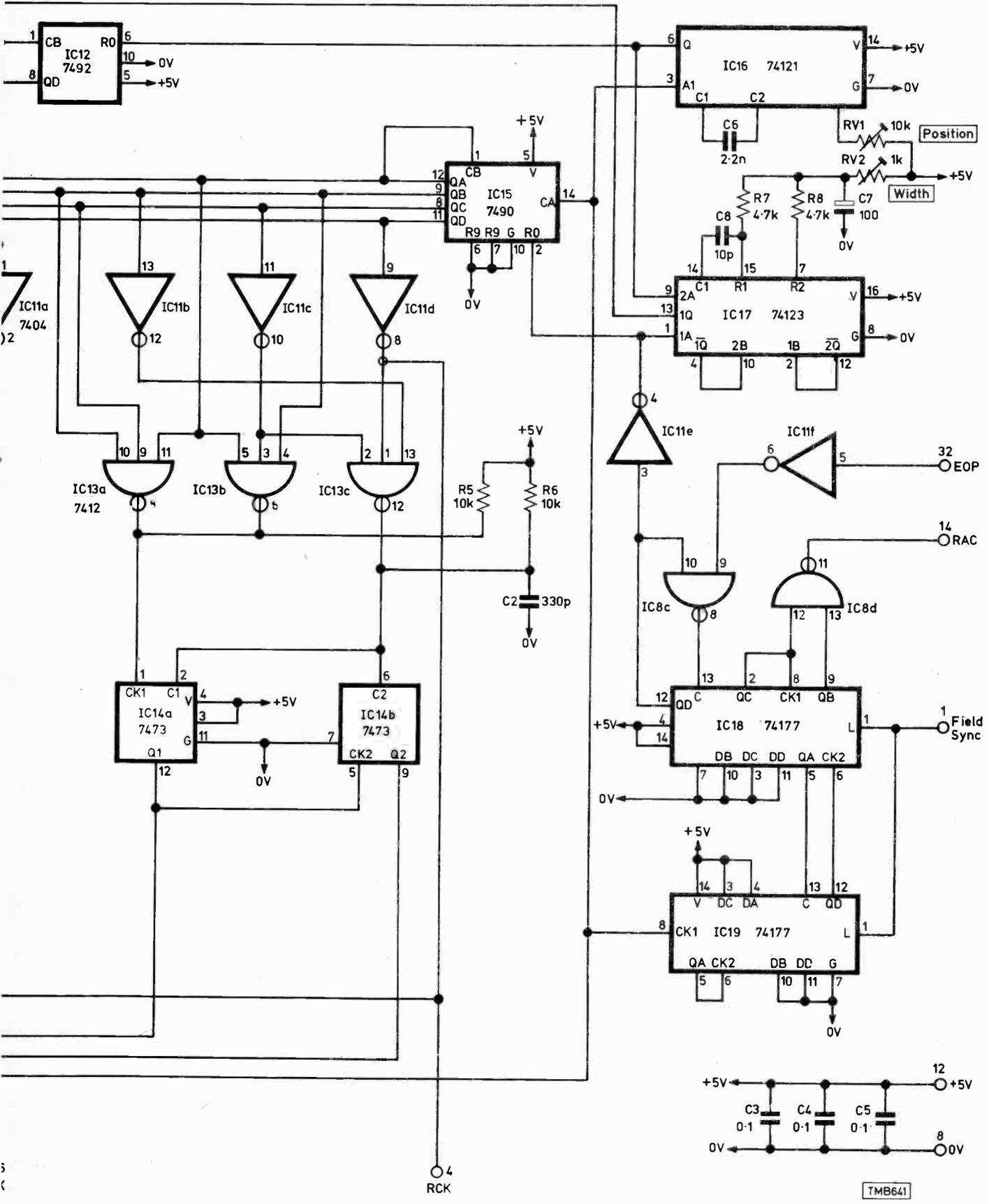

of the display logic card.

Your PROBLEMS solved

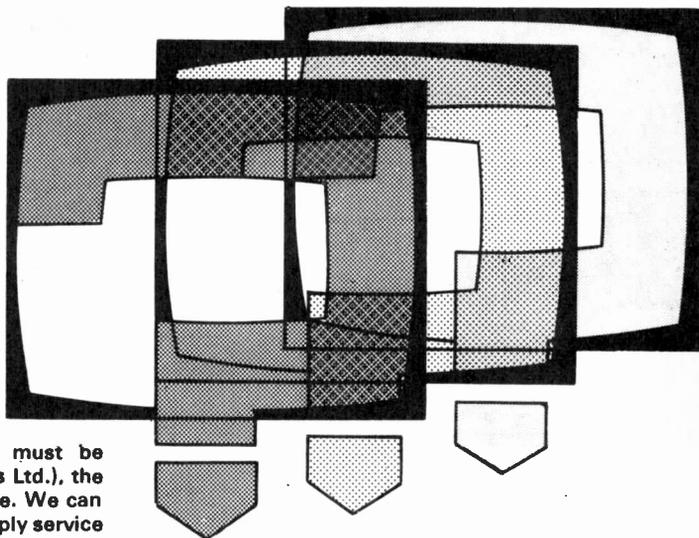

Requests for advice in dealing with servicing problems must be accompanied by a 50p postal order (made out to IPC Magazines Ltd.), the query coupon from page 497 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

THORN 1590 CHASSIS

There are white lines about three-quarters of an inch apart, from left to right diagonally, across the screen. The lines vary in intensity with changes in picture contrast. Any ideas for removing them?

The lines are caused by the field flyback appearing on the screen because it's not being blanked out. For field flyback blanking, a pulse is applied from the field output stage to the emitter of the video output transistor. There are two coupling components, C82 (0.1 μ F) and R114 (12k Ω). Either the capacitor is faulty or not connected, or the circuit is not completed electrically.

PHILIPS 210 CHASSIS

When the brightness or contrast controls are adjusted for a normal picture two pictures appear with a sideways wobble. On increasing or decreasing either control the raster returns to normal. All the line timebase valves and the sync/video valve have been replaced, and the components in the line oscillator, video and sync circuits checked.

There is a waveform shaping network from the control grid of the PL504 line output valve to chassis. It consists of 220pF (C2062) in series with 82k Ω (R2172). The trouble is likely to be due to the capacitor: try shunting another 220pF one across it.

THORN 3500 CHASSIS

The trouble with this set is wrong colours due to loss of green. Unfortunately the fault is intermittent, making fault finding awkward.

We have had several cases of intermittent loss of one colour on this chassis due to leakage across the switches connected to the sliders of the c.r.t. first anode preset controls. These are about half way up the left side of the convergence board. The green one is the centre one and it is a simple matter to cut the print under the switch (it can be joined up later) to prove whether the switch is responsible for the loss of first anode voltage, if indeed this is much lower than the red and blue first anode voltages – the drill is to check these voltages. If they are roughly the same, clearing this part of the circuit, check the green output transistor VT212 whose collector voltage, with no signal input, should be 160V. If this is in order check the green channel clamp diode W207.

GEC 2000 SERIES

The fault with this set is lack of width. Both the line output valve and the boost diode have been replaced without improving matters. On turning up the brightness, the picture balloons and goes out of focus, leaving a dark area in the centre of the screen even with the contrast control turned right up. Is the v.d.r. in the width circuit suspect?

The problem is poor e.h.t. regulation along with lack of width. The first suspect should be the DY86 e.h.t. rectifier – also make sure that the 0.4 Ω resistor in series with its heater is in order. The line output transformer could be defective but before condemning it we suggest you check the width control and its 470k Ω series resistor and the high-value resistors (3.3M Ω and 1M Ω) in the line output valve's control grid circuit. The v.d.r. could be at fault but this is not common.

THORN 3500 CHASSIS

There was about three quarters of an inch of foldover at the bottom of the picture. I got rid of this by adjusting the field timebase preset controls, but of course the linearity is now wrong.

The field charging capacitors C427 (25 μ F) and C428 (10 μ F) may be defective – as these charge up, the driver transistor is driven towards cut-off, C432 (250 μ F) which decouples the supply to the field output stage can also cause this problem. Finally, suspect the field output transistor VT424 (BD116).

DECCA 30 SERIES

The trouble with this set is that the h.t. fuse F1 keeps on blowing at switch on – accompanied by a slightly acrid smell. The PCF802 line oscillator valve glows brightly when this happens, but this might not be related to the fuse blowing.

If a cold resistance check does not reveal a short-circuit across the h.t. line, check the PL509 line output valve, the line output transformer tuning capacitor C435 (150pF) which is on the transformer assembly and the boost capacitor C436 (0.22 μ F) which is on the timebase panel. The PCF802 could be faulty, drawing excessive current and thus glowing and blowing the fuse: a leak in the pentode section's control grid coupling capacitor C427 (470pF) could have the same effect.

a must for your bookshelf

RADIO, T.V. & AUDIO TECHNICAL REFERENCE BOOK

NEW

Edited by S.W. AMOS

- * All the facts and data spanning the whole spectrum of Radio, TV and Audio.
- * Brings together 31 contributors, each one expert in his subject.
- * Aimed mainly at the technician who has to operate and maintain electronic equipment, the service man, and the amateur radio and audio enthusiast.
- * Extensive work containing:
 - 1172 pages
 - 94 photographs
 - 1150 drawings

CONTENTS

Fundamentals of Sound Transmission. Fundamentals of Television Transmission. Passive Components. Transmission Lines. Thermionic Valves. Electron Optics. Cathode-Ray Tubes. Picture Tubes. Camera Tubes. Semiconductor Devices. Basic Electronic Circuits. Modern Methods of Manufacture. Microphones. Loudspeakers. Disc Recordings and Reproduction. Magnetic Recording and Reproduction. High-Fidelity Amplifiers. Sound Studios and Studio Equipment. Sound Transmitters. Television Studios and Studio Equipment. Telecine, Video Tape and Video Disc Equipment. Television Transmitters. Radio-Wave Propagation. Antennas. Sound Receivers. Black-and-White Television Receivers. Colour Television Receivers. V.H.F. and U.H.F. Land-Mobile Radiotelephone Communication Equipment. Batteries. Rectifying and Converting Equipment. Transmitter Power Supplies and Cooling. Test Equipment. Transmitter Installation and Servicing. Sound Receiver Installation and Servicing. Television Receiver Installation and Servicing. Tape Recorder Installation and Servicing. Electrical Interference Suppression. Formulae and Equations. Appendix 1: Classifications of Emissions. Appendix 2: First Aid in Case of Electric Shock. Index.

ORDER NOW from your local bookseller or from
NEWNES-BUTTERWORTHS
Borough Green, Sevenoaks, Kent TN15 8PH

0 408 00259 X. 1172 pages. 222 x 141mm. £24.00

<p>TTLs by TEXAS</p> <p>7400 16p 74170 30p 741SOO 32p 74SOO 40p 7401 18p 7402 18p 7403 18p 7404 24p 74HO4 40p 7405 25p 7406 45p 7407 45p 7408 25p 7409 27p 7410 18p 741H10 30p 7411 28p 7412 28p 7413 36p 7414 96p 7416 35p 7417 40p 7420 18p 7421 43p 7422 27p 7423 36p 7425 33p 7427 40p 7430 18p 7432 34p 7437 37p 7438 37p 7440 18p 7441 85p 7442 75p 7443 130p 7444 130p 7445 108p 7446 108p 7447 90p 7448 90p 7450 18p 7451 18p 7453 18p 7454 18p 7460 20p 7470 32p 7472 32p 7473 36p 7474 37p 7475 48p 7476 37p 7480 54p 7481 108p 7482 85p 7483 95p 7484 103p 7485 130p 7486 36p 7489 340p 7490 30p 7491 90p 7492 55p 7493 43p 7494 96p 7495 75p 7496 90p 7497 340p 74100 116p 74104 60p</p>	<p>74105 60p 74107 36p 74109 70p 74110 55p 74111 80p 74116 220p 74118 90p 74120 95p 74121 32p 74122 53p 74123 73p 74125 70p 74126 76p 74128 90p 74132 76p 74136 81p 74141 85p 74142 300p 74145 90p 74147 275p 74148 173p 74150 135p 74151 77p 74153 92p 74154 164p 74155 97p 74156 97p 74157 96p 74158 160p 74159 220p 74160 120p 74161 120p 74162 120p 74163 120p 74164 130p 74165 150p 74166 136p 74167 340p 74170 250p 74173 160p 74174 130p 74175 92p 74176 130p 74177 130p 74180 118p 74181 324p 74182 88p 74185 144p 74186 995p 74190 155p 74191 160p 74192 130p 74193 130p 74194 130p 74195 104p 74196 130p 74197 130p 74198 214p 74199 214p 74201 175p 74251 151p 74265 97p 74278 314p 74279 151p 74283 205p 74290 162p 74293 162p 74298 216p 74365 162p 74366 162p 74390 216p 74393 243p</p>	<p>C-MOS ICs</p> <p>4000 21p 4001 21p 4002 21p 4006 110p 4007 22p 4009 67p 4011 21p 4012 21p 4013 55p 4014 110p 4015 120p 4016 54p 4017 110p 4018 120p 4019 54p 4020 95p 4022 100p 4023 21p 4024 75p 4025 21p 4026 220p 4027 81p 4028 152p 4029 120p 4030 59p 4040 130p 4042 90p 4043 100p 4046 150p 4047 110p 4049 68p 4050 54p 4055 120p MC1351P 104p MC1358P 195p MC1495 370p MC1496 115p MC3340P 160p MFC4000B 90p NE504L 175p NE555 40p NE556 90p NE561 425p NE562 425p NE565 200p NE566 200p NE567 200p SG3402N 275p SL432A 475p SL437F 960p SL901B 520p SL917A 675p SL918A 760p SN72710N 45p SN72733N 150p SN76003N 150p SN76008 275p SN76013N 175p SN76018 275p SN76023N 175p SN76033N 275p SN7660N 90p TAA350 205p TAA570 240p TAA621A 275p TAA661B 150p TBA120 75p</p>	<p>OP AMPS</p> <p>1458 75p 301A 40p 3130 100p 3140 105p 3500 70p 7097 30p 741 25p 747 70p 748 40p</p> <p>Linear ICs</p> <p>AY-1-0212 650p CA3028A 112p CA3046 85p CA3048 275p CA3053 75p CA3080 97p CA3089E 250p CA3090AQ 500p LM318N 175p LM380 115p LM381 190p MC1310P 200p MC1330P 102p MC1351P 104p MC1358P 195p MC1495 370p MC1496 115p MC3340P 160p MFC4000B 90p NE504L 175p NE555 40p NE556 90p NE561 425p NE562 425p NE565 200p NE566 200p NE567 200p SG3402N 275p SL432A 475p SL437F 960p SL901B 520p SL917A 675p SL918A 760p SN72710N 45p SN72733N 150p SN76003N 150p SN76008 275p SN76013N 175p SN76018 275p SN76023N 175p SN76033N 275p SN7660N 90p TAA350 205p TAA570 240p TAA621A 275p TAA661B 150p TBA120 75p</p>	<p>TBA480Q 200p TBA570 145p TBA641B 300p TBA651 275p TBA800 100p TBA810 125p TBA820 100p TDA2020 400p ZN414 140p AC125 20p AC126/7 20p AC128 20p AC141/2 20p AC176 20p AC187/8 20p AC187K 25p AC188K 25p AD149 58p AD161/2 32p AF114/5 22p AF116/7 22p AF124 36p AF127 36p AF139 43p AF239 48p BC107/8 10p BC158/9 12p BC109/C 11p BC147/8 9p BC149/C 10p BC157 11p BC158/9 12p BC169C 16p BC172/8 12p BC177/8 20p BC179 20p BC182/3 12p BC184 14p BC187 32p BC122 14p BC213 12p BC214 16p BC337 27p BC338 27p BC378 32p BC470 20p BCY70 24p BD115 90p BD131 40p BD132 43p BD135 54p BD136 55p BD139 56p BD140 44p BDY56 225p BF115 24p BF173 25p BF178 27p BF179 40p BF179 40p BF180 40p BF184 30p BF194/5 12p BF196/7 18p BF200 40p BF244 40p BF257/8 36p BF336 32p BF337 32p BF338 34p BFR39/40 34p BFR79/80 34p</p>	<p>BFR88 40p BFX29/30 34p BFX84/85 30p BFX86/7/8 30p BFY50 18p BFY51 16p BFY52 18p BRV39 45p BSX19/20 20p BU105 175p BU108 31p MJ2955 130p MJE340 45p MJE2955 130p MJE3055 97p MFF102/3 40p MPSU56 98p MPSA06 37p MPSA12 61p MPSA56 37p MPSU06 78p MPSU56 98p OC75 79p OC35/36 79p OC171 25p R2008B 225p R2101B 225p TIP29A 52p TIP29C 62p TIP30A 60p TIP30C 72p TIP31A 56p TIP31C 56p TIP32A 63p TIP32C 85p TIP33A 97p TIP34A 124p TIP35A 243p TIP35C 290p TIP36A 297p TIP36C 360p TIP41A 70p TIP42A 84p TIP42A 76p TIP42C 96p TIP2955 76p TIS43 40p TIS93 30p ZTX108 12p ZTX300 16p ZTX500 20p 2N697 25p 2N698 40p 2N706/8 22p 2N918 43p 2N930 19p 2N1131/2 25p 2N1304/5 54p 2N1306/7 54p 2N1613 22p 2N1711 22p 2N1893 32p 2N2160 99p 2N219 22p 2N222 22p 2N2369 15p 2N2484 32p 2N2646 48p 2N2904/A 22p 2N2905/A 22p 2N2906/A 24p 2N2926RB 9p</p>	<p>2N29260YG 11p 2N3053 20p 2N3054 54p 2N3055 54p 2N342 51p 2N3702/3 14p 2N3704/5 14p 2N3706/7 14p 2N3708/9 14p 2N3733 320p 2N3819 27p 2N3820 50p 2N3823 54p 2N3866 95p 2N3904/5 22p 2N3906 25p 2N4060 11p 2N4123/4 22p 2N4125/6 22p 2N4401/3 34p 2N4427 97p 2N4871 64p 2N5296 65p 2N5457/8 40p 2N5459 40p 2N627 60p 2N6107 70p 2N6247 200p 2N6254 140p 2N6292 70p 3N128 97p 3N140 105p 3N141 97p 3N187 200p 40361/2 45p 40409/10 65p 40411 325p 40594 90p 40595 97p 40673 70p</p>	<p>VOLTAGE REGULATORS (Plastic) Fixed</p> <p>1 Amp +ve 5V 7805 130p 12V 7812 130p 15V 7815 130p 18V 7818 150p 24V 7824 150p</p> <p>1 Amp -ve 5V 7905 200p 12V 7912 200p 15V 7915 200p 18V 7918 200p 24V 7924 200p</p>	<p>TELETEXT DECODER <i>(as being featured in current issue)</i> SPECIAL OFFER TO CONSTRUCTORS AT REDUCED PRICES:- COMPLETE SEMICONDUCTOR KIT Comprising Voltage Regulator ICs, TTLs, MOS ICs (RAMs & ROMs), Diodes, Rectifiers, and Low Profile DIL Sockets (all devices as specified in the product). Please send SAE for details. First Grade Branded Products Only</p>	<p>Miscellaneous</p> <p>BYZ 13 55p 1A DIL Bridge 40p 10000uF 16V Cap. 250p Transformer E6 7805/12 130p 2102 RAM 220p 14 pin Skt 13p 16 pin Skt 14p</p>	<p>MEMORY BOARD</p> <p>7 - 2102 2 - 74175 1 - 74157 4 - 74177 1 - 7400 1 - Transistor</p> <p>All devices by TEXAS INSTRUMENTS available as a kit for £20.20 inc.</p> <p>Power Supply Unit Kit £19.00 inc. Input Logic Card Kit £14.25 inc.</p> <p>Above kits contain all the components listed in each article (except PCBs).</p>
---	---	---	--	--	--	---	--	---	---	--

PHILIPS 320 SERIES

Sometimes when the set is switched on there is a white raster with black specs on the screen instead of a picture, and a loud rushing noise on the sound. By rotating the channel selector to another channel, usually BBC-2, then back again normal results are obtained. Also a slight background noise occurs, with a small drop in the volume level, after about twenty minutes. This can be cleared by rotating the selector to another channel and back again or by moving the fine tuner slightly – it may be necessary to do this several times before the set settles down.

In some sets the tuning range control R2114 is changed to a 1.5k Ω fixed resistor, with a 27k Ω resistor (R2115) added in series with the tuning voltage feed to the tuner, i.e. between pin 4 of plug B and the junction of C2104/pin F of the tuner. See that this is so in your tuner, and set the h.t. rail to 158V. If the trouble continues, check the 22k Ω resistor R2111 from HT1 to the tuning voltage circuit and the TAA550 regulator. If these items are in order, replace the tuner.

THORN 3000 CHASSIS

The picture keeps pulling (jerking) to the side at irregular intervals. As it pulls to the side colour is lost and the picture often breaks up completely for a few seconds. The fault developed gradually over several weeks – at first there were periods of several days between jerky spells but the fault is now there almost constantly. Adjusting the line hold control gives some improvement but this lasts for only a few seconds or minutes.

The symptom is called line twitch and can be caused by several components on the line-timebase board. In order of likelihood these are as follows: the two 22 μ F electrolytics C506 and C511 in the flywheel filter and reactance transistor circuits, the flywheel sync discriminator diodes W501 and W502, the supply line decoupler C508 (100 μ F), and the reactance transistor VT501 (BC183LA).

BUSH TV161 SERIES

Once the picture has come on the field starts to run at a very fast speed. After a further four minutes or so the set will lock, remaining stable except on very dark scenes.

A failing PCL805 field timebase valve is the most common cause of this symptom. Other possibilities are: the interlace diode 3MR3, the field sync pulse coupling capacitor 3C29, and the PFL200 video/sync valve and its associated screen grid and cathode decoupling electrolytics 2C48 (8 μ F), 2C44 (10 μ F) and 2C45 (320 μ F).

GRUNDIG 5011GB

About a quarter of an hour after switching on there is a pronounced whistle, lasting for perhaps half an hour. A vertical bar, slightly brighter than the overall picture brightness and approximately half an inch wide, frequently appears to the left of centre on the screen.

There is a clip on the top of the input/commutating transformer 9245-834-21 in the line output stage. Check that this is secure and that the cores of the other wound components in the line output stage are neither cracked nor loose. Check Tr506 (BF259) which drives the width stabilising transducer, and the associated diodes, particularly Di504 (1N4004) which is in series with the transducer.

THORN 1590 CHASSIS

The problem is that the 2.5A fuse between the rectifiers and the regulator blows when the set is switched on – the 250mA mains fuse remains intact. I take it there is a short-circuit somewhere but everything seems to be in order.

Towards the right side there is a large metal heatsink with the AU113 line output transistor mounted on it. The transistor is secured by two nuts and screws. Only one screw and nut is in actual contact with the print. Remove these, thus isolating the transistor's collector, then check whether the fuse still blows. If it doesn't, check the transistor for a collector-emitter short. If the transistor is all right check the two rectifiers W13 and W14 which are fed from the line output transformer. If one of these is found to be short-circuit check its reservoir capacitor, C110 (10 μ F) and C111 (1 μ F) respectively.

GEC HYBRID COLOUR CHASSIS

The problem with this set is that line hold is lost after two-three hours and by this time the hold control is at the end of the track. There is also tearing and bending of the top verticals at intervals. If the set is allowed to cool down the control and the set operate normally.

The items to check are the PCF802 line oscillator valve, C508 (4 μ F) which decouples the supply to the oscillator, the line sync discriminator diodes D500a/b, R503 which is in series with the hold control and R502 which is in series with its slider, the sync separator's collector resistors R500 and R501, and the reference pulse feedback resistor R507. The process could be speeded up by heating the individual items with a hairdryer and rapidly cooling with a freezer aerosol.

PHILIPS 210 CHASSIS

The sound behaves oddly on this set. After switching on, the sound appears just after the vision on 625 lines but takes six minutes to appear on 405 lines. When the set has been operating for a while switching from 405 to 625 is normal but on switching from 625 to 405 lines there is a delay of about thirty seconds in the appearance of the sound. I've changed the sound output valve and probed for dry-joints, but nothing has come to light.

Fixed bias is applied to the first sound i.f. transistor on 625 lines, but on 405 lines the transistor is biased by an amplified a.g.c. feed which comes from the cathode of the triode section of the PCL82 audio valve. When this valve is operating normally there should be 2.1V across the triode's cathode bias resistor R2099. It's anode load resistor R2101 should have a value of 100k Ω , giving 135V at the anode. Also check the cathode decoupler C2020 (25 μ F) and R2090 (1M Ω) via which the triode's control grid is returned to chassis on 405 lines.

KB VC1 CHASSIS

This set works well on 405 lines but on switching to 625 lines the field collapses, leaving a horizontal white line across the screen. The system switching seems to be o.k. and the scan coils and field output valve have been checked by substitution.

On 625 lines an extra preset height control R147 (300k Ω) is added in the feed from the boost rail to the field charging circuit. Check this control, which is second from the right at the back of the set.



An HMV Model 2701 (Thorn 2000 chassis) was giving a predominantly red display which could not be fully corrected by adjusting the appropriate presets. This chassis, like the KB CK500 in last month's Test Case, uses primary-colour drive to the tube cathodes (in fact it was one of the first receivers to use this sort of drive). It differs in detail from the KB chassis in that a colour-difference preamplifier is employed while the primary-colour matrixing occurs in the lower transistor in each of the cascode output stages. Video gain for each colour is controlled by a preset between the output of the colour-difference preamplifier (VT7/VT8 in the red channel, see Fig. 1), and the emitter of the matrixing transistor, to whose base the luminance signal is applied. Clamping is by a transistor whose base is driven by +30V line pulses. The transistor is VT9 in the red channel.

Red video bias is controlled by a preset (R42) in the clamp transistor's base circuit. There is also a tint control which provides a differential change in the clamp transistor biasing between the red and blue channels.

Tests revealed that the c.r.t.'s red cathode was below the correct voltage, meaning that there was excessive drive to the c.r.t.'s red gun.

Standing bias is applied to the clamp transistor base from a potential divider circuit consisting of R41, R42, R44 and R45. The voltage at the junction of R44/R45 is coupled to the base of VT9 via W4 and the parallel combination W3/R40. R45 and C20 at the bottom of the potential divider chain provide a time-constant for the clamping action. The bias for VT7 provided by the clamp action is developed across C18.

Having in mind the general circuit round the troubled area, have you any idea of the component most likely to be responsible for the symptom? See next month's Television

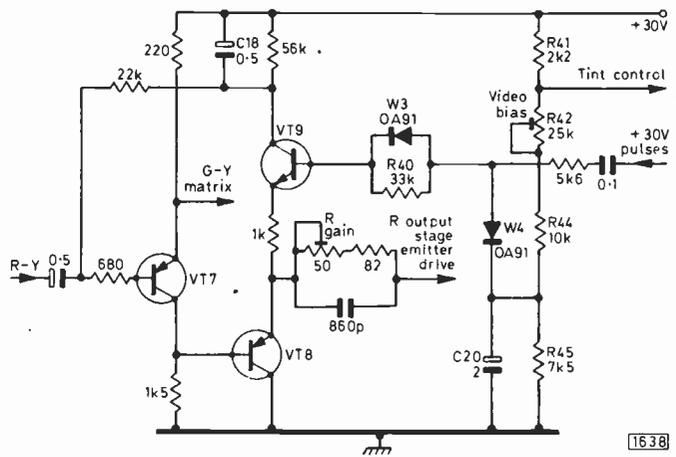


Fig. 1: R-Y preamplifier and clamp circuit used in the Thorn 2000 dual-standard colour chassis. The clamp transistor VT9 is cut off except when a 30V line frequency clamp pulse appears at its base, VT8 conducting via the cascode pair of transistors in the R output stage. When VT9 conducts, C18 is charged to the potential at the junction of R44/R45, set by the video bias control R42. The voltage on C18 sets VT7's base bias and the conditions in the following d.c. coupled stages.

for the solution and for a further item in the Test Case series.

SOLUTION TO TEST CASE 174 (page 441 last month)

The Test Case report last month included two clues to the cause of the fault. One was that it was the background of the display which was tinted. The other was that the primary-colour signal, after the matrix stage, was capacitively coupled to the blue driver stage.

By using a colour-bar generator and checking the amplitude of the blue signal at various points from the matrix to the tube's blue gun cathode it was found that the amplitude of the signal was greater at the matrix stage output than at the input to the blue driver stage. The coupling here is by a 2.2μF capacitor (C187d). This was found to have an intermittent fault, falling in capacitance as the temperature increased. Replacing the capacitor restored the blue drive and allowed the blue drive preset to be set more towards the centre of its range.

QUERY COUPON

Available until 18 July 1977. One coupon, plus a 50p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 494.

TELEVISION JULY 1977

Published on approximately the 22nd of each month by IPC Magazines Limited, Fleetway House, Farringdon Street, London EC4A 4AD. Filmsetting by Pacesetters, London SE1. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R ONE. Sole Agents for Australia and New Zealand - Gordon and Gotch (A/sia) Ltd.; South Africa - Central News Agency Ltd. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

TELEVISION TUBE SHOP

NEW TUBES AT CUT PRICES

A28-14W Equivalent.....	£17.95
A31-410	£16.95
AW59-91/CME2303	£15.50
CME1201/A31-18W	£13.50
CME1220/A31-120W	£15.95
CME1420/A34-100W	£16.50
CME1520/A38-160W	£17.50
CME1601/A40-11W	£12.50
CME1602/A40-12W	£13.50
CME1713/A44-120	£17.50
CME1906/A47-13W	£12.50
CME2013/A50-120	£17.95
CME2306/A59-13W	£14.50
CME2313/A59-23W	£18.95
CME2413/A61-120W	£18.95

SPECIAL OFFER

FOR K.B. FEATHERLITE VC11 TSD282/217..... £7.50

JAPANESE etc. TUBES

9AGP4 Equivalent	£17.50
190AB4	£15.00
190CB4	£15.00
230ADB4	£14.50
230DB4/CT468	£15.95
CT507	£17.50
240AB4A	£12.00
310DMB4/DGB4	£15.50
310DWB4/DJB4	£15.50
310EUB4	£19.50
310EYB4	£16.50
310FXB4 Equivalent.....	£15.95
310GNB4A	£25.19
340AB4	£19.50
340AYB4	£22.00
340CB4	£19.95
340RB4	£19.95
340AHB4	£24.50

COLOUR TUBES	
A47-342X	£75.00
A49-191X/120X	£52.00
A51-220X/510DJB22.....	£59.00
A56-120X	£62.00
A56-140X/410X	£55.00
A66-120X	£75.00
A63-11X/120X	£69.50
A67-120X	£77.00
A66-140X/410X	£55.00

ALL TUBES GUARANTEED 12 MONTHS

CARRIAGE:

Mono £1.50. Colour £2.50
N. Ireland £4.00

ADD VAT TO ALL PRICES

TELEVISION TUBE SHOP

52 BATTERSEA BRIDGE RD., LONDON, SW11. Tel. 228 6859.

WE GIVE GREEN SHIELD STAMPS

SOUTHERN VALVE COMPANY

Upper Floor, 8 Potters Road, New Barnet, Herts.

Telephone: 01-440/8641.

MAIL ORDER ONLY

MINIMUM ORDER 65p

ALL NEW & BOXED, "QUALITY" BRANDED VALVES GUARANTEED 3 MONTHS. BVA ETC. (TUNGSRAM ETC.).

NOTE:

PLEASE VERIFY CURRENT PRICES.

8% ALLOWED IN LIEU OF GUARANTEE! ALREADY DEDUCTED FROM OUR PRICES!

AZ31 80p	EL509 £2.75	PCL82 40p	UBF89 40p
DY86/7 39p	EM84 50p	PCL83 POA	UCC85 46p
DY802 50p	EY51 50p	PCL84 48p	UCH42 72p
EB91 18p	EY86/7 38p	PCL85 } 45p	UCH81 45p
ECC81 36p	EY500A £1.60	PCL86 } 45p	UCL82 45p
ECC82 36p	EZ80 39p	PCL86 60p	UCL83 58p
ECC83 36p	EZ81 38p	PCL200 £1.40	UF41 70p
ECC85 40p	GY501 £1.10	PD500 £3.25	UF89 45p
ECC88 50p	GZ30 70p	PFL200 73p	UL41 75p
ECH42 80p	PC86 63p	PL36 70p	UL84 45p
ECH81 44p	PC88 63p	PL81 50p	UY85 40p
ECH83 82p	PC97 67p	PL81A 55p	U25 60p
ECH84 58p	PC900 50p	PL82 35p	U26 60p
ECL80 52p	PCC84 35p	PL83 50p	U191 50p
ECL82 48p	PCC85 44p	PL84 48p	6/30L2 75p
ECL83 68p	PCC88 62p	PL500 } 68p	6B/7 75p
ECL86 80p	PCC89 50p	PL504 } 60p	6F23 60p
EF80 33p	PCC189 53p	PL508 £1.10	6F28 70p
EF85 38p	PCF80 41p	PL509 £2.10	6V6 & 6L6 99p
EF86 52p	PCF82 45p	PL519 £2.80	10F1 68p
EF89 39p	PCF86 58p	PL802 £2.10	20L1 70p
EF183 40p	PCF200 99p	PY33 50p	20P4 70p
EF184 40p	PCF801 50p	PY81/3 40p	30C1 41p
EH90 50p	PCF802 57p	PY88 50p	30C15 78p
EL34 £1.10	PCF805 £1.45	PY800 50p	30C17 78p
EL41 70p	PCF806 75p	PY801 50p	30C18 £1.45
EL84 39p	PCF808 £1.45	PY500 } 50p	30F5 50p
EL90/1 47p	PCH200 85p	PY500A } £1.30	30FL1 £1.00

Correct only at time of going to press.

Some leading makes available.

VAT invoices issued on request.

We offer return of post service.

CWO ONLY. No C.O.D.

Post free over £15.

£6 to £15 - 75p (max.)

Items in stock at time of going to press but subject to possible market fluctuations if unavoidable.

ENQUIRIES WELCOMED FROM TRADE & RETAIL (same prices)

EMO - EUROSONIC

• ALL SPARES READILY AVAILABLE

• PANEL REPAIR SERVICE

PLUS ALMOST ANY OTHER T.V. COMPONENT supplied by return "off the shelf" e.g. LOPTX - EHT trays - droppers - osc coils - switches - cans - smoothers - speakers etc. etc.

PLUS a host of special components (the ones you can wait weeks for) for all British T.V.'s + Teleton + Grundig.

TELEPART (WTON) THE TELECENTRE, WORCESTER ST., WOLVERHAMPTON (0902) 772293

FAIRCREST TUBES

THE BEST IN REGUNNED TELEVISION CATHODE RAY TUBES

2 or 4 year guarantee on all tubes

OR

REGUN YOUR OWN TUBES!

Equipment, supplies, spares, pumps, ovens
TRAINING

Sales Office: 1 Mayo Road, Croydon, CR0 2QP

01-684 9917

MAIL ORDER ONLY

NO CALLERS.

PHILIP H. BEARMAN

6 & 8 POTTERS ROAD, NEW BARNET, HERTS. Tel: 01-449 1934/5

NEW COLOUR TUBES

New tubes, fully tested

NEW MONO TUBES

Carriage £3.00		
EXPORT	A44/271X	£55.00
ENQUIRIES	A49/191X }	£52.50
WELCOMED	A49/192X }	
PPICES	A51/110X }	£65.00
CORRECT	510DNB22 }	
AT TIME OF	A56/120X	£65.00
GOING TO	A63/11X	£75.00
PRESS	A63/200X	POA
SHORT SEA	A66/120X	£82.50
JOURNEY £1	A67/120X	£89.50
EXTRA.	A67/150X	£89.50

One year guarantee. (Add £9.00 for 4 years where available)

NOTE:

All prices subject to alteration due to market fluctuations and inflation.

110° prices usually as above. £5 allowed on old colour tube.

Occasionally seconds available cheaper, enquiries welcomed.

SPECIAL NOTE

NEW MONO

TUBES AVAILABLE

A31/410W £18.00* |

CME1220/A31.120 £18.00* |

CME1420/A34.120 £19.50* |

CME1520/A38.160 £21.00* |

CME1713/A44.120 £21.00* |

CME1913/A47.26WR £21.00* |

Limited stocks

2 year guarantee

MAZDA, TOSHIBA, USA, ETC.

OTHERS AVAILABLE SHORTLY.

* £1 less } 1 year

† £2 less } g'tee

Carriage £1.50

MW31/74 £3.00 |

14" except 110° £5.00 |

12"/14" 110° Prices as per centre column. |

A47/14W £11.50 |

AW47/91 rebuilds £7.50 |

(1 year guarantee)

limited stocks.

A50/120WR £18.00 |

A61/120WR £21.00 |

A59/23WR £22.50 |

A59-23WR £22.50 |

Others often available.

£1 less for one year guarantee.

Mostly two year guarantee.

SAE with enquiries please.

Prices include VAT.

TV's

TV's

TV's

ATTENTION Southern Ireland Dealers

Large stocks of used colour and mono available. Ferguson, Bush, Pye, Philips and Sobell. Colour from £110.00 working. Mono from £16.00 each.

All prices include V.A.T.
All cabinets polished.
Delivery can be arranged.
Representative will call on request.
Fresh stocks weekly.

T.V. Wholesale Dist. Ltd.
EDI House,
Kylemore Park West,
Industrial Estate,
Dublin 10.
Tel: 364139.

VALVE BARGAINS

ANY 5-64p, 10-£1.10, 50-£5.00.
YOUR CHOICE FROM THE LIST BELOW:
ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL86, PCL805, PL504, PY81/800, PY88, 30PL14, 6F28.

COLOUR VALVES - PL508, PL509, PL519, PY500/A. ALL TESTED, 35p EACH.

TELEVISION AERIAL SPLITTERS, 2 WAY. INSIDE TYPE. £1.50.

PRESS BUTTON UHF TUNERS - 4 BUTTON TRANSISTOR - BRITISH MADE - £2.50 EACH.

AERIAL BOOSTERS

AERIAL BOOSTERS CAN PRODUCE REMARKABLE IMPROVEMENTS ON THE PICTURE AND SOUND, IN FRINGE OR DIFFICULT AREAS.

B11 - FOR THE STEREO AND STANDARD VHF/FM RADIO.
B12 - FOR THE OLDER VHF TELEVISION - PLEASE STATE CHANNEL NUMBERS.

B45 - FOR MONO OR COLOUR THIS COVERS THE COMPLETE UHF TELEVISION BAND.

ALL BOOSTERS ARE COMPLETE WITH BATTERY WITH CO-AX PLUGS & SOCKETS. NEXT TO THE SET FITTING. £3.80.

250,00

Capacitor Clearance Sale

ALL MULLARD C280 AND C281 RANGE OF POLYESTER FILM CAPACITORS 250 AND 400 VOLTS WORKING. VERY GOOD MIXED SELECTION OF VALUES FROM .01µf TO 1.5µf.

PRICE 100-£1.50, 500-£7.00,
1000-£12.00.

ALL PRICES INCLUDE VAT. P&P 20p PER ORDER. PLEASE SEND UNCROSSED P.O. OR CHEQUES FOR RETURNING IF WE ARE OUT OF STOCK OF CAPACITOR BARGAIN PACKS.

ELECTRONIC MAILORDER LTD,
62 BRIDGE STREET, RAMSBOTTOM, BURY, LANCs.
TEL: RAMS (070 682) 3036.

ENGINEERS

FREE



YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44 page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

CHOOSE A BRAND NEW FUTURE HERE



Tick or state subject of interest.
Post to address below.

- | | | |
|--|---|---|
| <input type="checkbox"/> ELECTRICAL ENGINEERING City & Guilds Wiring and Installations | <input type="checkbox"/> RADIO & TV Colour TV Servicing C & G Radio, TV & Electronic Mechanics | <input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Draughtsmen & Designers |
| <input type="checkbox"/> C. G. Electrical Tech-Primary Gen. Electrical Eng. | <input type="checkbox"/> Gen. Radio and TV Eng. Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> General Draughtsmanship Architectural Draughtsmanship Technical Drawing |
| <input type="checkbox"/> AERONAUTICAL ENGINEERING Air Registration Board Certificates | <input type="checkbox"/> Practical Radio & Electronics (with self-build kit) Radio Amateurs' Exam | <input type="checkbox"/> CONSTRUCTION & BUILDING Institute of Building Construction |
| <input type="checkbox"/> Gen. Aero Engineering | <input type="checkbox"/> ELECTRONIC ENGINEERING Gen. Electronic Eng. Practical Electronics (with kit) | <input type="checkbox"/> Surveyor's Inst. Clerk of Works Diploma C. & G. Building Quantities |
| <input type="checkbox"/> AUTO ENGINEERING City & Guilds Auto Engineering Practice Inst. Motor Industry | <input type="checkbox"/> M.A.A./I.M.I. Management Diploma Gen. Auto Engineering | <input type="checkbox"/> General Building General Civil Eng. Heating, Ventilating & Air Conditioning |
| <input type="checkbox"/> Auto Diesel Maintenance Motor Mechanics Service Station and Garage Management | <input type="checkbox"/> REFRIGERATOR SERVICING MECHANICAL ENGINEERING Society of Engineers | <input type="checkbox"/> Carpentry & Joinery Painting & Decorating Plumbing |
| <input type="checkbox"/> TELECOM-MUNICATIONS City & Guilds Telecommunications | <input type="checkbox"/> Inst. Engineers and Technicians General Mechanical Eng. Welding Maintenance Eng. General Diesel Eng. | <input type="checkbox"/> C.E.I. (Part 1) Inst. Cost Management Accountants Works Management etc. etc. |



G.C.E.

- 58 'O' & 'A' Level Subjects
- over 10,000 Group Passes!

Aldermaston College

Dept. TTV 14, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals).....


ADDRESS.....

..... Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

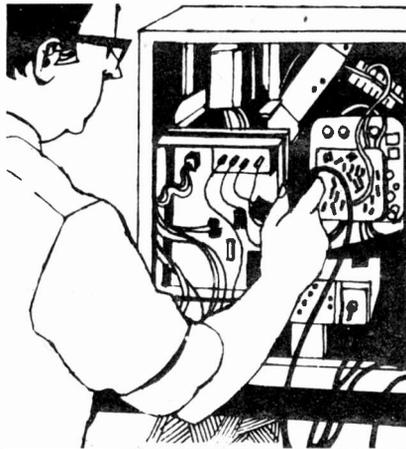HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



SETS & COMPONENTS

COLOUR T.V.'s FROM £20 + VAT

BUSH, GEC, PHILIPS, DECCA, PYE, Etc.
19", 22", 25", 26"
SINGLE AND DUAL STANDARD.
GOOD SELECTION SURPLUS TUBES,
PANELS, CABINETS, TUNERS, Etc.

Free details:
"REVELEC"
128, ANSLY COMMON, NUNEATON.
Phone: 0203-394315.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

COLOUR TV PANEL REPAIR SERVICE

Thorn - Full Range, RBM - Full Range, Philips, Pye, Invicta - Full Range, GEC - Full Range, Decca - Full Range, Etc.

90 Day Guarantee on all Repairs.
Same Day Postal Service.

Campbell Electronics Ltd.

Factory Unit E5, Halesfield 23,
Telford, Shropshire TF7 4OX.
Telephone: Telford (0952) 584373, Ext. 2.
S.A.E. for further details and price list.
Trade enquiries welcome.

COLOUR TV's £60-£150. All makes, some as new. The TV Exchange Centre, 60 Golborne Road, Kensington, London W10. 01-969 3722.

SHEFFIELD PANEL REPAIRS

Offer you a High Speed Repair and Return Service on all BRC Colour Panels.

30 Hollybank Drive, Sheffield, S12 2BT.

FOR DETAILS RING
(0742) 745168.

ELECTRONICALLY TESTED TV VALVES

DY86/7	15p	PC88	15p	PCL86	18p
ECC82	15p	PC97	15p	PCL805/85	20p
EF183	15p	PCF802	15p	PL504	20p
EF184	15p	PCL82	12p	PL36	15p
PC86	15p	PCL84	15p	U26	20p

COLOUR TYPES

GY501	35p	PD500	50p	PL508	35p
PL509	40p	PL802	45p	PY500/A	35p

Many others available, please send list of types required with s.a.c. for quotation. All valves subject to availability. P. & F. 9p first valve, thereafter 6p each, max. 75p. Orders over £10 post free.

Mail order only.

L. & D. COMPONENTS LTD.

71 WESTBURY AVE., LONDON N22 6SA

MAINS DROPPERS

37-31-97-26-16852	50p.
25-35-97-59-3052	50p.
14-26-97-16052	50p.
14-26-97-17352	50p.
15-19-20-70-63-28-6352	50p.

Post free. C.W.O.

Durham Supplies
367 Kensington Street, Bradford, 8, Yorkshire

SMALL ADS

The prepaid rate for classified advertisements is 13 pence per word (minimum 12 words), box number 40p extra. Semi-display setting £7.00 per single column inch (2.5cm). All cheques, postal orders, etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

PYE, EKCO, PHILIPS, INVICTA.

Genuine manufacturers spares for all products. Components and valves, new life colour tubes - 4 year guarantee. S.A.E. or call -

Teesdale & Jones Ltd., 54 Manchester Road, Swindon, Wilts. 0793 22025

VALVE BARGAINS

ANY 1-12p, 5-60p, 10-£1.00, 50-£4.50

ECC82, ECH84, EH90, DY86/7, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85/805, PCL86, PY81, PY800, PY88, PL36, PL504, 6F28, 30PL14.

COLOUR VALVES 30p EACH

PY500/A, PL508, PL509.

Postage & Packing 25p, no VAT

VELCO ELECTRONICS

9 Mandeville Terrace, Hawkshaw, Via Bury, Lancs.

VALVES

Radio - TV - Industrial - Transmitting

We dispatch valves to all parts of the world by return of post, Air or Sea mail. 2,700 types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 a.m. to 5.00 p.m., closed Wednesday 1.00 p.m. We wish to purchase all types of new and boxed valves.

COX RADIO (SUSSEX) LTD., Dept. PT,
The Parade, East Wittering, Sussex, PO20 8BN.
Tel: West Wittering 2023 (STD Code 024366).

100 MULLARD C280 Capacitors. 0.1mF, tested. £1.00 post free. Mail Order only. B. Malloy, 66 Woodvale Avenue, Belfast, BT13 3EX. N. Ireland.

EX RENTAL TV

19" UHF 625 £4.50
23" UHF 625 £6.00
Colour from £40.00

EDWARDS & SONS

103 Goldhawk Road, London W12
Tel: 01-743 6996

200 NEW RESISTORS, well assorted. $\frac{1}{2}$ Watts. Carbon-Hi-Stab Oxide, etc. £1.50 post free. Whitsam Electrical, 33 Drayton Green Road, London W13.

UHF/VHF MONO T.V.'s

SKANTIC 12 inch Portable - £99
17 inch Portable - £110
SOUND SPACING SWITCHABLE (AT EXTRA COST) IF REQUIRED.

PORTATEL CONVERSIONS LTD.,
24 SUNBURY CROSS CENTRE,
SUNBURY-ON-THAMES, MIDDXX.
(TEL: SUNBURY-ON-THAMES. 88972)

POLYESTER CAPACITORS. Price per 100 including postage: C280 - 0.01, 0.022, 0.033, 0.068 £2.25; 0.22 £2.50; 0.33 £3.50; 0.47 £4.00. C281 - 0.01, 0.015, 0.33, 0.47 £2.25. B. Malloy, 66 Woodvale Avenue, Belfast BT13 3EX.

BRC 2000, 3000, 3500, 8000, 8500.

Philips G8, Pye 691, 697, 713.

Bush Murphy 802, 823.

Panel Repair/Exchange Singles or Bulk.

MODULAR ELECTRONICS

160 Brabazon Road, Hounslow, TW5 9LP.
Telephone 01-897 0976.

VALVE LIST

ALL VALVES FULLY TESTED

Five valves or over postage paid
Under five valves postage 6p each

DY86/87	15p	PC900	8p	PCL85/805	20p
EB91	12p	PCC84	8p	PL36	20p
ECC82	10p	PCC85	20p	PL504	25p
ECL80	8p	PCC89	8p	PY32/33	15p
EF80	8p	PCC189	8p	PY81/800	15p
EF85	8p	PCC805	15p	PY801	20p
EF183	10p	PCF80	8p	U191	15p
EF184	10p	PCF86	15p	6F23	15p
EH90	13p	PCF805	20p	6/30L2	15p
EY86/87	13p	PCL82	15p	30F5	10p
PC86	15p	PCL83	15p	30FL1	20p
PC88	15p	PCL84	15p	30PL14	15p

AND MANY MORE AVAILABLE

S. W. ELECTRONICS

114 Burnley Road, Rawtenstall, Rossendale, Lancs.

COLOUR TV's

Many working for disposal, trade only. All sizes and makes available. Mono sets also available.

INGERTONE (LONDON)

24 Dames Road, Forest Gate, London E7.
Tel: 01-555 5569.

INGERTONE (BRISTOL)

28 St. Thomas St., Bristol 1.
Tel: 0272-211179 (5063).

SURPLUS STOCK

COLOUR TUBES used from£10
S/S COLOUR TUBES new from£25
S/S P.I.L COLOUR TUBES new from£25
PORTABLE TUBES Mono Available
CABINETS, COLOUR, MONO, from£2
S/S COLOUR SETS MURPHY from£60
RING:- JEFFRIES 01-845 2036.

BOOKS & PUBLICATIONS

DX-TV

Identify your DX-TV signals with the unique book entitled, "Guide To World-Wide Television Test Cards". Over 260 photo's of Test Cards, Clock and Identification captions, etc., plus additional information on transmission standards and Services.

Available, price £1.30 including postage world-wide, from:-

HS PUBLICATIONS

Dept. T(A), 7 Epping Close, Derby. DE3 4HR.

SIMPLIFIED TV REPAIRS. Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique TV Publications. (Auset) 76 Church Street, Larkhall, Lanarkshire.

**SERVICE SHEETS. SERVICE MANUALS
PRACTICAL AND TECHNICAL BOOKS**

COVERING COLOUR & MONO TELEVISIONS, RADIOS, RECORD PLAYERS, TAPE RECORDERS, ETC.

SERVICE SHEETS 75p PLUS S.A.E. SERVICE SHEET CATALOGUE 50p

BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

SOLID STATE COLOUR TELEVISION CIRCUITS by G. R. Wilding.....	£6.05
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 1.....	£6.95
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 2.....	£6.95
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 3.....	£8.35
COLOUR TELEVISION SERVICING by G. J. King. 2nd Edition.....	£7.05
COLOUR TELEVISION THEORY by G. H. Hutson.....	£6.55
COLOUR TELEVISION PICTURE FAULTS by K. J. Bohlman.....	£2.70
COLOUR TV WITH REFERENCE TO THE PAL SYSTEM by G. N. Patchett.....	£5.40
MAZDA BOOK OF PAL RECEIVER SERVICING by D. J. Seal.....	£5.45
TELEVISION (COLOUR & MONOCHROME) Part 3 by G. N. Patchett.....	£4.10
TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition.....	£5.85
BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition.....	£2.45
BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition.....	£2.45
CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett.....	£3.85
SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition.....	£5.25
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. Revised Edition.....	£5.00

(SEND LARGE S.A.E. FOR FREE BOOK LISTS)

COLOUR TV MANUALS

COVERING FOLLOWING MAKES

ALBA, BRC, BUSH, DECCA, GEC, DEFIANT, MARCONI, EKCO, PYE, FERGUSON, DYNATRON, NATIONAL, HITACHI, INVICTA, ITT/KB, RGD, GRUNDIG, SOBELL, STELLA, SONY, MURPHY, PHILIPS, HMV, ULTRA.

PLEASE SEND S.A.E. FOR QUOTATION

"COMPREHENSIVE TV REPAIR MANUALS"
by McCourt. In 7 Volumes

These unique Books save time and money on repairs and cover most British Colour & Mono sets. Price £4.00 per volume plus 45p POST, or complete 7 volumes for only £27.00 POST FREE. SEND FOR FREE LEAFLET.

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS. FROM VOLUME ONE UP TO 1976-77 EDITION. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 15p POSTAGE PER COPY.
P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, R. CONSTRUCTOR, ELECTRONICS TODAY, ELEKTOR.

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

**LARGE SUPPLIERS OF SERVICE SHEETS
AND COLOUR MANUALS**

TV, RADIO, TUNERS, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS. ALL AT 75p EACH EXCEPT COLOUR & CAR RADIOS.

PLEASE STATE IF CIRCUIT WILL DO, IF SERVICE SHEET NOT IN STOCK. LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS OTHERWISE CANNOT BE ATTENDED TO. UNCROSSED P.O.'s OR CROSSED P.O.'s RETURNED IF SERVICE SHEETS ARE NOT AVAILABLE. ALL SERVICE MEN, PLEASE NOTE, WE OPERATE A SAME DAY RETURN SERVICE, ALL CLAIMS OF NON-DELIVERY SHOULD BE MADE WITHIN SEVEN DAYS. NO OVERSEAS MAIL PLEASE. MAIL ORDER ONLY OR 'PHONE 01-458 4882. FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER.

C. CARANNA, 71 BEAUFORT PARK, LONDON, NW11 6BX.

SERVICE SHEETS - COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p.

Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers by return Post.

B.R.C. PYE EKCO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON H.M.V. MARCONI AND MANY MORE. LET US QUOTE YOU.

Please send a Stamped Addressed Envelope for a prompt reply.

COMPREHENSIVE TV REPAIR MANUALS BY J. MCCOURT

Mono Volumes 1, 2, 3 and 4. Colour Volumes 2, 3 and 4

A must for the repair man, loaded with faults and cures, all at £3.80 each plus 35p post.

Build yourself "The Colour TV Signal Injector", manual £1.45. Manual with printed circuit £2.30 post paid.

The McCourt circuit diagram manuals Mono and Colour. Send S.A.E. for full details.

Export enquiries welcome. International Reply Coupon please.

G. T. TECHNICAL INFORMATION SERVICE

10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA

MAIL ORDER ONLY

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio, TV, etc., 10,000 models. Catalogue 24p. plus S.A.E. with orders enquiries. Telray, 154 Brook Street, Preston, PR1 7HP.

LADDERS

ALUMINIUM Roof Crawlers. Sizes 12ft - 24ft. Also make aluminium ext. up to 62½ft. Leaflets. The Ladder Centre (TFL) Halesfield (1) Telford. Tel: 586644. Callers Welcome.

FOR SALE

THREE LABGEAR Tele-verta's Ideal for DX-TV or relay systems. £10.50 each. Phone Wellingborough (Northants) 677396 after 6 p.m.

MANOR SUPPLIES MK4 Colour-Bar and Cross-Hatch Kit with case and battery holders. NEW. Duplicated Gift. Complete untouch £30, plus P & P. Brocklehurst, 14 Park View, Crewkerne, Somerset.

TELEVISION 22" Colour receiver nearly complete with Tube, £55 o.n.o. Maidstone 861617.

TELEVISION COLOUR RECEIVER, all panels assembled. "TELEVISION" aligned i.f. strip. Veneered cabinet. Cheap. Stanchens, 97 Aireville Road, Frizinghall, Bradford BD9 4HN, Yorks.

12" AUSTRALIAN made H.M.V. B/W Mains and 12V Portable. Excellent condition. Phone 4496085.

Colour Televisions From £25.00 VAT inc.
D/S Mono From £4.00 VAT inc.
S/S Square Screens From £12.00 VAT inc.

VISIT OUR WAREHOUSE AND SEE FOR YOURSELF,
 WE HAVE 4 DELIVERIES OF FRESH STOCK WEEKLY.

TELECARE

BRITAIN'S LARGEST USED T.V. DISTRIBUTOR.


Unit B.1, Eley Road, Eley Estate,

Edmonton, London N18.

Tel: 01-807 5908/9 807 5900.

MISCELLANEOUS

BEC CABINETS

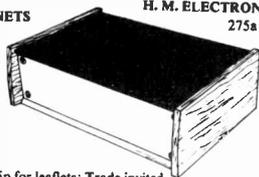

H. M. ELECTRONICS (TV.1.)
 275a Fulwood Rd
 Broomhill
 Sheffield
 S10 3BD.

Suitable
 for all
 projects
 Amps: P.A.:
 Decoders etc.

Please send 15p for leaflets: Trade invited

EMO/EURAVOX/ EUROSONIC ETC.

Spares, Panel repairs, Manuals. Circuit
 diagram £1.10 incl. postage.
 Also Grundig 5010/6010 panel repairs,
 remote controller repairs.

ELECTRONIC ENGINEERING SERVICES

Cambridge Street, Rotherham,
 S. Yorks.

RECHARGEABLE BATTERIES

'AA' pcell (HP7) £1.26; Sub 'C' £1.29; 'C' (HP11) £2.38;
 'D' (HP2) £2.92; PP3 £4.98. Matching chargers £5.91
 each except PP3 charger £4.99. Charging holders for 2, 3,
 4, 5 or 6 pcells 35p 'C' & 'D' size holders, 4 cell only 50p.
 Prices include VAT. Add 10% post, package and insurance
 orders under £20, 5% over £20. SAE for full details plus
 50p for 'Nickel Cadmium Power' booklet.
 Mail orders to SANDWELL PLANT LTD., 1 Denholm Rd,
 Sutton Coldfield, West Midlands. TEL: 021-354 9764.
 Callers to T.L.C., 32 Craven Street, Charing Cross, London
 W.C.2.

TV SOUND - kit including drilled PCB to build the
 Hi-Fi News TV sound isolator. Enables TV sound to
 be played through a hi-fi system. Only £3.75 inc.
 P&P. TVS Electronics, 95a Ardwell Avenue,
 Barkingside, Ilford, Essex.

REGUNNING EQUIPMENT

DETAILS FROM

BARRETT'S

1 Mayo Road, Croydon CR0 2QP

Tel: 01-684 9917

WANTED

WANTED - NEW VALVES, TRANSISTORS.
 TOP PRICES, popular types. Kensington Supplies
 (A) 367 Kensington Street, Bradford 8, Yorkshire

WANTED NEW Valves, transistors, L.Cs, amplifiers,
 receivers, televisions (anything useful) any quantity.
 Stan Willetts, 37 High Street, West Bromwich.
 Tel: 021 553 0186.

WANTED For parts: VC Cassette(s), Tape unim-
 portant. £3 offered. Harlow (0279) 25647.

V.H.F. 4 button tuners required for Bush and Fergus-
 on in large or small quantities. T.V. Wholesale Dist.
 Ltd., EDI House, Kylemere Park West, Industrial
 Estate, Dublin 10.

TURN YOUR Surplus Components into Cash.
 Phone 0491-35529 (Oxon).

NEW VALVES and CRT's required, PCL805,
 PL504, PL509, PY500A etc. Cash waiting. Bearman,
 6/8 Potters Road, New Barnet, Herts. Tel. 01-449
 1934/5.

WANTED. Set of "Radio, TV Servicing" Books.
 Southend 545984 after 6 p.m., or weekends.

EDUCATIONAL

BETTER JOB! BETTER PAY!

GET QUALIFIED WITH ICS IN:
 COLOUR & MONO TV SERVICING
 COLOUR & MONO TV ENGINEERING
 COLOUR & MONO TV MAINTENANCE
 PLUS: Telecommunications, radio, elec-
 tronics, electrical engineering, technical
 communications, radio communications,
 etc., etc.,
**NEW: Self-build radio courses with free
 kits**

Train in your own home, in your own
 time with ICS, the world's most experi-
 enced home study college.

RETURN THIS COUPON TODAY
 FOR FREE BROCHURE!

ICS

Int Correspondence Schools
 800H Intertext House Stewarts Rd
 London SW8 4UJ Tel: 01-822 9911

Name

Address

TELEVISION TRAINING

12 MONTHS' full-time course in Radio &
 TV for beginners. (GCE - or equivalent -
 in Maths. and English.)

26 WEEKS' full-time course in Mono &
 Colour TV. (Basic electronics knowledge
 essential.)

13 WEEKS' full-time course in Colour TV.
 (Mono TV knowledge essential.)

These courses incorporate a high percentage
 of practical training.

NEXT SESSION starts on September 12th.

PROSPECTUS FROM:

London Electronics College, Dept. TT7
 20 Penywern Road, London SW5 9SU.
 Tel. 01-373 8721.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME

ADDRESS

Send to: Classified Advertisement Manager,
 TELEVISION,
 GMG, Classified Advertisement Dept., Rm. 2337,
 King's Reach Tower, Stamford Street,
 London SE1 9LS. Telephone 01-261 5846.
 Rate
 13p per word, minimum 12 words. Box No. 40p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Fault Ferreters wanted

If you have a good knowledge of basic electronics and can ferret out circuit faults down to component level, then we'd like to meet you. If you also have experience of working on operational amplifiers or integrated logic circuits, you'll be even more welcome here at Marconi-Elliott Avionic Systems in Rochester.

For its here that we're looking for Electronic Test Technicians, men or women, to join teams working on calibration and fault finding on both analogue and digital solid state systems.

It's interesting work on highly advanced avionics equipment for flight control, navigation and surveillance systems on such aircraft as Nimrod, Harrier and Tornado.

So if you have the experience we're after, possibly gained as a TV Engineer or in the

Forces as an Electronics Technician, you could be in line for a well-paid career with the world leader in avionic systems. If necessary, we'll assist you with relocation expenses.

Write now with details of your experience and qualifications (we would expect you to have City & Guilds, ONC or equivalent), to: Mr. T. Jones, Marconi-Elliott Avionic Systems Limited, Airport Works, Rochester, Kent. Tel: Medway (0634) 44400.

MARCONI ELLIOTT AVIONICS

A GEC-Marconi Electronics Company

COLOUR T.V.'s UNTESTED

Most Dual-standard; R.B.M., Philips G6, Decca, Pye, etc., from £25 + VAT.

Single-standard from £35 + VAT. Most makes available.

Monochrome from £3 + VAT. 'Square screen' from £6 + VAT. Circuit Diagrams available most sets £1 extra.

All working sets demonstrated. All untested sets can be fully inspected before purchase.

Ring or send s.a.e. for current prices and stock.

Usually scrap sets of many makes available from £10 + VAT.

Fresh stock of Castor Stands just in!

West Midlands TV Trade Sales
1532 Pershore Road (Main A441)
Stirchley, Birmingham, B30 2NW
(*Phone 021-458 2208)

Open all day Mon, Tues, Thurs, Fri, Sat. Half day Wed.

THE UM4 "COLOURBOOSTER" UHF/625 LINE

Can produce remarkable improvements in colour and picture quality in fringe or difficult areas with significant reduction in noise (snow).

High gain - very low noise. Fitted fly lead - installed in seconds. Highest quality components.

WHITE PLASTIC CASE $3\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ FELT BASE

CHANNELS: Group A, Red code 21-33

Please Group B, Yellow code 39-51

Specify Group C-D, Green code 52-68

EQUALLY SUITABLE FOR BLACK AND WHITE

Also the M4 DUAL BAND VHF UNIT

Boosts all Band III and any specified Band I channel simultaneously. Nominal gain 16-18 dB both bands.

PRICES BOTH TYPES INCLUDING VAT & POSTAGE:

Battery model £7.75 Self contained Mains version £9.95

TRANSISTOR DEVICES LIMITED

Suite E, Georgian House, Trinity Street, Dorchester, Dorset.

BENTLEY ACOUSTIC CORPORATION LTD.

The Old Police Station, Gloucester Road, LITTLEHAMPTON, Sussex.

PHONE 6743

ALL PRICES INCLUSIVE OF V.A.T. AT 12½%. NOTHING EXTRA TO PAY

OA2 0.85	6DT6A 0.85	20P4 0.84	ECC83 0.34	EY500 1.45	PY80 0.50
OB2 0.40	6E5 1.00	30C15 0.77	ECC84 0.35	EZ40 0.52	PY81 0.50
1B3GT 0.55	6EW6 0.85	30C17 0.77	ECC85 0.39	EZ41 0.52	PY82 0.40
2D21 0.55	6F1 0.80	30F5 0.70	ECC88 0.72	EZ80 0.35	PY88 0.60
SCG8 0.75	6F18 0.60	30L15 0.75	ECC807 2.80	EZ81 0.40	PY500A 1.35
5R4GY 1.00	6F23 0.65	30L17 0.70	ECF80 0.60	GY501 0.95	PY800 0.50
SU4G 0.60	6F24 0.80	30P12 0.74	ECF82 0.50	GZ32 0.60	PY801 0.50
5V4G 0.60	6F25 1.00	30P19 0.90	ECF86 0.80	GZ34 0.75	PZ30 0.50
5Y3GT 0.55	6F28 0.74	30PL1 1.00	ECH42 0.71	HN309 1.70	QQV03/10
5Z3 1.00	6GH8A 0.80	30PL13 1.00	ECH81 0.40	K T66 3.00	QV06/20 2.00
5Z4G 0.48	6GK5 0.75	30PL14 1.29	ECH83 0.50	K T88 6.75	QV06/20 4.40
6/30L2 0.79	6GU7 0.90	50CD6G	ECH84 0.50	P61 0.60	R19 7.75
6AC7 0.55	6HG6T 0.30		ECL80 0.45	PC86 0.62	UABC80 0.45
6AG7 0.60	6J5GT 0.65	85A2 0.75	ECL82 0.50	PC88 0.62	UABC80 0.45
6AH6 0.70	6J6 0.35	150B2 1.00	ECL83 0.74	PC92 0.55	UABC80 0.45
6AK5 0.45	6J8A 0.90	807 1.10	ECL86 0.64	PC97 0.75	UAF42 0.70
6AM8A 0.70	6K7G 0.35	5763 1.65	EF22 1.00	PC900 4.00	UBC41 0.50
6AN8 0.70	6K8G 0.50	AZ31 0.60	EF40 0.78	PCC84 0.39	UBC81 0.55
6AQ5 0.68	6L6GC 0.85	AZ41 0.50	EF41 0.75	PCC85 0.47	UBF80 0.50
6AR5 0.80	6L7(M) 1.50	B36 0.75	EF80 0.29	PCC89 0.49	UBF89 0.39
6AT6 0.50	6N7GT 0.70	DY86/7 0.35	EF83 1.25	PCC189/0.52	UC92 0.50
6AU6 0.40	6Q7G 0.50	DY802 0.50	EF85 0.36	PCF80 0.40	UCC85 0.45
6AV6 0.50	6Q7GT 0.50	E80CF 5.00	EF86 5.00	PCF82 0.45	UCF80 0.60
6AW8A 0.84	6SA7 0.55	E88CC 1.20	EF89 0.42	PCF86 0.57	UCH42 0.71
6AX4 0.75	6SG7 0.55	E180F 1.15	EF91 0.50	PCF200 1.20	UCH81 0.50
6BA6 0.40	6V6G 0.30	E188CC2.50	EF92 0.50	PCF201 1.00	UCL82 0.55
6BC8 0.90	6X4 0.45	EA50 0.40	EF183 0.42	PCF801 0.49	UCL83 0.57
6BE6 0.40	6X5GT 0.45	EABC80	EF184 0.42	PCF802 0.54	UF41 0.70
6BH6 0.70	9D7 0.70		EH90 0.45	PCF806 0.53	UF42 0.80
6BJ6 0.65	10C2 0.70	EAF42 0.70	EL34 1.00	PCH200 1.00	UF80 0.40
6BK7A 0.85	10DE7 0.80	EAF801 0.75	EL41 0.57	PCL82 0.54	UF85 0.50
6BQ7A 0.60	10F1 0.67	EB34 0.30	EL81 0.65	PCL83 0.49	UF89 0.45
6BR7 1.00	10F18 0.65	EB91 0.20	EL84 0.35	PCL84 0.46	UL41 0.70
6BR8 1.25	10P13 0.80	EBC41 0.75	EL95 0.67	PCL86 0.65	UL84 0.54
6BW6 1.70	10P14 2.50	EBC81 0.45	EL360 1.80	PCL805 0.60	UM80 0.60
6BW7 0.65	12AT6 0.45	EBF80 0.40	EL506 1.20	PFL200 0.70	UY41 0.50
6BZ6 0.60	12AU6 0.50	EBF83 0.45	EL509 2.50	PL36 0.60	UY85 0.35
6C4 0.50	12AV6 0.60	EBF89 0.40	EM80 0.55	PL81 0.49	U19 4.00
6CB6A 0.50	12BA6 0.50	EC86 0.84	EM81 0.60	PL81A 0.53	U25 0.71
6CD6G 1.60	12BE6 0.55	EC88 0.84	EM84 0.45	PL82 0.37	U26 0.60
6CG8A 0.90	12BH7 0.55	EC92 0.55	EM87 1.10	PL83 0.45	U191 0.50
6CL6 0.75	12BY7 0.85	ECC33 2.00	EY51 0.45	PL84 0.50	U404 0.75
6CL8A 0.95	19AQ5 0.65	ECC35 2.00	EY81 0.45	PL504 0.90	U801 0.80
6CM7 1.00	19G6 6.50	ECC40 0.90	EY83 0.60	PL508 1.30	VR150 0.50
6CLU5 0.90	19H1 4.00	ECC81 0.34	EY87/6 0.37	PL509 2.20	YR150 0.75
6DE7 0.90	20P1 1.00	ECC82 0.34	EY88 0.55	PY33/2 0.50	X41 1.00

All goods are unused and boxed, and subject to the standard guarantee. Terms of business: Cash or cheque with order only. Despatch charges: Orders below £15, add 25p extra per order. Orders over £15 post free. Same day despatch. Terms of business available on request. Any parcel insured against damage in transit for only 5p extra per parcel. Many other types in stock. Please enclose S.A.E. with any enquiries. Special offer of EF50 VALVES, SOILED, BUT NEW AND TESTED £1 EACH.

Vital Parts Revealed Each Month



DON'T MISS NEXT MONTH'S ISSUE!

FROM SOMEONE WHO KNOWS WHAT YOUR AFTER!

EHT Trays
ALL TYPES IN STOCK AT ATTRACTIVE PRICES.
 Introductory prices E.G.
 Thorn 3000/3500 £6.00
 Thorn 9000 £6.70

Capacitors
 Electrolytic
 Polyester
 Mixed Dielectric.
FULL RANGE OF ALL TYPES SEND FOR LIST.

Multi Section Capacitors

150.150.100/350	115p
175.100.100/400/350	185p
1000/63	68p
2500.2500/63	165p
2500.2500/30	115p
600/300	155p
200.300/350	180p
600/300	155p
400.400/350	245p
600/300	155p

Special Opening Offer
DON'T MISS IT!

Mains Droppers
30 DIFFERENT STYLES
 E.G. Thorn 3000/3500 75p
 RR1 - TV 161 80p

Resistors
 Power Wirewound - 2.5w - 5w + 10w - Full range.
 High stability carbon film - 0.5w - 1w + 2w Full range.

Semi Conductors

AC 107	28p
AC 126	27p
AC 127	22p
AC 128	17p
AC 128K	33p
AC 141	27p
AC 141K	37p
AC 142	20p
AC 142K	40p
AC 151	31p
AC 154	20p
AC 155	20p
AC 156	31p
AC 176	24p
AC 176K	38p
AC 187	22p
AC 187K	40p
AC 188	27p
AC 188K	42p
AC 193K	40p
AC 194K	39p
AD 140	78p
AD 142	74p
AD 143	72p
AD 149	79p

SEND FOR OUR FULL LIST

SIDS Components

FAST, RELIABLE AND COMPETITIVE

Cash with all orders - Add 12½% VAT. Minimum Order £2.00 - No postal or packing charge.

SIDS full stock + price list available - Just telephone 061.480 8244 or write to - SIDS (Electronic Components) Ltd. 251, Wellington Road South, Stockport, Cheshire.

Tubes
 Colour + Black + White - Full size range 14" to 26" send for our special list + details of our guaranteed 'Regun' colour tubes.

Integrated Circuits

SN 76013N	186p
SN 76013ND	157p
SN 76023N	186p
SN 76023ND	157p
SN 76033N	276p
SN 76110N	196p
SN 76226N	247p
SN 76227N	186p
SN 76532N	180p
SN 76533N	180p
SN 76544N	200p
SN 76650N	168p
SN 76660N	75p
SN 76666N	124p

PART OF OUR STOCK
AT UNBEATABLE PRICES

All Plessey or Toshiba new Stock.

Valves
A SELECTION OF OUR RANGE
UNREPEATABLE PRICES.
WHILE CURRENT STOCKS LAST.

PCF 86	62p
PCF 801	67p
PCF 802	70p
PCL 82	64p
PCL 84	72p
PCL 85	70p
PCL 86	67p
PFL 200	84p
PL 36	76p
PL 84	57p
PL 504	115p
PL 508	118p

Fuses
 Full range of metric and imperial sizes - Anti Surge + Quick Blow.

RADIO AND TV SPARES ALL COMPONENTS BRAND NEW. CASH WITH ORDER ONLY. P & P 35np. ALL PRICES INCLUDE VAT. AT 12½% CARRIAGE ON TUBES £1.25 EXTRA

MAIL ORDER ONLY. NO CALLERS.

PHD COMPONENTS DEPT 2, UNIT 7, CENTENARY ESTATE, JEFFERIES ROAD, ENFIELD, MIDDX. TELEX 261295.

MULTISECTION CAPACITORS

Description

400-400/350	3.00
200-200-150-50/300	2.50
1000-2000/35	80p
600/300	1.90
600/250	1.55
200-300/350	2.05
1000-1000/40	1.00
2500-2500/30	1.30
300-300/300	2.25
200-200-75-25/350	2.40
100-300-100-16/275	1.60
150-100-100-100-150/320	2.60
150-150-100/350	1.50
175-100-100	2.35
220/100	32p
2500-2500/63	1.70
700/200	1.30
400/350	1.55

DROPPER SECTIONS

16p each

MAINS DROPPERS

Pye 11062	75p
Pye 11009	1.20
BRC Mono 1400	80p
BRC Mono 1500	75p
BRC Colour 3000/3500	75p
BRC Colour 8000	75p
BRC Colour 8500	75p
Phillips G8	50p
Phillips 210 (with link)	55p
Phillips 210	65p
RRI Mono 141	75p
RRI Mono 161	80p
GEC 27840	75p
GEC 2000	75p
Phillips G9	35p

THYRISTORS

2N4443	1.20
TV106	1.80
BR101	45p
BR100	35p
BR101	45p
BR100	35p

Bridge Rectifiers

BY164	50p
BY179	65p

High Voltage

TV20	1.90 each
------	-----------

DIODES

AA113 14p	OA81 11p	BA100 14p	BA164 17p
AA116 14p	OA85 11p	BA102 24p	BAX13 5p
AA117 14p	OA90 6p	BA130 35p	BAX16 6p
AA119 8p	OA91 6p	BA145 16p	BAY38 10p
OA47 6p	OA95 6p	BA148 16p	IN4148 4p
OA79 6p	OA202 11p	BA154 12p	BY206 30p
		BA155 15p	

RECTIFIERS

BY100 21p	IN4001 4p	TUNER
BY126 15p	IN4002 5p	ELC1043/05
BY127 15p	IN4003 6p	5.50 each
BY133 22p	IN4004 7p	
BY182 2.00	IN4005 8p	CRYSTAL
BY238 40p	IN4006 9p	4.43 MHz
BYX10 14p	IN4007 10p	1.90 each

INTEGRATED CIRCUITS

MC1307P	1.50	SL901B	5.00
MC1310P	2.50	SL917B	7.00
TAA350	1.90	SN76003ND	1.70
TAA550	50p	SN76013N	1.80
TAA630S	4.00	SN76013N07	1.80
TBA120S	1.50	SN76013ND	1.60
TBA120SQ	1.50	SN76023N	1.85
TBA520Q	3.00	SN76023ND	1.60
TBA530Q	2.50	SN76033N	2.75
TBA540Q	3.00	SN76665N	2.50
TBA550Q	4.00	CA3065	2.50
TBA560CQ	4.00	MC1358P	2.50
TBA750Q	2.20	MC1327P	2.00
TBA800	1.60	MC1327PQ	2.50
TBA920Q	4.00	MC1330P	1.50
TBA990Q	4.00	MC1351P	1.20
SN76003N	2.75	MC1352P	1.60

REPLACEMENT COMPONENTS

Aerial Isolators	1.00 each
Lopt Korting	10.00 each
BRC 3500 Cutouts	1.60 each

VALVES

DY86/87 50p	PCF80 75p	PL36 90p
DY802 50p	PCF86 1.50	PL84 70p
ECC82 50p	PCF801 60p	PL504 1.20
EF80 450	PCF802 1.50	PL508 2.00
EF183 46p	PCL82 75p	PL509 3.00
EF184 46p	PCL84 1.00	PL519 3.00
EH90 90p	PCL85 90p	PY500A 1.90
PCC89 1.20	PCL86 90p	PY800 65p
PCC189 1.60	PFL200 85p	PL802 4.00

EHT TRIPLERS (Priced each)

BRC950	2.65	Pye CT205	5.50
BRC1400	2.65	Pye 731	8.25
BRC1500 (17")	2.65	Decca 2030	6.60
BRC1500 (24")	3.00	GEC 2028	7.10
BRC3500	6.60	GEC 2110	7.10
BRC8000	2.90	ITT CVC5	6.60
BRC8500	5.50	RRI 111/174	10.00
BRC9000	7.75	RRI A823	7.70
Decca CS190	7.10	Korting 90°	7.10
Philips G8	7.30	Tanberg	7.10

TRANSISTORS	AF179 55p	BC182L 10p	BD138 49p	BF257 48p
AC107 33p	AF180 53p	BC182LB 10p	BD139 80p	BF258 65p
AC126 23p	AF181 49p	BC183L 10p	BD144 2.10	BF271 15p
AC127 30p	AF186 39p	BC183LB 10p	BD155 74p	BF273 15p
AC12701 50p	AF239 39p	BC184L 10p	BD157 74p	BF274 15p
AC128 23p	AL102 1.05	BC186 24p	BD183 55p	BF336 34p
AC12801 50p	AU107 1.05	BC187 26p	BD235 74p	BF337 34p
AC141 24p	AU110 1.85	BC203 15p	BD237 74p	BF338 34p
AC141K 40p	AU113 2.20	BC204 15p	BD238 74p	BF458 59p
AC142 24p	BC107 10p	BC205 15p	BDX32 2.50	BFX29 29p
AC142K 25p	BC108 10p	BC206 15p	BF115 19p	BFX84 24p
AC153 23p	BC109 10p	BC207 15p	BF118 25p	BFX85 25p
AC176 24p	BC113 12p	BC208 11p	BF121 24p	BFX88 23p
AC17601 50p	BC114 19p	BC209 15p	BF152 30p	BFX89 30p
AC187 23p	BC115 19p	BC212L 11p	BF154 30p	BFY50 22p
AC187K 24p	BC116 19p	BC213L 11p	BF157 30p	BFY51 22p
AC188 24p	BC117 19p	BC214L 11p	BF158 24p	BFY52 22p
AC188K 40p	BC118 28p	BC225 15p	BF163 24p	BU105/01 1.90
AC193K 29p	BC119 28p	BC237 15p	BF167 24p	BU105/02 1.90
AC194K 31p	BC125 21p	BC238 11p	BF173 24p	BU105/04 2.50
AD140 45p	BC126 19p	BC251A 16p	BF177 29p	BU108 3.00
AD142 50p	BC136 19p	BC301 32p	BF178 32p	BU126 2.90
AD143 50p	BC137 19p	BC303 59p	BF179 32p	BU204 1.90
AD145 50p	BC138 19p	BC307 11p	BF180 34p	BU205 1.90
AD149 1.00	BC139 19p	BC308 9p	BF181 32p	BU206 1.90
AD161 45p	BC142 29p	BC327 12p	BF182 43p	BU208 3.00
AD162 45p	BC143 34p	BC328 12p	BF183 43p	MJE340 65p
AF114 50p	BC147 12p	BC337 15p	BF184 25p	MJE520 80p
AF115 23p	BC148 11p	BC547 12p	BF185 25p	MJE2955 1.10
AF116 23p	BC149 13p	BD115 64p	BF194 14p	MJE3055 73p
AF117 19p	BC153 19p	BD116 60p	BF195 14p	MPSU05 65p
AF118 48p	BC154 19p	BD124 79p	BF196 14p	MPSU55 1.25
AF121 30p	BC157 14p	BD131 44p	BF197 14p	R2008B 3.00
AF124 23p	BC158 12p	BD132 49p	BF198 19p	R2009 3.00
AF125 23p	BC159 14p	BD133 49p	BF199 24p	R2010B 3.00
AF126 23p	BC171 14p	BD134 49p	BF200 34p	TIP31A 60p
AF127 23p	BC172 13p	BD135 39p	BF240 19p	TIP32A 60p
AF139 34p	BC178 21p	BD136 45p	BF241 21p	
AF178 53p	BC179 19p	BD137 47p	BF256LC 44p	