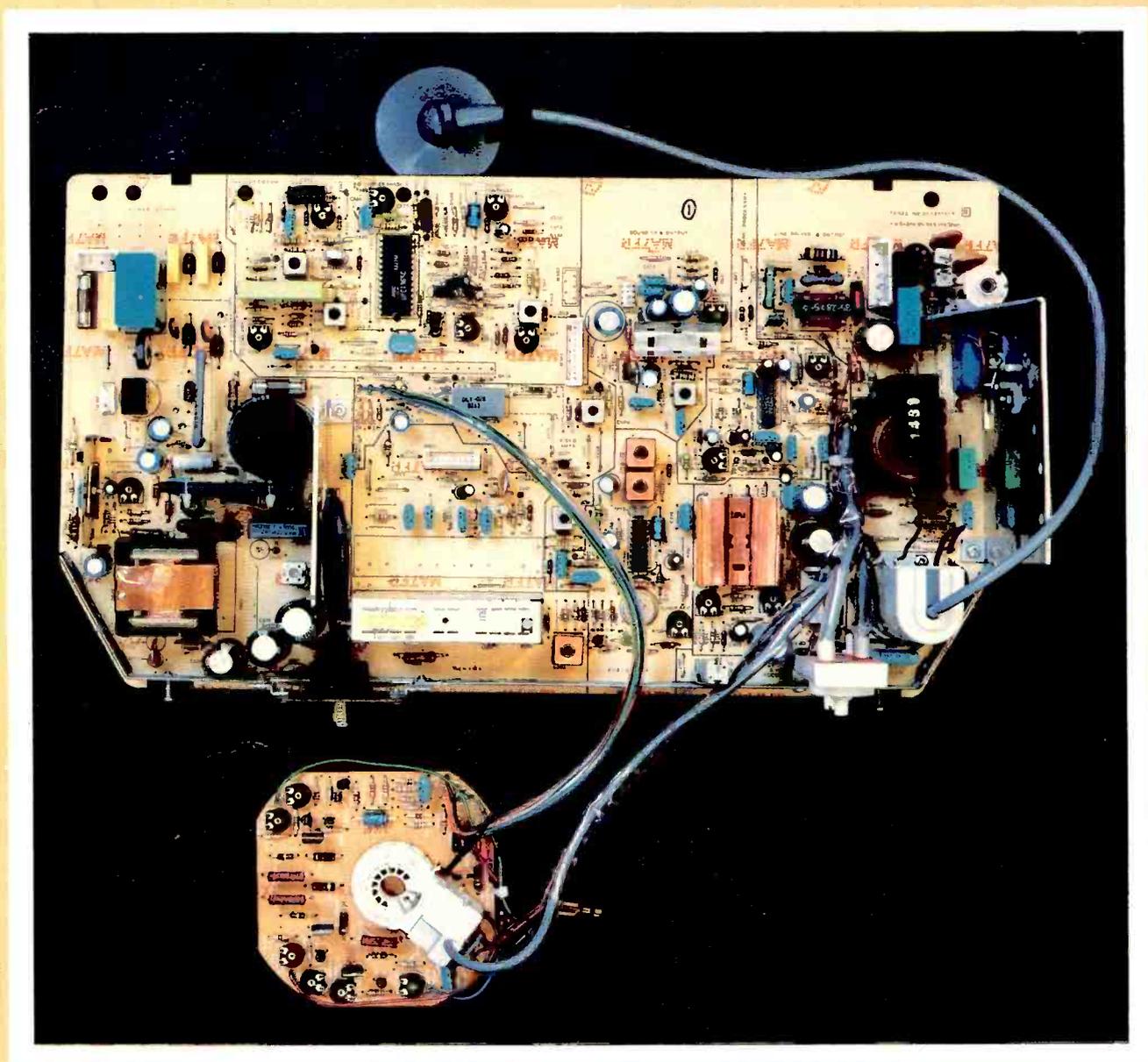


NOVEMBER 1981


70p

TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS



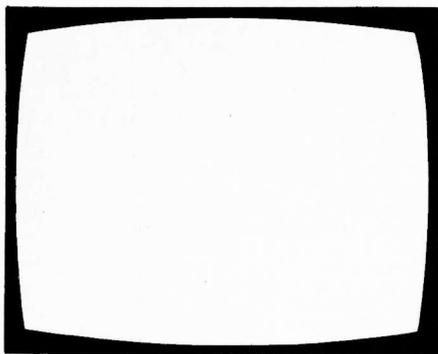**TV RECEIVER DESIGN-THE
NEW DECCA COLOUR CHASSIS
DIGITAL SIGNAL PROCESSING
SERVICING LUXOR 110° HYBRID CTVs
VCR TOPICS: TV STANDARDS**



TELEVISION

November
1981

Vol. 32, No. 1
Issue 373

COPYRIGHT

©IPC Magazines Limited, 1981. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

SUBSCRIPTIONS

An annual subscription costs £10 in the UK, £11 overseas (\$24.20 Canada or USA). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

BINDERS AND INDEXES

Binders (£4.40) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 85p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month

- 9 **Leader**
- 10 **Teletopics**
- 15 **TV Receiver Design: The Decca 120 Series, Part 1**
by Ray Wilkinson
- Features of the latest UK designed colour TV chassis to go into large-scale production, with an account of the considerations behind the design.
- 18 **Fault Report**
by Steven Knowles
- Troubles with a variety of receivers – in particular line output stage problems with a Philips G6.
- 20 **Digital Signal Processing**
by Arthur Mole
- The next step with TV receiver design could be digital signal processing. An account of the system designed by ITT Semiconductors for processing the video, audio and deflection signals in digital form.
- 22 **Servicing Luxor 110° Hybrid CTVs, Part 1**
by Mike Phelan
- These well designed Swedish sets were imported during the colour boom and seem to have a good life. Common faults, starting with the power supplies and signal circuits.
- 24 **Colour Portable Project, Part 7**
by Luke Theodossiou
- The cable loom, interconnecting the boards, c.r.t. connections and the manual control option.
- 26 **TV Pattern Generator**
- PCB print patterns for last month's project.
- 27 **Renovating N1700 Head Drums**
by C. J. Lowdon, B.Eng. (Hons), C.Eng., M.I.E.E.
- What to do when one of the heads fails – including the ultimate step, transplanting a known good one.
- 28 **Practical TV Servicing: Replacing the C.R.T.**
by S. Simon
- How to go about fitting a new colour c.r.t. and setting it up. Plus safety precautions.
- 30 **Long-Distance Television**
by Roger Bunney
- DX reception and conditions, plus news from abroad.
- 33 **VCR Servicing, Part 3**
by Mike Phelan
- This month a look at the Philips N1500/N1700 servo system, and the luminance circuitry used in the basic JVC machine on record.
- 35 **Readers' PCB Service**
- 36 **TV Standards**
by David K. Matthewson, B.Sc., Ph.D.
- The various TV standards used world wide cause many problems. A basic guide to TV systems and multistandard possibilities.
- 37 **Next Month in Television**
- 38 **Focusing Systems**
by Richard Blenheim
- A look at some of the focusing arrangements used in more recent receivers.
- 39 **Letters**
- 40 **VCR Clinic**
Reports from Mike Phelan and Steve Beeching, T.Eng. (C.E.I.)
- 41 **Service Notebook**
by George Wilding
- TV faults and how to tackle them.
- 42 **Video Review: Toshiba V8600 VCR**
by Steve Beeching, T.Eng. (C.E.I.)
- One of the most interesting new machines, with its extra heads to give good still and slow-motion displays.
- 43 **New Tuner for DX Use**
by Hugh Cocks
- The new NSF ET021 v.h.f./u.h.f. tuner covers a wide frequency spectrum and has excellent performance.
- 44 **Service Bureau**
- 46 **Test Case 227**

OUR NEXT ISSUE DATED DECEMBER WILL
BE PUBLISHED ON NOVEMBER 18

MANOR SUPPLIES

NEW MKV CHEQUERBOARD & PAL COLOUR TEST GENERATOR FOR TV & VCR.




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.

PRICE OF KIT £80.50.
DE LUXE CASE (10"×6½"×2½") £8.50
Post/Packing £2.00.

ALL ABOVE PRICE INCLUDE VAT 15%.

PAL COLOUR BAR GENERATOR (Mk 4)

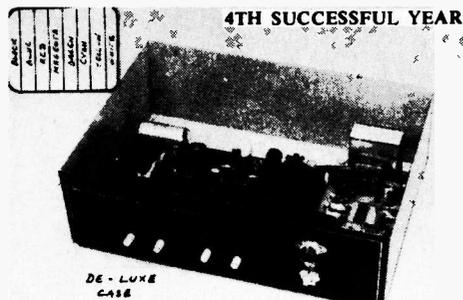

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £40.25 P&P £1.20. DE-LUXE CASE £5.95.
ALUMINIUM CASE £3.30, P&P £1.20, BATT HOLDERS £1.70 P&P 85p, ALTERNATIVE STAB. MAINS SUPPLY KIT £5.55 (Combined P&P £1.80).

MK 4 DE LUXE (BATTERY) BUILT & TESTED £66.70 + £1.80 P & P.
MK 4 DE LUXE (MAINS) BUILT & TESTED £80.50 + £1.80 P & P.
VHF MODULATOR (CHI to 4) FOR OVERSEAS £4.60.
EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

(ALL PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETEXT ADAPTOR KITS

Remote control of stations & teletext.
MK 1 (Texas XMII) £170.20.
 Further details on request P/P £2.80.

TELEVISION PROJECTS & SERVICE SPARES

"TELEVISION" NEW COLOUR PORTABLE PROJECT (Parts available)
SWITCH MODE POWER SUPPLY KIT £26.00 p.p. £1.60. SIG BOARD KIT (Incl. ALT. SAW IF) £70.00 p.p. £1.60. TIME BASE £44.80 p.p. £1.60. CRT BASE £2.60 p.p. 60p.
 (PHONE, CALL, SEND FOR LIST). FULL TECHNICAL ADVICE & PANEL TEST SERVICE FOR OUR CUSTOMERS.
 "TELEVISION" TV PATTERN GEN. PARTS AVAILABLE.
 "TELEVISION" MONITOR PARTS AVAILABLE.
 "TELEVISION" MONO PORTABLE RECEIVER PARTS AVAILABLE. WORKING MODELS & PANEL TEST SERVICE.
 "TELEVISION" COLOUR RECEIVER (LARGE SCREEN) PROJECT ALL PARTS AVAILABLE. SEND OR PHONE FOR LIST. WORKING MODEL ON SHOW WITH TELETEXT. (PANEL TEST SERVICE) NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR T.V. SOUND & VISION £32.80 p.p. £1.20 (SUITABLE FOR USE WITH TELEVISION SIGNAL BOARDS).
**SPECIAL OFFER TEXAS XMII TELETEXT MODULE NEW & TESTED, LIMITED QUANTITY AT HALF PRICE £69.00 p.p. £1.60. TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE £7.80 p.p. £1.20. XMII INTERFACE PANEL (THORN) £2.10 p.p. 75p. CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £12.65 p.p. 60p. (ALUM CASE £2.60 DE LUXE CASE £5.50 p.p. £1.00.) ADDITIONAL GREY SCALE KIT £3.35 p.p. 45p. UHF SIGNAL STRENGTH METER KIT £20.00 (VHF VERSION £21.60). ALUM CASE £2.00 DE LUXE CASE £5.95 p.p. £1.80. CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO £28.00 p.p. £2.00.
 BUSH Z718 BC6100 SERIES IF PANEL £5.75 p.p. 90p.
 BUSH A816 IF PANEL (SURPLUS) £1.90 p.p. 90p.
 BUSH 161 TIMEBASE PANEL A634 £3.25 p.p. £1.40.
 DECCA "Bradford" IF T.B. POWER ex rental £5.75 each p.p. £1.40.
 DECCA 80, SERIES, IF FRAME TB £7.90 each p.p. £1.40.
 GEC SERIES I MONO PANELS £2.10 p.p. £1.30.
 GEC 2110 Decoder. RGB panels (ex rental) £5.75 each p.p. £1.00.
 GEC 2010 SERIES TIMEBASE PANEL £1.15 p.p. £1.00.
 GEC 2040 (TYPE) CDA PANEL £2.88 p.p. £1.25.
 PYE 713/715 Convergence £5.75 each p.p. £1.40.
 PYE 697 Line T.B. P.C.B. type salvaged £4.80 p.p. £1.50.
 THORN 3000 LINE TB PCB £5.75 each p.p. 85p.
 THORN 3000 VID, IF, DEC, Ex Rental £5.75 each p.p. £1.30.
 THORN 8500 Series channel selector & front control unit £4.37 p.p. £1.80.
 THORN 8000/8500 IF/DECODER PANELS salvaged £5.52 p.p. £1.60.
 THORN 8000/8500 FRAME T.B. PANELS salvaged £5.52 p.p. £1.40.
 THORN 8000/8500 POWER/SALV. SPARES £2.88 p.p. 60p.
 THORN 9000 LINE T.B. (incl. Lopt etc.), Salv., spares £8.62 p.p. £1.60.
 THORN 9000 SERIES TOUCH TUNE REMOTE CONTROL UNIT PLUS ULTRASONIC TRANSMITTER HANDSET £19.32 p.p. £1.84.
 THORN 9000 IF/DECODER PANELS Salvaged £8.90 p.p. £1.60.
 PHILIPS 210, 300 Series Frame T.B. Panels £1.15 p.p. 80p.
 PHILIPS G8/G9 IF/DECODER Panels for small spares £4.80 p.p. £1.30.
 G8 IF Panels for small spares £1.75 p.p. 95p.
 G8 Decoder panels salvaged £4.25. Decoder panels for spares £2.00 p.p. £1.35.
 VARICAP, U321, U322, ELC 1043/06 £7.82, ELC 1043/05 £6.35 p.p. 60p; G.I. type (equiv. 1043/05) £4.00 p.p. 60p. Control units, 3PSN £1.40, 4PSN £1.75, 5PSN £2.00, 6PSN £2.88 p.p. 60p.
 BUSH "Touch Tune" and Vancap Control Unit £4.40 p.p. 95p.
 VARICAP UHF-VHF ELC 2000S £9.80. BUSH TYPE £8.60 p.p. 85p.
 VARICAP VHF MULLARD ELC 1042 £7.95 p.p. 60p.
 UHF/625 Tuners, many different types in stock. UHF tuners transisted. incl. s/m drive. Mullard 4 position push button £4.80 p.p. £1.30.
 TRANSISTORISED 625 IF for T.V., sound, tested. £7.82 p.p. 95p.
 MULLARD EP9000 Audio Unit incl. LP1162 Module £4.38 p.p. 85p.
 LINE OUTPUT TRANSFORMERS. New guar. p.p. £1.25.**

BUSH 145 to 186SS series £9.20
 BUSH, MURPHY A816 series £9.80
 DECCA 20/24, 1700, 2000, 2401. £8.80
 FERG., HMV, MARCONI, ULTRA
 850 to 1580 £6.80
 THORN 1690, 1691 £10.15
 GEC 2000 to 2038 series £7.80
 GEC series 1 & 2 £9.20
 INDESIT 20/24/EGB £8.80
 ITT/KB VC1 200, 300 £8.80
 MURPHY 1910 to 2417 series £8.80
 PHILIPS 19TG 170, 210, 300 £8.80
 PYE, INVICTA, EKCO, FERR.
 368, 169, 569, 769 series £8.80

COLOUR LOPTS p.p. £1.30 (BOBBINS 80p)

R.B.M. A823 £5.60
 R.B.M. Z179 £6.70
 R.B.M. T20, T22 Bobbin £6.44
 DECCA Bradford (state Model No.) £10.15
 DECCA 80, 100 £9.50
 GEC 2028 £7.82
 GEC 2040 £11.30
 GEC 2110 Series £12.20
 ITT CVC 5 to 9 £10.15
 ITT CVC 30 Series £10.15
 PYE 691-697 £14.80
 PYE 713-715 £7.85
 PYE 731 to 741 £7.85
 PHILIPS G8, G9 £10.15
 PHILIPS 570 £7.85
 THORN 3000/3500 SCAN, EHT £7.85
 THORN 8000/8500 £14.80
 THORN 9000 £10.15

SPECIAL OFFER

GEC 2114J/FINELINE £5.50
 PYE 40, 67 £5.50
 THORN 1590/1591 £5.50
 KB VC ELEVEN (003) £3.25

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.T.S.

TRANSDUCTORS Suitable for G8, A823, Bradford etc. £1.72 p.p. 60p.
 THORN 950 3 Stick Tray £1.15 p.p. 55p. Most others available.
 THORN 3000/3500, 8000, 8500, MAINS TRANSF. £10.15 p.p. £1.80
 6-3V CRT Boost Transformers £5.80, Auto Type £3.20, p.p. £1.20.

CALLERS WELCOME AT SHOP PREMISES Telephone 01-794 8751/7346
 THOUSANDS OF ADDITIONAL ITEMS AVAILABLE. ENQUIRIES INVITED
 LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS


MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
 W. Hampstead British Rail Stn. (Richmond, Broad St.) (St. Pancras, Bedford)
 W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.


ALL PRICES INCLUDE VAT AT 15%

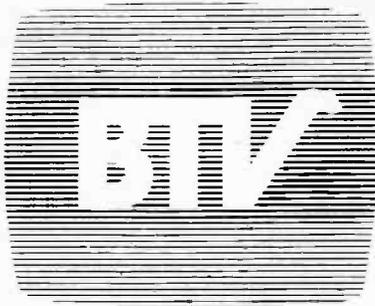

There's never been a better time to buy from Briarwood TV.



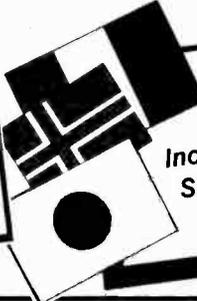**Any 5 British Makes
GOOD WORKING**
Including: Thorn 3500 +
8500 — PYE Solid State
G8 — ITT/KB — GEC 2100 ETC.
£55.00 EACH + VAT



**Any 5 Foreign Makes
GOOD WORKING**
Including: Hitachi — Grundig — Luxors
Saba — ASA — Mitsubishi — Etc.
£55.00 EACH + VAT

Colour TVs with tested tubes... Guaranteed 100% complete!

	In 10's	In 20's	Good Working in 10's
PYE 691	£18.00 each	£15.00	£33.00
PYE 697	£21.00 each	£18.00	£38.00
GEC 2040	£18.00 each	£15.00	£33.00
BUSH 184	£23.00 each	£20.00	£38.00
THORN 3000 19"	£28.00 each	£25.00	£43.00
THORN 3500 26"	£28.50 each	£25.00	£43.00
DECCA BFD - 30's	£28.00 each	£25.00	£43.00
KORTING	£25.00 each	£22.00	£45.00
TELPRO	£28.00 each	£25.00	£43.00

Please note — 15% VAT on all above prices.

**100's OF SINGLE/STANDARD MONO
- 100% COMPLETE
I.E. THORN 1300 - PYE 169 - PHILIPS 300 -
GEC FINELINE - BUSH/MURPHY -
INDESIT - ITT/KB ETC.
£7.00 each + VAT**

**100's OF COLOUR
TV'S 100% COMPLETE
AS THEY ARRIVE — IN
BATCHES OF TEN
BRIARWOOD SPECIAL CLEARANCE
PRICE £15.00 per set! + VAT**

**TUNE IN TO THESE BRIARWOOD BARGAINS
ALL SETS IN BATCHES OF FIVE
— ALL GOOD WORKING**

5 - 25" 3000 THORN OR
5 - 26" PYE WITH DOORS!
@ £40.00 each + VAT

5 - 25" BUSH WITH DOORS
OR 5 - 26" GEC 2040
@ £40.00 each + VAT

5 - 26" THORN WITH DOORS
OR 5 - 26" KORTING WITH DOORS
@ £40.00 each + VAT



**RING BRADFORD (0274) 306018 FOR DETAILS OF
SPECIAL PRICES FOR SINGLE SETS!**

BRIARWOOD TELEVISION LIMITED



BRIARWOOD

QUALITY SELECTED EX EQUIPMENT SPARES

MISC S/Output Trans. £11 + VAT + P&P
F/Output Trans. £1.25 + BAT + £1 P&P
Scancoils £1.50 + VAT + £1 P&P. Other spares available, please write or phone for details.

MONO TUNERS

6 button integrated all at £4.00
U.H.F. P/Button D/S £3.60. U.H.F. P/Button S/S £4.00. Rotary £3.00 + £1 P&P

MONO TUBES

(tested)
19" Ringuard £3.00
23" Ringuard £4.00
20" Ringuard £5.00
24" Ringuard £6.00 + £5.00 P & P

MONO LOPTS

All D/Standard Lopts at £4.00 + £1 P&P.
All S/Standard at £4.00 + £1 P&P.

MONO PANELS

i.e. Philips, Bush, etc. £3.50 + £1 P&P.
Quotations for complete S/hand chassis if required. (Diff. prices)

PLEASE ADD 15% V.A.T. TO ALL ITEMS AND OVERSEAS AT COST. CASH WITH ALL ORDERS.

VALVES (MONO & COLOUR)

PCL82	0.10	30C1	0.10	PCC189	0.10	EF183	0.10	PL504	0.25	ECL80	0.10
PCL83	0.25	30C17	0.10	30C15	0.10	EF184	0.10	6/30L2	0.10	PL509	1.00
PCL84	0.10	PCF802	0.10	30C18	0.25	6BW7	0.10	30PL1	0.25	PY500	1.00
PCL85	0.10	PCF805	0.25	PC97	0.20	EH90	0.10	30PL13/4	0.10	GY501	1.00
PCL86	0.10	PCF806	0.10	PC900	0.10	DY802	0.10	30FL1/2	0.25	PL508	0.50
PFL200	0.10	PCF808	0.25	EF80	0.10	PY800/1	0.10	ECC82	0.10	PCF200	0.50
PCF801	0.10	PCF80	0.10	EF85	0.10	PL36	0.25	ECC81	0.10	EY51	0.15

Please note there is 50p Postage and Packing per order.

WE DO NOT SELL RUBBISH AT BRIARWOOD TV

BRIARWOOD TV LTD (Export Division)

TEL: 0274-306018 FOR PRICES & FREIGHT DETAILS

COLOUR & MONO TV'S ALWAYS AVAILABLE FOR WORLDWIDE USE

Briarwood T.V. Ltd., have international experience in quality used T.V. supply. Fully tested & converted where necessary – by our experienced Export Division.

S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	12.00	—	6.00	6.00	12.00	—
GEC Hybrid	6.00	6.50	9.00	—	5.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	5.00	—	—	6.00
Thorn 3000	6.00	6.00	6.00	—	5.00	15.00	15.00	6.00
Pye 691/693	6.00	6.00	8.00	—	5.00	—	15.00	5.00
Thorn 3500	6.00	6.00	6.00	6.50	12.00	15.00	15.00	6.00

Korting and other foreign panels available on request.

Postage & Packing £1.25

COLOUR TUBES

17"	£15.00
18"	£15.00
19"	£15.00
19" A49/192	£18.00
20"	£18.00
22"	£20.00
25"	£15.00
26"	£22.00

Plus P&P £6.00
New rebuilt tubes available on request.

COLOUR TUNERS

Bush	£5.00
GEC	£5.00
Philips G6 S/S	£5.00
Pye 691	£5.00
Thorn 3000	£5.00

Some new tuners in stock, can supply on request. Many Foreign Tuners also available on request. Plus P&P £1.

COLOUR LOPTS

Most Lopts available from £5.00. Both British & Foreign makers. Please ring or write. P&P per Lopt £1.00

MISC.


S/Output transformer from £1.50.
F/Output from £1.25.
Scancoils from £5.00.
P&P £1.00
Other spares available on request.

THORN 1500 TUNERS
NEW SPECIAL OFFER
AT £8.00

Postage & Packing £1.00

NEW PRODUCTS!

£2.50 each
£1.00 p&p

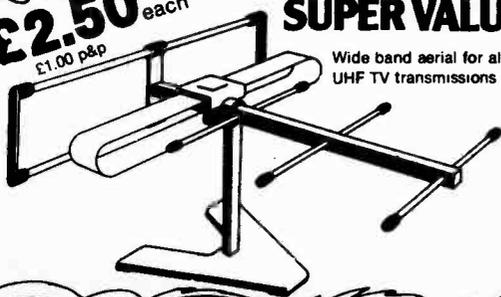


SUPER VALUE - SUPER QUALITY

Wide band aerial for all UHF TV transmissions

£5.95 each
£1.75 p&p

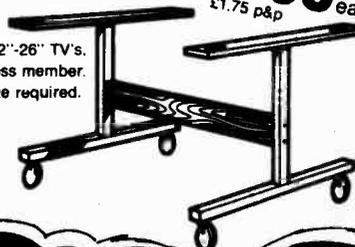Fits 22"-26" TV's.
wood finished cross member.
State size required.



TV scores with quality

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED

NEW SPARE SELECTION

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £
AC107	0.24	AF181	1.00	BC179	0.12	BD137	0.30	BF218	0.12	OC36	0.90	2N3053	0.21
AC113	0.22	AF186	0.90	BC182L	0.09	BD138	0.31	BF219	0.12	OC38	0.90	2N3054	0.60
AC115	0.23	AF239	0.46	BC183L	0.09	BD139	0.40	BF220	0.12	OC42	0.45	2N3055	0.60
AC117	0.30	AU113	1.40	BC183LA	0.10	BD140	0.37	BF221	0.21	OC44	0.60	2N3442	1.00
AC125	0.23	BA130	0.08	BC183LB	0.10	BD144	1.39	BF222	0.12	OC45	0.50	2N3702	0.15
AC126	0.23	BA145	0.14	BC184L	0.09	BD145	0.50	BF224	0.18	OC46	0.39	2N3703	0.12
AC127	0.22	BA148	0.21	BC186	0.21	BD177	0.50	BF256	0.37	OC70	0.39	2N3704	0.18
AC128	0.22	BA155	0.08	BC187	0.21	BD178	0.50	BF258	0.30	OC71	0.39	2N5705	0.18
AC131	0.13	BAX13	0.05	BC209	0.11	BD203	0.40	BF259	0.30	OC72	0.39	2N3706	0.14
AC141	0.24	BAX16	0.08	BC212	0.09	BD204	0.70	BF260	0.25	OC74	0.39	2N3707	0.14
AC142	0.24	BC107	0.11	BC212L	0.09	BD222	0.73	BF262	0.28	OC75	0.39	2N3708	0.14
AC141K	0.31	BC108	0.11	BC213L	0.09	BD233	0.36	BF263	0.25	OC76	0.39	2N3772	2.00
AC142K	0.31	BC109	0.11	BC214L	0.09	BD234	0.34	BF271	0.27	OC77	0.50	2N3773	2.50
AC151	0.21	BC113	0.11	BC237	0.09	BD237	0.44	BF272	0.27	OC78	0.23	2N3619	0.30
AC165	0.21	BC114	0.11	BC238	0.09	BD238	0.44	BF273	0.16	OC81	0.26		
AC166	0.21	BC115	0.11	BC240	0.31	BDX22	0.73	BF336	0.30	OC810	0.14		
AC168	0.22	BC116	0.11	BC249	0.35	BDX32	1.98	BF337	0.29	OC82	0.26		
AC176	0.22	BC117	0.12	BC251	0.22	BDY18	0.80	BF338	0.29	OC820	0.20		
AC176K	0.28	BC119	0.24	BC257	0.20	BDY60	0.80	BF479		OC83	0.30		
AC178	0.23	BC125	0.15	BC262	0.18	BF115	0.30	BFT	0.27	OC84	0.30		
AC186	0.26	BC126	0.15	BC263B	0.20	BF121	0.29	BFT	0.27	OC85	0.28	DY87	0.60
AC187	0.23	BC136	0.15	BC267	0.19	BF154	0.12	BFX84	0.27	OC123	0.25	DY802	0.64
AC188	0.23	BC137	0.17	BC281	0.24	BF158	0.19	BFX85	0.27	OC169	1.20	ECC82	0.60
AC187K	0.30	BC137	0.23	BC300	0.27	BF159	0.24	BFX	0.30	OC170	1.20	EF80	0.55
AC188K	0.30	BC139	0.23	BC301	0.27	BF160	0.23	BFY37	0.22	OC171	0.92	EF183	0.70
AD130	0.58	BC140	0.24	BC302	0.30	BF163	0.30	BFY50	0.21	OA91	0.07	EF184	0.70
AD140	0.68	BC141	0.27	BC303	0.27	BF164	0.30	BFY51	0.21	BRC4443	0.65	EH90	0.75
AD142	0.80	BC142	0.27	BC307	0.11	BF167	0.30	BFY52	0.21	R2008B	1.50	PC86	0.85
AD143	0.70	BC143	0.27	BC307A	0.11	BF173	0.21	BFY53	0.27	R2009	1.30	PCC89	0.65
AD145	0.70	BC147	0.10	BC308A	0.12	BF177	0.26	BFY55	0.33	R2010B	1.50	PCC189	0.80
AD149	0.64	BC148	0.10	BC309	0.14	BF178	0.24	BFX		R2265	1.50	PCF80	0.80
AD161	0.42	BC149	0.10	BC337	0.12	BF179	0.28	BHA0002	1.90	R2305	0.38	PCF86	0.72
AD162	0.42	BC153	0.12	BC338	0.15	BF180	0.30	BSX20	0.23	R2305	0.38	PCF801	0.70
AD161(1)		BC154	0.12	BC487	0.20	BF181	0.34	BSX76	0.23	BD222	0.37	PCF802	0.85
AD162(1)	1.00	BC157	0.12	BC547	0.10	BF182	0.30	BSY84	0.36	R2540	2.50	PCL82	0.75
AF106	0.42	BC158	0.12	BC548	0.11	BF183	0.29	BU105	1.00	S2802		PCL84	0.80
AF114	0.37	BC159	0.12	BC549	0.11	BF184	0.27	BU105 02	1.50	SCR957	0.65	PCL86	0.85
AF118	0.45	BC160	0.26	BC557	0.12	BF185	0.29	BU105 04	2.00	TIP31A	0.38		
AF121	0.37	BC161	0.26	BCX33	0.10	BF186	0.32	BU126	1.40	TIP32A	0.36	PCL805	0.82
AF125	0.30	BC167	0.11	BD112	0.39	BF192		BU205	1.20	TIP3055	0.53	PLF200	1.00
AF126	0.30	BC168	0.11	BD113	0.65	BF194	0.15	BU206	1.60	TIP31B	0.39	PL36	£1.10
AF127	0.30	BC169	0.11	BD115	0.32	BF195	0.13	BU208	1.60	TIS90	0.23	PL84	0.80
AF139	0.40	BC171	0.10	BD116	0.47	BF196	0.13	OC22	1.10	TIS91	0.25	PL504	£1.30
AF150	0.27	BC171A	0.10	BD124	1.30	BF197	0.13	OC23	1.30	TV106	1.09	PL508	1.50
AF151	0.30	BC172	0.10	BD131	0.36	BF198	0.12	OC24	1.30	MJE340	0.50	PL509	2.45
AF170	0.92	BC173	0.12	BD132	0.36	BF199	0.14	OC25	1.00	MJE520	0.45	PL802	£2.75
AF172	1.00	BC177	0.12	BD133	0.37	BF200	0.28	OC26	1.30	2N2219	0.40	PY88	0.75
AF178	1.00	BC178	0.12	BD135	0.30	BF216	0.12	OC28	1.30	2N2646	0.40	PY500A	1.60
AF180	1.00	BC178A	0.12	BD136	0.30	BF217	0.12	OC35	1.00	2N2926	0.15	PY81 800	0.70

E.H.T. Trays

Colour

TYPE PRICE £

Pye 691 693	4.50
Pye 715/731/735	5.50
Pye 737	5.40
Decca (Large Screen)	
CS2030/2232/2630/2632/2230/2233/	
2631	5.00
Decca 80	5.30
Decca 100	5.30
Philips G8	
520/540	5.30
Philips G9	5.50
Philips 550	5.30
GEC C2110	5.50
GEC Hybrid	
CTV	5.10
Thorn 3000/3500	5.00
Thorn 800	2.42
Thorn 8500	4.75
Thorn 9000	5.50
GEC TVM25	2.50
ITT KB CVC	
5/7/8/9	5.10
ITT KB CVC	
20/25	
30/32	5.50
Bush CTR25	
MK3	
Quadrupler	8.00
Bush X179	4.50
RRI (RBM)	
A823	5.00
Bang & Olufsen	
4/5000 Grundig	
5010/5011/5012/6011/6012/7200/2052/2210/2252R	
Tandberg (radionette)	
Autovox	6.60
Grundig	
3000/3010	
Saba 2705/3715	
Telefunken	
709/710/717/2000	6.80
Korting	6.80

VALVES

DY87 0.60

DY802 0.64

ECC82 0.60

EF80 0.55

EF183 0.70

EF184 0.70

EH90 0.75

PC86 0.85

PCC89 0.65

R2010B 1.50

R2265 1.50

R2305 0.38

R2305 0.38

PCF801 0.70

PCF802 0.85

PCL82 0.75

PCL84 0.80

PCL86 0.85

PCL805 0.82

PLF200 1.00

PL36 £1.10

PL84 0.80

PL504 £1.30

PL508 1.50

PL509 2.45

PL802 £2.75

PY88 0.75

PY500A 1.60

PY81 800 0.70

All transistors, IC's offered are new and branded. Manufactured by Mullard, I.T.T., Texas, Motorola etc.

Please add 15% VAT to all items and overseas at cost.

P & P U.K. 50p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice.

MAIL ORDER TV BARGAINS

PYE 691	22" @	£55.00
PYE 691	26" @	£55.00
PYE 697	22" @	£65.00
PYE 697	26" @	£65.00
BUSH 184	19" @	£70.00
BUSH 184	22" @	£70.00
BUSH 184	26" @	£70.00
GEC 2040	19" @	£55.00
GEC2040	22" @	£55.00
GEC 2040	25" @	£55.00
GEC 2040	26" @	£65.00
KORTING	22" @	£70.00
KORTING	26" @	£80.00
THORN 3000	19" @	£70.00
THORN 3000	25" @	£60.00
Good working mono's Pye, GEC, Bush etc.		
20" & 24" S/S		£20.00
20" & 24" D/S		£18.00
19" & 23" D/S P/Button		£15.00
19" & 23" D/S Rotary		£12.00

Cheques, P.O. or Cash with orders Please.
Please note there is 15% VAT on all the above prices. Plus £10.00 p & p for colour TV. £5.00 for mono. ENGLAND, WALES and SCOTLAND Inland N & S IRELAND £15.00 for colour. £7.00 for mono.

TYPE PRICE £

IC's

BTT6018	1.00
CA3605	1.20
MC7/c	
MC14016	0.50
SN76003N	1.40
SN76023N	1.20
SN76110N	1.00
SN76226DN	1.50
SN76227N	1.20
SN76532N	1.30
SN76550N	0.30
SN76666N	0.70
TAA570	1.38
TBA120AS	1.00
TBA120S	0.75
TBA120SQ	0.75
TBA395	2.20
TBA341	0.97
TBA520	1.40
TBA520Q	1.10
TBA530Q	1.10
TBA540	1.30
TBA540Q	1.45

TBA550Q	1.40	BAX13	0.08
TBA560C	1.50	BAX16	0.10
TBA560CQ	1.50	BY126	0.10
TBA570	1.00	BY127	0.10
TBA570Q	1.00	BY164	0.40
TBA800	1.00	BY179	0.57
TBA810	1.50	BY226	—
TBA920	2.00	BY227	0.12
TBA920Q	1.50	BYF206	0.14
TBA990Q	1.50	1N4001	0.04
TCA270SQ	1.45	1N4002	0.05
TCA270SA	1.45	1N4003	0.06
TCA270Q	—	1N4004	0.07
TCA1327B	1.00	1N4005	0.07
TCA800	2.00	1N4006	0.08
TDA1010	—	1N4007	0.08
TDA1327B	1.00	1N4148	0.05
SBA750	1.75	1N4751	0.14
SC9503P	1.20	1N5401	0.12
SC9504P	1.20	1N5403	0.12
SL901B	5.00	1N5404	0.14
SL917B	7.00	1N5405	0.14
		1N5406	0.14
		1N5408	0.25
		BR100	0.22
		BR101	0.28
		BT106	1.19
		BT108	1.23
		BT109	1.09
		BT116	1.60
		BT120	1.60

P. V. TUBES

Telephone: Accrington (0254) 3652 1

38A WATER STREET, ACCRINGTON, LANCS BB5 6PX.

WHOLESALE SUPPLIERS OF TELEVISION COMPONENTS

TRADE COUNTER OPEN MON-FRI 9 a.m.-4.30 p.m. SAT MORN. 9.30 a.m.-12 noon.

INTEGRATED CIRCUITS

MC1307 1.00	ML922 3.29	SN76131N 1.30	TAA350A 80	TBA120B 1.30	TBA570 1.00	TCA800 1.00	TDA2540 3.04
MC1327 1.00	ML926 2.18	SN76228(D) 1.55	TAA300 58	TBA120SB 1.30	TBA841-B11 2.40	TCA940 1.00	TDA2541 2.05
MC1330P 90	ML928 2.18	SN76227N 1.10	TAA310 2.83	TBA120U 1.00	TBA841 BX1 2.00	TDA440 2.20	TDA2560 1.90
MC1349 1.20	SA5560S 1.80	SN76532N 1.50	TAA320 58	TBA395 2.20	TBA890 1.50	TDA1004A 2.95	TDA2581 2.25
MC1350 86	SA5570S 1.80	SN76533N 1.30	TAA550 28	TBA396 80	TBA673 1.10	TDA2540 3.15	TDA2591 3.25
MC1351 1.00	SA5580S 2.90	SN76033N 1.53	TAA570 1.80	TBA440N/TBA1441 1.80	TBA700 2.12	TDA1170 1.90	TDA2593 2.50
MC1352 1.00	SA5590S 2.90	SN76544N 1.35	TAA630 2.50	TBA440 2.75	TBA7200 2.12	TDA1190 2.90	TDA2800 3.25
MC1358P0 1.50	SL9018 4.45	SN76850M 89	TAA630S 2.50	TBA480 1.20	TBA750 2.05	TDA1270 3.73	TDA2811A 1.85
MC1495L 1.00	SL9178 8.25	SN76668N 80	TAA621 AX1 3.00	TBA480Q 1.20	TBA800 89	TDA1327 1.00	TDA2840 2.25
MC14011BCP 42	SL1310 1.80	SN76668N 70	TAA840/S1 1.80	TBA480Q 1.20	TBA810AS 1.35	TDA1352B 1.00	TDA2890 1.90
MC14049BCP 43	SL13270 1.20	SN76668N 70	TAA700B 1.70	TBA500P 1.50	TBA820 1.70	TDA1412 1.20	TDA3950 2.38
ML2318/ETTR6016 2.20	SL76544 2.00	SN76668N 70	TAA700 1.70	TBA510 3.00	TBA890 3.94	TDA2020 4.60	UPC568H 2.95
ML232/ETTR6016 2.20	SN76003N 1.75	SN76668N 70	TAA661B 1.20	TBA520Q 1.20	TBA920 1.00	TDA2030 2.00	UPC575C2 3.40
CA3065 2.20	SN76013N 1.50	SN76668N 70	TAA840 1.20	TBA530Q 1.20	TBA9200 1.80	TDA2521 4.17	UPC1025H 4.50
ML236 5.35	SN76013ND 1.50	SN76668N 70	TAA840 1.20	TBA530 1.20	TBA950(2X) 2.40	TDA2522 2.40	
ML237 1.95	SN76023N 1.45	SN76668N 70	TAA840 1.20	TBA540 1.40	TBA990 1.40	TDA2523 2.20	
ML238 4.20	SN76023ND 95	SN76668N 70	TAA840 1.20	TBA550 1.80	TCA160 1.20	TDA2530 1.95	
ML239 2.50	SN76110N 89	SN76668N 70	TAA840 1.20	TBA550Q 1.60	TCA760 2.30	TDA2532 2.45	
ML920 4.12	SN76115N 2.27	SN76668N 70	TAA840 1.20	TBA5600 1.50	TCA270SQ 1.25	TDA2524 2.25	

SOCKETS IC		
8 pin 24	16 pin 20	
14 pin 18	14 pin Di/Du/2	

WE NOW HAVE THESE SPECIAL CB INTEGRATED CIRCUITS

TA7205AP 3.72	MSN5807 7.87	PLLO2AG 8.89	LC7120 5.97	Please enquire for others
2SC1909 1.41	AN7150 4.07	MCI351P 1.00	TA7204P 3.77	
2SC495 1.10	TA7222 3.87	AN214Q 3.91	TA7130P 1.93	
LC7130 5.93	TA7310P 2.78	LA4031P 3.21	UPC1158H 4.20	
AN240 3.84				

SEMICONDUCTORS

AC126 22	AU110 2.00	BC171 9	BC261B 15	BD138 23	BF115 35	BF259 24	BFY90 75	OC79 20	2N3706 10
AC127 22	AU113 1.40	BC171A 10	BC262A 15	BD139 28	BF117 36	BF262 84	BR100 17	R2008B 1.80	2N3708 17
AC128 20	BC107 20	BC171B 10	BC262B 15	BD140 31	BF125 26	BF263 50	BR101 30	R2010B 1.80	2N2904 30
AC128K 32	BC107A 20	BC172 9	BC300 33	BD144 1.20	BF127 26	BF271 24	BRCA443 80	R2265 1.40	2N5294 40
AC141K 34	BC107B 20	BC172B 10	BC301 28	BD159 65	BF154 12	BF273 12	BRK46 40	R2322 50	2N5298 40
AC142K 30	BC108 20	BC172C 12	BC303 28	BD160 1.30	BF158 18	BF310 30	BRV39 30	R2323 67	2N5298 89
AC176 25	BC108A 20	BC172C 12	BC307 10	BD166 52	BF160 27	BF311 30	BRV56 57	R2461 1.50	2N5496 53
AC176K 32	BC108B 20	BC174AB 10	BC308AB 17	BD179 52	BF167 24	BF336 36	BT106 1.00	R2540 2.00	2N6107 75
AC187 28	BC108C 20	BC182 9	BC327 11	BD182 72	BF173 22	BF337 30	BT108 1.24	RC416334 90	2SC643A 1.50
AC187K 28	BC109 20	BC182LB 10	BC328 9	BD183 75	BF177 35	BF338 34	BT116 1.21	RC416335 80	2SC1172Y 2.20
AC188 25	BC109B 20	BC183LB 10	BC337 11	BD201 85	BF178 28	BF355 37	BU104 2.00	TIP29C 43	
AC188K 37	BC109C 20	BC184 9	BC338 9	BD202 80	BF179 28	BF362 37	BU105 1.25	TIP30C 43	THERMISTORS
AD143 82	BC114 12	BC184 10	BC461 30	BD203 80	BF180 38	BF363 33	BU108 1.80	TIP31C 41	VA1104 75
AD149 79	BC116A 12	BC204 10	BC547 10	BD204 84	BF181 36	BF371 30	BU124 1.30	TIP32C 42	VA8650 55
AD161 42	BC117 20	BC208 13	BC548 10	BD222 46	BF182 30	BF457 35	BU126 1.49	TIP33B 75	VA1039 35
AD161/2 1.15	BC119 24	BC209 10	BC549 8	BD223 56	BF184 30	BF458 30	BU204 1.50	TIP41C 46	VEC Dual 1.50
AD162 42	BC140 32	BC212 9	BC550 7	BD225 47	BF185 30	BF459 35	BU205 1.34	TIP42C 47	Posistor 1.50
AF14 40	BC141 26	BC212L 9	BC557 8	BD232 45	BF194 11	BF639 28	BU206 1.00	UP47 70	VEC Dual 1.50
AF18 62	BC142 21	BC213 9	BC558 9	BD233 35	BF195 11	BF742 28	BU208 1.00	TIP2955 90	2040 1.50
AF121 56	BC143 24	BC213B 10	BCY72 13	BD234 37	BF196 10	BF743 30	BU208A 1.00	TIP3055 63	
AF124 34	BC147 9	BC213L 9	BD115 32	BD235 33	BF197 11	BFW10 10	BU208/02 2.10	TIS91 21	CERAMIC FILTERS
AF125 35	BC148 9	BC214 9	BD116A 65	BD236 40	BF198 10	BFX29 30	BU326A 1.42	TV106/02 1.55	6MHz 74
AF126 34	BC149 9	BC214L 10	BD124P 60	BD237 33	BF199 15	BFX84 28	BU407 1.25	2N896 21	5.5MHz 74
AF127 32	BC157 11	BC2378 12	BD131 33	BD238 36	BF200 30	BFX85 28	BU500 1.95	2N2905 28	
AF139 42	BC158 10	BC238A/B/C 6	BD132 35	BD410 55	BF241 15	BFX86 15	BU500 1.95	2N2905 28	
AF239 45	BC159 10	BC238 12	BD133 40	BD434 55	BF256 28	BFX88 25	BU500 1.95	2N2905 28	
AL102 2.00	BC160 25	BC252A 12	BD135 26	BD517 60	BF256 28	BFY50 28	BU500 1.95	2N2905 28	
AU106 2.50	BC161 28	BC252B 12	BD136 27	BD520 75	BF257 28	BFY51 22	MJ3000 2.38	2N3703 10	CRYSTALS
AU107 2.00	BC170B 15	BC261A 18	BD137 26	BDX32 1.50	BF258 25	BFY52 20	MJ3000 2.38	2N3705 10	4.3MHz 1.30
							OC71 27	2N3705 10	8.8MHz 1.30

NEW VALVES

30F12 1.41	EY500A 1.33	PCL85/805 79
OY802 72	EZ80/1 56	PC186 81
DY86/7 66	GY501 1.45	PD500 2.93
ECC81 60	GZ34 1.56	PLF200 1.35
ECC82 60	KT66 5.00	PL36 1.15
ECC83 60	KT88 6.00	PL81 94
ECC84 60	PC86 81	PL82 46
ECC85 60	PC88 81	PL83 1.43
ECC88 1.35	PC92 80	PL84 84
ECC89 80	PC97 1.14	PL95 1.04
ECC82 60	PC90 80	PL96 1.32
ECC81 1.04	PC84 70	PL508 1.43
ECC84 1.13	PC85 85	PL509 2.70
ECC80 84	PC88 82	PL519 2.78
ECC82 77	PC89 79	PL802 2.45
ECC86 84	PC189 1.02	PY33 81
ECC86 78	PCF85 1.40	PY88 81
ECC80 68	PCF80 75	PY600A 1.40
ECC85 68	PCF86 1.13	PY800/1 60
ECC86 1.19	PCF200 1.23	UCF80 87
ECC89 1.43	PCF800 1.38	UCH81 1.43
ECC83 68	PCF801 1.13	UCL82 94
ECC84 98	PCF802 86	UCL83 94
ECC80 1.02	PCF805 1.63	UL84 1.02
EL34 1.63	PCF806 1.30	U26 1.30
EL81 86	PCF808 1.63	U191 95
EL84 68	PCH200 1.45	6F23 85
EL90 82	PCL82 78	UY85 80
EL509 2.22	PCL83 2.90	PL802T 2.50
EY86/7 68	PCL84 81	

All valves are new - boxed - guaranteed. Please add 15% VAT to ALL items.

DIODES

AA119 9	BY210/800 33	IN5401 12
BA102 17	BY298 22	IN5402 14
BA115 13	BY299 22	IN5403 12
BA145 17	BYX10 20	IN5404 12
BA148 17	BYX36/10 30	IN5405 13
BA154 6	BYX36/600 35	IN5406 18
BA155 14	BYX55/600 30	IN5407 18
BA156 15	BYX71/600 90	IN5408 18
BA317 25	0A47 9	ITT44 4
BAX13 4	0A90 8	ITT2002 11
BAX16 8	0A91 8	Y969 89
BB105B 30	0A95 8	
BB105G 30	0A202 11	
BY126 12	IN914 4	
BY127 11	IN4001 4	
BY133 15	IN4002 4	
BY164 45	IN4003 4	
BY176 85	IN4004 5	
BY182 87	IN4005 5	
BY184 55	IN4006 5	
BY223 90	IN4007 6	
BY198 38	IN4148 2	
BY206 14	IN4448 10	

ZENER DIODES

BZ201/BZ205C(1.3W)	BZY88-(400MW)
6V2-7V5-8V2-9V1	2V7-3V-3V3-3V6
10V-11V-12V-13V-15V	3V9-4V3-4V7-5V1
16V-18V-20V-22V-24V-	5V6-6V2-6V8-7V5
27V-30V-33V-36V	8V2-9V1-10V-11V
39V-47V-56V-68V	12V-13V-15V-18V
75V	24V-27V.

Price 20p each Price 10p each

ACCESS ACCEPTED

RECTIFIER TRAYS

THORN 950 Mk II	4.25
THORN 1400 3 Stick	4.25
THORN 1500 3 Stick	3.85
THORN 1500 5 Stick	4.25
THORN 1600	8.80
THORN 2000	8.80
THORN 3000/3500	3.55
THORN 8000	6.40
THORN 8500/8800	7.43
THORN 9000	6.35
DECCA CTV 19/25	3.80
DECCA 1730/1830	5.82
DECCA 1910/2213 Bradford	5.82
DECCA 30	4.20
DECCA 80	8.04
DECCA 100	5.40
UNIVERSAL 1TT	5.84
GEC 2040/2028	5.84
GEC 2110 Pre Jan '77	9.05
GEC 2110 Post Jan '77	9.05
PHILIPS G8 Short Focus Lead	5.85
PHILIPS G8 Long Focus 550	5.85
PHILIPS G9	6.33
PYE 691/3	5.13
PYE 713 4 Lead	7.00
PYE 731/25	5.85
R B M. AR23 (plug in) AV	5.80
R B M. AR23	5.70
KORTING (similar to Siemens TVK1)	8.85
ITT KB CVC5/9	5.35
ITT KB CVC20/25/30 (Mullard Type)	5.35
RRI T20	8.80

RECTIFIER STICKS

TV11	74
TV18	81
TV20	85
TV13	75

TRANSFORMERS

L.O.P.T.

R.B.M. A774 Mono	11.74
R.B.M. 2179	15.00
R.B.M. 2718 22"	18.50
R.B.M. T20A	13.95
PHILIPS 210/300 Mono	

P. V. TUBES

Telephone: Accrington (0254) 36521

REPLACEMENT ELECTROLYTICS

DECCA 30 (400/400/350V)	2.98
DECCA 80 (400/350V)	3.15
DECCA 100 (800/250V)	3.15
DECCA 1700 (200/200/400/350V)	4.83
PHILIPS 68 (800/300V)	2.21
PHILIPS 69 (800/300V)	2.21
PHILIPS 611 (470/250V)	4.60
PYE 691/7 (200/300/350V)	2.39
PYE 731 (800/300V)	2.31
RBM A823 (2500/2500/300V)	1.28
RBM A823 (12500/2500/25V)	1.15
RBM A823 (800/300V)	2.30
RBM 2148 (300/300/350V)	3.15
ITT CVCS/9 (200/200/75/25)	2.47
ITT CVC 20 (220/400V)	2.00
GEC 2110 (800/250V)	1.04
GEC 2040 (1000/200/35V)	1.19
GEC 2040 (300/300/150/100/50)	4.10
THORN 3500 (400/40V)	30
THORN 950 (100/300/100/18/275V)	1.83
THORN 1400 (150/100/100/100/150/320V)	2.78
THORN 1500 (150/150/100/300V)	2.01
THORN 1500 (12/300V)	31
THORN 3500 (175/100/100/400/350V)	2.48
THORN 3500 (1000/63V)	85
THORN 3500 (1000/70V)	84
THORN 8000/8500 (2500/2500/63V)	1.54
THORN 8000/8500 (1700/250V)	2.31
THORN 8000/8500 (400/350V)	2.68
THORN 9000 (400/400V)	3.95

WIREWOUND RESISTORS

PREFERRED VALUES		price each
4W/5W	1R-1K5	28
	2K2-3K3	28
	4K7-6K8	28
	10K	28
7W	1R-4K7	21
	5K8-12K	21
	15K-22K	21
11W	1R-8K8	24
	10K-15K	24
	22K	24
17W	1R-10K0	28
	15K-22K	28

RESISTORS

A range of the following at Preferred Values

Price per 10 pack		
0.25W	28p	
0.5W	38p	
1W	10R to 10M	38p
2W	10R to 150K	82p
2W	10M	82p

MIXED DIELECTRIC CAPACITORS

Value DC		
500V	0.1 mFd	38
	0.01 mFd	29
1000V	0.047 mFd	29
	0.1 mFd	32
	0.22 mFd	48
	0.47 mFd	75
1250V	0.1 mFd	45
	0.0022 mFd	18
500V	0.0047 mFd	28
	0.022 mFd	24
	0.033 mFd	68

CAPACITORS

AXIAL TYPE

Value	MF	Price	Value	MF	Price
10	22	7	100	10	12
	47	7		22	14
	100	8		47	18
	220	11		100	20
	470	18		220	28
16	1000	28			
25	10	7	100	10	12
	22	7		22	14
	47	8		47	18
	100	10		100	20
	220	17		220	28
	470	22		300	30
	1000	30		450	1
	2200	48		4.7	28
	4700	88		10	28
40	22	9		22	68
	50	38		33	82
	83	1		500V	1
		2.2			38

DISC CERAMIC CAPACITORS

High Voltage		
8KV d.c. - 12KV d.c.	180pF	38
39 pF	200pF	38
140pF	220pF	38
150pF	250pF	38

TEST EQUIPMENT

Portable Oscilloscope	150.00
Probes x 10	£10.99
TF200 Frequency Metre	155.00
CRT Tester/Rejuvenator	172.00
LABGEAR Colour Bar/Cross Hatch	215.00
LABGEAR Pattern Generator (Pocket Size)	87.50

EAGLE PRODUCTS

SE500 Headphones	3.75
SE540 Headphones with Volume Control	5.50
SE600 Lightweight Headphones	7.95

SKELETON PRESET POTENTIOMETER HORIZONTAL and VERTICAL

price each 14	
MINIATURE	
100R-220R-470R-10K-2K2-4K7-10K-22K-47K-100K	
220K-470K-1M0	
STANDARD	price each 14
100R-220R-470R-10K-2K2-4K7-10K-22K-47K	
100K-220K-470K-1M0-2M2-4M7	

'MIOGET' CONTROLS

Insulated spindle length 44mm.

LESS SWITCH	39p
Lag or Lin.	
5K-10K-25K-50K-100K-250K-500K-1M	
WITH D.P.S.T. SWITCH	
Lag: 5K-10K-25K-50K-100K	81p
250K, 500K, 1M, 2M	

SLIDER POTENTIOMETERS

Lin or Lag	55p	4K7	55p
470R	55p	10K	55p
1K	55p	47K	55p
2K2	55p		55p

MULTITURN POTENTIOMETERS

100K	55p
GEC/DE	55p
PHILIPS 68	55p
DECCA/RANK	55p

THICK FILM RESISTOR NETWORKS

THORN 3500 (5 pin connection)	1.99
PYE 731 (8 pin connection)	2.29
THORN 9000 (Circuit Ref. R704/7)	1.99

CONVERGENCE PRE-SET POTS

3 Watt complete with knob	each
5R0-8R8-10R-15R-20R	35
50R-100R-200R-500R	35

METRIC CONVERGENCE POTS

Philips 68	
5R-10R-20R-50R	35

EAGLE PRODUCTS

Please send large S.A.E. for full EAGLE Catalogue.

Multimeters		
KEW 7H	2,000 spv	5.25
EM5	5,000 spv	8.95
EM10	10,000 spv	11.50
EM50	50,000 spv	19.95
EMC321 Carrying Case for above		2.25
Digital Meter TS1000		44.50
KHP 30N Measuring Probe (30kV) (E.H.T.)		28.95
T1206 2 Station Intercom.		8.85

ELECTRONIC TUNERS AND ASSEMBLIES

Mullard ELC1043/05	7.60
Mullard ELC1043/08	7.60
4 P/B DECCA/GEC/ITT	6.90
6 P/B DECCA/GEC/ITT	7.80
4 P/B PYE	8.00
6 P/B PYE	16.00
PHILIPS 68 Tuner	18.50
PHILIPS 68 Ass. (Square/Early)	13.50
PHILIPS 68 Ass. (Sloping/Late)	13.00
PHILIPS 69 Tuner	18.50
PHILIPS 611 Tuner	8.90
ITT/PYE/GEC 7 Button P/B	13.95
GEC 2110 6 way P/B	7.75
U321 UHF Tuner	7.80
THORN 8800 SELECTOR	7.50
THORN 9000 SELECTOR	11.48

SUNORY TUNER ACCESSORIES

RANK Tuner Push Button 1 1/2" x 1/2" dia.	30p
RANK Tuner Push Button 2" long x 1/2" dia.	30p
RANK Tuner Push Button 2" long x 1/2" dia.	30p
GEC Tuner Neons 2110 chassis.	14p
Drive Cam	10p each

SWITCHES

4A Double Pole On/Off Switch General Purpose Push/push	62
Philips 68 Push On/Off Switch	1.38
4A Double Pole Rotary On/Off	82
A1 Beam Switch (THORN 3500)	50
A1 Controls 5m (THORN 3500)	88
GEC 2110 A1 Control (MS (Red, Blue, Green))	each 58p
GEC 2040 On/Off Switch	each 88p

THERMAL CUT OUT

THORN 3000 2A Metal	1.80
THORN 8500 2.5 Plastic	1.60
GEC 2040 Metal	2.50

PYE LABGEAR

CM8040/MB UHF Masthead (ch21-68)	18.88
CM7025 UHF High Gain M.H.A. 24V (specify group A, B or CD)	14.81
CM7081 Power Unit (12V)	18.84
CM7085/MB VHF/UHF M.H.Amp (12V)	12.80
CM7073 VHF/UHF Dist Amp (8-11)	37.80
CM7053 'Behind the set' UHF Amp. (main)	18.73
CM7043 'Behind the set' 2nd Set Amp. (UHF-2 outputs)	18.80
CM8008 UHF 6 way Passive Splitter	18.72
CM7042 TV Games Combiner	3.31
CM9003 Flush Mount Single Outlet Isolated	1.75
CM9009 Flush TV/FM Diplex Outlet Isolated	3.80
CM7089 Tri Star Amplified Set Top Aerial (ch21-68) UHF	17.50
CM8038 VHF/UHF 625 TV Part Generator	87.50
CM8052 UHF/VHF Pal Colour Bar Generator	215.80
7058 TELETEXT ADAPTOR (Converts any set to remote)	298.00
AMPLIFIED CARAVAN AERIAL (All Channels)	18.50

FUSES

	Pack of 10
1 1/2" QUICK BLOW	48
100ma	48
250ma-500ma-750ma-1A	48
1.5A-2A-2.5A-3A-5A	48
1 1/2" ANTISURGE	
250ma, 500ma, 600ma, 830ma, 750ma, 850ma, 1A, 1.25A	
1.5A, 2A	1.41
2.5A, 3A, 5A	2.18
20mm ANTISURGE	
80ma	3.11
100ma, 180ma, 200ma	2.88
315ma, 500ma, 830ma, 800ma, 1A, 1.25A, 1.6A, 2A	1.97
2.5A, 3.15A	1.43
20mm QUICK BLOW	
100ma	45
250ma, 500ma, 630ma, 800ma,	37
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A	37
1" MAINS	
2A, 3A, 5A, 10A, 13A	84

MAINS DROPPERS

DECCA 20	2.28
R.B.M. A823	77
R.B.M. 181	85
GEC 2000/2018	78
GEC27840	84
PYE 713/15 3R5/15/45R	1.45
PYE 725/31 3R0/58R/27R	84
PYE 725 58R/27R	82
PHILIPS 50501	88
PHILIPS 210/50511/LINK	84
PHILIPS 68/50832	88
PHILIPS 68 47R section	38
THORN 1500	85
THORN 3500	75
THORN 8000	88
THORN 8500	88

SUNDRIES

ANTIFERRE Super Set Top	6.88
ANTIFERRE Car antenna	7.80
ANTIFERRE Xtra Boost UHF Amp.	15.48
ANTIFERRE SB11 Splitter	2.48
Surface Mounting Aerial Outlets	88
Cable Clips	per 100 1.18
Transductor 90°	2.88
EMT Final Anode Cap	53
Delay Line CTAV 82/DL50/SOL141	2.29
EMT Cable 30kV	25p per mtr.
Coax Plugs	pack of 10 1.88
Focus control GEC/THORN	1.83
PVC Tape	7.88
FM Plugs	25
PL259 Plugs	48
DECCA 30 Series width control	58
DECCA 3.9M Modelohm	88
Line Connectors	35
6.3V CRT boost trans	4.25
ANTIFERRE XGB High Gain Aerial (Stereo Channel)	18.88
Reducers for PL259	18
N.B. We have a full range of aerials and accessories available from the trade counter.	

SOLDERING EQUIPMENT

WELLER Iron Kit 15W	3.88
WELLER Iron Kit 25W (inc. tips)	4.88
WELLER Iron 25W	3.88
WELLER 3/18" Single Flat Tips	51
MIN Soldering Iron	5.88
WELLER Heat Gun Kit	14.88
WELLER Heat Gun	11.88
(Pair) Tips for Gun	38
WELLER Cartridge Iron	24.78
ANTEX Soldering Iron 25W	4.88
Solder Remover Sucker	8.50
Solder May	78
500G Heat Solder	7.88
DIY Type Solder	43
250G Solder	3.58

DATA BOOKS NO VAT

Transistor Equivalent	
TVT 80 A-2 only	3.75
TVT 80 2N/2S series only	4.88
TVT 80/80 A-2 and 2N/2S together	7.50
LIN IC Books LIN 1	5.95
LIN 2	5.95

SERVICE AIDS

SERVISOL France-R	88
SUPER SERVISOL	75
SERVISOL Foam Cleanser	78
SERVISOL Plastic Seal	88
SERVISOL Silicone Grease	78
SERVISOL Tubes Silicone Grease	1.88
SERVISOL Aero Klea	83
SERVISOL Aero Duster	78
SERVISOL Excel Polish	52
Penetrating Fluid	78
Fire Extinguisher 640G	1.88
Heat Sink Compound 25G	1.88
Silicone Rubber Tube 1108	2.88

ELECTROLUBE PRODUCTS

Electro-Mech lubricant	1.38
Elect. cleaning solvent	1.58
Freezer	1.38
Foam cleanser	1.88
Heat transfer compound	1.87
Silicone compound	1.81
Special contact fluid (Snorkel)	2.87
Permagard	1.43
Elect. mech lubricant pen	88

HOW TO ORDER

ADD 15% VAT to all Prices.
Add 75p per order P&P - First Class Mail is used whenever possible.



Goods for U.K. supply only.
For orders of very small odd items, i.e. IC's, Trans, Diodes. - Customers need send only 30p.

For Aerosol's please add 30p per can. (These are very heavy!)

Orders over £25 before VAT are Post Free except when the order contains AEROSOLS.

Carriage on Tubes is as stated on list.

ALL ENQUIRIES SAE PLEASE

VAT invoices on request.

We do regret any posted increases but we try our best to give a speedy and efficient service, at a fair price

Same day dispatch

TRANSISTORS, ETC.


Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
AC107	0.48	AU103	2.40	BC282	0.16	BC377	0.28	BD234	0.68	BF222	0.81	BU109	0.82	MG505	0.66
AC117	0.38	AU107	2.75	BC204*	0.39	BC394	0.38	BD235	0.63	BF224 & J	0.72	BR101	0.83	MP5U06	0.76
AC126	0.36	AU110	2.49	BC205*	0.39	BC440	0.82	BD236	0.63	BF240	0.32	BR103	0.64	MP5U5	1.26
AC127	0.84	AU113	2.80	BC206*	0.37	BC441	0.89	BD237	0.68	BF241	0.31	BR303	0.86	MP5U56	1.32
AC128	0.46	BC107*	0.18	BC207*	0.39	BC461	0.78	BD238	0.68	BF244*	0.81	BRC4443	1.76	MP5U60	0.82
AC128K	0.85	BC108*	0.18	BC208*	0.37	BC477	0.30	BD239	0.65	BF245*	0.43	BR339	0.60	MPU131	0.89
AC141	0.85	BC109*	0.16	BC209*	0.39	BC478	0.25	BD410	1.66	BF254	0.48	BR556	0.44	OC26	1.90
AC141K	0.70	BC113	0.22	BC211*	0.36	BC479	0.28	BD433	0.65	BF255	0.58	BSS27	0.92	OC28	1.49
AC142	0.80	BC114	0.22	BC212*	0.17	BC547*	0.13	BD436	0.70	BF256L*	0.49	BT106	1.50	OC29	1.60
AC142K	0.85	BC115	0.24	BC212L*	0.17	BC548*	0.13	BD438	0.71	BF257	0.44	BT109	1.99	OC35	1.28
AC151	0.31	BC118	0.25	BC213*	0.16	BC549*	0.15	BD437	0.74	BF258	0.54	BT116	1.48	OC36	1.28
AC152	0.36	BC117	0.30	BC213L*	0.16	BC550	0.24	BD438	0.75	BF259	0.54	BT119	1.18	OC42	0.90
AC153	0.42	BC118	0.24	BC214*	0.18	BC556	0.23	BD519	0.88	BF262	0.73	BU102	3.38	OC44	0.88
AC153K	0.52	BC119	0.34	BC214L*	0.18	BC557*	0.16	BD520	0.88	BF263	0.88	BU105	1.80	OC45	0.83
AC154	0.41	BC125*	0.30	BC225	0.42	BC558*	0.16	BD599	0.87	BF270	0.70	BU105/02	1.95	OC70	0.85
AC176	0.46	BC126	0.30	BC237*	0.16	BC559*	0.17	BD600	1.23	BF271	0.42	BU108	2.98	OC71	0.73
AC178	0.51	BC132	0.20	BC238*	0.15	BCY10	0.30	BD663BR	0.86	BF272A	0.80	BU126	2.91	OC72	0.70
AC179	0.55	BC134	0.22	BC239*	0.22	BCY30A	1.06	BDX1B	1.55	BF273	0.33	BU204	2.50	OC81	0.83
AC179K	0.56	BC135	0.21	BC251*	0.25	BCY32A	1.19	BDX32	2.95	BF274	0.24	BU205	2.68	OC81D	0.95
AC187K	0.65	BC136	0.22	BC252*	0.26	BCY34A	1.02	BDY16A	0.63	BF336	0.63	BU206	2.89	OC139	1.30
AC188	0.52	BC137	0.30	BC253*	0.38	BD172	1.27	BDY18	1.85	BF337	0.68	BU208	2.78	OC139	1.30
AC189K	0.51	BC138	0.30	BC261A*	0.28	BD175	1.35	BDY20	2.29	BF338	0.68	BU210	1.35	OC139	1.30
AC193K	0.70	BC140	0.36	BC262A*	0.28	BD123	1.50	BDY58	1.38	BF397	0.67	BU277	2.50	OC171	0.82
AC194K	0.74	BC141	0.44	BC263*	0.28	BD124	1.50	BF15	0.48	BF382	0.48	CI06D	0.80	OC200	3.90
AC197	1.20	BC142	0.35	BC267*	0.20	BD130Y	1.56	BF117	0.48	BF363	0.48	CI06F	0.43	OC201	3.95
AC199	0.95	BC143	0.38	BC268*	0.28	BD131	1.58	BF120	0.55	BF370	0.29	CI11E	0.44	OC202	2.40
AC28	0.96	BC147*	0.12	BC286	0.40	BD132	0.68	BF121	0.85	BF451	0.43	OC205	3.95	OC205	3.95
AC39	2.02	BC148*	0.12	BC287	0.49	BD133	0.70	BF123	0.48	BF457	0.46	E300	2.42	OC241	1.98
AD140	1.79	BC149*	0.13	BC291	0.27	BD135	0.37	BF125	0.85	BF458	0.49	E1222	0.47	ON236A	0.94
AD142	1.90	BC152	0.42	BC294	0.37	BD136	0.38	BF127	0.51	BF459	0.82	E5024	0.19	R2008B	2.72
AD143	1.78	BC153	0.38	BC297	0.38	BD137	0.40	BF137F	0.78	BF594	0.16	GE7872	0.48	R2010B	2.79
AD149	1.42	BC154	0.40	BC300	0.42	BD138	0.46	BF137F	0.78	BF595	0.17	GE7872	0.48	R2010B	2.79
AD161	1.86	BC157*	0.15	BC301	0.38	BD139	0.46	BF138	0.47	BF596	0.17	MJ520	1.85	TI311C	0.87
AD161/162	1.22	BC158*	0.12	BC302	0.86	BD140	0.50	BF159	0.27	BF597	0.19	MJ521	0.95	TI322A	0.67
AD162	0.71	BC159*	0.14	BC303	0.84	BD144	2.24	BF160	0.20	BF598	0.20	MJ522	1.20	TI322A	0.67
AF14	1.32	BC160	0.52	BC304	0.44	BD145	0.51	BF161	0.64	BF599	0.20	MJ525	1.20	TI322A	0.67
AF15	1.26	BC161	0.58	BC307*	0.17	BD150A*	0.51	BF162	0.65	BF610	0.29	MJ525	1.20	TI322A	0.67
AF16	1.28	BC167B	0.15	BC308*	0.14	BD155	0.50	BF164	0.95	BF611	0.29	MJ525	1.20	TI322A	0.67
AF17	1.32	BC168B	0.14	BC309*	0.18	BD157	0.51	BF166	0.50	BF612	0.28	MJ525	1.20	TI322A	0.67
AF18	0.85	BC170*	0.15	BC317*	0.18	BD158	0.78	BF167	0.38	BF613	0.28	MJ525	1.20	TI322A	0.67
AF19	1.28	BC171*	0.15	BC318*	0.18	BD159	0.68	BF173	0.35	BF614	0.28	MJ525	1.20	TI322A	0.67
AF20	0.38	BC172*	0.12	BC319*	0.19	BD160	2.89	BF177	0.38	BF615	0.29	MJ525	1.20	TI322A	0.67
AF26	0.36	BC173*	0.15	BC321A&B	0.17	BD163	0.78	BF178	0.58	BF616	0.29	MJ525	1.20	TI322A	0.67
AF27	0.86	BC174A & B	0.28	BC322	0.28	BD166	0.88	BF180	0.53	BF617	0.48	MJ525	1.20	TI322A	0.67
AF139	0.68	BC175	0.26	BC323	1.16	BD175	0.90	BF181	0.53	BF618	0.55	MJ525	1.20	TI322A	0.67
AF147	0.52	BC176	0.22	BC327	0.16	BD177	0.98	BF182	0.44	BF619	1.02	MJ525	1.20	TI322A	0.67
AF149	0.45	BC177*	0.20	BC328	0.18	BD178	0.98	BF183	0.52	BF620	2.58	MJ525	1.20	TI322A	0.67
AF178	1.36	BC178*	0.22	BC337	0.17	BD181	1.94	BF184	0.44	BF621	0.19	MJ525	1.20	TI322A	0.67
AF179	1.36	BC179*	0.28	BC338	0.17	BD182	2.10	BF185	0.42	BF622	0.20	MJ525	1.20	TI322A	0.67
AF180	1.36	BC182*	0.15	BC340	0.19	BD183	1.34	BF186	0.42	BF623	0.65	MJ525	1.20	TI322A	0.67
AF181	1.33	BC182*	0.15	BC347*	0.17	BD184	2.40	BF187	0.44	BF624	0.38	MJ525	1.20	TI322A	0.67
AF186	1.46	BC184*	0.14	BC348A & B	0.17	BD187	1.20	BF188	0.42	BF625	0.42	MJ525	1.20	TI322A	0.67
AF202	0.27	BC183L*	0.15	BC349B	0.17	BD188	1.25	BF189	0.14	BF626	0.38	MJ525	1.20	TI322A	0.67
AF239	0.73	BC184*	0.14	BC350*	0.24	BD222	0.91	BF197	0.15	BF627	0.37	MJ525	1.20	TI322A	0.67
AF240	1.40	BC184L*	0.15	BC351*	0.22	BD225	0.91	BF199	0.29	BF628	0.36	MJ525	1.20	TI322A	0.67
AF279S	0.91	BC185	0.36	BC352A*	0.24	BD232	0.91	BF199	0.29	BF629	0.36	MJ525	1.20	TI322A	0.67
AL100	1.30	BC186	0.25	BC352A*	0.24	BD233	0.91	BF200	0.25	BF630	1.98	MJ525	1.20	TI322A	0.67
AL103	1.59	BC187	0.27	BC360	0.89	BD232	0.82	BF218	0.42	BF632	1.82	MJ525	1.20	TI322A	0.67

Alternative gain versions available on items marked*

For matched pairs add 20p per pair.

LINEAR IC's

Type	Price (£)						
BRC1330	0.83	SN76003N	3.32	TBA240A	3.98	TY114	0.60
CAB100M	2.44	SN76015N	2.52	TBA281	2.07	BY118	1.10
CA3005	1.85	SN76023N	3.52	TBA395*	2.58	BY210	0.20
CA3012	1.45	SN76023ND	2.52	TBA396	2.40	BY212	0.21
CA3014	2.23	SN76023ND	1.40	TBA400	2.20	BY333	0.35
CA3018	0.71	SN76033N	2.20	TBA450Q	1.84	BY340	1.40
CA3020	0.89	SN76110N	1.20	TBA500*	2.21	BY126	2.75
CA3028A	1.80	SN76111N	1.75	TBA510*	2.21	BY178	0.83
CA3028B	1.80	SN76116N	1.80	TBA520*	2.21	BY282	1.14
CA3045	3.75	SN76131N	2.10	TBA540*	2.88	BY184	0.44
CA3046	0.70	SN76226N	2.60	TBA550*	3.13	BY189	5.30
CA3065	1.74	SN76227N	1.61	TBA560*	3.18	BY190	4.90
CA3068	1.90	SN76228N	1.80	TBA570*	3.29	BY206	0.26
CA3130S	1.57	SN76502N	1.92	TBA611B	2.68	BY238	0.25
FCH181	2.40	SN76530P	0.97	TBA841	2.55	BYX10	0.20
FCJ101	3.32	SN76533N	1.38	TBA841A12	2.55	BYX38/800	0.70
LM309K	1.98	SN76544N	1.85	TBA841B11	2.90	BYX70/500	0.63
LM390N-14	1.08	SN76548N	1.85	TBA851	2.42	E299DH	0.08
LM1303N	1.03	SN76570N	1.81	TBA873	2.31	IT74	0.68
MC1307P	1.82	SN76620AN	1.81	TBA900*	2.50	IT210	0.63
MC1310P*	1.84	SN76650N	0.99	TBA720AQ	2.38	IT827	0.80
MC1312P	2.34	SN76650N	1.48	TBA720Q	2.38	IT828	0.80
MC1327P*	1.86	SN76660N	0.64	TBA750*	2.18	IT829	0.80
MC1330P*	0.83	SN76666N	0.9				

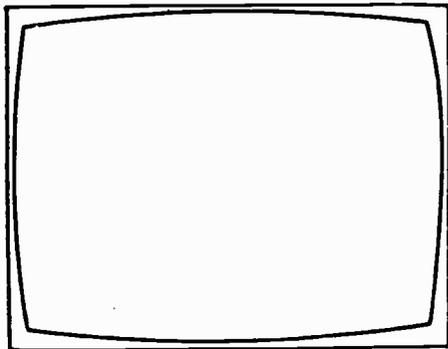

TELEVISION

Futurology

Maybe I'm getting old, or maybe some real change in human expectations has come about, but whichever it is I find it harder and harder to look into the future and see anything other than more of the same – plus some rather grisly thoughts, such as will all those military rockets and things remain unused? It wasn't always the same. There was a time when you could really see the world changing around you – “modern architecture”, the streamlining of cars, trains, household appliances, and so on. The 1939-45 war produced, as wars usually do, major technological breakthroughs, and for those of us then young the prospect seemed to be one of endless scientific innovation. For a time it appeared to be turning out just so. The breaking of the sound barrier; the discovery of the transistor effect and the consequences this had for electronics; the achievement of rocket thrust sufficient to escape gravity; nuclear power; the development of computers both large and small – to name only some obvious items. More recently, men have walked on the moon, rockets have sent pictures back from Saturn, while satellite communications have, in one sense, made the world a smaller place. Yet we don't seem to be all that good at feeding ourselves, keeping the peace, or providing even basic amenities for a large proportion of mankind.

In the past, some prophets have been remarkably perceptive. *Wireless World* last month reprinted Arthur C. Clarke's famed article of October 1945, in which he predicted satellite broadcasting and communications. At that time it was still an open question as to whether rocket propulsion could ever attain the velocity required to achieve an orbital station. Despite that, Arthur Clarke was able to predict a complete system – the orbital positions for geostationary satellites, and transmitter powers and frequencies. He was a bit out in mentioning solar engines “which employ mirrors to concentrate sunlight on the boiler of a low-power steam engine”, but did go on to talk of “photo-electric developments (that) may make it possible to utilise the solar energy more directly.” In fact he got it about 95% right, which was truly remarkable (he'd certainly done his homework first).

The field of radio/electronics has never been short of prophets – predictions of television, stereo and so forth go back far in time. The only thing that wasn't foreseen was the development of semiconductor technology – the transistor was discovered almost by accident, though once it was understood all manner of developments followed. Right now however one has this feeling that most of what's feasible has already been achieved. Three-dimensional TV is still not a practical proposition; there are those who feel that larger displays with high-definition TV systems are a prospect for the not too distant future; there's all this talk about the information age; and those video discs haven't yet reached the high street shops. Let's look at these briefly.

I remember seeing 3-D TV at an Earl's Court Radio Show in the fifties: very good, but you had to wear special glasses. A cable company in California experimented with 3-D TV some months back, using specially processed tapes, but again the viewer required special glasses. At this Summer's Chicago Consumer Electronics Show, Matsushita demonstrated a system in which left- and right-eye signals from a pair of cameras were displayed on alternate fields – the special glasses this time had shutters that were synchronised with the left- and right-eye fields. No one would be very happy watching for any length of time under these conditions.

A lot of work seems to be going into the development of high-definition TV systems at present – with 1,000 lines or so. Apart from bandwidth, the problems are not all that great, but the fact is that 625 lines provide perfectly adequate definition for viewing under normal domestic conditions. In fact some of the work on high definition TV seems to have more to do with achieving equivalent definition to 35mm film, with the aim of simplifying programme making. As for the information age, the computer has indeed enabled vast stores of information to be easily tapped – but how many people need access to it, and for what purposes? Very few one suspects, and only for specific reasons such as stock control and so on. More important is the way in which the microprocessor has added a new dimension to automation, but that's another matter entirely.

The video disc is already giving rise to second thoughts – because the more versatile VCR has established itself so rapidly. Discs may be cheaper and give superior quality, but once people have become used to cassettes and to recording what they want when they want, will they take to discs as a second source of video material?

One's left with the feeling that apart from shoving a dish aerial on the roof in a few years' time, dual-channel sound, and continuing improvements to existing video/TV hardware, there's not all that much to look forward to. Does it matter? Well, it could be a part of the reason for the advanced economies running out of steam, and if that gets much worse one wonders how the wider problems of poverty, decay and so on can ever be tackled.

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTISEMENT MANAGER

Roy Smith

01-261 6671

CLASSIFIED ADVERTISEMENTS

Colin R. Brown

01-261 5762

COVER PHOTO

Our cover photograph this month shows the printed-circuit boards (main and c.r.t. base) used in the new Decca/Tatung 120 series chassis. Our thanks to Tatung (UK) Ltd. for supplying this.

CORRECTION

The value of the capacitor added across transistor T1535 in the Philips K30 and KT3 chassis (to increase the field flyback blanking period) was given as 15pF instead of the correct 0.015 μ F on page 409 of our June 1981 issue (see Service Notes from Philips).

LLJ

Les has been inundated with sets that keep going hrrump bonk. Never fear, he'll be back with us next month.

QUERY SERVICE

We regret the need to increase the charge for replying to readers' servicing queries to £1 (including VAT) from this issue. It's some two years since the charge was last increased, and inflation continues to affect our costs.

value of the flyback tuning capacitor to be selected so that, without having to increase the transistor's maximum voltage rating, the scan coils can be driven from a secondary winding on the transformer – in the TX10, the “flyback” pulse is used only to provide an input to the diode-split e.h.t. rectifier system.

The new circuit will operate with mains voltages between 165-265V. The source impedance of the e.h.t. system is low (i.e. good e.h.t. regulation), and the overall power consumption is less than 40W. It seems bound to turn up in someone's chassis sooner or later.

TELETEXT RETROFIT KIT

ITT have introduced a simple teletext “retrofit” kit to enable remote control versions of their current 22in. and 26in. Trimline models to be converted for teletext use “in a matter of minutes”. The conversion kit has three colour-coded plug-in connectors, and can be held by the dealer in his showroom and used to convert existing stock as required. The idea is to be able to sell “teletext ready” sets to customers who are hesitant about whether or not they want teletext. ITT also report that 35% of all TV sets now being sold feature some form of remote control.

NEW THORN PORTABLES

The latest Thorn portables – the 1696-1697 series – employ a compact, horizontally mounted panel with low component count – five i.c.s, including the 33V stabiliser, and seven transistors. The i.f. strip uses a BF199/SAWF/TDA440 combination, the intercarrier sound/audio channel a TDA3190, the field timebase a TDA1044 and the sync/line generator department a TDA1180. A BC308A is used for a.g.c. inversion, a BF391 for video output and a BU807 as the line output device. The series regulator is a bit unusual for Thorn in employing a differential amplifier as the error detector. Rotary tuning is retained with the varicap tuner, and the tube operates with a 90V first anode supply. Initial models are the 38000 and 38010 (12in.), and the 3870 and 3871 (14in.).

TAKE IT TO SOTHEBY'S

Amongst the things now being handled by the Belgravia, London branch of Sotheby's is vintage TV sets. At a recent auction a set dating from the late forties, with a walnut-veneered cabinet and 13in. viewing mirror in the top, sold for £286. The set also incorporated a radio receiver. Our report didn't mention the make, but it sounds like one of those EMI sets (see for example our October 1980 issue).

ENHANCED TELETEXT

As part of a development programme supported by the Department of Industry, the BBC has produced equipment for use in studying the enhancement of the UK teletext system. One of the initial uses was in the development of an improved teletext decoder using high-quality character generation. When the teletext specification was written five years ago, improvements were anticipated and the shape and style of the characters were left undefined: spare signalling capacity was provided to enable improved character sets to be used. Advances in i.c. technology have now made such character generators, which are compatible with current transmissions, feasible, and it's expected that manufacturers will in due course provide the option of decoders that give higher-quality character displays.

Further use of the equipment will be in investigating



This photograph of the Ceefax Citynews Diary page shows the much improved text quality that can be obtained from recent BBC teletext transmissions.

coding methods for high-quality graphics, using the redefinable character, alphageometric and alphaphotographic techniques. Demonstrations have already been carried out at the June IEEE Conference in Chicago and at the Berlin Radio Show.

VIDEO PROGRAMME VENTURE

Thorn EMI Video Programmes and MCA Video Disc have formed a joint venture international video programme production company based in Los Angeles. The aim is to draw on the resources of the two partners and to produce video programmes anywhere in the world, with the emphasis on material for the VHD and LaserVision disc systems (MCA produce the LaserVision discs in the USA). It seems that the movie world is fast moving into video, which brings us to our next item.


HIGH-DEFINITION TV

Various firms are working on high definition TV systems. Sony recently demonstrated a 1,125-line, 60-field system, and in Europe a 1,250-line system has been proposed. Since the latter is 2×625 lines, the idea is that a dual-standard signal source could be provided, with every other line being used for 625-line equipment. The higher-definition signals would be used with large-screen projectors. The Sony system, which uses three 30MHz RGB channels, is aimed at giving picture quality at least equal to that obtained with 35mm. film. The idea is to simplify programme production, with the programme material stored using a new lin., wideband tape system. It's understood that the system matches up with conventional standards conversion coding arrangements.

NEW VCRs

New “basic” VCRs have been introduced by JVC and Ferguson – Models HR7200 and 3V29 respectively. The machines have similar specifications but differ markedly in styling and control layout. Ferguson have also introduced an up-rated version of the machine, Model 3V30, featuring Dolby noise reduction, a more sophisticated timer unit, and remote control as standard. There is no JVC equivalent to this machine, whose specification was devised by Thorn.

Also new to the Thorn range is the 3V28

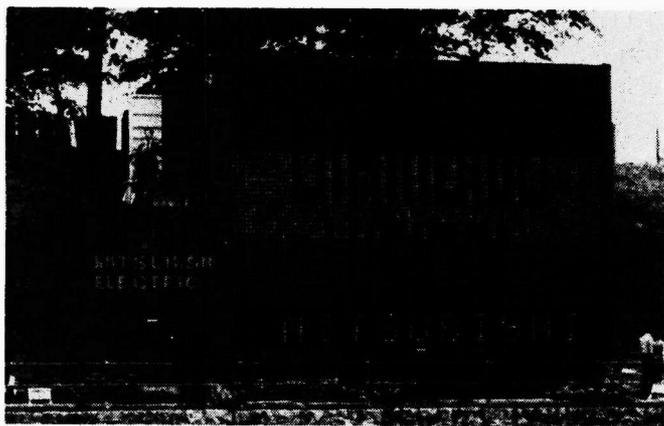

The world's "largest portable colour television", the Mitsubishi "Diamond Vision". The picture is produced by a matrix of 192 x 130 2in. colour tubes. Photo by George Egerton.

tuner/timer/mains adaptor/battery charger unit, which is designed for use with the 3V24 portable VCR. The new combination enables eight programmes to be recorded over fourteen days, with serial recording if required. There's also a ten-minute battery back-up facility for clock and programming.

Philips have introduced two new V2000 system machines, the VR2021 which replaces the original VR2020, and the VR2022 which includes the additional features of freeze-frame and fast picture search both forwards and backwards.

CLEANING TAPE FROM SONY

Sony have introduced a cleaning cassette, type L25CL, for use with Betamax VCRs. The cassette is inserted, run for half a minute, then removed without rewinding. If an obvious improvement with a short test recording is not obtained, the machine requires servicing attention. The tape, which should give some 200 cleaning operations, is expected to retail at around £10.

MANOR SUPPLIES TEST GENERATOR

The new Mk. V colour test pattern generator from Manor Supplies certainly has a lot to offer for £90.50 (kit plus deluxe case, VAT and post/packing). There are 40 different patterns and variations, available at u.h.f. or video, for checking TV sets and VCRs. The kit is easy to build, with only two adjustments – no special test equipment is required. The u.h.f. output is to broadcast standard, fully interlaced and with correct picture blanking.

NEWS FROM GRUNDIG

Grundig have introduced a new range of nine TV sets in the UK, with screen sizes from 14½in. to 26in., using the new Grundig Compact Universal Chassis. The remote control models can be converted for teletext operation simply by fitting an extra PCB.

Looking ahead, Grundig have secured a technical agreement with the Japanese developers of the Funai compact cassette combined video camera/recorder. The Funai "cam-corder" was shown by Sulkin at the May trade shows earlier this year. Grundig's agreement includes PAL system rights.

A few early Grundig 2 x 4 VCRs had lip synchronisation problems when used with cassettes

recorded on Philips V2000 series machines – due to the sound heads being mounted in slightly different positions. The machines concerned have serial numbers whose first three digits of the six digit number are 009 or less – the number is on a yellow and orange label at the back. Grundig have now offered to modify these machines free of charge.

MITSUBISHI'S DIAMOND VISION

Heralded as "the largest portable colour television in the world", Mitsubishi's "Diamond Vision" was installed opposite Caernarfon Castle to relay the Royal Wedding live earlier this year. The massive screen, 6 x 8m (i.e. almost 40ft.), consists of a matrix of 24,960 separate 2in. red, green and blue c.r.t.s arranged in RGRGRG and GBGBGB form on alternate rows, i.e. there are twice as many green tubes as blue and red ones. Reader Glyn Dickinson reports that the picture was sharp, even in bright sunlight – and the geometry first class! Sound is provided by horn speakers mounted above the screen, computer techniques being used to form the picture, i.e. generate the drives to the c.r.t.s. Apparently Mitsubishi have four of these displays world wide, the other three being permanently sited in Japan and the USA.

AERIAL EQUIPMENT

Wolsey Electronics have introduced a new range of high-gain aerials with multidirector assemblies. There are two models, the HG20 with eight director assemblies and the HG36 with 16 director assemblies. Gain figures quoted are 15dB and 18dB respectively. The HG36 offers an improved beamwidth ($\pm 15^\circ$) and front-to-back ratio.

Antiference have introduced a new range of single-stage masthead preamplifiers – Models UP1300/W and UP1300/V for u.h.f. and v.h.f. respectively. There are accompanying power supplies and diplexers.

TRANSMITTER NEWS

The following relay transmitters are now in operation:

Belcoo (Fermanagh) Ulster television ch. 41, BBC-2 ch. 44, TV4 (future) ch. 47, BBC-1 ch. 51.

Braemar (Scotland) BBC-1 ch. 39, Grampian Television ch. 42, BBC-2 ch. 45, TV4 (future) ch. 49.

Bushmills (Co. Antrim) Ulster Television ch. 41, BBC-2 ch. 44, TV4 (future) ch. 47, BBC-1 ch. 51.

Cilfrew (Glamorgan) BBC-Wales ch. 39, BBC-2 ch. 45, HTV-Wales ch. 49, Sianel 4 Cymru (future) ch. 52.

Gortnalee (Fermanagh) BBC-1 ch. 21, Ulster Television ch. 24, BBC-2 ch. 27, TV4 (future) ch. 31.

Gulval (Cornwall) Westward Television ch. 23, BBC-2 ch. 26, TV4 (future) ch. 29, BBC-1 ch. 33.

Plymouth (Victoria Park) BBC-1 ch. 40, Westward Television ch. 43, BBC-2 ch. 46, TV4 (future) ch. 50.

Lavington (Wiltshire) BBC-1 ch. 21, HTV-West ch. 24, BBC-2 ch. 27, TV4 (future) ch. 31.


Workington (Cumbria) TV4 (future) ch. 54, BBC-1 ch. 58, Border Television ch. 61, BBC-2 ch. 64.

The above transmissions are all vertically polarised.

The Home Office has approved the use of two extra lines per field for teletext transmissions. The following lines will be used: 15, 16, 17, 18. Under the terms of the IBA's Code for Teletext Transmissions, advertising pages may not exceed 15% of the total number of pages and adverts carried on otherwise editorial pages may not exceed 15% of the page area.

**THE VERY LATEST SC110 LOW POWER,
FULLY PORTABLE OSCILLOSCOPE.**

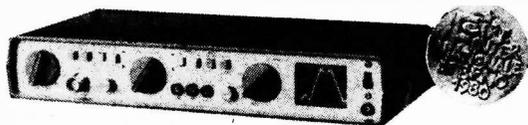The new Thandar SC110 represents a break-through in oscilloscope development. The SC110 is LESS THAN TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope.



1980 GOLD MEDAL winner of the B.R.N.O. EXHIBITION, the largest Trade Fair held in Eastern Europe.

Full Sized Performance

- 10 MHz bandwidth.
- 10 mV per division sensitivity.
- Full trigger facilities are provided including TV frame, or TV filtering.
- Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- Size 255mm x 148mm x 50mm.

- Scope **£139.00** + £20.85 V.A.T.
 - Carry case **£7.70** + £1.16 V.A.T.
 - x 1 Probe **£8.50** + £1.28 V.A.T.
 - x 10 Probe **£10.00** + £1.50 V.A.T.
 - (AC Adaptor **£4.95** + £0.74 V.A.T.)
- (Overseas purchasers please state voltage.)
Re-chargeable cells **£7.50** + £1.13 V.A.T.

THANDAR TM354 HAND HELD LCD DIGITAL MULTIMETER

The TM354 is a compact 3½ digit hand held multimeter featuring a **LARGE 0.5"** liquid crystal display, 0.75% basic accuracy and a **2000 HOUR** battery life. The meter provides five functions in fourteen ranges.



- DC voltages 1mV to 1000V
- AC voltages 1V to 500V
- DC current 1µA to 2Amps
- Resistance 1Ω to 2MΩ
- Diode check

Complete with test prods and vinyl pouch.
£39.95 + £5.99 V.A.T.

World-wide post free service. Overseas orders welcome. Please deduct U.K. V.A.T. Mail Order only. Callers by appointment. Barclaycard/Access orders welcome, Cheque/Bank draft etc., with order please.

Large S.A.E. for technical leaflet and complete Thandar list.

B. K. ELECTRONICS, Dept. 'T',
37 Whitehouse Meadows, Eastwood,
Leigh-on-Sea, Essex SS9 5TY.
Tel: (0702) 527572.

LOOK!

Phone: LUTON
BEDS. 38716

**OPPORTUNITIES
TRADE SALES**

**ALL SETS GUARANTEED
COMPLETE**

OVER SIX HUNDRED SETS

ALWAYS IN STOCK

Pye 20T, Philips G8;

Ferguson 3-3k5

Murphy, Bush, Decca, GEC

All from

£35.00 £50.00

Square Screen, Mono's from

£5.00 ALL MODELS

Sets for spares from

£2.00

All include VAT

OPPORTUNITIES

9A, Chapel Street, Luton, Beds.

LUTON 38716

9.30-6.00 p.m. Weekdays, 10.30-1.00 p.m. Sundays.

Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs - and they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

City and Guilds Certificates:-

Telecommunications Technicians,
Radio, TV and Electronics Technicians,
Electrical Installation Work,
Technical Communications,
Radio Amateur,
MPT General Radio Communications Certificate.

Diploma Courses:-

Electronic Engineering,
Electrical Engineering,
Computer Engineering,
Radio, TV, Audio Engineering, Servicing and Maintenance. (inc. Colour TV)
New Self-Build Radio Courses with Free Kits.

Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful - at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name

Address.....

..... Phone No:

ICS International Correspondence Schools,
Dept. 285N Intertext House,
LONDON SW8 4UJ. Tel. 622 9911
(all hours)

Interested in Television Servicing?

Try a ZED Pack. Effect Repairs at Minimum Cost.

Z1 300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt and miniature resistors £1.95	Z20 10 Assorted switches including: Pushbutton, Slide, Multipole, Miniature etc. Fantastic Value £1.20	Z44 TO3 Mounting kits (BU208) 8 for 60p
Z2 150 mixed 1 and 2 watt resistors £1.95	Z21 100 Assorted Silver Mica caps £2.20	Z45 TO220 Mounting kits (TIP33) 10 for 60p
Z3 300 mixed capacitors, most types amazing value £3.95	Z22 10 Mixed TV convergence Pots £1.00	Z46 TO126 Mounting kits (BD131) 12 for 60p
Z4 100 mixed electrolytics £2.20	Z23 20 Assorted TV Knobs including: Push Button, Aluminium and Control types £1.20	Z47 Pack of each Mounting kit. All include insulators and washers £1.50
Z5 100 mixed Polystyrene Capacitors £2.20	Z24 10 Assorted Valve bases B9A, EHT, etc. £1.00	Z48 3a 1000v Diodes (IN5408 type) 8 for £1.00
Z6 300 mixed Printed Circuit Components £1.95	Z25 10 Spark Gaps £1.00	Z49 Brushed Aluminium Push Button Knobs, 15mm long x 11mm Diam. Fit standard $3\frac{1}{4}$ mm square shafts 10 for £1.00
Z7 300 mixed Printed Circuit resistors £1.45	Z26 20 Assorted Sync Diode Blocks £1.00	Z50 Chrome finish 10mm x 10mm Diam as above 10 for £1.00
Z8 100 mixed High Wattage Resistors, wirewounds etc. £2.95	Z27 12 Assorted IC Sockets £1.00	Z51 Aluminium Finish. Standard Fitting Slider Knobs. (Decca) 10 for £1.00
Z9 100 mixed Miniature Ceramic and Plate caps £1.50	Z28 20 General Purpose Germanium Diodes £1.00	Z52 Decca "Bradford" Control Knobs Black and Chrome. $\frac{1}{4}$ " Shaft 8 for £1.00
Z10 25 Assorted Potentiometers £1.50	Z29 20 Assorted Miniature Tantalum Capacitors. Superb Buy at 40 Miniature Terry clips, ideal for small Tools etc. £1.00	Z53 Tuner P/B Knobs, Black and Chrome. Fit most small Diam Shafts, ITT, THORN, GEC etc. 8 for £1.00
Z11 25 Assorted Presets, Skeleton etc. £1.00	Z30 5 CTV Tube Bases £1.00	Z54 Spun Aluminium Control Knobs (ITT) $\frac{1}{4}$ " Shaft, suitable for most sets with recessed spindles 8 for £1.00
Z12 20 Assorted VDR's and Thermistors £1.20	Z31 10 EY87/DY87 EHT bases £1.00	Z55 14 Pin DIL I.C. Sockets 12 for £1.00
Z13 1 lb Mixed Hardware, Nuts, Bolts, Selftappers, "P" clips etc. £1.20	Z32 20xPP3 Battery Connectors £1.00	Z56 16 Pin Quil I.C. Sockets 12 for £1.00
Z14 100 mixed New and marked transistors, all full spec. includes: PBC108, BC148, BF154, BF274, BC121L, BC238, BC184L and/or Lots of similar types ONLY £4.95	Z33 6x Miniature "Press to Make" Switches, Red Knob £1.00	Z57 16 Pin DIL TO QUIL I.C. Sockets 10 for £1.00
(Z14A) 200 Transistors as above but including power types like BD131, 2N3055, AC128, BFY50 etc. £9.95	Z34 12 Sub Min S.P.C.O. Slide Switches £1.00	Z58 22 Pin DIL I.C. Sockets 10 for £1.00
Z15 100 Mixed Diodes including: Zener, Power, Bridge, Signal, Germanium, Silicon etc. All full spec. £4.95	Z35 12 Min D.P.C.O. Slide Switches £1.00	Z59 B9A Valve Bases P.C. Type 20 for £1.00
Z16 20 IN4148 Gen Purpose Diodes £1.00	Z36 8 Standard 2 Pole 3 Pos Switches £1.00	Z60 0.47 Ω $\frac{1}{2}$ Watt Emitter Resistors 40 for £1.00
Z17 20 IN4003/10D2 £1.00	Z37 4xHP11 Batt Holders (2x2 Flat type) 4 for £1.00	Z61 Chassis Coax. Socket 6 for £1.00
Z18 20 Assorted Zeners. 1 watt and 400 mw £1.50	Z38 3.5mm Jack Sockets, switched, enclosed Type 8 for £1.00	Z62 Chassis 5 Pin Din Socket. 8 for £1.00

ELECTROLYTIC

1 μ f 63v	20 for £1.00
1 μ f 350v	10 for £1.00
2.2 μ f 63v	20 for £1.00
4.7 μ f 63v	20 for £1.00
4 μ f 350v*	10 for £1.00
10 μ f 400v	8 for £1.00
22 μ f 16v	20 for £1.00
100 μ f 25v	20 for £1.20
160 μ f 25v*	20 for £1.50
330 μ f 25v	10 for £1.00
400 μ f 40v*	8 for £1.00
470 μ f 25v	10 for £1.00
470 μ f 35v	8 for £1.00
1000 μ f 16v	10 for £1.00
1000 μ f 25v*	8 for £1.00
1000 μ f 35v	6 for £1.00

TANTALUM

0.15 μ f 40v	12 for £1.00
0.22 μ f 10v	12 for £1.00
0.33 μ f 40v	12 for £1.00
0.47 μ f 40v	12 for £1.00
0.68 μ f 40v	12 for £1.00
2.2 μ f 40v	12 for £1.00
3.3 μ f 16v	12 for £1.00
12 of each value	£6.00
Pack of 20 Assorted, our selection	£1.20

SPECIAL OFFERS

100 Assorted Polyester Capacitors. Mullard C296's and others	
160v-400v only	£2.00
100 Assorted Mullard C280's Cosmetic imperfections etc.	£2.00
200 Mullard Miniature Electrolytics Cosmetic imperfections etc.	£2.00
PACK OF EACH	£5.00

ZENER DIODES

0v7, 2v7, 4v3, 4v7, 5v6, 6v2, 6v8, 7v5, 27v, 30v. ALL 400mw.	
10 of one value	80p
10 of each	£6.60
1.3 watt, 12v, 13v, 18v	
10 of one value	£1.00
10 of each	£2.50

DIODES

25 x IN4002	£1.00
10 x SKE 4F2/06 (600v 2a fast switching)	£1.00
12 x BY127	£1.00
10 x BA158 (600v 400ma)	£1.00
IN5402 3a 200v	8 for £1.00
BY142 3a 1.750v	5 for £1.00
6A. 100V. Bridge Rectifier. Very small.	80p ea. 3 for £2.00

I.C.'s

CA270AE	£1.00	6 for £5.00
MC1327P	£1.00	6 for £5.00
TB810P	£1.00	6 for £5.00
555 Timer 30p		4 for £1.00

LEDS

3mm Crystal Clear, very pretty.	
Red, Green, Yellow.	
10 of one colour	£1.00
10 of each	£2.50
TIL209 3mm Red	12 for £1.00
5mm Red	10 for £1.00
Red Triangle	8 for £1.00
Green Rectangle	8 for £1.00
Infra Red, LED Transmitter, Til 38.	
Hi-Power.	50p each. 3 for £1.00

MISCELLANEOUS

Line Output transformer for RBM 823A	£4.25 each, 3 for £10.00
ITT VC200 4P/B Transistor Tuner. Suitable for some Pye and Philips sets. 3 hole fixing	£2.75 each
Decca Bradford Tuners. 5 button type	£3.00 each, 5 for £12.50
Decca Bradford Triplers	£3.00 each
UHF Modulator UHF out Video in. Ch. 36. 21"x2"x1" complete with 9 foot coaxial lead and plug. With connection data	£3.00 each, 2 for £5.00
Video Game Boards. All new but incomplete. Hundreds of useful components. C.M.O.S. IC's, transistors, diodes, sockets, switches etc. Pack of five assorted boards	£2.50
GEC Hybrid 2040 series Focus Assembly with lead and VDR rod	£2.00 each, 3 for £5.00
Convergence Panel for above. Brand new leads and plug.	£3.00 each
GEC 2010 Transistor Rotary Tuner with AE, SKT, and leads	£1.95 each, 3 for £5.00
Bush CTV 25 Quadrupler type Q25B equivalent to ITT TU25 3QK	£3.00 each, 2 for £5.00
PYE 697 Line and power Panel, damaged with some components missing but ideal for spares	£2.20 each, 3 for £6.00
Grundig UHF/VHF Varicap Tuner for 1500 GB, 3010 GB	£12.50 each, 3 for £30.00
EHT Lead with Anode cap (CTV) suitable for split Diodes sets 1m long	60p each, 3 for £1.50
EHT Cable	30p per metre. 10 metres £2.50
Anti Corona Caps	3 for £1.00
4.433 Mhz CTV Crystals	£1.00 each, 3 for £2.50
Cassette Mains Leads. 7ft with fig 8 plug	60p each, 3 for £1.50
6 MHz sound filters, ceramic 3 pin "TAIYO" type	50p each, 3 for £1.00
10.7 MHz Ceramic Filters "Vernitron" FM4	50p each, 3 for £1.00
PYE CT200 Control Knobs	8 for £1.00
High quality Metal Coax Plug. Grub screw fixing	5 for £1.00, 100 for £12.50
Cassette/Calc Leads. 2m long, figure 8 skt. to flat pin.	60p each, 3 for £1.50
3.5mm Jack Plug on 2m of screened lead	5 for £1.00
T.V. Game Remote Controls. Contains 22k thumbwheel pot on 2m of screened lead with 3.5mm plug	2 for £1.00
Mains Neons	10 for £1.00
Mini Grundig Motors. Regulated, variable.	
9/16" x 1/4" 1-6V	60p each, 3 for £1.50
2k2 Screenfeed Resistors.	
White ceramic, 9 watt, with fusible link.	8 for £1.00
Phillips G8 Transductor.	£1.20 each, 3 for £3.00
Mullard LP1173, 10 watt.	
Amplifier module with circuit diagram.	£3.50 each, 2 for £6.00
E.H.T. Discharge probe, with heavily insulated handle, with lead and chassis connector.	60p each, 3 for £1.50

CAN TYPES

100+200 350v	£1.00
2000 μ f 100v	£1.00
1000 μ f 100v	60p
2.200 μ f 40v	60p
2.200 μ f 63v	70p
3.500 μ f 35v	50p
220 μ f 400v ITT/RBM	£1.00
10,000 μ f 35v 24"x1 1/2" with fixing stud and nut.	£1.00 6 for £5.00

TRANSISTORS

BC154, BC149, BC157, BF195, BF495, PBC108, BF393S	
12 of one type	£1.00
12 of each	£6.00
2N3055H	60p each
BD181	50p each
BD131	4 for £1.00
BD132	4 for £1.00

CONVERGENCE POTS

5 Ω , 10 Ω , 20 Ω , 30 Ω , 50 Ω , 100 Ω , 200 Ω , 1K. 8 of one type	£1.00. 8 of each type £6.00.
--	-------------------------------------

THORN SPARES

"3500" Transductor	£1.20, 3 for £3.00
"3500" Focus Assembly with VDR	£1.50
"8500" Focus Assembly. Rotary type	£1.50, 3 for £4.00
"8500".0022 2000v Line Capacitor	10 for £1.00
"1590/91" Portable metal boost Diode (W11)	5 for £1.00
"1500" Bias Caps 160 μ f 25v	20 for £1.50
"1500" Jellypot. L.O.P.T. Pinkspot	£3.50
"900/950" 3 stick triplers	£1.00, 3 for £2.50
"1600" Dropper 18 + 320 + 70 + 39 Ω	3 for £1.50
"950" Can. 100 + 300 + 100 + 16 μ f	£1.00

THYRISTOR

SS106 (BT106)	65p each
3 for £1.50, 10 for £4.50	

33v REGULATOR

Equivalent to TAA550, SN76550, ZTK33 etc. **8 for £1.00**

EHT STICKS

TV18 KV	50p each, 3 for £1.00
Replacement Tripler Sticks (Thorn)	10 for £1.00

EHT DIODES

Very small. 20kV 2.5ma. 30ma peak **50p ea. 3 for £1.00**

GEMINI ELECTRONIC COMPONENTS

Dept. TV, The Warehouse, Speedwell Street, London S.E.8.

Please quote ZED code where shown. Send cheque* or Postal Order. Add 60p P&P and 15% VAT.

*Schools etc. SEND OFFICIAL ORDER

ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8.

Send Large S.A.E. for list of Quantity, Prices and Clearance Lines etc.

THORN SPARES

"3500" Transductor	£1.20, 3 for £3.00
"3500" Focus Assembly with VDR	£1.50
"8500" Focus Assembly. Rotary type	£1.50, 3 for £4.00
"8500".0022 2000v Line Capacitor	10 for £1.00
"1590/91" Portable metal boost Diode (W11)	5 for £1.00
"1500" Bias Caps 160 μ f 25v	20 for £1.50
"1500" Jellypot. L.O.P.T. Pinkspot	£3.50
"900/950" 3 stick triplers	£1.00, 3 for £2.50
"1600" Dropper 18 + 320 + 70 + 39 Ω	3 for £1.50
"950" Can. 100 + 300 + 100 + 16 μ f	£1.00

THORN SPARES

"3500" Transductor	£1.20, 3 for £3.00
"3500" Focus Assembly with VDR	£1.50
"8500" Focus Assembly. Rotary type	£1.50, 3 for £4.00
"8500".0022 2000v Line Capacitor	10 for £1.00
"1590/91" Portable metal boost Diode (W11)	5 for £1.00
"1500" Bias Caps 160 μ f 25v	20 for £1.50
"1500" Jellypot. L.O.P.T. Pinkspot	£3.50
"900/950" 3 stick triplers	£1.00, 3 for £2.50
"1600" Dropper 18 + 320 + 70 + 39 Ω	3 for £1.50
"950" Can. 100 + 300 + 100 + 16 μ f	£1.00

THORN SPARES

"3500" Transductor	£1.20, 3 for £3.00
"3500" Focus Assembly with VDR	£1.50
"8500" Focus Assembly. Rotary type	£1.50, 3 for £4.00
"8500".0022 2000v Line Capacitor	10 for £1.00
"1590/91" Portable metal boost Diode (W11)	5 for £1.00
"1500" Bias Caps 160 μ f 25v	20 for £1.50
"1500" Jellypot. L.O.P.T. Pinkspot	£3.50
"900/950" 3 stick triplers	£1.00, 3 for £2.50
"1600" Dropper 18 + 320 + 70 + 39 Ω	3 for £1.50
"950" Can. 100 + 300 + 100 + 16 μ f	£1.00

TV Receiver Design: The Decca/Tatung 120 Series

Ray Wilkinson

HANDEL is supposed to have taken only three weeks to produce the "Messiah", but he used material he'd written previously. Looking at my notebook I see that our laboratory at Bradford developed the Decca 120 colour chassis in about a year though, as you'll see, we used some "previous material" in the form of proven circuitry from the preceding 70/90/110 series chassis.

Design Considerations

Before going into the details of the new chassis I'll summarize briefly some of the factors we had to consider in arriving at the final design. This will illustrate why particular electronic and mechanical arrangements were adopted.

First, the range of models. We started off by producing a low-cost 14in. colour portable for the UK market. The early prototypes looked good, so we thought maybe it would drive bigger tubes successfully – say 20in. ones. Then we thought we might be able to adapt it for v.h.f. reception for export. And so, quite soon, the basic requirements expanded to cover the full range of possibilities – driving 14-22in. 90° tubes and 22-26in. 110° tubes, with receivers for the home and export markets. In other words, the chassis had to be capable of working in a sophisticated full-facility large-screen set as well as our original starting point, a bottom of the range portable. This meant a small chassis with very good performance, easily adaptable to different broadcast standards and colour systems and to more sophisticated control and channel selection arrangements. On top of which it had to be inexpensive to produce!

To cater for the variety of control arrangements envisaged, with infra-red remote control one of the options, all the customer controls (colour, brightness, contrast and volume) had to operate with d.c. voltages. In order to drive the 30AX 110° tube on the other hand slightly different timebase circuitry was required: this variant came to be known as the 130 chassis. At least three-quarters of the 120 and 130 series chassis are identical however, reducing considerably the design, manufacturing, testing and servicing problems.

Our other main objectives with the design, compared to our previous chassis, were: cost reduction; as good or better performance, particularly in respect of the picture and sound quality and reception under adverse signal conditions; and as good or better reliability.

Let's take cost reduction first. It's comparatively easy to reduce costs if performance and/or potential reliability are degraded. This doesn't do your reputation much good however. We went about the problem by reducing the component count (these chassis use the least number of components of any chassis known to us); by reducing the size (and quantity) of printed circuit boards – all the circuitry except that on the c.r.t. base panel is on a single board; and by improvements in production methods – for example a larger percentage of the components are auto-


inserted, which provides the bonus of increased consistency with a dramatic reduction in the number of rejects at the test station. The auto-insertion machine determined the maximum size of the main board – two of them can just be accommodated on its table.

The standard of performance achieved is the result of careful attention in the design to each parameter, usually working in close contact with i.c. manufacturers whose recommendations for device usage often require modification and some redesign before they can be used in a practical receiver design that's to go into large-scale production. We've optimised the transient response of the i.f. and video amplifiers for the display of text, and have retained the adaptive sync separator with field sync count-down (as in the 70/90/110 series) to obtain the best sync performance under peculiar signal conditions.

Good reliability is something that comes through close control at each stage of design and manufacture. In designing the chassis we had to ensure that no combination of tolerances can result in any component (particularly semiconductor devices) being overrun due to either excess voltage, current or power, even at the highest or lowest temperatures and humidities in which the sets are likely to be operated (and, believe me, some countries are very hot and wet and some have peculiar leaping-about mains supplies!).

In manufacture, reliability has been ensured by techniques such as goods inwards component checking; sophisticated and rapid automatic testing of all appropriate voltages and currents in the sets, using microprocessor-controlled machines which have been designed and built in-house and allow for operator checks and adjustments as required; giving each receiver a 24-hour soak test before carrying out final checks and boxing; and by quality control checks on samples taken from each batch of receivers.

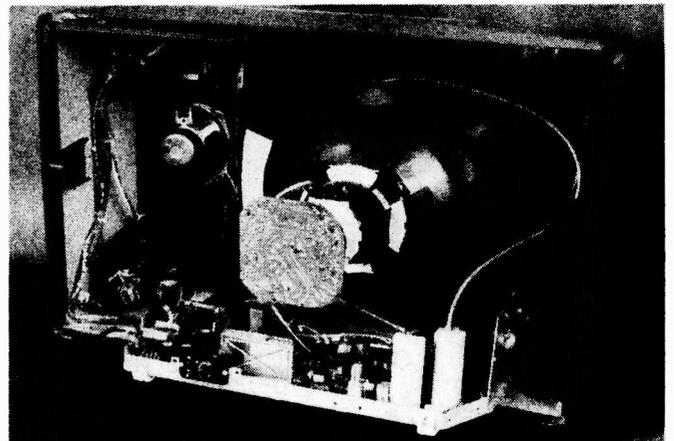Even that's not the end of the story. Any faults that show up during the 24-hour soak test are analysed and, if



Interior view of one of the prototype receivers.

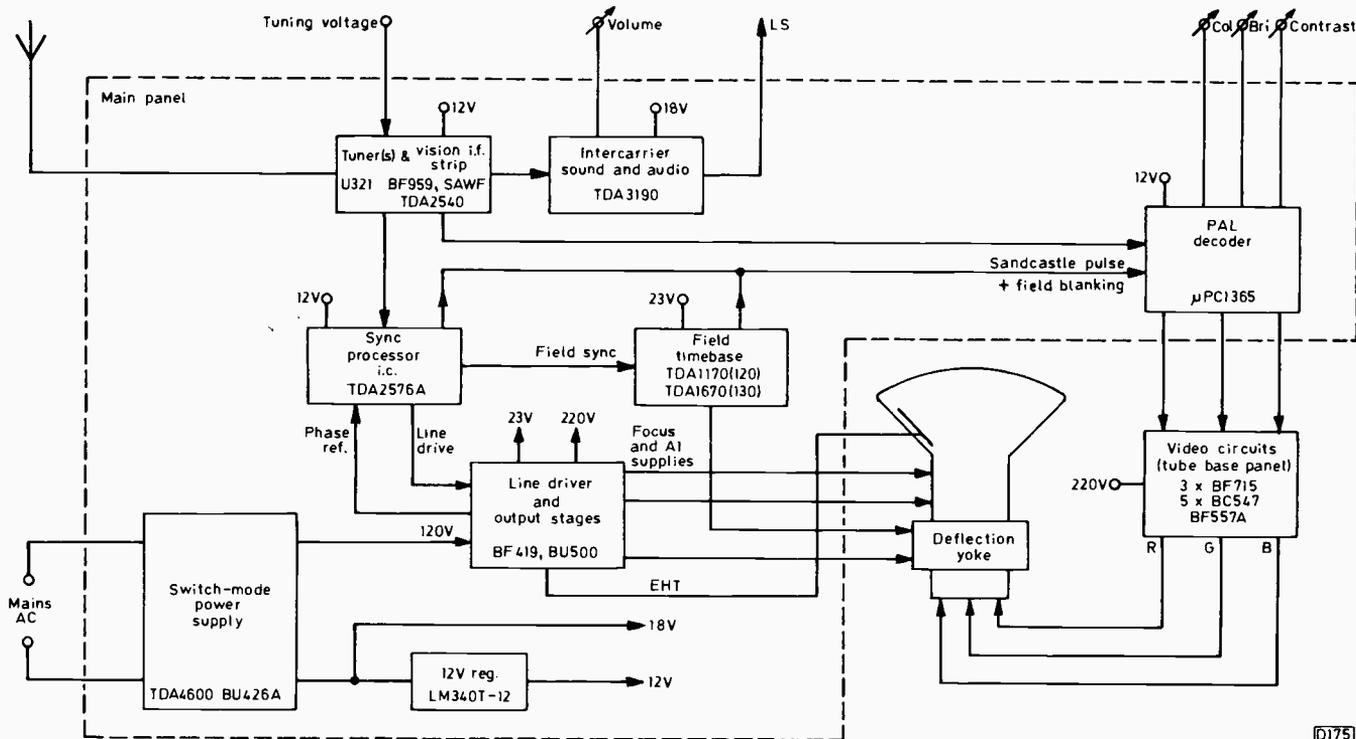


Fig. 1: Simplified block diagram of the 120/130 series chassis.

there's a fault pattern rather than random failure, corrective action is taken – either in the manufacturing process, or with the component supplier, or if necessary by reconsidering the design.

The Sets Themselves

Now let's take a closer look at the sets themselves. We've retained the simple DZUS fastener for fixing the cabinet back. On removing the back however anyone familiar with previous Decca receivers will immediately notice a difference (see the accompanying photograph). With the simpler, smaller chassis (comparable in size to a monochrome set), we've fixed it at the bottom of the set rather than mounting it vertically with the hinge-up servicing position previously provided. A servicing position has not been forgotten however, though we hope it won't be needed: you just loosen two screws and a plastic clip holds the chassis vertically, giving access to both sides.

The 120 chassis is a true single-panel design, with no plug-in or soldered-in subpanels. The mains filtering, degaussing, power supply, timebase, PAL decoder and i.f. circuitry, plus the tuner(s), are all on the one board, with the video circuits on the tube base panel – the best place for them. The metalwork has also been reduced to a minimum: just a simple strengthening bar at the back and a few heatsinks. Dual-standard PAL/Secam sets require an extra plug-in subpanel, allowance for the plug being included on the main panel.

The Electronics

A simplified block diagram of the chassis is shown in Fig. 1: most of the semiconductor devices used in the chassis are indicated.

The tuner(s) and the i.f. section are virtually identical to those employed in the 70/90/110 series chassis, since nothing giving comparable performance at the same cost is available in quantity so far. One change here is the use of a single-transistor preamplifier stage to replace the SL1430

i.c. previously used to make up for the insertion loss of the SAW filter. The sound department employs an SGS TDA3190 combined intercarrier/audio chip – this is basically the same as the TDA1190Z we used previously, the new i.c. having a slightly cheaper package.

The field timebase employs the trusty TDA1170 i.c. from SGS (and others now). We've used this chip since 1975 (I believe we were the first UK setmaker to use it, in the 80 series chassis). The 30AX tube calls for higher scanning power, so the 130 chassis uses a TDA1670 i.c. in the field timebase.

The TDA2576A sync processor i.c. is one we've not used before. I'll return to this later.

The line output stage is traditional, with a line output transformer and a tripler in preference to the use of a diode-split line output transformer. We still don't feel that the latter has significant cost or reliability advantages in comparison with the conventional system, while there can be problems with the breathing performance and radiation into the rest of the receiver. In addition, having to replace the complete transformer because of a faulty diode is expensive! The new line output transformer we've used is quite a bit smaller than previous designs, and the tripler is the new Mullard BG200. We're also using a new thick-film potted resistive unit for both the focus and c.r.t. first anode supplies.

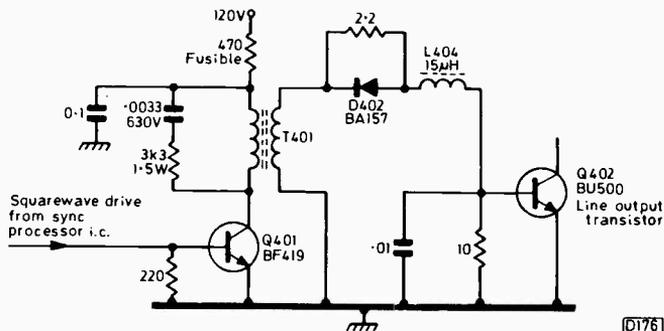


Fig. 2: The line driver stage.

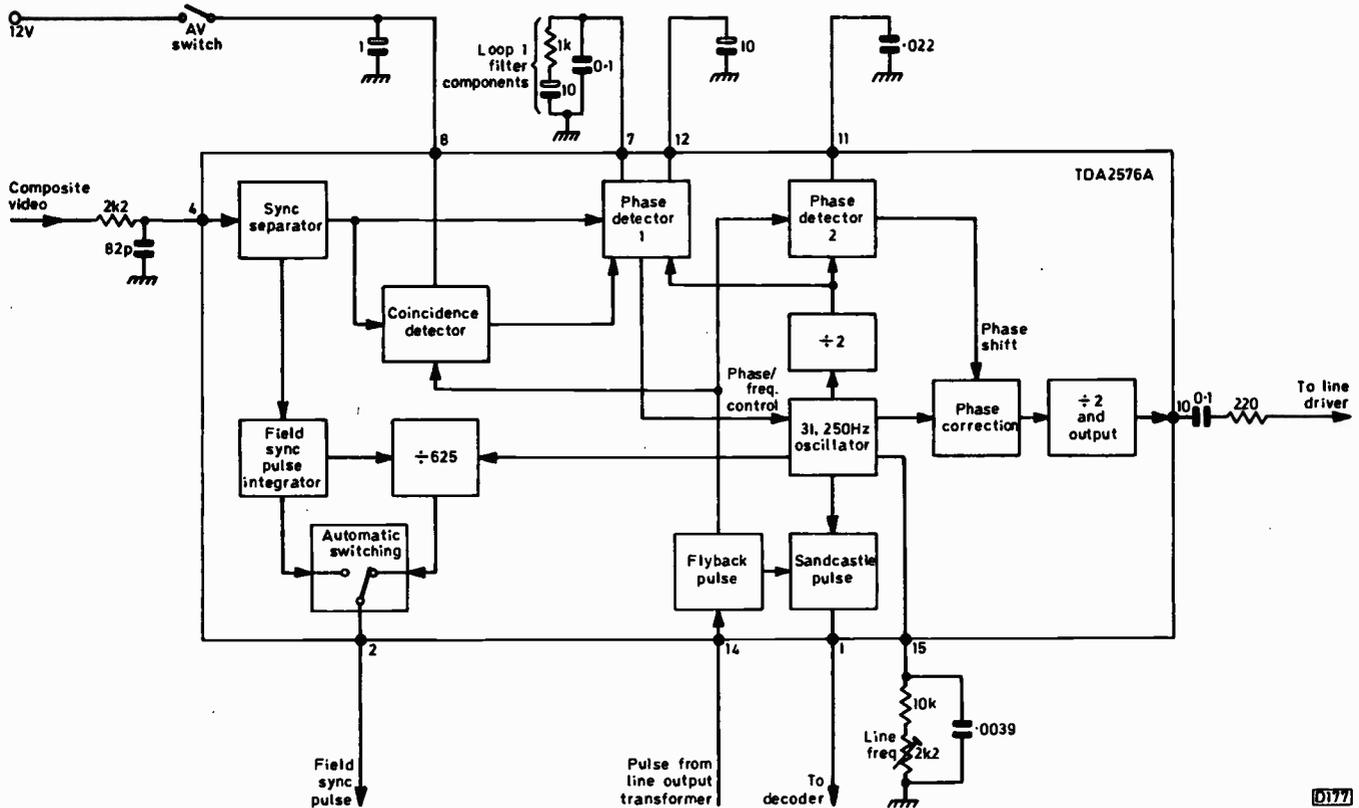


Fig. 3: Simplified block diagram of the TDA2576A sync processor i.c.

The 90° tubes we're using are from a new pincushion-distortion free range produced by Toshiba and Mullard. So we don't need the transductor circuitry used in the 70/90 series chassis. The 110° 30AX tube still requires some EW correction, which is provided on the main board by a simplified diode-modulator with a driver – the circuit is almost identical to that used in the 110 series chassis.

This leaves the PAL decoder, the video circuits and the power supply. These are all new to our receivers and will be dealt with in detail later.

Although quite a bit of previous circuitry has been used in the new chassis, the different chassis concept and the new board layout resulted in a considerable amount of development work. As with previous chassis, the component spacings required for auto-insertion, and the test pads and location holes required for auto-testing, all placed constraints on the layout – while the elimination of pick-up and radiation from high-energy spikes (especially noticeable in Band I) takes ages.

In the 70/90/110 chassis the switch-mode power supply operated at line frequency – in fact it formed a phase-locked loop with the line timebase. The chopper transformer had a winding which provided the drive to the line output transistor, while the line output transformer provided a phase reference pulse which was fed back to the TDA2581 power supply control i.c.

We've reverted to completely independent power supply and line output stage circuits in the new chassis. This means that a separate line driver stage is required – a conventional circuit (see Fig. 2) similar to that employed in the 80 series chassis is used. The independent line output stage also means that a different sync processor i.c. is necessary. The TDA2571A used in the 70/90/110 chassis didn't contain the phase-locked loop required to compare the line output phase reference and the line oscillator signals – this loop was incorporated in the TDA2581 power supply control i.c. The TDA2576A contains this

loop (see "phase detector 2", Fig. 3). In the way in which its separate sections are interconnected, the i.c. is similar to the familiar TBA920: the oscillator runs at twice line frequency however, and field sync pulse and sandcastle pulse generators are incorporated. The circuit techniques are much more sophisticated than those used in the TBA920, which dates from the early seventies – much of it is very similar to the TDA2571A.

The sync separator is of the adaptive type, which gives improved performance and is especially effective where noisy, ghosty or cross-modulated signals are all you've got to go on. In this type of circuit (see Fig. 4), a variable gain amplifier ensures that the height of the separated mixed sync pulses is kept constant. A small slice through the centre of each pulse is then amplified, giving a very solid sync signal.

Like the TDA2571A, the TDA2576A has a field countdown chain (divide by 625) whose output is constantly checked with the integrated field sync pulses. This gives a "flywheel" effect to the field sync, with good, solid field lock. If a sync source which doesn't have the correct 625:1 ratio between twice line frequency and the field frequency is used (a video game for example), the circuit automatically reverts to use of the normal integrated field sync pulses.

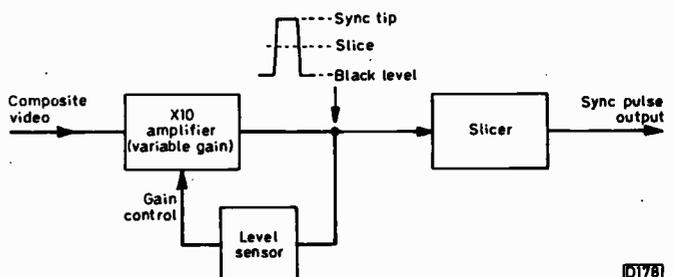


Fig. 4: Principle of the adaptive sync separator.

Fault Report

Steven Knowles

G8 Trouble

I had double trouble recently with a Philips set fitted with the G8 chassis. The original complaint was "no results", and on inspection the 3.15A mains fuse was found to have blown. The first thing I did was to look at the rear of the panel – if the rectifier/regulator thyristor shorts in this chassis it often blows a length of the print off the board. The print was all intact however, and on checking with a meter the thyristor showed no signs of a short. The next likely suspect was the mains filter capacitor, but on looking at this it was obvious that it had been fitted fairly recently. It was not a set I regularly service incidentally. The fuse's blackened appearance definitely suggested that there was a dead short somewhere, but checking from the fuseholder to chassis again drew a blank.

I decided to fit a new fuse therefore and see what happened. The new fuse didn't blow, but apart from the tube heaters lighting up the set remained dead. Check for a.c. at the anode of the thyristor: nothing. Check back to the 2.2Ω surge limiter section of the power resistor: voltage at one end, not the other. Remove panel, replace power resistor, refit panel and switch on. All o.k. Still suspicious of thyristor, so replace it to be on the safe side. Check setting of the h.t. control, replace back and leave set on soak test.

Two Hours Later

Some two hours later, just as I was finishing off a single-standard G6 which had had various problems in its field timebase (two capacitors blown off the board, both drop-off cathode resistors dropped off, and a burnt out linearity control), the G8 suddenly went dead. Suspect that the mains fuse has again blown, but no – the tube heaters were alight. Remove back and find 800mA h.t. fuse on line scan panel blown. Remove flying lead PC1 to isolate the line output stage, replace fuse and switch on. Fuse holds. Switch off, reconnect PC1, switch on again. Fuse blows after approximately two seconds, proving that the fault is in the line output stage. Can't find ammeter, so fit another fuse and disconnect tripler, transducer connection plug and line scan coils plug. Switch on and fuse blows again. Check line output transistors which seem to be o.k., and notice that the flyback tuning capacitors are of the green type which are not normally troublesome. Try replacement line output transformer, which restored normal operation. In fact we're getting more and more G8s in with line output transformer trouble. Thinking back, most Philips sets from the 210 chassis and the earlier Style 70 series onwards seem to have been prone to this sort of trouble.

A Visit to the Barbers

Paid a visit to the local barber, whom I'd not frequented for many years, recently and noticed on a high shelf and displaying an admirable picture an old Ferguson 306T. Memories came flooding back. The 306T (17in.) and 308T (21in.) date from around 1956 and were, in my opinion, one

of the most reliable chassis of that era. The components were mounted on a fairly small vertical panel, the massive cabinet being required to house the large 70° tubes. Reliability seemed to decrease after that. I can't recall ever having had to replace the dropper in one of those old sets. Compared with the rate of dropper failure in these days, well...

No One Touched Them

We get all sorts of silly faults to deal with sometimes – like the Thorn 1500 with no results due to a wire coming adrift in the mains plug, and the 1400 with a shorted mains filter capacitor due to someone having fitted a 300V component. Then there was the time I was asked to look at a washing machine (yes, a washing machine!) that insisted on drying the clothes before it washed them! We take all these things in our stride, don't we? But there's one thing that irritates me no end, those (few) people who seem to take you for some sort of fool. Typical example: "the BBC-1 button gets BBC-2 and the ITV button gets BBC-1." You go to look at the set and know damn well that someone's been at the buttons, but will they admit it? Oh no! "We never turn those buttons", or "we never touch those little wheels." "It went like that overnight!" You know they're lying, but what can you do? Personally I like a quiet life and simply grit my teeth whilst viciously resetting the tuning. Maybe I'm too introverted.

Curiosity Won the Day

Had a Bush TV161 in recently with the complaint "sound, no picture". Remove back and see large hole in the print around the PCL805. Question owner. "Yes, it used to keep going into a white line all the time, then it went altogether." Examine print further and see signs of frantic repair work around the PCL805 and dry-joints all over the place. Instinct tells me to refit the back and forget the whole thing, but curiosity won the day.

Resolder all suspect joints and switch on, expecting sound but no picture. No sound either! Make a few tests and replace on-off switch/volume control. Valves now light up, sound appears, but still no raster. Remove line output stage screening cover and notice that the DY802 e.h.t. rectifier is glowing bright blue instead of red. Try another which also glows blue. Remove top cap (anode) and try again. Rectifier now lights up normally, while a healthy spark can be drawn from the top connector. Refit connector: rectifier glows blue again, but notice that the heater is still alight and there's still a spark from the anode cap.

Jump to wrong conclusion and check c.r.t. first anode voltage – o.k. Short together tube's cathode and grid – still no raster! Starting to get annoyed, so make cup of tea. On returning to the fray I did what I should have done in the first place – remove the e.h.t. lead from the tube and try again. The rectifier was still bright blue, while no spark could be drawn from the loose tube connector. Examine line output transformer more closely and notice that the heater winding seems tacky. Snip it off, wind a new turn round with e.h.t. cable and connect up. Normal results at last!

Grundig 5011

A Grundig 5011 came along with the complaint "lack of width, poor focus and foldover at the bottom of the raster". Previous experience with these sets suggests carrying out an inspection of the condition of the printed board and the

wound components in and around the line output stage. This time we found that the core of the combi coil 9245-834-21 was cracked in half, with an eighth inch gap between the two halves. We held the two sections together with the set working and the symptoms all cleared. So we ordered and fitted a replacement to complete the repair.

A 24in. Indesit

The next job was an Indesit T24EGB – an early one fitted with a mechanical tuner. The complaint was “weak unstable picture, suspect tube low.” The picture was indeed very grey, but whether the tube was low or not was impossible to tell because of the presence of a dirty great black hum bar which travelled up the screen and tripped both timebases each time it reached the top.

The 24V supply for the transistorised sections of the receiver is obtained from the earthy end of the heater chain in this chassis, and it seemed to us that something was wrong with the smoothing here. There’s a multiple smoothing filter (C914/R908/C915/R909/C916), and on checking up we noticed that C914 (500 μ F) is sandwiched at the top of the chassis between the dropping/smoothing resistors and the PCL805 field timebase valve. It’s obviously subject to a lot of heat, and was completely dried up. Replacing this restored normal results, with a crisp, well-contrasted picture, but something was amiss with the tuner – the resetting was something terrible.

The resetting accuracy of the buttons on these sets is not particularly good at the best of times, but this was too bad to let pass. We removed the tuner and control panel complete, but couldn’t see anything wrong with the operating bar and return spring. So we decided to remove the inspection cover. We could see, on moving the outside linkage, that there was quite a bit of movement not being transmitted to the moving gang. Closer inspection revealed that the moving gang is connected to the outside linkage by two small clips – one at each end. These had loosened slightly over the years, causing a certain amount of play: it was possible to tighten them up to complete the job.

That Fine Ferguson Failed

The phone then rang – it was the barber. “You remember that old Ferguson set you were admiring so much the other week? – it’s gone wrong.” So down I went, and as usual the shop was full of customers. Now I don’t like working in front of an audience, but . . . Apparently the set would come on all right, then the picture would get darker until it became too dark to see – though it didn’t vanish completely. In fact it started to get noticeably darker some four-five minutes after I switched the set on – the width also started to come in at the sides. As I stared at the old set something clicked in the back of my memory. Surely this used to be a stock fault years ago? – the old Ferguson low width fault. Then I remembered – a leaky 0.001 μ F coupling capacitor between the line oscillator and the line output valve. And so it was that without making any tests I was able to remove the cabinet shell, snip out the faulty capacitor, fit a new one, put everything back together and get a picture that stayed on. In front of an audience too! It’s nice to be able to do things like that from time to time . . .

Up The Garden Path

I’ve long been convinced that the proverbial “trip up the garden path” starts when you remove the back of a TV set. The one in question was a dual-standard Philips G6 that I’d

sold some years previously to friends of mine. It had been fairly trouble free, requiring only the odd adjustment or valve replacement from time to time, but now seemed to have something more serious wrong with it – the symptoms were described as follows: an odd smell was noticed after the set had been on for a couple of hours, and on looking at the screen the picture was observed to have shrunk by about an inch and a half all round. The set had then been switched off and allowed to cool, but on switching on the fault was sound but no raster. The owners were going away on holiday for a month (sigh of relief): they left me the keys so that I could look in when I’d an opportunity.

I called round one evening and found the symptoms as described – no raster, no line output stage activity, no h.t. to the line output stage due to the fusible feed resistor having sprung open. Resolder it and switch on. The sound came through but the line output valve started to glow cherry red. Switch off, replace the PCF802 line oscillator valve and try again. Once more a cherry red line output valve. Decide to replace the PL509 and PY500. No difference. Unhook e.h.t. and focus rectifiers. PL509 still cherry red, and so was my face. What next? Disconnect one end of boost capacitor, PL509 starts to . . . That left the line output transformer and the d.c. feed choke to the line output valve as suspects. The choke sometimes develops shorted turns, but this is usually quite obvious from its appearance. This one looked quite clean, so I made a note to order a new line output transformer next day.

As I prepared to leave the house, I became vaguely aware of a flashing blue light. Open front door and come face to face with two police officers on the doorstep. What was I doing as the owners were on holiday? My first attempt at an explanation – “I’m doing a job” – resulted in a further twenty minutes of questioning before I was eventually allowed to go home.

Back with the New Transformer

In due course I returned with the new transformer. Fit it, switch on, get sound then . . . I couldn’t believe it – the PL509 was cherry red! Better take the set back to the workshop. With it on the bench I started to check just about everything there was to check – all the capacitors, resistors and valves in the line timebase, change the d.c. feed coil, monitor the line drive waveform, disconnect the transducer and scan coils, but the PL509 continued to glow. Eventually I found myself checking things that couldn’t possibly have any bearing on the fault.

Maybe the new transformer . . .? This seemed unlikely, since new transformers are rarely defective while the likelihood of a new one producing exactly the same symptoms as the old one seemed improbable. And I’d not got another one to try. After long deliberation I returned the transformer with an accompanying letter. A replacement arrived a week later, and was fitted with little optimism. Switch on and wait. Sound, then all of a sudden the generator starts up and the line whistle comes through along with a rustle of e.h.t. Throw – sorry, put – the whole lot back together, check the boost voltage, tweak up the grey scale and the convergence and that’s that. What a performance!

The Moral?

The moral (if there is one) for newcomers is to try and remain logical. It’s not always easy I know. If you come up against a really sticky fault, it’s best to leave it for a while and return to it later. Bye for now . . .

Digital Signal Processing

Arthur Mole

FOR several years now the use of digital techniques in television has been growing. A considerable impetus came initially from the need for high-quality TV standards conversion. The IBA's DICE (Digital Intercontinental Conversion Equipment) standards converter came into operational use in 1972. It's success demonstrated convincingly the advantages of processing video signals in digital form – digital signals are neither phase nor level dependent. The trend since then has been towards the all-digital studio: digital effects generators have been in use for some time, and digital telecines were announced earlier this year.

An earlier example of the application of digital techniques to television was the BBC's sound-in-syncs system, in which the sound signal is converted to digital form so that it can be added to the video signal for network distribution. The sound-in-syncs system first came into use in 1969, and is now widely employed.

Digital techniques have already appeared on the domestic TV scene. The teletext signals are digital, and require digital processing. In modern remote control systems the commands from the remote control transmitter are in digital form, and require digital decoding and digital-to-analogue conversion in the receiver before the required control action can be put into effect. Allied to this, digital techniques are used for the more sophisticated channel tuning systems. The basic TV receiver itself continues to use analogue techniques however. Are we about to see major changes here?

ITT Semiconductors in W. Germany have been working on the application of digital techniques to basic TV receiver signal processing since 1977, and at the recent Berlin Radio Show presented a set of digital chips for processing the video, audio and deflection signals in a TV receiver. The set consists of a couple of l.s.i. and six v.l.s.i. chips – and by very large scale integration (v.l.s.i.) we're talking about chips that contain some 200,000 transistors.

What are the advantages? For the setmaker, there's reduction in the component count and simpler, automated receiver alignment – alignment data is simply fed into a programmable memory in the receiver, which then adjusts itself. Subsequently, the use of feedback enables the set to maintain its performance as it ages. From the user's viewpoint, the advantages are improved performance and the fact that extra features such as picture-within-a-picture (two pictures on the screen at the same time) and still pictures become relatively simple to incorporate.

The disadvantage of course is the need for a lot of extra circuitry. Since the received signals remain in analogue form, analogue-to-digital conversion is required before signal processing is undertaken. As the c.r.t. requires analogue drive signals, digital-to-analogue conversion is required prior to the RGB output stages – the situation is somewhat different in the timebase and audio departments, since the line drive is basically digital anyway and class D amplifier techniques can be used in the field and audio output stages. In between the A-D conversion and the various output stages, handling the signals in digital form calls for much more elaborate circuitry – hence those chips with 200,000 or so transistors. The extra circuitry is all incorporated

within a handful of chips of course, but the big question is if and when the use of these chips will become an economic proposition, taking into account reduced receiver assembly/setting up costs, compared to the use of the present analogue technology – after all, colour receiver component counts are already very low.

With the present digital technology, it's not feasible to convert the signals to digital form at i.f. So conversion takes place following video and sound demodulation. Fig. 1 shows in simple block diagram form the basic video and deflection signal processing arrangement used in the system devised by ITT Semiconductors.

Before going into detail, two basic points have to be considered – the rate at which the incoming analogue signals are sampled for conversion to digital form, and the number of digits required for signal coding.

Consider the example shown in Fig. 2. At both (a) and (b) the signals are sampled at times T1, T2 etc. In (a) the signal is changing at a much faster rate than the sampling rate. So very little of the signal information would be present in the samples. In (b) the rate at which the signal is changing is much slower, and since the sampling rate is the same the samples will contain the signal information accurately. In practice, the sampling rate has to be at least

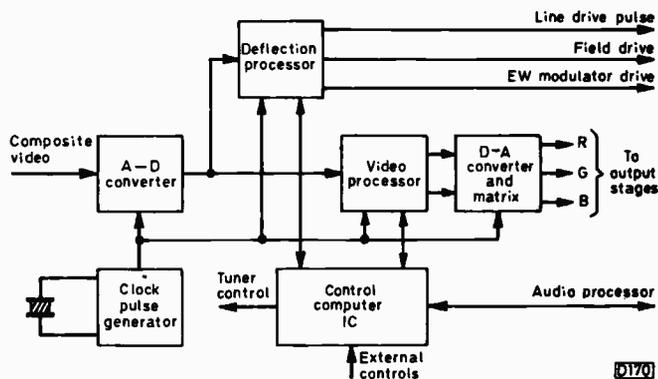


Fig. 1: Block diagram of the digital video and deflection signal processing system devised by ITT Semiconductors. A-D and D-A conversion of the video signals is carried out by a single chip which ITT call the video codec.

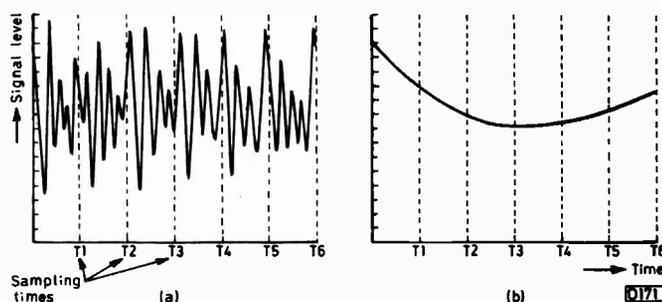


Fig. 2: Principle of signal sampling and conversion to digital form. If the signal is sampled at a much lower frequency than the rate at which it is changing, as at (a), most of the signal information will be lost. Signal resolution, once the signal has been converted to digital form, depends on the number of digits used to represent each signal sample. Voltage comparators are used to sample the signal and convert it to digital form.

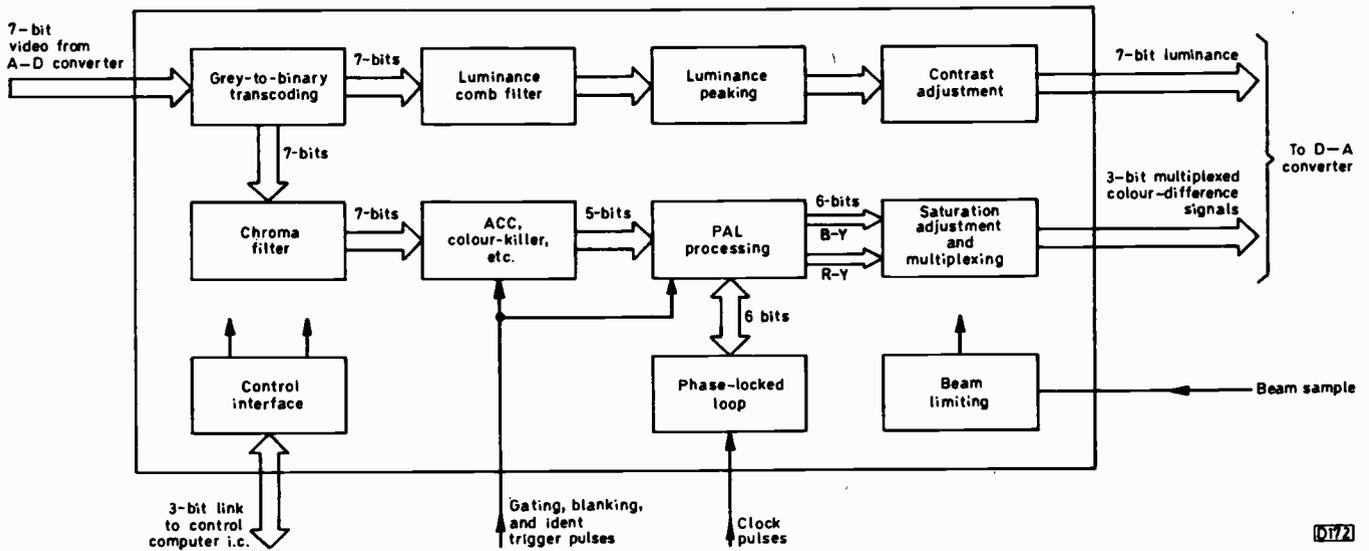


Fig. 3: Simplified block diagram of the video processor i.c.

twice the bandwidth of the signal being sampled.

Once you've got your samples, the next question is how many digits are required for adequate resolution of the signal, i.e. how many steps are required on the vertical (signal level) scale in Fig. 2? The use of a four-digit code, i.e. 0000, 0001 etc., gives 16 possible signal levels. Doubling the number of digits to eight gives 256 signal levels and so on. ITT's experience shows that the luminance signal requires 8 bits (digits), the colour-difference signals require 6 bits, the audio signal requires 12 bits (14 for hi-fi quality) while 13 bits are required for a linear horizontal scan on a 26in. tube. These digital signals are handled as parallel data streams in the subsequent signal processing.

Returning to Fig. 1, the A-D and D-A conversion required in the video channel is carried out by a single chip which ITT call the video codec (coder/decoder). A clock pulse generator i.c. is required to produce the various pulse trains necessary for the digital signal processing, and a control i.c. is used to act as a computer for the whole digital

system and also to provide interfacing to enable the external controls (brightness, volume, colour etc.) to produce the desired effects. In addition, the control i.c. incorporates the digital channel selection system.

The video codec i.c. uses parallel A-D/D-A conversion, i.e. a string of voltage comparators connected in parallel. This system places a high premium on the number of bits used to code the signal in digital form, so ITT have devised a technique of biasing the converter to achieve 8-bit resolution using only 7 bits (the viewer's eye does some averaging on alternate lines, as with Simple PAL, but this time averaging luminance levels). The A-D comparators provide grey-encoded outputs, so the first stage in the video processor i.c. is a grey-to-binary transcoder.

As Fig. 3 shows, the processes carried out in the video processor i.c. then follow the normal practice, though everything's done in digital form. The key to this processing is the use of digital filters. These are clocked at rates up to 18MHz, and provide delays, addition and multiplication. The glass chroma delay line required for PAL decoding in a conventional analogue decoder consists of blocks of RAM (random-access memory) occupying only three square millimeters of chip area each. As an example of the ingenuity of the ITT design, the digital delay line used for chroma signal averaging/separation in the PAL system is used in the NTSC version of the chip as a luminance/chrominance signal separating comb filter.

Fig. 4 shows the basic processes carried out in the deflection processor i.c. This employs the sorts of techniques we're becoming used to in the latest generation of sync processor i.c.s. Digital video goes in, and the main outputs consist of a horizontal drive pulse plus drives to the field output and EW modulator circuits. The latter are produced by a pulse-width modulator arrangement, i.e. the sort of thing employed with class D output stages. The necessary gating and blanking pulses are also provided.

A further chip provides audio signal processing. One might wonder why the relatively simple audio department calls for this sort of treatment. The W. German networks are already equipping themselves for dual-channel sound however, and the audio processor i.c. contains the circuitry required to sort out the two-carrier sound signals.

These chips represent a major step in digitalizing the domestic TV receiver. It seems likely that some enterprising setmaker will in due course announce a "digital TV set". The interesting point then will be whether the chip yields, and the chip prices as production increases, will eventually make it worthwhile for all setmakers to follow this path. ■

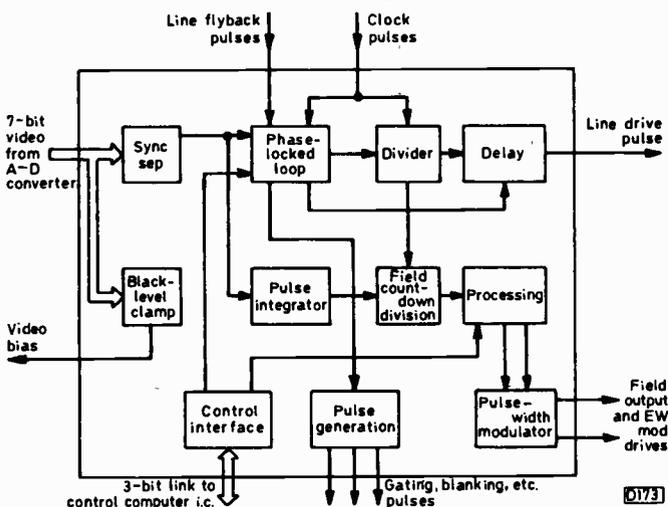


Fig. 4: Simplified block diagram of the deflection processor i.c. The line drive output is conventional. The field and EW modulator outputs consist of pulse-width modulated wave trains. These can be amplified by a class D amplifier and then filtered to provide sawtooth and parabolic field frequency outputs (the principle of this was described in *Teletopics*, January 1977). The i.c. also contains a black-level clamp whose output is used to clamp the black level of the demodulated video to a fixed voltage to ensure that the A-D converter operates at the optimum level.

Servicing Luxor 110° Hybrid CTVs

Part 1

Mike Phelan

LUXOR 110° hybrid colour TV sets were imported from Sweden during the 1973–74 colour boom period: the design is fairly sound, and large numbers are still giving good service. They also represent a good prospect for renovation, often being available from disposal outlets at reasonable prices – many rental companies seem to be getting rid of their continental sets, probably because a lot of their technicians are reluctant to get to know about anything that has a foreign sounding name. There are also 90° Luxor hybrid colour receivers around: these were imported by Rediffusion, and will be the subject of a subsequent article in the magazine.

The main 110° model is the 2621. It has an attractive cabinet which houses a 110°, delta-gun 26in. tube – the cabinet was available in rosewood, teak, walnut, mahogany or white. Some of the models had a lockable door covering the front controls, a separate on–off switch being provided on the back cover. Most sets have a 25W bulb at the back to give “background” illumination. The front controls are as follows, from top to bottom: push-push switches for on–off and bass cut; four slider controls for treble, volume, brightness and colour; a rotary contrast control; then seven pushbuttons for channel selection and band switching. A window beside each pushbutton shows a moving ribbon type channel display.

The internal appearance is reminiscent of many early UK produced hybrid sets, but the accessibility is far better. The convergence controls and raster correction panel are contained in a hinged frame which is attached to the top of the cabinet. The main chassis contains five large, non-removable printed boards in a metal frame. Vertically mounted at the left is the audio and l.t. board; below it at the bottom are the power supply, decoder and timebase panels, the sync/line oscillator i.c. being on a small plug-in module attached to the latter; the vertical panel on the right contains the line output stage, while the CDA panel is attached to the rear chassis rail. The i.f. stages are in a screening can mounted above the tuner on the back of the control panel.

To gain access to the CDA panel, slide it horizontally and swing it down through 90°, after removing the latch – if this is still present. Take care to remove the c.r.t. leads from the clip on the convergence board. The whole chassis slides backwards when the springs at either side are eased out: for access to the underside, the chassis can be tilted forwards after the spring-loaded peg near the mains transformer has been pulled out. After slackening the two screws below the line output stage screening can and the two corresponding ones behind, the whole line output section folds down flat. To get at the i.f. stages or the tuner, slide the chassis out, remove the knobs, then the two long screws that hold the control panel/i.f. strip/tuner: the whole assembly can be “hung” on the two hooks on the left-hand vertical chassis member for servicing.

Now to the circuit and the faults to which it is prone.

Power Supply Faults

We'll start with the power supplies (see Fig. 1). The h.t.

rails are produced by a bridge rectifier directly from the mains. Another bridge rectifier, fed from the mains transformer, produces a 31V supply. An AD149-type series regulator (Q276) produces a stabilised 24V line from this supply. Three EF184 valves are used in the colour-difference output stages, their heaters being fed from a winding on the mains transformer. The heaters of the five other valves are connected in a series chain across the mains, via dropper resistors. The latter (R605 39Ω and R606 82Ω) cause more than their share of trouble: they are tucked away in the corner near the left rear chassis upright and run very warm. When you find that all the heaters apart from the EF184s are out, tip the chassis up and have a look under R605 and R606. If you are lucky, one or both will be found dry-jointed: if you are not, there will be a hole burnt in the board. The best cure is to replace both resistors with a single 120Ω “polo mint” type bolted to the chassis somewhere.

The other various wirewound resistors on the power supply panel can go open-circuit, particularly R610 (4.7Ω) which feeds the line output stage. When checking around with the Avo, ignore R612 (7.5kΩ) which is connected between the 220V rail and chassis.

Another fault that occurs quite often is a 100Hz hum bar: it will usually be found that every pin on both the large electrolytic cans is dry-jointed. If the hum affects the picture brightness and the sound, the fault is in the l.t. supply, to which we'll return.

If one or both of the mains fuses S601-2 (3.15A anti-surge) has blown, one might suppose that one of the five mains filter capacitors C601-5 has given up. We've never had one of these fail however: the reason for the blown fuse(s) is likely to be one of the diodes D601-4 in the h.t. bridge rectifier circuit or one of the small 0.005μF capacitors C606-9 connected across them. If two of the diodes fail immediately after they've been replaced, fit a new PY500A boost diode – the old one will have a heater-cathode short which will effectively short out one half of the bridge.

The l.t. supply is straightforward and doesn't cause many problems. One rather baffling fault occurs when the error detector transistor Q275 (BC141) goes open-circuit. The symptoms are a blank raster of reduced width with a fold in the centre, and no sound. The line linearity coil L851 and R921 (1.5kΩ) also overheat. The latter component is mounted on the plug at the back of the line output stage. If you are fortunate, you will find that the l.t. rail has fallen to about 8V – but placing a meter prod almost anywhere usually clears the fault. The 24V series stabiliser transistor Q276 (TI3027 or AD149) sometimes goes short-circuit, giving severe hum on sound and picture – this fault can also be caused by the 31V supply reservoir capacitor C285 (2,200μF) drying up.

Signal Circuits

The ELC2000 v.h.f./u.h.f. tuner and its push-button unit cause more trouble than the rest of the set. Drifting is a common problem, and the push-button unit is the most

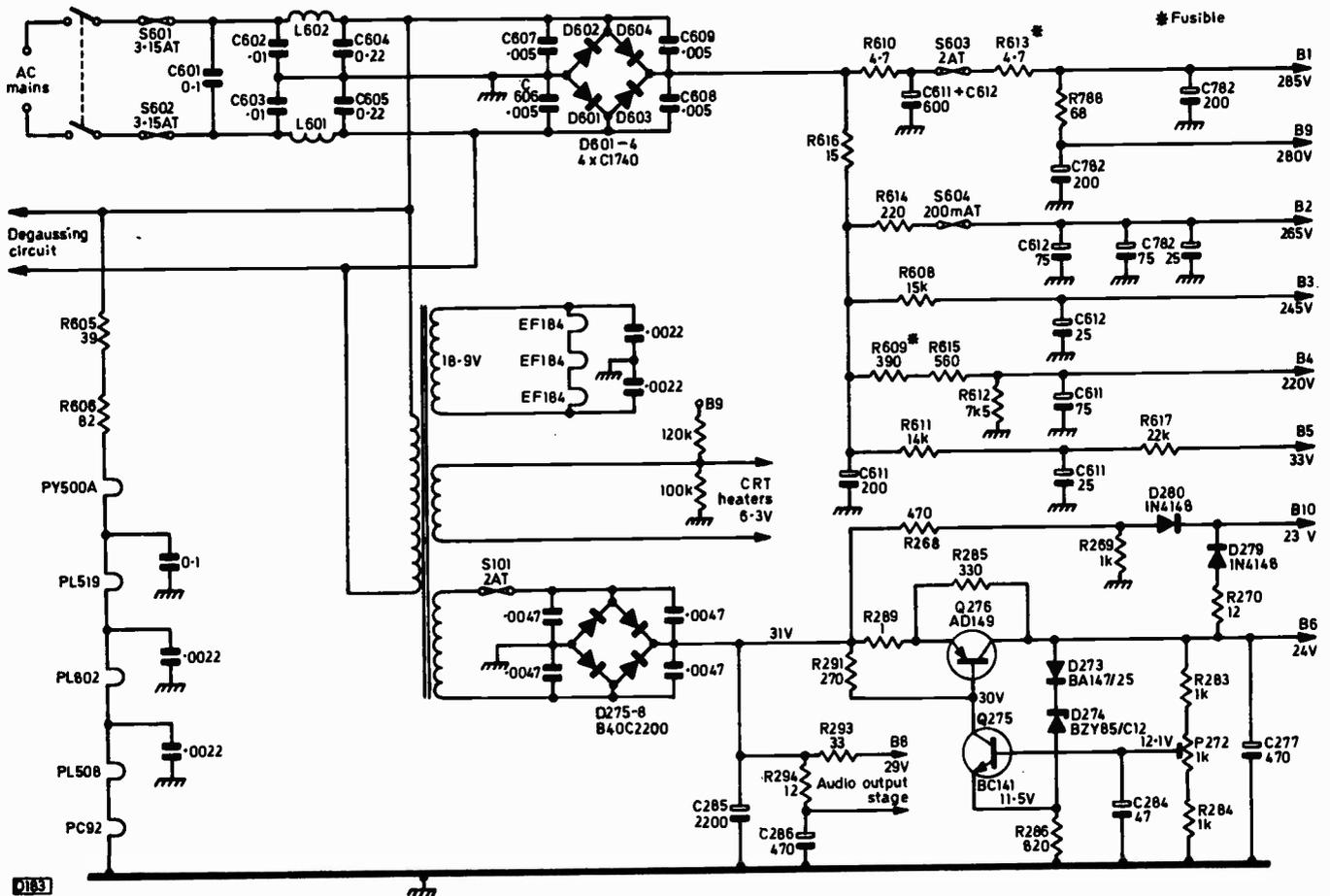


Fig. 1: Power supply circuitry. There's also a 12V regulator, on the i.f. panel.

likely cause. Less often the tuner itself is responsible: only on very rare occasions is the ZTK33/TAA550 33V stabiliser the culprit. The problem with the push-button unit is that the printed potentiometer tracks alter in value: replacement is the only cure, cleaning being a waste of time. Anyone who has worked on other sets (Rank, Kuba, ITT) using the same make of push-button unit will be familiar with the trouble.

The tuner itself can be responsible for patterning and low gain. The latter fault is often caused by the wire-wrap trimmer C67 in the u.h.f. r.f. amplifier stage going short-circuit. This can, with care, be repaired by unwrapping the wire slightly. First however check that the tuner a.g.c.

voltage (pink lead) is about 2.5V – sometimes the 8.2V zener diode D232 in the tuner a.g.c. circuit goes open-circuit, giving rise to a grainy picture. This component is to be found in the i.f. can.

The i.f. strip has two MC1350P (or SN76600P) i.c.s to provide the gain. These are followed by two BF199 (or BF173) transistors, one of which (Q201) drives the 6MHz intercarrier sound detector whilst the other (Q202) drives the video detector. The intercarrier sound goes off to the usual TBA120 chip. The video goes to Q203 (BC147B), which provides a video feed and drives the a.g.c. circuit from its emitter, with a feed to the sync circuit from its collector. The i.f. stages are supplied by a 12V stabiliser circuit which is also inside the i.f. can.

With the exception of the previously mentioned zener diode D232 and the TBA120, the only failures we've had in the i.f. section have been due to Q203 going short-circuit between its emitter and base, giving intermittent loss of sync. The i.f. unit has otherwise proved itself to be extremely reliable.

The same remark applies to the decoder, which rarely gives any trouble. It's conventional apart from the colour-killer arrangement, which is a bit unusual (see Fig. 2). The colour-killer transistor Q308 (BC148C) is driven by a phase detector (D306-7) which is in parallel with the burst detector (D304-5). Whilst the burst detector produces a positive-going output, the colour-killer detector produces a negative-going output (-1.2V at the base of Q308) when the 4.43MHz reference oscillator is locked to the burst. Q308 is thus turned off when a colour signal is present and the reference oscillator is locked correctly. When Q308 switches off, the bases of the R - Y and B - Y preamplifiers Q307 and Q313 receive forward bias via R373 and R369 respectively. To override the colour-killer.

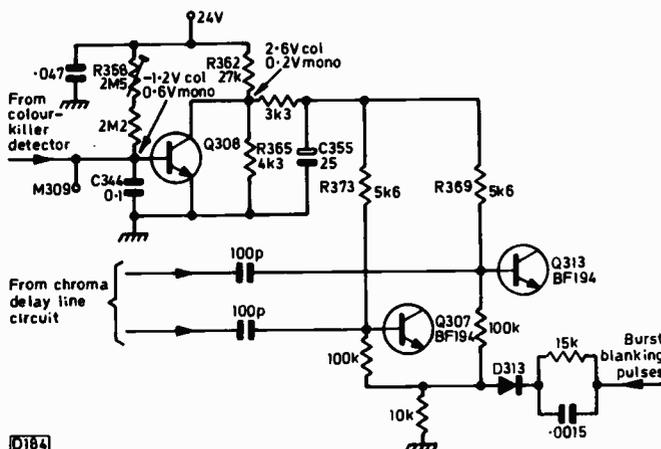


Fig. 2: The colour-killer circuit. The colour-killer detector is a synchronous type driven by the burst phase discriminator transformer – so there'll be no colour on the screen when the reference oscillator is unlocked.

connect point M309 to chassis. On monochrome, the voltage at the base of Q308 is 0.6V.

From time to time we've had to replace either the 4.43MHz crystal, or the 6.8V zener diode D308 which stabilises the oscillator's base bias, to cure complaints of intermittent colour. Very occasionally one or other of the chroma amplifier transistors Q301 (BF195) or Q302 (BF194) fails, giving the same result.

If there's no colour and the voltage at M309 is zero or negative, either the delay line driver transistor Q303 (BC147A) is faulty or the colour control or its connections are. Note that there's a second saturation control ganged with the contrast control. All the sliders on this chassis tend

to become noisy – they can be dismantled and cleaned with care.

One strange fault that crops up from time to time concerns the bistable circuit (Q311-2, BC147Bs), which may stop and start erratically. You may find that after replacing both transistors, the ident diode D314 (OA91), and checking the presence of triggering pulses etc. the thing still won't work. Measure the values of the 470Ω load resistors R3101 and R3113: despite their size these two resistors can, and indeed do, increase in value.

That sums up the troubles likely to be experienced with the decoder. Next month we'll continue with the CDA panel and the timebases.

Colour Portable Project

Part 7

Luke Theodossiou

By this time all the modules are built, visually inspected and ready for connecting up. At this stage, the tube size has to be selected in order to determine the degaussing coil and the cabinet. So far, we have been unable to arrange for a cabinet to be made available to readers, largely due to the number of different sized tubes available. This makes the stocking task somewhat difficult and suppliers are reluctant to commit themselves to stocking the various types. There are several alternatives; readers can purchase a cabinet and back from the spares department of virtually any manufacturer to suit their own personal taste. A cheaper solution is to use the cabinet from an inexpensive non-working ex-rental set, but it may prove difficult to find one for the 14" or 16" tubes. In both instances, the control panel will have to be modified to suit the remote control since there is an absence of the usual sliders on the front panel. Perhaps the best solution is to make a cabinet using either Perspex, veneered chipboard or plywood. With a little effort and dexterity, the result can be very pleasing.

The wire loom details for interconnecting the boards are shown in Fig. 1. We suggest the use of 16/0.2mm wires twisted together for each run. The actual connections are:

Signals Board:

Connector A: Aerial input lead (use coaxial cable) from aerial isolator socket.

Connector B: This connects to the following points on the remote control interface board:

B1 (+33V)	to connector B8
B2 (VCR switch)	to connector B7
B3 (+24V)	to connector B2
B4 (Earth)	solder to 'common' terminal of IC2 on underside of R/C interface board
B5 (Volume)	to connector B5
B6 (Tuning voltage)	to connector B6
B7 (Colour)	to connector B3
B8 (Contrast)	to connector B1
B9 (Brightness)	to connector B4

Connector C: RGB outputs. Connect to the appropriate points on the c.r.t. base socket using separated video type cable.

Connector D: This connects to connector A on the timebase board.

D1 (VCR switch)	to A4
D2 (+24V)	to A6
D3 (+220V)	to A5
D4 (Earth)	to A1
D5 (Sandcastle)	to A3
D6 (Video)	to A2

Connector E: Leads to 16Ω loudspeaker. Do *not* use a speaker with a ferrite magnet due to excessive stray field which will affect colour purity.

Timebase Board:

Connector A: See signals board connector D.

Connector B: This is the power supply input and connects to the switch mode power supply module on connector C.

B1 (+220V)	to C1
B2 (Earth)	to C4
B3 (+24V)	to C2
B4 (+118V)	to C3

Connector C: This carries the heater, A1, grid and earth connections to the appropriate points on the c.r.t. base board.

Connector D: This connects to the line and field deflection coils on the tube. Connect a wire link between D3 and D4.

SMPS Module:

Connector A: Mains input via on-off switch.

Connector B: Use pins B1 and B2 only to connect to degaussing coils.

Connector C: See timebase board connector B.

Remote Control Interface Board:

Connector A: This connects to the R/C preamplifier module.

A1 is +18V

A2 is Earth

A3 is input from preamplifier

Connector B: See signals board connector B.

Connector C: This connects to the solenoid of the mains switch, and to the momentary local channel step-through switch. The latter may be located either on the front or back of the receiver and serves as emergency channel

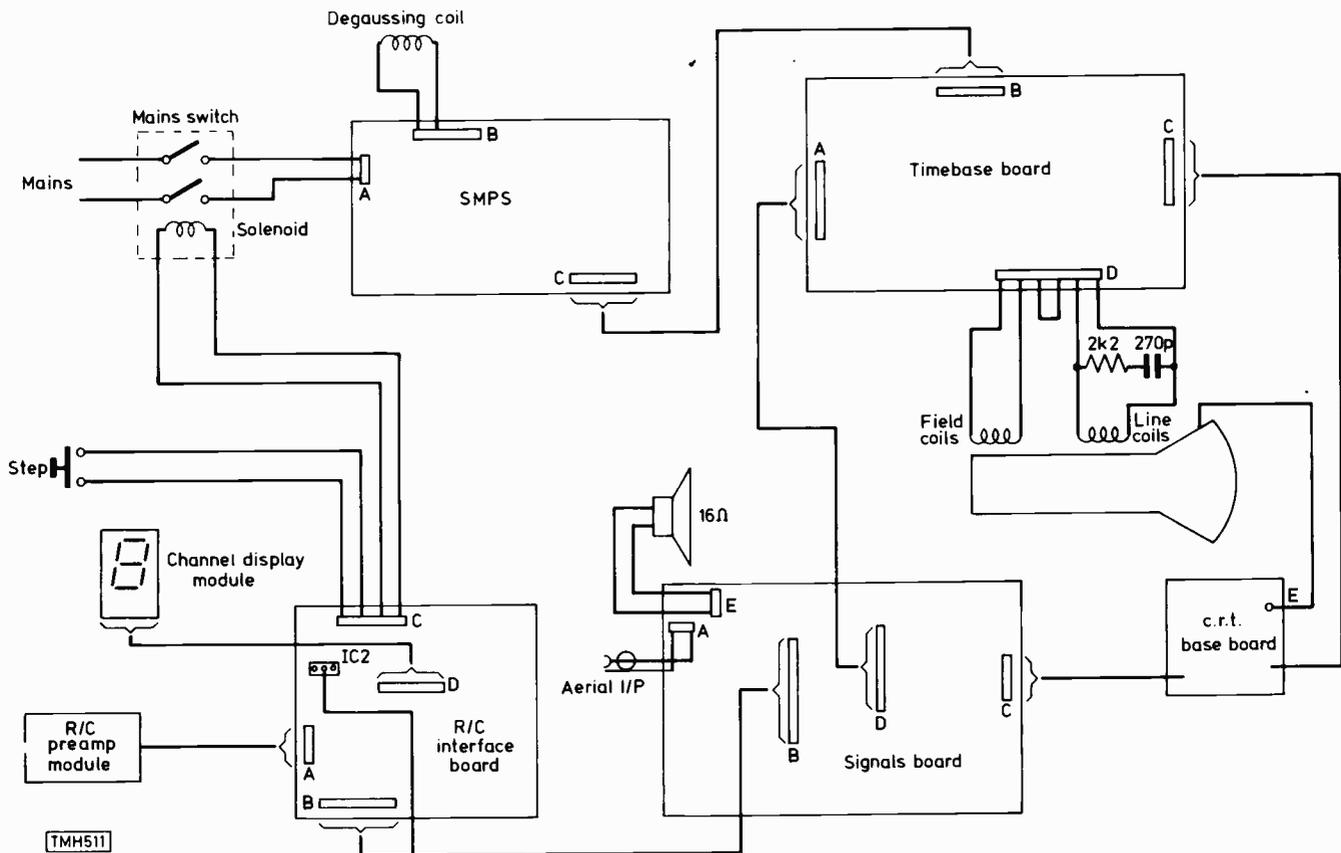


Fig. 1: Board interconnections. See text for details of individual connectors.

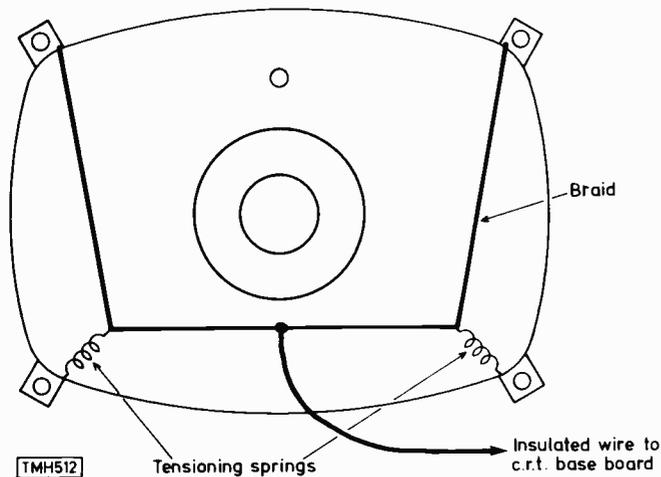


Fig. 2: Tube earthing arrangement.

change in case of R/C transmitter failure (e.g. low battery).

- C1 Earth to solenoid
- C2 Earth to step switch
- C3 Drive to solenoid
- C4 To step switch

Connector D: This connects the channel display module at the appropriate points which are shown in Fig. 11, p. 591 in the September 1981 issue.

The connections to the scan coils on the yoke are made via some solder tags and the safest method of determining the line and field coils is to measure the resistance: the line coils are around 2 ohms, whilst the field coils are about 15Ω. Don't forget to include the RC network across the line coils.

The c.r.t. rimband and Aquadag are earthed to the c.r.t.

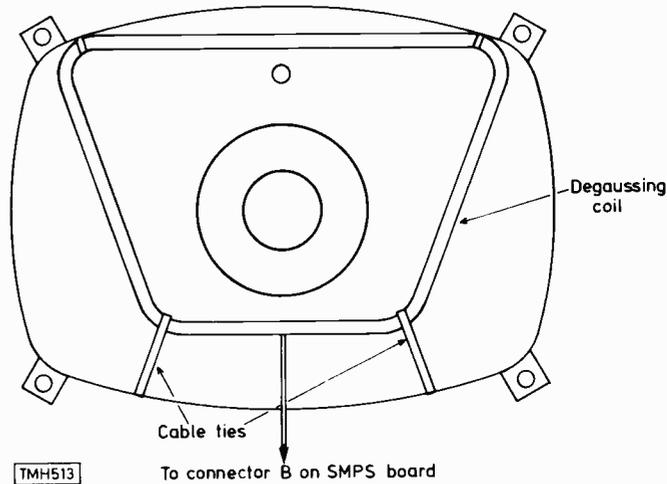


Fig. 3: Mounting the degaussing coil.

base board. In order to ensure good contact with the graphite surface of the tube, a braided cable is used together with two tensioning springs. The idea is shown in Fig. 2.

In addition, the degaussing coil needs to be attached to the tube and the arrangement is shown in Fig. 3.

It is obviously desirable to keep cable runs as short as possible, and a little thought beforehand will reveal the best arrangement. The use of cable ties or lacing cord is recommended for anchoring cables to the cabinet. Do double check the interconnections using the circuit and overlay diagrams – mistakes in wiring up can prove disastrous.

Manual Control Version

For those constructors who wish to keep building costs to a minimum, omitting the remote control can result in a

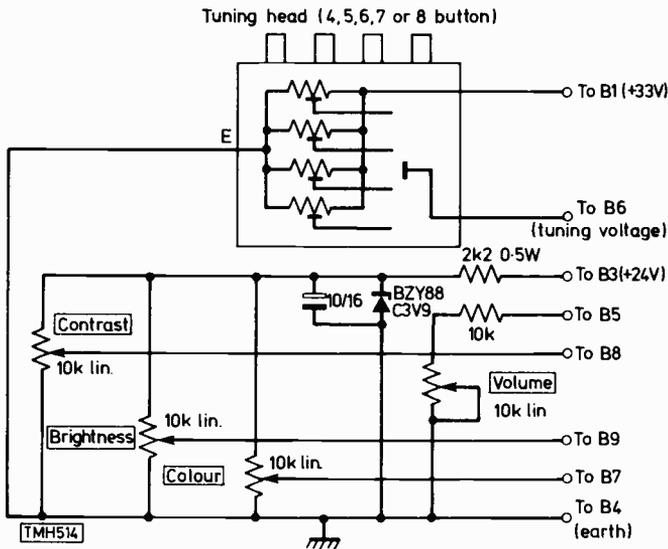


Fig. 4: Front panel control circuit for use when the remote control system is not used.

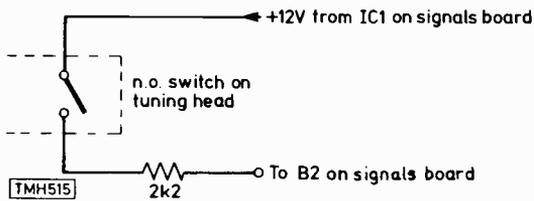


Fig. 5: VCR switching without remote control.

substantial saving. Since there is no provision for driving the channel display module other than by way of the remote control interface board, this will have to be omitted as well as the transmitter, preamplifier and interface board.

The mains switch can now be a standard push-to-make/push-to-break type, rated at 4A. Connector B on the signals board carries all the required connections to the manual front panel controls, i.e. the channel selector and control potentiometers. A suitable circuit for the front panel controls is shown in Fig. 4. Some tuning heads have an additional switch for VCR operation, usually making contact when the last push-button is depressed. In that case the circuit shown in Fig. 5 may be used to provide the facility of optimising the line timebase for VCR operation.

Degaussing Coils

The degaussing coil may be obtained from:
 Forgestone Colour Developments Ltd.,
 Ketteringham,
 Wymondham,
 Norfolk NR18 9RY.

The price is £2.65 inclusive of p.&p. and VAT. Don't forget to specify the tube size.

Demonstration Receiver

Manor Supplies have informed us that they have a demonstration model of the receiver using a 20" tube. This may be viewed at their premises at 172 West End Lane, London NW6.

TV Pattern Generator

FIGS. 4 and 5 below show the print track patterns on the top and bottom of the board designed for the TV Pattern Generator project (for further details see last month's issue).

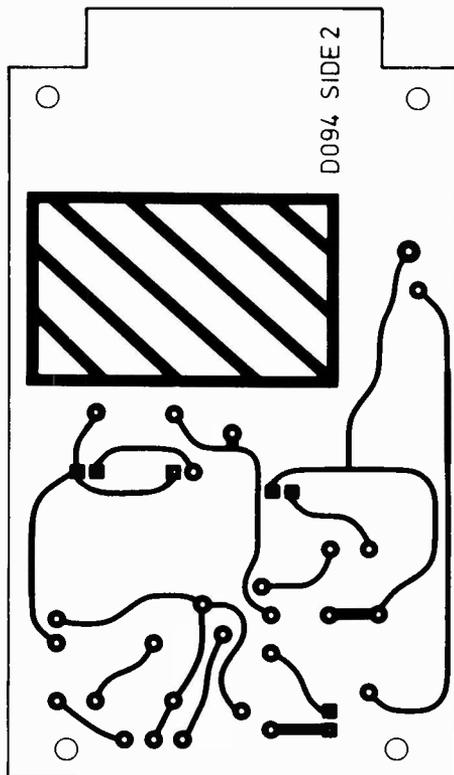


Fig. 4: Top track pattern.

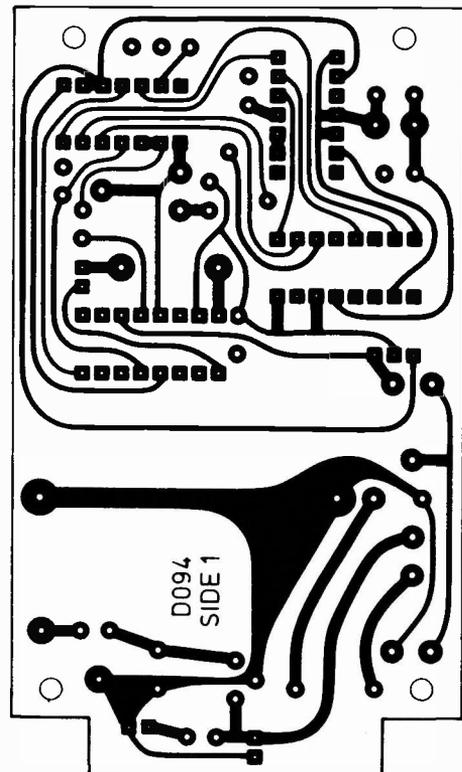


Fig. 5: Bottom track pattern.

Reusing Heads

C. J. Lowdon, B.Eng. (Hons.),
C.Eng., M.I.E.E.

A VCR's head drum usually contains two ferrite video record/playback heads. These are wired in series with the primary of a rotary transformer, and scan the tape one at a time as the drum rotates. Obviously if either head fails the machine requires service attention. A cleaning tape can be tried, but if this fails to restore the performance more drastic steps need to be considered. The aim of the present article is to outline the procedures I follow with Philips N1700 machines.

The first thing to suspect is head clogging. Remove the head drum and if possible spin it at speed in a cleaning fluid (ideally isopropyl alcohol). If this is not convenient, it may be possible to clean the faulty head separately.

To identify the faulty head, use a scope to monitor the output from the head preamplifier board. As a head wears out, its upper frequency response falls off. Since the modulation system used is f.m., the effect of wear is streaking on peak white areas of the picture. Two heads in good condition should produce two balanced signal envelopes on the scope's display. Short-circuiting one head will remove the corresponding signal envelope, enabling you to identify which head is which. Don't apply the soldering iron to the head terminals for more than about two seconds. After removing the drum, try cleaning the faulty head with a child's paint brush and cleaning fluid. Do this carefully, and on no account apply any stress to the head vertically nor any pressure to its face.

Head Transplants

If cleaning is unsuccessful, it can be concluded that the particular head is worn out. This leaves only one experimental course of action, one which I've carried out successfully on a number of worn out N1700 head drum assemblies – two faulty head drums are used to produce one working drum. This unlikely refurbishing process consists of using one of the usable heads as a transplant to replace one of the worn out heads.

The two heads in an N1700 head drum differ slightly. Since the machines use the slant-azimuth technique, the two heads in each drum have oppositely slanting head gaps. It's

necessary therefore to transfer a head of the right sort – the type can be identified by the colour of the wire wound on it.

Procedure

To remove an old head, carefully unsolder the wires from the head to the solder pins. The wires can then usually be pulled from the sealing paint. If there's some resistance, carefully chip the paint away, working in towards the head to raise the wires from the drum. Once the wires are free, the remaining paint can be chipped out (a fine precision screwdriver is useful for this purpose).

The heads are held in position by means of a small amount of adhesive. Application of gentle heat makes it possible to shear the head off. I've developed the following technique for doing this. Prepare a small wooden tool – see Fig. 1(a) – for applying smooth surface pressure to the rear edge of the head. Next turn the drum upside down and immerse part of the metallic section of the drum immediately beneath the ferrite head in boiling water for about thirty seconds – take care not to get water on the head itself. Hold the head securely and apply firm pressure to its rear edge – see Fig. 1(b).

When the recovered, usable head and the defective head have been removed, the transplant can be carried out – after removing the remaining adhesive. The recovered head can be glued in place directly, but it's advisable to use double-sided adhesive tape to position the head first – see Fig. 1(c). The tape should be of similar thickness to the original adhesive – I use Scotch "electrical tape".

Stick a small square of tape firmly on the prepared drum as shown in Fig. 1(c). Then mount the head in a position relative to the drum face matching that of the original head. Once the head has been positioned, apply even pressure very carefully to stick the head firmly to the adhesive tape. Then rotate the drum, observing from above the relative overhang of the two heads. If necessary the transplanted head can be coaxed into a more accurate position by applying pressure to the edges – on no account apply pressure to the centre of the head face. The final step is to solder the wires back on to the pins – see Fig. 1(d). The heads are not polarity conscious.

Testing

Replace the head drum in the machine and give it a try – make a trial recording and replay it, observing the playback signal envelopes with the scope as before. If the transplanted head has been reasonably positioned but the result is unsatisfactory, the head has not survived the treatment. If the replay is o.k., try the machine using a test tape recorded by a known good machine. With luck this will also be o.k. If not, a decision has to be taken whether to leave well alone or try adjusting the head's position to obtain an improved response. If there's a tracking error with the test tape, the head is misaligned vertically – possibly because it's not evenly stuck. Loss of colour may be due to angular misalignment. Any head movement should be done with the wires unsoldered, as they are extremely delicate. Finally, a small amount of resin adhesive can be placed around the head to hold it in place – I've not found this strictly necessary however.

Try the procedure outlined above on two known faulty heads before you tackle a working head. A usable head that fails to replay normal N1700 tapes correctly can still be used for making and replaying temporary recordings. The technique described above has not been tried on any other types of video heads. ■

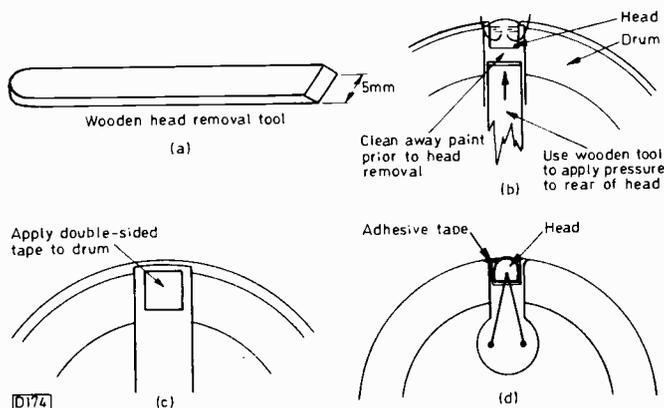


Fig. 1: Head transplant details.

Practical TV Servicing: Replacing the Tube

S. Simon

HAVING decided that a new tube is necessary, we have to face up to the sometimes tedious task of fitting it in the set. There are normally few problems, but on occasions the unexpected happens and a straightforward job then becomes a test of nerves and patience – how that lead become disconnected (when you find it) you'll never know. We're concerned here with tube changing rather than fault finding however, so we'll confine ourselves to routine matters and hope that the unexpected doesn't happen to you. The subject is colour tubes.

Dismantling the Set

The first thing to check is the type of tube fitted in the set – there are some odd ones around, mainly in the less common sets, and this can be confusing when the label is missing. Next survey the cabinet, noting any obstructions that will be left to impede tube removal once the chassis has been withdrawn. This applies particularly to those sets with a vertical main panel, such as the Bush-Murphy A823 series, where there are top and bottom obstructions. It's sometimes easier to remove the fixing screws of any such mountings before withdrawing the chassis, so that they all come out together. Then remove the tube base socket and slacken the clamp of the blue lateral magnet, which is mounted immediately behind the purity rings – we're assuming that the tube is of the older delta-gun type rather than the more recent in-line gun type (PIL, 20AX, 30AX etc.).

Depending on their type, the scanning and convergence assemblies can either be removed together or separately. Also the clamp screw may not be in an obvious position. It's normally recessed between the two units, on the right-hand side. If these assemblies have easily reached plug and socket connections, it's sometimes better to disconnect them and leave the assemblies themselves on the tube neck until the chassis has been removed, rather than having the assemblies dangling around half way through the proceedings.

After you've removed the tube base and the blue lateral magnet, note the position of the purity rings before removing them: try not to disturb them too much, as this can save much time when the new tube is being fitted. If the work bench is wide enough, the chassis can be swung round at an angle so that the tube can be taken out without removing the tuner and the front controls. Note also the positions of the convergence and scan coils, so that they can be put back in near enough the same positions on the neck of the new tube.

There are also connections to the degaussing coils: these may consist of a simple plug and socket, but in some chassis the leads extend back to the tube base socket, together with one or more earthing leads from the degaussing shield – you may find them screwed or soldered to the tube base. Carefully note each lead's position and tag. With more recent tubes there's no separate degaussing shield – the shield is within the tube, the degaussing coils being hung on the tube.

Before the chassis can be withdrawn it will also be necessary to remove the e.h.t. connector, which goes to the top or bottom of the bowl depending on which way up the tube is mounted. Note that in some cases this contact can hold a charge for a considerable period. It's prudent therefore to touch the clip to chassis after disconnecting it, and to discharge the tube's connector to the degaussing shield – this is in contact with the tube's outer coating – using a convenient lead or screwdriver blade.

Tube Removal

With all the leads off, check how the degaussing shield is held in place. This is sometimes done by means of screws or nuts at the four corners, sometimes by means of springs. If nuts are used, remove one of the lower ones to see if it also secures the tube – there are not always two lots of nuts and washers. If the shield and the tube's mounting band are held by the same nuts, care must be taken to support the tube when the shield is removed, i.e. when the nuts fixing the shield have been removed there may be no further tube fixing, so that the tube will be loose.

It's far safer to lay the receiver face down on a soft surface and support the chassis on a stool or box rather than work on a bench. By doing it this way, the tubes can be lifted in and out vertically with less risk of strain. Support the cabinet so that the face of the tube protrudes without touching the surface.

Note also that there is additional earthing between the tube's mounting band and the degaussing shield, via a high-value resistor. Make sure that this resistor is fitted with the new tube, and that it's not open-circuit. Poor earthing accounts for the sometimes strange effects encountered when a new tube has been fitted – instead of the results you hoped for, you may get variations in picture size and general fluctuation etc.

Fitting the New Tube

Having stripped any earthing clips and braiding from the old tube, fit these to the new one in the same positions. Present the new tube to the cabinet, ensuring that the e.h.t. connection is in the same position as before, generally at the top but sometimes at the bottom (particularly with Thorn sets).

The method of fixing the tube's lugs to the cabinet varies from set to set. When the tube and shield have been firmly fitted and the earthing leads have been correctly connected, the scan coils and the convergence assembly can be slid on to the tube's neck and provisionally clamped, observing the note you made of their original positions. Next fit the purity magnets if these are separate from the convergence assembly, then the blue lateral magnet clamp, the tube base and the e.h.t. connector (once the chassis has been replaced to enable this to be done).

Run through the plug and socket connections to ensure that none have been forgotten, and resolder or otherwise reconnect the earthing leads from the degaussing shield and

the tube's outer coating to the base panel. Reconnect the degaussing coils, and when you've done all this double check everything again. It's all too easy to overlook a disconnected lead or plug, and the extra trouble taken at this stage can save a lot of heartache later on.

Purity and Convergence

When you switch the set on, the images displayed on the screen may appear a trifle strange. First switch off the blue and green guns to leave what should be a red only display. If it's pure red you're in luck and the other guns can be switched on again and the convergence carried out. If the red raster is impure, i.e. other colours are present with the blue and green guns switched off, you will have to carry out the purity procedure first.

Slacken the wing nuts securing the scan coils and slide the assembly back. Then adjust the purity magnets to obtain a large area of red in the centre of the screen, rotating the rings relative to each other until the central area is free from anything other than red. If difficulty is experienced, degauss the tube manually. When you've got a good central red area, slide the scan coils forward to spread the red area out to the edges of the screen. Some fine adjustment of both the rings and the coils may be necessary. Switch off the red gun and switch on the other two guns in turn to ensure that the blue and green rasters are pure.

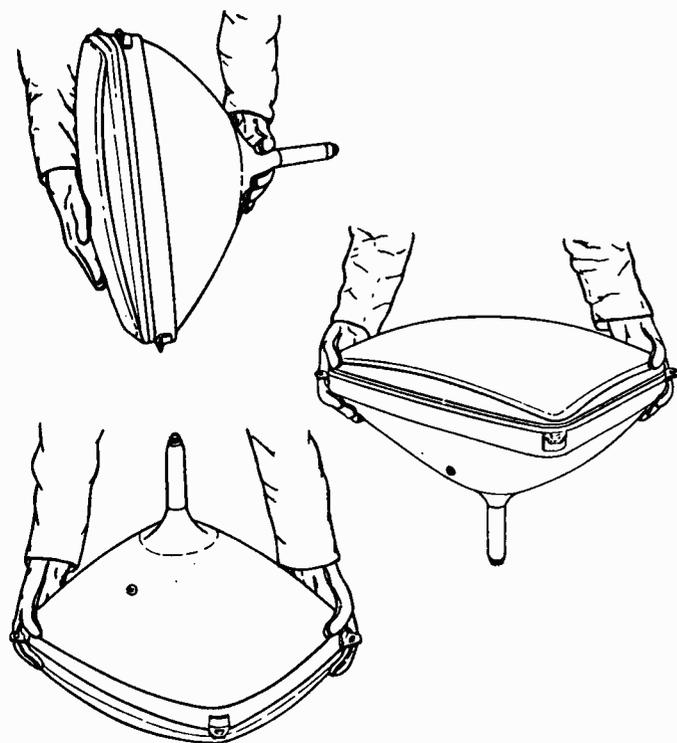


Fig. 1: Handling tubes. Due to their high internal vacuum, tubes are dangerous and should be handled with care. The drawings above show recommended methods, when lifting the tube from the edge-down position (top), when lifting the tube face up (right) and when lifting it face-down (bottom). Under no circumstances should any force be applied to the neck of the tube, its most vulnerable point. If any risk is likely to be encountered, protective clothing, particularly eye shielding, should be worn. The lugs are provided for mounting the tube. Push the scan coils fully forward during the warm-up and preadjustment periods: keep the period during which they are pulled back to the absolute minimum (the average beam current should not exceed 200µA per gun during this time). Illustrations and details courtesy of Mullard Ltd.

Having obtained acceptable purity, one must face the fact that doing this will have had a profound effect on the convergence, so that it will be necessary to go through the convergence procedure. Again we must stress that these notes apply only to delta-gun tubes.

In a delta-gun tube the blue gun occupies a central position at the top or bottom depending on which way up the tube is fitted, the red and green guns being angled to the sides. The static convergence magnets occupy corresponding positions, and are used to move the beam positions accordingly, i.e. blue up and down and the other two diagonally. The idea is to converge the red and green images first, then move the blue one to marry up, using the blue static magnet for vertical movement of the blue display and the blue lateral magnet at the rear of the tube to obtain horizontal registration. This gets things right at the centre of the screen. Some adjustment will also have to be made to the dynamic convergence controls on the convergence panel. We described this in an earlier article (see November 1979). Adjusting the static convergence effects the purity, which will have to be checked again: resetting this will make some static convergence readjustment necessary – carry on until a happy balance is obtained.

Tube Drive

Since the old tube will probably have been set up to obtain a reasonable grey scale with guns whose emission differed, the even emission of the guns in the new tube will probably mean that the c.r.t. first anode controls need adjustment. You'll usually find them on the convergence panel, occasionally elsewhere. Adjust them for nice mid and dark greys (no colour), with the video drives set to obtain light greys and white. Once a happy balance has been achieved, turn up the colour or tune it in. The aim is to get good flesh tones – good colour cannot be achieved unless the grey scale has first been set for a good black-grey-white picture.

Miscellaneous Points

It must in fairness be pointed out that the foregoing is an over-simplified account of tube changing. It has to be, since each different model requires a different drill. If the appropriate manual gives the required information, this should be followed. In the absence of such information, a preliminary examination will generally show what the snags are and whether the construction is such that the main panel or chassis can be removed in one piece to expose the tube.

With chassis such as the Pye 725 series, which has separate vertical panels, the process becomes more tedious due in this case to the multitude of plug and socket connections between the right-hand side power supply panel and the left-centre timebase panel, not to mention the rear centre dropper resistor unit. The left side panel can be left in place, since it doesn't impede tube removal, but removal and replacement of the other two requires a measure of patience and dour determination. Lots of other sets call for dexterity and industry, so that all in all tube replacement is not a job that should be undertaken lightly just because doing it the first couple of times presented few problems.

Remember that PIL tubes have the scan coils etc. permanently fixed, so that the replacement will come with the coils and magnets already fitted and aligned. This is another reason for having the new tube to hand before removing the old one – so that you know what you're dealing with.

Long-distance Television

Roger Bunney

THERE was a slight fall off in propagation conditions during August, but overall and compared to the usual conditions in August it was an extremely active month. It was also (in the UK) a very dry and hot month, which gave improved tropospheric conditions for much of the period. The most unusual phenomenon occurred during the 4th-6th August, when the weather was very hot and humid with intense thunderstorms: several enthusiasts reported that the local u.h.f. signals faded out, suffering from some form of absorption. Here at Romsey the local Rowridge services, which are normally noise-free, were fading into the noise, the picture being subject to co-channel interference. The effect was particularly marked on the 4th. Fortunately Sporadic E propagation has remained very active, the following log of SpE reception being compiled from my own and several other enthusiasts' reception.

- 2/8/81 RTVE (Spain) chs. E2, 3, 4; RTP (Portugal) E3; RAI (Italy) IA; JRT (Yugoslavia) E3; NTV (Nigeria) E3 - received by Cyril Willis in Cambridge!; plus several unidentified stations and the Italian NCT "free" station which transmits between chs. E3/IA.
- 5/8/81 MTV (Hungary) R1; DFF (E. Germany) E3; TVP (Poland) R1; JRT E3, 4; TSS (USSR) R1.
- 6/8/81 CST (Czechoslovakia) R1; TVP R1; JRT E3; Switzerland E3; plus unidentified signals.
- 7/8/81 RAI IA; RTP E3.
- 8/8/81 NRK (Norway) E2, 3, 4; YLE (Finland) E4; TSS R1, 2; RTVE E3; JRT E4.
- 9/8/81 RTVE E2, 3, 4; Switzerland E2; ORF (Austria) E2a; RAI IA; NCT E3/IA; JRT E3, 4; MTV R1, 2.
- 10/8/81 TSS R1; RAI IA; RTVE E3.
- 11/8/81 MTV R1, 2; JRT E3, 4; RAI IA; NCT E3/IA; RTVE E2, 3, 4; TVP E3. There was good MS (meteor scatter) reception this day.
- 12/8/81 TVR (Rumania) R2; NCT E3/IA; RAI IA, B; JRT E3; Switzerland E2, 3; RTVE E2, 3; NRK E2, 3.
- 13/8/81 TSS R1, 2; SR (Sweden) E2; TVP R2; RAI IA; YLE E3; NRK E2, 3, 4; plus unidentified signals on chs. R1, 2, 3.
- 14/8/81 TSS R1; YLE E2, 3.
- 15/8/81 SR E2, 3; RTVE E2, 3, 4; JRT E3. Plus many unidentified signals.
- 16/8/81 RTVE E2, 3, 4; RAI IA, B; JRT E3, 4; TSS R2; MTV R1; RTS (Albania) IC; plus unidentified signals.
- 17/8/81 TSS R1, 2; CST R1; TVP R1, 2; RAI IA, B; RTVE E2, 3, 4; RUV (Iceland) E4.
- 18/8/81 TSS R1, 2, 3; CST R1; RUV E3; NRK E2; MTV R1, 2; TVP R1, 2; JRT E3; plus many unidentified signals.
- 21/8/81 TSS R1, 2.
- 22/8/81 RTVE E2; RAI IA.

- 23/8/81 MTV R1; RAI IA; TSS R1, 2; JRT E4; plus many unidentified signals.
- 24/8/81 CST R1; TVP R1.
- 25/8/81 SR E2, 3; NRK E3; TSS R1.

More exotic reception during the month was as follows. On the 14th there were very strong ZTV (Zimbabwe) signals from Gwelo on ch. E2, with clear pictures and sound, including "The Incredible Hulk" followed by "Mixed Blessings" (1800-1830). There was further reception from ZTV on the 14th and 15th, including part of the "Salisbury Show". Hugh Cocks (E. Sussex) logged NTV (Nigeria) on the 2nd and 14th. JTV (Jordan) ch. E3 was logged on the 16th and 17th during the early evening period. The 15th produced Arabic f.m. signals at 95MHz, coinciding with ch. R5 programmes. One continuing mystery has been the repeated reception, again by Hugh, of a system M (525 lines) ch. A2 signal carrying AFRTS programmes, via SpE from the south east. We are awaiting information from AFRTS as to whether the Iraklion (Crete) transmitter is still in operation.

Tropospheric Conditions

Tropospheric propagation during the period was also well above average. Following the excellent opening on July 31st, the first week of August produced enhanced W. German, French, Swiss (chs. E4, 6, 12 and 27) and Irish signals, also the "usual" GDR ch. E6/34 signals. DR (Denmark) was well received on the 6th in the south east. There was another lift on the 12th-14th, when noise-free signals from the Channel Isles were received here at Romsey on chs. 41/54. The 13th produced extremely intense French (TDF) signals in both Band III and at u.h.f. Improved conditions continued throughout the rest of August, peaking on the 17th (with Switzerland at u.h.f.), the 18th, the 19th (with RTVE), the 25th (RTVE again, including ch. E11) and the 27th (with W. German signals). The weather pattern at the time of writing (on the 28th) suggests that there will be further tropospheric activity within the next few days.

In General

It became very evident during the recent enhanced tropospheric conditions that the French are testing their new channel allocations. Hugh Cocks has been receiving 625-line system L signals on ch. 6 on a daily basis and, following a recent visit to Paris, John Tellick confirms that ch. 6 is being tested between 0900-1800 with colour bars and "message bands" advertising French teletext.

TSS have been using a new test pattern on ch. R2. It originates from Tallinn, Estonia, and carries a station identification. Let's hope that this progressive move will extend to the rest of the network!

The most important development this month is unofficial confirmation that Morocco has a ch. E4 transmitter in operation - their first in Band I and currently the only such Band I transmitter in N. Africa. This station has been received daily in the south of France via tropospheric propagation, and also here (unknowingly!) on July 10th at 2300, with local news, and by myself on July 30th at 2030 with a modified EBU bar pattern. We're awaiting further details from RTM as to location, transmitter power, etc.

My thanks to the following who provided various reception reports quoted above: Ray Davies (Norwich), Hugh Cocks, Ryn Muntjewerff (Holland), Martin Reynolds (Nuneaton), Cyril Willis (Cambridge), George North

(Walton), Nicholas Brown and Mark Baldwin (both Rugby) and Keith Hamer (Derby).

News Items

Luxembourg: Following our report last month, we understand that the entire RTL mast structure subsequently collapsed. Hugh Cocks reports (August 26th) that RTL ch. E7 is back on air, at greatly reduced power. It seems that Belgian transmitters may be used to maintain the RTL services.

W. Germany: According to Alexander Wiese (Munich), 27 ZDF transmitters have been modified for dual-sound transmissions. He also reports that the E. German Helpterberg station is now transmitting DFF-1 on ch. E37 (in addition to DFF-2 ch. E22).

Spain: RTVE has been experimenting with the use of solar-powered relay transmitters at five sites throughout Spain. The results have been successful, and a further fifty transmitters, with powers less than 1W, are to be installed. The aim is eventually to use 5W solar-powered relay transmitters.

Eire: A bill has been published to permit the formation of a broadcasting body, similar to the IBA, to issue contracts for commercial broadcasting. RTE, Reception Investigations, Donnybrook, Dublin 4, Eire have published an interesting transmitter and reception folder listing their u.h.f. transmitters and including coverage maps - it's called "Reception of RTE Television Programmes at U.H.F. - What You Should Know", and is highly recommended.

Hungary: The Antiope and UK teletext systems are to be tested during 1982, with a view to starting a teletext service in 1983.

ATV: Blean Video Systems, 4 Mount Pleasant, Blean Common, Canterbury, Kent CT2 9EU have sent us details of their comprehensive range of ATV receiver and transmitter modules. If you want details, send 20p with a foolscap s.a.e.

From Our Correspondents . . .

Paul Barnaby (Hull) has modified a Bush TV161 series receiver for operation on systems B/G/L and is using it in conjunction with a WB2 (Band I) and a Colour King (u.h.f.) aerial. He's been very successful with west and east European reception during the past three months - via SpE and tropospheric propagation. Lille chs. 21/24 are weak but regular signals, as are many Dutch and Belgian transmitters. He's had problems with CB interference, but having contacted the operators succeeded in getting low-pass filters fitted.

William Rhodes (Rednal, Birmingham) is another Colour King user. He has to have his aerial in the roof space, but with a low-noise head amplifier reports good reception - during the opening on the 31st, he received many u.h.f. stations including a remarkable catch, the "RS-KH" electronic pattern from Zilina (Czechoslovakia) on ch. R35.

Brian Penforth (Chippenham, Wilts) is using an old Wenvoe (ch. B5) X aerial with an up-converter to feed his rented Baird receiver. During the past SpE season he's been successful in logging signals from most of Europe with this simple installation. During the July 28th-31st opening he achieved quite startling results with a hand-rotated multiple-director u.h.f. array. CB interference is again a problem. I've heard, incidentally, that in the Folkestone area cordless 'phones operating in the 49MHz band - this is within the passband of the Folkestone relay transmitter's B2 receiver from Dover - are being up-converted and transmitted via

GOLDEN ANODISED AERIALS: SUPERB ECONOMY AMPLIFIERS:

EST. 26 YRS. ALL PRICES INCLUDE VAT. EST. 26 YRS.

Masthead Amps	Type	Gain	Price
Astrax 1441	VHF/UHF	21dB	£12.82
Astrax 1450 LN	Bands 4&5 (TV)	28dB	£15.49
Astrax 1455	Bands 1&3 (TV)	25dB	£16.81
Astrax 1520	power unit for above amps		£9.15

All mast amps require a 1520 power unit.

SPECIAL OFFER HIRSCHMANN ROTATOR £42.95

IMPORTANT Quote TVM

For highly graphic lists and Brochure, Send 52p. Refund of 30p on 1st purchase over £5.

Stockists of the finest aerials available in Britain:

OPTIMAX (Malta)
FUBA TV & FM aerials (W.Ger.)
MARGON TV aerials (Hol.)
UKW FM aerials (E.Ger.)
ANTIFERENCE TV & FM aerials (U.K.)

ESTABLISHED
26 YEARS



The fabulous golden anodised FUBA XC391

We specialise in
Rotator & DX work.
Bands I & III stocked.

ASTRA (GOLDEN D.I.Y.) AERIALS SOME OF OUR SUPERB TV & FM AERIALS.

Name	Group & W/Band	Gain dB	Price	After discount
Margon 103 (TV)	both stocked	19.5/21.5	£61.41	£52.19
Margon 91 (TV)	both stocked	18.5/20.5	£44.18	£37.53
Fuba 91 (TV)	both stocked	18.5/20.5	£48.61	£43.75
Optimax 14 (FM)	Band 11 W/B	14	£57.50	£48.88
Optimax 8 (FM)	Band 11 W/B	9.5/10.5	£32.54	£29.29
Fuba 8 (FM)	Band 11 W/B	10.5	£40.85	£36.77
Fuba 9 (FM)	Band 11 W/B	11.0	£45.85	£41.27

Over 3,000 aerials stocked; all transmitters; poles; lashings; rotators; clamps; wall brackets; amplifiers; diplexers; triplexers; notch filters; coax white or brown.

Many of our customers come from recommendation.

53 WHITEHORSE ROAD, CROYDON, SURREY.

Nr. Spurgeons Bridge Tel: 01-684 4300

Open 9.00-5.30 TUE-SAT.

01-684 5262

Closed 12.30-1.30 Closed All Day Mon.

24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY

South West Aerial Systems

10 OLD BOUNDARY ROAD,
SHAFTESBURY, DORSET, SP7 8ND

tel. 0747 4370



The PLUSTRON 5" TVR5D 'Euro TV' features VHF/UHF TV coverage with system B/G/I (5.5/6MHz) sound switching and MW/LW/VHF-FM radio facilities. Operating from internal/external batteries or AC mains, it features good sensitivity and selectivity via its integral whip or external (coaxial socket) aerial input. The receiver is ideal for basic TV and FM DXing. Other Plustron models are available, send SAE for leaflet.

Our comprehensive range of aerials, amplifiers, filters and accessories for TV/FM DXing, domestic/fringe installations, deflector and 2nd channel reception is detailed in our catalogue. We make our own range of wide-band Band 1, Band 2, air/marine PSB aerials, a CB 1/2 wave dipole, and a customer consultancy service is available to resolve reception problems.

Plustron TVR5D 5" mono TV (Securicord delivery)	£96.50
SWAS - WB3 Wideband Band 1 (47-68MHz) 3 element yagi	£26.75
Jaybeam ABM8 Wideband Band 3 (175-230MHz) 8 element high gain yagi	£18.20
Wolsey 'Colour King' wideband UHF (470-860MHz) 4 bay bowtie aerial	£21.75
Babani BP52 (2nd edition) Roger Bunney's book on DXTV technique/practice	£2.35
BATC 'Amateur Television Handbook' (3rd edition), ATV technique/practice	£2.35


All prices include VAT, carriage and packing. Include SAE with ALL enquiries. Our comprehensive catalogue costs 45p.



Hugh Sculley (BBC Nationwide) received in Cape Town by Paul Johnson.



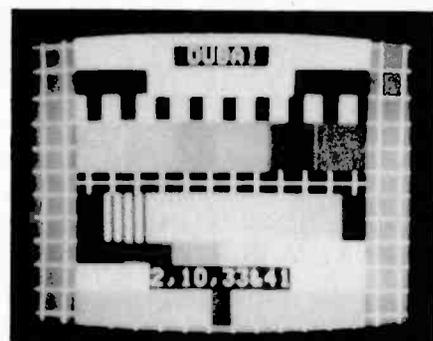Moscow ch. R3 (programme-4) received in Holland by Ryn Muntjewerff.



The Dubai square PM5544 pattern (ch. E2). Photo from H. Lloyd-Bennett.

the Folkestone B4 transmitter . . .

John Reed works and lives at Jeddah, Saudi Arabia. His reception, using a variety of aerials, makes envious reading – Syria ch. E4, Dubai E2, Jordan E3, RTVE E2/3 plus other European transmitters, the “local” Aramco TV ch. E3 and suspected NTV (Nigeria) ch. E3, all via SpE, while Sudan TV from Omdurman at 600 miles (ch. E5, 2.4kW) is received daily. On July 28th he logged a ch. E5 signal from the south – a programme called “Watch Mr. Wizard”. Excluding the Sudan and Ethiopia, the source is probably one of the two Yemens. The local Saudi Arabian television is listed as ch. 25, but additional unlisted stations are in operation. Those received in Jeddah are on ch. E21 to the south, on chs. E42/3 to the north and chs. E50/1 to the north east. John is currently using a JVC CX610 receiver; he’s obtaining a Sony system A receiver in the hope of catching Crystal Palace ch. B1 – we await the results with interest!


The subject of Crystal Palace is also dear to the heart of Paul Johnson (ZS1BR) in Cape Town. He’s been receiving the BBC-1 signals for some time – one of our photographs shows Hugh Sculley (BBC “Nationwide” programme) on April 3rd this year. The signals are mainly propagated via early evening trans-equatorial skip, though daytime F2 propagation also occurs. There’s evidence of tropospheric enhancement at the receiving end of the signal path. The polarisation seems to be random, and an aerial orientated away from the correct direction will often give enhanced picture quality with reduced multipath distortion/smearing. The receiver being used is a Bush Model TV141U, with a vertically mounted three-element Yagi aerial. The TF-1 (France) ch. F2 sound is also often well received.

Finally, H. Lloyd-Bennett (Dhahran, Saudi Arabia) has sent us several photos showing local TV signals: the ch. E2 Dubai signal is the “square PM5544” often received last winter via F2.

N7118 PAL COLOUR BAR GENERATOR

An extremely light, compact and durable instrument, designed for mobile Colour T.V. Maintenance in the customers home. The basic model includes a built-in rechargeable battery plus a Power Unit/Charger. (A fully charged battery gives 10 hours continuous use). All patterns and sync. pulses are derived from a single crystal controlled oscillator, producing extremely accurate, stable displays. The patterns available are: Standard Colour Bars, Red Raster, Linearised Grey Scale Step Wedge, Crosshatch and Peak White Raster. A Coaxial Socket on the rear panel provides a modulated UHF or VHF (please specify) signal of approx. 1mV for direct connection to Receiver Aerial Socket. An (optional) integral Sound board is available, producing a Sound Carrier (6MHz or 5.5MHz), frequency modulated by a 1KHz Sinewave. The N7118 will also house a third board that provides a 1 Volt p to p, 75 ohm Video Signal to a rear panel B.V.C. Socket.

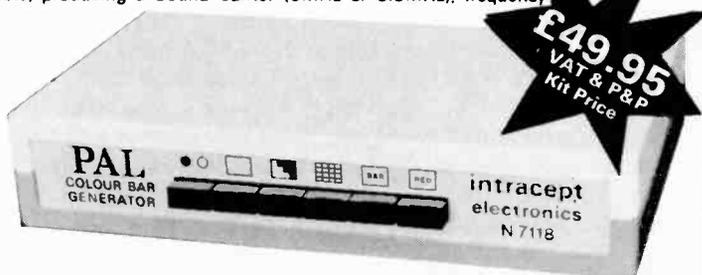
Complete kit, including a professional finished case, screen printed P.C.B., Ready Built P.S.U., and all components – **£59.50** inclusive. Sound and Video Boards, add **£10.29** per board. Ready Built – **£88.25** inclusive, Sound and Video Boards add **£11.45** per board. S.A.E. for details and specification.



N7121 VIDEO PATTERN GENERATOR

This Generator, based on the N7118 is designed for the mobile servicing of Colour Monitors and V.D.U.'s. It produces three separate Colour output signals at 1 Volt peak to peak into 75 ohms. Also provided is a separate sync. output which may be adjusted for positive or negative-going sync. tips. The Generator may be operated at 625/50MHz or (by operating a push switch on the rear panel) 525/60Hz.

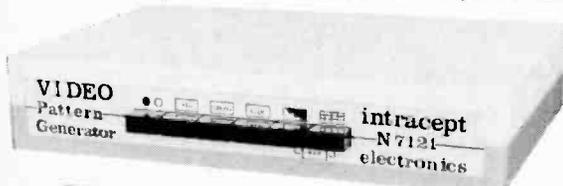The patterns available are colour bars, crosshatch, 8 step grey scale wedge, peak white plus many other combinations i.e., red raster, blue raster, yellow crosshatch etc., as defined by the three (red, green – blue) beam switches on the front panel. The generator is powered by an internal Ni-Cad battery and is supplied complete with the Charger/Power Unit.



Price (Built & Tested) **£75.00** + VAT & p. & p. Total **£88.25**.



INTRACEPT ELECTRONICS LIMITED

203 Picton Road, Liverpool L15 4LG.

Tel: 051-733 3042.

VCR Servicing

Part 3

Mike Phelan

LAST month we discussed the servo systems required in a VCR, with specific reference to the arrangements used in the basic JVC HR3330 machine. If the subject of servos seems a bit on the complicated side, just remember that what happens is much the same as what happens in a TV set's flywheel line sync circuit. In modern VCRs, much of the servo circuitry is incorporated in special-purpose i.c.s, so the servo circuit component count is fairly low.

Let's summarise briefly the minimum requirements of a VCR servo system:

- (1) It must ensure that the head drum and the tape-drive capstan rotate at constant speeds, the same on both record and playback.
- (2) The positions of the video heads must be referenced to the field sync pulses during recording.
- (3) Control pulses derived from the field sync pulses must be recorded on the tape.
- (4) On playback, either the head drum or the capstan must be referenced to the recorded control pulses. The item not referenced to the control pulses is speed controlled only.

The fourth requirement ensures that the heads scan the recorded tracks accurately. Clearly it doesn't matter whether the machine is "drum controlled", as with the HR3330 we described last month, or "capstan controlled". The simplest example of the latter approach is probably the Philips N1500/N1700 series, so to round off our introduction to VCR servos we'll take a brief look at the arrangements these use.

Philips Servo System

In the N1500 and N1501 the circuitry is all discrete, while in the N1502, N1700 and N1702 there are a few logic and linear i.c.s involved. The basic principle of operation remains the same however, despite the fact that the N1500 uses a.c. induction motors with eddy current brakes. To go off the track for a minute, the latter fact means that the motors are arranged so that they run slightly fast, the servo system applying a braking effect. An alloy disc on the motor or driven element passes through a polepiece carrying a coil fed from a power transistor, the transistor being the final item in the servo chain – like the motor drive transistor in the arrangements we described last month. The circuit is arranged so that when this transistor is at the centre of its operating curve, the current through the braking coil maintains the correct motor speed.

Fig. 19 shows the N1500's servo system in block diagram form. It's very simple and very effective with, basically, only three things being switched. A 25Hz reference is used on both record and playback. As usual, the field sync pulses provide the record reference, after division by two. On playback the reference signal comes from the power supply, again at 50Hz then divided by two. This division by two is carried out by an astable multivibrator which acts as a voltage-controlled oscillator to the incoming reference signals, providing a 25Hz squarewave output. This output is applied to the control track head on record, meeting requirement (3) above, and is processed to provide ramps for the capstan and head drum

servo sample-and-hold circuits, meeting requirement (2). The drum servo compares the ramp with feedback pulses from the head drum on both record and playback. The capstan servo compares the ramp with servo head feedback pulses on record, and with the off-tape control track pulses on playback. Requirements (1) and (4) have thus been met. In connection with the latter, note that the tracking control affects the phasing of the playback sample pulses in the capstan feedback control loop.

Back to the HR3330

We'll return now to the JVC HR3330 machine, to examine the signal sections in more detail, starting with the machine in the record mode. The tuner unit, channel selector and i.f. strip are conventional, and will therefore be left out of our description. The tuner is preceded by an aerial amplifier and splitter (see Fig. 20), the splitter being necessary to divide the signal between the VCR's tuner and the tuner in the associated TV set – otherwise you'd have to change the aerial connections over to watch an off-air transmission with the VCR not in use, or when a different channel was being recorded. If the channel being recorded is also being watched, this can either be done in the normal manner or via the VCR. In the latter case the receiver's

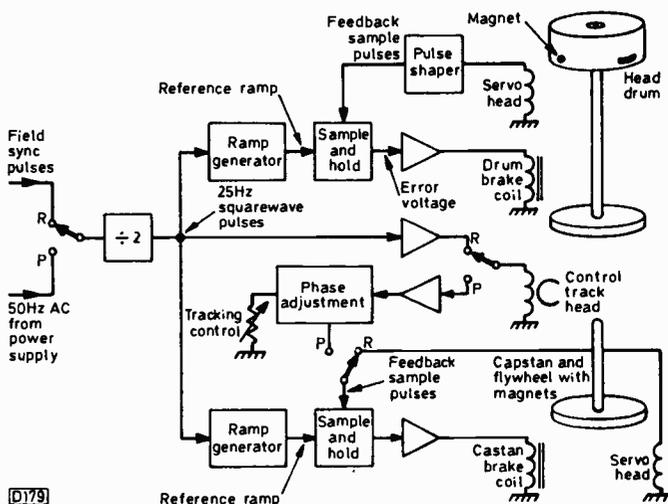


Fig. 19: Servo system used in the Philips N1500 VCR. Note that the control track is at the top edge of the tape in the Philips system.

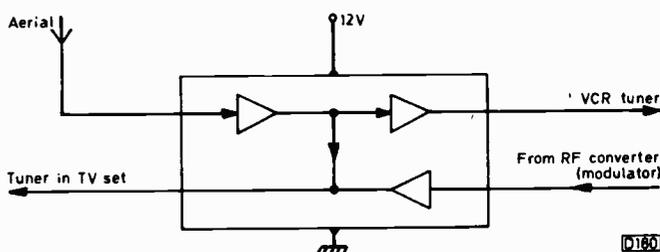


Fig. 20: The signal splitter/preamplifier arrangement used in the JVC HR3330 VCR.

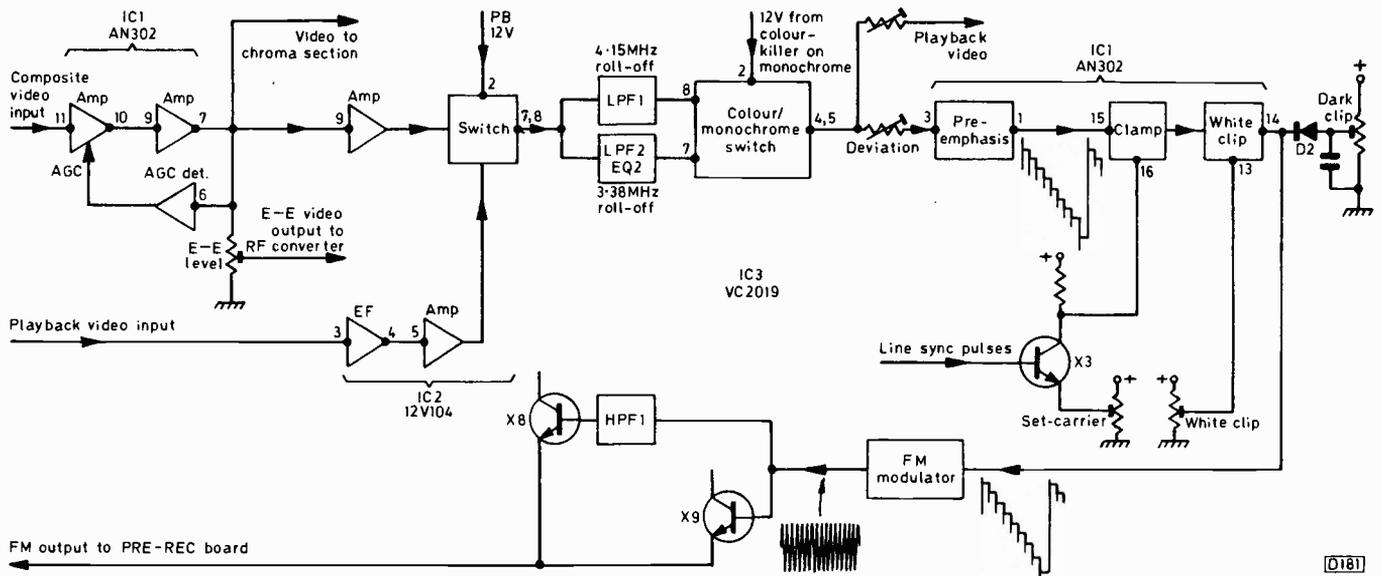


Fig. 21: Block diagram of the luminance signal path on record.

“VCR channel” is selected, the signal going through the VCR’s tuner and i.f. strip, then back out via the r.f. converter where it’s remodulated on to a u.h.f. carrier, round about channel 37. The r.f. converter’s output can be adjusted up or down a few channels – there would otherwise be severe patterning if one of the local channels was close to the VCR’s output channel. Using the machine in this manner is known as the E-to-E mode. Direct off-air viewing will give better results of course, as the signal goes through only one tuner and i.f. strip. The amplifier in the “mix booster” (as it’s called) makes up for the insertion losses introduced by the splitter.

The audio signal produced by the sound detector passes via an equalizing amplifier to a push-pull oscillator which adds an h.f. bias signal of 70-80V peak-to-peak prior to the signal being recorded on the top edge of the tape by the audio head. The h.f. oscillator also feeds the erase head, the latter erasing the full width of the tape. On VHS machines there’s an “audio dub” facility, enabling the audio track only to be erased and re-recorded without affecting the picture. This necessitates an extra slide switch and an extra erase head that covers only the audio track – the latter is part of the same assembly as the audio/control head.

Luminance Signal Path

The video signal from the i.f. strip, or from the video input socket if the mode switch is in the “camera” position, enters IC1 on the Y-C (luminance-chrominance) board – see Fig. 21. It goes through two stages of amplification in IC1, the first being gain-controlled because the luminance signal must be of constant amplitude before conversion to f.m.

The signal leaving pin 7 of IC1 is split three ways. The first branch goes to the chroma processing circuit via a 4.43MHz bandpass filter. The second branch goes to the r.f. converter via the E-to-E level preset, to be remodulated on to a u.h.f. carrier so that the recording can if necessary be monitored. The final branch goes to a further stage of amplification, in IC2, and then to an electronic switch, operated by the PB 12V supply, in the same i.c. This switch is included so that some of the recording circuit can also be used on playback.

The signal path then splits again, via two filters giving 3.38MHz and 4.15MHz roll-offs. The following i.c. (IC3) is switched by the colour-killer. This is done so that the

signal with the higher frequency roll-off can be used on monochrome, the 3.38MHz roll-off removing the colour from the luminance channel on a colour recording. If the colour signal was still present when the luminance was converted to f.m., there’d be some very strange effects indeed. In later versions of the machine only the 3.38MHz filter is incorporated, LPF1 being removed and IC3 being replaced by an emitter-follower, the response then being the same on both colour and monochrome.

The luminance signal, with the chroma now removed, then returns to IC1 for pre-emphasis. The preset marked “deviation” adjusts its amplitude – we’ll see why in a moment. A sync-pulse driven clamp, consisting of transistor X3 and yet another part of IC1, then restores the signal’s d.c. level, the “set carrier” control adjusting the clamping level. This is followed by white and dark clipping to remove the spikes produced by the pre-emphasis (where they exceed a certain level). The white clip circuit is again within IC1, the dark clip circuit consisting of a simple, adjustable diode clipper.

The signal has now been prepared for f.m. modulation. The circuit of the f.m. modulator, which consists of a

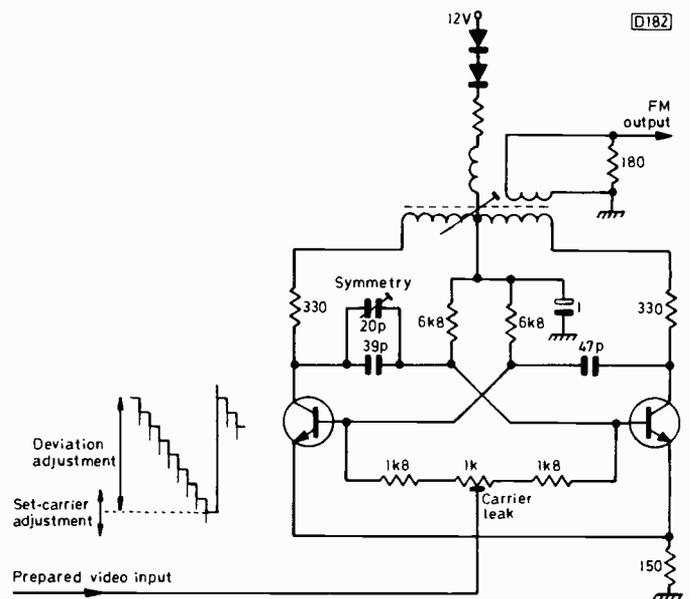


Fig. 22: The f.m. modulator circuit used in the JVC HR3330 VCR. Later machines use an i.c.


voltage-controlled multivibrator (a Kalitron to be exact), is shown in Fig. 22. The higher the voltage fed into the video input, the higher the output frequency. As we mentioned in an earlier instalment, a swing of 3.8MHz for the sync tips to 4.8MHz for peak white is used in the VHS system.

The reason for the set-carrier and deviation controls shown in Fig. 21 should now be apparent. As the sync tips are clamped, the set-carrier control is adjusted so that an input at the same d.c. level as the sync tips produces a 3.8MHz output (to put it another way, we're adjusting the overall d.c. level of the signal so that the oscillator's output is at 3.8MHz during the sync period). The deviation control adjusts the signal amplitude and thus the output frequency at all levels above the sync tips (the adjustment is for peak white at 4.8MHz). Don't attack the nearest VCR with your trimmers - we'll give the correct method of

adjusting these two controls later. They need adjustment only if replacements have been carried out in this part of the circuit - or if the "phantom twiddler" got there first . . .

The f.m. modulator in the HR3330 is contained in a screened box and uses discrete circuitry - in later models an i.c. is used. The two controls within the modulator adjust the mark-space ratio without modulation (symmetry) and when fully modulated (carrier leak).

Back to Fig. 21. The resultant f.m. carrier is then split, one side going to X9 and the other to X8 via HPF1. This filter removes the lower f.m. sidebands to leave room for the down-converted chroma signal. X9 is switched on with a monochrome signal, bypassing the filter. The signal then leaves the Y-C board to go to the pre-rec board where the chroma signal is added. After that it passes to the rotary head transformer.

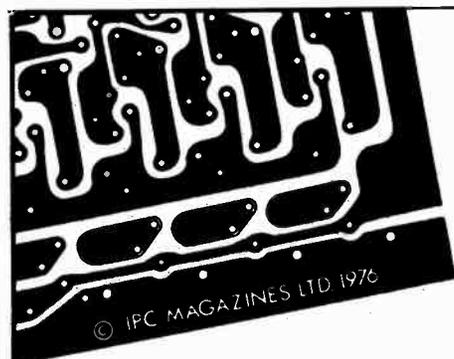


TELEVISION

READERS PCB SERVICE

Issue	Project	Ref. no.	Price
November 1976	Ultrasonic Remote Control	D007/D008	£3.85 per set
March 1977	Teletext Decoder Power Supply	D022	£3.75
May 1977	Teletext Decoder Input Logic	D011	£12.50
June 1977	Wideband Signal Injector	D031	£1.00
June 1977	Teletext Decoder Memory	D012	£10.50
July/Aug 1977	Teletext Decoder Display	D013	£11.00
September 1977	Teletext Decoder Switch Board	D021	£1.75
April/May 1978	CRT Rejuvenator	D046	£3.00
October 1978	Colour Receiver PSU Board	D052	£4.00
January 1979	Colour Receiver Signals Board	D053	£10.75
February 1979	Commander-8 Remote Control System	D054/5	£6.00 per set
March 1979	Colour Receiver Timebase Board	D049	£17.13
July 1979	Colour Pattern Generator	D062	£14.50
		D063	£9.15
		D064	£8.50
September 1979	Teletext Decoder Options Board	D065	£6.00
August 1979	Teletext Decoder New Mother Board	D067	£4.00
August 1979	Simple Sync Pulse Generator	11331	£8.00
September 1979	New Teletext Signal Panel	D057	£3.50
October 1979	Teletext Keyboard	D058	£5.00
October 1979	Teletext Interface Board	D066	£5.00
November 1979	Colour Receiver Remote Control	D061	£3.75
January 1980	Remote Control Preamplifier	D070	£9.50
February 1980	Teletext/Remote Control Interface	D071	£4.00
February 1980	LED Channel Display	D072	£3.25
March 1980	Improved Sound Channel	D074	£6.25
May 1980	Monochrome Portable Signals Board	D075	£7.75
June 1980	Monochrome Portable Timebase Board	D076	£1.00
July 1980	Monochrome Portable CRT Base Board	D077	£9.50
Sept/Oct 1980	New CTV Signals Panel	D078	£8.50
January 1981	Small-screen Monitor Board	D079	£4.50
December 1980	Video Camera Pulse Generator Board	D080	£5.50
December 1980	Video Camera Video/Field Timebase Board	D082	£2.00
January 1981	Video Camera Power Supply Board	D083	£4.00
January 1981	Video Camera Line Timebase/H.T. Board	D086	£4.50
Feb/March 1981	Video Mixer	D089	£6.75
May 1981	Switch-mode Power Supply	D088	£10.00
June 1981	Simplified Signals Board	D091	£9.00
August 1981	Timebase board	D087	£2.00
August 1981	CRT base board	D085	£1.00
September 1981	Remote Control Preamplifier	D090	£7.00
September 1981	Remote Control Interface	D095	£1.00
September 1981	Channel Display Module	D084	£4.00
October 1981	Remote Control Transmitter	D094	£6.50
October 1981	TV Pattern Generator		

All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

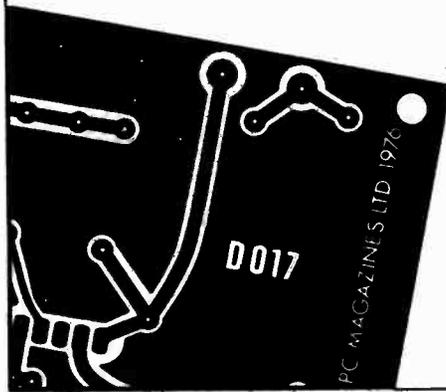Any correspondence concerning this service must be addressed to **READERS' PCB SERVICES LTD**, and not to the Editorial offices.



To:- Readers' PCB Services Ltd. (TV); Fleet House, Welbeck St., Whitwell, Workaop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME _____

ADDRESS _____

Post Code _____

TV Standards

David K. Matthewson, B.Sc., Ph.D.

I HEARD a sad story the other day of a chap who had purchased a Sony VCR whilst on a business trip to the USA, intending to use it on his return to the UK. He'd been attracted by the very low price of \$600 (about £280 at the time). The machine was an SL5700, the US equivalent of the C7 Betamax VCR. When our business man returned, he called upon the local TV shop to set the machine up and was rather taken aback when the engineer informed him that no way would his VCR work, as it was designed for the US TV system. The owner protested that the American salesman had sold him a transformer to make the machine work in the UK, for which he'd paid an extra \$34... The last I heard was that the gent concerned was seeking an export market for his brand new but useless VCR, without much luck.

This little tale is typical of the confusion that has always surrounded the various TV systems in use and their compatibility. The situation is likely to get worse, since video equipment seems to be cheaper in many foreign markets. One can imagine TV games cartridges, video discs and other software being bought whilst on holiday with little thought being given to the technical parameters concerned. Let's consider the problems then, and some possible ways in which they can be avoided.

If we take for example a colour TV set, the following factors would need to be taken into consideration: mains supply (voltage/frequency); line standard (mainly 625 and 525 lines); colour system (NTSC/PAL/Secam); the channel bandwidth and vision/sound signal spacing; the polarity of the vision modulation (positive- or negative-going); and the sound modulation (a.m. or f.m.).

TV Systems

Table 1 shows the main characteristics of the principal TV systems in use world wide. Within particular geographical regions, the problems are not so great. For

Table 1: Characteristics of TV Systems.

System	Lines	Channel bandwidth (MHz)	Vision bandwidth (MHz)	Sound/vision spacing (MHz)	Vision modulation	Sound modulation
A	405	5	3	- 3.5	Positive	a.m.
B	625	7	5	+ 5.5	Negative	f.m.
C	625	7	5	+ 5.5	Positive	a.m.
D/K	625	8	6	+ 6.5	Negative	f.m.
E	819	14	10	±11.15	Positive	a.m.
G/H	625	8	5	+ 5.5	Negative	f.m.
I	625	8	5.5	+ 6	Negative	f.m.
L	625	8	6	+ 6.5	Positive	a.m.
M	525	6	4.2	+ 4.5	Negative	f.m.
N	625	6	4.2	+ 4.5	Negative	f.m.

Notes: The UK uses system I at u.h.f. Most of W. Europe uses system G at u.h.f. System H has a wider vestigial vision sideband than system G. System K1 has a wider vestigial vision sideband than system K. System D is used in E. Europe. France uses systems E and L - system K is used in French overseas territories.

instance, with a monochrome portable receiver in W. Europe the main problem will be the different vision/sound signal spacing, plus in the case of France the different vision modulation and sound modulation systems.

Another difference is that whereas v.h.f. is being phased out for TV use in the UK, in other areas v.h.f. is still very much alive. In most European, American and African countries a multiband tuner will be required.


The three main colour systems NTSC, PAL and Secam - there are variants, particularly of the latter - are totally incompatible. The problem with PAL/Secam operation has become less with modern i.c. decoder designs, since some sets of chips will automatically switch between these two systems.

Though the 405- and 819-line systems still linger on, there are basically only two line standards to be reckoned with today - 625 lines (50 fields) and 525 lines (60 fields). The use of 525 lines and the NTSC colour system go together, i.e. the USA, Japan and various countries in the Americas. The use of 625 lines is linked with the PAL and Secam colour systems. It's possible to display a monochrome 525-line picture on a 625-line receiver and vice versa, but the picture geometry will be incorrect. Adjusting the controls will alleviate this problem. It's not possible unfortunately to record a 625-line picture on a 525-line VCR or vice versa, a problem that's plagued broadcasters for years (see Table 2).

Multi-standard Equipment

Having considered the main differences between the various TV standards, let's consider some ways in which the problems can be alleviated.

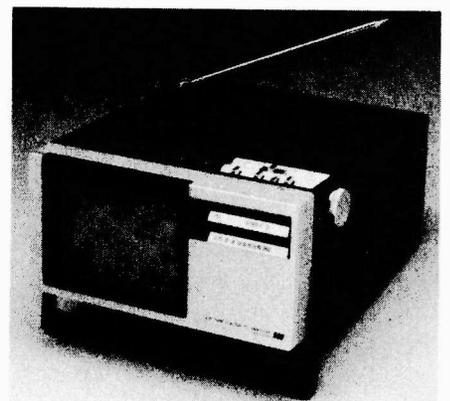Multi-standard receivers to operate on the various different standards used in W. Europe have been available for some years - the Belgian Barco company produce such sets for example, though their price has tended to restrict



The JVC Model CX610GB. This 6in. colour receiver/monitor has a v.h.f./u.h.f. tuner and can be used to receive system B, G, D, K, K1 and I transmissions, with either PAL or Secam colour. For monitor use, video and audio input and output sockets are provided.

Table 2: Replaying videotapes.

VCR	Cassette	TV set operating on:		
		PAL	NTSC	Secam
PAL	PAL	Colour	Mono	Mono
	NTSC	—	—	—
	Secam	Mono	Mono	Colour*
NTSC	PAL	—	—	—
	NTSC	Mono	Colour	Mono
	Secam	—	—	—
Secam	PAL	Colour	Mono	Mono
	NTSC	—	—	—
	Secam	Mono	Mono	Colour

*Note: VHS Secam tapes are recorded using different standards depending on whether they are intended for the French or Middle Eastern markets. Thus a French Secam tape played on a Middle Eastern market VCR such as the Portatel VHS conversion will produce a monochrome picture. French Secam tapes played back on a PAL VCR will appear in monochrome, whereas Middle Eastern tapes will usually produce a colour picture.

them to professional use. A cheaper solution is now available in the form of the JVC Model CX610GB, a small portable colour set capable of receiving 625-line programmes on systems B, G, D, K, K1 and I, in either PAL or Secam colour. It's also possible to obtain sets capable of 525/625-line operation. Some of these sets will automatically switch to the correct line standard. The Sony Model PVM1850PS is capable of receiving both PAL and Secam off-air transmissions, and will display modified NTSC pictures replayed via a suitable VCR.

VCR Problems

When it comes to using VCRs in different countries, the problems become more complex. A 625-line UK TV set will display a 525-line picture without much trouble as the range of timebase adjustment is quite wide – often a small adjustment to the field hold control is all that's needed, though the picture geometry will not be quite right. Standard VCRs are not so tolerant, and are designed to cope with either 50Hz or 60Hz field pictures, not both. If you attempt to record UK TV on an NTSC machine it just won't work, as much of the timing circuitry is controlled by the received sync pulses. The servo system will try to divide 50 by two and expect 30, and when it gets 25 instead it gets confused! Conversely a 625-line VCR won't record US transmissions.

The broadcasters get around these problems by using standards converters – but even optical units cost in excess of £100,000. The low-cost solution was pioneered by Sony: when they introduced their semi-professional U-matic range of VCRs in the UK, they designed them to be capable of playing back NTSC tapes recorded on NTSC machines in the USA or Japan. The signal provided by these machines is not to the PAL standard when an NTSC tape is being played back but, interestingly, neither is it to the NTSC standard! Instead, a special standard called NTSC 4.43MHz is used, with 525 lines, a 60Hz field frequency and a 4.43MHz colour subcarrier. This enables a relatively conventional type of PAL monitor to be used to view the tapes. The system has since been adopted by other manufacturers, and has been applied to domestic VCR systems, including VHS and Betamax. ■

next month in

TELEVISION

● **PROGRAMMABLE CLOCK-TIMER**

Our next project is a microcomputer based clock-timer unit. Its original purpose was to augment the rather basic timers used in most older VCRs. The final design adopted is so versatile however that many other applications will be found for it around the home or workshop – for example for switching lights on and off to deter burglars, for switching domestic appliances, including central heating controllers, radio and TV sets, electric blankets and so on.

The unit has four totally independent switched outputs, each capable of 2.5A r.m.s. (600W load). This can be increased to 10A by adding external switching elements. Features include 224 switching times; 4-digit, 7-segment display to indicate real time, turn on/off times and reset times; individual LEDs indicating the day of the week, switch and status; a reset function allowing continuous or manually initiated time looping from minutes up to one week; a period feature which calculates and enters the turn-off time when an on period is entered; memory view; memory clear allowing total, specific switch or individual deletions to be made (e.g. for correcting errors); and manual control of any output.

The unit is self-contained and built on two small single-sided PCBs. For long-term reliability and noise-free operation, solid-state relays are used as the output switching elements. A comprehensive programming guide will be given, together with full constructional details.

● **SERVICING FEATURES**

A guide to the Philips K12 chassis, with some common faults. More on the Luxor 110° hybrids and VCR servicing. Les is back – with Desperate Dan.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO (Name of Newsagent)

Please reserve/deliver the December issue of TELEVISION (70p), on sale November 18th, and continue every month until further notice.

NAME

ADDRESS.....

Focusing Systems

Richard Blenheim

A RECENT article in the Practical TV Servicing series drew attention to the focus circuits used in colour receivers. The emphasis was on older models and their tubes, since these are the ones most likely to require servicing. There have been some developments in tube focusing systems in recent years however, and it's worth summarizing them. Apart from the technical interest, it's as well to be aware of the features of different types of tube to ensure that replacements are of the correct type.

The vast majority of colour tubes in use are of the bipotential variety, which means that the first anodes are operated at around 500V whilst the focus electrodes are operated at some 4.5kV. The main exception amongst older tubes is the unipotential type, such as the Mullard 18in. A47-342X tube, which is operated with much the same voltages on the first anodes and the focus electrodes. The trend in recent times has been to obtain improved focus performance by operating tubes with a higher voltage on the focus electrodes. Both the 30AX and modern 90° tubes operate with a focus voltage of about 7kV, which is around 28% of the e.h.t. instead of the 20% used with bipotential tubes. Mullard use the term hibi (high bipotential focus) to describe the new type of electron gun used in their latest 90° narrow-neck tubes. Chassis that use this type of tube include the Thorn TX9 and the new Decca/Tatung 120 series.

The Hibi Gun

Fig. 1 compares the conventional bipotential gun with the newer hibi type. The main beam focusing action occurs between the focus electrode and the final anode: the reason for increasing the focus voltage is to reduce the beam magnification, and thus the spherical spot distortion, in the main lens. Reducing the main lens magnification means that the focus electrode has to be lengthened in order to maintain the correct spacing between the beam crossover point and the main lens. This in turn means that prefocusing is required to prevent the beam becoming too wide. Prefocusing is achieved by modifying the first anode structure as shown. Corner resolution is improved by

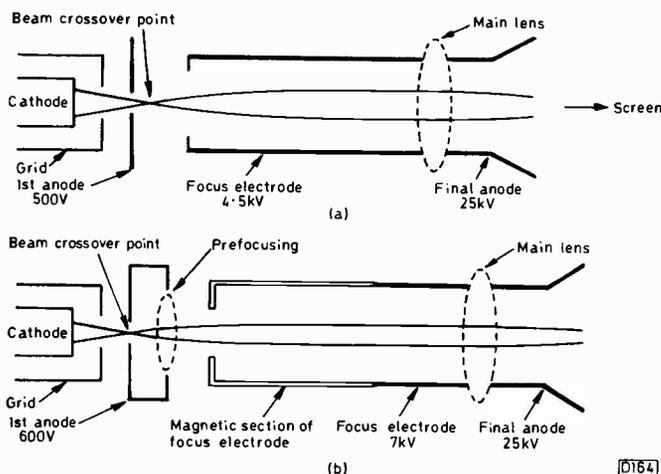


Fig. 1: Comparison between the conventional bipotential tube gun (a) and the newer hibi type (b).

making the initial part of the focus electrode of a magnetic material such as NiFe 42.

In comparison with the conventional bipotential gun, the spot size with the hibi gun is reduced by 20% at the centre of the screen. At the corners the spot width is reduced by 15% and the spot height by 30%. The overall result is greatly improved resolution, which is of particular importance for text displays.

The hibi gun has an increased cut-off voltage (about 140V), which means that the first anode voltage should be somewhat higher – about 600V. Since the first anode voltage determines the prefocusing effect, any marked change will adversely affect the focusing. The hibi gun also calls for a different focus spark gap and tube base socket (the focus pin has to be more heavily insulated). A suitable base is the JEDEC type B10/277. Printed spark gaps are not suitable at 7kV. The printed type used with bipotential tubes allows slight leakage across the board. This is not serious, even with high humidity. At 7kV however, the leakage can be sufficient to cause the focus voltage to vary, so that a spark gap physically separate from the board is necessary.

Some Other Techniques

An alternative approach to obtaining improved focus

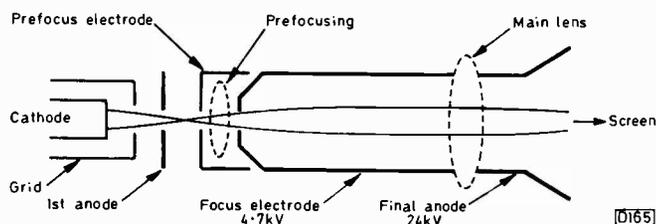


Fig. 2: Additional electrode used in the National Panasonic Quintron tube to provide prefocusing and thus improved overall focus performance.

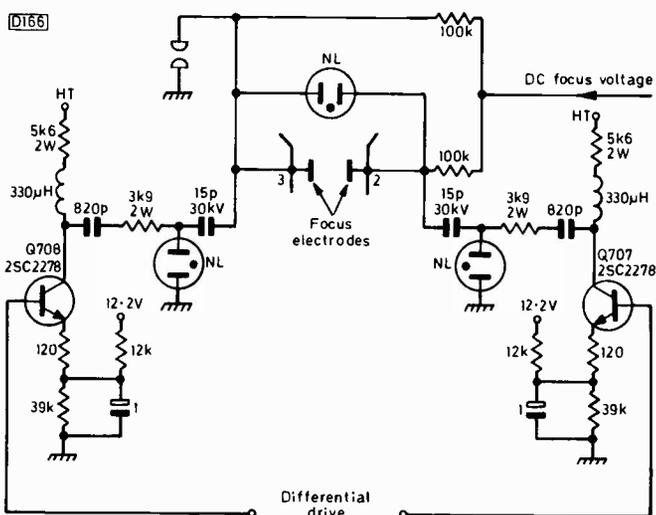


Fig. 3: Circuit used in the Sony 27in. Model KV2704UB to apply a.c. and d.c. voltages to the focus electrodes. Sony call this the "Turbo Trinitron" system.

performance is used in the National Panasonic Quintrix tube, which employs an additional electrode between the first anode and the focus electrode to provide prefocusing. The arrangement is shown in Fig. 2, the additional electrode being operated at a lower voltage than the first anode. National Panasonic have been using this type of tube since 1975.

Something quite different is used by Sony in their Model

Letters

As far as heat and solid-state circuitry are concerned I must confess to being rather paranoid, my efforts to detect and eliminate "hot spots" in the various pieces of equipment that appear on my workbench often bordering on the frantic. The worst problem is intermittent faults in circuitry that's apparently working within specification. I've now come across a useful dodge that often provides a cure however. The clue as to what's wrong is provided when an "educated" finger tip detects an untoward temperature rise in an otherwise well behaved chip.

When I first came across this problem I thrashed around for a solution and, as I usually do when all else fails, stared moodily into the junk box. There, staring back at me, were several stone dead SN76023N type devices complete with beautiful five-fin heatsinks. So I carefully dug the corpse of the dead device out of one of the heatsinks and glued it, using a touch of super glue, to the offending though working device in the problem set. Some hours later my good lady, who is also the chief soak tester, informed me that the set had worked faultlessly all day – with the back on at that. Since then I've used this dodge to good effect on many occasions – in fact I'm now looking for a source of supply of five-fin 45mm wide heatsinks that doesn't depend on customers extending their speaker leads!

The dodge is worth a try and, in this era of house-coded special devices with any number of pins you can think of besides 14 and 16, can save a lot of time – some of these devices take ages to turn up and often fail to cure the problem when they do. It also saves the customer a bunch of notes.

In closing, keep it up Les! It does my heart good to read you once a month. Hearing of other sufferers' problems is better than Valium any day!

Anthony Beddow,
Minions, Cornwall.

ITT CVC32 CHASSIS

The intermittent loss of field scan at the top of the screen, mentioned in the September *Service Bureau*, is a common fault with the ITT CVC32 chassis. The cause is a dry-jointed connection where the emitter of the lower field output transistor T9 is returned to chassis.

J. Tayler,
Arbroath.

USE OF SOLDERING FLUX

While browsing through a local hardware shop recently I noticed some small, flat round tins which had a dark green label and seemed vaguely familiar. Bringing one of them into the focus range of my ageing bifocals, I noticed that they were something I'd not seen for a very long time, not since the advent of resin cored solder – they were tins of

KV2704UB. This set has a 114° 27in. tube, and to achieve improved focus performance uses a split focus electrode system (pins 2 and 3) with both d.c. and a.c. voltages applied to the focus electrodes. The a.c. drive is differential (see Fig. 3), and is used to alter the spot shape on picture transients. For this purpose a signal is tapped from the luminance channel via a high-pass filter and fed via a phase-splitter to separate driver and output stages. ■

fluxite. Now whether due to some unaccountable impulse or simply nostalgia I'll never know, but I added one of these tins to my other purchases, took it home – and promptly forgot about it.

Some weeks later I came across the tin and decided to see whether its contents had a place in this modern world. I was pleasantly surprised to find that a small amount of flux applied to such items as transistors, i.c.s and other printed panel mounted components made removal much more easy. Indeed where additional solder is applied to aid removal, a saving can be made in view of the present cost of a reel of solder. Other uses include tinning leads, component ends and heavy-duty soldering. Excessive flux can lead to tracking, so any surplus should be removed.

A tin of sticky brown paste may perhaps be an unwelcome item on a busy work bench, but if the tin is kept covered when not in use it can be a very useful friend. After cleaning the tip of the soldering iron with a file, a quick dab into the flux not only produces a perfect tool for modern soldering techniques but also brings back memories with the familiar brief hiss. Perhaps the only thing missing is the blue/green flame when the iron was returned to the gas ring for reheating! Are there many of us left?

A. S. Foster,
Brixham, Devon.

SOLDERING-IRON STAND

I've recently made a simple, folding soldering-iron stand which is not only very stable but, as it folds up, occupies the minimum amount of space, making it ideal for outside work. The whole thing can be made from reasonably thick mild steel wire – I used 3mm wire. Fig. 1 shows the details – (a) in use and (b) when folded. To fold the stand, swing the holder backwards. Make the "U-turns" at the ends of the holder after passing the wire through the "eyes" in the base – the eyes should be just wide enough for the ends of the holder to pass through. The four thick rubber sleeveings are optional, but avoid slipping when the stand in on a smooth surface. It's as well to incorporate them – before the eyes are formed of course.

Victor Rizzo,
Msida, Malta.

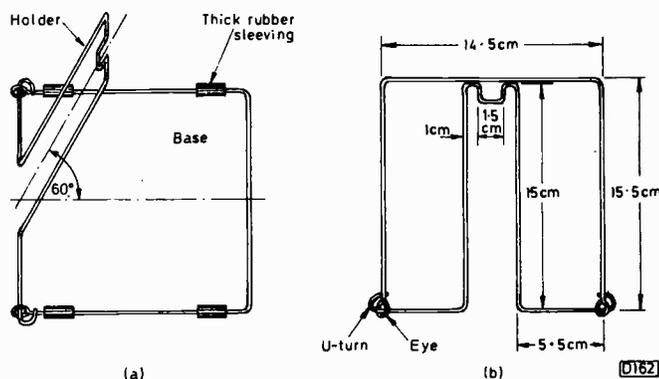


Fig. 1: Details of the folding soldering-iron stand devised by reader Victor Rizzo. (a) In use. (b) Folded.

VCR Clinic

Reports from Mike Phelan and Steve Beeching, T.Eng. (C.E.I.)

We've had a couple of cases this month of machines that played back all right but refused to record correctly. The first one made recordings that were covered with black streaks and noise – it was a Ferguson 3V00 (JVC HR3330). We connected a scope to TP1 on the pre/record board to take a look at the f.m. output to the heads, and found that the waveform had a brightening effect at the centre – see Fig. 1(a). When we expanded the trace to show individual cycles of the waveform these were found to be nothing like sinewaves – in fact the effect looked like crossover distortion in an audio amplifier – see Fig. 1(b). This gave us our clue. The record output amplifier circuit is shown in Fig. 1(c). The waveform was o.k. up to the bases of the driver transistors X4/5, but the voltages at the output transistors X6/7 were incorrect. In fact bias diode D2 was short-circuit, giving us what was indeed crossover distortion. We find it a good rule to say that if a luminance fault does not seem to be like any of those encountered in a TV set, the cause is probably in the f.m. sections of the machine.

The recordings made by the next machine looked very similar, but this time we had more of a chase before tracking down the cause of the trouble. The waveform at TP1 was perfect. On playing the tape back however we had a picture that was discernible but covered with white dots, just as if one head was giving no or a low output. We connected the scope to TP7 on the same board to check the off-tape f.m. signal and found that this was very low on every other field. So we switched to record and connected the scope directly to the head connections (42 and 52, see Fig. 2). There was about 2V of f.m. at both points. We next checked the connections to the rotary transformer, but these were o.k. Clutching at straws we changed the head drum. The problem remained as before, and we became resigned to the idea of changing the lower drum assembly, which is not a very pleasant job. Inspiration then suddenly came – we made scope checks at the earthy ends of the connections (41 and 51) of the rotary transformer. Connection 41 was o.k. (no signal), but connection 51 had 2V peak-to-peak signal, the same as at 52! This was simply due to the fact that X11, which earths point 51 on record, was not being switched on. R30 in series with its base was dry-jointed. Notice that opposite ends of the transformer are used on record and playback, the earthy ends being connected to chassis via switching transistors.

No Colour

After resoldering R30 we gave the machine a test and found that the colour suddenly disappeared on playback. Checking with a prerecorded tape showed that the fault was in the machine's playback system.

In cases of no colour the things we check first are the presence of sync pulses at TP213 on the luminance/chrominance board, of a 4.433619MHz signal at TP215 and a 5.06MHz carrier at TP219. These were all present. The colour/monochrome switch at the rear of the machine was then tried, but there was still no trace of any colour. The next step should be to check through the signal

path with the scope. TP202 and TP203 (see Fig. 3) both had good 626.9kHz signals and, proving that frequency conversion was taking place, there was a 4.43MHz signal at pin 7 of IC202. So even if the frequency of the colour signal had been wrong there should have been some trace

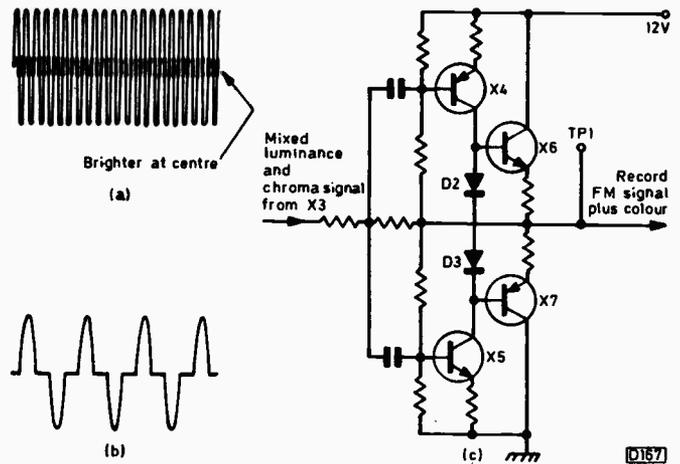


Fig. 1: (a) Faulty luminance signal at TP1. (b) Expanded trace of the signal at TP1. (c) Record driver and output stage circuit (simplified).

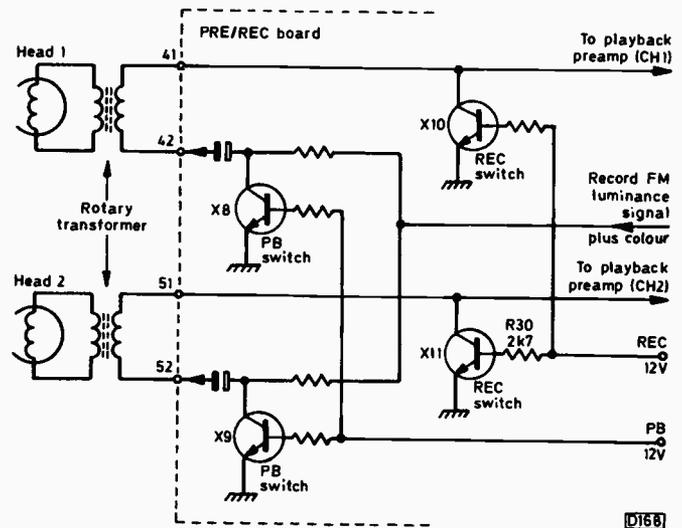


Fig. 2: Record/playback switching at the heads – simplified circuit. X8/9 are switched on during playback. When recording, X10/11 are switched on.

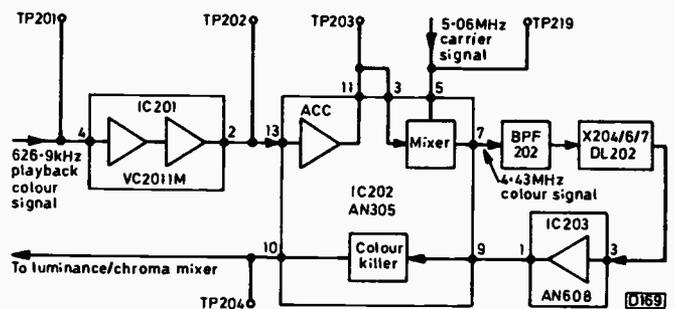


Fig. 3: Block diagram of the colour signal path on replay.

of colour on the screen with the killer overridden. The signal was still present at pin 3 of IC203, but nothing was coming out at pin 1. A replacement AN608 i.c. (it looks like a four-legged transistor) put matters right. **M.P.**

A Delivery of Toshiba VCRs

Another delivery of Toshiba VCRs came in recently. Most were up to specification, but two failed our stringent testing procedure. The first one had a buzz on audio: it could be heard during recording and was in fact being recorded on the tape. There was no buzz when a known good tape was replayed, nor when recording was tried from an external line input. With the scope we traced the buzz back towards the sound demodulator in the .i.f. section,

and eventually discovered that on the rear connector panel the cables lie near the servo output circuits – the buzz was interference being picked up from the power servo stages.

The next problem was worse. Andy had noticed that the machine produced Micky Mouse audio in the cue and review modes, when the audio should be muted. Furthermore the audio was at a very low level when the machine was in the record mode. Again we checked around with the scope, and found that two record muting transistors were being turned on by a small voltage which came from the Play-12V line. It took some time to check around this supply line, but I eventually traced the cause of the trouble to a Sony CX141 i.c. on the servo panel. The Play-12V supply switches one of its inputs, and the relevant output was at 3V when it should have been at 0V. **S.B.**

Service Notebook

George Wilding

"One Channel" Faults

Two sets came to our attention recently with faults on one channel only. The first was an ITT hybrid monochrome set (VC200 chassis) with the complaint that the sound on BBC-2 had got progressively more distorted, though the quality on the other channels was excellent. Slight readjustment of the cores in the sound discriminator transformer cured that, and whilst their positions were found to be fairly critical on BBC-2 the conditions on BBC-1 and ITV were normal.

The second receiver was a Pye hybrid colour set which had a marked ripple on the BBC-1 picture, suggesting inadequate smoothing of the supply to the line oscillator. The BBC-2 and ITV pictures were quite free from the effect however. The set was being used with a mains-powered aerial amplifier, and on switching this off the ripple immediately disappeared while the contrast fell as the amplifier transistors used up the supply from the reservoir capacitor. As it happened we didn't need to service the amplifier's power supply – a local relay had come into operation since the original installation of the set and its aerial. Greatly improved results were obtained by removing the amplifier, repositioning the aerial and retuning the set.

We often come across sets being operated with an aerial amplifier in order to pick up the signal from a distant transmitter, the owners being unaware that local transmitters have since come into operation. If the local channel frequencies are not too far from those of the distant transmitter you may be able to use the same aerial, but where the transmitters operate at the other ends of the bands, as in my area, a new aerial is a must. Sometimes an owner will simply retune to the new transmitter without bothering about the aerial, not even changing its direction. The result is usually some ringing and evidence of mismatching, and there can be a wide disparity in the signal strengths obtained on the three local channels. It's quite astonishing the poor picture standards that some people will accept, especially when the impairment has been gradual.

Decca 30 Series

Lack of width was the problem with a Decca hybrid colour set (30 series chassis) – the picture was about an inch short on both sides. Pushing the slider of the width control to one

extreme produced a big improvement, but there was still a slight gap at each side, while normally these sets produce full width with the slider of the width control midway. New valves failed to make any significant improvement, so the resistors in the width circuit came under suspicion. All relevant resistors were found to be within their tolerance limits however. Fortunately we'd another 30 series set in the workshop, so before delving into other possibilities we swapped over the timebase panels. The problem remained, so obviously the fault was due to something not on the panel – the possibilities were low h.t., the line output transformer or one of the capacitors mounted on it, or the tripler.

The h.t. was right up to the mark, but the 8kV fifth harmonic tuning capacitor C435 was somewhat blackened. As a quick first move, this was replaced. No improvement! The tripler wasn't running warm as far as it was possible to judge, but since changing the line output transformer is such a time consuming job on these Decca sets another tripler was tried. Needless to say after all this the transformer turned out to be the culprit. This was unusual however: usually, when the line output transformer in a colour set breaks down the symptoms are much more decisive.

In another of these sets the h.t. fuse had blown. The first step to take is to check for a short by connecting the meter on a medium resistance range between the PL509 line output valve's top cap (anode) and chassis. A "short" reading here usually indicates that the boost capacitor C436 has succumbed. Another possibility is a heater-cathode short in the PY500 boost diode – disconnecting its top cap (cathode) will isolate that. These items proved to be o.k. however, the short remaining. On inspection the harmonic tuning capacitor C435 was found to be blackened at one point on its edge, where an arc had jumped across to the earthed core of the line output transformer. Replacing this capacitor and the fuse restored normal operation.

Loss of Colour – ITT Hybrids

Loss of colour with ITT hybrid sets can be difficult to deal with since many stages, scattered all over a very large printed panel, are involved. The first thing to do is to check the voltage across the colour-killer reservoir capacitor C162 (4.7 μ F): it should be 0.1V on monochrome, rising to about 7.8V on colour. If the voltage is absent, you can override the colour-killer by connecting a 12k Ω resistor from the positive side of C162 to the 20V rail. Since C162 is normally charged from the PAL switch bistable, the resultant colour will suffer from blinds. Nevertheless this action will prove whether the chrominance signal path is intact and whether the reference oscillator is working.

I find it quicker however to start by checking the voltage across C218 (also 4.7 μ F). This voltage is provided by rectifier diode D37 when the 7.8kHz ident stage is working. The voltage at this point on monochrome is 4.7V, rising to about 11V on colour. In most cases of no colour you'll find that the voltage is low, due to failure of the ident stage, the burst gate/amplifier stage, the reference oscillator or one of the first two chroma stages. Voltage checks will then indicate where the fault lies.

In a recent case we found that there was no voltage at the emitter of the second chroma amplifier transistor T28 (BF241) instead of the scheduled 1.8V. A check on the transistor revealed that its base-emitter junction was open-circuit, a replacement restoring normal colour.

Loss of colour on these sets is usually due to a faulty transistor in the decoder. It can also occur should the output from the ident stage be inadequate, due to drift or misalignment of its output coil L75.

Video Review: Toshiba V8600 VCR

Steve Beeching, T.Eng. (C.E.I.)

It came to pass that we were delivered of some Toshiba V8600 VCRs – the new ones with four video heads to give improved still pictures and slow-speed playback. The styling is sleek and compact (see photo), with a slope on the push-button assembly. It's smaller than its predecessor, except in depth, and is slightly heavier – by a couple of pounds.

The controls along the front are standard – eject, rewind, stop, fast forward, pause, audio dub, record, review, play and cue. The tuner and timer controls are hidden away under flaps on the top of the machine. The tuning assembly consists of potentiometers instead of digital storage, though the latter was not a source of agitation: an a.f.c. on/off switch is also provided for preset tuning. Timer setting has now turned to microprocessor techniques, and is similar to that used on the JVC HR7700 machine. There are three time slots over seven days – these are called programme memories 1-3. Two buttons only set the timer: the “enter” button allows you to select any portion of the programme (indicated by the digits flashing), the “set” button enabling you to set the selected digits to the required value. Setting up progresses from selecting the day and start times, then the recording length in minutes, tens of minutes and hours. Finally the channel is set and the programme ends. The programme must be finished by entering “end” or it won't memorise. Programmes can be set to record every day of a week: programme 3 will record during the first week and then if left will repeat in the second week. If two programme times overlap the second one will be cancelled.

There's a noise reduction system: BNR (Beta Noise Reduction system, what else?). This is switched in and out on the front. A tape recorded without noise reduction and then played back with it will lose treble.

Useful and on the front are the tracking control, TV/line switch and the remote control socket. The least useful features on the front are the video and audio input sockets: the complementary outputs are at the rear – not a good point in my opinion. Whilst in a critical vein, the machine has a VTR-TV/VTR switch. In the TV/VTR position there are normal TV and VTR playback outputs. To see the V8600's tuner input however you have to move the switch to the VTR position, when you lose the TV throughput. Why a simple u.h.f. mixer system was not used to make this switch redundant defeats me.


On the good side there's the counter search mode, using the counter to stop the recorder during rewind. In addition to the counter memory there's the PQS (Picture Quick Search) option. When this is “on” the recorder will stop at the beginning of a recording during fast forward or rewind, triggered by a pulse put on the tape whenever the record button is pressed.

The remote control unit has play, cue and review on the top row of buttons, stop in the centre, and slow motion, still and double speed on the bottom row. Also on this unit are a slow motion speed control and a slow motion tracking control (the latter is on the side). Later this year an infra-red remote control system will become available – the present cable connected remote control system comes with the machine as a standard item.


The performance is excellent – Toshiba after all did invent the helical-scan VTR system, a point which doesn't seem to be too well known. Record and audio dub are single touch switches, i.e. you don't have to press play as well: they are inset to prevent accidental operation. The extra facilities provided by the new machine are still frame, fast cue and review, very fast cue and review, and slow motion with variable speed.

Cue or review can be selected in the play mode. When either button is pressed and then released the recorder will work at seven times the normal speed. If the buttons are held down, the recorder operates at 25 times the normal speed. After using other recorders you can very easily be caught out and miss the bit you wanted to stop at, because cue and review lock in at seven times normal speed and you have to press stop or play. So there you are merrily whizzing through at 25 times normal speed and up comes the bit you want: you release the button but the recorder doesn't stop, it just drops to seven times normal speed. Then there's a panic whilst you scramble to find the stop button and then move to cue or review again to get back to the bit you overshot. Don't say I didn't warn you!

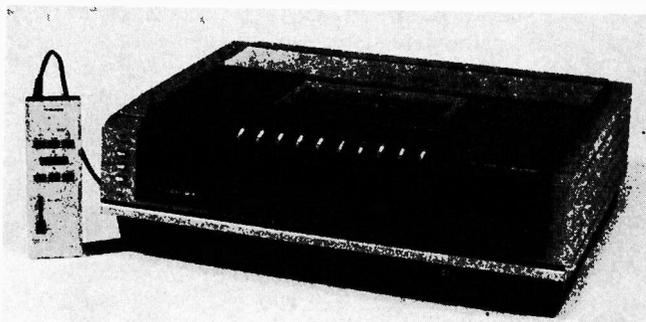Toshiba have gone to a lot of trouble with this machine to produce what must be the best ever slow motion and still pictures with a Betamax machine. The V8600 uses a technique (four heads) that some reviewers will doubtless say is new (but remember the Sanyo time-lapse monochrome reel-to-reel machine of about 1975), just like they said that the wobbling heads used with the



The Toshiba V8600 VCR.

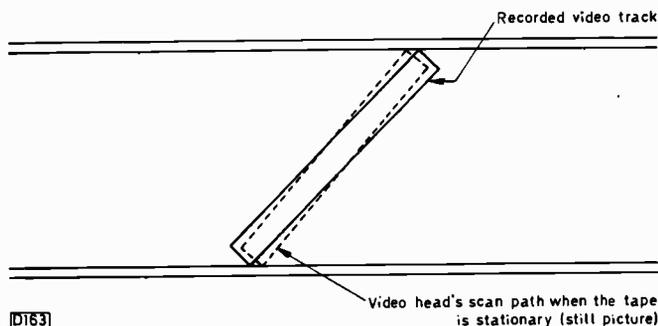

DT63

Fig. 1: The still picture problem with a VCR. Normally the tape and the heads move. If the tape is stopped to get a still picture, the heads will no longer scan the tracks correctly. Toshiba solve the problem by using separate, wider heads for stills and slow motion. The heads both scan the B head tracks, avoiding the picture jitter that occurs when a still is formed from an A and a B head track.

Philips/Grundig V2000 system were new (Ampex were using the technique back in 1972). The technique is to use two extra video heads to ensure that the recorded track is fully replayed without bits missing – this is what causes the

noise band in so many machines (see Fig. 1). The four heads are mounted around the drum at the 90° points.

The two extra heads are referred to as B1 and B2 (they both replay the B head's tracks) and are thicker than the normal (A and B) heads: or, put another way, they are wider than the recorded tracks. The extra width allows the heads to maintain contact with the recorded track in replay throughout the length of the track so that there are no noise bars. The fact that the heads are B track heads eliminates the field jitter that's so obvious on fast-moving scenes with other systems. Vertical resolution is reduced because you see only one 312-line field. So what? the still pictures and slow motion are excellent – surpassed only by Grundig's V2000 still frames with jitter.

Top Machines

To sum up, the V8600 is a good machine. Nothing in this world is perfect, but at around £600 the V8600 certainly represents good value for money and, in my book, places it in the top three. What are these? The JVC HR7700, the Grundig 2 × 4 Super and the Toshiba VR8600: each machine is without much doubt tops in its particular system (VHS, V2000 and Beta respectively). ■

New Tuner for DX Use

Hugh Cocks

FOR some years now DXers have used varicap tuners to cover the TV bands, both v.h.f. and u.h.f., the ease of operation being much better than with the old turret/rotary mechanical tuners. Unfortunately what all varicap tuners suffer from, more so at u.h.f. than at v.h.f., is cross-modulation/intermodulation affecting the channels adjacent to strong local ones. This makes weak signals on these channels well nigh impossible to see, and the problem will be all the worse when the TV4 service comes into operation. A tuner that solves a great deal of this problem has now appeared on the market however – the ET021 mosfet v.h.f./u.h.f. tuner made by NSF.


Mosfet v.h.f. tuners that cover Bands I and III have been around for many years. Some v.h.f./u.h.f. versions employ a bipolar transistor u.h.f. section that often seems to overload more easily than "all bipolar" tuners! The ET021 covers a very wide range – 41-105MHz, 100-300MHz and 438-870MHz. Virtually every earthbound TV frequency is thus covered, and with slight adjustment it should cover the amateur TV channels (this should be done only by experienced enthusiasts however, as much tighter r.f. coupling is used with mosfets). Physically the ET021 is identical to earlier NSF v.h.f./u.h.f. tuners it will directly replace them.

Tuning across the u.h.f. bands with this new tuner is a delight! Signals that were previously lost in cross-modulation in the group C/D channels appear with ease, even when a bipolar transistor preamplifier is used. The tuner has a lower noise figure than more conventional types, and will produce a weak signal on ch. 59 when this is just not visible using an ELC2000 tuner. There is also a slight increase in v.h.f. sensitivity, which may help to reduce the 27MHz CB interference on Band I for those now plagued by this new problem.

One thing one has to get used to is the exact point in the 100-300MHz coverage where Band III appears – approximately 6-12V tuning potential will cover this band.

A.G.C. action is very smooth compared with all the previous types of tuner I've encountered. Mosfet tuners in general produce less noise on the screen than bipolar transistor tuners, due to their low noise figure: this can be a little off putting at first sight, though one soon gets used to it.

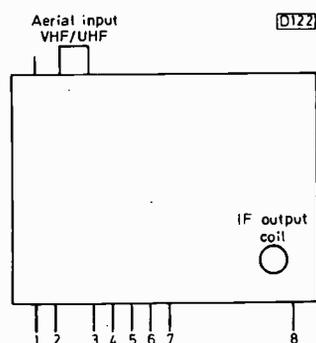Inside, the tuner is a complex beast, containing no less than six transistors – the only bipolar device employed is an AF379 u.h.f. oscillator/mixer. The v.h.f. department has two r.f. amplifier transistors side by side – possibly one for each of the v.h.f. ranges, though no circuit information is available at present.



Pin connections:

- 1 I.F. output
- 2 12V for low v.h.f.
- 3 Tuning voltage
- 4 12V for u.h.f.
- 5 12V supply
- 6 No connection
- 7 12V for high v.h.f.
- 8 A.G.C. About 8V maximum, 3V minimum

Fig. 1: Connections to the ET021 tuner unit.

The image channel rejection at u.h.f. is vastly improved, which helps with the problem of local Group B and C signals appearing at twice the i.f. below their proper tuning point – indeed with a 6mV input from a local Group C channel the image is very weak (some early varicap tuners were very poor in this respect).

The tuner costs a little more than a bipolar type, but the improvement is certainly worthwhile. It's available from Sendz Components at £10 plus VAT and 50p postage. ■

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon from page 45 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

DECCA 30 SERIES CHASSIS

The problem with this set is low e.h.t. with slightly too much width. A known good e.h.t. probe produces a reading of 18kV, and by trying other e.h.t. tapping points on the line output transformer I can't get more than 20kV on a blacked out screen. A new PL509 line output valve has been tried and the width circuit checked, but the problem persists. Otherwise, despite the low e.h.t., the brightness, contrast, focus and colour are good.

These symptoms usually mean that either the line output transformer is faulty or the harmonic tuning of the transformer is incorrect. Ensure that the white flying lead is present on TP402 (pulse feedback to the width circuit), then check that the fifth harmonic tuning capacitor C435 and the damping capacitor C433 (both mounted on the transformer) are present and correct. If so, it's likely that the line output transformer has failed.

THORN 3000 CHASSIS

I've a tricky power supply fault on this set. Several components have been replaced and a thorough check has been carried out for dry-joints, but the following problem remains – 30V supply o.k., but the 60V h.t. appears only about one in five times after switching on, with erratic shifting of the picture after a few minutes. When the set fails to start up, a scope check reveals a correct drive waveform, though of reduced amplitude, at the collector of the chopper driver transistor VT605.

The TRC100P diode W609, in series with the emitter of the chopper transistor, can be responsible for this sort of thing. Replace it with two 1N4002 diodes connected in parallel. If this fails to cure the problem, suspect internal trouble in the chopper driver transformer T602 – but check R616/R650/C636 in the drive circuit first.

ITT CVC5 CHASSIS

There's excessive brightness which cannot be reduced by turning the brightness control to minimum – also the contrast control has little effect.

First check the voltage at the c.r.t.'s grid pins (3, 7, 12). If this is in excess of 32V, check the VDR R409 and D57 – these components are connected between the boost line and chassis (the tint control, which acts on the c.r.t. grids, is fed from the boost line). Next check the first anode voltages. If in excess of 500V, check whether R266 which returns the first anode presets to chassis is open-circuit (it's in the convergence box). Finally, check the c.r.t.'s cathode voltages if necessary. If these are below 120V, check the

brightness clamp diode D17 (BA157), R100 (8.2kΩ) which is in series with it, and the other components in the brightness control network.

THORN 1600 CHASSIS

There seems to be an overload in this set, as the fusible surge limiter resistor in the h.t. supply circuit has opened. The mains fuse is o.k. however, and there are no signs of any overheating anywhere.

First check whether the h.t. rectifier diode W24 (BY127) is short-circuit. If this is o.k., the fault is probably in the line output stage. Check the line output transistor VT16 (BU205), the e.h.t. rectifier stick W35 (by disconnection), and the two rectifier diodes fed from the line output transformer – W34 (BYX70) and W33 (BA159).

GRUNDIG MODEL 6011

There are momentary flashes across the whole screen, sometimes in magenta, sometimes green. There's also a general lack of redness, i.e. the reds tend to be brown/orange, though this occasionally corrects itself after one of the flashes. Do you consider the tube to be suspect?

The tube could be defective, but it's more likely that the fault is in the colour-difference amplifier module: replacing the three BF459G output transistors and cleaning drive controls R573/R583/R593 may well solve the problem. Then set up the grey scale.

THORN 3500 CHASSIS

After about an hour, the screen will blank out and then try to come back again. The brightness control has no effect when this happens, and a vertical bar, about ¼in. wide with movement inside, can be seen on the left-hand side of the screen. The bar is coloured dark green on the left and bluish-brown to the right.

This sort of thing is usually caused by poor connections in the long plug/socket that connects the power supply panel to the wiring harness, or by components on the back of the line timebase panel touching the chassis as a result of the panel not being properly clipped to the frame at the back. Tapping and probing with the fault present should lead to the source of the trouble.

TOSHIBA C400B

The fault is a bright raster with some white lines and no sound. Unfortunately the fault is intermittent, the set often working normally for a week or so. When the fault is present, the 15V supply near the video transistors on the main board is at zero volts: on attempting to carry out tests however the set comes on normally. The problem doesn't appear to be due to a dry-joint, because tapping doesn't affect it.

The fault probably is due to a dry-joint however – one associated with the double-sided print on the main panel. The fact that tapping has no effect is normal with this type of dry-joint on these Toshiba sets. Check the voltage at the 15V supply smoothing choke L404 (to the rear, right of the panel) when the fault is present. If the 15V supply is absent, the fault lies in L404, F401 (loose in holder?), the 15V rectifier D408, its surge limiting resistor R448 or the connection from pin 2 on the main panel to the line output transformer. If 15V is present at L404, check the voltage at both sides of R210, which is near the video transistors. If the voltage is low at both sides, there's a faulty connection

between L404 and R210 – this involves connections through the board and a track across the component side. If 15V is present at one side of R210 but not the other, the third video transistor Q203 is being turned hard on. In this case, check the base voltages of Q201, Q202 and Q203 (should be 3.8V, 4.5V and 2.4V respectively). If Q201's base voltage is incorrect, the problem is probably in the i.f. module. Otherwise, check around the video amplifier stages. It would be best to resolder all joints concerned with the 15V supply before doing anything else however.

GRUNDIG 1500GB

The problem is tuning drift, though the set often works perfectly for two-three hours before acting up. Checks reveal that the voltage at the 33V stabiliser remains rock steady at all times, but the voltage at the junction of the channel selector/tuner unit varies when the fault occurs.

The trouble could be in the channel selector bank, but on this model the tuner is almost always to blame. The cause is usually leakage in the tuning voltage feedthrough capacitor C24 – it can be replaced using a beefy soldering iron.

RANK A816 CHASSIS

There's sound but no e.h.t., with the HT1 supply to the line output stage low at only 75V instead of 170V – the HT2 supply is o.k.

The low HT1 reading indicates that this supply is heavily loaded. The trouble could be caused by short-circuit turns in the line output transformer but is more likely to be due to the e.h.t. stick rectifier 3D13 (TV20 – remove it from circuit to check), one of the two rectifier diodes 3D11/12 fed from the transformer or a faulty BU105-01 line output transistor.

BEOVISION 3400 CHASSIS

The set went faulty whilst in operation. Inspection showed that the fusible resistor 9R13 which feeds the screen grid of one of the two PL509 line output valves had opened. As a check it was resoldered and the set switched on. The result was normal sound but a picture only eight inches (horizontally) by six inches (vertically) – with misconvergence.

This chassis is unusual in having in effect two line output stages, the main one which produces the e.h.t. and half the horizontal deflection power and the auxiliary one which provides the rest of the deflection power. The symptom described is the result of failure of the auxiliary generator. Check the lower 400mA fuse and the lower PL509, PY88 etc. If the PL509 is cold, your fusible resistor might be open-circuit.

ITT CVC8 CHASSIS

The trouble is unlocked colour, sometimes affecting one colour only, though the fault is not discernible on transmitted colour bars. The effect was first noticed after work had been done in the reference oscillator circuit and its control loop to cure an intermittent colour fault – that was traced to a defective reference signal output transistor (T39).

There's little doubt as to where the fault lies, but an oscilloscope is almost essential to check and rectify it. Either the timing of the burst gating pulse is incorrect, or it's misshapen. As a result, the reference oscillator synchronisation is being upset by the presence of the chroma signal at the beginning of each line. The first of the transmitted colour bars is colourless, which is why the fault

doesn't show up on colour bars. Check the burst pulse coupling components C201 (680pF) and R277 (39k Ω) for a start.

THORN 2000 CHASSIS

The trouble is that the first anode supply is way down at only about 370V instead of 900V. All the waveforms in the line timebase up to and including the driver stage are o.k., and I've checked the components in the line output stage as best I can – the flyback tuning capacitors C21/2 have been replaced, also the first anode supply rectifier W5. Unfortunately I've no data on the R1039 output transistors VT4/5 – are there any substitutes?

It could well be that one of the output transistors is defective, though they usually go short-circuit which would show up with simple resistance checks. Thorn transistor types R2008 and R2009 (as used in the 3000 series) work successfully in these positions. The alternative possibility is that something is loading down the line output stage. Apart from W5 and its reservoir capacitor C23 (0.047 μ F), the suspects are the shift choke L5, the shift rectifier diodes W6/7 and the shunt efficiency diode W7. L5 can be checked by disconnecting it and running the set with it out of circuit.

RANK Z718 CHASSIS

There's a no colour fault on this set. The TBA540 reference oscillator i.c. has been replaced twice, on both occasions restoring colour for two-three weeks. The colour would then start coming and going, disappearing completely a few days later. Colour was on one occasion restored by mistuning, but the picture was very grainy and the colour lasted for only a few minutes.

The small electrolytic capacitors can cause misleading symptoms in this type of decoder. We suggest you replace 3C22, 3C24 (both 10 μ F), 3C27 (2.2 μ F) and 3C37 (15 μ F), then set up the decoder as per the manual. If unlocked colour is obtained with the colour killer disabled (link 3LK2 open-circuit) and cannot be set up with 3C35, the 4.43MHz crystal is suspect.

THORN 3500 CHASSIS

The problem is no results, with the 30V line low at approximately 15V. The voltage at the base of the 30V regulator transistor VT601 was also found to be 15V. The transistor and the components in its base circuit are o.k., and if the 30V supply fuse is removed the voltage at the emitter of VT601 rises to 30V. Any ideas?

This puzzling symptom is quite common, and is almost always due to failure of the 30V supply reservoir capacitor C607 (1,000 μ F, 70V) – it's at the input (collector) side of VT601. Replacing this component should restore the 30V line and get the set working normally.

QUERY COUPON

Available until 18th November, 1981. One coupon, plus a £1.00 (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 44.

TELEVISION NOV. 1981

GEC C2110 SERIES

There's a good black and white picture but no colour. The reference oscillator and demodulator/RGB output panels have been tried out in another set and found to be o.k., so the fault appears to be on the chroma/luminance panel. Disconnecting the colour killer link produces no trace of colour however, while replacing the TBA560CQ i.c. and the set burst potentiometer P203 has made no difference.

The electrolytic capacitors associated with the TBA560CQ i.c. sometimes play up – the ones to go for are C216 (4.7 μ F), C217 (10 μ F) and C218 (10 μ F), at pins 14, 13 and 12 respectively. Also check the continuity and jointing of the set burst phase control L206.

RANK A816 CHASSIS

The set went dead after running only very briefly. On inspection I found that the thermal cut-out wire had broken away from one end of the 6.2 Ω h.t. surge limiter resistor 3R119. The link was resoldered, but 3R119 then got very hot whilst smoke came from the line output cage.

If the 6.2 Ω surge limiting resistor is overheating whilst the higher value h.t. smoothing resistors 3R117 (302 Ω) and 3R116 (560 Ω) are not being distressed it's likely that the fault is confined to the power supply. We suggest you replace the h.t. rectifier diode 3D14 and check the h.t. reservoir capacitor 3C69 and rectifier protection capacitor 3C70 for leaks.

TEST CASE

227

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Of the many hybrid colour receiver designs produced in the early and mid-seventies, some are best forgotten about (and have been, except by those who still have to service them!). Others were good designs, the sets well outlasting the nominal seven years that seems to be the expected life of a TV set. Many of them continue to bang on into the eighties – even being offered in showrooms as cheap rentals for the less affluent (like myself!) who can't afford to rent or buy the latest boxes of tricks.

What we are leading up to is a certain Decca colour set, Model 2230, which had been refurbished and repolished and was sitting amongst the shiny new Fergusons and Sonys awaiting a "no deposit, £6.50 a month" customer. At least it boasts a real wood cabinet, something which none of its flashy companions can.

"Red convergence out" said the salesman, proud of his ability to display a little technical knowledge. The service engineer looked at the set with a jaundiced eye – after all, he'd called only to pick up some repairs . . . Summoning a little enthusiasm and a crosshatch generator, he attempted to set up the convergence on the spot – with no success whatsoever. Switching off blue and green, and trying to forget that he was parked on a yellow line, he studied the red crosshatch and found that it was a little indistinct – defocused almost. Curiously, only the verticals were affected, the horizontal lines being quite sharp. "Astigmatism" said the helpful salesman. But careful adjustment of the focus control failed to improve the fuzzy verticals, and the engineer began to suspect that the tube was faulty – he'd known slight heater-cathode leakage to

be the cause of this sort of thing.

To prove the point, he swapped over the red and blue tube cathode leads at the top of the decoder board. The red crosshatch pattern, now coming from the blue output transistor TR215, came up crystal clear, while the output from the red department, now displayed in blue, showed the same fault previously displayed in red – smeary verticals and sharp horizontals. Seeing a traffic warden hovering, the harassed engineer hastily fitted a spare decoder panel he happened to have with him, clearing the fault. He then made his way back to the service department, where the board was left with a colleague who repaired the fault by replacing a single component – this feat was accomplished purely on the basis of the outside engineer's description of the fault! What was the faulty component, and how did it cause this defocusing effect on one axis only? Answer next month, along with another test case item.

ANSWER TO TEST CASE 226

– page 662 last month –

The tale recounted last month concerned a Philips G8 whose line output stage drew excessive h.t. current. There was some uproar in the service department when the suspected line output transformer turned out to be innocent! We left the technician muttering in the corner of the workshop, between trips to the stores for fuses – the line drive, the loading on the transformer's secondary windings, the tripler, the line output transistors and the flyback tuning capacitors had been checked previously.

The technician concerned sets great store on measuring the flyback period as an aid to diagnosis when confronted with an ailing line output stage. In this case he found that the flyback time was way out – in so far as it could be measured. All was revealed when he removed the two line output transistors to measure them for reverse leakage. The insulating washer used in the G8 chassis is a large, rectangular one made of a mica-like material. Under the upper transistor (TR5531) there was a large, irregular burn hole with blackened edges. The washer had been breaking down when the transistor was operational, due to the high peak voltage then present – this was the reason for the crackling noise that emanated from the area.

Bounce? The set's not been back again – as yet!

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £10, Overseas £11 per annum payable to IPC Services, Oakfield House, Perymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Britain's biggest name in used T.V.'s

MTV ARE MOVING TO BIGGER PREMISES

**UP TO 50% OFF
SELECTED TV'S**

To celebrate their move and mark the big occasion MTV are slashing up to 50% off selected TV's. Don't miss this fantastic opportunity!



As from 26th October 1981 Britain's biggest name in quality used T.V.'s are moving to even bigger premises to house their huge stocks and cope with ever-growing demand from home and abroad.

Your Personal Invitation

Old and new trade customers are invited to our new premises to inspect our huge stocks for themselves on 26th October 1981. Bar and buffet all week.

MAKE A NOTE OF OUR NEW ADDRESS:

Midland TV Trade Services,
Campion Industrial Estate, Franchise Street,
Kidderminster, Worcs.
Tel: (0562) 743735 (4 lines)



TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY Z146 A840 A774 A816 A792 A793 A823 A823b A823av colour	INDESIT 20EGB 24EGB mono
DECCA 1700 2001 2020 2401 MS2000 MS2400 2404 2420 2424 mono CS1730 1733 '30' series BRADFORD colour CS1830 1835 80 100 series colour	KB-ITT VC200 VC205 VC207 CVC5 CVC7 CVC8 CVC9 colour CVC20 CVC30 CVC32 series colour
FERGUSON HMV MARCONIA ULTRA THORN 1590 1591 1592 1593 mono 1600 1615 series mono	PHILIPS 170 series dual std mono G8 series 210 300 series mono G9 series
G.E.C. 2000 to 2064 dual std mono 2047 to 2105 3112 to 3135 DUAL STD hybrid colour SINGLE STD hybrid colour	WALTHAM 125
PRICES INCLUDE P. & P. & 15% VAT COLOUR LOPTS £10.50 RETAIL £9.00 TRADE MONO LOPTS £9.50 RETAIL £8.00 TRADE	WINDINGS RANK BUSH MURPHY Colour hybrid quadrupler type T20a T22 Z719 Z722 Pry & Sec £6.00 Z718 series primary £6.00 Z718 series EHT overwind £7.00 ULTRA THORN 1690 1691 EHT overwind £7.00 PHILIPS G6 EHT (exchange basis only) £7.00 G6 primary £5.00 PYE 691 to 697 EHT overwind £3.00 691 to 697 primary* £4.00

All lopts and windings are new and guaranteed for 6 months.

Open Mon.-Fri. 9 to 5.30 pm

Repair Service Available

**PAPWORTH
TRANSFORMERS**
80 Merton High Street
London SW19 1BE

Barclaycard and
Access welcome



01-540 3955

ARE YOU

USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling **used colour televisions from home** in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial **CASH INCOME** with a starting capital of less than £20. Our new unique publication "**How to Deal Successfully in Used Colour Televisions**" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can **succeed immediately**.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure **certain success**. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail - for both televisions and new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. **Plus FREE on-going advice and FREE regular updating service.**

You can start tomorrow - but you'll need our guide. The latest big illustrated edition is out now, and costs just **£4.95** - a small price to pay for financial independence!

ORDER TODAY FROM:

GLOBUS INDUSTRIES LTD., UNIT 18, DARLEY ABBEY MILLS, DERBY.

To: Globus Industries Ltd., Unit 18, Darley Abbey Mills, Derby.
Please send by return post "How to Deal Successfully in Used Colour Televisions".
I enclose cheque/p.o. for £4.95.

NAME

ADDRESS

TRICOL REBUILT SONY TRINITRON TUBES

Two years guarantee with a four year option.

Hot pumped at 400°C.

Rf bombed at 800°C.

Armoured faceplate replaced (where applicable).

Rebanded for maximum safety.

18"-22"

£57 + VAT

Portable 330AB22 etc.

£46 + VAT

Please add £1.50 per CRT to cover cost of picking up and delivery by Securicor Parcel Service.

Also available: Matsushita Panasonic 470 ESB 22 at Carriage £1.50.

£49 + VAT

The above CRT's are offered on a "Regun of your own suitable glass" basis. Send your CRT securely packaged and clearly labelled with your name, address and telephone Nos via your nearest **SECURICOR PARCEL DEPOT [Carriage Paid by TRICOL]**. Rebuilt CRT's will be invoiced, and then delivered on receipt of payment. We buy Sony Glass.

Send your CRT or Telephone for details to:-

TRICOL,
CUPAR TRADING ESTATE, CUPAR, FIFE KY15 4SX
Tel. Cupar [0334] 55348

(N.B. Glass is breakable, please ensure correct packaging.)

Newnes Technical Books present

Beginner's Guide to VIDEO

by David K Matthewson

- ★ Down-to-earth - non-technical explanation of video
- ★ For owners or would-be owners of video equipment
- ★ The latest in the rapidly growing series of Beginner's Guides

The recent boom in domestic video sales has produced a need for a down-to-earth explanation of the technicalities of video for the layman.

If you own video equipment, or are about to buy it, you will find in these pages clear and easy-to-read explanations of the operation of video cassette recorders, cameras and video discs which will help you understand and get the best from your equipment.

Illustrated Paperback 186 x 123mm 0 408 00577 7 £3.60
200 pages

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH

A Division of Butterworths
ORDER NOW
- from your local bookseller.
Write for full details of all our books or in case of difficulty send cash with order to Patricia Davies, Marketing Manager at the address above.

QUALITY COLOUR TV'S

<p>DECCA BRADFORD 18" 20" 22" 26" ITT CV5 20" 22" 26" £36 EACH WORKING</p>	<p>THORN 3500/8500 ALL SIZES FROM £30 EACH WORKING ECKO 262 110 22" OR 26" £56 EACH WORKING</p>
---	---

Plus off the pile at giveaway prices!

XTELCO TEL RICHARD GOLDSBOROUGH
0274 665670
OR CALL
1043 LEEDS ROAD
THORNBURY BRADFORD
(Link Motorway M606 from M1 M62)

EXPORT ENQUIRIES
TELEX 557323 TRISTO G

APOLLO

HIGH TEMPERATURE PUMPED COLOUR TUBES

Fast Mail Order service to any part G.B. Just phone for a quotation. Delivery Manchester area free. Two year guarantee. Fitting while you wait or in your home £20 extra.

18"	A47 - 342 x 343 x	£37.00
19"	A49 - 120 x / 192 x	£37.00
20"	A51 - 220 x / 110 x	£38.00
22"	A56 - 120 x / 123 x / 140 x	£38.00
25"	A63 - 120 x	£39.00
26"	A66 - 120 x A67 - 120 x / 140 x / 150	£39.00

These tubes replace many Toshiba types.
Callers welcome, please phone first.
061 799 0854 24 hour answering service.
Reg Office:
**43 Clarke Cres, Little Hulton,
Nr. Manchester M28 6XM.**

**NEW
LONDON
BRANCH OPEN**

**1000 colour TV's
MUST
BE CLEARED**

● **THORN ● DECCA ● GRUNDIG**
● **SABA ● TELEFUNKEN etc. etc.**
Special prices to celebrate our new branch opening

REASONABLE OFFERS ACCEPTED FOR BULK PURCHASE!!

● Export enquiries welcome ● Call any branch ● All sets guaranteed complete

CELTEL

**NEW
BRANCH**


WARNERS MILL, SOUTH ST.,
BRAintree, ESSEX. 0376 43685

3A, KEMPS SHIPYARD, QUAYSIDE RD.,
SOUTHAMPTON. 0703 331899

110 SHACKLEWELL ROAD,
LONDON N16

TELEPART

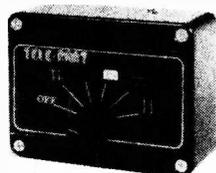13 WORCESTER ST.,
WOLVERHAMPTON,
WV2 4LJ
Tel: (0902) 773122
Telex: 336810



**Telepart
Pattern Generator**

- Exceptionally light and durable
- Pocket size for outside service
- PP3 battery power source
- Five different test patterns for colour and mono TV
- Cross hatch grid
- Dot matrix
- White raster
- Horizontals
- Verticles

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.)

POST & PACKING £1.04



**Telepart
Colour Bar Generator**

- Exceptionally light & durable
- Compact 13x17.5x5.5 cms
- Battery powered for mobility
- Cross hatch grid
- White raster
- Grey scale
- Colour bars
- Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

PRICE £49.95 (Subject to V.A.T.)

POST & PACKING £1.04

Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

PRICE £5.50 (Subject to V.A.T.)

TELEVISION TUBE SHOP LTD

BRAND NEW TUBES AT CUT PRICES

A28-14W.....	£21.95	9AGP4.....	£21.82
A31-19W/20W.....	19.95	190AB4/C4.....	23.00
A31-120W/300W.....	17.95	230ADB4.....	28.50
A31-410W/510W.....	17.95	230DB4/CT468.....	26.60
A34-100W/510W.....	18.50	CT507 equiv.....	21.95
A38-160W/170W.....	17.50	CT512.....	27.50
A44-120W/R.....	27.00	310DGB4/DMB4.....	23.00
A50-120W/R.....	17.95	310EUB4.....	19.95
A59-23W/R.....	21.50	310EYB4.....	18.75
A61-120W/R.....	19.95	310FXB4.....	17.50

**Some Rebuilt Japanese
& European Types
Available from
£14.00 + VAT £2.10**


COLOUR TUBES (NEW & MULLARD/THORN COLOREX)*			
12VARP22.....	£62.50	A56-120X.....	£54.00
330AB22.....	73.50	A63-120X.....	69.50
A44-271X.....	60.00	A66-120X.....	65.00
A47-342X.....	63.00	A66-140X/410X.....	70.50
A47-343X.....	63.00	A67-120X.....	65.00
A49-191X.....	53.00	A67-140X/200X.....	69.50
A51-161X.....	67.00	A67-150X.....	75.00
A51-220X.....	64.00		

Old Bulb Required for Colourex

ADD 15% VAT TO ALL THE ABOVE PRICES.

ALL TUBES TESTED BEFORE SALE & FULLY GUARANTEED
52 BATTERSEA BRIDGE RD., LONDON, SW11.
Tel. 228 6859/223 5088 CARRIAGE: Mono £3, Colour £10

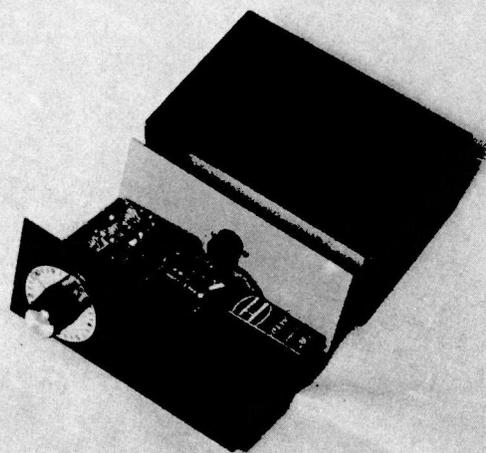IDEAL FOR FEEDING INTO YOUR HI FI TELEVISION SOUND



TV Sound Tuner Kit
£9.50 plus VAT plus 50 pence P.&P.

SENDZ COMPONENTS

63 Bishopsteignton,
Shoeburyness, Essex SS3 8AF.

COLOUR BAR GENERATOR UHF AERIAL INPUT PATTERN GENERATOR

- ★ GREY SCALE
- ★ WHITE
- ★ HORIZONTALS



- ★ VERTICALS
- ★ DOT MATRIX
- ★ CROSS HATCH

★ ADD ON PAL COLOUR BARS ★

Send SAE for full specifications.
Batteries not included.

PG6RF Kit	£28.75	Built	£37.95	ACCESS
C6 Kit	£20.75	Built	£29.90	ORDERS
CPG6RF Kit	£48.30	Built	£72.45	ACCEPTED



Price includes P&P and 15% VAT.
VHF versions available.
Full 12 month guarantee on built units.

MAIL ORDER ONLY FROM

TECHNALOGICS LTD. (Dept TV),
394 SCOTLAND ROAD,
TAYLOR STREET INDUSTRIAL ESTATE,
LIVERPOOL, 5.
051 207 3799

WITWORTH TRANSFORMERS

TV LINE OUTPUT TRANSFORMERS

*BUY DIRECT FROM THE MANUFACTURERS
OF THE LARGEST RANGE*

OF LOPT'S IN THE COUNTRY:

**150 DIFFERENT TYPES IN STOCK
TOP QUALITY. COMPETITIVE PRICES**

All items new and guaranteed.

**Contact your nearest depot for service by return.
Callers welcome. Please phone before calling.
PHONE, OR S.A.E. WITH YOUR REQUIREMENTS.**

Tidman Mail Order Ltd.,
236 Sandycombe Road,
Richmond, Surrey.
Approx 1 mile from Kew Bridge.
Phone: 01-948 3702

Mon-Fri am to 12.30 pm.
1.30 to 4.30 pm.
Sat 10 am to 12 pm.

Hamond Components
(Midland) Ltd.,
416, Moseley Road,
Birmingham B12 9AX.
Phone: 021-440 6144.

Mon-Fri 9 am to 1 pm.
2 pm to 5.30 pm.

FAST RETURN OF POST SERVICE

CARDIFF CENTREVISION

EX RENTAL T/V's

*In stock now. Philips G8 Thorn 3500

Philips K9 26" 110° VCR Position from **45.00**
Capacity to supply 300 working sets weekly.
Large range of spares. Call and see our 4000
sq. ft. warehouse, you won't be disappointed.

Over 1,000 sets in stock

Unit 2 corner of Penarth Road and Hatfield Road.
Tel. Cardiff 0222 44754

MAIL ORDER ADVERTISING

British Code of Advertising Practice
Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme
If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

(1) You have not received the goods or had your money returned; and
(2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded."

WMTV LTD. - THE TV PROFESSIONALS

With Discount TV's

- ★ Britains most reliable source of Quality T.V.'s.
- ★ Hundreds of working polished T.V.'s.
- ★ Full customer testing facilities.
- ★ Thousands of untested S/S Colour T.V.'s from **£10.**
- ★ Quantity deliveries arranged anywhere in Britain or the World.

MAIL ORDER TV's - Fully Tested

- ★ BRC 22"/26" **£70**
- ★ BRC 8000 17" **£65**
- ★ BUSH 184 22" **£40**
- ★ BUSH A823 22"/26" **£60**

Above MAIL ORDER prices include V.A.T. but please add **£12 p & p/T.V.Set.**

- ★ New T.V.Stands.
- ★ Fully adjustable.
- ★ **£6.25** plus **£1.75 p & p.**
- ★ Quantity discounts.
- ★ Price inc. V.A.T.



With Express Spares Service

★ Ex-equipment Panels

ALL PRICES INCLUDE VAT

	Con	Power	Line	Decoder	Video	IF	Frame	Tripler	LOPTX
RBM 823	7.00	6.00	14.00	14.00	—	6.00	9.00	3.00	3.00
BRC 3000	6.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
BRC 3500	9.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
GEC 2100	6.00	—	—	8.00	8.00	6.00	10.00	5.00	5.00
PYE 205	6.00	—	12.00	8.00	7.00	6.00	5.00	5.00	7.00

Postage & packing **£1.25** Panels **50p** Triplers

Ex-Equipment Valves

Untested

ECC82	10
PCF80	10
PCF802	9
PCL82	10
PCL84	10
PCL85/805	9
PCL86	10
PFL200	10
PL36	10
PL504	18
PL508	30
PL509	30
PL519	40
PL802	—
PY500	20
PY800/81	10
PY801/88	10
30FL1/2	20

- ★ p & p paid but minimum order of **£3.00** please.
- ★ Deduct 10% discount on orders over **£20.00.**

Ex-Equipment Colour Tubes

All fully tested

17" (A44-271X)	£18.00
18" (A47-342X)	£18.00
18" (A47-343X)	£18.00
19" (A49-191X)	£18.00
20" (A51-120X)	£25.00
22" (A56-120X)	£17.00
25" (A63-200X)	£10.00
26" (A66-120X)	£20.00
26" (A67-120X)	£17.00

Please add **£5.00 p & p** per C.R.T.

Equipment Spares

*Always available

- ★ Colour and Mono Scan Coils **£1.50 + £1.00 p & p.**
- ★ Tuners for all makes of Colour and Mono **£4.00 + £1.00 p & p.**
- ★ Mono Tubes fully tested. Callers only **£3.00.**
- ★ Reconditioned 50p meters **£92.00/Box of 10** incl. p & p.
- ★ PLESSEY SL918 colour ICs with ● circuit for substitution of SL917 **£2.00 + 25p p & p.**
- ★ NEW VHF/UHF Varicap Tuners with circuit and full data **£1.25 + 75p p & p.**

WMTV LTD. 92 HIGH STREET, KINGS HEATH, BIRMINGHAM B14 7JZ TEL: 021-444 6464/2575

REBUILT CATHODE RAY TUBES IN

C.R.T. SERVICES LTD.

274 Chepstow Road, Newport, Gwent.

Tel. Newport (0633) 272005.

Also available from the following stockists:

L. R. Jones,
Manorbier,
Nr. Tenby.
Tel. 083-482 630

G.R.T.
Talwrn-y-Bont,
Pontrhydfendigaid,
Nr. Aberystwyth.
Tel. 09745 629.

THE NO. 1 SOURCE IN THE SOUTH

Colour From **£15**
Mono From **£2**

BULK DISCOUNTS, DELIVERY ARRANGED.

1000's OF SETS TO CHOOSE FROM

TELETRADERS

ST. LEONARDS WAREHOUSE
ST. LEONARDS ROAD, NEWTON ABBOT, DEVON

Telephone: (0626) 60154

LIVER QUALITY COLOUR TUBES | MULLARD COLOUREX TUBES

A56/120X 22"£30.00 A67/120X 26"£32.00 19" Special Offer..£28.00 A56/120X 22"£36.00
A66/120X 26"£32.00 A51/110 20"£32.00 A51/110 20"£34.00 A66/120X 26"£38.00
2 YEAR GUARANTEE. 4 YEAR OPTION. OLD GLASS RETURNABLE. ALL PRICES PLUS VAT. PERSONAL CALLERS WELCOME

MAIL ORDER:-
For Scotland send to Hamilton address.
For England send to Morley address.

ADD **£6** until old glass is returned in delivery carton (credit by return)
ADD **£6** Delivered anywhere Mainland UK. All plus VAT.




LONDON
Nobel Road.
Eley Estate.
Edmonton,
London N18
North Circular Road
Tel: (01) 807 4090

WEST
Bulward Ind. Estate.
Chepstow,
Nr. Bristol
Junction 22 M4
Tel: Chepstow
(02912) 6652

NORTHERN
Ebenezer Chapel.
Fountain Street,
Morley
Junction 28 M62
Tel: (0532) 532022

SCOTLAND
Peacock Cross
Industrial Estate,
Burnbank Road,
Hamilton
Off M74 motorway
Tel: (0698) 282141

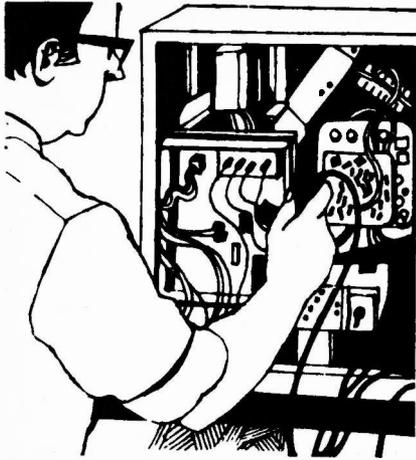WARRINGTON
21 Ravenshurst Court,
Risley Road,
Birchwood,
Warrington
Junction 11 M62
Tel: (0925) 817578



SETS & COMPONENTS

STS

FOR
QUALITY
USED T.V.s

200 EX RENTAL
COLOUR AND MONO TVs
ARRIVING WEEKLY
GOOD CLEAN CABINETS
THIS MONTHS SPECIAL OFFERS

Thorn 3000 25" £17.25

Thorn 3500 26" £23.00

Many other makes £17.25
Good Mono sets from £3.45

ALL SETS COMPLETE WITH
GOOD CABINETS.

DELIVERY IF REQUIRED

Call or phone now to:

SOUTHERN TRADE SERVICES
21 COLINDALE AVE.,
LONDON NW9
TEL 01-200-7337.

EX-EQUIPMENT TELEVISION PANELS, for details and price list please send SAE to: 3, Roseberry Road, Smethwick, Warley, West Midlands.

**PHILIPS N1700 VIDEO
CONVERSION KITS**

5 HOUR DUAL SPEED RECORDINGS,
EASY FIT - SUPERB PICTURE QUALITY.

NEW... ADD ON MODULE WITH FREEZE,
PAUSE, FRAME ADV, SLO-MO & SEARCH.

For details of all our Philips conversions contact

EVANS VIDEO SERVICES
ON 061-439 8696... NOW

SMALL ADS

The prepaid rate for classified advertisements is 29p per word (minimum 12 words), box number 60p extra. Semi-display setting £5.64 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

**NOTICE TO
READERS**

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

**TRADE ONLY
N. W. ELECTRONICS**

Have for disposal large quantities of good class

COLOUR TVs,

Bush, Pye, GEC, Thorn, Hitachi, Philips, etc. (Ex Co-op). Not junk, very clean cabinets.

Genuine change over TVs and repossessions.

From only £20. Delivery arranged.

We export large quantities of TVs weekly, can we help you?

Call now and see our selection, over 1000 TVs to choose from.

N. W. Electronics, Bolingbroke Buildings,

Bolingbroke Street, Bradford 5.

3 Mins from Motorways.

Tel. 0274 390121.

EXCELLENT QUALITY
USED COLOUR TV's
CHOOSE UNTESTED
OR FIRST CLASS
WORKERS ENGINEERED
IN OUR WORKSHOP.

TELFURB T.V. LTD.
WHEATLEY, OXFORD.
08677 3849

CAMPBELL ELECTRONICS LTD.

Distributors of specialist spares to
radio and television service depts.

We stock semiconductors, I/Cs, special
T.V. and audio spares, service aids, rebuilt
CRTs etc.

Fast off the shelf delivery of stock items.

Send S.A.E. or telephone for full catalogue
and price list.

CAMPBELL ELECTRONICS LTD.,

Unit 5, Heath Hill Estate,
Dawley, Telford, Shropshire.
Telephone Telford (0952) 502422.

TV DX

Back in the U.K. Schraders Aerial amplifiers. UHF. RB45/45a masthead, remotely controlled, tunable amp.ch 21-65/17-65. Gain 22-26dB. Noise ratio 3.5dB. Overload 7.5-10mV. Price £33.00.

VHF. RB3 masthead, remotely controlled, tunable amp.ch 5-11. Gain 22-30dB. Noise ratio 2.5dB. Overload 10mV. Price £48.00.

2nd line amp. SBB268-V ch 2-68. Gain 15-12dB with DC bypass. Price £14.50.

UHF ch.amp (state) with 2nd unamplified UHF input. Gain 26dB. Bandwidth 10-15mH. Price £31.00.

UHF ch.amp (state) converted to other ch. with 2nd unamplified UHF input. Gain 26dB. Price £37.50.

Power-supply V12 18v/50mA 2 outp. Price £8.00. Power-tuning supply VR12/01 2 outp. Price £11.50.

Power-tuning supply VR12/6 preset. Price £25.00.

All prices include P&P. Trade enquiries welcome.

Reystronics, 28 Pemberton Road, East Molesey, Surrey. Phone: 01-979 7380.

T.V.s FOR EXPORT

We have a selection of Bush and Ferguson colour T.V.s in good working order.

VHF/UHF suitable for countries using PAL system. We also supply The Home Market.

Write:

Tele Spares Ltd.,
7 Walkinstown Road,
Dublin 12, Ireland.
Tel: Dublin 520485.

When replying to Television Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

TELEVISION

**R
A
D
E**

WE HAVE WAYS OF MAKING YOU BUY. WE ARE GOING TO THUMP YOU WITH BARGAINS, MAKE YOU SQUEAL WITH PAIN AT THE BIG DISCOUNTS, TWIST YOUR ARM WITH LOW PRICES.

NOW YOU'VE HAD ENOUGH, GET YOUR CASH AND A WAGON & COLLECT (OR YOU'LL BE SORRY!).

GENERAL FACTORS

GOOD MOTORWAY ACCESS
EXPORT ENQUIRIES

UNION ST, DONCASTER DN1 3AE
TELEPHONE (0302) 49583-68416

OPEN MON to SAT

THORN 3000/3500. Scrap sets, complete £10. Untested from £29. Working from £39. Ex-equipment spares available. Panels repaired/exchanged. Telephone Peterborough 253480.

QUALITY REBUILT TUBES

HIGH TEMPERATURE PUMPING

COLOUR (2 year Guarantee)

90° up to 19" **£33**
90° 20" - 22" **£35**
90° 25" - 26" **£36**
110° and PIL **£40**

MONO (including thin necks) from **£14.**

All prices + VAT

Delivery UK Mainland £6.

4 year Optional Guarantee

Send or phone for full list and terms.

WELTECH PICTURE TUBES

Unit 3-10 Wembley Commercial Centre,
East Lane, Wembley, Middx.
01-908-1816

Telephone: Northwood (Middx.) 27019 01-845 2036

RETACH LTD.

Rear 78 High St., Northwood, Middx.

NOW OFFER!!!

RANK 823 and THORN COLOUR from £20

ALSO

REBUILT COLOUR TUBES.

2 year Guarantee. From £28

ALL PRICES + VAT.

CAMPBELL ELECTRONICS LTD. COLOUR T.V. PANEL EXCHANGE/ REPAIR SERVICE

THORN, RANK, PHILIPS, GEC,
DECCA, TELPRO, GRUNDIG etc.
90 Day Guarantee on all repairs - same
day postal service.

Telephone Telford (0952) 502422
for catalogue and price list.

CAMPBELL ELECTRONICS LTD.,
Unit 5, Heath Hill Estate,
Dawley, Telford, Shropshire.

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

TRIANGLE TELEVISIONS, Coleraine, N.I. Quality working sets. Clean cabinets, Decca, Bush, Kirting. Phone Coleraine 3600.

EX RANK, BUSH, MURPHY SPARES
New T24 Chassis, A51-570X Tubes,
Isolating Transformers, Panels and
Components.

S.A.E. for Lists
West Devon Electronics,
15 Station Road, Horrabridge,
Yelverton, Devon PL20 7ST.

TURN YOUR SURPLUS capacitors, transistors,
etc., into cash. Contact Coles-Harding & Co., 103
South Brink, Wisbech, Cambs. 0945 4188. Immediate
settlement.

SUFFOLK TUBES LIMITED

214 Purley Way, Croydon, Surrey.
Tel: 01-686 7951/2/3/4

SUPPLIERS OF MONO AND COLOUR TUBES TO MAJOR RENTAL COMPANIES.

ALL COLOUR TUBES HOT PUMPED AT 385c AND REBANDED TO BRITISH STANDARD. 415 1972 CLAUSE 18-2.

19" and 22" TUBES APPROVED. OTHER TYPES PENDING.

BRITAINS LARGEST INDEPENDENT REBUILDER FOR 21 YEARS.

COLOUR T.V.s

PHILIPS G8 COMPLETE

22" £45 26" £55

DISCOUNT FOR
BULK BUYERS

TEL: 965 1230 & 961 3997

SMITH

ELECTRONICS

43-43A, PARK PARADE,
HARLESDEN,
LONDON N.W.10.

Southern Valve Co.,

2nd Floor, 8 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked. SAE Lists, Cash with order. Same Day Postal Despatch. (Mornings Preferred). Not Thurs.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter. NO COD. Speedy Despatch assured. No order under £1.

Philip Bearman, 8 Potters Road, New Barnet, Herts.
Tel: 01-449 1934/5 (1934 Recording Machine).
Closed Thurs. Please phone for opening hours.

T.V. PATTERN GENERATOR

UHF output plugs straight into aerial socket no other connection required.

Features:

- ★ Crosshatch
- ★ White Raster
- ★ Grey Scale
- ★ UHF Output
- ★ Battery Powered
- ★ Pocket sized
- 100 x 75 x 40mm

Built ready for use **£17.75.**
Price includes P&P and VAT.

C. L. JERVIS
15 Mercer Grove,
Wolverhampton, WV11 3AN.
Tel. (0902) 23916.

LOOK!

THORN 3000/3500 & 9000 TRIPLERS

High Quality Silicon Replacement Units
T3500 only **£4.95** inc. P.P. Add 74p V.A.T.
T9000 only **£5.45** inc. P.P. Add 82p V.A.T.
Quotes for 50+ 1 Year Guarantee

WING ELECTRONICS

15, Waylands, off Tudor Road, Hayes End,
Middlesex.

COLOUR TUBES £24

Re-gunned 20", 22". 1 year guarantee.
Ex-equipment JIG tested, 20", 22" £18 each, 2 for
£32. 3 month Guarantee. No need to spend £5
returning old tube.

No V.A.T. £5 del. U.K. mainland.

U. VIEW (TUBES)

29, Warmaworth Road, Doncaster, Yorks. DN4 0RP.
Tel. 855017.

WANTED

RADIO AND T.V. Service Books wanted from 1970/71 to date. Tel. Bradford (0274) 497779 evenings.

EX-RENTAL televisions wanted for export. Must be complete for refurbishing. Terms strictly cash. Phone 0272 775865.

WANTED. Early model transistorised Sony portable television Model No. TV990VB in any condition. Telephone (01) 242 3732.

WANTED. "Thorn 1500" sets working order preferred. Valente, 8, Braeside Avenue, Glasgow G6 26LH. Phone 041-956 4164.

WANTED DEAD OR ALIVE, early type R.F. heater suitable for CRTS. Phone after midday 01-520 2907.

WANTED CONTINUED

NEW VALVES and CRT's required, PCL805, PL504, PL509, PY500A etc. Cash waiting. Bearman, 8 Potters Road, New Barnet, Herts. Tel: 01-449 1934/5.

WANTED B.R.6. 2000 six button tuner, preferably new. Telephone Crowthorne, Berkshire (03446) 2476.

FOR SALE

FOUR COLOUR TELEVISIONS ITT CVC8, THORN 3500, various sizes, all working. £190 ono. Tel. Twyford (0734) 340299.

NEW BACK ISSUES of 'Television' available 95p each post free. Cheque or uncrossed P/O returned if not in stock. - BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

EAGLE K200 FET-VOM Brand New. Boxed small quantity £40 including postage. Tel. 0284 61030.

TVDX EQUIPMENT. System L TV sets for French TV from £45. Vhf/Uhf converter £10.50. BI mosfet preamplifier high gain, low noise. Mains powered £25.95. Band III type £25.50. Tunable masthead Uhf preamplifier plus set side power/tuning unit £35.00. Sae data, lists to: H. Cocks, Cripps Corner, Robertsbridge, Sussex. Tel. 05083-317.

FORGESTONE 400 TUNER/IF Panel and Decoder Panel assembled, not tested for sale. Also manual £35.00. Ruislip 75769.

BUSH 24"/20" S/S MONO'S, good working order clean, polished. £10 each, minimum ten. Delivery anywhere (0706) 623091.

TELEVISION COLOUR RECEIVER PROJECT 1979/80 22 in. G8 cabinet complete working order. offers. Perez, Sandown 405190.

EDUCATIONAL

TELEVISION COMPUTER RADIOCOMMUNICATIONS & RADAR SERVICING

TWO YEAR full-time Modular Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- MICROELECTRONICS & DIGITAL TECHNIQUES
- MICROPROCESSORS & COMPUTERS
- RADIOCOMMUNICATIONS & RADAR

Each of the above Modules are 13 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £1575 per year (i.e. £525 per Module).

Next session starts January 4th.

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept: TT, 20 Penywern Road, London SW5 9SU. Tel: 01-373 8721.

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest Discount catalogue out now. Phone C.W.A.S. Alarm. 0274 682674.

T.V. Repair TOOL KIT

Bigger and better, 48x38x11 cm

Show your customers you have the know how and impress them by using our executive style case. Supplied with case, large cutters, pliers, small cutters, small snipe and round nose pliers, solder pump, tweezers, neon, tester, screwdrivers 6", 4", 2 1/4", crosspoints 6", 2 1/4", nut spinners 0, 2, 4, 6. B.A. large component box. Plenty of spare space. £79.90, post and packing add £2.50. (Minus tools case £35.00)



Money refunded if dissatisfied.

KITONICS,
7 The Meadows, Berwick-Upon-Tweed.

C.E.D., C.R.T., tester reactorvator suitable for most types of colour and mono including P.I.L. and 20AX types, checks emission, detects and measures inter electrode leakage, incorporates a very effective boost facility. Not a kit but a professional instrument £85.10 inc. VAT. 10 day money back assurance. C.E. Developments, 54, Baronsmead Road, High Wycombe, Bucks HP12 3PG. Tel. High Wycombe 30307.

RIGONDA AGENTS. For all spares and repairs. Fast despatch trade service available. 01-476 1298. Star Radio, 272 Barking Road, London E13.

PRE-PACKED. Screws, nuts, washers, solder tags studding. Send for price list. A1 Sales (TV), P.O. Box 402, London SW6 6LU.

ASSORTMENT OF OBSOLETE and secondhand TV valves. Send requirements. Average price 50p + postage. A Stark & Son, 43 Thicketford Road, Bolton. 26684.

SUCCESSFUL PATTERN GENERATOR, rights available. Trade enquiries Box 164.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME.....

ADDRESS.....

Send to: Classified Advertisement Manager,
TELEVISION,
Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846.
Rate
29p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

SERVICE SHEETS

Thousands of different full size service sheets (Many of above are unique to us and obtainable nowhere else.)
 Thousands of different manuals of all kinds in stock.
 Updated collection of British colour TV circuits/layouts etc. Contained in 3 huge binders - special price £39.50.
 Revised foreign C.T.V. Repair System in 2 huge binders plus 3 Repair Manuals for £39.50.
 (Foreign C.T.V. Repair Manual No. 3 - £6.)

Contains chassis from Grundig, Hitachi, Korting, Kuba, Luxor, Mitsubishi, National P, Nordmande, Sharp, Skantic, Toshiba, Zanussi.
 Complete set of 11 unique TV repair manuals - only £55. Mono + colour from dual standards to latest models, McCourt & Tunbridge.
 S.A.E. any quotation, also price lists, newsletter, bargain offers, details of our unique TV repair system. £1 + large S.A.E. any single service sheet.
 Phone: 0698 883334, anytime. Callers 4-6 pm. weekdays, Saturday from 10 am.

G.T. TECHNICAL INFORMATION SERVICE
 76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.

30,000 SERVICE SHEETS IN STOCK COLOUR-MANUALS ALSO AVAILABLE

TV Monos, Radios, £1.25. Tuners £1.25. Tape Recorders, Record Players, Transistors and Stereograms + S.A.E. from £1.25 each except Colour TV Circuits £2. Car Radios £2.00 + SAE. All Radiograms FROM £1.25.

State if Circuit will do, if sheets are not in stock. All TV Sheets are full length 24 x 12, not in Bits & Pieces. All other Data full lengths.
 Free Fault Finding Chart or TV Catalogue with order. Crossed PO's Returned if Sheets Not in Stock.

£2 Old Valve Radios.

C. CARANNA, 77 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882.

MAIL ORDER
 SAE.

SERVICE SHEETS, Radio, TV, etc., 10,000 models.
 Catalogue 25p plus SAE with orders-enquiries.
 Telray, 5 Henderson Street, Preston PR1 7XP.

SERVICE SHEETS, Radio, Television, Stereo etc.,
 from 50p. Catalogue 25p. S.A.E. with orders, en-
 quiries. Hamiltons, 47 Bohemia Road, St. Leonards,
 Sussex.

BOOKS & PUBLICATIONS

OUT OF PRINT BOOK SERVICE, 17, Fairwater
 Grove (E), Cardiff. Send S.A.E. for details.

ANY SINGLE SERVICES SHEET £1. L.S.A.E.
 Thousands different repair/service manuals/sheets in
 stock. Repair data your named TV £6 (with circuits
 £8). S.A.E. Newsletter, price lists, quotations. AUS
 (T), 76 Church Street, Larkhall, Lanarkshire.
 (0698 883334).

COURSES

BE A COLOUR TV ENGINEER

Two years full time Higher Diploma
 Course in Electronics, Colour TV and
 V.C.R.

Next course commences Sept 81
 and Jan 82.

APPLY:

Registrar, Reeswood College,
 299a Edgware Road,
 London W2 1BB.
 Tel. 01-402 9985.

SANDHURST PUBLICATIONS

Television Service Sheet Specialists

Workshop Manuals, large selection Japanese TV
 Sheets. Callers 5.30-6.30 pm. S.a.e. for catalogue
 and enquiries:

49C Yorktown Road,
 Sandhurst, Camberley, Surrey GU17 7AG.

VETERAN & VINTAGE

"SOUNDS VINTAGE"

The only magazine for all vintage sound
 enthusiasts packed with articles by top
 writers covering gramophones, phono-
 graphs, 78s, wireless, news, history
 reviews, etc.

All back numbers to No. 1 available. Send
 75p for sample copy.

28 Chestwood Close, Billericay, Essex

ADVERTISERS PLEASE NOTE

Our Box Number
 Service is **NOT**
 available for Mail-
 Order Advertising

N.G.T. COLOUR TUBES

First Independent Rebuilder with

B.S.I. CERTIFICATION

(Certificate No. 004)

2 year guarantee: 4 year option

All Colour Tubes are debanded, high temperature pumped
 and rebanded using new adhesives and new tension band.

19" £30, 20" £32, 22" £33, and 26" £38.

Exchange prices: add VAT at 15%

N.G.T. ELECTRONICS LTD.,

120, SELHURST ROAD, LONDON S.E.25

Phone: 01-771 3535.

20 years experience in television tube rebuilding.

EMO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
 ETC., ETC. ● ALL SPARES READILY AVAILABLE ●
IMMEDIATE CREDIT AVAILABLE—TRADE ONLY

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX -
 EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc., etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
 TV COMPONENT BY RETURN
 IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

S.A.E. FOR FREE WALL CHART

TELE-PART (WTON) THE TELECENTRE, WORCESTER ST.,
 WOLVERHAMPTON (0902) 773122



**SHIELDWAY
 LIMITED**
 Quality rebuilt
 Cathode Ray tubes

TYPE	PRICE
A44-271X	£36-00
A47-342/343X	£36-00
A49-191X	£36-00
A51-110X	£37-00
A56-120X/140X	£37-00
A63-120X	£37-00
A66-120X/A67-120X	£38-00

- All prices are inclusive of VAT. ●
- All tubes guaranteed 2 years ●
- Many inline types available ●

U.K. Mail Order telephone for quotation.
 Delivery service available within a 20 mile
 radius of Bolton

**SWAN LANE MILL
 HIGHER SWAN LANE
 BOLTON BL3 3BJ.
 TEL: 0204 64746**

p- (ii) triple £6 1/2
p 2- LOPT £10

DISPLAY ELECTRONICS

**LEADERS
IN TUBE
TECHNOLOGY
SINCE THE 60's.**

**REGUNNED
COLOUR TUBES
2 YEAR GUARANTEE**

Up to 19".....	£29.50
20".....	£31.50
22".....	£33.50
25".....	£35.50
26".....	£37.50

The above prices are for standard 38mm Delta Gun Types. Prices on application for P.I.L. Tubes etc. Some types available without pre-supply of glass at extra cost.

**REGUNNED
MONO TUBES
2 YEAR GUARANTEE**

20".....	£11.00
24".....	£13.00

BUDGET CORNER

Buy any 5 mixed types Cash 'n Collect - Take 20% discount.

OR

Buy any 5 Mono mixed sizes Cash 'n Collect at **£8.50** (20") and **£10** (24").

PLEASE ADD 15% VAT.

CALLERS WELCOME

Late night Thursdays until 8pm
Saturdays until midday.

N.B. Customers intending to collect orders are requested to telephone in advance:— even popular types may be out of stock for short periods.

V.D.U./RADAR TUBES

Home and export enquiries for Radar Display Tubes manufactured from new (with phosphors to specification) are invited.

**WATERLOO ROAD,
UXBRIDGE,
MIDDLESEX**

Telephone: Uxbridge 55800

p 5- £5 1/2 *p 6- £5 1/2*
p 5- ring of price *p 6- £8*

STANDARD T.V. TUBE

**HIGH QUALITY COLOUR
REPLACEMENT TUBES AT
COMPETITIVE PRICES.**

- ★ Complete New Gun fitted to every Tube.
- ★ Two year Guarantee
- ★ Every Tube Electrically Tested.
- ★ Every Tube Picture Tested.
- ★ Supplier to Major Rental Companies.

18", 19"	£25
20", 22"	£27
25", 26"	£29

All prices quoted assume the return of your old glass rebuildable condition. Old CRT cash/cheque with order. Please add VAT at 15%.

**S.STANDARD TV TUBE CO.
11-29, Fashion Street,
London E1**

Tel. 01-247 3097

It's easy to complain about advertisements.

Every week, millions of advertisements appear in the press, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice and are legal, decent, honest and truthful.

But if you find one that, in your opinion, is wrong in some way, please write to us at the address below.

We'd like you to help us keep advertising up to standard.

**The Advertising
Standards Authority.** ✓

A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

p 50 - ring | service sheets p 55
p 47 - £10 | p 55 - ring | 100 staples

"TUBE REPLACEMENTS" PROUDLY OFFER

"WELLVIEW" EXCHANGE COLOUR

A44-271X	£29
A47-342X	£29
A47-343X	£31
A49-120X	£29
A51-110X	£29
A51-110LF	£31
A55-14X	£33
A56-120X	£33
A63-120X	£38.50
A66-120X	£38.50
A66-140X	£38.50
A67-120X	£38.50
A67-150X	£38.50

"WELLVIEW" EXCHANGE MONO

A44-120 WR	£11
A47-26 WR	£12
A50-120 WR	£11
A59-120 WR	£12.50
A61-120 WR	£13.50
A31-300 NEW	£15
A34-100-510 NEW	£16

All above plus VAT @ 15%.
Carriage £4.50 inc. VAT.

**ALL TUBES 18 MONTHS
GUARANTEE**

ALSO YOUR VALVE SUPPLIER NEW AND BOXED (inclusive of VAT)

DY802=74p	ECC81=64p	EF183=78p
EF184=64p	ECC82=64p	PCF802=98p
PCL82=78p	PCL84=92p	PCL805=97p
PFL200=£1.15	PCL86=97p	PL504=£1.38
PL509=£2.82	PL508=£1.30	PY88=70p
PY800=70p	PL509-19=£2.92	PY500A=£1.52

Postage and Packing 10p per valve. All orders over £10 Free of charge.

Colour Sets

1000 ex-rental TVs
Good sets good prices
Sets from £10 only
Bush, Pye, GEC,
Grundig, ASA, BRC,
Philips, Skantic
The prices will amaze
you.

TUBE REPLACEMENTS
Unit No. 1, Monmouth St.,
Bridgwater, Somerset.
Tel. 0278 425690-722816

Empire #32 ↓

EHT lead for split diode LOPT. £1.00	GEC 8 ohm. 70p GEC 15 ohm. 70p	NEW SONY KV.1400. Chroma Panel cost £60.00 Tuner unit £3.50 Touch button unit with I.C. £3.50
6 push button unit UHF. For Pye £7.00	NE 2B6H 2 small neon lamps used in GEC. 4p	FRONT END FOR MUSIC CENTRE VHF/MW/LW size 13x3 1/2". 4 push button unit, 7 transistors, V/condenser, 10 coils rod aerial I/C decoder CA 758E (no power supply and output stage). Circuit supplied. £6.00 Output stage for music centre. £6.00
CVC 9 ITT Control panel. £4.00	Red and Green LED, 14 mixed. £1.00	
CVC 20 ITT 6 push button unit & Input panel. £5.00	TLR 102 small red LED. 5p 20 small red LED. £1.00	Mains on/off rotary. 13p Mains on/off push. 20p D/P push button on/off. 10p ITT mains on/off push button switches. 25p
Philips TV IF Modules 38 Mc/s 1st and 2nd IF. each £1.50	MAINS DROPPERS Thorn 50R-40R-1K5 50p Thorn 6+1+100r. 35p Pye 6r-161. 40p Pye 147+260r. 40p (731) 3+56+27r. 50p	TS25-11TBW fits Autovox, Saba, Bang Olufson, Grundig, Tanberg. £3.75
3500 6 push button unit for Thorn 3500. Varicap £1.00	CERAMIC FILTERS 5.5 MHz. 15p 6 MHz. 25p	Chroma Panel ITT. CVC 20.25.30.35.40. New £10
6 position 12.5KV Resistor Unit for varicap. 50p	3.5mm Jack socket. 7p	Grundig 3000/3010, Seimens TVK 52. £3.00
I.T.T. (CVC 5) 7 push button unit for V/cap tuning £7.00	NPN/PNP 60v 5 amp/80w, pair. 660-661. 20p	ITT LP 1174/NC. £3.00
New portable T/V chassis. Mono £10.00	6 way ribbon cable, per metre. 20p	MULTI CAPACITORS 1000 + 2000/35v. 25p 2000 + 2000/35v. 30p 2500 + 2500/63v. 50p 150 + 200 + 200/300v. 70p 100 + 200/325v. 40p ELC 1043 on panel for 400 + 200 + 200M 350v £2.00 600/250v 60p
New I.F. panel T/V 3 I.C. TBA750 & SC950 MSC950 £3.00	TV XTALS 4.433; 610 KHz. 50p	175 + 100 + 100/350v to fit 3500 Thorn. £2.00
ELC 2000M New. £7.00	6 volt 23 watt soldering iron. £2.00	For T/V Sony Transformer & Lead & Sockets for earpiece. 8 ohms. £1.00
ELC 2060 New £7.00	Infra-red emitting diode, TIL30. 20p	THORN SPEAKERS 1500 5 1/2 x 2 1/2 3R 3500 7 x 3 80R 3500 5 x 3 80R 9000 7 x 3 16R 5 x 3 loudspeaker for GEC 15 £1.00
V/U Meter 50p	750 MFD 50V. 10p	25 ohm 6x4 G11 Philips £1.00
GEC VHF/UHF 8CH touch tune units 41C 1xSN 29862N+1xSN 16861NG+2xCBF 16848N. £5.00	THERMISTORS 200+200+75+25 4 fuse holder +2BY133+resistors. I.T.T. panel. CVC 9. £1.50	UHF Modulator, CCIR. £3.00
New circuit supplied. CVC panel with pots and main switches 250K, 100K, 423 500K. £1.00	ITT PT266 3W12 (Thermistor degaussing) fits most sets. 15p PTH451A or B. 20p PT 37P. Fit Pye, Bush etc. 25p	Circuit supplied. Flush mounting socket. FM/TV 35p
New (NSF/AEG) UHF/VHF Varicap tuner units. Cost £10. only £4.00	H.T. thermistor neg. VA1104 35p	ELC 1042. Mullard. £6.00 ELC 1043/05. Mullard. £6.00
Convergence panel for GEC 2040, 11 pots, 5 coils, 2 resistors etc. New. £1.50	GEC 4700M/25v. 15p	Moss Fits VHF/UHF D.X.T./Unit N.S.F. £10.00
PYE 731 6 push button unit and 100KA pots. £3.00	1000M/63v ITT axle. 15p	Power supply 30V 1 amp Reg. £2.00
New circuit supplied with UHF 8ch Light action unit 4 i/c for Varicap tuning GEC C2001/C2201. £5.00	22M/375v ITT. 20p	Small DX Tuner V/cap 48-88 MHz and 175-220MHz automatic changeover. £5.00
GTE SYLVANIN F60B tuner unit. VHF/UHF £5.00 V/Cap	THYRISTORS Philips G11. G122M. 60p	New V/Cap tuner £3.50 50MHz to 300MHz Automatic Changeover
ITT Control Panel with Mains lead, 4 slider pots, Mains filter. £2.50	5 amp/300v. 25p	Thorn Transductor. £1.00
4 push button unit (for Varicap Tuning) 20K. 50p	52600D 7 amp/400v. 30p	Transductor AT4041/41 50p
4 pots and 6 push button unit for Varicap. Mains on/off switch + Mains filter. I.T.T. CVC 20. £3.50	RCA 40506. 50p	RANK TOSHIBA & ITT mains on-off solenoid switch £1.50
Philips T/unit UHF. £2.00	PYE 22N4444. 85p	R2540. £1.00
Transistor UHF units with Ae socket and leads. GEC 2000 rotary type. £2.00	MR 501 3 amp/100v. 7p	BUY 69 (RCA 1693). £1.00
Thorn UHF tuner unit and panel for 900 series. £8.00	MR 508 3 amp/800v. 12p	
Thorn 900 frame panel. £9.00	MR 856. 12p	
Mullard VHF Tuner V/cap V314. £5.00	SP 8385 Thorn. 25p	
U321 T/unit V/cap. £6.00	ELC 1043 AEG. £4.00	
U322 T/unit V/cap. £6.00	PHILIPS SNIPS: CUTS MOST THINGS. £1.50	
Thorn 3500. Thorn 8500 focus unit. Decca focus unit. Large or small. £1.00 each	CO-AX plugs. 12p	
BUW 84 40p	UHF Aerial socket and leads. PYE, ITT, THORN. 35p	
Decca Bradford Tuner, 5 button (4 push). £2.75	AE Isolating socket. UHF and lead, PYE, THORN, ITT. 35p	
Line O/P Trans. CVC 20. £5.00	Plug and socket 3+6 pin printed circuit type, pair. 10p	
12" TV tube Hitachi A31/300W. £12.00	GEC aerial T/V socket & lead 35p	
SPEAKERS 5x3 80r or 50r. 50p G9 70r. £1.00 5x3 35 ohm. 75p 6x4 15 ohm. £1.00 Philips G11 £1.00	GEC Mains and battery switch. Or stand by. 30p B9A print V/holder. 5p PYE 697 long. 15p TV 11 25p TV 13 25p TV 18 EHT. 40p	
	100k 40 turn pots for V/cap tuning. G9-G11 & Thorn. 20p	
	IF Mod CVC25 £5.00	
	ITT CVC23 Decoder £10 NEW	
	ITT CVC20 Audio amp £1.50	
	ITT CVC20 Driver mod £1.50	
	ITT CVC9 Power supply board £1.50	
	Neon Screwdriver 50p	

SENDZ COMPONENTS

63 BISHOPSTEIGNTON,
SHOEBURYNESS,
ESSEX SS3 8AF.


Reg. Office only.

Callers by appointment only.

Add 15% VAT.
Add 50p P. & P.

Add postage for all overseas parcels

VOLTS-OHMS-MILLIAMPERES MULTIMETER

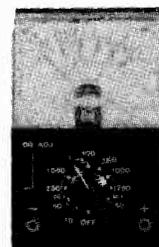

£4.00

1KΩ/V on DC/AC

Equivalent EQ TCA 270 series	I.C.'s—cont.	Semiconductors—cont.	Semiconductors—cont.	100 W/W resistors
CA270CE 50p	SN76532 50p	BF198 7p	TIP32 20p	200 ceramic and plate condensers £1.00
CA270CW 50p	SN76533 £1.00	BF200 20p	TIP33B 10A/80V 25p	2-7 meg & 4-7 meg 10% resistor 100. OFF 50p
CA3089Q 50p	SN76544N £1.00	BF237B 7p	TIP36 30p	300 Carbon film 1/4W 1R to 2M ITT £1.50
MC1327 I.C.'s £1.00	SN76546 No. 7 £1.00	BF240 7p	TIP41A-42 pair 50p	20 slider knobs £1.00
MC476P 50p	SN76550 15p	BF245A 7p	TIP100 30p	1800/4K V 5p
MC1349 50p	SN76570 50p	BF263P 15p	TIP2955.S 40p	4-7NF/5K V 10p
MC1352P 75p	SN76620 90p	BF264 20p	NPN TIP130 60V/8A 25p	180PF/6K V 10p
MC1748CPI 50p	SN76650N 50p	BF273 7p	IN60 3p	210PF/8K V 10p
PUA758PC £1.00	SN76660N 50p	BF274 7p	IN3899 50p	270PF/8K V 10p
S7246/N64100 £5.00	SN76666N 50p	BF337 24p	IN4003 5p	330PF/8K V 10p
SA11020 £6.00	SN76707N 50p	BF355 30p	IN4005 5p	1000PF/10K V 10p
SA11021 £5.00	TBA820 £1.00	BF458 PNP 7p	IN4006 5p	1200PF/12K V 10p
SA11024 £4.00	Touch Tune I.C. ML236E £2.00	BF458 NPN 12p	IN4007 5p	1000PF/12K V 10p
SA11025 £5.00	FT3055 10p	BF458T 12p	XK3123 4000 Thorne £1.00	6200PF/2000V 10p
SA15000 £3.00	Thorn 3500 A1 diodes 15p	BFR79 15p	IR106 40p	BYW56 1000V/2A G11 10p
SAS550 £1.00	AD149 £1.00	BFT34 20p	Y716 20p	TIC126N Thyristors 800V/12A 65p
SAS570 £1.00	BZW70 6-2 10p	BFT43 20p	Y827 30p	4000 Thorn Set Thick Films in Stock.
SBA750B £1.00	BD116 25p	BFY90 15p	1 amp/400V 20p	8" Insulated Pliers £2.00
SL901 £3.00	*Denotes with heatsink.	BR100 30p	1 amp/1600V 7p	7 Lamps for Push Button Units 10p
SL918 £3.00	Semiconductors	BSS68 20p	3 amp/100V 7p	U322 V/Cap T/Unit U.H.F. £6.00
TAA320A 50p	AC128 25p	BSX20 5p	3 amp/300V 10p	47M/250V 10p
TAA470 £2.00	AC153K 25p	BSY79 7p	3 amp/1200V 7p	680M/40V 10p
TAA550 20p	AC176K 25p	BT100 30p	W04 bridge 15p	8M/300V 5p
TAA570 £1.00	AC187/8K pair 50p	BT106 £1.00	W05 bridge 25p	1.000 volts/2A G.11 H.T. Recs (BYW56) 4 for 30p
TAA700 £2.00	AF139 25p	BT106 special 50p	ITT bridge 1 1/4 C73 20p	LM340T/12 12 volt Reg. 20p
TBA120A 40p	AU113 £1.25	BT109 £1.00	3 amp bridge 25p	1.000 volts/2A G.11 H.T. Recs (BYW56) 4 for 30p
TBA120AS 40p	BA159 7p	BT116 £1.00	B30C 600A6 12p	LM340T/12 12 volt Reg. 20p
TBA120B 40p	BA182 7p	BT119 £1.00	B30C 500 12p	9000 Thorn Line O/P Transistors with Heatsink T903 8V £1.00
TBA120C 40p	BA248 7p	BT138/10A 70p	1 amp/100V 20p	SW150 Surface Acoustic Wave Colour T.V. Filters £1.00 each
TBA120SA 40p	BAV10 7p	BT146 25p	NKT279, AC128 12p	Bridge Rec. KBL005 4 amp 50v 30p
TBA120SB 40p	BB103VHF 7p	BT151/800R 70p	MC724CP 40p	8 mixed gun switches £1.00
TBA120U 40p	BB105UHF 7p	BT1822 £1.00	Condensers	RANK TOSHIBA Transducers £1.00
TBA1441 £1.00	BC107 7p	BT1822A £1.00	4700/25 25p	RANK T/V TOSHIBA
TBA396 £1.00	BC108 7p	BT820 20p	470/25 10p	BF858 50p
TBA480Q £1.00	BC109 7p	BU105 50p	220/40 5p	TDA2541 £1.00
TBA510 £1.00	BC139 7p	BU105/04 £1.00	1500/40 10p	TA7315 £1.00
TBA520Q £1.00	BC142 15p	BU108 £1.00	1250/50 10p	TDA2522 £1.00
TBA530 £1.00	BC147C 7p	BU124 50p	220/63 10p	TDA2653 £1.00
TBA540 £1.00	BC148B 7p	BU126 £1.00	1000/63 15p	TDA2560 £1.00
TBA550Q £1.00	BC149C 7p	BU137 60p	700/250 35p	TA7609 £1.00
TBA560CQ £1.00	BC154 7p	BU204 40p	800/250 30p	TDA1010 £1.00
TBA560Q £1.00	BC157 7p	BU205 £1.00	400/350 50p	TDA2650 £1.00
TBA570 £1.00	BC158 7p	BU208 £1.00	220/450 50p	2SC2068 30p
TBA625 £1.00	BC171 7p	BU208A £1.00	33/500 10p	2SC2073 30p
TBA641 £1.50	BC171B 7p	BU208/02 £1.00	1/1000v 15p	2SC1222A 30p
TBA651 80p	BC173 7p	BU326 60p	047/1000 10p	H.T. Rec. BYV958 10p
TBA673 £1.00	BC173C 7p	BU407 50p	017/1000 10p	Delay Line £1.00
TBA720A £1.00	BC174 7p	BU500 £1.00	47/1000 30p	SDL145 £1.00
TBA750Q £1.00	BC182L 7p	CA270 50p	0047/1500 10p	TAU80 £1.00
TBA800 40p	BC183 7p	CA270EW 50p	IN8/1500 10p	DL50 £1.00
TBA810S £1.00	BC183B 7p	E1222 20p	2N2/1500 10p	DL700 £1.00
TBA820 £1.00	BC207 7p	R2008B £1.00	4N7 250v A/C 10p	8807/238KHz Crystal £1.00
TBA890 £1.00	BC212LT 7p	R2010B £1.00	Various Mixed Packs	3115 A/5 Fuse 5p each
TBA920 £1.00	BC213LA 7p	R2603 50p	20 Mixed Convergence Pots £1.00	We have a number of ITT spare panels for CVC 25, 30, 35, 40 and 45.
TBA920Q £1.00	BC237B 7p	RCA16573 30p	100 Mixed EHT Rectifier Sticks £1.00	50-300MHz Varicap Tuner Unit. £25.00
TBA950 £1.00	BC238 7p	OA90 7p	10 Thermistor 50p	
TBA950Q £1.00	BC238A 7p	OT112 £1.00	20 Slider Pots £1.00	
TCA270 £1.00	BC238C 7p	MJESIT NPN 300V 4A-25p	30 Presets 50p	
TCA270Q £1.00	BC245 7p	MJE2955/15A 50p	40 Pots £1.50	
TCA270SQ £1.00	BC250 7p	MJE2801 30p	300 Condenser £1.50	
TCA4500A £1.00	BC251A 7p	BY127 10p	300 Resistor £1.50	
TCA640 £1.00	BC252C 7p	BY133 10p	150 Electrolytic £2.00	
TCA650 £1.00	BC257 30p	BY176 type 18Kv/2M/A 50p	15 bulbs 45p	
TCA740 £1.00	BC300 30p	BY179 35p	100 diodes £1.00	
TCA800 £1.00	BC303 30p	BY184 25p	100 20mm fuses £2.00	
TCA830S £1.00	BC307 7p	BY187/01 10p	Tuner Units Varicap and Mechanical repaired—Please ask for estimates.	
TCE82 30p	BC308B 7p	BY190 40p		
TCE340 30p	BC327 7p	BY204/4 7p		
TCE120CQ £1.00	BC336 20p	BY206 10p		
TCE157 20p	BC337 7p	Fast Recovery Diodes 2 amp 600 to 800 volts 8p each		
TCE527 20p	BC338 7p	BY164 30p		
TCEP100 £1.20	BC350 20p	BY210/400 7p		
TDA1003 £1.00	BC365 10p	BY210/800 10p		
TDA1170 £1.20	BC413C 7p	BY225 5A/1500V 25p		
TDA1190Z £1.20	BC454 7p	BY226 10p		
TDA1327 £1.00	BC455 7p	BY227 16p		
TDA2530 £1.00	BC462 20p	BY296 10p		
TDA2600 £2.60 each	BC463 7p	BY298 12p		
TDA1412 50p	BC464 7p	BY299 10p		
TDA2522 £1.50	BC546 7p	BX407 10p		
TDA2540 £1.00	BC548A 7p	BYN3123 wire end 50p		
TDA2002 £1.00	BC559 7p	BYF3126 wire end 60p		
TDA2640 £1.00	BD124 £1.50	BYF3214 20Kv 50p		
TDA2680 £1.00	BD131 30p	BYX36/600 40p		
TDA2690 £1.00	BD132 30p	BYX38/600 50p		
TDA3960 £1.50	BD135 & BD136 Pair 30p	BYX/300 25p		
TDA3560 £1.50	BD207 30p	BYX55/350 10p		
SN1682AN £1.00	BD221 20p	BY255 4.8 amps 10p		
SN16964AN 50p	BD228 25p	BYX38/300 25p		
SN29764 £1.00	BD238 20p	BYX71/350 25p		
SN29848 50p	BD239 12p	BXY72/300 25p		
SN75108AN £1.00	BD331 25p	2N390 7p		
SN76001 £1.00	BD332 25p	2N2222 7p		
SN76003 £1.00	BD253B 35p	2N3055 35p		
SN76003* £1.50	BD416 25p	2N3566 7p		
SN76008KE £1.00	BD561/2 pair 30p	2N4355 7p		
SN76018KE £1.00	BD595 35p	2N4442 60p		
SN76023* £1.50	BD596 35p	2N4444 £1.00		
SN76033 £1.00	BD681 25p	2N5983 30p		
SN76033* £1.50	BD807 10a/70V 25p	2N6099 25p		
SN76115 50p	BD534 25p	2N6348 50p		
76131 50p	NPN 9 watt 25p	2N6399A 30p		
SN76226 £1.00	BF127 20p	2SK30A 7p		
SN76227 50p	BF137 20p	TIP29C 20p		
I.L.I. Infrared Led Phototransistor Opto Isolators 50p	BF157 20p	TIP29A 20p		
Breakdown Voltage 2.500V	BF180 20p	TIP30A 20p		
SN7630P 50p	BF181 20p	TIP30A 20p		
SN7650N £1.00	BF182 20p	TIP31A/B 20p		
	BF185 20p			
	BF195 7p			

SENDZ COMPONENTS
63 BISHOPSTEIGNTON,
SHOEBURYNESS,
ESSEX, SS3 8AF
Reg. Office Only.
Callers by appointment only.
Add 15% VAT and 50p P. & P.
All items subject to availability.
Add postage for all overseas parcels.