

# CIRCULATES IN EVERY COUNTRY IN THE WORLD!



## ROUND *the* WORLD of WIRELESS

### Our Second Combined Issue

**T**HIS is the second combined issue of those two famous journals, "Practical Wireless" and "Amateur Wireless." Just as we go to press we learn that the first issue is completely out of print, and letters from the readers of both papers are pouring into these offices bearing messages of congratulation on our important amalgamation, which, coming as it does in what promises to be the most important period in the history of wireless—for television is imminent—provides a most powerful force in radio journalism, destined to play a vital part in the perfecting of the new science.

This journal has, during the whole of its career, enjoyed a world-wide reputation. It circulates and is keenly read in every English-speaking country in the world. More, its contents have been translated and published in practically every country in the world!

### An Enlarged Short-wave Section

And so "Practical and Amateur Wireless" will lead the way in the short-wave field. In anticipation of the turn which television developments are likely to take, last year we produced a valuable handbook dealing in a popular way with all of the branches of this fascinating new hobby—we refer to our "Television and Short-wave Handbook," many thousands of copies of which have been supplied to our readers. The publication of this book was, indeed, timely, for it is quite obvious that television and short waves will go hand in hand.

It is with especial pleasure, there-

fore, that we announce as from next week's issue a greatly-increased short-wave section, informative, up to date, and attractively illustrated.

The short-wave section of this journal has always been a popular and keenly-read feature—the best, in fact, in radio journalism; but the needs of this branch of radio telephony have rapidly outgrown the

*Owing to the Growing Importance of Short-wave Radio, we take pleasure in announcing that as from next week's issue, the Short-wave Section of "Practical and Amateur Wireless" will be developed and enlarged.*

space allocated to it. So we are providing it next week with ampler quarters, enabling our Short-wave experts adequately to deal with all branches of it.

### A Twenty Hour Day!

**T**HE German high-power long-wave station has extended its transmissions, and is now on the air on most days from G.M.T. 05.00 until 01.00 the following morning. Cologne, Frankfurt, and Stuttgart are now also late birds, and many nights weekly may be heard working long past midnight.

### 100-Kilowatt for Manchukuo

**T**HE Manchuria Telegraph and Telephone Company has installed a high-power station at Hsinking, the capital city of the new Kingdom of Manchukuo. So far it is the most powerful broadcasting station in the Far East, and is to be used to combat propaganda transmitted to that region by the Soviet transmitters. The

broadcasts are regularly picked up in Kharbin, Mukden, and in the later evening hours, in Japan.

### New Wireless Electric Clock

**I**T is reported that at one of the principal New York railway termini, engineers have installed a clock which is entirely controlled by radio transmission. The clock is operated from the Arlington wireless station. All clocks on the railway system are now being set in accordance with this novel timekeeper. If, after several months' testing, the principle gives full satisfaction, similar clocks are to be installed in other public institutions.

### Listen to Mexico

**N**OW that broadcasts from the United States and from the Argentine Republic are regularly heard in the United Kingdom, an effort should be made to tune in some of the Mexican radio entertainments. Stations already logged here are XENT, Nuevo Laredo, 267.7 metres (1,120 kc/s); XEW, Mexico City, 337.1 metres (890 kc/s), and XEPN, Piedras Negras, 508.5 metres (590 kc/s). Broadcasts from XEW are particularly well received on favourable nights between G.M.T. 02.00—04.30. The interval signal is reminiscent of a clock chiming the quarters (four bells). Announcements are made in both Spanish and English.

### When You Miss the B.B.C. Weather Forecast

**A**IR MINISTRY weather forecasts and reports are transmitted daily from Heston Airport (Middlesex) on 1,202 metres (249.5 kc/s) at G.M.T. 08.45, 09.30, then hourly, with the exception of 13.30, until 16.30 during the winter months. Although they are essentially destined to civil aviation, the broadcasts are very useful to the general public.

### Holland's Time Problem

**T**HE Dutch Government is considering a proposal to adopt Central European time. The suggestion of making the clocks in that country coincide with G.M.T., as is the case in Belgium, has been turned down. So far, Dutch time is twenty minutes *behind* Central European time, a condition which somewhat complicates railway time tables.

# ROUND the WORLD of WIRELESS (Continued)


## Belgium's Proposed Third Transmitter

ALTHOUGH the idea of a third station for this little Kingdom had been cast aside in favour of an increased power for the twin transmitters at Velthem, near Louvain, which broadcast the Brussels No. 1 and No. 2 programmes, the suggestion has

### INTERESTING and TOPICAL PARAGRAPHS

purely of an experimental nature, the call heard, in the course of the broadcast, may be that of the Warsaw studio from which the programmes are relayed.

### THE YOUNG IDEA

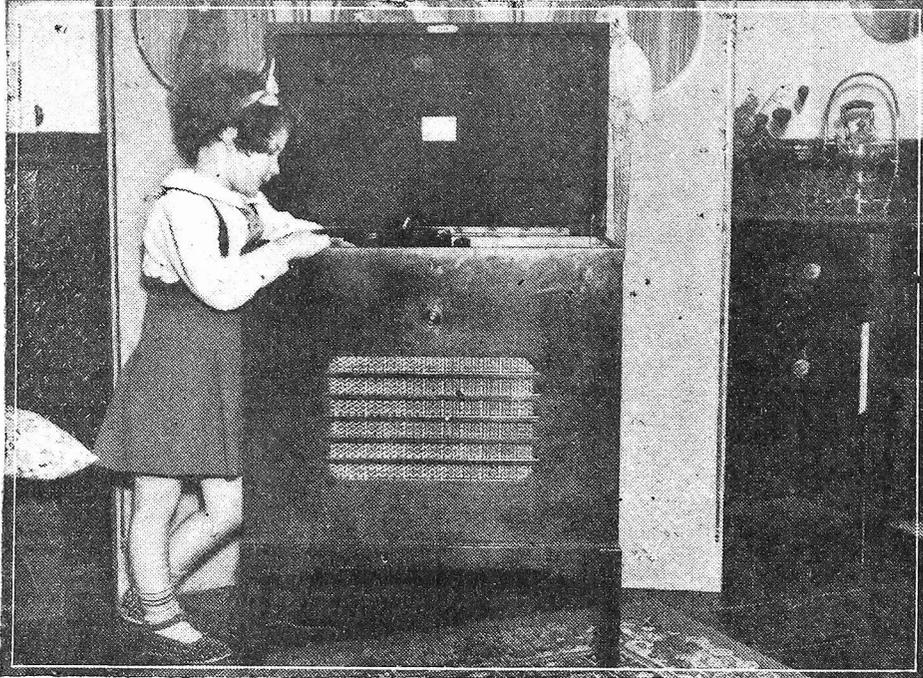

A small enthusiast preparing a programme to be heard on her "His Master's Voice": "Super-het Fluid-light Autoradiogram."

now been revived by one of the political parties, and is receiving serious consideration. A definite proposal has now been put forward to erect a third station on the Eastern frontier.

### To Honour the Marchese Marconi

AT the birthplace of this famous radio pioneer, Bologna (Italy), it has been decided to build a 50-kilowatt transmitter entirely of Italian manufacture. It will be run by the E.I.A.R. (the Italian Broadcasting Authorities), and is to be known as the *Stazione Guglielmo Marconi*.

### Another Russian Giant

THE Soviet Government, in order to provide adequate service to the Siberian republics, and also for transmissions to listeners dwelling in the Manchukuo and Japanese Empires, have planned a 500-kilowatt transmitter to be installed at Khabarovsk. It is to be built on the same lines as the high-power Moscow station.

### Droitwich's Berlin Rival

THE 150-kilowatt transmitter to be built at Brueck, some thirty miles from Berlin, according to a German report, will prove the most up to date of all European stations. A new aerial system consisting of seven pylons, 825ft. high, set in a circle, will, it is stated, prove an effective cure of "fading."

### New Polish Broadcaster

TESTS are now being carried out on 304.3 metres (986 kc/s) by the new 24-kilowatt station erected at Mokre, near Torun (Poland). As the transmissions are

### The B.B.C. Symphony Orchestra

THE B.B.C. Symphony Orchestra continues its provincial tour, visiting Bristol on February 13th. Its subsequent visits are Birmingham, February 27th; Dundee, April 2nd; and Brussels, March 12th. So much interest has been occasioned at Bristol by the visit of this enormous orchestra, which is the biggest permanent musical combination in Europe, that the B.B.C. has already received an inquiry for a block of tickets of 400 from one school.

### "Mother Goose"

ON February 2nd, Francis Laidler's pantomime, "Mother Goose" (founded on the book by J. Hickory Wood), will be relayed to Northern listeners from the Theatre Royal, Leeds. The cast includes Vera Lennox (Principal Boy), Connie Graham (Mother Goose), Albert Modley (Jack, the Widow's Son), and Olga May (Principal Girl). A Flying Ballet, a Rolls Royce Chorus, and a troupe of Little Sunbeams will also take part.

### Wagner's Music from Manchester

THE second half of the William Rees Society's Concert will be relayed to Northern listeners from the Milton Hall, Manchester, on February 2nd. Conducted by William Rees, the William Rees Orchestra will play a programme of Wagner's music, including "Forest Murmurs," from "Siegfried," "Dreams," and the Overture to "Tannhäuser." Supported by the orchestra, Frank Titterton, well-known Northern tenor, will sing "The Prize Song" from "The Mastersingers."

### Choral Concert from Ulster

TWELVE Belfast choirs, totalling in all something over four hundred voices, will be seen on the platform of the Ulster Hall on February 1st, when they will appear at a concert given in co-operation with the Belfast Corporation.

### "Breakfast in Evening Dress"

CHARLES BREWER, one of the producers of the Light Entertainment Department, has written the book of a musical comedy called "Breakfast in Evening Dress," to be broadcast on February 6th. The music is by Alan Paul. The story revolves round the extraordinary steps needed to comply with a most eccentric will. The cast is a strong one, headed by Wynne Ajello. Opposite her will be Michael Cole, while the humour is in the hands of Dick Francis and Claude Hulbert. Supporting these are Gladys Marlowe, Cyril Nash, and Ernest Sefton. Mark Lubbock will conduct the revue chorus and the B.B.C. Orchestra.

### Recital of Russian Songs

MADAME SPIRIDOVITCH is giving a song recital in the National programme on February 10th. She is a well-known Russian singer of Russian gipsy and folk songs and has a large public in Paris. In this recital she will include, in addition to Russian songs, a group of Neapolitan folk songs and also a group of songs by Gretchaninoff.

### Rugby Male-voice Choir

THIS well-known choir, which was founded over twenty years ago, will give a programme of part songs in a Midland studio on February 3rd. The conductor, Mr. George Pritchard, was responsible for the reorganisation of this choir in 1930, and since then it has won many awards. In the same programme, Winifred Browne, the Birmingham pianist, will play Dr. Byrd's Pavan, "The Earle of Salisbury," and other pieces.

(Continued on page 733)

## SOLVE THIS!

### Problem No. 124.

Wilkinson built a three-valve variable-mu battery-operated receiver employing separate dual-range tuners for the aerial and inter-valve circuits. These tuners were not fitted with their own wave-change switches, but a three-point on-off switch was used to short-circuit the long-wave windings of the two coils. On completion of the set it was found that fairly good reception was obtained, but the volume-control potentiometer used in conjunction with the variable-mu valve was inoperative on the medium-wave band. What mistake had Wilkinson made?


Three books will be awarded for the first three correct solutions opened. Mark your envelopes Problem No. 124 and address them to: The Editor, PRACTICAL AND AMATEUR WIRELESS, Geo. Newnes, Ltd., 8-11, Southampton Street, Strand, London, W.C.2. Entries must be received not later than first post on Monday, February 4th.

### Solution to Problem No. 123.

The anode resistance in Welbeck's receiver had developed an open circuit, so that there was scarcely any voltage reaching the anode of the detector valve. A very low voltage was passed on to the valve due to leakage, but this was not sufficient to provide reaction. The following three readers have correctly solved Problem No. 122, and books are being sent to them: J. Orr, 9, West End Place, Edinburgh; W. Shortland, 34, Malvern House, Stamford Hill, N.16; J. Dawney, 39, Courtenay Gardens, Uppminster, Essex.

# HALF-HOUR EXPERIMENTS

By BERNARD DUNN

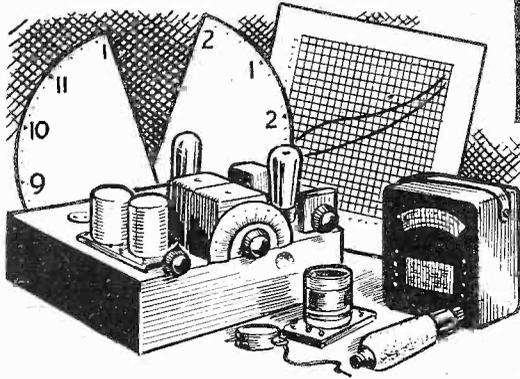

SEVERAL readers have expressed interest in the articles in this series that have dealt with the question of taking voltage and current measurements, and have asked for more complete particulars. They have pointed out that although the details given were sufficient to enable them to calculate the values of shunt and series resistances when converting a milliammeter for universal readings, they prefer to elimi-

Details are Given for the Construction and Calibration of a Multiple Testing Unit Employing a Moving-coil Milliammeter of Any Type.

### Variable Shunt Resistance

For increasing the current reading of the meter it will first of all be necessary to obtain a variable resistance or potentiometer (not of the graded type) having a resistance value of about twice that of the meter, and this should be of the type having a definite "off" position; in other words, the slider should leave the resistance element at one end of its travel. Alternatively, the resistance purchased may be of the type fitted with an on-off switch, since this will produce the same effect. Variable resistances with values between 2 and 50 ohms (type FR), or from 50 ohms upwards (type ST5C) are made by Colvern and cost 3s. 6d. each. As an alternative to buying a new component it will often be found possible to re-wind an existing potentiometer with 36-gauge Eureka resistance wire, which has a resistance of approximately 15 ohms per yard, or with 40-gauge Eureka, which has a value of about 37 ohms per yard.

The method of connecting the variable resistance is shown in Fig. 3, where it will be seen that the centre terminal (slider) is

connected to one terminal of the milliammeter, and one of the end terminals is joined to the other terminal of the meter. The next task is to calibrate the resistance for various "multiplication factors." This means that a large circular paper or celluloid scale must be made to fit under the mounting nut, and that a corresponding pointer should be fitted to the knob. Another method is to use an old condenser dial, gluing a ring of white paper round its bevelled edge.

### Current Calibration

Now connect the meter in series with a battery and fixed resistance, as shown in Fig. 3, the resistance being of such a value that the meter shows practically a full-scale deflection. This means that, assuming the use of the 6-volt tapings of an H.T. battery, the resistance should be 6,000 ohms for a 1-m.a. meter, 3,000 ohms for a 2-m.a. meter, about 1,200 ohms for a 5-m.a. meter or 600 ohms for a 10-m.a. meter. The full-scale reading should be obtained when the variable resistance is in the "off" position, or is disconnected. Make a very careful and accurate note of the exact reading, and then rotate the knob of the variable resistance until the current passing through the meter is exactly halved; that setting of the resistance will give a "multiplication factor" of 2, or, in other words it will double all the scale readings obtained. Therefore make a mark on the resistance scale and place a figure 2, 4, 10 or 20 beside it, according to

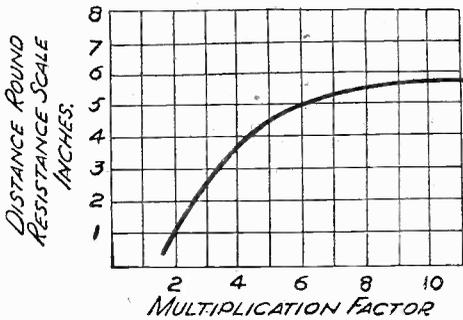


Fig. 1.—A graph can be made to obtain calibration points for currents higher than those for which the battery is suitable by drawing a graph as shown here.

nate mathematics as far as possible. Even those readers who have no fear of the calculations involved are in many cases "stumped," due to the fact that they are unaware of the resistance of the particular milliammeter that they happen to possess.

It would therefore seem to be very desirable this week to deal more fully with the matter of making a multi-purpose test instrument, making the information so general that it can be applied in any particular case, and of such a form that mathematics of every description can be ignored. It must be made quite clear that the degree of accuracy to be secured by following the methods to be outlined will not approach the 100 per cent. mark, although it will be adequate for all normal purposes, when a tolerance of, say, 5 per cent. is easily allowable.

### A Suitable Meter

The first requirement is a moving-coil milliammeter—this is essential, for a cheap meter of the moving-iron type is entirely unsuitable for our purpose. The meter may be one having a full-scale reading of between 1 and 10 milliamps, and the resistance of this will in all probability lie between 100 ohms (for the lower reading) and 10 ohms (for the higher reading). In the same way it may be considered for the preliminary experiments that meters with other readings will have resistances in the proportions mentioned. That is, a 2-m. liamp. meter will have a resistance of about 50 ohms, and a 5-milliamp. meter will have about 20 ohms resistance.

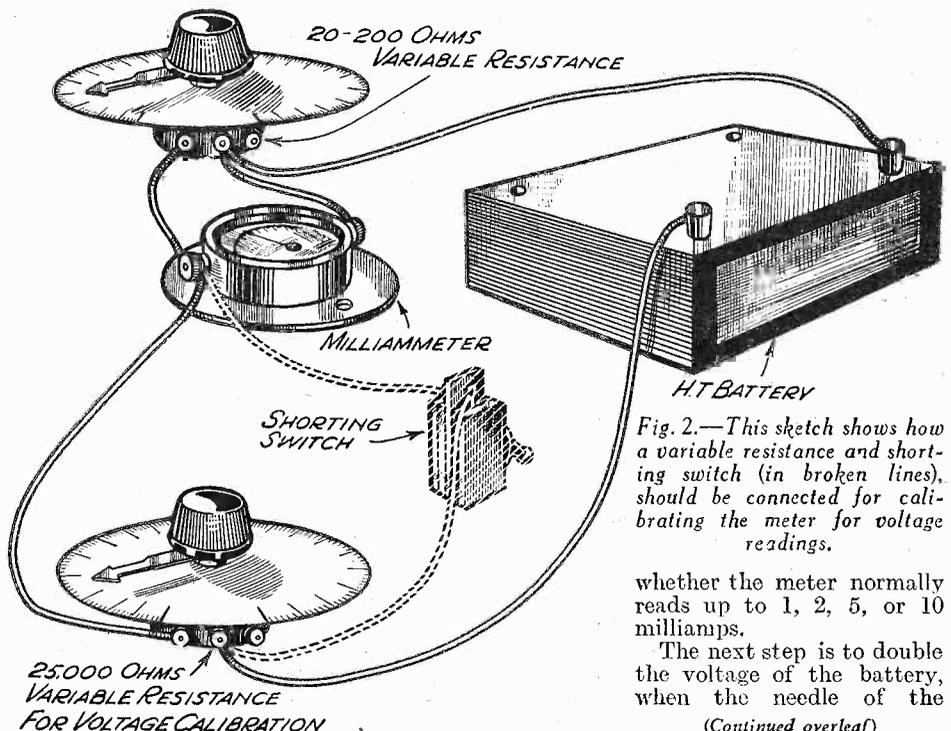


Fig. 2.—This sketch shows how a variable resistance and shorting switch (in broken lines), should be connected for calibrating the meter for voltage readings.

whether the meter normally reads up to 1, 2, 5, or 10 milliamps.

The next step is to double the voltage of the battery, when the needle of the

(Continued overleaf)

(Continued from previous page)

meter should return to its first position. The process previously described should then be repeated to determine the setting of the parallel resistance that gives a "multiplication factor" of 4. This method of calibration may then be repeated until the "multiplication factor" is such that the maximum current that can be read is about 25 milliamps, although if a super-capacity H.T. battery, or a set of H.T. accumulators, is available it may be continued up to 100 milliamps or so, taking care that this heavy current only flows for a second or two.

It might seem that the limit of calibration has been reached at much too low a value, but further calibration points can be obtained by drawing a graph showing the positions of the resistance pointer that have been located. For instance, if the distances of the marks around the circumference of the scale are measured—by means of a tape measure, say—and plotted on a sheet of squared paper against the "multiplication factors," as shown in Fig. 1, a variety of other calibration points can be located with fair accuracy.

### Measuring Voltages

Having made the current calibrations, it will next be necessary to provide for voltage measurements, and this can be done by connecting a variable resistance in series with the meter, as shown in Fig. 2. The resistance in this case should be of much higher value than before, the resistance being approximately 25,000 ohms to give a maximum reading of 100 volts with a 5-milliamp. meter, or with the parallel resistance set to ensure a full-scale deflection of this amount. If the meter gives a maximum reading of 10 milliamps., the same value of resistance can still be used, but the adjustments to be described will then be made until the meter shows a reading of only one-half of the maximum.

The idea is to connect the meter and series resistance in series with a 100-volt battery (a new one of reputable make is

best), first setting the resistance to its "all-in" position. In these conditions a reading of rather less than 5 milliamps. should be obtained, but a slight variation of the resistance should bring the reading to exactly 5 milliamps. A word of warning is necessary here, because if any mistake were made in connecting the series resistance, or if the component were faulty, there would be a danger

of damaging the meter. To avoid anything of this kind it is best to start by inserting the wander plug into the 1½-volt socket, advancing it by short steps until the full voltage is reached, if it is found that the meter reading is always below the maximum.

### Up to 400 Volts

Having found that the resistance is of suitable value a scale can be made for it similar to that used for the parallel resistance, and this can be marked with the position of the pointer for the 100-volt reading. Readings up to 200 volts or 400 volts can then be obtained simply by moving the parallel resistance from the 5-milliamp position to those giving 10 and 20 milliamps respectively. On the other hand, the same result could have been achieved by using a 100,000-ohm series resistance and, after finding the setting for 100 volts, rotating the knob until the meter showed a half-scale (200 volts maximum) or a quarter-scale (400 volts maximum) reading. The latter method is better in some respects, because it makes for simplification and avoids the possi-

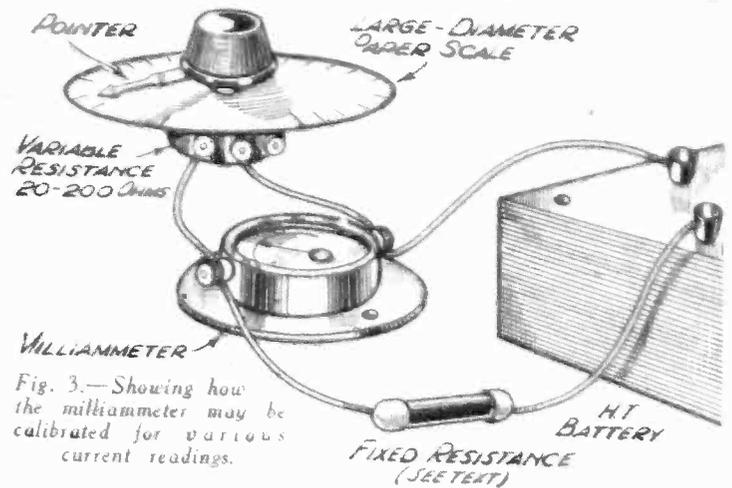


Fig. 3.—Showing how the milliammeter may be calibrated for various current readings.

bility of confusion between the two controls.

It is not satisfactory, however, when voltages lower than 100 are to be measured, and it will generally be desirable to calibrate the meter for reading up to 10 volts or so. When using the 25,000-ohm resistance, this can be done by reducing the voltage of the H.T. battery to 9, and then setting the resistance until a reading equal to nine-tenths of that of the whole scale is obtained. Other scale readings can be obtained by following the same idea.

### Mounting the Parts

It is scarcely necessary to give practical details concerning the assembly of the two variable resistances and the meter in a box, since every experimenter will be able to devise a suitable arrangement. A cigar box, however, might be suggested as a container for the components, and a long flexible lead, or plug sockets, can be fitted for connection purposes. A switch will be required for cutting out the series resistance when taking current measurements, and this will be connected as shown in broken lines in Fig. 2.

### Short Wave Notes

## LONG-DISTANCE DAYLIGHT RECEPTION

Stations to Search For During the Hours of Light

HAVE you tried your receiver out during daylight? If so, you were doubtless surprised at the number of stations which provided loud-speaker reception. If not, you have a pleasant surprise awaiting you. During the mornings, Hilversum, Fécamp, Breslau, Berlin, Langenberg, Athlone, Rome, and a host of other stations provide good loud-speaker reception upon the average receiver. Many distant stations are also audible.

For instance, Budapest provides a good programme during the afternoons, and this station can frequently be heard well as early as 1 p.m. In roughly the same direction, but farther afield, Ljubljana, the well-known Yugo-Slavian station, provides a moderately powerful signal upon many occasions.

### Russian Stations

Special attention should be given to Russian stations, for many of them are audible during daylight. Perhaps you have heard RW39, Moscow-Stalino, which operates upon 386.6 metres. If not, I certainly recommend you to tune to that wavelength upon some afternoon—this station provides an astonishingly good signal upon most occasions—when, unless conditions are bad, you will hear Moscow. Because Toulouse PTT and Fredrikstad operate upon its wavelength during the night this station is best heard during

daylight. If you are fortunate you may hear Astrakan, RV35, which, although located near the Caspian Sea, provides a good signal upon many occasions.

Some persons—the writer among them—consider that long-distance reception is unobtainable from Europe. In short, we feel that any part of Europe is too near to be labelled "DX."

### Asia During Daylight

Therefore DX enthusiasts will be interested to know that what is termed "DX" reception is forthcoming during daylight. Tashkent, on 1,170 metres, provides a good signal upon most afternoons despite the fact that it is just north of India. Even more remarkable is Alma-Ata. This station, which is situated north of Burma, may be heard around 410 metres on most nights after 11 p.m. More remarkable still is the fact that it provides a fair signal during the daylight.

Other Russian stations worth looking for are: RW49, Tomsky, which operates upon 554 metres; Makhatch, 563 metres, and either Nijni-Novgorod or Gorki

(RW42) which both operate upon 598 metres. All the above, and many others, are audible during the afternoons unless conditions are particularly bad.

### America in the Afternoon

Occasionally one or more American stations can be heard during the afternoon, but this is uncommon. When American stations do come in they are generally situated between 200 and 220 metres. On one or two occasions, however, WBZ, Boston, on 301 metres, has been heard as early as 1 p.m., and it is quite possible to hear this station at fairly good volume around 7 p.m.

On occasions WKBW, Buffalo; WGAR, Cleveland; WLAC, Nashville; and WJSV, Washington, are audible at moderate strength. However, the reception of America during the afternoon is, as remarked above, rather rare. Between the hours of 6 and 9 p.m. many American stations can generally be heard and, because many are low-powered stations broadcasting DX programmes, are generally worth receiving.


### Africa Also

In conclusion, another station may be mentioned which is heard best during daylight. It is Cairo, on 480 metres. During the evening it is interfered with by Brussels, but during daylight it provides a passable signal on most occasions.

# MAKING A DROITWICH SUPPRESSOR

Full Constructional Details are Given in this Article of an Easy-to-make Wavetrapp for Cutting Out Interference from the Powerful Droitwich Station.

By W. B. RICHARDSON

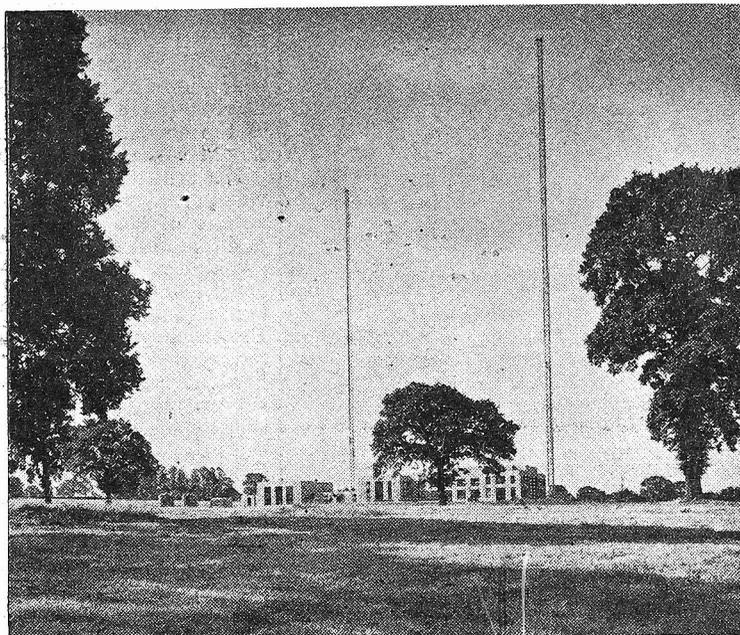

A general view of the Droitwich transmitting station from the north side.

SINCE the opening of the new high-power transmitter at Droitwich many listeners are experiencing considerable interference on the long-wave bands. In fact, in some cases this station spreads over practically the whole of the dial and renders the reception of other stations almost impossible.

In such instances the usual dodges for increasing selectivity are entirely inadequate. For example, the use of a small condenser connected in series with the aerial, or the employment of a smaller aerial would only sharpen the tuning at the expense of volume. In most cases the degree of selectivity required is such, that the loss in sensitivity attendant upon these methods would be too great. In other words the weaker stations would probably disappear altogether. A better solution is to be found in the use of a wavetrapp. This consists of a small unit which is connected between the aerial and the receiver. The unit comprises a tuning coil and a variable condenser and can quite easily be made up from odds and ends obtained from the average constructor's junk box.

## How It Works

Before engaging on the construction of the actual unit it is just as well to have some idea of the principle on which it works. Reference to Fig. 1 will show that the coil and condenser are connected in parallel in just the same way as an ordinary tuning circuit. Actually there are two condensers shown—one fixed and one variable—but this is done for practical reasons. Theoretically this amounts to the same thing as using one condenser.

The coil and condenser together form what is called a *resonant rejector circuit*.

The action of this will no doubt be clearer from a study of Fig. 2 which shows the basic circuit. Such a circuit will *resonate* at a certain frequency dependent on the values of the inductance (coil) and the condenser. This means that if an alternating voltage of this particular frequency be applied to the circuit at the points A, B, it will set up an oscillating current in the circuit as indicated by the arrows. This oscillation gives rise to an alternating voltage at A, B, which absolutely coincides in point of time and magnitude with the applied voltage (this is assuming that the circuit has no resistance). Therefore no current can flow through the circuit from outside. It is this property which is made use of in a wavetrapp. If a resonant rejector circuit of this type be connected between the

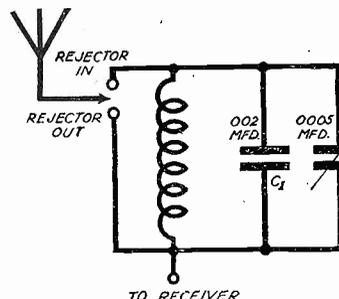


Fig. 1.—Circuit diagram of the eliminator.

the receiver, as in Figs. 2 and 3, it will prevent any alternating current flowing through it which has the same frequency as the resonant frequency. Of course, by the choice of suitable values for the inductance and the condenser the circuit can be made to resonate at any desired frequency. In the case of Droitwich, therefore, the wavetrapp is designed to resonate at 200 kilocycles. It thus acts as a barrier to signals from this station. Actually it does not offer a

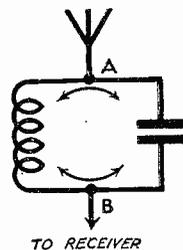


Fig. 2.—A simple aerial of rejector circuit.

perfect barrier, although it allows only a very small current to pass. This is because in practice the rejector circuit always contains some resistance. In the rejector shown here, approximate values are chosen for the inductance and condenser and the final adjustment is made by means of the variable condenser C2. When the eliminator is connected to the receiver its effect is to reduce the sensitivity of the latter to practically nil at 200 kilocycles. However, the sensitivity increases rapidly on either side of this point, and thus other stations can be received on other parts of the scale. Incidentally the selectivity of the unit is an important point, since it is highly desirable to confine the rejector action to just the frequency of Droitwich and for it to pass all frequencies on either side of this point. If the tuning is flat the rejector action will decrease only slowly on either side of the 200 kilocycles point and thus other stations nearby will be also reduced in strength. The degree of selectivity depends on the ratio of inductance and capacity. Thus with a large inductance and a small capacity the tuning will be comparatively flat while a small inductance and a large capacity will give a more selective circuit. In the unit described here a coil of 100 turns of wire is used in conjunction with a total capacity of about .0025 mfd. On the other hand it would be quite in order to use a coil of 150 turns and a condenser of .0005 mfd. This would have an even more powerful rejector action at the resonant frequency, but there would be some reduction in the strength of nearby stations as well.

perfect barrier, although it allows only a very small current to pass. This is because in practice the rejector circuit always contains some resistance.

In the rejector shown here, approximate values are chosen for the inductance and condenser and the final adjustment is made by means of the variable condenser C2. When the eliminator is connected to the receiver its effect is to reduce the sensitivity of the latter to practically nil at 200 kilocycles. However, the sensitivity increases rapidly on either side of this point, and thus other stations can be received on other parts of the scale. Incidentally the selectivity of the unit is an important point, since it is highly desirable to confine the rejector action to just the frequency of Droitwich and for it to pass all frequencies on either side of this point. If the tuning is flat the rejector action will decrease only slowly on either side of the 200 kilocycles point and thus other stations nearby will be also reduced in strength.

The degree of selectivity depends on the ratio of inductance and capacity. Thus with a large inductance and a small capacity the tuning will be comparatively flat while a small inductance and a large capacity will give a more selective circuit. In the unit described here a coil of 100 turns of wire is used in conjunction with a total capacity of about .0025 mfd. On the other hand it would be quite in order to use a coil of 150 turns and a condenser of .0005 mfd. This would have an even more powerful rejector action at the resonant frequency, but there would be some reduction in the strength of nearby stations as well.

## Constructing the Unit

The Droitwich eliminator consists essentially of a tuning coil wound on a 2in. cylindrical former, a fixed condenser, and a variable condenser for making the final adjustment. The coil consists of 100 turns of 28 gauge d.c.c. wire wound in a single

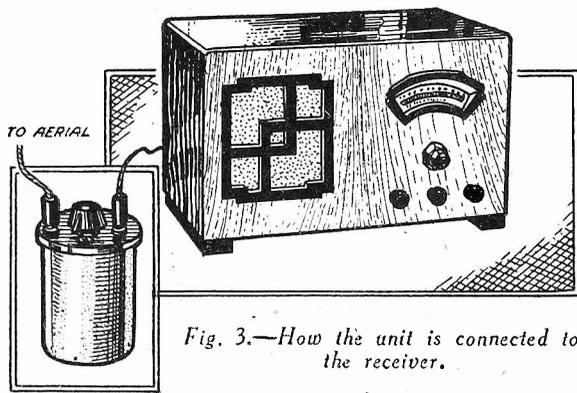


Fig. 3.—How the unit is connected to the receiver.

### LIST OF PARTS

- One J.B. "Dilecon" variable condenser, .0005 mfd.
- One .002 mfd. Dubilier fixed condenser, type 670.
- Three Belling-Lee insulated sockets with plugs. Paxolin former 2in. diam., by 3in. long.
- Parts for case as detailed in the text.

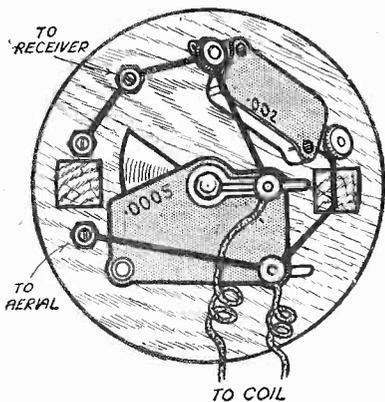


Fig. 4.—Wiring diagram from underside of lid.

layer on a 2in. paxolin former 3in. long. Two small holes are pierced through the former about  $\frac{1}{4}$ in. from one end and the wire threaded through in the usual manner, leaving a few inches for connecting purposes. The wire is then wound on tightly and evenly until the 100 turns have been completed, when two more holes are pierced and the wire threaded through as before. The 100 turns should occupy about  $2\frac{1}{2}$ in.; thus the winding should end within  $\frac{1}{4}$ in. of the end of the former.

When the coil is completed it should be put aside while the other parts are being assembled. The top of the unit consists of a round disc of hard wood. Any local hand-crafts shop would be able to turn this up for a few pence, but failing that it could be made in a hexagonal form. This can be cut out quite easily with a tenon saw by the average handyman. When the top is finished it is drilled with the necessary holes to take the condenser and the sockets. These parts are then mounted in position together with the fixed condenser and are wired up as shown in Fig. 4.

The next job is to mount the coil on its base. This latter consists of a wooden disc, which is a push-fit in the end of the 3in. cardboard tube which forms the body of the unit. The method of mounting the coil on the base will be quite clear from a glance at Fig. 5. A wooden strip is bradded and glued in position on the base, and the former is then fixed to each end of this with the aid of brads. The card body of the unit is fixed in position next. One or two fine brads are used and driven through the tube into the base. Before placing the top on the unit the two wires from the coil are connected to the terminals of the variable condenser. The unit should then be tested out before the top is finally secured in position.

To test the wavetrapping the receiver should be connected to the aerial in the usual way, and then tuned exactly to the Droitwich wavelength. If, owing to the tuning spread, the exact position is not very definite, then the volume control should be turned right down. This will, of course, reduce the spread and enable the exact wavelength to be determined more easily. These remarks apply to the ordinary type of volume control and not to a combined selectivity and volume control in the form of a variable condenser. This latter type usually alters the tuning slightly when it is turned down. Having tuned-in to Droitwich the set should be switched off and the wavetrapping connected up. One socket on the unit is connected to the aerial terminal or socket on the receiver and the other to the aerial. The third socket is left unconnected. The receiver is then switched on again and the volume turned up. The tuning control on the unit is slowly rotated until the signals from

Droitwich reach a minimum strength. If the instructions have been followed carefully this will occur at a position somewhere near the midway setting of the condenser. Having found this position, a movement of the condenser knob in either direction should cause an increase in volume.

With the control set to give the minimum volume, a mark is made opposite the pointer of the unit in order to mark the position, and the wavetrapping should then be left alone. Tuning of the receiver is then carried out in the usual way. It will be found that the reduction in volume from Droitwich will allow other stations to be received free from interference. There is just one warning. With some receivers the tuning positions will be altered very slightly when the eliminator is in use, but the actual amount depends on the nature of the tuning arrangements employed in

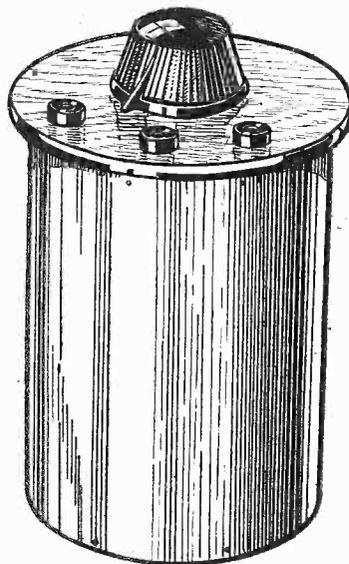


Fig. 6.—The completed wavetrapping.

the set. Regarding the setting of the wavetrapping, this would normally be left at its original setting, but slight variations can be made to suit particular conditions. For instance, it is sometimes found that a station above the wavelength of Droitwich can best be received with the wavetrapping pointer turned a little to one side of the normal position in an anti-clockwise direction. A station below Droitwich, on the

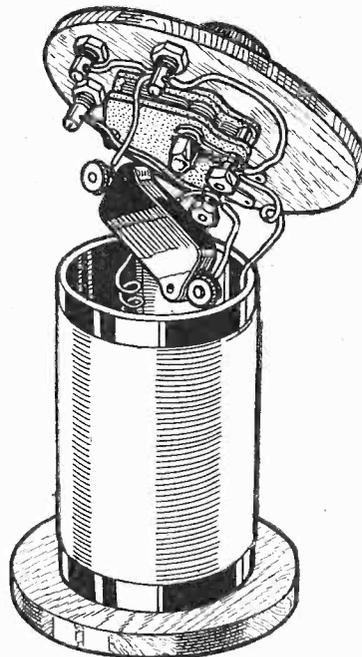


Fig. 7.—How the wavetrapping is assembled.

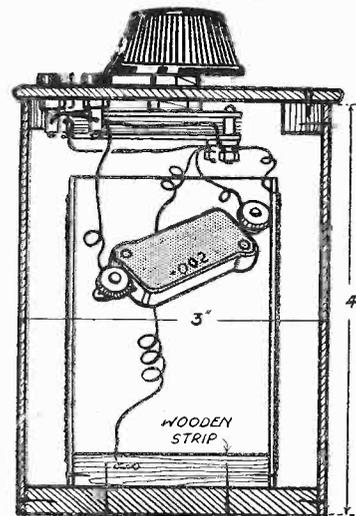


Fig. 5.—Sectional view of the unit showing how the coil is mounted.

other hand, may be found to come through with better strength with the pointer set slightly in the opposite direction. When it is desired to listen to Droitwich there is no need to alter the setting of the eliminator. All that is necessary is to remove the aerial from its socket and to plug it in to the vacant socket. This cuts the wavetrapping out of the circuit.

Those who are interested in experimenting may care to try variations in the ratio of inductance to capacity. As an example the fixed condenser might be increased to .004 mfd. when the coil would need to be reduced to about 60 turns. On the other hand, a more powerful rejector action, but less localised, could be obtained by using an ordinary plug-in coil of 150 turns tuned by the .0005 mfd. condenser only.

### HIGH-EFFICIENCY VALVES

IT is amazing to note the progress that has been made in valve design during the last couple of years or so. We all know of the mains pentode valves that enable a signal output of something like  $2\frac{1}{2}$  watts to be




The Valves used in Mr. F. J. Camm's New Receiver—The A.C. Hall-Mark.

obtained with the comparatively small input supplied by the average leaky-grid detector, but I learnt the other day that a directly-heated mains pentode is shortly to be placed on the market that gives an output of 3,800 milliwatts with an input grid voltage of rather less than 6.

An Interesting New Series

# PROGRESSIVE HOME CONSTRUCTION

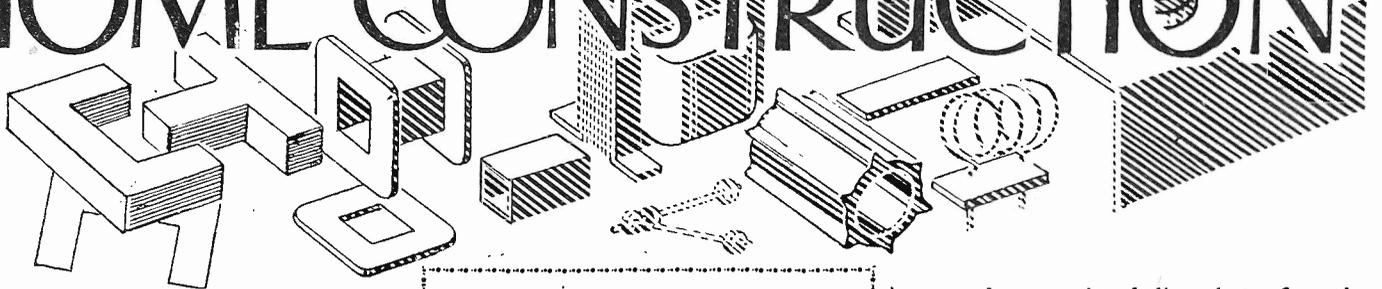

WE hope that you have by now been able to make the coil, reaction condenser, and wave-change switch, for which details were given last week, and trust that no difficulty has been experienced in carrying out the interesting work. Now we must push on and deal with the fixed grid condenser, grid leak, H.F. choke, and on-off switch. Actually, a valve-holder is needed in addition to the components just mentioned, but most readers will prefer to buy that as a ready-made job, since it costs only a

In this Second Article of the New Series the Authors Describe the Construction of the Remaining Parts Required for the Single-valve Home-made Receiver

by The Experimenters

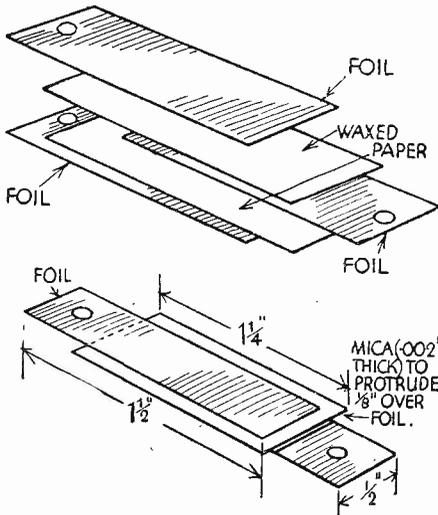


Fig. 1.—Dimensions of the foil and mica for the fixed grid condenser are given in this drawing. Above is shown how the sheets of foil and dielectric are interleaved.

matter of pence, and cannot be made very easily if the sockets are to be a perfectly good fit with the valve pins.

### The Grid Condenser

The grid condenser should be considered first, bearing in mind that this component should have a capacity of approximately .0003 mfd. The exact value is by no means critical, but it is possible to work to fairly close limits if the size of the plates, thickness of the dielectric material, and the dielectric constant are known. You probably think that the last remark means that the accurate capacity could be obtained by a physicist equipped with a variety of measuring instruments and having access to an extensive laboratory; anyhow, you need not be discouraged, for we have cut out all the theoretical work for you and simply say that the correct capacity can be obtained by using two plates of tin or copper foil measuring

1 1/2 in. by 1/2 in. with a sheet of mica measuring 1 1/4 in. by 1/2 in. separating them. As a matter of fact, this assumes the thickness of the mica to be just two-thousandths of an inch, but this is no need to take micrometer measurements. If you have any difficulty in getting hold of the mica you can use thin waxed paper instead, the paper being not much more than tissue thickness. When this is used it is necessary to have about six sheets of foil with a sheet of waxed paper between each (because waxed paper has a lower dielectric constant than mica); the foils (condenser plates) and strips of waxed paper (dielectric) are arranged as shown in Fig. 1.

Just a note about the waxed paper; if you cannot find a piece of suitable material ready for use, just take a short end of clean candle, place it in a small jar, and immerse it in a bath of hot water. When the wax is quite molten put a sheet of thin, soft paper into it and allow it to remain for a short time until thoroughly soaked. After that, lift out the paper and let all the superfluous wax drain off. When the wax has become quite cold the separate sheets can be cut out and the condenser assembled. The method of assembly is shown in Fig. 2, where it can be seen that the set of plates and dielectrics are placed together on a small ebonite sheet fitted with terminal holes, after which washers and nuts are securely tightened over the ends of the foil strips.

### An Ebonite Baseplate

Before mounting the condenser proper on to the baseplate, however, care must be taken that the plates and dielectrics are all pressed firmly together. To ensure this when using mica dielectrics it is best to brush a little *very thin* shellac varnish over each surface of the micas, place the foils in position, and then place the whole assembly under a heavy book, leaving overnight until the varnish sets perfectly hard. When using waxed paper there is

no need to apply shellac, but after the plates have been interleaved the condenser should be tightly pressed with a *warm* (not hot) iron. When the wax has properly cooled the condenser can be mounted on the baseplate.

### Making a Grid Leak

So much for the condenser; and now for the grid leak. This requires to have a resistance of about 2 megohms, but again the exact value is not at all critical. The best and simplest arrangement is that shown in Fig. 3, where a strip of ebonite of the dimensions indicated has a wide pencil line drawn on it. Before making the line the surface of the ebonite should be roughened slightly by rubbing it with fairly fine glasspaper, and the two holes shown should be drilled. Then take a "B" pencil and scribble a ring round the terminal holes, afterwards joining the two rings with a line 1/4 in. thick. Apply a fair pressure with the pencil, and go over the line a few times until there is a little graphite dust loose on the surface. Then knock off the dust and fit the terminals, placing a large washer between the nut and the pencilled circles. The resistance between the two terminals will now be just about correct, but the graphite might be rubbed off when the leak is in

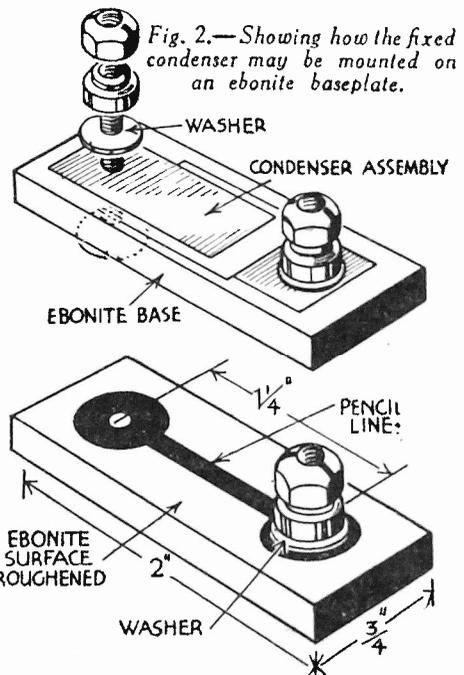


Fig. 3.—The lower sketch shows how the grid leak is easily made.

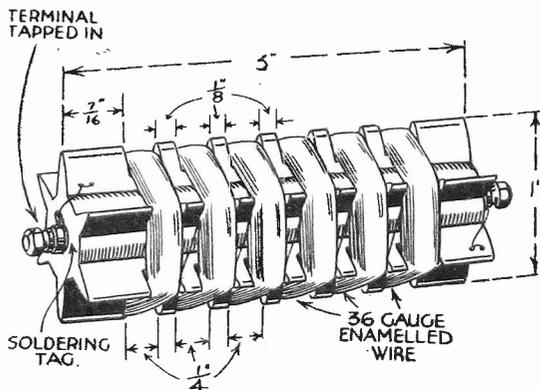


Fig. 4.—Constructional details are given here for the H.F. choke.

use, or alternatively the resistance might vary due to the formation of moisture on the surface of the ebonite. To prevent either of these eventualities the ebonite should be given a couple of light coats of shellac or other varnish.

**The H.F. Choke**

We have agreed to buy a valve-holder (if there aren't already several spare ones in the junk box), so we can now look to the high-frequency choke. This should have a fairly high inductance if it is going to be of any real value, whilst its self-capacity should be as low as possible. Because of this it is best to divide the winding into a number of separate sections. This can most easily be done by placing the windings on a length of lin. diameter ribbed coil former, after slots have been made in the ribs in the same way as in the case of the coil described last week. The handiest type of former for the purpose is "Becol" No. 2, which has a 1/4 in. diameter hole running through the centre, and which costs 4d. for a 3 in. length, such as is required.

The arrangement of the six slots is shown in Fig. 4, where it will be seen that they are each 1/4 in. wide and about 1/8 in. deep. They can be made, as described in connection with the coil, by means of a file, a few broken hack-saw blades clamped together, or in a lathe. When either of the two former methods is to be used it will be found most convenient first of all to make a cardboard or metal template so that the slots in each of the six ribs will be in line and exactly the same distance apart. After the slots have been made, a terminal should be fitted into each end of the former, a soldering tag being placed under the first nut. The correct method of fitting the terminals, of course, is to tap the hole in the ebonite to the same thread as that on the terminal, but when a suitable tap is not to hand the job can be carried out quite easily by using an old terminal of the same size as those to be fitted. First file the end to a taper of square section, then warm the terminal in a gas flame and screw it into the hole, gripping it with a pair of pliers. After forcing it partly into the hole it might be necessary to give the terminal a second warming, but it should soon be possible to tap the hole in this manner for the required distance.

For the windings a little 36-gauge enamelled wire will be required; a 1oz. reel will be ample, and this can be bought from any good wireless shop, or from an electrician. Start by scraping the enamelled covering from one end of the wire, taking care not to cut it, and then solder this to one of the tags provided. Now commence to wind the wire into the first slot, placing the turns as evenly as possible and continue until the slot is full. Without breaking the wire continue to the next slot, winding in the same direction, and so on until all have been filled. Finally cut off the wire, scrape the end clean and solder to the second tag, so completing the choke. A slight refinement on

the method just described, and one that produces a more robust finish, is to solder a short length of thicker wire to the end of the 36-gauge material and use this for making connection with the tags, and winding it round the former for a few turns.

**The On-off Switch**

It is unnecessary to give full constructional details for the on-off battery switch, since this is almost identical with the wave-change switch described last week. The difference is that only two contacts are required, and therefore connection need

only be made to the two soldering tags under the screws tapped into the end of the ebonite base. Alternatively, one of these terminal points could be used, the second connection being made to the single screw which serves to anchor the end of the spring contact plate.

**Assembling the Components**

Now that all the components have been made they can be assembled on a baseboard or chassis and wired up. Most readers will prefer to use a chassis, and this can be made, as shown in Fig. 5, from a few pieces of 5-ply wood, or a metallised chassis can be bought ready made from Messrs. Peto-Scott. The valve-holder, coil, and a couple of small ebonite terminal strips can be mounted as shown, the two variable condensers, on-off switch, and wave-change switch being attached to the ply-wood (or ebonite) panel. The rest of the parts are placed beneath the chassis, the grid condenser and grid leak being mounted near to the grid terminal of the valve-holder, and the H.F. choke being suspended in the wiring.

The connecting wires, by the way, may consist of any form of insulated wire, although the type known as "push-back"—with which the insulation can simply be pushed away from the ends by means of the finger and thumb—will be found most convenient.

Many readers will wish to have until next week before completing the wiring and testing of the complete set, and so the drawing showing the simple connections required is being held over until the next issue, when notes on using the set, and also on adding a few refinements, will be given.

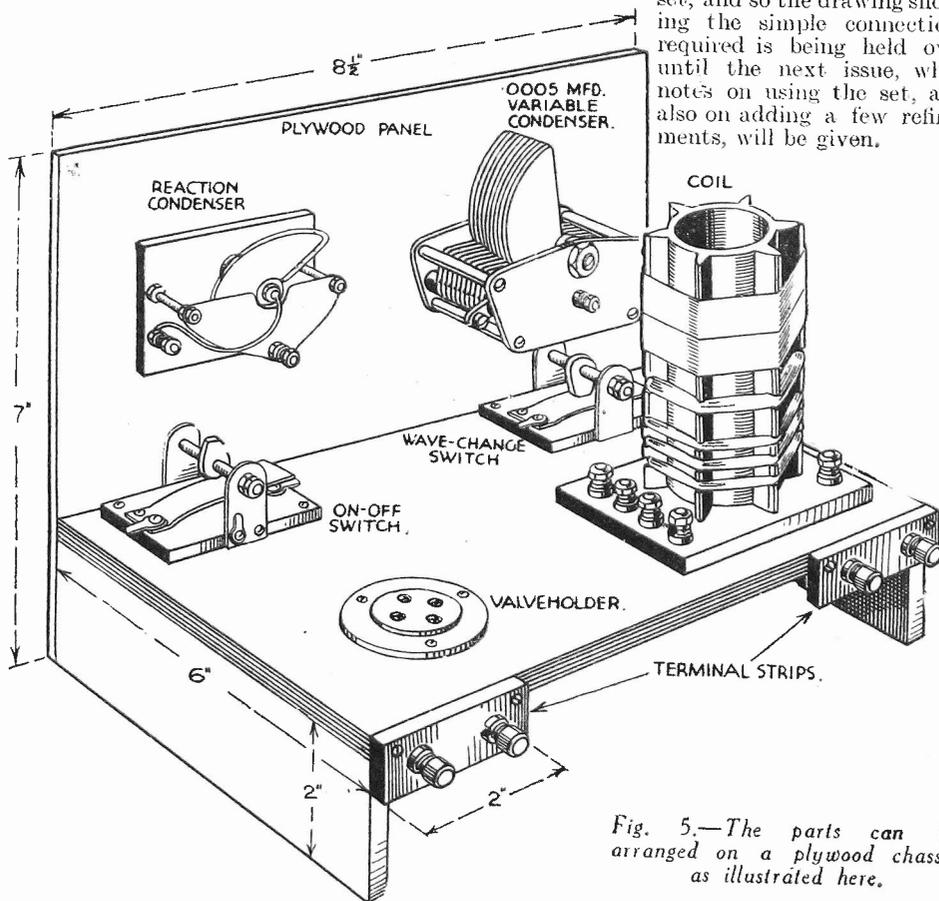


Fig. 5.—The parts can be arranged on a plywood chassis as illustrated here.

**New Weather Forecasts**

BY order of the Air Ministry, the Marconi Company will erect at the Cranwell (Lincolnshire) Aerodrome a telephony transmitter of which the sole service will be the broadcast of weather bulletins and warnings for aviators. When the station is ready for regular operation the Heston transmitter (1,202 metres) will close down and its duties taken over by Cranwell.

**BROADCASTING NOTES**

**Ultra-short Waves Replace Telephone Cables**

THE new ultra-short-wave service between Portpatrick and Belfast, via Ballygomartin, has proved an unqualified success inasmuch as it has greatly relieved the pressure on the long-

distance telephone traffic between Great Britain and Ireland. The Post Office has already installed five circuits and is using them to their utmost. Across relatively short distances, such as the Bristol Channel, ultra-short waves have proved invaluable. It is expected that a similar service will be shortly tried out with the European Continent, as the system is far less costly than the laying of cables.




# READERS' WRINKLES

THE HALF-GUINEA PAGE
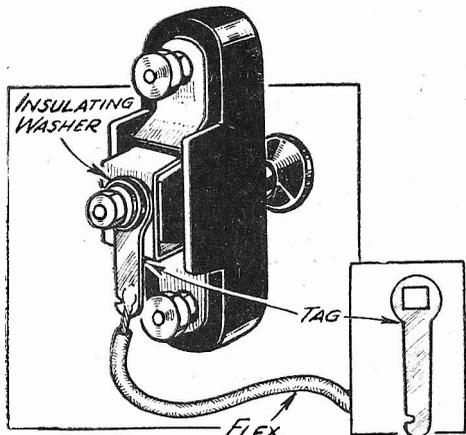
## A Simple Switch Conversion

HERE is a simple method of converting a two-point switch to a three-point one. First, remove the nut and washers holding the moving switch plate to the spindle of a non-rotating switch of the




A simple switch conversion.

type shown in the sketch. Place a large-size soldering tag, with hole filed square, over the spindle end, replace the insulating washer, ordinary washer, and nut, and tighten up. To the soldering tag solder a length of flex to suit requirements. The same method applies for converting a three-point switch to a four-point one.—R. M. ROSS (Alness).
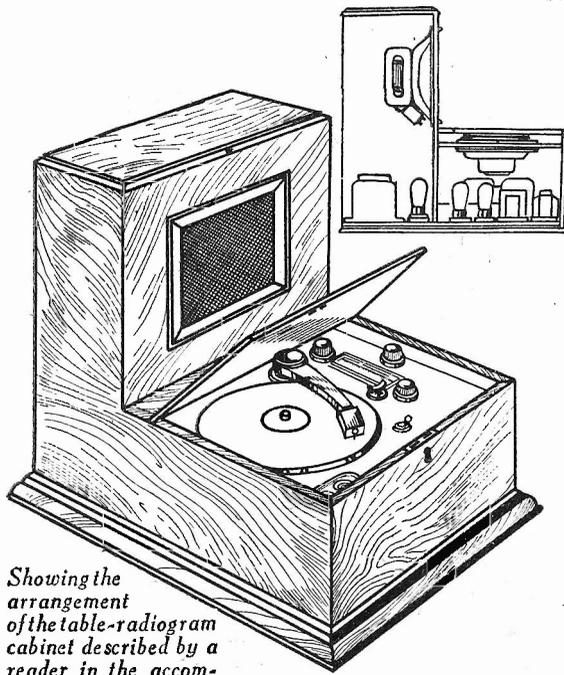
## A Novel Table-radiogram Cabinet

THE accompanying sketches illustrate an idea for a compact table-radiogram cabinet. The turntable, pick-up, controls, etc., after adjustment are totally enclosed by the top lid. The speaker of medium dimensions is housed in the top compart-



Showing the arrangement of the table-radiogram cabinet described by a reader in the accompanying paragraph.

## THAT DODGE OF YOURS!

Every Reader of "PRACTICAL AND AMATEUR WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay £1-10-0 for the best wrinkle submitted, and for every other item published on this page we will pay half-a-guinea. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL AND AMATEUR WIRELESS," George Newnes, Ltd., 8-11, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Radio Wrinkles." Do NOT enclose Queries with your Wrinkle.

ment, as can be seen, the front of which is made of thicker wood so as to act as a good baffle. Underneath, and at the bottom of the speaker is conveniently housed the rectifying unit or accumulator and H.T. battery, if a battery-operated set is used. There is ample room. The set is built directly under the controls, and the majority of the components are mounted on the right-hand side, whilst the gramophone motor is fixed underneath the motor board in the usual way.

A manual volume control is placed outside in the centre front, so that the volume may be adjusted without having to open the cabinet. The principal dimensions of the cabinet are: height 18in., length 22in., width 17½in. The height of the front part is 7in. The plinth may be built according to the maker's own taste, and a station chart, etc., may be placed underneath the lid, for quick reference.



I have made a cabinet to the dimensions given, in figured oak, and can thoroughly recommend it to any reader wishing to construct a very compact, efficient and convenient table-radiogram cabinet.—H. J. COLEBROOK (Sandwich, Kent).

## A Condenser Switching Device

IT is sometimes found, when using a dual-range coil, that although reaction on medium waves is quite satisfactory, the set fails to oscillate on long waves. This is probably due to the capacity of the reaction condenser being too small for this waveband, and a method of overcoming the difficulty is illustrated in the accompanying sketch. The wavechange switch, in the long-wave position, presses against a small block of ebonite fixed to a metal strip which, in turn, makes contact with another metal strip, thereby placing the .0002 condenser in parallel with the reaction condenser. For convenience, the theoretical circuit is also shown, as, in the event of a different type of circuit being used, slight modifications may be necessary in the assembly.—F. C. BIDDLECOMBE (St. Margarets).

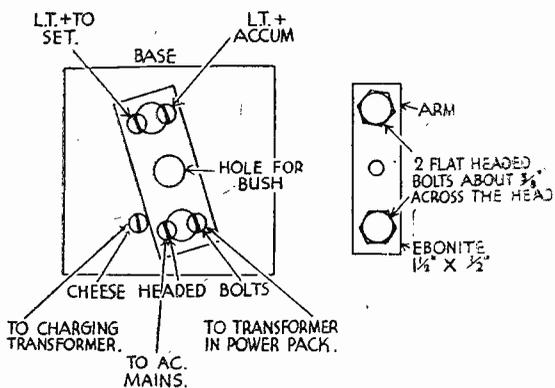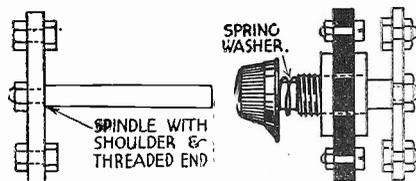
## A Five-point Switch from Junk

THE accompanying sketches show a five-point switch I have just constructed out of junk. I am using it to switch the power from the power-pack to the charging transformer, and also to break



A five-point switch made with odds and ends.

the connection between the L.T. and the valves in one operation. It is fool proof because the valves cannot be switched on when the accumulator is charging. The parts required are:—1 piece of ebonite 2in. square, 5 cheese-headed bolts about ¼in. long, 1 piece of ebonite 1½in. long by ½in. wide. The bush and spindle out of an old push-pull switch, or out of an old reaction condenser, and a suitable knob will also be required. The accompanying sketches show clearly how the parts are put together, the small bolts being arranged so the heads of the larger bolts will bridge two of them in one position.—J. PICOT (Rochester).

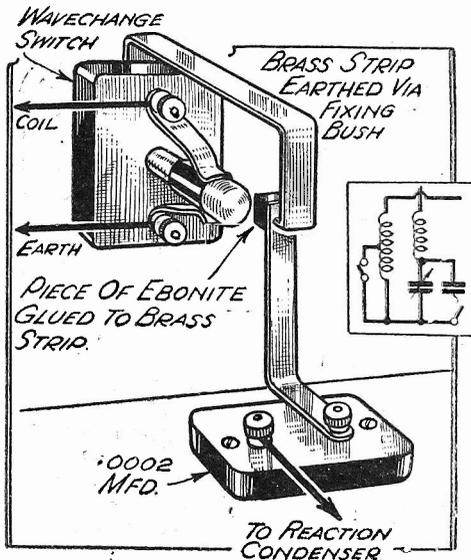

A condenser switching device.

READERS' WRINKLES

(Continued from previous page)

Slotting Ribbed Formers

I NOTICED a rather ingenious method of marking a coil former with a steel dog-comb in the issue of PRACTICAL

SHOWING COIL WOUND BY DOG COMB METHOD

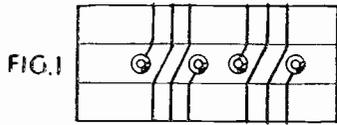


FIG. 1

SHOWING REGULAR TURNS USING STRIP OF PAPER

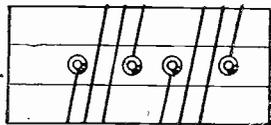


FIG. 2

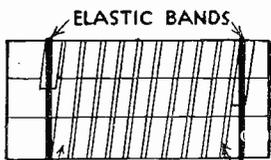


FIG. 3

STRIP OF PAPER SPACE FOR SAWCUT


A simple method of slotting ribbed formers.

WIRELESS for January 12th, but the saw-cuts made between the teeth of the comb run parallel to the end of former, and when winding a coil to work on the 15-metre band, on which the windings are approximately  $\frac{1}{4}$  in. apart (say, taking two teeth for each saw-cut) the finished coil appears as shown in Fig. 1.

To obviate this, an expedient method of marking a former is to cut a strip of paper with a knife and straight edge, the width of the strip being made according to the distance between the windings desired. Wind the paper strip on the former, leaving sufficient space between each turn to receive a saw blade, and anchor both ends of the strip by fixing an elastic band on each end of the former, as in Fig. 3. The cuts with the saw blade can now be made between each turn. A coil wound by using this method would appear as shown in Fig. 2. Any irregularities in the windings of a short-wave coil are, of course, apt to cause fading.—F. W. RITCHIE (Macduff).

A Simple Grid Leak

THE following method of quickly making a grid leak may interest the wireless constructor who likes to make his own components. It is really practical, is easy to make, and when completed has a real commercial-looking appearance. To make the grid leak, drill a small hole at each end of a piece of  $\frac{1}{4}$  in. dowel rod which is about  $1\frac{1}{2}$  in. long. Having done this, draw a thick line in Indian ink, or with an H.B. pencil, from one hole right along the dowel rod, to the other hole. Now screw two small terminals into the holes drilled in the rod and the grid leak is complete. Its resistance will be about two megohms, but, of course, by drawing two ink or pencil lines on the rod, its resistance may be varied as required.—G. R. WILDING (Liverpool).

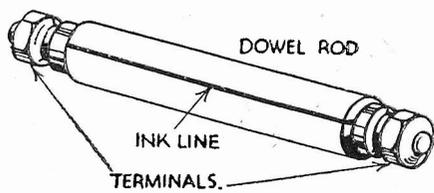


An easily-made grid leak.

Rejuvenating Faulty Condensers

WHEN large condensers of the wax-paper type begin to leak badly they need not be discarded. They can quite easily be rejuvenated by the method described below, after which they will last for a considerable time. A leak is usually caused in a condenser by damp having caused the insulating paper between the plates to become conductive. It is thus necessary to remove this damp, and at the same time to re-insulate.

The top of the condenser may be removed by re-heating the solder, at the same time keeping the whole condenser slightly warm so that the contents slip out easily once the top is removed. When this is done the top is taken off the wires, leaving what looks like a roll of paper with a covering of wax. This is now placed in a tin or can, which must be clean, and gently heated. Bits of clean candle are then added until the condenser is submerged in a bath of molten wax. A piece of thin wood should be placed over the can and the condenser suspended in the wax so that the paper may not be burnt against the hot sides. The heat should then be increased slightly until bubbles are seen coming from the condenser, and when the

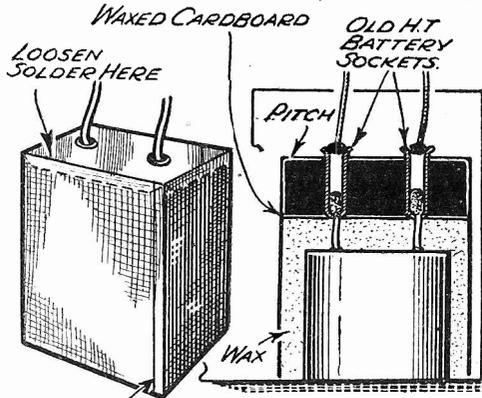


JOIN ALONG CASE WHERE AIR GAPS MAY EXIST

A method of rejuvenating faulty condensers.

bubbles have ceased, the can and contents are removed from the source of heat. The container of the condenser may then be examined for holes, which should then be soldered. The condenser is then lifted out of the wax, placed in its container, and molten wax poured in until the level is as shown in the sketch. A piece of stout cardboard is then waxed and cut into shape, and placed on top of this, two holes being made for the wires to come through. Slightly warmed pitch is then stuffed and packed in tightly after the wax has become cool and firm. This layer should be put on carefully so that no air is admitted to the condenser. The wires are then ready for soldering to the set. If preferred, two sockets from an old H.T. battery can be inserted and soldered to the wires before putting in the pitch. Wander plugs can then be used to connect up.—J. DIAMOND (Greenock).

A Polarity Indicator

A USEFUL polarity indicator, or general-utility current detector, can easily be made from material in the scrap box. The illustration shows the simple construction of the instrument. A wire of moderate resistance is stretched between the terminals A and B beneath a card on which is mounted a compass needle. The card is marked as shown in the sketch. This marking is the most important part of the construction. Four small stops are provided to prevent too violent movement of the needle when the instrument is in

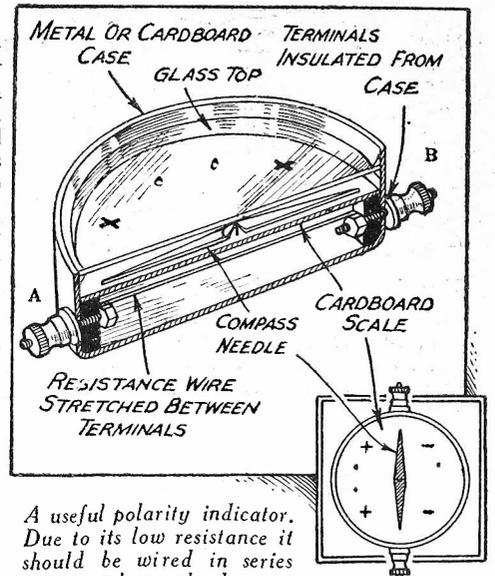


A useful polarity indicator. Due to its low resistance it should be wired in series with one lead.

use. The operation of the instrument is as follows: The case is turned until the needle lies over the one drawn on the card. The wires of unknown polarity are then touched against A and B when the needle at once swings to indicate the polarity of A and B. As previously mentioned, this simple instrument may also be used as a current-detecting device. For small currents the card may be calibrated by means of a standard instrument to read in milliamps. Other possible uses will probably occur to the reader. If any reader does not understand the principle underlying the instrument, it may be noted that it is based on Oersted's Experiment and Ampere's Rule.—H. F. DICKIE (Taunton).


A Handy Coil Former

A HANDY coil former, with connections for tappings, can be made as follows: Cut a square piece of wood or ebonite, about 2 in. square, and a circular piece 2 in. in diameter. Four pieces  $\frac{1}{4}$  in. by  $\frac{1}{4}$  in. by  $\frac{1}{4}$  in. will also be required. Fix the parts together, as shown in the sketches, the square piece for the base, the round piece for the top, the four pieces at each corner, and another piece about 4 in. by  $\frac{1}{4}$  in. by  $\frac{1}{4}$  in. along the middle of one of the sides, as shown. This piece forms the terminal strip.

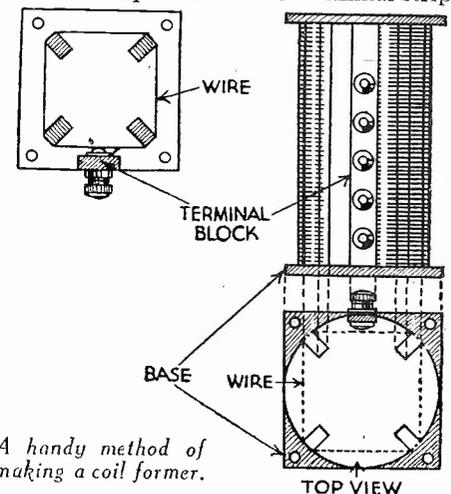

A handy method of making a coil former.

To save filing grooves to take the wire at each corner, four  $\frac{1}{4}$  in.-diameter screwed rods can be used instead of the four pieces of wood. These rods should be covered half way round with insulation tape, where the wire rests, the tape being pressed into the threads of the rod to form the grooves. Finally, bore four holes in the projecting corners of the base, for screwing to the baseboard.—J. S. WATTS (Bristol).

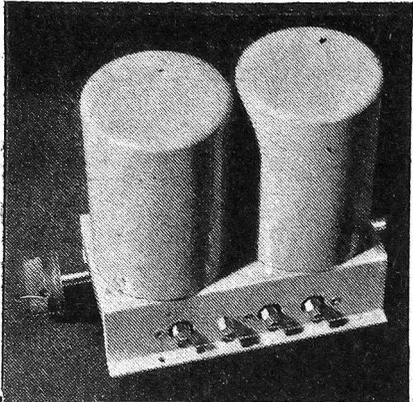

**THE  
'MAKING'  
OF THE  
HALL-MARK  
4**

**—demands Colvern Coils and only Colvern**

To "make" this brilliant receiver employ Colvern Coils—as specified solely by the designer. The tremendous care with which they are made, and the repeated tests to which Colvern Coils are put, ensures the most outstanding results possible. Make no mistake—fit Colvern. As specified for the HALL-MARK 4:—One 2 Coil Assembly Type T.D.S. 15/6 per pair.

● Write to-day for latest Colvern Booklet. *Gratis and Post Free on request*  
**COLVERN LTD., ROMFORD, ESSEX.**

**COLVERN**

Helpful Books for the Practical Man

The  
**Home Mechanics**  
Series

Price 1/- net each; by post 1/2 each

**THE HOME WOODWORKER**

The various examples of wood-work described in this Handbook have been designed by practical craftsmen. They are modern in style, and their construction is well within the powers of the average home-worker who follows the instructions given.

**25 SIMPLE WORKING MODELS**

All the models described in this book can be constructed from the simplest materials and with very modest equipment. None requires lathe-work. 147 illustrations.

**TOY MAKING FOR AMATEURS**

Over 200 illustrations. Instructions and diagrams are given for the construction of innumerable toys of all kinds, from the simplest to the more complicated mechanical sorts.

**SIMPLE ELECTRICAL APPARATUS**

Interesting and useful apparatus, easily constructed, with which the student is enabled to test for himself the theory and practice of Electricity as laid down in the text-books.

**MOTOR CAR OVERHAUL AND UPKEEP**

Many, by undertaking their own repairs, can afford to run a Car, and it is the purpose of this handbook to show how the Owner-Driver may carry out most of the adjustments and repairs which every Car sooner or later needs.

**ACCUMULATORS**

An Accumulator (whether for Wireless or the Car), if properly used and cared for, is an extremely reliable piece of apparatus. This book shows how to get the best out of it.

Send post card for full List

From all Booksellers, Newsagents, etc., or by post, 1s. 2d. each from the Publishers:—

**GEO. NEWNES, LTD., 8-11, Southampton St., Strand, W.C.2**

Geo. Newnes, Ltd.



*"I've bought a Blue Spot Speaker  
For my rich Uncle Bill,  
So now I can be sure of  
A place in Uncle's Will"*


Leslie knows how many beans make five. When he heard his uncle cursing the wireless, he slipped out and bought him a new Blue Spot "Star" Loudspeaker. Was uncle pleased? He was. Who wouldn't be delighted to have his radio entertainment made crisp and clear and true with every word and note perfect instead of sounding as though it were being strained through wire gauze. Get a Blue Spot Speaker for your set and see what a difference it makes.

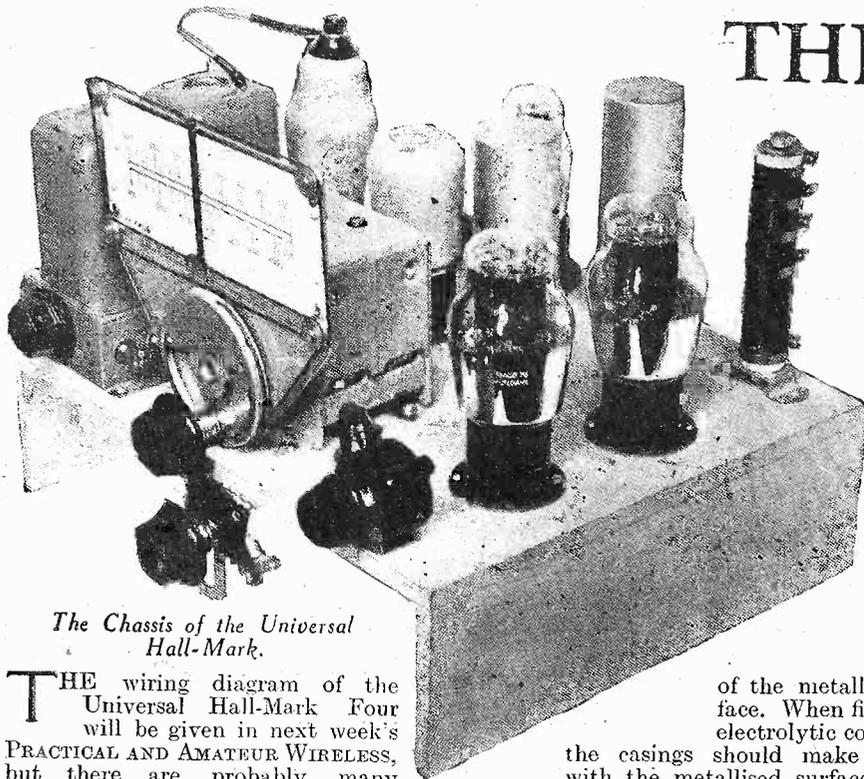**SEND FOR LOUDSPEAKER PAMPHLET No. P.R.4.**



**THE BRITISH BLUE SPOT COMPANY, LTD.,**  
Blue Spot House, 94-96, Rosoman St., Rosebery Ave., London, E.C.1. Telephone: CL Erkenwell 3570.

Distributors for Northern England, Scotland and North Wales: H. C. RAWSON (Sheffield and London) Ltd., 100 London Road, SHEFFIELD; 22, St. Mary's Parsonage, Manchester; Strawberry Lane, Gallowgate, Newcastle-on-Tyne; 37, 38, 39, Clyde Place, Glasgow; 45, Springbank, Hull.



The Chassis of the Universal Hall-Mark.

THE wiring diagram of the Universal Hall-Mark Four will be given in next week's PRACTICAL AND AMATEUR WIRELESS, but there are probably many receivers who prefer to build their receivers from the theoretical diagram, and therefore, this week, we propose to give you a few advance constructional details. Most of the instructions for the A.C. Hall-Mark also apply to the universal model, but there is one point that must be particularly stressed in connection with the latter. The earth lead must not be connected to the metallised surface of the baseboard, as this procedure might possibly cause a mains short-circuit in cases where the supply is D.C. with the positive mains lead earthed. For the same reason a condenser is connected in the aerial lead. This component is the pre-set condenser C3, and in addition to insulating the aerial, it may be used for controlling selectivity, in cases where the receiver is used in close proximity to a transmitting station.

A 1½ in. drill should be used for V1, V3, V4, V5 and rectifier valve-holders, and a ½ in. drill for V2 holder. As in all receivers employing a Metaplex chassis, care should be taken to keep the valveholder pins clear

#### LIST OF COMPONENTS.

One 2-gang set coils, types Q and T.—Wenrite.  
 One 2-gang .0005 mfd. midget condenser with type V.P. drive with wavelength scale (C1, C2)—Polar.  
 One .00015 mfd. reaction condenser (C3)—Graham Farish.  
 Four .5 mfd. fixed tubular condensers (C6, C11, C14, C15)—T.M.C.  
 Two 1 mfd. fixed tubular condensers (C4, C5)—T.M.C.  
 Three .05 mfd. fixed tubular condensers (C20, C21, C22)—T.M.C.  
 One .0001 mfd. fixed tubular condenser (C7)—T.M.C.  
 Three .0002 mfd. fixed tubular condensers (C9, C12, C13)—T.M.C.  
 One 2 mfd. fixed condenser (C10)—T.M.C.  
 Three 25 mfd. electrolytic condensers (C8, C16, C17)—Dubilier.  
 Two 8 mfd. electrolytic condensers (C18, C19)—Dubilier.  
 One .0003 mfd. pre-set condenser (C23)—Formo.  
 Fourteen fixed resistances, 30,000 (R2), 25,000 (R1), 2,000 (R5), 500,000 (R6), 20,000 (R8), 30,000 (R9), 1,000 (R7), 250 (R12), 250 (R13), 50 (R15), 50 (R16), 10,000 (R10), 10,000 (R11), 200 (R3)—Graham Farish.  
 Two potentiometers 2,000 ohms, type V.C.26 (R4) and 5,000 ohms, type V.C.29 (R14)—Bulgin.  
 One Mains dropping resistance (R17)—B.T.S.  
 One snap H.F. choke—Graham Farish.  
 One L.F. choke H.T.11—Wright and Weaire.  
 One Input push-pull transformer type D.P.36—Varley.  
 Three potentiometer brackets—Peto Scott.  
 One Mains on/off switch, type S.80—Bulgin.  
 Five valveholders, 4, 7-pin, 1, 5-pin—Clix.  
 Two .5 amp mains fuses—Microfuse.  
 One mains lead and plug—Belling and Lee.  
 Five valves, types H.P.2118, R.2018, P.P.4118, P.P.4118, P.V.3015—Tungsram.  
 One loudspeaker, type F.R.7. F.M.24—Rola.  
 One Metaplex chassis—Peto Scott (12 x 10 x 3½ ins.).  
 A.E. strip and plugs—Belling Lee.  
 One Hall-Mark Four cabinet.

# THE UNIVERSAL HALL-MARK FOUR

Further Constructional Details and Wiring Diagrams Next Week!

diagram will be given in next week's issue of PRACTICAL AND AMATEUR WIRELESS.

#### Using a Pick-up

As this receiver has an undistorted output of approximately 6 watts it is very suitable for gramophone reproduction. Constructors who do not wish to fit a radiogram switch need only fit a pick-up strip at the back of the chassis, and connect the

#### SPECIAL FEATURES OF THE UNIVERSAL HALL-MARK FOUR

Suitable for all A.C. or D.C. Mains.  
 Large Output—6 watts maximum.  
 Wavelength—Calibrated Dial.  
 Smooth Control of Volume.  
 Absence of Mains Hum.  
 Absolute Safety in Use.

of the metallised surface. When fitting the electrolytic condensers the casings should make contact with the metallised surface of the baseboard, as the casing is the negative terminal of this type of condenser.

#### Mounting the Volume Control

The bracket for the volume-control potentiometer should contact with M.B., but great care should be taken when screwing down the reaction condenser bracket. It is important that the screws do not pierce the metallised surface of the baseboard as this would result in a short-circuit of the reaction winding.

As the smoothing choke partly covers one of the output valve-holders, it will be advisable to fix this component after the valve-holder wiring has been completed.

#### The Mains Dropping Resistance

This component should be wired to suit the mains supply voltage. The heater pin of V3 should be connected to the lower terminal of the resistance for all supply voltages, but C22 and the fuse terminal should be connected to the second terminal (viewed from the bottom end of the resistance), for a voltage of 200 to 205, to the third terminal for 220 to 230 volts, and to the fourth terminal if the voltage is 240 to 250.

#### Speaker Leads


The three loud-speaker leads should be soldered to the tags on the Rola speaker transformer, the outer leads (from valve anode) being fixed to the outer tags, and the lead from C18 to the centre tag. A word of warning can be added concerning the speaker. This has a specially selected push-pull transformer attached, and if best results are desired, this must not be substituted. The push-pull valves have an undistorted output of approximately 6 watts, and therefore a small speaker would be hopelessly overloaded.

Further details of this receiver—including trimming and adjusting instructions—and a wiring

grid of the R2018 (V2) valve via a .5 mfd. condenser to one of the sockets, and the other socket via a .5 mfd. condenser to the metallised surface of the baseboard. When gramophone reproduction is desired the pick-up leads should be plugged into the sockets, and the volume control on the receiver set at minimum in order to prevent the radio signals from passing to the detector valve.
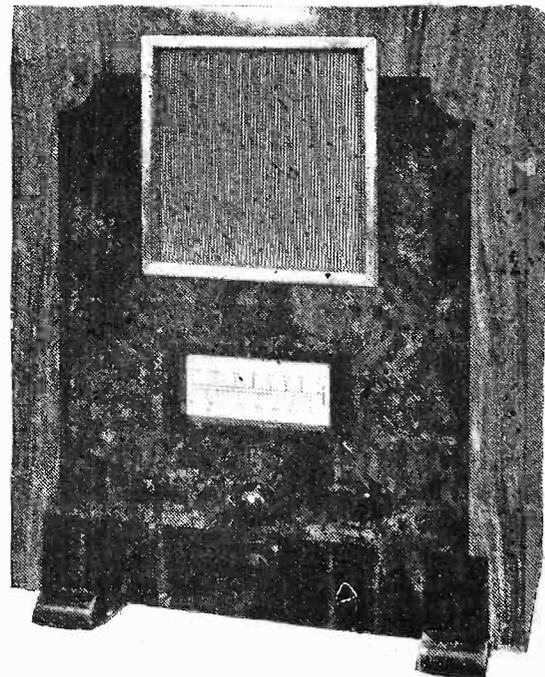
#### Microfuses Ltd.—Change of Address

Readers should note that the address of Microfuses Ltd., makers of the fuse specified for the Hall-Mark receivers, has been changed to 4, Charterhouse Buildings, Goswell Road, London, E.C.1.



Here is the Universal Hall-Mark in its attractive cabinet.

# On Your Wavelength

by Thermion

## The Modern Tower of Babel

**M**OST of my readers will be acquainted with the verbose and tergiversatory circumambulation (!) of Dr. Johnson, who, in compiling that ridiculous first English Dictionary, really wrote a satire on the human race. His definition of patriotism, for example, was "The last refuge of a scoundrel"! In his lives of the poets, the following phrase occurred:—

"Let observation, with extensive view,  
Survey mankind from China to Peru."

I expect you will also be aware of Coleridge's scathing comment on this: that it really meant "Let observation with extensive observation observe mankind." Now lexicography has been, with me, a *bele noire* ever since I learned to read. I have always been irritated by the fanciful imaginations of those who compile our dictionaries and merely hazard guesses at the derivation and pronunciation of some words. Too long has it been anybody's job to produce dictionaries of the English language. I have no doubt that if a Welsh scholar were given the opportunity to compile an English dictionary it would be smothered with Welsh words and Welsh pronunciations, and really be a piece of veiled propaganda for the Welsh race. In other words, a Welshman (where doubt existed regarding the origin or pronunciation), would quite naturally be tempted to give it to the Welsh. The same argument applies (perhaps with greater force) if you placed the job in the hands of a Scot. A language belongs to a nation, and not to particular individuals, and as such the compilation of a dictionary should be a government job. There is no standardisation about language at all. Anyone can publish a dictionary and invent any sort of pronunciation, word, or meaning, at variance with all the other dictionaries. Once it is in print it has the authority of the printed word. You may observe from this the point to which I am leading. The B.B.C. has its own committee on words and their pronunciations, which I think is all to the good. I do not know the members of the committee or their nationality, but it would be comforting to know that it does not intend to make an effort to upset pronunciations of words on which almost all dictionaries agree. As an Englishman, I am always careful in my choice of dictionaries. I prefer them to emanate from an English publisher and to have been compiled and edited by Englishmen. Confusion will be worse confounded if, in addition to our dictionaries, we are to have a radio dictionary as well. Do you agree? My "Shorter Oxford" is a treasured possession.

## Where Are the Aerials?

**I**T does not seem so many years ago since part of the divertisement of my daily journey to town consisted of observing the various types of aerials and counting the weekly increments. Latterly, I have watched their gradual decline as, paradoxically enough, the number of radio sets has increased. On my twenty-five-mile journey I can now count six aerials where formerly they were uncountable. This is silent tribute to the increased efficiency of modern valves and wireless receiving apparatus. It spells the death of the

outdoor aerial, with the possible exception of those small and neat commercial aerials which in most cases are more efficient than indoor aerials, and are also of great use in rooms where an indoor aerial is impracticable. Ten years ago there were dozens of different (and indifferent) types of outdoor aerials—unsightly-looking contraptions which did much to retard the progress of radio because people would not spoliolate the appearance of their suburban chateaux. A modern receiver does not require a long outdoor aerial.

## Fading

**N**ONE of my quondam critics will disagree with me when I state that fading has nothing to do with the receiver. It is purely a transmitting problem, and as such I have always contended that it should be solved at the transmitting end. I do not see why I or any other listener should buy expensive apparatus in the form of A.V.C. units and equipment, merely to get over a problem which comes strictly within the domain of the designers of transmitting apparatus.

Whatever form of A.V.C. is fitted means a loss of efficiency in the receiver. It would be just as sensible for car manufacturers to make all of their cars to suit one-legged drivers because a few people are deprived of one of their limbs. My advice to commercial set designers is this: Supply your receivers without A.V.C.



Members of the staff of Whiteley Electrical Radio Co. Ltd., at the annual works dance recently held at Mansfield.

A station which fades is not worth listening to, anyway, and if customers had the point carefully explained to them, they would not require to listen to a station on which fading is consistently bad. There are other reasons I know which cause fading, and which are quite outside the ken even of the transmitting engineer; but even so, I contend that it is not a problem to be tackled at the receiving end. I always believe in tackling the cause rather than the effect!

## A Precocious Schoolboy

**I** AM reminded of the old quotation:—  
"And still he spoke, and still the wonder grew,  
That one small head could hold one half it knew."

by the correspondence I sometimes receive from schoolboys. If, in my urge to feed our panting printing presses I fail to cross an i or dot a t, I am certain to be reminded of it in a voluble fashion from a callow youth in his early teens; which is all to the good, keeps me up to the scratch and all that, and reminds me of the fact that a journalist should write for those who don't know rather than for those who do. The former class will learn something whilst the latter will have their knowledge confirmed and regard the contribution purely as an *aide memoire*. I am always pleased to hear from schoolboys and to advise them. We are apt to forget that a new generation of home constructors enters our ranks every year, and we must not hence shirk the irksomeness of going over the same old ground.

## The £5 Three-valve Superhet

**I** AM always an unwelcome visitor to the PRACTICAL AND AMATEUR WIRELESS laboratory. On those occasions, however, when I pry into that holy of holies, I make it my business to ask the why and wherefore. The other day, a reader had called to make an inquiry regarding the £5 Superhet., out of which he couldn't get a note. One of the technical assistants had connected an oscillator to his receiver, and was

busy trimming the I.F. transformers. Within five minutes the receiver burst into life, and it was, indeed, a pleasant thing to watch the barometric change on the reader's face—from extreme gloom to the apogee of pleasure! I imagine from the conversation that he had ignored every instruction regarding matching and trimming, and had turned every knob and screw willy nilly, with the net result that he was entirely lost. He walked away another

(Continued overleaf)

(Continued from previous page)

satisfied reader, paying glowing eulogies to the PRACTICAL AND AMATEUR WIRELESS service.

### Thanks!

MANY thanks to the many readers who have written to me messages of good will on the transference of my weekly platform. "On your Wavelength" has been a regular feature for many years, and some readers expressed the fear that the amalgamation of the two wireless journals comprised by PRACTICAL AND AMATEUR WIRELESS might see the demise of the feature. Not so! Your unworthy *Thermion* will continue to expatiate on sundry subjects and to hurl his weekly brick bats behind the comfortable anonymity of his pseudonym. Set your fears at rest. All the same, I blush at the soft impeachment!

### Anode Connections

I HAVE always loathed the terminal caps fitted to the top of screen-grid and similar valves, and have more than once had the misfortune to find them damaged. But last week I cursed them even more than usual, for they let me down badly just when I wished to demonstrate a new home-made receiver to some friends. The set was a battery-operated one, and I wished to employ the H.F. pentode from a portable that did good service last year. On going to the latter receiver, however, I found that the anode terminal was locked almost solid, presumably due to slight corrosion by fumes from the battery acid. A little hot water was run round the terminal nut, and this appeared to loosen it, but when an attempt was made to remove the terminal the whole cap turned round and parted company with the glass bulb. I blamed myself for my carelessness, and went to the nearest wireless shop to buy another valve. As soon as this was removed from its carton, however, it was discovered that the terminal cap on this valve also was loose—so loose, in fact, that I dare not touch the terminal. The result was that I could not demonstrate the new set after all, and since that time my name has been "mud" with my wireless friends. Some constructors have criticised the new form of metal cap connector, but I am all in favour of it—more so now than ever.

### Radio Relays

FROM information that is constantly reaching me, it appears that the wireless relay services that are in operation in various parts of the country are receiving increasing patronage. All those firms who are operating relay stations are reporting increasing business, and appear to be enjoying prosperous times.

I find it difficult to form a reason for this, since relay subscribers are limited to one or two programmes, and must accept whatever the engineer in charge prefers to give them in the way of entertainment. Although I am by no means an "ether-scourer" myself, I do like to be able to turn to the foreign stations once in a while, and, moreover, I frequently enjoy many of the broadcasts from European stations. Admittedly, the bulk of my listening is in connection with the local stations, but even so I often find pleasure in alternative programmes that are sometimes sent out by the Midland and North Regional transmitters. It is therefore hard to understand why other people—and there must be many thousands of them—can be content to have one, or perhaps two, programmes from which to choose.



## Notes from the Test Bench

### Fitting Variable-mu Valves

A READER who had built the PRACTICAL WIRELESS Leader Three decided to fit a variable-mu S.G. valve and an S.G. bias potentiometer control. He wired the earth end of the grid coil (terminal 3) to the centre terminal of the potentiometer in the usual manner, and connected a .1 mfd. condenser between this terminal and MB. Results were quite satisfactory on the long-wave band but he found that the control did not function on medium waves. This is rather a common fault, and is due to the .1 mfd. condenser being short-circuited by the wave switch when the latter is in the medium-wave position. The remedy is very simple; it is only necessary to connect a .1 mfd. condenser between the switch terminal of the coil (terminal 2) and the switch lead.

### Push-pull Output Circuits

WHILE testing an experimental receiver having two pentodes in push-pull, slight distortion was experienced; this was traced to the use of push-pull valves that were not exactly matched. To obtain the full benefit of a push-pull output stage, the same amount of current must pass through each half of the output transformer primary. When this condition exists, the magnetising effect of the direct current on the core is nullified because the direction of current flow in one half of the transformer primary winding is opposite to that in the other half. As it is difficult to obtain two pentodes that pass exactly the same value of anode current, experiments were conducted with various methods of equalising the consumption of the two valves, and it was eventually found that a very good control could be obtained by connecting the priming grids of the pentodes to the end terminals of a 5,000-ohm potentiometer and then joining the centre terminal of the potentiometer to H.T. A rotation of the potentiometer slider increases the voltage on one priming grid and at the same time decreases that on the other priming grid, thus affording the listener a simple means of equalising the anode current consumption of the valves.

### Aerial Volume Control

SOME S.G. receivers employing an S.G.-H.F. stage rely on the detector reaction condenser for volume control. This control is not sufficiently effective when the aerial is in close proximity to the transmitter, however. A .0005 variable condenser connected in series with the aerial lead will control the volume, but in most cases this also affects the tuning of the aerial circuit because its operation varies the aerial capacity effect. The following is a simple method of overcoming this effect: connect the terminal of the aerial series condenser to one end of a 50 turn winding of 34 S.W.G. wire wound on a small cardboard former, and connect the other end of the winding to the earth terminal. This former should then be placed inside the existing grid winding former, its best position being found by experiment. The required size of the extra former will be governed by that of the grid winding former—there should be a clearance of at least  $\frac{1}{4}$  in. between the two.

### Receiver Hire

PERSONALLY, I should have thought that those listeners who are not interested in making a set of their own, or who are not prepared to go to the expense of buying a high-class ready-made receiver, would much prefer to hire a set of reputable make from one of the many firms whose job it is to supply sets on hire terms. I know of several firms who are prepared to loan receivers for quite a few shillings per week, this charge covering all servicing and, in some instances, the replacement of the set by a new model after a certain period.

### Interference-proof Receivers

IT was with interest that I read the other day of an appeal made by the section engineer of the Birmingham P.O. Engineering Department to the Midland Radio Luncheon Club. His appeal was to the effect that radio manufacturers should make their receivers static-proof by fitting apparatus that would prevent the set from picking up electrical interference from outside sources. This, to me, seems all wrong, and in my opinion it is the makers of electrical machinery and fittings who should be called upon to fit suppressors to the appliances which they manufacture. It seems rather like "putting the cart before the horse" to allow electrical apparatus to be so designed and made that it constantly radiates interference, and then to attempt to suppress that interference when it is detected by the receiver. The argument in favour of modifying the set will probably be that the set came after the electrical machinery, but surely that is not a good excuse.

If I drive a car the exhaust of which emits an ear-splitting noise when the car is driven down the street, I am liable to be summoned for causing a public nuisance, and yet the maker of, say, an electric hair-dryer, that may be productive of equally ear-splitting noises in the loud-speakers of hundreds of receivers, gets away scot-free.


### Wireless Dealers

WHY is it that there is so much incompetence in the wireless trade? At various times I suppose I have been into hundreds of wireless shops, and on only very few occasions have I found that the owner or assistants had any more than a very nodding acquaintance with wireless theory and practice. In one particular instance I found a so-called service engineer carefully "testing" the various components of a simple three-valve battery set which "would not work." At the very first glance it was evident that the constructor of the set had made various "earth" connections to the wooden chassis—which was not metallised. And yet this engineer (?) was non-plussed, and could not understand why the set was so absolutely dumb! It is a pity that manufacturers of wireless components and receivers cannot institute some system whereby unqualified people would not be allowed to sell articles of which they have no knowledge. I do not suggest that intending traders and assistants should be compelled to pass a stiff examination, but if they were required to answer a few simple questions put by a competent person a large number of those who are in the wireless business to-day would be compelled to study the fundamentals—or else earn their living in some other manner. A test on these lines would be of considerable assistance to the wireless trade as a whole, and would certainly be to the advantage of the novice and beginner in home construction, as well as to the listening public in general.

# TRIMMING, MATCHING AND OPERATING THE
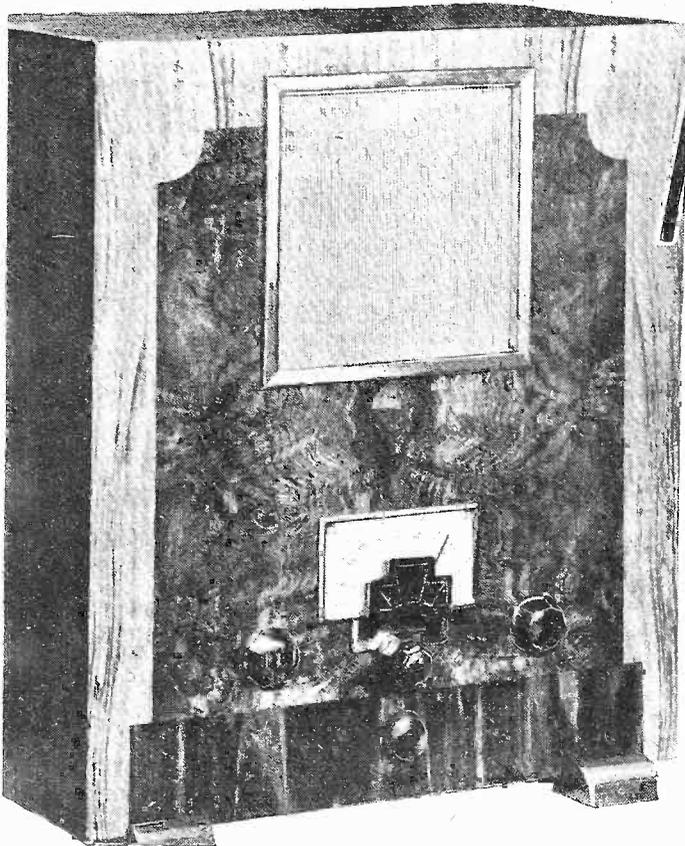
# A.C. HALL-MARK

Mr. F. J. Camm's Latest Mains Receiver. Battery and Universal Models are Described on Later Pages



satisfied that the receiver works directly you attach your aerial and earth to it. For this, of course, it is bound to do if the components and the wiring instructions have accurately been followed.

### Final Instructions

Before giving the final instructions, there are a few points regarding the construction to be given. For example, before mounting the ganged condenser and coils, be very careful to ascertain that the under-

neath surfaces of the components themselves are clean, as it is these surfaces which provide the earth-return path *via* the metallised Metaplex chassis.

### The Electrolytics

Another point: The bracket holding the reaction condenser must not be in contact with the metallised baseboard, and it is particularly necessary, therefore, to ensure that the screws holding this component to the chassis do not make contact with the metallised surface. I stress this point

### The Mains Switch

because I have found in the past that many readers who have failed to obtain successful results have used screws which have passed through and made contact with the metallised surface, thus in many cases completely blotting out signals.


The wiring of the electrolytics was mentioned in last week's issue, but as this cannot very clearly be shown on the blueprint, owing to their position, we would particularly emphasise that the casing of C15 (the inner condenser of the two) must not make contact with the metallised baseboard, and the two leads indicated on the sub-baseboard wiring diagram shown connected to the electrolytic condenser fixing nuts must pass through the condenser fixing hole and make good contact with the condenser casing.

**E**VEN at this early stage it is evident that some thousands of the A.C. Hall-Mark, with its quality and large undistorted output, are in process of construction throughout the British Isles. Aided by the free-gift blueprint which was given last week, the construction presents no difficulty at all and, as a fact, can be accomplished within a couple of evenings. The ample diagrams, instructions, and photographs also included with last week's issue make the position of every component and every wire crystal clear, even to the veriest beginner.

It is not possible to convey by means of diagrams the niceties of adjustments and the fineness of trimming and matching which make all the difference between obtaining perfect results and indifferent results. Even with the most expensive motor-car there are the adjustments to the carburetter, to the driving position, and to the ignition, which differentiate the article as it leaves the workshop from the well-tuned product as it reaches the purchaser.

A home-constructed receiver has that great advantage over the commercial product. It has all the sturdiness and reliability of the hand-made job and the almost incalculable advantage that it does not, like so many commercial receivers, present the appearance of the internals of a telephone switch-box when you remove the back to find out what has gone wrong.

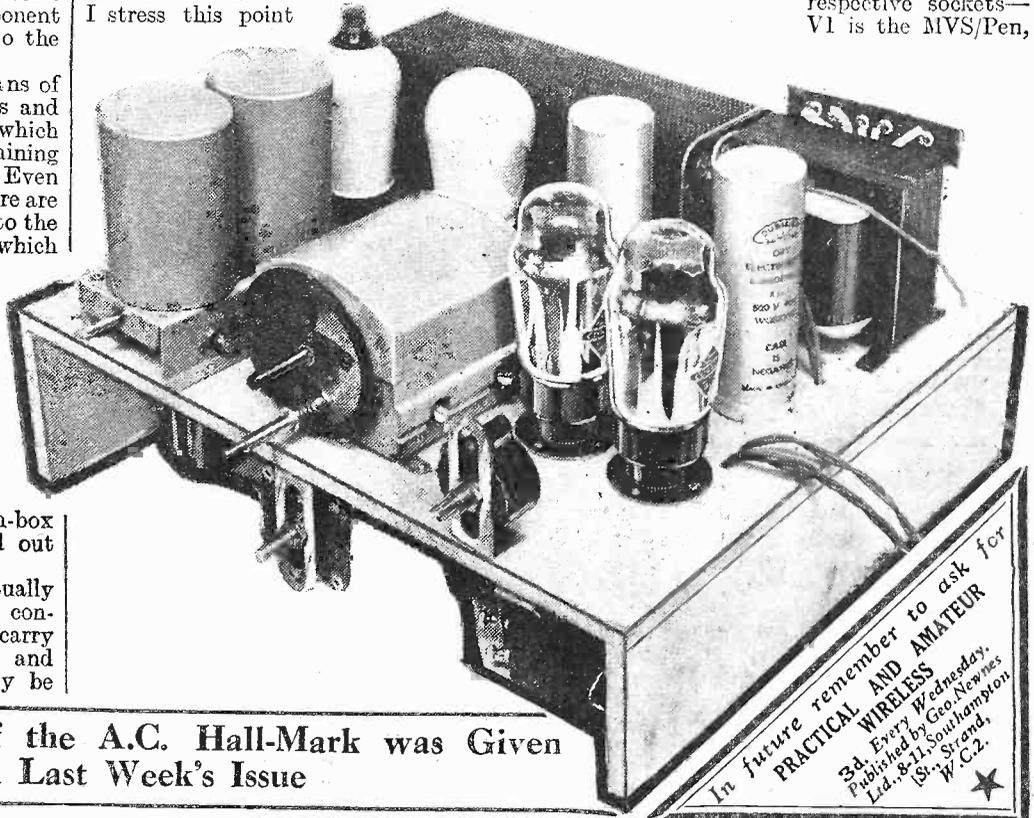
A receiver which you have actually made is known to you in all its constructional elementals, but you must carry out very carefully the matching and trimming operations, and not merely be



**A Full-size Blueprint of the A.C. Hall-Mark was Given Free with Last Week's Issue**

In future remember to ask for  
**PRACTICAL AND AMATEUR WIRELESS**  
 3s. Every Wednesday.  
 Published by Geo. Newnes,  
 Ltd., 8, 21, Southampton  
 St., Strand,  
 W.C.2.

## F. J. CAMM'S A.C. HALL-MARK

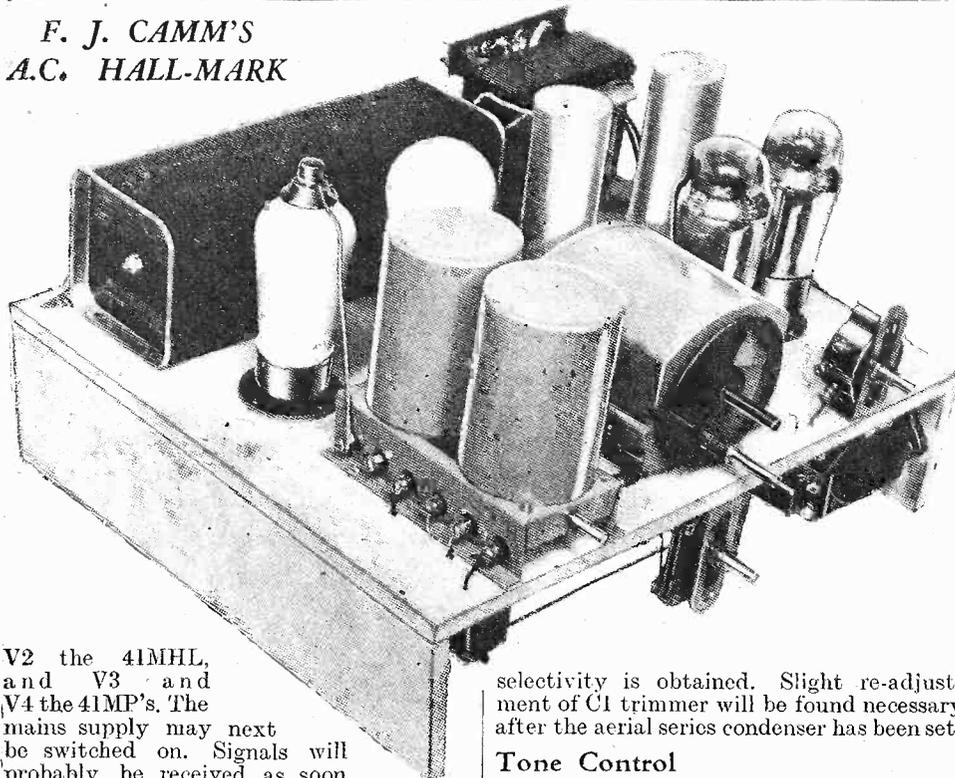

V2 the 41MHL, and V3 and V4 the 41MP's. The mains supply may next be switched on. Signals will probably be received as soon as the aerial and earth leads have been connected and the dial rotated.

Best results, however, cannot be expected unless the gang-condenser trimmers are carefully adjusted. Fortunately, the trimming of a double-tuned-circuit receiver can very easily be effected. First adjust the two trimmers to their mid-way positions. The local station may now be tuned in and the front section (C1) trimmer adjusted for maximum volume. A more distant station should then be tuned in and the two trimmers slightly readjusted for best results. The trimmer position should now hold for stations on all parts of the dial. If this is not the case, it indicates that the coils are not correctly matched.

### Selectivity Control

For best quality reproduction from the local station the reaction condenser should be set at its minimum position—this is done by rotating the control knob in an anti-clockwise direction—and volume should be controlled by means of the 2,000-ohm potentiometer. When listening to distant stations, however, sensitivity and selectivity may be improved by rotating the reaction condenser very nearly to its oscillation point. Those who live very near a transmitting station may find that the selectivity does not quite meet with their requirements, and therefore it is suggested that a .0003 pre-set condenser be connected between the aerial terminal and terminal I of the coil. The setting of this component may then be adjusted until the required degree of

selectivity is obtained. Slight re-adjustment of C1 trimmer will be found necessary after the aerial series condenser has been set.

### Tone Control

The condensers shown in dotted lines on the theoretical diagram may be added if more mellow reproduction is desired. These two condensers are connected between G and G.B. terminals of the push-pull transformer.


These tone-compensating condensers simply serve to attenuate the higher frequencies and have no other effect; that is, they do not reduce volume, and their value is sufficiently low to avoid any "boominess" or other unpleasant form of reproduction. As, however, many readers will prefer the rather "crisp" reproduction that the set normally provides, the condensers will not be required in all cases. Much depends upon the position of the loud-speaker and also on the furnishings of the room in which it is situated, for if there is a good deal of upholstered furniture this will itself tend to give a "mellowing" effect.

## LIST OF COMPONENTS

- One A.C. Hall-Mark Four Console Cabinet—Peto-Scott.
- One Metaplex chassis, 12 $\frac{1}{2}$ in.×12in. with 3 $\frac{1}{2}$ in. runners—Peto-Scott.
- One 2-gang variable condenser, complete with drive—Formo.
- One 2-coil assembly, type TDS.—Colvern.
- One reaction condenser, .00015 mfd.—Polar.
- One input push-pull transformer, type DP.36—Varley.
- Twelve 1 watt fixed resistances, 50,000 ohms, 30,000 ohms, 25,000 ohms, 10,000 ohms, 10,000 ohms, 750 ohms, 250 ohms, 350 ohms, 350 ohms, .5 megohms, 20,000 ohms, and 2,000 ohms.—Amplion.
- Three tubular fixed condensers, .1 mfd., .1 mfd. (type 4403), .5 mfd. (type 4406)—Dubilier.
- Two fixed condensers, .0001 mfd., .0002 mfd. (type 65)—Dubilier.
- Three electrolytic condensers, 25 mfd., 25 volt working (type 3046)—Dubilier.
- Two electrolytic condensers, 8 mfd. 500 volt working (type 0218)—Dubilier.
- One fixed condenser, 500 volt working, 4 mfd. (type LEC)—Dubilier.
- One screened H.F. Choke, HFPJ.—Wearite.
- One QMB. on/off switch, type S.80—Bulgin.
- One 10-way group board—Bulgin.
- One 2,000 ohm potentiometer, type VC.26—Bulgin.
- One mains transformer—B.T.S.
- One H.T.10 metalrectifier—Westinghouse.
- One .5 amp. fuse and holder—Microfuse.
- One twin socket strip, with plugs marked A. and E.—Belling-Lee.
- Four valves, MVS Pen., 41MHL, 41MP, 41MP—Cossor.
- One mains-energised loudspeaker, type "Practical Wireless"—W.B.
- Two fixed condensers, 1 mfd., 2 mfd., type BB—Dubilier.
- Two component brackets.—Peto-Scott.
- Four valve holders, 1, 7-pin, 3, 5-pin—Clix.
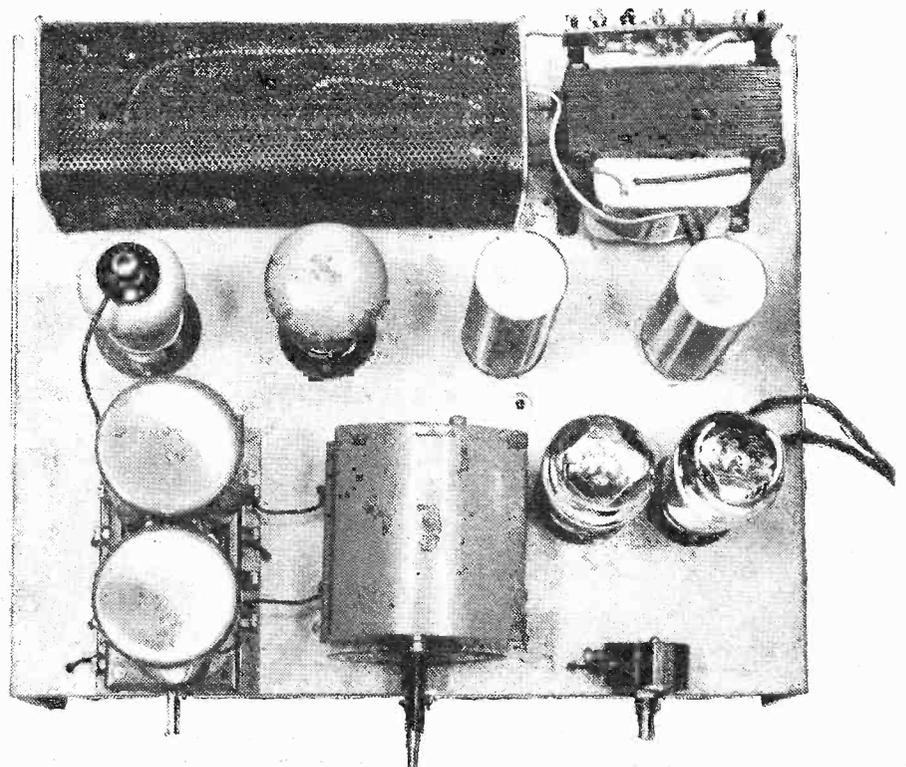
### Fitting the Set into the Cabinet

The cabinet is a soundly made job and no difficulty will be experienced in marking out the front for the various spindle holes. An excellent method of doing this is to put a spot of ink on the centre of the projecting ends of the control spindles and then to slide the chassis into the cabinet, so that the longest spindle transfers its ink to the inside of the front of the cabinet. This hole should then be drilled with a wood-worker's centre-bit, drilling through from both sides of the cabinet. Next pass the chassis in again and proceed to mark and drill the other holes in a similar manner.



## COMPONENT VALUES

Values of components shown in the circuit given last week are as follows:

R1, 50,000 ohms; R2, 25,000 ohms; R3, 250 ohms; R4, 2,000 ohms; R5, 2,000 ohms; R6, .5 meg.; R7, 750 ohms; R8, 30,000 ohms; R9, 20,000 ohms; R10, 10,000 ohms; R11, 10,000 ohms; R12, 350 ohms; R13, 350 ohms; C1, .0005 mfd.; C2, .0005 mfd.; C3, .00015 mfd.; C4, .1 mfd.; C5, .1 mfd.; C6, 1 mfd.; C7, .0001 mfd.; C8, 25 mfd.; C9, .0002 mfd.; C10, 2 mfd.; C11, .5 mfd.; C12, 25 mfd.; C13, 25 mfd.; C14, 4 mfd.; C15, 8 mfd.; C16, 8 mfd.

# BUILDING POWER AMPLIFIERS

Practical Details of Two Different Types of A.C. Amplifier Suitable for Outputs of Three and Four Watts are Given

By  
**FRANK PRESTON**


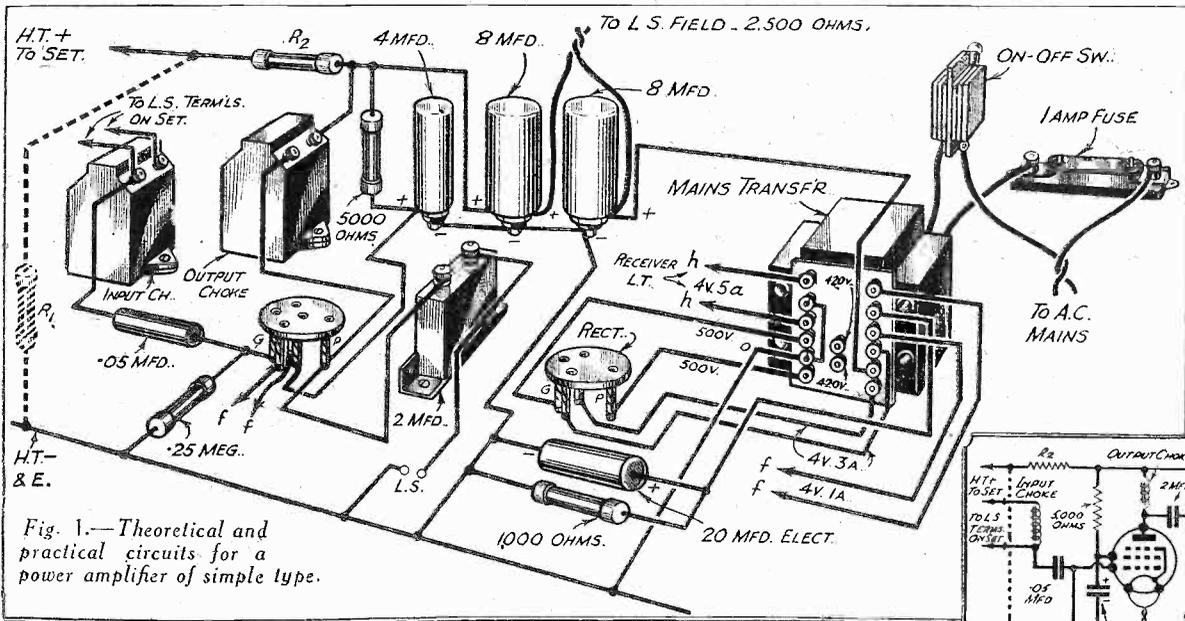


Fig. 1.—Theoretical and practical circuits for a power amplifier of simple type.

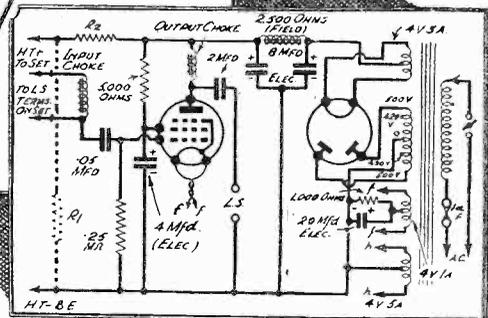

THERE are many arguments both for and against the use of high-power amplifiers to feed the loud-speaker, but the fact remains that greater undistorted outputs are coming into wider favour. Whereas an undistorted output of about 1 watt was considered high a few years ago, it is now the rule to find that the average mains receiver has a maximum output well in excess of this; in fact, it is probably true to say that the average output is something like 2 watts. There are many listeners who desire an output higher than this, however, and it is for such people that this article is written. Details will be given of amplifiers suitable for outputs between 2 and 5 watts, so that the units described will be appropriate for use with the average receiver when it is wished to operate a few speakers at full volume or to obtain good reception in a large room. The amplifiers can also be used—in a very limited way—for public-address work indoors, although they are not suitable for use in the open air, when the output should be something like 20 watts.

## The Power Supply

The conditions set out preclude battery amplifiers, since to secure more than 2 watts from a battery set it becomes expensive to obtain the necessary current, and the choice of valves is limited.

When it is proposed to fit a power amplifier to an existing mains receiver it is first necessary to decide whether or not the power-supply unit in the receiver has sufficient "reserve" to enable it to feed the amplifier as well. In the majority of cases it will be found that the mains portion has an output only just sufficient for the receiver itself, and it will therefore be necessary to provide a separate unit for the additional amplifier. It will nearly always be found, however, that the new mains unit can be made to give sufficient output for the receiver and amplifier without going to any additional expense. For that reason it might be found convenient to remove the power-supply com-

ponents from the set and use some of them in the amplifier. The amplifier circuits to be described will be shown complete with power units, and it will be explained how these can be employed to feed the receiver.

## A Single-Valve Pentode Amplifier

The simplest possible type of amplifier is that shown in Fig. 1, and this employs a single directly-heated pentode, fed from a choke-capacity filter circuit. This amplifier is well suited to follow a receiver having a small power valve in the output circuit and having only a single L.F. stage. It is not suitable for use after a powerful set, since the pentode would be overloaded in such circumstances. When the Cossor PT 41 B valve is used the undistorted output is over 3 watts. This valve requires an anode voltage up to 400 and consumes 36 milliamps of anode and screen current, so that it is necessary to employ a rectifier valve of the C class, the maximum output from which is 500 volts at 120 milliamps. A 2,500-ohm loud-speaker field winding is included in the positive lead, and this accounts for a voltage drop of 90 at the H.T. current of 36 milliamps. The bias voltage required for the PT 41 B is 40, so that the voltage actually applied between the anode and cathode is 350, allowing for a drop of some 20 volts across the winding of the output choke.

## Component Values

The various resistance and condenser values are indicated in Fig. 1, whilst suitable voltage outputs for the mains transformer are marked. It will be seen that the H.T. secondary winding of the transformer is tapped so that voltages of 500 or 420 can be applied to the anodes of the full-wave valve rectifier. When the amplifier only is being fed from the mains equipment the lower tapplings must be used to prevent the voltage from rising to a figure in excess of 500, as it would when the total load on the rectifier is only 36 milliamps. When the mains unit is also being used to feed a receiver, however,

the maximum (500-volt) tapplings can be used, the total load being made up to 120 milliamps by connecting a fixed resistance in parallel with the output, as shown at R1. The value of this resistance can be found by dividing the difference between the total current consumed and 120 milliamps into 500, and the result will be in thousands of ohms. The resistance must, of course, be of large enough power-handling capacity to deal with the current involved.

The resistance shown at R2 is for the purpose of limiting the output voltage to that required by the receiver, and its value may be calculated in the usual manner by dividing the current into the voltage to be dropped.

The mains transformer shown has a separate 4-volt, 5-amp. winding for supplying the heaters of the receiver, but the actual current output for this should be chosen according to the set in use.

With regard to the components required for the amplifier mains unit, it should be stated that these should all be of the best quality obtainable. Remember that high voltages are being dealt with, and act accordingly! The electrolytic condensers used for smoothing the H.T. supply should have a rated working voltage of not less than 600, whilst that used in the grid-bias circuit need be rated at 50 volts working. The first L.F. choke, used for coupling the amplifier to the receiver, must have a current-carrying capacity of only about 20 milliamps at the marked inductance, but the output choke should be designed to carry up to 50 milliamps, and should have an inductance of 15 to 20 henries when carrying the maximum current. This choke should have a D.C. resistance of about 400-500 ohms. All other details required can be obtained from Fig. 1.

(Continued overleaf)

AN A.C.-  
OPERATED  
PUSH-PULL  
CIRCUIT

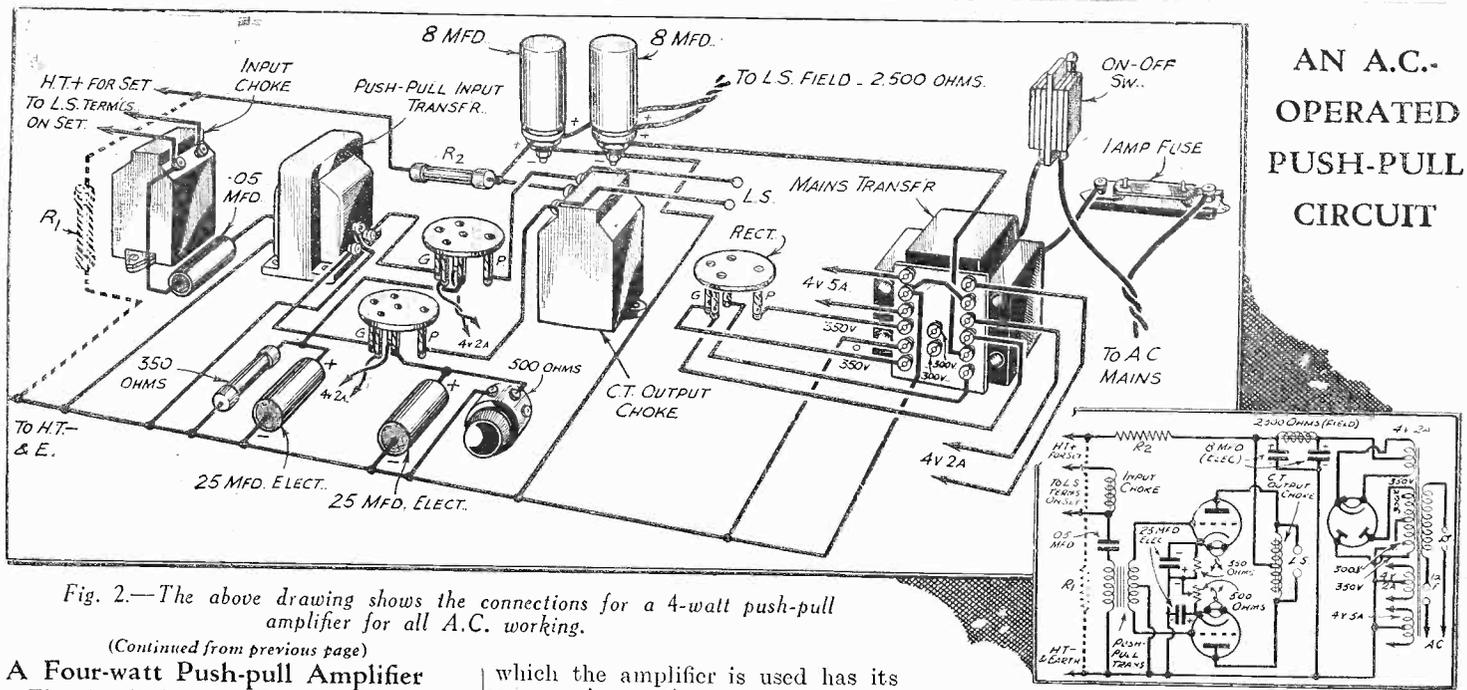


Fig. 2.—The above drawing shows the connections for a 4-watt push-pull amplifier for all A.C. working.

(Continued from previous page)

**A Four-watt Push-pull Amplifier**

The circuit shown in Fig. 2 is for a push-pull amplifier giving an output of rather more than 4 watts when a pair of Cossor indirectly-heated 41 MXP valves are employed. The component values indicated in the theoretical and practical circuits apply to these valves, but only slight modifications would be necessary if two valves of similar type but of other make were used. This amplifier is suitable for use after a receiver with an appreciable output, since the valves mentioned do not afford such a high degree of amplification as the pentode specified for the first circuit, and are not so easily overloaded. As the valves require an anode voltage of only 200 it is possible to use a rectifier valve of the B type, which gives an output of 350 volts at 120 milliamperes, and still to have a sufficiently high voltage to afford the drop occasioned by the use of a 2,500-ohm energised moving-coil speaker.

Directly-heated valves are often specified for push-pull circuits, but by using indirectly-heated ones it is possible to obtain a certain amount of decoupling in the cathode circuits and also to "balance" the two valves, if necessary, by slightly altering the value of one of the biasing resistances; it is for this reason that one bias resistance is shown as being variable. The H.T. secondary of the mains transformer is again shown as being tapped, this time at 300 volts, so that the voltage on the anodes of the valves may be kept down to 200 volts when the receiver with

which the amplifier is used has its own mains equipment.

**The Push-pull Components**

A suitable input push-pull transformer is the Ferranti AF5C, but this should be choke-capacity fed, the choke Ch.1 being chosen to match the output valve in the receiver. Where the receiver is provided with choke-capacity output the choke and condenser may, of course, be omitted. The H.T. smoothing condensers in this case should be rated to work at not less than 400 volts, although the voltage will not rise unduly due to the fact that an indirectly-heated rectifying valve is employed. The bias by-pass condensers should have a working voltage of 25, the bias voltage being 12.5.

If the speaker employed is fitted with its own output transformer this will probably be unsuitable for carrying the full anode current of the two push-pull valves (80 milliamperes), and a centre-tapped output choke is therefore shown. Where the speaker is not provided with a transformer, one having a ratio of 40:1 can be used in place of the output choke. This ratio is suitable for a speaker having a speech-coil impedance of 5 ohms, but would have to be modified for other speech-coil impedances. For example, if the speech coil were 12.5 ohms the ratio should be 25:1, or if it were of 7 ohms, the ratio should be about 30:1.

**The Choice of a Speaker**

It need scarcely be mentioned that the

speaker used with an amplifier of either of the types described must be capable of dealing with the fairly large outputs involved. It is useless to obtain a small unit intended for use with an output valve of, say, the 1-watt class. In the case of the first amplifier described the energising wattage available, for a 2,500-ohm field winding, is only about 3½ watts. This is rather low, so that with some speakers it might be desirable to use the 500-volt transformer tapplings, and to adjust the parallel resistance to such a value that a sufficiently high current is passed through the field winding. An alternative method, which is often very satisfactory, is to employ a speaker with a field winding designed for use with D.C. mains, and having a resistance of about 6,500 ohms. In this case the winding can be connected in parallel with the smoothed D.C. output, replacing the field winding in the circuit shown by a field-replacement choke. The disadvantage of this method of feeding the speaker is that the energising winding cannot be used as a smoothing choke, and expense is therefore increased to a certain extent. When a permanent-magnet speaker of suitable type is already available this can, of course, be used in either of the circuits shown, simply by replacing the field winding by a field-replacement choke as mentioned in the case of a 6,500-ohm speaker.

**Chamber Concert from Midlands**

THE second of the Chamber Concerts of music by Midland composers is devoted to Gustav Holst, who was born in Cheltenham and got his early training in choral work in Gloucestershire. The Birmingham Ladies' String Quartet and the Midland Wireless Singers will give a Holst programme on February 4th.

**"Ahab and Elijah"**

BLACK Country character and humour will be represented in Midland programmes in a short series centring round an imaginary character named Joe Guttridge. In the first of these series, to be given on February 8th, Joe tells, from inside knowledge, some remarkable stories of experiences during the production of a play called "Ahab and Elijah," which

**HERE AND THERE**

was written as well as acted by Black Country workers.

**B.B.C. Midland Orchestra**

MARJORIE WESTBURY is the vocalist with the B.B.C. Midland Orchestra in a programme of Italian music to be given on February 9th. Leslie Heward will conduct. The orchestral works include Corelli's Concerto Grosso in G Minor and Respighi's "Trittico Botticelliano" Triptych.

**Saturday Concert from Walsall**

LATER in the same evening (February 9th) one of the Popular Saturday Concerts at the Central Hall, Walsall, is to

be relayed for Midland listeners. The artists are Essie Ackland (contralto), Albert Hodgson (entertainer at the piano-forte), and Miroslav (violin).

**Clearing a Channel**

ON 514.6 metres, namely, between Vienna and Stuttgart, you will now pick up a French transmission at fairly good volume; it is Grenoble P.T.T., whose channel has now been abandoned by the newly-reconstructed Radio Agen (France). On the other hand, the position taken up by Agen on 309.9 metres is an unfortunate one, inasmuch as owing to its frequent deviations it is causing interference to Poste Parisien (Paris). It is difficult to understand why these small private stations cannot be made to work on a national common wave.

# VALVE TYPES AND USES—6

This Week Three Special Hivac Battery-operated Output Valves Are Considered.

THE output circuit of the battery-operated receiver was revolutionised about a couple of years ago by the introduction of quiescent push-pull, for this form of output made it possible to feed a power of between one and two watts to the loud-speaker. When Q.P.-P. was first introduced there were many snags and difficulties, but these have now been overcome, principally due to the improvements in valve design and manufacture that have gradually been introduced. The result is that to-day the quiescent output stage, in one of the two forms in which it can be provided, is thoroughly reliable and not only permits of ample outputs being

two pentodes at first used in Q.P.-P., the cost of the output valve and the driver together, with the additional L.F. transformer required to feed the driver, is nearly as great as that of the two pentodes for quiescent push-pull.

### A Double Pentode

Because of the facts enumerated above, Class B came into wider use than the previous system, and it is only within fairly recent times that Q.P.-P. has begun to stage a "come-back." The reason is that several makers have produced a double pentode especially designed for Q.P.-P. The two halves of the valve are accurately balanced,

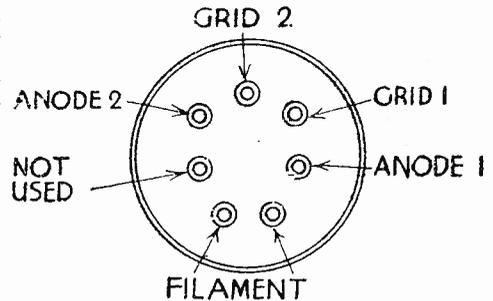


Fig. 2.—Valve-base connections for the B230 Class B valve.

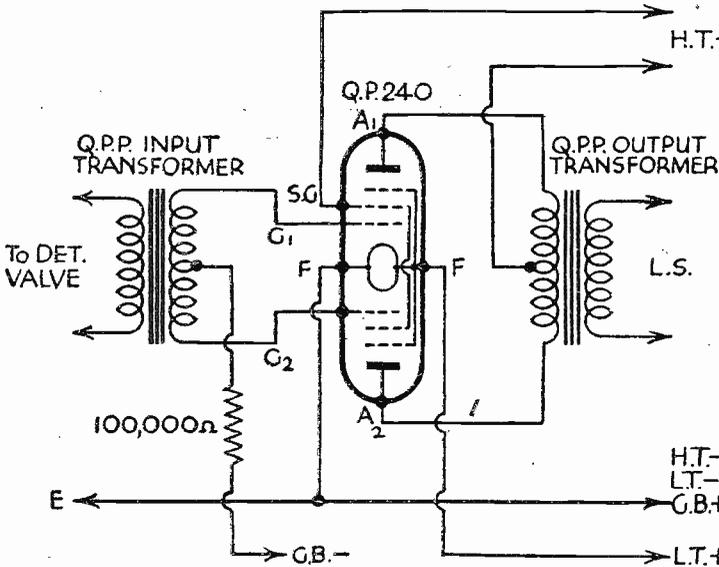


Fig. 1.—This circuit shows how the QP 240 is connected. Valve-base connections are shown below.

economically secured from battery-operated sets, but also ensures high-quality reproduction.

### The Development of Quiescent Amplification

It is interesting to recall a few of the developments which led up to the introduction of the economy-with-volume output valves now available. In the first place the Q.P.-P. arrangement was rather unpopular, due to the fact that it was expensive, since two high-efficiency pentodes were required, in addition to a special type of push-pull input transformer, and also a special loud-speaker or output transformer. There was also the difficulty of accurately matching the two pentode valves in working conditions, and this often precluded the satisfactory use of Q.P.-P. by the inexperienced constructor.


Shortly after Q.P.-P. had been introduced in this country, and before it had "got into its stride," the Class B valve came along, and rapidly gained in popularity at the expense of the rather similar previous system. As is generally known, the Class B valve consists of two three-electrode valves in a single glass bulb, and the two halves are perfectly matched by the manufacturers, thus entirely removing this difficulty so far as the user is concerned. The chief objection to Class B amplification, however, is that the output (Class B) valve requires to be preceded by a driver valve, so that, although the output valve itself is cheaper than the

and the combination valve can be bought for as little as 19s. 6d. (which is the price of the Hivac QP 240, of which details are given in a panel on this page). As may be seen, the maximum undistorted output to be obtained from this valve is 1,400 milliwatts, which is adequate for most requirements. The quiescent anode current (when no signals are being received) is 8 milliamps, and the average current during reception is 12 milliamps; this assumes that the valve is being employed with the maximum high-tension voltage of 150, and in such conditions that the

conditions it is capable of extraordinarily good results. The correct conditions can be enumerated briefly as follows: The input transformer must have a ratio of between 1 : 8 and 1 : 10 (overall); the valve must follow directly after the detector (if an L.F. stage were interposed there would be a risk of overloading); the G.B. battery should have a maximum voltage of not less than 18; the output transformer must be of the special Q.P.-P. type, having a primary resistance of not more than about 300 ohms; the H.T. supply must be well "regulated" and capable of supplying a "peak" current of, say, 40 milliamps.

All except the last condition will doubtless be quite easily understood, even by the beginner, but further information may be desirable concerning the matter of H.T. supply. It is not the purpose of this series of articles to deal with the theory of valves, but it can be stated briefly that the whole principle of quiescent working is that the anode current passed by the output valve(s) is proportional to the volume of sound being reproduced at any instant. Thus, although the average anode-current consumption of the QP 240 is only 12 milliamps, it might well rise, for very short periods, to 35 or even 40 milliamps, after which it might fall immediately to 8 milliamps. If the valve is to function correctly the anode voltage must remain constant irrespective of the

(Continued on page 729)

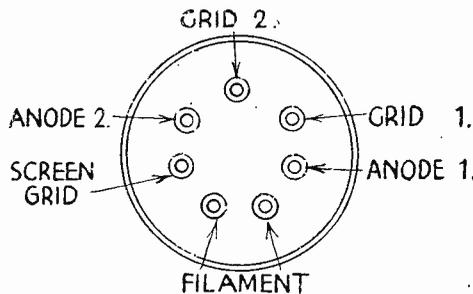

maximum undistorted output is available on the louder passages. It will be evident that the average anode current is rather higher than that taken by the Hivac B 230 Class B valve, plus that of an L 210 used as driver, but it must also be borne in mind that the maximum output is also greater than that from the Class B. From the point of view of efficiency there is little to choose, therefore, between Class B and Q.P.-P., although the latter has the advantage that it may be used directly after a detector valve, whereas the former must be preceded by an L.F. stage.

### Using the QP 240

The connections for the QP 240, which has a 7-pin base, are shown in Fig. 1, where it may be seen that one terminal only is provided for the screening grid of both pentode sections. This is an extremely likable valve, and when used in the correct

### VALVE TYPES AND USES.

#### HIVAC QP 240 (Double Pentode for Q.P.-P.)

Chief Characteristics:—	
Filament Voltage	2
Filament Current	.4 amp.
Maximum Anode Voltage	150
Quiescent Anode Current	8 milliamps
Average Anode Current (for full output)	12 milliamps
Grid Bias (for max. anode voltage)	18 volts
Optimum Load (anode to anode)	14,500 ohms
Maximum Output	1,400 milliwatts

#### HIVAC B 230 (Class B)


Chief Characteristics:—	
Filament Voltage	2
Filament Current	.3 amp.
Maximum Anode Voltage	150
Quiescent Anode Current	2.5 milliamps
Average Anode Current	5.5 milliamps
Optimum Load (anode to anode)	14,500 ohms
Maximum Output	1,250 milliwatts

#### HIVAC DB 240 (combined Driver and Class B)

Chief Characteristics: As B 230, excepting the following:—	
Filament Current	.4 amp.
Total Quiescent Anode Current (Driver and Class B)	5.5 milliamps.
Average Anode Current (driver and Class B)	8.5 milliamps.
Driver G.B. Voltage (for max. anode volts)	4.5
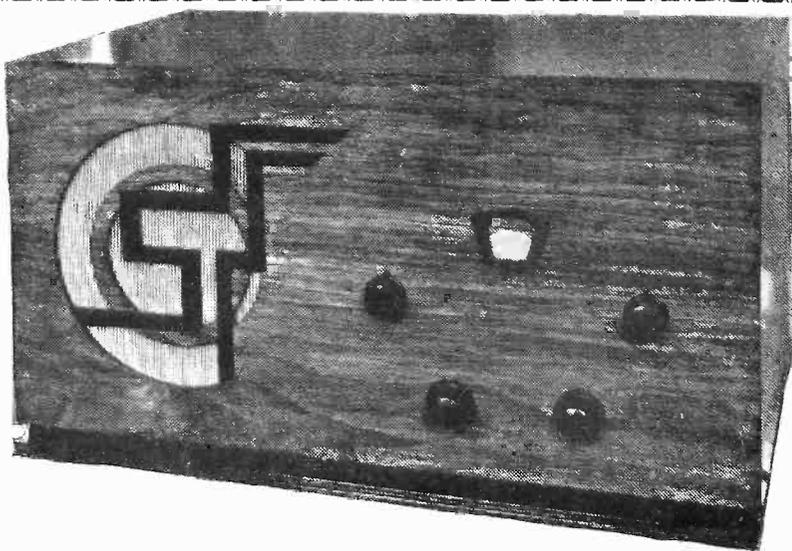
# THE BAT HALL-MARK

Constructional Details for This Set Given Here. Operating Notes will



Here is the battery model of the Hall-Mark Four in its attractive cabinet.

LAST week we gave some brief particulars of the circuit and general arrangement of the battery-model Hall-Mark Four, and from the letters we have since received it is evident that there is a large number of readers who contemplate the construction of this set. In the first place we would say that the constructional work involved is of an extremely simple and straightforward nature, as may be gathered by examining the photographs reproduced on this page. The components are few in number and are easily accommodated on the small metallised chassis. Even though the chassis is small there is no crowding and every terminal to which connection has to be made is easily accessible.

### Preparing the Chassis

Some readers may prefer to purchase the chassis ready drilled, but those who prefer to drill it themselves should start by marking out and drilling the four holes for the valve-holders. These are all 1in. in diameter, and their positions can readily be determined from the scale wiring plan given. After mounting the valve-holders it will be found most convenient to fix in


place all those components that are situated underneath the chassis, starting with the push-pull input transformer. After that, the two component brackets can be fitted and the reaction condenser and volume-control potentiometer attached to them.

It will be seen that the fixed condensers and fixed resistances are not attached to the chassis, but are supported by their connecting wires. The next step is to mount the third component bracket, variable condenser, and coil assembly on the upper surface of the chassis. Again the correct positions (which are not too critical, by the way) can be found by making reference to the wiring plan. One point that should be watched, however, is that the condenser must be exactly in the centre, so as to make the drive central. It should also be noted that the end of the condenser spindle should be in line with the front edge of the chassis—not overhanging, as might be supposed. This is because the collar on the slow-motion drive has to fit over it, the spindle from this actually passing through the front of the cabinet.


The position is rather different in the case of the wave-change switch rod on the coil assembly, since this must project, and the coil base is so placed that it just lines up with the front of the chassis.

tion, since it is evident from the wiring plan, but it should be explained that several wires pass through the chassis from components mounted on the upper surface to others that are underneath. The holes through which the wires pass are numbered on the two wiring plans, so that the "run" of every wire can easily be traced. It will also be observed that two "earth-return" leads are attached to a wood screw fitted into the chassis just beside the on-off switch; one of the leads is from the on-off switch and the other is from the volume-control potentiometer.

To those who are conversant with theoretical circuits it might appear that there are more terminals on the coil assembly than are actually required, and that some of the connections are duplicated. This is explained by the fact that certain of the coil connections are brought out to two terminals, one situated on each side of the coil base. There is a very good reason for this, which is that it ensures short, direct connections to the fixed vanes of the variable condenser and also to the grid circuits of the first two valves.

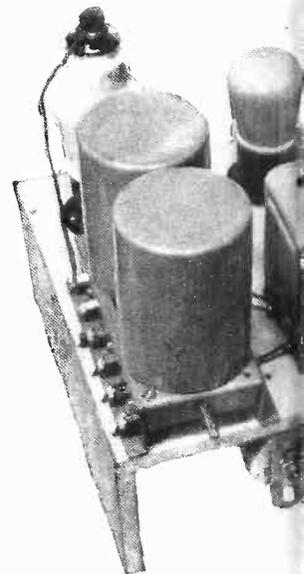

Three-quarter front view of

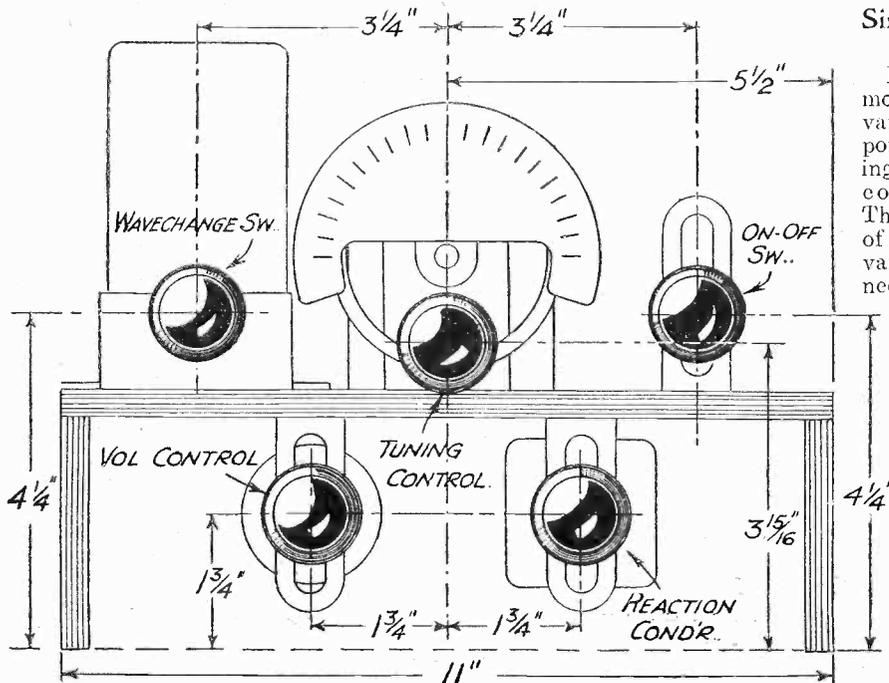

Front view of chassis, giving dimensions for drilling the cabinet.

### Simple Wiring

Having mounted the various components, wiring may be commenced. The method of making the various connections calls for little explanation.

### "Earth-Return" Connections

In making the connections to the components on the underside of the chassis it will be seen that several leads are taken to a bolt (marked M.B.). These are "earth-

### LIST OF COMPONENTS FOR THE

- One Metaplex chassis, 10in. x 8in. with 3in. runners—Peto-Scott.
- One 2-gang condenser, Baby type with dial—J.B.
- One 2-coil assembly, type T.D.S.—Colvern.
- One reaction condenser, .0003 mfd. (C3)—Graham Farish.
- One pre-set condenser, .0003 mfd. (C4)—Formo.
- Four fixed condensers, two .5 tubular (C7 and C10), two .1 tubular type 250 (C5 and C6)—T.C.C.
- Four .0002 fixed condensers, type "M" (C8, C9, C11, C12)—T.C.C.
- One 50,000 ohm potentiometer (R1)—B.T.S.
- Four ohmic resistances, 1 meg. (R2), 30,000 (R3), two 10,000 ohms (R4 and R5)—Graham Farish.
- One input push-pull transformer, type DP36—Varley.
- One H.F. choke, type H.F.8—Bulgin.

# ATTERY K FOUR

ating Receiver are  
Given Next Week

eturn" leads, and it is therefore important  
that the head of the bolt should make good  
contact with the metallised upper surface.  
To ensure this it is well to fit a large washer  
under the bolt head, and also to place a  
similar washer over the looped ends of the  
wires before fitting the nut.

It is most unlikely that any reader will  
experience difficulty in following the wiring  
diagrams, but anyone who does should  
remember that our Advice Bureau is open  
to them free of charge, and that we shall  
be glad to assist any constructor  
who is in difficulty. But do not do as  
a few have done when building pre-  
vious sets described by us and employ  
parts different from those specified.  
The receiver has been designed to give  
perfectly satisfactory results when certain  
components are used—it may, or may  
not provide good reception if altera-  
tions are made.

Battery Hall-Mark Four.



### The Output Valves


It will have been noticed by readers that  
in the circuit diagram given last week the  
output valves in the push-pull stage are  
represented as power triodes, whilst in the  
list of components these valves are listed  
as pentodes. The point is that the extra  
volume available by employing pentodes  
fully justifies their slightly greater expense,  
and for this reason these valves are recom-  
mended. Triodes, such as the Cossor  
220 PA, can, however, be used if desired.

### BATTERY HALL-MARK FOUR

- potentiometer brackets—Peto-Scott.
- terminal strips, A, E, and L.S./P.U.—Clix.
- valves, 210 VPT, 210Det., and two 220HPT—Cossor.
- resistor—W.B.
- off switch (three point)—Graham Farish.
- pin valve-holders—Clix.
- pin valve-holders—Clix.
- l-Mark cabinet—Peto-Scott.
- 12-volt H.T. battery.
- 6-volt G.B. battery.
- 6-volt accumulator.
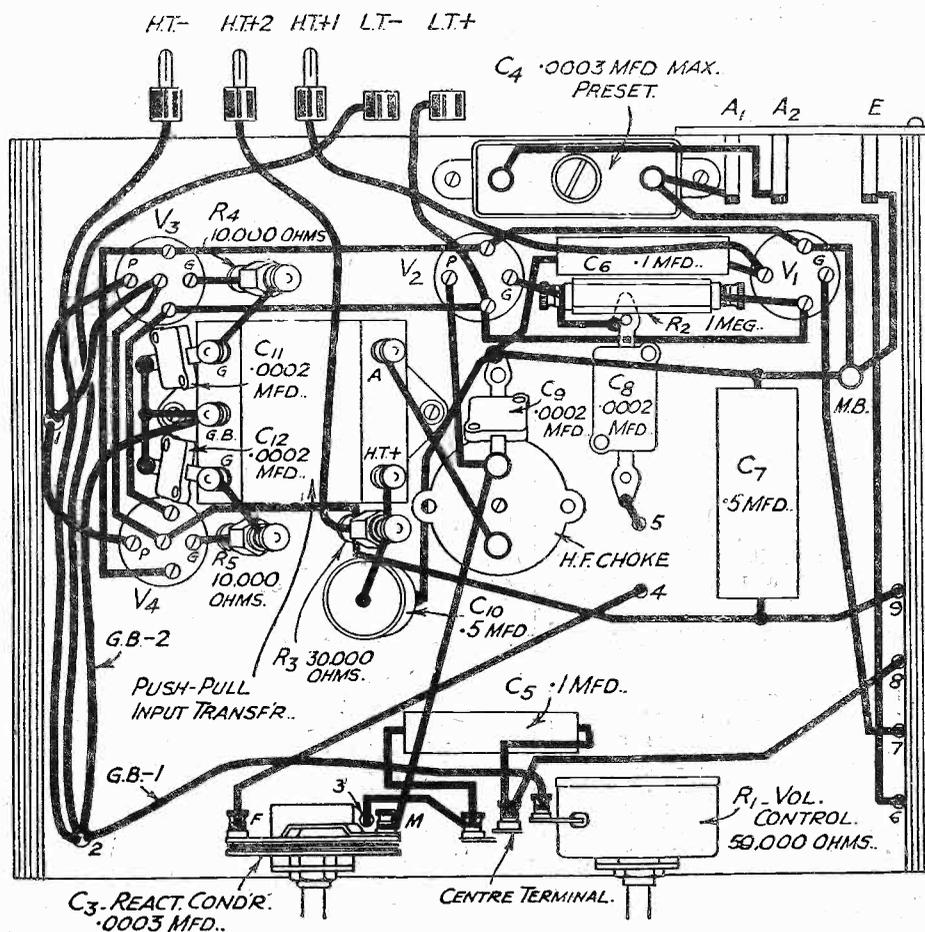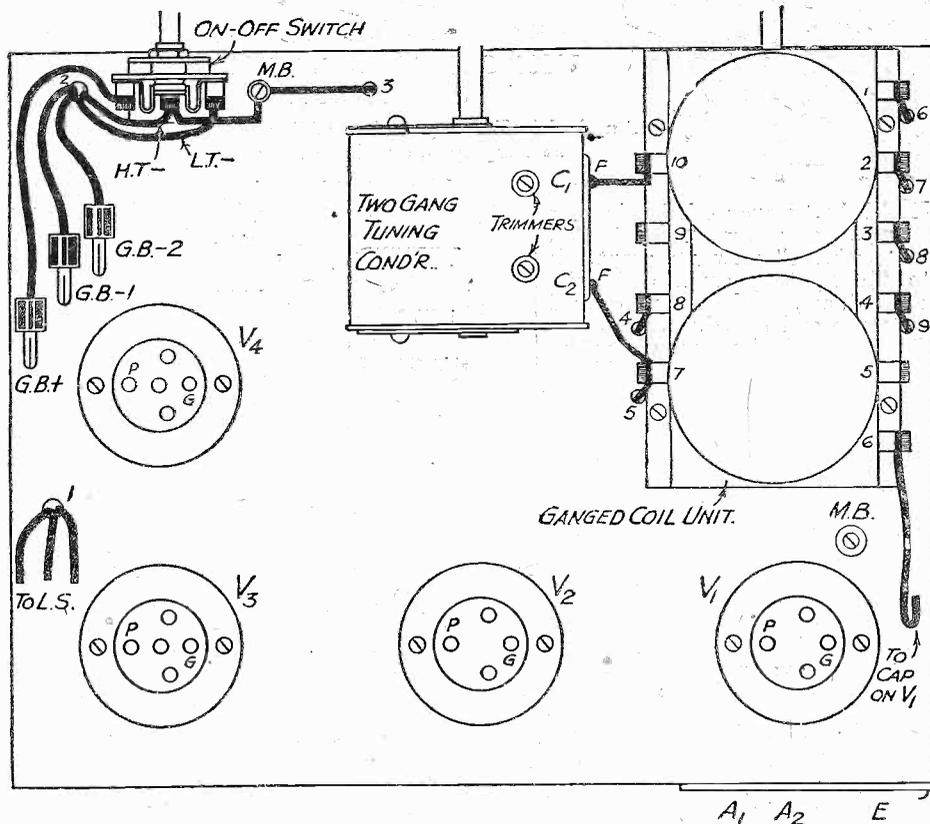
## Top and Sub-chassis Wiring Diagram of the Battery Hall-Mark Four



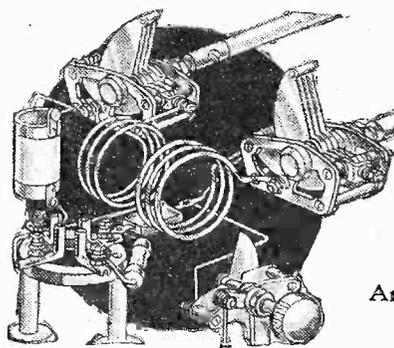

# Short Wave Section

## USING MAINS UNITS WITH SHORT-WAVERS

An Article Explaining How They Can Successfully be Employed, and How Any Difficulties May be Overcome

connected to earth. Decoupling has now been effected and a variable arrangement for detector H.T. voltage provided at the same time. This has thus overcome what was one of the difficulties of using a mains unit with a short-waver, for critical control of detector H.T. is often necessary in order to obtain smooth reaction. Besides the detector valve an intermediate L.F. valve may also be found to require decoupling, whilst if an output pentode is being used, decoupling of its auxiliary grid may be useful. These suggestions having been carried out it may be found that, although the set works quite successfully,

WHEN short-wave work first became popular many "fads" and "fetishes" grew up around it owing to the frequent small difficulties which occurred, and which often were cured by some strange and unorthodox arrangement. Because of the immense difficulties which always seem to have been considered to surround their use with short-wavers, mains-units have never, until perhaps very recently, come into favour with the short-wave experimenter. The writer is convinced that, provided a little care is taken in the first setting-up of the combination, a short-waver and a mains-unit can form a very successful arrangement. It is hoped in this article to show how such can be arranged and how likely snags that arise may be overcome.

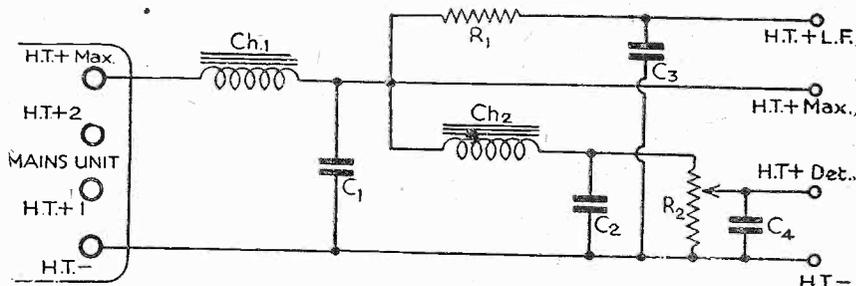


Fig. 3.—Showing the circuit of the simple and useful unit described.

if it is already included, an alteration is suggested, the circuit shown in Fig. 2 being advised. A 50,000-ohm potentiometer is wired right across the H.T. supply—one terminal to H.T. positive, the other to H.T. minus. The detector H.T. lead is taken to the slider, from which a lead is also taken to one side of a 2-mfd. condenser, the other side of this condenser being

with the mains unit a troublesome percentage of hum and, perhaps, other noises are heard. It is the writer's opinion that some of the mains units on the market are not suitable for immediate use with a short-waver without the addition of smoothing, and Fig. 3 shows a small unit which it is advised should be made up and used between the set and the unit.

Ch.1 should be a good L.F. choke of about 20 henries inductance at the current required. Ch.2, which feeds the detector only, may be the primary or secondary of an old L.F. transformer, or, better still, a high-inductance L.F. choke (about 100 H.) such as used to be used for L.F. coupling when choke-capacity coupling was popular. There are many such chokes on the market which can be purchased quite cheaply. Condensers C1, C2, C3, C4 should be 2 mfd. each and R1 should have a resistance of 20,000 ohms. R2 is a 50,000 ohms variable potentiometer which, together with C4, makes up the variable detector tapping mentioned earlier in this article. The position shown in Fig. 3 is correct for these components when this smoothing unit is used. This unit is applicable to either D.C. or A.C. mains units and should be connected right across H.T. + maximum and H.T. —, all intermediate tappings on the mains unit being ignored. Residual hum should now be nil, or else

(Continued on page 724)

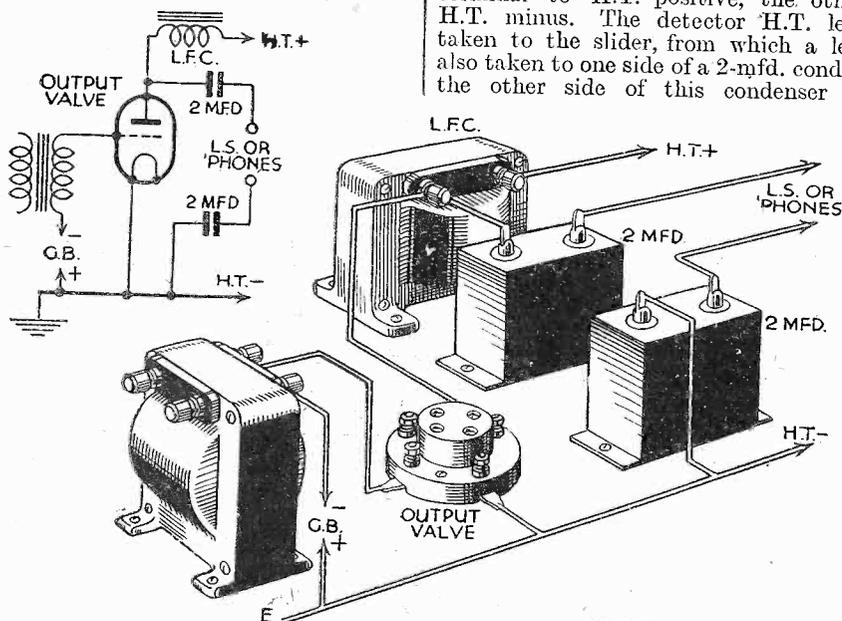


Fig. 1.—Showing how 'phones can safely be used with a mains receiver.

### Curing Instability

The first point to consider is that very frequently headphones are used with a short-wave set, and it is definitely not recommended that a mains-unit should be used with 'phones unless with a safe and efficient output filter. A diagram showing the correct circuit to be used is given in Fig. 1. Note that both 2-mfd. fixed condensers should be included in order completely to isolate the headphones. Indeed, this addition is to be advised even though 'phones are never used, as it greatly assists in smoothing out hum, and curing any instability that may arise. The question of instability is the second point which occurs, as, owing to the higher resistance of the mains-unit compared with that of a battery, even a simple two-valver which is not decoupled is liable to become unstable and difficult to handle. If decoupling is to be added, and

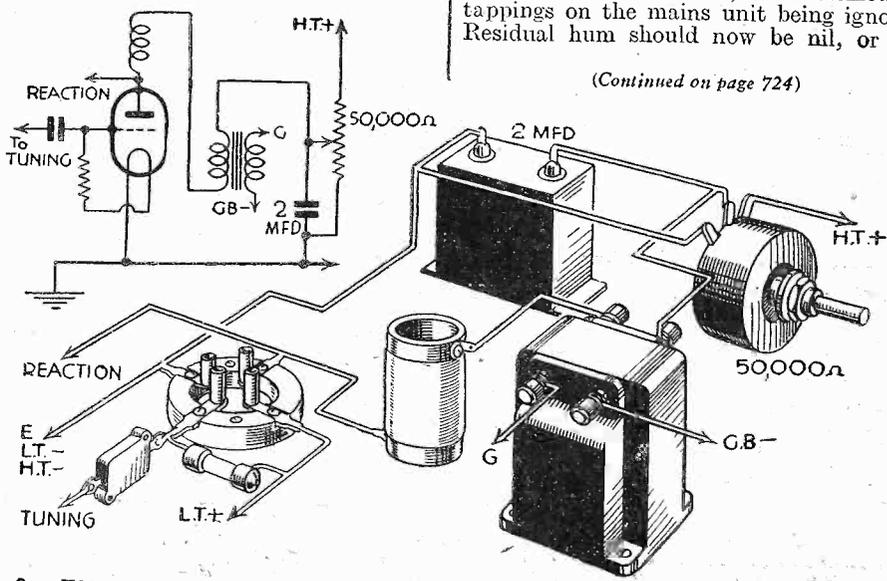


Fig. 2.—This circuit shows how the output circuit can be decoupled, as described in the text.



# PILOT AUTHOR KIT EXACT TO SPECIFICATION



Miscellaneous Components, Parts, Kits, Finished Receivers or Accessories for Cash or C.O.D. or H.P. on our system of Easy Payments. Send us a list of your wants. We will quote you by return. C.O.D. orders value over 10/- sent carriage and post charges paid (GREAT BRITAIN ONLY). OVERSEAS CUSTOMERS CAN SEND TO US WITH CONFIDENCE. We carry a special export staff and save all delay. We pay half carriage—packed free. Send full value plus sufficient for half carriage. Any surplus refunded immediately. Hire Purchase Terms are NOT available to Irish and Overseas customers.

**W.B. STENTORIAN**  
ANY MODEL  
YOURS FOR  
**2/6**  
DOWN

BRITAIN'S FINEST MOVING-COIL SPEAKERS—BRITAIN'S LOWEST EASY TERMS!


Peto-Scott offer you the lowest terms and fairest dealing in the Country. Strict Privacy guaranteed. Immediate Delivery from stock to approved accounts.

**W.B. STENTORIAN STANDARD** (Illustrated). For Power, Super-Power, Pentode and Class B. Yours for 2/6; balance in 11 monthly payments of 3/-. Cash or C.O.D. Carriage Paid, £1/12/6.

**W. B. STENTORIAN SENIOR**. For Power, Super-Power, Pentode and Class B. Yours for 2/6; balance in 11 monthly payments of 4/-. Cash or C.O.D. Carriage Paid, £2/2/0.

**W.B. STENTORIAN BABY**. Yours for 2/6; balance in 9 monthly payments of 2/6. Cash or C.O.D. Carriage Paid, £1/2/6.

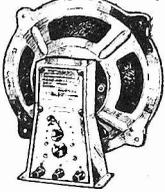
**W.B. TYPE E.M.2 SPEAKER**. Specified for the A.C. HALL-MARK 4. Cash or C.O.D. 2/6 or 2/6 deposit and 11 monthly payments of 2/6.



## Peto-Scott LUCERNE SG.3


Complete Kit of Parts for building, less Valves and Cabinet. Send only 2/6; balance in 11 monthly payments of 3/9. Cash or C.O.D. Carriage Paid, £1/19/6. Complete with Valves and Peto-Scott Walnut Table Cabinet. Cash or C.O.D. Carriage Paid, £4/2/0. or send only 5/-; balance in 11 monthly payments of 7/9.

**2/6**  
DOWN

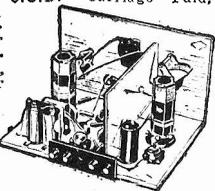

## PETO-SCOTT 75/- DISC TELEVISION KIT

ASSEMBLED in 30 MINUTES

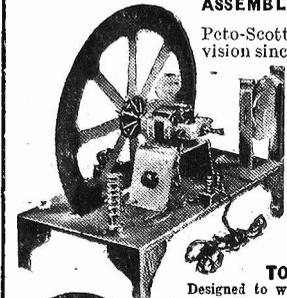

Peto-Scott, Pioneers in Television since 1927, have, after considerable research, produced this "up-to-the-minute" Disc Television Receiver Kit, of which Efficiency and Economy are the Keynotes.

NO SPECIAL TOOLS REQUIRED.

Designed to work from almost any 3-valve battery or mains set. Comprises Peto-Scott Universal Television Motor and Stand; controlling resistances; illuminated and ready assembled chassis; stroboscopic 10-in. scanning disc; lens and lensholder; neon lamp and holder, together with sundry small parts. Full-size Blueprint with assembly, wiring and operating instructions included with every Kit. Cash or C.O.D., Carriage Paid, 75/-.

**10/-**  
DOWN


and 11 monthly payments of 6/6.

## ATLAS ELIMINATOR

Model T10/30. For Class B and Q.P.P. A.C. 200/250 volts 40/120 cycles. Three tapings: 10, 20, or 30 ma. at 120/160 volts.

Trickle charger incorporated 2 volts 5 amp.

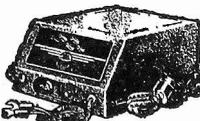Send only 5/-; balance in 12 monthly payments of 6/-. Cash or C.O.D. Carriage Paid, £3/9/6. Atlas Model C.A.25. Cash or C.O.D. Carriage Paid, £3/19/6, or 5/- deposit and 11 monthly payments of 5/6.



**5/-**  
DOWN

## A.C. HALL-MARK 4

KIT "A" Cash or C.O.D. £8:1:6  
Carriage Paid. or Yours for 15/- and 11 monthly payments of 15/-

Author's Kit of first specified parts, including ready drilled Metaplex chassis, less valves, cabinet and speaker.

**KIT "B"** As for Kit "A," but including set of 4 specified valves, less cabinet and speaker. Cash or C.O.D. Carriage Paid, £11/0/6, or 12 monthly payments of 20/3.

**KIT "C"** As for Kit "A," but including valves and Peto-Scott A.C. Hall-Mark 4 Cabinet, less speaker. Cash or C.O.D. Carriage Paid, £13/0/6, or 12 monthly payments of 24/-

**KIT-BITS** You pay the Postman. We pay post charges on all orders over 10/-. GREAT BRITAIN ONLY.

- |  |   |   |
|--|---|---|
| 1 Peto-Scott Ready Drilled Metaplex Chassis, 12 1/2 in. by 12 in. by 2 1/2 in.                 | 4 | 0 |
| 1 B.T.S. Mains Transformer   | 1 | 2 |
| 1 Westinghouse Metal Rectifier, type H.T.10  | 1 | 0 |
| 1 Varley Input Push-Pull Transformer, type D.P.36  | 1 | 5 |
| 1 Colvern 2-coil Assembly, type T.D.S.   | 1 | 5 |
| 1 Set of 4 Specified Valves  | 2 | 9 |
| Peto-Scott De Luxe Walnut A.C. Hall-Mark 4 Consolette Cabinet, Carriage and Packing 2/6 extra. | 2 | 0 |
| W.B. EM2 P.V. Speaker  | 1 | 9 |
| or 2/6 deposit and 11 monthly payments of 2/9.   |   |   |

## UNIVERSAL HALL-MARK 4

KIT "A" Cash or C.O.D. £7:6:6  
Carriage Paid. Or Yours for 13/6 and 11 monthly payments of 13/6

Author's Kit of first specified parts, including Ready Drilled Metaplex Chassis, less valves, cabinet and speaker.

**KIT "B"** As for Kit "A," but including set of 5 specified valves, less cabinet and speaker. Cash or C.O.D. Carriage Paid, £10/10/6, or 12 monthly payments of 19/6

**KIT "C"** As for Kit "A," but including valves and cabinet, less speaker. Cash or C.O.D. Carriage Paid, £12/10/6, or 12 monthly payments of 23/-

**KIT-BITS** You pay the Postman. We pay post charges on all orders over 10/-. GREAT BRITAIN ONLY.

- |   |   |   |
|---|---|---|
| 1 Peto-Scott Ready drilled Metaplex Chassis, 12x10x3 1/2 in.  | 4 | 0 |
| 1 B.T.S. Mains Dropping Resistance  | 3 | 0 |
| 1 Write set of 2 gang coils, types Q and T  | 1 | 5 |
| 1 Polar 2 gang Midgeet condenser, with V.P. dial  | 1 | 7 |
| 1 Varley Input Push-Pull transformer, type D.P.36   | 1 | 5 |
| 1 Set of 5 Specified valves   | 3 | 4 |
| Peto-Scott De Luxe Walnut Universal Hall-Mark 4 Consolette Cabinet. Carriage and Packing 2/6 extra. | 2 | 0 |
| Rola PRT Speaker  | 2 | 9 |
| or 4/6 Deposit and 11 monthly payments of 4/6.  |   |   |

## BATTERY HALL-MARK 4

KIT "A" Cash or C.O.D. £4:5:0  
Carriage Paid. or Yours for 7/9 and 11 monthly payments of 7/9

Author's Kit of first specified parts, including ready drilled Metaplex chassis, less valves, cabinet and speaker.

**KIT "B"** As for Kit "A," but including set of 4 specified valves, less cabinet and speaker. Cash or C.O.D. Carriage Paid, £6/11/0, or 12 monthly payments of 12/-

**KIT "C"** As for Kit "A," but including valves and Peto-Scott Battery Hall-Mark 4 Cabinet, less speaker. Cash or C.O.D. Carriage Paid, £7/10/6, or 12 monthly payments of 13/9.

**KIT-BITS** You pay the Postman. We pay post charges on all orders over 10/-. GREAT BRITAIN ONLY.

- |   |   |   |
|---|---|---|
| 1 Peto-Scott Ready Drilled Metaplex Chassis, 10x8x3 1/2 in.                               | 3 | 6 |
| 1 J.B. 2-gang Baby condenser, with disc drive   | 1 | 4 |
| 1 Colvern 2 coil assembly, type T.D.S.  | 1 | 5 |
| 1 Varley Input Push-Pull transformer, type D.P.36   | 1 | 5 |
| 1 Set of 4 specified valves   | 2 | 6 |
| Peto-Scott De Luxe Walnut Battery Hall-Mark 4 Consolette Cabinet                          | 1 | 9 |
| Carriage and Packing 2/6 extra.   |   |   |
| W.B. Speaker, Cash or C.O.D. Carriage Paid, or 2/6 Deposit and 11 monthly payments of 4/- | 2 | 2 |

## BATTERY HALL-MARK 3

KIT "A" Cash or C.O.D. £2:5:0  
Carriage Paid. or 5/- deposit and 11 monthly payments of 4/-

**KIT "A"** Author's Kits of First Specified parts, including pair of B.T.S. Hall-Mark 3 Coils, less valves, cabinet and speaker.

**KIT "B"** As for Kit "A," but including set of 3 Specified Valves, less Cabinet and Speaker. Cash or C.O.D. Carriage Paid, £3/5/9, or 12 monthly payments of 6/-

**KIT "C"** As for Kit "A," but including valves and Peto-Scott Walnut Consolette Cabinet, less speaker, Cash or C.O.D. Carriage Paid, £4/0/9, or Deposit 7/6 and 11 monthly payments of 7/3.

**B.T.S. HALL-MARK 3 COILS**  
Specified and used by Mr. F. J. Camm for the Hall-Mark 3.  
None genuine without his signature. THERE ARE NO SUBSTITUTES. With coloured Leads for easy identification.  
THE PAIR **7/6**  
Postage 9d. extra.

## THE FAMOUS B.T.S. SHORT-WAVE COILS

Standard 4-pin valve-holder fitting.

- No. 1. 13-26 metres 4/- SET of 4
- No. 2. 24-52 metres 4/- **16/-**
- No. 3. 46-96 metres 4/6
- No. 4. 90-190 metres 4/6 Post Free

Wavelength of Every Coil clearly marked on the Top.  
**FREE BLUEPRINT**

WITH EACH SET OF B.T.S. COILS. WORKING BLUEPRINT of latest design and wonderfully efficient DISCOVERER 3-Valve Pentode S.G., Detector, Pentode Output Short-Wave Receiver (13-95 metres) incorporating the consistently specified B.T.S. SHORT-WAVE COILS.

SEND FOR SHORT WAVE LISTS



## The GRAMADAPTOR

CONVERTS your PRESENT SET to a MAGNIFICENT 1935 Radiogram!

STAND your Mains or Battery Set on this remarkable unit... give it all the qualities of a costly 1935 Radiogram. Connected in an instant... plays with front open or closed. Sensitive Pick-up. Volume Control. 2 needle cups. Walnut polished Cabinet. Height, 8 1/2 in.; width, 10 1/2 in.; depth, 14 1/2 in.

**7/-**  
DOWN  
and 11 monthly payments of 7/6.

**A.C. MAINS MODEL**  
Incorporates Simpson's 1935 Improved Model Electric Turntable and Synchronous Motor... 12 in. turntable... constant speed... safe, silent, strong—nothing to wear out or go wrong. A.C. Mains only. 100/150 or 200/250 volts, 50 cycles. Cash or C.O.D. Carriage Paid, £3/19/6.

**BATTERY MODEL** Similar specification, but with Garrard Double Spring Motor. Same price and terms. State which model required when ordering.

77, Pr.W.7, CITY ROAD, LONDON, E.C.1.  
Phone: Clerkenwell 9406/7.  
West End Showrooms: 62, High Holborn, London, W.C.1  
Phone: Holborn 3248.

# Buy by Post—its Quicker—CASH—C.O.D.—EASIWAY

**PETO-SCOTT CO. LTD.**

## USING MAINS UNITS WITH SHORT WEVERS.

(Continued from page 722)

very small indeed, and may either be due to interaction between the mains unit and the set, or else due to H.F. on the mains. In the former case the remedy is obvious—separate set, mains unit and additional smoothing unit from each other as much as possible and always, in any case, keep aerial and speaker leads well away from mains equipment. If it is found that even with it at the most reasonable distance away from the set hum is still picked up by the latter from the mains-unit, complete screening of the unit should effect a cure. This screening must be carried out with iron or tin, and must be earthed. A large biscuit tin forms a very good screening box, but care must be taken to see that the lid makes efficient contact with the rest of the box.

### H.F. Hum

With regard to H.F. creeping through from the mains, a remedy that is fairly simple may first be tried. It is merely to connect a .001 mfd. condenser between one side of the mains and earth, reversing the plug once or twice to see which way round gives the least hum. Failing this, two .01 mfd. condensers in series across the mains with the mid-point earthed should effect a cure. In the event of still troublesome H.F. hum and noises on the

mains, two H.F. chokes specially designed for mains working may be added as shown in Fig. 4. Reducing the value of the grid leak frequently assists in eradicating

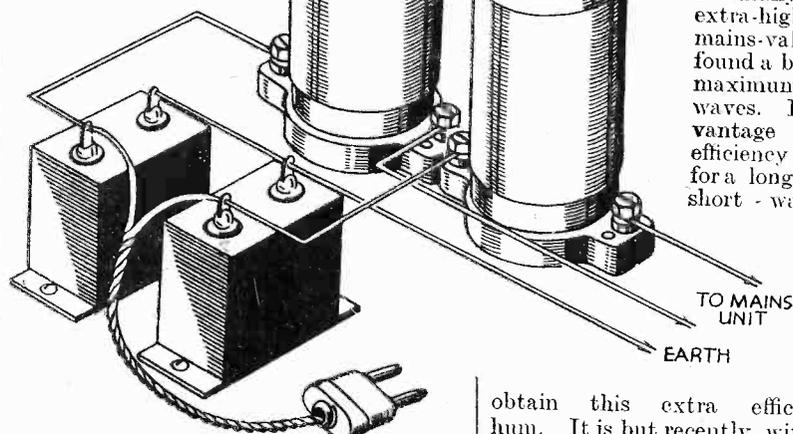


Fig. 4.—Special mains H.F. chokes, connected as shown here, will often prevent mains interference.

hum, and it is obvious that all grid leaks, condensers and resistances must be in first-class order, for with mains working the slightest variation is liable to cause crackle or hum.

It is sufficient proof of the fact that a mains-unit can be used with a short-waver to say that all A.C. short-wave sets are now being designed. Naturally enough, the extra-high efficiency of mains-valves has been found a boon in obtaining maximum results on short waves. Indeed, the advantage of this extra efficiency has been realised for a long time, as many short-wave experimenters have been using indirectly-heated A.C. valves run off batteries in order to

obtain this extra efficiency without hum. It is but recently, with the improvement in indirectly-heated valves, as well as in mains components and the provision of high-capacity electrolytic condensers for smoothing, that all A.C. short-wavers have come into their own. The ease and reliability of mains working are great assets well worth the slight effort required to put the few foregoing hints into practice.

# METAL SHIELDING AND SHORT-WAVE RECEIVERS

THE keen amateur who, as a rule, studies commercial and sponsored designs is quick to realise the advantages to be derived from efficient screening. After carefully studying the fundamental principles followed by a series of practical experiments, the advantages of screening properly and correctly applied are obvious.

Unfortunately many experimenters are less thorough, and regard screening as but a simple undertaking—simply the placing of screens around coils and between stages, and using a metal chassis foundation. Practical experiments on the above lines, as is to be expected, usually end in dismal failure.

Do not imagine, however, that screening is best left alone; this is by no means the case, because screening when correctly applied is a definite advantage. Quite apart from technical considerations, experimental screening will prove of interest to the amateur, who naturally wishes to obtain the maximum efficiency from his receiver.

As previously mentioned, the fundamental principles must be understood in order to reap the benefits of screening, and avoid snags and consequent disappointment.

The purpose of this article is to deal with various points, advantages and snags, all of which are associated with screening and the design of screened short-wave receivers.

### Chassis Construction

The foundation of a modern receiver is the chassis. Aluminium is the most common metal used for chassis construction. It is, of course, by no means cheap to buy and must be of a rather heavy gauge in order to avoid whip or fracture. This point is worth remembering. If the chassis is of light-gauge material it is absolutely useless because power trans-

### This Article Deals with the Various Points, Advantages and Snags Associated with Screening, and the Design of Screened Short-wave Receivers

formers, chokes and gang condensers are heavy components which require a solid foundation. To handle a flimsy chassis upon which components of the above nature are mounted is simply asking for trouble, which will undoubtedly be experienced sooner or later.

One of the chief objections to the use of aluminium as a material for chassis construction is that it cannot be soldered. Commercial practice is to solder tags to all leads at earth potential and bolt them to the chassis. This method is quite satisfactory.

### The Use of Sheet Steel

The steel chassis is rapidly gaining favour, steel, of course, being cheaper than aluminium. Many experimenters will undoubtedly fancy this steel-chassis idea as sheet steel, in addition to its relative cheapness compared with aluminium, is available in most places. It should be remembered, however, that the shielding efficiency of steel is less than that of aluminium owing to its greater resistance, and much greater losses are to be expected.

It is possible to build a satisfactory receiver into a metal or steel cabinet, but there is no doubt that a cabinet made of sheet aluminium would provide better screening. This, of course, does not mean that to use the former type of cabinet or screening box is definitely bad. As a matter

of fact, the best and most sensitive 0-v-2 receiver the writer has ever built is housed in a cabinet of this type. The main point is to know exactly what to avoid and, so far as construction is concerned, act accordingly.

Commercial practice, it will be noticed, is to use steel chassis construction in some instances, but this is not just a case of buying sheet steel in bulk, cutting and pressing to shape and finally arranging various components on both sides. Examination will show that the chassis is either cadmium plated, or copper plated, and later painted. By adopting these methods the skin effect is taken into consideration, for, as is well known, H.F. current travels on the surface. (Incidentally, the same applies to the metallised wooden chassis.) It will be seen, therefore, that cadmium plating is not carried out merely for the sake of appearance, but to increase the shielding efficiency of the steel chassis.

### Coil Screening

Next, let us consider coil shielding or screens. Which, quite apart from space, is the most efficient and satisfactory type of coil screen, large or small; that is, of course, relative to the size of the coil to be used in conjunction with it?

For example, our H.F. transformer or coil is 1½ in. diameter, and we have choice of two sizes of screening can; one is 2 in. diameter and the other 3 in. diameter. We may try each in turn, but as the bases must be bolted or riveted to the chassis we cannot entertain the idea of drilling extra holes.

The first point to remember is that if coil shields, or screens, are to be used the coils must be wound suitably in order to cover the desired wave-range. By screening

(Continued on page 727)



# THE EASY ROAD TO RADIO.

## THE BEGINNER'S SUPPLEMENT

### ELECTRIC CURRENTS IN WIRELESS (Part I)

A Clear and Concise Explanation of the Various Currents which Traverse the Circuits of a Modern Radio Receiver, with Particular Reference to the Oscillatory Currents of the Tuning Circuits and the Currents Within the Valves

A WIRELESS set is essentially an electrical machine, and to understand its working it is necessary to understand something about electricity. Electricity may remain static or it may move in the form of current. In wireless we are chiefly concerned with current electricity. Perhaps one of the simplest illustrations of an electric current is afforded by the working of an electric torch. Current from the battery passes through the fine wire filament of the lamp and causes it to become white hot. The current in this case consists of a steady flow from one pole of the battery, through the lamp, to the other pole.

#### Electricity a Fluid

From the fact that an electric current is always spoken of as "flowing" from one point to another it would naturally be assumed that electricity is a fluid. This is correct, but it should be explained that it is a fluid in the same sense that the sand in an hour-glass is a fluid, the sand being formed of individual grains. In the case of an electric current the "grains" are electrons or negative particles of electricity, and as a collection these electrons constitute a fluid. It does not mean to say that the electrons themselves are necessarily fluid. Modern theory explains that all matter is composed of electricity. Each little atom of substance is composed of a collection of positive and negative particles of electricity. In the ordinary way these protons and electrons, as they are called, are kept in place within the atom by mutual attraction, and the substance displays no electrical properties. However, some of the electrons are very loosely linked to the rest of the protons and electrons, and under certain conditions can be made to travel about between the atoms. It is the movement of these electrons which constitutes an electric current. If a number of them can be made to leave the atoms to which they are attached and to travel through the substance, say a piece of wire, until they arrive at the other end then that end is said to be *negatively* charged with electricity, while the other end, which is left with a deficiency of electrons, is said

to be *positively* charged. It must be emphasised that it is not the atoms themselves which move, but only the electrons. They can move in the spaces between the atoms and can also join up with, or leave, the atoms.

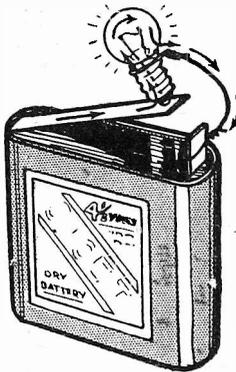


Fig. 1.—A simple example of the flow of a direct current is provided by this torch battery and bulb. The arrows show the path of the current.

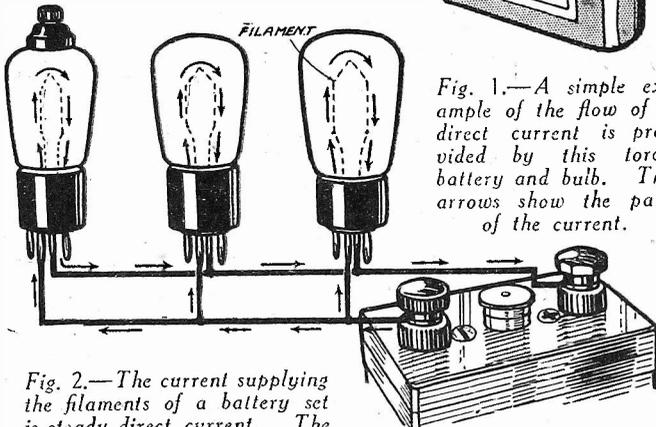


Fig. 2.—The current supplying the filaments of a battery set is steady direct current. The path of the electrons which constitute the current is shown by the arrows.

#### Different Kinds of Current

We have stated that the current flowing through the filament of an electric torch consists of a steady flow of electrons passing in one direction only. It is, in other words, a steady *direct* current. The currents in a wireless receiver are, however, of a more complex nature than this. Practically the only part of the circuit in which pure direct current is met with is in the filament circuit of a battery set. Here a steady

current passes from the accumulator through each of the valve filaments (see Fig. 2) in the same way that the current from the torch battery passes through the bulb. The valve filaments become hot through the passage of the current (although it is not necessary in this case to bring them to white heat), and this causes some of the electrons in their jostling struggle through the restricted path of the filament to be thrust out into space. In other words a shower of these crowded-out electrons flies off in all directions.

The current flowing through the torch bulb or through the filament of a battery-operated valve may be compared with an even flow of water through a pipe. However, the flow need not necessarily be steady. The current from a dynamo, for instance, is never as steady as that from an accumulator. It fluctuates slightly all the time, one moment rising and the next moment falling. This is a fluctuating or impure direct current. The third type of current is one which flows first in one direction and then in the other. This is called an *alternating* current, and according as the alternations are slow or rapid it is known respectively as a *low-frequency* and a *high-frequency* current. A good example of a low-frequency alternating current is provided by the house lighting supply. If the house is supplied with "A.C.," it means that the current when it passes first one way through the filament and then the other way, this change of direction taking place about 50 times per second. This is so rapid that the cooling down of the lamp filament as the current dies down between each change of direction of the current is not perceptible to the eye. The lamp appears to give a steady light as though it were fed with a pure direct current. Of course, 50 cycles is not the only speed at which a low-frequency current can alternate and currents which change their direction of flow as many as 10,000 times or more in a second are still considered to be "low-frequency" currents.

#### High-frequency Current

The best example of a high-frequency alternating current is provided by the current which traverses the aerial circuit of a wireless set when it is tuned to a broadcasting station. This is produced by the wireless waves which strike the aerial in rapid succession. It is an alternating current because it travels first in one direction and then in the other, but the speed or frequency with which it

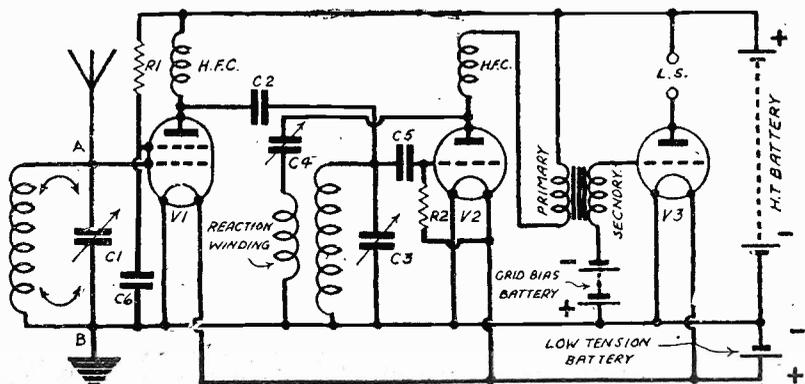


Fig. 3.—The three-valve circuit referred to in the article. The thick arrows show the path of the H.F. currents in the aerial circuit.

# Let Us Send You This 28-Page Booklet—Free



It gives all particulars of various Courses that cover every phase of Radio work. The Radio industry is progressing with amazing rapidity. Only by knowing thoroughly the basic principles can pace be kept with it. I.C.S. Instruction includes American broadcasting as well as British wireless practice. It is a modern education, covering every department of the industry.

### OUR COURSES

Included in the I.C.S. range are Courses dealing with the Installing of radio sets and, in particular, with their Servicing, which to-day intimately concerns every wireless dealer and his employees. The Operating Course is vital to mastery of operating and transmitting.

There is also a Course for the Wireless Salesman. This, in addition to inculcating the art of salesmanship, provides that knowledge which enables the salesman to hold his own with the most technical of his customers.

Then there are the Preparatory Courses for the City and Guilds and I.W.T. Exams.

We will be pleased to send you details and free advice on any or all of these subjects. Just fill in, and post the coupon, or write in any other way.

International Correspondence Schools, Ltd.,  
Dept. 94, International Buildings,  
Kingsway, London, W.C.2.

Without cost, or obligation, please send me your "Radio" booklet of information about the Courses I have marked X

- COMPLETE RADIO
- RADIO SERVICING
- RADIO EQUIPMENT
- RADIO SERVICING AND SALESMANSHIP
- WIRELESS ENGINEERING
- WIRELESS OPERATORS
- EXAMINATION (state which)

Name..... Age.....

Address .....


changes its direction is colossal—a million or more times per second!

From this very brief description of some of the forms which an electric current may take we can proceed to the study of the wireless receiver itself and analyse the currents in the various parts of the circuit. The circuit illustrated in Fig. 3, which is necessarily made as simple as possible for the sake of clarity, represents a typical three-valve arrangement. Starting from the aerial we come to the aerial tuning circuit. This is also shown separately in Figs. 4-6. The point A is connected to the aerial and the point B to the earth. The incoming waves on striking the aerial set up a high-frequency current which surges up and down it. If the aerial were connected direct to the earth instead of having the coil and condenser interposed these currents would simply flow direct to earth and back again. However, the introduction of the tuned circuit offers an opposition to the passage of the current. The amount of opposition offered depends on the size of the tuning coil and condenser. By using the right number of turns of wire and by adjusting the condenser to just the right size it is possible for the circuit to provide almost a complete barrier to the flow of current through it.

that a collection of electrons attempts to flow into the circuit at B from the earth direction, but they are here met by those which have just travelled round the circuit to D. Incidentally, from an electrical point of view, B can be taken as being contiguous with D and likewise A with C. Since like repels like the newcomers are repelled by the electrons which have collected on D and thus they are unable to pass through to A and up the aerial.

By the time the aerial current reverses again the current in the circuit has also reversed, the electrons having been ejected by D and sent bouncing round to A to meet and oppose the aerial current at this point. This process goes on all the time the circuit is tuned to the incoming waves, the electrons flowing from C, through the coil, to D and back again continuously. This oscillation set up within the circuit is called the *circulating current*.

It must be understood that the arrival of the electrons at each end of the circuit coincides exactly in point of time with the arrival of those forming the aerial current, and thus the latter are met and opposed every time they try to pass through the circuit. However, if the circuit conditions are altered by, say,

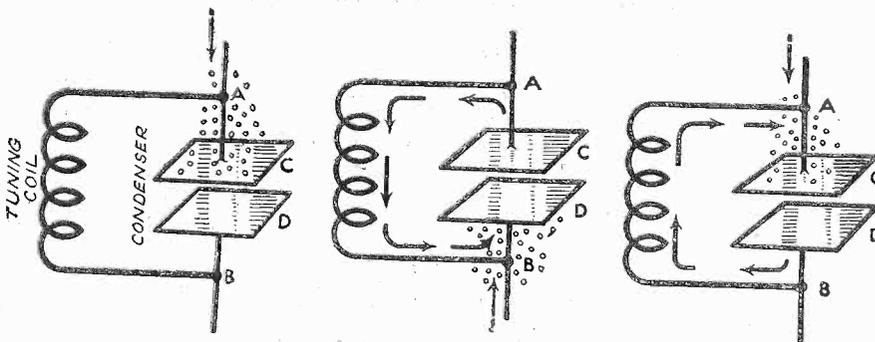

Figs. 4-6.—Diagrams illustrating the movement of the high-frequency currents in the aerial circuit of a wireless set.

When these conditions are arrived at the circuit is said to be "tuned" to the incoming waves.

### H.F. Currents and Tuning

It must be explained why the tuning circuit opposes the passage of the aerial current through it. It is due to the combined action of the condenser and coil, which forms an *oscillatory circuit*. The current induced in the aerial by the incoming waves takes the form of electrons passing up and down it at a very high speed. When they come down the aerial they arrive at the point A (see Fig. 4) and immediately pour into the condenser and fill up the plate C. This action is similar to that of filling a toy balloon with air. However, as soon as the electro-motive force which has sent the electrons into the condenser dies down, as it naturally does before the current changes its direction, the electrons are ejected from the condenser like air from a collapsing balloon. These electrons, or at any rate some of them, instead of going up the aerial again, travel on round the circuit as shown by the arrows in Fig. 5. They pass through the tuning coil and into the other plate of the condenser. In the meantime the current flowing up and down the aerial has reversed its direction and electrons are travelling up the aerial. This means

increasing or decreasing the effective size of the condenser then this balanced state will be disturbed. The circulating current will oscillate slower or faster, as the case may be, than the aerial current, and thus some current will be allowed to pass through the circuit. In this case the circuit is said to be detuned.

This brief explanation of the action of the oscillatory circuit is of necessity not absolutely complete, nor as regards the building up of the circulating current is it strictly accurate since other factors, such as the effect of the inductance of the coil, to avoid confusion, have not been mentioned. However, the ultimate effect is, as we have described, the production of an oscillating current resulting in the piling up of electrons alternately at A and B.

(To be concluded.)

A Fine Book for Beginners

## EVERYMAN'S WIRELESS BOOK

By F. J. CAMM

5/-, or 5/6 by post from Geo. Newnes, Ltd.,  
8-11, Southampton St., Strand, W.C.2.

**METAL SHIELDING AND SHORT-WAVE RECEIVERS**

(Continued from page 724)

a coil we automatically reduce its maximum tuning range. If our shielding can is too small in diameter the spread over of the magnetic field produced by the tuning coil is very restricted, and thus the overall efficiency of the tuned circuit or circuits will be considerably reduced. To counteract this defect a large screening can with low resistance is required, therefore it is necessary to use a stout gauge of aluminium, or better still, copper.

When purchasing a coil can remember that if it is of stout gauge, and is fitted with a detachable bottom and spigot for chassis use, it is quite suitable. Do not attempt, however, to make a steel chassis and use open-ended cans or nothing but trouble will result. Quite definitely, unless a steel chassis is plated as outlined previously it is better not to use it at all. The writer is strongly in favour of the metallised or copper-foil-lined wooden chassis, for cheapness and efficiency together with ease of construction.

The experimenter with considerable experience may wish to build a receiver which has a professional appearance, and no doubt will make a good job of it. The beginner should not be too hasty and attempt to design before he can construct. Better far to have an amateur-looking receiver which works like a professional job and gives results, than to build a rather professional-looking job which refuses to function. When choice between steel and aluminium chassis is to be made the latter is to be recommended.

**Tuning Condensers**

Variable condensers especially designed for short-wave work are available. Gang condensers are, however, expensive, and for experimental work readers may wish to use a broadcast type which will allow of the number of plates being reduced to suit requirements.

A condenser of this type, if well made mechanically, will be quite satisfactory, provided that trimmers are fitted on the top, and each unit is shielded from the other, with a separate connection provided for wiring each unit of moving vanes to chassis.

Chassis-type valve-holders should be of reputable make, as flimsy affairs will most likely cause crackling and various other troubles. Make quite sure that the chassis and panel are effectively earthed, and mount the earth terminal directly on the chassis.

All leads which are at earth potential go to the chassis. Do not, however, take three or four of them to the same point, but to the chassis at separate points, which will allow a short and direct lead, remembering that a potential difference exists at different parts of the chassis, panel, and screens.

In modern tuning condensers, metal frames and end plates are used. In these, the moving vanes are earthed (except in trick circuits) by mounting them directly on the metal panel or, in the case of a gang condenser, on the chassis.

Chassis construction reduces the amount of wire required in a receiver and may make a difference of many inches. The writer remembers rebuilding a baseboard short-wave receiver on chassis lines, which reduced one lead previously a foot in length to one inch, and readers who adopt the same methods will be surprised at the amount of connecting wire they have left over.

**EXCLUSIVELY SPECIFIED for the 'HALL-MARK FOUR'**



There can be no better evidence of the W.B. Stentorian's really outstanding performance than this significant fact—that for each one of his important receivers since August Mr. Camm has *exclusively* specified the use of this amazing new instrument. "As near perfection as I believe perfection possible," he said recently. Can there be higher praise?

The W.B. Stentorian's startling performance is no mere accident. Years of research were necessary to produce a magnet giving nearly double strength at equal cost—which the exclusive Stentorian magnet achieves. The exclusive Whiteley speech-coil, with its better bass response and crisper attack, was only perfected after unremitting experiment. The improvement which these and other exclusive features bring must be heard to be believed.



**Model PMS1**

- Stentorian Senior (PMS1). 100 per cent. dust protection. Oversize cone **42/-**
- Stentorian Standard (PMS2) **32/6**
- Stentorian Baby (PMS6) **22/6**

Ask your dealer about the newest "Stentorian" model, the "Baby," complete in walnut-veneered cabinet at the astounding price of 22/6.

You must hear the astonishing new volume and realism a Stentorian will bring to your set. Ask your dealer to-day—you will be *amazed*.

Write for New W.B. Stentorian Leaflet.

**STENTORIAN PERMANENT MAGNET MOVING-COIL SPEAKERS**

Whiteley Electrical Radio Co. Ltd. (Technical Dept.) Radio Works, Mansfield, Notts.  
Sole Agents in Scotland: Radiovision Ltd., 233 St. Vincent Street, Glasgow, C.2.  
Sole Agents in I.F.S.: Kelly & Shiel, Ltd., 47, Fleet Street, Dublin.

"A really gorgeous text-book."

**WIRELESS FOR THE MAN-IN-THE-MOON**

By Coulombus and Decibel.

2/6 net, by post, 2/10

"If you want a really gorgeous 'text book,'" says the *Manchester Evening News*, "read WIRELESS FOR THE MAN-IN-THE-MOON."

And, writing about the same book and its authors, the *Midland Daily Telegraph* says, "They succeed in imparting a real knowledge about Wireless. It is both good fun and sound theory."

This book will be read with profit and enjoyment by every wireless enthusiast—beginner or expert.

From all Booksellers, or by post from

**GEORGE NEWNES, LTD., 8-11, Southampton St., Strand, London, W.C.2.**

SUPPLEMENT TO "PRACTICAL AND AMATEUR WIRELESS"

# AMATEUR TELEVISION

## TRANSMITTING "STILLS"

By H. J. BARTON CHAPPLE, B.Sc., A.M.I.E.E.

THESE are many amateurs who have carried out a number of experiments in connection with the reception of television, but only a few have turned their attention to the question of providing their own television signals for test purposes. While admitting that the outlay incurred for apparatus would be somewhat high if everything that was required was purchased brand new, it will be found frequently that much of the material is available in experimental apparatus which every wireless enthusiast collects over a period of time.

### Apparatus Required

The best way to make a start is in the transmission of "stills"; that is, magic lantern slides or single-frame pictures selected from any standard 16- or 35-millimetre film suitably mounted. The first requirement is some form of projector; that is, a housing for a source of light (arc or metal-filament projection lamp fed from A.C. mains through a step-down transformer), together with a focusing lens. (An old magic lantern outfit will do quite well here.) Next is needed the single spiral apertured scanning disc together with the driving motor. In the case of the disc, a standard twenty- or sixteen-inch receiving disc is quite satisfactory, provided it is free from mechanical errors, primarily in connection with the positioning of the holes. Naturally, the correct type of heavy fly-wheel scanning disc is best for transmitter work, but the substitute suggested is capable of giving results far in excess of what may be anticipated originally.

Assuming that the television signals generated will be observed on the standard type of television receiver built or purchased for looking in at the B.B.C. transmissions, then the square holes need to be of the correct size and appropriately positioned to give the seven-by-three ratio picture having a thirty-line dissection. Designs for discs of this character have been described from time to time in this supplement, or alternatively a ready-made disc can be purchased for a sum as low as 12s. 6d.

### Setting Up

The motor should be of good quality and capable of running at a dead steady speed of 750 revolutions per minute. If preferred, a synchronous A.C. motor can be used, but failing that, use a motor with a smooth form of speed control and stroboscopic speed observation to ensure correct running.

Employ a light source as intrinsically brilliant as possible, and position this together with the lantern slide or film still and focusing lens, so that the resultant

picture projected on to the disc is properly focused and bright. The exact size of the picture on the disc will depend on the disc diameter, but it should have dimensions which will allow it to be just scanned by the first and last holes of the disc. An arrangement suitable for amateur use is one consisting of the parts previously referred to, the light source and photo-cell being mounted with their axes in line, and one on each side of the disc. Lamp projector and focusing lens are mounted on the left, while the scanning disc is driven by a mains fed motor having a belt drive.

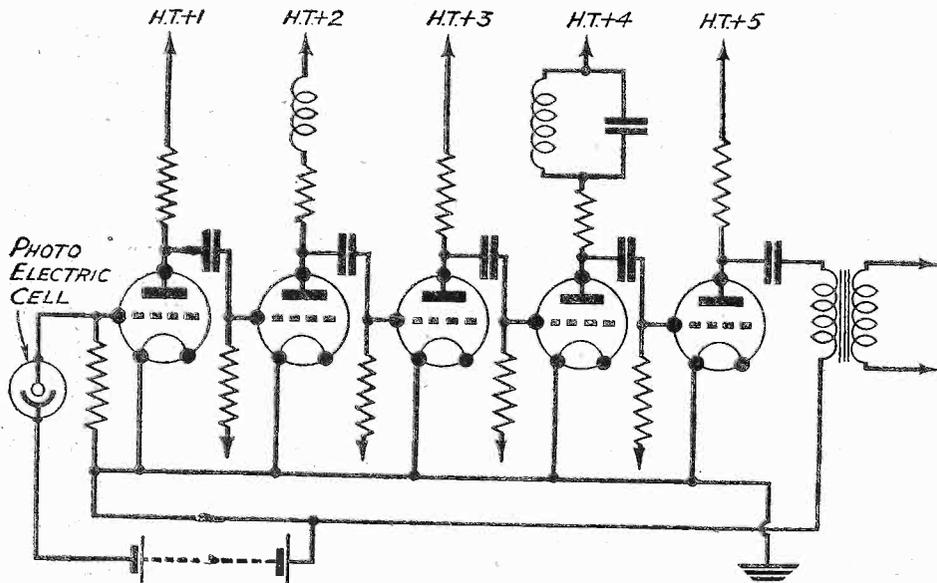


Fig. 1.—The simplified diagram of the photo-electric cell or "A" amplifier.

As the disc revolves the individual apertures dissect the projected picture into the thirty strips as they pass across. Since the picture is made up of various light and dark shades this process of scanning will cause varying small quantities of light to pass through the holes to the other side. These light signals must then be made to influence a single photo-electric cell mounted immediately behind the disc and in the correct optical path of the penetrating light. It is often desirable to have a focusing lens between the back of the disc and the photo-electric cell (the cell being enclosed in a light-screening box with a small window aperture of just sufficient size to take the whole of the scan) and placed opposite to the light source.

### Cell Amplifier

The rapid light variations activating the electrodes of the single photo-electric cell produce corresponding voltage variations of equiv-

alent amplitude. Quite a wide choice of cells are open to the experimenter, but a very efficient one for the purpose is that designated the C.M.G.8 and made by the G.E.C. Full details for operating the cell are furnished by the makers, so this question need not be gone into here.

The voltage variations produced by the cell are very minute and need amplification in what is commonly termed an "A" amplifier. This is a resistance-capacity-coupled amplifier having, for the best results, a reasonably low gain per individual stage. Furthermore, this amplifier must be quite clear of parasitic noises, otherwise the picture signal will not be considerably above the "mush" level, and imperfect images will result.

One circuit diagram for an amplifier of this type is given in simplified form in Fig. 1, battery fed valves being used for simplicity and stability, each anode being supplied by a separate H.T. feed. The cell

is connected direct to the grid of the first valve with the appropriate battery voltage in series. Another point to notice is the inclusion of "boosters" in the second and fourth valve anode circuits. The first is a single inductance, while the second is a similar inductance tuned with a fixed condenser. The values of these components must be chosen to suit individual conditions, but they serve the purpose of maintaining a level frequency response up to well over 10 kilocycles.

The layout of an amplifier of this character is very important, as stray capacities and long leads must be reduced to a minimum. In Fig. 2 is shown one design which proved particularly efficient for some initial thirty-line television experiments of this nature. The valve-holders are partly stripped and mounted on a central platform, while the output transformer is an O.P.2 (step-down).

The resultant vision signals from this amplifier are passed to the normal power amplifier associated with the vision receiver, so that the images can be watched and very many interesting tests made by the experimenter. The effects of using film stills of varying densities can be tried and the limiting factors associated with the detail permitted by thirty-line scanning observed.

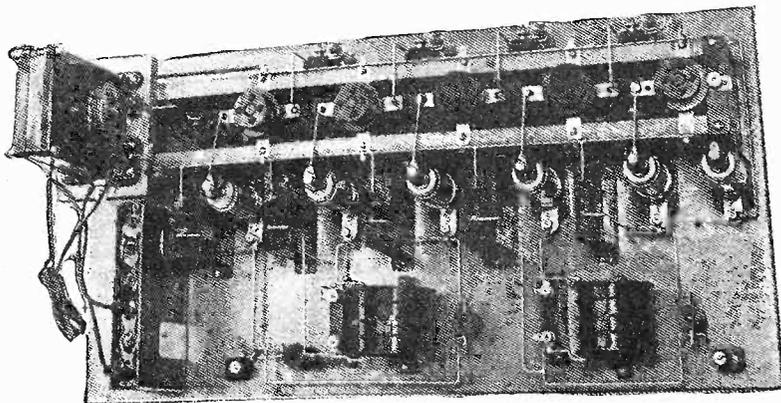


Fig. 2.—A photo-electric cell amplifier layout which avoids unwanted capacity and keeps connecting leads short.

**VALVE TYPES AND USES**

*(Continued from page 719)*

current "load," and, therefore, the H.T. supply must be capable of providing up to the maximum current taken by the valve without its voltage dropping.

**The High-tension Supply**

There is no difficulty in securing this result when using a large-capacity H.T. battery or an H.T. accumulator, but conditions are vastly different when a standard-capacity battery or an eliminator is concerned. The small battery will certainly give the maximum current, but in doing so its voltage will drop appreciably, especially when the battery has been in use for a short time. It will be evident, therefore, that the very efficient QP valve is wasted if the H.T. supply is inadequate; in addition to this it must be pointed out that small batteries would prove very expensive, whereas the cost of H.T. current is extremely moderate where a super-capacity battery is employed.

The average eliminator is even worse than a small battery with regard to the voltage output in various conditions of "load," so that if this kind of unit were employed reproduction would be terribly distorted,

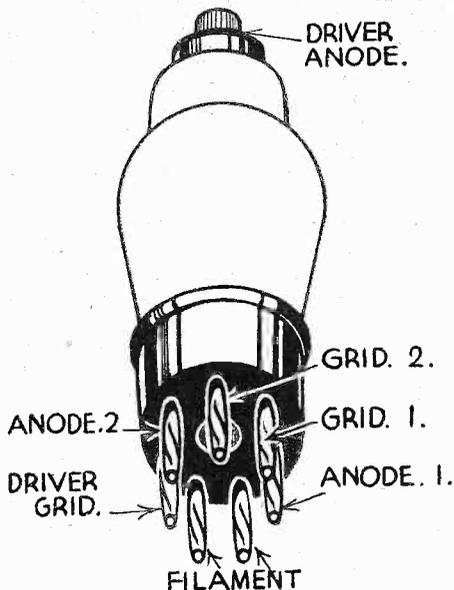


Fig. 3.—This sketch shows the connections for the driver and Class B valve.

and the user might condemn Q.P.-P. as unsatisfactory—which it certainly is not. Eliminators especially suitable for Q.P.-P. working are available and cost little more than those of normal type, whilst an existing unit can be modified by connecting a neon stabiliser across its output terminals. Actually there are a few simple points to be considered in doing this, but these were clearly explained in an article in PRACTICAL WIRELESS dated November 18th, 1933.

Little has been said in this article concerning Class B amplification, chiefly because class B is so well known and has been adequately described in many previous issues of both of the journals which have now come together under the name of PRACTICAL AND AMATEUR WIRELESS. The connections for a Class B and driver stage are shown on another page in this issue under the heading "Valve Couplings," whilst the connections for the 7-pin base are given in Fig. 2 which accompanies this article.

The Hivac B 230 Class B valve, of which characteristics are given in an accompanying panel, is particularly economical in  
*(Continued on page 733)*

*Have a Capstan!*



10 FOR 6<sup>D</sup>  
20 FOR 11<sup>D</sup>  
Plain or  
Cork Tipped

*— you'll  
like it better*

*For  
Pipe  
Smokers*

WILLS'S **CAPSTAN** NAVY CUT TOBACCO  
READY RUBBED  
2-OZ. POCKET AIRTIGHT TIN 2/2

Issued by The Imperial Tobacco Company (of Great Britain and Ireland), Ltd.



C.C. 463

# FACTS & FIGURES

*Components tested in our Laboratories*
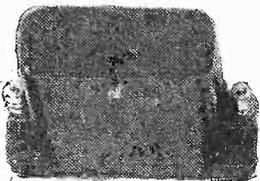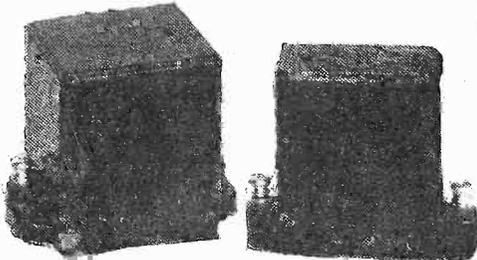
## Amplion Fixed Condensers

WE have recently had under test a number of fixed condensers made by Amplion (1932) Ltd. Of neat appearance they are certainly a very workmanlike job, which is the keynote of components turned out by this well-known firm. Obtainable in four types, TB, SH, RH and PH, respectively, they range from .1 mfd. to 4 mfd., at varying prices. Type TB (700 volts D.C. test, 350 volts D.C. working) range in price from 1s. 10d. to 5s. 6d.; type SH (1650 volts D.C. test, 600 volts D.C. working) 2s. 6d. to 10s. 6d.; type RH (2,000 volts D.C. test, 800 volts D.C.



*A group of Amplion fixed condensers which are of neat appearance and sound design.*

working) 2s. 9d. to 15s., and type PH (2,500 volts D.C. test, 1,000 volts D.C. working) 3s. 6d. to 19s. 6d. Under test they were found to give very good results under their stipulated working voltage and their capacity ratings were within a small percentage margin of the measured values.

## A General-purpose Triode

THE range of Mullard "Universal" (A.C./D.C.) valves has recently been augmented by the release of a general-purpose triode, known as type H.L.13. The principal application of this valve will be as low-frequency amplifier following a diode detector, in which position it may also be employed as first low-frequency amplifier for gramophone reproduction. It can also be used as speech detector in cases where an amplifying detector is required, and in such instances, also, the valve can be used as the input valve for gramophone reproduction. Like the other valves in the Mullard A.C./D.C. range, the H.L.13 has a heater rated at 0.2 amp., the heater voltage being approximately 13. The characteristics at anode volts, 100, and grid volts, zero, are: anode impedance 10,000 ohms; amplification factor 40; and mutual conductance 4.0 mA./V. The price is 13s. 6d. This valve is available with metallised bulb only, and has the standard Mullard side-contact base, the control grid being connected to a top thimble terminal.

## A High-class Radiometer


THE "Pifco" de luxe model "All-in-One" radiometer is a moving-coil instrument suitable not only for testing battery receivers, but also for testing all-mains sets. It is suitable for voltages up to 250 and shows 500 ohms resistance per volt. The diameter of the dial is 2½ in. The instrument is finished in mottled bakelite, and is sold complete with velvet-lined case at £2 2s. Adaptor sockets for use in testing 7- and 9-pin valves are available at 3s. This is a most useful instrument for the dealer, the experimenter, and the electrician. Particular care has been given to finish, accuracy, and high-class workmanship. In short, this expertly-designed instrument is suitable for the accurate testing of all classes of electrical and radio apparatus.

## A New H.T. Battery

THE Fuller Accumulator Co (1926) Ltd., are now manufacturing a new Fuller "Sunbeam" high-tension battery, supplies of which are now on the market. The prices are: 60 volt, 3s. 6d.; 100 volt, 5s. 6d.; 120 volt, 6s. 6d. Samples of these batteries have been subjected to various tests in our laboratories and have proved to have a capacity fully equal to that of the average standard-capacity battery.
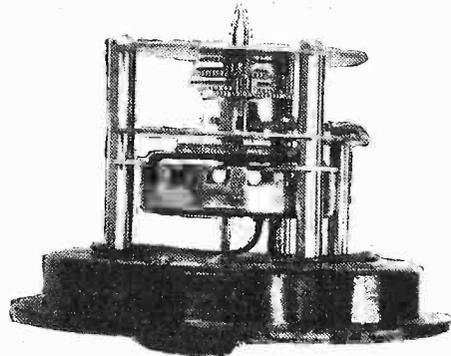
## A Synchronous Clock Movement

WE show on this page a scientifically designed electric-clock movement recently produced by the Automatic Coil Winding Co., which can easily be fitted into an ordinary clock in place of the clockwork movement. The movement is fitted with a 15 per cent. cobalt-steel magnet, and the epicycloidal cut gears ensure silent running. Of robust design it is mounted on a mottled bakelite back, through which project a knurled knob for starting the motor when connected to the mains, and a second knob for adjusting the hands. Below these knobs are fitted two pins, with the necessary plug for facilitating connection to the mains supply. Three fixing holes are drilled in the back, thus making it possible to fix it securely



*Of efficient workmanship, this synchronised electric-clock movement can be fitted to an ordinary clock in place of the clockwork movement with which it was originally fitted.*


inside the desired clock case. Selling at the reasonable price of 15s. it will keep very accurate time, and is certainly a useful appliance.

## The Erie Volume Control

THE Erie volume control, which is fitted with a composition type resistance element, is available in five standard sizes, ranging from 25,000 ohms to 500,000 ohms in value. A thin bakelite disc 1½ in. in diameter forms the body of the component, and to this are attached the three soldering tags, a single-hole fixing bush, and the metal protecting cover.

The moving contact is insulated from the spindle and fixing bush, and consists of a light spring terminating in a small graphite

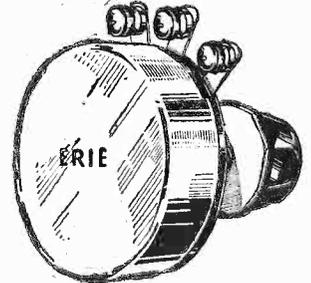
*An Erie volume control which is available in five standard sizes ranging in value from 25,000 ohms to 500,000 ohms.*



stud. The movement is quite smooth, yet a sure contact is made throughout, the pressure being just sufficient to ensure this, but not so heavy that it imposes undue wear on the element. The resistance is graded to give a smooth and even control, and is quite silent in operation. The price of the Erie volume control is 3s. 6d., or with mains switch, 5s.
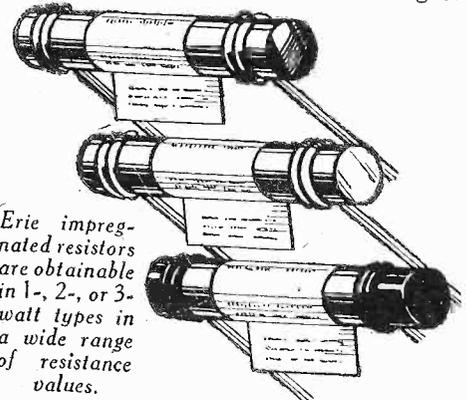
## Erie Impregnated Resistors

ERIE resistors, which are suitable as grid leaks as well as for voltage-dropping and grid-bias purposes, are made of a composition of carbon and rare earth, the resistance depending upon the quantities of the minerals. Stability of resistance is obtained by a special process by which damp is expelled, after which the resistors are specially impregnated to ensure that variation of humidity in the atmosphere does not affect the resistance value. The tips of each carbon resistor are copper impregnated to ensure a good



*Erie impregnated resistors are obtainable in 1-, 2-, or 3-watt types in a wide range of resistance values.*

soldered joint for the lead which makes contact with it. They are obtainable in one-, two-, and three-watt types in a wide range of resistance values.

Erie resistors are colour coded, and every genuine Erie carries a label giving the value. Price: 1s. per watt.

Prepare for the Television Boom:

Read the  
**TELEVISION AND SHORT-WAVE  
HANDBOOK—5/-.**

5/6 by post from Geo. Newnes, Ltd., 8-11, Southampton St., Strand, London, W.C.2

# RADIO CLUBS AND SOCIETIES

Club Reports should not exceed 200 words in length and should be received First Post each Monday morning for publication in the following week's issue.

## ANGLO-AMERICAN RADIO AND TELEVISION SOCIETY

THE midnight radio party held by the West Middlesex and East Buckinghamshire branch of the Anglo-American Radio and Television Society was held on January 18th instead of the 19th.

WCAU was the best station tuned in, although WBZ, WJZ, WTIC, and WBT were good seconds. Among the stations heard were WAAB, Boston (500 watt); WHN, New York; WCCO, Minneapolis; WHAS, Louisville; WGY, Schenectady; WLW, Cincinnati; WEAF, New York; WIOD, Miami; WNAC, Boston; WHO, Des Moines; KYW, Chicago; WABC, New York; WHAM, Rochester; and WTAM, Cleveland. The meeting held on the 17th was also a success.

There are no charges in connection with joining the A.-A.R. and T.S., and particulars may be obtained from Leslie W. Orton, "Kingsthorpe," Willowbank, Uxbridge.

At 8 p.m. on February 6th the Huddersfield branch of the Society is giving a public lecture-demonstration. The lecturer will be Mr. J. Louis Orton, who will describe some interesting radio experiments, using G-5XK for transmission. Full particulars from Mr. Leonard Goucher, 10, West Grove Avenue, Dalton, Huddersfield.

## INTERNATIONAL SHORT-WAVE CLUB (LONDON)

THE London Chapter held a very interesting meeting on Friday, January 18th, at the R.A.C.S. Hall, Wandsworth Road, S.W.8. The first half was given to Morse instruction, there being one class for beginners and another for advanced pupils. The second half of the meeting was taken up by a demonstration and description by Mr. W. H. S. Vincent, A.M.I.E., of the "Hyvolstar" All-wave Superhet 5. The circuit consisted of a heptode frequency changer, var.-mu pentode, I.F., metal oxide second detector, metal oxide A.V.C. rectifier, triode I.F., pentode output, and half-wave valve rectifier. Very good reception was obtained from W8XK, 48.86 metres. The aerial in use at the Chapter is an inverted V.—A. E. Bear, Secretary, 10, St. Mary's Place, Rotherhithe, London, S.E.16.

## THE CROYDON RADIO SOCIETY

AT a meeting of this society, held on January 15th, in St. Peter's Hall, South Croydon, Mr. O. Tooth gave a talk on "Modern Gramophone Recording." After showing the meeting a wax disc prior to being recorded upon, he went on to consider apparatus used in recording. First came the microphones which were wired and followed by the amplifier, and ultimately the cutter. He had much to say on microphones, having brought several models with him, and interesting points of such types as the Rein and Condenser microphones were followed with interest. Cutters came in for much mention, and Mr. Tooth drew sketches of their mechanism, explaining why the cutting edge of sapphire was ground by a specialist.

On Tuesday, February 5th, the vice-chairman, Mr. W. J. Bird, is lecturing on "Electrical Condensers: a brief survey of their theory, manufacture, and application to modern circuits." He is an authority on this topic, and PRACTICAL AND AMATEUR WIRELESS readers are invited to come and hear him.—Hon. Secretary, E. L. Cumbers, Maycourt, Campden Road, South Croydon.

## SLADE RADIO

AT a meeting of the Slade Radio Society on Thursday, January 17th, Mr. D. A. Drew, a member of the amateur crew who sailed Mr. Sopwith's Endeavour in races against Rainbow in America last year, gave an address upon the mechanical and electrical side of yacht racing. Mr. Drew described many of the amusing episodes that happened to him and his colleagues, and gave some very interesting descriptions of the wind-measuring instruments and other mechanical apparatus, such as the capstans, and methods of tensioning the hawsers.

Dr. Ratcliffe loaned and operated his cinema projector, and Mr. Drew had two rolls of films which he obtained from Mr. Sopwith, in London.—Hon. Secretary, Chas. Game, 40, West Drive, Heathfield Park, Handsworth, Birmingham.

## SHORT-WAVE RADIO AND TELEVISION SOCIETY (THORNTON HEATH)

A MEETING of this society was held at St. Paul's Hall, Norfolk Road, on Tuesday, January 15th, under the chairmanship of Mr. R. E. Dabbs. Mr. J. L. Hills, of All-wave International Radio and Television Ltd., gave a talk and demonstration on the Allwave international superheterodyne. This receiver tunes from 14-2,000 metres and incorporates high-speed automatic volume control. Two I.F. stages are used, followed by two diode detectors in push-pull, one L.F. stage, and power pentode output. It can be used on either D.C. or A.C. mains, and has provision for an additional speaker. The receiver was then demonstrated and it created a good deal of interest. Particulars of future meetings can be obtained from the Secretary, Mr. Jas. T. Webber, 368, Brigstock Road, Thornton Heath.


# EASY TERMS

We specialise in the supply of all good quality Radio sets, components and accessories on easy terms. Send list of requirements and keen quotation will be sent promptly. Cash and C.O.D. orders despatched by return of post.

SEND 7/-
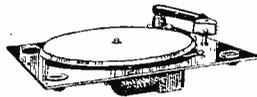
## GARRARD RADIO-GRAM UNIT

Model A.C.6, complete with volume control ready for use. This unit converts any radio receiver into a high class radio-gram.



Cash Price £4.0.0, or 7/- with order and 11 monthly payments of 7/4.

SEND 5/-

## ATLAS H.T. ELIMINATOR

Model T 10/30 with trickle charger. For QPP and Class "B" and all types of sets. Output 30 Milliamps, 3 HT tapplings.



Cash Price £3/9/6, or 5/- with order and 12 monthly payments of 5/11.

SEND 2/6

## W.B. STENTORIAN

### VALVES.


Every type of valve replacement supplied on convenient terms.

3-Valves Mullard, Cossor, Marconi. S.G. Det. Power. Cash Price £1/5/0, or 5/- with order and 5 monthly payments of 4/7.

Revitalise your set with Senior P.M. Speaker.

Cash Price £2/2/0, or 2/6 with order and 11 monthly payments of 4/-.

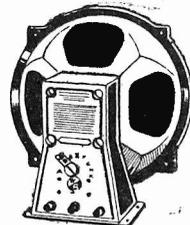Standard P.M. Speaker. Cash Price £1/12/6, or 2/6 with order and 11 monthly payments of 3/-.



Epoch 20 CP Unit 35/-.

Rola P.R.7 PM-24 Unit 49/6.

Rothermel Tweeter Unit R-155 21/-.

The above supplied on lowest terms.

## SHORT-WAVE CONVERTER

Telex Short-Wave Converter with Valve, for battery receiver. Cash Price £2/18/0, or 6/6 with order and 11 monthly payments of 5/3.

6/6 Secures delivery

8/- extra if required for Mains Receiver.

This is the best short-wave converter on the market.

5/6 Secures delivery

New Rothermel-Brush Piezo-Electric Pick-up. Cash price £2/2/0, or 5/6 with order and 8 monthly payments of 5/-.

## AVOMINOR TEST METER

5/- Secures delivery

A most valuable instrument enabling faults to be rapidly traced. Cash Price £2/0/0, or 5/- with order and 7 monthly payments of 5/9.

Full specification and illustrated list of any of the above will be sent on request.

ALL CARRIAGE PAID.

ESTD - 1925

THE PHONE NAT 1977

# LONDON RADIO SUPPLY CO

11, OAT LANE, NOBLE ST, LONDON, E.C.2

# THE OUTLINE OF WIRELESS

By RALPH STRANGER

8/6 net.

The author has an easy and informative style coupled with a thorough knowledge of his subject and the rare faculty of presenting scientific facts in simple language. The result is a book which covers the theory and practice of Wireless Reception from A to Z and makes everything plain, even to the most "non-technical" reader. Fourth Edition, revised and up to date. 816 pages, profusely illustrated. A complete work of reference which should occupy a prominent place in every wireless enthusiast's library.

From all Booksellers or by post 9/- from


GEORGE NEWNES LTD.

8-11 SOUTHAMPTON STREET, STRAND, LONDON, W.C.2

**TROUBLE  
FREE!!  
SERVICE WITH THE NEW  
HEAYBERD  
MAINS UNIT  
150 VOLTS AT 15-50 MA.**

Voltage regulation practically constant throughout the whole range of current. Suitable for any set from a one valve to a seven valve superhet. Specially suitable for Class 'B' and Q.P.P. working. **FREE FROM ALL HUM AND BACKGROUND**  
**GUARANTEED 3 YEARS**

PRICE  
88/6

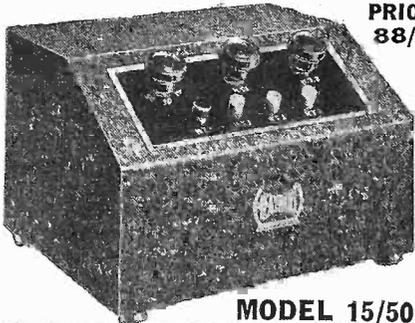

MODEL 15/50

SEND NOW FOR FREE DESCRIPTIVE LISTS.

Mr. ....


Address.....

..... PRA

**F. C. HEAYBERD & Co.** 10 FINSBURY ST.,  
LONDON, E.C.2.
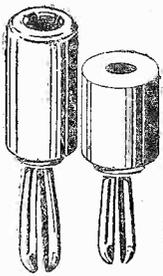
# CLIX

Specified by Mr. F. J. Camm for the  
"HALL-MARK" SERIES



### CLIX "MASTER" PLUGS.

Give firm grip and full contact with ALL sockets with internal diameters from  $\frac{1}{4}$  in. to 5-32 in. battery socket. Curved ends for easy insertion. H.T. or C.B.  $1\frac{1}{2}$ d  
Each.....



### CLIX SPADE TERMINALS.

Positive metal-to-metal wiring is fully protected from creeping acid by a specially designed collar making corrosion impossible. 2d each

### CLIX TERMINAL STRIPS

Aerial-Earth 7d. Loudspeaker-Pick up 8d.


### CLIX CHASSIS MOUNTING VALVE-HOLDERS

4-pin ..... each 8d.

5-pin ..... " 9d.

7-pin ..... " 1/-.

CLIX LIST "N" FREE

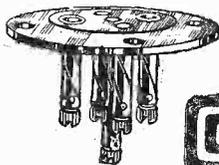

# CLIX

LECTRO LINX, LTD.,  
79<sup>a</sup> ROCHESTER ROW LONDON S.W.1

# PRACTICAL LETTERS FROM READERS

The Editor does not necessarily agree with opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## Listening Conditions in S. Africa

SIR,—As a regular reader of your paper I have been very interested in your £5 superhet, especially the A.C. model. The only snag so far as South African readers are concerned is that the coils are practically no use to us. Our listening is done on the medium band and the various short-wave bands on 16, 25, 31, and 49 metres. On the medium waves our stations lie between 314 metres and 536.

I am therefore writing to ask whether it would be practicable to substitute other coils in place of the coils specified.

We find that the ordinary straight set (I use a four-valver of my own design) gives excellent results so far as power is concerned, but selectivity, particularly on the 25m. band, leaves much to be desired; for example, it is practically impossible to separate DJD and GSD. When one is tuned in there is a background of the other and, if the aerial is swaying at all, they come in and out alternately. This presumably would be largely rectified by using a superhet circuit.

It is for this reason that American sets hold such a prominent place in the market out here. For some time "all wave sets" have been on the market. The British sets, on the other hand, are for long and medium waves, and it is necessary to obtain a short-wave convertor, which many people will not be bothered with.

The British components and valves are recognised as vastly superior, and many more would build sets if they could find a design suitable for the conditions prevailing in this country. The same would apply to Australia and Canada. One dial tuning would be essential to make it a true family set.—GEO. K. MALLORY (King William's Town, S. Africa).

[An article in our issue dated January 26th, 1935, gives particulars of suitable alternative coils for use with the £5 A.C. Superhet.—ED.]

## Australia and U.S.A. on a "Practical Wireless" One-valver

SIR,—A few weeks ago I wrote to you mentioning the good short-wave reception I had last summer on the s-wave set that was described in PRACTICAL WIRELESS of April 14th, 1934.

Having become accustomed to the use of a three-valve S.W. set of late, I thought I would give the above-mentioned one-valve set a trial as a change to the more elaborate three-valver. Appended are a few of the long-distance transmissions heard. On Friday, January 11th, at 11 p.m., PRF5, Rio de Janeiro, Brazil (31.58 m.) was a good signal at R8 on the 'phones, when we had a short talk in English on cocoa production in Brazil.

On Sunday, January 13th, at 2 p.m., VK2ME (31.28 m.), Sydney, Australia, was in fine form, opening with the laughter of the kookaburra (transmission 4), then followed the call signal "VK2ME, Sydney, the Voice of Australia," and "Good afternoon listeners in the United Kingdom." Then followed an interesting programme of gramophone records by such well-known bands as the B.B.C. Wireless Military Band, the Regimental Band of H.M. Grenadier Guards, The Australian Common-

wealth Band, Eric Coates and the Symphony Orchestra, and organ recitals by Nicholas Robins at the Arcadia Theatre, Chatwood, Sydney.

This transmission was concluded at 4 p.m. The same evening at 5.20 p.m. I located W2XAF, Schenectady, U.S.A., on 31.48 m., coming over with some punch behind it! A talk was in progress by the Federal Housing Committee, and was followed at 5.30 p.m. by a "Watch Tower Hour" service from Los Angeles, California. In conclusion I would like to thank you for the helpful hints and tips about short-wave reception that have appeared in PRACTICAL AND AMATEUR WIRELESS recently.—STEPHEN J. KEEN (Cirencester)

## "Admirable and Entertaining"

SIR,—Good luck to your admirable and entertaining journal, which I think strikes the right note every time. When can we expect an A.C. version of the "Hall-Mark Three" please?—CHAS. H. WOODS (London, E.).

[See last week's issue for full particulars of the A.C. Hall-Mark.—ED.]

## A South-African Reader's Thanks

SIR,—I wish to extend to you my sincere thanks for having put me in touch with numerous readers of PRACTICAL WIRELESS, who reside in England. Owing to various reasons, I am unable to communicate with every person who has written to me, but I would nevertheless like to thank everyone who has taken the trouble to write.—H. CROUCH (Ladysmith, S. Africa).

## Another Appreciation from S. Africa

SIR,—In connection with your various presentation schemes in *Practical Mechanics* I wish to thank you for the two books and the Wireless Constructor's Tool Kit just received. The books are interesting and entertaining, and the tool kit is very useful, and quite the thing in these out-of-the-way places, where the nearest third-rate shop is over twenty miles away. I see there are two more papers—*Practical Television* and *The Practical Motorist*. Is it possible to get these papers from No. 1, and what is the yearly subscription, please?—[Yes—ED.]

As an interested reader of Mr. F. J. Camm's articles in *Work* years ago, and later in the *Motor Cyclists' Review*, I am pleased to see him at the helm of *Practical Mechanics*, and wish it continued success. I have written to Peto-Scott for a 5-valve superhet set, as described in the June issue of *Practical Mechanics*, and will let you have a note regarding its possibilities when I try it out.—GEO. SCHOFIELD (Natal, S. Africa).

## Our Short-wave Section

SIR,—As a regular reader since No. 1 I agree with A. Blakeley (Newton-Le-Willows), who asks for one more page on short-wave work. I am writing for myself and four friends. I have all your gift books and they are very helpful. I use an adaptor (2 L.F.) for short waves, and although I have tried many circuits, I do not seem to get satisfactory results. Will you please publish

(Continued on facing page)

(Continued from facing page)

a circuit of superhet adaptor using short-wave plug-in coils. I have not built any of your sets yet but hope to when circumstances permit. I live in a swamp area ten miles from Moorside Edge, and get good results using SG., Det. 2 LF. and a wave-trap. I like your superhet 3, and I think that PRACTICAL WIRELESS is the best book of its kind on the market.—H. R. BUTTERWORTH (Oldham).

(See Special Announcement on page 701—Ed.)

**A Super Set**

Sir,—With reference to several of your readers' pleas for a super set, may I offer my suggestions? I am of the opinion that a set as outlined below would find plenty of support from your readers, and if the L.F. unit was published first, the total cost would be divided over a period, and so by adding a simple bandpass aerial filter it could easily be made into a high quality local station receiver, besides reproducing records for use with a "mike."

I am personally anxious to see a circuit published, which with an automatic record changer would make an outstanding set. The features embodied should include a paraphase amplifier of above 5 valves, giving approx. an output of 4/5 watts. Response curve nearly flat from 50 cycles to 6,000 or more. Reproduction as distortionless as possible. Sufficient amplification for use with an average pick-up. Effective volume control, and facilities for high-tension connection to H.F. stage. The circuit for the paraphase amplifier could be similar to the one published on page 101 of the issue for October 6th, 1934.—W. J. ABBOTT (Clapham Common).

**A Quality Short-waver**

Sir,—With reference to a letter, "A Short-waver Wanted," in your issue of November 17th last, I consider that a short-wave design, with the medium band as a secondary consideration, is what is wanted in Kenya, and suggest a really powerful battery-driven superhet which will enable the most distant stations to be picked up at programme value. Personally, I should like a design that does not try to cut down the initial cost too closely.—D. B. CRAMPTON (Cherangani, Kenya Colony).

CUT THIS OUT EACH WEEK.

*Do you know*

- THAT electrolytic condensers can be used in a voltage-doubler rectifier circuit?
- THAT the polarity of the voltage applied to certain electrolytic condensers may be reversed without causing damage?
- THAT an earth lead can be used for an aerial by connecting it to the aerial terminal?
- THAT a long earth lead should be insulated?
- THAT the peak-voltage rating of a fixed condenser should be at least twice the voltage normally applied to the condenser?
- THAT the use of a choke-capacity output filter often prevents L.F. instability?

The Editor will be pleased to consider articles of a practical nature suitable for publication in PRACTICAL AND AMATEUR WIRELESS. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL AND AMATEUR WIRELESS, Geo. Neuenes, Ltd., 8-11, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

**CATALOGUES RECEIVED**

To save readers trouble, we undertake to send on catalogues of any of our advertisers. Merely state, on a postcard, the names of the firms from whom you require catalogues, and address it to "Catalogue," PRACTICAL AND AMATEUR WIRELESS, Geo. Neuenes, Ltd., 8-11, Southampton St., Strand, London, W.C.2. Where advertisers make a charge, or require postage, this should be enclosed with applications for catalogues. No other correspondence whatsoever should be enclosed.

**MAGNUM COMPONENTS**

WE have received a folder from Burne-Jones and Co., Ltd., giving particulars and prices of this firm's chassis assemblies, coils, switches, etc. Also included in the list are metal screening boxes, solid dielectric variable condensers suitable for tuning, reaction, or series aerial use; a dissolver for controlling the volume of radio-gramophones, or two pick-ups; and a neat and efficient multi-contact switch. Copies of this folder are now available, on request.

**BOOKS RECEIVED**

**BROADCAST TALKS**

A BOOKLET containing the B.B.C. programme of talks to be given from Droitwich National and London Regional transmitters during the present session is now available to the public.

The series on India provides the most imposing list of speakers. The talks will be in the National programme at 10 p.m. on consecutive Tuesdays and Fridays until February 5th. The remaining speakers in this series are: Mr. George Lansbury and Mr. Stanley Baldwin.

Details of a further series of talks to be given on alternate Sundays at 9 p.m. are also given. These talks will include news from the Law Courts, headlines from foreign newspapers, extracts from Blue Book publications, important new scientific discoveries, etc. Particulars of other talks to be given for listeners in unemployed clubs and centres are also included. The booklet can be obtained free from the Publications Dept., B.B.C., or any local B.B.C. office.

**NEW FEATURES IN THE PRACTICAL ELECTRICIAN'S POCKET BOOK**

SOME of the most important of the new sections in the "Practical Electrician's Pocket Book, 1935" are evidence of the rapid changes in the electrical industry. Noise measurement appears for the first time. A complete new chapter on traffic signalling is introduced. The wiring notes are based on the 10th Edition of the I.E.E. Regulations. Trolley buses are discussed in the chapter on tramways.

Complete revision has been made of the sections on the control of lighting circuits, joints, and connectors, measuring instruments, armature construction, and railway signalling.

In addition, Mr. A. P. M. Fleming, C.B.E., M.Sc., M.I.E.E., F.Inst.P., has contributed a valuable twenty-page summary of the high spots of electrical progress in 1934.

The system, introduced last year, of sectionalising the sixty chapters is retained, and rearrangements have been made to give more logical order and to assist general study of any one department of electrical activity.

By means of the 1,000-subject index any obscure electrical fact can be found in a moment. There is also an extensive guide to mains-voltages in the United Kingdom covering sixty-two pages and indexing 5,000 places. This guide has been fully revised and brought right up to date.

The book is a little giant of information on a wide variety of subjects and well maintains its position as one of the leading reference books of the industry. It is published at the very reasonable price of 2s. 10d. post free by Odhams Press Technical Book Department, 85, Long Acre, London, W.C.2.

**THE 1935 BROADCASTER ANNUAL**

AN encyclopaedic survey of the Radio Industry and its technicalities is given in the 1935 edition of the "Broadcaster Radio and Gramophone Trade Annual," just published by the Broadcaster and Wireless Retailer, of 29, Bedford Street, Strand, London, W.C.2. Much of this work has gone into the technical sections. Radio Servicing, to which thirty pages are devoted, is divided into four "chapters."

Radio design is looked after by two abacs, a section on simplified circuit design, three pages of essential electrical formulae and data, and a valve chart giving detailed characteristics of every valve on the market.

There are six parts of the Annual which contain directory information. The Directory Section proper has nearly eighty pages. It gives manufacturers' and wholesalers' names, addresses, telephone numbers and telegraphic addresses; an index of trade names in radio, and a section giving the names of all firms making standard types of apparatus.

**IF YOU WANT  
A BLUEPRINT—  
CONSULT OUR BLUEPRINT  
SERVICE**

(See page 736)

**VALVE TYPES AND USES**

(Continued from page 729)

respect of both high-and low-tension requirements, but the same remarks apply as in the case of the QP valve with regard to the source of H.T. supply, because the anode current is constantly varying with the volume of reproduction.

**A Combined Driver-Class B Valve**

Another Class B valve that is made only by Hivac is the DB 240, and this is of particular interest in that it actually consists of three valves in one—a triode L.F. driver and two Class B triodes. The valve can thus be used directly after a detector valve, the usual input L.F. and driver transformers being connected as in the case of a normal Class B amplifier. The driver-class B valve has a 7-pin base, the connections being as shown in Fig. 3; whilst an eighth connection is made to a terminal mounted on top of the bulb; this is in contact with the anode of the driver section. It will be seen from the tabulated details that the total quiescent current passed by the complete valve is 5.5 milliamps, whilst the average working current is 8.5 milliamps. The Class B section is exactly the same as the B 230 and, apart from its external appearance, the valve may be considered as identical in every respect with two separate normal valves of the L.F. and Class B type. It is extremely convenient, especially in portable receivers or others in which space is limited.

**ROUND THE WORLD OF WIRELESS**

(Continued from page 702)

**Proposed S.B. Programmes for Morocco and Algeria**

WITH the completion of an underground pupinised cable some 2,500 kilometres in length, between Tunis and Morocco, it is hoped in the near future to effect exchanges of broadcast programmes between Radio Maroc and Algiers, and later with the new transmitter to be erected in Tunisia by the French Colonial Authorities. As the power of the Rabat and Algiers transmitters is to be increased, the programmes would be available to listeners in the greater part of Southern and Western Europe.

**Broadcast Station for Singapore?**

UP to the present, British residents in the Straits Settlements have relied for their radio entertainments solely on a local amateur broadcaster; but it is now reported that an official transmitter is to be owned and operated by the municipal authorities. The station will be built and erected by two British concerns, namely, General Electric Company, Limited, and Standard Telephones and Cables, Limited. When completed this year, it will offer a regular service of radio programmes on a wavelength between 300 and 600 metres.

**Solving the Wavelength Problem**

THE Soviet Government, in addition to installing high-power stations, has decided to cover the country with a network of small, low-power transmitters, working on channels between 120 and 150 metres. As a start, over two thousand are to be erected in State farms and other agricultural colonies. As their power is low and the effective area covered not greater than about 100 square miles, little interference between stations working on common wavelengths is anticipated. The transmitters will take their main programme from Moscow.


THE BEST SPEAKER!  
FOR THE BEST SET!

# ROLA

MODEL FR7-PM-24 (49/6)

is the **ONLY**  
Speaker Specified  
by Mr. F. J. CAMM  
for the  
UNIVERSAL  
**HALL-MARK 4**

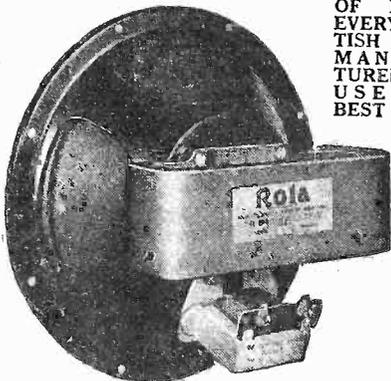Rola wish to emphasize that the above-mentioned speaker is the sole specification for this outstanding set. In order to get the best results from your Universal Hall-Mark 4 it is essential to use this Rola model. Rola quality is recognised by the leading constructor set designers as being absolutely supreme in the realm of radio reproduction. **WHY NOT FOLLOW THE LEAD**



OF NEARLY  
EVERY  
BRITISH  
RADIO  
MANUFACTURER  
AND  
USE THE  
BEST?

## EXTENSION SPEAKERS

Your dealer has a Rola Extension Speaker Showcard which shows that there is a Rola Extension Speaker which exactly matches the speaker in any British factory-built receiver. Exact matching is essential if the highest quality reproduction is to be obtained. Remember, too, that Rola Extension Speakers are absolutely dust-proof and do not employ multi-tapped transformers. The whole of the transformer is always in use, thus ensuring maximum efficiency. Ask your dealer for the correct Rola model, or write for the Rola Extension Speaker Broadsheet and Rola folder.

Model FR6-P.M.M., without transformer.... 32/-  
Model FR6-P.M. with transformer, as per our

Extension Speaker Broadsheet..... 39/6

### CABINET MODELS

Model 1 Complete with FR6-P.M. Speaker  
with transformer as per our Extension Speaker  
Broadsheet..... £3.10.0

Model 2 Complete with FR6-P.M.M. Speaker  
(without transformer)..... £3.2.6

CABINET alone (with Celotex sounding board  
attached)..... £1.10.0

# ROLA

the World's Finest Reproducers

THE BRITISH ROLA CO. LTD.

MINERVA ROAD, PARK ROYAL, N.W.10.

Phone: Willesden 4322-3-4-5-6.

A REVIEW OF THE  
LATEST RECORDS



By  
T. O'nearm

### Decca Records

THE new titles for January are not, perhaps, quite so interesting, as they have not become widely popular yet. For that reason I will not attempt to suggest a choice, but leave it to you to select your own. You will not be disappointed in any of them.

Roy Fox, who will in future be heard more regularly on the air, has also given us two new records. He has been touring the country for the best part of the past year, and in the majority of towns his band has played to capacity, beating box office records on all sides. There is no question of Roy Fox's popularity, and the sales of his records alone place him as one of England's greatest attractions.

It is my personal opinion that the singing of Denny Dennis has brought Fox still further friends. Dance vocalists are so few and far between that one only has to listen in to the majority of dance band broadcasts to wish sincerely that Parliament would immediately place a ban on crooners.

### An Amusing Record

It is interesting to pause a moment to consider this point. Have you ever heard a really good tenor, or baritone, singing a vocal dance refrain? If not, hear the record Decca made two years ago. For a joke, Al Bowlly sang the song selected by Owen Bryngwyn "Glorious Devon" and Bryngwyn sang Al Bowlly's song "Let's put out the Lights and go to Sleep" (Decca F.3369). The interesting point was that Bowlly's technique resulted in a really pleasant rendering of "Glorious Devon," whilst Bryngwyn's "crooning" appeared so amateur as to be somewhat amusing (I hope Mr. Bryngwyn will not take offence at my remarks).

This example alone proves my point. Crooners, as such, are born and not made. The chief difficulty a band has to-day is to find a good vocalist, and you may have heard of certain vocalists being shared amongst several broadcasting bands to-day. Musicians can be found with comparative ease, but vocalists have grown to become one of the most important selling factors in a band's success. For instance, when Al Bowlly left Roy Fox to join Lew Stone, Fox searched the country unceasingly, knowing that it would be impossible to get hold of one of the few accepted vocalists, as they were too strongly tied to their respective outfits. It was over a year before he chanced upon Denny Dennis, and he quickly snapped him up and has worked really hard on the boy's development. The result to-day is that Roy Fox has one of the few really pleasing dance band vocalists broadcasting.

It is interesting to look back on this somewhat new development in dance band business. Little did any of us realize the importance that the singing of the chorus would have on the sale of a dance

record. Broadcasting has, of course, enhanced this importance.

So Roy Fox, apart from his older stalwarts, such as Peggy Dell, is now a complete and best selling unit, and he is, in addition, one of the most efficient leaders in this country.

"June in January"—F.5351—is a title of which great things are expected, and I would like you to hear Fox's record of this, and "Give me a Heart to Sing to"—F.5352.

"Be Still My Heart" and "If I Had a Million Dollars," sung by Al Bowlly on Decca F.5326, is the first record of Bowlly recorded in America, and very good it is, both sides of it.

Another good record is Tessie O'Shea singing "No One Loves a Fairy When She's Forty" and "Live and Let Live" on Decca F.5336.

### The Sixteen Singing Scholars

I think that their record, Decca F.5359, will become a big novelty seller. Sixteen Welsh scholars have been selected to make this record, one of them, Master Cyril Lewis, having already made solo Welsh records for Decca. Two well-known ballads have been chosen, and these boys have performed them both as part songs, and very interesting they are. Whilst they were in London, the B.B.C. put them on the air in "In Town To-night," and I understand that they were very popular.

### Brunswick Records


A new star appears in the Brunswick list for this month. Lanny Ross jumped into prominence in the film "Melody in Spring," and there were numerous inquiries for his records. He had not, however, made any records until Brunswick gave him a contract following his success in "College Rhythm," which is shortly to be generally released in this country. "Stay as Sweet as You Are" and "Let's Give Three Cheers for Love," Brunswick O1936, is his first record, and I think you will enjoy it. The numbers are from his new film "College Rhythm."

A splendid record by the Boswell Sisters appears this month; "If I Had a Million Dollars" and "Rock and Roll," on Brunswick O1957. The titles should be good sellers, as they are from the film "Transatlantic Merry-go-round," in which the Boswell Sisters make a personal appearance. Incidentally it is the longest part they have ever played in a film, as usually they are only used to sing one or two numbers, which are usually interpolated and have little bearing on the story. The girls are, as I think I have told you, still in Hollywood, where they are broadcasting regularly with Bing Crosby on a "Commercial Hour." This is a typical Boswell Sisters' record.

Connie Boswell gives us another record, too (Brunswick O1895), "Lost in a Fog" and "Isn't it a Shame."

REPLIES TO

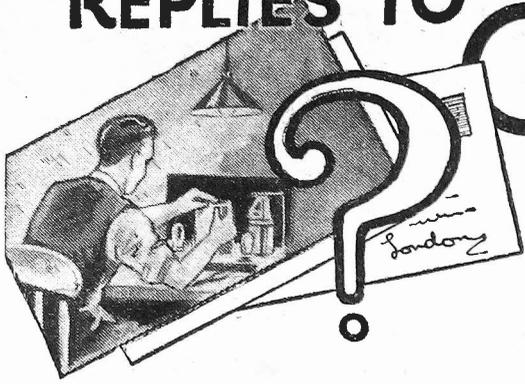LET OUR TECHNICAL STAFF SOLVE YOUR PROBLEMS



If a postal reply is desired, a stamped addressed envelope must be enclosed. Every query and drawing which is sent must bear the name and address of the sender. Send your queries to the Editor, PRACTICAL AND AMATEUR WIRELESS, Geo. Newnes, Ltd., 8-11, Southampton Street, Strand, London, W.C.2.

The coupon on Page 740 must be attached to every query.

QUERIES and ENQUIRIES by Our Technical Staff

SPECIAL NOTE

We wish to draw the reader's attention to the fact that the Queries Service is intended only for the solution of problems or difficulties arising from the construction of receivers described in our pages, from articles appearing in our pages, or on general wireless matters. We regret that we cannot, for obvious reasons—

- (1) Supply circuit diagrams of complete multi-valve receivers.
- (2) Suggest alterations or modifications of receivers described in our contemporaries.
- (3) Suggest alterations or modifications to commercial receivers.
- (4) Answer queries over the telephone.

Please note also that all sketches and drawings which are sent to us should bear the name and address of the sender.

Use For a 20-volt Rectifier

"I have just dismantled a mains receiver, and have taken from it a 20-volt, 1-amp. rectifier which was apparently used to supply the field winding of the moving-coil speaker. Could you please tell me of any use to which the rectifier could be put, and advise me if it will be suitable for charging 10-volt, 5,000 m.a.-hour H.T. accumulator units?"—J. A. P. (Liversedge, Yorks).

The rectifier unit (complete with the appropriate transformer) could certainly be used for charging purposes, and you could charge approximately eight 2-volt accumulators at 1 amp. It might also be employed for charging the H.T. units you mention by connecting four or five of these in parallel, and regulating the charging current by means of a 10-ohm variable resistance connected in series with one lead from the rectifier.

Leader Three Coils

"Could you please tell me if the twin-coil assembly recently introduced by Wearite could, with advantage, be used in place of the Wearite "Universal" coils specified in your issue?"—M. C. (Arbroath).

The coil assembly to which you refer is not suitable for the Leader Three, and we strongly advise you to employ the exact parts specified, to ensure the excellent results of which this receiver is capable.

Building A Trickle Charger

"I have recently made a mains transformer giving an output of 12 volts, and as I have a silver-oxide rectifier marked S.C.A.2 I should like to know if I can use these two parts together in order to charge a 2-volt accumulator."—B. M. J. (Swansea).

We regret to advise you that we do not know the type of rectifier you mention, and as you do not state the current and voltage rating it is not possible to say whether or not the component is suitable for use with the mains transformer that you have made. If you can give more complete details of the rectifier, at the same time stating the current output from the transformer secondary, we shall be pleased to give you further assistance.

Preventing Voltage Surge

"As I am using an indirectly-heated rectifier I have been warned that the voltage

surge on first switching on is likely to damage the transformer windings. Instead of using a thermal-delay switch I have been considering the possibility of connecting a fixed resistance across each half of the secondary winding of the mains transformer. Will this be satisfactory, or will the resistances interfere with rectification?"—H. G. (Leigh-on-Sea).

It appears that you have been misinformed; the object of an indirectly-heated rectifier is to avoid a voltage surge on the D.C. side, and this it does satisfactorily. There will no doubt be a certain voltage surge across the secondary terminals of the transformer, but this will not cause any trouble provided that the transformer is of sound construction. We do not consider it necessary to fit the resistances you mention, for there will be no harm done by the rising voltage so long as the insulation used in the transformer is adequate.

Coils For The 60/ Three

"As I am constructing the 60/- Three described in "Practical Wireless," dated December 2nd, 1933, I would like to wind my own coils and H.F. choke. Could you please supply the necessary constructional data?"—L. R. (Brentford).

We cannot, in the course of a reply through this Free Advice Bureau, give constructional details for components, and in any case would strongly recommend you to obtain the coils specified in making the 60/- Three. We might add, however, that details for making various coils were given in the series of articles published in the issues of PRACTICAL WIRELESS, dated December 9th, 1933, to January 6th, 1934, under the title, "Making Your Own Screened Coils."

A One-Valve Loud-speaker Receiver

"In the issue of your paper, dated October 20th, 1934, there appeared a very interesting article describing the construction of a one-valve receiver for universal operation. It was stated that a 16-volt D.C. valve should be used, and the circuit showed a metal rectifier. Could you please tell me the correct type of rectifier to use in this circuit as I propose to build a receiver round the design given?"—W. L. (Parkstone, Dorset).

The type of rectifier was not stated because it is not very important and there are several Westinghouse units suitable for this circuit. Actually, however, the type H.T.12 is as suitable as any, although the H.T.7 or H.T.8 could be employed.

Short-wave Coil Construction

"I should be obliged if you could give me some information with regard to the construction of a coil to cover the wavelength range from 140 to 200 metres. I have made several short-wave coils, employing valve bases for mounting purposes, and these have proved very satisfactory on every short-wave range except that mentioned. When I do wind a coil for the higher range (I never use the receiver for wavelengths higher than 200 metres) trouble is experienced due to poor reaction control or lack of selectivity."—K. A. C. (Westcliff-on-Sea).

From the particulars you give it seems that the set you are using is designed essentially for short-wave reception, and it is probable, therefore, that the detector H.F. choke is of the short-wave pattern, and is unsuitable for use on wavelengths above, say, 100 metres. If this is the case, good reception on the waveband you mention could probably be obtained by employing a new choke, of a type suitable for all-wave working, or by connecting a normal reaction choke in series with that already fitted, the new choke being placed between the previous one and the L.F. transformer.

Assuming that your coil is to be wound on a ribbed ebonite former 2in. in diameter approximately 18 turns of 22-gauge d.c.c. wire would be required for the tuned winding, and 30 turns for reaction. Both windings should consist of side-by-side turns, and there should be a space of about 1/4in. between the ends of the two.

THERE IS NO MYSTERY ABOUT THE PIX


It is a variable condenser specially designed to enable anyone to balance the capacity of the aerial circuit, and so obtain optimum selectivity on any set. Over a movement of 2ins. the range is from .000004 to .000167 mf. (Faraday House Test Report), giving easy adjustment for hair-line tuning.

BRITISH PIX CO., LTD., 118, Southwark Street, S.E.1.



WITH HANDY HOLDER 2/6



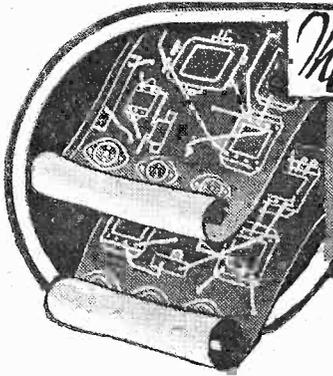

# The PRACTICAL AND AMATEUR WIRELESS Blueprint Service

These blueprints are full-size. Copies of appropriate issues of "Practical Wireless," "Amateur Wireless" and of "Wireless Magazine" containing descriptions of most of these sets can be obtained at 4d. and 1s. 3d. each, respectively, post paid. Index letters "P.W." refer to "Practical Wireless" sets, "A.W." refer to "Amateur Wireless" sets and "W.M." to "Wireless Magazine" sets. Send, preferably, a postal order (stamps over sixpence unacceptable) to "Practical and Amateur Wireless" Blueprint Dept., Geo. Newnes, Ltd., 8-11, Southampton Street, Strand, W.C.2.

### PRACTICAL WIRELESS.

<b>Blueprints, 1s. each.</b>		
Dolphin Straight Three	24.9.32	PW1
Long-Range Express Three	24.9.32	PW2
Mains Express Three	8.10.32	PW3
Sonotone Four	15.10.32	PW4
Bijou Three	29.10.32	PW5
Argus Three	12.11.32	PW6
Argus Three Mains Unit	26.11.32	PW6A
Empire Short-Wave Three	3.12.32	PW7
Solo Knob Three	10.12.32	PW8
Midget Two	17.12.32	PW9
Autokoil Pentode Two	31.12.32	PW9A
Selectone Battery Three	14.1.33	PW10
Fury Four	28.1.33	PW11
Stand-By Two-Valver	18.2.33	PW11A
Featherweight Portable Four	6.5.33	PW12
Q.P.P. Three-Four	4.3.33	PW13
Alpha Q.P.P. Three	25.3.33	PW14
Ferrocart Q.P.P. Hi-Mag Three	25.3.33 and 1.4.33	PW15
Supersonic Six	8.4.33	PW16
Beta Universal Four	15.4.33	PW17
A.C. Twin	22.4.33	PW18
Selectone A.C. Radiogram Two	29.4.33	PW19
A.C. Fury Four	25.2.33	PW20
Radiopax Class B Full	27.5.33	PW21
Three-Valve Push-Pull Detector Set	4.3.33	PW22
Double-Diode Triode Three	10.6.33	PW23
Three-Star Nicore	24.6.33	PW24
Class B Detector Two-Valver	17.6.33	PW24A
D.C. Ace	15.7.33	PW25
Arady Portable Three	15.7.33	PW25A
Superset	19.8.33	PW26
Auto-B Three	19.8.33	PW27
All-Wave Two	19.8.33	PW28
A.C. Three	16.9.33	PW29
Premier Super	23.9.33	PW30
Experimenter's Short-Wave Three	23.9.33	PW30A
A.C.-D.C. Two	7.10.33	PW31
All-Wave Unipen	14.10.33	PW31A
Orbit (Transfer Print)	4.11.33	PW32
Luxus A.C. Superhet	14.10.33	PW33
A.C. Quadpak	2.12.33	PW34
Sixty-Shilling Three	2.12.33	PW34A
Nucleon Class B. Four	6.1.34	PW34B
Fury Four Super	27.1.34	PW34C
A.C. Fury Four Super	10.2.34	PW34D
Leader Three	10.3.34	PW35
Pocket Portable	10.3.34	PW35A
D.C. Premier	31.3.34	PW35B
A.C. Leader	7.4.34	PW35C
Prima Mains Three	5.4.34	PW35D
Master Midget Two	12.5.34	PW35E
Atom Lightweight Portable	2.6.34	PW36
Ubique	28.7.34	PW36A
Four-Range Super-Mag. Two	11.8.34	PW36B
Summit Three	18.8.34	PW37
Armada Mains Three	18.8.34	PW38
Midget Short-Wave Two	15.9.34	PW38A
All-Pentode Three	22.9.34	PW39
£5 Superhet Three	27.10.34	PW40
A.C. £5 Superhet Three	24.11.34	PW41
D.C. £5 Superhet Three	1.12.34	PW42
Hall-Mark Three	8.12.34	PW43
Universal £5 Superhet	15.12.34	PW44
A.C. Hall Mark	26.1.35	PW45

### AMATEUR WIRELESS AND WIRELESS MAGAZINE. CRYSTAL SETS.

<b>Blueprints, 6d. each.</b>		
Four-station Crystal Set	31.3.34	AW427
1934 Crystal Set	4.8.34	AW444
160-mile Crystal Set	27.9.34	AW450

### STRAIGHT SETS. Battery Operated.

<b>One-valvers: Blueprints, 1s. each.</b>		
B.B.C. One-valver	28.5.32	AW344
B.B.C. Special One-valver	6.5.33	AW387
Twenty-station Loud-speaker One-valver (Class B)	27.9.33	AW449
<b>Two-valvers: Blueprints, 1s. each.</b>		
Melody Ranger Two (D, Trans)	13.5.33	AW388
Full-volume Two (SG, Det, Pen)	17.6.33	AW392
Iron-core Two (D, Trans)	29.7.33	AW395
Iron-core Two (D, QPP)	12.8.33	AW396
B.B.C. National Two with Lucerne Coil (D, Trans)	17.2.34	AW377A

Big-power Melody Two with Lucerne Coil (SG, Trans)	17.2.34	AW388A
Lucerne Minor (D, Pen)	24.3.34	AW426
Family Two (D, Trans)	Apr. '32	WM278
<b>Three-valvers: Blueprints, 1s. each.</b>		
£8 Radiogram (D, RC, Trans)	21.5.32	AW343
New Regional Three (D, RC, Trans)	25.6.32	AW349
Class-B Three (D, Trans, Class B)	22.4.33	AW386
New Britain's Favourite Three (D, Trans, Class B)	15.7.33	AW394
Home-built Coil Three (SG, D, Trans)	14.10.33	AW404
Fan and Family Three (D, Trans, Class B)	25.11.33	AW410
£5 5s. S.G.3 (SG, D, Trans)	2.12.33	AW412
1934 Ether Searcher: Baseboard Model (SG, D, Pen)	20.1.34	AW417
1934 Ether Searcher: Chassis Model (SG, D, Pen)	3.2.34	AW419
Lucerne Ranger (SG, D, Trans)	3.3.34	AW422
Coscor Melody Maker with Lucerne Coils	17.3.34	AW423
P.W.H. Mascot with Lucerne Coils (Det, R.C., Trans)	17.3.34	AW337A
Mullard Master Three with Lucerne Coils	24.3.34	AW424
Pentaquester (HF, Pen, D, Pen)	14.4.34	AW431
£5 5s. Three: Do-luxe Version (SG, D, Trans)	19.5.34	AW435
Lucerne Straight Three (D, RC, Trans)	9.6.34	AW437
All-Britain Three (HF Pen, D, Pen)	6.9.34	AW448
"Wireless League" Three (HF Pen, D, Pen)	3.10.34	AW451
Transportable Three (SG, D, Pen)	Feb. '32	WM271
Multi-Mag Three (D, 2 Trans)	June '32	WM288
Percy Harris Radiogram (HF, D, Trans)	Aug. '32	WM294
£6 6s. Radiogram (D, RC, Trans)	Apr. '33	WM318
Simple-tune Three (SG, D, Pen)	June '33	WM327
Tyers Iron-core Three (SG, D, Pen)	July '33	WM330
C.-B. Three (D, LF, Class B)	Sep. '33	WM333
Economy-pentode Three (SG, D, Pen)	Oct. '33	WM337
All-wave Three (D, 2LF)	Jan. '34	WM348
"W.M." 1934 Standard Three (SG, D, Pen)	Feb. '34	WM351
£3 3s. Three (SG, D, Trans)	Mar. '34	WM354
Iron-core Band-pass Three (SG, D, QP21)	June '34	WM362
1935 £6 6s. Battery Three (SG, D, Pen)	Oct. '34	WM371
<b>Four-valvers: Blueprints, 1s. 6d. each.</b>		
65/- Four (SG, D, RC, Trans)	17.12.32	AW370
"A.W." Ideal Four (2SG, D, Pen)	16.9.33	AW402
2 H.F. Four (2SG, D, Pen)	17.2.34	AW421
Crusaders' A.V.C. 4 (2 HF, D, QP21)	18.8.34	AW445
(Pentode and Class-B outputs for above; blueprints 6d. each)	25.8.34	AW445A
Quadradyne (2SG, D, Pen)	Feb. '32	WM273
Calibrator (SG, D, RC, Trans)	Oct. '32	WM300
Table Quad (SG, D, RC, Trans)	Nov. '32	WM303
Calibrator de Luxe (SG, D, RC, Trans)	Apr. '33	WM316
Self-contained Four (SG, D, LF, Class-B)	Aug. '33	WM321
Lucerne Straight Four (SG, D, LF, Trans)	Feb. '34	WM350
<b>Five-valvers: Blueprints, 1s. 6d. each.</b>		
Super-quality Five (2 HF, D, RC, Trans)	May '33	WM320
New Class-B Five (SG, D, LF, Class B)	Nov. '33	WM340
Class-B Quadradyne (2 SG, D, LF, Class B)	Dec. '33	WM344
<b>Mains Operated.</b>		
<b>Two-valvers: Blueprints, 1s. each.</b>		
Consolelectric Two (D, Pen) A.C.	23.9.33	AW403
Economy A.C. Two (D, Trans) A.C.	June '32	WM286

<b>Three-valvers: Blueprints, 1s. each.</b>		
Home-lover's New All-electric Three (SG, D, Trans) A.C.	25.3.33	AW383
S.G. Three (SG, D, Pen) A.C.	3.6.33	AW390
A.C. Triodyne (SG, D, Pen) A.C.	19.8.33	AW399
A.C. Zentaquester (HF Pen, D, Pen) A.C.	26.6.34	AW439
D.C. Calibrator (SG, D, Push-pull Pen) D.C.	July '33	WM328
Simplicity A.C. Radiogram (SG, D, Pen) A.C.	Oct. '33	WM333
Six-guinea AC/DC Three (HF, Pen, D, Trans) A.C./D.C.	July '34	WM364
Mantovani A.C. Three (HF, Pen, D, Pen) A.C.	Nov. '34	WM374

<b>Four-valvers: Blueprints, 1s. 6d. each.</b>		
A.C. Melody Ranger (SG, DC, RC, Trans) A.C.	4.3.33	AW380
AC/DC Straight A.V.C.4 (2 HF, D, Pen) A.C./D.C.	8.9.34	AW446
A.C. Quadradyne (2SG, D, Trans) A.C.	Apr. '32	WM279
All Metal Four (2SG, D, Pen) A.C.	July '33	WM329

### SUPER-HETS.

<b>Battery Sets: Blueprints, 1s. 6d. each.</b>		
1934 Century Super	9.12.33	AW413
Super Senior	Oct. '31	WM256
1932 Super 60	Jan. '32	WM269
Q.P.P. Super 60	Apr. '33	WM319
"W.M." Stenode	Oct. '34	WM373
Modern Super Senior	Nov. '34	WM375

<b>Mains Sets: Blueprints, 1s. 6d. each.</b>		
1934 A.C. Century Super, A.C.	10.3.34	AW425
1932 A.C. Super 60, A.C.	Feb. '32	WM272
Seventy-seven Super, A.C.	Dec. '32	WM305
"W.M." D.C. Super, D.C.	May '33	WM321
Merrymaker Super, A.C.	Dec. '33	WM345
Heptode Super Three, A.C.	May '34	WM359
"W.M." Radiogram Super, A.C.	July '34	WM366
"W.M." Stenode, A.C.	Sep. '34	WM370

### PORTABLES.

<b>Four-valvers: Blueprints, 1s. 6d. each.</b>		
General-purpose Portable (SG, D, RC, Trans)	9.7.32	AW351
Midget Class-B Portable (SG, D, LF, Class B)	20.5.33	AW389
Holiday Portable (SG, D, LF, Class B)	1.7.33	AW393
Family Portable (HF, D, RC, Trans)	22.9.34	AW447
Town and Country Four (SG, D, RC, Trans)	May '32	WM287
Two H.F. Portable, (2 SG, D, QP21)	June '34	WM362
Tyers Portable (SG, D, 2 Trans)	Aug. '34	WM363

### SHORT-WAVERS. Battery Operated.

<b>One-valvers: Blueprints, 1s. each.</b>		
S.W. One-valve	23.1.32	AW329
S.W. One-valver for America	31.3.34	AW427
Roma Short-waver	10.10.34	AW452
<b>Two-valvers: Blueprints, 1s. each.</b>		
Home-made Coil Two (D, Pen)	14.7.34	AW440
<b>Three-valvers: Blueprints, 1s. each.</b>		
World-ranger Short-wave 3 (D, RC, Trans)	20.8.32	AW355
Experimenter's 5-metre Set (D, Trans, Super-regen)	30.6.34	AW438

<b>Four-valvers: Blueprints, 1s. 6d. each.</b>		
"A.W." Short-wave World Beater (HF Pen, D, RC, Trans)	2.6.34	AW486
Empire Short-waver (SG, D, RC, Trans)	Mar. '33	WM318

<b>Super-hets: Blueprints, 1s. 6d. each.</b>		
Quartz-crystal Super	Oct. '34	WM372

### Mains Operated.

<b>Two-valvers: Blueprints, 1s. each.</b>		
Two-valve Mains Short-waver (D, Pen) A.C.	10.10.34	AW453
"W.M." Band-spread Short-waver (D, Pen) A.C./D.C.	Aug. '34	WM368

<b>Three-valvers: Blueprints, 1s. each.</b>		
Emigrator (SG, D, Pen) A.C.	Feb. '34	WM352

<b>Four-valvers: Blueprints, 1s. 6d. each.</b>		
Gold Coaster (SG, D, RC, Trans) A.C.	Aug. '32	WM292

Miscellaneous Advertisements

Advertisements are accepted for these columns at the rate of 3d. per word. Words in black face type and/or capitals are charged double this rate...

PREMIER SUPPLY STORES

ANNOUNCE a City Branch at 165 and 165a, Fleet St., E.C. (next door to Anderson's Hotel) for the convenience of callers; post orders and callers to High St., Clapham.

OFFER the Following Manufacturers' Surplus New Goods at a Fraction of the Original Cost; all goods guaranteed perfect; carriage paid over 5/-, under 5/- postage 6d. extra, I.F.S. and abroad, carriage extra.

ALL-ELECTRIC 3-stage Amplifiers, 200-250V. 40-60 cycles, 10 watts undistorted output, complete with 5 valves, and Magnavox Super 66 energised speaker, £12/10/0.

ELIMINATOR Kits, including transformer, choke, Westinghouse metal rectifier, condensers, resistances, and diagram, 120v. 20 m.a., 20/-; trickle charger, 8/- extra; 150v. 30 milliamps with 4v. 2-4 amps, C.T., L.T., 25/-; trickle charger, 6/6 extra; 250v. 60 milliamps, with 4v. 3-5 amps, C.T., L.T., 30/-; 300v. 60 m.a., with 4 volts 3-5 amps, 37/6; 200v. 50 m.a., with 4v. 3-5 amps, L.T., 27/6.

PREMIER Chokes, 40 milliamps, 25 hys., 4/-; 65 milliamps, 30 hys., 5/6; 150 milliamps, 30 hys., 10/6; 60 milliamps, 80 hys., 2.500 ohms, 5/6; 25 milliamps, 20 hys., 2/9; 250 milliamps, 30 hys., 20/-.

ALL Premier Guaranteed Mains Transformers Have Engraved Terminal Strips, with terminal connections, input 200-250v., 40-100 cycles, all windings paper interleaved.

PREMIER H.T.7 Transformer, output 135v. 80 m.a., for voltage doubling, 8/6; 4v. 3-4a, C.T., L.T., 2/- extra; with Westinghouse rectifier, giving 200v. 30 m.a., 17/6.

PREMIER H.T.8 and 9 Transformers, 250v. 60 m.a. and 300v. 60 m.a. rectified, with 4v. 3-5a, and 4v. 1-2a, C.T., L.T. and screened primary, 10/-; with Westinghouse rectifier, 18/6.

PREMIER H.T.10 Transformer, 200v. 100 m.a., rectified, with 4v. 3-5a, and 4v. 1-2a, C.T., L.T. and screened primary, 10/-; with Westinghouse rectifier, 19/6.

PREMIER Mains Transformer for H.T.11, rectified output 500v. 120 milliamps or 450v. 120 milliamps with 3, 4 volt C.T. Windings, 22/6, with Westinghouse rectifier, 42/6.

PREMIER Mains Transformers, output 350-0-350v. 120 m.a., 4v. 3-5a, 4v. 2-3a, 4v. 1-2a (all C.T.), with screened primary, 10/-.

PREMIER Mains Transformer, output 250-0-250v. 60 m.a., 4v. 3-5a, 4v. 2-3a, 4v. 1-2a (all C.T.), with screened primary, 10/-.

PREMIER Auto Transformers, 100-110/200-250v. or vice versa, 100-watt, 10/-.

WESTERN ELECTRIC Mains Transformers, 300-0-300v. 65 m.a., 4v. 1-2a, 4 v. 2-3a, 6/6; 500-0-500v. 150 m.a., 4v. 3-5a., 4v. 2-3a, 4v. 2-3a., 4v. 1a. C.T., 4v. 1a. C.T., 19/6.

SPECIAL Offer of mains Transformers, manufactured by Philips, input 100-110v. or 200-250v., output 180-0-180 volts 40 m.a., 4v. 1 amp., 4v. 3 amps., 4/6.

PREMIER L.T. Charger Kits, consisting of Premier transformer and Westinghouse rectifier, input 200-250v. A.C., output 8v. 1/2 amp., 14/6; 8v. 1 amp., 17/6; 8v. 2 amp., 27/6; 30v. 1 amp., 37/6; 2v. 1/2 amp., 11/-.

B.T.H. Trusped Induction Type (A.C. only), Electric Gramophone Motors, 100-250v., 30/- complete. D.C. model Trusped, 100/250v., 45/-.

COLLARO Gramo. Unit, consisting of A.C. motor, 200-250v. high quality pick-up and volume control, 49/-.

EDISON BELL Double Spring Gramophone Motors, complete with turntable and all fittings, a really sound job, 15/-.

SPECIAL Offer of Wire-Wound Resistances, 4 watts; any value up to 50,000 ohms, 1/-; 8 watts any value up to 15,000 ohms, 1/6; 15 watts, any value up to 50,000 ohms, 2/-; 25 watts, any value up to 50,000 ohms, 2/6.

CENTRALAB Potentiometers, 400 ohms., 1/-; 50,000, 100,000, 1/2 meg., any value, 2/- 200 ohms, wire wound, 1/-.

SPECIAL OFFER. Kolster-Brandes (shop-soiled) 2-valve Battery Pup, with self-contained Speaker, Valves and Batteries, 27/6.

AMERICAN Triple gang 0.0005 Condensers, with Trimmers, 4/11; Polar bakelite condensers, 0.00035, 9d.

RELIABLE Intervalve Transformers, 2/-; multi-ratio output transformers, 2/6; Microphone transformers, 50-1 and 100-1, 2/6; 1-1 or 2-1 Output Transformers, 2/6.

RELIABLE Canned Coils and Circuit accurately matched, dual range, iron cored, 2/11 each.

Easy Terms

ALL MANUFACTURERS' COMPONENTS and ACCESSORIES IN STOCK. SEND US YOUR ENQUIRIES

STENTORIAN STANDARD

For Power, Pentode and Class B. Send only 2/6 balance in 11 monthly payments of 3/-. Cash or C.O.D. Carriage Paid, £1/12/6. W.B. Stentorian Senior. Cash or C.O.D. Carriage Paid, £2/2/6, or 2/6 deposit and 11 monthly payments of 4/-.



ROLA F.R.5 PERMANENT-MAGNET M.C. SPEAKER


With universal tapped Transformer. Send only 2/6, balance in 10 monthly payments of 3/-. Cash or C.O.D. Carriage Paid, £1/9/6.

ROLA P.M. M.C. SPEAKER. Cash or C.O.D. Carriage Paid, £1/19/6, or 2/6 deposit and 10 monthly payments of 4/3.




GRAHAM FARISH RAIDER 3 KIT

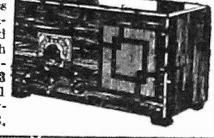Complete Kit of parts for building, lens valves and cabinet. Send only 5/-. Balance in 11 monthly payments of 6/3. Cash or C.O.D. Carriage Paid, £3/7/6. If valves and cabinet required add £2/19/6 to Cash Price, or complete for 11/3 deposit and 11 monthly payments of 11/3.




B.T.S. Universal TELEVISION MOTOR

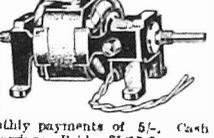For both 16in. and 26in. scanning discs. Universal A.C. or D.C. Mains, 200-240-volts. A.C. 30-60 cycles or Battery Model, 6-volt. Send only 5/-, balance in 7 monthly payments of 5/-. Cash or C.O.D. Carriage Paid £1/15/0.



ATLAS ELIMINATOR

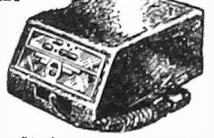Model C.A.25. For all outputs up to 25 m.a. 100/250 volts A.C. Send only 5/-, balance in 11 monthly payments of 5/6. Cash or C.O.D. Carriage Paid £2/19/6. Model T 10/30. Cash or C.O.D. Carr. Paid £3/9/6. 5/- down and 12 monthly payments of 6/-.



NEW GARRARD A.C.6. INDUCTION ELECTRIC MOTOR

Complete with 12" turntable, 12" Unit Plate and fully automatic Switch. For A.C. mains only. Send only 2/6, balance in 11 monthly payments of 4/-. Cash or C.O.D. Carriage Paid £2/2/6.



New Garrard A.C.4 A.C. Mains Electric Motor, 12-in. turntable, motor, plate, automatic stop. Cash or C.O.D. Carriage Paid, £2/2/6, or 2/6 down and 11 monthly payments of 4/-. New Garrard Model 202a. 12-in. turntable, Electric motor for A.C. mains. Cash or C.O.D. Carriage Paid, £2/10/0, or 5/- down and 10 monthly payments of 5/-.

SEND FOR LATEST LISTS New Times Sales Co. 56, (Pr. W2.) LUDGATE HILL, LONDON, E.C.4.

(Continued from foot of column one)

MAGNAVOX D.C. 152, 2,500 ohms, 17/6; D.C. 154, 2,500 ohms, 12/6; D.C. 152 magna., 2,500 ohms, 37/8, all complete with humbucking coils; please state whether power or pentode required; A.C. conversion kit for above types, 10/-; Magnavox P.M. 7in. cone, 16/6. 9in. cone, 22/6.

UTILITY 8-gang Condensers, 0.0005, fully screened, with trimmers, ball bearing shaft or superhet, 6/0, complete; with illuminated disc drive, 7/11, the best 8-gang available.

T.C.C. Condensers, 250v. working, 1 mf., 1/3; 2 mf., 1/9; 4 mf., 3/-; 4 mf. 450v. working, 4/-; 4 mf., 750v. working, 6/-; 2 mf., 750v. working, 3/-.

VARLEY Constant Square Peak Coils, band-pass type B.P.7 brand new, in maker's cartons, with instructions and diagram, 2/4.

VARLEY H.F. Intervalve Coils, B.P.S., band-pass, complete with instructions, in original cartons, 2/6.

SCREENED H.F. Chokes, by one of the largest manufacturers in the country, 1/6.

PREMIER British-made Meters, moving iron, flush mounting, accurate, 0-10, 0-15, 0-50 m.a. 0-100, 0-250 m.a., 0-1 0-5 amps.; all at 6/-.

WESTERN Electric Condensers, 250v. working, 1 mf., 1/-; 2 mf., 1/3; 4 mf., 3/-.

WIRE-WOUND Potentiometers, 1,000, 2,500, 10,000, 50,000, 500,000, 2/- each; 1,000 ohm, semi-variable, carry 150 m.a., 2/-.

LARGE Selection of Pedestal, table and radio-gram cabinets, by best manufacturers at a fraction of original cost. Send for list.

THE following lines 6d. each, or 5/- per dozen.—Chassis valve holders 3-, 6-, or 7-pin, screened screen-grid leads, any value 1-watt wire resistances, wire end condensers 0.0001 to 0.1, 3 amp. mains switches, Cydon capacitors; double trimmers.

SUPER-MOVING Coil Speakers, handle 10 watts, energised directly from A.C. mains, manufactured by world-famous radio and gramophone company, 40/-.

T.C.C. Electrolytic condensers, 8 mf. 440v. working, 3/-; 4 mf. 440v. working, 3/-; 15 mf. 50v. working, 1/-; 50 mf. 12v. working, 1/2; 15 mf. 100v. working, 1/3; 6 mf. 50v. working, 6d.; 2 mf. 100v. working, 6d.

DUBILIER Dry Electrolytic Condensers, 12 mf. 20v. working, 6d.; 50 mf. 50v. working, 1/9.

CONDENSER Blocks, H.M.V. 400v. working, C 4+2+1+1+1+1+1+1, 3/9; 2+2+1+1+1+1+1+1, 3/-; Dubilier 300v. working, 4+4+2+2+1, 3/-; Philips 6+4+2+2+1+1, 4/6.

PREMIER SUPPLY STORES Announce the Purchase of the Complete Stock of a World Famous Continental valve manufacturer, all the following standard main types, fully guaranteed, 4/6 each; H.F. Pentodes, Variable-Mu H.F. Pentodes, H.L.L. power, medium, high, low mag, and variable-mu screen-grids, one, three and four watt A.C. output, directly heated pentodes, 250v. 60 m.a., full wave rectifiers D.C. types, 20v. 18 amp., filaments, screen grid V.M. H., H.L. Power, Pentodes, H.F. Pentodes, Variable-Mu H.F. Pentodes.

THE Following Types, 5/6 each: 350v. 120 m.a., full wave rectifier, 500v. 120 m.a., full wave rectifier, 2 1/2 watt indirectly heated pentode.

THE Following American Types, 4/6: 250, 112, 171, 210, 245, 226, 47, 40, 24, 35, 51, 67, 58, 55, 37, 80, 6A7, 2A7, 83, 27.

THE Following Types, 6/6 each: 42, 77, 78, 25Z5, 36, 38, 83, 39, 44, 53, 6B7, 2A5, 2A6, 207, 5Z3, 6C6, 6A4, 6D6, 6F7, 43, 59. Send for Complete Valve list.

GRAMPIAN Permanent Magnet 9 inch Moving Coil Speakers, handles 4 watts, Universal transformers, 18/0. Ditto Energised handles 5 watts, 2,500 ohms, 21/-.

WILKINS AND WRIGHT. Full-vision dials with Escutcheon, 2 1/11.

SCOTT Aerial and Anode Coils. Dual Range with Circuit, 2/6 per pair.

ELLIOTT Moving-Coil Milliamperes projecting type, 2 1/2in. diameter, 0-10, 0-30, 0-50, 0-150, 15/-.

DARIO directly-heated 1 watt, 200v. Mains Power Valves, 2/6.

BLUE SPOT 45 P.M. Speaker, multi-ratio transformer, handles 4 watts, listed 45/-, at 25/-, or in handsome walnut cabinet, 35/-. Blue Spot 99 P.M. Speaker, multi-ratio transformer, handles 5 watts, listed 59/6, at 31/-.

BLUE-SPOT Energised Speakers, 2,500 ohms type B 29D.C., Power and Pentode Transformer, 9/11.

BLUE-SPOT P.M. Speaker with Multi-ratio Transformer, special offer, 16/-.

LISSÉN 3-gang Super-het coils with switching and circuit, 6/-.

LOTUS 8-gang Band-pass coils with switching, 12/6.

PREMIER SUPPLY STORES (Dept. G.N.), 20-22, High St., Clapham, S.W.1. Phone: Macaulay 2188. Nearest station: Clapham North, Underground.



**BIRMINGHAM RADIOMART**

**RADIOMART** Offers. Sensational Prices, Perfect Goods and a Square Deal Always.

**RADIOMART** Radiophone short-wave condensers, all brass on Steatite Bases (the finest made), offered quarter list. Single .00016, 3/6; 2 gang .00016, 5/6.

**RADIOMART** British Radiophone, fully screened 2-gang .0005, top trimmers, latest compact type, 5/11.

**RADIOMART** Radiophone 3-gang as above. 7/6.

**RADIOMART** Radiophone 4-gang superhet. 9/6. All boxed.

**RADIOMART** British Radiophone 2-gang as above, but fitted Uniknob trimming; wavelength moving scale dials, 8/3.

**RADIOMART** Polar Arcuate full vision dials. Handsome bakelite escutcheon, 3/9. Illuminated.

**RADIOMART** Polar moving scale illuminated two-colour dial; few only, 2/9 complete.

**RADIOMART** Radiophone straight line dial, latest pattern, with wavelength and degrees, two-colour dial, 3/-.

**RADIOMART** Radiophone I.F. transformers, 110kc, top trimmers, 2/6. Also few 117 and 126 kc.

**RADIOMART** Utility super 2-gang .0005, ball-bearing, fully screened, with trimmers, 5/11; with disc dial, 6/11.

**RADIOMART** Utility 3-gang, as above, straight or superhet, 6/9; with dial, 7/11.

**RADIOMART** B.T.H. 7in. latest 2,500 ohm moving coils, humbucker 4-watt model, 12/6.

**RADIOMART** Sonochorde super sensitive P.M.'s Class B or Universal (ideal battery sets), 16/6.

**RADIOMART** Pushback, the wire used by set-makers, ready timed and sleeved, 6yds. 9d.

**RADIOMART** Screened flex, H.F. or pick-up, single 6d. yd., twin, 9d. yd.

**RADIOMART** Resincored solder, 3ft. 6d. Bulgin lamp fuses, 2d. Bulgin twin fuseholders, 4d.

**RADIOMART** Non-inductive tubulars, 1, 500v., .0003, 0.02, 4d.; 0.01, 0.02, 0.04, 0.05, .1, 6d.; 0.2, 0.25, 8d.; 0.5, 9d.

**RADIOMART** Differentials; Telsen, .0001, .00015, 1/-; Polar, .0003, 1/3; ebonite panels, 16x8, 1/6.

**RADIOMART** Lissen, 12/6; chokes, 25hy., 70ma., 4/6; 32hy., output, 4/6; 3-1 pentode output transformers, 4/6.

**RADIOMART** Brand new condensers, eminent makers, 500v. working, 4mfd., 3/6; 2mfd., 1-10; 1mfd., 1/6.

**RADIOMART** 350v. working 4mfd., 2/9; 2mfd., 1/8; 1mfd., 1/4; 250v. working, 4mfd., 2/3; 1mfd., 1/2; 0.5mfd., 9d.; 0.1x0.1mfd., 9d.

**RADIOMART** Supreme battery economisers incorporating Westinghouse rectifier, halves consumption (list 27/6), 7/6.

**RADIOMART** Stal tapped Class B chokes (list 9/6), 3/6. Transformers: Ericsson (15/-), 1/3. Microphones, 2/6. Igranic Drivers, 1/11.

**RADIOMART** Air-spaced variable condensers, .0005, 1/9; bakelite, 1/3. Philips tubular, .0001, .001, 2d.

**RADIOMART** Screened iron-cored dual-range coils with reaction circuit, 2/11. Igranic short-wave iron-core dual-range, 3/3.

**RADIOMART** Telsen 1-watt wire-ended resistors, 6d. Telsen cartridge resistances, tubular condensers, 6d.

**RADIOMART** Telsen latest reaction, .0001, .00015, 10d. Lotus, .0003, 1/-; Utility, .0005, 1/3.

**RADIOMART** Special offer, dozen assorted wire-ended resistances, all different, most famous makes, our selection only, 2/6.

**RADIOMART** Triotron Class B units complete driver transformer, new B.V.A. valve (list 64/-), 32/-; Less valve, 25/-.

**RADIOMART** Regentone latest 30ma. A.C. eliminators (list £37/6), 39/6. Telsen 28ma. with 4V.A.C. (list £37/6), 37/6.

**RADIOMART** Telsen, Radiophone dolly toggle switches, 6d. Lotus radiogram switches, 9d.

**RADIOMART** Radiophone H.F. chokes (manufacturers), honeycomb wound, 1/-; Metvick, 9d.

**RADIOMART** Years of transmitting experience makes possible a specialised service in short-wave material which can be relied upon.

**RADIOMART** G.E.C. all brass, .0003 condensers with real slow motion, ideal short-wave (listed over £1), 2/9.

**RADIOMART** Western Electric, 21/-; microphones, 2/9; transformer, 2/6. Telsen dual-range short-wave coils, 2/6.

**RADIOMART** Brass ball-bearing 100mfd. short-wave condensers, pigtail, noiseless, 1/6. Extension brackets, 3d. Short-wave valve holders, 4d.

**RADIOMART** Milliammeters, flush, 2 1/2in., 5/9, 2 1/2in., 6/9. All ranges above 25 ma.

**RADIOMART** Purchase over-produced stock Leading Continental Valve Maker. Super valves, sensational prices.

**RADIOMART** A.C. types at 4/6, H.F. Pen., M.H., M.H.L., V.M.S.G., P.T.4, S.G.L.A., S.G.H.A., American A.C. types, 4/6.

**RADIOMART** 2 volt types H.F., Detector, L.F., 2/3; Power, 2/9; Super Power, 3/3; Screen-grid, Pentode, 5/6.


**RADIOMART** January Catalogue gives characteristics, all other components (largest in trade).

**RADIOMART** cannot send catalogue or answer enquiries without stamp. Goods over 6/- post free.

**RADIOMART**, The Square Dealers, 19, John Bright Street, Birmingham.

**50 ohms to 100,000**

**WIRE-WOUND RESISTORS**

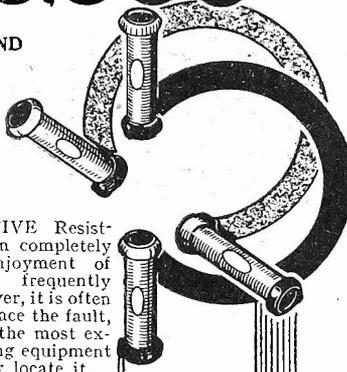

A DEFECTIVE Resistance can completely ruin the enjoyment of radio — and frequently does. Moreover, it is often difficult to trace the fault, as none but the most expensive testing equipment can definitely locate it.

When building your next set, or overhauling your present equipment, change over to Amplion resistors. They are colour coded, compact and sturdy, and all values are wire wound, this method of construction giving the most reliable and constant form of resistance.

Price 1/- each; all values.

Specified for the **A.C. HALL-MARK FOUR**

**AMPLION**

**AMPLION (1932) LTD.**  
81-84 Rosoman Street, Rosebery Avenue, London, E.C.1

There was a young fellow named Jim

Complained that his Set had gone 'dim.'

He found on inspection —

An unsoldered connection —

So **FLUXITE** put THAT right for HIM!



See that **FLUXITE** is always by you—in the house—garage—workshop—anywhere where simple speedy soldering is needed. Used for 30 years in government works and by the leading engineers and manufacturers. Of all Iron-mongers—in tins, 4d., 8d., 1/4 and 2/8.


Ask to see the **FLUXITE SMALL-SPACE SOLDERING SET**—compact but substantial—complete with full instructions, 7/6.

Ask also for Leaflet on **CASE-HARDENING STEEL** and **TEMPERING TOOLS** with **FLUXITE**

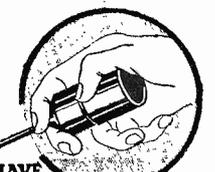**THE FLUXITE GUN**

is always ready to put Fluxite on the soldering job instantly. A little pressure places the right quantity on the right spot and one charging lasts for ages.

The Gun also projects grease into bearings, etc.; and is used for grease like an oil-can for oil. Price 1/6.



**ALL MECHANICS WILL HAVE FLUXITE IT SIMPLIFIES ALL SOLDERING**

FLUXITE, LTD. (Dept. 202), DRAGON WORKS, BERMONDSEY STREET, S.E.1.

**PEARL & PEARL**

190, Bishopsgate, London, E.C.2. All the following bargains guaranteed new goods. Cash or C.O.D. Carriage Paid.

**RECEIVERS. 3-VALVE "CLASS B" BURGOYNE RECEIVERS.** Complete with Mullard valves; Exide H.T. and L.T. batteries, M/C speaker. Artistic cabinet of highly polished Walnut. Chromium fittings. Brand new in original cartons; 1935 Model. List £6 10. Our price £3 19 6. Carriage Paid.

**SPEAKERS.** Lissen plaque speakers, wonderful tone. List 15/-. Our price 5/11. Lotus permanent magnet, with universal transformer giving 10 alternative tapings. Eight-inch cone—wonderful tone. List 27/6. Our price 14/11.

**CONDENSERS.** British Radiophone .0005 ganged, screened variable condensers with trimmers. 2-gang, 6/6; 3-gang, 8/6.

**VALVES.** Triotron (all types) G.P., 3/6; Power, 4/6; S.G., 9/6; clear or metallized; all in makers' sealed cartons.

**RADIOPAK** by British Radiophone (Type 535 C). Comprising 3 matched coils and 3-gang condenser with trimmers. Clearly engraved scale marked in metres, pilot light fitting, engraved terminal strip showing all connections. The whole mounted on grey metal chassis. Guaranteed new. Limited quantity only, at special low price of 29/6 complete.

**ELIMINATORS.** Special purchase of large quantity of Lincoln-Stewart Eliminators enables us to offer them at sacrifice prices. All models O.K. for 200-250 v. D.C. 25 milliamp output, 9/11; A.C. 30 milliamp output with Westinghouse Rectifier, etc., 24/11, or with half-amp. Trickle Charger incorporated, price only 37/6. All fully guaranteed.

**COILS.** Lincoln-Stewart screened dual-range iron cored coils; complete with circuits and wiring diagrams. List price 6/6, our price 2/6. Lotus triple-ganged bandpass coil unit, complete. Suitable for mains or battery sets. Comprises 3 screened coils on metal base, wavechange and radiogram switch; all terminal connections shown engraved. Full instructions with every unit. List 27/6. An outstanding bargain at 12/11 each. Lissen L.N.5181 3-ganged superhet coil units for A.C. or battery sets; with circuits and diagrams. Over 1,250 already sold to "P.W." readers. List price 30/-; now offered at special price, 6/6 only. ALL above post paid and guaranteed new in makers' original cartons. New Lucerne coils 1/8 each.

**CONDENSERS.** Lotus variable (2-gang .0005) condensers, screened; complete with illuminated friction drive dial, knob and trimmers. Our price, 2-gang 8/6, 3-gang 11/6.

**TRANSFORMERS.** Igranic Class B Transformers, tapped 1-1 and 1 1/2-1. List price 11/6. Our price 4/11. Amplion Class B Output Chokes, tapped 1-1, 1.5-1 and 3-1. Ideal for matching m/c speakers. List 9/6. Our price 4/11.

**CABINETS.** Ultra polished walnut receiver cabinets (for set and speaker combined). Height 17in. width 15in. Depth 8in. Only 5/11 each.

**CROMWELL Cabinets** (for set and speaker combined). Horizontal type, 23in. wide, 8in. deep, 11 1/2in. high. Polished Walnut veneer, additional baffle behind speaker grille. Just secured on terms which enable us to offer them at the astoundingly-low price of only 4/11 each.

**LARGE Receiver Cabinets,** highly polished, as used for "Cromwell" 8-valve Superhet. Measurements: 22in. high, 17in. wide, 11 1/2in. deep. Finished in contrasting rosewood and walnut veneer. Special additional baffle on speaker fret. Cost over £2 to make. Few only left at 15/- each.

**NOTE.** All Cabinets supplied for Cash with order only and sent carriage forward.

**SPECIAL SUNDRY BARGAINS.**

**THESE special bargains** are sent for Cash with order only. Please add 3d. for postage.

Tonastat Selectivity Unit, 1/10; Biflo static cut-out, 2/3. Igranic 1 mfd. condensers 1/3 each; 2 mfd. 1/9 each. Table Microphone complete with transformer in base, 6/11. Triotron electrolytic condensers; 8 mfd., 450 volt working, 2/11 each; 25 mfd., 350 volt working, 3/6 each. Triotron Class "B" Valves, type B220B. List 10/6; our price 5/1. Amplion Binocular H.F. Chokes. Totally enclosed in bakelite case. List 4/6. Our price, 2/3. Lots of 3 dozen assorted Dubilier fixed condensers, 1/9 each lot. 4-pin Chassis-mounting Valve holders, 5d. each; 6 for 2/-.

Variable tuning condensers, .0003 mfd., 1/- each. Igranic 2-pole rotary switches, 1/- each. Igranic Short-wave chokes, 1/- each. Double reading voltmeters, 1/9 each. Accumulator Hydrometers, complete with float, 1/- each. Sovereign lightning arresters, 6d. each.

**FREE.** Our latest fully revised Bargain List "N," now ready. Send p.c. for your copy.

All Mail Orders Direct to

**PEARL & PEARL,**  
190, Bishopsgate, London, E.C.2. Tele.: Bishopsgate 1212.



RADIO CLEARANCE, 280, High Holborn, W.C.1 offer the following stupendous bargains, limited quantities only, all orders over 5/- post free.—Phone: Holborn 4631.

RADIO CLEARANCE First Bargain List is now Available, send 11d. stamp to cover cost and postage; 7 valve superhet. chassis by Plessey made for a well-known proprietary firm whose name we are not allowed to mention, 7 tuned stages, amplified delayed A.V.C., local distance switch, 7 k/c separation, size of chassis 13 1/2 in. x 9 1/2 in., A.C. 200-250 volts for use with energised speaker, 2,500 ohms, demonstrations daily at 94, High Holborn, chassis complete with Mullard valves, less speaker and cabinet. Brand new; £7/10.

RADIO CLEARANCE Makes Special Offer of a Limited quantity S.T.600 Dorchester Kits to Designers' Specification, including Colvern coils, Polar condensers, T.C.C. fixed condensers, R.I. Hypernite transformer, ready drilled panel and terminal strip, list price £5/17; our price, £3/10.

RADIO CLEARANCE.—Dorchester 3-valve service grid, detector, power or pentode battery chassis including all first-class components, brand new, completely wired; at 30/- each, less valves.

RADIO CLEARANCE.—Plessey main transformers—primary input 200-250 volts, secondaries 350-0-350 at 120 m.a., 4 volts 2 1/2 amps, 4 volts 6 1/2 amps, screened primary, exceptional value; 7/6 each.

RADIO CLEARANCE.—Standard Telephones and Cables mains transformers, shrouded type, for H.T.S rectifier with 4v. 4 amp. C.T., L.T. winding; exceptional value at 6/- each.

RADIO CLEARANCE.—British Radiophone 3-gang Midget type superhet, condensers, fully screened with trimmers 2.0005 sections and 110 k/c oscillator section; 7/6 each.

RADIO CLEARANCE.—British Radiophone 3-gang Midget type straight condensers, fully screened, with trimmers, 3.0005 sections; 7/6 each.

RADIO CLEARANCE.—British Radiophone 3-gang superhet, condensers, unscreened, 2.0005 sections and 110 k/c section, complete with trimmers, dial, pilot light and escutcheon; 6/6.

RADIO CLEARANCE.—British Radiophone 110 kc/s. intermediate frequency transformers; 3/- each.

RADIO CLEARANCE.—British Radiophone set of band-pass coils, manufacturers' type, with circuit diagram, suitable for tuned grid or tuned anode; set of 3 coils, 4/-.

RADIO CLEARANCE.—British Radiophone set of superhet. coils, manufacturers' type, with circuit diagram, suitable for use with above advertised condensers, 5/6 per set.

RADIO CLEARANCE.—8 mfd. dry electrolytics—500v. working, well-known make; 2/6 each.

RADIO CLEARANCE.—1/25 h.p. inotors (Gilbert), 100-115 volts A.C., for television, suitable for 200-250v. if used with suitable resistance or lamp; 8/6 each.

RADIO CLEARANCE.—Variable power resistances by well-known maker, 0-100 ohms; 2/6 each.

RADIO CLEARANCE.—8,000 ohms volume controls, log type, with Q.M.B. switch, by G.E.C.; 2/- each.

RADIO CLEARANCE.—50,000 ohms Centralab potentiometers; 1/6 each.

RADIO CLEARANCE.—25,000 ohms British Radiophone graded potentiometers; 1/9 each.

RADIO CLEARANCE.—1 watt resistances, well-known make, all sizes; 6d. each.

RADIO CLEARANCE.—Wego 2 mfd. condensers, canned type; 10d. each.

RADIO CLEARANCE.—1mm. white sleeving; 9d. per doz. lengths.

RADIO CLEARANCE.—Telsen .0001 and .00015 reaction condensers; 5d. each.

RADIO CLEARANCE.—Steel chassis, cadmium plated, drilled ready for use; 3 valve, 1/-; 4 valve, 1/6 each.

RADIO CLEARANCE.—Steel chassis, cadmium plated, 2 and 3 valve type, fitted valve holders and terminal strips; 2/- each.

RADIO CLEARANCE.—T.C.C. condensers, 0.5 mfd., 800 v. working, 1/-; T.C.C. 1 mfd., 800v. working, 1/6; T.C.C. 1 mfd., 250v. working, 1/-; T.C.C. 2 mfd., 450 v. working, 1/6; T.C.C. 4 mfd. block condensers, 0.5, 0.5, 0.5, 0.5, 0.5, and 1 mfd. 250 A.C. working, 1/9 each.

RADIO CLEARANCE.—Earl Permanent Magnet Moving-Coil Speakers, brand new, boxed. List at 29/6; our price, 10/11.


RADIO CLEARANCE, 280, High Holborn, W.C.1. Phone: Holborn 4631.

CAMCO RADIOGRAMPHONE CABINET at 40/-. Special offer of Mahogany Radiogramophone Cabinet complete with polished panel, 18in. x 7in. Listed at £6/15/0, now 40/-. Send for list.—Carrington Mfg. Co., Ltd., Camco Works, South Croydon.

ALCO eliminators and chargers. 4 H.T. tappings, 18/-; with charger 26/-; Charger alone, 6/6. 1 amp., 11/-. Year's guarantee. Stamp details.—P. & D. Radio, 1, Goodinge Rd., N.7.

LISSSEN battery valve bargains; pentode 3/6, detector 2/10, screened grid 5/-.—Service Radio 72, Bruce Grove, Tottenham.

**FULL of INTEREST**

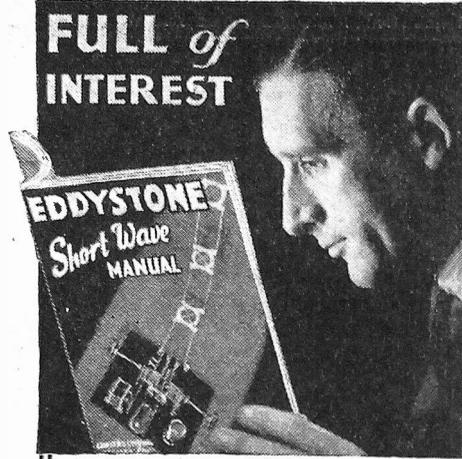

**EDDYSTONE Short Wave MANUAL**

Fully illustrated with constructional details for building Battery and Mains S.W. Receivers—8v. S.W. Super-het with A.V.C.—All-Wave Wavometer—5-metre Receiver—Simple 5-metre Transmitter—Crossfeeder Aerial System—Battery and Mains S.W. Converters—Amateur Bands Receiver—100 watt Transmitter—Eliminators, etc. COMPILED BY THE LEADING SHORT WAVE SPECIALISTS. Obtainable from your radio dealer, W. H. Smith, or in case of difficulty, direct from STRATTON PRICE & CO., LTD. (Dept. 21), Bromsgrove Street, Birmingham. London Service Depot: Webb's Radio, 14, Soho St., Oxford St., W.1. Glasgow Service: J. R. Hunter, 138, West Nile St.

**1935 EDDYSTONE SHORT WAVE MANUAL**

**RADIO GRAM CABINETS**  
As supplied to B.B.C.


**65/- POLISHED 35/- CABINET FOR 35/-**  
No Middle Profits.

Famous maker offers finest Radio Furniture. As supplied to B.B.C., a quality and value impossible to better. Beautifully hand-polished! GUARANTEED Piano-tone acoustically.

**DIRECT—on FREE TRIAL (or 10/- monthly). LIST FREE! From makers**

**PICKETT'S**  
Piano Tone  
Cabinet (P.R.) Works, Albion Road, Bexleyheath, near London.

**CUT H.T. BILLS IN HALF**

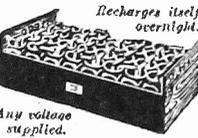

Recharges itself overnight.

Why not end the bother and expense of constant H.T. renewals and falling reception once and for all with a Standard Wet Battery. Gives abundant, 100 per cent. pure H.T. year in year out, with cheap replenishment at long intervals and without extra accumulators.

"It has been running a two valve set, Det. and Pentode since Sept. '32 (2 years), so I think it well repays the little extra trouble in the first place," writes W.D. You too will find Standard Batteries a real money saving source of H.T. 120-v., 12,500 m.a. £2 carr. paid. H.P. terms arranged. Wates L.T. Battery, ample current for 1 year. £1 carr. paid. Lists free from Wet H.T. Battery Co. (Pr.), 95, Dean St., Oxford St., W.1. Gerrard 6121.

**10,000 MOTORS; Spring and Electric for RADIOGRAMS or GRAMOPHONES in stock.**

Thousands of components: Tone arms, soundboxes, pick-ups, Horns, pedestal-portable cabinets, hinges, lidstays, springs, gears, repairs, Portable Gramos from 18/-, Violins, strings, Accordions, etc. 64-page Catal. how to make them, 2d. All 1935 Brands Radio 70-page Catal. 4d. Est. 30 yrs.

The Regent Fittings Co. (D285), 120, Old St., London, E.C.1.



**SOUTHERN RADIO'S WIRELESS BARGAINS**

**RECEIVERS.**—Osram 4-Valves (Actual) Sets. Complete with Four Osram Valves, Moving-Coil Speakers, Pedestal Cabinet. Ready for use on all Voltages A.C. In sealed cartons, £6/0/0 (List £15/15/-).

**BURGOYNE Class "B" Sets.** With Three Mullard Valves, Exido Batteries and Accumulators, Moving Coil Speakers. In modern Cabinet beautifully finished in Chromium plate. Ready for use. In sealed cartons, £3/18/6 (List £6/10/-).

**LISSSEN 2-Valve D.C. Sets.** Complete with Valves, Speakers in attractive Bakelite Cabinet. Ready for use, on all Voltages D.C. £2/15/- (List £7/7/-).

**FERGUSON Radio Midget Sets.** 4-Valves (Actual) T.R.F. Complete with Moving Coil Speaker, Valves. Ready for use on all Voltages A/C or D.C. In sealed cartons, £3/12/- (List £8/8/-).

**COILS.**—Irranic Superhet Four Coils (1 OSC, 2 I.F., with pigtails, 1 I.F. plain). 9/- per set (50/- List).

**VARLEY Constant Square Peak Coils B.P.5,** with all accessories, 2/3.

**PICK-UPS.**—Marconi Model K25 (1935 Issue), 21/- (List 32/6).

**CONDENSERS.**—Plessey Four-Gang Condensers with Oscillator Section for Superhet. Fully Screened with trimmers, 7/3 each (List 45/-). LOTUS Three-Gang, 12/6; 2-Gang 8/6. All Lotus Condensers are complete with Dials, Escutcheons, fully screened with trimmers. Dubilier 4-mfd. (2+1+1) 1,000 Volt, 2/9 each; 4.5 mfd. (2+2+2) 3/-; T.C.C. 0.1+0.1, 1/3. Dubilier 0.1, 9d.

**SPEAKERS.**—Blue Spot 60 L Units, 10/6. Mounted on Blue Spot Chassis, 16.6 (List 45/-). Blue Spot Permanent Magnet Moving Coil Speakers. Universal Transformers for Power, Super-Power, Pentode and Class "B." All Brand New 1935 Series in sealed cartons. Type 90P.M. 30/- (List 59/6); 45P.M. 24/- (List 45/-); 62P.M. (in Cabinet), 38/- (List 67/6); 32 P.M. in magnificent cabinet, 45/- (List 87/6). W.B. Stentorian Permanent Magnet Speakers with universal Transformers, 21/- each (List 32/6).

**ELIMINATORS.**—Regentone Eliminators W.5a. Complete with Trickle Charger for 200/250 volts, 39/6 (List £3/17/0). A small quantity only of Ecco Eliminators for 100/125 volts only. Type K25 with Trickle Charger, Output 25 m.a., 35/- (List £4/12/6). Type K.18 with Trickle Charger output 18 m.a., 32/6 (List £4/7/6). All Brand New in original sealed cartons.

**MISCELLANEOUS.**—Westinghouse Metal Rectifiers, H.T.6, 7, 8, 9/3 each. Morse Tapping Keys with flash signal and buzzer. Complete with Battery and bulb, 2/-. Biffo Static Cut-out, definitely eliminates noise and interference, 2/3 (12/6 List). Telsen Binocular H.F. Chokes, 2/4 (List 4/6). Variable Volume Controls, all capacities, 2/- each. Lewcos Spaghetti Resistances, all capacities. New and boxed, 1/6 dozen assorted.

Many More Bargains at our various Branches. Every Article Guaranteed and sent Post Paid.

**BRANCHES at 46, Lisle Street, W.C.2; 271-275, B High Road, Willesden Green, N.W.10. All Mail orders to 323, En-don Road, N.W.1.**

**SOUTHERN RADIO, 323, EUSTON ROAD, S LONDON, N.W.1 (near Warren Street Tube). Phone: Museum 6324.**

**WOBURN RADIO'S NEW YEAR SALE.**

ALL orders over 7.6 sent C.O.D. charges paid.

**BRITISH RADIOPHONE** semi-screened midget condensers, smallest made, .0005 with side trimmers. Brand new and boxed. 2 gang, 5/6, 3 gang, 7/6. Few only ordinary size, 4 gang, 9/6.

**W.B. P.M. Speakers,** with multi ratio output transformer (7 ratios), including Class B, 20/6. Rothermel P.M. 8in. cone power and pentode transformers, 18/6.

**WESTINGHOUSE Metal Rectifiers,** manufacturers' type, H.T.8 and 9, 8/11. Transformers for same with 4v. Ja. C.T. L.T. winding, 6/9. Western Electric Microphones, 2/3. Mike transformer for same, 85-1, 2/3.

**T.C.C. dry electrolytes** 8 mfd., 550v., 3/3, 4 mfd., 550v., 3/-, 4 mfd., 55v. (wet), 3/-, 50 mfd., 50v. (dry), 3/-. T.C.C. 6 mfd., 50v., 15 mfd., 100v., 25 mfd., 25v., 50 mfd., 12v., 1/3. Tubular condensers: 01, 02, .1, 6d. Dubilier wire end resistances, all values, 6d. Truwind wire-wound resistances, all values to 50,000, 3/6 doz. Formo 1 mfd., 1,000v. test, 1/-, 2 mfd., 1,000v. test, 1/3. Wego 4 mfd., 750v. test, 2/3. Chassis mounting valve-holders, 4.5 plu, 1/3 half-dozen; 7 plu, 6d. Toggle, 6d. Statoflex, 7yds., 6d. Pye S.W., valve-holders, 3d. Lucerne iron-cored canned coils boxed with circuit, 2/6.

**ROTHERMEL Piezo Electric Pick-ups,** new and boxed, 30/-. Marconi K25, 21/-. Wates Universal Meters, listed 12/6, few only, new and boxed, at 7/-.

**TRADE** enquiries invited, send stamp and heading for list.

**WOBURN RADIO CO., 9, Sandland St., Red Lion Street, W.C.1. Holborn 7289.**

HIGHEST possible allowance made on used wireless goods in exchange for new sets, components, or Peto-Scott kits. All latest receivers supplied on easiest of terms.—R. Wigfield, Furlong Road, Goldthorpe, Yorks.

HALL-MARK THREE, Superhet Thre, ST600 Guaranteed First Specified Kits—Lowest Prices—Easiest Terms—Lists Free—McClif-rad, Queen's Place, Hove. (Trade Supplied.)

**V**AUXHALL.—Magnavox permanent magnet Speakers universal for Class B, power, pentode or push-pull: 7in. cone, 16/6; 10in. cone, 22/-.  
**V**AUXHALL.—Magnavox energised types, 2,500 or 6,500: 10in. cone, 22/-; 7in. cone, 15/3. All brand new complete with humbucking coils, state power or pentode. Other speakers. Send for particulars.  
**V**AUXHALL.—Practical Wireless Universal super-het chassis, completely built as specified with valves and Magnavox or Rola speaker, carriage paid, £8/15/0.  
**V**AUXHALL.—Radiophone radio-paks R.F. super-hets complete with volume control, escutcheon, new Lucerne station named dial, 34/-.  
**V**AUXHALL.—Radiophone Intermediate frequency transformers, centre tapped primary, secondary on bases with terminals, 5/6.  
**V**AUXHALL.—Radiophone three gang condensers, piano type superhet, or straight fully screened, 8/6; two gang, 6/6.  
**V**AUXHALL.—Benjamin. Class B. transformers 1-1/2 to 1. Terminals fixing, 6/6 boxed.  
**V**AUXHALL.—Radiophone volume controls, all values from 5,000 to 500,000 with switch, 3/6.  
**V**AUXHALL.—Westinghouse rectifiers set, manufacturers surplus skeleton type H.T.S. 9/6; HT9-10, 10/-.  
**V**AUXHALL.—Westinghouse Westectors. W.4. W.X.6, 5/9. Regentone transformers with terminals and H.T.S. 17/6.  
**V**AUXHALL.—Rothermel Piezo electric pick-ups, 30/-; Marconi K25, 21/-; B.T.H. senior, 29/-; Minor, 16/6. Sealed cartons.  
**V**AUXHALL.—Gramophone motors: Collaro 32 model, 32/6. Universal model for 110, D.C. 200/250 AC/DC, 47/6.  
**V**AUXHALL.—B.T.H. Truspeed AC. 30/-; B.T.H. Universal model 110 D.C. 200/250 AC/DC. 47/6.  
**V**AUXHALL.—Utility dials and drives complete with escutcheon, state black or brown, 5/-.  
**V**AUXHALL.—Dubilier condensers, 4 or 8 M.F.D. dry electrolytic, 500V working, 3/-; 50 MFD.50V. working, 1/8; 50 MFD.15V., 1/6.  
**V**AUXHALL.—Dubilier or Radiophone tubular condensers non-inductive .1 9d. .05 6d.; .002, .0002, and .0005, 4d. 1 mfd. Mainsbridge, 1/3; 2 mfd, 2/-; T.C.C. .002 mica, 2,000v. test, 10d.; .01, 1/-.  
**V**AUXHALL.—Dubilier all values, 1 watt. resistances, 7d.; Clix valveholders with terminals 5 pin, 7d.; 7 pin, 9d.; Continental 7 pin, 9d.; W.B., 4/5 pin, 4d. Post paid, 2/6, or over or C.O.D.  
**V**AUXHALL-UTILITIES. 163a Strand, London, W.C.2, over Denny's the Booksellers. Temple Bar 9338. Send postcard for new lists free.

**T**HE following unused set manufacturers' Surplus; all goods guaranteed perfect; immediate delivery.  
**M**AGNAVOX speakers, complete with hum-bucking coil, output transformers, etc. DC152 (9in. cone), 22/6. DC154 (7in. cone), 16/-. All with 2,500 or 6,500 ohms fields.  
**W**ESTINGHOUSE rectifiers, HT8, 9/6. HT9, 10/-, HT10, LT5, LT4, 10/9. Regentone transformers for HT8 or HT9, with 4v. 4amp. LT winding, 7/-. Eliminators, first-class make. Outputs 150v. 25ma. SG and detector. AC type with Westinghouse rectifier, 25/-. AC type with .5 amp. trickle-charger, 30/-. DC type, 12/6.  
**D**UBLIER or TCC dry electrolytic condensers 8mfd or 4mfd, 500v working, 50mfd, 50v, 200mfd, 10v, 3/3. 50 mfd, 15v, and 15 mfd, 100v, 2/3. 50mfd, 12v, 2/-. TCC type "M" condensers, any value up to .001mfd, 6d. Erie resistances, 1 watt type, 7d., 2 watt, 1/2, 3 watt, 1/9. Send for comprehensive list.  
**W**ARD, 45, Farringdon Street, London, E.C.4. Telephone: Holborn 9703.

**W**ANTED, good modern wireless parts, sets, eliminators, meters, valves, speakers, etc. Spot cash waiting. Exchanges. Send or bring. We pay more than any other dealer. Open 9-8.—University Radio, 142, Drummond St., Euston, N.W.1. Phone: Museum 3810.

**R**ADIALADDIN (Disposals), Ltd. Exchange your old set for any new model, balance cash or H.P. Write for free quotation to largest radio exchange in U.K. Also clearance sale of reconditioned sets and radiograms at gift prices £1 to £10. Write for list.—46, Brewer Street, Piccadilly Circus, W.1. Gerard 4055.

**A**LL REPAIRS to Moving Coil Speakers, prices quoted. Loud-speakers, L.F. and Speech Transformers, 4/- each. Post free. Satisfaction guaranteed. Prompt service.—L.S. Repair Service, 5, Balham Grove, London, Battersea 1321.

**I**NDIVIDUAL SETS DESIGNED.—Quotations given for theoretical or practical circuits. Queries fully answered, 1/- each, 2/6 for three. Cash with order.—The Expert Radio Service Bureau, 29, Orford Road, London, E.17.

**B**ANKRUPT BARGAINS.—List free. ST600 kit, 60/-; 3v. kit, 15/-. Pilot 6v. Super Hets. 4 wavebands, 10-2000 metres. Frequency changed for S.W. Very latest American 12 gns. Ferguson 6v. 3 wavebands chassis with Rola, only £8/15/0. 4v. Midget Universal, 85/-. Many other sets at best prices. Phillips 12 gn. A.C., 8 gns. Lotus M.C. speaker, 12/6. Blue Spot 45 P.M., 25/-. Very large stock eliminators, speakers, valves, and all smaller parts. Part exchange.—Butlin 143B, Preston Road, Brighton. (Preston 4030.)

# FOR BETTER RADIO solder your contacts electrically

Plug in your Solon Electric Soldering Iron to the nearest lampholder and you know it'll be ready to make good jobs in three minutes.

**IT'S QUICKER BETTER · MORE ECONOMICAL AND EFFICIENT**



**W. T. HENLEY'S TELEGRAPH WORKS CO., LTD., DEPT. 22Y.O., HOLBORN VIADUCT, LONDON, E.C.1.**

## 1935 EDITION... FREE!

A New and greatly enlarged edition of "ENGINEERING OPPORTUNITIES" is just off the Press. It describes the easy way in which you may become an **A.M.I.C.E., A.M.I.Mech.E., A.M.I.E.E., A.M.I.A.E., A.M.I.W.T.,** etc., and contains the world's widest selection of courses in all branches of **Civil, Mech., Elec., Motor, Aero., and Radio Engineering, Building, etc.**

*If you are earning less than £10 per week, you cannot afford to miss this unique guide to a first-class job.*



**DON'T DELAY**—send for your FREE copy of the Handbook to-day. No cost or obligation of any kind.

**THE BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY,** 409, Shakespear House, 29/31, Oxford Street, London.

# 362 VALVES

**THE VALVE WITH THE SIX MONTHS GUARANTEE!**

### FREE ADVICE BUREAU COUPON

This coupon is available until February 9, 1935, and must be attached to all letters containing queries.  
**PRACTICAL AND AMATEUR WIRELESS,** 2/2/35.

### HULBERT, 6, CONDUIT STREET, W.1.

Read below:  
 If you are requiring realistic reproduction at remarkable low cost, send for one of the following high-grade speakers. Repeat orders are coming in daily.  
**10/5** only. Brand-new manufacturer's surplus moving-coil speakers, made by one of the best-known British makers. Energised, 2,000, 2,500, or 6,500 ohms field windings, power or pentode transformer, 5in. cone, 10/6 each.  
**12/5** only. As above, but with 10in. cone. A very powerful speaker capable of handling large outputs.  
**15/5** only. Brand-new manufacturer's surplus moving-coil speakers, made by one of the best-known British makers. Permanent-magnet model of high efficiency with power or pentode transformer, 5in. cone, 15/6 each.  
**17/5** only. As above, but with 10in. cone. Ideal for use with quality receivers such as the £5 3-valve Super Het.  
**2/9** only. Brand-new cabinets suitable for above speakers, 2/9 each only. Secure one of these amazing speaker bargains now. Repeat orders are coming in daily. Cash with order or C.O.D.

**HULBERT, 6, CONDUIT STREET, W.1.**

**U**TILITY SALES.—We have splendid Reports from Amateurs who made our Two-valve Short-wave. LL parts ready to assemble, 45/-; ready assembled, 50/-.—Apply FREE Circuit.  
**E**LMINATORS.—With Trickle charger. "Regentone" W.A.5, 25 ma, all variable tappings, 1 amp. charger, 40/-  
**M**ICROPHONES.—Our Western Electric the Best, Hanging model, 2/6; Transformer, 3/6. Table model, transformer in base, 8/6.  
**L**OTUS.—Triple Ganged Band-pass coil unit, listed, 27/6; with circuit, 12/-.  
**C**ELESTION PPMW.—Listed, 45/-. Permanent Magnet, 7in. Cone Universal transformer, 18/6.  
**M**ILLIONS of articles to be Cleared cheap during Sale. Wonderful values.—Apply for lists.  
**U**TILITY SALES, Fairitone Corner, 57, Praed Street, London. (Paddington 0251.)

**M**AINS Transformers, chokes, etc., to specification, repairs promptly executed. Guaranteed satisfaction. Prices on request. Henry Peace, Ltd., Wednesbury, Staffs.

**T**RANSFORMER and Choke Stampings, instrument and Resistance wires, spools and insulation. Lists Free.—Lumen Electric Co., 9, Searisbrick Ave. Litherland, Liverpool 21.


**T**HE SWIFT SERVICE AND SUPPLY CO. **HALL-MARK THREE.** COMPLETE KIT OF GUARANTEED COMPONENTS, 30/- POSTAGE PAID. (Including B.T.S. specified Coils and Drilled Chassis). **B.T.S. HALL-MARK THREE** (COILS, 7/6 per pair. POSTAGE 3d. **HIVAC** SPECIFIED VALVES, £1/0/9 per set. **IMMEDIATE DELIVERY.** SEND 1d. STAMP FOR DETAILS OF "SWIFT" SHORT-WAVE KITS AND OTHER INTERESTING BATTERY CIRCUITS. ALL STANDARD COMPONENTS AND ACCESSORIES SUPPLIED.  
**T**HE SWIFT SERVICE AND SUPPLY CO. (HM6) 3, FEATHERSTONE BUILDINGS, HIGH HOLBORN, LONDON, W.C.1. PHONE: HOLBORN 1336.

**W**EEEDON P.L.R. Co. **SPEAKER & REWINDING SERVICE.**—Mains transformers, etc. New Cones, Coils and Centres fitted M/c speakers, 5/-. Guaranteed.—Dept. C., 80, Lonsdale Avenue, London, E.G. (Grangewood 1837.)

### ADVERTISEMENT INDEX

Amplion (1932), Ltd. . . . .	Page 738
British Blue Spot Co., Ltd. . . . .	711
British Institute of Engineering Technology . . . . .	740
British Rola Co., Ltd. . . . .	726
Colvern, Ltd. . . . .	711
Cossor, A. C., Ltd. . . . .	Inside Front Cover
Fluxite, Ltd. . . . .	738
General Electric Co., Ltd. . . . .	Back Cover
Heayberd, F. C. & Co. . . . .	732
International Correspondence Schools . . . . .	725
Lectro Linx, Ltd. . . . .	732
London Radio Supply Co. . . . .	731
New Times Sales Co. . . . .	737
Peto-Scott, Ltd. . . . .	723
Picketts . . . . .	739
Pix . . . . .	735
Regent Fittings Co. . . . .	739
Stratton & Co., Ltd. . . . .	739
362 Radio Valve Co., Ltd. . . . .	740
W. T. Henley's Telegraph Works Co., Ltd. . . . .	739
Wet H.T. Battery Co. . . . .	739
Whiteley Electrical Co., Ltd. . . . .	727
Wills, W. D. & H. O. . . . .	729



# Keep UP-TO-DATE!

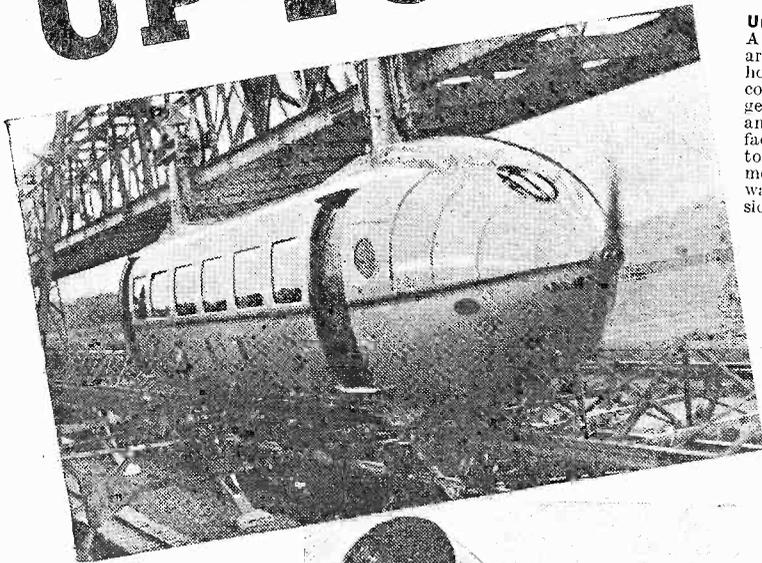


**Unusual Railways.**  
A well illustrated article explaining how engineers have conquered the ruggedness of nature and brought the facilities of transport to countries where mechanical travel was formerly considered to be impossible.

**PRACTICAL MECHANICS** is the only magazine dealing with modern subjects in everyday language. It affords an intriguing, valuable and cheap means of keeping yourself up to date with modern technical and practical tendencies.

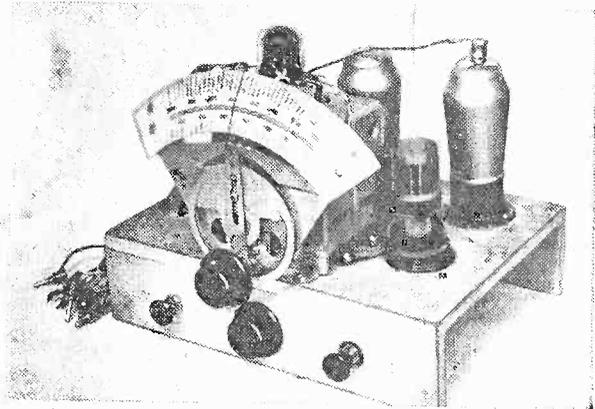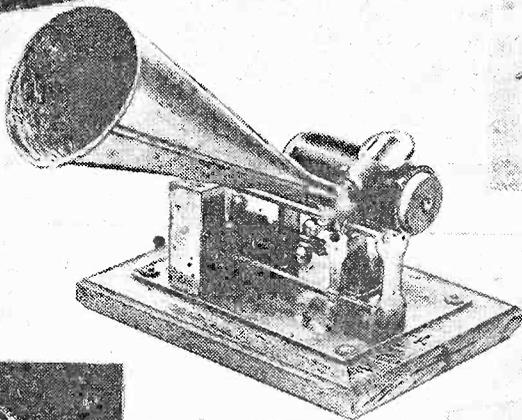
**Development of the Talking Machine.**  
Many valuable and historic photographs illustrate this article which deals with the earliest models of Edison's phonograph and traces developments down to the present day.



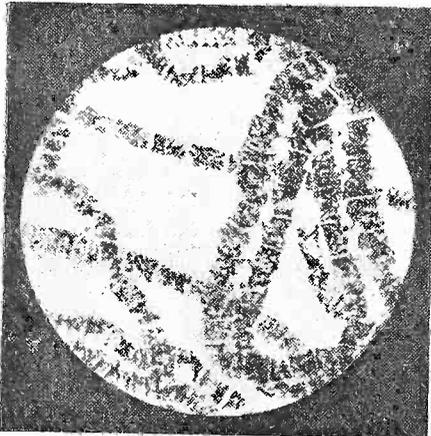**The Two-Guinea Three-Valver.**  
Complete wiring diagrams for making an ultra-efficient yet cheap three-valve set.



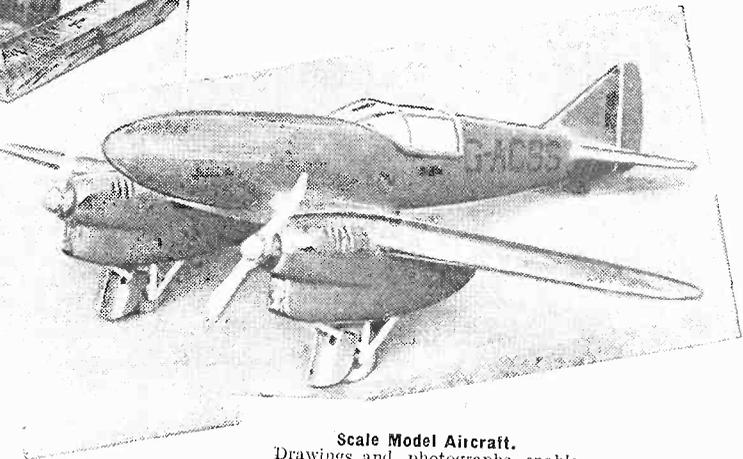**What is the Spirogyra?**  
Many valuable photo micrographs illustrate this interesting article which deals with an interesting form of pond life.



**Scale Model Aircraft.**  
Drawings and photographs enable the reader to make a scale model of a DH Comet.

The above small reproductions are merely a few extracted at random from the fascinating and lavishly-illustrated pages of the current issue of this new and vital Monthly. There are dozens of similar illustrations in line and half-tone illustrating a wide range of interesting subjects explained in language which everyone can understand.

NOW ON SALE

6<sup>d</sup>

# PRACTICAL MECHANICS

# Give Your Set a Tonic!

## Get improved long range reception

A falling off in the sensitivity of a Set which makes reception of distant stations increasingly difficult probably indicates that the mutual conductance of the screen-grid valve has fallen below standard. In an H.F. Amplifier the overall magnification per stage is a function of the mutual conductance of the valve coupled with its interelectrode capacity.

The design of modern OSRAM Screen-Grid Valves maintains an exact balance between these characteristics and a type is available for every class of Receiver. You would not run your car with the brakes on — make sure that you are not operating your Set with a worn-out screen-grid valve, thus limiting its full capabilities with the risk of losing a foreign programme of particular interest.

Fit a new OSRAM Screen-Grid Valve for long range reception



# Osram Valves

MADE IN ENGLAND

Sold By All Radio Dealers.

## A TONIC TO ANY SET

### OSRAM SCREEN-GRID VALVES

<b>S 23</b>	For 2-volt Battery Kit Sets and Portables	12/6
<b>V S 24</b>	For 2-volt Battery Sets with variable mu grid control	12/6
<b>MS 4 B</b>	For all A.C. Mains Sets with single stage H.F.	17/6
	or <b>MS 4 B CATKIN</b>	
<b>MS 4</b>	For A.C. Mains Sets with two stages H.F.	17/6
<b>VMS 4</b>	For A.C. Mains Sets with variable mu grid control	17/6
	or <b>VMS 4 CATKIN</b>	
<b>DSB</b>	For 0.25 amp. D.C. Sets	17/6
<b>VDS</b>	For 0.25 amp. D.C. Sets (variable mu)	17/6

WRITE for the OSRAM VALVE GUIDE (1934 Edition). Sent post free.

Advt. of The General Electric Co., Ltd., Magnet House, Kingsway, London, W.C.2.