

THINKING ABOUT PORTABLES— See Page 29

Practical and Amateur Wireless

3^d
EVERY WEDNESDAY

Edited by F.J. CAMM

GEORGE NEWNES
Publication

Vol. 34. No. 340.
March 25th, 1939.

AND PRACTICAL TELEVISION

F. J. Camm's

50/- ALL-WAVE 3

Further Details!



EVERYBODY'S GETTING THE EDDYSTONE SHORT WAVE MANUAL

Would you like to receive a Book, that with the friendly freemasonry of a clever fellow experimenter, goes thoroughly into the matter of modern Short Wave practice—showing how to build, gripping your enthralled interest with clear-cut demonstrations of little understood Short-Wave appliances?

Such a book is the Eddystone Short Wave Manual. It contains Price 1/- from W. H. Smith, Radio Dealers or 1/2 Post Free

pages and pages of information—illustrated constructional articles for building simple S.W. Receivers, low and medium power Transmitters, Amateur Communication Receiver Presselector, Cathode-Ray Oscilloscope, etc., etc. 30 photographs, nearly three dozen diagrams, details of "how to build," etc. Every page alive with up-to-the-minute interest for people like YOU. from Stratton & Co., Ltd., Eddystone Works, Bromsgrove Street, Birmingham. Don't miss it! GET YOUR copy TO-DAY.



*If a man can't
take a hint*



It may not be Leap Year but you can propose to him that when he offers you a cigarette it should be a Wills's Gold Flake. Let him know that your taste in cigarettes is the same as his—that the flavour of the fine Virginia tobaccos of which Gold Flake are made appeals to women as much as to men. The other alternative is to buy your own and show him that young women to-day can have Wills of their own.


WILLS'S
GOLD FLAKE
*is the man's cigarette
that women like*

N.B. You can get Wills's Gold Flake CORK-TIPPED as well as Plain. Ten for 6d. Twenty for 1/-

G.F.B. 642

A Career in Aviation

NAVIGATION AND RADIO

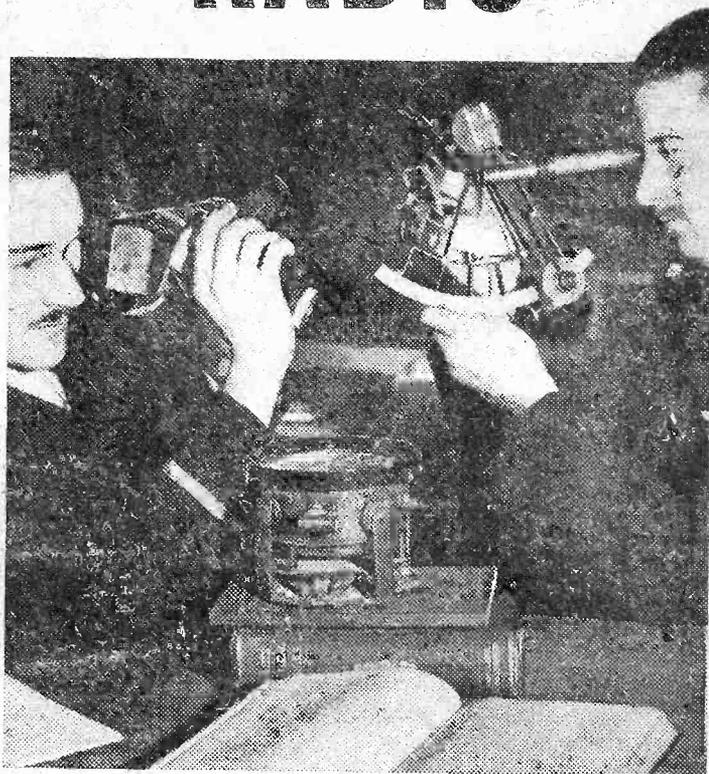

Two pilots
at Imperial
Airways
Air Navigation
School

This authoritative article tells you how the rapidly growing importance of radio in relation to aviation means increased opportunities for those seeking careers in this field. FLYING also invites you to write for any special information you require on this subject.

Take advantage of this offer—get FLYING to-day!


in this week's

FLYING

The Popular Air Weekly

all Newsagents and
Bookstalls **3^d.** EVERY
FRIDAY

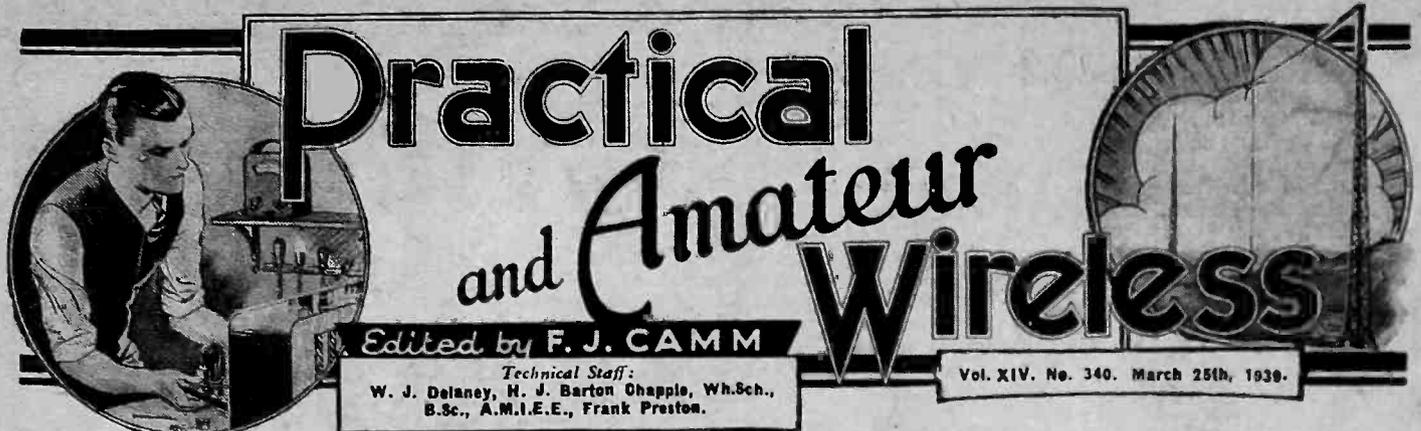EXPERIMENTAL A.C. MAINS AMPLIFIER— *See Page 36*



Practical and Amateur Wireless

Edited by F. J. CAMM

Technical Staff:
W. J. Delaney, N. J. Barton Chapple, Wh.Sch.,
B.Sc., A.M.I.E.E., Frank Preston.

Vol. XIV. No. 340. March 25th, 1939.

ROUND *the* WORLD of WIRELESS

Valve Types

THE newcomer may be pardoned for expressing ignorance concerning the appropriate type of valve to be used in a given stage of a modern receiver. Tetrodes, which at one time were only used in H.F. stages and which were otherwise known as S.G. valves, are now regularly employed in the L.F. stages, and in at least one range of valves have replaced output pentodes. Pentodes are suitable for use in any stage of a receiver, although made in different types. No doubt there will be a time when valves will be standardised and reduced to a minimum of types, but in the meantime a careful check has to be kept of new types and the passing out of old ones. In this issue we continue the details given concerning pentodes and tetrodes, and we hope this will clear up the matter for those who are finding it confusing to know just what each valve type is intended for, and will enable every constructor to select a suitable valve for any particular circuit which he may desire to make up or with which he may wish to experiment.

Television in Germany

RUMOURS have been current that the German authorities intended to close down or move the television transmitter situated on Amerika House. It is now officially stated, however, that there is no intention of closing down the transmitter, but as it does not fully serve the main part of Berlin it has been considered whether or not there is not some alternative site which would be more effective.

Broadcasting in Ceylon

THE total number of licence-holders in Ceylon is approximately 6,000, it was stated by the Minister of Communications recently in welcoming the Governor of Ceylon to the thirteenth anniversary celebrations of the Colombo Broadcasting Service.

All-India Radio Additions

NEW stations shortly to be opened by All-India Radio will be situated at Bengal, Dacca and Trichinopoly. These will be independent stations broadcasting their own sectional programmes. The establishment of a 5-kW station at Trivendram (Travancore State) to operate on the medium-waveband is also being contem-

plated. It is also stated that the Government of the Travancore State proposes to install 100 receivers in various State colleges and schools.

New Italian Stations

ITALY has introduced some 42-metre transmissions, operating with call-signs I2RO11, I2RO12 and I2RO13. The wavelength being used by I2RO11 is 41.55 metres.

The Atomic World

OF special interest to technical-minded readers will be the talk to be given on March 28th (Wales) by E. J. Williams, Professor of Physics at the University College of Wales, Aberystwyth. The talk is entitled "The Atomic World."

An Hour at the Opera

THE Torquay Municipal Orchestra, led by Harold F. Potts and conducted by Ernest W. Goss, with Nan Maryska (soprano) as the soloist, will broadcast a concert entitled "An Hour at the Opera" from the Marine Spa, Torquay, on March 29th. The Marine Spa was formerly the principal concert hall in Torquay, and the concerts by the Municipal Orchestra are being held there during the reconstruction of the Pavilion, which was opened in 1912.

Il Trovatore

REPLACING "Der Freischütz," Verdi's "Il Trovatore" has been scheduled as the last of the current quarter's series of full-length studio opera productions. It will be broadcast from St. George's Hall on March 31st (National) and April 3rd (Regional). During the summer, opera broadcasts are expected to be available from Covent Garden, Glyndebourne and Sadler's Wells, and Stanford Robinson, chief of the B.B.C. Music Productions Section, has therefore postponed "Der Freischütz" until next autumn.

"This and That"

PROFESSOR JOHN HILTON, one of the outstanding personalities of radio, has not been broadcasting regularly since 1937. Listeners should be interested to hear that he is returning to the microphone in a series of thirteen weekly talks to be given on Sundays. As on previous occasions his talks will be entitled "This and That," and he will be speaking on anything that has occurred to him as interesting, amusing or exciting during the previous week. Perhaps the secret of Professor Hilton's success as a broadcaster lies in the fact that there is practically nothing under the sun that he does not find interesting, and in his ability to communicate his interest in a vivid manner to his unseen audience. The first talk will be given on April 2nd.

ON OTHER PAGES	
	Page
F. J. Camm's 50s. All-wave Three	27
Thinking About Portables	29
On Your Wavelength ..	31
Short-wave Section ..	33
Readers' Wrinkles ..	35
An Experimental A.C. Amplifier	36
Those Puzzling Pentodes—2	38
Practical Television ..	40
Practical Letters	43
Club Reports	44
Queries and Enquiries ..	47

Listeners Answer Back

WHEN the B.B.C. Exhibition was at Nottingham Denis Morris, Midland Public Relations Officer, answered at the microphone a number of questions and comments by listeners. A similar idea is being tried in an outside broadcast (Midland, March 29th) from a hall in Kettering, when Mr. Morris will address a meeting there. The last few minutes of his speech will be broadcast and then listeners in the audience will have an opportunity of putting their own points of view about broadcasting at portable microphones for about a quarter of an hour. Their points and the speakers' replies will thus make the bulk of the broadcast programme. It is hoped to follow a similar procedure at one or two other places later in the year.

ROUND the WORLD of WIRELESS (Continued)

Turkey Popularises Broadcasting

THE Turkish Government has decided to import or manufacture 50,000 wireless sets free of duty, and to distribute them to the population in out-of-the-way villages at very low prices. No licence tax, at first, will be charged, in order to encourage the people to become radio-minded. The receivers will be of such a type that the Ankara broadcasts may be heard in every district of Turkey in Europe, and Asia. The Ministry of Public Works which is sponsoring this system of education will hold the monopoly for trading in cheap receivers, leaving the private dealers to handle the more expensive sets.

Australia's New High-powered Station

ACCORDING to a recent report, the new high-powered naval radio station at Canberra, which is claimed to be the largest in the southern hemisphere, is nearing completion. Five separate transmitters are being installed, all of which may be used simultaneously.

Obituary

WE regret to record the death of Mr. Robert Chignell, O.B.E., the celebrated composer and singer. Mr. Chignell, who was fifty-six, lived at Aucassin,

INTERESTING and TOPICAL NEWS and NOTES

bouts in each pool meeting until the champion is decided. This broadcast will be given in the Regional programme.


City of Birmingham Orchestra

REGIONAL as well as Midland listeners will hear on March 23rd the City of Birmingham Orchestra's performance of Elgar's symphonic poem, "Falstaff," which is the chief work in their concert at the Birmingham Town Hall. Leslie Heward is the conductor.

Variety from Northampton

THE variety bill on March 29th will be broadcast from the New Theatre, Northampton, and will be heard by Regional as well as Midland listeners. The principal

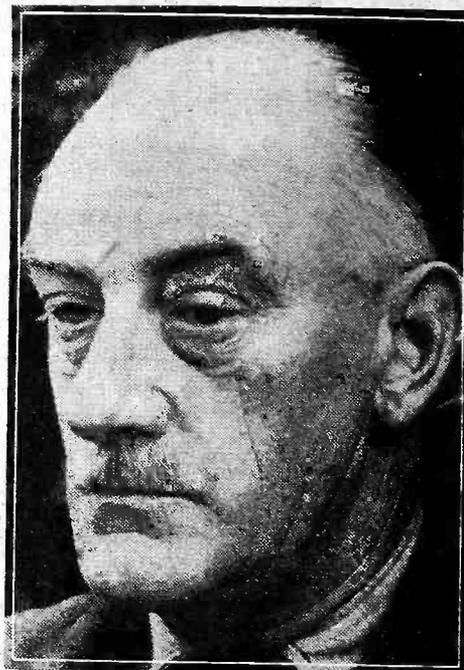Littler's pantomime at the Prince of Wales Theatre, Birmingham, as the chief contributor. The others will include Dorothy Summers, Marjorie Westbury, Cicely Gay and Stuart Vinden.



Mr. Robert Chignell, O.B.E., the well-known composer, whose death is recorded on this page.

"Music Hall" from Hull

A BROADCAST from the Alexandra Theatre at Hull will be heard on March 31st, not only on the Northern wavelength but in the Regional programme also. Besides a variety excerpt from the theatre at night, listeners at noon on the same day will be able to take a peep by radio into the theatre during a rehearsal for the evening's show.


SOLVE THIS!

PROBLEM No. 340

Houten decided to build a superhet and purchased a set of coils and I.F. transformers by a well-known maker. He found a number of useful parts in his spares box, including a superhet type ganged condenser—which he verified by checking that the vanes in one section were cut away. He built the circuit to a standard design, but found that he could not obtain satisfactory tracking throughout the entire range. He checked the wiring of the circuit and all values and found that these were perfectly in order. What was the trouble? Three books will be awarded for the first three correct solutions opened. Entries must be addressed to the Editor, PRACTICAL AND AMATEUR WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. Envelopes must be marked Problem No. 340 in the top left-hand corner and must be posted to reach this office not later than the first post on Monday, March 27th, 1939.

Solution to Problem No. 339

When Kennedy connected the primary winding between anode and earth he short-circuited signals and H.T. He should have taken the other end of the primary winding to H.T. positive, or choke-fed it. The following three readers successfully solved Problem No. 338, and books have accordingly been forwarded to them: J. P. Cook, "Aintree," Chestow, Mon.; M. S. Crothall, 4, Chart Road, Folkestone; Wm. A. Geddis, 15, Rugby Terrace, Larnie, Co. Antrim.

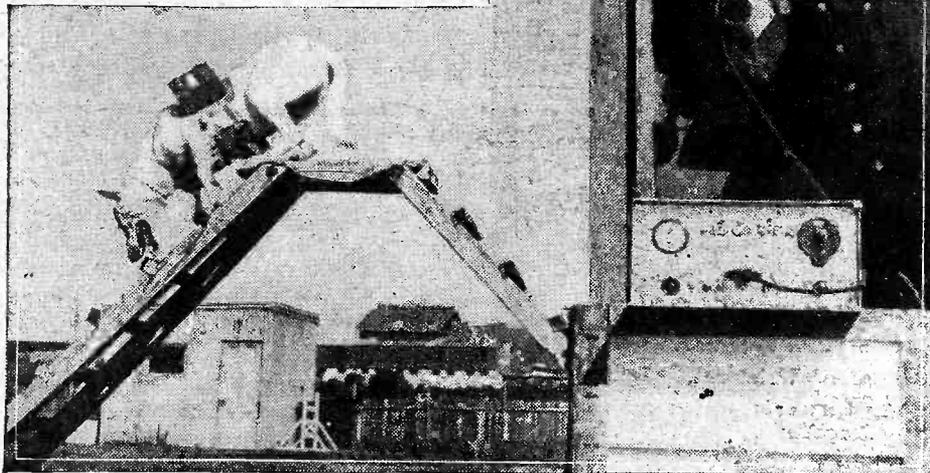

Zoe, a remarkable Alsatian police dog attached to the Sydney (New South Wales) police force, is here seen obeying instructions from her trainer, Constable Denholm, of the Bourke Street Police Barracks. With a miniature receiving set strapped to her back, Zoe performed numerous tricks at the direction of Denholm, who was seated at a microphone 50 yards away. She walked up and down ladders, turned a tap on and off, put on her own collar, took it off again, and filled a billycan from a tub of water.

Horley, Surrey. The name of Robert Chignell must be familiar to all owners of radio sets, for in fourteen years no fewer than 2,500 of his works, including many special arrangements, have been broadcast. Mr. Chignell specially composed the music for the series of broadcasts of the adapted version of Victor Hugo's novel, "Les Miserables."

Fencing

CHARLES DE BEAUMONT, Epée champion of Great Britain for the last three years and captain of the fencing team which represented Britain at the Olympic Games in Berlin in 1936, will give a commentary on the Final Pool of the Foils Championship of Great Britain, which will be staged at the Salle Bertrand on March 31st. The championships organised on the pools system, the winners of the

turns are well-known broadcasters—Anona Winn; Cavan O'Connor, The Vagabond Lover; Jack Wilson and Harry Engleman, syncopating pianists, who will be making their first appearance as a double act on the halls; and Ivan Huckerby and his Aston Hippodrome Orchestra, playing from the stage.

Bath Music Festival

PART of the programme of a concert from Bath on March 22nd will be broadcast on the Regional wavelength, when Albert Sammons will play Elgar's Violin Concerto in E minor.

Cinderella Comes to Supper

"CINDERELLA Comes to Supper" is the title of a programme of music, songs and stories in the form of a drawing-room concert, with the Cinderella of Emile

Further Details of F. J. Camm's 50/- All-wave Three

Completing the Constructional Work, and Operating Details of this Remarkable Low-priced All-wave Receiver


IN last week's issue we gave the main constructional details of this new receiver, and no difficulty should have been experienced in this part of the work. The wiring, whilst not difficult, must be carried out carefully, and this applies particu-

larly to the switch unit. In the wiring diagram which was published last week the artist drew the contacts in the form of two rows, so that the relationship between them could more easily be seen. In Fig. 5 in that issue we showed a rear view of the switch and indicated how the centre six contacts related to the surrounding 18. It is thus possible to connect the first grid, for instance, to any of the internal six contacts, provided that the associated three contacts are immediately above, as shown in Fig. 5. If, however, you regard the lower row of contacts in the wiring diagram as representative of the internal row in Fig. 5, reading from left to right and starting with letter A, then the upper row, in the same order, will commence at A1 and proceed logically to F3. A good plan when wiring a switch of this type

is to take one section at a time, and to check as the wiring is completed by means of a meter and battery. This avoids the necessity of taking down all connections afterwards should it be found that a mistake has occurred.


Battery Leads

There are no difficult points in wiring, other than the taking of the usual precautions to make certain that components which are held in position by wiring are rigidly attached. The short-wave choke, for instance, should be wired to the switch with fairly stout wire so that it remains up against the side runner in the position shown in the diagram, whilst the resistances and chokes should all occupy the positions shown. The use of screened sleeving should be carefully noted, and in the case of the reaction condenser the return from the moving vanes is taken via the screening of the wire for the fixed vanes. In other words, only one lead is taken to the reaction condenser, and this is for the fixed vanes, but the moving vanes are joined to earth through the screened sleeving and the associated wiring. The lead from the reaction coil and from the reaction condenser are run together near the

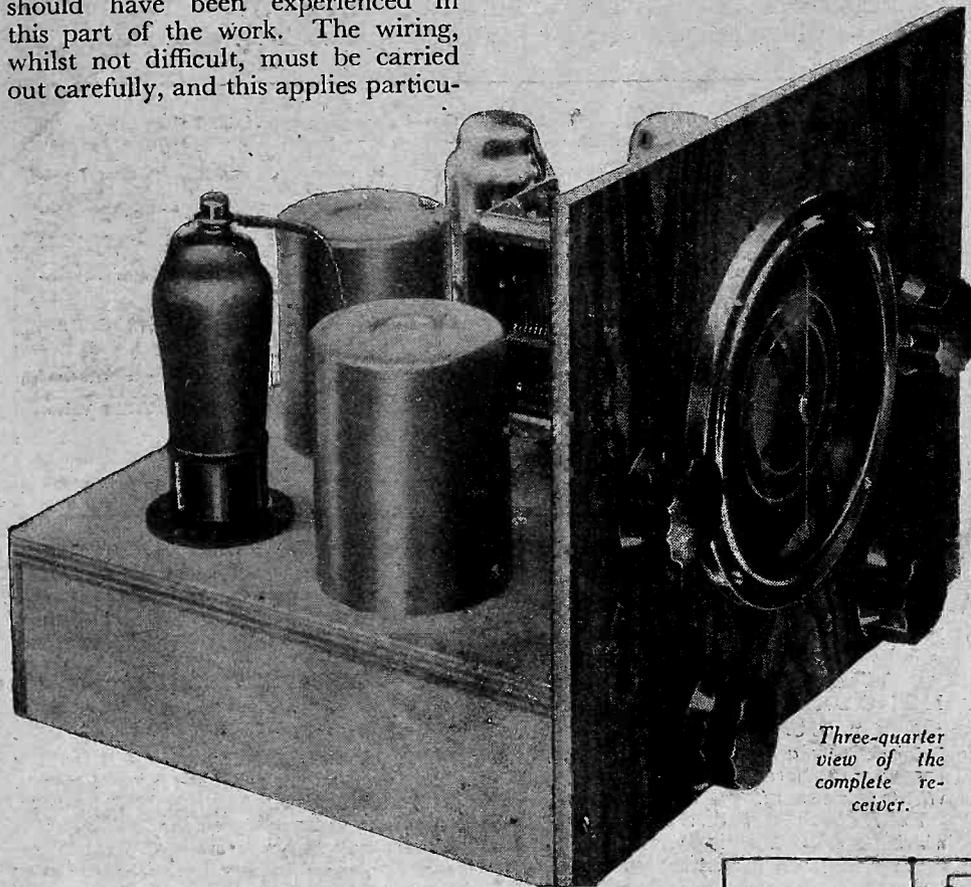

Three-quarter view of the complete receiver.

larly to the switch unit. In the wiring diagram which was published last week the artist drew the contacts in the form of two rows, so that the relationship between them could more easily be seen. In Fig. 5 in that issue we showed a rear view of the switch and indicated how the centre six contacts related to the surrounding 18. It is thus possible to connect the first grid, for instance, to any of the internal six contacts, provided that the associated three contacts are immediately above, as shown in Fig. 5. If, however, you regard the lower row of contacts in the wiring diagram as representative of the internal row in Fig. 5, reading from left to right and starting with letter A, then the upper row, in the same order, will commence at A1 and proceed logically to F3. A good plan when wiring a switch of this type

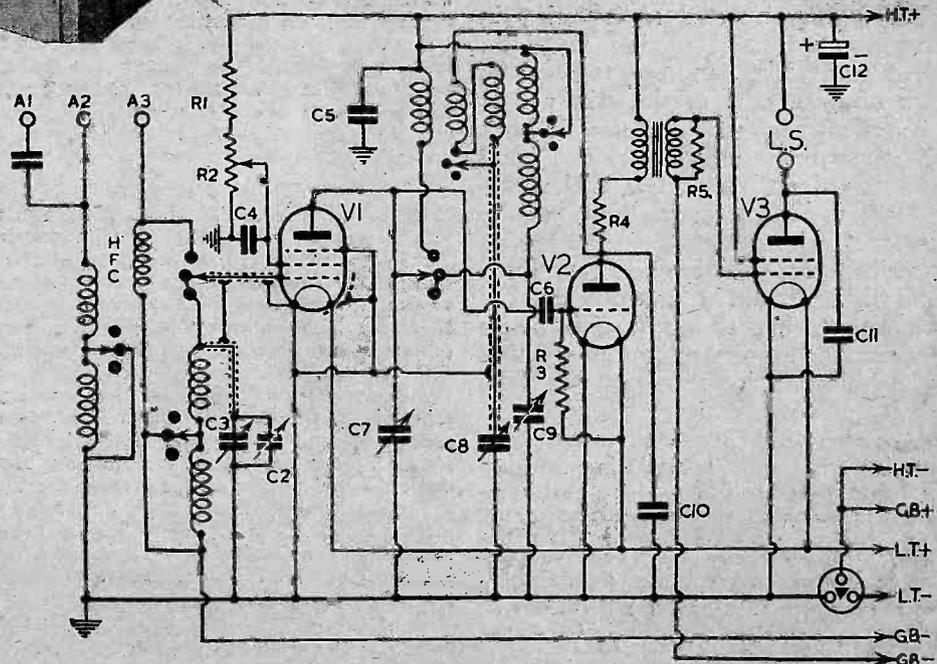

Theoretical circuit of the 50/- All-wave 3.

F. J. CAMM'S 50/- ALL-WAVE THREE

(Continued from previous page)

switch and the screened sleeving is there soldered together with a short length of bare wire, and this is taken through hole 5 in the chassis and returned to the moving vanes of the ganged condenser through the projecting arm on the centre plate. Battery leads are attached at the point indicated, and although these are shown projecting through the rear runner this has only been done for clarity and it is not essential to take them through this part of the chassis. In the chassis drilling details in Fig. 3 last week, we did not show a hole for these leads as it was thought desirable to leave the placing of this to individual requirements. In some cases a constructor may wish to use a horizontal type of cabinet with the speaker at one side of the set, and thus the batteries would have to be placed at the side of the set. There is ample room at hole 4 to enable all leads to be brought through at this point and this may therefore be used for the purpose. Alternatively, a clearance hole may be placed at any other part of the chassis, provided that care is taken to knot the cords or otherwise guard against their being pulled away from the point of contact when handling the plugs.

Trimming

Before testing the receiver the trimmers on the ganged condenser should be removed entirely. To do this, unscrew the adjusting nut and then carefully unscrew the small bolt which may be seen near the end of the soldering tag connection. When this has been removed the trimmer plate and mica washers may all be taken away, but the small bolt should be reinserted as it assists in holding the fixed section in place. It is preferable, therefore, to bend up the circular part of the trimmer to a vertical position and screw it back on the condenser, but do not bend the top down so that it will short-circuit to the projecting screw of the original trimmer.

When construction is completed the wiring should be carefully checked before placing valves and batteries in circuit. When quite certain that everything is in order connect the aerial and earth, using the medium-wave position for the aerial for preliminary tests. The bias applied to the first coil circuit should be 1.5 volts for preliminary tests. This may be modified as desired, the valve in that stage being a variable- μ type and increase of bias will decrease sensitivity. The bias for the output valve, with a 120-volt

H.T. battery, should be 3 volts. With these bias voltages the total H.T. consumption is approximately 10 milliamps. A reduction may be effected by increasing the bias on the output valve, at the sacrifice of the power-handling capacity and quality given by the set. Next switch the set on by means of the combined volume-control and on-off switch, and turn the wave-change switch to the central position (medium waves). Stand the set on its side and rotate the main tuning condenser until the local station is heard. The two small trimmers underneath will now enable you to bring the station into line with the engraving on the

dial and also to line up the two tuning circuits. When this has been done turn to a point at the top end of the medium-wave band and see if any adjustment is needed. The setting should hold good for long waves. On the short waves, of course, the trimmer for the aerial is not in circuit and the aerial is aperiodically coupled to the first valve. When satisfied that the trimming has been properly completed, the set may be turned over and is ready for installation in a cabinet. The correct impedance load for the output valve in this particular model is 16,500 ohms and the appropriate setting on the loudspeaker should be made for this value.

SPECIFICATION FOR F. J. CAMM'S 50/- ALL-WAVE THREE

One set of coils—broadcast, short-wave—and special S.W. choke (Peto-Scott), 10s. 6d.
 One .00043 mfd. two-gang condenser (C3 and C7) (New Times Sales), 4s. 6d.
 One slow-motion drive assembly, including scale, escutcheon, etc. (Peto-Scott), 5s. 6d.
 One plain wooden chassis with 3 runners (Peto-Scott).
 One multi-point switch, type S.208 (Bulgin), 3s. 9d.
 One reaction condenser, type C.V.19 (C8) (Bulgin), 2s. 6d.
 Two trimmers, type S.W. 99 (C2 and C9) (Bulgin), 9d.
 Six fixed condensers: two .0001 mfd., type P.C.301 (C1 and C6); one .0002 mfd., type P.C. 302 (C10); one .005 mfd., type P.C. 205 (C11); two .1 mfd., type P.C. P1 (C4 and C5) (Bulgin), 3s. 3½d.

One L.F. transformer, L.F.58 (Bulgin), 4s. 3d.
 One 8 mfd. electrolytic condenser, type 3017 (C12) (Dubilier), 2s.
 Four fixed resistors: one 25,000 ohm 1-watt (R1); one 2,000 ohm ½ watt (R4); one 250,000 ohm ½ watt (R5); one 2 megohms ½ watt (R3) (Erie), 1s. 3d.
 One volume control with D.P. switch (R2) (Erie), 4s. 6d.
 One 4-pin, one 5-pin and one 7-pin chassis-type valveholders (Clix), 1s. 8d.
 Six type 8 sockets (Clix), 6d.
 One component-mounting bracket (B.T.S.), 4d. (See text).
 Six No. 5 master plugs (Clix), 9d.
 Connecting wire, flex, one length screened sleeving, screws, etc.
 One V.P.215, one D210 and one Y.220 valve (Hivac).
 One 120-volt H.T. battery.
 One 2-volt L.T. accumulator.
 One W.B. Stentorian Junior loudspeaker.

TELEVISION FEATURES

TELEVISION DELICACY IN HONOUR OF FRENCH PRESIDENT

MARCEL BOULESTIN, the cookery expert, is devising a special television delicacy in honour of President Lebrun, who is on a State visit to this country.

M. Boulestin will describe his new dish, which he calls "Rouget Marseillaise," in the evening television programme on March 24th. "It will be patriotic—red, white and blue," says M. Boulestin. "To the red of a mullet, I shall add 'the blue of the sea,' and the bread will supply the splash of white. The whole will be perfumed with rustic poetry—and garlic."

"MAGYAR MELODY"

"**MAGYAR MELODY**," Eric Maschwitz's musical romance at His Majesty's Theatre, will be the first complete musical comedy to be televised direct from a theatre. Viewers will see the entire play on the evening of March 27th beginning at 8.30 p.m. and continuing with intervals until after 11 p.m.

Produced by William Mollison, the play is the work of Eric ("Balalaika") Maschwitz, former B.B.C. Director of Variety, Fred Thompson and Guy Bolton. Lyrics have been written by Harold Purcell and Eric Maschwitz, and the music is by George Osford and Bernard Grun.

The cast includes Binnie Hale, Arthur Margetson, Stella Arbenina, Roger Treville, Betty Warren, Jimmy Godden, Jerry Verno and Betty Bucknell. Walford Hyden conducts his Magyar Symphony Orchestra.

Three television cameras will be used, one being installed in a stage box for "close-ups" and two in the dress circle.

DINGHY SAILING

DINGHY sailing will be televised direct from the Thames at Putney on the afternoon of March 26th, when some thirty or forty of these small boats will come into the picture. The commentary will be given by Peter Scott, one of the outstanding dinghy enthusiasts in this country, who has represented Great Britain in dinghy races in America. Dinghy is an Indian word for "small boat." Viewers will see a large number of the twelve-foot type of dinghy assembled for a race. The boats must be passed as seaworthy, though this does not absolve the crews from acting as ballast; dinghies have no keels, and it requires some gymnastic skill to maintain stability in a squall.

"THE SWITCHBACK,"

A JAMES BRIDIE COMEDY

JAMES BRIDIE'S comedy, "The Switchback," which is to be televised in the evening programme on March 24th, deals with the adventures of a country doctor who believes he has discovered a cure for phthisis. But his cure is found to be based on a fallacy and the doctor after being involved in a newspaper stunt is struck off the Medical Register. It is then that his adventures begin, and he tastes the delights of freedom, described with all the fun and wisdom which are to be expected from a Bridie play.

James Gibson will play Dr. Mallaby, and the part of the errant Mrs. Mallaby will be taken by Leslie Wareing. The producer will be Moultrie Kelsall.

"The Switchback" will be repeated in the afternoon television programme on March 28th.

THINKING ABOUT PORTABLES

(Continued from previous page)

H.T. current consumption and the particular pentode employed. The current consumption is also governed by the voltage of the H.T. battery, of course. When the total current consumption is known, the value of the bias resistor can be calculated by dividing the G.B. voltage required by the current in milliamps, and multiplying the result by 1,000. Thus, if the total current were 8 mA and the voltage required 4, the value would be 500. As a matter of fact, this value is most frequently required.

Construction

With regard to the form of construction to be adopted, much depends upon the shape of container preferred, or upon the carrying case into which the set is to be fitted, assuming that a case is available. An old gramophone record case is often convenient, when the set can be made on a chassis built up from sheet aluminium and plywood as shown in Fig. 2. All receiver components are mounted on a strip of metal sheet made into a channel section about 2½ in. wide and 10 to 12 in. long. The tuning condenser, whether single or a two-gang unit, must be of the midget type and can be mounted on the metal strip. The speaker unit—a 5-in. cone would be necessary—is mounted as near as possible to the receiver components on the five-ply board, so that there is room for the batteries at the other side of the case. This general form of construction could be followed whether making a two- or three-valve receiver. It will be understood that a circular hole or a fancy fret would have to be cut in the side of the carrying case; this could be of greater diameter than the speaker cone, and could therefore be made central in the side of

be available, although these are not now made. A solid dielectric condenser would in any event be used for reaction.

It can be seen from Fig. 4 that a complete inner frame is made for the case, this being built from plywood and aluminium sheet; this makes the complete set easily removable from the case when it is desired to modify it. The speaker is mounted on a thin five-ply sheet, which also serves to conceal the batteries. This five-ply could be held rigid by passing screws through the

withdrawn the spring is stretched. Consequently, as soon as the end of the wire is released the spring rotates the spool and winds on the wire. Thin rubber-covered flex is most suitable for the aerial wire since it is easily coiled. The method of fastening the string to the spindle is to clamp it between two nuts or to tie it to a collar clamped to the spindle. It will be seen that the greater the diameter of the spool in relation to the diameter of the spindle, the greater is the length of wire

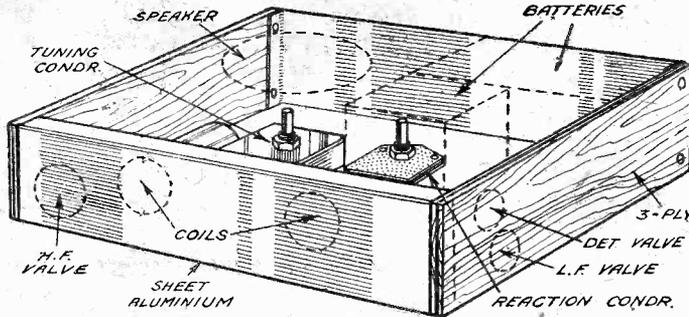


Fig. 4.—The illustration on the left gives an idea for the layout of a small portable to be carried in an attaché case of standard proportions.

edge of the case into small wooden blocks glued and nailed to the plywood, or by fitting such blocks to the sides of the inner frame and passing screws into these through the plywood.

Self-winding Aerial

It has been assumed so far that a throw-out aerial would be used. This is certainly recommended, partly because it is often more effective than a frame, but also because it considerably simplifies ganging difficulties. When using a frame considerable trouble is always experienced before two condensers—one acting on the frame and one on the inter-valve coil—can be made to line up; this is because of the entirely different inductive and capacitive

that will be self-winding. Usually a few feet is sufficient, but when a greater length can conveniently be used, an additional piece can be twisted round the end of the wire of the built-in aerial. Note that the end of the aerial wire is taken through a slot in one side of the spool and soldered to

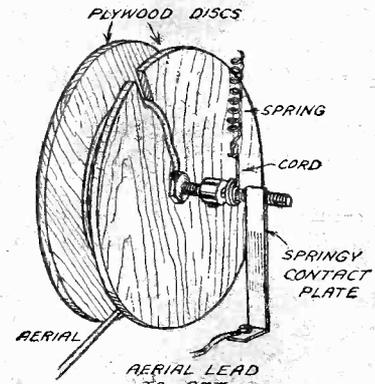


Fig. 5.—How a self-winding throw-out aerial can be made when the space permits. The "wheel" should be as large as permitted by the design of the set.

the spindle. Connection to the set is obtained through a springy contact plate.

Frame-aerial Data

As most readers are aware, if a frame is to be wound, the medium-wave section should consist of approximately 60ft. and the long-wave section of about 150ft. when the aerial is about 1ft. square. These lengths are given as approximate because they depend to a certain extent on the perimeter of the aerial. The lengths finally chosen must be decided by trial, arranging them so that the setting of the two tuning condensers (assuming that a separate one will be used for the frame) require to be set to about the same reading for any particular station.

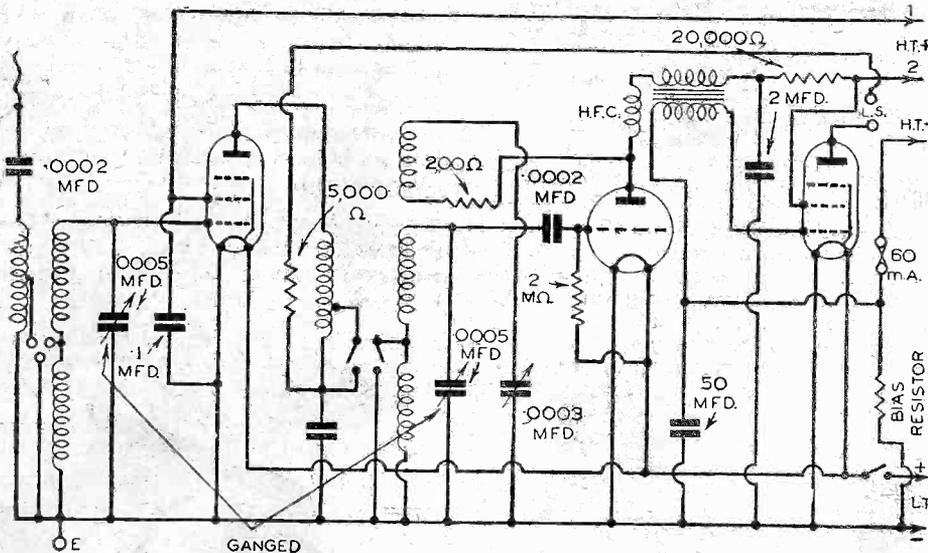


Fig. 3.—A three-valve circuit, with H.F. stage, which is more effective than the arrangement shown in Fig. 1.

the carrier. A large sheet of speaker silk could be glued over the plywood board to face the hole in the container.

For an Attaché Case

If the set were to be built into an attaché case of standard proportions the arrangement shown in Fig. 4 would prove convenient. In this case it would be necessary to use two separate condensers for tuning (if the H.F. circuit were adopted) unless the case were unusually deep. Alternatively, a two-gang solid dielectric condenser might

properties of the coil and frame. If it can be arranged, an excellent idea for the throw-out wire is that shown in Fig. 5, where it will be seen that the wire is self-winding on a spool.

The spool can be built up from discs of plywood or even stout card, and is firmly fixed to a 4 B.A. or 2 B.A. threaded spindle. A coil spring is anchored to the case and a length of thin, strong string is passed from this to the mounting spindle. When the wire is coiled on the spool the spring is not tensioned, but as the wire is

LATHE WORK FOR AMATEURS

By F. J. CAMM

1/-, or 1/2 by post from

George Newnes, Ltd., Tower House, Southampton St., Strand, London, W.C.2.

ON YOUR WAVELENGTH



Wireless Licence Increases

THE great increase in the listeners' army goes on, for the Post Office, in February, issued 839,500 receiving wireless licences, which represents an increase of 14,409 in the number of licence holders after making allowance for expired licences and renewals. The approximate total number of licences in force at the end of February, 1939, was 8,944,300, as compared with 8,561,340 at the end of February of 1938, an increase during the year of no less than 382,960. During the month there were 375 successful wireless prosecutions. These figures seem to indicate that very shortly the wireless market must depend for its profits upon replacements, or rather the sale of replacement sets, unless, of course, someone radically changes design by discovering some new principle, or inventing some new device which will render all our sets obsolete. It seems to me that the only thing in the scientific offing which can do this is the television receiver, for sometime in the not too distant future we shall all want to own television sets. We are told that television is here, and "you can't shut your eyes to it." Remember the old sets which were sold in thousands about a dozen years ago? No one thought that they would be obsolete within a couple of years. As soon as television has become a national service, and I hope it will be soon, our present receivers will be scrapped. I feel that the sooner the B.B.C. embarks upon a national television service the better. At present it is causing sales to languish, for people are awaiting its arrival, and they are afraid to purchase a new receiver lest it go out of date within a few months. When television is a national service I am certain that the licence figures will reach astronomical limits.

The Perfect Earth

BETWEEN moments of a calligraphical evisceration of my opinions, "Torch," as you know, bursts into song. I do not know whether the spring is responsible for the following, but as I should hate to think of "Torch" suffering from an ingrowing poem, once again I accord

By *Thermion*

him the privilege of my space for the following :

My bomb-proof shelter has arrived ;
 At present it's unused,
 And at such waste of useful space
 I am indeed bemused.
 Let's hope no swarms of foreign 'planes
 Will ever cloud our skies ;
 And, whilst we're waiting, cannot I
 Some useful end devise ?

" A hen-pen for some Plymouth Rocks ? "
 The wife says, " Just you dare !
 No beastly hens shall ever scratch
 My flowers up, I swear. "
 " A kennel, then, for Fido ? "
 The wife lets out a squeal ;
 " My darling Fido shall not sleep
 Inside those walls of steel ! "

" Some flowers, then, to fill the eye
 With pleasure and delight ? "
 " No, that's no use, for flowers need
 A good supply of light. "
 " Well, what about a rustic bower,
 In which to take our tea ? "
 The missus gives a nasty look,
 And says : " You're telling me ! "

" Then would it be of any use
 To do your weekly wash ? "
 " The laundry, sir, takes care of that ;
 Why must you talk such bosh ? "
 " An outdoor dormitory, then,
 When your relations come ? "
 The wife says, " Sure ! You sleep in it ;
 I hope you'll find it fun. "

* * *

Hush ! Half a mo ! I feel a rush
 Of brains towards my head !
 A length of insulated wire
 To it shall soon be led.
Three feet it's buried in the soil ;
 At last I see its worth.
 Loud cheers ! Whilst waiting for the bombs,
The perfect radio earth !

The " Comb "

IN a recent case in which twelve individuals were charged with and pleaded guilty to operating wireless sets without a licence, it was stated that Government officials had toured various streets in the town with an apparatus called the "comb," which enables them to detect houses in which radio sets are being used. I should very much like to know

how this particular piece of apparatus is able to detect a non-oscillating radio set. These Post Office people are very clever, I know, and I do not have sympathy for those who try to rob the B.B.C. of its small licence fee. You cannot obtain for 10s. such a service in any other industry, in any other country in the world, but my thirst for knowledge is whetted by the thought that they can detect a non-oscillating wireless set.

A Bigger and Better Radiolympia

I WAS present at a luncheon the other day where the guest of honour was Sir Stephen Tallents. He spoke on the B.B.C.'s plan to assist in making Radiolympia the biggest and best ever.

Emphasising the ambitious nature of the plans for this year's show, which will open on August 23rd, Sir Stephen said that the B.B.C. was already hard at work, in collaboration with the organisers—the R.M.A.—devising new attractions which would demonstrate to the public in a way which had never been done before the tremendous range of entertainment offered by modern broadcasting.

It was too early yet to give details of the lines on which they were working, but the B.B.C. looked forward to Radiolympia as their great opportunity and to taking a large and interested public behind the scenes of sound and vision broadcasting. He was certain that Radiolympia, 1939, would attract a record attendance to see and hear in novel form the latest developments in sound broadcasting and television.

Speaking of the R.M.A.'s plans Colonel Ozanne (Chairman of the R.M.A. Exhibitions Committee) stressed the diversity of the attractions which would be found at this year's Show. As well as being the focal point of radio interest throughout the country, Radiolympia would have something to interest everybody—young or old, technical or non-technical ; the enthusiast or the occasional listener.

Radiolympia, 1939, would, of course, show the world the very latest developments in British radio and television, but it would do very much more than that. Visitors

would be able to find a whole day's entertainment, whether by witnessing the dramatisation of broadcasting technique and personnel or in the many other features that were being planned, of a kind that could not be seen or heard anywhere else.

The Show would also be designed to bring home to listeners a fuller realisation of what they were missing by continuing to use old and out-of-date sets which could not possibly do justice to the realism of modern broadcasting. Some novel ideas were being developed to help the public to recapture the thrill and the imaginative appeal of radio.

With all these attractions, and with the earlier and more extensive publicity which was also being planned, a record attendance was expected this year, and the whole exhibition was being laid out on new lines making for the greatest possible comfort of the visitors.

"Each Instrument is Heard"

I MENTIONED the other week that one of the modern slogans is that the modern set enables you to hear all of the instruments in the band. My comment was as far as jazz is concerned that it is an argument in favour of an old set. The following rhyme summarises the situation:

Do we feel much exultation when we hear
a mighty "Bong,"
When a drummer too exuberant gives a
whack at brassy gong?
Does it introduce new pleasure in the bosom
of our home,
When we hear those dirty noises played
upon the saxophone?
Are we filled with joys ecstatic when the
cornet goes "wah-wah"?
And the trombone starts its wailing like
an elephant's pa-pa?
When with tintinnabulation which is
childish and absurd,
Is there any great advantage when "each
instrument is heard"?
And is there not more solace for our tired
and weary soul
When the instruments are blended into
one harmonious whole?
When the "Uke" is heard a-wailing and
the violin a-screach,
Are we not too sadly tempted for some
hefty thing to reach
To pitch at our poor radio set and stop
the beastly row,
Of bands and crooners making noises like
some love-sick cow?
And almost futile "Better Sets" to which
our fancies bend
Without improvement here and now—
from the "transmission end."
A better set becomes much worse! This
should not be forgotten!
When childish tintinnabulations make half
the programmes rollen.

Summer Use of Sets

AT the luncheon to which I have referred Sir Stephen Tallents dealt with the B.B.C. market research system which showed conclusively

Notes from the Test Bench

Hum and the Pick-up

ONE of the main difficulties which confront the user of a pick-up associated with A.C. mains apparatus is hum. In many cases when an existing set is modified so that a pick-up may be used it is found that hum cannot be removed. Screening the leads and with effective earth connections to the screens fails to effect any improvement. In several cases it has been found that the trouble is not due to the leads nor to the method of connecting the pick-up. The trouble in these instances has been direct induction between the motor and the pick-up coils. Where a synchronous motor is used it may be found that if the pick-up is held just above the turntable and slowly moved towards the centre the hum will increase as the pick-up nears the centre of the table. In some cases a sheet of metal on top of the motor-board, directly beneath the turntable, connected to earth may prevent the trouble, but several instances have been met where it has been impossible to cut out the hum unless the pick-up were changed.

Aerial Insulation

THE efficiency of the aerial is recognised as being one of the most important points of installation by most constructors, but the method of carrying out the best arrangement from an insulation point of view is not always appreciated. In many cases a good single insulator is used and thought to be sufficient. It must be remembered, however, that when an insulator is exposed to the air, especially in big cities, it quickly becomes coated with a film of soot which is conductive, and it is thus possible for the insulator to be short-circuited. A chain of insulators, even of very small dimensions, is preferable as, although these may also become coated, they will move in the wind and the risk of a continuous conductive path between each one will thus be removed. A long leakage path is the point to aim at.

Volume Controls

THE question as to whether or not a wire-wound volume control may be used in any particular circuit is not always simple of solution. Wire-wound components may be inductive, but apart from this fact the question of the current-carrying capacity has to be borne in mind. The wattage rating of the component should, therefore, be the first consideration, and a suitable component then selected at that rating. In H.F. circuits it is generally desirable to avoid inductive components.

that in the summer months the listeners who used their sets between 6 p.m. and 8 p.m. were 60 per cent. of the maximum winter total for that period, while after 8 p.m. the percentage was as high as 85.

Sir Adrian Boult to Visit Preston

THOUSANDS of music lovers in Preston, Blackburn, the Fylde, and North-west Lancashire generally, are looking forward to March 29th as the day which will bring a rare musical "treat" and the outstanding event of the music season in the north-west—the visit of the full B.B.C. Symphony Orchestra, under its conductor, Sir Adrian Boult, to Preston to give a public concert there.

It will be the seventeenth journey into the provinces to be made by this "crack" orchestra (of 119 players) which has a world-wide reputation. Since December, 1934, when the orchestra first appeared out of London—at Manchester—it has travelled as far north as Aberdeen and Dundee, as far west as Plymouth and Swansea, as far south as Southampton, and has played at most of the important centres of the Midlands and the northern counties of England.

Skilled Porters' Feat

IN its travels, undertaken in pursuance of the B.B.C.'s policy of making its Symphony Orchestra a national rather than a metropolitan institution, it has also gone abroad: in 1935 it played at Brussels, and in 1936 in Paris, Zurich, Vienna, and Budapest. Its appearances at these European cities, as at the British centres, were outstandingly successful.

It is a tribute to those responsible for the orchestra's journeyings that, in all the thousands of miles it has covered, not one of the 119 players' instruments has suffered.


Toscanini's Praise

THE orchestra has also in recent years had the honour of playing under the world-famous conductor, Toscanini, who, after their first series of concerts under his baton in 1935, said: "The B.B.C. Symphony Orchestra is one of the best I have ever conducted." In 1937 the orchestra gave two more series with Toscanini, summer and autumn, and a fourth in the summer of 1938. In May this year they will once again be conducted by the maestro in seven concerts of works by Beethoven. This will be the B.B.C.'s principal contribution to the London Music Festival, and the Queen's Hall is already sold out for all the seven concerts.

SHORT-WAVE SECTION

(Continued from previous page)

fication and obviously signals will be weaker. When headphones are used, however, it is surprising what range may be covered, and a study of the logs which have been published from time to time on our Letters page will show that this type of circuit in the hands of the amateur gives the best results. It needs a certain amount of patience to tune in stations from the most distant parts of the world, but when conditions are right it can be done. When conditions are wrong, then it will generally be found that the multi-valver will also be found wanting. For the beginner who is anxious to carry out real experimental work, we therefore recommend the detector L.F. combination, and when this is working properly time should be devoted to aerial design, with a view to overcoming the effects of fading. A careful note should

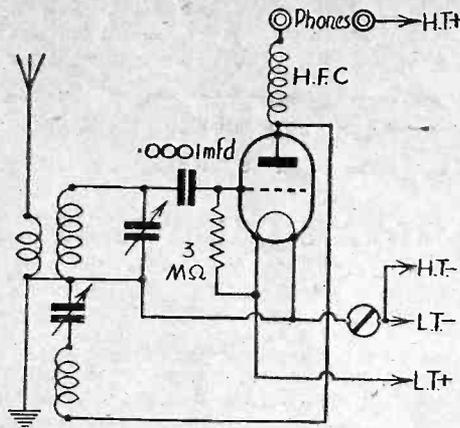

A single-valve receiver is often used with good effect by the beginner, in spite of its simplicity.

be kept of the experiments and the results obtained. Do not be haphazard in the experiments. Every change should be carefully recorded so that it is not difficult to know just what may be responsible for any change in the results obtained. Rotatable aerials; aerials with rotatable reflector systems; aerial networks and similar devices are undoubtedly the most practicable devices for the beginner, but unorthodox ideas should certainly be tried, as it is obvious that the characteristics of short waves are still only partly understood and it is often found that departure from orthodox methods usually results in discoveries which revolutionise modern practice.

The two extremes in short-wave receiver design are illustrated in this article, but it must again be emphasised that it is impossible to guarantee any particular performance for a short-wave receiver.

Leaves from a Short-wave Log

A 60-kilowatt for Lithuania

THE Lithuanian Government has earmarked in this year's budget a substantial sum of money to defray the cost of a 60-kilowatt short-wave station to be installed near the capital for the broadcast of the Kaunas radio programmes throughout the world. It is hoped to bring the new station into operation by the spring of 1940. In the meantime LYR on 32.21 m. (9.32 mc/s) is relaying these radio entertainments, but is likely to be replaced shortly by one of the following channels: LYZ2, 31.5 m. (9.523 mc/s); LYZ3, 25.21 m. (11.9 mc/s), or LYZ4, 19.61 m. (15.3 mc/s).

Albania Carries Out Further Tests

ZAA, Tirané (Albania), is trying out a series of channels; latest reports show the logging of experimental broadcasts from this station on 30.04 m. (9.987, 4 mc/s) between G.M.T. 20.45-21.00. Other channels tested are 19.03 m. (15.765 mc/s); 29.71 m. (10.097 mc/s); 40.07 m. (7.487 mc/s); and 41.61 m. (7.21 mc/s).

Addis Ababa Again Logged

THE Abyssinian short-wave transmitter has been heard working on 31.06 m. (9.66 mc/s) between G.M.T. 19.00-20.00. This is the channel used by LRX, Buenos Aires (Argentine Republic).

News from British Honduras

NEWS bulletins in the English language are broadcast daily at G.M.T. 01.30 every Wednesday, Friday and Saturday by ZIK2, Belize (British Honduras), on 28.3 m. (10.6 mc/s).

Latvia Tests on 10-metre Band

LISTENERS report reception of the first ultra-short wave broadcasts from a station giving the call YL2CB, and believed to be situated at Riga (Latvia). The channel used was 28.8 mc/s in the experimental amateur transmitter band: time: G.M.T. 15.00-15.30.

Proposed Short-wave Station for Palestine

IT is stated that a new short-wave transmitter is to be erected in the immediate vicinity of Jerusalem. Although, so far, no mention is made of the channel allotted, it is expected that it will be in the region of 14.4 mc/s.

Radio Eireann Testing

THE 1½-kilowatt short-wave station erected at Moydrum, near Athlone (Eire), is carrying out test broadcasts daily on 16.82 m. (17.84 mc/s) and on 31.27 m. (9.495 mc/s). Other channels to be tried out are 25.55 m. (11.74 mc/s) and 48.47 m. (6.19 mc/s).

Proposed Iranian Broadcasting Network

A CONTRACT has been placed with a British concern by the Iran (Persian) Government for the erection of a network of short-wave transmitters, including one of 2 kilowatts, and of which the power can eventually be increased tenfold. The channels allotted to this station are 30.99 m. (9.68 mc/s) and 48.74 m. (6.155 mc/s), and the call-signs are EQC and EQB respectively.

Radio Relays from Hawaii

THE channel adopted for the relay of programmes from Hawaii, and, in particular, running commentaries on football matches played in that island, for re-broadcast over the North American networks, is KQH, Kahuku, on 20.11 m. (14.92 mc/s).

Good Signals from Mexico City

BROADCASTS from the 10-kilowatt station XEWW in Mexico City, on 31.58 m. (9.5 mc/s), are easily logged between midnight G.M.T. and 01.00, i.e., on Sunday night-Monday morning, when an educational programme is transmitted in the English language. The call is *Radio Nacional Mexicana, La Voz del America Latina* XEWW (Aykis-ay-doble-vay). The interval signal heard consists of 4 chimes (ascending scale). The studio closes down with the call, and a message in the morse code, at about G.M.T. 05.00.

Broadcasts from China

IN addition to the transmissions made daily on 31.56 m. (9.5 mc/s), XGOY, Chungking, appears to be working also on 26.32 m. (11.4 mc/s) from G.M.T. 06.00-06.30. Listeners also state that broadcasts have been heard on 19.75 m. (15.19 mc/s). The station is on the air daily continuously between G.M.T. 21.00-23.30 with news bulletins in the English, German and French languages, and with a concert of Chinese native music.

New Swiss Radio Schedule

THE temporary 100-watt transmitter which is being tested by the Swiss Federal Communications Company (Radio Section) at Schwarzenburg (Switzerland) is now broadcasting regularly every week-day on 31.46 m. (9.535 mc/s) from G.M.T. 18.00-19.00; on 19.6 m. (15.305 mc/s) from G.M.T. 22.45-00.45, and on 25.28 m. (11.865 mc/s) from G.M.T. 01.00-02.00. Other channels to be tested are 11.7 m. (25.64 mc/s); 13.94 m. (21.52 mc/s); 16.87 m. (17.784 mc/s), and 49.55 m. (6.055 mc/s). The station will shortly be endowed with a 25-kilowatt transmitter.

Listen to Malaya

CAREFUL tuning in the afternoon hours may bring you a good programme from ZHP, Singapore, on 30.96 m. (9.69 mc/s). The studios are on the air from Monday to Saturday inclusive between G.M.T. 09.40-14.40, but the best time for reception in Western Europe is from G.M.T. 13.20 when the English news bulletin is given. If you hear our National Anthem at the close-down you may be sure of your correct identification.

Another Change in Colombia

HJ6ABA, Pereira, formerly on 48.82 m. (6.145 mc/s), then on 49.58 m. (6.054 mc/s), has reappeared in a new guise as HJ6AFC on 61.04 m. (4.915 mc/s). The call is: *Aquí la Voz de Pereira*, and a gong is heard as interval signal. Mention is frequently made in the programmes of "General Electrica." Address: Radiodifusora HJ6AFC, Señores Cesar y Mario Arango, Pereira (Republic of Colombia) South America.

A FINE TECHNICAL LIBRARY OF STANDARD WORKS

	Price.	By Post.
Practical Wireless Service Manual	5/-	5/6
Wireless Transmission for Amateurs	2/6	2/10
Sixty Tested Wireless Circuits	2/6	2/10
Wireless Coils, Chokes and Transformers and How to Make Them	2/6	2/10
Wireless Constructor's Encyclopaedia	5/-	5/6
Everyman's Wireless Book	3/6	3/10
Television and Short-Wave Handbook	5/-	5/6

THOSE PUZZLING PENTODES

(Continued from previous page)

were of the early large diameter air-cored class.

Single H.F. Stage

For a single H.F. stage circuit, it is permissible to use a straight or variable-mu S.G. or H.F. pentode, as the input, unless one is living in the swamp area of a transmitter, will not be too powerful for the valve to handle. The advantages of the variable mu type should not, however, be overlooked, so far as volume control is concerned, even in a simple set of this nature, especially if powerful signals are likely to be received. In the case of a two H.F. or a superhet receiver, it would be better to use a "straight" for the first stage and a variable mu for the second, while with a superhet the variable mu would be better for any pre-H.F. stages and the I.F. circuits.

Those particularly interested in quality reproduction, using, say, a one or two H.F. plus detector unit feeding into a high grade amplifier, do not always appreciate the advantage offered by the 7-pin type of H.F. pentode which, as will be seen by the diagrams, has its suppressor grid brought out to a separate pin. For example, when receiving the local station and requiring the best quality, the full gain and selectivity of the H.F. stages is not usually required. The normal volume control can be used, but that will not have the actual effect desired in such cases, but if a negative potential is applied to the suppressor grid, not only will the efficiency of the stages be decreased, but the selectivity will also be reduced, thus allowing the reproduction to be free from any frequency

cutting. The voltage will depend on the type of valve, though a maximum of 30 volts will be usually found sufficient.

MODERN PRODUCTION METHODS

ALMOST everyone is interested in mass-production methods, which are now widely applied to the construction of radio parts and receivers, but the motor industry is probably best known as the "home" of mass production.

It is fascinating to watch the assembly of a car chassis as it passes along an endless-belt conveyor. First there is the frame; then axles and wheels are attached; the engine is fitted; and so the work proceeds. The processes involved are interestingly explained in the issue of our companion journal, *Practical Motorist*, dated March 18th, now on sale. The explanation is well illustrated by photographs.

In the same issue maintenance of the B.S.A. "Scout" is fully dealt with, whilst there are many other practical articles and touring features. "Replies to Readers' Queries," "Notes from a Garage Mechanic's Diary," "At the Wheel," "Topical Notes of the Week," and "Sportfolio" are other popular items included in every issue.

PATENTS AND TRADE MARKS

Any of our readers requiring information and advice respecting Patents, Trade Marks or Designs, should apply to Messrs. Rayner and Co., Patent Agents, of Bank Chambers, 29, Southampton Buildings, London, W.C.2, who will give free advice to readers mentioning this paper.

BOSWORTH RECORDINGS

EXPERIMENTERS and quality enthusiasts will be interested in a series of records obtainable from Messrs. Bosworth and Co., Ltd., of 8, Heddon Street, Regent Street, London, W.1. These are standard 10in. discs designed for a standard playing speed of 78 r.p.m. They are designed primarily for dubbing on cine film, and to this end they all bear on the label the exact time of playing. Furthermore, in addition to standard melodies, there are a number of special recordings, such as trumpet fanfares (six to a disc); short sound titles each of .07 seconds duration; etc. Although many of the discs contain a single tune per side, there are quite a number in which two or more melodies are contained on each side and there is a short silent period between the tunes. The track is, however, continuous. We have used some of these records for test purposes and are much impressed with the wide overall frequency response and absence of surface noise. After several hundred playings one of these discs is only just showing signs of breaking down.

New Melodies

From an entertainment point of view the melodies available are a complete change from the hackneyed tunes which one now hears every day, and to assist customers to select appropriate discs the makers have prepared a useful list which bears a classified section, dividing the records into Agitato, Furiosos, Comedy and Light Novelties, Galops, Martial, Eccentric, Grotesque, etc.

The records cost 2s. 6d. each and a descriptive list may be obtained on application to the above-mentioned address.



HALF-PRICE QUALITY MIKES

ENTIRELY new models for professional use, P.A. work and Home Broadcasting. For use with Peto-Scott amplifiers or simply attach to your present radio. Supplied with 25ft. of Flex-Desk Model in beautiful bakelite mounting. Cash or C.O.D. only 25/- or 2/6 and 9 monthly payments of 3/-. Professional chromium-plated floor stand model 42/- only or 2/6 down and 10 monthly payments of 4/6.

7 WATT AMPLIFIER

A.C. You pay a third of the usual price for this powerful unit. Employs 4 valves, two in push-pull providing 7 watts undistorted output for Club or P.A. use. Wide sound range. Connections for Mike or Gramo. Our price 23.10.0 or 5/- down and 11 monthly payments of 6/9. S/W ADAPTOR/CONVERTER for A.C. or battery receivers. 13.74 metres. Employs switched coil unit, metal chassis and panel. Amazingly simple to assemble. Complete Kit, with instructions, 25/- or 2/6 down and 9 monthly payments of 3/-. Battery Valve, 3/9 extra; Mains type 6/6.

TROPHY S/WAVE RECEIVERS. You'll buy a TROPHY sooner or later for best short-wave listening. Secure your model now. You contact the world with a TROPHY—hosts of transmissions to be heard, impossible on the ordinary type of set.

TROPHY 8. Communication type. Wave-range 7-550 metres. 8 valves. Bandspread tuning. All refinements for the Amateur Transmitter. Phone Jack. Housed in pleasing cabinet with sockets for using separate P.M. speaker. Price 12 gns. or 15/6 down and 18 monthly payments of 15/6. For A.C. mains only.

TROPHY 5. The amazing shortwave, recently praised by Mr. Cann. 5 valves. Wave-range 10-550 metres. Bandspread tuning. A.V.C. B.F.O. Built-in speaker and phone jack. For A.C. mains use. Cash or C.O.D. 29, or 10/9 down and 18 monthly payments of 10/9. A junior communication model you will be proud to own.

TROPHY 3. Battery and A.C. 3-valvers which have sold to short-wave listeners better than all other makes put together. Coverage 6-550 metres. Self-loading coils. Calibrated scale. Built-in speaker. Phone Jack. Pleasing cabinet as illustrated.

BATTERY model, £5.15.0 or 7/- down and 18 monthly payments of 7/-. A.C. Model 6 gns. or 7/6 down and 18 monthly payments of 7/9. Supplied with coils for 12-52 metres.

Your ££££'s Saving

SHOPPING GUIDE

See previous issues for detailed specifications or lists sent FREE.

MR. CANN'S AMAZING ALL-WAVE 3 PILOT KIT "A" comprising all components for receiver kit, including specified Peto-Scott Chassis, Panel, Coils, Choke, Station-name Scale, Bulgin Switch. All remaining necessary parts, wire, flex, screws, but less valves and speaker. Cash or C.O.D. 50/- or 4/6 down and 12 monthly payments of 4/6. 3 specified valves 21/9, or add 1/9 to deposit and 1/11 to monthly payments.

PRESS-BUTTON CHASSIS
With Manual Tuning also

ALL-WAVE 7-Stage S/HET Battery Model 903. Modern 4-valve circuit arrangement as Model 902, but with the addition of 6-station press-button tuning. Complete with 4 valves. Normal list value, 7 gns. OUR PRICE, 25/12/6, or 6/9 down and 18 monthly payments of 6/10. We Save You 1/14/6.

ALL-WAVE 6-Stage S/HET A.C. Model 905. Employs all the desirable features incorporated in Model 904, but with 6-station press-button tuning in addition. 3 watts output. Complete with 4 valves. Normal list value, 28/19/6. OUR PRICE, 26/19/6, or 9/6 down and 18 monthly payments of 8/7. We Save You 22/0/0.

ALL-WAVE 7-Stage S/HET A.C. Model 908. An excellent 5-valve, 7-stage replacement chassis. 18-2,100 metres. A.V.C. and Tone control. 6-station press-button tuning, in addition to 5-junction manual tuning. Complete with 5 valves. Normal list value, 41/0/2/6. OUR PRICE, 27/12/6, or 9/6 down and 18 monthly payments of 9/4. We Save You 42/10/0.


ALL-WAVE 8-Stage S/HET A.C. Model 909. This advanced 8-stage 6-valve chassis represents wonderful value for the connoisseur. Wave-range 10-2,000 metres. A.V.C. Station and metre calibrated scale. 6-station press-button tuning. Pick-up sockets. 2 watts output. Complete with 6 valves. Normal list value, 41/0/10/0. OUR PRICE, 27/19/6, or 9/9 down and 18 monthly payments of 9/9. We Save You 42/10/6.

SPEAKERS for chassis 901, 902, 903, 21/- extra, or same deposit but add 1/5 to monthly payments (add 2/- to payments for 901 chassis). Speaker for 904, 905 and 908 chassis, 19/6 extra, or add 1/4 to chassis monthly payments. Speaker for 909 and 909M.T. chassis 27/6 extra, or same deposit, but add 1/10 to monthly payments.

PETO-SCOTT MAINS UNIT. Suitable for all battery sets requiring up to 12 m/a. Employs metal rectifier. For A.C. mains only. 200/250v. Special Bargain 19/6. Available H.P. with other goods.

A.C. TRICKLE CHARGER. Does away with constant L.T. upkeep. Merely connect to mains and your L.T. accumulator. A.C. 200/250 supplies only. Special Offer 10/-.

Enjoy noise-free listening

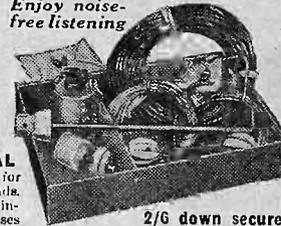

2/6 down secures complete outfit with instructions. Cash or C.O.D. 17/6 or 2/6 down and 8 monthly payments of 2/6.

MANUAL TUNING CHASSIS
See centre column for Press-Button models

ALL-WAVE S.G.3. Battery Model 901. Proved sensitive 3-valve H.F. Pent., Det. and Harries distortionless output Pentode. Wave-range, 18-2,100 metres. Station and metre-calibrated scale. All-world reception. Low H.T. consumption. With all valves. Normal list value, 5 gns. OUR PRICE, 23/12/6, or 5/- down and 12 monthly payments of 6/2. We Save You 1/12/6.

ALL-WAVE 7-Stage S/HET. Battery Model 902. Sensitive and selective 4-valve circuit. All-waves, 18-2,000 metres. Phatted output. Station-name and metre calibrated scale. Complete with 4 valves. Normal list value, 26/19/6. OUR PRICE, 24/17/6, or 5/- down and 18 monthly payments of 6/1. We Save You 21/19/0.

ALL-WAVE 6-Stage S/HET. A.C. Model 904. Amazingly selective 4-valve circuit. All-world reception on 18-2,000 metres. Volume and Tone Controls. 3 Watts output. With all valves. Normal list value, 27/10/0. OUR PRICE, 25/19/6, or 7/3 down and 18 monthly payments of 7/3. We Save You 21/10/6.

ALL-WAVE MODEL 909 M.T. (Illustrated.) Exactly as Model 909 (centre col.), but for those who prefer hand tuning only. List value 29/19/6. Our price 26/19/6 or 8/9 down and 18 monthly payments of 8/9. We Save You 23. ALL MODELS EMPLOY DIAPHRAGM ILLUSTRATED.

12 MONTHS' GUARANTEE

IMMEDIATE DELIVERY All lines from stock for personal shoppers. All branches given below. Delivery by return on all post orders. Over 100 post and C.O.D. charges paid. (Overseas orders extra). LISTS FREE.

PETO-SCOTT Co., Ltd., 77 (P.W.32) City Rd., London, E.C.1
Tel. Clissold 9875 and HOLBORN 3248

SAVE! Buy a Chassis

Practical Television

March 25th, 1939.

Vol. 4.

No. 144.

Picture Examination

THE acceptability of television pictures to the general public has been the subject of many close investigations by various scientists who have brought physical, physiological, and psychological factors to bear on the problems involved. It is open to question at the moment, however, as to whether the scientist can really interpret these matters from the point of view of the home, where individual atmosphere and environment must play an important part in assessing the home entertainment value. Even so, it is both interesting and instructive to examine the conclusions arrived at by these researches into human problems, and one of the most thorough was that undertaken in Germany where, strangely enough, no real public service of television yet exists. The results, therefore, although interesting, are not actually based on public experience, but represent the findings of an investigator who has endeavoured to place himself in the position of a domestic or family viewer. One conclusion which seems fairly reasonable is to the effect that the normal contrast range in modern television receivers using cathode-ray tubes satisfies all requirements, provided that stray light is excluded from the vicinity of the screen. Where stray light does interfere, however, then it is said that the brightness level in interlaced images is limited by flicker. This is important when it is remembered that in many households, viewing is undertaken with some of the room lighting operative. The more light present, the brighter the cathode-ray tube has to run, and the less is the contrast range in the observed picture. In dealer demonstration rooms, some have adopted the policy of having an amber coloured light during transmission periods. This avoids any groping in the dark for late comers, and in no way interferes with the picture.

Other Factors

THIS same German investigator has come to the conclusion that with a 441 line definition such as is used for the transmissions in that country, the picture size should not exceed about 12in. by 10in. There is no doubt that the dimensions of the receiver image have been the subject of many debates, and it is generally agreed here that a 15in. diameter cathode-ray tube represents a reasonable maximum for the ordinary-sized room, while the 12in. diameter tube giving a 10in. by 8in. picture is undoubtedly the most popular in the average household. The very large screens

in home sets where a projection C.R. tube is employed need quite big rooms, and a long viewing distance, to do real justice to the reproduced image. Another very interesting point raised by the same investigator is to the effect that since television, in his opinion, can be considered as the optical counterpart of audio broadcasting, it calls for very high acoustical reproduction to be acceptable. The reason advanced for this is the conclusion that the success of sound motion pictures, and the justification for their existence as an entity, depend upon the quality of silent motion pictures considered by themselves. It is, of course, known that with the present B.B.C. television service the sound signals are far superior in quality to ordinary radio, because a wider sideband is permissible on the ultra-short waves.

A Limitation

IT is generally conceded that one of the limitations existing insofar as television engineering is concerned, and one which is emphasised in large-screen work, is an inherent difficulty at the transmitting end. At the moment no two television cameras are identical in all their electrical characteristics; a point brought home quite

forcibly when three or four cameras are in use for a single production, and fading from one to the other is essential to give full programme entertainment. Lighting suitable for one is unsatisfactory for another camera, and rapid light changes are both difficult to achieve, and cause very unpleasant shading effects if they are introduced. Evidence of this is forthcoming whenever a feature film is shown, and the alterations in light level brought about by changes in light density destroy for a time the tonal value of the received picture. Better cameras in conjunction with improved methods for tracking, and lens focus adjustment, have helped matters considerably of late, but as programmes become more and more ambitious film studio technique will have to be studied very carefully. This again is yet another reason why the basic problems of film and television requirements should merit a closer co-operation. Any segregation of the old and new arts will only add to confusion, and it is encouraging to find that in some quarters a better understanding is prevailing, a factor which cannot fail to benefit the one who, after all, must have the final say in the matter—that is, the set user, whether domestic or otherwise.



Mr. A. P. Herbert, M.P., who is steeped in the lore of canals and waterways of England, was commentator when life on the barges was televised by the B.B.C. last week. The cameras were placed on a stretch of the Grand Union Canal, round a lock which is a favourite meeting-place for the barges and their families. The camera is here seen televising Mr. Herbert whilst he is chatting to Mr. and Mrs. Edwards on their barge at Clitheroe Lock, Brentford.

TELEVISIONS

Signal Attenuation

ALTHOUGH as a general rule the aim of television engineers is to secure the maximum signal strength available at any given area, there are many occasions which arise in practice that call for a television signal attenuated in magnitude. When close to the transmitting station the direct signal pick-up with a normal aerial may be sufficient to overload the cathode-ray tube with normal receiver control knob settings, with the result that the gain control has to be turned back to a setting where the vision chassis is not functioning efficiently and distortion can occur. By introducing a simple combination of resistances between the feeder cable termination and the set input, the signal strength can be reduced to any desired value simply by using the correct resistance values in the attenuator pad, as it is generally referred to by most engineers. It is essential that uniformity in impedance is maintained at the input and output terminals of this resistance junction, otherwise phase reflections can occur which will mar what would otherwise be a good picture. This problem of reducing the amplitude of an available signal by a given amount is met with in other television equipment, and it was therefore interesting to find that a scheme has been proposed whereby attenuation can be carried out electronically. The signals to be attenuated are applied to a grid mesh electrode of a special type of electron multiplier in such a way that they control a stream of electrons provided by a light activated cathode. The emerging stream is magnetically directed towards another set of electrodes where the potentials applied to them are controlled in such a manner that the predetermined fraction of signal is derived from a perforated grid.

A Man of Vision

NO one can deny the sincerity of Gerald Cock for television, and his position as B.B.C. director of the service has enabled him to make some very interesting contributions to the various opinions which exist as to the best method of expanding the service. Bearing in mind the details given in various notes in these pages it is useful to know that Mr. Cock envisages a five-year plan for the expansion of television to cover the whole country. He favours the erection of relay stations which will be able to transmit the programmes provided from a central source of production, for in this way it is claimed that wasteful and expensive duplication of plant, staff and material will be avoided. The length of

weekly programme desired by viewers in general is also a matter undergoing investigation at the moment. At present it averages between 19 and 20 hours per week. Although it is realised that television viewing demands concentration on the part of those looking in, this hardly seems sufficient to meet all needs. The programmes must be varied, and any extension of choice will naturally mean a longer time on the air per week. Each week it is possible to select a number of outstanding items which give remarkable entertainment value, but with a public who have been satiated with forms of amusement both radio and otherwise which give many alternatives, it seems certain that an extension of hours is imperative if more and more people are to acquire sets for home use. The problems associated with this are not easy, because of rehearsal periods, but no doubt those in authority will eventually find means for satisfying the wishes of the public.

MORE IMPORTANT BARGAINS

This Week's Best Sellers—Order NOW

VALVES FREE! with these

N.T.S. Short-wave Kits
 1-Valve SHORT-WAVER. 12/94 metres. All coils, lightweight phones [and free matched valve. List value 55/- BARGAIN. 21/7/6 or 2/6 down and 12 monthly payments of 2/6.

4-VALVE BANDSPREAD
 Powerful S.G., Det. L.F., Pentode receiver with bandspread tuning. Amazing efficiency over the effective wave-range of 9-200 metres. Complete down to the last screw, coils for 12-94 metres. 4 FREE valves. 49/6 cash or 3/6 down, and 12 monthly payments of 4/3. SEND FOR SHORT-WAVE BOOK.



MORE CHASSIS BARGAINS
 Amazing with every confidence. Complete specifications available on request.

SPECIAL OFFER CLASS "B" 4-valve CHASSIS. Powerful new model giving volume equal to a mains set. Amazing range and sensitivity. Full-vision scale calibrated 200-2,000 metres. Steel chassis and screened coils. Complete with all valves. Fully tested. List value 5 gns. BARGAIN 59/6, or 5/- down and 12 monthly payments of 5/3. Order type 60410.

A.C. S.G.4. BANDPASS CHASSIS. A few left. Wave-range 200-2,100 metres. Wonderful selectivity and sensitivity. Output 3 watts, P.U. sockets. Steel chassis and screened coils. Complete with 4 British Matched valves. Ideal replacement chassis for A.C. mains. Fully tested. List value 45/15/0. BARGAIN 55/- Yours for 5/- down and 12 monthly payments of 5/- Order type 7033.

BATTERY ALL-WAVE CHASSIS SNIP. Wave-range 14-2,000 metres, station-name scale. Complete with S.G. Det. and Pentode valves. New, fully tested. BARGAIN 65/- or 5/- down and 15 monthly payments of 5/-.

RIGHT-PRICE PARTS

BARGAIN PARCELS. No Constructor, Experimenter or Serviceman must miss this opportunity. 1 each 2 and 3 gang variable condensers, 1 screened coil, 1 audio transformer, 3 valve holders, 6 resistances, 6 fixed condensers, 1 doz. various control knobs and 1 brand-new ready-drilled plated steel chassis. List value 45/- BARGAIN 5/9, plus 9d. for special packing and postage. ORDER EARLY.

BAR-TYPE 2-GANG CONDENSERS. .0005 mfd. each section. Brightly plated, size 3in. x 2 1/2in. x 2 1/2in. New, worth 12/- BARGAIN, 2/3.

METAL CHASSIS. Steel, ready drilled for 1.8 valve-holders. Electrolytics and mains transformer. Size 10in. x 9in. x 3in. grey enamel finish, brand new. BARGAIN, 2/- each. Also Brand new heavy gauge Cadmium-plated steel chassis, 14 1/2 x 7 1/2 x 2 1/2in., ready drilled for 5 v-holders, mains transformer, etc. BARGAIN, 2/- Post 6d. extra.

COILS. Parcel of 4 assorted screened and unscreened coils for experimenting. Well-known makes. BARGAIN, 2/9

TRIPLE CHARGER. 2, 3 amp. Model. Metal Rectifier, 10/-


KNOBS. 1 doz. assorted control knobs, 12/-

VOLUME CONTROLS, POTENTIOMETERS. Well-known makes, all values up to 1 meg, 2/-; with switch, 2/6.

HEADPHONES. Supersensitive type, 3/6 per pair. Post 6d.

RESISTORS. All values, 1-watt, 4d.; 3/8 doz. 1-watt, 5d.; 4/8 doz. 2-watt, 8d.; 6/8 doz. 3-watt, 9d.; 8/- doz.

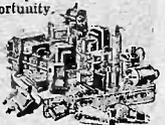
COSMOCORD PICK-UPS. Brand new, complete with screened lead and rest. List 15/- BARGAIN, 6/6.



BARGAIN NEWS!!
N.T.S. HAVE SECURED—

... a further limited quantity of famous Peto-Scott all-wave battery receivers offered to you at practically half cost.

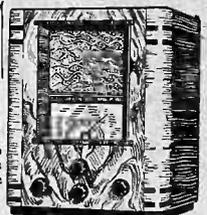5/- secures this
 down SUPER ALL-WAVE BATTERY S.G.3.



List value 28.15.0 BARGAIN 24.19.6. Wave-range 14-2,100 metres. Modern HF, Det. and Harries Pentode output circuit. Easy-to-read station dial, superb walnut veneer cabinet. Less batteries. 5/- down only, balance in 18 monthly payments of 6/4. YOU MUST ORDER EARLY.

TESTED KITS—VALVES FREE

"World" All-Wave Kits are supplied less coils to accommodate those who already possess famous B.T.S. self-locating indicators.

ALL-WAVE WORLD S.G.3. Wave-range 9-2,000 metres, slow-motion tuning. Station-name scale. Kit includes all parts with transformer, etc., and FREE S.G. Det. and Pentode valves. List value of 41/15/0. BARGAIN 29/6 or 2/6 down and 12 monthly payments of 2/10.

ALL-WAVE WORLD S.G.4. Employs one more S.G. audio stage than the 3-valve model and all extra components. Station name scale. 4 valves given FREE. Astounding BARGAIN at 42/- cash or C.O.D., or 2/6 down and 12 monthly payments of 3/6.

COILS. Complete set of 10 coils, 9-2,000 metres. List 27/6. N.T.S. BARGAIN, 17/6, or add 1/6 to World Kit deposit and to each monthly payment. N.T.S. SHORT-WAVE BOOK—FREE.

POST ORDERS. All goods offered sent carriage or post charges paid. C.O.D. charge extra on orders under 10/-. Overseas orders carriage extra.

CALLERS. All lines available to callers at our only address. Call in for complete bargain lists without obligation to purchase.

FREE Send now for your copy of the N.T.S. Short-Wave Bargain booklet; also Bargain A.C. and Battery Chassis List and valve replacement chart.

BOOSTER BARGAIN
4-WATT BATTERY AMPLIFIER

55/- CASH List value **4/6** down
 C.O.D. 24.4.0.

balance in 12 monthly payments of 4/8. Improved 1939 model, 4-valve circuit with push-pull output. 4-watts output. Ideal unit for use with microphone or amplifying gramophone records. Recommended for boosting up existing battery receiver where 1-4 watts output is needed. Avoid disappointment—ORDER NOW.

LIST "V" Every "Practical Wireless" reader should be in possession of this money-saving valve list. N.T.S. can offer you a British mains or battery valve replacement for any required type ALL AT AMAZING BARGAIN PRICES.

3 MATCHED Battery Type VALVES Bargain **5/6**
 2-volt type (1A4E, 1B4E, 2,101), 2 S.G. H.F.'s and one Output Pentode; List value 35/- YOURS FOR 5/6 only, POST FREE. 3 valve-holders, data and circuits given FREE. Ideal valves for experimental purposes. Short-Wave, and All-Wave receivers and replacement. Secure your set NOW.

PERSONAL PARAGRAPHS

Mr. M. M. Stockley has resigned his position as London sales manager of British Belmont Radio, Ltd.

Mr. L. Glazer, after three years' association with Philco, has left to join Arvin Electric, Ltd., as sales manager for Arvin Autovox car radio receivers.

Sir Allan Powell, the newly appointed chairman of the B.B.C., will take over his new duties on April 20th. Sir Allan, who is at present the Mayor of Kensington, succeeds Mr. R. C. Norman at the B.B.C.

The Postmaster-General has appointed Mr. D. J. Lidbury, D.S.O., Regional Director of the London Postal Region; Mr. V. R. Kenny, M.B.E., Regional Director of the North Western Region; and Mr. C. A. Taylor, M.C., Regional Director Designate of the London Telecommunications Region, to be members of the Post Office Board. The appointments will take effect from May 1st, 1939.

WORKSHOP CALCULATIONS, TABLES AND FORMULAE
 3/6, by post 3/10 from
 George Newnes, Ltd.,
 Tower House, Southampton St., Strand, W.C.2

NEW TIMES SALES CO.
 58 (Pr.W.32), LUDGATE HILL, LONDON, E.C.4.
 Phone: City 5516 Est. 1924



FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I. C. S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 94A, International Buildings, Kingsway, London, W.C.2.

Please explain fully about your Instruction in the subject marked X.


Radio Engineering Radio
Radio Servicing Television

If you wish to pass a Radio examination, state it here.....

Name..... Age.....

Address.....

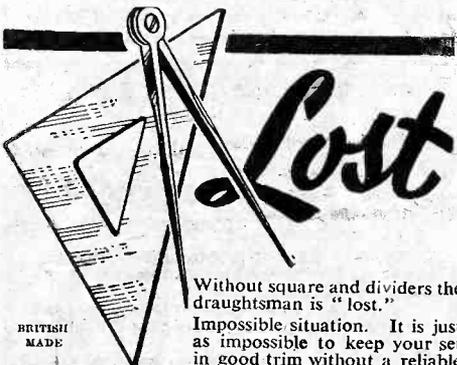When writing to Advertisers please mention "Practical and Amateur Wireless"



Without square and dividers the draughtsman is "lost."

Impossible situation. It is just as impossible to keep your set in good trim without a reliable meter. The D.C. AvoMinor tells you all you want to know; troubles are instantly traced; falling-off in performance is immediately checked.

45/- in case, with instruction booklet, leads, interchangeable test prods and crocodile clips.

DEFERRED TERMS IF DESIRED.

Voltage	
0- 6 volts	0-240 volts
0- 12 volts	0-300 volts
0-120 volts	0-600 volts
Current	
0- 6 m/amps.	
0- 30 m/amps.	
0-120 m/amps.	
Resistance	
0-10,000 ohms	
0-60,000 ohms	
0-1,200,000 "	
0-3 megohms	

The D.C. AVOMINOR

Regd. Trade Mark

ELECTRICAL MEASURING INSTRUMENT

Write for fully descriptive leaflet

Sole Proprietors & Manufacturers:-

Automatic Coil Winder & Electrical Equipment Co., Ltd.
Winder House, Douglas St., London, S.W.1. Phone: Victoria 3404/7.

Items of Interest

Arthur Askey to Make Films

SO the man who kept the British Public at home on Wednesday nights is to go on the films. Arthur Askey is not the first radio favourite to be lost to listeners, and he won't be the last.

According to the well-known film critic, C. A. Lejeune, writing in this month's *Screen Pictorial*, "Big-hearted Arthur" is to make films for the next five years for



Arthur Askey in one of his characteristic poses.

Gainsborough. Three film companies offered him contracts. "The first was good," he says. "The second, better, and the third, magnificent."

"The Prisoner of Zenda"

WHEN he invented the imaginary country of Ruritania, Anthony Hope, even in his most sanguine moments, can have had little idea of the world-wide success that his romance would enjoy. "The Prisoner of Zenda" has been translated into practically every language in the world, in addition it has come before the public as an operetta, a play, a silent film and a talkie, and has been the model on which countless works of the cloak and sword type have been based.

The book has been adapted by Jack Inglis as a serial play for broadcasting and nine instalments will be heard on consecutive Sundays, the first broadcast being on April 2nd, in the National programme. The two chief rôles, Rudolf Rassendyll and Colonel Sapt, will be played by Robert Douglas and Milton Rosmer respectively, and the production will be in the hands of Leslie Stokes.

Just before his sudden death recently, Robert Chignell was engaged in writing special music for this serial. He had finished a melody for the Ruritanian National Anthem, and this will be orchestrated and variations of it prepared by Leslie Woodgate. The music will be recorded by the B.B.C. Symphony Orchestra, Section C.

Crosley Corporation Applies for Television Construction Permit

THE CROSLLEY CORPORATION, operators of Station WLW (Cincinnati) recently filed an application with the Federal Communications Commission for permission to construct a television transmitter in Cincinnati. The application filed is for a construction permit only. This entails building two transmitters, one for video or visual broadcasting, and the other for audio or sound broadcasting in connection with the video transmitter.

In the event of the application being granted, the Corporation has six months in which to construct the television station.

The station, according to the plan, will be of 1,000 watts power, and will operate on a frequency band between 50 and 56 megacycles. A leeway of this magnitude is necessary for television, engineers pointed out, adding that the one station would require a band six times wider than the present standard broadcasting band of from 550 to 1,500 kilocycles.

Deputy Television Announcers

WE are informed by the B.B.C. that Miss Olga Edwardes, and Miss Eileen Bennett, have been booked as deputy television announcers during the absence on annual leave of the two regular announcers, Miss Jasmine Bligh and Miss Elizabeth Cowell.

Miss Edwardes, deputising for Miss Cowell, has been booked for dates between March 30th and April 17th.

Miss Bennett, who will be deputising for Miss Bligh, will be on duty at intervals from March 24th till April 4th.

Miss Edwardes, who is twenty-two years of age, is a brunette, and is already well known to viewers as an actress, her most recent appearances being in "Condemned to be Shot," by Reginald Brooke, and Noel Coward's "The Young Idea." Beginning as a ballet dancer trained by Anton Dolin and Brigitta, she has taken both stage and film parts, her last engagement being in the film version of "The Dominant Sex." She prefers stage acting to films.

Miss Bennett, who is nineteen years of age, is a blonde, and was trained at the Royal Academy of Dramatic Art. She has had considerable recording experience in plays and sketches, and has just taken the juvenile lead in a new film, "The Trunk Crime."

PRACTICAL LEATHERWORK AND OTHER ALLIED CRAFTS

By Fred Jace

This handbook not only deals exhaustively with leatherworking, but other crafts such as Appliqué, Gesso, Raffia, Batik, stencilling and rugmaking. It contains 96 pages and 179 photographs and diagrams.

From all Booksellers, 1s., or by post 1s. 2d., from the publishers, George Newnes, Ltd., (Book Dept.), Tower House, Southampton Street, Strand, W.C.2.



LETTERS FROM READERS

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

A Simple U.S.W. Adapter

SIR.—Regarding the letters of W. W. Llewellyn and T. A. Lane in the issues of February 18th and March 11th respectively, I also should like to see a U.S.W. adapter described which could be plugged into the P.U. terminals to receive the television sound, especially for mains operation.—**GEO. S. COLLIE** (West Looe, Cornwall).

SIR.—I follow with interest the letters from readers which appear in your journal, and I would like to say a word in favour of T. A. Lane's request for an ultra-short-wave adapter to receive television sound.

Most of the letters seem to come from short-wave enthusiasts who proudly display their various logs, but I am interested in amplifying equipment. I am also interested in "Class B" amplification. I would like to correspond with another reader interested in these subjects, preferably in the Birmingham district.—**J. PARKER** (40, Shakespeare Street, Stratford-on-Avon).

Sets Using Old Components

SIR.—I think the idea of describing sets to make use of old components a splendid one. We like the actual building of sets, and having many components on hand wish to use these if it can be done without spoiling the set design.

Can you give us such a one using a band-pass arrangement? Selectivity is very bad in this district on the medium band; in fact, sometimes it is impossible to hear the West or North. Wishing you increasing success.—**H. EDGAR PARKER** (Southampton).

Station XGOY, Chungching, China

SIR.—It may be of interest to other readers of "Leaves from a Short-wave Log" to know that on Monday, the 27th ult., I logged the station XGOY, Chungching, China. The announcer informed listeners at 22.00 hours G.M.T. that the station was inaugurated on Sunday the 26th ult., and was working on a carrier-frequency of 9.5 mc/s (31.6 m.). He then gave news of the week of this, the present capital of China, and also said that there would be English news next week at the same time. The transmission was received on a 5v. commercial set, and the signals were QSA5 R9+.

I have been an enthusiastic reader of your paper for some time, and wish it every success in the future.—**ERIC H. WILLIAMS** (Wallasey).

"Audible" Radiations

SIR.—I was very interested in the remarks by B. H., of Nuneaton, about radio reception from an amplifier. I have had the same experience, and found that any attempt to apply coil and/or condenser to the grid for tuning purposes simply lost the signal which came out of the amplifier L.S. These signals were received with A. and E. in the usual connection but no

tuning capacity or inductance whatever. One reader suggests a pick-up as an inductance, but I possess no pick-up, so the reason is to be found elsewhere. One person said the local relay was to blame. I wonder! I agree with D'Arcy Ford who says that the output L.F. of a radio set must be half-wave H.F., and this is what the relays are putting out on their wires.—**A. W.** (Bridlington).

Correspondent Wanted

SIR.—I have been a regular reader of PRACTICAL AND AMATEUR WIRELESS for the past three years, and would like to correspond with any reader living abroad and interested in short-wave reception and transmission.—**D. SHAFSBY** (46, Bath Street, Southport).

A 5-valve Battery S.W. Receiver!

SIR.—In your issue of January 21st, 1939 you invite the opinion of readers on the suggestions of Mr. C. Heyne for a 5-valve battery S.W. receiver. I am in entire agreement as to his suggestion for a PRACTICAL AND AMATEUR WIRELESS powerful S.W. receiver, but why superhet, unless required for some particular frequency? After listening to the "cavernous" (let us call it) reception on the higher frequencies from the latest expensive "all-wave superhet" commercial receivers, it is a relief to the ear to get back to a hefty S.W. "straight" circuit even though it is composed (with the exception of modern valves) entirely from junk.—**C. F. ARMSTRONG** (Kenya, S. Africa).

SIR.—Mr. Heyne's letter published recently in PRACTICAL AND AMATEUR WIRELESS, and your request for opinion on the suggestion offered, encourage me to again ask that consideration be given to publishing a circuit of 6 to 7 valves for operation from a 6-volt battery.

I think, however, an all-wave receiver (9 to 2,000 metres) for broadcast reception would more meet the needs of the majority and would be particularly welcomed in this area.

We are well over 3,000 miles from the B.B.C. and the more important European stations. The set must be sufficiently powerful to give all-day reception of these particular stations.—**C. R. MALONEY** (St. Kitts, B.W.I.).

SIR.—Under the heading, "A Battery S.W. Superhet," I notice that C. H. Williams gives a combination of Mullard valves. I think it would be better, as the suggested circuit is for short waves, to use a Mullard FC2A, instead of FC2, for frequency changer, a Mullard VP2B, instead of VP2, as I.F. and A.F. I think that the I.F. transformers should be very carefully chosen, and would suggest Varley BP95. These have air dielectric trimmers,

which reduce the losses and simplify trimming, and also the coupling between the two windings can be varied. I would like two I.F. stages. I have been a regular reader of PRACTICAL AND AMATEUR WIRELESS for years, and I think your journal gets better and better.—**T. G. MITCHELL** (Maidenhead).

Logged on 20 Metres

SIR.—Listening on the 20 m. band on Tuesday, February 28th, between 6.50 p.m. and 9.45 p.m., I heard the following stations:

KBY, ZS1T, SU1GP, SU1DM, HA8S, K4SAY, HA1P, SU1DF, K4FAY, CT1PM, W2EI, CT1PW, W2EUI, WB1BQ, W1FMP, W1DQ, VQ1AY, W1FMP, W3AEP, W1HRC, W4DHQ, W2KFA.

I picked up these stations on a seven-valve superhet with a 35ft. outdoor vertical aerial.—**VINCENT RICHARDSON** (Andover).

Wind-driven Charging Plant

SIR.—May I complete the triangle with our friends in Kildare—and in Orkney—in asking you to publish an article on wind-driven charging plants. In many out-of-the-way places such plants would be a great boon. From another point of view, in these troublous times, it is almost a matter of national importance, as the dislocation of power plant, broken cables, etc., in an emergency, and perhaps the diversion of power to other purposes would make home-made current invaluable. And dry batteries might not be so easy to get; but with a few accumulators and wet H.T.—and wind cheap—the problem would be solved. As the Government will communicate, nationally speaking, through the B.B.C. network, in an emergency, I think the more we are independent of the Grid System, the less likely we are to be at a loss to maintain communications.—**W. H. STACEY** (Kingsbridge, Devon).

CUT THIS OUT EACH WEEK.

Do you know

—THAT when an external aerial is attached to a frame aerial the directional properties of the latter are lost.

—THAT soft copper wire may be strengthened for wiring purposes by stretching it until it gives.

—THAT wire which has been treated as above should not be used for ultra-short-wave apparatus as the surface is damaged.

—THAT stranded wire for aerial purposes should preferably be enamelled—each separate strand being enamelled before twisting.

—THAT a loose flexible lead to the cap of an H.F. valve can result in erratic tuning effects in a powerful receiver.

—THAT peak or instantaneous values should be considered when calculating the rating of resistors and condensers.

The Editor will be pleased to consider articles of a practical nature suitable for publication in PRACTICAL AND AMATEUR WIRELESS. Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, PRACTICAL AND AMATEUR WIRELESS, George Neumes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in PRACTICAL AND AMATEUR WIRELESS is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Radio Clubs and Societies

Club Reports should not exceed 200 words in length and should be received First Post each Monday morning for publication in the following week's issue.

THE CROYDON RADIO SOCIETY

Headquarters: St. Peter's Hall, Ledbury Road, S. Croydon.

Meetings: Tuesdays at 8 p.m.

Hon. Pub. Sec.: Mr. E. L. Cumbers, 14, Campden Road, S. Croydon.

MEMBERS of the above society met in St. Peter's Hall, S. Croydon, on Tuesday, March 7th, to hear Mr. P. G. Clarke, the chairman, demonstrate his new high-quality apparatus. The vice-chairman, Dr. R. A. Bailey, presided. As was expected, Mr. Clarke had scorned the superheterodyne and used a straight H.F. unit, followed by a resistance coupled amplifier. He described how permeability tuning provided constant selectivity over the whole waveband. Of special interest was his use of a tone-control valve, and he made it quite clear how variation of bass and treble was effected. This valve preceded the main amplifier. The loudspeaker equipment included a large Magnavox 66 unit handling bass notes, with a Piezo electric unit for the upper notes.

Demonstrating the apparatus, Mr. Clarke secured splendid reproduction from both radio and records. He is the proud possessor of a very fine library of records, having one hundred records from which to choose on this occasion. Thanking him, Dr. Bailey said that this lecture should encourage members to persevere in high-quality reproduction, and then come forward to benefit the society with a demonstration. Next Tuesday, March 28th, is the Annual General Meeting for election of officers. The vice-president, Mr. G. S. Vellacott, will preside, and the evening will conclude with a selection of ten-minute talks from members.

THE ILFORD AND DISTRICT RADIO SOCIETY

Hon. Sec.: C. E. Large, 44, Trelawney Road, Barking, Essex.

RECENT activities of this society have included a lecture by Mr. Parr, of Messrs. Ediswan, on Cathode-ray Tubes and the Encephalograph, and a lecture by Dr. F. C. Stephan, of the Telegraph Condenser Co., Ltd., on Electrolytic Condensers. Mr. Haynes, of Haynes Radio (president of the society), also gave a lecture and demonstration on Cathode Gear and Amplifiers, and a junk sale was held at headquarters, the results of which were very gratifying.

Forthcoming programme.—March 30th: Lecture by Messrs. Tungram Electric Lamp Works, Ltd. April 13th: Transmitter demonstration by Mr. E. G. Coe. April 20th: Demonstration by Mr. H. T. Stott, Gramo. evening.

BRENTWOOD AND DISTRICT RADIO SOCIETY

Hon. Sec.: B. A. Pettit (G3VD), "The Laurels," Werrin Road, Sheenfield, Brentwood.

AT a meeting recently, a lecture on Direction Finding was given, a subject of much interest to members who will be taking D.F. seriously in the coming season. Another excellent lecture by R. A. Rothermel and Co., Ltd., on their crystal products, and a lecture by the Ediswan Electrical Co., Ltd., have been recent events. A visit to the Cable and Wireless Transmitting Station at Ongar is an expedition much looked forward to, as also is a practice D.F. field day with the Romford and District Radio Society after Easter, weather permitting. It is intended to hold D.F. tests throughout the summer with the other Essex radio societies as well as individual ones using the society's transmitter G8HV (portable). Attendances at recent meetings have been poor owing to the influenza epidemic, but a revival is anticipated now that it is passing off. Meetings are held at the QRA of G8KM on the first and third Thursday of each month. Inquiries regarding the society should be addressed to the hon. secretary at the above address.

SHEPPEY AMATEUR RADIO CLUB

Headquarters: "Oddfellows Arms," Halfway, Sheerness.

Meeting Nights: Thursdays at 7.30 p.m.

Hon. Sec.: F. G. Maynard (2CVM), 160, Invicta Road, Sheerness, Kent.

THE above club held its usual meeting on Thursday, March 9th, and a very pleasant evening was spent. After the usual meeting formalities had been observed a general discussion took place concerning the new headquarters which had been obtained through the efforts of the chairman (G3GW). The headquarters are more suitable in every respect, and possess all the facilities required for transmitting and receiving, as well as being spacious enough to accommodate an increased membership and for the use of lectures. Application to the authorities has now been made for a "full licence," and the club receiver is nearly completed.

An anonymous gift of 15s. has been received by the chairman from two friends towards the cost of a licence.

which was greatly appreciated by the club. A DX Contest is now running for receiving members on the 3.5 mc/s amateur band, and results will be based upon the best individual DX station received (with verification). Owing to prevailing conditions on that band at the present time, it will be more or less an endurance test for careful listening, as well as efficiency of receiver and antennae. Results will not be known until June 4th, when it is hoped a detailed report can be made.

Information regarding lectures and demonstrations from manufacturers of amateur gear, etc., will be appreciated.

Further particulars of the club can be obtained from the hon. sec., at the address given above.

ROMFORD AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec.: R. C. E. Beardow (G3FT), 3, Geneva Gardens, Chadwell Heath, Essex.

AT our meetings held on February 21st and 28th lectures were given by Mr. Townsend, of the Hivac Valve Co., and Mr. Betteridge, of The Marconi-Phone Company, on the construction and uses of Cathode-ray Tubes. Our last meeting was devoted to the demonstration of an Evrizon amateur receiver owned and operated by G3CQ. A surprising amount of DX was heard under trying conditions, and we shall be looking forward to a demonstration of their latest model, which will be demonstrated by G3CQ on behalf of that firm.

THE EAST SURREY SHORT-WAVE CLUB

Meetings: Alternate Thursdays at 8 p.m.

Hon. Sec.: Leslie Knight (G5LK), 13a, Hatchlands Road, Redhill, Surrey.

ON February 16th Mr. Basil Wardman (G5GQ) gave an interesting talk on transmitter design, which proved to be very popular, as the club consists mainly of transmitters and A.A. licence-holders.

On the evening of March 2nd the club's receiver was installed, but owing to difficulty in erecting a good aerial reception was poor and members were not very successful when trying to tune in the amateur band. On the same evening G6JF introduced VU2AE from India, who is staying in this country for a short while.

The first year's balance sheet has been prepared and presented to members showing a balance in hand of over £7. The first annual dinner will be held at the "Old Wheel," Reigate, on April 13th; assemble 7.30 p.m. Dinner 8 p.m. All local enthusiasts are welcome.

SLOUGH AND DISTRICT SHORT-WAVE CLUB

Headquarters: 35, High Street, Slough, Bucks.

Meetings: Alternate Thursdays at 7.30 p.m.

Hon. Sec.: Mr. R. J. Sly, 16, Buckland Avenue, Slough, Bucks.

AT the last meeting held at headquarters on March 2nd, the club was honoured by a visit from VP6AH, who gave a very interesting talk on the difficulties of the amateur in Barbados. A very interesting time was had by members in constructing the club receiver.

The agenda for the next meeting includes a talk on microphones and amplifiers by G8XH, as well as further work on the club receiver, and the usual Morse practice.

THE MEDWAY AMATEUR TRANSMITTERS SOCIETY

Headquarters: The Navy Wives' Club Hall, Dock Road, Chatham.

Meetings: Every Tuesday at 8.15 p.m.

Hon. Assistant Sec.: R. Nicholson, 8, Pine Road, Strood, Rochester, Kent.

AT the meeting held on February 14th Mr. J. E. Bryden (2BOL) gave an interesting talk on television equipment and displayed for inspection a very fine sound and vision receiver of his own design and construction.

The president (G6NU) has commenced a series of informal technical discussions of an elementary nature for the benefit of those new members who are newcomers to amateur radio, and these are proving very popular.

Arrangements for the forthcoming Radio and Television Exhibition, which the society is organising, are well in hand, and technical details of the necessary equipment for demonstrating several television receivers, etc., are receiving the attention of the members detailed for this work.

On March 28th, Messrs. British Television Supplies, Ltd., are giving a demonstration and talk on their popular "Trophy" receivers, and 2BOL will continue his television series on April 11th. Alternate meetings

are devoted to Morse code practice and informal technical discussions.

Readers of PRACTICAL AND AMATEUR WIRELESS are especially invited to meet the local hams on Tuesday evenings at 8.15 p.m. To reach the M.A.T.S. room at the Navy Wives' Club Hall, enter by the main door, and inquire of the caretaker at the buffet, who will be pleased to point out the way.

HODDESDON AND DISTRICT RADIO SOCIETY

Headquarters: Blairgowrie, Station Road, Broxbourne, Herts.

Hon. Sec. and Treasurer: T. Knight, Jr., Caxton House, High Street, Hoddesdon, Herts.

THE society operates under call G5HO, and has a permit to operate on the 1.7, 7, 14, 28, and 56 mc/s bands as a fixed and a portable station. Gear consists of a loose-coupled Hartley plate modulator, and an M.O./P.A. with relay break-in and voice-controlled break-in (not yet working) for 100 metres. A C.O./E.D./P.A. (RFP15) for 20m. and 40m. A 56mc/s TX was built some years ago before any really suitable valves were available and then shelved in favour of 1.7 mc/s, but it is now being reconstructed, together with two receivers. A new communications receiver for the amateur bands is nearing completion.

Aerials in use are a 132ft. Marconi for 160 metres, a 40-m. doublet, and an 8JK for 20 metres.

Meetings are held every second and fourth Wednesday of each month, from 8 to 10 p.m. We have at present four members with A.A. licences, two of whom have passed the G.P.O. test.

ASHTON-UNDER-LYNE AND DISTRICT AMATEUR RADIO SOCIETY

Headquarters: Commercial Hotel, 86, Old Street, Ashton-under-Lyne.

Secretary: K. Gooding (G3PM), 7, Broadbent Avenue, Ashton-under-Lyne.

AT a meeting held on March 8th, the date of the "Hamfest" was definitely fixed for April 2nd next. An entertaining programme is being compiled, and it is hoped that all local amateurs (including non-members of the society) will give the event their full support.

The society also held their first "junk sale," and as it proved a huge success it was decided to repeat the event at future meetings.

A letter was read by the secretary from the Derby Short-Wave Society, and it was resolved to co-operate with this society on field days. On the suggestion of Mr. W. P. Green a "panel" of listening stations is being drawn up in order to provide a practically full-time listening service in connection with organised tests.

PAISLEY SHORT-WAVE CLUB

Headquarters: 2, Park Road.

Meetings: Mondays at 7.30 p.m.

Hon. Sec.: Mr. James M. Arthur, 9, East Buchanan Street.

THE above club paid a visit to the Glasgow Police Radio station on February 23rd. The system was explained in detail with the aid of maps. The Teletype rooms were visited, and messages were watched being typed out, and these, it was explained, were received simultaneously in five different districts. The answers could be seen typing themselves out. The garage also was visited, where patrol cars were inspected with great interest.

Application for a transmitting licence has been made for the club under the name of Mr. Peter P. Brown.

Wednesday nights are devoted to Morse practice. Saturday nights are quite popular, being informal nights.

Membership has been steadily increasing, and now stands at about 40. The entry fee is 2s., and weekly subscriptions 6d., junior members 3d. per week. Members have their own key, and have access to the club at all times. Anyone interested will be welcomed on Monday evenings.

BRADFORD SHORT-WAVE CLUB

Hon. Sec.: G. Walker, 33, Napier Road, Thornbury, Bradford, Yorks.

ON Sunday, March 5th, another trip was taken by the members of the above club along the channels of the 1.7 mc/s band, and a call was made at one or two local stations, the farthest call was G6PY, at Barnsley. It has been decided, after one or two reports that have been received by the secretary, to rebuild the station, and this work will be in progress by the time this report goes to press.

The last lecture in the winter syllabus will be given by Mr. Beaumont, of Ambassador Radio Co., Brighouse, and his subject will be "Short-wave Receiver Design." Further information of the club's activities, summer syllabus, etc., can be obtained from the secretary.

THE MERSEY-SIDE AMATEUR TRANSMITTING SOCIETY

Secretary: C. E. Cunliffe, 368, Stanley Road, Bootle, Liverpool, 20.

LAST month the above society had quite a full programme, including a lecture on all types of crystal oscillators, followed by a practical demonstration. On discussion night we cleared up many points regarding members' radio queries. We now have three more call-signs: 2BMB (Mr. Mooney) and G6PM. Mr. H. Forster is now 2FZK, while several of the A.A. members have applied for full permits. We are all looking forward to one or two field days this year, weather permitting.

If any persons, novice or expert, would care to join the society, please write to the secretary at the above address.



Impressions on the Wax

A REVIEW OF THE LATEST GRAMOPHONE RECORDS

THERE are some very attractive light orchestral records in this month's releases. The London Palladium orchestra, under Clifford Greenwood, plays a selection of Sousa Marches and "March of the Bowman" from the conductor's "Robin Hood" suite—*H.M.V. C 3079*.

Barnabas Von Geczy, one of the most famous of Continental light orchestra leaders, takes the "Lambeth Walk" and "The Donkey Serenade" and makes a fine job of them on *H.M.V. B 8871*.

Louis Levy's Orchestra gives a melodious selection of the best tunes in the latest Macdonald-Eddy film, "Sweethearts," on *H.M.V. BD 668*. His trick of giving some of the violins a sort of roving commission above the "top line" is quite fascinating. Anton and the Paramount Orchestra, with Al Bollington at the organ, give charming renderings of Elgar's morceau "Salut d'Amour" and Drdla's "Serenade"—*H.M.V. BD 660*.

Apart from the music they play, Alan Helm's Accordion Orchestra has other points of novelty. Its 120 members are all employees of Hohner's Concessionaires, who make the instruments on which they play, and the accordions themselves range in size from the midget to the mammoth. They play a piece specially written for them by G. S. Mathis, who conducts—a short symphonic poem, "Spring"—*H.M.V. BD 664*.

Vocal

IT is surprising that Meliza Korjus, who is such ideal material for the films, has not been seized upon and "starred" before. Her first film, "The Great Waltz," is a vehicle for the tunes of Johann Strauss in their most elaborate arrangements.

Meliza Korjus gives some amazing examples of vocal acrobatics, or, as the musicians say, coloratura singing, and these records were made direct from the sound track of the actual film. They include "Tales from the Vienna Woods"—*H.M.V. B 8862*, "One Day When we Were Young" and "There Will Come a Time"—*H.M.V. B 8863*.

Cicely Courtneidge and Jack Hulbert sing the duet "Together Again" from their sensational new show "Under Your Hat." The other side of the record carries "If You Want to Dance," by Jack Hulbert and the Rhythm Brothers, on *H.M.V. B 8864*.

For years Peter Dawson has been regarded as the ideal exponent of the hearty and forthright ballad. Of late he has shown his more serious yet equally attractive side, and these two fine examples of the English art song have figured with great success in his recent programmes. They are Elgar's "Speak, Music" and "Raun of Exile," by Bax, on *H.M.V. B 8866*.

Arthur Askey, radio's No. 1 comedian, is delightful in two of his latest absurdities, "The Cuckoo" and "All to Specification"—*H.M.V. BD 656*.

Swing Music

PROMINENT among the new records of swing music is the first *H.M.V.* record by Arrie Shaw and his Orchestra. In the space of only one year Shaw has risen out of nowhere to take his place as America's most popular swing band. As a clarinettist he is as at home in the classics as he is in jazz. He is also an arranger and composer for his own orchestra.

On one side of *H.M.V. B 8869* you will hear his own arrangement of the famous "Indian Love Call" from "Rose Marie." Shaw agrees that the tune is lovely—too lovely to suffer from an occasional bit of fun such as this. So he deliberately pokes fun at the modern "swing" style of jazzing up the classics and light classics. By emphasising all the bad points in modern jazz—the introduction is nearly half the record, the men in the band sing "Cheep Cheep" for no reason at all behind the vocal; in fact, Shaw has produced a classic of better jazz phrasing. On the reverse of this record is his theme song, "Nightmare," which he composed himself.

One of the most popular of recent record issues was an actual recording of Max Miller's complete turn as it was snapped at the Holborn Empire.

It was so successful, in fact, that in response to the amazing public enthusiasm, *H.M.V.* have had to go back to the Holborn to make yet another set of records by the "Cheekie Chappie." Apart from his signature tune at the beginning and end, this turn is completely different from the first one recorded. Fresh songs—three complete sides of patter. *H.M.V. BD 646-8*.

Decca

AMBROSE and his Orchestra have two new records this month featuring four of the most popular tunes of the moment. "I Miss You in the Morning" is on one side of *Decca F 6965*, whilst on the reverse is "If Ever a Heart was in the Right Place"; and the other record, *Decca F 6966*, contains "I Shall Always Remember you Smiling" and "Grandma Said." The last tune looks like being a "hit."


"Romany" and "There's Something About an Old Love" on *Decca F 6972* suit Vera Lynn perfectly. This artist is one of the "stars" of the famous Ambrose Octet.

Bob Crosby and his colleagues, with Marion Mann as vocalist, proffer first-class records. *Decca F 6968* is a good example of the right presentation of two excellent numbers—"What Have You Got that Gets Me?" and "You're Lovely, Madame."

"The Palais Stroll" has "caught on," as it were, and here on *Decca F 6959* Josephine Bradley presents it in strict tempo so that the ardent dancer can dance it in comfort. The coupling is a slow fox-trot, "My Own," from the film "That Certain Age."

Charlie Kunz makes yet another piano medley on *Decca F 6971*. As usual this medley contains the best of to-day's tunes.

MORE FINE BARGAINS

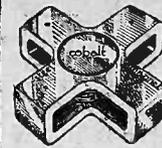

5/- Powerful New Steel Moving-Coil SPEAKER-MAGNETS.

Four-claw 4 1/2 lbs. 10 watt M.C. Speaker Permanent Magnets at manufacturer's price. A great opportunity for

CONDENSERS. Fixed electrolytic 12 + 4 mfd. = 16 mfd. 275 volts 1/6; 6 + 6 = 12 mfd. 250 volts, 1/6; 8 + 8 = 16 mfd. 350 volts 1/6; 24 + 8 = 32 mfd. 400 volts, 2/6; 8 mfd. 500 volts, 1/6; Mansbridge Paper and Mica, 4 mfd., 3/6; 8 mfd., 5/6; 10 mfd., 7/-; Dubilier .01 for 1,000 volts, 1/8; .005 Mica Trans. 5,000 volts, 2/6; 10,000 volts, 5/-; .25 mfd. mica, 4,000 volts, 6/-; Oil Condensers, 1 mfd. 3,000 volts, 5/6. Special Condenser Bargain to clear surplus. Western Electric 1 mfd. & 2 mfd., 2d. each, 1/6 doz; 12/- gross, carriage forward. Ideal for makers of smoothing and filter circuits. Offer open till cleared.

BLUE BOTTLES. Glass enclosed, and 1 watt Resistors, .01, .025, .05, .1, 1/2 and 1 meg., List 1/-; Sale 1/- per doz., any of these sizes, 3/- per gross.

COIL WINDERS. Hand drive, level friction, 8" high, 2/6.
COILS. S.W. plug-in, 1/8. Ribbed formers, 9d. Long wave and B.C. 2-pin, 1/-. Reaction tuners, 9d. H.F. twin chokes, mains, 9d. Rugby and other coils in stock. All wavelengths in 2-pin, 1/3. S/W. Formers ribbed and slotted, 4d.

PANELS. Aluminium 16- and 18-gauge one side enamelled. Paxolin and Ebonite, any size, from 2 1/4in. x 2 1/4in. at low prices.

VARIABLE CONDENSERS. .005 mfd. Tokade, 1/3; .00075 Polar Compax, 1/-; S/W. Formo 2 1/2; J.B. Midget, .0001, 1/6; 2-gang variable, .0005, 2/6; 3-gang, 3/6.

PROJECTION LANTERNS, on Stand, with 250-watt focus bulb 25/-; Arc lamps, Slide lanterns, Film projectors, and Sound heads, cheap.

MAGNETIC SOUND RECORDING. Stille Steel Tape, 9d. yd.

EARTH SPIKES. Massive R.A.F. earth spikes, with terminal for Aerials and Telephone lines, 1/- or 9/- doz.

MOTOR BARGAINS in Midget H.P. Motors for A.C. or D.C. 200/230 volts, 110th H.P. D.O.T. type, totally enclosed KB Cover, 2,000 revs., at a price never before offered, 7/6 only. Next larger G.M. No. 2 type, high speed 1/60 H.P., 4,000 revs. 9/6. Larger still, 1/4th H.P., Model G.E. No. 1, 12/6. All as new and first rate for model drive or light duty.

MORSE RECORDING OF WIRELESS SIGNALS. These well-known service paper tape Inkers record messages on any wavelength at speed. Recorders add enormously to interest. Magnificent British work, mahogany drawer containing tape reel. Such apparatus cost 240/- 22 to 26 10s. each.

ELECTRIC SOLDERING IRONS. Heavy workshop type, 125 watts.

220/230 volts, 2/6. Big 220v. Alarm Bells, 10" gong, 3/6.

220 VOLT FOOTWARMER. Electric Mats, covered fabric, 7/6.

Bed-warmer Blanket Pads, 220 volts, 12/6, 110 volts, 10/6.

3-VALVE (part finished) BATTERY SETS with oak cabinet ready wired and fitted 2 condensers and engraved panel, 13 x 7 x 6in., 15/-.

PUSH BUTTON TUNING. 6-way Gang Push, metal cover, 1/6.

Multiple Cord, 6d.

STATIC CONVERTERS. A.C. mains to D.C. 40 watts output, steel cased. Output 440 volts, 60/100 m.a. D.C. with valves, 45/-; A.C. mains to D.C. 120 watts at 1/2 amp. for 220 v. D.C. sets, steel-cased, valves, 50/-.

SOUND RECORDING AT HOME at a reasonable cost. No fancy prices for elaborate gear. The Feich records on any discs.

The FEICH RECORDER fits any Gramo., has positive drive by ball-bearing worm gear and rack. The Recording Stylus is tracked across blank at the exact grooving spiral. Price complete, as illus. with Tone Arm and cutter with real diamond, 37/6. All-Metal discs, 3/3 doz.

Latest Bargain List "N" Free on Request.

ELECTRADIX RADIOS

218, UPPER THAMES ST., LONDON, E.C.4

Telephone: Central 4611



Latest Bargain List "N" Free on Request.

ELECTRADIX RADIOS

218, UPPER THAMES ST., LONDON, E.C.4

Telephone: Central 4611

ENGINEERING OPPORTUNITIES

Free!

268 PAGES

This unique Handbook shows the easy way to secure

A.M.I.C.E.,
A.M.I.Mech.E., A.M.I.E.E.,
A.M.I.A.E., A.M.I.W.T.,
A.M.I.R.E., and similar qualifications.

WE GUARANTEE—NO PASS—NO FEE. Details are given of over 150 Diploma Courses in all branches of Civil, Mech., Elec., Motor, Aero, Radio and Television Engineering, Building, Government Employment, etc. Write for this enlightening Handbook to-day **FREE** and post free.

British Institute of Engineering Technology,
409, Shakespeare House, 17, 18, 19, Stratford Pl., W.1

THE FINEST CHASSIS VALUE OBTAINABLE ARMSTRONG RADIOGRAM CHASSIS

COMPLETE WITH SPEAKER
MODEL 3 NBE/T. 7-Valve ALL-WAVE Radiogram Chassis, complete with 8in. Matched M.C. Speaker, Cathode Indicator. Short Waves from 15.9 to 50 m.

CASH PRICE £7.18.8 or **12/6** WITH ORDER and 12 monthly payments of 13/4.

WRITE FOR LIST OF ALL MODELS.

THE LONDON RADIO SUPPLY CO. (Est. 1925),
11, OAT LANE, NOBLE STREET, LONDON, E.C.2.

LATEST PATENT NEWS

Group Abridgments can be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, either sheet by sheet as issued on payment of a subscription of 5s. per Group Volume or in bound volumes, price 2s. each.

CATHODE-RAY TUBES.—Baird Television, Ltd., Szegho, C., and Tomes, G. A. R. No. 496,778.

In a cathode-ray tube of the kind having a luminescent, the screen is arranged so that light from the side which is scanned by the cathode ray may be projected or viewed through a substantially plane part of the envelope without interception by any electrode. As shown, the luminescent screen which may be translucent or transparent is formed on the plane back wall of the tube which may be provided with a reflecting backing 4 (Fig. 1) of silver, etc. The image passes through the front 5 of the tube which is plane and may be parallel to the screen. The gun 2 is displaced to the side of the tube. Specification 469,420 is referred to.

TELEVISION RECEIVERS.—General Electric Co., Ltd., and Jesty, L. C. No. 496,835.

The optical distance of an image of the reproduced picture from the screen 2 (Fig. 2), on which the picture is formed, is so varied in dependence on the optical distance of the sheet 5, which is viewed, from the screen that the image is formed on the sheet in every position of the sheet in which it can be viewed. The sheet can be viewed either in the horizontal 5B or the vertical position 5A. The screen 2 is horizontal and a mirror 7, which is in-

clined at 45° to the horizontal, enables the sheet in the horizontal position to be viewed horizontally and, when the sheet is vertical, deflects the optical axis through a right-angle. According to a modification, the sheet has two vertical positions and two alternatively operative mirrors deflect the optical axis through a right-angle.

TELEVISION.—Scophony, Ltd., and Jeffrey, J. H. No. 496,964.

An optical system 14..20 (Fig. 3) forms on a receiving-screen 5 a cylindrical image, with definition in the direction of scanning, of modulated supersonic waves in a cell 2, and also forms a cylindrical image of the illuminated surface of a high-speed scanner 3 on the screen with definition at right-angles to the direction of the scanning-lines. An intermediate cylindrical image of an illuminated aperture 1 is formed in the cell, and a cylindrical image of the intermediate image is formed on the surface of the high-speed scanner. The direction of definition of both these images is at right-angles to the direction of movement of the supersonic waves.

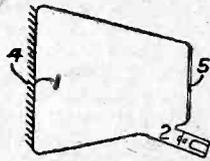


Fig. 1.

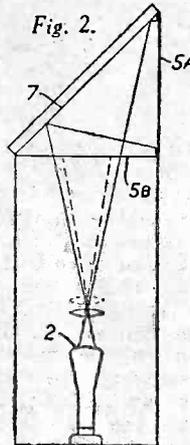


Fig. 2.

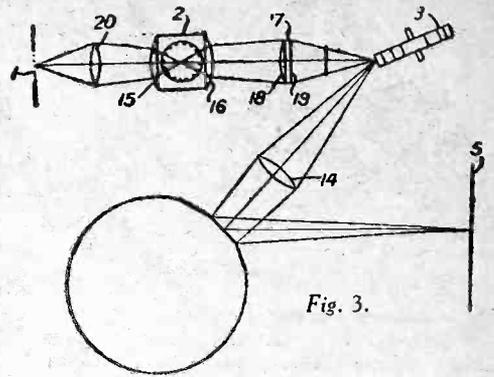


Fig. 3.

According to a modification, the intermediate image is omitted. Specifications 439,236 and 451,132 are referred to.

TELEVISION FACTS AND FIGURES

WITH the idea of securing some concrete information concerning the present television service, the Postmaster-General was asked the following question in the House of Commons the other day: What is the present approximate number of licences in force in respect of television receivers; what is the approximate annual revenue therefrom; what has been the annual cost of the television service since its introduction, and who has borne the difference between this cost and the revenue? There is no doubt that the main idea behind this question was to ascertain some figure which could be said to represent authoritatively the number of sets sold for viewing purposes, but due to the way it was worded the P.M.G.'s assistant was able to be quite non-committal on this point. In his reply he stated what all readers of this journal know—namely that the reception of television is at present covered by the ordinary wireless receiving licence and that no special television licence is necessary. It seems certain, however, that later on a further effort will be made to obtain a figure which can represent the number of television sets sold so far by manufacturers, although it is generally accepted that this has now passed the five-figure mark and is rising rapidly. On the question of cost it is interesting to note that the amounts given by the B.B.C. for the annual revenue costs of the television service, together with depreciation on capital expenditure were: £111,500 in 1936, £277,149 in 1937, and £352,846 in 1938. This rising cost in expenditure was met by the Government returning to the B.B.C. a larger proportion of the licence revenue than had been done in the past. It emphasised that the ordinary listener is not being made to suffer on account of television, but merely that the Government is withholding less of the licence revenue than it has previously, an action which it is unlikely would have occurred but for the incidence of the television service.

NEW PATENTS

These particulars of New Patents of interest to readers have been selected from the Official Journal of Patents and are published by permission of the Controller of H.M. Stationery Office and the Official Journal of Patents can be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1s. weekly (annual subscription £2 10s.).

Latest Patent Application.

- 6189.—Baird Television, Ltd., and Baird, J. L.—Colour television systems. February 24.
- 6673.—Baird Television, Ltd., and Tomes, G. A. R.—Television, etc., systems, etc. March 1.
- 5974.—Duckworth, S.—Short wave wireless receiving sets. February 23.
- 6067.—Fokerd, A. R.—Method, etc., for the remote control of wireless receivers. February 23.
- 6265.—General Electric Co., Ltd., and Clark, F.—Mounting devices for radio apparatus. February 25.
- 6701.—General Electric Co., Ltd., and Jones, F. R.—Tuning devices for wireless receivers. March 1.
- 6030.—I. M. K. Syndicate, Ltd., Nagy, P., and Goddard, M. J.—Light-modulating devices for use in television receivers. February 23.
- 6123.—Kallmann, H. E.—Television transmitting, etc., systems. February 24.
- 6240.—Monge, G. de.—Elimination, etc., of disturbing noises in the reception of radio transmissions. February 24.
- 6045.—Murphy Radio, Ltd., and Hawkins, G. F.—Television receivers. February 23.
- 6408.—Philco Radio and Television Corporation.—Remote control for radio receivers, etc. February 27.

Specifications Published.

- 501,042.—Radio Corporation of America.—Sound-recording.
- 501,043.—Radio Corporation of America.—Sound-recording.
- 501,051.—Telefunken Ges. Fur Drahtlose Telegraphie.—Aerial systems for radio receivers.
- 501,410.—Milnes, H. R., and Milnes Radio Co., Ltd.—Thermal generation of electric current.
- 501,411.—Milnes, H. R., and Milnes Radio Co., Ltd.—Apparatus for thermal generation of electric current.
- 501,348.—Marconi's Wireless Telegraph Co., Ltd., and Norwood, H. C.—Adjustment mechanisms for tuning condensers in radio receivers and for like purposes.
- 501,352.—Kolster-Brandes, Ltd., and Smith, K. G.—Padding condensers for superheterodyne radio receivers.
- 501,370.—Mitchell, F. A.—Tuning devices for radio receivers.
- 501,152.—General Electric Co., Ltd., and Brittain, F. H.—Loudspeakers.
- 501,375.—Standard Telephones and Cables, Ltd.—Television transmission tubes.
- 501,179.—Standard Telephones and Cables, Ltd.—Cathode-ray device.
- 501,251.—Telefunken Ges. Fur Drahtlose Telegraphie.—Direction finding radio receivers.
- 501,254.—Marconi's Wireless Telegraph Co., Ltd.—Modulated carrier-wave receivers.

Printed copies of the full Published Specifications may be obtained from the Patent Office, 25, Southampton Buildings, London, W.C.2, at the uniform price of 1s. each.

PRACTICAL WIRELESS SERVICE MANUAL

By F. J. CAMM.

From all Booksellers 5/- net, or by post 5/6 direct from the Publishers, George Newnes, Ltd. (Book Dept.), Tower House, Southampton Street, London, W.G.2.



QUERIES and ENQUIRIES

Microphone Transformer

"As a result of the information I have got out of your paper I have now succeeded in getting my A.A. Licence. I have built the 2½-watt transmitter but am in difficulty with regard to the microphone. Speech is in "the background," and I wonder if the connections to my transformer are correct. This is a Bulgin microphone transformer with five coloured leads and I should like to know the connections for this."—D. S. (Old Holpatrick).

THE secondary of the transformer in question has the leads coloured red and green, the latter being joined to the grid. The primary has blue ends with the centre-tap yellow. For a standard microphone you need a high step-up and therefore should use half of the primary, which will give you approximately 70 to 1 ratio. Therefore, join your microphone and battery in series across the yellow and one blue lead.

Electrolytic Condenser Connection

"I had a little difficulty in my set with an electrolytic condenser breaking down, and I saw by the case that this was two 8 mfd. units in one case. I have bought a new one and connected this up but am doubtful as to the suitability as a friend who has seen it has told me it is joined backwards. I am sending a sketch of the set and the condenser and should be glad to know whether he is right."—J. E. D. (N.W.5.)

IN the circuit you send the two electrolytic condensers are joined on either side of the smoothing choke, with a common negative lead to earth. The component you have obtained, however, has a common positive connection and thus you have joined the two condensers the wrong way round in the circuit. You will note from the marking on the condenser case that correct polarity must be observed and therefore should order an 8—8 mfd. unit, not an 8+8 unit.

Blue Glow

"I noticed something a little strange about a new American valve I purchased the other day to replace a valve in an amplifier. While a record was being played through a kind of purple band of light at the top of the valve, which appears directly the amplifier is switched on, darts and jumps about with every beat of the music, or loud passages on the record. I haven't seen one like it before and I am curious—so should be glad if you could explain it."—F. C. (Chiswick, W.4).

WHEN a standard type of valve is over-run—either by supplying too much H.T. or too little G.B., what is known as "blue glow" takes place and residual gas in the bulb glows with the characteristic colour you mention. The electronic flow in the bulb sets the gas in motion and thus causes the glow to dance or keep time with the current fluctuations. The remedy is to reduce H.T. or apply correct bias, although if this is in order, and the valve

still glows it may indicate a faulty valve. Certain modern output valves are purposely provided with a gas content and may glow slightly, but it should not be of large proportions.

H.F. Pentode Connections

"In an article I read some time ago it stated that the H.F. pentode was obsolete. Do you mean the one to be used was 4-pin in S.W. modification, or was there a 5-pin H.F. pentode with no cap at one time—the top cap being taken to a pin on the base making it a 5-pin base? Mr. Camm specifies a 4-pin H.F. pentode in the Acme

RULES

We wish to draw the reader's attention to the fact that the Queries Service is intended only for the solution of problems or difficulties arising from the construction of receivers described in our pages; from articles appearing in our pages, or on general wireless matters. We regret that we cannot, for obvious reasons—

- (1) Supply circuit diagrams of complete multi-valve receivers.
- (2) Suggest alterations or modifications of receivers described in our contemporaries.
- (3) Suggest alterations or modifications to commercial receivers.
- (4) Answer queries over the telephone.
- (5) Grant interviews to querists.

A stamped addressed envelope must be enclosed for the reply. All sketches and drawings which are sent to us should bear the name and address of the sender.

Requests for Blueprints must not be enclosed with queries as they are dealt with by a separate department.

Send your queries to the Editor, PRACTICAL AND AMATEUR WIRELESS, George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. The Coupon must be enclosed with every query.

receiver, and therefore it cannot be obsolete, so I should be glad if you could explain this."—W. I. (Hull).

THE H.F. pentode battery valve is available with either a 4-pin or a 7-pin base, and both types are standard and current. The 7-pin valve has the advantage that the metallising may be separately earthed when desired but in all other respects it is identical. In some cases the suppressor grid may be joined to one of the pins but this is not standardised.

Old-pattern Coil

"I am thinking of making an all-wave receiver incorporating an all-wave coil which I have. This is of the panel-mounting type and there are five coloured leads—black, red, blue, white and green. Could you tell me their actual meaning and a suitable condenser for reaction and tuning?"—A. J. K. (Bow, E.3).

FROM your description we think we recognise the component as an all-wave oscillator coil designed by Lewcos. This was intended for a superhet circuit using an I.F. of 126 kc/s and thus would not be suitable for a simple receiver, and I.F. transformers are not now easily obtainable for this frequency. Furthermore, coils (oscillator) for this frequency and superhet condensers of the same type are also now out of date and therefore we think you will find it difficult to make use of this particular component.

Transverse Current Microphone

"Would you please explain what is a transverse current microphone; the method

of connecting to a receiver for home broadcast; method of connecting to a transmitting set? Is this type of microphone superior to the post office ex-telephone type largely on sale at the present time?"—A. S. (New Malden).

IN the type of microphone referred to there are two fixed carbon electrodes, the intervening space being filled with carbon granules. The diaphragm rests against these granules and thus varies the conductivity of the path between the electrodes. It may be treated in all other respects in exactly the same manner as a standard carbon mike, using a step-up transformer for matching purposes. The advantage over the type of microphone mentioned is one of quality and the sensitivity is probably not so high as the standard carbon instrument. If you intend to use the mike for transmitting purposes the transverse current instrument is definitely preferable to the simple alternative type mentioned by you.

Push-pull and Recording

"I recently built your 2½-watt amplifier. Seeing that its output is push-pull and as I wish to do some home-recording, I should like to know how I connect the pick-up to the same."—V. H. P. (Brighton).

THE method adopted for connecting a pick-up for recording purposes in a push-pull stage is exactly the same as that employed for connecting an extension speaker. A centre-tapped choke must be joined to the output terminals, the centre tapping being joined to H.T. positive. A 2 mfd. fixed condenser should then be connected to each anode and the pick-up joined to the other terminals on the two condensers. This is, in effect, an output filter circuit with the exception that two condensers are used.

Signal Strength for Recording

"I have purchased a home-recording apparatus and I am using as a cutting head an ordinary H.M.V. reproducing pick-up. This makes a perfect spiral, but without the sound waves. Do I need a special recording head?"—E. D. (Eberston).

YOUR trouble is probably due to the fact that you are not feeding a sufficiently strong signal into the pick-up to obtain a good cut on the record. You should also use a proper cutting needle with sapphire or diamond point. You can use an ordinary playing needle (steel) provided that has been used to play one or two surfaces first, but the sapphire gives best results.

Crystal Set Results

"I have constructed a crystal set which gets the London Regional very clearly, but however much coil I put in the circuit I cannot get any other stations. Can you assist me in this difficulty?"—F. M. (Rickmansworth).

WE note that you live very close to the London transmitter, and in view of the poor selectivity of the average crystal receiver you are probably unable to reduce the spread of the station in order to hear other stations. We therefore suggest that you choose a time when London Regional is not transmitting and then make a careful search on the dial, when you will be able to ascertain whether or not any stations are within range with your particular aerial system.

The coupon on page iii of cover must be attached to every query.

Practical and Amateur Wireless BLUEPRINT SERVICE

These Blueprints are drawn full size. Copies of appropriate issues containing descriptions of these sets can in some cases be supplied at the following prices, which are additional to the cost of the Blueprint. A dash before the Blueprint Number indicates that the issue is out of print.

Issues of Practical Wireless .. 4d. Post Paid.
Amateur Wireless .. 4d. " "
Practical Mechanics .. 7d. " "
Wireless Magazine .. 1/3 " "

The index letters which precede the Blueprint Number indicate the periodical in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, P.M. to Practical Mechanics, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint and the issue (stamps over 6d. unacceptable) to PRACTICAL AND AMATEUR WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

PRACTICAL WIRELESS No. of Date of Issue. Blueprint

CRYSTAL SETS.		
Blueprints, 6d. each.		
1937 Crystal Receiver	PW71	
The "Junior" Crystal Set	PW94	27.8.38
STRAIGHT SETS. Battery Operated.		
One-Valve : Blueprints, 1s. each.		
All-wave Unipen (Pentode)	PW31A	
Beginner's One-valver	PW85	19.2.38
The "Pyramid" One-valver (HF Pen)	PW93	27.8.38
Two-valve : Blueprints, 1s. each.		
Four-range Super Mag Two (D, Pen)	PW36B	
The Signet Two (D & LF)	PW76	24.9.38
Three-valve : Blueprints, 1s. each.		
The Long-range Express Three (SG, D, Pen)	PW2	24.4.37
Selectone Battery Three (D, 2 LF Trans)	PW10	
Sixty Shilling Three (D, 2 LF RC & Trans)	PW34A	
Leader Three (SG, D, Pow)	PW35	22.5.37
Summit Three (HF Pen, D, Pen)	PW37	
All Pentode Three (HF Pen, D Pen, Pen)	PW39	29.5.37
Hall-mark Three (SG, D, Pow)	PW41	12.6.37
Hall-mark Cadet (D, LF, Pen, RC)	PW48	16.3.35
F. J. Camm's Silver Souvenir (HF Pen, D Pen, Pen) (All-wave Three)	PW40	13.4.35
Genet Midget (D, 2 LF Trans)	PM1	June '35
Cameo Midget Three (D, 2 LF Trans)	PW51	8.6.35
1936 Sonotone Three-Four (HF Pen, HF Pen, Westector, Pen)	PW53	
Battery All-Wave Three (D, 2 LF RC)	PW55	
The Monitor (HF Pen, D, Pen)	PW61	
The Tutor Three (HF Pen, D, Pen)	PW62	21.3.36
The Centaur Three (SG, D, P)	PW64	14.8.37
F. J. Camm's Record All-Wave Three (HF Pen, D, Pen)	PW69	31.10.36
The "Colt" All-Wave Three (D 2 LF RC & Trans)	PW72	18.2.39
The "Rapide" Straight 3 (D, 2 LF RC & Trans)	PW82	4.12.37
F. J. Camm's Oracle All-Wave Three (HF, Det, Pen)	PW78	28.8.37
1938 "Triband" All-Wave Three (HF Pen, D, Pen)	PW84	22.1.38
F. J. Camm's "Sprite" Three (HF Pen, D, Tet)	PW87	26.3.38
The "Hurricane" All-Wave Three (SG, D Pen, Pen)	PW89	30.4.38
F. J. Camm's "Push-Button" Three (HF, Pen, D Pen, Tet)	PW92	3.9.38
Four-valve : Blueprints, 1s. each.		
Sonotone Four (SG, D, LF, P)	PW4	1.5.37
Fury Four (2 SG, D, Pen)	PW11	8.5.37
Beta Universal Four (SG, D, LF, Cl B)	PW17	
Nucleon Class B Four (SG, D, SG, LF, Cl B)	PW34B	6.1.34
Fury Four Super (SG, SG, D, Pen)	PW34C	
Battery Hall-Mark 4 (HF Pen, D, Push-Pull)	PW46	
F. J. Camm's "Limit" All-Wave Four (HF Pen, D, LF, P)	PW67	26.9.36
All-Wave "Corona" 4 (HF Pen, D, LF, Pow)	PW79	9.10.37
"Acme" All-Wave 4 (HF Pen, D Pen, LF, Cl B)	PW83	12.2.38
The "Admiral" Four (HF Pen, HF Pen, D, Pen RC)	PW90	3.9.38
Mains Operated.		
Two-valve : Blueprints, 1s. each.		
A.C. Twin (D Pen, Pen)	PW18	
A.C. D.C. Two (SG, Pow)	PW31	
Selectone A.C. Radiogram Two (D, Pow)	PW19	
Three-valve : Blueprints, 1s. each.		
Double-Diode-Triode Three (HF Pen, DDT, Pen)	PW23	
D.C. Ace (SG, D, Pen)	PW25	
A.C. Three (SG, D, Pen)	PW29	
A.C. Leader (HF Pen, D, Pow)	PW35C	
D.C. Premier (HF Pen, D, Pen)	PW35B	31.3.34
Ubique (HF Pen, D Pen, Pen)	PW36A	28.7.34
Arnada Mains Three (HF, Pen, D, Pen)	PW38	
F. J. Camm's A.C. All-Wave Silver Souvenir Three (HF Pen, D, Pen)	PW50	11.5.35
"All-Wave" A.C. Three (D, 2 LF RC)	PW54	
A.C. 1936 Sonotone (HF Pen, HF Pen, Westector, Pen)	PW56	
Mains Record All-Wave 3 (HF Pen, D, Pen)	PW70	5.12.30
All-World Ace (HF Pen, D, Pen)	PW80	28.8.37
Four-valve : Blueprints, 1s. each.		
A.C. Fury Four (SG, SG, D, Pen)	PW20	
A.C. Fury Four Super (SG, SG, D, Pen)	PW34D	
A.C. Hall-Mark (HF Pen, D, Push-Pull)	PW45	24.7.37
Universal Hall-Mark (HF Pen, D, Push-Pull)	PW47	9.2.35
A.C. All-Wave Corona Four	PW81	6.11.37

SUPERHETS.		
Battery Sets : Blueprints, 1s. each.		
£5 Superhet (Three-valve)	PW40	5.6.37
F. J. Camm's 2-valve Superhet	PW52	13.7.35
F. J. Camm's £4 Superhet	PW58	
F. J. Camm's "Vitesse", All-Waver (5-valver)	PW75	27.2.37
Mains Sets : Blueprints, 1s. each.		
A.C. £5 Superhet (Three-valve)	PW43	
D.C. £5 Superhet (Three-valve)	PW42	1.12.34
Universal £5 Superhet (Three-valve)	PW44	
F. J. Camm's A.C. £4 Superhet 4	PW59	31.7.37
F. J. Camm's Universal £4 Superhet 4	PW60	
"Qualitone" Universal Four	PW73	16.1.37
Four-valve : Double-sided Blueprint, 1s. 6d.		
Push-Button 4, Battery Model	PW95	22.10.38
Push-Button 4, A.C. Mains Model		
SHORT-WAVE SETS.		
One-valve : Blueprint, 1s.		
Simple S.W. One-valver	PW88	9.4.38
Two-valve : Blueprints, 1s. each.		
Midget Short-wave Two (D, Pen)	PW38A	
The "Fleet" Short-wave Two (D HF Pen, Pen)	PW91	27.8.38
Three-valve : Blueprints, 1s. each.		
Experimenter's Short-wave Three (SG, D, Pow)	PW30A	30.7.38
The Perfect 3 (D, 2 LF RC and Trans)	PW63	7.8.37
The Band-Spread S.W. Three (HF, Pen, D Pen, Pen)	PW68	1.10.38
PORTABLES.		
Three-valve : Blueprints, 1s. each.		
F. J. Camm's ELF Three-valve Portable (HF Pen, D, Pen)	PW65	
Parvo Flyweight Midget Portable (SG, D, Pen)	PW77	19.6.37
Four-valve : Blueprint, 1s.		
"Imp" Portable 4 (D, LF, LF, Pen)	PW86	19.3.38
MISCELLANEOUS.		
S.W. Converter-Adapter (1 valve)	PW48A	
AMATEUR WIRELESS AND WIRELESS MAGAZINE		
CRYSTAL SETS.		
Blueprints, 6d. each.		
Four-station Crystal Set	AW427	23.7.38
1934 Crystal Set	AW444	
150-mile Crystal Set	AW450	
STRAIGHT SETS. Battery Operated.		
One-valve : Blueprints, 1s. each.		
B.B.C. Special One-valver	AW387	
Twenty-station Loudspeaker One-valver (Class B)	AW449	
Two-valve : Blueprints, 1s. each.		
Melody Ranger Two (D, Trans)	AW388	
Full-volume Two (SG det. Pen)	AW392	
Lucerne Minor (D, Pen)	AW426	
A Modern Two-valver	WM409	
Three-valve : Blueprints, 1s. each.		
Class B Three (D, Trans, Class B)	AW386	
Fan and Family Three (D, Trans, Class B)	AW410	25.11.33
£5 5s. S.G. 3 (S.G. D, Trans)	AW412	2.12.33
Lucerne Ranger (SG, D, Trans)	AW422	
£5 5s. Three De Luxe Version (SG, D, Trans)	AW435	19.5.34
Lucerne Straight Three (D, RC, Trans)	AW437	
Transportable Three (SG, D, Pen)	WM271	
Simple-Tune Three (SG, D, Pen)	WM327	June '33
Economy-Pentode Three (SG, D, Pen)	WM337	Oct. '33
"W.M." 1934 Standard Three (SG, D, Pen)	WM351	
£3 3s. Three (SG, D, Trans)	WM354	Mar. '34
1935 £6 6s. Battery Three (SG, D, Pen)	WM371	
PTP Three (Pen, D, Pen)	WM389	
Certainty Three (SG, D, Pen)	WM393	
Minutube Three (SG, D, Trans)	WM396	Oct. '35
All-Wave Winning Three (SG, D, Pen)	WM400	
Four-valve : Blueprints, 1s. 6d. each.		
65s. Four (SG, D, RC, Trans)	AW370	
2HF Four (2 SG, D, Pen)	AW421	
Self-contained Four (SG, D, LF, Class B)	WM331	Aug. '33
Lucerne Straight Four (SG, D, LF, Trans)	WM350	
£5 5s. Battery Four (HF, D, 2 LF)	WM381	Feb. '35
The H.K. Four (SG, SG, D, Pen)	WM384	Mar. '35
The Auto Straight Four (HF Pen, HF Pen, DDT, Pen)	WM404	Apr. '36
Five-valve : Blueprints, 1s. 6d. each.		
Super-quality Five (2 HF, D, RC, Trans)	WM320	
Class B Quadradyne (2 SG, D, LF, Class B)	WM344	
New Class B Five (2 SG, D, LF, Class B)	WM340	

Mains Operated.		
Two-valve : Blueprints, 1s. each.		
Consoclectric Two (D, Pen) A.C.		AW403
Economy A.C. Two (D, Trans) A.C.		WM236
Unicorn A.C. D.C. Two (D, Pen)		WM394
Three-valve : Blueprints, 1s. each.		
Home Lover's New All-electric Three (SG, D, Trans) A.C.		AW383
Mantovani A.C. Three (HF Pen, D, Pen)		WM374
£15 15s. 1936 A.C. Radiogram (HF, D, Pen)		WM401
Four-valve : Blueprints, 1s. 6d. each.		
All Metal Four (2 SG, D, Pen)		WM326
Harris' Jubilee Radiogram (HF Pen, D, LF, P)		WM386
July '33		
May '35		
SUPERHETS.		
Battery Sets : Blueprints, 1s. 6d. each.		
Modern Super Senior	WM375	
'Varsity Four	WM395	Oct. '35
The Request All-Waver	WM407	June '36
1935 Super Five Battery (Superhet)	WM379	
Mains Sets : Blueprints, 1s. 6d. each.		
Heptode Super Three A.C.	WM359	May '34
"W.M." Radiogram Super A.C.	WM366	
PORTABLES.		
Four-valve : Blueprints, 1s. 6d. each.		
Holiday Portable (SG, D, LF, Class B)		AW393
Family Portable (HF, D, RC, Trans)		AW447
Two H.F. Portable (2 SG, D, QP21)		WM363
Tyers Portable (SG, D, 2 Trans)		WM367
SHORT-WAVE SETS—Battery Operated.		
One-valve : Blueprints, 1s. each.		
S.W. One-valver for America	AW429	15.10.38
Rome Short-waver	AW452	
Two-valve : Blueprints, 1s. each.		
Ultra-short Battery Two (SG det, Pen)	WM402	Feb. '36
Home-made Coil Two (D, Pen)	AW440	
Three-valve : Blueprints, 1s. each.		
World-ranger Short-wave 3 (D, RC, Trans)		AW355
Experimenter's 5-metre Set (D, Trans, Super-regen)		AW438
Experimenter's Short-waver (SG, D, Pen)		AW463
The Carrier Short-waver (SG, D, P)	WM390	July '35
Four-valve : Blueprints, 1s. 6d. each.		
A.W. Short-wave World-Beater (HF Pen, D, R.C. Trans)		AW436
Empire Short-waver (SG, D, RC, Trans)		WM313
Standard Four-valver Short-waver (SG, D, LF, P)		WM383
Mar. '35		
Superhet : Blueprint, 1s. 6d.		
Simplified Short-wave Super	WM397	Nov. '35
Mains Operated.		
Two-valve : Blueprints, 1s. each.		
Two-valve Mains Short-waver (D, Pen) A.C.		AW453
"W.M." Band-spread Short-waver (D, Pen) A.C. D.C.		WM368
"W.M." Long-wave Converter		WM380
Three-valve : Blueprint, 1s.		
Emigrator (SG, D, Pen) A.C.		WM352
Four-valve : Blueprint, 1s. 6d.		
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans)		WM391
Aug. '35		
MISCELLANEOUS.		
S.W. One-valve Converter (Price 6d.)		
Enthusiast's Power Amplifier (1/6)		AW329
Listener's 5-watt A.C. Amplifier (1/6)		WM887
Radio Unit (2v.) for WM392		WM392
Harris Electrogram (battery amplifier) (1/-)		WM398
De Luxe Concert A.C. Electrogram		WM309
Mar. '36		
New Style Short-wave Adapter (1/-)		WM388
Trickle Charger (6d.)		AW462
Jan. 5, '35		
Short-wave Adapter (1/-)		AW456
Superhet Converter (1/-)		AW457
B.L.D.L.C. Short-wave Converter (1/-)		WM405
May '36		
Wilson Tone Master (1/-)		WM406
June '36		
The W.M. A.C. Short-wave Converter (1/-)		WM408

Miscellaneous Advertisements

Advertisements are accepted for these columns at the rate of 3d. per word. Words in black face and/or capitals are charged double this rate...

RECEIVERS, COMPONENTS AND ACCESSORIES

Surplus, Clearance or Secondhand, etc.

SOUTHERN RADIO: Big new bargains. Coil Units, Push-button Units and Kits.

49/6. 1939 ALL-WAVE Tuning Units. Exceptional offer. List value £4/10/0. Factory wired, tested and aligned, ready to connect to amplifier.

22/6. 5-BAND 3-valve Pentode battery kits. An unbeatable bargain. Large numbers sold. Latest 1939 design.

10/-. A.R.P. Radio Outfits, comprising finest crystal set, pair headphones, aerial and earth equipment, switch, etc.

3/11. A.R.P. Crystal Receivers. Finest quality with semi-permanent detectors.

5/-. SOUTHERN'S famous bargain parcels of useful radio components: coils, transformers, resistors, circuits, etc., value 21/-.

8/6. TELSEN A.C./D.C. 5-range multi-meters; 4/- Ace "P.O." Microphones.

2/6. ORMOND Loudspeaker Units, new and boxed. Unshrouded type, 2/-.

3/6. TELSEN W349 Midget Iron Core coils; dual-range coils, 2/6; with aerial series condenser, W76, 3/3.

6/6. COMPLETE 2-way Morse Practice Outfits, each instrument comprising key, buzzer and code on bakelite base.

10/-. PARCEL of assorted servicing components. At least 100 articles: resistances, tubulars, mica's, variables, electrolytics, wire, sleeving, volume controls, etc.

SOUTHERN RADIO, 46, Lisle Street, Leicester Square, London, W.C. (Gerrard 6653).

VAUXHALL.—All goods previously advertised are still available; send now for latest price list, free.—Vauxhall Utilities, 163a, Strand, W.C.2.

BARGAINS from Id. to 2/6. Coils, Transformers, Condensers, Valves, Chokes, Cabinets, Speakers, Meters, etc. Stamp for Lists.—Reed, 11, Eterby Seaur, Carlisle.

NEW RECEIVERS, COMPONENTS AND ACCESSORIES

BANKRUPT BARGAINS.—List free. State requirements. All new goods. Ferguson 5v. superhet chassis all-wave, speaker and valves, 75/-.

BANKRUPT BARGAINS.—Brand new 1938 radio sets in makers' cartons with guarantees at less than half retail prices: send 1d. stamp for list bargains.—261-3, Lichfield Road, Aston, Birmingham.

LOUDSPEAKER REPAIRS

REPAIRS in Moving Coil Speakers, Cones and Coils fitted and Repwound. Fields altered. Prices Quoted including Eliminators, Loudspeakers Repaired, 4/-; L.F. and Speech Transformers, 4/-, post free.

LOUDSPEAKER repairs, British, American, any make. 24-hour service, moderate prices.—Sinclair Speakers, Alma Grove, Copenhagen Street, London, N.1.

VALVES

AMERICAN Valves in Sealed Cartons, all types 5/6 post paid.—Valves, 661/3, Harrow Road, N.W.10.

PREMIER 1939 RADIO

PREMIER BATTERY CHARGERS. Westinghouse Rectification. Complete. Ready for use. To charge 2 volts at 1 amp, 10/-; 6 volts at 1 amp, 16/6; 6 volts at 1 amp, 19/6; 12 volts at 1 amp, 21/-; 6 volts at 2 amps, 32/6.

CARDBOARD ELECTROLYTIC CONDENSERS, 4 mf. or 8 mf. 500 v., 1/6 each. 8+4 mf. 500 v., 2/3, 8+8 mf. 500 v., 2/6, 4+4+4 mf. 500 v., 2/6, 16+8 mf. 500 v., 3/6.

TUBULAR METAL CAN ELECTROLYTICS by famous makers. 4 or 8 mf. dry, 500 v., 2/6 each. 8 mf. wet, 450 v., 2/3. 8 mf. 650 v., Peak dry, 4/-.

RIAS CONDENSERS, 6 mf. 50 v., 6d.; 50 mf. 12 v., 1/-; 25 mf. 25 v., 1/-; 50 mf. 50 v., 1/9.

Premier Transverse Current Microphone, 20/-; Microphone Transformer, 6/-; Table Mike Stand, 7/6.

BRAIDED METAL SCREENED WIRE for mikes, pick-ups, etc. Single, 4d. yd.; Twin, 6d. yd.

GOSMOCORD PICK-UP HEADS. Will fit any tone-arm, 4/6. Piezo Electric Pick-ups with arm. List price, 42/-.

PREMIER S.W. H.F. Chokes, 10-100 metres, 9d. each. Pie-wound, 1/6 each. Screened, 1/6 each.

SHORT-WAVE COILS, 4- and 6-pin types, 13-20, 22-47, 41-94, 78-170 metres, 1/9 each, with circuit.

Special set of S.W. Coils, 14-150 metres, 4/- set, with circuit. Premier 3-band S.W. coil, 11-25, 19-43, 38-86 metres. Suitable any type circuit, 2/6.

COIL FORMERS, 4- or 6-pin low-loss, 1/- each.

UTILITY Micro Cursor Dials, Direct and 100:1 Ratios, 3/9.

PREMIER Short-Wave Condensers, all-brass construction, with Trolitul insulation. 15 mmf., 1/6; 25 mmf., 1/7; 40 mmf., 1/9; 100 mmf., 2/-; 160 mmf., 2/3; 250 mmf., 2/6.

TROLITUL DOUBLE SPACED TRANSMITTING CONDENSERS. 15 mmf., 2/9; 40 mmf., 3/6; 160 mmf., 4/6.

AMERICAN VALVES. We hold the largest stocks of U.S.A. tubes in this country and are sole British Distributors for TRIAD High-grade American Valves.

EUROPA MAINS VALVES, 4v. A.C. Types. A.C./H.L., A.C./L., A.C./S.G., A.C./V.M.S.G., A.C./H.P., A.C./V.H.P., A.C./P., and 1 watt D.H. Pentodes, all 4/6 each.

A.C./Pens., I.H., 5/6; A.C./P.X.4, 6/6; Oct. Freq. Changers, 8/6; Double Diode Triodes, 7/6; Triode Hex. Freq. Ch., 8/6; Tri. Grid Pen., 10/6; 3/- watt D.H. Triode, 7/6. 350 v. and 500 v. F.W. Rect., 5/6.

13 v. 2 amps. Gen. Purpose Triodes, 5/6; H.F. Pens. and Var.-Mu. H.F. Pens., Double Diode Triodes, Oct. Freq. Changers, 7/6 each. Full-wave and Half-wave Rectifiers, 5/9 each.

Premier Short-Wave Kits

Complete to the last detail including all Valves and coils, as well as theoretical and wiring diagrams and lucid instructions for building and working. Each kit is supplied with a steel Chassis and Panel and uses plug-in coils to tune from 13 to 170 metres.

- 1 Valve Short-Wave Receiver or Adapter Kit ... 17/6
1 Valve Short-Wave Superhet Converter Kit ... 20/-
1 Valve Short-Wave A.C. Superhet Converter Kit ... 22/6
2 Valve Short-Wave Receiver Kit ... 25/-
3 Valve Short-Wave Screen Grid and Pentode Kit ... 58/6

Premier Moving Coil Meters

Table with columns for Model No. 21 (3in. square case) and Model No. 311 (3 1/2in. diameter round case) listing various meter types and prices.

Model 311. 0-1 m/A. movement, with calibrated scale, volts-ohms-m/A., 25/-.

VOLTAGE MULTIPLIER RESISTANCES, guaranteed accuracy ± 2 per cent. All standard ranges, 1/3 each.

TAPPED SHUNT to provide readings of 5 m/A., 25 m/A., 250 m/A., and 1,000 m/A., 5/6.

MOVING IRON METERS. 2 1/2 inch flush case. Milliamps ranges from 10 m/A. to 500 m/A. 1; 3; 5; 10 or 30 amps. 6 or 16 volts. All 5/9 each. 0-250 volts, 10/6 each.

Our City Branch is moving from 165 to 169, Fleet Street. You are invited to inspect the many BARGAINS at our CLEARANCE SALE—NOW ON at 165, Fleet Street, E.C.4. Callers only.

Have you had our 1939 Catalogue, Handbook and Valve Manual? 90 pages of Radio Bargains and interesting Data. Price 6d.

ALL POST ORDERS TO: Jubilee Works, 167, Lower Clapton Road, London, E.5. Amherst 4723. CALLERS TO: Jubilee Works, or 169, Fleet Street, E.C.4. Central 2833, or 50, High Street, Clapham, S.W.4. Macaulay 2381.

NEW RECEIVERS AND CHASSIS

ALL ARMSTRONG Radio chassis, including Press Button models, 9 latest models, can be seen and heard at our Showrooms. Demonstrations daily.

SITUATIONS VACANT

TELEVISION.—All those who wish to enter this new profession should apply at once for free handbook to British Institute of Engineering Technology, 18P, Stratford Place, London, W.1.

MISCELLANEOUS

METAL chassis, panels and cabinets, from 2/6; made to your requirements. Prompt quotations and satisfaction guaranteed.—The Universal Productions, Rigby Lane, Bromsgrove, Worcs.

300 Back Issues "P. and A. W." "P. W." "W. W." 37/6 lot.—Searle, 164, Queen Anne Avenue, Bromley, Kent.

THERE'S MONEY IN RADIO!—If you understand radio you can make substantial profits in spare time. For hints and ideas get MONEY-MAKING MADE EASY, by L. Harvey Wood.



See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for 30 years in government works and by leading engineers and manufacturers.

Write for Free Book on the art of "CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE."

TO CYCLISTS! Your wheels will NOT keep round and true, unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with FLUXITE—but IMPORTANT.

THE FLUXITE GUN

is always ready to put Fluxite on the soldering job instantly. A little pressure places the right quantity on the right spot and one charging lasts for ages. Price 1/6, or filled 2/6.



ALL MECHANICS WILL HAVE

FLUXITE

IT SIMPLIFIES ALL SOLDERING

FLUXITE LTD. (Dept. W.P.) DRAGON WORKS, BERMONDSEY STREET, S.E.1.


FREE ADVICE BUREAU COUPON

This coupon is available until April 1st, 1939, and must accompany all Queries and Wrinkles. PRACTICAL AND AMATEUR WIRELESS, 25/3/30.

A Book of Vital Importance to Everyone

“COMMONSENSE and A.R.P.”

FACED with the urgent necessity of providing ourselves with adequate defence against air raids, elaborate precautions are now being made to safeguard the public. Many schemes have been proposed by the Government, but all entail considerable expenditure which the man in the street, small trader, and many house-owners may find beyond their means. The book has been specially prepared for this large proportion of the population, **SHOWING HOW TO MAKE THE BEST USE OF EXISTING PREMISES** when no adequate shelter can be provided without undue expense and interference with normal business and factory production.

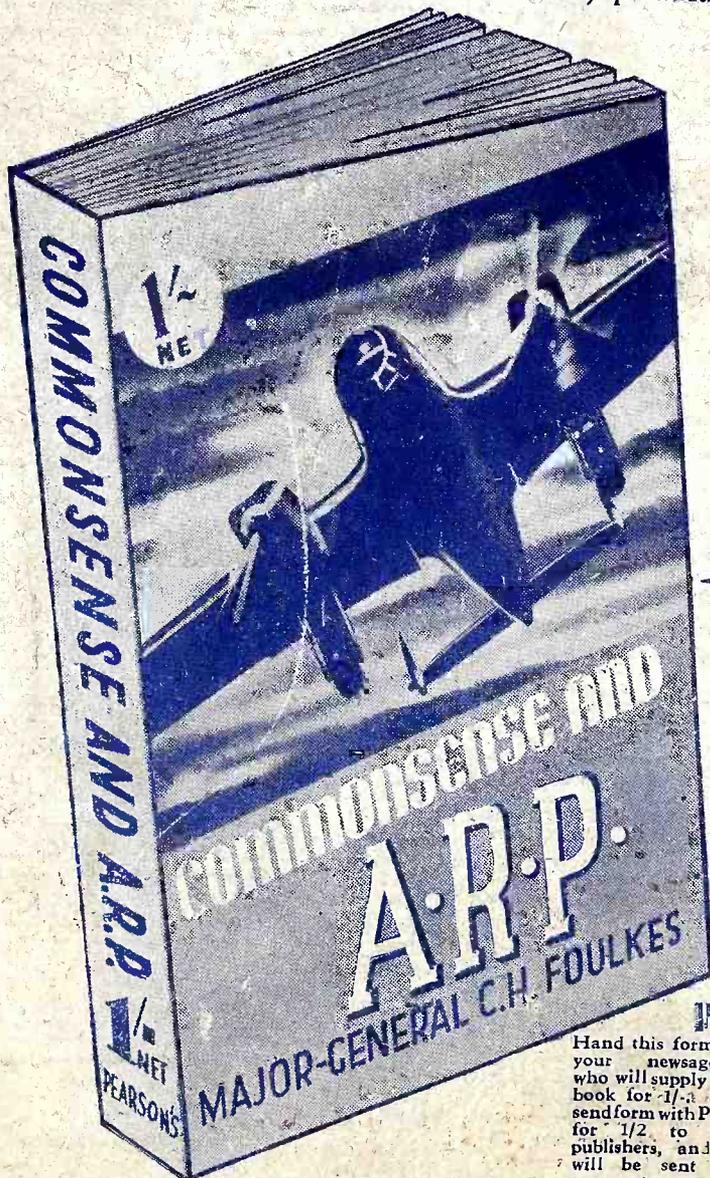

Hand this form to your newsagent, who will supply the book for 1/- net. Or send form with P.O. for 1/2 to the publishers, and it will be sent by return.

What the Press Says!

“You will have less to fear from air-raids if you will take heed of this little book.”—*Daily Sketch*.

“This is one of the most useful of all books on the subject. No words are wasted, yet its contents are comprehensive. At a shilling it is wonderful value.”—*Telegraph and Argus*.

“Major-General Foulkes is thorough. He seems to have covered everything in this invaluable little book. It should be read by all interested in A.R.P.”—*A.R.P. News*.

SOME OF THE A.R.P. SCHEMES PREPARED By MAJOR-GENERAL C. H. FOULKES, C.B., C.M.G., D.S.O.

Messrs. N. M. Rothschild & Sons. Central Electricity Board (Headquarters). British American Tobacco Co., Ltd. (Millbank). Messrs. Carreras Ltd, Ruberoid Co., Ltd. Messrs. Charrington & Co., Ltd. Messrs. Mann Crossman & Paulin Ltd. Messrs. Macleans Ltd. The Marmite Food Extract Co., Ltd. Messrs. Pearce Duff & Co., Ltd. The Halifax Building Society (Halifax). National Provincial Bank Ltd. Royal Bank of Scotland (London, Edinburgh and Glasgow). General Accident Fire & Life Assurance Corporation Ltd. The De Havilland Aircraft Co. (Hatfield). Messrs. Brooke Bond & Co., Ltd.

Contents include:—

General Considerations. Air raid targets. Attack of civil populations futile—bombing in the last war, and in Spain and China. Incendiary bombs—anti-aircraft fragments—gas—poisonous smokes. High-explosives—direct hits—splinters—blast. Indirect effects. General safety measures—evacuation—dispersal. Shelters—trenches—steel and concrete sections. Buildings—basements—upper floors—tenants—multi-office buildings—blocks of flats. Protection against gas. Extemporisation. Public shelters. Fire precautions. Rescue work. First aid. Gas detection. Decontamination. Central Control. Communications, etc., etc.

ORDER FORM

To The Publisher, C. Arthur Pearson, Ltd. (Book Dept.), Tower House, Southampton Street, Strand, London, W.C.2. Please supply copy(ies) “COMMONSENSE AND A.R.P.” 1/- net or by post 1/2

Name

Address

P.W. 25.3.39

C. Arthur Pearson, Ltd.

Published every Wednesday by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and Printed in England by THE NEWNES & PEARSON PRINTING CO., LTD., Exmoor Street, London, W.10. Sole Agents for Australia and New Zealand: GORDON & GOTH, LTD. South Africa: CENTRAL NEWS AGENCY, LTD. *Practical and Amateur Wireless* can be sent to any part of the World, post free, for 17s. 8d. per annum; six months, 8s. 10d. Registered at the General Post Office as a newspaper and for the Canadian Magazine Post.