

PRACTICAL WIRELESS, OCTOBER 1948.

RECEIVER REMOTE CONTROL


Practical Wireless

9^D EVERY MONTH

Vol. 24. No. 507. ||

Editor: F. J. CAMM & ||

OCTOBER, 1948

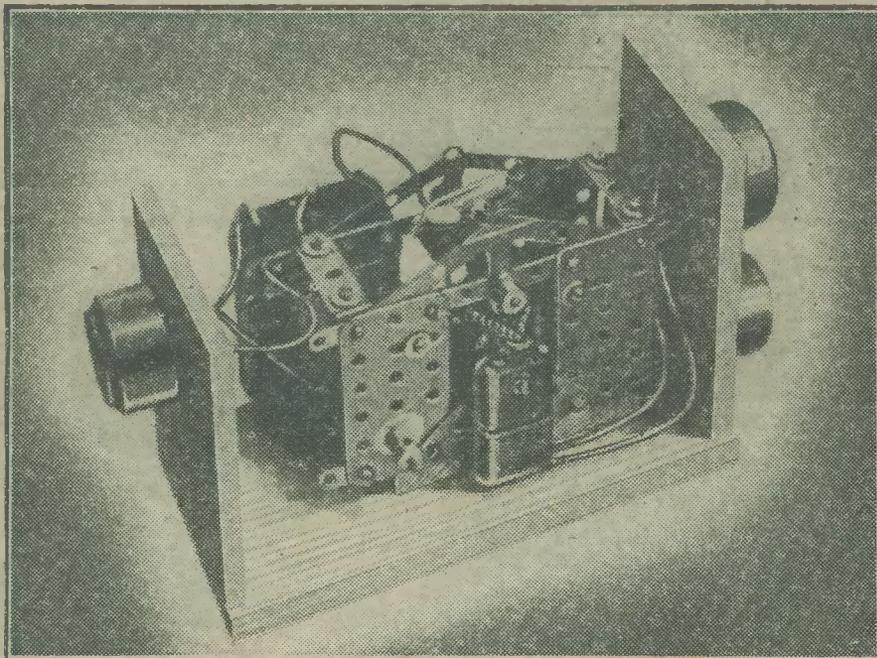

See Page 415

PRINCIPAL CONTENTS

High-Fidelity Amplifier
Practical P.A. Working
Mercury Vapour Rectifiers
Recording Technique

Television Topics
Insulation Tester
Modulation
Noises in Receivers

Connoisseur



At last a gramophone motor to match the performance of the famous Connoisseur Pick-up. Voltage: 220-250 volts A.C., 50 cycles. Rim drive with speed variation. No governors and no gearing. Heavy non-ferrous turntable, machined to run dead true, fly-wheel action—no "WOW." Main turntable spindle hardened, ground and lapped to mirror finish, running in special phosphor bronze bearings. Motor runs in needle-point, self-adjusting bearing. Motor Board in plastic. Pressure on Drive-wheel released when not in use, to obviate forming flats and noisy action.

Apply to

A. R. Sugden & Co. (Engineers) Ltd.

Made by

A. R. Sugden & Co. (Engineers) Ltd., Brighouse, Yks.

HENRY'S

RADIO COMPONENT SPECIALISTS.

A few more selected items from our very comprehensive price list, which will be despatched on receipt of stamp.

CHOKES L.F. 10H, 40 m.a., 5 $\frac{1}{2}$ "; 40H, 30 m.a., 1,250 ohms, 5 $\frac{1}{2}$ "; 10H, 70 m.a., 6 $\frac{3}{8}$ "; 20H, 25 m.a. Fully shrouded, 25/-.

"Q-MAX" CHASSIS CUTTERS. Size 1in., complete with key (suitable for button-base), 10/3; size 1 $\frac{1}{2}$ in. and 1 $\frac{1}{2}$ in. with key, 13/6.

VALVES, EX-GOV'T. VR91 (EF50), 5/- ea. VR92 (EA50), 5/- ea. Guaranteed.

VOLUME CONTROLS. Carbon by Morganite, Centralab, etc. Full range in stock less switch, 4/3; with switch, 6/-.

VOLUME CONTROLS. Wire wound, 2-3 watt, complete range, at 3/6 ea., less switch.

TRANSFORMERS, MAINS. PORTHMINSTER: 200-250 volts, Output, 350-0-350 80 m.a., 4 v., 2.5 amps., 4 v., 5 amps., fully shrouded, 28/6. Available in 6.3 v., 3 amp., 5 v., 2 amp., 28/6. STEWART: 250-0-250, 6 v., 3 amps., 5 v., 2 amps., 80 m.a., 27/6. 350-0-350, 6 v., 3 amps., 5 v., 2 amps., 120 m.a., 32/6. 350-0-350, 6 v., 3 amps., 5 v., 2 amps., 150 m.a., 50/-.

VARLEY: 500-0-500, 200 m.a., 6.3 v., 3a., 5 v., 2.5 a., 2-0-2 v., 4 a., 22/6. 350-0-350, 200 m.a., 6.3 v., 3 a., 5 v., 3 a., 2-0-2 v., 4 a., 33/6.

PORTHMINSTER: 350-0-350, 250 m.a., 6.3 v., 6 a., 4 v., 8 a., 0-2-6 v., 2 a., 4 v., 3 a., 75/- (As specified in "Electronic Engineering").

K.C. 221. FREQUENCY METER. American, crystal-controlled, 2 6S37, 6E8, plus complete set spare valves. Coverage 125-20,000 kc/s. Calibrated charts and instructions booklet supplied. Battery operation, 130 v., H.T., 6 v. L.T. Ample space available for easily constructed mains pack. New, 215 only.

TELEVISION COMPONENTS BY "SCANCO" High grade tested components. Standard fitting. Guaranteed 100%. Focus Coil, 37/6. Scanning Coils, 35/-. Line Transformer, 30/-. E.H.T. Transformer, 4,000 v. with 4 v. and 2 v. heaters, 59/6 only. Suitable for "Electronic Engineering" designs.

R.1636 EX-A.M. RECEIVER. Comprising 10 valves EF50, 2 EB 34, 21 volt Rotary Generator, relays and hundreds of resistors and condensers, complete in metal case. Brand new, 75/- only.

In addition to the above few items, we have probably the most up-to-date stock of Radio Components in the trade. Also over 10,000 valves in stock.

TRADE SUPPLIED.

Send stamp for latest Comprehensive Component List.

HENRY'S, 5, Harrow Road, W.2 PADDINGTON 1098/9.

PROMPT MAIL ORDER SERVICE

DENCO TECHNICAL BULLETIN No. 2.—Contains complete data, and recommended circuits employing Denco Coil Turrets CT6 and CT7, alignment procedure and much useful information on all-wave receivers, 3/2 post free.

DENCO COIL TURRET CT6.—Covers 30 Mc/s. to 150 kc/s. in 5 bands. Fitted with 2-gang condenser, slow motion drive, glass scale calibrated in frequency and station names. For 465 kc/s. I.F. Circuit of modern 5-valve mains receiver supplied. 44/19/6. CT7. Denco Coil Turret less slow motion drive and calibrated scale, 23. Denco Maxi-Q Plug-in and chassis coils. Full range in stock.

TELEVISOR MANUAL by Electronic Engineering, 2/9 post free. This manual contains full details of how to build a modern home-built televisor of sound design with all circuits, layouts and photographic illustrations.

VISION PANELS.—Brand new units containing 6 ceramic B9G valveholders and two diode valveholders, coil forms with adjustable slugs, interstage screens. Complete in aluminium box 15in. x 3 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. to exact specification in above manual and ready to wire. Circuit: 4 RF stages, diode detector, video amplifier, DC restorer and output, 22/6.

SOUND PANELS.—As specified in above manual. Unit size as vision panel containing 2 B9G ceramic valveholders, one amphenol octal valveholder, interstage screens, 3 coil forms with adjustable slugs, ready to wire, 18/9.

H.T. TRANSFORMERS.—Primary for 210, 230, or 250v. HT 4,000v., LT 2 or 4 volts at 2 amps., 72/6. Other components for use in the above televisor available.

EDDYSTONE "640" 9-valve Communications Receiver now available at 227/10/0. Write for details of H.P. on this model. "640" Manual with circuit, etc., 1/8 post free.

EDDYSTONE SEMI-AUTOMATIC MORSE KEY.—See page 325, August issue. Immediate delivery, 23/17/6.

HAM CATALOGUE No. 6.—If you do not already possess a copy of this we would advise you to send 9d. now. 60 pages full of illustrations printed on fine art paper with replaceable price sheets, containing well over 1,000 lines by the leading makers.

BARGAIN LIST B6.—This latest list contains a number of ex-Gov't. and new lines at bargain prices. Price 3d. post free. Please include postage on orders under 22 unless otherwise stated.

SOUTHERN RADIO & ELECTRICAL SUPPLIES

85, FISHERTON ST., SALISBURY, WILTS

Telephone: Salisbury 2108



Whatever your soldering job, in your home or workshop, you will prefer to use Ersin Multicore Solder. No extra flux is required. Multicore is the simple and precision method of making sound soldered joints for all household purposes. Just apply it simultaneously with the soldering iron; the three cores automatically provide correct proportions of flux to solder.

6^{d.}
CARTON
Shown above

WORKSHOP SIZES 4/10 - 6/9 each.

MULTICORE SOLDERS LTD.

Mellier House, Albemarle Street, LONDON, W.1

Tel.: REgent 1411

Resistances. A parcel of 100 popular assorted values: 1 watt, 86 per 100; 1/2 watt, 116 per 100. Trade enquiries invited.

Vibrator Transformers. 6v. in. 250-0-250 v. 100 m.a. out (also available in 12 v.), 86.

Motor Rectifiers.

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

Westinghouse: 0.5 m.a., 311; 0.10 m.a., 76; 0.1 m.a., 106.

Selenium Rectifiers. H.T. h/wave: 250 v. 50 m.a., 59; 200 v. 100 m.a., 59; 250 v. 100 m.a., 76; 250 v. 300 m.a., 12.9.

Bridge Rect. 6 v. 11 amp. 63; 12 v. 11 amp., 12.6; 12 v. 3 amp., 24.; 12 v. 6 amp., 37.6; 36 v. 11 amp., 23.6; 70 v. 11 amp., 37.6. Also L.T. 2.4 v. 1 amp., h/wave, 3.6.

Television. Focus coil, 30-. Scanning coil, 30-. Line Transformer, 23.6.

Television Transf. E. H. T. 4,000 v. 3 m.a., 2 v. 11 amp., 45.-; 500-0-500 v. 250 m.a., 4 v. 5 a., 6.3 v. 8 a., 75.-; 350-0-350 v. 250 m.a., 6.3 v. 6 a., 4 v. 8 a., 4 v. 3 a., 6.3 v., (tapped 2 v.), 2 a., 72.6.

Charger Transf. Input 200-230-250 v., outputs 4 v., 8 v., 15 v., and 24 v., at 3 amp., 27.6.

Ex-Govt. T. M. C. Reed-type Headphones. 70 ohms, 1.9 each (3.6 pair with leads). Single Earphones, 75 ohms, with adjustable headband, 1/6. Ultra Midget 'O'ut Ttr., 32.1.

and Paraflex Ttr. 4-1, both 1in. x 1in. x 1in., 3.- each. P Pull Intervalve, 2.51 each half, and 'O'ut Ttr. 60-1, both 1 1/2in. x 1 1/2in. x 1in., 3.- each. Tanoy Transverse Carbon Mike Inset, 3.-. L.F. Choke, 15 Hny. 300 ohms, 175 m.a., 12.6. M Coil Mike, 2.6. I.F. Ttr., 6.8 m.c., 6.6 pr. Midget Intervalve Ttr., 3-1, 5-1, or 10-1, 3.9 each. Multi-ratio Matching Ttr., 4 windings (2 C.T.) over 10 ratios between 10 and 100-1, 2in. x 1 1/2in. x 1 1/2in., 3.9.

EX-R.A.F. Test Set 74. Special Purpose Oscilloscope, easily converted to a good-class GENERAL PURPOSE OSCILLOSCOPE. Complete in grey metal case. Price £10 10s. includes a circuit of, and all necessary components to effect conversion. (Carr. 10.- extra.)

★ Send 2/d. stamp for very full Stock Lists. When ordering, please cover packing and postage.

STERN RADIO, LTD., 109 & 115, Fleet St., E.C.4
Telephone: CENTral 5814 and 2280.

BACK ROOM STORY

Supremacy is not easily gained—and held. The proud position of STENTORIAN Speakers is due in the main to two factors: specialisation and centralisation.

A firm that has been designing and developing loudspeakers for more than 25 years, not only knows most of the answers but also is able to put them to practical use—and every part—down to the smallest screw—is made in the Whiteley works, by a team which has grown up with the industry.

That, briefly, is the story behind Stentorian; a "back room" story that has brought Whiteley products very much to the fore. Your dealer will be pleased to amplify it.

★ Stentorian Extension Loudspeakers, in handsome polished walnut cabinet, range from £5 15s. 6d. for the SENIOR, to £2 5s. 6d. for the MINOR (or from £5 2s. 6d. to £1 19s. 6d. without matching transformer). Chassis model—12in. P.M. units, £6 6. 0.



—the finest extra SPEAKER for any set
WHITELEY ELECTRICAL RADIO CO. LTD., MANSFIELD, NOTTS

AMERICAN FREQUENCY METERS BC.221.—Contains a Crystal Controlled Oscillator, A Heterodyne Oscillator, and an Audio Frequency Amplifier. Frequency range 125 Kcs. —20,000 kcs. with better than .01 per cent. accuracy over whole scale. Eminently suitable as a VFO. All instruments complete with crystal, valves, calibration book, instruction manual, etc. BRAND NEW. ONLY £15. An illustrated leaflet is available on request.

5 METER CONVERTER.—Ex R.A.F. RF Unit type 36. A superb tuneable unit covering 45-50 meg. Fitted with 3in. Illuminated Slow Motion Dial, and complete with 2 valves. ER54 and EC42 (RF Mixer and Oscillator), 7 meg. I.F. Output. Operating voltages 6.3 v. and 220 v. BRAND NEW, IN MAKERS CARTONS. ONLY 35.

BATTERY SUPERSÉDER.—A vibrator power unit operating from only 2 volt input and delivering 90 v. and 180 v. at 35 mills, 1.4 v. L.T. and G.B. Fully smoothed and requiring little alteration for normal use, these superb units are U.S.A. made. Current consumption is approximately 1 amp. Supplied complete with Instruction Book giving full circuit details. ONLY 60.- (postage 2.-), or with two 2 volt accumulators and completely enclosed with them in a steel case, ONLY 90.- (carriage 5.-). Illustrated leaflet available on request.

R.A.F. H.L.N. 1156 PANEL.—Contains shoals of TX gear, including 2 large .0002 mid. variable caps, variable inductances, switching, 2in. bar and knurled knobs, etc., etc. BRAND NEW IN MAKERS CARTONS. ONLY 9.11 (carriage 3.6).

CONVERTED R.1155 RECEIVER.—In response to numerous requests, we can now supply this famous R.A.F. Communications Receiver modified for normal mains use, and complete with speaker. Unlike other modifications, the power pack, output stage and speaker are fitted into a specially designed cabinet which fits on top of the receiver. The whole makes a presentable installation without using several small units connected by unsightly trailing wires. A really superb Communications Receiver covering 75 kcs.—13.0 mcs. in five wavebands. Fully illustrated leaflet available on request. Only £18 10.- (carriage 12.6. returnable transit case 10.-), or the unmodified version £12 10.-.

C.W.O., Please. S.A.E. for Lists.

U.E.I. CORP

THE RADIO CORNER,
138, Grays Inn Road, London, W.C.1
Phone: TERminus 7937
Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn 5 mins. from Kings Cross.

FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I.C.S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

Write to the I.C.S. Advisory Dept., stating your requirements. It places you under no obligation

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 94, International Buildings, Kingsway, London W.C.2

Please send me your free booklet describing I.C.S. instruction in the subject marked X.

Complete Radio Engineering	Elementary Electronics
Radio Service Engineers	Elementary Radar
Radio Service and Sales	Advanced Short-wave Radio
Elementary Radio	

If you wish to pass a Radio examination, indicate it below

British Institute of Radio Engineers
P.M.G. Certificate for Wireless Operators
City and Guilds Telecommunications
R.A.F. Wireless Operator and Mechanic

Examination students are coached until successful


Name: Age

(USE BLOCK LETTERS)

Address

BUILT TO LAST

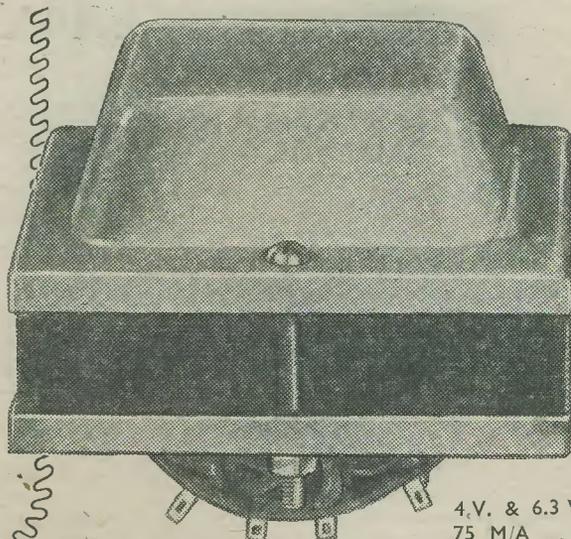Attention to detail and finish makes R.M. Mains Transformers the best value on the market today. Their sound mechanical and technical design and low operating temperature make long service a certainty.




R.M. Mains Transformers

4 V. & 6.3 V. types.
75 M/A ... 37/6d.
120 M/A .. 45/-

M.C.T. RANGE.

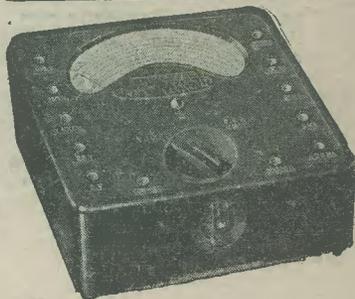R. M. ELECTRIC LTD., TEAM VALLEY, GATESHEAD, II.



'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark.

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set. Stocks are now available of these two famous "Avo" Instruments. If you have any difficulty in obtaining one locally, please send us the name and address of your nearest Radio Dealer.

The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance; 22 ranges of readings on a 3-inch scale. Total resistance 200,000 ohms.

Size: 4 1/2 ins. x 3 1/2 ins. x 1 1/2 ins.

Net weight: 18 ozs.

Price: £8 : 10 : 0

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

D.C. Voltage	A.C. Voltage
0-75 millivolts	0-5 volts
0-5 volts	0-25 "
0-25 "	0-100 "
0-100 "	0-250 "
0-250 "	0-500 "
0-500 "	
	Resistance
D.C. Current	0-20,000 ohms
0-2.5 milliamps	0-100,000 "
0-5 "	0-500,000 "
0-25 "	0-2 megohms
0-100 "	0-5 "
0-500 "	0-10 "

The D.C. AVOMINOR

is a 2 1/2-inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4 1/2 ins. x 3 1/2 ins. x 1 1/2 ins.

Net weight: 12 ozs.

Complete as above.

Price: £4 : 4 : 0

GUARANTEE: The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new AvoMinor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

Sole Proprietors and Manufacturers:—

AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
Winder House, Douglas Street, London, S.W.1

Phone: VIctoria 3404-9

Practical Wireless

16th YEAR
OF ISSUE

and PRACTICAL TELEVISION

EVERY MONTH
VOL. XXIV, No. 507 OCTOBER, 1948

Editor E.J. CAMM

COMMENTS OF THE MONTH

BY THE EDITOR

Better Listening

OUR leader last month on the Campaign for Better Listening has brought a number of illuminating letters indicating that the B.B.C. is not really in touch with the listening public. We are aware that it has its own research bureau which purports to analyse public reactions to programmes and to estimate public taste. If the bureau had operated as intended, many of the programmes which we are told by the B.B.C. are popular would be abolished; for example, none of our readers who has written concerning the campaign likes "Twenty Questions," less than 2 per cent. like crooners and none of them likes the talks on gardening. One of our readers suggests that every listener should compile a black list of programmes and radio personalities he does not like and, as soon as the programme or name is announced, switch over to another programme or switch off.

There seems to be lack of co-ordination within the B.B.C. itself. It consists of a number of small cells containing a producer and the artistes working in entire ignorance of, and without a care for, what is happening in other studios.

A number of readers feel that the campaign will fail purely because it is being launched at the wrong time. There is not the money about that there was two years ago. The sellers' market has gone and the listeners are hanging on to their old receivers waiting for prices to come down. The reduction in purchase tax has not encouraged sales, and we suggest that the campaign should be accompanied by the additional encouragement of a reduction in the prices of all radio and television receivers, and particularly in the latter. This would have the strongest appeal and be far more productive in results than a campaign based on slogans.

There is a general feeling among listeners that the B.B.C. does not exist to provide them with what they want, that it has become a bureaucratic caucus, dictatorial in its attitude and enjoying a form of self-government with powers transcending those of Parliament itself.

There could be a considerable reduction in the number of programmes. It is on tap all day long, every day in the year, and

there can be little wonder that people are sated with radio and are not anxious to spend a considerable sum of money on a new receiver. These are the days when we are told to economise, not to buy things unless they are really essential, and to save more. The purchase tax, indeed, was designed to destroy home sales and force manufacturers to export a high percentage of their productions. The Government campaign to destroy sales has succeeded and, having succeeded, it attempts to recant by reducing the purchase tax. The trade should press for the abolition of the purchase tax altogether, and it should carefully examine its costings to see whether price reductions at this stage are possible.

The bicycle trade some years ago was confronted with a similar slump. It organised a National Bicycle Week and a considerable amount of money was spent in the national press drawing attention to the pleasures of cycling and the beneficial results of cycling upon the health of its devotees. The campaign, however, did not improve sales. The manufacturers then turned to the alternative of reducing prices, and sales enormously increased as a result. Thus, it was proved that the slump was due to the high prices then prevailing. We suggest that the radio trade might follow the example.

One other point; we hope manufacturers will discontinue their practice of employing "stylists," so called, to produce streamlined cabinets with futuristic streaks of chromium plate, in an attempt to emulate the absurd styles common in America.

Editorial and Advertisement Offices:
"Practical Wireless," George Newnes, Ltd.,
Tower House, Southampton Street, Strand,
W.C.2. Phone: Temple Bar 4363.
Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for transmission by
Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.
Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

Contributions

We welcome contributions from readers and particularly articles of a practical nature, describing receivers and components which the reader has built himself. Articles should be accompanied by theoretical and practical wiring diagrams (drawings need only be in pencil), list of components and, where possible, photographs. Articles must, of course, be the original work of the contributor. We especially require descriptions of mains receivers and short-wave receivers. Intending contributors should, in the first place, submit a precis of the proposed article for consideration.

ROUND THE WORLD OF WIRELESS

Broadcast Receiving Licences

THE following statement shows the approximate numbers of licences issued during the year ending June 30, 1948.

Region	Number
London Postal	2,100,000
Home Counties	1,475,000
Midland	1,601,000
North Eastern	1,737,000
North Western	1,471,000
South Western	979,000
Welsh and Border	652,000
Total England and Wales	10,015,000
Scotland	1,059,000
Northern Ireland	186,000
Grand Total	11,260,000

The above number includes 54,850 television licences, an increase of 2,350 over the previous month.

Eight hundred and thirty-nine successful prosecutions for operating wireless receiving sets without licences were undertaken during June—a record number for any single month.

The British Institution of Radio Engineers

MR. W. E. MILLER has been nominated for election as a vice-president of the British Institution of Radio Engineers.

In approving this nomination at a recent council meeting, Admiral Mountbatten referred to Mr. Miller's 20 years' membership of the Institution and the fact that Mr. Miller was one of the signatories to the incorporation of the Institution in 1932.

Mr. Miller qualified for membership shortly after graduating from Cambridge University, and in addition to having served on all the Institution's committees, has also several times been elected a member of the General Council.

Mr. Miller is well known as the editor of "The Wireless and Electrical Trader" and the author of several books.

General Sikorski Memorial Fund

RECENTLY £3,500 worth of Philips X-ray and electro-medical apparatus was officially handed over to the Children's Clinic of Poznan University, Poland, by the General Sikorski Memorial Hospital Fund.

The presentation took the form of a ceremony held at Century House, Shaftesbury Avenue, the headquarters of Philips Electrical, Ltd., makers of the equipment.

His Excellency, the Polish Ambassador, representing Poznan University, received an illuminated scroll commemorating the event, presented to him jointly by Mrs. E. d'A. Willis, and Major Rowland Sanders, Trustees of the General Sikorski Memorial Hospital Fund.

Phototelegraph Service by Wire Reopened

THE public phototelegraph service by wire to Belgium, France, Denmark, Italy, Norway and Sweden was reopened recently.

The service can be used for the transmission of photographs, drawings, manuscripts or printed matter and particulars of the charges, hours of service, etc., may be obtained from the following post offices in London.

London Chief Office, King Edward Street, E.C.1.
Fleet Street Branch Office, E.C.4.
Leicester Square Branch Office, Charing Cross Road, W.C.2.

South Western District Office, Howick Place, S.W.1.

Western District Office, Wimpole Street, W.1, and from the head post offices in Manchester, Liverpool, Birmingham, Edinburgh, Glasgow and Newcastle-on-Tyne.

Radar Patent

THE original Radar Patent, filed on September 17th, 1935, and until now on the secret list, is now released. It is number 593,017 and may be obtained from the Sales Branch, The Patent Office, 25, Southampton Buildings, London, W.C.2, price 1s.



Mr. P. B. Whiteley (Director of the well-known W/B establishment) and his bride.

Whiteley Electrical Wedding Bells

THE marriage recently took place of Mr. P. B. Whiteley (a new director of the makers of the well-known W/B speakers and other components), and Miss O. M. Marchant, daughter of Mr. R. P. Marchant, a well-known solicitor in the Midlands.

The bells of St. Peter's Church, Mansfield, where they were married, had to be dismantled some time ago, but before this happened a recording of them was made, and by the use of amplifiers in the church tower a most realistic effect of the original bells was obtained.

Sir Clifford Paterson, O.B.E., D.Sc., F.R.S.

THE General Electric Co., Ltd., deeply regrets to announce the death, on Monday, July 26th, after a short illness, of Sir Clifford Paterson, O.B.E., D.Sc., F.R.S., at the age of 68.

Clifford Copeland Paterson was born on October 17th, 1879, at Stamford Hill, and was educated at Mill Hill School.

He joined the G.E.C. in 1919 to establish and direct the G.E.C. Research Laboratories. Under his guidance, these laboratories, which began with a staff of 29, have developed into the largest of their kind in the country with a present staff of 1,750. He was appointed to the board of the G.E.C. in 1941 and received his knighthood in the Birthday Honours List of 1946.

Radar for Tilbury-Gravesend Ferry Service

BRITISH Railways (London Midland Region) are installing radar at Tilbury so that a better ferry service can be provided in foggy weather.

The apparatus is being fitted in Riverside Station, where a picture of the river and its shipping, gathered by a revolving scanner above the clock tower, will be recorded on an indicator screen situated in a darkened control room.

An operator watching the screen will use a wireless telephone to advise the Masters of the ferry steamers where they are in relation to other vessels and, of course, how they are placed in relation to the ferry landings.



Mr. A. W. Welton, Financial Controller of Mullard Electronic Products Ltd.

International Short-wave Club

A VERY special broadcast for short-wave listeners from Radio Leopoldville in the Belgian Congo is to take place on Wednesday, September 15th, at 19.00 G.M.T. and also on Thursday, September 16th, at 02.00 G.M.T. Frequency 9.768 Mc/s (30.71 metres).

New Amateur Band

THE Postmaster-General announces that, as from September 1st, 1948, holders of Amateur Wireless Station licenses may use telegraphy and telephony on any frequency between 145 and 146 mc/s, with power not exceeding 25 watts, subject to the general conditions of their licences and subject to no interference being caused with the working of other services.

Vital wireless services are operating in the 144 to 145 mc/s and 146 to 148 mc/s bands; and amateurs must ensure that no transmissions are made by them in these adjacent bands, outside the authorised limits 145 to 146 mc/s.

Miscellaneous Goods Amendment Order

THE Board of Trade, in consultation with the Central Price Regulation Committee, have made the Miscellaneous Goods (Maximum Prices) (Amendment No. 2) Order, 1948, which came into operation on Tuesday, August 17th. This Order makes minor amendments to the Miscellaneous Goods (Maximum Prices) (Amendment) Order, 1948; S.I. 1948, No. 776. It varies the scope of that Order by including hard haberdashery and excluding thermal storage water heaters and certain types of wireless sets; and it alters the definition of excluded iron and steel articles in the Second Schedule.

Brazilian Transmitters

THE new Marconi-equipped broadcasting station at Recife, Brazil, was recently inaugurated. It includes a medium-wave transmitter rated at 20 kW and two short-wave transmitters of 25 kW each.

Station WRUL

PERMISSION is being sought for an increase in power to 250,000 watts for station WRUL at Boston, Mass. If sanctioned, this increase will make the transmitter the most powerful broadcaster in the Western hemisphere.

Aircraft Interference

INTERFERENCE was recently experienced with aircraft radio from Oregon to Puerto Rico and far east into the Atlantic. This was eventually traced to an electronic heater in a Johnstown (Penn.) chair manufacturing plant.

Ahmedabad Station

WE understand that the proposed capital of Maha Gujerat will soon have an up-to-date radio station. It is learned that the details of the whole project are complete and the necessary arrangements will soon be completed to instal the studio temporarily in a private building until a permanent home is available.

A High-fidelity Amplifier

Contrast Expansion and Tone Controls are Included in This Design

By P. E. TOOKE

BEING a lover of music, and possessing quite a collection of records, I started work some months ago on designing and building a really high-fidelity amplifier that would leave hardly anything to be desired.

Consequently, this circuit I am about to describe is the outcome of six previous circuits, incorporating all their good points and, I hope, not many bad.

It is, I am the first to admit, elaborate, but to achieve the perfection I wanted I was prepared to go to extreme lengths. If any reader is not so critically inclined, several of the stages can be cut out, such as the contrast and tone-control circuits, so bringing down the cost of construction.

To proceed, I intend to give a brief description of the line-up, and then take the whole apparatus stage by stage, giving the faults and any hints as I found them.

To make it easier to follow I have broken the diagram into three units: first, "the contrast and tone-control stages"; second, "voltage amplifier, phase splitter and output"; and thirdly, "the power pack."

The first two units mentioned were on a chassis

20in. by 9in., and well spaced out. The power unit, which includes rectifiers and smoothing networks, etc., was built on a chassis 10in. by 6in.

The valve line-up is: EF39, side amplifier for contrast expansion; 6H6, expansion rectifier; 6C5, tone-control stage; 6K7, controlled voltage amplifier; 6C5, phase splitter; and 6V6s in parallel, push-pull output. Two 6V6s in normal push-pull run very well, but I needed plenty of output to play with, and the quality is improved by using four. The power-pack uses an FW4/500 for supplying the output tubes only, and a 5Z4G for the rest.

Also, it will be noticed that a 6X5 is used as a half-wave rectifier for the speaker field, which is a Magnavox Duode.

General Construction

All the main components were obtained and laid out as balanced as possible, being consistent with good wiring practice. The stages ran straight up the centre of the chassis so that the first stage was at one end and the output valves at the other. Wiring was carried out with heavy gauge wire

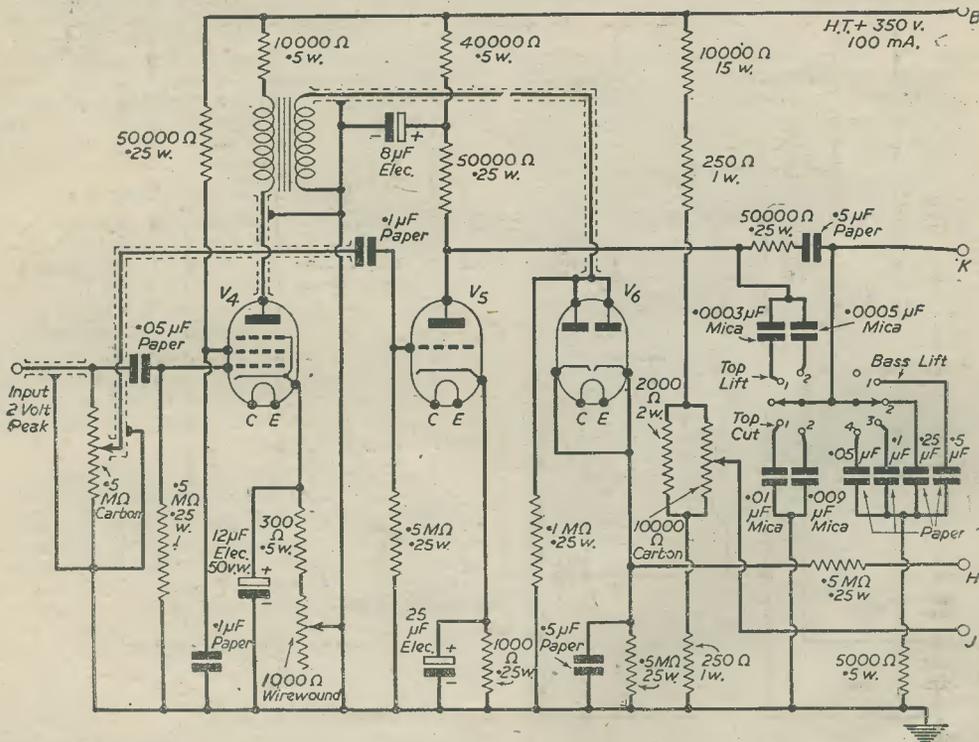


Fig. 1.—The contrast and tone control stages. Recommended valves are: V4 EF39, V5 6C5G, and V6 6H6G.

found that by choosing a good transformer and para-feeding it with a large condenser, results were just as good, if not better, than with R.C. coupling, also you got more stage-gain and therefore a second audio stage was done away with.

The phase-splitting stage V_8 is a normal circuit, and apart from measuring up the resistors to make sure they are matched, care is all that matters in

at 100 mA. for all the rest of the gear. The smaller transformer supplies all the heaters, and a 200 ohms relay is fitted in the H.T. line of this transformer, so when the heaters of the 6V6s are hot, the relay switches on the mains to the large transformer, as the FW4/500 is directly heated; this saves the high voltage building up across the condensers and blowing them.

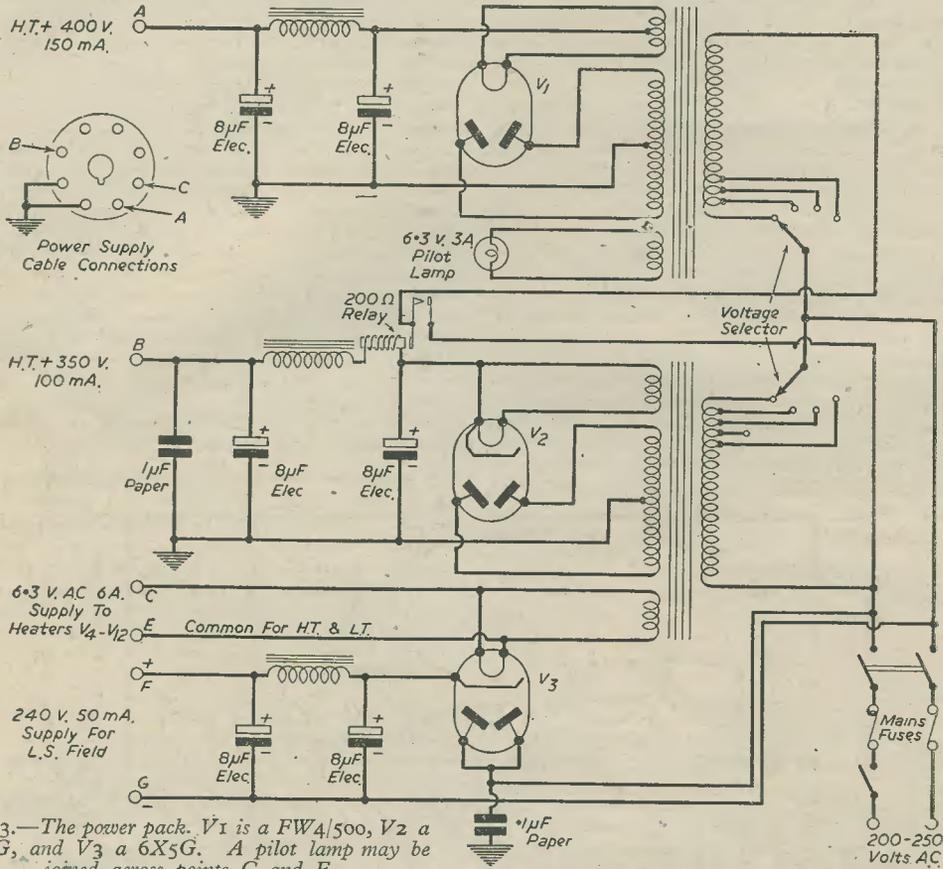


Fig. 3.—The power pack. V_1 is a FW4/500, V_2 a 5Z4G, and V_3 a 6X5G. A pilot lamp may be joined across points C and E.

the layout. The output (four 6V6s) are all supplied with grid and plate stoppers. The original design omitted these and the output stage howled. By fitting the stoppers right on the valve-pin, this is cured instantly. A preset potentiometer was fitted for bias. This is not strictly necessary, as a fixed resistor can be used just as well. The bias voltage was adjusted to 13 or 14 volts, which seemed to suit the valves admirably.

The output transformer is a "Premier Matchmaker" working a Magnavox Duode speaker at present. The baffle is a piece of $\frac{3}{4}$ in. wood 5ft. by 4ft., and seems ample for the speaker.

The Power Pack

This is shown in Fig. 3, and, as I have mentioned, is built on a separate chassis.

Two transformers are used—one 450-0-450 at 150 mA. for the output valves; the other, 350-0-350

at 100 mA. for all the rest of the gear. The smaller transformer supplies all the heaters, and a 200 ohms relay is fitted in the H.T. line of this transformer, so when the heaters of the 6V6s are hot, the relay switches on the mains to the large transformer, as the FW4/500 is directly heated; this saves the high voltage building up across the condensers and blowing them.

The rest of the power unit is general and I do not think needs further explanation. If the reader builds this amplifier for gramophone reproduction, for which it was designed in the first place, a word or two here on the pick-up would not be out of place.

I used a crystal pick-up, which suits this circuit very well. If it seems a little peaky on top frequencies, the tone-control stage looks after that. Against my better judgment, but owing to the high cost of records, I have used thorn needles, and top notes and transients are faithfully reproduced.

So far I have not had the chance to try a moving-coil pick-up on this amplifier, but it should, with proper matching, give a better performance than a crystal.

MINISTRY APPEALS TO HOUSEWIVES
Keep Waste Paper separate, dry and clean for salvage.

Crystal-grinding Technique

How to Adjust ex-Government Crystals for Your Own Frequencies

By J. N. MALONEY (ZL3DE)

ANY amateurs during or since the end of the war have, by many and devious means, acquired quartz crystals somewhere in the range 2,000-7,000 kc/s. Owing to the widespread use of crystals for radio communication during the war, particularly in aircraft H.F. and V.H.F. transmitters, large quantities have been declared surplus by the many Allied Governments. These have been selling at very reasonable prices. However, it is reasonable to assume also that many crystals have come into possession of "hans" as souvenirs.

As most of these "rocks" are outside the present amateur bands, they have either been regarded as useless or thrown into the junk box after several abortive attempts at grinding them to a desired frequency.

The purpose of this article, which is reproduced by courtesy of the New Zealand amateur magazine, "Break-in," is to enlighten those who have obtained disappointing results, either through inexperience or lack of sufficient data on this subject.

For the information of those interested in this subject, crystals coming into the above category are usually divided into two types of cuts, notably the AT and the BT cut. It is not intended in this article to enter into a discussion on the derivation of these cuts, as the information is readily available on this matter in most copies of the "Radio Amateurs' Handbook." However, it will be found that almost without exception crystal blanks in the range between 2 and 4.5 Mc/s are AT cut, and those between 4.5 and 7 Mc/s are BT cut. Mention of these cuts will be made later in the article.

Apparatus Required

Before commencing the grinding process it will be necessary to have on hand the following equipment:

- (1) A sheet of plate glass approximately 6in. by 6in. (an old piece of window pane will do). This must be perfectly flat and free from any scratches, cracks and abrasions.
- (2) A basin of clean water (warm).
- (3) A quantity of clean, lintless cloth (an old handkerchief is ideal).
- (4) An ordinary lead pencil.
- (5) The grinding compound.
- (6) Not absolutely essential but of great help, a 1in. micrometer, reading in tenths of a thousandth of an inch.
- (7) A test oscillator (the rig's crystal oscillator will do).
- (8) A heterodyne type frequency meter or calibrated receiver.

Now, the first procedure is to test the blank (in its original holder, if possible) for frequency and activity as indicated by a good minimum dip in the oscillator plate milliammeter, or maximum grid current in the following stage if the transmitter is

being used as a test oscillator. The magnitude to be expected in these readings may easily be determined by first noting the readings obtained when a good 3.5 Mc/s or 7 Mc/s crystal, known to be active, is placed in the test oscillator.

Having satisfied yourself on this requirement, disassemble the crystal unit, exercising extreme caution as quartz blanks are very susceptible to damage such as chipping of corners or edges, and even complete or partial fracture when being removed from or placed in a holder. Place the blank in a safe position and prepare the plate of glass for the grinding or lapping operation. The choice of the grinding compound will depend on how close to the desired frequency the blank oscillates. For blanks within approximately 300 kc/s of the frequency wanted, Grade No. 900 carborundum powder or standard jewellers' rouge will be necessary. Incidentally, jewellers' rouge in powder form is readily obtainable from any optician at a very moderate price. For blanks more than 300 kc/s lower than the required frequency, a rougher grade of compound is first required, and the No. 500 grade carborundum powder is recommended, finishing with No. 900 grade or jewellers' rouge.

After determining the grade of compound necessary for the particular blank in hand, shake sufficient of the powder on to the plate of glass so that when water is added to the mixture a creamy paste is formed over most of the plate. In subsequent grinding it may be necessary to add a little water to maintain this consistency.

Now, take up the crystal blank. Mark one side carefully with the pencil, either writing on the present frequency or the letter R, meaning that this side will be the reference side of the blank. Note carefully that *all* grinding must be performed on the opposite face of the blank. Failure to observe this precaution will result in certain trouble owing to the fact that the crystal will not have its faces parallel to one another.

Grinding

If the blank is the $\frac{1}{2}$ in. by $\frac{1}{2}$ in. size, grinding is best performed by placing the ball of the second finger on the centre of the blank, remembering, of course, to keep the reference side uppermost at all times. Commence grinding slowly with a figure eight motion, covering an area of 9 to 16 square ins. After about eight or 10 evolutions give the blank a quarter turn and repeat as above until the crystal has been turned around each quarter. Repeat the complete cycle of operations once more. Due to the fact that the weight of the finger has been on the centre of the blank it will tend to grind thinner there than on the edges. Therefore, after each two lapping operations as above, it is wise to place the edge of the first finger on each corner of the blank in turn and make about eight figure-of-eights on each one. This technique, if carefully and conscientiously

carried out, will result in the blank being kept perfectly flat during the whole grinding process. Consequently, little or no trouble will be experienced in making the blank oscillate each time it is tested. Those possessing a micrometer will find that instrument invaluable in checking for the above after each sequence of operations.

The next step is to lift the crystal very carefully from the plate, rinse it thoroughly and cautiously in the bowl of warm water, then dry same with cloth, holding the blank by its edges so that no grease or perspiration is allowed on its surface. Ensure that the pencil marking has not been erased during the grinding or rinsing process. Replace in its holder and check for frequency and activity.

With the larger blanks a similar procedure is adopted with two exceptions. First being that the first and second fingers are placed on the crystal and the same motions carried out. Secondly, when grinding the corners the first and second fingers are placed diagonally across the corners, turning the blank four times to complete the operation. Because of the larger area of the blank, this procedure is essential, as the quartz has a certain amount of spring in it when subjected to even relatively light pressure during grinding.

Governing Factors

The following factors govern the increase in frequency after each cycle of operations. Grade of abrasive, finger pressure, consistency of paste, area covered in each stroke, size of blank, and type of cut. Only with practice can the frequency increase be judged, taking into account the above factors. Therefore, it is wise to observe extreme caution when grinding a blank for the first time, and use only light pressure on each stroke.

When the desired frequency is being approached add more water to the paste, lighten the pressure, make fewer evolutions or cover a smaller area on each figure eight motion. With practice, a crystal can be ground to within a few cycles plus or minus that intended.

For the benefit of those amateurs who have a micrometer on hand, the thickness for the two most common types of cut are given. Whilst grinding, this will obviate the necessity of having to check the crystal for oscillation after each cycle of operation, providing, of course, that the blank is kept flat over each face. An AT cut crystal at 3,500 kc/s is approximately .019in. in thickness, while at 7,000 kc/s it will be near .0095in. ($t=66.2/f$). The BT cut crystal at 3,500 kc/s is about .0288in. and at 7,000 kc/s it is around .0144in. ($t=100.8/f$). By frequent checking with the micrometer, grinding may be carried out with confidence until the blank is within .0005in. of the final thickness over its entire area, when it should be inserted in its holder and checked in the oscillator after each grinding operation until the required frequency is arrived at.

During the process of grinding it may be found that the crystal will cease to oscillate. This is a fairly common occurrence, particularly in the case of higher frequency crystals. Several factors exercise their influence over this condition, the most common being that the blank has not been ground evenly and the face being ground may either be

concave or convex with respect to the reference side. Chipped edges or corners are also likely to cause a crystal to be inactive or to oscillate very weakly only.

A crystal will often refuse to oscillate, even if both sides are perfectly flat and parallel and the edges are free from chips or cracks, because an oscillating quartz crystal has, a definite relationship between its linear dimensions, and it is possible that if it has been ground down to any great extent it will have to have its dimensions reduced in proportion. This may be done by holding the blank between the thumb and forefinger, and grinding two adjacent, or all, edges until normal activity is restored.

Frequent trouble may be encountered with faulty electrodes. By the simple expedient of changing electrodes an otherwise dead crystal may be made to oscillate beautifully.

The height of the lands or raised corners on an electrode have a very marked effect on the performance of a crystal, and, to a certain degree, on the frequency. The frequency at 7 Mc/s may be increased by as much as 1 to 2 kc/s when a pair of electrodes having high lands are substituted for the original set.

Crystals having cracked or chipped edges or corners may be made to oscillate much better if the edges are cleaned up by edge grinding, and the corners rounded where cracked or broken. This operation will have a negligible effect on the crystal frequency and improve activity considerably.

Dirty crystals are a bad cause of trouble. They are best cleaned in warm, soapy water with a toothbrush, exercising due care in doing so, and rinsing in clean warm water before thoroughly drying and replacing in the holder.

Bevelling the edges of a crystal by holding it at an angle between 30 deg. and 60 deg. to the grinding plate will help in restoring activity if other methods fail, but will make the edges much more susceptible to chipping when replacing the crystal in its holder or when removing it.

Last, but not least, electrode pressure has also a somewhat critical effect on crystal operation, not only in regard to activity but also to the frequency. This point, therefore, must not be overlooked when attempting to make a crystal oscillate.

In conclusion, the writer hopes that this article may be of some practical value to those who lack sufficient knowledge of the art of crystal grinding and maintenance. These points have been learned through several years of grinding crystals for service and amateur application. There is no reason why any amateur cannot achieve results almost equal in quality to those commercially employed in the art, although this will only be possible with patience and practice.

Radio Engineer's Vest Pocket Book

3/6, or 4/- by post

from GEORGE NEWNES, LTD., Tower House,
Southampton Street, Strand, London, W.C.2.

An Insulation Tester

How to Make a Useful Accessory for Use at 500 to 7 Volts.

By J. G. PICOT

A FEW months ago the writer decided to devise some method of measuring insulation at different voltages met with in ordinary domestic receivers and to measure the insulations of everyday domestic electrical appliances.

The voltages decided upon were: 500v., 400v., 300v., 200v., 100v., 50v., 25v., 7v.

The indication is a 100 microamp F.S.D. meter and the max. resistance that can be measured at 500v., is 245 megohms (this gives a reading of two microamps)—after this, infinity.

The leakage current across switches, etc., is one microamp at 500 volts.

The Circuit

The power is obtained from 230 volt 50 c. mains and is fed via one amp. fuses into a 230v. to 250v. transformer (the writer used one half of a 250-0-250 the second half being O/C), feeding a metal rectifier in a voltage doubler circuit, the voltage doubler condensers being 1 μ F. 450 volt working.

The D.C. output is selected by means of one section of a double-bank, 10-way uniselector switch, Fig. 1 (Sw 1), and is then fed through a one-megohm variable resistor R., to the series resistor, which is again selected by a uniselector switch (Sw 2), ganged to the chain potentiometer switch. From here it passes through the meter, through the external load, back to the negative side of the supply.

The switch shown in Fig. 1 (Sw 4), is across the output terminals, and is closed to balance the meter with the variable resistor at F.S.D.

The selector switch is fitted with an aluminium disc, cut as shown in Fig. 2, so that the power toggle switch Sw 3 must be put in the off position before rotating the selector switch. This is a safeguard against arcing at switch contacts.

The writer successfully ganged together two 10-way uniselector switches by coupling the spindles and using longer bolts to lock the units together.

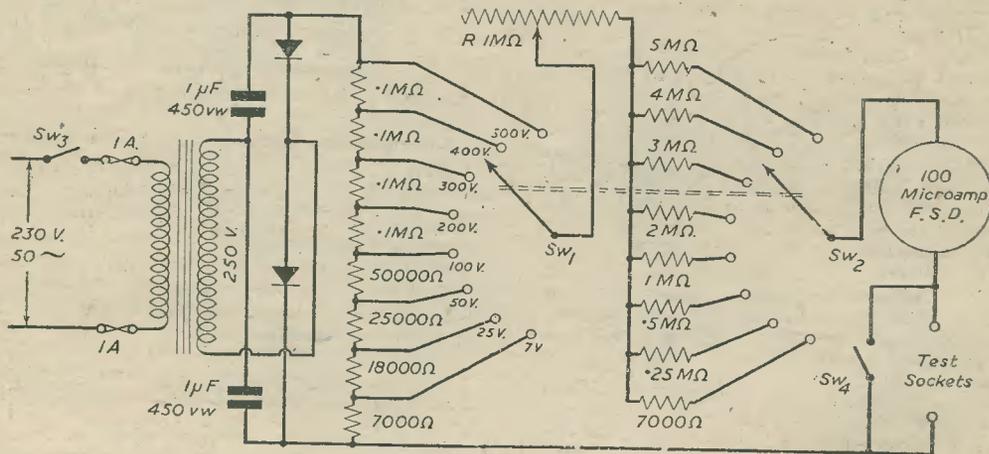


Fig 1.—Theoretical circuit of the tester.

A word of warning may be given here. Some constructors might be tempted to omit the transformer and feed straight from the line. This practice would work, and is sometimes used, but as one lead is in direct connection with the line via the bottom doubler condenser, there is the possibility of shock to the operator. Also, if one test lead is earthed, it is possible to blow the fuses.

The D.C. output is fed through a chain potentiometer tapped at each junction, and made up of the following resistors:

Four 100k., one 50k., one 25k., one 18k., one 7k., all $\frac{1}{2}$ watt, making a total of 500k. This network passes 1 mA at 500 volts.

Series Resistors

The series resistors were found to be rather critical and were made up in the following manner:

Eight pieces of heavy cardboard $\frac{1}{4}$ in. long by $\frac{1}{8}$ in. wide, drilled each end to take No. 6 B.A. bolts.

Coat one side of former $\frac{1}{8}$ in. from each end (see A, Fig. 3), using a soft graphite pencil, then cut 32 strips of aluminium $\frac{1}{8}$ in. wide $\frac{1}{8}$ in. long (electrical cable clips are ideal for this), drill these to take No. 6 B.A. bolts and bolt them on to the formers as tightly as possible. Next cramp the clips each side of the bolts in a vice to make sure of the graphite-to-metal connection.

Ohm's law will give the value needed and as high resistances cannot be measured accurately on the normal universal meters, it is better to get a high approximation of the value needed and then make the final adjustment in the instrument, for example,

$$R = \frac{E}{I} = \frac{500 \text{ volts}}{100 \text{ microamps}} = 5 \text{ megohms}$$

Connect each one in circuit and fill in with graphite pencil till the meter reads F.S.D. (see Fig. 3).

Using the Instrument

To use the instrument turn the variable resistor till maximum resistance is in circuit; select voltage required; place Sw 4 in closed position; switch on power Sw 3, and adjust meter to F.S.D. by varying the variable resistor.

Switch off power; return Sw 4 to O/C position; connect output leads to component to be measured, and switch on power. The meter will read X microamps, and by using Ohm's law the resistance in megohms can be found.

The operator must remember to subtract the series resistor from the answer, as this is in series with the external load:

$$R = \frac{E}{I} = \frac{500 \text{ volts}}{10 \text{ microamps}} = 50 \text{ megohms} - 5 \text{ megohms}$$

Answer = 45 megohms.

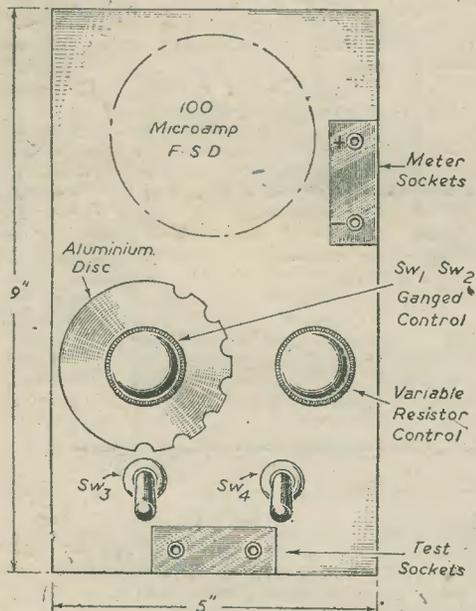


Fig. 2.—Constructional details of the tester.

The instrument is housed in a ply box 9in. long 5in. wide and 3in. deep.

The writer is using the 100 microamp range of a Western Analyser for the meter, plugging it into the circuit as shown in Fig. 2, but if one wishes to include a meter in the unit itself the modification would be quite easy.

Allowances would have to be made for the physical size of the meter in the construction (see Fig. 2).

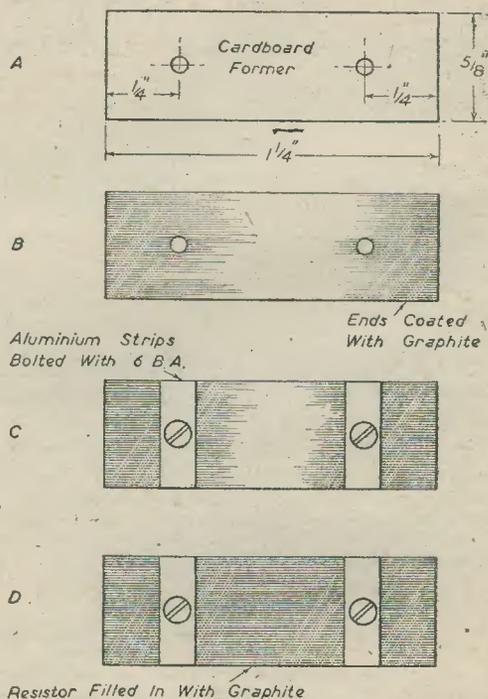


Fig. 3.—Method of making up the series resistors.

It is advisable before using the instrument to let it warm up for a minute or two with Sw 4 closed.

Condenser insulation with the working voltage applied should be 100 megohms per microfarad for mica types and 50 megohms per microfarad for paper types.

Long Distance Radio Communication

A BOOKLET issued to the Services during the war interpreted the results of observations of conditions in the ionosphere into instructions for procedure in operating the many and complex radio services required during the war. It has now been made more generally available to radio technical workers and students as "Radio Research Special Report No. 17—Fundamental Principles of Ionospheric Transmission," published for the D.S.I.R. by H.M.S.O., price 1s. 6d. (U.S.A. 55 cents.), by post 1s. 8d.

Throughout, the text is of a descriptive theoretical nature, but the use of mathematics has been kept to a minimum so that the treatment can be followed by as wide a circle as possible of those interested in this subject.



ON YOUR WAVELENGTH

By THERMION

Television Tie

A COLLEAGUE of mine, a keen television enthusiast, who has built his own television receiver, which is equal in performance to the best on the market, tells me that the visual programme has one drawback—you cannot turn your back on it, otherwise you have lost the continuity of the programme. With radio so many people carry on their conversation whilst the programme is in progress that I should have thought that the rapt attention necessary with television was a definite advantage. It has been the complaint of critics for years that so many people use a radio as a mere background and that they are not really paying attention to what is being said over the air. I checked this the other evening by asking two people carrying on a lively discussion on the advantages and disadvantages of Socialism in our time what programme they had been listening to and whether they could name any of the items or artists. They could not, and I pointed out that it was a sheer waste of electrical power.

A television programme is tantamount to a play at the theatre. When you go to a theatre you do not carry on an animated conversation with your companion. You listen to the show. I cannot understand, therefore, why people cannot do the same when watching the end of a television tube. It is the counterpart of the home cinematograph. You would be shown the door at a theatre or a cinema if you wished to converse during the run of the show.

My colleague tells me that the programmes have greatly improved in quality. There are fewer breakdowns, although interference from passing cars is still a source of annoyance in spite of the efforts which are being made to persuade motorists to fit suppressors. This problem will never be solved until suppression is made compulsory, and that time is not far distant.

Radio and the M.E. Exhibition

AS a model engineer myself, I take a keen interest in the Model Engineering Exhibitions held annually at the Horticultural Hall. I was present at the preview this year and, whilst I was, as always, impressed by the high quality of the models displayed and the ingenuity of the exhibitors, I was astonished to find so little there of a radio or electronic interest. I wonder why. A model of a transmitter, for example, should provide plenty of interest for the model engineer, and so would a model of a television receiver. It would seem that model engineers confine their interest entirely to mechanical matters and that electricity and electronics remain mysteries to them.

The Better Listening Campaign

THE article which appeared in the previous issue of this journal on the Better Listening

Campaign has produced a batch of interesting letters of which those I quote are typical. Mr. S. Tyser, of Acomb writes, "I was very interested in your Editorial in the current issue of 'P.W.' and the campaign for selling more sets. I think it is apparent that there is not the money about that there was 12 months ago, which suggests that the cost of current models is far too great to warrant a second set. Most makers produce a three wave-band job, and in the experience of my friends and myself rarely touch the S.W. band. For the ordinary person S.W. tuning is too critical and the 'ham' prefers a S.W. set. An examination of wavelengths shows that the medium band gives 'Home' and 'National' programmes together with a few useful foreigners. I therefore seriously suggest that sets with only the M.W. band (thus cutting costs) are likely to be suitable for sale as a second set. I refrain from making technical suggestions. From an interest point of view I may mention that I have one communication set (home designed), one domestic set (commercial), one portable and two others on the way. My first thought on reading your Editorial was to suggest the equivalent of the German People's set." And here is another letter from W. Watts of Watford: "I think we may call ourselves average listeners. I took out an experimental licence in 1921 and have bought many wireless sets in my time and made an even greater number. I think every licence holder should be given an opportunity, say, once every three years, to tell the B.B.C. his likes and dislikes. We have in our home a black list and, as their names are announced, we carefully switch off or over. (List of names enclosed.) A friend of ours who happened to observe our list a while ago said they quite agreed with it. I dislike dance bands and crooners, also announcers, talks, 'Twenty Questions' and plays connected with the war. There is room for another receiver in the home and in every bedroom, as you suggest."

The idea of a black list of radio bores is good, and I must instal one. Much better however to write to the B.B.C. and tell them the items you do not like. My reader's suggestion that the B.B.C. should conduct a plebiscite of its listeners every three years is also good, notwithstanding the fact that it has its own Listeners Research Bureau. I should like to know how that Bureau works. No one has ever asked me, nor any of my friends, questions concerning B.B.C. programmes.

WATCH YOUR DUSTBIN

Waste Paper, Cartons, Cardboard, should be kept separate, dry and clean for salvage.

Television Topics

How to Make Use of the B.B.C. Test Card "C" and Set Up New Receivers or Check Existing Ones

By W. J. DELANEY (G2FMY)

JUDGING from our correspondence quite a number of readers have built satisfactory television receivers, but cannot adjust them for the best results. Queries are often asked by readers who cannot gain access to commercial receivers—how to judge, for instance, whether the synch. separator is working satisfactorily. Every part of the modern television receiver can, however, be checked to a very high standard by means of the special test card which is radiated by the television transmitter every morning (except Sundays) from 10 to 11 a.m. The new card now in use is known as Test Card "C," and this transmission is stationary for the whole hour period. It is extremely difficult, of course, to try and make adjustments on a normal picture transmission, as not only are the figures and scenery moving, but light and shade are changing, and as soon as some adjustment is made to the equipment the scene may change, and it is not easy to see whether the desired effect has been obtained. On the other hand, the stationary geometrical pattern is constant and quite a lot can be done in one hour by way of adjustments or in making experiments.

Aspect Ratio

The first and most important part of the adjustment is the proportion between width and height. As most readers know this is called the "aspect ratio" and bears the relation 5 to 4; that is, for 5 units in a horizontal direction the height is 4 units. When, therefore, the "picture width" and "picture height" controls are correctly adjusted to the ratio 5:4, the concentric black and white circles in the centre of the pattern will appear truly circular. There is, of course, a circle in the centre of the standard tuning signal, but this is somewhat smaller and it may be possible to get a true circle here and find that the outsides are not correct. When making all adjustments on the test card, the height and width controls should be set so that the black and white border just fills the tube mask or viewing area. When the adjustments are correctly made it may be found desirable in some cases to readjust these two controls so that the mask is just outside the mask area.

Resolution and Band Width

To obtain ideal results, the band width accepted by the vision receiver and the effect of any high-note filters or similar circuit accessories should be such that every shade of detail in a white dress, stitch lines on a gentleman's black evening-dress, etc., are visible. To assist in ascertaining what width is obtained on the receiver there are two groups of frequency gratings inside the two circles just mentioned. These gratings have black and white alternating stripes (similar to those in the centre of the circle in the tuning signal, which, incidentally, represents 2.5 Mc/s).

The fundamental frequencies shown by the gratings on the test card are 1.0, 1.5, 2.0, 2.5 and 3.0 Mc/s. On the left-hand side the 1.0 Mc/s grating is at the top and on the right-hand side the order is reversed. To receive an ideal picture with the existing transmission response should be uniform up to 2.7 Mc/s and therefore it should be possible to separate the 3.0 Mc/s grating bars. Every endeavour should be made to receive the 2.5 Mc/s, and nothing less than this should be tolerated in a home-built receiver. When adjusting a receiver to separate these lines, make sure that no fictitious result is obtained due to "black after white," a form of misadjustment which gives "all black objects a white outline. The two concentric circles will assist in seeing that this is not taking place.

Contrast

The full range of tones from black to white are covered by a five-step wedge, which is in the centre of the card. The top square is white, corresponding to 100 per cent. modulation, and the lowest square is black, corresponding to 30 per cent. The three intermediate squares should range through pale, middle and dark grey.

Linearity

The background of the card is a middle grey and is ruled into squares. The vertical and horizontal lines should be equally spaced so that in every part of the picture the background is divided into equal squares. Line and frame linearity controls should be adjusted and modified, if necessary, to obtain this effect.

Synch. Separator

In some cases readers have wondered if picture impulses are getting into the time bases. The synch. separator is a tricky circuit and various schemes are used. The efficacy of the circuit may be judged by the black and white squared border and the two vertical lines at each side of the central circles. The border should not be jagged, and the two vertical lines should be without any kinks. These two lines are also an indication of the reception of reflected signals. There should be no positive or negative images at the right-hand side of the lines.

L.F. Response

The white rectangle, with a black rectangle inside it should, in an ideal system, be exactly reproduced as just described. There are, however, imperfections in the system as at present transmitted, and it will not be found possible to obtain a clear-cut black rectangle inside the white one. On the right-hand side of the black will be a slight streaking or shadow, so do not waste too much time trying

(Continued at foot of next page)

Mercury Vapour Rectifiers

The Care and Maintenance of ex-Service Valves

By E. G. BULLEY

WHEN hostilities ceased, surplus Government valves were released, at controlled rates, on the commercial market. Among these valves were mercury vapour rectifiers, and many of these valves have been purchased by radio amateurs who are not fully aware of the care and maintenance that they require.

Mercury vapour rectifiers, unlike the vacuum

drop, one finds that the voltage drop has increased. To avoid this increase, which will shorten the life of the valve, it is essential that the maximum peak anode current is not at any time exceeded.

Maximum Peak Anode Current

The maximum peak anode current is the highest instantaneous current that the rectifier can stand in the direction in which it is designed to pass current. It can be stated that it is also a function of the electron emission available.

To limit this, a protective fuse of suitable rating should be included in the rectifier anode circuit. The presence of this will not only safeguard the rectifier but also the power pack in which it is incorporated.

The filament potential in any mercury vapour rectifier is also an important factor, because, should the filament voltage be below normal, flashback or arcing will occur. This phenomenon is due to the breakdown of the mercury vapour, which results in conduction in the opposite direction to that which the rectifier is designed to pass current. It is essential, therefore, that when first installing mercury vapour rectifiers the filament voltage should be carefully checked to ensure that the correct voltage is being applied.

Another important point to remember is that the anode potential must always be delayed so as to enable the filament to reach its correct operating temperature and thus enable it to supply full emission. Failure to delay the anode voltage will result in the voltage drop becoming excessive, which in turn will cause ionic bombardment of the filament. This bombardment will, as mentioned previously in this article, destroy the emissive properties of the filament and result in the ultimate destruction of the valve.

Delay of the anode potential can be accomplished by automatic means, and this method is advised; by making a reference to the illustration the reader will appreciate the operation of such a circuit.


The delaying of the anode voltage can be effected by means of a vacuum delay switch type DLS10 incorporated in the primary side of the transformer. However, to appreciate the principle, it is necessary

(Concluded from page 410)

to obtain a clean white background. The shading is not very bad, but is definitely noticeable, and experience will show whether or not the low-frequency response of the receiver is normal.

Focus

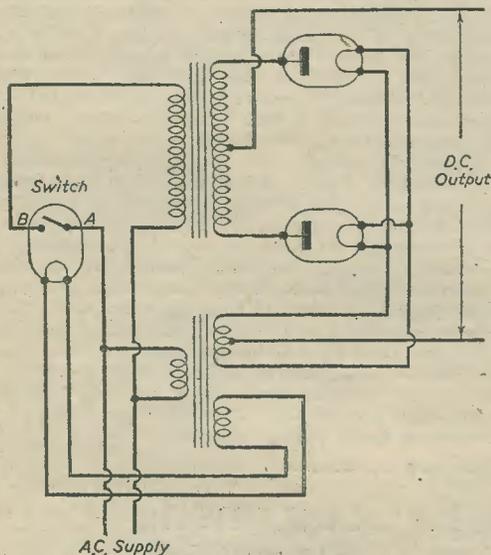Finally, to assist in ascertaining whether the focus coil is correctly positioned and the tube electrode structure in order, there are four diagonal areas of black and white in each corner. These correspond in frequency detail to 1.5 Mc/s and should, therefore, all be resolved uniformly with better clarity than the middle squares of the frequency gratings referred to earlier.



Rectifier Circuit with the inclusion of a Thermal Delay Switch.

type, depend entirely upon the current being carried by mercury ions which are produced by the electrons colliding with the molecules of mercury vapour that are present in the bulb. In actual operation, however, the bulb is filled with a blue glow which is in effect "created ionisation"; this is a characteristic of all mercury vapour rectifiers. This ionisation neutralises the space charge and so reduces the internal resistance of the valve.

Mercury vapour rectifiers have the characteristic of being able to carry fairly large currents, which is the result of the neutralisation of the space charge and also of the voltage drop being constant when the valve is operated up to maximum ratings.

The voltage drop across the rectifier should be carefully checked at frequent intervals, and so long as the low voltage drop is maintained (usually 15 volts), there is little danger of positive ion bombardment of the filament. However, if this bombardment does occur, the emissive properties of the filament will be damaged and the valve eventually destroyed.

Anticipation of the life of the rectifier can therefore be determined, if, when measuring the voltage

to give a brief description of the actual switch and the method by which it delays the anode voltage.

Vacuum Delay Switch

The switch consists of a small filament mounted upon a glass stem, and adjacent to a bimetal strip. Attached to this bimetal is a contact (A), which in turn is spaced a short distance from another fixed contact (B). When the filament has been alight for a specified period, the bimetal expands and in so doing it forces over contact A to "make" with contact B. This contact remains so long as the filament of the delay switch remains alight.

In the illustration, the reader will notice that the filament of the switch is switched on simultaneously with the filaments of the rectifier valves. Thus, when the bimetal strip is heated sufficiently by the radiated heat from the filament, it expands and thereby allows the H.T. to be applied to the rectifier anodes. The delay period is equal to the time the filament takes to heat the bimetal and so cause it to expand.

In the actual operation of this type of valve, it is essential that the valve be worked within the specified peak inverse voltage. Failure to do so will result in arcing back and will have a similar effect upon the valve as if the filament were operated at a lower voltage than that specified.

The maximum peak inverse voltage is the highest peak voltage that the rectifier will stand in the direction opposite to that in which it is designed to pass current.

Arcback can also result from the valve being operated within the specified peak inverse voltage but at a much higher ambient temperature. To prevent this, if the valve is to be operated at a higher ambient temperature, the peak inverse

voltage rating must be greatly reduced. This can be clarified by remembering that high condensed mercury temperatures reduce the voltage required for striking and at the same time reduce the peak inverse voltage rating, whereas low condensed mercury temperatures increase the striking voltage and cause cathodic sputtering. However, both these conditions are not favourable to filament life.

Avoiding Leakage

When first installing mercury vapour rectifiers, it is advisable to wipe the bulb clean of all dust or dirt; this will avoid any electrical leakage and so prevent local heating.

The next consideration is to run the rectifier with only the filament potential being applied; this should be of the order of 15 minutes, and by so doing, the mercury evaporates from any of the electrodes to which it had adhered. This will prevent excessive pressure being concentrated at the place at which it had adhered and thus avoid flashovers between the electrode structure.

By giving the filament a preheating period, it also removes the mercury that may have got splashed on to the interior of the bulb, which in turn would cause excessive heating of the bulb and so result in a higher ambient temperature.

Mercury vapour rectifiers should always be mounted vertically and in a well-ventilated position. They should be screened from any source of R.F. energy otherwise the life of the valve will be affected. It is as well to mention, however, that electrostatic and electromagnetic fields are detrimental to the mercury vapour rectifier, and if screening is adopted to protect the valve, adequate ventilation must also be provided.

New Standard S.H.F. Components

THE ever-widening use of the S.H.F. (Super High Frequency) section of the radio spectrum has created a demand for a range of standard components suitable for wavebands between 100 Mc/s (3 metres) and 10,000 Mc/s (3 cms.).

To meet this demand the Plessey Company, Ltd., Ilford, who have carried out considerable research in the S.H.F. region have introduced a range of connectors to cover a wide field of application. Although designed primarily for S.H.F. equipment, these connectors are ideally suited for use in frequency bands down to the V.H.F. region.

Standardisation of the design has been achieved in the company's own range, and by the incorporation of special mating features, no confusion can arise in interconnection between various S.H.F. devices; a problem ever present in previous designs.

The connections have been designed for 70-80 ohm coaxial lines and give very low reflection losses up to the highest frequencies; the limit being set by higher modes and discontinuity reflection. Female types have been designed for power outlets and male types for power inlets.

Two series of connectors, major and minor, are available, with each series consisting of four types. These are: free straight, free right angle, bulkhead mounting and panel mounting. Each type is

produced in both male and female versions. This, of course, ensures complete control of the matching of all S.H.F. devices. Facilities are provided for any type of coaxial waveguide transformation.

Male and female types are interchangeable, and to avoid confusion both inner and outer conductors of a particular connector assembly are both male or both female. To ensure correct mating and therefore matching continuity, all female connectors are provided with locking rings. These have a coarse diamond knurl, coloured black, to distinguish them from the finer knurl of actual connector assemblies.

Intercoupling between minor and major components is achieved by the introduction of major or minor adaptors, so designed to maintain the correct impedance of 70-80 ohms.

All connectors and adaptors are precision machined from brass and to ensure high conductivity have a burnish silver finish. Spacing dielectrics are made from Distrene.

The cable types of connector have a compression cone anchorage from the cable-conducting braiding while the inner conductor is arranged for solder connection. To avoid damage to the spacing dielectric the plug on the centre pin is readily removable and the spacers, being split and cone wedged, can if damaged be easily replaced.

GALPINS

ELECTRICAL STORES
408, HIGH STREET, LEWISHAM,
LONDON, S.E.13.

Telephone: Lee Green 0309.

Near Lewisham Hospital.

TERMS: CASH WITH ORDER. NO C.O.D.

EX - NAVAL (SELF - ENERGISED) TELEPHONE HANDSETS, 10/6 each, or complete Telephones, Magneto Ringing with Neon Light, 35/- each, post 2/6.

MAINS TRANSFORMERS (Auto Wound). Voltage Changers tapped 10, 20, 25, 90, 130, 150, 190, 210 and 230 volts, all at 1,000 watts, a combination of 34 voltages can be obtained from this transformer. New ex-Government Stock, **£5/10/0** each, carriage 5/-. Mains Booster Transformer, tapped 0, 6, 10, 19, 175, 200, 220, 225, 240 and 250 volts at 1,500 watts (new, ex-Government), **£5/10/0** each, carriage 5/-. Another 200 volts input, 240 volts output at 2,500 watts, **£7/10/0**, carriage 7/6. Another 2 to 1 ratio, 110 volts input, 220 volts output, or vice versa, at 4,000 watts, **£12/10/0**, carriage 10/-. Another 230 volts input, tapped output 40, 41, 42, 44, 46, 47, 49 and 52 volts at 100 amps., **£15/0/0** each, carriage 10/-. The latter two are double wound. Another Auto Wound, tapped 0, 110, 150, 190, 210 and 230 volts at 1,500 watts, **£6/10/0** each, carriage 5/-. Ditto, 2,000 watts, **£7/5/0**, carriage 5/-.
MAINS TRANSFORMERS, EX-GOVT. All 50 cycles input. 230 volts, input 500/0/500 volts at 250 mamps. L.T. 5 v. 3 a. **37/6** each, carriage 3/6. Another 50 volts at 30 amps. output, 75/- each, carriage 6/-. Another two L.T. windings, 6½ volts at 10 amps., **27/6** each. Another 230 volts input, 700 volts at 150 mamps., 4 v. 2 a., 4 v. 1 a. output, **27/6** each, carriage 3/6. Another 700/0/700 volts, 80 ma., 12 v. 1 a., 4 v. 2 a. output, **30/-** each.

MAINS TRANSFORMERS (NEW). Input 200/250 volts 50 cys. 1-ph., output 350/0/350 volt at 180 mamps. 4 v. 4 a. C.T. 6.3 v. 4 a. C.T. 5 v. 3 a., **37/6** each, post 1/6; ditto, 500/0/500 v. 150 mamps. 4 v. 4 a. C.T. 6.3 v. 4 a. C.T. 5 v. 3 a., **47/6** each, post 1/6; another tapped 6, 12 and 24 volts at 10/12 amps., **45/-** each, post 1/6. Auto wound Voltage Changer Transformers, tapped 0, 110, 200, 220, and 240 volts 250 watts, **45/-**; 350 watts, **55/-**; 500 watts, **70/-** each, carriage 1/6. (Please note, these Transformers can be delivered, 10 days from receipt of order.)

EX-GOVERNMENT (G.E.C.) ELECTRIC FANS, 12 volts, A.C./D.C. laminated field, complete with 5-in. impeller. New, boxed, **20/-** each, post 1/-. Transformer to suit, 230 volts, input, 12/16 volts at 4 amps. output, **32/6** each.

MAINS VARIABLE RESISTANCES (slider type), new, ex-Govt., 14 ohms, carry 1 to 4 amps., graduated, useful as dimmers, etc., **25/-** each; another, 0.4 ohms, carry 25 amps., **25/-** each, post 1/6. Ex-Govt. Moving-coil Cell Testers, 3-0-3 volts (new), **25/-** each. Ex-Govt. (G.P.O.) Pattern Handsets, combined microphone, earphone, black bakelite, 10/6 each, post 1/-.
EX-GOVERNMENT (NEW) MAINS TRANSFORMERS, 200/250 volts, 50 cycles, 1-phase input, 525/0/525 volts, 150 mamps., 6.3 volts, 5 amps. 5 volts, 3 amps. output, standard rating, 35/- each, post 2/-. Mains Smoothing Chokes, 10 hy. 150 mamps., 180 ohms D.C. Res., **8/6**. Ditto, 100 mamps., 5/6 each, post 9d. All the above can be offered in large quantities. Please write for special quotation.

EX-R.A.F. ROTARY CONVERTORS. 12 volts D.C. Input 220 volts A.C. 50 cycles at 100 watts output, condition as new, **85/-** each.



Webb's Radio Map of the World

INDISPENSABLE FOR THE RADIO 'SHACK'

Shows the true directivity of any place in the world and gives amateur radio international prefixes, also indicates the time of day for the world. Originally printed in 1936, many thousands of radio men have proved its use time and time again.

We now have a NEW 1948 PRINTING

with revised and up-to-date Call Signs prefixes, coded to Country and time-Zones, combined with improved printing in multi-colours. Printed in full colours on heavy white paper, size 4oin. x 3oin., price 4/6, plus 6d. postage. (Also on heavy linen rollers, price 11/6, plus 9d. postage.)

This Map is drawn on an azimuthal projection and looks strange to those accustomed to Mercator's projection, but, giving directivity and Great Circle distances, it performs many functions for radio men that the ordinary map cannot do. Printed on the margin is an index to Call Signs and full explanation of use of time-zones and "Great Circle" projection.

14, SOHO ST., OXFORD ST. LONDON, W.1. Telephone: GERrard 2089

Note our SHOP HOURS: 9 a.m. to 5.30 p.m. Sat. 9 a.m. to 1 p.m.

-BULLS 32L7-

Replacement with Instructions

BRIMAR.—R2, R3, 5Y3, 5U4, 80, 8Z3, 5Z4, 6X5, 5V4, 1D5, 25Z4, 1D6, 0Z4, 35Z4, 15D1, 15D2, 9D2, 8D2, 10D1, 11D3, 11D5, 7D5, 4D1.

COSSOR.—442BU, 43TU, 4THA, 41STH, MVSPenB, MSPen, MSPenB, DDL4, DDT, 4M1TL, 4M1HL, 41MP, MPPen, PT41, 2P, 41MXP, 202STH, 13VPA, 18SPA, 202DDT, 210VPA, 210HF, 210DDT, 215P, 240CP, 215SG, 210LF, 4TSP, 4TSA, 202VFB, OM4, OM6.

MARCONIOSRAM.—U10, U14, MU14, U18/20, U50, U52, U31, U74, U76, X41, VMP4C, M54B, MSP4, KTZ41, D41, MH4, MH4, M4, MKT4, KT41, PX4, DA30, VMS4B, M30, XG3, X65, KTW63, KTZ63, KTW61, D63, H63, L63, DH83, DL63, KT63, KT66, KT61, X63, KX71, X81M, KX74, XG3, KT33C, X24, Z22, HD24, L2P, K2P, E2P, GP21, Z14, N16, D42, U16, U17, GT1C, GU50, KT44.

MAZDA.—U05, AC7H1, V914, ACP, AC5PenDD, HL41, HL41DD, VP41, P41, T41, DD41, HL42DD, VP1322, PenDD4020, TH321, VP133, Pen453DD, HL133DD, QP230, TP23, Pen 25, QP25, TP25, TP25, DD207, HL23, HL23DD, VP23, SF2220, SF42, U22.

MULLARD.—DW2, DW4 350, IW4 350, DW4 500, IW4 500, AW1 500, AZ1, AZ21, UR3C, TH4B, FC4, VP4, V4B, VB4, Z4A, TDD4, 354V, TT4, PM24M, PenDD, PenB4, AC044, D04, Pen428, TH21C, TH30C, VP13A, SP13, Pen36C, CL4, Pen40DD, CCH35, DAF2, D31, D39, D31, D31, D31, EA50, EBC3, EBC3, EBC31, ECC31, DL32, ECH33, ECH35, EF9, EF22, EF36, EF37, EF39, EF50, EF54, EK32, EL2, EL6, EL32, EL43, EL35, EL37, EL38, EM1, EM4, EM34, VP2B, SP2, VP13K, FC2, FC2A, DK32, DAC32, CL33, CBL1, CBL1, EBL21, UBL21.

PHILIPS.—1821, CY31, C1C, C1, CYL.

TUNGSRAM.—1D210, LP220, LL4, APPAC, APP4C, APV4, BZ4, 2A6, 2A7, 2B7, 6A7, 6B8, 6C8, 6D8, VP13K, P35, HL13, 6AC7, 12C8, 25YG, 25X5, HF4106, HP1016, HP4101.

HIVAC.—XL, XD, XY, XP, XSG, XH.

AMERICAN.—0Z4, 1A4, 1A5, 1B5, 1D7, 1LN5, 1LC8, 155, 1T4, 1T5, 1V, 2A3, 2X2, 2A6, 2A7, 2B7, 3A3, 354, 305, 5U4, 5V4, 5Y3, 5Z3, 5Z4, 6A3, 6A7, 6A8, 6AB7, 6AC7, 6AD5, 6AB26, 6B7, 6B8, 6C4, 6C5, 6C6, 6C8, 6D3, 6D8, 6D9, 6E6, 6F6, 6F8, 6C6, 6H6, 6J5, 6J5, 6K5, 6K6, 6S27, 6S47, 6S7, 6X3, 7A7, 7H7, 7B6, 10, 12A5, 12A6, 12C7, 12B5, 12K7, 12BK, 12Q7, 12SA7, 12SF5, 12SK7, 12SL7, 12SQ7, 12SR7, 14A7, 14B7, 14B6, 14Q7, 15, 17, 18, 20, 22, 25Z4, 26, 27, 32, 34, 35A5, 35L6, 35Z4, 35Z5, 37, 38, 41, 32, 43, 45, 49, 49, 50, 53, 55, 56, 59, 71A, 76, 77, 78, 79, 80, 83, 84, 89, 89A, 89A, 895, 956, 9001, 9002, 9003, 9004, 9005, 9006, and 101 more types.

JUST IN.—1A5, 1A7, 1E5, 1F7, 1G6, 1H4, 1H5, 1J6, 1N5, 1S4, 6A6, 6N6, 12S7, 25L6, 25Z6, 33, 4Z5, 85, 83Z-EBL1, EBL1, Pn 353, Pm 2A, PP13A, (D78, N30), PP3-250, PX23, X76M, U403, UR1C.


Order C.O.D. above listed numbers or equivalents (subject to stock). Please enquire for any valve you require, even if not listed. We may have it. Old and new types are arriving daily.

THIS MONTH'S SPECIAL OFFER.—Potentiometers, 10,000 ohms, wirewound, 2/-; Soldering Irons, heavy duty, on/off switch, 230/250 v., 18/9; 8in. Speakers, with Transl. 30/-; Speaker Fabric, 1sq. ft., 3/6; Service Sheets (our selection), 10/-; Pencil Soldering Iron, new Model, 10/6; Sleeving, per yard, 3d; Television: Bairds new Model, "The Lyric."

STOP PRESS.—Microphone stand with switch plus headphones (send and receiver unit), 11/-, two (21/-). Will provide home intercommunication, no batteries required. Electric mixer, and whisk with three attachments, 30/10. Aerial, 7 extensions, 14ft., collapsible, 7/6. Aerialite television magnifiers, **£8/16/6**. Easy terms on all Taylor Instruments.



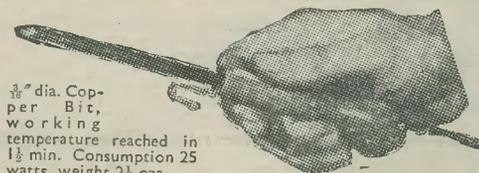The "ADCOLA" Soldering Instrument
Designed for Wireless Assembly and Maintenance



$\frac{3}{16}$ dia. Copper Bit, working temperature reached in 1½ min. Consumption 25 watts, weight 2½ ozs.

Supplied in voltage ranges from 67v to 230.250v.

Price 22/6d. each. British and Foreign patents pending.

Sole manufacturers: **ADCOLA PRODUCTS LIMITED**, Alliance House, Caxton Street, London, S.W.1. Tel: WHI. 0030

MIDCO RADIO

COIL PACKS, Standard L. M. S. Silver, S.S. S. S. M., 33/-, or with RF stage, 50/-. 160 PF tuned all S.W. pack, 10-100 m., 33/-. Any type of coil pack can be built to specification.

DIALS, super modern types now available, horizontal type, 10in. x 4½in., calibrated in station names, frequencies and wave lengths. The dial for that super set complete on sub chassis, 22/6. Square type dial, clear calibrations, with station names, complete with drum drive pointer, etc., 7/6.

MAINS TRANSFORMER, new type, completely shrouded, 350/80 m.a., 6 and 5 v., 24/6.

SUNDRIES. Coils for 10-2,000 m., 2/9. Perm. tuned IF transformers, high "Q," small size, 14/6 pr. Special fitted octal vholders, etc., 12/6. Steel chassis as used in the MIDCO. Special prices for complete assemblies. Write for our new lists, 3d. stamp only. Trade Supplied. C.O.D. any value. Post paid on orders over £1.

MIDLAND RADIO COIL PRODUCTS
19, Newcomen Road, Wellingborough

METEOR 2 WAVE COILS.

TRF & SUPERHET

1B2T and 1B2S

1/1 TYPE FOR NEW MIDGET 375 PF TUNING CONDENSER

Price :- 7/6 Pair



METEOR ELECTRONICS

Gloucester Row, Weymouth.

M. & J. PEARSON, 373, Eglinton St., Glasgow, C.5.

Special Offer

RECEIVERS

R.11.55A Limited number only, good condition, 29 each, carr. paid, P.58 Naval receiver, 13 valves, superhet with power pack, running range 280-650 megcs. Complete in packing case, £7/10/- each. B.C. 455 - 6 valves superhet, 6-9 megcs., £2/10/- ea., carr. paid. R.11.32A, 7 valve superhet, tuning range 100-125 megcs. Good condition, £4/10/- each, carr. paid.

ELECTROLYTICS

4 mfd., 450 volt, metal, 25 mfd., 25 volt, cardboard, 75 mfd., 50 volt, Bakelite, all 10/- half dozen : £4/10s. half gross, £8 per gross. These will be mixed as ordered.

TUBULAR—1 350 volt, 5/- doz., 20/- per half gross, 35/- per gross; 1 mfd., 1,000 volt, 9/- doz.; .25 mfd., 350 volt, 5/- doz.; .1 mfd., 450 volt, 8/6 doz.

METERS

FERRANTI—0-500 - microammeters, grade 1, moving coil, 2½in. flush mounting, new and boxed, 16/6 each. 0-100 microammeters, 2½in. flush mounting, calibrated 0-1,500 vds., new and boxed, 20/- each. 0-300 volts A.C., 2½in. flush moving iron type, new and boxed, 8/6 each.

TERMS: We pay all Carriage (Gt. Britain only) and Cash With Order Please. No Lists issued.

COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925

NOW READY

1948/9 RADIO COMPONENT CATALOGUE

DETAILS OF THOUSANDS OF RADIO & TELEVISION COMPONENTS FROM A WASHER TO COMPLETE TEST GEAR. ALL CONSTRUCTORS, EXPERIMENTERS, SERVICE ENGINEERS, DEALERS & MANUFACTURERS SHOULD SEND FOR THE MOST COMPREHENSIVE CATALOGUE PUBLISHED TODAY. SEND 3d. IN STAMPS.

COVENTRY RADIO
DUNSTABLE ROAD, LUTON. Phone : Luton 2677

VALUE! MATT has it

Order with confidence. Full satisfaction assured.

SPECIAL OFFERS

HEADPHONES.—Wlead and Jack Plug, 3/11 pair (Boxed 2 pairs), 42/- doz. pairs.
LINE CORD.—3 amp. 60 ohms, per ft. 2-way, 1/6 yd., 3-way, 2/- yd.
TUNING CONDENSERS.—0005 Polar Midget, 11/6; .0005 Standard 5/6. MIDGET I.P. TRANS., 465 kc/s, 16/- pair.
CONDENSERS.—002 2/6 doz.; .006 3/- doz.; .1 .01, 9/- doz.; 16 mfd./500v. canned, 8/6; 8 mfd./350v. midgets, 3/-; 8 mfd./450v. 4/-; 4+4 block, 3/-.
SPEAKERS.—P.M. (less trans.), 5in., 12/6; 6in., 24/-; Limited quantity 8in. TRUVOX P.M. SPEAKERS, 16/6. Trans. to match, 5/8. Multi Ratio Do., 7/6.
VOL. CONTROLS.—All values (Centralab), L/S, 3/6. W/S, 4/9.

Postage extra.

Let us have your enquiries for all Radio Components. Competitive prices.

MATT RADIO SERVICE
Kingston 8353

29, Castle Street, Kingston-on-Thames, Surrey.

THESE ARE IN STOCK

- Brimar Radio Valve Manual, 1947-8. 2s. 6d. Postage 3d.
- Amateur Radio Valve Technique. 3s. 6d. Postage 2d.
- Radio Circuits, by W. E. Miller. 3s. 6d. Postage 3d.
- Television Receiving Equipment, by W. T. Cocking. 12s. 6d. Postage 4d.
- Television Receiver Construction—Ten Articles from W.W. 2s. 6d. Postage 2d.

We have the finest stock of British and American radio books. Complete list on application.

THE MODERN BOOK CO.
(Dept. P.8), 19-23, Praed Street, London, W.2

H.A.C.

Short-Wave Equipment

Noted for over 15 years for Short-Wave Receivers and Kits of quality

One Valve Kit, Model "C" .. Price 20/-
Two " " " " "E" .. " 43/-

These kits are complete with all components, accessories, and full instructions.

Before ordering send stamped, addressed envelope for descriptive catalogue.

Note new sole address:—

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. TH) 66 New Bond Street, London, W.1

Receiver Remote Control

A Simple Mechanical Multi-point Switching Arrangement

By F. F. TOWNDROW (Assoc.I.E.E.)

THE use of an extension speaker or speakers is now more or less an accepted convenience in many homes to-day, but the problem so often arises how to operate easily and cheaply the switching on and off of the set from these extension positions.

relay was constructed from the remaining retailers' stock of Meccano parts in the early war years, and the enclosed mercury switch (to control up to three amps) was obtained from one of the makers of this

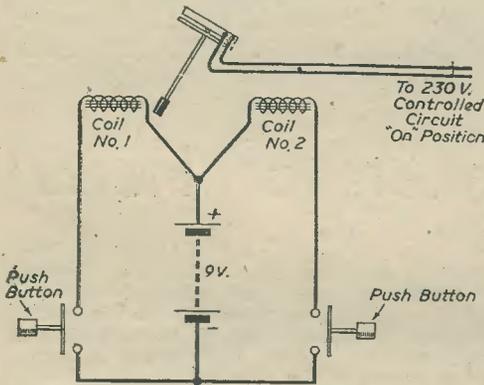


Fig. 1.—Basic Circuit of the relay.

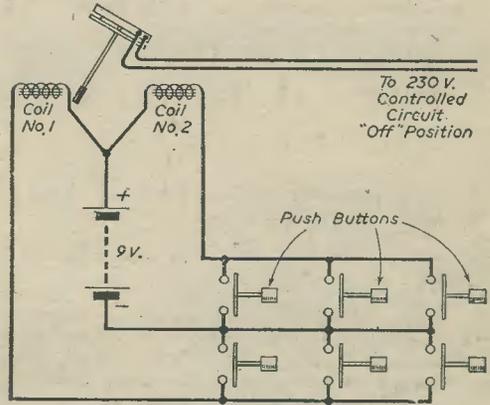


Fig. 2.—Actual Circuit showing the method of including additional push-buttons.

The relay and circuit, etc., described, has been in operation for several years, during which time the writer has only had to renew the two 4.5 volt standard flat torch cells every 12 months.

These renewals of cells could be obviated by the use of a small capacity 230-9 volt transformer of the bell type, but, taking into consideration the very intermittent demand of 100 mA during the operation of the on-and-off pushes, it does not appear to warrant the continual use of the energising current of the transformer.

The Circuit

The simple circuit of the relay is shown in Fig. 1, which is the wiring for energising of the two horizontally opposed ex-bell indicator coils on the low-voltage side (9v.), and the gravity operated mercury switch on the high-voltage side (230v.).

The relay which is adjacent to the set can be operated from any number of selected positions in the house (in the case of the writer this is the kitchen, dining-room, lounge and two bedrooms, which comprise a circuit length of approximately 40ft. from the relay to the most distant push-button position).

To prevent excessive voltage drop, standard two-core with earth 3/029 C.T.S. house wiring cable was used, utilising the earth wire for the common return conductor, this cable being taken to the end push-button position with the remaining push-buttons connected from it at various room positions. The

type of switch, the coils being obtained from an early pattern type of bell indicator, connectors, terminals, etc., obtained from usual workshop oddments box.

Operation

The operation of the relay is as follows: on the pressing of the "on" push-button (red) No. 1 coil is energised and attracts the armature attached to the mercury switch, this tilting the switch to a position where the mercury covers the two internal contacts. It is held in this position by weight of the mercury. On pressing the "off" button (black) the armature is attracted to No. 2 coil, when the

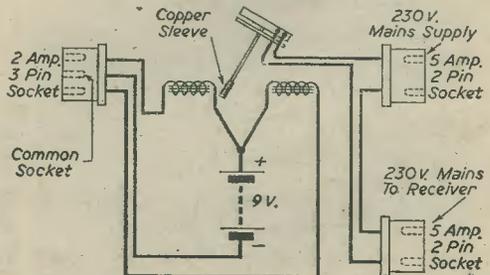


Fig. 3.—Wiring with interconnecting power plugs.

switch will be returned to its original position. It was found advisable to fit a copper sleeve over the lower part of the armature to prevent residual magnetism and sticking to the iron core of the coils.

The whole of the relay, etc., is enclosed in a small wooden case with a sliding lid for inspection and renewal of cells, all H.V. connections being connected to five-amp two-pin sockets and L.V. connections to three-pin two-amp sockets. An additional refinement was made in the form of a small double-push control, connected with light-class flexible wire to a three-pin two-amp plug, which could be plugged into sockets to enable the relay to be operated from either the dining-room table or the armchair in the lounge.

Note: The volume control on the set is always left in the "full-on" position, the speakers being adjusted for their respective volume by their independent resistance controls.

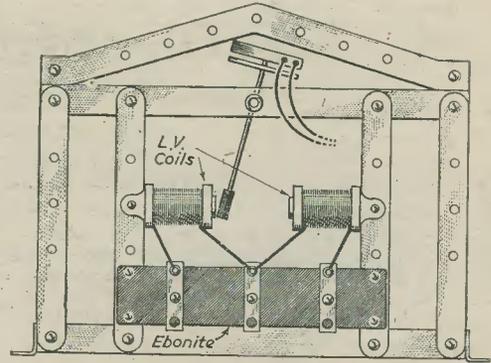



Fig. 4.—Relay (Showing L.V. Coils and connections)

Supersonic Detection of Flaws

A New Device Using the C.R. Tube

THE detection of flaws in metals—without having to destroy the work during testing—has long been a subject of both interest and importance. In this sphere the use of X-rays has played a prominent part. Recently, however, compact and portable equipment has been evolved which makes use of a cathode-ray tube. An example of equipment making use of a cathode-ray tube for the detection of faults in metals is the supersonic flaw detector evolved by Henry Hughes and Son, Ltd., their model 2B being seen below. In this apparatus two small searching units,

or probes—which are connected to the equipment by flexible screened and armoured leads—are applied by hand, and usually in close proximity to each other, to the surface of the material under test. Across the C.R. tube screen appears a luminous straight line, along the length of which can be observed certain sharp deflections. From these deflections and their relative positions the presence and depth of a flaw in the area of the material under examination can be deduced. Probes have a contact surface of about $\frac{1}{16}$ in. in diameter and, provided the surface explored is reasonably smooth, it need not be machined or otherwise specially prepared. Oil is commonly used to improve surface contact. Surfaces having a radius of curvature of less than 5 in. require to be explored with special curved probes.

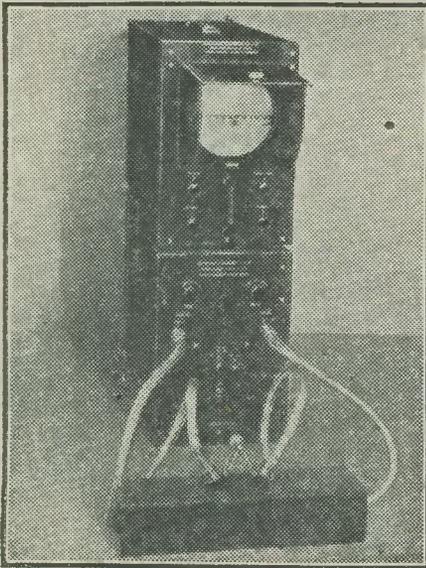

The Hughes Supersonic Detector.

Principle of Operation

In operation, one of the two probes acts as a transmitter and, when applied to the surface it is required to explore, directs into the material a narrow beam of supersonic energy. The other probe acts as the receiver for energy reflected from any flaws in the path of the beam and from the opposite boundary of the material. The sharp deflections of the luminous image on the screen of the cathode-ray tube correspond to the point of entry of the beam into the material. This point is called the transmission mark. The point of reflection of part of the beam from a flaw is the flaw mark, while the point of reflection of the beam from the boundary of the material is the bottom mark. The magnitude of the flaw can be gauged from the size of the deflection of the flaw mark, whilst its location can be deduced from the position of the probes on the surface and from the depth of the flaw below the surface. This depth is accurately determined by the relative distances between the transmission mark, the flaw mark and the bottom mark, as measured on the scale attached to the screen.

Practical Hints

Bandset Selector Switch


THE accompanying diagram more or less is self-explanatory, but a couple of points are worthy of note.

First, the Yaxley switchgear is the type that uses a standard 1/2 in. spindle instead of the flat bar type.

The one I have in use was obtained from Government surplus gear, and after stripping off the switch wafers, etc., was ideal for the job, giving nine bandset positions to 180 deg. track of condenser vanes.

The second point covers choice of bandspread condenser, one with a capacity suitable to give complete coverage between bandset positions is an advantage.

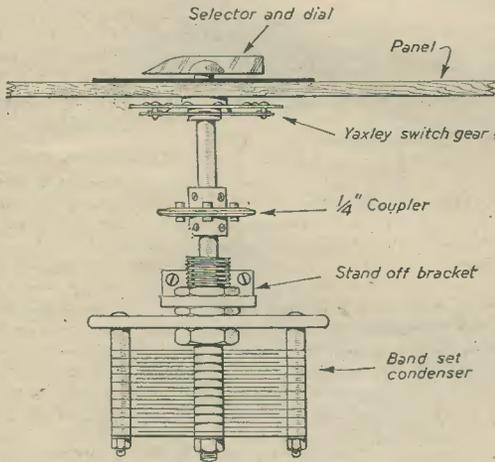Adjustments for any band can easily be made



A novel bandset idea.

by loosening off the coupler and setting the bandset to required band. When this has been done the bandset can be relocked to the switchgear by tightening up the coupler.—J. ENTWISTLE (Darwen, Lancs).

Useful Pendant Suspension

LIKE many others, I suspend my electric pendants on wires over the work bench.

It became necessary to find a method whereby these could be raised and lowered and left to "stay put" without elaborate balance weights or expensive fittings.

I accordingly bent a piece of 16-gauge copper wire as shown, threaded the flex through without removing shade or holder by sliding it sideways into the loops and then squeezing the latter together.


A gentle pull on loop will allow the flex to

be slid up or down and the greater the weight at the lamp end the more firmly it is retained at whatever height one leaves it.—JAMES D. BURGE (Birkenhead).

Improved Test Meter

AT times it is found that a suitable test meter is not available, and it should be pointed out that certain makeshift tests can be carried out, and the following ideas will give an idea of the lines which may be adopted. A standard voltmeter

of the pocket-watch type may be used as a continuity or current tester if connected in series with a circuit. The exact range to be used (in the case of a dual-range or similar meter) will have to be carefully chosen. It may be possible to calibrate a meter used under such conditions. Similarly, a standard meter reading, say, up to 1 mA may be used with a 1.5 volt cell in series to check circuit continuity, bearing in mind that if the circuit resistance is likely to be very low a resistance of about 1,000 ohms should also be included in series to avoid damaging the meter. Once the main idea has been grasped quite a number of improvisations of this type may be made.—G. WALDE (N.W.9).

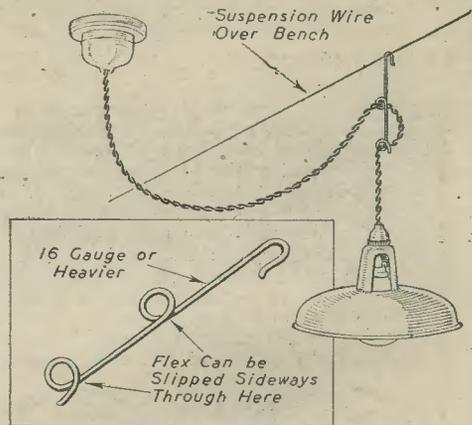

A useful device for the workshop.

THAT DODGE OF YOURS!

Every Reader of "PRACTICAL WIRELESS" must have originated some little dodge which would interest other readers. Why not pass it on to us? We pay half-a-guinea for every hint published on this page. Turn that idea of yours to account by sending it in to us addressed to the Editor, "PRACTICAL WIRELESS," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Put your name and address on every item. Please note that every notion sent in must be original. Mark envelopes "Practical Hints."

SPECIAL NOTICE

All hints must be accompanied by the coupon cut from page iii of cover.

MASTERING MORSE

By the Editor of "Practical Wireless"

3rd Edition.

1/-, or 1/2 by post, from George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

TO commence an article with the adjoined title may seem rather ambitious when we consider that the C.R.O. can be applied to any problem that can be made to provide a voltage in relation to some other axis, which may be time, frequency, etc. These problems may vary from hum tracing in a radio receiver to the tracing of algebraic curves on the C.R.O. screen.

To clarify the meaning of the heading, let us look into the uses of the C.R.O. with regard to problems relating to the practical radio engineer and the amateur transmitter. This narrows down the field a little, but even so the possibilities are tremendous, depending for the most part on the ingenuity of the user.

At the present day, due for the most part to the low cost of ex-Service gear, there is a considerable amount of information in the technical press regarding the construction of basic oscilloscopes, suitable amplifiers, time bases and "wobbly" oscillators for visual alignment. This is all very well in its way, but the average user of such equipment does not always know exactly what is being observed, even if the connections to the gear under test and the C.R.O. are correct. The result is that if a fault is present it always shows up on the oscillograph screen, and the user is at a loss to diagnose the cause. The old adage, "A little knowledge is a dangerous thing," applies here, as the user may think he is observing one phenomena when other conditions are present which completely alter the trace. The result is disillusionment and, eventually, chaos.

This article will try to remedy this, and at the same time provide food for thought on how to obtain a solution to your own particular problem.

Equipment Necessary

Assuming a basic C.R.O., i.e., tube and power supply, a time base which is linear from about 10 c.p.s. to 10,000 c.p.s. will be needed, together with an amplifier linear from at least 10 cycles to 10,000 cycles and preferably extending to 500 kc/s or even 2 Mc/s. A single stage amplifier will be sufficient for most observations, but if possible both X and Y plates should be push-pull fed so as to minimise distortion. It should be noted that a well-known manufacturer produces a 4½ in. C.R. tube that is free from nearly all forms of distortion, and in addition it has a double beam. The advantage of this cannot be stressed too highly, as it enables the user to observe with accuracy two

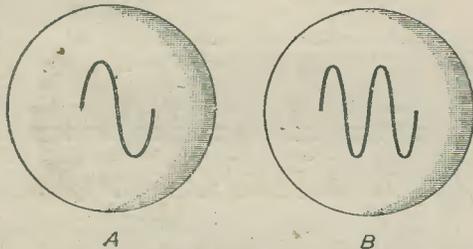


Fig. 2.—A, single cycle, and at B the result of halving the frequency.

Using the Osc

The Cathode Ray Instrument

By H. R. McDE

independent effects that occur simultaneously. Also P-P deflection is not required for good results. The go-ahead experimenter should purchase one; he will never regret it!

Fundamental Operation

To gain proficiency in the operating procedure used for the oscillograph, connect up the circuit shown in Fig. 1, this supplying about 40 v. A.C. to the vertical plates—no amplifier being needed. If a suitable mains isolating transformer is available, the condensers may be dispensed with and the circuit will not be alive with regard to the mains—a good point! With the time base switched off, a vertical line will appear on the screen. The focus and brilliance controls are then adjusted to suitable positions.

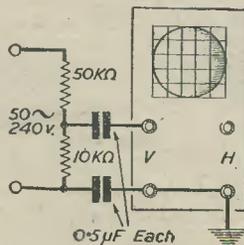


Fig. 1.—An elementary hook-up to give an idea of the operating procedure of the 'scope.

This vertical line is directly proportional to the applied E.M.F., i.e., if it is 4 cms. long and the voltage applied is 40 v., then 1 cm. represents 10 volts. Similarly, a trace of 6 cms. length indicates 60 volts. It should be noted here that the results are almost independent of frequency, R.F. potentials being measured just as easily as audio and supply voltages. From the previous few lines it will have been noted that a ruled transparent scale placed in front of the tube screen is a distinct advantage for quick reading of voltages.

If we now switch on the time base and set its frequency at 50 cycles, the vertical line is drawn out to the single trace as Fig. 2A. Suppose we now lower the T.B. frequency to 25 cycles, the trace then consists of two complete waves similar to Fig. 2B. If the T.B. frequency is lowered further still, three whole waves will appear, the frequency being 50/3 cycles, which is 16.67 cycles per second. If the frequency of the wave being examined was 400 cycles, a T.B. frequency of 100 c.p.s. would produce 400/100, i.e., four whole waves on the screen. The pattern will be stationary if the synchronising terminal is connected to the vertical input. A little experimenting with the mains and/or an audio oscillator will soon enable the user to proceed to more serious investigations.

Oscilloscope-1

ment and Its Applications.
MADERMOTT

Signal Source

In many of the operations to be described a pure source of audio energy is required. A fixed frequency is not objectionable as long as it is a pure sine wave, free from any trace of distortion. It is obvious that if we are to attempt to trace distortion by normal methods then it is essential that the input potential be free from such distortion. Very few of the normal servicing signal generators with provision for an audio output will be found to have a pure sine wave modulating tone. Because of this, it has been thought necessary to give a

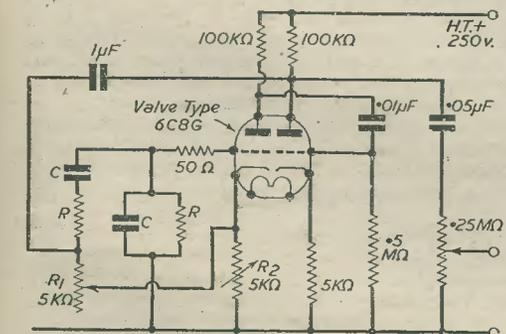


Fig. 3.—A Wien oscillator circuit.

brief description of a suitable oscillator. It will, in any case, prove of great use in the amateur shack.

The circuit consists of a Wien bridge oscillator using a double triode with feed back. The ex-Government valve 6SN7 could be used, but care should be taken in the values of the bias resistors chosen, as the performance may suffer. If satisfactory results are not obtained, measure the bias resistors as they are often well away from their stated value. Below are given two sets of R-C values for frequencies of 400 and 1,000 cycles.

400 c.p.s.	R-200,000	C-0.002
1,000 c.p.s.	R-160,000	C-0.001

The C.R.O. now makes itself useful in the calibration of the oscillator. We will consider the frequency of the latter to be nearly 400 cycles. The oscillator is switched on and allowed a few minutes to attain working temperature. During this period the time base is set to 100 c.p.s. This may be done by using the A.C. mains as previously described and adjusting the time base control until the pattern of Fig. 4A appears on the screen. The T.B. is then operating at 100 c.p.s.

The next step is to feed the oscillator into the vertical input of the C.R.O., apply synch., and vary R1 until a stationary pattern consisting of four whole waves, similar to Fig. 4B, is seen on the tube screen.

To achieve this it may be necessary to vary R2 slightly. It should, however, be kept as near maximum resistance as possible; for if it is lowered too far the valve will be overloaded and a far from pure output will result. If, even after adjusting R2, it is found impossible to obtain the required pattern on the screen, the values of R and C in the bridge circuit should be examined; it is probable that they are not quite correct. To assist this, a small trimmer may be placed in parallel with each of the bridge condensers or the resistors may be changed. When these adjustments are completed, i.e., four waves appear on the screen, the oscillator is working at 400 c.p.s. Although the setting up of the oscillator may appear to be rather complicated, in practice it is very simple and at the same time accurate.

In this series of articles it is proposed to cover some very interesting practical applications of the C.R.O. in the radio field, nearly all of which can be performed by the amateur. A list of the main subjects follows:

- Frequency Calibration.
- Depth of Modulation in Transmitter.
- Depth of Modulation Monitor.
- Viewing valve characteristic curves.
- The C.R.O. as a Bridge Null Indicator.
- Wave Propagation.
- Amplifier Characteristics.
- Receiver Characteristics.
- Alignment of Straight and Superhet receivers.

Frequency Calibration

(a) Frequency calibration, of which an example has already been given, i.e., the calibration of the fixed frequency oscillator, is probably the best way really to get to know your 'scope and "get the feel" of the controls. The main thing, at first, is to get to know approximately where to find certain much-used frequencies of the time base, such as 25, 50 and 100 cycles. An idea would be to incorporate a small transformer in the C.R.O. to provide about 50 peak volts A.C. to a terminal on the panel so as to have to hand a means of ensuring that the time base is actually working at the desired multiple or sub-multiple of the mains when such operation is desired.

(To be continued)

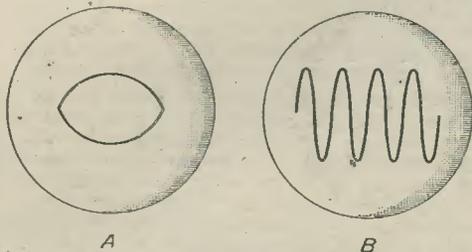


Fig. 4.—Two traces developed from the oscillator as described above.

Recording Technique-4

This Month the Question of Volume Levels is Discussed.

By K. KEMSEY-BOURNE

PREVIOUS articles in this series have dealt with monitors and volume indicators, both devices that help the recordist to operate his equipment in the best way. Before we start to consider the other end of the recording chain and such topics as studio acoustics, microphone placing and recording from broadcasts it may be well to mention a type of occupational disease not listed in medical works of reference and known as "Mixer's Itch" or "Knob Twitch." This malady affects recordists, and in particular those whose apparatus does not include volume-compression devices.

The suffering recordist feels compelled to make sudden or ill-advised changes of the gain controls during cutting, and these changes lead to wide and obvious variations in the level of reproduction. The affliction is brought on by two main causes—lack of experience of the material being recorded (usually music) and the desire to record quiet sounds at too high a level.

Imagine that the operator is recording a song or other piece of music that contains a climax following a quiet passage, which is commonly the case. He comes to the conclusion that the quiet passage is being cut at too low a level; although he can hear it on his monitor the V.I. seems barely to be moving and the needle flickers feebly at about 15 dB. down, or 20 per cent. full modulation. Accordingly, he brings up the gain until the needle averages 5 dB to 7 dB down, about 50 per cent. modulation. When the peak or climax comes to take him by surprise the V.I. flicks hard over, well above the 100 per cent. level for good cutting. The unhappy fellow turns down the control in something of a panic; perhaps he overshoots to the other extreme, and then has to bring the gain up again to reach the correct level. On playback the disc sounds as though gremlins have done their worst.

The cure for this sort of trouble is clearly to set up the controls so that the peaks will be comfortably handled; this is roughly analogous to the photographic maxim, "Expose for the shadows." If it is necessary to fade up very quiet passages or to diminish loud noises of abnormal intensity then the controls must be moved smoothly and evenly at the right moment and returned to their normal setting equally smoothly at the first possible opportunity.

The recordist must know the minimum and maximum handling capacities of his gear if he is to interpret correctly the indications of his V.I. His satisfactory recording range is limited to about 20 dB. Since the difference between a faint whisper and a loud shout can be 60 dB, and the range of orchestral music is estimated as 70 to 80 dB, it becomes evident that some control (or compression) is necessary. In the studio it is not difficult to rehearse an item several times to ensure that the relative levels of different sections are known, and adjustments can be made accordingly. On the

contrary, radio or "off-the-air" recording must be handled satisfactorily first time; there is no possibility of going back for another trial.

Variations in Level

Singers are notorious for exceeding during the final recorded performance the levels at which they sang during rehearsals. Recognise this as a natural artistic desire to put out their best for the recording, and allow for it where possible. Soprano voices in particular will indicate wide V.I. differences on different notes, even when the singer is trying to maintain a constant level, and even expert singers have notes on which they tend to peak.

All these various types of peaks, including the rise in power at the conclusion of a piece, must be made to lie within the 100 per cent. modulation level unless they are of very short duration.

Ordinary speech presents no range difficulties, since the average range for the fundamental speech sounds over the band 250 to 6,500 cycles is 20 dB.

Instrumental Ranges

The peak pressures of sound waves generated by playing various instruments vary with the instrument and cover a considerable range of values. Recordists must know something of these peak pressures because they determine the amplitudes that microphones and amplifiers must handle. This aspect of the subject has a bearing also on microphone placing, although as we shall see it is not possible to position microphones entirely by rules or calculations.

Let us consider the average and peak pressures set up by various instruments or combinations. Certain figures are set out in the table overleaf. A violin played at the lowest level normally usable produces an average pressure of about 0.5 dynes/sq. cm.; that is the average over its full frequency range, measured at a distance of 3ft. away. At the same distance a bass drum, which is the most powerful single instrument and can dissipate up to 25 watts of power, can have peaks as high as 1,260 dynes/sq. cm. Thus the ratio of pressures between these two cases is 2,520 : 1, which corresponds to a difference of approximately 68 dB. It stands to reason that to record these two instruments, playing at the same intensities as above, inside a 20dB. range the level of the drum must be reduced relatively to that of the violin, and the simplest way to do this is—place the drum farther from the microphone than the violin, and so decrease the pressure at the microphone due to the drum. Extending this further, it follows that the order of distances of the different instruments from the microphone will be directly proportional to their individual pressures.

The table represents six instruments separately, a small orchestra (15 players) and a symphony orchestra. With the exception of the piano all the

single instruments were at a distance of 3ft., the piano pressure was measured at 10ft. The figures for the orchestras are not directly comparable with those of the separate instruments, since these pressures are at 6ft. and 15ft. respectively from the nearest instrument.

What the table shows is the relation between the average and the peak pressures for each case, and this has been expressed as a decibel range. Where the dB. range is greater than that of the recording equipment then such peaks as occur in the material recorded will have to be diminished.

Studio Acoustics

The reverberation, "liveness" or "deadness," of a studio affects the apparent loudness of any sound, especially since the reverberation is not constant for all frequencies, and this has a notable

effect on the quality of recording. Recording up to 4,000 cycles in a "live" studio may sound better than working up to 8,000 cycles in a "dead" or lifeless one.

The following table shows the relation between average and peak pressures for various instruments. Pressures are in dynes/sq. cm.

Instrument	Average Pressure	Peak Pressure	Peak Average	Decibel Ratio
Bass drum ..	40	1260	31.5	30
Snare drum	15	365	24.4	28
Trombone ..	6.5	230	35.5	31
Trumpet ..	8.5	55	6.5	16
Clarinet ..	3.5	26	7.4	17
Piano ..	2.5	24	9.6	20
Orchestra ..	8	120	15	23
Symphony Orchestra	5	130	26	29

Noises in Radio Receivers

Aerial Design, Noise Limiters and Other Aids Described.

By J. CARTWRIGHT, A.M.I.R.E.

WITH the availability of surplus ex-Service equipment, many amateurs are constructing or modifying superhet receivers for short-wave operation. It may be of interest, therefore, to consider the factors affecting the signal-to-noise ratio obtainable. It is of no use having a really high gain receiver, if the noise level is so high that it swamps all but the strongest signal. An analysis of the various sources of noise will show what may be done to reduce the noise level to the lowest possible value in any particular case.

For our purpose all random signals may be classified as noise and they may be considered under the following headings:

- (A) Noise external to the receiver.
 - (1) Radiated.
 - (2) Mains-borne.
- (B) Noise inherent in the receiver.
 - (3) Faulty components.
 - (4) Circuit or thermal noise.
 - (5) Valve noise.

sensitive receiver. The effect of these discharges of natural electricity produce most interference at low frequencies and the effect decreases as the frequency increases, becoming negligible at 20-25 Mc/s. At V.H.F. "cosmic noise" is encountered. It is believed that this is due to disturbances of the sun's surface, probably associated with some form of particle emission. It is noticeable as an increase in "hiss" noise level.

Radiated man-made noise is most commonly due to car ignition systems, diathermy or induction heating apparatus. The radiation may take place

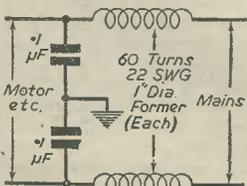


Fig. 1.—Circuit details of a simple mains interference suppressor.

Radiated noise, that is noise picked up by the receiver aerial, may be due to natural or man-made causes. Of the natural causes, the thunderstorm is the most usual. A bad storm as far as 1,000 miles away may produce the familiar crackle on a

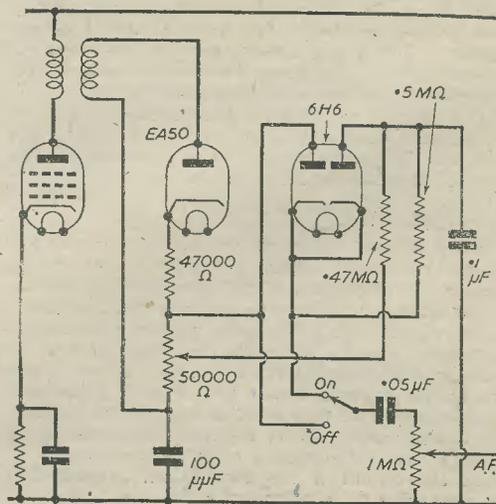


Fig. 2.—A simple but efficient noise-limiting circuit.

directly from the source or by radiation from overhead telephone or power lines. The interference field decreases sharply with distance from the source, so that the aerial should be as high as possible and far away from overhead wires. If the aerial must of necessity be near overhead lines, then the main direction of the aerial pick-up should be at right-angles to them. A screened or balanced feeder should be used in order to eliminate pick-up on the feeder where it passes through the interference field. A high aerial is in any case advantageous in increasing the signal voltage induced in the aerial.

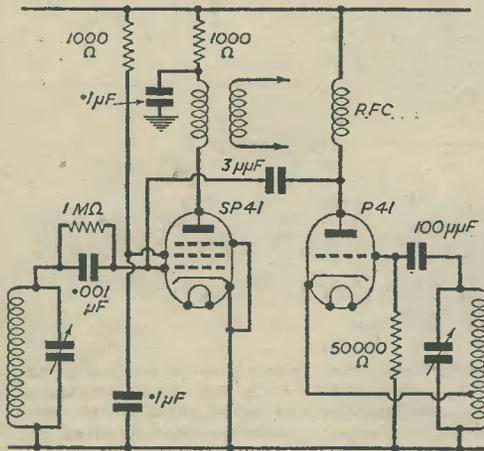


Fig. 3.—A frequency-changing stage with grid leak bias.

Of mains-borne interference, that is interference voltage present on the house mains wiring, the most common source is probably the household vacuum cleaner. Suppression of the interference at the source is, of course, the ideal solution, but so often impossible, because the source happens to belong to someone else. A simple filter of the type shown in Fig. 1 will usually provide the cure. If the trouble lies in sparking at the brushes of a motor, a couple of .1 μ F condensers from brushes to frame will often be a useful addition. If the matter has to be tackled from the receiver end, a filter of the type shown should be inserted in the mains lead close to the mains transformer.

Noise Limiter

Many of the types of noise so far mentioned consist of sharp pulses of voltage very much greater in amplitude than the required signal. By limiting the receiver response to the amplitude of the signal, the noise output is reduced to the same level, thereby rendering the signal more easily readable. The circuit shown in Fig. 2 is a simple but highly efficient audio limiter and is actually a modification of that used in the AR88 receiver. The circuit automatically adjusts itself to the signal amplitude and the diodes come into operation to block the circuit if the modulation exceeds 100 per cent. due to a noise pulse.

Dealing now with noise inherent in the receiver, the method of preventing noise due to faulty

components is obvious. Dry joints, dirty connections to the moving vanes of a condenser or a resistance which is being overheated may all contribute their quota of hiss and crackles.

On the other hand, every circuit component produces a small noise which cannot be eliminated. The electrons in, say, the copper wire of a tuning coil are in constant motion and although the average effect is zero, over a short period of time this random movement does represent the generation of a voltage. This voltage has components covering an exceedingly wide frequency range, but due to the response of the receiver and, the human ear it is audible as a hiss. This is commonly called thermal agitation noise. The value of the thermal noise voltage is proportional to the square root of the impedance of the source and the square root of the bandwidth of the circuit. It is sufficiently small to be of importance only for the first tuned circuit in any normal receiver. As an example, the approximate value for a tuned circuit with an impedance of 100,000 ohms and a bandwidth of 10 kc/s is 4 μ V. However, if this circuit feeds a non-linear device such as a frequency changer valve the noise voltage is effectively greater since I.F. noise components can be produced by R.F. noise components outside the nominal bandwidth, owing to interaction with oscillator harmonics, second channel effects, etc. The amplified noise plus signal voltages are so much greater than the thermal noise voltage generated in the second stage that the contribution of this stage is negligible.

Valve Noise

In much the same way, all valves produce noise in varying degrees because the anode current consists of individual electrons and there will be short period variations even though the average anode current is constant. In the case of the diode and triode, the "shot noise" voltage produced is proportional to the anode current divided by the square of the mutual conductance. For a multigrid valve, the total space current is divided between the anode and one or more screen grids, and in consequence the noise voltage as calculated on the anode current must be multiplied by a factor greater than one. To obtain the minimum noise voltage, therefore, the screen current should be small compared with the anode current and the mutual conductance should be large. Special valves having these characteristics have been produced by both British and American manufacturers, typical examples being the television pentodes EF50, SP41 and 6AC7. For the normal types of frequency changers the screen current is high and the effective mutual conductance, i.e., the conversion conductance, is low and consequently the noise level is high.

It is usual to express the "noisiness" of a valve as the "equivalent shot noise resistance." This is the value of resistance which, under standard circuit conditions, would produce the same thermal noise voltage as the actual valve noise voltage. By using this equivalence, it is possible to compare the merits of various valves and to compare the relative importance of valve and circuit noise. Typical values for various types of valves are:—

Triode—200 to 500 ohms.

Television pentode—2,000 to 4,000 ohms.

Normal pentode—20,000 to 50,000 ohms.

Frequency changer—50,000 to 150,000 ohms.

In practice the value is even higher in an actual frequency changer circuit since the oscillator contributes a certain amount of noise in addition to that produced by the hexode or heptode due to the interaction between noise voltages outside the nominal passband of the receiver with oscillator harmonics to produce components falling within the I.F. passband.

Having now briefly considered the sources of noise, we may consider how to apply these facts in a practical case. Suppose the aim is a general coverage superhet, 1.7 Mc/s to 30 Mc/s, of high sensitivity and signal/noise ratio. From the figures given above it is obvious that at least one stage of R.F. amplification must precede the frequency changer, since for optimum performance the valve noise should be less than the circuit noise. At the low frequency end of the range, one R.F. stage, using EF50 or SP41, will give satisfactory results, but at 30 Mc/s, where tuned circuits have of necessity much lower impedances two stages would be better. However, a very satisfactory compromise is to use a single high- μ R.F. stage, followed by a similar valve as a frequency changer. This type of frequency changer has a higher conversion conductance than any of the more normal circuits. An SP41 in the circuit shown in Fig. 3, has a conversion conductance of 2.7 ma/V., and a noise level little greater than that of the same valve used as an amplifier. The difficulties normally encountered with grid injection are largely overcome by using grid-leak bias for the mixer.

The R.F. circuits should have as low loss as possible, with the layout arranged to give minimum stray capacities. Plug-in coils enable a number of bands to be covered with the maximum efficiency, but switched coils in a turret form of construction can be very nearly as good. The aerial coupling circuit is of vital importance and the number of turns on the aerial coil should be adjusted to give optimum signal transfer, that is the feeder impedance should be matched. Although this adjustment does not in theory give the best signal/noise ratio, the difference is not normally detectable in practice.

Two Stages

If an I.F. of 465 kc/s is chosen, two stages using iron cored coils and normal R.F. pentodes will give adequate selectivity for phone reception, with maximum usable sensitivity. The overall bandwidth will be determined almost entirely by the I.F. amplifier, since the R.F. circuits will be comparatively flatly tuned, especially at the higher frequencies. This will give a bandwidth of about 5 kc/s at 30 dB. down which is a compromise giving high signal/noise ratio with reasonable audio quality. A double diode triode, as detector and L.F., feeding a power pentode such as a 6F6 completes the lineup. To deal with pulse type interference a noise limiter between the detector and audio stage will prove a very worth-while addition.

Above 30 Mc/s very much the same considerations apply, provided that it is remembered that the stage gain decreases due to the difficulty of obtaining high impedances in the tuned circuits. Above 100 Mc/s other desirable properties of the valve have to be sacrificed to obtain minimum inter-electrode

capacities. The acorn valves, such as the 954, or their equivalents in the 9,000 series of the miniature range are the usual types. The latest releases for U.H.F. use the 6AK5 and the 6J6, which is a special double triode.

As a matter of interest it may be noted that the old controversy of whether the superhet or the reacting detector receiver is the more sensitive for weak signal reception cannot be settled simply by calculating the theoretical signal-to-noise ratios. The sensitivity of a reacting detector depends far more on the skill of the operator than on the circuit. The author of this article had occasion to make a series of tests on receivers of this type and a variation of 10 to one in the sensitivity figure for any particular set was found, depending on whether the operator was skilled or unskilled.

In conclusion, it may be of interest to describe an easy check on the efficiency of an R.F. stage. The aerial is removed and a condenser of $.1\mu\text{F}$ connected from grid to ground. If the thermal noise due to the tuned circuit is the limiting factor, as it should be, then the noise output will decrease on connecting the condenser.

Microwave Multichannel System

THE Plessey centimetric (microwave) radio link has been developed to provide multi-channel two-way radio telephone communication in situations where the provision of landline equipment is either not possible or is undesirable. The microwave radio "beam" is extremely narrow, and is not unlike the beam produced by a searchlight. Provision has been made for eight duplex channels (speech or telegraph) of a 4 kc/s. bandwidth over one R.F. carrier in the 6 cm. waveband (i.e., a carrier frequency of about 5,000 megacycles per second).

Receiver

The receiver is a superheterodyne type with a V.M. local oscillator, which is of similar construction to that of the carrier oscillator. The mixer is of the cavity type into which is injected, by means of a loose coupling, power from the local oscillator. The receiver line from the aerial hybrid is matched into the mixer cavity. The first detector is a silicon crystal capsule, feeding directly into a 60 mc/s head amplifier.

The I.F. amplifier is designed to have a gain of 92 dB. at a mid-band frequency of 60 Mc/s with a bandwidth of 10 Mc/s., the input impedance being 75 ohms.

The detected output provides the demodulated signal in a video-frequency band with a flat characteristic from 20 c.p.s. up to 5 Mc/s. from a low internal impedance. The A.F.C. control voltage operates on the grid of the local oscillator valve.

The I.F. amplifier may be regarded as comprising two separate three-stage amplifiers connected in tandem. The wide bandwidth is obtained by means of feed-back, using special low-capacity resistors.

The video output signal from the detector passes through a video amplifier and is fed into a group pulser and separator unit in the second bay.

Modulation-3

In Concluding This Series "DYNATRON" Deals With Amplitude Modulation

TRUE amplitude modulation as generally understood is a result of adding a third carrier frequency, giving the wave of Fig. 1 (b).

We have just seen how a "simple beat" between sidebands (i.e., minus the carrier) results in Fig. 1(a). If now the carrier is reintroduced in correct frequency, magnitude and phase, the pulsating envelope, with frequency-doubling, will be transformed into the true sinusoidal envelope of Fig. 1(b).

In Fig. 8, we have two sideband vectors OA and OB, revolving relative to the carrier vector OC.

As its frequency is higher than the carrier, OA will be revolving faster than OC, therefore slowly gaining upon OC. Similarly OB will be falling behind OC at the same rate as OA is gaining.

Actually, OA, OB and OC are all revolving anti-clockwise extremely rapidly—all being "high" frequencies. But *relative to OC*, OA is revolving (gaining) anti-clockwise, whilst OB has a relative clockwise (falling behind) motion.

At all times, however, OA and OB will be symmetrically placed relative to OC—will make the same angles with OC. Therefore, the vector resultant OD will always fall in line with OC; either in-phase as in 8(a) and 8(b), or diametrically opposite as in 8(c).

In one case, OD will be adding to the carrier amplitude to raise the modulation to a "peak"; when the sideband vectors have positions such as in (c), OD will be of opposite phase to the carrier, subtracting therefrom to cause the "trough" in the modulation envelope.

Which explains what we mean in saying that A.M. is a "complex beat" between sidebands and a carrier.

As in simple beats, the modulation envelope is a "difference-frequency": the difference $(fc + fm) - fc$, or $fc - (fc - fm)$, the answer being the modulating frequency fm in either case.

The upper sideband is $(fc + fm)$; the lower, $(fc - fm)$: "sum" and "difference" frequencies, but of an altogether different type to those we have been discussing in the case of beats.

As explained before, the *beat-difference* between the sidebands is, $(fc + fm) - (fc - fm) = 2 fm$ (we get frequency-doubling). With a carrier, the beat differences are, $(fc + fm) - fc$, or, $fc - (fc - fm)$, as above.

Here, we get a difference between either sideband-frequency, and a *mean* frequency fc , which gives the correct modulating frequency fm .

But in speaking of "sums and differences," no one should be so foolish as to confuse sidebands with what we do to find a beat-difference. For

example, the so-called "sum frequency" in beat-rectification is not a "sideband" (!), but a second harmonic of a resultant mean frequency.

Is it anything else in a modern mixer?

A Little Mathematics

How do we derive an expression for an amplitude-modulated wave?

First, an alternating current of steady amplitude (or an unmodulated carrier) is denoted by,

$$A \sin 2\pi fct, \text{ or } A \sin \omega t,$$

where A stands for the constant amplitude.

Suppose, now, the amplitude, instead of being constant at the value A, is varying sinusoidally at an audio rate represented by B sin pt, Fig. 1(b).

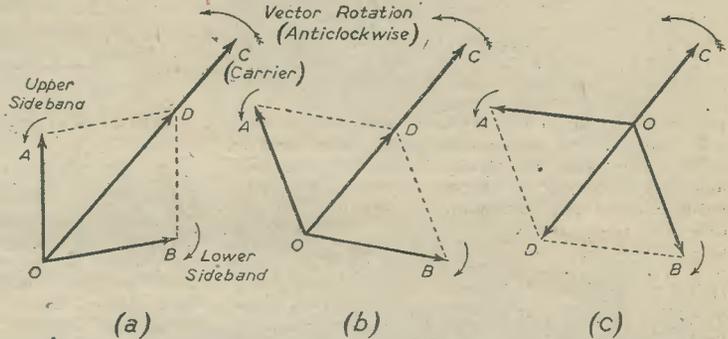


Fig. 8.—Vector picture of a "Complex Beat" between carrier and sidebands. Tailed arrows show rotation of the vector system as a whole; small arrows show relative rotation of the sideband vectors with respect to the carrier. Resultant OD always falls in-phase, or at 180 deg. to the carrier vector OC, i.e., adding or subtracting to the amplitude.

Then, the amplitude will rise to a maximum of $(A+B)$. During a modulation cycle, the peaks of successive H.F. cycles will be close enough together for us to write:

$$\text{Instantaneous Amplitude of a given H.F. cycle} = A + B \sin pt,$$

i.e., considering how the H.F. amplitude is changing over the modulation cycle.

But, next, we want a general expression of the form $A \sin \omega t$, to give the *instantaneous value at any point in any H.F. cycle, during modulation.*

It is quite simple. Instead of having the constant value A, the amplitude is now $(A+B \sin pt)$, so, therefore:

$$\begin{aligned} A \sin \omega t, \text{ becomes, } & (A+B \sin pt) \sin \omega t. \\ & = A(1+B/A \sin pt) \sin \omega t. \\ & = A(1+m \sin pt) \sin \omega t, \end{aligned}$$

where, $m = \text{the modulation factor } B/A.$

For example: $20(1+0.8 \sin 2\pi (1,000)t) \sin 2\pi 10^6 t$

states we have a wave—or an alternating current—of 20A. peak (unmodulated), and of frequency 10^6 cycles/sec. ($=1.0 \text{ Mc/s}$); it is modulated 80 per cent. ($m=0.8$) by a sinusoidal current at 1,000 c/s,

The "20" might equally well stand for 20 volts, or 20 kV. in transmission problems.

If simply superimposed, the expression is, $A \sin \omega t + B \sin pt$.

For frequencies in the ratio of 2/1 or more, this equation says the waves remain entirely independent as explained in reference to Simple Superposition. If in a ratio less than 2 (if the frequencies are within the same "octave"), mutual interference would take place to give a simple beat, Fig. 1(a) and Fig. 7.

But in A.M., f_c and f_m are widely different frequencies. Simple addition, as above, would leave the waves independent, Fig. 6(a). *Modulating A*

$\sin \omega t$ by $B \sin pt$ implies multiplication of instantaneous values:

$A \sin \omega t \times B \sin pt$, and not $(A \sin \omega t + B \sin pt)$.

A non-linear device is essential to accomplish this.

Two high-frequency sidebands are generated, when we may apply beat principles as in Fig. 8; the carrier and sidebands are all frequencies within the 2/1 ratio limit.

It may be interesting in a later article to try to understand how a non-linear device can "multiply" the instantaneous values of two (or more) sine waves.

Practical P.A. Working-4

Microphones and Loudspeakers are the Subject of This Article.

By R. SELBY

THE ribbon velocity microphone is capable of giving first-class reproduction, being free from resonances and having a very wide frequency response. It has a definite directional pickup which may or may not be an advantage. The chief difficulty lies in its very low output. Owing to the very low impedance of the ribbon, a step-up transformer must be mounted inside the microphone casing, and, unless the ratio (and therefore the output voltage) is low, a screened cable must be used for connection to the amplifier. The small mass of the ribbon means that it is not likely to be harmed by dropping, but it is liable to damage by wind or by speakers blowing into the microphone, an unpleasant habit which some users adopt for finding whether the microphone is alive or not. Taking all these factors into consideration, it may be said that the ribbon is an excellent microphone, provided it is handled considerably, and that it finds its principal application in indoor use.

Crystal microphones are of two types—the diaphragm and the sound-cell. Both have an excellent high-frequency response. The former has an output comparable with that of a moving-coil and is useful for some purposes, particularly in mobile loudspeaker vans, but it cannot be considered a high-fidelity instrument and will not be considered further. The sound cell type consists of one or more Rochelle salt crystals embedded in wax and lightly suspended inside a protective and screening case of metal gauze. Sound waves impinging directly on the crystal cause it to generate a corresponding voltage. Sound pickup is substantially non-directional and frequency response is excellent, but output is low and the high impedance of a capacitive nature presents some difficulties. The load imposed on the microphone by the grid resistor of the input valve must be not less than 2 megohms if loss of bass is to be avoided, and the connections from microphone to grid of the valve

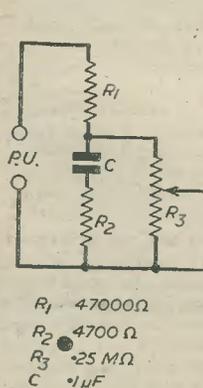


Fig. 3.—Tone-controlled input circuit.

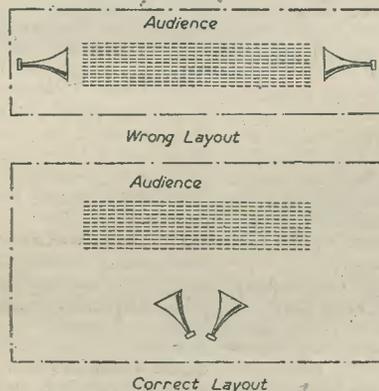


Fig. 4.—Two speakers may be arranged as shown above.

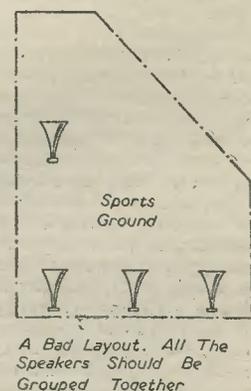


Fig. 5.—Another incorrect speaker layout.

Trade Notes

Varley Transformer

TO meet the popular demand for "Universal Output" transformers, Oliver Pell Control, Ltd., have recently put into production a new model listed as Varley D.P.61

This heavy duty model is a multi-radio output transformer, capable of handling 20 watts without distortion, and meets the needs of those who require a high-quality component. It is specially suitable for 6L6 valves or equivalents. The sectional and interleaved windings are carefully balanced to ensure a level response over a wide frequency range.

The D.P.61 transformer is enclosed in stoved enamel grey shrouds, giving a minimum loss of power. It is supplied in 11 ratios for a single valve and 11 ratios for "push-pull." Other details are as follows:—

Primary Inductance ..	45 henries
Primary Resistance ..	300 ohms each half
Primary current ..	100 mA. each half
Output (maximum) ..	20 watts
Ratios ..	13:1-100:1
List price, 45s.	

"Bafflette" Console Model

THIS speaker is so designed that it will stand in a corner or normal floor model position. It is of highly-polished walnut, black plinth, horizontal inlays at top and bottom. Its dimensions are 26in. x 17in. x 6in.

The speaker aperture is set back at an angle to prevent attenuation of the higher register; strong shallow cabinet eliminates unwanted "box" resonance. The quality of reproduction is consequently better than the average table model and comparable with a good console radio receiver.


The price is £6 15s. (8s. 6d. extra with transformer).

C.-R. Tubes with Standard Heaters

DESIGNERS of D.C./A.C. television receivers will be particularly interested in two new cathode-ray tubes which have recently been announced by Mullard Electronic Products, Ltd. These tubes, a 9in., type MW22/14C, and a 12in., type MW31/14C, have heaters rated at 6.3 volt, 0.3 amps., and may, therefore, be series run with the valves in the television receiver. Although the maximum first anode voltage has been reduced from 400 to 300, in practice this does not prevent direct interchangeability with older tubes as these are invariably operated at a first anode voltage below 300, this being usually obtained from the 300 volt line less the appropriate bias. The new tubes can thus be used as direct replacements in sets which have been using the Mullard types MW22/7 or MW31/7, according to whether a 9in. or 12in. tube has been fitted.

In addition to the MW22/14C another tube, type MW22/14, is also in production. This is similar to the MW22/14C, but has a coating of Aquadag applied externally to the flare of the tube, the purpose of which is to act as one electrode of a smoothing capacitor for the E.H.T. supply. This

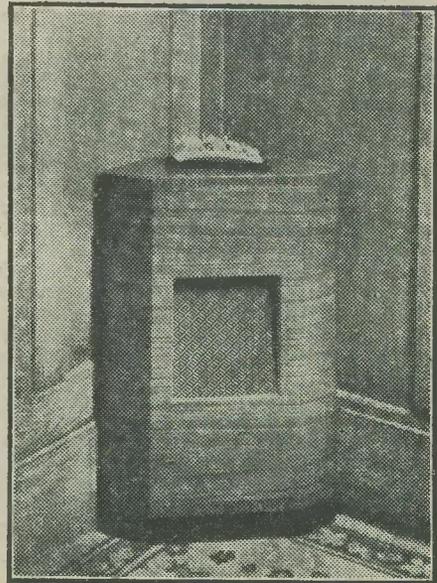has the advantage that it eliminates the necessity of using a standard smoothing capacitor, thus reducing the cost of the equipment. It should be noted, however, that although the MW22/14 has



The new "Bafflette" Console Model Extension Speaker.

identical operating conditions and characteristics to the MW22/14C, it is not directly interchangeable with this latter tube on account of the external conducting coating.

R.G.D., Ltd.

THE following changes of address and sales policy are announced by Radio Gramophone Development Co., Ltd.:

The London Depot, Dealer, Sales Service and Export Department is now at 3-4 Hampton Court Parade, East Molesey, Surrey. Telephone; Molesey 4357/8.

The Publicity Department has moved to 21 Bloomsbury Street, London, W.C.1. The telephone number is Museum 1600.

(Continued from page 427)

Some readers may consider that differentiation is unnecessary in the case of the last two classes! Propaganda is a difficult item to cover, since, as indicated earlier in this article, its motives may frequently be achieved by omission. However, I think all viewers will agree that it is high time that television adhered to certain standards of taste and that a classification of appeal, as indicated above, would be a valuable guide.

CLYDESDALE

For Ex-Services Radio Bargains

BRAND NEW RADIO COMPASS RCY UNIT, EX-U.S.A.F.
BC-454-A or C, 15 v. Rcvr. 200-1,750 mcls, 8½ x 21 x 12in., plus BC-454-A Control Box, 7½ x 4 x 7½in., with "5" meter, etc., plus flexible tuning shaft, plus Service Manual.

CLYDESDALE'S PRICE ONLY £6/15/0 per set. Carriage Paid.

BRAND NEW, in maker's cartons, complete.
R.F. UNIT 26, 65-50 mcls, 5-6 metres, at 35/- each. Carriage paid.

R.F. UNIT 27, 85-65 mcls, 3.5-5 metres, at 35/- each. Carriage Paid.

HALF-WAVE DIPOLE AERIAL, 9ft. 3in., with reflector, 9ft. 7in. and Crossarm 4ft. 11in., plus 39ft. 80 ohm. co-axial cable, approx. 6 metres, light-weight tubular metal, mounting optional, at 21/- each. Carriage Paid. Or packed in a wood case, at 28/6 each. Carriage Paid.

BC-453 A or B, 550-190 mcls IF 85 kc/s with valves, less dynamotor. Brand New, at 50/- each, or Unused, but case slightly dented, at 37/6 both Post Paid. **BC-454-A or B**, 3-6 mcls IF 1,415 mcls with valves, less dynamotor. Brand New, at 30/- each. Or Unused, but case slightly dented, at 25/- each, both Post Paid.

BC.221 FREQUENCY METER Ex-U.S.A.A.F.
Complete with valves, 0.01 per cent. accuracy, for battery operation.

CLYDESDALE'S PRICE ONLY £9/19/6 each. Carriage Paid.

ALSO LARGE SELECTION VALVES, TRANSFORMERS, ETC.
Send now for new illustrated lists; print name and address.

CLYDESDALE SUPPLY CO., LTD.
2, BRIDGE STREET, GLASGOW, C5. Phone: SOUch 2706/9
Visit our branches in Scotland, England and Northern Ireland

PITMAN'S

for PRACTICAL Books

Radio Receiver Servicing and Maintenance

By E. J. G. Lewis. Here is reliable, up-to-date assistance for the radio dealer and service engineer in the technical details of their work. A handy fault-finding summary forms a useful feature of the book. Fourth Edition, 8/6 net.

Classified Radio Receiver Diagrams

By E. M. Squire. A series of diagrams covering most of the types of circuit found in modern receivers. Second Edition, 10/6 net.

Electronics

By F. G. Spreadbury, A.M.Inst.B.E. The practical applications of electronics are worth watching, and this book is the most up-to-date, comprehensive and reliable guide yet published to theory and applications alike. With numerous diagrams. 700 pages, 55/- net.

PITMAN, Parker St., Kingsway, London, W.C.2.

H.B.L.

FOR THE HOME CONSTRUCTOR

We specialise in supplying complete kits and individual component parts for all circuits described in this journal.

5-VALVE A.C. MAINS SUPERHET KIT, 3 waveband, 16.5-50, 200-550, and 800-2,000 metres, complete with valves and speaker, £14 7 1; also supplied to cover 12.5-37, 36-120, and 200-550 metres.

SHORT WAVE COILS, 4-pin. set of 3, covers 12 to 80 metres. Complete with circuit, 9/9.

WEARITE "P" Coils. Full range in stock as shown in our catalogue, 3/- each.

ALUMINIUM CHASSIS (22 gauge), 8in. x 6in. x 2½in. undrilled, 5/-, drilled to own specification at extra cost.

HOME INTERCOM. (Described in Aug. issue). Complete Kit of Components and Valves, £8. (Speakers and Switches as required.)

ETRONIC 6 VALVE A.C. MAINS SUPERHET RECEIVER, in walnut cabinet, wave range 15-61, 190-550, and 900-2,200 metres "Magic Eye" tuning, £21 13s. 9d., or on H.P. Terms Deposit, £5 8s. 6d. and 11 monthly payments of £1 12s. 6d.

Send 21d. stamp for our Brochure of Kits. Also details of our Practical How-to-Build-it Books, complete instructions and designs for the HOME CONSTRUCTOR.

HENBEST BROS. LTD.
26, Green Lanes, London, N.13
Telephone: BOWEN PARK 6293.

TUNING SCALES

Types available on White translucent plastic or transparent Perspex for our

COILS

COIL PACKS

PERMEABILITY TUNERS

Send for details

LOOK OUT FOR—

B5 and B6 COIL PACKS

Highest possible performance with size of only 3" x 2½" x 1½"
Full details will be announced in the Technical Press shortly.

WEYMOUTH RADIO MANUFACTURING CO., LTD.

Crescent Works
WEYMOUTH

LYONS RADIO

3, Goldhawk Road, Shepherds Bush, W.12

Telephone: Shepherds Bush 1729

AMPLIFIER UNIT Type A362A
Brand new units in well-constructed metal chassis with cover 12in. x 9in. x 9in. approx. Fitted with 2-807s, 1-EP50, 1-6U4, 1-VR92 and other useful components, including 2-L.F. chokes, over 20 resistances, metal rectifier, ceramic valve bases, etc. Price 30/- (carriage 2/6).

AMPLIFIER Type A1261
A single stage audio unit fitted with EF36 valve and transformers, relay and volume control. In 3in. cube metal box. Price 9/6 (postage 1/-).

DESK MICROPHONE
Similar to those used on R.A.F. ground stations; 12in. high, with adjustable head. Fitted with highly-sensitive carbon insert. Complete with lead. As new. Price 7/6 (postage 1/6).

HIGH RESISTANCE HEADPHONES
Super quality R.A.F. pattern with moulded rubber headband and detachable ear cushions. As new with flex and plug. Price 12/6 pair (postage 1/6).

THERMAL DELAY SWITCHES
Standard "Varley" pattern, 4v. operation. Brand new. Price 2/6 (postage 3d.).

MOVING COIL MILLIAMMETERS
0.150 mA. 2in. dia. Brand new. Best makes, 7/6 (postage 9d.).

WIRE WOUND VITREOUS RESISTANCES
Big range, all at bargain prices. The following are typical examples: 500 ohms, 55 watts, 1/9; 20,000 ohms, 75 watts, 2/3; 500 ohms, 100 watts, 3/-; 15,000 ohms (tapped at 2,000 ohms), 50 watts, 2/3 (postage extra).

ELECTRADIX Bargains!

SOLENOIDS. Powerful electro magnetic D.C. iron clad Solenoid $\frac{3}{4}$ in. core, weight 1 lb., 10 ozs., screw-in core for use on 6-25 volts to lift 7-28 lbs., Type No. 1, 4/-; Type No. 2, with 3 separate windings, 4/6. Wound Solenoid coils, 27 gauge enamelled wire, excellent as H.F. smoothing filter choke, 2/3 each.

MAGNETS. D.C. Electric magnets, weight 10 oz., lift on 2 volts 1 lb., 4 volts 3 lb. 6, volts 4 lb., new surplus, 7/6 each. Permanent powerful flat bar magnets, $\frac{23}{32}$ in. x $\frac{1}{2}$ in., drilled 2 holes each end, and any pole pieces, 2/- pair. The wonder Midget magnets. Alni perm. steel disc; $\frac{3}{16}$ in. diam. $\frac{3}{16}$ in. thick, with 3/16 in. centre hole 3/16 each. Large stock of Horseshoe magnets. Send for special Magnet Leaflet.

METERS. D.C. moving iron ammeters, panel mounting 2 in. dial, bakelite case, 0-5 amps, 12/6. D.C. moving coil milli-ammeters, 2 in. dia., flush panel, 0-1 m.a. 35/-. D.C. moving coil Weston meters, 2 in. flush fitting f.s.d., 500 m.l.a., reading 15 volts and 600 volts with extra resistance, resistance not supplied with meter, 20/-.

DYNAMOS. 12 volt 10 amp. D.C. machines, 1,400 r.p.m., new condition, 45/-; 24 volt 30 amp., 24; 30 volt 5 amp., 25.

ELECTROLYTIC CONDENSERS. 150 watt working 64 M.F.D. metal can type with base clip, 2/6.

DIMMER RESISTANCES. Totally enclosed panel type, 100 ohms $\frac{1}{2}$ amp. or 50 ohms $\frac{1}{2}$ amp., 2/6 each, post 6d. Open type wire wound, porcelain base, 10 ohms 1 amp., 2/6.

CUTOUTS. Auto non-mercury in bakelite case, 3 x 3 x $\frac{23}{32}$ in., 18 volts 30 amps., 21/-. G.E.C. 12 volts 15 amp. non-mercury auto cutouts, 4/6.

BELLS. G.P.O. Circular Bell on bakelite base, 5/-. Magneto bell in Mag. box 8 x 6 x $\frac{3}{4}$ in., 5/-. Heavy I.C.A.C. 230 volt alarm bells, 6 in. gong, 42/-.

TELEPHONES for House or Office. Constructors' Parts for your own set-up. Ex G.P.O. stocks, wall type, comprising Bracket Mike, Transformer and Condenser, Magneto Bell in walnut cabinet, 8 in. x 6 in. x $\frac{3}{4}$ in., fitted terminals and connections, Switch Hook and Contacts, Hand Magneto Generator and G.P.O. Receiver, 35/- per pair, with wiring diagram.

WIRELESS CONTROL UNITS, ex-R.A.F., contain Yaxley switch and knob, connection strips, fuse and holder, coil socket and connections, 2/6, postage 9d. Larger model with 2 Yaxley switches and pilot lamp, 4/-, plus 1/- postage.

HAND MAGNETO GENERATORS. 4 and 5 magnet type, 150 volts 50 ma., A.C. output, new condition, P.M. Steel magnet and gearing in handle, 12/6, postage 1/-.

TERMINAL BOXES. Bakelite power terminal boxes $\frac{3}{4}$ x $\frac{23}{32}$ x $\frac{23}{32}$ highly polished black with $\frac{1}{2}$ in. centre fillet and screwed cover 2-pole 5/16 in. connection studs and nuts. Admirable terminal or branch top on large transformer, 2-pole lights, power or charging circuits 10/50 amps. Wall or ceiling fixing, 2/6 each, 20/- per dozen.

PARCELS. 10 lbs. useful oddments for the junk box. All clean, dismantled from Government and other surplus apparatus, 7/7 post free. (Not for Overseas buyers.)


Please include postage for mail orders.

ELECTRADIX RADIOS

214, Queenstown Road, London, S.W.8

Telephone: MACaulay 2159.

A NEW

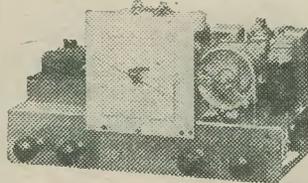TELERADIO,**CHASSIS
MODEL A70**

6-valve A.C. MAINS R.G. CHASSIS, 15-50, 200-600, 540-2,000 Metres with TUNING INDICATOR, TONE CONTROL. 14 gns., plus P.T. £3.3.0, or in kit form from £8.10.0

Also available as tuning unit feeding push-pull amplifier. Blueprints can be supplied for home construction if desired. Send 2½d. stamp for full illustrated lists to

THE TELERADIO CO. 157, Fore Street, London, N.18

Tel.: Tott. 3386.

Export enquiries for full range of Kits and Chassis invited.

**NEW G.P.12
CRYSTAL PICK-UP
with permanent sapphire stylus**

—was fully described in *The Wireless World's* recent article "Crystal Pick-ups—Basis of Design for Fidelity Reproduction."

This remarkable pick-up, which represents the ultimate in high-fidelity reproduction, is now available in limited quantities through your radio dealer, price 104/- incl. P.T.

FREE ILLUSTRATED FOLDER describing this new pick-up may be obtained by returning the coupon below.



TO COSMOCORD LTD.
ENFIELD, MIDDXX.

Please send folder of ACOS Pick-ups.

NAME _____

ADDRESS _____

P.W.

**CHARLES BRITAIN RADIO LTD.**

11, UPPER ST. MARTIN'S LANE, W.C.2 Telephone: Temple Bar 0545
(1 minute from Leicester Square Tube Station, Up Cranbourne Street.)

WE ANNOUNCE WITH PLEASURE THAT AS FROM SEPTEMBER 1st WE ARE OPENING MORE SPACIOUS PREMISES AT ABOVE ADDRESS.

We cordially invite both old and new friends to call and inspect our

**VERY SPECIAL OPENING BARGAINS
VIDEO FILTER UNIT**

This job contains a really excellent power pack operating from 250 cycle mains, contains transformer giving 350-0-350 120 millamps; two 5 v. 2 amp., one 6.3 v. 2 amp., one 2 v. 1 amp. windings; and the following valves: 5, EF50; 1, EF55; 8, EA50; 1, R1; numerous jacks coils, resistors, tag panels, handsome blue front panel, size 17 in. x 10 in. x 8 in. Price £2 17s. 7d. Callers only.

**AMERICAN INDICATOR TYPE ID6
APN4**

Contains 26 valves, types: 3, 5L7 G.T.; 14, 6SN7 G.T.; 8, 6H6 G.T.; 1, 6J7 G.T.; 1, 5 in. C.R.T. Type 5CP1, and 100 Kc. crystal. PRICE £3 19s. 6d. Callers only.

THIS MONTH'S SPECIAL OFFER

Indicator type 62. Size 9 in. x 12 in. x 18 in. Contains VCR97 tube (non Persistent); 16, SP61; 2, EB34; 2, EA50; 16 pot-meters, Muirhead dial, 117 Mc/s. crystal, various switches, knobs, transformers, etc. £2 19s. 6d. Callers only.

Note: All C.R.T.s will be demonstrated to callers.

RECEIVER 3090

Complete in case size 12 in. x 8 in. x 12 in. Contains the following valves: 4, SP41; 2, 6J5; 1, EB34; 2, EA50; 2, CV6; 1 motor generator, numerous relays, pot-meters, resistors, etc. The generator, which is complete with all gears, etc., can be easily converted to a small motor for A.C. or D.C. operation. This really is a genuine bargain, at only 19/6, plus 5/- carriage and packing. Get one now while stocks last.

TYPE 26 R.F. UNITS.

Tuned 5 metre Converters. Brand new in makers' cartons. Price only 27/6 post free.

RI124 RECEIVER

Range 30 to 40 Mc/s. Contains six new valves: 3, 9D2; 1, 8D2; 1, 15D2 (Frequency Changer); 1, 4D1; 24 ceramic trimmers, 6 ceramic valveholders, 6 valve screening cans, 30 resistors, 3 pot-meters, mica and tubular condensers, ceramic coil formers, 5-way 4-bank switch with long spindle and IF transformers, etc. A real buy at only 19/6, plus 2/6 carriage and packing.

SUB CHASSIS

Complete with 3, EF50; 2, EA50; ceramic valveholders, resistors, condensers; etc. 16/6 post free.

I.F. TRANSFORMERS.

465 Kc/s., adjustable iron cores, very high Q. Can size $\frac{3}{4}$ in. x $\frac{1}{2}$ in. x $\frac{1}{2}$ in. 8/6 pair.

SPECIAL VALVE OFFER.

All guaranteed. 6V6, 7/6 each; EF36, 6/- each; 5Z4, 7/6 each; KT33C, 8/6 each; SP61, 3/- each; SP41, 3/- each; 6Q7, 7/6 each; EA50, 3/- each; 807, 8/6 each.

It will pay you to pay us a visit.
CHARLES BRITAIN RADIO, LTD.
(NOTE NEW ADDRESS ABOVE.)

Programme Pointers

This Month Our Music Critic, MAURICE REEVE, Deals With
the "Pairing Off" of Musicians

COMPARISONS are odorous, said Shakespeare, but musicians would seem to take little heed of his wisdom, so far as the critical members of the fraternity are concerned. I don't know how many of my readers are given to the habit of pairing off the great musicians when engaged in musical discussion, but I have noticed with unflinching regularity that certain composers get sorted out, or fall, into pairs as naturally and as inevitably as bacon goes with eggs or strawberries with cream. And as it always occurs of our desire either to praise or belittle someone, the habit, or one might almost call it custom, may afford us some interest.

The most notable instance is, I suppose, that of the three great Bs, to wit, Bach, Beethoven and Brahms. These three giants, whose combined span from Bach's birth in 1685 to Brahms's death in 1897 covers the entire period of the German domination of the musical world, really form two pairs: Bach-Beethoven and Beethoven-Brahms. Bach and Brahms are not, I think, compared with each other to nearly the same extent, partly because of the great gap of time between the two, but chiefly because of Beethoven's commanding position between the two and because Brahms worked almost entirely in Beethoven's medium rather than Bach's.

I don't think I have ever heard the merits or the demerits of a Beethoven symphony, concerto or piece of chamber music expounded upon except to the holding of Brahms's works in the same genres as justification. And vice versa, of course. One person's remark that the Emperor Concerto is "divine" and the "greatest of all concertos" at once begets the reply, "I disagree. I don't think it's a patch on the second Brahms." Similarly, someone else only has to say they would walk a mile to hear Brahms's first symphony when they court the rejoinder that the other party wouldn't go a yard to hear it, but they'd go 20 miles to hear Beethoven's seventh! And so on and so on. Neither ever seems to be compared to his forbears Mozart, Haydn or Schubert, to his contemporaries, more or less, Schumann or Mendelssohn, and naturally never with anyone so entirely different as Tchaikowsky or Sibelius. It must be with each other, and always against each other; they never stand alone. Neither, as I said, do they invite comparison with each other. Were someone to say they preferred a Brahms or Beethoven symphony to one by, say, Sibelius, the reply would inevitably be that one can't compare the two. Why not?

Other "Rivals"

Other inseparable companions in rivalry who readily occur to the mind are Mozart and Haydn, Chopin and Liszt (also Schumann and Chopin and, less often, Schumann and Liszt), Liszt and Berlioz, Debussy and Ravel, and Elgar and Delius. Wagner, being Wagner, seems not to arouse any rival emotion in particular. It has become just as

natural and inevitable to couple these names and to mete out praise for one with blame for the other all in the same breath and as part of the same sentence as it is to remark on what a lovely day it is, but you don't think it will last very long.

The reason for these pairings lies, usually, in certain similarities in the work of the two composers, similarities of style and thought due to a common outlook on their art and their approach to it. Not always, of course, because no two writers could be more dissimilar than Elgar and Delius. They have obviously been "made" to invite comparison by being easily the two most distinguished British composers of their day. Apart from that accident, neither seems to meet on common ground at any point. Both have their artistic roots planted in entirely separate allotments: the former being English to the very core but moulding his genius in a symphonic style, whilst Delius, who lived most of his life in France, gained his inspiration from that impressionable country plus a damp mistiness bequeathed by his native Yorkshire.

Pianists on Common Ground

Chopin, Liszt and Schumann, so far as their piano music is concerned, are, on the contrary, on the most uniquely common ground, though of three different nationalities. They were all actually born about the same time and were firm friends. Though so different in individuality, which is imprinted on every page of their music, each approached his keyboard tasks through the common medium of being great pianists (Schumann early on destroyed this side of his career by trying to practise with a gadget on his fingers) and through the artistic approach of the newly found romantic movement which they did more than anyone to build up to its greatest heights.

But they parted company at the piano. Chopin, of course, never wrote for anything else, and, in spite of the masterpieces of his two contemporaries and his forerunners and successors, his contribution to the literature of that instrument remains, and is likely to remain, unique and incomparable. Liszt and Schumann, on the other hand, left a vast output other than their piano works. Liszt, to the end of his long life, was ever the iconoclast and revolutionary, creating his own forms and writing in an idiom like no one else's, even in his Piano Sonata, which is still a great sonata for all that. His work ranged over a wide field, and I suppose he has influenced his successors to a greater extent than anyone else, Beethoven alone excepted. Schumann, on the other hand, and away from the piano—for which he was such an incomparably greater writer than for anything else—worked in the classical German symphonic mould at symphonies, concertos, chamber music, etc., though his idiom was always that of the incurable romantic. Chopin died at 39, Schumann at 46, Liszt at 76.

Liszt was a kindred spirit of Berlioz, born in 1803, whose music has a modernity about it which often belies its 100 years' old existence. He was one of the greatest of French composers, but an individuality and a temperament as ardent as Liszt's were not long likely to remain under any one man's domination. He was the product of his age and his many-sided genius, taking him down roads that all looked ahead, influenced all who came after, none more so than Wagner. Wagner's overwhelming genius, however, canalised all music into his own operatic conceptions, and presided there without competitor or rival.

Debussy or Ravel

The æsthetics of Debussy and Ravel, 1862-1918 and 1875-1937 respectively, based largely on their

prodigal use of the tonal scale, have inevitably coupled them together in the listener-critic's mind, together, perhaps, with their common nationality. But these two great French masters are just as individual and different, each to the other, as are any one of the others I have mentioned. It would again seem to be in their piano music with its narrower frontier as compared to orchestral writing, that the greatest similarities occur.

Sullivan and Offenbach, Dvorak and Smetana, Borodin and Moussorgsky are among many other "pairs" which readily come to the mind. But space prevents their discussion. I would suggest, however, that a more general mixing of these great names in our musical criticism, and a less provincial and accepted attitude, would not only brighten things up considerably but might lead to undiscovered sources in the critic's art.

News from the Clubs

THE HOUNSLOW AND DISTRICT RADIO SOCIETY

Hon. Sec.: A. Pottle, B.Sc., 11, Abinger Gardens, Isleworth, Middx.

THE hon. secretary is now giving a course of talks on "Fundamental Radio" to the Hounslow and District Radio Society, which meets on alternate Wednesdays, at 7.30 p.m., at the Grove Road Schools, Cromwell Road, Hounslow—autumn session commencing September 8th.

SOUTHAMPTON RADIO CLUB

Hon. Sec.: John H. Sillence, 80, The Drove, Coxford, Southampton.

THE third annual general meeting of the Southampton Radio Club was held recently at 9, Bullar Road, Bitterne Park, Southampton. The main business of the meeting was the election of club officials for the following year, and the discussion of club policy and programme for that period.

Mr. P. Neves, A.M. Brit. I.R.E., A.M.I.E.T., Mem. R.S.G.B., the principal of the B.O.A.C. Radar School, Hythe (near Southampton), was elected president.

The president, in his opening address, stressed the fact that the rapid progress in radio during recent years was largely due to the efforts of the amateur enthusiast, and he felt sure that with increasing interest in radio as a hobby even greater progress would be made in the future. He hoped that educational authorities would give every encouragement to youth to take up radio, either as a career or a hobby. He added that in order to keep the club and its activities before the public eye, a number of popular lectures, to which the public would be invited, would be arranged. In the discussion which followed, it was decided that Morse practice would be continued, in addition to which facilities would be made available to members or intending members wishing to take up Morse at a later date. It was decided to supplement practical work with instruction in radio principles, designed to meet the requirements of members. It is proposed to build up a reference library, with donations of books by club members, further books to be added as and when club funds allow.

Anyone desiring details of the club's activities or to apply for membership, should write to the secretary, as above.

ST. PANCRAS RADIO SOCIETY

Hon. Sec.: H. Brown, 84, Blenheim Gardens, Willesden Green, N.W.2.

AFTER a most active and interesting session, the club has closed down for a summer recess. Main activities have this session been chiefly centred around the design and building of television sets from ex-Service radar equipment. This has been very satisfactorily done and sets were demonstrated to the public at an open meeting in July. As a result of much publicity there has been quite an influx of new members wishing to gain the necessary knowledge to build these sets for a cost of about £10, hence it is hoped to have a special television session when the club restarts in September.

Details of meetings and activities can be obtained from the secretary.

OSWESTRY AND DISTRICT RADIO SOCIETY

Hon. Sec.: A. D. Narraway (G2APW), "Lamorna," Pant, Oswestry, Salop.

ACTIVITIES recently include N.F.D. participation and the recent 5-metre field day. In the latter, G4LU, G2AUZ, G3ASC and G2APW organised and ran a site in Denbighshire, 1,300 feet above sea level, and at times above cloud level and almost "airborne," so strong was the gale force. The equipment was 1133G modified TX run at 6 watts; the RX was converted into R107. At a recent society meeting, G5JU travelled from Birmingham to lecture on 144 Mc/s. to a crowded meeting. Great interest is shared by a group in the society on 144—one member being kept busy on technical articles relating to 144 Mc/s.

At the annual general meeting the following officers were elected: chairman, Mr. E. D. Power (G3ASC); vice-chairman, Mr. S. Brown (G4LU); hon. sec., Mr. A. D. Narraway (G2APW); assist hon. sec., Mr. C. H. Banner (G3AHX); hon. treasurer, Mr. P. J. Fay (G3AKG); and a committee of four, viz., Mr. Woodhead (G2NX), Mr. N. Brown, Mr. A. E. Smith, Mr. K. Lord (G3AOX). The committee were requested to explore the possibility of a "shack," equipment for which had already been promised, and to draw up a programme suitable for all members on a weekly basis at the "shack." All interested are invited to communicate with the hon. sec., as given above, enclosing a stamped, addressed envelope. The society librarian continues to be Mr. J. Cripps, 11, Legge Street, Oswestry. The society has decided to co-operate in the newly organised Association of Midland Radio Committees' activities, the headquarters of which is Wolverhampton.

DERBY AND DISTRICT AMATEUR RADIO SOCIETY

Hon. Sec. and Treas.: F. C. Ward, G2CVV, 5, Uplands Avenue, Littleover, Derby.

ACTIVITIES in the society are increasing steadily. Meetings are held fortnightly, at present on Wednesday evenings. A series of lectures and demonstrations relating to television is now in progress. Morse classes are being arranged, and it is hoped to cater for all members' interests during the coming winter season.

New members will be welcomed and are asked to communicate with the hon. sec.

THE WEST MIDDLESEX AMATEUR RADIO CLUB

Hon. Sec.: Mr. C. Alabaster, 34, Lothian Avenue, Hayes, Middx.

THE above club continues to be extremely active, in spite of the summer season. Recent lectures were concerned with frequency modulation and radio-frequency heating.

One of the assets of the club is a small library of radio and technical books donated by members. The club also subscribes to two difficult-to-obtain American radio magazines which are circulated amongst members at a nominal fee.

Meetings are held on the second and fourth Wednesdays of every month at 7.30 p.m., at the Labour Hall, Uxbridge Road, Southall, Middlesex.

modern electrics

WE GUARANTEE IMMEDIATE DELIVERY.—Collaro Gram-unit chassis, with magnetic pick-up and auto stop, £9/13/2. Collaro auto changer ready for mounting, £23/2/0. C.W.O. only.

TEST INSTRUMENTS.—The entire range of Taylor Instruments now available on Hire-Purchase. S.A.E. for Catalogue and Terms.

STROSCOPES.—Single speed, 78 r.p.m., 50 cycles. 6d. each, 81d. post free.

SPEAKERS.—Unrepeatable offer, 6in. Celestion P.M. less transformer. New, boxed, guaranteed, 12/6 ea.

CONDENSERS. 2-gang, suitable for miniature sets, 350p.f., size 1 1/2in. x 1 1/2in. x 2 1/2in., 9/- each.

COILS.—“Hi Q” iron-cored, miniature L.M.S.; Ac, H.F. and Osc., 2/6 each.

SPECIAL OFFER OF ELECTROLYTICS. Not ex-Government. T.M.C., 32 mfd., 4/6; 16 and 8 mfd., 5/-; 16 mfd., 4/-; 8 mfd., 4/-.

CONNOISSEUR PICK-UPS.—We are still able to offer these at the pre-budget price of £4/4/7, including Transformer.

Under 20/- C.W.O. only. C.O.D. or C.W.O. over 20/- When ordering C.W.O. please allow sufficient for packing and postage.

MODERN ELECTRICS LIMITED,
164, Charing Cross Road, London, W.C.2. Tel.: Temple Bar 7587.

A FREE BOOK on Morse Code Training



There are Candler Morse Code Courses for **Beginners and Operators.**

Send for this Free “**BOOK OF FACTS**” It gives full details concerning all Courses.

THE CANDLER SYSTEM CO. (S.L.O.)
121, Kingsway, London, W.C.2.

Candler System Co., Denver, Colorado, U.S.A.

AN INDICATOR UNIT FOR 50/-!

Brand new type 73 Indicator units in maker's cartons.

Specification: 3 1/2in. C.R. Tube VCR.138A. Four H.F. Pentodes VR.65 (SP.41). One double diode VR.32 (EB.4), one diode VR.52 (EA.50). Four-position 10 water wave-change switch. Many potentiometers, resistors, condensers, viewing hood, etc. All in grey metal case, 5 1/2in. x 1 1/2in. x 12in. **NOTE:** VCR.138A has 4v. 1 A. heater and needs 1.50w. H.T. It is the best tube for oscilloscope work with a fine green trace of 5 milliseconds duration. (Equivalent ECR.35). The indicator unit packed in maker's carton for 50/-, plus 10/- for carriage by passenger train. Satisfaction guaranteed.

VCR.138A (for superscope) in stock.
A. McMILLAN,
5, Oakfield Road, Bristol, 8.

PRATT'S RADIO,

1070 Harrow Rd., London, N.W.10. (nr. Scrubs Lane). Phone: LAD. 1734.
AMPLIFIERS.—College AC10C, 10 watt, 4-valve, separate mike stage, separate mike and gram. inputs and faders, tone control, A.C. feedback. Price, £8/15/6. Model AC15E—15 watt 6-valve, with Push-Pull output stage. Feedback over 2 stages. Separate mike stage. Separate mike and gram. inputs and faders, tone control, complete with case. A.C. Supplies H.T. and L.T. to radio feeder unit. £14/14/0. Model U10E—10 watts output. Similar to AC15E, but for D.C./A.C. mains. Complete with case, £12/12/0. Model U10C—Similar to U10E, but chassis type amplifier, £10/15/6. All above match 3, 8 and 15-ohm speakers. Model AC4C—A.C. 4 watt, chassis, pick-up or radio amplifier. 3 valves. Feedback. Complete with o/transform. (3 ohms), £5/9/6. Model U4C—As AC4C but for D.C./A.C. mains, £5/5/0. Demonstrations available.

AMPLIFIER ACCESSORIES.—Speakers, Goodmans 12in., 130/-; Celestion 12in. 75/-; Goodmans 10in. 28/6; Rola 8in. 24/-; Microphones, Rothermel Crystal 60/-; 105/-; Pick-ups, Rothermel Crystal 60/-; Gramophone Motors, “Conrad” constant speed with 9in. turntable. A.C. 82/5.

MISCELLANEOUS.—Wearite P. Coils, 3/- each. Dual range Coil with reaction, 4/6; Standard Icore I.P.S. 483 kc/s, 13/9; Wearite £1; Wearite M400, 21/- pair; Midget I-valve Xformers, 3-1, 6/3, 5-1 6/6; Speaker Xformers: Pentode 5/9, Midget Universal 4/6, 5w. Multi-ratio 7/6, 30-watt 23/9; Class B Driver 7/6; Mains Xformers, Shrouded 350-0-350v., 6v., 5v., 80 m/a., 23/6; 100 m/a. (also 4v., 4v.), 27/6; 150 m/a. Unshrouded, 35/-. Presets, 50 pf. 10d., 100 pf. 1/3, 250pf. 2/-, .0005 2/3. Line cord, 2 or 3 way, 60 ohms ft., 8d. ft. V. clippers, with ft., 2s. (4,000 ohm), 3s. (800 ohm), 4/10 each. Speakers: 5in. P.M. w/tr., 17/6; 5in. P.M. 1/tr., 13/6; 8in. P.M. 19/6. Octal bases 6d. Condensers: 25 mfd. 25v. 1/8; 8 mfd. 500v. 3/6; 16 x 8 mfd. 450v., 6/6; 16 x 16, 450v., 7/9, etc. Dielectric Variables, .0003 and .0005, 3/-.

VALVES.—PRACTICALLY ANY STANDARD VALVE AVAILABLE EX-STOCK. 2/d. stamp for list or enquiries. C.O.D. or C.W.O. Post paid over £1. New goods only.

YOU can become a first-class RADIO ENGINEER

We are specialists in Home-Study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

T. & C. RADIO COLLEGE

KING EDWARD AVE., AYLESBURY

— Post in unsealed envelope 1d. postage —
| Please send me free details of your |
| Home-Study Mathematics and Radio |
| Courses. |
| NAME |
| ADDRESS..... |
| P. 93

L-R'S IN STOCK

CASH or EASY TERMS

- Goodmans “Axiom Twelve” Speaker Unit.—One of the finest quality speakers available to-day. Cash price **£8 8 0**
 - Avo Model 7 Cash price **£19 10 0**
 - Valve Tester, complete **£16 10 0**
- And practically the whole AVO range.
Avo Wide Range Signal Generator
An R.F. Generator of remarkably wide range and accuracy of performance. **£18**
Cash price
- Specifications of the above on request.

We can supply on convenient terms much of the Radio and Electrical Equipment at present available, all transactions being strictly between customers and ourselves.
Please let us know your requirements.

THE LONDON RADIO SUPPLY CO.
(Est. 1925)
BALCOMBE, SUSSEX

CALLING AMATEURS with BUCCLEUGH

Precision Built Equipment

Steel Chassis Smooth Black, 17 1/2in. x 10 1/2in. x 2 1/2in., 9.9. 17in. x 10in. x 2in., 8/9.



P.N.R.S. CRACKLE

19in. x 3 1/2in. 4/-
19in. x 7in., 6/9.
19in. x 8 1/2in., 7/9. 19in. x 10 1/2in., 8/9.
Angle Brackets, 12in. long, pr. 7/6. (Bright aluminium, same cost.)
RACK ASSEMBLY (Rigid 4-pillar), 3 1/2in., £2 5s. 63in., £3 5s. Chassis to order. Charges are as example, depth less than 3in. Example: 7in. x 5in. x 2 1/2in. totals 14in., at 6d. per inch—7/-.
Drilling Charges: Holes up to 1/2in., 3d. 1in., 1/2in. or 1 1/2in., 9d. each. Large, 2/3. Small square, 2/3. Large square, 3/6.

BUCCLEUGH RADIO MANUFACTURERS
1 & 2 Melville Ter., Edinburgh, 9.


DUNK & HEALEY AUTO-TRANSFORMERS

We announce a new range of finest quality auto transformers. Grade 1 stalloy cores, heavy cast shrouds, fitted terminal block. Standard ratings, 110v. to 230v. Type 14, 350 watts, £3/10/0; Type 17, 250 watts, £2/15/0; Type 20, 100 watts, £1/17/6. Other ratings and voltages to order. All brand new and guaranteed. Post Free.

REMOTE CONTROL RELAYS

Type AM6. By S.T.C. G.P.O. type, 6 to 12v. operating. Platinum contacts, 4-pole 2-way change over. Micro adjustments, 6/- each, post 6d.
Mail order only. C.W.O. or C.O.D. 2/d. Stamp brings list. All goods carry money back guarantee.
67 Osnaburgh St. London, N.W.1

H.P. RADIO SERVICES LTD. OFFER

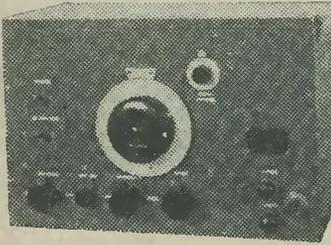

Brand New Ex-R.A.F. R1224a Battery Communication Receiver.

5 Valve Superhet of Exceptional Efficiency, 3 Wavebands: 30-70 m., 70-150 m., 150-300 m. Valves: 2 VP23s, FC2A, HL2, PM2A, all included. Has R.F. Stage, Muirhead precision Dial, Two Output Jacks, Low H.F. Consumption. Cabinet finished AIR MINIS-CRY grey. Size 13in. long, 10in. high, 8in. deep. Requires Aerial, 120 v. H.T., 2 v. L.T., 9 v. C.B. and Loud Speaker or 'phones to put into immediate operation. A Super DX receiver. Easy operation. All leads marked. Ideal for the Radio Amateur, Yachtsman, Lighthouse Keeper, Met. Stations and all remote locations.

Price £5 10s.. Carriage Paid per pass. train. Instant Delivery. Satisfaction Guaranteed or Money returned within 7 days.

H.P. RADIO SERVICES LTD.

Britain's Leading Radio Mail Order House,
55, COUNTY ROAD, WALTON,
LIVERPOOL 4

Tel.: Aintree 1445. Established 1935.
Staff Call Signs G3DLV, G3DGL.

SUPACOILS

COIL PACK "A"—3-waveband, 16-50/200-650, 800-2,000 metres superhet coil pack completely assembled and wired; incorporates 6 permeability tuned coils with adjustable trimmers for absolute accuracy in ganging and tracking. One guinea.

COIL PACK "B"—as above, with provision for R.F. Stage. Two guineas. I.F. TRANSFORMERS—465 kcs. High "Q" Litz wound, permeability tuned. 5/6 ea.; 10/- pair.

COILS—All normal frequency coverages. Permeability tuned. 2/- each. **TWO GANG CONDENSERS**—7/9 ea. **THREE GANG CONDENSERS**—13/4 each.

These are a selection from our shelves. All other radio and television components in stock at keenest prices. 21d. stamp for complete price list. Mail order only. C.W.O. under £2.

SUPACOILS

98 Greenway Avenue, London, E.17

THE LATEST IN KITS!

Complete in every detail including Beautiful Walnut Cabinet 13in. x 8in. x 6in. deep **for £7 - 17 - 6d.**

All main components mounted on chassis and wired. Simplest instructions and circuit included for completing in one hour. 3 valves plus rectifier. A.C./D.C. mains. 4 controls: Vol./Off—Tone—Wk—Tuning. C.O.D. or C.W.O. and Enquiries from:

LEWIS RADIO KITS
(Dept. A2), 322, High Road, Wood Green, London, N.22. 'Phone: BOW 5997

RADIOMART LIMITED

BARGAINS IN
EX-GOVERNMENT

EQUIPMENT for the AMATEUR

Variable Inductances for P.A. or Aerial Tuning. All ceramic construction by Johnson and others. 3½in. diameter x 6in. coil of 1/16in. x ½in. copper strip (26 turns) on rotating former, variable contact by means of heavy spring-loaded wheel bearing on outside diameter. A really superb job. Price only 20/- plus 2/- packing and postage. Smaller version of above (2½in. former) having 8 turns of 14 s.w.g., otherwise same principles. Price 10/- plus 1/- packing and postage.


R.A.F. Dipole Aerial 27in. (approx. 215 mc/s) with 3ft. Co-ax and Pye Plug, and built-in matching Transformer. Ideal for making into any frequency dipole. Price 2/6. Postage 1/-

Brand new Moving Coil 2½in. diameter flush msg. Meters, 0-50 m/A., 0-100 m/A., 0-500 m/A., 15/- each. Many other bargains in Meters. See our list. We have large stocks of high grade Co-axial Cable, ¼in. diameter 9d. per yard; ½in. diameter, 1/- per yard. Will never be repeated at these prices. Our List No. 7 contains many Special Offers. Send S.A.E. for your Copy to-day.

48 HOLLOWAY HEAD
BIRMINGHAM 1

Tel.: Midland 3254

THE ETA TUNER

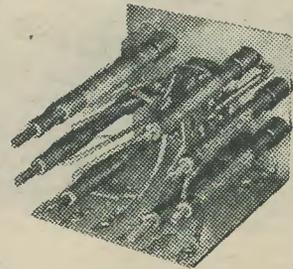

Type TS41
(Patent Applied For)

- ★ Is a complete pre-set tuning unit for use in superhet circuits.
- ★ Gives a choice of four stations, three MW and one LW.
- ★ Requires no tuning condenser, trimmers, or other extra components.
- ★ Uses a new type of inductor giving maximum sensitivity and stability.

Supplied with full instructions and a complete receiver design.

Price **33/-** (No Purchase Tax)

Obtainable from your local dealer or direct from

ELECTRO TECHNICAL ASSEMBLIES
West Hill, St. Leonards-on-Sea,
Sussex.

RADIOELECTRON

22, Frances St., Scunthorpe, Lincs.
New Goods Only.

ELECT. CONDENSERS, 500v., 4 mfd., 2/9. 8 mfd., 3/6. 8-9 mfd., 5/9. 8-16 mfd., 6/3. 50 x 50v., 2/8. 25 x 25v., 2/2. mfd. 350v., 1/1d. 25 mfd., 350v. "Metpack," 1/3. **TUNING CONDS.** Single Gang Const., 4005 mfd., 4/-.

VOL. CONTROLS, 5 k., 10 k., 25 k., 50 k., 100 k., 250 k., 500 k., 1 m., 2 m. Lg. Spdles. 3/3. with Sw., 5/-, 5 watt. Wire wound 2 k., 5 k., 7.5 k., 10 k., 25 k., 30 k., 50 k., 60 k., 80 k., 100 k. Less Sw., 5/-, 2 P., 2 W. Yaxley Type Switches, 2/-, T.R.F. Coils, M & L. Wave, 7/9 pr.

CARBON RESISTANCES all values, ½ watt., 5d., 1 watt., 8d. **PICCO ALL-IN-ONE RADIOMETERS**, 25/-.

VALVE HOLDERS, Brit. 4, 5 and 7-pin. 6d. Oct., 7d. U.X. 4, 5, 6 and 7-pin, 6d. Maz. Oct., 6d. Terms: Cash with order, post free over 10/-, under add 4d., C.O.D. extra. A 21d. stamp will bring you a copy of our latest list.

TELEVISION COMPONENTS SCANNING UNIT, to "Electronic Engineering" Spec., 30/- each.

LINE TRANSFORMER to match, 30/- each. **FOCUS COIL** (Electro Magnet), 36/- each. **SET OF THREE ABOVE**, £415/0 complete, carriage paid.

Complete set of blueprints and drilling templates ready shortly for home constructors of television receivers. S.A.E. for details.

A CRYSTAL SET FOR SIX SHILLINGS—All you require is a DUSTPROOF DETECTOR, price 2/6; SPECIAL TUNING COIL, price 3/6.

This coil is of very simple construction, there is no need to use a tuning condenser. Wiring instructions are enclosed with each coil. Any handyman should be able to make a novel little set using these two components plus a few odd pieces of wire and one or two terminals, etc., in an hour.

Trade supplied.
MORTONS
13, Camden Road, Walthamstow,
London, E.17.

BULGIN

A Name
famous
in Radio



A. F. BULGIN & CO., LTD.
Bye Pass Road, Barking, Essex
Tel: RIPpleway 3474 (5 lines).



'Radiospares'

Quality Parts

The

Service Engineer's

First Choice



Impressions on the Wax

Review of the Latest Gramophone Records

THIS month sees the issue of the second volume of the Medtner Society, which owes its inception to the munificence of H.H. the Maharajah of Mysore. The main work in the new volume is one appropriately dedicated to His Highness, namely, the Third Pianoforte Concerto, Op. 60. The composer himself plays the solo part in this and, as in the previous volume, he takes the keyboard where it is required in the remaining items. There are two of these. In the first, Margaret Ritchie's fine voice is heard in the Sonata-Vocalise, Op. 41; in the second, Medtner plays his Improvisation, Op. 31, No. 1. The seven H.M.V. records, which are available to special order only, constitute a survey of Medtner's music which will be found quite as attractive as that in the first volume.

Debussy's "Cathédrale Engloutie" is based upon an old Breton legend of a cathedral under the sea, whose bells may be heard tolling amid the sound of the waves. This legend seems a favourite one among Celtic peoples, for a variant of it exists in North Wales. "Clair de Lune," from the Suite Bergamasque, probably excels its companion piece in popularity owing to its use as a leading motif in the romantic "Frenchman's Creek" released a few years ago. Both of these piano pieces are played by Harriet Cohen on *Columbia DX1496*.

An interesting release which should have a wide appeal is Handel's "Royal Firework Suite," played by the Liverpool Philharmonic Orchestra, conducted by Sir Malcolm Sargent, on *Columbia DX1494-5*. Handel's original score specifies nine trumpets, nine horns, 24 oboes, and 20 bassoons, with optional strings. Georgian England liked its open-air music to be audible, and Handel assembled this massive array of wind with the English taste in view. To us, all these oboes and bassoons are far too top-heavy, and a body of strings to balance them would be unwieldy for ordinary concert purposes. To Sir Hamilton Harty goes the credit of bringing this excellent music to manageable proportions by making a selection of the numbers, scored for a normal modern orchestra, constructing a "Fireworks Music" suite on the same lines as his "Water Music" arrangement.

Maurice Ravel's Concerto for the Left Hand was written in 1931 for Paul Wittgenstein, an Austrian pianist whose right arm had been amputated during World War I. If you did not know for a fact that the concerto was specifically designed for a one-armed executant it would be hard to imagine so from hearing the records. It is played by the French pianist, Robert Casadesu, with the Philadelphia Orchestra, conducted by Eugene Ormandy, on *Columbia LX1088-9*.

Vocal

That very popular tenor, Beniamino Gigli, sings in Italian in his latest recording of "Segreto" and "Nostalgia d'Amore," on *H.M.V. 6705*. Tosti wrote multitudes of admirable songs during his settlement in England as singing-master to the Royal Family. These songs come into the category

of drawing-room ballads, but the best of them are free from the rather milk-and-water sentiment sometimes found in the Victorian salon song "Segreto," of course, merely means secret, and the secret concerned is evidently one of the heart. "Segreto" pairs well with "Nostalgia d'Amore," whose title we need not translate.

Another popular tenor is Josef Locke, and he has recorded two Irish songs in "Dear Old Donegal" and "The Rose of Tralee," on *Columbia DB2429*. He arrived at fame by way of Irish festivals, and it was John McCormack who advised him to develop especially his talent for ballad-singing.

Mme. Welitsch scored a triumph at the Cambridge Theatre this spring, being acclaimed especially for a superb performance of Donna Anna in a new production of "Don Giovanni." Opera of many kinds is her province, and in giving us this month a recitative and aria from Weber's "Der Freischütz," on *Columbia LX1090*, she has provided highly interesting and attractive fare for listeners to whom this opera means only the great, but over-worked, overture.

Variety and Dance Music

Bill Johnson is heard in a new song, "Siesta Serenade," on *Columbia DB2433*. As the name implies, the song has Spanish overtones. Turning over the record we find "Calling for You," English version of the famous Italian song, "Core 'Ngrato," which was featured in the British film, "Man About the House."

Dinah Shore, now in this country, has recorded "Crying for Joy" and "Little White Lies," on *Columbia DB2430*, whilst Frank Sinatra sings "If I Only Had a Match" and "We Just Couldn't Say Good-bye," on *Columbia DB2431*.

Tony Martin has recorded the impressive "Tenement Symphony" which he sang to good effect in the M.G.M. film, "The Big Store," on *H.M.V. B9666*, and the popular French singer, Jean Sablon, sings "Miranda" and "Don't Take Your Love from Me," on *H.M.V. B9667*.

Geraldo and his Orchestra have made two records this month in "A Kiss and a Rose" and "Woody Woodpecker," on *Parlophone F2305*, and "October Twilight" and "When You're in Love," on *Parlophone F2306*. These latest recordings bear witness to Geraldo's musicianship and band-leading ability, and provide his large following with the instrumental and vocal blend that has made him such a constant favourite.

SAVE THAT CARTON

Every empty breakfast-food, sugar, cigarette, soapflake packet is urgently needed for salvage.

ALEC DAVIES SUPPLIES LTD.

18, Tottenham Court Rd., London, W.1.

Tel.: Mus. 4539. Tel.: Mus. 2453.

Introducing a few of our very many attractive Surplus Lines:

VCR97 6in. electrostatic C.R.T.s, new and boxed in original cardboard cartons (Callers only), 39/6.

Mu-metal screens for use with the above, only 2/6.

Silicon H.F. crystals for use up to 10,000 Mcs., standard midget type CS7A, post free, 5/-.

Low resistance headphones complete with lead and jack plugs. Postage, etc., 6d., 2/6. Balanced armature phones, complete with switchable balanced armature desk mic. and stand. Postage 6d. 7/6.

Training buzzer and Morse Key mounted on solid wooden baseboard. Complete except for 6v. bell battery. Postage 8d. 3/6. Metal screening box in thin sheet metal, sprayed inside and outside. Detachable lids at both ends. Size 4in. x 4in. x 8in. Ideal for small screening boxes. Postage 6d. 1/-.

Sound power hand sets. Similar in appearance to standard G.P.O. type, but for use without battery. Postage 9d. 7/6.

Standard 3-gang, .0005 variable condenser for use with drum drive. Spindle length 15/32in., spindle diameter 11/32in. Postage 3d. Only 3/6 each.

Permanent crystal Detectors, all new and boxed. Postage 3d. 2/6. Replacement crystal elements. Postage 1d. 6d.

Medium wave single winding coil for crystal set. Postage 3d. 1/6.

.0005 Variable Condenser, solid dielectric type. New and boxed. Postage 3d. 4/6.

Stockists of Radio and Television Components of All Types. Full range of Eric Resistances & TCC condensers always available.

Most People Stop

at PALACE GATE!

Many people, on buying an Amplifier make a tour from manufacturer to manufacturer. But most people stop at Palace Gate where the Concerto and the Kl are demonstrated. There must be a reason! Write today for our new 16-page copiously illustrated catalogue and interesting information on the complete range of Amplifiers and Tuning Units, in kits or complete form and a new corner chamber, supplied with or without loudspeaker, to Dept. P.W.1

Charles
AMPLIFIERS
1e PALACE GATE
KENSINGTON, W.8

Phone: WEStern 3350

CRAIG'S LATEST

Radio Circuit. Personally designed, tested and guaranteed. No experience needed to build this super T.R.F. 4-valve set. M.W. A.C./D.C. High Quality Output. Clear Diagrams. Detailed instructions, parts list, etc., 3/6.

R. CRAIG, 64, Conyer's Road, Streatham, S.W.16.

"Radio Unlimited," 16, Carnarvon Road, Leyton, E.10

"Return of Post" Mail Order Service. Outstanding items this month include: A.C. radiogram chassis, 3 wave, 4t watt output. Complete with valves and full size speaker. Price inc. tax, carriage, etc., 14 ens.

Quality radiogram cabinet, of acoustic artistic design, £25. 15 watt amplifier. Input, Mic/Gram./Radio. Tapped output 12 ens. A.C. gram. motor and table, £3 11s. M/Coil microphone 3/6. Phones, 3/6. S.A.E. for full detailed list

COMPARE OUR PRICES!

Standard I.F. transformers (465), Litz wound, iron-cored, in aluminium cans, 5/- ea. .0005 2-gangs, 7/6 ea. 3-wave s/het coil packs, aligned and tested (with circuit), 21/-, or with R.F. stage, 39/- I.F. filters, 2/- ea. Experimenters' parcels of first class radio gear (not junk), £1. All the latest radio books. 500µA meters, 7/6 ea. Chassis from 4in. ea. Mail order only. Send stamp for latest list in which all prices have been cut by nearly half to clear huge stocks of manufacturers surplus. All goods brand new. C.W.O. under £5. All orders nett. Post and packing extra.

RODING LABORATORIES (EL),
70, Lord Ave., Ilford, Essex.

O. GREENLICK, LTD.

TELEVISION COMPONENTS, for W.W. and E.E. circuits Scanning Coil unit, 30/-; Line Transformers, 30/-; Focus Coil, 32/6; Vision E.E. Chassis with wave holders and coil formers, 22/6; ditto Sound Chassis, 18/6; set of 8 coils fully wound, 15/-; Rubber Masks for 9in. tube, 15/-; E.E. Television Constructions Manual, 2/6.

TEST PRODS.—Polished ebontite prods. metal tipped 5ins. long on flexible leads with plugs, pair, 4/-.

CONDENSERS.—Ultra midget 2-gang condenser, as used for Personal portables, 10/-; standard ditto, 0.0005 mfd., 8/6; variable resistances, 350 ohms 1 amp., 15/-; 450 v., 2/6; 8 plus 16, 450 v., 5/6. Paper, 9d. and 65 mfd., 6/- dozen; 4 mfd., 100 v., 9d. each.

DIALS / DRIVES.—Horizontal Drive assembly, S.M.L. dial, 10 x 4ins., 2 hole fixing, 22/6; S.M.L. dial, 5ins. by 8ins., 4/6 Pan, 4/6. Escutcheon, 5/6. Full Visions Drive assembly, with glass escutcheon, etc., 7/ins. by 4ins., 12/6; ditto Square Plane, M.L. 4ins. by 3ins., 11/6; Dial, S.M.L. by 3ins., 1/-; ditto, 5ins. by 5ins., 1/6. Drum drive (drum, pulley, spring), 3/-; epicycloid drive, 2/-.

RESISTANCES.—Mains droppers, 600 ohms 0.3 and 1,000 ohms, 2/4- each. Heavy duty variable resistances, 350 ohms 1 amp., 15/-.

CABINETS.—Table Model Walnut veneered, 21ins. by 10ins. by 7ins., 40/-.

TRIMMER KITS.—In smart metal case, comprising 17 tools, for the service engineer. Quality product, 45/-.

SPEAKERS.—P.M. less trans, 5ins., 15/-; 8ins., 17/6; 6ins. O.M. with trans., 22/6.

ROTARY TRANSFORMERS, in 6/12 v. out 200/480 v., 50 mA., or as small motors, D.C. Mains, 15/-.

WIRE TAPERS.—Non Synchronous, 6 volt, 4-in. 6/-.

SWITCHES.—Yaxley type, 3-pole, 2-way; 2-; 4-pole, 3-way; 3-; 4-pole, 4-way, 3/6; midget ditto, 4-pole 2-way, 3/-; 4-pole 3-way, 3/-.

Our list at 21d., gives full details of all stocks.

Nr. Whitechapel Met. Station.
265, Whitechapel Road, London, E.1.

Phone: BIS. 5079

FIRST-CLASS RADIO COURSES . . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., M.I.E.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Matic., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSSES

NATIONAL INSTITUTE OF
ENGINEERING

(Dept. 461), 148, HOLBORN
LONDON, E.C.1.

HIGHSTONE UTILITIES

Crystal Sets.—Our latest Model is a real radio receiver, which is fitted with a permanent crystal detector. Why not have a set in your own room—9/6, post 6d. De Luxe Receiver in polished oak cabinet, 18/6, post 1/-.

Spare Permanent Detectors, 2/- each. When ordered separately, 2/6, post 3d.

Headphones, reconditioned and in good order, 5/6, post 6d. (better quality, 7/6).

New Headphones, 10/- a pair, post 6d. Balanced armature type, very sensitive, and very suitable for use with crystal sets).

12/6 a pair, post 6d. **New Single Earpieces**, 3/6. Bal. armature type, 4/6; ex-R.A.F. earpiece, 2/-, post 4d. **Headphones** with moving coil mikes, 15/-.

Similar phones with throat mikes, 12/6, post 8d. **Headphone Cords**, 1/3 a pair, post 3d. **Replacement Bands**, 1/3, post 4d. **Wire Bands**, 6d.

Hand Microphones, with switch in hand, 2/- each, 4/-.

Similar instrument moving coil, 7/6, post 6d.

Sparkling Plug Neon Testers with vest pocket clip, 3/3, and with gauge, 3/6, post 3d.

Telephone Sets, with ringing hand generators, bell, twin bells and C.T. type handcomb, 30/- each, carr. 2/6. 57/6 pair, carr. 3/6.

New handcomb sets, 7/6, post 6d. Telephone hand generator with handle, 9/6, post 1/6. Bell, 4/6, post 6d.

Ex-R.A.F. 2-valve (2-volt) Amplifiers, can be used to make up a deaf aid outfit, intercommunication system, or with crystal set, complete with valves, 20/-.

Meters, All brand new, 0-1 mA., 2in. m/c, 10/-; 3.5 amp., 2in., T.C., 7/-; 4 amp., 2in. thermo coupled in case with switch, 7/6. 600 mA., 3in., m/c, 15/-.

Double reading 40/120 mA., 2in., m/c, 8/-; 20 amp., 2in., m/c, 9/6; 15 volt 2in., m/c, 9/6; 30 amp., 6in., m/c. Switchboard mounting, 35/-; 6,000 v., 3in. m/c, 57/6. Post Extra.

Money refunded if not completely satisfied.

HIGHSTONE UTILITIES,

55, New Winstead, London, E.11.

Letters only.

New Illustrated List of above and other Lines enclosed with all orders on request, with 1d. stamp.

Open to Discussion

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

Photographing C.R. Tube Image

SIR,—I was interested in an article you published a few months ago on the photographing of cathode ray tube traces. The contributor infers that a camera of some sort is necessary.

I have recently experimented with gaslight paper applied direct on to the C.R. screen and have produced the enclosed. One is a 50 cycle sine curve and the other a distorted phase ellipse from an iron-cored choke. For this method of photography the trace must be steady, as the exposure time is about 30 seconds. The third oscillogram is a "printed through"; this forms a method of making many copies of one good oscillogram.

The great advantage of this method is its low cost, about four pictures for a penny. The oscilloscopes I use are one I made from a unit using VCR97 and the other one I built using a Mullard ECR.30.—F. F. LEE (Beverly).

[The "pictures" were quite good, and would serve, no doubt, for the majority of cases where permanent records were needed. We regret that they were not suitable for reproduction.—Ed.]

Push-pull R.F. Stages

SIR,—Readers may be interested in my experimental circuit from the discussion point of view.

A short time ago I was working out some details for a push-pull output stage when the thought struck me: "What advantage would be gained by having a push-pull R.F. stage?" Of course, a similar system has been used for the balance of dipoles, but not in commercial use for domestic receivers. I put the point to some leading engineers, but they could not give a satisfactory answer or deny the possibilities of such a system.

One point is, will it give a better signal-to-noise ratio, better amplification or even reduce fading to a minimum using the usual A.V.C. system? I have started to build a receiver using this method for the R.F. stage, and have yet to see the result. However, I can give a few details of the practical construction.

The two R.F. coils tuning the grids of V1 and V2 are a matched pair of P type coils with the aerial windings joined in series. The earthy ends of the grid windings are joined to a common point on the A.V.C. line (E), and the usual A.V.C. on/off switch is used to short the line to earth on the chassis.

The general snag came with the method to be used in getting a required centre tap to feed the H.T. to the anodes of V1 and V2; to unwind the primary of the H.F. coil and connect a centre tap without the use of a coil winding device would have been impracticable. The alternative was to couple an H.F. choke across the primary and place a centre tap on the choke where the two centre windings are joined. The secondary winding is used to tune the grid of the frequency changer as with conventional circuits. The tuning of the

circuits is carried out by using a four-gang .0005 μ F. variable condenser with small capacity trimmers to balance out any difference of capacity in the ganged condenser, especially in the first stage, which must be carefully balanced to prevent any difference in frequency between the two valves.

The last point is that R.F. valves V1 and V2 use a common bias network with the addition of a gain control of about 10k ohm.

This system is to be used with a superhet using push-pull output which requires the use of a 10 valve chassis.—F. P. SLEIGHT (Cleethorpes).

"What Is a Classic?"

SIR,—As regards the definition of a "classic," I have always regarded a "classic" as something which has stood the test of time. I apply this definition to all types of music, including jazz. In this way, I would call both "Tiger Rag" and one of Tchaikowsky's famous works, "classics."

I am inclined to reconcile this view with that of Mr. Steven Lane, for music which, played on an appropriate instrument, neither produces the desired effect nor a pleasing one can scarcely be expected to withstand the sharp scythe of Father Time!—D. R. H. DAVIS (Armagh).

C.R. Tube Data

SIR,—Some months ago you were good enough to publish a letter from me in which I urged readers who have purchased items of ex-radar equipment containing such things as cathode ray tubes VCR97, etc., to visit the Science Museum, Kensington, where they may recognise some surplus items which they might have purchased, set out and explained.

It is unfortunate that the publication of my letter coincided with the withdrawal of almost all of this equipment from the exhibition galleries.

However, it will all be on view again at the Radar Exhibition, which will, I understand, follow the present Illuminations Exhibition in the Science Museum.

A lot of people fail to understand that these tubes (VCR97, etc.) were not all made by one maker. They were all, like the VR91 (EF-50), made by various makers for the Government. I have seen VR91 valves which were made in America and Canada to the original Mullard specification. I believe the original VCR97 was G.E.C.

The one I purchased (in a 6A unit) had A¹ (pin 5) not connected to pin 5. But A¹ and A² are strapped internally and connected to pin 9. Pin 7 should, however, be connected to the coating and is so in my sample. (See C. R. Talbot's letter in the August issue of PRACTICAL WIRELESS.)

These tubes were used for different purposes. The unit 6A with a VCR97 was used in aircraft in connection with the "Aid to Surface Vessels" equipment, as was the 6C, both being fed from

a common transmitter and echo receiver, working from a positive pulse, the type 6 unit working from a negative pulse.

The 6A was used by the navigator and the 6C by the tail gunner of a bomber. (Tube type VCR 138.)

The type 6B unit was used in the F.A.A. in conjunction with transmitter type T3040E and receiver type R3839E.

Hoping this information will be of value.—
W. J. LAW (Ealing).

SIR,—I agree with Mr. C. R. Talbot (the C.R. is very appropriate) about the possibility of getting into trouble by making use of data in the April and February issues.

I must say that the articles by the Bristol correspondent were extremely valuable in other respects. The possible variations of VCR97 are: No. 5 to A¹ (if not already strapped internally to A³), No. 7 to graphite coating (if not already strapped internally to A³). The other connections which are standard being: No. 1 to modulator, No. 2 to cathode, No. 3 and 4 to heater, No. 6 to A³, No. 8 to Y², No. 9 to X², No. 10 to A³, No. 11 to X¹ and No. 12 to Y¹. The contact number is taken from location spigot, reading clockwise when looking into the base end of the tube and anti-clockwise when looking at the holder as when wiring up the unit. When, as is usually the case, the A³ is connected to the earthy end of E.H.T., it is best to connect A¹ (No. 5), graphite coating (No. 7) and A³ (No. 10) together in wiring up the holder, as this will take care of any possible variations of the VCR97.

I should be grateful if any reader could advise through this column on getting a Miller time base to synchronise with the signal and give fly back suppression without undue distortion of trace.

Also, where can I obtain high voltage H.W. metal rectifiers of 1,000 v. at a few mA and what are reference numbers of any suitable for C.R. use?—
H. COOPER (Shaw).

"Desert Air-mail"

SIR,—With reference to your article "The Desert Air-mail," a mistake has been made in the last line. Our basic salary was £6 5s. weekly plus the 5s. an hour flying pay.

I am the holder of the first "Working" Air P.M.G. Licence. Capt. Duncan Sinclair, the examiner, has No. 1, I have No. 2, and I was the radio officer on Imperial Airways' first DH.66 to leave Croydon on the way to open their Eastern Service between Cairo and Karachi. The Chief Pilot, Capt. Woolley Dodd, was in charge, and we had Air Vice-Marshal Sir Sefton Brankner, the Assistant Secretary of State for Air, with us.

Incidentally, I transmitted, on Sir Sefton's behalf, the first two "Air Telegrams" to be sent from a British aircraft. I still hold the originals in Sir Sefton's handwriting. One was to the Air Ministry, and the other to an address in New York. They were transmitted during the flight from Gaza to Rutbah Wells and accepted for re-transmission by Rutbah, the Iraq Posts and Telegraphs Station.

I would very much appreciate the present address of my old friend and colleague, N. E. Wood; we were together for many years in both the R.A.F. and Imps.—A. E. BOOTH (Redruth).

L.S. Output for R.1155

SIR,—Some time ago I bought an "1155" set, having to convert it myself. I managed to get circuit details of the set and so "rigged" it up O.K. The snag is that I want to convert it to L.S. output, and up to present I'm afraid I haven't been very successful.

I wonder if one of your readers has had the same difficulty! If so, perhaps he could forward on to me circuit details, etc., of a L.S. stage for the "1155." I will gladly answer all letters and return any books or notes which are wanted back.—F. G. SHEPHERD, 12, Mill Road, Waterlooville, Hants.

Ex-Service Equipment

THE co-operation of readers is sought in helping others out of difficulties regarding items of surplus gear as follows:

- W. G. W. Highfield, 91, Uplands Avenue, Wolverhampton, Staffs, wishes to contact a reader who may have experienced in converting the Test Set Type 72 to 2½ and 5 metre bands.
- T. B. F. Perkins, Slapton, nr. Towcester, Northants, is in need of circuits and technical data of Rx. 3554.
- G. Hughes, 14, Fraser Grove, St. Annes, Carlisle, requires data on the valve VCL11, from the German Sachsenwerk receiver.
- S. D. Dickinson, 12, Kingswood Road, Birmingham, 13, would like information on the Monitor Type 27 and German Services. Battery-Mains portable Siemens, K. 32.GWB.
- J. Agius, 69, St. John Baptist Street, Sliema, Malta, requires data on T.1154.F, especially so far as conversion for experimental purposes is concerned.
- J. M. B. White, 63, Alexandra Road South, Whalley Range, Manchester, 16, requires details of the power supply section, etc., of modulator type 60.
- F. Lewis, 1, Manor Crescent, Brampton, Chesterfield, Derby, would appreciate the load of the circuit of R.1124.C with a view to conversion to standard television reception.
- A. L. Moon, 1, Montague Cottages, Hankian, Wisham, Pevsey, requires circuit diagrams of C.R.P. Indicator unit, type 6a and 6b and Rx/Tx R.3003.
- J. W. Collier, 5, Crescent Road, Heybridge, Maldon, Essex, would like information of R.3170.A.
- R. J. Cox, 26, Gillingate, Kendal, Westmorland, requires circuit diagrams and any other details of B.C.342 or B.C.312.
- H. E. Rule, "Montaza," Kyle Avenue, West Hartlepool, wishes to contact any reader who has experimented with A.1134 from the point of view of making it into an inter-communication unit for the home.
- T. Mair, Homeleight, Papworth Everard, Papworth, Cambridge, would like assistance in converting the 33 A.F.V. Walkie-Talkie to dry-battery use.
- J. M. Henry, c/o Love, 99, St. Andrew's Road, Pollokshields, Glasgow, S.1, requires information, especially heater diagrams, of the B.C.454 series command receivers.
- H. G. Hartshorn, W/O and Sgts. Mess, No. 11 H.Q. Regt., R.E., Harper Barracks, Ripon, Yorks, wishes to convert indicator unit type 230 and wave meter unit W.1646 to a modulated signal generator.
- T. V. Attwood, 32, Park Lane, Netherton, Aintree, Liverpool, 9, needs information on T/R3523.E, and amplifier type 226.
- E. K. Rigby, 53, Alan Road, Withington, Manchester, 20 requires circuit diagram of T/R9.H.
- T. Young, 53, Limes Grove, Lewisham, S.E.13, requires circuit of R.1124.C and details of power supply.
- F. Taylor, 9, Bolton Road, Moses Gate, Farnworth, Lancs, requires information on Bendix B.C.433.G, and the number of the control box.
- J. A. Brockie, 77, Burns Road, Aberdeen, needs details of the sockets and terminals, etc., of the U.E.1, 12-volt Vibrapack.
- R. L. Woods, 27, Stavely Road, Leicester, would like details of Beacon receiver B.C.1206A.
- W. R. Blaxland, Eastern Garage, Shoreham-by-Sea, Sussex, would like particulars or service sheet of indicator unit ASB-8 radar unit R-9A/APN-4.
- E. H. Davies, 263, Endlesham Office, S.W.13, would like data on the R.1147A.
- J. Ewart, The Old Post Office, Ecclefechan, Dumfriesshire, would like details for fitting "S" Meter and converting for use on 10 and 20 metres, the receiver R.1224.A.
- P. N. Hollis, 143, Lynton Avenue, Leigh-on-Sea, Essex, is in doubt regarding the connections at the rear of No. 52 communications receiver.
- C. E. Jones, Tegfryn, Ruthin Road, Moki, Flints, is desirous of contacting anyone who may have experience in converting B.C.433.G, for mains operations.

CLASSIFIED ADVERTISEMENTS

RATES: 3/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless", Tower House, Southampton St., Strand, London, W.C.2.



By Order of the Minister of Supply WITHOUT RESERVE
STAVERTON, GLOS.
 A sub-site of No. 7 Maintenance Unit, R.A.F., on the main Gloucester-Cheltenham Road, about 4 miles from each.
PUCKLECHURCH, Near BRISTOL
 About 8 miles North-East from Bristol, and
BABDOWN, Near TEBURY
 About 3 miles from Tebury and 1 mile from the main Bath-Nailsworth Road.
J. PEARCE POPE & SONS
 Will Sell by Auction at **STAVERTON, GLOS.,**
 a Large Quantity of **A.F. & AMERICAN SURPLUS R.F. & AMERICAN EQUIPMENT**
 including:—
 Radio Receivers, modulators, Rectifiers, Transformers, Dynamotors, Balloons and Balloon Fabric, Generating Sets, Trolleys, Oil Refiners, Steel Cable, Ladders, Tools, etc., etc.

on **FRIDAY, SEPTEMBER 17th, 1948.**
 Commencing at 10 o'clock punctually.
VIEW DAY ON TUESDAY, WEDNESDAY,
and THURSDAY, SEPTEMBER 14th, 15th and 16th, from 10 a.m. to 4 p.m., also on day of Sale from 9 a.m. to 11 a.m.
 CATALOGUES, price 6d. each (postal orders only) may be obtained from **J. PEARCE POPE & SONS, ST. ALDATE CHAMBERS, GLOUCESTER.** Phone: 21274/5.

ADMISSION WILL BE BY CATALOGUE ONLY.
EDDYSTONE Short Wave Radio. Stratton and Co., Ltd., are now in a position to consider applications for a limited number of registered dealerships in areas not already covered. Applications are invited from expert and enthusiastic Shortwave specialists at home and abroad. Write Stratton and Co. Ltd., Eddystone Works, Alvechurch Road, West Heath, Birmingham, 31.

RADIO Constructor's Catalogue. 20-page Catalogue, packed with hundreds of items of interest to the constructor, service engineer and experimenter, plus details of our Technical Query Service. Price 4d., post free.—Cussins and Light, Ltd., The North's Leading Radio Engineers, King's Square, York.

R.S.G.B. TECHNICAL PUBLICATIONS. The following are of special interest to transmitting amateurs and short-wave enthusiasts.

VALVE TECHNIQUE. Presents the calculations associated with the application of thermionic valves. 104 pages. Fully illustrated, 3/9 post free.

V.H.F. TECHNIQUE. Comprehensive account of techniques employed for generation, propagation and reception of frequency between 30 and 300 Mc/s. 96 pages. Fully illustrated, 3/9 post free.

MICROWAVE TECHNIQUE. Describes theory and practice of microwave technique. 68 pages. Fully illustrated, 2/3 post free.

SERVICE VALVE EQUIVALENTS. Third edition. Lists commercial equivalents of Service and CV valves, also Cathode Ray Tubes. 36 pages, 1/- post free.

THE TRANSMITTING LICENCE. Second edition. How to obtain an amateur licence. 32 pages, 1/- post free.

R.S.G.B. BULLETIN. Monthly publication of R.S.G.B. 1/6 post free. (Free to Members.)

THE RADIO SOCIETY OF GREAT BRITAIN
 28, Little Russell Street, London, W.C.1

BARGAINS in ex-WD. equipment. 12 volt I.F.F. rec./transmitters, 10 valves, motor generator, etc. New in cartons, 25/- C.P. Transmitter tuning units. TUBB, TUBT, TUBOB. (Easily converted to simple transistor as per "Radio News" Nov. 1947.) Complete with black crackle case, 16/- C.P. Send S.A.E. for bargain list.—Fanthorpe, 6, Hepworth's Arcade, Hull.

RECEIVERS & COMPONENTS

KITS of Radio Receivers. Electric and Battery. New materials. Table and Semi-midset models. Cabinets. Latest kit, Wylywyn Star, 3 wave, connections for gram pick-up; ext. speaker. A.V.C. All kits have illustrated descriptive constructional details. Lists. Radio components, gram, turntables, motors, pick-ups. C.W.O. or C.O.D. Amateurs' queries welcomed. Good stocks Valves, Cathode ray equipment.—Islerwoods, Remo House, 81, Plunging Road, Preston, Lancs. Tel. 3848. Estd. 1936.

GLEN RADIO for quality components at lowest prices. Send for lists.—411, Union St., Aberdeen.

RADIO.—Huge purchase of ex-R.A.F. surplus radio gear for sale at bargain prices. Receivers, transmitters, power units, viewing units, black-out units, converters, control units, etc. etc. Bargain prices. Very useful gear. 7/6, 10/- and 20/-. Send S.A.E. for complete list—it will pay you.—L. Glasscock, Radio Shop, 25, Bridge Street, Downham Market.

MIDGET PENTODE OUTPUT TRANS.—35 m.a., 40:1, 3/- ea. P.M. Speakers, best makes, 5in., L.T. 10/11; 6in., with trans. 18/6; 8in., L.T. 16/9; 10in., L.T. 25/-. M.C. Transformers fully shrouded; 350-0-350 v., 100 m.a., 6.3 v. 3 a., 5 v. 2 a., 22/6; 350-0-350 v., 80 m.a., semi shrouded, 6.3 v. 3 a., 5 v. 2 a., 19/9; 275-0-275 v., 80 m.a., semi shrouded, 6.3 v. 3 a., 5 v. 2 a., 18/11. All with well screened primaries. Selection of Rectifiers, small sizes, 250 v., 60 m.a., 4:1; 50 v., 80 m.a., 5/6. Chassis, 16-gauge aluminium, 10x5x2in., 3/6; 11x8x2in., 4/-; 12x8x2in., 4/9; 16x8x2in., 5/9; 20x8x2in., 6/9. Govt. Surplus Lincs. Smoothies, Chokes, 40 m., 120 ohms, 30 ohms, 60 m., 10h., 100 ohms, 3/6. Mallory Vibrators, 12 v. 4-pin, 4/- ea.; Vibrator Transformers, 12 v. input, 240 v. output, 6/6; Condensers, wire-ended, .005 mfd., 1,000 v., 3/6 doz.; 1 mfd., 350 v., 3/9 doz.; 4+8; 3-way, 60 ohms, per ft., 6d. ft.; 2 a., 3-way, 90-100 ohms, per ft., 7d. ft. C.W.O. or C.O.D., postage extra. Lists 2d. Trade supplied.—Radio Supply Co., 15, Queen Square, Leeds, 2.

ALUMINIUM CHASSIS and panels. Any size made. Plain or punched for valve-holders, etc., from 3/9. Coils, superhet coils, I.P. transformers, gang condensers, etc. Lowest prices. All new and guaranteed. Technical data sheets and lists free on request.—Read, 13, Bence Lane, Darton, Barnsley.

R3515.—New 44. R1355 with R.F. Unit, 44. Circuits, etc., 6A. Indicator, 92 15s. R.F. 25 Unit, 10/-. Rotary 24 v. D.C. to 230 v. A.C., 250 watts, 44. EA50 with 44. Indicator, R. and C., 5/-. S.A.E. particulars.—G. Adcock, Norwich Road, Watton, Norfolk

SPARKS' DATA SHEETS provide detailed descriptive matter and full size Constructional Print of Designs Tested and Guaranteed by

L. ORMOND SPARKS
NEW DESIGNS:
THE "CRUISER"—An All-dry, High-efficiency 3-valve T.R. Circuit. Three Tubes. Fine range, power and quality. Low cost. Good selection of stations on M/L waves with short aerial. Designed for those wanting a compact, all-dry, trouble-free design for the home, caravan, camping, yachting, etc. ... 2/6
"OLD FOLK'S TWO"—An A.C./D.C. 2-Valver Plus Rect. for those who cannot be bothered with tuning. 3 Station Selection by Switch, L/M Waves, 31 Watt Output. Easy-tuning and Reception. 2/9
"THE CUB"—A Fine Little A.C./D.C. 2-Valver Plus Rect. M/L Wave receiver. Powerful, Inexpensive and Simple to Build. 31 Watts. Good response. ... 2/6
THE "CADET" A.C./D.C. AMPLIFIER—The youngest addition to my famous range of Amplifiers. A full 31 Watts Output. Vol. and Tone Controls. Good Quality. Ideal for P.U. ... 2/6
THE "CHALLENGER" PORTABLE—An Amazing A.C./D.C. Portable. 3-Valve Plus Rect. M/L Waves. Fine Power and Quality. No A. or E. needed. ... 2/9
MANY OTHER DESIGNS for Sets and Amplifiers available. Send S.A.E. for latest List and please include stamp with order. Prompt Service. Components supplied.
L. ORMOND SPARKS (P),
 9, Phoebeth Road, Brockley, S.E.4.
 (Nearest Station: Ladywell, S.R.)
 (Phone: Lee Green 0220)

SPECIAL THIS MONTH!—Exhaustive Constructional Manual, enabling even beginners to build a powerful 5-valve all-wave A.C. or A.C./D.C. Superhet of exceptional range, price 3/- (refundable). All parts available, including 23 cabinet cabinets. Full details of this and other bargains, 21d.

VICTORY 4in. 3-valve, plus rec., kit absolutely complete, valves, speaker, super cabinet, full instructions, 1mg and medium waves, A.C. or Universal model, 23 cabinet, p.d. **N.R.S. AUDIO AMPLIFIER** for A.C. 200-250 v., 4 watts undistorted, valves 607, 6V6 and 5Z4, pick-up and tuner inputs (volts available), volume, tone and feedback controls, tested, guaranteed, 45/19/6. Metal Rectifiers, 250 v. 45 m.a., 5/- (4/-); 350 v. m.a., 8/6 (7/6). Heater Transformers, 6.3 v. 1.5 amp., 12/6 (11/-). Universal type tapped at 4 v., 5v. and 6.3 v. 2 amps. each, 10/6. Iron-cored I.F.S., 465 kc/s, standard or midset, best quality, 19/6 pair. G.S.M.O. "Coil pack, L. M. and S., 33/-; Weartite ditto or med. and 2 short, gram position, 42/-; L.T.C. press-button coil pack, 3-wave and gram, 58/3, all with circuit. P.M. Speakers, 12 class, 4" and 5", E.M.M. 5in., 11/6; Plessey, etc., 6in., with trans. 25/6; R. & A., 8in., 21/-, with trans. 27/6; 10in. Goodman's, less trans. 30/-. Wharfedale, Goodman's Axiom, Vitavox and Parkers Hi-Fi models.

GRAMOPHONE EQUIPMENT.—A.C. motors with 9in. turntable, fixed speed, 82/5; ditto Collaro, 12in. table, variable speed, 118/4; Collaro motor/pick-up/auto-stop unit, latest de luxe model, 89, carr. 2/-; **GRAMO-T. VALVES**, guaranteed.—3/5, L63, EBC33, EF50, 5/6 (5/-).

BRAND NEW VALVES, best makes only, guaranteed: EF36, EF39, EL32, ECH35, 15D2, 6X5, 5Z4, 8/- (7/6); 6X8, 6KT, 6T7, 6V6, 6SN7, 6X4, 6X5, 6X6, 6X7, 6X8, 6X9, 6Y6, 6Z6, 6Z7, 6Z8, 6Z9, 6Z10, 6Z11, 6Z12, 6Z13, 6Z14, 6Z15, 6Z16, 6Z17, 6Z18, 6Z19, 6Z20, 6Z21, 6Z22, 6Z23, 6Z24, 6Z25, 6Z26, 6Z27, 6Z28, 6Z29, 6Z30, 6Z31, 6Z32, 6Z33, 6Z34, 6Z35, 6Z36, 6Z37, 6Z38, 6Z39, 6Z40, 6Z41, 6Z42, 6Z43, 6Z44, 6Z45, 6Z46, 6Z47, 6Z48, 6Z49, 6Z50, 6Z51, 6Z52, 6Z53, 6Z54, 6Z55, 6Z56, 6Z57, 6Z58, 6Z59, 6Z60, 6Z61, 6Z62, 6Z63, 6Z64, 6Z65, 6Z66, 6Z67, 6Z68, 6Z69, 6Z70, 6Z71, 6Z72, 6Z73, 6Z74, 6Z75, 6Z76, 6Z77, 6Z78, 6Z79, 6Z80, 6Z81, 6Z82, 6Z83, 6Z84, 6Z85, 6Z86, 6Z87, 6Z88, 6Z89, 6Z90, 6Z91, 6Z92, 6Z93, 6Z94, 6Z95, 6Z96, 6Z97, 6Z98, 6Z99, 6Z100. Matched pairs gladly supplied. We specialise in instruments by mail order. Immediate, safe delivery all AVO and Pullin models. Advice, literature, etc., free. Write to: W. D. D. brackets, lowest prices for lots of 3, postage extra under 45.—N.R.S., 102, Park-hill Road, London, N.W.3. Tele: Gulliver 1453.

EVERYTHING for the wireless constructor. Send stamp for price list.—H. Tabner, 118, Nightingale Road, Hitchin, Herts.

SOUTHERN RADIO'S WIRELESS BARGAINS

Bendix BC-453 Receivers (190-550 kc/s), 6 valves, (3) 12SK7, (1) 12A6, (1) 12K8, (1) 12SR7. 85 kc/s. I.F.s. Ideal for Qser (see Jan. QST), or can be converted to earphone. Brand New in original cartons. 35/- plus 1/6 postage. Bendix BC 454 Receivers (3-6 mers.), six valves, (3) 12SK7GT, (1) VT132, (1) 12SK7GT, (1) 12A6GT, (1) 12 SR7GT, 1.415 kc/s. I.F.s. Easily converted to 3.5 Wave radio. In original cartons. 35/- plus 1/6 postage. Bendix BC 455 Receivers (5-9 mers.), six valves, (3) 12SK7GT, (1) VT132, (1) 12SR7GT, (1) 12A6GT, 2.830 kc/s. I.F.s. 35/- each, post 1/6. New "Delco" hand generators, 6 volt 4 amps., in original cartons, 17/6 post free. Brand New Moving Coil Headsets. With moving coil microphone, aft. lead and plug, 12/6 per set, post free. R.A.F. Bombight Computers. With Sperry Gyro, 324 volt motors. Great for barometric bellows and counters. Ideal for experimenters. 55/- carriage 5/-. R.A.F. Morse keys, 1/6 each, post 4d. "Lufbra" adjustable cutters, for use on wood, metal and plastic, 5/- post 4d. Throat Microphones with lead and plug, 5/- post 6d. Brand new with lead and plug, 5/- post 6d. Permanent Crystal Detector, 2/6 each, post 4d. Double Sided Recording Discs, 5 1/2in., 1/- each, 10/6 per dozen. Westectors, W.X.6 and W.112, 1/- each, 9/- per dozen, post free. Inspection Lamps, with lead and Lucas plug, 3/6. Oscilloscope transformers, 6d. M.C.R. Batteries, 90 volts H.T. and 7 1/2 volts L.T., 6/6 each, post 9d. Moving Coil Motors, 2in. dia., 0.5 ma. or 0.5 amps., 8/- each. "Collaro" Gram. Units, Motor, 3-way pick-up, complete with speed regulator (A.C. Only), 100-250 volts, 50 c.p.s., 9/- carriage paid.

Radio Publications: Send 2d. stamp for full list of our latest publications. Southern Radio & Amp. Ltd., 46, Lisle Street, London, W.C.2. GERARD 6653.

97.6 CHARGING SWITCHBOARDS, 30v, 32v, 50 and 1,250 volts, amps., cut-outs, fuses, resistances, etc. 4 take-off, superb unit, in case; or send £5 carriage paid.

75 - DYNAMOS, 24 volts, 1,000 watts, 9in. by 7in., 4in. spindle, or send 80/- carriage paid.

75 - 230v./150, 1/5 h.p. ELECTRIC MOTORS, incorporating 1,260 cycle converter, or send 80/- carriage paid.

58 - MAINS TRANSFORMER SWITCHBOARDS, 230v., 12v., 5 separate take-offs, complete distribution panel, all switches, fuses, amps, etc., brand new, or send 60/- carriage paid.

55 - ELECTRIC MOTORS, 12v. and 24v., 14 h.p., 4in. by 4in., with 4in. spindle for drive, beautiful job, or send 60/- carriage paid.

45 - DYNAMOTOR UNITS, containing 12v., 24v., 130v., and 300v. D.C. dynamo, or suitable as 6v., 12v., or 24v. motor, approx. 4 h.p., 11in. by 5in. w. spindle to take small grinding, mop, etc. also contain adjustable 24v. cut-out, 12v. automatic voltage control, smoothing condenser, resistances, and many other extremely useful fittings, beautifully made, or send 50/- carriage paid.

38 - RADIO VAVEMETERS, adjustment dial, 350-370 Mc/s., beautiful instrument in case, or send 40/- carriage paid.

Most other valve equipment. Lists free. Best motors, Summerley Street, Earlsfield, S.W.18. WIM. 3833. (100 yds. S. Rly. Electric Line: 10 minutes Waterloo.)

VERSATILE TRANSFORMER. Another Oldchurch Laboratories Special. This is the most universally useful component yet offered to the "Ham." Has four separate windings, impregnated in screened container. Weighs 4 lbs. These are some of its uses: Modulation choke with 3 taps, modulation transformer with ratios of 3, 2, and 1 to 1, driver transformer, audio isolating transformer, mains, 100, 200, 300 and 400 v. step up or down transformer. Carries 30 w. in. in. in. and diagram, with each. You cannot afford to be without one. Brand new ex-Govt. Price 7/6 each. Three for £1 (plus post). E.F.F.50 valves. Emission tested. No cracked bases, £3 per doz. New Arrival, 1.55 Receivers, complete, in excellent condition. Very limited number. Each £9 (plus £1 deposit on case, returnable, plus 15/- carriage).—L.P. Dismore, 52c, Oldchurch Rd., Chingford E.4.

SPECIAL OFFERS. Brand new condition BC221s at £10.19.6. 1/5 h.p. Electric Motors (200-250 A.C.), 69/6. Super quality Phones. Low resistance cut-off pair. High resistance 7/6 per pair. Coil with M.C. Microphone, 10/6. 8 mid. 350 volt electrolytics (tubular), 19/6 per dozen. Hundreds of other bargains.—Lists 2d. stamp to Radio Constructors, 28, Spital Hill, Sheffield.

R.F. UNITS, type 24, 8/6 ea.; 25, 10/6 ea.; 27, 21/- ea.; 6-pin Jones' sockets to fit, 1/- ea. VCR97 C.R. Tubes, new, 55/- ea. Indicator Units with above and 7 valves, £3.10. H.V. Reels, V1111 and V1120, 9/- ea.; £22, 8/- ea. condensers, 02, 8,000 v., 3/6 ea. 1124 Receivers with 6 valves, 19/6, carr. paid. New valves: SP41, SP61, P41, P61, E.F.50, EBC33, EF39, EB34, EA50, 65H7, V761, 5/- ea. Special offer: SP61 and P61 in solid case, tested, £3.10. 8/- ea. 27/6 doz. 524, 6SN7, 6AC7, 6V6, 6A5, VCR, 6/9. 6A5, 6/9. 6A5, 9/001, 12/6 ea.; 955, 956, 10/- ea. Indicator type 62, VCR97 and 21 valves, £45/- ea., plus 10/- carr. Indicator lights, panel type, all bakelite, clear 1/- ea. Bulgin brass rod, 20 in. green, 2/6 ea. Bulgin small rod, 19 ea. Toggles, 1/- ea. Two-way on-off Bulgin 2/6 ea. Neon voltage stabilizers, VR130, Octal, 8/- ea.; 24 v. 60 amp. outlets, 8/6 ea.; 12 v. A.C. D.C. motors, 230 v. A.C. 50 watt transformer to suit, 9/6. Charger Kits, transformer and rectifier to suit, 230 v. A.C. 6 v. 1 amp. 15/-; 12 v. 1 amp. 21/-.

Balanced Armature Piepieces, suit low impedance output as pillow speakers, etc., 2/- ea. Moving-coil Phones, 7/6 pr. with mike, 12/6. Plugs and Jacks, 1/3 pr.: one-hole type 1/9; jack plugs, 9d. ea. Set of 7 V.H.F. coils, dust-tuned with ceramic trimmers attached, 5/- set, 50 assorted resistors, 7/6. 30 assorted 50 condensers, 10/-.

Jones' plugs, most types available, 1/6 ea. Boiling-Less 5-pin plugs and sockets, 2/- pr. Vibrator suppressor unit, 4-pin, U.K., 1/6 ea. Large metal rectifiers, 230 v., 2 amp. H.C. 57C, new, 21/- ea. S.A.E. for Lists.—H. English, The Mattings, Rayleigh Road, Hutton, Brentwood, Essex.

CHASSIS, metal work, panels, all types in 16 g. all, or dural, 1st class work only. Competitive price. Fast delivery. Lists 2d.—Hudson, 3B, Winner St., Paignton, Devon.

SPECIAL OFFER.—Selling below List recent huge purchase all types radio goods. New, branded, No W.D. surplus. Valves, speakers, chassis, everything. Send wants. List 2d.—Hudson, 3B, Winner St., Paignton, Devon.

KIT KITS WIRED.—Apparatus constructed to your design. Any receiver serviced. Send diagram or set for quotation, to F. A. Sharp & Sons, 53, Weedington Road, Kenilsh Town, N.W.5. Phone: GUL 1759.

H.R.O. COILS, H.F., 50/-; L.F., 40/- 18 sets less valves, 8/-, ARP12, AR3, 5/-, Iron core 465 kcs. Trans., 4/- each. Post free.—Fancourt, Kilburn, Derby.

TESTED GOODS.—Metal Rectifiers, 3/6 each, 30/- doz. Nuts, Bolts, etc., 2/- lb. Quality Speakers: New, Rola G12 plus, 40/-; Goodmans 12in., 46/15/-; Goodmans Axion 12, 28/8/-; Rola or Elac, 10in., 30/-; 8in., 23/6. Pifco Radiometers, 0.6v., 0.240v., 0.30 mA. A.C. or D.C. and circuit test, 25/-; Avomitor D.C., 24/4s. Avomitor A.C., £8 10s. Taylor 12A (1,000 ovy), £8 8s. Electrolytics, best makes, 0.01, 8 mf., 4/-; 8-8, 6/6; 16-8, 8/6. Many other lines, all brand new stock of best quality. Send S.A.E. for list, C.W.O. or C.O.D. Only for 12in. speakers, too heavy for C.O.D.). Carriage paid order £1.—Honey and Newey (Radio), Ltd., Dept. P. 211, Queens Road, Smethwick, Staffs.

RECORD PLAYING DESKS fitted with B.S.R. electric gram motor and pickup. A.C. mains, £8 8s., including tax. Below—Quality Speakers: New, Rola G12 plus, £6 10s.; Goodmans 12in., 46/15/-; Goodmans Axion 12, 28/8/-; Rola or Elac, 10in., 30/-; 8in., 23/6. Pifco Radiometers, 0.6v., 0.240v., 0.30 mA. A.C. or D.C. and circuit test, 25/-; Avomitor D.C., 24/4s. Avomitor A.C., £8 10s. Taylor 12A (1,000 ovy), £8 8s. Electrolytics, best makes, 0.01, 8 mf., 4/-; 8-8, 6/6; 16-8, 8/6. Many other lines, all brand new stock of best quality. Send S.A.E. for list, C.W.O. or C.O.D. Only for 12in. speakers, too heavy for C.O.D.). Carriage paid order £1.—Honey and Newey (Radio), Ltd., Dept. P. 211, Queens Road, Smethwick, Staffs.

SEND FOR LIST of ex-Government bargains—Transformers, Condensers, Chokes, Valves, Switches, Power Units, etc. Example: American IFF Receiver, 10 valves, 30/-; Heavy Duty Mains Transformer, 300-0.350 volts at 300 mA., 20/-; 20 volts, 2x 6.3 volts, 2 volt, 42/8/-; Honey Amplifier 15/-; WW Pots, 2/3; Bargain Parcels, 20 useful items, 5/-.—Cross, Skerries, Newton Lane, Grange, West Kirby, Cheshire.

MAINS TRANS., 16/6; Coil Packs, LMS, 455 kcs./15/-; I.F. Trans., 465 kcs., iron cored, 9/-; Solder Tags, Eyelets, etc., 1/- doz.; Ins. Sleeving from 1d. vard. 100 yds.; Ins. in England.—Sunder Electronics, Ltd., 4 Upper Beviden Avenue, Brighton, Tel. 4446.

COPPER WIRES, enamelled, tinned, Litz cotton, silk covered. All gauges. B.A. screws, nuts, washers, soldering tags, eyelets. Ebonite and laminated bakelite panels and tubes. Paxolin coil formers. Tufrol rod, Crystals, permanent detectors, headphones. Latest radio publications: full range available. List S.A.E. Trade supplied.—Post Radio Supplies, 33, Bourne Gardens, London, E.4.

SPECIAL Valves, PEN35C equiv. NEW, only 9/11 each. 5Y3, 5Z4, 6A7, 6A8, 6K7, 6K8, 6J7, 6J8, 6B8, 6G6, 6Q7, 6V6, 6Y6, 6X5, 6F6, 5T4, at 7/6 each, post 9d. Amplifier Chassis in case, 5in. x 3 1/2 in. x 2 1/2 in. with 6V valve, input and output trans., etc. w.c.t. and diagram, 6/6, post 1/3. Rn Unit, 24 and 25, as advertised, w/3 valves, 7/6 each, post 1/3. Featherweight 102in. telescopic aerial folds to 11in. a bargain at only 8/11, post 9d. W. or callers welcome at 36A, Dalston Lane, E.8. Tiny for Radio. Open Saturdays to 7.30 p.m.

FREQUENCY METERS, No. 221, £8 9/6. Frequency Meters No. 906, £2 12/6. Receiver No. 1066, £1 7/6. Signal Generator No. 196, £1 7/6. Radio Compass No. B.C. 433, £3 2/6. Receiver No. 966, £1. Transmuting Tuning Units No. 26B, 2,500 kcs., 5/-.

Radio Usage Control Panels, 80 volt A.C. 7/6. Ferranti Unit Test Set, 100 v. Type 2, £12/6. Indicator Unit Cathode Ray Tube (new), £17/6. Master Contactors (Precision windings clock movement), 12/6. Rectifier, Power Units (new), Type SP104A.P.T.E., £12/6. Cash with order carriage paid.—St. Mark's Garage, St. Mark's Street, Bolton. Phone 2632.

SHOP BY POST.—All our goods are carriage paid to any address in Great Britain. You pay no fancy prices. We are actual buyers direct from the Ministry of Supply. Here are a few examples of the value obtainable to-day—Modulator unit Type 206 contains 5-KT44 output pentodes, 2-U17 rectifiers, 1-MH41 triode, switches, transformers, chokes, resistances, etc., only 59/6. Receiver type R. 3067 contains 10 useful valves, 2-6F50, 2-CU8, 2-DY1 rectifiers, 4-SP61, 12 volt Rotary transformer, and a host of condensers, resistances, etc. The scrap value of this unit is over £10. Our price, 49/6. Ekide 10 volt 5,000 mA. H.T. accumulators, 5/- per unit. Teak case free with each 8 units. 2 volt 20 amp. unspillable accumulators, 10/-.

Complete Aircraft Aerials, Stainless Steel Wire Insulators, etc., 1.11 each. Single Plex in 12yd. coils, 1.3 coil. Twin tough Rubber Covered Cable, 5/- per doz. yds. Coax Cable, 6/- doz. yds., £2 10/0d. coil. Items advertised last month still available except receivers. Send S.A.E. to-day for our latest lists.

WALTONS WIRELESS STORES, 203, Stavely Rd., Wetherhampton, or callers only, 43, Stafford St., Wolverhampton.

ELECTRONIC novachord (similar parts/diagrams) wanted.—Jones, 4, Nugent Terrace, N.W.8.

WANTED, clean copy of "Amateur Wireless" containing description of 150 mile Crystal Set.—Box No. 163.

HEADPHONES M.C. (40 Ohms) and Tannoy power M.C., 7/6 per set. Post paid.—V. C. Terry, J. Peel St., Midstone.

SALE.—Midget Receiver, M.C.R.1, complete, as new, also 6in. 5in. and 3in. Speakers, £12.—Box No. 164.

NATIONAL Radio Service and Television Company, leading Radio and Television repair organisation in the country. All makes receivers, amplifiers, etc. Rewinds to transformers, field coils, armatures, etc. Rewinds fitted to loudspeakers. All types British and American valves stocked. Immediate service, collection, etc. any district.—63, High Street, N.W.8. Primrose 6725.

REWIN SERVICE.—Armatures, Gram. motors, Vacuum Cleaners, Drill and all small motor Transformers — Fields Pick-ups, Speakers—New Cones and Speech Cells. Service, entry and accessories supplied. All fitted—New Vac. Cleaners at £1. All work guaranteed and promptly executed. Special terms to the Trade. Send S.A.E. for Price List and Radio Spares.—A. D. S. Co., 261-3-5, Lichfield Road, Aston, Birmingham 6.

TUITION

THE INSTITUTE of Practical Radio Engineers have available Home Study Courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the tuition suitable coaching matter for I.E.E.E., Service, entry and progress rates, and tuitionary fees at pre-war rates are moderate. The Syllabus of Instructional Text may be obtained, post free, from the Secretary, Fairfield Road, Crouch End, N.8.

AMATEUR Radio Transmitting Licence. A 12 MONTH COURSE of instruction in the theory and practice of Wireless Telegraphy covers all requirements of the syllabus for the examination. Apply British School of Telegraphy, Ltd., 179, Clapham Road, London, S.W.9. (Estd. 1906.)

A.M.I.Mech.E., A.M.I.E.E., City and Guilds, etc., or NO PASS—NO FEE! For terms. Over 95 per cent. successes. For details of Exams and courses in all branches of Engineering, Building, etc., write for 108-page Handbook—FREE: B.I.E.T. (Dept. 242B), 17, Stratford Place, London, W.1.

COMPLETE CORRESPONDENCE COURSE, covering Amateur and C. and G.I. examinations, consisting of 12 lessons. Students trained for Certificates of the City and Guilds of London Institute. Send for particulars.—Ortho-Modern Institute, 72, St. Stephen's House, Westminster, S.W.1.

MERCHANT NAVY.—Here is an opportunity to train yourself as Radio Officer for merchant ships. The big money is open to you, but you must first qualify for P.M.C. Certificate. Established 30 years, we can put you through in the minimum of time. Prospectus from Director, The Wireless School, 21, Manor Gardens, Holloway, London, N.7. Phone ARC 3694.

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint.

F. J. Cannon's A.C. Superhet 4 .. — PW59
F. J. Cannon's Universal 24 Super-
het 4 .. — PW60
"Qualitone" Universal Four .. — PW73

CRYSTAL SETS

Blueprints, 1s. each.
1937 Crystal Receiver .. — PW71
The "Junior" Crystal Set .. — PW94

STRAIGHT SETS. Battery Operated

One-Valve: Blueprints, 2s. each.
All-Wave (Pentode) .. — PW31A
Beginners' One-valver .. — PW85
The "Pyramid" One-valver (HF
Pen) .. — PW93
Two-valve: Blueprints, 2s.
The Signet Two (D & F) .. — PW76
Three-valve: Blueprints, 2s. each.
Self-Start Battery Three (D, 2 LF
(Trans) .. — PW10
Sunomat Three (HF Pen, D, Pen)
Hall-Mark Odette (D, LF, Pen) (RC)
F. J. Cannon's Silver Souvenir (HF
Pen, D (Pen), Pen) (All-Wave
Three) .. — PW49
Capeo Midget Three (D, 2 LF
(Trans) .. — PW51
1936 Sonotone Three-Four (HF
Pen, HF Pen, Westcoater, Pen)
Battery All-Wave Three (D, 2 LF
(RC) .. — PW53
The Monitor (HF Pen, D, Pen) .. — PW55
PW81

The "Colt" All-Wave Three (D,
2 LF (RC & Trans) .. — PW72
The "Rapid" Straight 3 (D,
2 LF (RC & Trans) .. — PW82
F. J. Cannon's Oracle All-Wave
Three (HF, Det, Pen) .. — PW78
1938 "Triband" All-Wave Three
(HF Pen, D, Pen) .. — PW84
F. J. Cannon's "Sprite" Three
(HF, Pen, D, Det) .. — PW87
The "Hurricane" All-Wave Three
(SG, D, Pen, Pen) .. — PW89
F. J. Cannon's "Push-Button"
Three (HF Pen, D (Pen), Det) .. — PW92
Four-valve: Blueprints, 2s. each
Beta Universal Four (SG, D, LF
Cl, D) .. — PW17
Nucleon Class B Four (SG, D
(SG), LF, Cl, B) .. — PW34E
Fury Four Super (SG, SG, D, Pen)
Battery Half-Mark 4 (HF, Pen,
D, Push-Pull) .. — PW46
"Acme" All-Wave 4 (HF Pen, D
(Pen), LF, Cl, B) .. — PW34C
The "Admiral" Four (HF Pen,
HF Pen, D, Pen (RC)) .. — PW47

Mains Operated

Two-valve: Blueprints, 2s. each.
Selectone A.C. Radiogram Two
(D, Pow) .. — PW19
Three-valve: Blueprints, 2s. each.
Double-Diode-Triode Three (HF
Pen, D, D, Pen) .. — PW23
D.C. Ace (SG, D, Pen) .. — PW25
A.C. Three (SG, D, Pen) .. — PW29
A.C. Leader (HF Pen, D, Row) .. — PW36C
D.C. Premier (HF Pen, D, Pen) .. — PW36A
F. J. Cannon's A.C. All-Wave Silver
Souvenir Three (HF Pen, D, Pen)
"All-Wave" A.C. Three (D, 2
LF (RC)) .. — PW50
A.C. 1936 Sonotone (HF Pen, HF
Pen, Westcoater, Pen) .. — PW56
Mains Record, All-Wave 3 (HF
Pen, D, Pen) .. — PW70
Four-valve: Blueprints, 2s. each.
A.C. Fury Four (SG, SG, D, Pen)
A.C. Fury Four Super (SG, SG,
D, Pen) .. — PW34D
A.C. Half-Mark (HF Pen, D,
Push-Pull) .. — PW45
Universal Half-Mark (HF Pen, D,
Push-Pull) .. — PW47

SUPERHETS

Battery Sets: Blueprints, 2s. each.
26 Superhet (Three-valve) .. — PW40
F. J. Cannon's 2-valve Superhet .. — PW52
Mains Sets: Blueprints, 2s. each.
A.C. 25 Superhet (Three-valve) .. — PW43
D.C. 25 Superhet (Three-valve) .. — PW42

SHORT-WAVE SETS. Battery Operated

One-valve: Blueprint, 2s.
Single S.W. One-valver .. — PW86
Two-valve: Blueprints, 2s. each.
Midget Short-wave Two (D, Pen)
The "Fleet" Short-wave Two
(D (HF Pen), Pen) .. — PW91
Three-valve: Blueprints, 2s. each.
Experimenter's Short-wave Three
(SG, D, Pow) .. — PW30A
The Perfect 3 (D, 2 LF (RC and
Trans) .. — PW63
Tri-band "Broad" S.W. Three
(HF Pen, D (Pen), Pen) .. — PW65

PORTABLES

Three-valve: Blueprints, 2s. each.
F. J. Cannon's 2 LF Three-valve
Portable (HF Pen, D, Pen) .. — PW66
Parvo Flyweight Midget Portable
(SG, D, Pen) .. — PW77
Four-valve: Blueprint, 2s.
"Jump" Portable 4 (D, LF, LF,
Pen) .. — PW86

MISCELLANEOUS

Blueprint, 2s.
S.W. Converter-Adapter (1 valve) .. — PW48A

AMATEUR WIRELESS AND WIRELESS MAGAZINE

CRYSTAL SETS

Blueprints, 1s. each.
Four-station Crystal Set .. — AW427
Lucerne Tuning Coil for AW427 1s. .. — AW444
1934 S.W. Set .. — AW450
150-mic Crystal Set .. — AW450

STRAIGHT SETS. Battery Operated.

One-valve: Blueprint, 2s.
B.B.C. Special One-valver .. — AW387
Two-valve: Blueprints, 2s. each.
Full-voltage Two (SG det, Pen) .. — AW392
A.M. Three Two-valver .. — WM406
Three-valve: Blueprints, 2s. each.
E3 3s. S.G. 3 (SG, D, Trans) .. — AW412
Lucerne Rauger (SG, D, Trans) .. — AW423
E9 3s. Three De Luxe Version
(SG, D, Trans) .. — AW435
Transportable Three (SG, D, Pen) .. — WM271
Economy Pentode Three (SG, D,
Pen) .. — WM337
"W.M." 1934 Standard Three
(SG, D, Pen) .. — WM351
E3 3s. Three (SG, D, Trans) .. — WM354
1935 26 6s. Battery Three (SG,
D, Pen) (Pen, D, Pen) .. — WM371
FTF Three (SG, D, Pen) .. — WM389
Certain Three (SG, D, Pen) .. — WM393
All-wave Winning Three (SG, D,
Pen) .. — WM400
Four-valve: Blueprints, 2s. each.
65s. Four (SG, D, RC, Trans) .. — AW370
Self-contained Four (SG, D, LF,
Cl, B) .. — WM330
Lucerne Straight Four (SG, D,
LF, Trans) .. — WM350
E3 3s. Battery Four (HF, D, 2 LF)
The H.K. Four (SG, SG, D, Pen)
The Auto Straight Four (HF Pen,
HF Pen, D, D, Pen) .. — WM404

Five-valve: Blueprints, 2s. each.
Super-quality Five (2 HF, D, LF,
Trans) .. — WM620
Class B Quadradyne (2 SG, D, RC,
Class B) .. — WM344
New Class B Five (2 SG, D, LF,
Class B) .. — WM340

Mains Operated

Two-valve: Blueprints, 2s. each.
Conoco Two (D, Pen), A.C. .. — AW465
Economy A.C. Two (D, Trans), A.C. .. — WM286
Three-valve: Blueprints, 2s. each.
Mantovani A.C. Three (HF, Pen,
D, Pen) .. — WM374
213 13s. 1936 A.C. Radiogram
(HF, D, Pen) .. — WM401
Four-valve: Blueprints, 2s. each
All-Metal Four (2 SG, D, Pen) .. — WM329
Harris Jubilee Radiogram (HF,
Pen, D, LF, P) .. — WM386

SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodicals in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable)) to PRACTICAL WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

SUPERHETS

Battery Sets: Blueprints, 2s. each.
Varsity Four .. — WM395
The Request All-Waver .. — WM407
Mains Sets: Blueprints, 2s. each.
Heptode Super Three A.C. .. — WM353

PORTABLES

Four-valve: Blueprints, 2s. each.
Holiday Portable (SG, D, LF,
Class B) .. — AW393
Easily Portable (HF, D, RC,
Trans) .. — AW447
Tyers Portable (SG, D, 2 Trans) .. — WM397

SHORT-WAVE SETS. Battery Operated
One-valve: Blueprints, 2s. each.
S.W. One-valver for America .. — AW429
Roma Short-waver .. — AW432
Two-valve: Blueprints, 2s. each.
Ultra-short Battery Two (SG, det
Pen) .. — WM402
Home-made Coil Two (D, Pen) .. — AW440

Three-valve: Blueprints, 2s. each.
Experimenter's 3-metre set (D,
Trans, Super-regen) .. — AW435
The Carrier Short-waver (SG,
D, P) .. — WM390
Four-valve: Blueprints, 2s. each.
A.W. Short-wave World-beater
(HF Pen, D, RC, Trans) .. — AW436
Standard Four-valve Short-waver
(SG, D, LF, P) .. — WM383
Superhet: Blueprint, 3s.
Simplified Short-wave Super .. — WM397

Mains Operated

Two-valve: Blueprints, 2s. each.
Two-valve Mains Short-waver (D,
Pen), A.C. .. — AW463
Four-valve: Blueprints, 2s.
Standard Four-valve A.C. Short-
waver (SG, D, RC, Trans) .. — WM391

MISCELLANEOUS


S.W. 1-valve Converter (Price 1s.)
Enthusiast's Power Amplifier (10
Watts) (3/-) .. — WM327
Littner's 5-watt A.C. Amplifier
(8/-) .. — WM392
Radio Unit (2v) for WM392 (2/-)
Harris Electrogram battery am-
plifier (2/-) .. — WM399
De Luxe Concert A.C. Electro-
gram (2/-) .. — WM403
New Style Short-wave Adapter
(2/-) .. — WM388
B.I.D.L.C. Short-wave Converter
(2/-) .. — WM405
Wilson Tone Master (2/-) .. — WM406
The W.M. A.C. Short-wave Con-
verter (2/-) .. — WM408

HINTS COUPON

This coupon is available until Oct. 4th, 1943, and must accompany all Practical Hints.
PRACTICAL WIRELESS, OCT., 1943

Published on the 7th of each month by GEORGE NEWNES, LIMITED, Tower House, Southampton Street, Strand, London, W.C.2, and printed in England by W. SPEIGHT & SON, LTD., 15, Abchurch Lane, London, W.C.2. Sole Agents for Australia and New Zealand: GORDON & GOTCH (A/sia), LTD., South Africa: CENTRAL NEWS AGENCY, LTD. Subscription rates including postage: Inland 10s. 6d. per annum; Abroad 15s. per annum. Registered at the General Post Office for the Canadian Magazine Post. CONDITIONS OF SALE AND SUPPLY: This periodical is sold subject to the following conditions, namely, that it shall not, without the written consent of the publishers first given, be lent, re-sold, hired out or otherwise disposed of in any way of Trade except at the full retail price of 9d.; and that it shall not be lent, re-sold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade; or affixed to or as part of any publication or advertising, literary or pictorial matter, whatsoever.

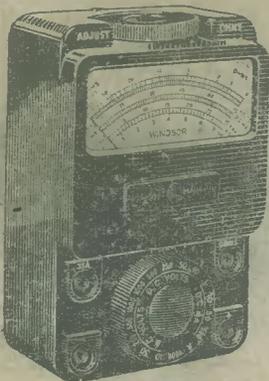The NEW Taylor (Pocket Size) Industrial AC/DC Test Meter



MODEL 125 A

17 ranges specially designed for TELEPHONE AND ELECTRICAL ENGINEER'S Requirements.

Features

- A.C./D.C. VOLTS 0-7.5v. to 0-750v.
- D.C. CURRENT 0-3mA to 0-15A
- RESISTANCE 0.2-100,000 ohms
(with internal battery)
- ROBUST METER Fitted with instantaneous OVERLOAD PROTECTION
- SHOCK-PROOF MOULDED CASE

PRICE £8 - 8 - 0

H.P. TERMS: £0.16.3 deposit and 11 monthly payments of £0.16.1



TAYLOR PRODUCTS INCLUDE - MULTIRANGE A.C. D.C. TEST METERS ● SIGNAL GENERATORS ● VALVE TESTERS ● A.C. BRIDGES ● CIRCUIT ANALYSERS ● CATHODE RAY OSCILLOGRAPHS ● HIGH AND LOW RANGE OHMMETERS ● OUTPUT METERS ● INSULATION TESTERS ● MOVING COIL INSTRUMENTS

TAYLOR ELECTRICAL INSTRUMENTS LTD
419-424 MONTROSE AVENUE, SLOUGH, BUCKS, ENGLAND

Telephone SLOUGH 21381. (4 lines)
Grams & Cables "TAYLINS" SLOUGH

PREMIER RADIO CO.

MORRIS & CO. (RADIO) LTD.

LOUDSPEAKERS BY FAMOUS MAKER

- 5in. P.M. 2-3 ohms 10 11
- 6in. " 2-3 " 16 6
- 8in. " 2-3 " 17 6
- 10in. " 2-3 " 23 6
- 12in. " 15 " 25 -
- 10in. Energised, 2,000 ohm field 25 -

ACCUMULATORS—2v. Bakelite-cased Accumulators by Oldham, Dagenite, Exide, etc. New and unused, unspillable tanks. 7in. x 4in. x 2in. 8/6 each.
BATTERY CHARGER KITS—3v. 1 amp. (tapped at 2v.). 22/6; 12v. 1 amp. 27/6. These incorporate Metal Rectifiers and Transformers. For 200-250v. A.C. mains.

H.T. REFINATOR AND TRICKLE CHARGER KIT—Consists of a complete Kit of Parts to construct an H.T. Eliminator with an output of 120 v. at 20 m.a. and provision for Trickle Charging a 2 v. Accumulator. Two Metal Rectifiers are employed. With Circuit. 35/-

COLLARO ELECTRIC GRAMOPHONE MOTORS with 12in. turntable. A.C. only, 100-250 v., £5 18/4.

COLLARO ELECTRIC UNIT with Magnetic Pick-up and Auto Stop. A.C. only, 100-250 v., £9 13/6.

DITTO UNIT with Crystal Pick-up. A.C. only, 100-250 v. £11 2/2.

COLLARO AUTO CHANGERS with Magnetic Pick-up. A.C. only, 100-250 v., £22 4/4.

CONRAD RIM DRIVEN ELECTRIC GRAMOPHONE MOTORS with 9in. Turntable. Fixed Speed (73 r.p.m.) for 200-250 v. A.C. only, £2 17/6.

C.R. TUBES VCR97. 6in. diameter, green screen, 4 v. 1 a. heater, 2,500 v. max. H.T. Complete with socket, in maker's original cartons, 55/-

MULLARD MW. 1S-2 TELEVISION TUBES, 7in. diameter, 2 v. heater, 5KV max. H.T. Mazda Octal Base, 25 19/6, in maker's cartons.

C.R. TUBES. We have available a large quantity of E.M.I. 41 Cathode Ray Tubes, 3 1/2in. diameter. Green screen. Short persistence. 4 v. 1.3 a. heater, 600 v. H.T. Complete with socket, 17/6 each.

C.R. TUBES V.C.R.138 (equivalent to E.C.R. 35). 3 1/2in. diameter. Green Screen. 4 v. 1 a. heater, 1,200 v. H.T. Complete with socket and Mumetal screen, 49/6 each.

THE FAMOUS R1155 RECEIVER

These are all brand new and unused. Frequency range, 7.5 mc/s —7 kc/s. in 5 wave bands. Complete with ten valves (including magic eye). Completely enclosed in a black cracked metal case. 16in. x 9in. x 9in. Brand New, £12.12 0. Used Models, £3/3 0.

RECTIFIERS—Westinghouse J.50 Rectifiers, 7/6 each.
SPECIAL HEADPHONE OFFER—High-grade Double Headphones, using balanced armature units, D.C. Res. 60 ohms; 3/6 per pair, 5/6 two pairs. Matching transformer if required, 2/6 each.

SPECIAL VALVE OFFER

6F6	—	10 6	VU134 (HVR2)	10/-
6V6	—	8 6	VU39 (R3)	9/-
CV6	—	5/-	VR137 (EC52)	5/-
VR65 (SP41, 6.3 v.)	5/-	5/-	VR138 (EF54)	7/6
VR92 (EA50)	5/-	5/-	VST0 (7475)	10/-
VR56 (EP36)	2 6	6/-	VT60A (807 Ceramic)	10/-
VR78 (DI)	2 6	7/6	—	7/6
VR78 (6K7 met)	10 6	12SH7	—	7/6
VR86 (KT33)	10/-	12SL7	—	10/-
VR503 (EF32)	7 6	12A6	—	7/6
954	—	5/-	VR91 (EF50)	7/6
6B8	—	5/-	RL18	12/6
6E7	—	5/-	6E8	6/6
1S5	—	5/-	—	6/6

MAINS TRANSFORMERS at exceptional prices. All are heavy duty and robust. All 230 v. 50 cycles input.

	Price
3 500-0-500 v. 150 m/a. 4 v. 2 1/2 a., 4 v. 5 a., 4 v. 1 a.	25/-
4 865-0-865 v. 500 m/a. tapped at 690 v. and 760 v. 4 v. 3 a.	21/-
31 40 v. 3 a. and 104 v. 1.5 a. (auto-wound)	21/-
32 700-0-700 v. 150 m/a. and 1,000 v. 30 m/a. 4 v. 1 a., 4 v. 4 a.	40/-
33 38 v. at 2 a. tapped at 35 v., 34 v., 32 v.	15/-
34 1500-0-1500 v. 120 m/a. 4 v. 2 3/4 a., 4 v. 2 3/4 a.	55/-
49 275-0-275 v. 120 m/a. 5 v. 2 a., 6.3 v. 2.5 a., 6.3 v. 3 a. ct.	29/-
42 500-0-500 v. 170 m/a. 4 v. 4 a., 43 v. 20 a.	35/-
46 100 watt auto. 230 v. 150 v. 100 v. 50 v.	25/-
	12/6

OUR 1943 LIST IS AVAILABLE.
All enquiries must be accompanied
by a 2d. stamp.

ALL POST ORDERS TO JUBILEE WORKS 167, LOWER CLAPTON ROAD, LONDON, E.5.
'Phone: Amherst 4723
ALL CALLERS TO 159, FLEET STREET, LONDON, E.C.4. 'Phone: Central 2833.