

RADIO...ELECTRONICS...INSTRUMENTS...AUDIO...

# practical WIRELESS


55p

Australia \$1.15  
New Zealand \$1.25  
Malaysia \$3.50

SEPT 1980
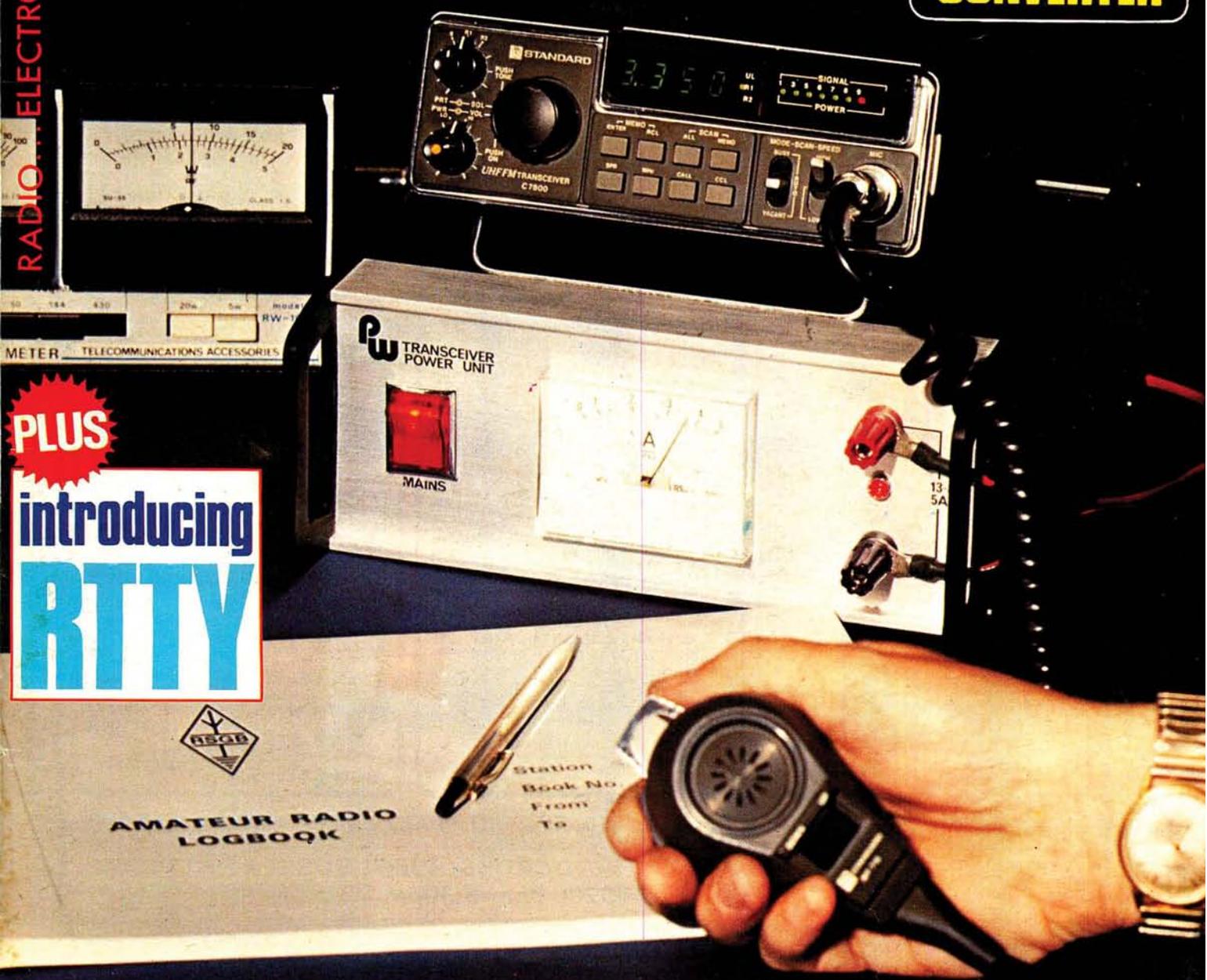
## the **Pw** TRANSCEIVER POWER UNIT

also:  
**Beginners'  
2 METRE  
CONVERTER**



**PLUS**  
introducing  
**RTTY**

  
AMATEUR RADIO  
LOGBOOK

# Bredhurst electronics

HIGH ST., HANDCROSS, W. SUSSEX O444 400786

## "THE" 2M HANDHELD TR 2400

**£210** inc VAT  
& Carriage



INCLUDES NICADS, CHARGER  
AND HELICAL AERIAL


### TR 2400 features:

- Large L.C.D. frequency readout. Readable in direct sun-light. Shows receive and transmit frequencies.
- 10 memories with battery back-up.
- Automatic memory scan for "busy" or "open" channels.
- Mode switch for simplex repeater offset. Full reverse repeater on momentary switch.
- Up/down manual scan in single or fast continuous 5kHz steps.
- Two lock switches to prevent accidental frequency change and accidental transmission.
- More than 1.5W output.

### PRODUCT NEWS
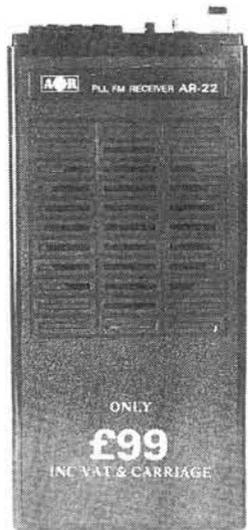
## The world's first FULLY SYNTHESIZED COMPACT VHF FM MONITOR RECEIVER

- FULL BAND COVERAGE, 141.000-149.995MHz
- DIRECT FREQUENCY READING IN 5KHz STEPS BY DIGITAL THUMBWHEEL AND SLIDE SWITCH
- AUTOMATIC ELECTRONIC RF TUNING SYSTEM FOR WIDE BAND COVERAGE
- COMPACT AND LIGHT WEIGHT
- RUGGED, RELIABLE DOUBLE SIDED GLASS-EPOXY PRINTED CIRCUIT BOARD
- HIGH PERFORMANCE MINI RUBBER FLEXIBLE ANTENNA
- INCLUDES NICADS AND CHARGER



ONLY

**£99**

INC VAT & CARRIAGE

### TRANSCEIVERS

<b>H.F.</b>		
TRIO TS120V		£347.00
DENTRON HF200A + PSU		£347.00
TRIO TS120S		£432.00
TRIO TS20SE		£437.00
YAESU FT707		£523.00
YAESU FT101Z		£574.00
YAESU FT101ZD		£661.00
TRIO TS180S (with DFC)		£679.00
YAESU FT107M		£859.00
<b>2.M. MOBILES</b>		
FDK Multi 700EX		£199.00
FDK FM2025		£250.00
STANDARD C8800		£250.00
ICOM IC255E		£255.00
TRIO TR7800		£265.00
<b>HANDHELDS</b>		
FDK PALM II		£99.00
YAESU FT202R		£119.00
FDK PALMSIZER		£149.00
ICOM IC2E		£159.00
FDK PALM IV		£159.00
AOR AR240A		£165.00
TRIO TR2300		£166.00
YAESU ET207R		£199.00
TRIO TR2400		£210.00
<b>2.M. MULTIMODES</b>		
FDK MULTI 750E		£299.00
ICOM IC260E		£339.00
TRIO TR9000		£345.00
ICOM IC251E		£479.00

### RECEIVERS

<b>H.F.</b>		
LOWE SRX30		£178.00
YAESU FRG7		£199.00
TRIO R1000		£298.00
YAESU FRG7000		£359.00
<b>2.M. F.M.</b>		
SEARCH 9		£45.00
A.O.R. AR22		£99.00
FDK TM56B		£105.00
BEARCAT 220FB		£258.00
<b>MARINE V.H.F.</b>		
SEARCH 9		£45.00
S.R.11 (+ scan)		£69.00
TM56B		£115.00
BEARCAT 220FB		£258.00
<b>AIRBAND</b>		
WALTHAM W144		£29.95
R517		£49.95
API2		£120.00
BEARCAT 220FB		£258.00

### SAFETY

#### KEEP BOTH HANDS ON THE WHEEL USING THE LATEST IN MOBILE MICROPHONES

These consist of a high quality condenser microphone used in conjunction with an F.E.T. preamplifier with approx. 12dB gain. Fix the boom microphone to a convenient point such as the sun visor. Position the amplifier and TX/RX switch on the gear lever. Connect the mic plug and power lead and its ready for use.

MM2025 £20.95 inc. VAT (carriage 50p)  
MEX55 £27.50 inc. VAT (carriage 50p)

### ACCESSORIES

(Carriage 75p)

<b>MICROPHONES</b>		
300 HAND		£6.75
SHURE 201 HAND		£14.50
YAESU YD148 DESK		£22.95
SHURE 444 HAND		£32.75
<b>WORLD CLOCKS</b>		
QTR24		£18.40
QTR24D		£24.50
<b>SWR METERS</b>		
SWR25		£13.00
SW110		£35.00
CN620		£52.81
<b>CO-AX SWITCHES</b>		
2 Way TOGGLE		£6.50
2 Way ROCKER		£9.80
5 Way ROTARY		£10.20
<b>A.T.V.'s</b>		
KX2 FOR LISTENERS		£29.95
TRIO AT120		£55.20
TRIO AT200		£82.80
<b>ROTATORS</b>		
TR1 (TV + FM)		£31.00
STOLLE 2050 (Light VHF)		£42.50
AR30 (Light VHF)		£47.15
9502 COLOROTOR (Med VHF)		£51.00
AR40 (Med VHF)		£59.00
KR400 (Med VHF)		£105.00
CD44 (Med H.F.)		£109.00
HAM IV (Large H.F.)		£166.75

TRY OUR

**MAIL ORDER  
SERVICE**

VISIT OUR

**RETAIL PREMISES**  
MON-SAT 9-5.30

INSTANT H.P. - ACCESS - BARCLAYCARD - PART EXCHANGE

MID SUSSEX HOUSE · HIGH ST. · HANDCROSS · WEST SUSSEX RH17 6BW

MAIL ORDER

TEL: 0444 400786 9am-5.30pm

RETAIL CALLERS

TO ORDER ANY OF THE ABOVE ITEMS SIMPLY WRITE, ENCLOSING A CHEQUE OR PHONE YOUR CREDIT CARD NUMBER

# practical WIRELESS

SEPTEMBER 1980  
VOLUME 56  
NUMBER 8  
ISSUE 882

BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR

Published by IPC Magazines Ltd., Westover House, West Quay Rd., POOLE, Dorset BH15 1JG

## QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, *Practical Wireless*, at the above address, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components are usually available from advertisers. A source will be suggested for difficult items.

## SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £11.80 per annum, from "Practical Wireless" Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

## BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 85p each, including post and packing to addresses at home and overseas.

Binders are available (Price £4.30 to UK addresses and overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

All prices include VAT where appropriate. Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

## COPYRIGHT

© IPC Magazines Limited 1980. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden.

All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## NEWS & VIEWS

- 19 **Leader:** Making Haste Slowly
- 20 **News . . . News . . . News . . .**
- 37 **Radio Special Product Report**  
Sugiyama F850 h.f./v.h.f. transceiver
- 62 **Air Test**  
*Datong* Up-converter and Trio TR-2400 2m hand-held transceiver
- 69 **Editorial Announcements**
- 70 **Production Lines** . . . . . Alan Martin  
Information on the latest products
- 49 **Kindly Note**  
Dual Trace Unit, Feb and March 1980

## FOR OUR CONSTRUCTORS

- 22 **PW "Tamar"—2** . . . . . R. S. Hewes  
Continuing the circuit description
- 32 **Linear Frequency Meter** . . . . . J. P. Macauley  
A useful instrument for the bench
- 44 **Transceiver Power Unit** . . . . . R. A. Ganderton  
Stabilised and protected for home use
- 55 **Beginners 2m Converter** . . . . . R. A. Penfold  
Listen to the 2m band on your s.w. receiver
- 64 **PW "Nimbus"—6** . . . . . M. Tooley & D. Whitfield  
Toneburst and Repeater Timer Module

## GENERAL INTEREST

- 28 **Audio Power Amplifiers—1** . . . . . M. J. Darby  
The how and why of amplifier design
- 40 **IC of the Month** . . . . . J. B. Dance  
The  $\mu$ A 78S40 switching regulator
- 50 **Introducing RTTY—1** . . . . . Jeff Maynard  
The history of this fascinating branch of communications
- 72 **On the Air**  
Amateur Bands . . . . . Eric Dowdeswell  
Medium Wave DX . . . . . Charles Molloy  
Short Wave Broadcasts . . . . . Charles Molloy  
VHF Bands . . . . . Ron Ham  
VHF Personality—George Grzebieniak . . . . . Ron Ham

Our October issue will be published about 5 September  
(for details see page 43)

# Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

## Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio, Engineering and Servicing
- Electrical Engineering, Installations and Contracting

## Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" &	Heating	Storekeeping
"A" levels	Industrial	Work Study
Accountancy	Management	
Air	Mechanical	
Conditioning		
Building		

**POST OR PHONE TODAY FOR FREE BOOKLET.**

## ICS To: International Correspondence Schools

SINCE 1890  
Dept. Y276 Intertext House, London  
SW8 4UJ or telephone 622 9911

Subject of Interest .....

Name .....

Address .....

Telephone Number .....

**MANOLITH**  
QUALITY REEL TO REEL & CASSETTE TAPE HEADS + MECHANISMS

**YOUR EXTRA HEAD!**



A NEW TAPE HEAD COULD TRANSFORM THE QUALITY OF YOUR TAPE RECORDER

MEET OUR NEW C42RPS18. THE HIGH PERFORMANCE STEREO HEAD WITH SEPARATE RECORD & PLAYBACK CHANNELS FOR IMPROVED DYNAMIC RANGE & RECORD MONITORING.

## POPULAR UNIVERSAL CASSETTE TAPE HEADS

B12-01 Mono Playback.....	£1.89	C42RPH04 Stereo GLASS FERRITE R/P.....	£11.60
B12-02 Mono Record/Playback.....	£4.02	C42RPS18 Stereo TWIN GAP R+P.....	£25.21
B24-01 Stereo Playback.....	£3.30	E12-09 Mono/stereo erase.....	£ 1.85
B24-02 Stereo Record/Plbk.....	£6.66	B22-02 Twin 1/2 track R/P.....	£ 5.97
B24-07 Stereo R/P, (Dolby Stm).....	£7.87	C44RPH03 Quad 1/2 track R/P.....	£13.17
C42RPH20 Stereo SENDUST R/P.....	£9.28	C44RP2ES01 Quad 1/2 track combined R/P + Erase.....	£26.45
C42RPE01 Stereo combined R/P + Erase.....	£10.93	C22ES02 Twin half track erase.....	£ 4.72

SEND FOR OUR TAPE HEAD CATALOGUE 50p

**MANOLITH**

THE MONOLITH ELECTRONICS CO. LTD.  
5/7 CHURCH ST. CREWKERNE, SOMERSET, ENGLAND (0460) 74321

PLEASE ENCLOSE 30p P&P WITH ORDER

ALL PRICES INCLUDE VAT

# FUEL ECONOMY in kit form



FUELSTRETCHER, the leading UK in-car petrol computer, now available in kit form to save £££££'s from start to finish.

You have a choice from two kits:

FSX20 gives accurate instantaneous digital mpg readings to obtain maximum fuel economy. Standard features include choice of two update frequencies, automatic clear down under idling and owner calibration facility.

FSX10 gives a digital gallons used reading to allow determination of total fuel and average mpg.

Kits are complete with all necessary components and comprehensive instructions. All components guaranteed for 12 months, full technical back-up services available.

ENVIROSYSTEMS LTD., Dept. PW  
Hampsfell Road, Grange-over-Sands, Cumbria, LA11 6BE.  
Tel: 044 84 4233/4

Name .....

Address .....

Phone your order with Access or Barclaycard

	inc. VAT & p&p.	Qty Rqd.	I enclose cheque/
FSX20	£47.50		POs for £ .....
* PI option	£65.90		Cheque No. ....
FSX10	£34.80		* Petrol Injection

Unique in concept - the home computer that grows as you do!

# New! - The Acorn Atom



**£120** An outstanding personal computer kit plus VAT and p&p.

Also available ready-built **£150** plus VAT and p&p


The ATOM - a definitive personal computer. Simple-to-build, simple-to-operate. But a really powerful full-facility computer. And designed on an expandable basis. You can buy a superb expanded package now - tailored to your needs. Or, you can buy just the standard Atom kit, and, as you grow in confidence and knowledge, add more chips. No need to replace your equipment. No need to worry that your investment will be overtaken by new technology. As you need more power, more facilities, you can add them!

\*The picture shown demonstrates mixed graphics and characters in three shades of grey provided by the Standard Atom.

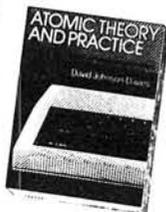**The standard ATOM kit includes:**

- Full sized QWERTY keyboard ● Rugged polystyrene case
- Fibreglass PCB ● 2K RAM ● 8K ROM ● 23 integrated circuits
- Full assembly instructions including tests for fault-finding. (Once built, connect it to any domestic TV and power source)
- Power requirement: 8V at 800 M A. ATOM power unit available.

See coupon. PLUS FREE MANUAL written in two sections - teach yourself BASIC and machine code for those with no knowledge of computers, and a reference section giving a complete description of the ATOM's facilities. All sections are fully illustrated with example programs.



**The ATOM concept**

Adding chips into sockets on the PCB allows you to progress in affordable steps to large-scale expansion. You can see from the specifications that the RAM can be increased to 12K allowing high resolution (256 x 192) graphics. Two further ROM chips, e.g. maths functions, can be added directly to the board giving a 16K capacity. In addition to 5 I/O lines partly used by the cassette interface, an optional VIA device can provide varied I/O and timer functions and via a buffer device allow direct printer drive. An optional module provides red, green and blue signals for colour. An in-board connector strip takes the ATOM communications loop interface. Any number of ATOMS may be linked to each other - or to a master system with mass storage/

hard copy facility. Interface with other ACORN cards is simplicity itself. Any one ACORN card may be fitted internally. So you can see there are a vast number of modular options and additions available, expanding with your ability and your budget.

**The ATOM hardware includes:**

- Memory from 2K to 12K RAM on board (up to 35K in case)
- 8K to 16K ROM (two 4K additions) ● 6502 processor ● Video Display allows high resolution (256 x 192) graphics and red, green and blue output ● Cassette Interface - CUTS 300 baud
- Loudspeaker allows tone generation of any frequency
- Channel 36 UHF Modulator Output ● Bus output includes internal connections for Acorn Eurocard.

**The ATOM software includes:**

- 32-bit arithmetic (±2,000,000,000) ● High speed execution
- 43 standard/extended BASIC commands ● Variable length strings (up to 256 characters) ● String manipulation functions
- 27 32-bit integer variables ● 27 additional arrays ● random number function ● PUT and GET byte ● WAIT command for timing ● DO-UNTIL construction ● Logical operators (AND, OR, EX-OR) ● LINK to machine-code routines ● PLOT DRAW and MOVE.



4a Market Hill, CAMBRIDGE CB2 3NJ

Your ACORN ATOM may qualify as a business expense. To order complete the coupon below and post to Acorn Computer for delivery within 28 days. Return as received within 14 days for full money refund if not completely satisfied. **All components are guaranteed with full service/repair facility available.**

Please send me the following items:			TOTALS
Quantity	Item	Item price inc. VAT+p&p	
	ATOM KIT 8K + 2K (MIN)	@ £140.00	
	ATOM ASS 8K + 2K (MIN)	@ £174.50	
	ATOM KIT 12 + 12K (MAX)	@ £255.00	
	ATOM ASS 12 + 12K (MAX)	@ £289.50	
	1K RAM SETS	@ £11.22	
	4K FLOATING POINT ROM	@ £23.30	
	PRINTER DRIVE 6522 VIA	@ £10.35	
	Buffer (LS 244)	@ £3.17	
	MAINS POWER SUPPLY (1.5 amps)	@ £10.20	
		TOTAL	

To: Acorn Computer Ltd., 4a Market Hill, CAMBRIDGE CB2 3NJ  
 I enclose cheque/postal order for £  
 Please debit my Access/Barclaycard No.  
 Signature  
 Name (Please print)  
 Address  
 Telephone No.  
 Registered No: 1403810. VAT No: 215 400 220 PW/9/80



### SUPERSOUND 13 HI-FI MONO AMPLIFIER



A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high  $\times$  6" wide  $\times$  7 1/2" deep. AC 200 250V. PRICE £18-40, P. & P. £1-60.

### HARVERSON MODEL P.A. TWO ZERO



An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp.). Input 1, 15mV into 47k. Input 2, 15mV into 47k (suitable for use with mic. or guitar etc.). Input 3, 200mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 30 watts music power. Very attractively finished purple built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240 volts. Size approx. 12 1/2" wide  $\times$  5 1/2" high  $\times$  7 1/2" deep. Special price £29-00 + £3-00 carriage and packing.

### "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2"  $\times$  14 1/2"  $\times$  1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £8-80 each + p. & p. (one £1-20, two £1-50).


STEREO MAGNETIC PRE-AMP. Sens. 3mV in for 100mV out. 15 to 35V neg. earth. Equ.  $\pm$  1dB from 20Hz to 20KHz. Input impedance 47K. Size 1 1/2"  $\times$  2 1/2"  $\times$  1 1/2" H. £3-20 + 22p P. & P.

### MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200 240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w  $\times$  4" h  $\times$  9 1/2" d approx. LIMITED NUMBER ONLY at £29-00 + £2-00 P. & P.

### 10/14 WATT HI-FI AMPLIFIER KIT

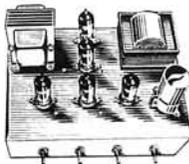

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 50p + SAE (Free with parts). All parts sold separately. ONLY £18-40, P. & P. £2-00. Also available ready built and tested £22-50, P. & P. £2-00.

### STEREO DECODER MK.II

SIZE 1 1/2"  $\times$  2 5/16"  $\times$  1 1/2" ready built. Pre-aligned and tested for 10-16V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions supplied £7-00 plus 25p P. & P. Stereo beacon light if required 40c extra.

Mullard LP1159 RF IF module 470KHz £2-50 + P. & P. 40p. Full specifications and connection details supplied. Pyc VHF FM Tuner Head covering 88-108MHz 10-7 MHz I.F. output. 7.8V  $\pm$  earth. Supplied pre-aligned, with full circuit diagram with precision geared F.M. gang and 323PF + 323PF A.M. Tuning gang only £3-40 + P. & P. 60p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £2-30 yd. length. P. & P. 70p per yd. (min. 1 yd). S.A.E. for samples.

### HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response:  $\pm$  3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M  $\Omega$ ; Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to  $\pm$  16dB. Negative feedback 18dB over main amp. Power requirements 35V. at 1-0 amp.

Overall Size 12" w.  $\times$  8" d.  $\times$  2 1/2" h. Fully detailed 8 page construction manual and parts list free with kit or send 50p plus large S.A.E.

AMPLIFIER KIT £14-95 P. & P. £1-20 (Magnetic input components 33p extra)

POWER PACK KIT £6-20 P. & P. £1-50  
CABINET £6-20 P. & P. £1-50

SPECIAL OFFER—only £25-80 if all 3 items ordered at one time plus £2-80 P. & P.  
Full after sales service

Also avail. ready built and tested £32-20, P. & P. £2-80.

### HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec. play socket are mounted on the printed circuit panel, size approx. 9 1/2"  $\times$  2 1/2"  $\times$  1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only £10-40 plus 90p P. & P. Mains transformer with an output of 17V a/c at 500mA can be supplied at £2-15 + 70p P. & P. if required. Full connection details supplied.


All prices and specifications correct at time of press and subject to alteration without notice.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

**HARVERSON SURPLUS CO. LTD.** (Dept. P.W.) 170 MERTON HIGH ST., LONDON, S.W.19. Tel.: 01-540 3985  
A few minutes from South Wimbledon Tube Station. Open 9.30-5.30 Mon. to Fri. 9.30-5 Sat. Closed Wed.
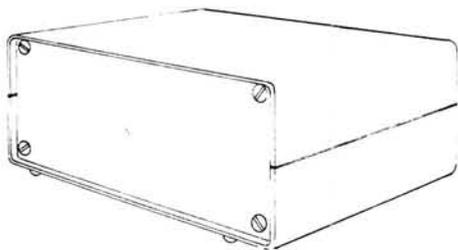
## TORNEL

Manufacturers of  
EZEAC. INSTRUMENT CASES



COMPONENT ACCESSABILITY  
IS THE KEY  
ACRYLIC PAINTED STEEL CASE  
CLEAR ANODISED ALUMINIUM  
PANELS

Please write for further details

TORNEL ENGINEERING CO. PARK HILLS  
COMBE MARTIN N. DEVON 0271 88 3308

## SUMMERTIME SPECIAL OFFERS

**FREE** DIGITAL WATCH **FREE**  
WORTH AROUND £12

On request with your order when you make any purchase from this section. Offer closes 30th September, 1980.

Watch is a current model from world famous manufacturer with a comprehensive display of hours, minutes, seconds, day and date.

**Watches:**  
95QS-42B 1/100 second chronograph, 12 or 24 hour, dual time £17.95  
56QS-38B 1/10 sec chrono. countdown. Digital/analogue. Chrome £24.95  
C-80 Calculator, dual time (24 hour), 1/100 sec chrono. Resin £24.95

**Calculators:**  
PW-81 Clock, alarm £14.95. MQ-6 Micro card, clock £19.95. AQ-1500 Clock, stopwatch £14.95. With alarm, stopwatch, calendar: AQ-2200 £19.95. MQ-12 £19.95. Musical alarms, stopwatch, calendar: ML-71 £22.95. ML-81 £22.95.

Ultra slim scientific: FX-3200 43 scientific functions £21.95  
OFFER SUBJECT TO AVAILABILITY.

**FREE** on request with your order when you make any purchase from this section before 30th September, 1980.

GENTS DIGITAL WATCH WORTH AROUND £17  
or LADIES DIGITAL WATCH WORTH AROUND £15  
or CALCULATOR/CLOCK WORTH AROUND £17

**Watches:**  
56QS-50B 1/10 sec chrono. countdown. Digital/analogue. S/S £34.95  
79QS-39B Alarm chronograph, universal calendar. Chrome. £29.95  
79CS-51B Alarm chronograph, universal calendar. S/S £39.95  
59CS-33B Dress watch with alarm. £44.95  
Scientific calculator, stopwatch, timers. FX-8000 £31.95

OFFER SUBJECT TO AVAILABILITY

PRICE includes VAT, P&P. Send your cheque, postal orders or phone your ACCESS or BARCLAYCARD number to:

**TEMPUS**

Tempus (Dept. PW)  
FREEPOST, 164-167 East Road  
Cambridge CB1 1BR. Tel. 0223 312866



# TUNE IN!

## Build the World Famous CHROMA-CHIME



Give your friends a warm welcome

This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

**ONLY £11.95**  
+ 75p p&p  
UK ONLY

\* Save pounds on normal retail price by building yourself.

## TMS 1000N



-MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed.

This unique chip can be used not only for electronic door chimes but for other projects requiring musical output:

- Car Horns
- Musical Boxes
- Amusement Machines
- Alarms
- Public Address etc

**£4.95** inc. p & p

Free applications manual and data supplied with device! (Or 30p separately)

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-21 DAYS FOR DELIVERY CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

Please send me: PW.9.80.

TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I enclose cheque/PO value £ \_\_\_\_\_


or debit my ACCESS/BARCLAYCARD account no. \_\_\_\_\_

Signature \_\_\_\_\_

# CHROMATRONICS

# ELECTROVALUE

## COMPONENTS THAT COUNT

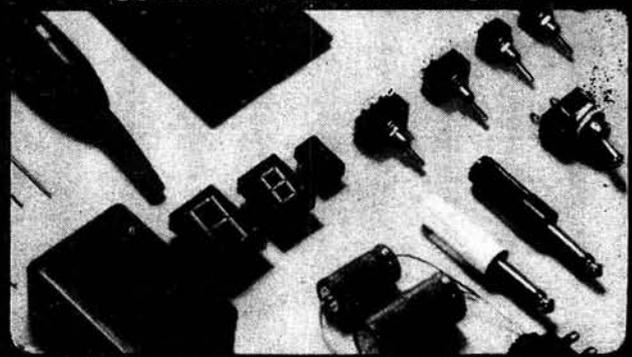

<b>SIEMENS</b> SEMI CONDUCTOR CAPACITORS FERRITES	<b>NASCOM</b> MICRO COMPUTERS AND ANCILLARIES	<b>VERO</b> BOARDS CASES & KITS
<b>ISKRA</b> RESISTORS	<b>RADIOHM</b> POTENTIOMETERS  OPTO-ELECTRONICS	<b>BREADBOARDS</b>  <b>SOLDER TOOLS</b>
		<b>SWITCHES</b> <b>CATALOGUE 10</b>

GOOD DISCOUNTS AND FREE POSTAGE ON U.K. ORDERS OVER £5.75  
COMPUTER-CONTROLLED SERVICE AIDS PROMPT DELIVERY  
128-PAGE CATALOGUE FREE FOR THE ASKING

**ELECTROVALUE LTD., 28 (PW8), St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London 87) STD 0784. Telex 264475.**

**NORTHERN BRANCH (Personal Shoppers Only): 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.**


VALVES		P0500/510		UAF42 1.20		5B/255M		6F12 1.50	
A1085 1.40	ECH42 1.20	EY81 0.65	PFL200 1.10	JBF80 0.70	11.50	6F14 1.15			
A2293 8.80	ECH81 0.70	EY88/87 0.60	2.80	JBF89 0.70	5B/258M	6F15 1.30			
A2900 9.20	ECH84 0.80	EY88 0.65	2.80	JBL1 1.25	8.80	6F17 1.15			
AR8 0.75	ECL80 0.70	EZ80 0.70	PL36 1.25	JBL21 1.75	5R4G1 1.30	6F23 0.75			
ARP3 0.70	ECL82 0.75	EZ81 0.70	PL81 0.85	UCC84 0.85	5U4G 0.75	6F24 1.75			
ATP4 0.60	ECL83 1.40	GY501 1.30	PL82 0.70	UCC85 0.70	5V4G 0.75	6F33 10.50			
B12H 3.90	ECL85 0.90	GZ32 1.05	PL83 0.60	UCF80 1.30	5Y3GT 0.80	6G8A 0.90			
CY31 1.40	ECL86 0.90	GZ33 4.20	PL84 0.95	UCH81 0.75	5Z3 1.50	6GH8A 0.90			
DAF96 0.70	EF37A 1.50	GZ34 2.30	PL504 1.45	UCB2 0.95	5Z4G 0.75	6H6 1.50			
DET22 21.95	EF39 1.25	GZ37 3.90	PL508 1.95	UF41 1.25	6Z30L2 0.90	6J4WA 2.00			
OF96 0.70	EF40 1.25	KT66 6.30	PL509 2.90	UF80 0.95	6Z4G 0.75	6J5 2.30			
OK96 1.20	EF41 1.30	KT88 8.95	PL519 3.20	UF85 0.95	6Z4GT 1.05	6J4 1.25			
DH76 0.75	EF80 0.65	13.90*	PL802 3.20	UL84 1.50	6AC7 1.15	6J5GT 0.90			
DL92 0.60	EF83 1.75	MH4 2.50	PY33 0.70	UL84 0.95	6AG5 0.60	6J6 0.65			
DY802 0.65	EF85 0.60	ML6 2.50	PY80 0.70	UM80 0.90	6AH5 1.15	6J6W 0.90			
E551 14.20	EF91 1.50	N78 9.90	0.80	UM84 0.70	6AK5 0.85	6J7 1.20			
EB8CC 1.60	EF92 2.90	DA2 0.70	0.65	UY82 0.70	6AL5 0.60	6K7 0.80			
EB8CCD1	EF95 0.65	0B2 0.80	0.80	UY85 0.85	6ALS5 0.85	6K7G 0.50			
3.10	EF95 0.65	PABC80 0.60	0.85	VR105/30	6AM5 4.20	6K8G 0.65			
E92CC 1.20	EF183 0.80	PC85 0.75	0.85	1.25	6AM6 1.50	6L8M 2.80			
E180CC 2.80	EF184 0.80	PC86 0.95	0.85	VR150/30	6AN8A 2.50	6L8G 2.50			
E180F 6.30	EF804 4.95	PC88 0.95	0.80	X66 0.95	6AD4 2.85	6L8GT 2.10			
E182CC 4.95	EF812 0.75	PC88 0.95	0.80	X61M 1.70	6A05 1.00	6L8 1.25			
EAT6 2.25	EF1200 1.85			XRI-6400A	6A05W 1.80	6L7G 0.65			
EABC80 0.60	EH90 0.85			82.90	6AS6 1.15	6L18 0.70			
EB91 0.60	EL32 1.10			2759 9.00	6AT6 0.90	6L8G 2.95			
ECB33 1.15	EL34 1.80			2749 0.75	6AU6 0.60	6LD20 0.70			
ECB90 0.90	2.90			2800U 3.45	6AV6 0.85	607G 1.30			
EBF80 0.60	EL37 4.40			2801U 3.75	6AX4GT 1.30	6SA7 1.00			
EBF83 0.60	EL38 4.60			2803U 3.95	6AX5GT 1.30	6SG7 1.15			
EBF89 0.80	EL41 1.40			2900T 2.45	6BBG 0.40	6SK7 1.05			
EC52 0.65	EL81 0.95			1A3 0.85	6BA6 0.55	6K7 0.95			
EC91 3.40	EL82 0.70			114 0.50	6BE6 0.60	6SL7GT 0.85			
EC92 0.85	EL84 0.80			1R5 0.60	6BE6G 1.60	6SN7GT 0.80			
ECC81 0.65	EL86 0.95			154 0.45	6B6 1.30	6SR7 1.10			
ECC82 0.60	EL90 1.00			155 0.45	6BD4 2.85	6S07 0.95			
ECC83 0.65	EL91 4.20			174 0.45	6BR7 4.40	6V6G 1.50			
ECC84 0.60	EL95 0.80			1U4 0.80	6BW6 5.20	6V6GT 0.95			
ECC85 0.60	EL504 1.70			1X2B 1.40	6BW7 0.90	6X4 0.75			
ECC86 1.40	EL509 2.70			2021 1.90	6C4 0.50	6X4WA 2.10			
ECC88 0.80	EL802 1.70			2K25 11.90	6C6 0.55	6X5GT 0.65			
ECC189 0.95	EL821 8.20			3A4 0.70	6CH6 8.20	6V6G 0.90			
ECC804 0.90	EL822 9.90			306 0.50	6CL6 1.70	6Z4 0.70			
ECF80 0.85	EM31 1.60			3022 23.00	6CY5 1.15	7B7 1.15			
ECF82 0.65	EM80 0.85			3E29 10.00	6D6 0.70	7Y4 1.00			
ECF801 1.05	EM81 0.85			354 0.60	6E8 1.60	902 0.70			
ECH34 2.25	EM84 0.85			5B/254M	6F6 1.10	10C2 0.85			
ECH35 1.70	EM87 1.15			14.00	6F5G 1.10	10F18 0.70			
					6F7 2.80	10P13 1.20			
					6F8G 0.85	10P13 1.20			

POSTAGE: £1-£3 30p. £3-£5 40p. £5-£10 45p. £10-£15 50p. Over £15 free. minimum order £1.  
A lot of these valves are imported and prices vary for each delivery, so we reserve the right to change prices for new stock when unavoidable.

**VALVES AND TRANSISTORS**  
Telephone enquiries for valves, transistors, etc.: retail 749 3934, trade and export 743 0899.

**COLOMOR** 907353/ London  
(ELECTRONICS) LTD.  
170 Goldhawk Rd., London W.12  
Tel. 01-743 0899  
Open Monday to Friday 9-12.30,  
1.30-5.30 p.m. Saturdays 9-12.45.
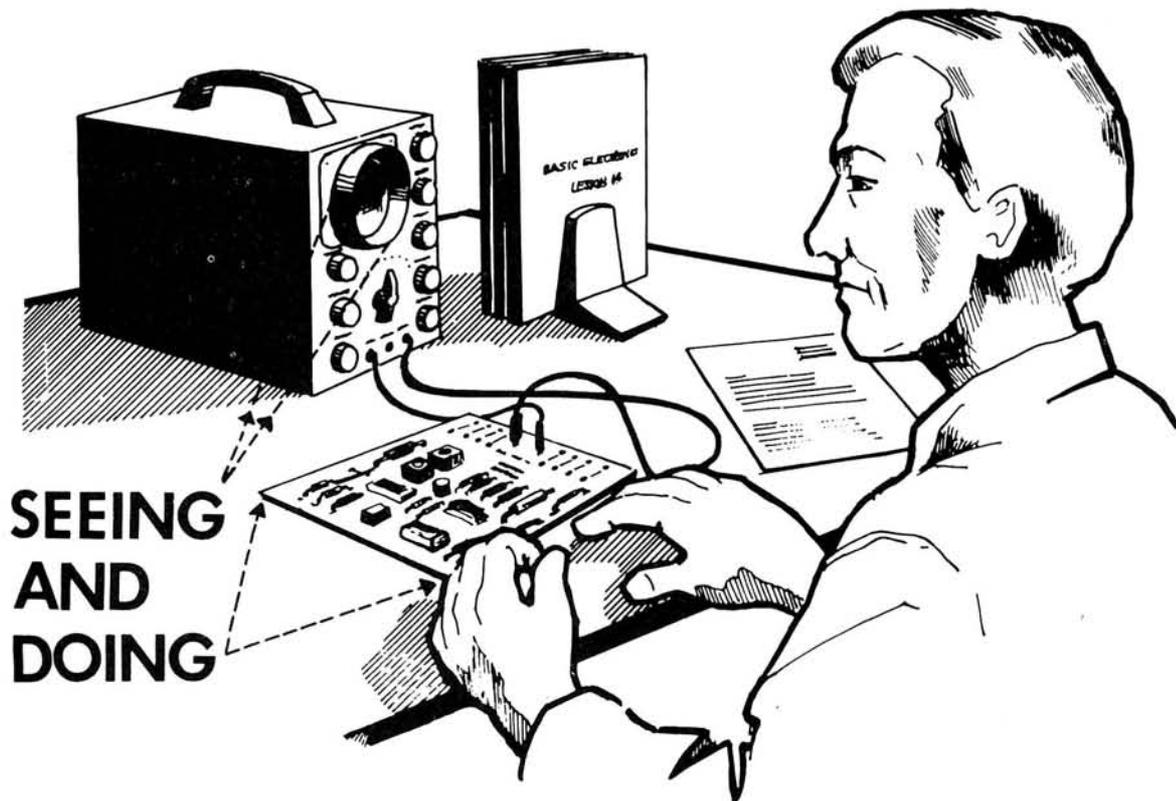
# Master Electronics the new Practical way.



SEEING  
AND  
DOING

## Conquer the 'Chip' — Easy-Fast-Exciting!

AND MASTER ALL THE NEW TECHNIQUES  
IN MODERN ELECTRONICS.

- Build an Oscilloscope.
- Carry out over 40 full experiments including work on Digital Electronic Circuits.
- Recognition of Electronic Components.
- Understand and draw Circuit Diagrams.
- Experience with handling Solid State Circuits and "Chips".
- Testing and Servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

Colour Brochure — without any obligation. Post to :—

PW/9/812

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**

4 Cleveland Road, Jersey, Channel Islands.

Name .....

Address .....

.....

.....

BLOCK CAPS PLEASE

TTLs BY TEXAS		74221 160p		74LS192 140p		74C157 250p		LINEAR I.C.s		MC1496 100p		TRANSISTORS		TIP41C 78p		2N3866 90p		DIODES																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
7400	11p	7497	180p	74251	140p	74LS193 140p	74C160 155p	AY1-0212 600p	MC1496 100p	AD127/8 20p	BFY51/2 22p	TIP42A 78p	2N3803/4 18p	BY127 12p	7401	12p	74100 130p	74259 250p	74LS195 140p	74C161 155p	AY1-1313 600p	MC3340 120p	AD149 70p	BFY56 33p	TIP42C 82p	2N3905/6 20p	OA47 9p	7402	14p	74104 65p	74285 90p	74LS196 120p	74C162 155p	AY1-5050 212p	MC3360 120p	AD161/2 45p	BFY90 90p	TIP2955 78p	2N4036 65p	OA81 15p	7403	14p	74105 65p	74278 290p	74LS221 100p	74C163 155p	AYS-1224A 225p	MF50398 750p	BC107/8 11p	BRV39 45p	TIP3055 70p	2N4058/9 12p	OA85 15p	7404	14p	74107 34p	74283 190p	74LS241 175p	74C164 120p	AY5-1315 900p	NE531 100p	BC109 11p	BSX19/20 20p	TIS43 34p	2N4060 12p	OA90 9p	7405	18p	74109 55p	74284 200p	74LS242 175p	74C173 120p	AY5-1320 320p	NE555 25p	BC147/8 9p	BU105 190p	TIS93 30p	2N4061/2 18p	OA91 9p	7406	32p	74111 70p	74285 400p	74LS243 175p	74C174 160p	AY5-1320 320p	NE556 70p	BC149 10p	BU205 220p	ZTX108 12p	2N4123/4 22p	OA95 9p	7407	18p	74112 70p	74290 150p	74LS244 100p	74C175 210p	CA5019 80p	NE561 70p	BC159 11p	BU208 240p	ZTX300 11p	2N4125/6 22p	OA200 9p	7408	19p	74116 130p	74293 150p	74LS245 100p	74C192 150p	CA3046 70p	NE561B 425p	BC169C 12p	BU406 145p	ZTX500 18p	2N4289 20p	OA202 10p	7409	19p	74118 130p	74293 150p	74LS245 100p	74C193 150p	CA3048 225p	NE562B 425p	BC172 12p	MJ2501 225p	ZTX504 30p	2N4401/3 27p	IN914 4p	7410	15p	74119 210p	74294 200p	74LS246 200p	74C194 220p	CA3080E 72p	NE565 130p	BC177/8 17p	MJ2955 190p	2N4427 90p	2N4427 90p	IN916 4p	7411	24p	74120 110p	74295 200p	74LS247 200p	74C195 110p	CA3089E 225p	NE566 155p	BC179 18p	MJ3001 225p	2N4471 60p	2N5087 27p	IN4148 4p	7412	20p	74121 28p	74296 200p	74LS248 248p	74C221 175p	CA3090A Q37p	NE567 175p	BC182/3 10p	MJE300 25p	2N5089 27p	2N5089 27p	IN4001/2 5p	7413	30p	74122 48p	74366 150p	74LS259 175p	4000 SERIES	CA3130E 100p	NE567 175p	BC184 11p	MJE305 70p	2N5172 27p	2N5172 27p	IN4003/4 5p	7414	60p	74123 48p	74367 150p	74LS373 200p	4000 SERIES	CA3140E 78p	CA3140E 78p	BC187 10p	MJE2955 100p	2N5179 27p	2N5179 27p	IN4006/7 6p	7416	27p	74125 55p	74368 150p	74LS374 195p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC212/3 11p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7417	27p	74126 60p	74390 200p	81LS95 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7420	17p	74128 75p	74393 200p	81LS96 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7421	40p	74132 75p	74399 225p	81LS97 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7422	22p	74136 60p	74490 225p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7423	34p	74141 70p	74490 225p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7425	30p	74142 200p	74500 140p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7426	40p	74145 90p	74502 18p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7427	34p	74147 190p	74504 14p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7428	36p	74148 150p	74508 22p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7430	17p	74150 100p	74510 28p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7432	30p	74151 70p	74513 38p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7433	40p	74153 70p	74514 70p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7437	35p	74154 100p	74520 22p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7438	35p	74155 90p	74522 28p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7440	17p	74156 90p	74527 38p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7441	70p	74157 70p	74530 22p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7442A	60p	74159 190p	74547 90p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7443	112p	74160 100p	74555 30p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7444	112p	74161 100p	74573 50p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7445	100p	74162 100p	74574 40p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7446A	93p	74163 100p	74575 50p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7447A	70p	74164 100p	74583 110p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7448	80p	74165 130p	74585 100p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7450	170p	74166 100p	74586 40p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7451	17p	74167 200p	74590 60p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7453	17p	74170 240p	74593 60p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7454	17p	74172 720p	745107 45p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7460	17p	74173 120p	745112 100p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7470	36p	74174 95p	745123 75p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7472	30p	74175 85p	745132 90p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7473	34p	74176 90p	745133 60p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7474	30p	74177 90p	745138 60p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7475	30p	74178 160p	745139 60p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7476	35p	74180 90p	745151 100p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7480	50p	74181 200p	745153 60p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7481	100p	74182 90p	745157 80p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7482	84p	74184 150p	745158 120p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7483A	90p	74185 150p	745160 100p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7484	100p	74186 600p	745161 100p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7485	110p	74190 100p	745162 140p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7486	34p	74191 100p	745163 100p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7489	170p	74192 100p	745164 120p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7490A	30p	74193 100p	745165 80p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7491	30p	74194 100p	745173 110p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7492A	46p	74195 95p	745174 110p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7493A	36p	74196 95p	745175 110p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7494	36p	74197 80p	745181 320p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7495A	70p	74198 150p	745190 100p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p	7496	85p	74199 150p	745191 100p	81LS98 140p	4000 SERIES	CA3160E 75p	CA3160E 75p	BC214 12p	MJE3055 70p	2N5181 83p	2N5181 83p	IN5401/3 14p



# Wilmslow Audio

**THE firm for speakers!**

**SEND 50p FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.**

AUDAX ● AUDIOMASTER ● BAKER ● BOWER & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNON ● VIDEOTONE ● WHARFEDALE ●

**WILMSLOW AUDIO (Dept. P.W.)**  
**SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF**

Tel: 0625 529599  
 FOR MAIL ORDER & EXPORT OF DRIVE UNITS, KITS ETC.  
 Tel: 0625 526213  
 (SWIFT OF WILMSLOW) FOR HI-FI & COMPLETE SPEAKERS

## AT BLINKIN' LAST

# COLOURBOARD II

THE NEW 50HZ COLOUR VERSION OF OHIO SCIENTIFIC'S SUPERBOARD II IS HERE AND LIKE A TON OF BRICKS DOWN CRASHES THE PRICE OF STANDARD SUPERBOARD II

50HZ UK BLACK AND WHITE SUPERBOARD II £159.95-15% VAT POST FREE.  
 COLOURBOARD II £205 + 15% VAT.


THE UNIQUE SPECIAL OFFER YOU CAN'T RESIST

\*\*\*\*\*  
 \* If bought with superboard or colour board these items are at the reduced prices shown first. Also sold separately at the bracketed prices. Add 15% VAT. Modulator and power supply kit £7.95 (£11). 4K extra ram £

# MORE BIG VALUE FROM YOUR TANDY STORE
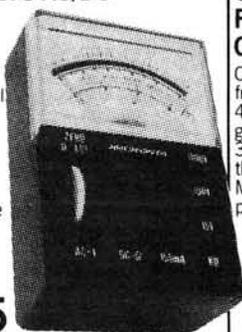
## 1000 OHMS/VOLTS AC/DC 8 RANGES

Handy multimeter for home and work-shop. Easy-to-read two colour 5cm meter, pin jacks for all 8 ranges. Reads AC and DC volts: 0-15-150-1000 DC current; 0-150 mA. Resistance: 0-100,000 ohms. Accuracy:  $\pm 3\%$  full scale on DC ranges,  $\pm 4\%$  on AC ranges. Complete battery. REG. PRICE 22-027.



**£6.95**

## 6-DIGIT FREQUENCY COUNTER

Counts frequencies from 100 Hz to over 45 MHz with 100 mS gate time. Accuracy is 3 ppm at 25°C or less then  $\pm 30$  Mhz on 10 MHz! Overload-protected 1-meg input. Sensitivity, 30 mV up to 30 MHz. Req. 9V battery. REG. PRICE 22-351.



**£79.95**

## MULTITESTER

Dual FET input for accuracy and minimum loading. 11.5cm mirrored scale. DC volts, 0-1-3-10-30-100-300-1000. DC current 0-100 a. 0-3-30-300 milliamp. Resistance 0-30-300-3k-301C-1 megaohm. 0-100-1k-101C-100K-3 megaohms. Req. 9V battery. 22-209.



REG. PRICE  
**£29.95**

## TRANSISTORIZED SIGNAL TRACER

Spot circuit troubles and check RF, IF and audio signals from aerial to speaker on all audio equipment. With 9V battery, instructions. 22-010.



REG. PRICE **£9.95**

## DIGITAL IC LOGIC PROBE




Unique circuitry makes it a combined level detector, pulse detector and pulse stretcher. Hi-LED indicates logic "1". Lo-LED is logic "0". Pulse LED displays pulse transitions to 300 nanoseconds, blinks at 3 Hz for high frequency signals (up to 1.5 MHz). Input impedance: 300K ohms. With 36" power cables. 22-300.

REG. PRICE **£19.95**
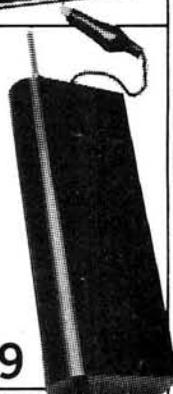
## SIGNAL INJECTOR

For RF, IF, AF circuits. Maximum accuracy. Easy pushbutton operation. Needs two "AA" batteries. 22-4033.



REG. PRICE **£2.79**

## AC/DC CIRCUIT TESTER

Accuracy in 1-300 volts ranges. Safe in live/dead circuits. Needs two "AA" batteries. 22-4034.

REG. PRICE **£1.99**

## REALISTIC DX 300

General coverage receiver. Quartz-synthesised tuning, digital frequency readout. 3-step RF Attenuator. 6-range preselector with LED indicators. SSB and CW demodulation. Speaker. Code oscillator. Batteries (not included) or 12V DC. 20-204.


REG. PRICE **£229.95**



## DYNAMIC TRANSISTOR CHECKER

Shows current gain and electrode open and short circuit. Tests low, medium or high power PNP or NPN types. Go/no-Go test from 5-50mA on power types. 22-024.

REG. PRICE  
**£9.95**

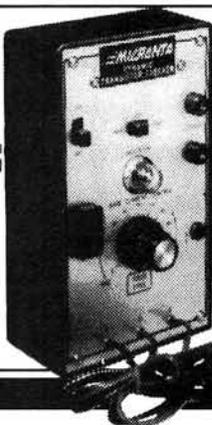

## VARIABLE POWER SUPPLY

Power project boards, IC's, other low-voltage DC equipment. Load regulation: less than 450mV at 1 amp at 24V DC. Ripple: less than 25mV. Maximum output current: 1.25 amps. Switchable colour-coded meter reads 0-25V. DC and 0-1.25 amps. Three-way binding posts take wires, banana plugs or dual banana plugs with 0.75" centres. For 220/240V AC. 22-9123

REG. PRICE **£35.95**



You save because we design, manufacture, sell and service. Tandy have over 7,000 stores and dealerships worldwide. Over 2,500 products are made

specifically for or by Tandy at 16 factories around the world. The quality of our products has been achieved by over 60 years of continuous technological advancement.

KNOWN AS RADIO SHACK IN THE U.S.A. MAKERS OF THE WORLD'S BIGGEST SELLING MICROCOMPUTER TRS80

# TANDY

The largest electronics retailer in the world.

Offers subject to availability. Instant credit available in most cases.

OVER 170 STORES AND DEALERSHIPS NATIONWIDE.



## TANDY DEALER

Most items also available at Tandy Dealers. Look for this sign in your area.



Access. Barclaycard and Trustcard welcome. Prices may vary at individual stores.

**POWER UNITS** as follows: all 240v I/P & tested. Small bench p.u. O/P var nom 5 to 15v DC stab at 2 amps max in neat case size  $9\frac{1}{2} \times 5\frac{1}{2} \times 7\frac{1}{2}$ " fitted fuse, on/off swt & ind with screw terminals for o/p with circ £27. **BENCH P.U.** Solartron HT o/p var 0 to 500v DC at 100Ma to 350v also 6.3v ac Ct at 3 amps fitted Volt/Ma meter in case size  $13 \times 13 \times 8$ " tested with circ £22. **BENCH P.U.** gives two separate stab O/Ps of 24v DC each rated 500Ma with S/C protection limited internal adjustment fitted AC/DC fuses & o/p terminals on front panel in case size  $17 \times 7 \times 9$ " with front cover tested, would mod for 1 amp o/p as dual sec C core mains trans fully enclosed unit £25.

**AUDIO TEST SET CT373** comprises Audio Osc 17c to 170Kc AF VTVM & Distortion measuring set all in same bench case, supplied with handbook circ etc further details on request £80.

**ADVANCE TYPE J.1 AF Osc** small bench unit range 15c/s to 50Kc in 3 ranges o/p at 5 & 600 ohm var up to 25v size  $13 \times 9\frac{1}{2} \times 7$ " good cond £45.

**TAPE RECORDERS E.M.I.** type TR52 series high grade unit 2 channel, two speeds, int mon speaker 3 & 600 ohm o/p, low imp & 600 ohm I/P in case size  $21 \times 18 \times 15$ " about 45Kg supplied with handbook, qty of tape etc further details on request £70.

**POWER UNIT** small sub unit made for use with BC221 or similar freq meter, fits in battery comp. gives +135v at 20Ma DC & 6.3 at 1 amp, stab HT, with C/Bx £12.

**HEADPHONES ARMY** type DLR.5 low res balanced armature type can be used as sound powered intercom £3.50 per pair or 2 prs £6.

**MAINS TRANS** all 240v as follows: A. Secs 340-250-0-250-340v at 210 Ma 6.3v 5 amps twice & 5v ct 5 amps £10.50; B. Auto Trans 200/250v 3 taps to 115v at 560 watts fully enc case size  $6\frac{1}{2} \times 4 \times 3\frac{1}{2}$  with term conn. £13.50.

**MONITOR 4436** General purpose scope unit suitable Radio & Audio Servicing Y Amp 10 Mill/V per Cm at 300Kc TB range 10c to 5Kc free running TB with int ext sync all normal scope controls fitted, 3" Tube green trace in case size  $12 \times 9\frac{1}{2} \times 23$ " about 30Kg, 240v 50c I/P supplied tested with handbook & circ. £50.

**ARMY FIELD CARRIER TELEPHONE UNITS** sold for breakdown, contain main frame in case size  $16 \times 12 \times 14$ " with 7 plug in modules plus two fixed units, these contain transis, elec & tant conds, high stab res, rot swt, tog, swts, fuses, large number of LF filters & trans, 3" speaker weatherproof, small meter, term posts, handset etc all in clean cond, unit works on 24v DC £25.

**RECORDING TAPE** by Ampex Mill Spec  $\frac{1}{4}$ " Audio type 3600' on  $10\frac{1}{2}$ " spools new £7.50.

**T.V. TUNERS UHF** type manual tuned with circ new transis £2.60 or 2 for £4.50 or 10 for £20.

**CONNECTORS** Plessey type 12 way in brass quick disc sqmt flange £1.50 per pair.

**DYNAMOTOR UNIT** I/P 24v DC O/Ps 210 & 400v DC can be used as motor by removing fan gives  $\frac{1}{4}$ " shaft will run on 12v DC size exc shaft  $6\frac{1}{2} \times 3\frac{1}{2}$ " dia £6.50.

**SIG GENs** Army No. 12 35kc to 18.3 Mc/s in 8 bands AM & FM on some bands int xtal check O/P var .1 Uv to 1v high revolution film scale standard mains I/P note heavy unit about 50Kg in transit case £45.

**HELIPOT DIALS & POTS** 10 Tr dial to fit 3/8th bush £1.50; Beckman 15 Tr to fit 3/8th bush £2.50; 30 or 100K Helipot £1 ea or 50p with dials.

**ARMY Tx/Rx unit** Mk.123 compact mains or 12v DC operated unit Rx tunes 2.5 to 20Mc/s in 3 bands with RF stage BFO etc O/P for phones, Tx covers 2.5 to 20Mc/s crystal controlled CW only about 15/25 watts over band, with built in morse key & tuning meter size inc mains p.u.  $30 \times 9 \times 14$  Cm about 4 Kg supplied with ext 12v Inverter p.u. tested with handbook mains lead & phones £58 also Hand Gen at £25.

**SMALL RX UNIT** 5 valve inc BFO battery operated Rx tunes 2 to 8Mc/s in two bands direct cal in case with circ req 135v HT & 1.5v uses B7g valves £13 also matching Tx unit crystal controlled CW only about 1 watt power as Rx with circ £5.50.

**INVERTOR UNITS** for use on 12v DC O/P 180v at 40Ma or 425v at 120Ma also 6v DC at 2.5 amps in case size  $5\frac{1}{2} \times 4 \times 3$ " tested with circ. £10.50.

**SLOW MOTION DRIVE** 9.1 with knob & scale also 2.5 or 25K 360' as req £3.

**HEAVY DUTY SLIDE RESISTORS** rated 1 ohm 12 amps £4.50.

**MAINS FILTERS** 250v 1.5 amp size  $2\frac{1}{2} \times 1\frac{1}{2} \times 1$ " new £2.20.

**MIRRORS** Searchlight mirrors silvered steel backed  $20\frac{1}{2}$ " dia  $3\frac{1}{2}$ " deep at centre with hole  $3\frac{3}{4}$ " dia clean may have some scratches due to storage £25.

Above goods ex equipment unless stated new, prices include Carriage & VAT. SAE for Enquiry or 2 x 10p stamps for list 25. We can also supply circs & handbooks for some equipments.

**A. H. SUPPLIES**  
122 HANDSWORTH RD,  
SHEFFIELD S9 4AE  
Phone 444278 (0742)

## PCB'S FOR PRACTICAL WIRELESS PROJECTS

Jan. 80.	Nimbus Radio Control Encoder	WR061	Price £2.28 30 pence p&p.
Jan. 80.	Nimbus Radio Control Rec.	WR064	Price £2.92 30 pence p&p.
Jan. 80.	A.F. Speech Processor	WR068	Price £2.28 30 pence p&p.
Jan. 80.	P.W. Parkhurst Alarm	WR063	Price £2.51 30 pence p&p.
Jan. 80.	Wide Band Pre Amp.	WR067	Price £0.70 30 pence p&p.
Jan. 80.	Nimbus Radio Control T.X.	WR062	Price £2.26 30 pence p&p.
Oct. 78.	Mosfet Converter	RO24	Price £2.50 30 pence p&p.
Jan. 78.	Direct Conversion Rec.	DO43	Price £2.50 30 pence p&p.
May 78.	DX Audio Filter	DO01	Price £2.50 30 pence p&p.
May 78.	Digital Lock	DO02	Price £1.40 30 pence p&p.
Mar. 80.	Duel Trace Unit	WR069	Price £7.10 30 pence p&p.
April 80.	Speed Controller	WR065	Price £1.50 30 pence p&p.
April 80.	Stereo Auto Fader		
	Mike Pre Amp.	WR071	Price £1.05 30 pence p&p.
April 80.	Stereo Auto Main Board	WR072	Price £3.16 30 pence p&p.
April 80.	Signal Generator	WR070	Price £2.71 30 pence p&p.
April 80.	P.W. Nimbus Relay	WR075	Price £0.55 30 pence p&p.
April 80.	P.W. Nimbus Modulator	WR074	Price £0.70 30 pence p&p.
April 80.	Nimbus Transceiver	WR073	Price £5.30 30 pence p&p.
May 80.	Hundred Second Photo Timer	WR078	Price £2.48 30 pence p&p.
May 80.	N.B.F.M. Demodulator	WAD509	Price £1.83 30 pence p&p.
June 80.	Audio Limiter Main Board	WK076	Price £2.00 30 pence p&p.
June 80.	Audio Limiter	WK077	Price £1.15 30 pence p&p.
June 80.	Audio Limiter RF Input Board	WR079	Price £1.30 30 pence p&p.
June 80.	VHF/UHF Repeater Timer Main	WR080	Price £1.90 30 pence p&p.
June 80.	P.W. Nimbus Base		
	Station Adpt.	WR083	Price £2.60 30 pence p&p.
June 80.	Acoustic Flash Trigger	WRK84	Price £1.25 30 pence p&p.

### FULL RANGE OF RS COMPONENTS AVAILABLE

THIS MONTHS SPECIAL OFFER

8" x 5" ELLIPTICAL SPEAKERS

£2.30 EACH PLUS 75p p&p.

RATED AT FIVE WATTS. 15 OHM SPEECH COIL.

**C. BOWES ELECTRONICS**  
252A Stockport Road, Cheadle Heath,  
Stockport, Cheshire SK3 0LX.  
Tel: 061-428 4497

Please enclose cheque or postal order with order.

## BOMB PROOF POWER!



The WINTON is still the OUTSTANDING KIT ACHIEVEMENT of the decade. Using POWER MOS-FET's in the OUTPUT STAGE it provides a 50+50 WATTS at less than 0.1% distortion over the whole audio band.

The Power MOS-FET's we use are practically 'Bomb Proof' without the need for distortion introducing protection devices, or as some coyly name them "Thermal Overload Cutouts". Our MOS-FET's don't suffer from thermal runaway or secondary breakdown as ordinary transistors do.

Requiring around twenty hours to build you finish up with an amplifier which is equal to, or better than ready built designs costing upwards of £600, and you have the enormous satisfaction of having built it yourself.

A 12p stamp will bring you the full details or better still, send your cheque for the best amplifier kit around. POWER MOS-FET's RULE, O.K.

COMPLETE KIT, of all parts necessary to build the P.W. WINTON £133.50

Order with complete confidence (C.W.O. only please) from:

**T.&T. ELECTRONICS**

Green Hayes, Surlingham Lane, Rockland St. Mary,  
Norwich, NR14 7HH. Telephone 05088 632

PRICE INCLUSIVE OF V.A.T. & CARRIAGE.

Callers by appointment only



WHAT WILL THEY THINK OF NEXT

NEW



**CASIO'S NEW LCD ANOLOGUE AND DIGITAL STOPWATCH 56 QS-508.** COUNTDOWN 12/24 hr DISPLAY. R.R.P. (£39.95) £24.45  
**TIME DISPLAY.** Digital. Hours, minutes, seconds, AM/PM (optional 12 or 24 hour display). Analogue. Seconds.  
**TIME-CALENDAR DISPLAY.** Digital. Month, date, day, Analogue. Hour, minute.  
**STOPWATCH.** Measuring net, lap and first and second place times from 1/10 second to 59 minutes 59.9 seconds.  
**COUNTDOWN.** Measuring capacity 60 minutes, in 1/10 second units. Setting to 1 second. Countdown can be stopped and restarted for net time measurement.  
**CALENDAR.** Auto 4 year. Case all stainless steel 8.3mm thick. Water resistant. Mineral Glass. Backlight. 2 year battery.  
 As above 56 QS-388 with chrome plated case. R.R.P. (£29.95) £24.45

BEST BUYS

**81 QS-358 ALARM CHRONOGRAPH.** Stainless steel. Mineral glass. Water resistant. 5 year battery. Hours, minutes, seconds, day, and date, month and year. 12 or 24 hour display. 24 hour alarm, hourly chimes. Stopwatch from 1/100 second to 7 hours, net, lap and 1st and 2nd place times. R.R.P. (£29.95) £24.45  
**83 QS-408** as above with chrome plated case. R.R.P. (£29.95) £24.45  
**83 QS-41B ALARM CHRONOGRAPH.** Stainless steel encased. Mineral glass. Water resistant. 3 year battery. Hours, minutes, seconds and date. AM/PM, or hours, minutes, alpha day, date, AM/PM. 24 hour alarm, hourly chimes. Stopwatch from 1/10 second to 12 hours; net, lap and 1st and 2nd place. Nightlight. R.R.P. (£29.95) £24.45  
**83 QGS-41B** as above gold plated case and strap. £29.95  
**F.80** as 83QS-41B black resin strap and case, stainless steel back and front trim. R.R.P. (£24.95) £19.45 only

C.80 CALCULATOR WATCH

Finger touch keyboard. Hours, minutes, seconds, AM/PM, day, date, month auto calendar programmed to 2003. With 24 hour stopwatch, net, lap and 1st and 2nd place times. To 1/100 sec. Dual time, 8 digit calculator. Nightlight, water resistant, mineral glass, black resin case/strap. R.R.P. (£29.95) ONLY £24.45



NEW

STAINLESS STEEL CASE/STRAP VERSION OF C.80. R.R.P. (£34.95) £29.45

ALL OTHER CASIO WATCHES  
EX STOCK MOST MODELS

NEW IT BRINGS MUSIC TO YOUR EARS AND EASY ON YOUR POCKET CASIO'S ML.90.

**CLOCK:** Hours, minutes, seconds, AM/PM  
**HOURLY TIME SIGNAL** Every hour on the hour.  
**CALENDAR** programmed to Dec 31 1999, year, month and date.  
**ALARMS:** Alarm 1 buzzer (30 secs) or 7 different melodies. Alarm 2 buzzer (30 secs) or a fixed melody.  
**DATE MEMORY.** 1. A fixed melody. 2. Two selectable melodies i.e. happy birthday, wedding march etc. Dec. 24-25 Jingle Bells. Tunes programmed 12 popular melodies.  
**STOPWATCH.** Up to 9 hrs, 59 mins, 59 secs, and 9/10 of a second. Net, lap and 1st and 2nd place times.  
**MUSICAL FUNCTION.** Manual or pre-programmed melody playing.  
**CALCULATOR** +/−/×/÷, automatic accumulation in four calculations. Memory, % √, 8 digits.  
 1 year continuous battery life.



**IF YOU WANT MUSIC WHILE YOU WORK PLAY A ML.90.** R.R.P. (£22.95) ONLY £19.45  
**ML 81 MUSICAL CLOCK CALCULATOR.** 2 musical alarms, countdown timer, stopwatch from 1/10 second to 12 hours. Net, lap, 1st and 2nd place. Calculator with full memory +/−/×/÷/√. 1 year battery. R.R.P. (£25.95) £22.45  
**ML 71** as above with one melody alarm mini-card. R.R.P. (£25.95) £22.45  
**ML 82 MUSICAL CLOCK CALCULATOR** with alarm, calendar, stopwatch. R.R.P. (£22.95) £19.95  
**AQ2200** permanent display of full month calendar, clock, alarm, hourly chimes, stopwatch from 1/10 second to 10 hours; net, lap, 1st and 2nd place times. Calculator with full memory % √. One year battery. R.R.P. (£21.95) £19.45  
**AQ1500** similar to above without month display. No alarms. R.R.P. (£17.95) £14.45

CASIO'S LATEST SCIENTIFIC CALCULATORS

**FX8100** Hours, mins, secs, AM/PM, day. Calendar pre-programmed to 1999. 24 hour alarm. Alarm timer, interval timer, or 1/100 sec. Stopwatch; net lap and 1st, 2nd place times. Fractions, % cube roots, 5 levels of parenthesis, hyperbolics, standard deviations, co-ordinates, conversions. 46 scientific functions. 1 year batteries. R.R.P. (£27.95) £24.45  
**FX7100** as FX8100 only 30 scientific functions, 8 digits, 1 alarm. No hyperbolics, fractions, or calendar. 1 countdown alarm or 24 hour alarm. Hourly chimes. Mini card size. Complete with leatherette wallet. R.R.P. (£27.95) £24.45  
**FX501P** 11 memories and 128 programming steps. 10 digit. R.R.P. (£64.95) £52.95  
**FX502P** 22 memories and 256 programming steps. 10 digit. R.R.P. (£84.95) £72.95  
**FA1** adaptor for 501P and 502P programme on to cassette tape. R.R.P. (£24.95) £18.95

ALL OTHER CASIO CALCULATORS  
EX STOCK MOST MODELS

CASIO Details. Send 20p for full details of Watches and Calculators. TERMS OF BUSINESS: Please note all CASIO items PRICE INCLUDES VAT, P&P and Insurance. Please send cheques or P.O.s or quote Access or Barclaycard No. to: B. BAMBER ELECTRONICS, 24 hour phone service. (0353) 860185. Callers welcome Tues-Sat 9.30-5.30 pm.



B. BAMBER ELECTRONICS DEPT: PW 5 STATION ROAD LITTLEPORT CAMBS 6BG 1QE




**TRIO CS1566** 20MHz triggered sweep oscilloscope. £339.00 + VAT  
**TRIO CS1562A** 10MHz triggered sweep oscilloscope. £259.00 + VAT  
**HAMEG** oscilloscope HM307 LPS triggering bandwidth d.c. to 10MHz. Component tester. Timebase 0.2 us-0.2 s/cm. £149.00 + VAT  
**HAMEG** HZ36 switchable probe for HM307. £11.00 + VAT  
**DACTRON** PX402 13.8 DC 3 amp continuous 4 amp max. Fully stabilised power supply with overload protection. £39.50 + VAT  
**DACTRON** PH 5000 13.8 DC 5 amp continuous. £39.50 + VAT  
**DIN PANEL METERS** DIN 75: 0-5 amps DIN 715: 0-150 volts DIN 730: 0-300 volts DIN 700: 0-500 volts 72 x 72 mm range. £8.00 + VAT  
**EAGLE** DD7 paging microphone impedance 600 ohm or 50K ohms sensitivity 2.25mV at 50K ohms. Frequency response 300-900Hz. Desk or wall mounted. £14.85 + VAT  
**EAGLE MULTI-METER.** EM50 50,000 DPV DC volts: 0-1200 volts AC volts 0-1200 volts. DC current 0-6A resistance 0-10 Meg ohms. £19.95 + VAT  
**DRAPER SUPER CHROME** 1/4" sq drive socket sets. 33 piece 9 AF hexagon 3 AF BI-sq sockets. 11 mm hexagon sockets 9 BA hexagon sockets 6 Access. £12.75 + VAT  
**SPIRALUX AND DRAPER** nut spanners and sets. Large selection. Refer to catalogue or SAE for full details.  
**WELLER TCP3** irons 24 volt series 3 wire power units. For application requiring earthed tip. Also PU30 power units. TCP3 £13.84 + VAT PU30 £24.12 + VAT  
**WELLER INSTANT HEAT GUNS** Model No 81000 £13.21 + VAT  
**WELLER CORDLESS** Model No WC100 £25.47 + VAT  
**SUPA SERVISOL** Switch cleaner £0.72 + VAT  
**MARYPLASS** storage boxes 5P2 combination draw pack interlocking storage boxes (contains 1 x 600 x 201 5 x 10) Per Pack £48.40 + VAT  
**DRYX DE-SOLDER TOOLS** Model SR3A desoldering pump with built in safety guard. Price £65.50 + VAT  
**I.C. TEST CLIPS** Clip over IC while still soldering to PCB or in sock. Gold plated pins. Ideal for experiments of service engineers. 28 pin DIL £1.75 40 pin DIL £2.00 or save buy one of each For £49.50 + VAT  
**I.C. AUDIO AMP P.C.B.** Output 2 watts into 3 ohm speaker. 12V DC supply. Size approx. 5 1/2 in x 1 1/2 in x 1" high with integral heatsink complete with circuit. £2.00 each + VAT

CALL IN AND SEE US  
OUR NEW SHOP IS OPEN

**CATALOGUE 1980.** Send 40p and you will receive our 104 page catalogue, products by Eagle, Yaezu, Standard, Trio, Hameg, Microwave Modules, Amtron Kits & Boxes, Vero, Draper, Spiralux, Knipex, Weller, Servisol, Jaybeam, Amtron by Barnard & Babani - Newnes and many more.  
**TERMS OF BUSINESS:** Cheques, P.O.s or Phone Access or Barclaycard No. 24 hour phone service. Please add VAT AT 15% on all above goods. CARRIAGE and packing charges for all orders under £5.00 nett invoice value add 75p. Orders over £5.00 and under £20.00 add 50p. Orders over £20.00 carriage free. Callers welcome 9.00 am-5.30 pm Tues-Sat. (0353) 860185.

TOP PRIORITY for every

constructor . . .

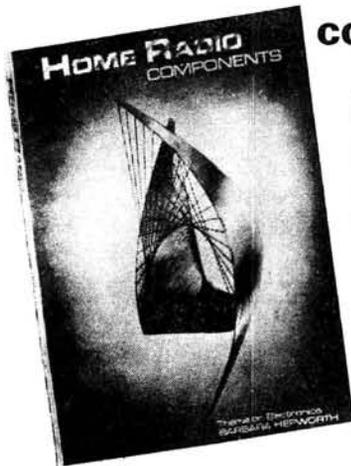

HOME RADIO CATALOGUE

- Over 2,000 items clearly listed.
- Profusely illustrated throughout.
- Over 100 A-4 size pages.
- Bargain list included free.
- Catalogue contains details of simple Credit Scheme.

HOME RADIO (Components) Ltd.,  
Dept. PW., P.O. Box 92, 215 London Road, Mitcham, Surrey.  
Phone 01-648 8422

POST THIS COUPON with cheque or P.O. for £1.30

Please write your Name and Address in block capitals

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_



HOME RADIO (Components) LTD., Dept. PW  
P.O. Box 92, 215 London Road, Mitcham, Surrey. Regd No. 912966 London

PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Ansell) Copy of original article supplied on request

IF Sub-Assembly (G8) £7.82. P&P 85p.  
 Mullard ELC1043 V'cap UHF Tuner £6.33. P&P 40p.  
 3-way Station Control Unit £1.38. P&P 30p.  
 6-way Station Control Unit (Special Offer) £1.15. P&P 35p.  
 Power Supply Prtd Circuit Board £1.15. P&P 35p.  
 Res, Caps, Semiconds, etc. for above £6.67. P&P 45p.  
 Mains Transformer for above £3.80. P&P 35p.  
 P&P all items £1.00.


(Price of goods and P&P includes 15% VAT)  
Callers welcome at shop premises.

MANOR SUPPLIES

172 WEST END LANE, LONDON NW6

(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

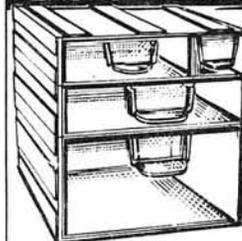NEAT! TIDY! HANDY! 1D 2D 3D 6D  
INTERLOCKING PLASTIC STORAGE DRAWERS



AS SUPPLIED: TO POST OFFICE & GOVT DEPTS


SINGLE UNITS (1D) (5in x 2 1/2in x 2 1/2in) £3.90 DOZEN  
 DOUBLE UNITS (2D) (5in x 4 1/2in x 2 1/2in) £6.50 DOZEN  
 TREBLE (3D) £5.90 for 8.  
 DOUBLE TREBLE 2 drawers, in one outer case (6D2) £8.90 for 8.  
 EXTRA LARGE SIZE (6D1) £7.90 for 8.

PLUS QUANTITY DISCOUNTS  
 Orders over £60, less 5%. PACKING/POSTAGE/CARRIAGE: Add £1.30 to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES. Please add 15% V.A.T. to total remittance. All prices correct at time of going to press.

FLAIRLINE SUPPLIES (PW9) 124 Cricklewood Broadway, London NW2 Telephone 01-450 4844

## Complete Audio/Tuner Kits

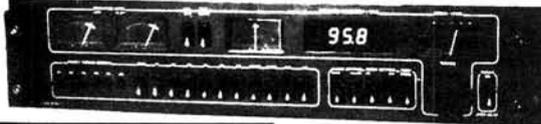

### Mk III FM Tuner series

Carriage for Mk III tuner £3 inc

The Mark III series FM tuner has been updated, and now includes a centre zero tuning meter as standard. The instruction manual has been meticulously revised, enabling easy assembly by constructors of various levels of experience - a preview copy may be purchased for £1.00.

Mark III A series 'Reference series' tuner modules .....£171.35 inc.  
Mark III B series 'Hyperfi' modules, with switched IF BW, pilot cancel decoder .....£198.95 inc.

A matching synthesiser unit will be made available later this year, and can be retrofitted to either version. All versions include digital frequency readout/clock, 10U deviation meters, 6 preset stations, 10 turn pot manual tuning, toroidal PSU, output level adjustment, 110/240v AC input. Full alignment service available.

### Power Amplifier

Style and performance - with a real 'belt and braces' PSU design.

After a couple of preview comments, it seems that many of you are waiting to hear about the matching HMOSFET power amplifier for the Mk III tuner. Well, it's out at last - complete with twin toroidal PSUs for comfortable 80W RMS per channel, over 100W peak, but limited by thermal shutdown of the HMOS. 10W-100W log LED output peak indicator, DC offset protection and switch-on pause relay. AC or DC input coupling, direct or relay protected output terminals. The works. Only one version of this item: Complete kit .....£178.25 inc. Carr. £5.

### Preamplifier

More features and facilities, thanks to DC switching and control design


Previewing the most comprehensive audio preamplifier yet..... DC switching of 7 inputs, plus two tape in/out, 2 low pass, 2 high pass active filters, genuine volume related loudness, 10dB channel matching, with DC volume, balance, bass and treble controls. Suitable for bus/remote control, tape dubbing, switched monitor etc. 80dB S/N, THD 75dB or better. Pluggable PU equalization boards, tone control override. Price for complete unit about £149 ex VAT.

## Semiconductors

### Radio/Communications ICs

FOR COMPLETE LISTINGS - SEE OUR NEW PRICELIST


CA3089E	2.11	HA1197	1.61	SD6000	4.31
CA3189E	2.53	CA3123E	1.61	TD4420	2.59
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38
HA11225	2.47	TBA651	2.53	MC1350P	1.38
HA12412	2.81	TDA1090	3.51	KB4412	2.24
KB4420	1.95	TDA1220	1.61	KB4413	2.24
TBA1205	1.15	TDA1083	2.24	KB4417	2.53
KB4406	0.80	TDA1062	2.24	MC3357P	3.16

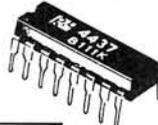

### VARICAP DIODES.....

A section from our PL:

BA102	0.35	16:1 ratio AM tuning
BB204	0.41	KV1215 9v triple
BB105	0.41	KV1211 9v dual
BB109	0.31	KV1225 25v triple
MVAM2	1.93	BB212 9v dual

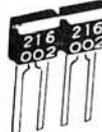

### POWER MOSFETS

100W PA's made simple

Since pioneering the 100W complementary MOSFET technique - Hitachi have developed a range of output devices and drivers that ought to revolutionise opinions and attitudes towards the design of all LF amplification systems. We have a new 48 page application note (£1.50 inc) and complete sets of parts, modules and now the new complete PA system (see above).

2SK133 120V N-ch 100W MOSFET £6.33 2SJ48 Pch complement £6.33  
2SK135 160V N-ch 100W MOSFET £7.29 2SJ50 Pch complement £7.39  
PA101B Kit for 100W MOSFET PA less Heatsink £16.10. (£23 inc heatsink/bkt)

### ULTRA LOW NOISE PU PREAMPLIFIER

The HA12017 is the last word in PU preamps, and general low noise audio design. It is an SIL IC, with 86dB S/N in RIAA configuration, 10v RMS output capability, 0.002% typ THD at 10v RMS output (imagine the overload margin !!). It comfortably supercedes discrete circuit designs in terms of price/performance, and takes the art beyond the TDA1042's capabilities. (Replaces HA1457) £1.80 each - or an RIAA applications PCB with two ICs for £5.75. Complete with Rs&Cs £9.95.

### Radio Control ICs

We have various RC ICs, including NE544 NE5044, and two new ones from OKI!

KB4445 - 4 channel dig.prop. FM TX IC. 30mW out (amplifiable) -£2.30 inc  
KB4446 - 4/5 ch. dig. prop FM RX IC. Suits KB4445 or RCME syst. £2.65.  
KB4445/6 pair: £4.75. New 8 page data sheet 35p + SAE. More RC ICs in list

### CMOS, LPSNTTL, TTL, MPU:

Most CMOS is available in low volume - also LPSN. Standard linears and TTL OK.

Listings in the new pricelist.

Things like ICM7216B, ICL8038, 8080A, 6800P, 2708, NE555, NE556, etc

### Coming Soon.....

Contain yourselves, RF fans! Not yet ready for a full launch until autumn, but previewed here:-

### SSB transceiver system : 10kHz to 1000MHz !!

A modular VLF to UHF SSB TX/RX system at last. With the correct first mixer, the basic PCB covers 10kHz to 1000MHz - using LO fed from ext. source (Our 2 IC Mullard synth for instance) and RF PA for TX. OP. 0.2uV basic sensitivity in HF, Typ cost for HF synth SSB RX will be less than £200. Add an RF PA for full TRX for another £50. See one in our foyer, and marvel.

Please send an SAE with all enquiries. Phone orders by ACCESS - but minimum £5. Callers welcome

CATALOGUES 60p ea., all three for £1.60. PRICES SHOWN HERE INCLUDE VAT. POST/PACKAGE CHARGE NOW 30p

**ambit**  
INTERNATIONAL

CWO PLEASE: Commercial MA terms on application. Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt.

**200 North Service Road, Brentwood, Essex**


TELEPHONE (STD 0277) 230909. TELEX 995194 AMBIT G. POSTCODE CM14 4SG

Parts 1-3 AMBIT catalogues 60p ea, or £1.60 the lot.

## Radio/Audio/Communications Modules
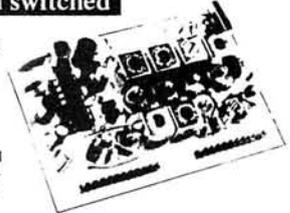
### LW-MW-SW-SW DC tuned and switched

91072- All switching of bands by a single pin to gnd. Varicap tuned, with LO output for synth. MW/LW version or MW/LW plus 1 or 2 SW bands. MW/LW: £15.58 +1SW £16.73



### VHF Tunerheads

Europe's largest stock range for broadcast and communications. Probably also the world's - details in the catalogues and PL. Specials are also supplied in the region 30-220MHz.

### Pilot Cancel PLL Stereo decoders

Again, Europe's widest range of stereo decoders including pilot cancel PLL types. The pic shows the 944378 - pilot cancel including post decoder 26/38kHz filtering and muting preamp output

944378-2 £26.45



### Switched bandwidth FM IF strips

Broadcast FM IF strips for all occasions, including the new 911225 - with diode switched narrow filter option, ultra linear phase ceramic filters, 84dB S/N, and 0.04% THD (40kHz deviation). Plus usual things like AGC, AFC, dev. mute, level meter drive. £23.95 (supplied in screen can with 0.1 edge connection system) Also the 7230 hyperfi series - as the 911225, but with slope controlled AFC that operates in conjunction with signal level - and an extra IF amp stage for DXing.

### Various digital frequency displays

The World's largest range of receiver DFMs is now joined by the DFM7 (shown) - and L shaped version of the DFM3 with remote display mount connector possibility. 1kHz SW resolution with 455kHz or 10.7MHz offsets, 100Hz res up to 3.9999MHz, and VHF to 299.99 MHz in 10kHz steps : £41.75



## Components

### Crystal Filters

Most popular types are available ex-stock, and in quantity.

10.7MHz	25kHz Channel spacing	8pole	£16.67
	12½kHz	"	£17.82
	2.4kHz SSB	"	£19.78
	Monolithic dual roofing filter		£2.30
34.5MHz	1.3dB loss, 80dB stopband	HF first filter in synth. RX	£36.80
RC XTALS	FM pairs (no spits)		£3.74
	AM pairs		£3.57
USB/LSB	Xtals for 10.7SSB filter		£2.88 ea



### Piezo Sounders

The most efficient warning sounders yet

The latest thing in electro-acoustic efficiency. 1mA of drive from CMOS will give an SPL of 83dB - 10v RMS drive from CMOS uses 3mA for 100dB SPL at 4.8kHz (88dB at 1.65kHz). The data sheets shows various drive circuits, and give full specifications with regard to broadband responses and power consumption etc. 1 off 44p inc. 100 off 28.75p (25p ex vat)

### Keyboard switches and caps

From the world's most widely used switch manufacturers - ALPS - come the biggest and best range of keyswitches, and data entry keyboard switches. The SCM81101 is shown here, with the KT5 2-part cap (with clear top, to enable easy fitting of your chosen legend. Other types are available with built in LED, 90° mounting etc. SCM81101: 17p, KT5: 16p - or 29p/pair



### LCD CLOCKS

Clocks use 1.5v at 15uA only - DVM 9v/1mA

### LCD DVM

CM161: 7mm LCD 12/24hr, alarms etc £11.44 each  
CM172: 13mm, 12hr, alarms, timer etc £14.32 each  
CM174: 13mm, 12hr, min/sec stopwatch £14.32 ea  
DVM 176: ICM7106 based LCD 3½digit £22.36 each



## WHAT'S NEW at AMBIT

**NEW PRICELIST/SHORTFORM:-**  
28 pages, FOC with A5 SAE pse

Bigger print than our recent one page list - and vastly extended

If you still need convincing to invest £1.60 in the cats, be mean and get this first.

**POWER MOSFET APPLICATIONS HANDBOOK by HITACHI :**

£1.50 each - or free with pairs of HMOS and the PA101B.

Everything you should know about HMOSFET devices theory and applications.

# RST

**VALVE MAIL ORDER CO.**  
**Climax House**  
**159 Fallsbrook Road, London SW16 6ED**

**SPECIAL EXPRESS  
 MAIL ORDER SERVICE**

Ep	Ep	Ep	Ep	Ep	Ep	Ep	Ep
AZ31	1-10	EY51	1-75	PY88	0-88	6AN8A	3-45
CL33	2-00	EY86	0-84	PY500A	1-80	6AQ5	0-96
DY86/7	0-84	EY88	1-75	PY800	0-84	6AR5	1-98
DY802	0-84	EY500A	1-84	PY801	0-84	6AS6	4-98
E88CC	3-36	EZ80	0-84	QV02-6		6AS7GA	6-75
E180F	8-40	EZ81	0-84		12-56	6AT6	0-85
E810F	14-47	GY501	2-75	QV03-10		6AU5GT	4-32
EABC80	1-20	GZ32	1-25		5-80	6AU6	1-08
EB91	0-82	GZ33	4-00	QV03-20A		6AW6A	3-39
EBF80	0-50	GZ34	2-50		17-50	6B7	1-50
EBF89	0-85	GZ37	4-00	QV06-40A		6B8	1-75
EC91	7-56	KT61	3-50		36-34	6BA6	1-00
ECC33	3-50	KT66	10-00	QV03-12	4-46	6BA7	5-12
ECC35	3-50	KT77	8-00	R18	4-25	6BE6	1-08
ECC81	0-88	KT88	12-00	R19	1-20	6BH6	1-52
ECC82	0-72	N78	9-00	SP41	6-00	6BJ6	1-08
ECC83	0-88	OA2	1-60	SP61	2-00	6BN6	1-65
ECC85	1-20	OB2	2-55	U19	13-75	6BQ7A	3-72
ECC88	1-90	OC3	1-92	U25	1-16	6BR7	4-00
ECC91	8-93	OD3	1-92	U26	1-44	6BR8	1-75
ECF80	1-08	PC86	1-40	U37	9-00	6BS7	4-00
ECH35	2-00	PC88	1-40	UABC80	1-25	6BW6	4-00
ECH42	1-15	PC92	1-28	UBF89	1-20	6BW7	1-52
ECH81	1-20	PC97	1-20	UCH42	1-20	6BZ6	2-37
ECL80	1-00	PC900	1-20	UCH81	2-32	6C4	0-88
ECL82	1-00	PCF80	1-00	UCL82	1-04	6C6	1-75
ECL83	1-50	PCF82	1-00	UCL83	1-44	6CB6A	2-49
ECL86	1-20	PCF86	1-60	UF89	1-44	6CD6GA	5-07
EF37A	3-50	PCF801	1-60	UL41	2-50	6CH6	8-50
EF39	2-75	PCF802	1-90	UL84	1-20	6CL6	3-72
EF41	2-00	PCF805	1-60	UY41	1-25	6CW4	7-68
EF42	2-00	PCF808	1-60	UY85	1-04	6D6	1-75
EF50	1-50	PCH200	1-60	VR105/30		6DQ5	5-94
EF54	5-00	PCL82	1-00		1-92	6EA8	2-94
EF55	2-50	PCL83	2-00	VR150/30		6EH5	1-85
EF80	0-80	PCL84	1-00		1-92	6F6	1-75
EF86	1-52	PCL85	1-08	Z759	16-80	6GK6	2-67
EF91	1-80	PCL86	1-08	Z803U	7-90	6H6	1-50
EF92	5-81	PCL805	1-08	ZD21	3-50	6HS6	3-77
EF183	0-80	PD500	3-60	3B28	16-80	6J5	2-50
EF184	0-84	PFL200	1-80	4CX250B		6J6	3-50
EH90	1-40	PL36	1-20		27-50	6J7	2-50
EL32	1-50	PL81	1-20	5R4G4	2-00	6JB6A	4-56
EL33	3-50	PL82	1-20	5U4G	1-52	6JS6C	5-58
EL34	2-20	PL83	2-22	5V4G	1-52	6K4N	1-25
EL36	1-60	PL84	1-08	5Y3GT	0-85	6K6GT	1-30
EL81	2-50	PL504	1-40	5Z3	1-50	6K7	1-50
EL84	1-00	PL508	1-80	5Z4GT	1-50	6K8	1-75
EL86	2-50	PL509	3-20	6/30L2	1-56	6KD6	6-36
EL91	7-14	PL519	3-20	6AB7	1-50	6L6G	2-50
EL95	1-32	PL802	2-96	6AH6	4-71	6L6GC	2-50
EL360	8-50	PY33	1-10	6AK5	3-60	6L7	2-00
EM81	1-00	PY81	0-84	6AL5	0-82	6LQ6	6-72
EM87	1-50	PY82	0-80	6AM6	1-80	6Q7	2-20
EN91	3-50	PY83	0-70	6AN5	4-74		

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.  
 Valves, Tubes and Transistors - Closed Saturday  
 Terms C.W.O. only - Tel. 01-677 2424-7  
 Quotations for any types not listed S.A.E.  
 Post and Packing 30p per order  
 Prices excluding VAT add 15% Telex 946708

Prices correct  
 when going  
 to press

## J. BIRKETT

25 The Strait, Lincoln. LN2 1JF

**UHF POWER AMPLIFIER MODULE** 50 mW Input, Output 2-5 Watt 420-480 MHz, 13 Volt, 50 ohm Type BGY22C \* £12.50.  
**BLY343 WATT 13VOLT 175 MHZ TRANSISTOR.** \* 75p.  
**HF-VHF POWER TRANSISTOR** Type 587BLY 28 to 70 MHz SSB, FM, 40 WATTS 28 Volt with data \* £3.  
**BLY55 175 MHZ 4 WATT 13 VOLT** with data \* £2.50.  
**BLY97 24 VOLT 175 MHZ 4 WATT** with data \* £3.  
**BFR64470 MHZ 13 VOLT 3 WATT** with data \* £4.  
**SPECIAL SUB-MINIATURE TUBULAR TRIMMER** 0-5pf to 3pf \* 15p.  
**H.P. HOT CARRIER DIODES** 5082-2800 at 40p each.  
**R.F. TRANSISTORS** 2N 918 \* 25p, AF 239, 2N 5179, 2N 5180 \* 50p. ea.  
**EDDYSTONE TRANSMITTING VARIABLE** 30-30pf (60pf) \* £2.20.  
**VHF-UHF STRIPLINE FET** Low Noise 2N 4417 \* £2.20.  
**FERRITE BEADS FX 1115** \* 15p doz, Long Type 3/4" \* 6 for 20p.  
**MINIATURE AIRSPACED TRIMMERS** 10pf at 20p each.  
**SOLDER-IN FEED THRU'S** 6-8pf, 300pf, 1000pf, All 20p doz.  
**MINIATURE VARIABLE CAPACITORS** 250-250pf (500pf) \* 85p.  
**VALVE HOLDERS** 87G, 89G \* 10p ea, Ceramic 89D \* 15p.  
**6 TO 12 VOLT MINIATURE SPCO RELAY** 5 amp Contacts \* 60p.  
**DISC CERAMICS** 22, 33, 270, 330, 0-01uf 50v, All 25p doz, 0-1uf 63v, \* 5p.  
**VHF WIRE ENDED R.F. CHOKES** 10UH, 30UH, 30UH All 7p ea.  
**TLI.C.'s** 7400, 7410, 74L00, 7453, 7430 All at 6 for 50p.  
**BUTTERFLY PRE-SER VARIABLE CAPACITORS** 25x25pf \* 50p, 38x38pf \* 60p, 38x38pf Wide Spaced \* 65p.  
**ELECTRET MICROPHONE INSERTS** with FET PRE-AMPLIFIER \* £1.85.  
**CAR TYPE LONG DOLLY ON-OFF SWITCHES** \* 35p.  
**VHF-UHF FETS** BF 256C 4 for 75p, E304 at 30p, 4 for £1.  
**1 WATT WIRE ENDED ZENERS** 3-6, 5-6, 6-8, 8-2, 9-1, 11, 12, 13, 15, 16, 20, 22, 27, 30, 36, 56, 62, 91, 110, 120, 130, 150, 160, 180, 200 Volt All at 15p each.  
**10 WATT STUD MOUNTING ZENER DIODES** 4, 7, 6-8, 7-5, 8-2, 12, 15, 18, 20, 24, 27, 30, 33, 36, 39, 43, 47, 51, 62, 68, 75, 82, 91, 100, 120, 130, 150, 180, 200 Volt. All at 50p each.  
**50 ASSORTED DISC CERAMICS** for 60p.  
**100 C280 MULLARD CAPACITORS** assorted \* 60p.  
**300 To 75 ohm BALUM TRANSFORMERS** \* 20p.  
**50 BC 107-8-9 TRANSISTORS** assorted untested \* 60p.  
**50 OC 71 TRANSISTORS** untested for 75p.  
**50 SILVER MICA CAPACITORS** assorted for 75p.  
**25 5 AMP STUD MOUNTING S.C.R.'s** untested \* 75p.  
**50 1 AMP S.C.R.'s** To 5 Can untested \* £1.  
**20 10 AMP STUD MOUNTING DIODES** untested \* 60p.  
**NKT 274 or NKT 214 PNP TRANSISTORS** \* 10p, 6 for 50p.  
**10-7 MHZ VERNITRON FM 4 FILTERS** \* 50p, 3 for 50p.  
**10-7 MHZ FILTERS MURATA TYPE SFC 10-7** \* 30p each.  
**200 ASSORTED 1/2, 1-WATT RESISTORS** for 75p.  
**RED CAPERIE MINIATURE DISCS** 0-1uf 100v, w., at 5p each.  
**WIRE WOUND POTENTIOMETERS** 2 Watt 2K, 5K, 10K, 4 watt 100K All 30p each.  
**50 TUBULAR CERAMICS** assorted for 60p.  
**MAINS TRANSFORMERS** 240 Volt input, Type 1, 2, 4 volt Tapped at 14 volt 1 amp \* £1.30 (P&P 25p). Type 2, 32-0-32 500mA \* £1.30 (P&P 25p).  
**DUAL GATE MOS FETS LIKE 40673** \* 33p, 4 for £1.10.  
 Please add 20p for post and packing on UK orders under £2. Overseas orders postage at cost.



## DEACs

VARTA BUTTON  
 (1-2.4V PER CELL)

VAT included  
 P+P 60p per order  
 RECHARGEABLE  
 BATTERIES.

Size/Cell  
 4-8V Pack  
 6-0V Pack  
 9-6V Pack

225mA DKZ  
 25mm dia x 9mm  
 £3-20

600mA DKZ  
 34 1/2mm dia x 10mm  
 £5-55  
 £6-94  
 £11-10

**CYLINDRICAL NICADS** HP7 Size £1-00 only; HP11 Size £2-35; HP2 Size £3-20; PP3 £4-00; PP3 Charger £5-00.

**CONSTANT CURRENT CHARGER** - Switched 9mA/25mA/50mA/120mA/200mA/400mA output - charges 1 to 12 nicads - £13-95.

## V & F SMALLCRAFT (POPLAR) LTD

38, STONELEIGH ROAD, CLAYHALL, ILFORD, ESSEX  
 Tel: 01-550-6642

LIMITED TRADE DISCOUNTS POSSIBLE ON DEACs.

## PROGRESSIVE RADIO

ALL ORDERS DESPATCHED BY RETURN POST

**SEMICONDUCTORS.** 2N5062 (100V 800mA) SCR 18p. BX504 opto isolator 25p. CA3130 95p. TBA800 50p. Tag4443 SCR 45p. Texas R1038 power trans, 50p. TDA1151 25p.  
**SWITCHES.** Min. toggles, SPST 8x5x7mm 42p. DPDT 8x7x7mm 55p. DPDT c/off 12x11x9mm 77p. HEAVY DUTY-DPDT 240VAC 10 Amp 38p. PUSH TYPE, push on 16x6mm 15p, push to break version 17p. 16 pin D.I.L. switch 40p.  
**DISPLAYS.** 4 digit LED clock displays with message center, 0.8" figures, com. cath. with data £3.25p. NSA1198 8 1/2 digit multiplexed displays, com. cath. with data sheet £1.45p. **SPECIAL OFFER** TIL209 Red LED's 10 for 75p.  
**LINEAR I.C.'s.** LM300 40p, LM301 55p, LM308 £1.30, LM324 £1.00, LM388 95p, LM358 50p, LM386 90p, LM3900 80p, LM3909 75p, CA1310 £1.70, CA3018 £1.00, CA3028 £1.30, CA3035 £2.20, CA3046 85p, CA3098 95p, CA3130 95p, CA3140 37p, MC1303 £1.40, MC1312 £1.60, MC1330 £1.40, MC1458 40p, NE550 £1.00, NE544 £1.40, NE565 £1.70, NE566 £1.70, TAA550 40p, TAA621 £2.20, TBA641 £1.30.  
**GPO TELEPHONE DIALS** £1.00 (new). JACKSONS C804 50pf var. capacitors 50p each.  
**TOOLS.** 5 piece precision screwdriver sets, individual handles only £1.05 set.  
**JUMPER TEST LEAD SETS.** 10 pairs of leads with insulated crocs each end 90p.  
**MURATA 40KHZ TRANSUDCERS,** RX/TX £3-50 pair.  
**STC BREAK GLASS FIRE ALARM UNITS,** new with mounting box £1.50p.  
**MINIATURE SOLID STATE BUZZERS.** 33x17x15mm, output at 3 feet 70db., 15ma drain, voltage range 4-15vdc 75p. Loud buzzers (mechanical) 6 volts 55p, 12 volt 65p.  
 Cash with order please, official orders welcome from schools etc., please add 30p postage and packing. VAT inclusive. SAE for latest illustrated stock list.  
**31, CHEAPSIDE, LIVERPOOL L2 2DY**

# You will not be too late

For most of the bargains listed in the newsletter reprinted below, even though it is our June/July issue, because of the part of the newsletter with the items in short supply is not reprinted. However, you will receive the whole or our Aug/Sept newsletter if you send us an order this month and as an extra inducement we will send you our Oct/Nov newsletter directly if it is printed, which is usually about two months before it can appear in this magazine.

## FOUR NEW KITS THIS MONTH

One is an anti-mugging device which you can carry in your pocket or handbag. Secondly we have a morse practice outfit. Thirdly we have a surveillance transmitter which can be made in a matchbox and fourthly a radio mike. The last two are given for interest purposes as at present it is illegal to use this type of equipment but in view of the fact that legislation due to come into Parliament shortly may legalise these or similar transmitters, we are making the kits available. It is of course not illegal to own them.

### MORSE TRAINER KIT

This kit consists of 5 items, morse tone module, morse key, battery connector, case and instructions. Price £2.60 + 35p.

### MUG STOP

With mugging on the increase we think more and more of our customers will want their womenfolk to carry a deterrent, hence this kit. Very easy to make up, only 4 items. Alarm, push on push off switch, battery connector and case. £2.00 + 35p.

### TRANSMITTER SURVEILLANCE

Tiny but easily hidden but which will enable conversations to be picked up with FM radio. Can be made in a matchbox—all electronic parts and circuit £2.00 + 30p.

### RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. All parts, mike and case £6.00 + 90p.

## PHILIPS ELECTRONIC KITS

Despite the fact that these were very fine kits they have been discontinued by Philips Electric. We have purchased the unsold stock and these are available now at very reasonable prices. A double page is devoted to them but in all cases stocks are limited so prompt action on your part is essential.

### WORKSHOP HINT

If you have to work on a mains operated device which has a metal case or chassis then do not connect the earth wire until you have found and repaired the fault. You will save yourself lots of fuses, shocks and damaged tools. Of course a final test should always be with earth connected and in fact with a neon tester to ensure that the earth is properly connected. Note: our mains quick connector is a real time saver, if you do repairs you will find that it will save its cost in no time at all and it's cheap at only £1.95.

### THIS MONTH'S SNIP

is a Bush mains, battery, portable radio offered at a very low price but with full maker's guarantee. Bush Radio Model No. SW5776 is a medium sized radio covering the FM, Medium and Long Wavebands. A portable so of course it is battery operated (four SP11) but with the ever increasing cost of batteries the makers wisely built a power pack into the radio. You will use it from the mains whenever possible thus saving the batteries for when you go camping or picnicking etc. Price £13.25 + £1.99.

### VERSATILE PLIERS

Insulated handles. Long nose, serrated jaws. With side cutter £1.50 + 22p.

### ALWAYS USEFUL CUTTERS

Insulated handles. Ideal for electronics. Approx. 5 1/2" £1.60 + 25p.

### NEON SCREWDRIVERS

Large, 60p + 8p, medium sized 50p + 7p.

## MAINS TRANSFORMERS MORE TYPES THIS MONTH

### 500 WATT TYPE

18v-0-18v at 15 amp or 36v at 15 amp or 18v at 30v. This big transformer has a double wound primary so can be used as 500 watt auto as well. There is also a second secondary 24v tapped at 6v but of course any load you put on this should not be allowed to take the total beyond 500 watt. Upright mounting with fixing lugs, ex-equipment but fully guaranteed £10 + £1.50 each postage £2.00. Note: our stock is approx. 200. 6V-0-6V @ 100 mA. This will be a regular stock line, miniature with feet and flying leads. £1.00 + 15p.

### 12V 1 AMP

Primary and secondary are on separate bobbins with feet and tag connections. £1.80 + 28p.

### POWER MOTORS

Most of our motors come from or were intended for computers, many have had little or no use, most are American makes and all are excellent quality and test before despatch. Most are capacitor run and reversible, prices depend on the actual motor but price for standard models 1/2 h.p. £7.50, 1 h.p. £12.50, 1 1/2 h.p. £17.50 plus 15% VAT and 25% carriage.

**SERVICEMAN'S SNIP—10 POTS IN ONE ONLY 20p**  
Four gang pots 4 x 50k log; miniature types with 1/2 spindle. By combining the sections in series or parallel at least 10 types and values can be substituted i.e. singles—0-12k, 0-18k, 0-25k, 0-50k, 0-100k, 0-150k, 0-200k. Stereos 0-50k & 0-100k. It will definitely be worth you having a few of these in stock. Price 10 for £2.00 + 30p.

**THIS MONTH'S ELECTRICIAN'S SNIP**  
is still the M.E.M. parcel but what a bargain this is you will soon realise at current prices its value is over £60. You get for only £28 + £4.20p white accessories—10 double 13 amp sockets and 5 single 13 Sw sockets with neon, 15 power 60 amp dt switches and 15 power neon lights, 10 single—one way, two way and intermediate switches and super free gift (worth £3). If not collecting please add £2.00.

### FLUORESCENT LANTERN

Hand held or free standing for car, boat, caravan or home use, gives excellent non-directional light, operates from its internal batteries or through its cable from a car cigar socket. Price £5.60 + 84p post £1.

### FLUORESCENT LIGHT

12v inverter with tube holders attached and lead for batteries which can be HP2s or a car battery complete with 12" fluorescent tube £4.60 + 69p post 60p. Plastic holder for 8 HP2s 60p + 9p.

### EXTRACTOR FANS

Mains operated, ex-computer. 5" Woods extractor £5 + 75p post 70p. 6" Woods extractor £6 + 90p post 80p. 6" Plannair extractor £8.50 + 97p post 90p. 4" x 4" Muffin 115v £4.00 + 60p. 230v £5.00 + 75p.

### BLOWERS

Mains operated, mostly new, we still have large stocks prices from £3.00. Note the Torrini Price £4.50 + 75p + £1.00 postage, makes a good desk fan (beat the heat-wave).

### TOGGLE SWITCHES

250v 2 amp chrome toggle—S.P.S.T. 30p + 5p dpdt 45p + 7p.

### SUB MIN TOGGLES

250v 2 amp S.P.S.T. 40p + 8p dpdt 60p + 9p.

## PHILIPS ELECTRONIC KITS

All kits have a properly prepared printed circuit board and this with all the other parts is nicely packaged in printed presentation boxes and are complete with ample data.

### 1000Hz GENERATOR

Gives a pure sine shaped signal and is ideal for Morse Code trainer, balance control in stereo chain, 'whistling' of amplifiers, modulation of signal-generator signals, audible zero-point indication, in bridging-circuits, summoning signals, etc. The size of the load does not affect the operation of the generator. The output is provided with an 'emitter follower'. Complete factory packed kit £2.00 + 30p. Ref. R6630.

### R & C MEASURING BRIDGE

Has built-in standard resistors and capacitors and is capable of measuring resistances valued 10 Ohms to 10M Ohms and capacitances from 10pF to 10uF in a simple but accurate manner. It is also suitable for the comparison of inductances. Complete factory packed kit £3.00 + 45p. Ref. R6516.

**ELECTRONIC TRANSISTOR AND DIODE TESTER**  
All types of transistors can be tested dynamically under operating conditions in an earthed emitter circuit at a collector DC current of 1mA and the small signal gain is determined. The method compares two signals originating from the same oscillator and consequently the measurement is independent of oscillator frequency or voltage and the supply voltage and ambient temperature over the temperature range -5° to +70° C. Diodes can be checked for good or faulty operation. Complete factory packed kit £3.00 + 45p. Ref. R6831.

### ELECTRONIC SWITCH

Is very versatile and suitable for switching, with changing temperatures, light, darkness, humidity, dryness, etc. A signal lamp, an electric buzzer and an electric motor, for example, can be connected directly with the switch. Extension with a holding circuit is possible in a very simple way. A simple time switch also requires only an extra capacitor and push-button. Complete factory packed kit £2.50 + 37p. Ref. H6715.

### ELECTRONIC BUZZER

Generates an alternating voltage which is converted into sound by a loudspeaker. The alternating voltage consists of several frequencies, from the electronic switch. Extension with a buzzer can be used in the same manner, for example, as an electric doorbell and thus be operated by means of a push-button switch. There are many possibilities if the buzzer is combined with an electronic switch type H6715. Switch ON and OFF will be possible by means of temperature, light, darkness, moisture, drought etc. It is also possible to use the electronic switch as a time-switch, so that the buzzer will continue to operate for some time. The buzzer can also be switched directly with light, darkness or temperature. The switching point is not adjustable, but in many applications this will not matter. Complete factory packed kit £2.00 + 30p. Ref. H6714.

**STEREO CARTRIDGE PRE-AMPLIFIER**  
Is designed to use a modern stereo cartridge with an ordinary amplifier. Magneto-dynamic or ceramic or Hi-Fi ceramic are all suitable cartridges. The response from the record will be corrected according to RIAA standards. As the distortion is very low, this pre-amplifier is ideal for Hi-Fi equipment. Complete factory packed kit £3.00 + 45p. Ref. NL3403.

**2 x 40 WATT HI-FI STEREO POWER AMPLIFIER**  
Will supply high power over a broad frequency range at very low distortion. The output stage is a push-pull circuit in such a way that the use of a too low load impedance and short-circuits in the loudspeaker leads cannot cause the amplifier to break down. The four output transistors are mounted on two heat sinks. Complete factory packed kit £10.00 + £1.50p. Ref. NL6920.

**60 WATT HI-FI POWER AMPLIFIER**  
This amplifier is specially designed to perform at high power over a broad frequency range with low distortion. A modern component line-up is incorporated in the circuit configuration, including Darlingtons transistors. A double protection circuit is built-in using five transistors, to guard against accidental over-loading or short-circuiting of the amplifier. With the exception of the two power transistors and an NT resistor, all the other components are mounted on the printed circuit board. The heat sinks should be positioned as close as possible to the p.c.b. For stereo applications two units are, of course, necessary. Complete factory packed kit £8.00 + £1.20p. Ref. NL3606.

**STABILISED POWER SUPPLY UNIT**  
For the 2 x 40 watt stereo-amplifier NL6920 supplies a current of 1A continuous (peak 2.2A) at an output voltage of 60V. The output is protected against short-circuits. Between the primary and secondary windings of the transformer, a screening (extra winding) has been applied which can also serve for the supply of an indicator lamp. Factory packed kit £10.00 + £1.50p. Ref. NL6924 (This will only be supplied if the amp is ordered)

**UNIVERSAL TRANSISTORISED PRE-AMPLIFIER**  
Can be used for many purposes, because the amplification and the input impedance can be adjusted within wide limits and you can select between amplification with RIAA correction (for pick-up elements) and 'straight' amplification (for microphones and other signal sources). Two different supply voltages can be used (9V and 18V) and the output impedance is low. A few examples of applications are: a) pre-amplifier for microphone and/or Hi-Fi pickup elements; b) with power amplifiers which are not designed for that purpose; c) complete Hi-Fi preamplifier in combination with tone control unit R6903 and noise and rumble filter NL6913. d) mixer-preamplifier, with tone-control unit R6903 and noise and rumble filter NL6913. e) baby-phone or intercom installation (with loudspeaker functioning as a microphone). Complete factory packed kit £2.50 + 37p. Ref. R6905.

**PLEASE NOTE:** The "+" sign after the amount shows the amount V.A.T. The postage, if quoted, is based upon the amount the article costs to send if it forms part of a larger parcel. Should your order be less than £10.00 however, please send an additional 50p. BARCLAYCARD & ACCESS WELCOMED. Phone 01-688 1833.

## J. BULL (ELECTRICAL) LTD

34-36 AMERICA LANE,  
NEW ENGLAND ROAD,  
HAYWARDS HEATH,  
SUSSEX.

## PHILIPS ELECTRONIC KITS

### 2 WATT I.C. AMPLIFIER KIT

A small amplifier, with a proportionally large power output, is suitable for many purposes. As an A.F. amplifier in a radio combined with a tuner unit for example, or as an amplifier for a record-player with a crystal ceramic pick-up head. All semi-conductors (transistors and diodes) and most resistors have been incorporated into one single integrated circuit (IC) TCA100C. The other components on the printed circuit board are mainly for the alignment of the I.C. and alignment of the pick-up element, the tuner and the loudspeaker. Complete factory boxed kit £3.00 + 45p.

### 1 WATT IC AMPLIFIER KIT

Similar to NL3402 but smaller output. Complete factory boxed kit £2.00 + 30p. Ref. NL6833.

### NOISE AND RUMBLE FILTER

This Filter Circuit contains two transistors which are used in such a way that the input impedance is high, the output impedance low and the input voltage is equal to the output voltage (amplification 1x). This applies in the 'flat' position for the whole frequency range. In this position there is no amplification or attenuation. If, however, the 'noise' and/or 'rumble' position is selected, the amplification between the adjusted 'noise' and 'rumble' points is still 1x, but the attenuation after the cross-over point(s) will be 12dB per octave. Because of the sharp cut off, the medium range is not affected, making it possible to reproduce well, for example, old gramophone records with a poor high and/or low registration. If the filter R6913 is combined with tone-control unit R6903, it is possible to obtain a gradual amplification or attenuation from 1,000Hz onwards both for 'high' and for 'low' independent of the adjustment of the filter. With this combination it is possible to adjust the most divergent frequency characteristics. Complete factory boxed kit £3.00 + 45p. Ref. R6913.

### TRANSISTORISED TONE CONTROL

Permits adjustment with very wide frequency limits. Complete factory boxed kit £2.50 + 37p. Ref. 6903.

### ELECTRONICALLY CONTROLLED STEREO PRESENCE UNIT

Attenuates or increases the tonal range to which the human ear is most sensitive (optimum speech range). This is achieved by one potentiometer applying a d.c. voltage to one point of an integrated circuit (i.c.) TCA740 both channels being controlled at the same time. The connections between the printed circuit board (p.c.b.) and the potentiometer can be fairly long as only d.c. voltage is used. This gives the constructor freedom in cabinet design of this unit or the complete set by being able to position the potentiometer freely. Complete factory packed kit £3.50 + 52p. Ref. NL3415.

### STEREO PRE-AMPLIFIER KIT WITH ELECTRONICALLY CONTROLLED VOLUME AND BALANCE

This unit can be fed from a tuner, or a record player, with a crystal or 'ordinary' ceramic cartridge having an output level of approximately 100mV. Volume and balance are d.c. voltage controlled. These voltages being connected to a r.c. TCA 750 and then adjusted by single slider potentiometers supplied with the kit. The amplification factor is a maximum of six times the input. The volume control circuit contains a physiology control which can be switched on or off by a push-button linking the i.c. to earth via a resistor. Considerable flexibility in assembly of the unit into a stereo system is achieved because only a d.c. voltage is used for control, thus enabling leads between the p.c.b. and controls to be as long as required. This allows the potentiometers and switches to be placed in the most convenient positions, enabling the system combined with the pick-up amplifier kit NL3403 the tone control kit NL3406 and the stereo presence unit NL3415, all units being electronically controlled. Complete factory packed kit £3.00 + 45p. Ref. NL3405.

### ELECTRONICALLY CONTROLLED STEREO TONE CONTROL UNIT

In this stereo tone control unit the low and high tones are controlled by a d.c. voltage, the d.c. voltage is connected to an integrated circuit TCA 740 to vary the d.c. voltage, slide potentiometers are supplied which are effective on both channels simultaneously. This unit can be combined with the NL3405 preamplifier where volume and balance are controlled electronically and with the NL3415 stereo presence control. Complete factory packed kit £2.50 + 37p. Ref. NL3406.

### PUSH SWITCH

250v 2 amp push to make, release to break, standard size 40p + 6p miniature 25p + 4p. Push to make push to break 30p + 4p.

### TV TURRET TUNER

A two transistor (BF180 & 81) continuous, capacitively tuned U.H.F. tuner, designed to receive television signals. It is operated by four push buttons which are fully adjustable. Millions of these were used mainly in black and white but also in colour. It was very extensively used by set makers and it would probably still be used to-day were it not for the fact that the Varicap tuner is so much easier and cheaper to make. Philips reference for the tuner is U.S. G.C. gave it several numbers: M95928 M (5932) etc. BR called it AT6382/15. We have acquired a large quantity of these and offer them at only a fraction of their original cost. £1.50 + 22p + 50p postage less quantity discounts.

### TV SOUND ONLY RECEIVER

We believe there is a demand for this and think the UHF tuner could be used for this. If any reader has already done work on this please let us know we will pay £100 for a good design. The same applies to any other device which could be made using the TV Turret tuner described above.

### PRECISION MAINS OPERATED CLOCK

For only £1.50 + 22p. Sounds unbelievable but that's what you can have if you send your order right away. The clocks which have large clear dials were made by the famous Smiths Company for use with their domestic cooker switch and are brand new and guaranteed and this batch have the 25 amp switches as well.

### LOW VOLTAGE THERMOSTAT

With remote sensor (joined to approach 36" of capillary. Dial calibrated 10-+20 degrees c, change over contacts so it can be used to switch on or off £3.00 + 45p.

### CAMBRIDGE INSTRUMENTS

This Company as many of you will know is famous for large dial remote operating temperature indicators. We have just received a small batch of these, assorted types covering temps such as 0-200c, 100°-500°F etc., some have 6" dials others have 3" dials. Most have a thermostatic switch incorporated. If you are looking for something like this please let us know. The price will be reasonable.

### LOW VOLTAGE REED RELAY

Normal 40 watt glass reed switch encased in metal tube which also holds the solenoid. 1 1/2 volt or 100mA will operate it. Ex G.P.O. equipment but unused 75p + 12p.

### 34 OHM 8-5A POWER RESISTOR

Slider type variable, made by Burco for machine control but also suitable for lamp dimming etc. ex-equipment but in very good order £4.00 + 60p post £2.00.

# Britain's first computer kit.

## The Sinclair ZX80.

# £79.95

Price breakdown  
 ZX80 and manual: £69.52  
 VAT: £10.43  
 Post and packing FREE

Please note: many kit makers quote VAT-exclusive prices.

You've seen the reviews...you've heard the excitement...now make the kit!

This is the ZX80. 'Personal Computer World' gave it 5 stars for 'excellent value.' Benchmark tests say it's faster than all previous personal computers. And the response from kit enthusiasts has been tremendous.

To help you appreciate its value, the price is shown above with and without VAT. This is so you can compare the ZX80 with competitive kits that don't appear with inclusive prices.

### 'Excellent value' indeed!

For just £79.95 (including VAT and p&p) you get everything you need to build a personal computer at home...PCB, with IC sockets for all ICs; case; leads for direct connection to a cassette recorder and television (black and white or colour); *everything!*

Yet the ZX80 really is a complete, powerful, full-facility computer, matching or surpassing other personal computers at several times the price.

The ZX80 is programmed in BASIC, and you can use it to do quite literally anything from playing chess to managing a business.

The ZX80 is pleasantly straightforward to assemble, using a fine-tipped soldering iron. It immediately proves what a good job you've done; connect it to your TV...link it to an appropriate power source\*...and you're ready to go.

#### Your ZX80 kit contains...

- Printed circuit board, with IC sockets for all ICs.
- Complete components set, including all ICs—all manufactured by selected world-leading suppliers.
- New rugged Sinclair keyboard, touch-sensitive, wipe-clean.
- Ready-moulded case.
- Leads and plugs for connection to domestic TV and cassette recorder. (Programs can be **SAVEd** and **LOADed** on to a portable cassette recorder.)
- FREE course in BASIC programming and user manual.

#### Optional extras

- Mains adaptor of 600 mA at 9 V DC nominal unregulated (available separately—see coupon).
- Additional memory expansion boards allowing up to 16K bytes RAM. (Extra RAM chips also available—see coupon).

\*Use a 600 mA at 9 V DC nominal unregulated mains adaptor. Available from Sinclair if desired (see coupon).

### The unique and valuable components of the Sinclair ZX80.

The Sinclair ZX80 is not just another personal computer. Quite apart from its exceptionally low price, the ZX80 has two uniquely advanced components: the Sinclair BASIC interpreter; and the Sinclair teach-yourself BASIC manual.

The unique Sinclair BASIC interpreter offers remarkable programming advantages:

- **Unique 'one-touch' key word entry: the ZX80 eliminates a great deal of tiresome typing. Key words (RUN, PRINT, LIST, etc.) have their own single-key entry.**
- Unique syntax check. Only lines with correct syntax are accepted into programs. A cursor identifies errors immediately. This prevents entry of long and complicated programs with faults only discovered when you try to run them.
- Excellent string-handling capability—takes up to 26 string variables of any length. All strings can undergo all relational tests (e.g. comparison). The ZX80 also has string input to request a line of text when necessary. Strings do *not* need to be dimensioned.
- Up to 26 single dimension arrays.
- FOR/NEXT loops nested up to 26.
- Variable names of any length.
- BASIC language also handles full Boolean arithmetic, conditional expressions, etc.
- Exceptionally powerful edit facilities, allows modification of existing program lines.
- Randomise function, useful for games and secret codes, as well as more serious applications.
- Timer under program control.
- PEEK and POKE enable entry of machine code instructions. USR causes jump to a user's machine language sub-routine.
- High-resolution graphics with 22 standard graphic symbols.
- All characters printable in reverse under program control.
- Lines of unlimited length.


### Fewer chips, compact design, volume production—more power per pound!

The ZX80 owes its remarkable low price to its remarkable design: the whole system is packed on to fewer, newer, more powerful and advanced LSI chips. A single SUPER ROM, for instance, contains the BASIC interpreter, the character set, operating system, and monitor. And the ZX80's 1K byte RAM is roughly equivalent to 4K bytes in a conventional computer—typically storing 100 lines of BASIC. (Key words occupy only a single byte.)



The display shows 32 characters by 24 lines.

And Benchmark tests show that the ZX80 is faster than all other personal computers.

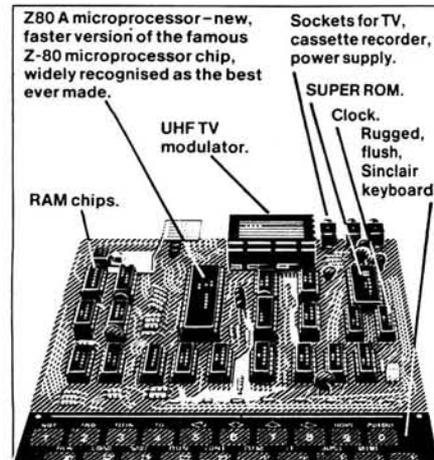No other personal computer offers this unique combination of high capability and low price.



# plete

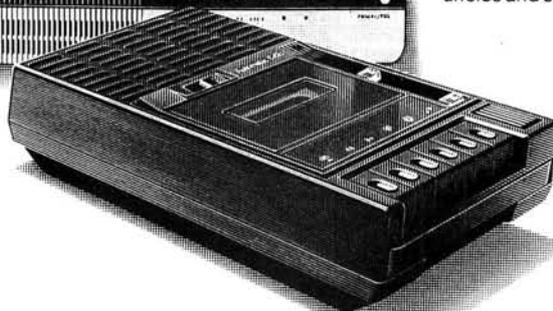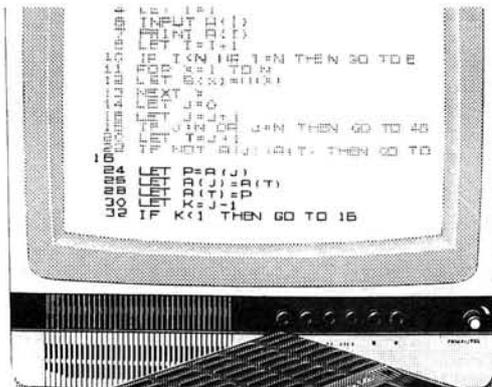

## ZX80 software – now available!

See advertisements in Personal Computer World, Electronics Today International, and other journals.

New dedicated software – developed independently of Science of Cambridge – reflects the enormous interest in the ZX80. More software available soon – from leading consultancies and software houses.

### The Sinclair teach-yourself BASIC manual.

If the specifications of the Sinclair ZX80 mean little to you – don't worry. They're all explained in the specially-written 128-page book *free* with every kit! The book makes learning easy, exciting and enjoyable, and represents a complete course in BASIC programming – from first principles to complex programs. (Available separately – purchase price refunded if you buy a ZX80 later.) A hardware manual is also included with every kit.

### The Sinclair ZX80. Kit: £79.95. Assembled: £99.95. Complete!

The ZX80 kit costs a mere £79.95. Can't wait to have a ZX80 up and running? No problem! It's also available, ready assembled and complete with mains adaptor, for only £99.95.

Demand for the ZX80 is very high: use the coupon to order today for the earliest possible delivery. All orders will be despatched in strict rotation. We'll acknowledge each order by return, and tell you exactly when your ZX80 will be delivered. If you choose not to wait, you can cancel your order immediately, and your money will be refunded at once. Again, of course, you may return your ZX80 as received within 14 days for a full refund. We want you to be satisfied beyond all doubt – and we have no doubt that you will be.

# sinclair ZX80

**Science of Cambridge Ltd**  
6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Tel: 0223 311488.

### ORDER FORM

To: Science of Cambridge Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Remember: all prices shown include VAT, postage and packing. No hidden extras. Please send me:

Quantity	Item	Item price £	Total £
	Sinclair ZX80 Personal Computer kit(s). Price includes ZX80 BASIC manual, excludes mains adaptor.	£79.95	
	Ready-assembled Sinclair ZX80 Personal Computer(s). Price includes ZX80 BASIC manual and mains adaptor	£99.95	
	Mains Adaptor(s) (600 mA at 9 VDC nominal unregulated)	8.95	
	Memory Expansion Board(s) (each one takes up to 3K bytes).	12.00	
	RAM Memory chips – standard 1K bytes capacity	16.00	
	Sinclair ZX80 Manual(s) (manual free with every ZX80 kit or ready-made computer).	5.00	

NB. Your Sinclair ZX80 may qualify as a business expense.

**TOTAL** £

I enclose a cheque/postal order payable to Science of Cambridge Ltd for £ \_\_\_\_\_

Please print

Name: Mr/Mrs/Miss \_\_\_\_\_

Address \_\_\_\_\_

PW 9/80

# NEW CONSTRUCTORS PACK 7

## ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

**\* EASY TO BUILD \* 5 PUSH BUTTON TUNING \* MODERN STYLING DESIGN \* ALL NEW UNUSED COMPONENTS \* 6 WATT OUTPUT \* READY ETCHED & PUNCHED P.C.B. \* INCORPORATES SUPPRESSION CIRCUITS**



The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

**£10.50** p&p £1.75


**CONSTRUCTORS PACK 7A** Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete. **£1.95** Per Pack, p & p £1.00. Pack 7A may only be purchased at the same time as Pack 7. **NOTE:** Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

**A FEATURED PROJECT IN PRACTICAL ELECTRONICS**



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only. 21C HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers. Mon-Sat 9.30am-5.30pm Closed Thursday

**NEW 12+12 AMPLIFIER KIT**

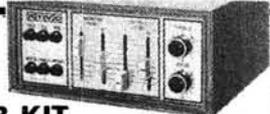

An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free Size 9 1/4" x 8 1/4" x 4" approx. with kit. **£13.95** p&p £2.55

**TWO WAY SPEAKER KIT** To suit above amp. Comprising 2, 8" approx Philips base unit, and 2, 3 1/2" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.65.

Available only to first time purchasers of the 12 + 12 kit.

**Mullard AUDIO MODULES IN BARGAIN PACKS**

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.

**CURRENT CATALOGUE PRICE AT OVER**

**£25 PER PACK SEE OUR PRICES**

**1** PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. **OUR PRICE p&p £5.00**

**2** PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. **illus. OUR PRICE £7.65 p&p £1.15**

**ACCESSORIES** Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus p&p £1.60

**Two Way Speaker Kit** Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. Per stereo pair plus p&p **£4.05**


**£76.00** p&p £4.00

**100 WATT MONO DISCO AMP** Brushed aluminum fascia and rotary controls. Size approx. 14" x 4" x 10 1/4" Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.

**EMI SPEAKER BARGAIN**

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max. 8 ohm impedance. **£18.25** Per stereo pair p&p £4.20

**50 WATT MONO DISCO AMP**

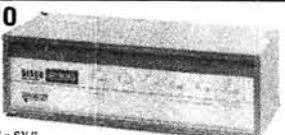

**£30.60** p&p £3.20

Size approx 13 1/2" x 5 1/4" x 6 1/4" 50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with infegral push-pull switches. Independent bass and treble controls and master volume.

**BSR P200** Belt drive chassis turntable unit semi-automatic, cueing device. p&p £3.00

Shure M75 6 Magnetic Cartridge to suit. **£7.95**

**BSR** Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 + 9 m spindle adaptor ideally suited for home or disco use. **OUR PRICE £12.25** p&p £2.75

**NOW AVAILABLE**



**30 + 30 WATT STEREO AMPLIFIER**

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder. DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 3" x 10" approx. **£32.90** p&p £3.30

**RTVC**

323 EDGWARE ROAD, LONDON W2  
21C HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers  
**ALL PRICES INCLUDE VAT AT 15%**  
All items subject to availability. Price correct at and subject to change without notice.  
All enquiries Stamped Addressed Envelope.  
**NOTE:** Persons under 16 years not served without parent's authorisation.


**PHILLIPS RECORD PLAYER DECK GC037**

HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete. UNBEATABLE OFFER AT BUYER COLLECT ONLY.

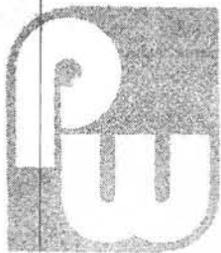**BARGAIN OFFER**

Ariston pick-up arm manufactured in Japan. Complete with headshell. **OUR PRICE £11.95** p&p £2.50

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers. GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY



# Making Haste Slowly

**EDITOR**  
Geoffrey C. Arnold G3GSR

**ASSISTANT EDITOR**  
Dick Ganderton  
C.Eng., MIERE, G8VFN

**ART EDITOR**  
Peter Metalli

**NEWS & PRODUCTION EDITOR**  
Alan Martin

**TECHNICAL ARTIST**  
Rob Mackie

**ASSISTANT ART EDITOR**  
Keith Woodruff

**SECRETARIAL**  
Sylvia Barrett  
Sharron Breeze

**EDITORIAL OFFICES**  
Westover House,  
West Quay Road,  
POOLE, Dorset BH15 1JG  
Telephone: Poole 71191

**ADVERTISEMENT MANAGER**  
Telephone: 01-261 6636  
Dennis Brough

**SECRETARY**  
Telephone: 01-261 6636  
Claire Gerrish

**AD. SALES EXECUTIVE**  
Telephone: 01-261 6807  
Roger Hall G8TNT (Sam)

**CLASSIFIED ADVERTISEMENTS**  
Telephone: 01-261 5762  
Colin R. Brown

**MAKE UP & COPY DEPARTMENT**  
Telephone: 01-261 6570  
Dave Kerindi

**ADVERTISEMENT OFFICES**  
King's Reach Tower, Stamford St.,  
London, SE1 9LS  
TELEX: 915748 MAGDIV-G

**A**S I write this leader, we are awaiting expectantly the publication of the Government discussion paper on the introduction in the UK of a Citizens' Band, or Open Channel as they plan to call it. Anyone who has carefully analysed the statement made on the subject in Parliament in May, will have realised that, apart from the announcement of the name and the discussion paper "to appear within a few weeks", this statement was merely a cunningly re-worded version of that given last November. I wonder just how long we are going to have to wait for some more positive action.

I get the impression, from snippets heard and read in various places, that the authorities are having much greater success than is realised, against the illegal users of 27MHz CB sets in the UK. Even so, it seems impossible that such use can be contained, when national economic pressures prevent the Home Office from deploying more effort towards tracking down the pirates. Every day that a decision on the format of the service to be introduced is delayed, makes it more certain that we shall eventually finish up with two services, one legal and one illegal, running in parallel.

A favourite suggestion for a suitable frequency for CB in the UK is some part of the present v.h.f. TV Bands I and III. It was announced in May that the close-down of the existing 405-line stations would begin in the Autumn of 1982, and be completed within "about four years". Unless it is arranged that one TV channel is completely vacated in one of the early batches (and this is not the case in the list for 1982), we would have to wait until 1987 at least for CB in these bands. And that's too long.

To those radio enthusiasts, licensed amateurs among them, who are against CB or are just not interested, and who wish that we, and everyone else would stop talking about it, I would point out that we are all having to live with the effects of illegal operation now. Certainly any amateur who operates mobile should know that he is liable to be stopped and questioned very closely about any "unusual" aerials and radio equipment fitted to his car. Policemen who may stop you initially under the "Prevention of Terrorism Act" cannot be expected to recognise the difference between illegal CB gear and legal PMR, radiotelephone or amateur sets, and could well delay your journey while they check it out. The present Amateur Licence does not have a very official air about it, being entirely a duplicated document, apart from the holder's name, callsign and address and dates of first issue and renewal on page 1. The Home Office have plans to introduce a new Amateur Licence format when all their records are computerised in a few years' time, and in the meantime, the RSGB (with the approval of the authorities) has instituted its identity card system for members, in an effort to produce a document more secure and more easily recognised by Police and other officials. It should be remembered, however, that no matter how recognisable and authoritative the licence document, it is no proof that you do not have illegal CB equipment in your car, and we understand that two licensed amateurs have recently been prosecuted for doing just that.

One thing that puzzles me is what is behind the decision to adopt the name Open Channel in the UK, instead of Citizens' Band, as used in just about every other English-speaking country, regardless of the official title there—Open Channel doesn't have the sound of an official title. Is it because the authorities want to set it apart by name from other systems? Is there anything sinister in the use of the word "Channel" instead of "Band"—they're surely not thinking of confining it to one channel? Perhaps the problem of confusion of abbreviations has something to do with it. Some-one connecting his new mobile transceiver to the electrical terminal marked "CB" in his car should get some interesting results! But Open Channel as "OC" could be even more confusing, as it means not only "open circuit", but also "ondes cortés" (short waves) in Spanish, which used to be, and maybe still is, marked on quite a few radio set dials.

\* \* \* \* \*

I wonder if one of our readers, somewhere, has a complete list of the phonetic spelling table used for telephone communications during the 1914-18 war. In researching an article on the subject, I have been unable to find a list earlier than 1924, by which time there had been several changes, for example, "Toc" had become "Tommy". Any assistance will be gratefully acknowledged.

*Geoff Arnold*

## RAE Courses

Classes to prepare students for the City and Guilds Radio Amateurs Examination, Course No. 765-02 are offered at the following locations:

*Mid-Warwickshire College of Further Education, Department of Engineering, Warwick New Road, Leamington Spa CV32 5JE. Tel: (0926) 311711.* Enrolment; 4 and 5 September, between 09.00 and 12.00hrs, 14.00 and 16.00hrs, and 18.30 and 20.00hrs. Commencing Thursday, 18 September, for approximately 30 weeks.

*Bracknell College, Church Road, Bracknell RG12 1DJ. Tel: (0344) 20411.* Enrolment; 11, 12 and 15 September. Commencing 29 September.

*Bournville Institute, Selly Park Centre, Pershore Road, Selly Park, Birmingham B29 7PL.* To be held on Thursday evenings between 19.15 and 21.00hrs. Enrolment as for other Adult Education Centres in Birmingham and will also be announced in the local press.

*North Wirral College of Technology, Borough Road, Birkenhead.* Enrolment; between 8 and 10 September. Commencing during the week beginning 15 September. Senior Lecturer; D. E. Owen G4GGB.

*College of Technology, College Square East, Belfast BT1 6DJ. Tel: 27244.* Enrolment; early September. Commencing Tuesday, 16 September, between 17.30 and 20.30hrs. A further class for Morse code instruction and practice for those intending to obtain a class A licence will be held on Thursdays between 18.00 and 20.00hrs. Lecturer; J. E. Wilson.

*Brooklands Technical College, Heath Road, Weybridge KT13 8TT. Tel: (0932) 53300.* Enrolment; 8, 9 and 10 September between 18.00 and 20.00hrs. Classes will be held on Wednesdays between 18.30 and 20.30hrs. Lecturer; Chris Roberts G4EVA.

*Melton Mowbray College of Further Education, Ashfordby Road, Melton Mowbray, Leics.* Enrolment early September. Details from the college or the Course Tutor G3WKM, Tel: Melton Mowbray (0664) 68810.

*Newport Amateur Radio Society, Brynglas House, Brynglas Hill, Newport.* Commencing: Monday, 8 September at 18.50hrs. Lecturers: GW4YTJ, GW4HYZ, GW3NWS and T. J. Wynn.

*Duston Upper School, Duston, Northampton.* Enrolment: 3, 4 and 8, 9 September. Commencing: Tuesday, 23 September between 19.00 and 21.00hrs. Lecturer: D. F. Watton G4AYZ. Fee for 30 lectures £15. Further information: Tel: Northampton (0604) 33834.

*Pendlebury High School, Cromwell Road, Swinton, Manchester.* Registration prior to first class. Commencing late September on Thursdays at 19.30hrs. Details from course instructor: P. Whatmough G4HYE. Tel: 061 794 3706.

*Gosforth Adult Association, Gosforth Secondary School, Gosforth, Newcastle upon Tyne.* Commencing: September on Tuesdays between 19.00 and 21.00hrs. Lecturer: D. R. Loveday G3FPE. Further details from: The Principal, Gosforth Adult Association. Tel: (0632) 668439.

*The Great Barr Institute, Church Lane, Birmingham B20 2HH.* Two courses are available, the first, a revision class for candidates required to re-take Part 2 only will be held on Wednesday evenings from September until December. The second course for beginners will be held on Tuesday evenings. Further details are available from the course lecturer: F. G. Fear G8CVR. Tel: Aldridge (0922) 52706.

## RAE Reprint

A reprint of the complete *PW* series—So You Want to Pass the RAE?—including details of the new examination format introduced in 1979, is now available.

Please note that the prices for the RSGB publications mentioned in the reprint have recently been changed. You should check with the RSGB for the latest information.

Order your copy by completing and returning the coupon on page 69.

## RCI Meets the Listener

Ian McFarland, host of Radio Canada International's weekly programme for short-wave listeners "DX Digest" recently visited Britain to meet some of the UK audience. A total of three meetings were held in London, Newark and Durham, and well over one hundred listeners travelled to the venues to find out more about Radio Canada and

short-wave broadcasting in general. Each meeting took the form of a slide presentation of some of the studios and transmitters used by the station, a film covering various aspects of life in Canada, a general discussion on various aspects of programmes and the technical side of SW Broadcasting. A competition was also held with Canadian records given as attractive prizes.



**Ian McFarland RCI hands a collection of LP's to competition prize winner Michael Burden at one of the RCI Listener meetings.**

Radio Canada International has also been holding phone-ins recently where UK listeners can phone a number in Britain to report on reception and leave a music request. This has proved popular and it has been interesting to note how reception varies on the different frequencies used in different parts of the United Kingdom.

The success of the recent meetings means that a further series are being considered for next year and advance details will appear in *Practical Wireless*. Programme schedules are available from the station by writing to *Radio Canada International, PO Box 6000, Montreal, Quebec, Canada H3C 3A8*.

RCI broadcasts to Europe in English with the following schedule: 1900hrs GMT: 7130, 9555, 15325 and 17875kHz; 2000hrs GMT: 7295, 9555, 15325, 17820 and 17875kHz. Note: The above frequencies are valid until 7 September. After this date: 1900hrs GMT: 5995, 7130, 15325, 17875 and 21695kHz; 2000hrs GMT: 5995, 15325, 17820, 17875 and 21695kHz. The DX programme "DX Digest" is heard in each Sunday broadcast.

### On the Move

Studio 99 Video, the video recording and c.c.t.v. specialists, announce the opening of their new Headquarters at Cricklewood Broadway.

An entire floor of 8000 sq ft will now house this fast expanding company. After twenty-one years of development in Fairfax Road, Swiss Cottage, the company is now able to offer greatly increased levels of professional service in systems design and engineering. Hardware and tape stocks have been substantially improved to meet escalating demand by clients at home and overseas.

Callers will be welcome at the Cricklewood Showrooms and offices at: 249 Cricklewood Broadway, Edgware Road, London NW2 6NX. Tel: 01-450 1313.

### Video disc Information

Thorn EMI Ltd. confirms the announcement made on 5 June, in New York, in which it was stated that discussions are being held by Thorn EMI, Matsushita Electrical Industrial Co. Ltd. (MEI) of Japan, Victor Company of Japan (JVC) and General Electric Company (GE) of USA to form three jointly-owned companies to support the introduction of the Video High Density (VHD) video disc system in the US market by the end of 1981.

The proposed joint ventures will consist of a hardware manufacturing company, a software management company, and a software manufacturing company.

Thorn EMI, MEI, JVC and GE believe that other hardware manufacturers and software companies will adopt the VHD system and that it will be accepted in the market as the best consumer choice.

Thorn EMI Ltd., Thorn House, Upper Saint Martin's Lane, London WC2H 9ED.

### Rallies and Events

The Peterborough Radio and Electronics Society will be holding its annual rally on Sunday, 21 September at Walton School, Mountsteven Avenue, Peterborough. All the usual attractions including talk-in on S22, SU8 and via GB3PB on RB10. Further details from: G8OUU, QTHR. Tel: Stamford, Lincs. (0780) 740456.

Telford Amateur Radio Rally Group hold their rally at Telford New Town Centre Malls, Telford, Shropshire on Sunday, 7 September, commencing 1100hrs. There will be full catering and licensed premises plus talk-in via GB3TRG on S22, SU8 and a free coach service to the famous Iron Gorge Open Air Museum nearby. Further details from: G8DIR (Tel: Shrewsbury 64273), G8UGL (Tel: Telford 584173) or G3UKV (Tel: Telford 55416). All QTHR.

Pembroke and District Amateur Radio Club has decided, after an absence of four years, to reinstate their "Bucket and Spade Party." The event will be held on Sunday, 14 September at The Regency Hall, Saundersfoot, commencing 1100hrs. There will be talk-in on S22, R7 and RB4 plus refreshments and licensed bar. Further details from: GW3XJQ. Tel: Carew (06467) 610.

### The Girl Technician Engineer of the Year

The search is now on to find the Girl Technician Engineer of the Year 1980. Nominations for this electrical and electronic engineering Award, and the accompanying £250 prize, are required by the closing date of 1 October 1980; and the winner will be announced at a ceremony in London during November.

Sponsored by the Caroline Haslett Memorial Trust and the Institution of Electrical and Electronics Technician Engineers, the Girl Technician Engineer of the Year has already established itself as a worthwhile and successful competition and is increasingly well recognised by the electrical and electronics industries.

The aim of the Award—in the realisation that the engineering industry needs to attract more young people of the highest calibre—is to focus attention on electrical and electronic engineering as a worthwhile professional career for women. By selecting the most outstanding Girl Technician Engineer—who will have successfully undertaken the necessary education and training, and have proved herself capable of holding a responsible job—it is the Award sponsors' express hope that she will, by her example encourage more girls to enter the electrical and electronic engineering profession. Naturally it is also to be

hoped that it will enhance the winner's own career prospects.

For further details, and copies of the 1980 Award nomination form, please apply to: Mrs Eileen Sheldon, IEETE, 2 Savoy Hill, London WC2R OBS. Tel: 01-836 3357.

### 23rd Queen's Award

A GEC-Marconi Electronics company has won the group's twenty-third Queen's Award.

This year's winner, Marconi Radar, has very nearly trebled its export sales over the past three years, increasing by 68% during the last year alone. Overseas business now represents some 48% of that company's total sales.


With the exception of 1974, the group has won at least one Queen's Award every year since the scheme's inception in 1966.

### Out of Thin Air

In response to the enormous interest shown in articles on aerials and associated subjects, the staff of *Practical Wireless* have compiled an 80-page book entitled "Out of Thin Air—A Guide to Aerial Theory, Design and Propagation".

The book consists of articles extracted from *PW*, new material and a directory of aerial suppliers.

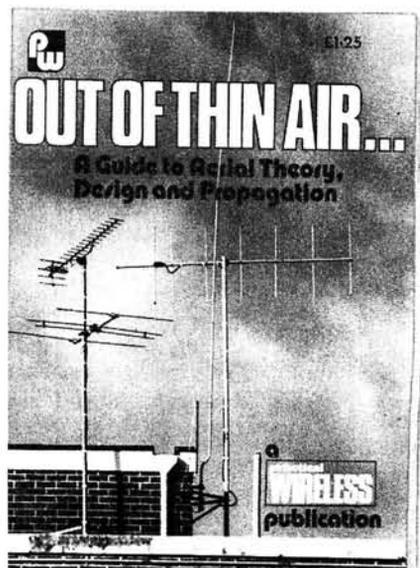"Out of Thin Air" is available from leading newsagents, priced £1.25 or by post. See page 69 for details.



# Pw 'TAMAR'

Part 2

## 28 MHz TRANSVERTER DRIVER

R. S. HEWES FSERT G3TDR

Readers who intend to operate the *PW* Tamar should be in possession of the appropriate licence issued by the Home Office to those who have passed the City and Guilds Radio Amateurs' Examination. Details may be obtained from: The Home Office, Radio Regulatory Department, Amateur Licensing Section, Waterloo Bridge House, Waterloo Road, London SE1 8UA.

In this issue the circuit description is continued, dealing with the transmitter section first, and finishing with the mechanical features.

### Microphone Amplifier

The integrated circuit IC4, a TDA1054, is primarily designed for use as a record/playback amplifier in cassette recorders, with d.r.c. (dynamic range compression) for high average level recording. The i.c. has four sections; a low-noise preamplifier, an operational amplifier with a high open loop gain of approximately 60dB, a linear d.r.c. (a.l.c.) generator and a supply ripple rejection circuit. The d.r.c. facility is used in this transceiver to produce a high average level of s.s.b. talk power.

With S2 set to "Mic", the input is routed to pin 11 of IC4c via SK4, R57, C63, and C64. Ferrite bead FB2 and capacitor C65 provide filtering of any r.f. signals present on the microphone cable. Capacitor C69 initiates the h.f. roll-off at 1.5kHz. Amplified signals at pin 13, across R65, are routed via R63 and C70 to the input of the d.r.c. circuit, pin 15, this circuit forming a feedback loop via S2b back to the input of the operational amplifier. The feedback transforms the output signal level information by means of the d.r.c. circuit peak-to-peak detector into a continuous voltage. Two perfectly matched internal transistors are driven by the detector.

A dynamic resistance is formed by these transistors which varies the d.c. voltage level at pin 16 and is seen at pin 1. This d.c. level is inversely proportional to the op. amp. output signal and symmetrical compression is obtained with minimal introduction of even order harmonic distortion. The system therefore allows wide control range, adjustable recovery times and a good signal-to-noise ratio to be obtained under varying operating conditions, therefore dispensing with the need for a manual microphone gain control.

Under controlled conditions the d.r.c. circuit produces a constant 1V r.m.s. across R65. Typically, the d.r.c. range is 46dB change in input for a 0dB change in output, thus it is not possible to overdrive the balanced modulator. The recovery time is 5 seconds and the s.v.r.f. section (IC4b)

offers a high level of rejection to supply interference with associated components R56, C61 and C62.

### Balanced Modulator

A potential divider formed by R64 and R69 sets the audio level from the microphone amplifier to 300mV maximum at pin 4 of IC5 (an MC1496), via C72. The carrier signal (approximately 60mV r.m.s.), from the c.i.o. running at 8998.5kHz is injected on pin 10 via C73. The resultant output at pins 6 and 12 is a d.s.b. signal with even order harmonic rejection due to the use of a centre tap on T5 primary, carrier rejection of approximately 50dB being optimised by adjustment of VR5. The signal is then routed to CF1 via T6 secondary, C81 and switching diode D9, a 1N4148, CF1 suppressing the lower sideband.

### Operation On CW

The low-noise preamplifier in this circuit (IC4a) functions as an audio phase shift oscillator producing a tone of approximately 1kHz. With S2 switched to "CW" this tone is routed to IC4c via RLD1, the reed relay, S2b disconnecting IC4d from the input to IC4c preventing d.r.c. on the output. When the key is depressed, the reed relay is actuated, the tone then modulates IC5, the level being preset by VR12 to about 300mV r.m.s. thus producing A2 output from IC5. The 1kHz tone is also routed via R53 and VR4 to IC3, preset by VR4 to a suitable level to give sidetone for monitoring the keyed output.


Semi "break-in" is provided for c.w. operation as follows. Switch S2d connects R189 and C171 in parallel with RLA, B and C. When the key is released, the one second time constant provided by R189 and C171 holds these relays in the transmit position for this period of time. After one second has elapsed the relays return the transceiver to receive and "break-in" and keying speeds down to six w.p.m. will hold the transceiver in the transmit condition. Diode D18 prevents "hold-in" on RLD allowing this relay to operate in synchronism with operation of the key.

### The IF Amplifier

The u.s.b. output from CF1 is routed via C85 to the gate of Tr7, a BF256C, which is the transmitter i.f. amplifier. Amplified signals at the drain of Tr7 appear across T7 primary which is tuned by C86.
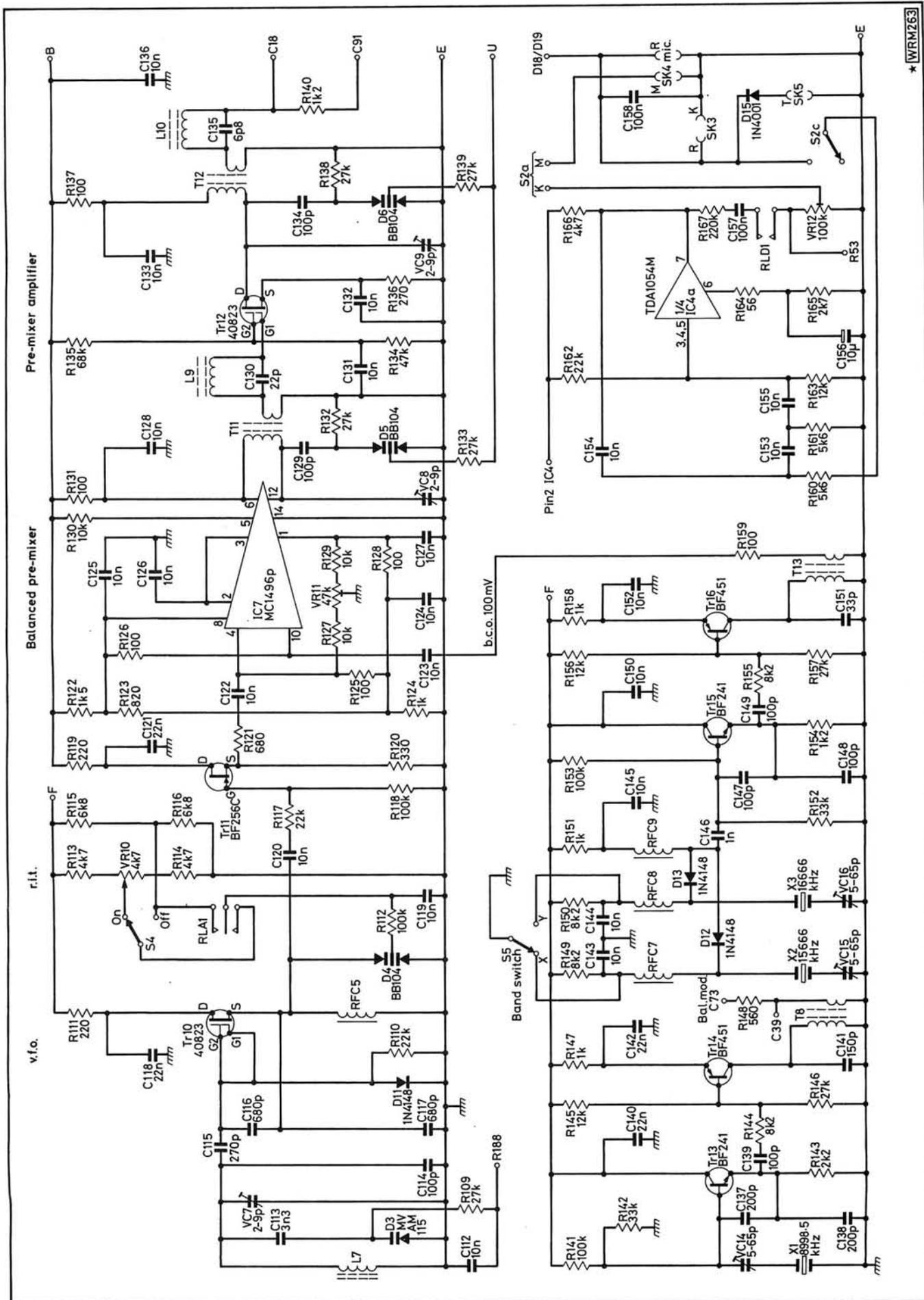
### The Mixer

A low impedance winding on T7 couples the signal to pin 4 of the double balanced mixer IC6, an MC1496, via



★ WRM263

R85 and C90. Local oscillator voltage of about 100mV at 19 to 21MHz from the pre-mixer is injected into pin 10 of IC6 via C91. The added resultant output of 28 to 30MHz at pin 12 appears across T9 primary, the local oscillator rejection at the output being optimised by adjustment of VR6.

## Class A Amplifier

The low impedance secondary on T9 couples the signal via C97 to gate 1 of class A amplifier Tr8, a 40822, and amplified signals at the drain of Tr8 appear across T10 primary. Variable capacitors VC1 and VC2 tune T9 and T10 respectively. This type of miniature capacitor being primarily intended for tuning Band II v.h.f. f.m. receivers, has a 20pF swing and is ideally suited for use in this transceiver for peaking the r.f. output power.

The r.f. drive to the linear class A amplifier is controlled by VR7. This control adjusts the voltage on gate 2 of Tr8 from -2V at minimum setting to +4V at maximum setting with respect to gate 1, varying the amplifier gain over a range of approximately 40dB. Control VR7 thus adjusts the output level on transmit for transverter and 10 metre linear power amplifier input drive requirements, with VR9 pre-setting transverter input levels to 500mW maximum at full setting of VR7.

## Class B Linear

The r.f. drive at T10 secondary is applied via the impedance matching network VC10, C102, VC11 and L5 to the base of class B linear amplifier Tr9, a 2N4427. The requirements for a "stiff" bias supply for linear operation are provided by R103, R104, R105, VR8, C103 and D14 and is applied to Tr9 base via RFC2. Control VR8 presets Tr9 quiescent current to 10mA with D14 clamping the bias voltage to about 0.7V preventing variations in bias level under all drive conditions. Diode D14 is thermally connected to Tr9 heatsink to provide thermal tracking thus minimising changes in quiescent current.

The output network at the collector of Tr9 consists of VC12, VC13 and L6 which transform the output impedance back to 50Ω. The amplified signal is then routed via C108 to S3 which routes the signal to either the transverter drive via FL1a and b to SK2 or 10 metre drive output socket SK1.

## The RF Output Meter

In the transmit mode, M1 is switched via RLB1/2 to monitor the collector current of Tr9 for setting quiescent current and indicating power output, the meter shunt R107 increasing the equivalent f.s.d. of M1 to 200mA, hence a meter calibrated for 200μA may be read by direct interpolation. Maximum p.e.p. from the 2N4427 corresponds to 200mA, the meter itself showing an average reading of 100mA collector current. Transistor Tr9 is not switched, therefore on receive the quiescent current of 10mA is maintained through Tr9 sustaining thermal stability.

## Variable Frequency Oscillator

The v.f.o. employs a MOSFET (Tr10), as the active component in a modified Colpitts oscillator circuit. Because the circuit is designed for maximum stability, the gates are not connected to the top of L7 but via a capacitor, C115; C116 and C117 operating at a feedback level of approx-

imately 35 per cent. The values of the divider capacitors C116 and C117 are made electrically large so that voltage division between gate and source and between source and ground is equal.

Gate resistor and forward diode biasing are utilised with advantage over source biasing for output voltage regulation and frequency stability. The v.f.o. covers 3.333MHz to 4.333MHz, L7 being tuned by D3, an MVAM115 variable capacity diode. An isolation amplifier incorporating a junction f.e.t. (Tr11) in grounded drain configuration, provides a low output impedance and eliminates all possibility of varying loads across R120 affecting the oscillator frequency. Diode D4, RLA1, S4 and associated components provide the "Receiver Incremental Tune" facility (r.i.t.), VR10 being the r.i.t. control on the front panel of the transceiver.

## Band Control Oscillator

The b.c.o. employs a bipolar transistor Tr15, a BF241, as the active component in a modified Colpitts oscillator circuit. Two crystals X2 and X3, 15.666MHz and 16.666MHz respectively, are switched into Tr15 base circuit via diode switches D12 and D13 to cover the 10 metre band in two ranges, 28-29MHz and 29-30MHz. The oscillator output from the emitter of Tr15 is routed to the buffer amplifier Tr16, a BF451, via C149 and R155. The resistor prevents overdriving of Tr16 and the amplified output appears across T13 which is tuned to 16MHz by C151.

## The Pre-mixer

This stage employs an integrated circuit double balanced mixer IC7, an MC1496P. The v.f.o. output, preset by R121, is injected via C122 to pin 4 and the b.c.o. output is routed via R159 and C123 to pin 10.

The injection levels are 20mV and 100mV respectively, r.m.s. The resultant sum output (19 to 21MHz) at pin 12 appears across T11 primary which is tuned by D5. Capacitor C129 limits the frequency coverage and R132 provides a d.c. return path for the top diode in D5. A low impedance secondary on T11 couples the pre-mixer output to gate 1 of MOSFET pre-mixer amplifier Tr12, a 40823.

The amplified output at the drain appears across T12 primary which is tuned by D6. Capacitor C134 and resistor R138 perform similar functions to C129 and R132. A total output level of about 1.5V r.m.s. is available across T12 secondary. This level is applied to gate 2 of the receiver mixer, Tr3. A level of about 100mV r.m.s. preset by the ratio of R140 and R90, is applied via C91 to pin 10 of transmit mixer IC6. Optimum b.c.o. rejection in the pre-mixer output is obtained by adjustment of VR11, with L9/C130 and L10/C135 providing optimum harmonic rejection.

## Carrier Insertion Oscillator

The c.i.o. employs a h.f. transistor Tr13, a BF241, again in a modified Colpitts oscillator circuit. The 8998.5kHz crystal is a parallel mode crystal and is set exactly to this frequency by VC14. The oscillator output from the emitter of Tr13 is routed to the buffer amplifier Tr14, a BF451, via C139 and R144, the resistor preventing overdriving of Tr14 base. The amplified output appears across T8 primary which is tuned to about 9MHz by C141. The total output of approximately 500mV r.m.s. appears across T8 secondary, and is applied to pin 10 of

the product detector IC2. A level of 60mV approximately is set by R148 and applied to pin 10 of the balanced modulator IC5 via C73.

## Transceiver Tuning

Frequency setting of the v.f.o., tracking of the receiver aerial and r.f. circuits for maximum sensitivity, and tracking of the pre-mixer and p.m. amplifier for constant i.o. output is controlled by VR14. This control is a high grade 10 turn potentiometer with a circular calibrated scale fitted to the outer 1:1 driven spindle. Minimum reverse voltage (3V), is controlled by R183. Resistors R184, 185, 186 and 187 in conjunction with S5b set the reverse voltage on D1, 2, 5 and 6 to between 3–6V and 6–10V when S5 is set to 28–29MHz and 29–30MHz respectively, to maintain optimum tracking.

An extremely stable voltage is required for the varicap control line in terms of d.c. variations in p.s.u. output and in temperature changes. This stable voltage is provided by Tr21, Tr22, D27, D28 and associated components, being

initially preset by VR13. The temperature coefficient of varicap diodes is such that an increase in temperature fractionally increases the varicap diode capacitance, i.e., giving a downward v.f.o. frequency shift and vice-versa.

The voltage stabiliser counteracts this effect by fractionally increasing the d.c. control line voltage with increasing temperature, decreasing varicap diode capacitance and hence negating any frequency changes. The full 10V rail supply is used for three oscillators and their amplifiers, i.e., Tr10, 13, 14, 15 and 16.

## The Power Supply Unit

The transceiver will operate from a.c. mains or from 11–14V d.c. e.g., a 12V car battery. The mains p.s.u. consists of T14, bridge rectifier D20 to D23 and C173. The secondary of T14 supplies 20V a.c. to the bridge rectifier, the resultant 100Hz pulses charging C173 to give 24V un-stabilised d.c. off load, with some a.c. ripple at S6b, the inverter on/off switch combined with S6a. When S6 is switched for mobile operation, S6a connects the battery to

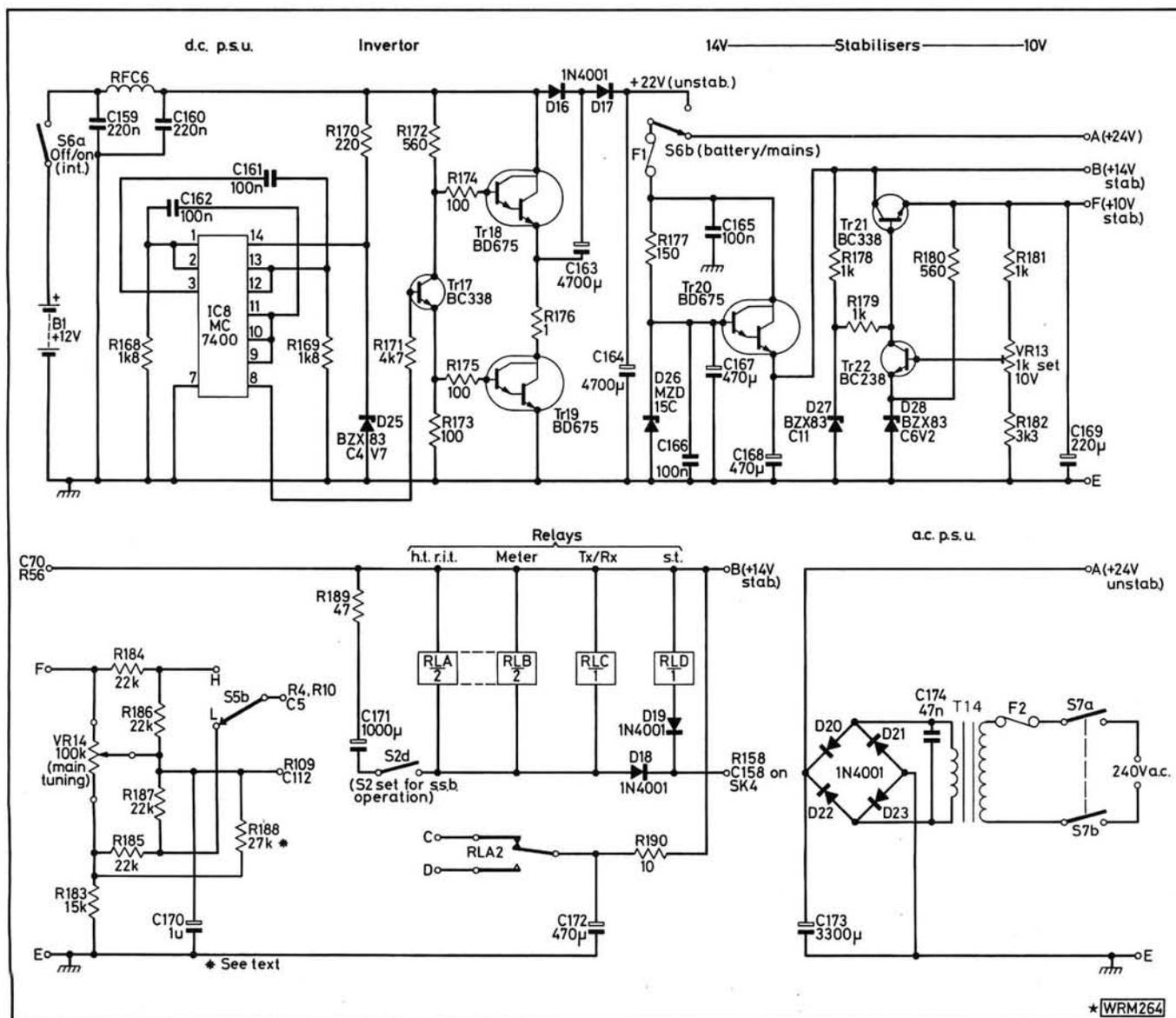


Fig. 5: Power supply, tuning and relay circuits. On the p.c.b. pattern shown in Fig. 7, RLA and RLB have been combined into a single 4-pole changeover relay

## PRINTED CIRCUIT BOARDS

Full-size paper prints of all the "Tamar" p.c.b. track patterns are available from the Editorial offices at Poole. Please, a large (10 x 8in) stamped addressed envelope

the inverter. Device IC8 generates a 7kHz squarewave, the frequency being controlled by C161 and C162.

As IC8, a 7400, is a TTL i.c. it has its 5V supply rail stabilised by D25. The output at pin 8 is applied to phase splitter Tr17 via R171. The 180 degree out-of-phase outputs at Tr17 collector and emitter are applied via R174 and R175 respectively, to Tr18 and Tr19 (BD675) Darlington transistors with a minimum  $h_{FE}$  of 750 at 1A.

The amplified, square waveform at the junction of Tr18 emitter and Tr19 collector is applied to the Cockcroft-Walton voltage doubler consisting of D16 and D17, C163 and C164. The doubler delivers 22-24V d.c. depending on the d.c. input from the battery. Choke RFC6 with C159 and C160 prevent 7kHz pulses on the h.t. line radiating interference from the battery leads. Switch S6b selects either the mains or mobile p.s.u. output which is applied to the 14V regulator consisting of Tr20 (BD675), another Darlington transistor and associated components.

The resultant output across C168 is a fully stabilised and virtually ripple free 14V d.c. with F1 protecting the stabiliser should an h.t. short occur in the transceiver. The stabiliser output is routed to the transceiver circuits, relays and the 10V stabiliser. In the author's transceiver the mains p.s.u. is fitted externally in a separate box but it may, however, be mounted within the transceiver cabinet for "one unit" portability.

## Mechanical Features

Six p.c.b.s carry all the transceiver circuitry including relays and are allocated as follows:

1. Mode switch (s.s.b., c.w., c.w. filter in/out).
2. Mobile p.s.u., 14V stabiliser and the h.t., r.i.t. and meter relay.
3. Linear amplifier, filter FL1 and transmit/receive relay bias network.
4. Transmit mixer and class A amplifier.
5. All receiver circuits, transmitter, balanced modulator and i.f. amplifier.
6. The v.f.o., relay RLD, c.i.o. and amplifier, b.c.o. and amplifier, pre-mixer and amplifier, mic. amplifier and sidetone generator and 10V stabiliser.

Boards 3-6 can be fitted in diecast boxes with lids or alternatively p.c.b.s 2-5 can be bolted to an aluminium sheet with vertical screens between p.c.b.s 3-6.

A further mounting configuration is to set p.c.b. 6 over p.c.b. 5 and p.c.b. 4 over p.c.b. 3 hence saving horizontal area although increasing the height of the transceiver.

Figures 6 to 11 show the component disposition on each of the p.c.b.s and terminal pins are fitted where external connections are made. All interconnecting wiring is carried out with pvc covered instrument wire except for the signal leads, where miniature coaxial cable should be used. The disposition of controls and dial assembly on the cabinet front panel may be varied to suit individual taste but the layout illustrated in the photo gives the best compromise between control positions and their connection points on the p.c.b.s.

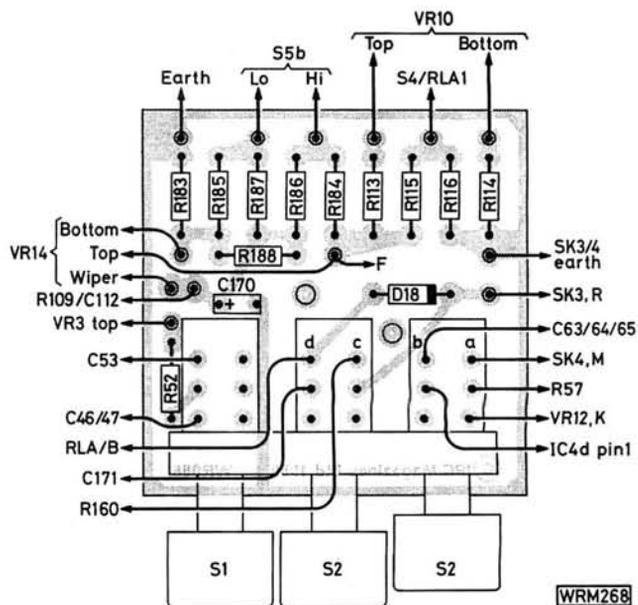


Fig. 6: Mode switch and bandswitch/r.i.t. component layout (Board 1)

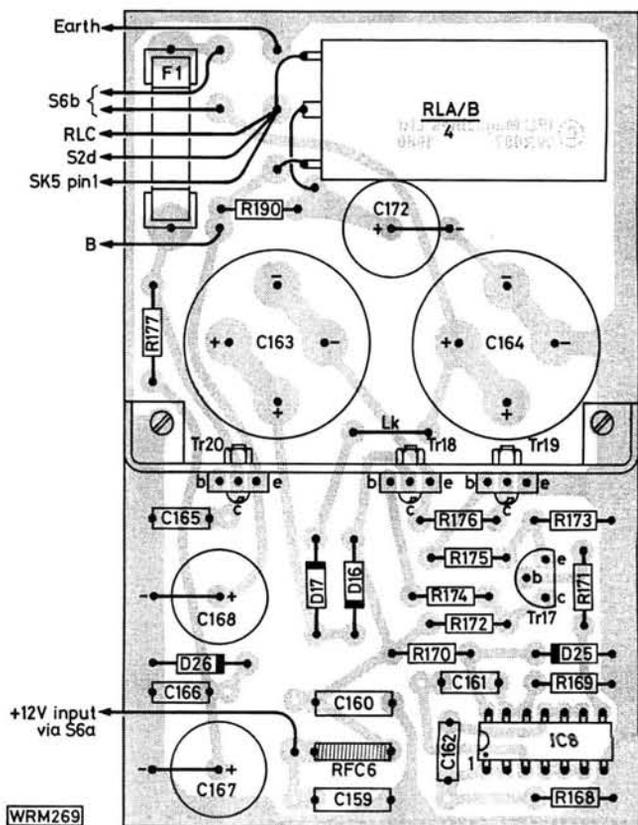


Fig. 7: The d.c./d.c. power supply unit, stabilisers and relay board layout (Board 2)

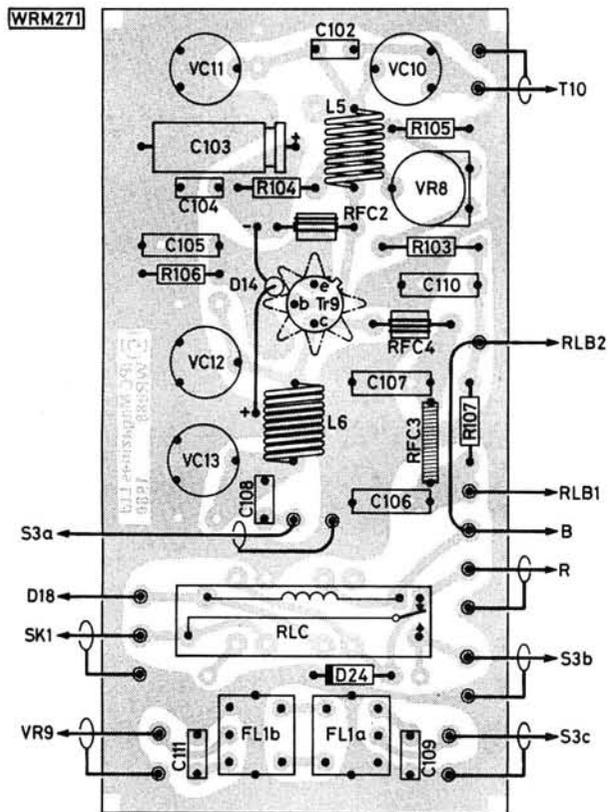


Fig. 8: The linear amplifier, T/R relay and 28MHz filter board layout (Board 3)

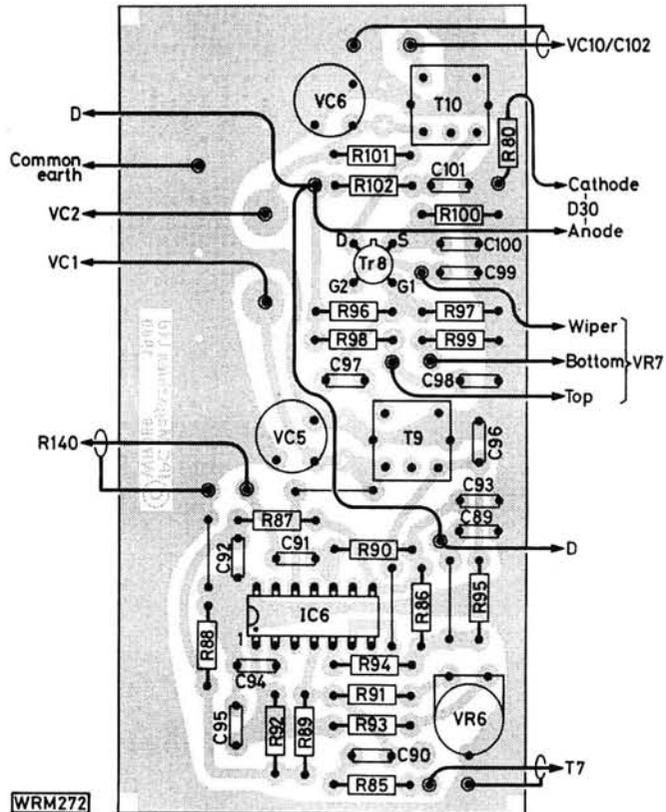


Fig. 9: Transmitter balanced mixer and class A amplifier board layout (Board 4)


Table 1: Winding details of remaining inductors

Coil	Turns	Wire		Notes
		s.w.g.	Type	
L5	4	26	enam	6mm i.d. 12mm long
L6	7	26	enam	6mm i.d. 12mm long
RFC2	4	26	enam	on FX1115 ferrite bead
RFC3	2	26	enam	on FX1115 ferrite tube
RFC4	3	26	enam	on FX1115 ferrite bead

The brackets for mounting the tuning potentiometer and function switch were formed from aluminium sheet and are fixed to the front panel by the nuts and bushes of the r.i.t. and a.f. gain controls and also by the bushes of SK3 and 4 to avoid the use of untidy screws and nuts.
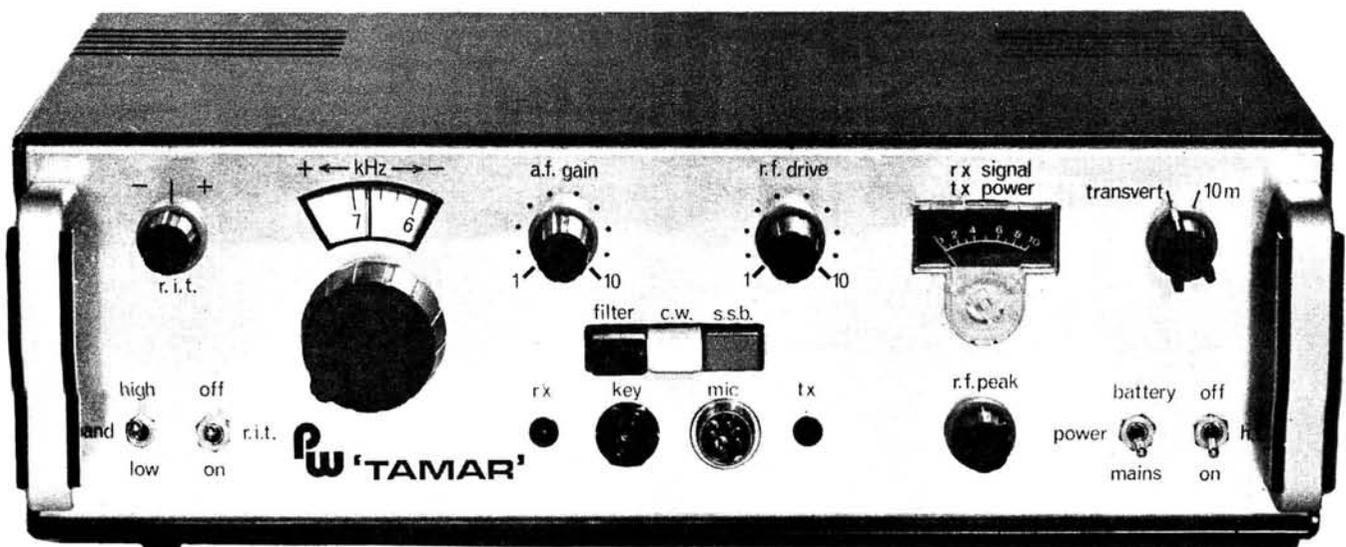
### Next Issue

Component layouts for the two remaining p.c.b.s will be given in the final part of this series next month, together with full alignment details and instructions on driving transverters with the PW "Tamar" transceiver.



# AUDIO POWER AMPLIFIERS

## PART 1

M. J. DARBY

This short series of articles has been written to explain in fairly simple terms how conventional transformerless solid-state audio power amplifiers using bipolar transistors function. Although various circuits will be discussed, it is not intended to describe the detailed construction of any particular amplifier design. However, readers who study these articles should be able to look at most power amplifier circuits and understand the principles of their operation. Calculations have been simplified as far as possible to render the articles more easily readable.

When designing an audio amplifier, it is usually most convenient to start thinking about the type of output stage one requires to give the desired output, and to work back gradually towards the input. This is the basic pattern we shall follow before looking at some complete amplifier circuits.

### Basic Output Circuit

Let us use the simple basic output circuit shown in Fig. 1 to understand how the amplifier controls the power being fed to the loudspeaker. The power transistors shown in Fig. 1 are a complementary pair (an *npn* and a *pnp* transistor), but the somewhat similar circuit of Fig. 2 using two *npn* transistors operates on generally similar principles. The load shown is a loudspeaker; for most purposes it can be treated as a purely resistive load, whilst in some applications it can be replaced by a resistor.

The circuits shown employ two balanced supply lines, one being positive and the other an equal amount negative with respect to 0V. As indicated by the dotted arrows in Figs. 1 and 2, each transistor passes a current in one direction only. This direction is shown by the arrow on the circuit symbol for the transistor concerned. During positive-going parts of the input waveform, a current passes from the positive power supply line through the *npn* transistor of Fig. 1 to the amplifier output and hence through the loudspeaker to 0V; the amplifier output voltage becomes positive at this time so that it can drive the current through the load. The current in the *pnp* transistor at this stage is quite small.

During the negative-going parts of the input waveform a current passes from 0V through the loudspeaker into the *pnp* transistor and hence to the negative power supply line. The amplifier output voltage is negative at this time and the current in the *npn* transistor is quite small.

The use of two output transistors in this basic circuit therefore allows the current to pass through the loudspeaker first in one direction and then in the opposite direction producing an alternating voltage across the loudspeaker. The control signals which must be applied to the transistor bases will be considered later, but it should be noted that it is these signals which control the flow of current from the power supply lines through the loudspeaker.

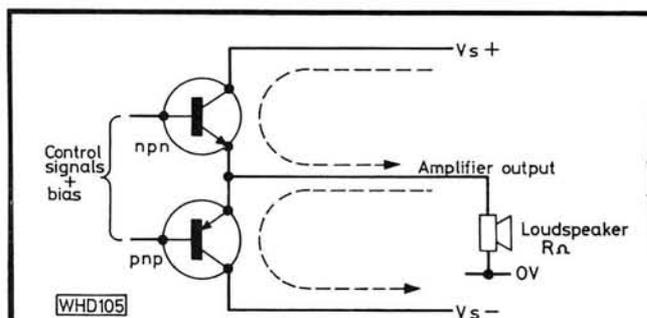


Fig. 1: A complementary transistor output stage showing current flow

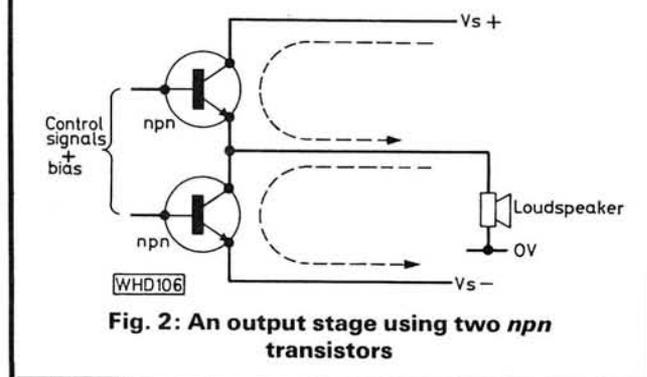


Fig. 2: An output stage using two *npn* transistors

### Maximum Power Output

As the alternating input voltage applied to an amplifier is increased, the output power increases, since more power flows in the load as the amplifier output voltage swing increases. However, there is a fairly sharply defined point at which the distortion commences to rise very rapidly indeed with increasing input voltage; the power output at this point may be regarded as the maximum power output of the amplifier into the load concerned. This output power is very dependent on the power supply line voltages.

What causes this sudden increase in distortion? The maximum positive potential to which the amplifier output can rise is a little less than the positive supply voltage,  $V_s^+$ , because there must be a small voltage drop across each transistor to enable it to operate correctly. If this small voltage is  $v$ , then the maximum positive output voltage of the amplifier is  $(V_s^+ - v)$ , whilst the greatest negative voltage is  $(V_s^- - v)$ ; the maximum positive and negative swings should be almost equal.

If a sinewave of gradually increasing amplitude is applied at the input, initially a similar but amplified sinewave will be present at the output as shown in Fig. 3(b). As the input voltage rises further, however, the peaks of the output voltage waveform will be clipped, as shown


in Fig. 3(c), because the output potential cannot rise or fall beyond a certain value which can be denoted  $V_{o(max)}$ .

Any waveform which shows appreciable clipping on an oscilloscope, even if the clipping is far less than that shown in Fig. 3(c), will be badly distorted if used as an audio signal. Thus it is the onset of waveform clipping which limits the maximum output power obtainable from an audio amplifier feeding a specified load impedance.

The level at which clipping commences is determined by the power supply voltage. If the output transistors are not being operated at their maximum voltage, current and power, more output power can be obtained by increasing the power supply voltage somewhat. However, if an excessive voltage is employed in an attempt to obtain high power, the transistors may be damaged.

Similarly, one cannot reduce the loudspeaker impedance below a certain value with a specified power supply voltage in order to obtain more output power because the output current would then become large enough to damage the transistors. Thus the maximum output power supply is determined by the values of the loudspeaker impedance and the power supply voltage, but these values are in turn limited by the ratings of the particular output transistors employed.

What is the maximum output power developed in a loudspeaker? If the peak output voltage (positive or negative) is  $V_{o(max)}$ , the peak current passing through the loudspeaker will be  $V_{o(max)}/R$  where  $R$  is the speaker

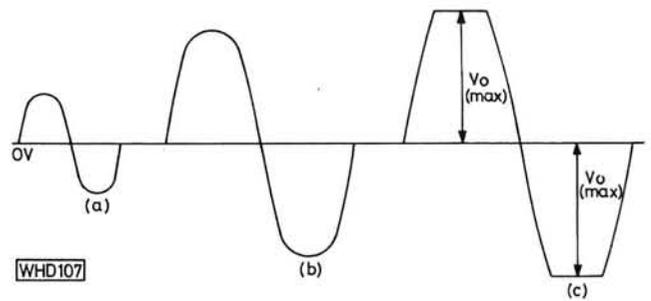

**Fig. 3: (a) Amplifier input waveform (b) normal output and (c) clipped output waveform**

impedance in ohms. The instantaneous maximum power is equal to the product of the peak voltage across the loudspeaker and the peak current passing through it, namely  $V_{o(max)}^2/R$ . As  $V_{o(max)}$  is only a few volts less than the power supply line potential, the output power is approximately proportional to the square of the power supply voltage for any given speaker impedance.

### Mean Power

The instantaneous maximum power output at the peak of the waveform has the value we have just derived of  $V_{o(max)}^2/R$ , but during most of the waveform the power will be much less than this peak value. If the signal is a sine wave, it can be shown that the power averaged over a whole number of cycles is one half of the peak power.

This mean power is often referred to as the r.m.s. output power, because it is the product of the r.m.s. voltage and the r.m.s. current flowing through the load, but this use of the term "r.m.s. power" is actually incorrect. Audio equipment sold in Europe is rated on the maximum mean power output which it can deliver, namely  $(V_{o(max)}/\sqrt{2})^2/R = V_{o(max)}^2/2R$ .

Table 1 gives some general indication of the maximum mean power output levels one may expect to obtain using amplifiers with various values of balanced power supply voltages and various load impedances. It has been assumed that the output voltage,  $V_{o(max)}$  can swing to within 5V of either supply line voltage. Low value current stabilising resistors are often employed in the emitter circuits of the output transistors and the voltage drop across these resistors can reduce the maximum value of the output voltage. Thus the power levels in Table 1 can be taken as being only very approximate values when the actual peak output voltage is not known.

### Single Supply

Balanced power supplies are used in the circuits discussed, but some power amplifiers use only a single supply line. The output stage of a circuit of this type is shown in Fig. 4. The quiescent voltage at the junction of the two emitters is about half the positive supply potential, so a blocking capacitor,  $C$  is required to prevent a steady current from flowing through the speaker; such a current would heat the speaker coil and displace it in the magnet gap. The value of this capacitor must be large enough to ensure that its impedance is lower than that of the loudspeaker at the lowest frequency at which the circuit is likely to be used, otherwise the bass signals will be attenuated.

The circuits in Figs. 1 and 2 have the advantage over the circuit of Fig. 4 that their low frequency response is not limited by any coupling capacitor, so they can operate down to zero frequency if necessary. In addition, the circuit of Fig. 4 has the disadvantage that a high charging

**TABLE 1**

**Typical values of the maximum mean power output from amplifiers using various balanced supply voltages and speaker impedances. In all cases it has been assumed that the peak output voltage is 5V less than the power supply voltage**

Power Supply $\pm V$	Peak Output Voltage $\pm V_o$	Peak Load Current (A)	Peak output power (W)	Maximum mean output power (W)
<b>LOAD IMPEDANCE 16Ω</b>				
55	50	3.125	156	78
45	40	2.5	100	50
35	30	1.875	56	28
25	20	1.25	25	12.5
15	10	0.625	6.2	3.1
<b>LOAD IMPEDANCE 8Ω</b>				
55	50	6.25	312	156
45	40	5.0	200	100
35	30	3.75	112	56
25	20	2.5	50	25
15	10	1.25	12.5	6.2
<b>LOAD IMPEDANCE 4Ω</b>				
55	50	12.5	625	312
45	40	10	400	200
35	30	7.5	225	112
25	20	5	100	50
15	10	2.5	25	12.5
<b>LOAD IMPEDANCE 2Ω</b>				
55	50	25	1250	625
45	40	20	800	400
35	30	15	450	225
25	20	10	200	100
15	10	5	50	25

current flows into the coupling capacitor when the power is first applied and this causes a loud "plop" noise to be emitted from the loudspeaker. This noise can be greatly reduced by using the circuit of Fig. 5 at the expense of circuit complexity. Balanced power supplies are usually used at power levels over about 30W in high-quality amplifiers.

The maximum mean power output from the circuit of Fig. 4 or 5 is somewhat less than  $V_s^2/8R$  where  $R$  is the loudspeaker impedance.

## Transistor Ratings

When the *npn* transistor of Fig. 1 is heavily conducting, the output voltage will rise towards the  $V_s$  level. Thus the voltage across the *pnp* transistor is almost equal to the sum of the two supply voltages,  $2V_s$ , but at this time the *pnp* transistor is taking little current. The transistor must therefore have a collector-emitter voltage rating at zero base current,  $V_{CE0}$  of not less than  $2V_s$ . The *npn* transistor should satisfy this same condition.

The output transistors must also have a maximum continuous current rating,  $I_c$  of not less than the peak output current from the amplifier (Table 1). If the manufacturer's recommended maximum current rating is exceeded, the bonding wire inside the transistor can fuse. This is likely to occur if the amplifier output is shorted to ground.

Power ratings for a transistor are a little more complex, since the quoted power rating is normally the maximum power which may be dissipated in the transistor when the case is at 25°C. As one operates power transistors with their cases at higher temperatures, one must reduce the internal power dissipation so that the device junctions are not damaged by overheating.

The maximum instantaneous power is fed to the load when the output voltage from the amplifier is a maximum. However, the voltage across the conducting output transistor is then quite small, so the internal power dissipation in this transistor is not the maximum value. It can be shown that the maximum internal dissipation occurs in the output transistors with a sinewave input when the peak output voltage is approximately equal to  $2V_s/\pi$ . For a sinewave input the maximum total dissipation in both transistors is approximately  $4/\pi^2$  (or about 40%) of the maximum power which can be delivered to the load using a larger input amplitude.

Thus in a 100W amplifier, the maximum internal dissipation in the output transistors will be about 40W with pure sinewave inputs. However, odd harmonics increase the internal dissipation until one reaches the worst possible case of an internal dissipation of 50% of the rated power output when the input is a squarewave. Even harmonics normally lower the internal dissipation. Loud music can easily dissipate 25% of the rated output power in the output transistors even though the average output power is quite low. There is some variation from one amplifier circuit to another, but generally it is wise to allow an adequate margin of safety by assuming a maximum internal dissipation of some 60 to 70% of the rated power output, since it is not worth risking considerable damage to the amplifier by thermal runaway.

If one considers the MJ802 *npn* transistor and its complement, the *pnp* MJ4502, these have a 90V  $V_{CE0}$  rating and a 30A collector current rating. The maximum dissipation is 200W and the maximum junction temperature 200°C. The thermal resistance from the junction to the case is 0.875°C/W, so if the dissipation is 200W, the case temperature must not exceed  $200 - (200 \times 0.875) = 25^\circ\text{C}$ .

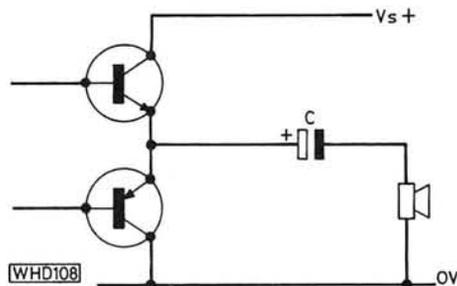


Fig. 4: Output stage fed from a single power supply line

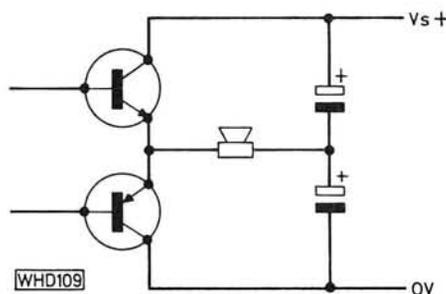


Fig. 5: A method of reducing the switch-on transient

It would be very difficult to maintain the case of the transistor at this temperature without cooling, so one normally uses a higher case temperature and reduces the internal dissipation. For example, a maximum dissipation of 80W will produce a junction-to-case temperature difference of  $80 \times 0.875 = 70^\circ\text{C}$ . The maximum case temperature will then be  $200 - 70 = 130^\circ\text{C}$ . If the maximum ambient temperature is 30°C, the case to ambient thermal resistance will be  $(130 - 30)/80 = 1.25^\circ\text{C/W}$ . Even if the output transistor is mounted directly onto the heat sink, the latter should have a thermal resistance to ambient of no more than 1.1°C/W so as to allow for the contact resistance.

In very high power amplifiers it is difficult to insulate the transistors from the heat sink, since a TO3 mica or polyester washer itself has a thermal resistance of about 0.8°C/W. Hard anodised aluminium washers have a value of about 0.4°C/W and aluminium oxide washers about 0.3°C/W. Beryllium oxide washers are very expensive, but have a thermal resistance of about 0.1°C/W and ideal electrical properties. Note that, in common with all beryllium compounds, beryllium copper is **highly toxic** if ground, drilled or filed.

## Driver Stages

The circuit of Fig. 1 is often fed by driver transistors as shown in Fig. 6. The base current required by each output transistor, Tr2 and Tr4, is quite large—perhaps about 300mA when the output transistor is passing 10A. The current amplifier transistors Tr1 and Tr3 are therefore used before each output transistor, these additional transistors being connected to the output transistors so that two Darlington pairs are formed.

The *npn* and *pnp* Darlington pairs are fed from an amplifier, but the bases of Tr1 and Tr3 cannot be connected directly together and to the output of the

amplifier shown in Fig. 6, since a positive quiescent bias voltage is required at the input to the *pnp* Darlington pair, but a negative bias is required at the input to the *npn* Darlington pair. The load resistor R and the components in the block marked "bias" provide the required bias difference to the two driver transistors.

Each of the four transistors requires a base-emitter voltage of about 0.6V before it commences to conduct, that is,  $V_{BE} = 0.6V$ . The  $V_{BE}$  of Tr1 is effectively added to that of Tr2, so the total voltage between the base of Tr1 and the emitter of Tr2 is  $2V_{BE}$ . Similarly, the base of Tr3 is at a potential of  $-2V_{BE}$  relative to the emitter of Tr4. This means that a bias voltage of about  $4V_{BE}$  will be required to ensure both Darlington pairs are conducting in the quiescent state.

In principle it would be possible to provide a suitable bias voltage by using a resistor between the base of Tr1 and the base of Tr3 in Fig. 6. However, a resistor would not provide the required variation of bias voltage with temperature. This variation is required because it follows from the band-gap theory of semiconductor materials that  $V_{BE}$  varies with temperature. As the transistors in Fig. 6 become hotter,  $V_{BE}$  becomes smaller and a constant bias would result in an increased output transistor current; this would cause the transistors to become hotter still and give rise to the possibility of thermal runaway.

In small amplifiers the bias network may consist of series-connected silicon diodes which are kept at about the same temperature as the power transistors. When the diodes become hot, their forward voltage falls (and hence the bias also) with the same temperature coefficient as the  $V_{BE}$  of the transistors. Thus the collector current of the transistors remains fairly constant with temperature. The only disadvantage with this form of biasing is that the bias cannot be varied with a preset resistor; such variation is desirable so that one can set the quiescent current for minimum distortion.

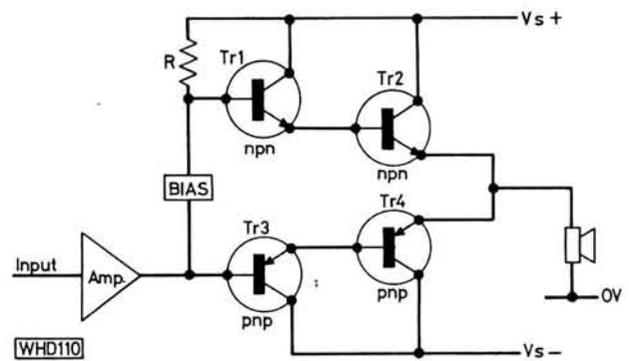


Fig. 6: A basic amplifier circuit


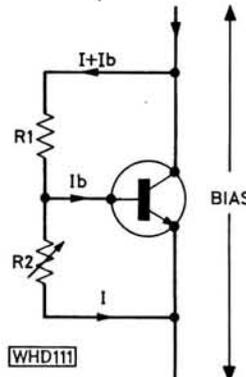


Fig. 7: (left) A  $V_{BE}$  multiplier circuit for providing suitable bias for an amplifier output stage

Fig. 8: (below) A waveform with crossover distortion

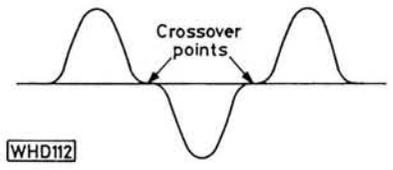

## $V_{BE}$ Multiplier

A better solution is the use of the simple transistor circuit of Fig. 7 as the bias network in Fig. 6. This single transistor circuit is known as a " $V_{BE}$  multiplier", since the  $V_{BE}$  of the transistor is effectively multiplied by a variable factor to provide the bias. The temperature coefficient matches that of the power transistors.

In the circuit of Fig. 7, the bias voltage across the whole circuit is equal to  $(I + I_b)R1 + IR2$ , whilst the  $V_{BE}$  of the transistor is equal to  $IR2$ .

$$\frac{\text{Bias}}{V_{BE}} = \frac{(I + I_b)R1 + IR2}{IR2} = \frac{R1 + R2}{R2}$$

provided that  $I$  is much greater than  $I_b$ . Thus the bias voltage provided by this circuit is approximately equal to  $V_{BE}(R1 + R2)/R2$  and is thus directly proportional to  $V_{BE}$ . Any transistor with a gain of 10 or more is satisfactory for use in the Fig. 7 circuit, the collector emitter voltage being quite small.

If  $R2$  in Fig. 7 is increased, the bias (and hence the power transistor current) will be reduced and vice-versa. It is normally better to make  $R2$  variable rather than  $R1$ , since there is always a chance of a variable resistor becoming open circuit and, if this happened in the  $R1$  position, a huge increase in the bias and therefore in the power transistor current would occur with possible damage.

Optimum temperature stabilisation of the circuit will be obtained only if the multiplier transistor of Fig. 7 is mounted near the power transistor heat sinks so that the temperature of this transistor is kept near to that of the

power transistors. This may not be very convenient, but in some designs it can allow a smaller heat sink to be used with safety. Perfect thermal compensation with the power transistor quiescent current remaining constant with temperature variation will never be obtained, but the Fig. 7 circuit can greatly reduce changes with temperature.

Various minor variations of the Fig. 7 circuit are possible. For example, it is a good idea to replace  $R2$  with a fixed resistor in series with a variable resistor. This will be to prevent the bias from becoming excessive if the value of the variable resistor is set near to zero. A capacitor may be connected across  $R2$ ; its value is effectively multiplied by the transistor gain so that it reduces the impedance of the bias circuit at audio frequencies.

## Crossover Distortion


If the bias voltage is too small, a particularly objectionable form of distortion known as crossover distortion becomes noticeable. It occurs when one of the output Darlington circuits of Fig. 6 does not take over smoothly from the other Darlington as the input voltage passes through the zero point. On an oscilloscope the waveform with crossover distortion appears as in Fig. 8 at low signal amplitudes; at high amplitudes the effect tends to be masked by the height of the peaks.

When setting the bias of an amplifier ( $R2$  of Fig. 7), a low amplitude signal should be applied to the amplifier at a high frequency—perhaps 10kHz. Under these conditions any crossover distortion shows up more clearly. When adjusting the bias, it is almost essential to monitor the power transistor current so as to ensure this does not become excessive at any time.

In Part 2 of this series, we shall be looking at quasi-complementary output stages, input amplifier circuits and power supply requirements.

# LINEAR FREQUENCY METER


J. P. Macauley

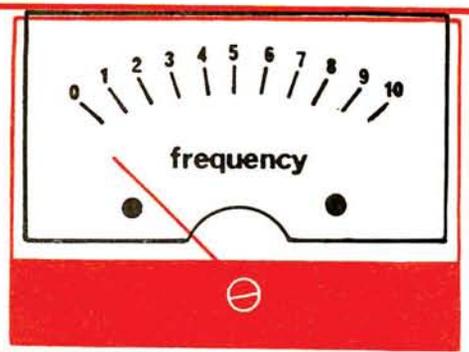

There is no doubt that digital frequency meters have become commonplace nowadays and very much the accepted method of accurate frequency measurement. But, for the home constructor, building a full-blown d.f.m. does have disadvantages and the most significant snag for most people is that old bogey, cost.

A good digital display is not cheap at £40 or so and, considering the amount of use that the instrument will have in the average amateur's workshop, such an outlay can hardly be justified. As an economical alternative, why not consider an analogue design and build *PW*'s Linear Frequency Meter? This design is cheaply and simply made, with its electronics mounted on Veroboard and has a frequency range of 10Hz–100kHz (suitable for a.f. and logic applications, etc.) in four ranges; it is accurate to  $\pm 2\%$ .

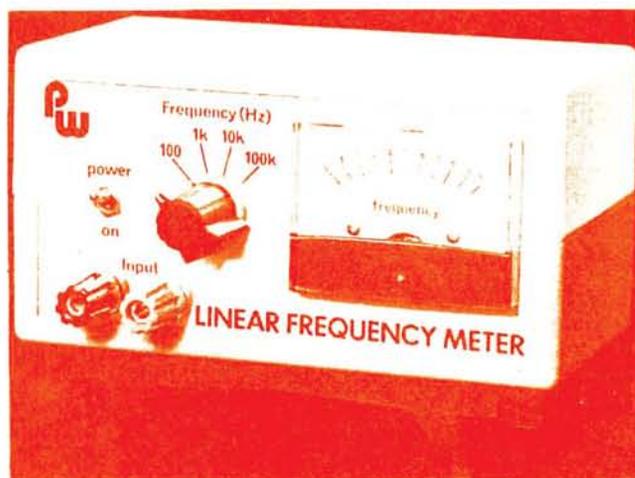The display used is a 1mA f.s.d. panel meter and the instrument is small, portable and, with a current consumption of 14mA, is easily powered by a PP3 battery. So, if you are looking for an inexpensive and unsophisticated means of frequency measurement, this could be your answer.



The amplified output from Tr1 is fed to IC1, a 555 timer used in the Schmitt trigger mode. The output (pin 3) is a squarewave with a respectably fast rise-time which, after differentiation by R7 and C3, is fed to IC2—another 555 connected as a monostable. This input to pin 2 of IC2, is a series of positive and negative-going spikes—the device produces a fixed-width pulse for each positive-going spike, which causes current to flow through the meter. The more fixed-width pulses, the more current and therefore the current through M1 is directly proportional to the input frequency to the instrument. All that is necessary to obtain a direct read-out of frequency is a suitably calibrated scale, such as that shown in Fig. 3 which is designed for the specified panel meter.

Switch S1 selects one of four 2% resistors (R8–R11) and therefore determines the frequency represented by the full scale deflection of M1.

## Circuit

The circuit diagram of the instrument is shown in Fig. 1. The input signal whose frequency is to be measured is applied to the base of Tr1 via R1 and C1. Capacitor C1 blocks any d.c. that may be present in the circuit under test, and R1 serves to limit the base current of Tr1 when relatively high-amplitude inputs are applied. Diode D1 performs a similar function for large negative excursions of the input waveform.

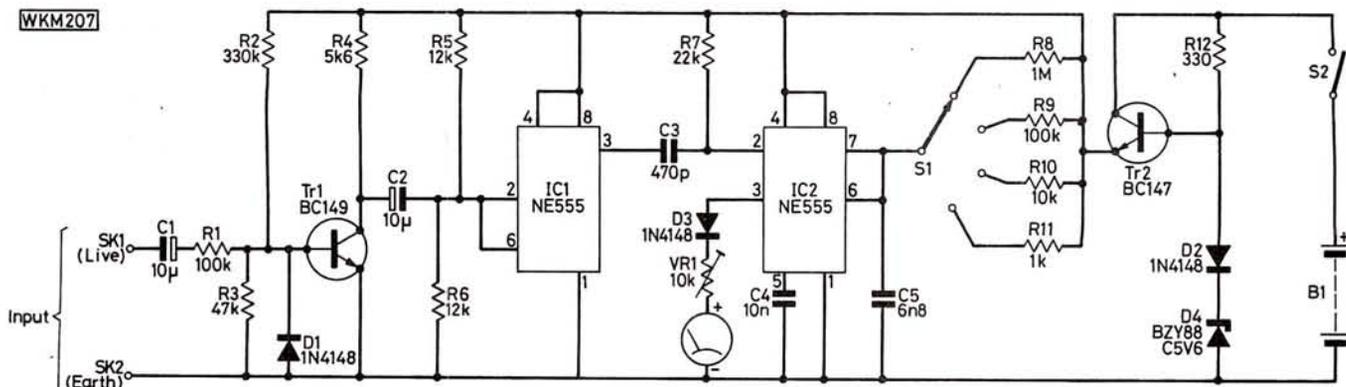


Fig. 1: Circuit diagram of the Linear Frequency Meter

Track breaks at :-

- B5, 21, 32, 40
- C5, 40
- D5, 40
- F32
- I20, 23, 32
- J20, 23, 32
- K20, 23, 32
- L20, 23, 32
- N23
- O23
- P15, 23
- R15, 25
- S7
- U11
- W5, 40
- X5, 40
- Y5, 40

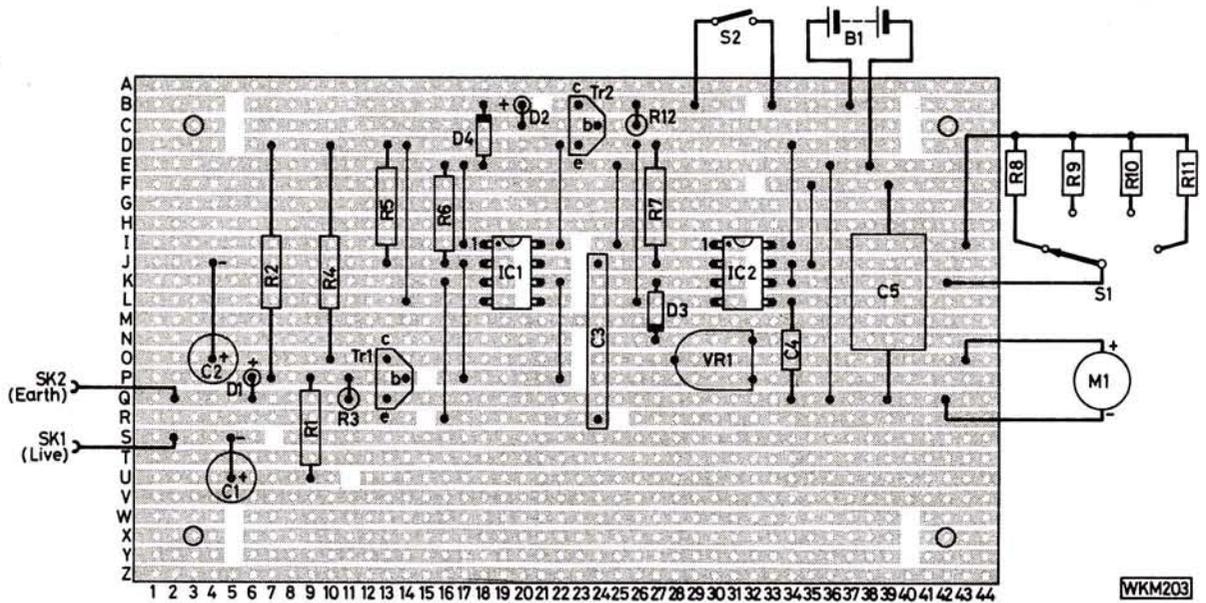


Fig. 2: The suggested Veroboard layout (full size) including track breaks

## Construction

Start by making the breaks in the Veroboard tracks and then carefully solder the components onto the Veroboard panel which should be the same size as that shown in the component layout diagram (Fig. 2). Take care to ensure that the semiconductors and electrolytic capacitors are correctly orientated, and that the wire links are neatly inserted in the correct positions.

The face diagram of the front panel (Fig. 4) may be used as a drilling template—the cut-out and mounting holes are correct for the specified meter (see advertisers' catalogues) so if you decide to use a different type you

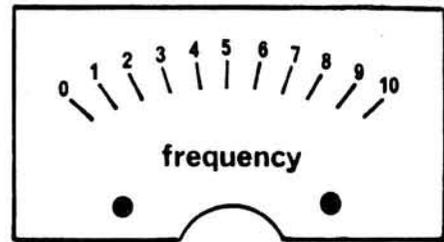


Fig. 3: The scale for the panel meter (full size)

## ★ components

### Resistors

$\frac{1}{2}$ W 5%

330 $\Omega$	1	R12
5.6k $\Omega$	1	R4
12k $\Omega$	2	R5,6
22k $\Omega$	1	R7
47k $\Omega$	1	R3
100k $\Omega$	1	R1
330k $\Omega$	1	R2
1M $\Omega$	1	R8

$\frac{1}{2}$ W 2%

1k $\Omega$	1	R11
10k $\Omega$	1	R10
100k $\Omega$	1	R9

### Potentiometers

Min. open preset, horizontal mounting

10k $\Omega$	1	VR1
--------------	---	-----

### Capacitors

Electrolytic 63V

10 $\mu$ F	2	C1,2
------------	---	------

Polystyrene

470pF	1	C3
6.8nF	1	C5
10nF	1	C4

### Semiconductors

Diodes

1N4148	3	D1,2,3
BZY88C5V6	1	D4

Integrated circuits

555	2	IC1,2
-----	---	-------

Transistors

BC147	1	Tr2
BC149	1	Tr1

### Switches

Midget wafer

3p4w	1	S1
------	---	----

Min. toggle

s.p.d.t.	1	S2
----------	---	----

### Miscellaneous

PP3 battery plus holder and snap-connector; Veroboard Type 75-1239K, or similar case; 0.1in Veroboard (115 x 65mm); 2in panel meter, ME4-T24, 1mA f.s.d.; knob, small, 15mm collet type with wing; tilt-leg assembly (optional); 4mm insulated terminals, red (1) and black (1); equipment wire, fixings, Letraset, etc.

will need to modify the mechanical arrangement accordingly, of course.


The PP3 battery which powers the instrument is best accommodated in a panel-mounting holder as shown in the photograph (Fig. 5)—make a 58 × 24mm cut-out in the rear panel to hold it securely. Incorporating this type of holder avoids having to open the case each time the battery requires changing; once snapped together the recommended type (Verobox Type 75-1239K) can be a bit awkward to reopen.

In constructing the test model, we added the matching tilt-leg assembly which makes the instrument easier to read during bench use and adds a neat and inexpensive touch.


The obvious accurate frequency source for calibration is the mains electricity supply—not a direct connection, of course, but at a very much reduced voltage! In fact, you may find it possible to calibrate the meter by simply plac-

ing a finger on its live input (not to be confused with mains “live”!) and using the a.c. induced in your body to do the job! This will, however, depend very much on your individual physiology and location so you may find it more satisfactory to connect the frequency meter to the secondary of a mains step-down transformer via a suitable divider network. Aim at an input level of 1V peak-to-peak or thereabouts, switch to the 0–100Hz range and adjust VR1 for half-scale deflection; as R8–R11 are 2% types, the other ranges should fall into line.

When it was tested in the *PW* workshop, the instrument returned a sensitivity figure of 100mV r.m.s. up to 20kHz and 1V r.m.s. at 35kHz; it then fell off to 2V r.m.s. at 100kHz. The sensitivity at the higher end of the instrument’s frequency range can be improved by reducing the value of C3, incidentally—but if you do this, you must be prepared to accept less sensitivity at the lower end! ●

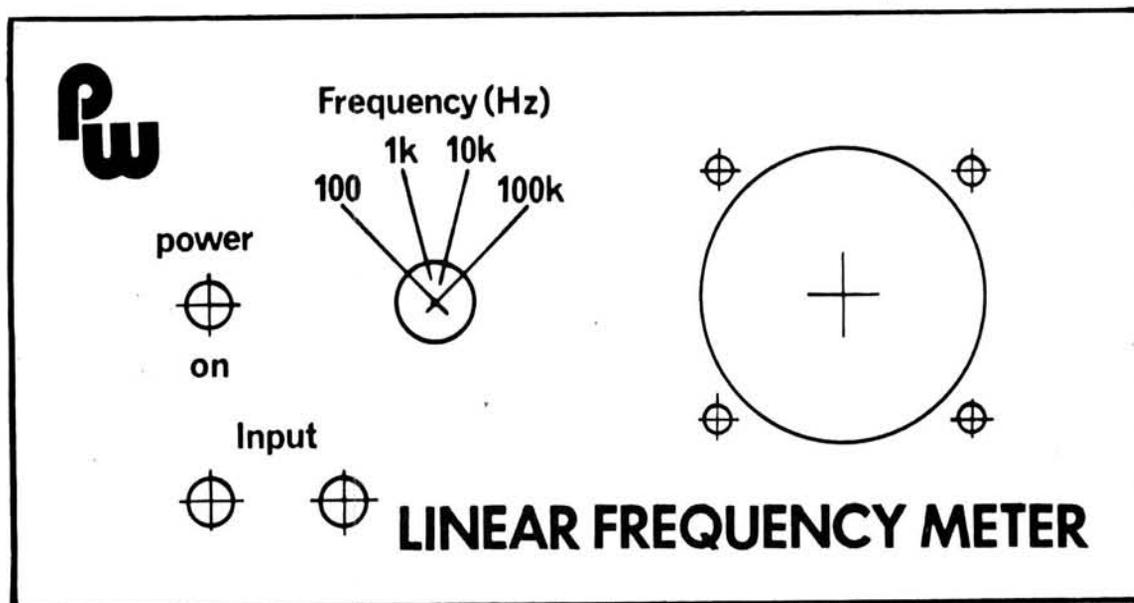


**Fig. 4:** The front panel design (full size). It can be used both as a drilling template and to enhance the appearance of the finished instrument

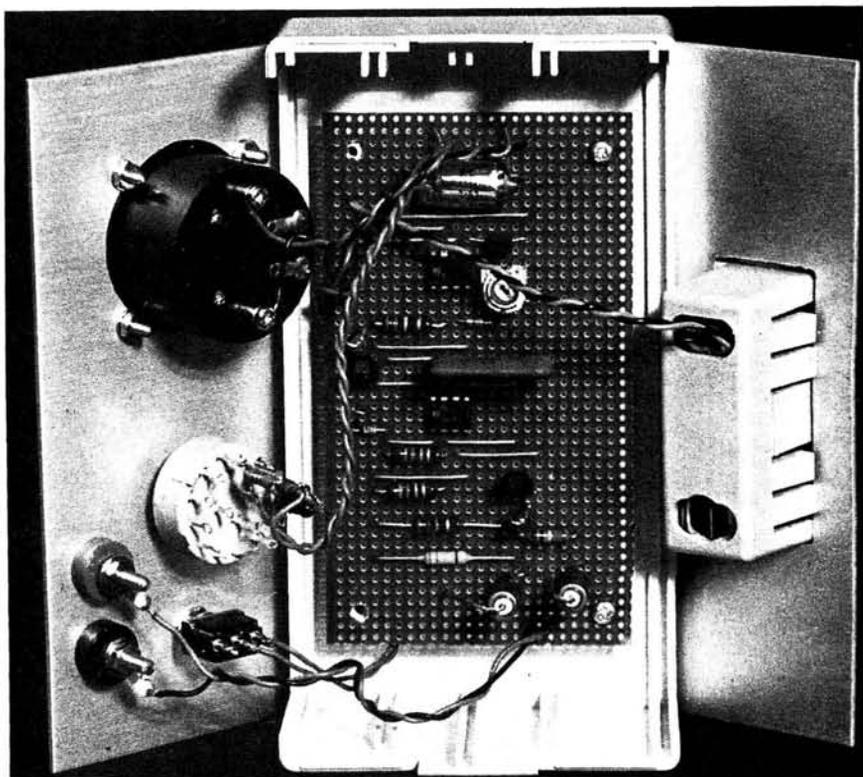

**Fig. 5:** Interior view of the completed unit
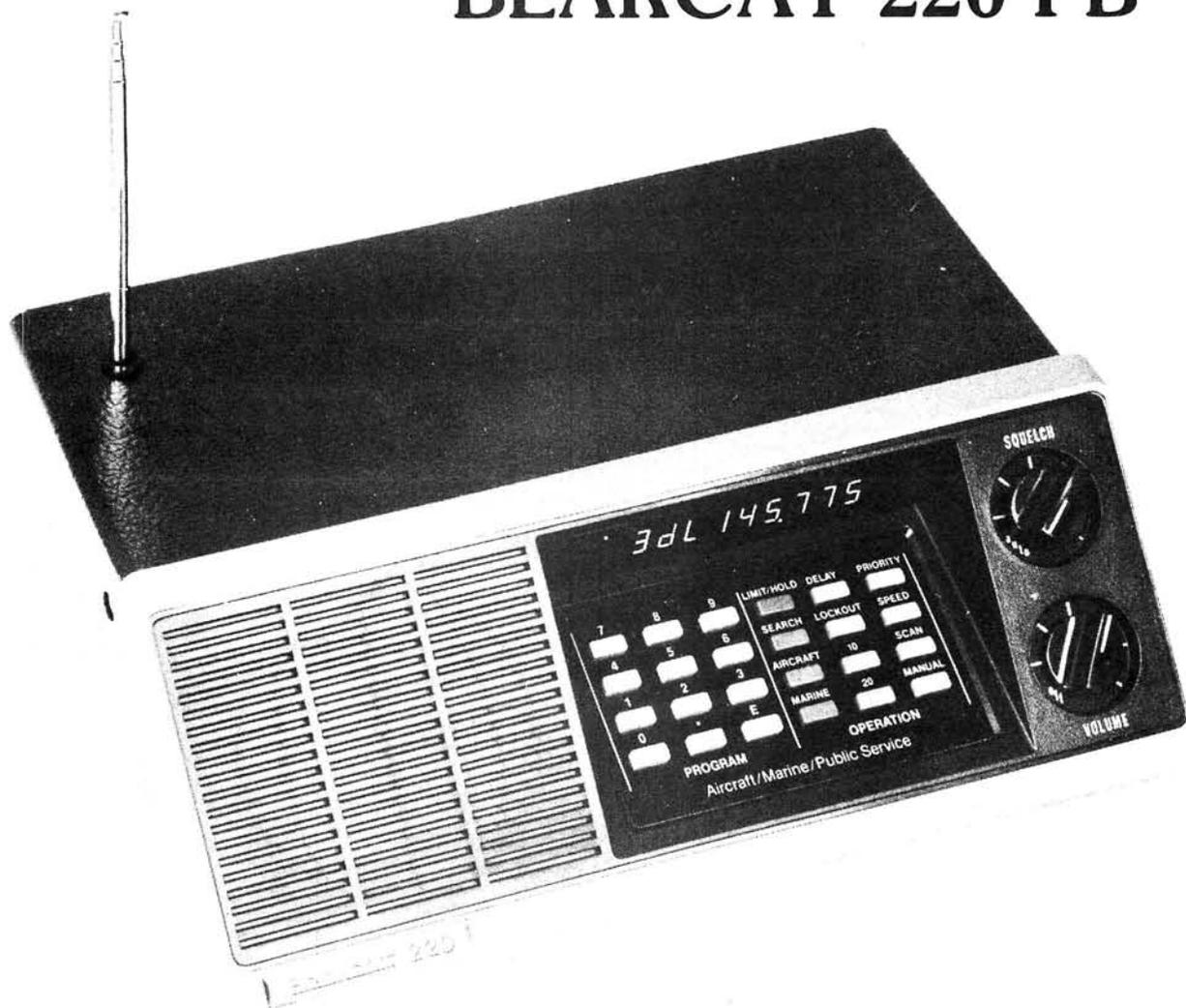
# BEARCAT 220 FB



£258.75 inc. VAT. Delivery by Securicor

*FREQUENCY COVERAGE .....66 - 88 MHz FM; 118 - 136 MHz AM (Aircraft Band); 144 - 174 MHz FM; 420.45 - 512 MHz FM. This coverage includes the 70 cm; 2m; 4m FM AMATEUR BANDS. To programme this Receiver you simply punch in the frequencies you wish to monitor. To AUTOMATICALLY SEARCH MARINE FREQUENCIES YOU JUST PRESS ONE BUTTON. The Bearcat 220 FB will also AUTOMATICALLY SEARCH the AIRCRAFT BAND.*

*Power requirements: 240 VAC/12v DC. Accessories included in the price are - Mounting bracket and hardware, DC cord and telescoping antenna.*

**UK IMPORTERS & DISTRIBUTORS**

Please send 25p stamps for details.

**ACCESS**

★ SALES ★ SERVICE ★

**BARCLAYCARD**



**RADIO SHACK LTD.** 188 BROADHURST GARDENS, LONDON NW6 3AY


Giro Account No. 588 7151 Telephone: 01-624 7174 Cables: Radio Shack, NW6.

Telex: 23718


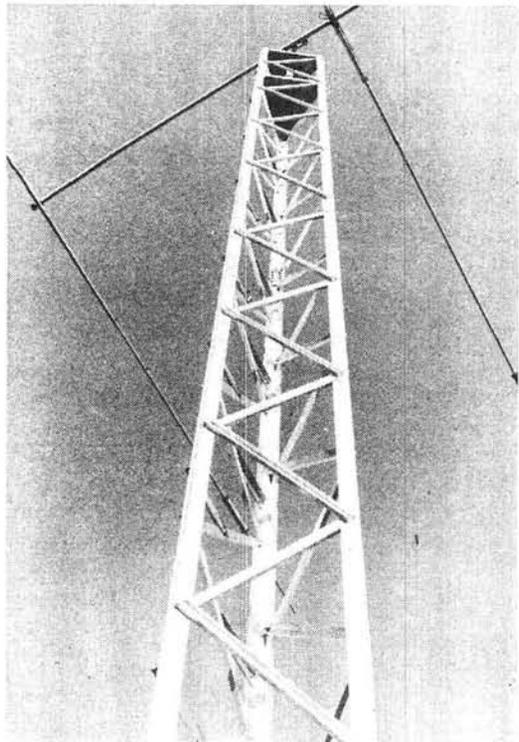
# Western

The UNIQUE **ALUMAST**  
LIGHTWEIGHT ALUMINIUM MAST



- ★ LIGHTWEIGHT
- ★ EASILY ASSEMBLED BY ONE PERSON
- ★ NO SPECIAL TOOLS NEEDED
- ★ SELF-SUPPORTING TO 9m (30ft)
- ★ GUYED MODELS TO 75m (250ft)
- ★ BUILT-IN CLIMBING RUNGS
- ★ CORROSION RESISTANT, HIGH-STRENGTH ALLOY
- ★ SELF-LOCKING NUTS FOR SECURITY

## Western ANTENNAS

A FULL RANGE OF BRITISH MADE ANTENNAS for the AMATEUR HF BANDS

- ★ DX-5V — 5 band Vertical
- ★ DX-31 — 10-15-20m Rotary Dipole
- ★ DX-32/33/34 — 10-15-20m Beams (2, 3, 4 element)
- ★ DX-103/105 — 10m Monobander Beams
- ★ Insulators ★ Dipoles ★ Accessories

FULL DETAILS & PRICES ON REQUEST

### Western Electronics (UK) Ltd

Head Office (All Mail/Enquiries)  
FAIRFIELD ESTATE  
LOUTH, LINCS, LN11 0JH  
Tel: Louth (0507) 604955/6/7

FOR ALL YOUR  
S.W.L. AND AMATEUR  
REQUIREMENTS

## M.R.S.

COMMUNICATIONS LTD.

76, Park Road, Whitchurch,

# CARDIFF

TEL. 616936

OPEN  
9 am to 5 pm  
6 Days



### LOW COST AUDIO SIGNAL GENERATORS

(Sine & Square Waves)  
10Hz-100kHz  
Very low distortion (x0015%)  
£41.40 (or in kit form) £35.65  
p.p. and ins. £2

Model 146

ALSO

Model AO113. Sine/Square. 1 volt  
into 600 Dist .02%. £31.60 (Kit  
version £26.50) p.p. £1.



TELERADIO ELECTRONICS

325 Fore Street, Edmonton, London N9 0PE  
S.A.E. for leaflets . . . Closed all day Thursdays . . . 01-807 3719

## STEPHENS-JAMES LIMITED

COMMUNICATION ENGINEERS

47 WARRINGTON ROAD, LEIGH WN7 3EA

ENGLAND

Telephone (0942) 676790

Everything for the Short Wave Listener.

We stock receivers and listening aids by most of the world's leading manufacturers. Full range of VHF receivers—transceivers. Mobile equipment pre-selectors—filters—antennas. Stabilised power supplies from 2 to 20 Amp. Antenna switches—converters. Aluminium masts—clamps. Antenna rotators.

#### Trio R1000 Receiver

Digital readout general coverage receiver covering 200kHz to 30MHz with a P.L.L. synthesiser. Also incorporating quartz digital clock. £298.00.

#### Trio R820

Amateur Band Receiver £690.00.


Send for full specifications of our full range of receivers covering from 200kHz to 520MHz. Our secondhand equipment changes daily. Send SAE for up to date lists. Part exchange welcome. Good clean Equipment bought for cash.

#### Antenna Multituner MK2

Designed and manufactured by ourselves. Frequency coverage 500kHz to 30MHz. Will match any antenna over 5m in length to practically all receivers. In production for over four years and now used in over 55 countries.
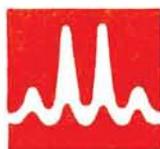
#### Bearcat 220FB Receiver

Scanning Receiver. 66-88MHz-118-136MHz. 144-148MHz-144-148MHz. 420-450MHz-450-470MHz. 470-512MHz £258.75. Send S.A.E. for details of our range Aircraft Band Receivers.



SUGIYAMA

# F850 HF/VHF TRANSCEIVER

The Sugiyama F850 is a most unusual animal among amateur transceivers, covering as it does, all UK bands (pre-WARC '79) from 160—2 metres, and all modes. In fact, within its power limitation, it comes close to being a "universal" amateur station, being really three transceivers in one.

The first impression (having recovered from lifting the set from its packing!) was of a superbly engineered piece of equipment, not flashy, but very professional. This was confirmed by the feel of the controls and switches, even before power was applied, and also by the internal construction, with one minor reservation, but more of that anon.

The need for the review set to be returned for an exhibition appearance meant that we did not have time to carry out the sort of measurements that we normally perform on h.f.-band rigs, and the views here are the result of a couple of weeks of testing on the air.

## Features

Perhaps the best way to give a run-down on the operating features is to describe the function of each control and connector. Starting at the top left-hand corner of the front panel, we find a large illuminated meter, controlled by two push-button switches. This indicates r.f. power output or the compression level of the speech processor when on transmit, and received signal strength or f.m. tuning point (centre zero) on receive. The 5-digit frequency display is bright, and stable in the last digit (100Hz) and indicates true transmit and receive frequencies, including any shifts.

Band switching is by push-button, and is arranged in 500kHz sections. To reduce the number of push-buttons required for band switching, two banks of eight are provided, one covering the eight bands, the other the eight 500kHz-wide sub-bands. In the UK model, only the lower four sub-bands are used, but in export models for Regions 2 and 3, a 4MHz spread is required on the 6-metre (fitted in place of the UK 4-metre band) and 2-metre bands. An invalid selection of bands or sub-bands will cause the frequency display to flash, alerting the operator to his error.

Below the band and sub-band switches, is another bank of 16 buttons. Four of these allow the transmit and receive frequencies to be controlled from the internal v.f.o. or an external source, as desired. A further four buttons select the receive i.f. bandwidth on c.w., a.m. and s.s.b. Only the 2.4kHz filter is fitted as standard, the remainder being optional extras. The bandwidth on f.m. is fixed at 16kHz.

The lowest row of buttons control a 10dB r.f. attenuator, a noise blanker, a 25kHz crystal calibrator and select the mode—c.w., u.s.b., l.s.b., a.m. and f.m.

At the bottom right-hand corner of the front panel are the receiver incremental tune ( $\pm 5$ kHz) and variable b.f.o. ( $\pm 2$ kHz) controls, each with its on/off selector button and warning l.e.d. indicator. When on 2m f.m., these push-buttons instead select repeater shift and automatic 1750Hz toneburst respectively, though there is no indication of this on the front panel markings.

The main tuning control is a heavy flywheel knob, approximately 55mm in diameter, with a finger-dimple for rapid winding, and placed well clear of all other controls. The tuning rate is about 16kHz per revolution. Like all the rotary controls on this set, the operation is silky smooth.

To the left of the main tuning are four knobs: the microphone gain control, setting speech level and compression; the r.f. power control, allowing the output to be varied between 1W and 10W (nominal) on f.m. and c.w.; the squelch control (f.m. only) which is of the "gradual" type, rather than the "step" type, and so is precisely settable, rather than having hysteresis; the receive volume control (a.f. gain). A large push-button switch turns the power on and off, and three smaller ones connect the p.t.t. lines and select "fast" or "slow" VOX time constants. Normally, "fast" would be used for c.w. (the Morse key controls a tone oscillator, which provides sidetone and keys the transmitter via the VOX), and "slow" would be used for speech. Connectors for headphones (4–8 $\Omega$ ), and 600 $\Omega$  microphone with p.t.t. complete the front panel features.

On the rear panel are three sockets, all SO-239 u.h.f. type, for h.f., 4m and 2m aerials, plus connectors for external v.f.o., linear amplifier, p.t.t., key, extension loudspeaker (4–8 $\Omega$ ) and power. Two power leads are provided, one for a.c. mains, the other for 13.5V d.c. M or /P operation, and both fitting the same connector.

## Operating Impressions



Contacts were made on all bands except 70MHz, and all modes, over a period of about two weeks in March this year. No stations were heard on 70MHz, though on an admittedly makeshift aerial. Contacts on c.w. with W/VE-land on 20m, 15m and 10m, all brought reports of around the S4–S6 mark, which can't be bad for a set pushing out a measured 12–14W via a Z-match into a 60ft long wire. Similar results were obtained on 80m and 40m, with European stations.

Phone contacts around the UK brought reports of really excellent speech quality on 80m and Top Band, the latter using a large "T" aerial at a different QTH, as the long wire refuses to tune at those frequencies.



Front panel view of the F850 showing the various controls and indicators. The frequency is displayed as a digital readout with an analogue S meter to its left

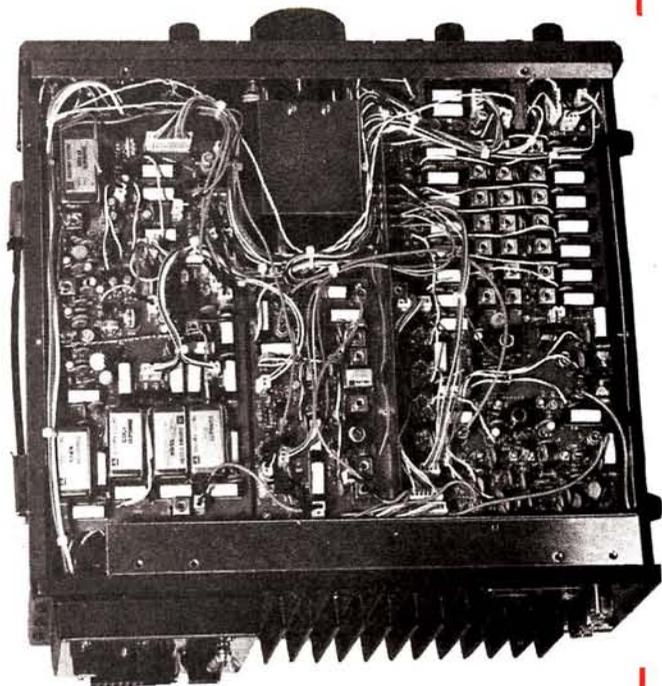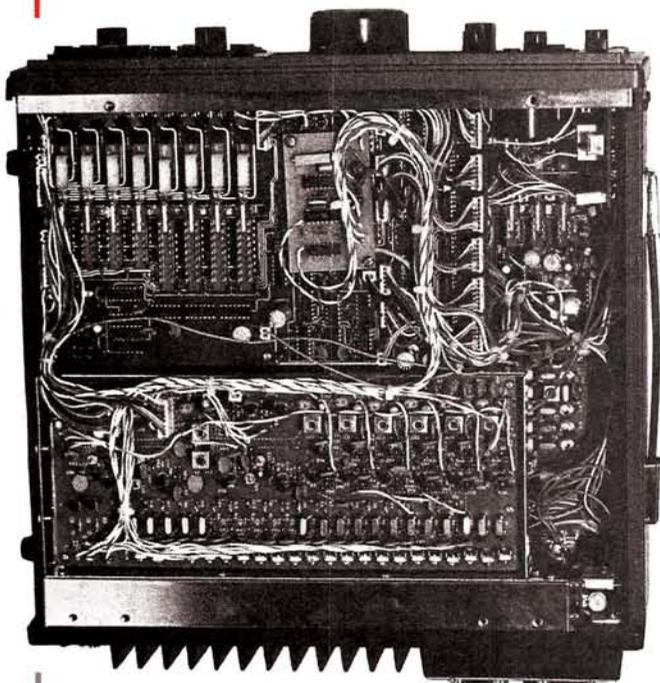Bottom view of the transceiver gives some indication of the excellent workmanship as well as the complexity of the rig



This top view shows the complexity of the switching arrangements together with the many crystals needed to cover the bands

As well as acting as the main heat-sink for the unit the rear panel also carries the various aerial sockets and the power inlets



## ★ specifications

### Frequency coverage:

1.5–2.0MHz  
 3.5–4.0MHz  
 7.0–7.5MHz  
 14.0–14.5MHz (extended to  
 15MHz on receive only)  
 21.0–21.5MHz  
 28.0–30.0MHz  
 70.0–71.0MHz  
 144.0–146.0MHz

### Types of emission:

A1, A3, A3J, F3

### Power output:

A1, A3J, F3:10W, A3:5W

### Carrier suppression:

Better than 40dB

### Sideband suppression:

Better than 40dB at 1kHz

### Spurious radiation:

Down 50dB or more  
 (1.8–28MHz band)  
 Down 60dB or more  
 (70–144MHz band)

### Harmonic radiation:

Down 60dB or more  
 (1.8–28MHz band)  
 Down 70dB or more  
 (70–144MHz band)

### Distortion products:

Down 30dB or more

### Aerial output impedance:

50Ω unbalanced

### Frequency stability:

Less than 100Hz drift in any  
 30 minute period

### Receiver sensitivity:

Better than 0.3μV for 10dB S/N  
 (1.8–14MHz band)  
 Better than 0.2μV for 10dB S/N  
 (21–144MHz band)

### Selectivity:

0.4kHz, 1.2kHz, 1.8kHz, 2.4kHz  
 (–6dB): A1, A3, A3J  
 16kHz (–6dB): F3

### Intermodulation—

#### 2-tone dynamic range:

100dB (1.8–14MHz band)  
 95dB (21–144MHz band)

#### Intercept point:

28dBm (1.8–14MHz band)  
 13dBm (21–144MHz band)

### Intermediate frequency:

12.375MHz (single conversion)

### Image rejection:

Better than 60dB

### IF rejection:

Better than 70dB

### Squelch sensitivity (F3):

0.33μV or better

### Audio output:

2.5W

### Power consumption:

240V 50/60Hz; 50VA (receive)  
 118VA (transmit)  
 13.5V d.c.: 1.5A (receive)  
 3.5A (transmit)

### Dimensions:

356 x 153 x 356mm

### Weight:

13.6kg (approx)

On 2m f.m., a rather poorly sited "Slim Jim" brought an S9 report from a hand-held, operating indoors, about five miles away on the other side of a hill. Other contacts around the district seemed to produce similarly respectable results. A quick test on 2m s.s.b. using an 8-element Yagi at a different QTH seemed to suggest that receive sensitivity was somewhat down, by comparison with another rig.

Apart from this, the receiver side performed superbly, the very low rate of the main tuning making s.s.b. operation a joy. The r.i.t. rate was, as on almost all sets looked at recently, greater than desirable, or indeed necessary. As to the switchable bandwidth facility, the basic 2.4kHz performed well on s.s.b. and a.m., whilst 1.2kHz was good for c.w. searching, and 0.4kHz excellent for winking out c.w. from the QRM. The 1.8kHz filter did not seem to fill any particular need. The audio output quality was reasonable, but suffered from being emitted from an upward-facing loudspeaker. An external speaker was not tried.

The operating manual supplied with the set very definitely did not match up to its quality, being a duplicated typewritten document just 13 pages long. No technical description of any sort was included, though there was a circuit diagram on a loose sheet. This had obviously been reduced from a very much larger original, and would require either extremely good eyesight or a magnifying glass to be of much practical use. The operating instructions given were quite comprehensive. We understand that a better manual is in preparation.

I mentioned earlier one reservation on the internal construction, and this was regarding the linkage between some of the push-buttons and their switches. However, the remainder of the set gives such an impression of being designed and built by people who know exactly what they are about, that I'm prepared to give them the benefit of the doubt on this point. Certainly, I had no problems during the tests, and the importers say they have had none either.

So there we are. The F850 is a bit weighty, and rather low in power, though the importers, Zycomm, do offer a suitable 220W linear for the h.f. bands at around £80 including VAT. On a value-for-money basis, it seems pretty competitive with an assemblage of sets and converters to provide the same facilities, though it does sound a lot of money for a 10W transceiver at first sight. There is, I suppose, the "eggs in one basket" aspect as well. Finding a spot for mobile installation will prove a problem in most cars.

### Price

The Sugiyama F850 is currently priced at around £900 with all filters fitted, and is available from **Zycomm Electronics Limited, 47/51 Pentrich Road, Ripley, Derby DE5 3DS, telephone Ripley (0773) 44281**, to whom we offer our thanks for the loan of the review unit.

**PLEASE MENTION  
 PRACTICAL WIRELESS  
 WHEN REPLYING  
 TO ADVERTISEMENTS**

# OF THE MONTH

Brian DANCE M.Sc

## $\mu$ A78S40 SWITCHING REGULATOR

During the past few years quite a number of monolithic linear i.c.s have been introduced which contain all of the semiconductor devices needed for use in a switching regulator circuit. The Texas Instruments TL496 and TL497 have already been discussed in *PW* together with the principles of operation of switching regulator circuits. This month's device operates in circuits of the same general type as those used with the TL497 i.c. and readers who wish to understand the operational principles of such circuits should refer to our December '79 issue.

### Comparison

The Fairchild  $\mu$ A78S40 performs functions rather similar to those of the TL497—there are various differences between the two devices, however. For example, the Fairchild  $\mu$ A78S40 can operate from input voltages in the range 2.5V to 40V, whereas the recommended range for the TL497 is 4.5V to 12V (with a 15V absolute maximum). The  $\mu$ A78S40 can provide an absolute maximum output voltage of 40V whereas the TL497 has an absolute output maximum of 35V. The minimum output voltage in the step-down configuration is limited in both devices by the value of the internal reference voltage source, quoted as 1.3V for the  $\mu$ A78S40 and 1.2V for the TL497. The  $\mu$ A78S40 can provide output currents of up to 1.5A without the use of external transistors, and the TL497 can handle 0.5A; however, much higher currents can be obtained from circuits using either device if one or more external transistors are employed. The i.c. then switches the transistors (mounted on suitable heatsinks) between the "conducting" and the "non-conducting" states so as to maintain a constant output voltage.

A particular advantage of the  $\mu$ A78S40 is the low standby current drain (typically 2.3mA to 2.8mA, compared with approximately 6mA, in the case of the TL497). The  $\mu$ A78S40 is supplied in a 16-pin d.i.l. package (the TL497 has a 14-pin d.i.l. case) and both devices have on-chip protection circuits which limit the maximum current to a value small enough to prevent damage in the event of the output becoming short-circuited, etc.

### Connections

The pin connections and internal configuration of the  $\mu$ A78S40 switching regulator sub-system are shown in Figs. 1 and 2. The circuit blocks on the chip include an oscillator whose frequency is determined by the value of a capacitor connected to pin 12. A portion of the output voltage is tapped off by a potential divider and the internal comparator is used to compare this fraction of the output voltage with the internal temperature-compensated reference voltage.

The comparator, in turn, feeds a logic circuit controlling

a driver transistor; this feeds an internal power transistor which acts as a switch for fairly high voltages and currents. The power diode (D1) required for the step-down and step-up voltage circuits is integrated onto the chip, but an external diode is used in the voltage inverter circuit design, which will be described later. The diode has the same current and voltage ratings as the transistor output device; typical switching times of 300 to 500ns are obtainable.

An operational amplifier has been included (in order to increase the circuit flexibility) although this is not required in the basic circuits in which the device is normally employed. The performance of this op. amp. is rather similar to that of the well-known 741 device, but a power output stage has been incorporated so that it can deliver an output current of up to 150mA and so that it can accept (or sink) a current of up to 35mA. The input circuit of this amplifier has been modified so that it will operate correctly with input voltages right down to the negative supply line potential, which enables the amplifier to be used with a single power supply (when the input could fall to 0V) instead of the more normal positive and negative arrangement.

### Applications

A few typical applications of the  $\mu$ A78S40 are given in this article but the design of switching regulator power supplies is a complex subject and it is possible only to scratch its surface in the space available here! For simplicity's sake, the discussion is limited to advising readers as to how they can make some typical circuits work without much trouble, rather than covering details of the numerous circuits in which this very versatile device can be employed by an experienced and clever circuit designer! Much more detailed circuit designs have been published by Fairchild (Application Note 344) but it is, as we said, a complex matter indeed.



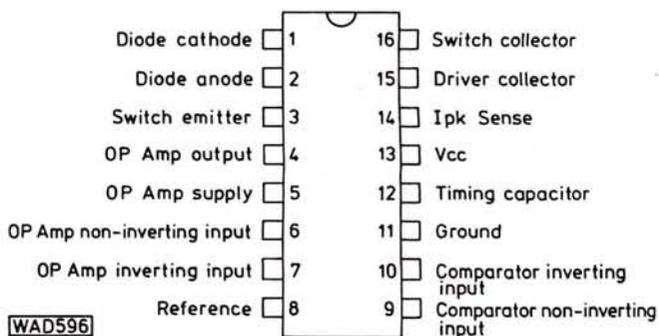



Fig. 1: Pin connections to the  $\mu$ A78S40

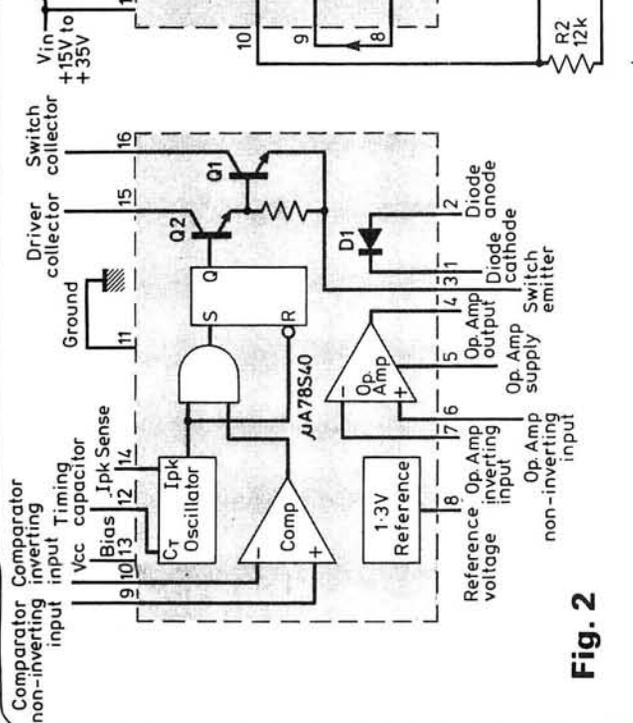


**Fig. 2**

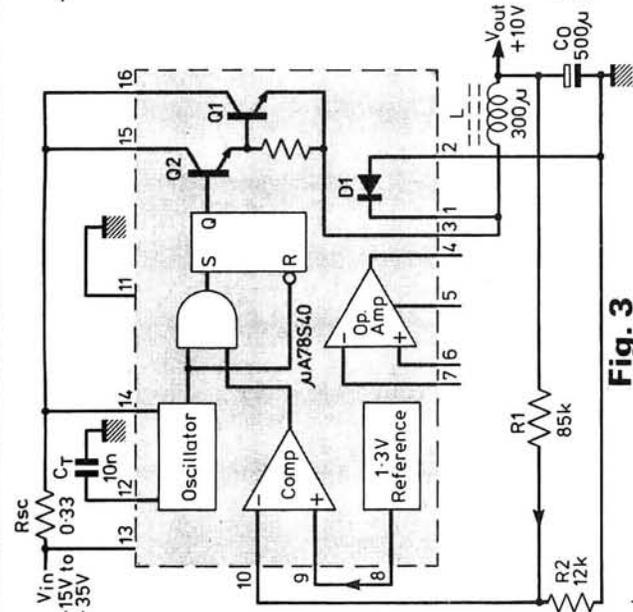


**Fig. 3**

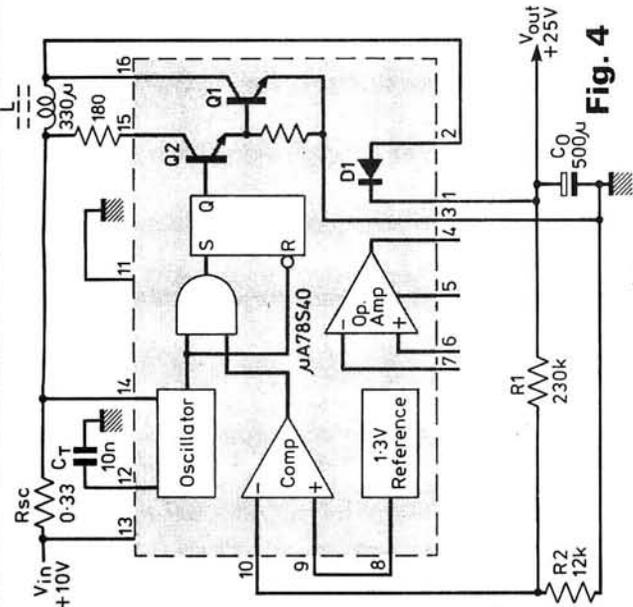

**Fig. 4**

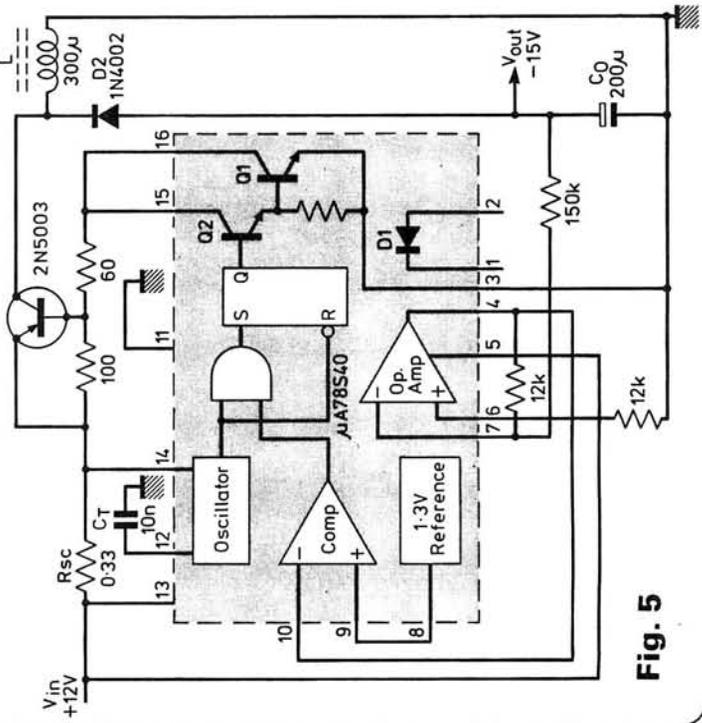

**Fig. 5**

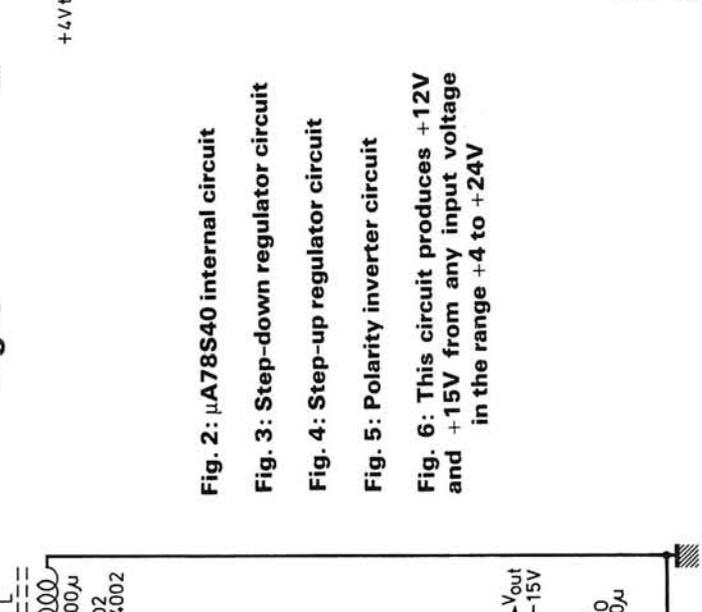

**Fig. 6**

**Fig. 2: μA78S40 internal circuit**

**Fig. 3: Step-down regulator circuit**

**Fig. 4: Step-up regulator circuit**

**Fig. 5: Polarity inverter circuit**

**Fig. 6: This circuit produces +12V and +15V from any input voltage in the range +4 to +24V**

## Step-down Regulator

A simple step-down circuit using the  $\mu\text{A}78\text{S}40$  is shown in Fig. 3. When the component values shown are used, this circuit accepts an input supply of about 15V to 35V and produces an output of +10V at a current of up to approximately 0.5A. Unlike series voltage regulator i.c.s, the input power is used with a relatively high efficiency, typically 74% when the output current is 200mA. Thus the output current normally exceeds the input current—if the input voltage rises, then the input current automatically falls (assuming that the output current is being drawn), since the input power is used so efficiently.

A portion of the output voltage is tapped off by means of the potential divider circuit R1/R2. This portion of the output voltage is fed to the inverting input of the comparator while the 1.3V reference voltage is fed to the non-inverting input. The circuit feedback system ensures that the output voltage changes so as to keep the two inputs to the comparator at almost the same level; the output voltage is equal to the 1.3V internal reference multiplied by:  $(R1 + R2) \div R2$ .

In this case, it works out as just over 10V, but the value of the internal reference can be from 1.18V to 1.31V depending upon the individual device; if an output of exactly 10V is required, arrangements must therefore be made to vary the ratio of the potential divider accordingly.

In a typical circuit the output voltage varied by only 1.5mV as the input supply voltage was increased from +20V to +30V—similarly as the output current was increased from 5mA to 300mA, the output voltage changed by only 3mV. The output ripple at the switching frequency was about 50mV in this type of circuit.

The op. amp. is not used in the Fig. 3 circuit and can therefore be used for any other appropriate purpose. The reference voltage is also available (pin 8) for other purposes, but the maximum current that may be drawn from this pin is 10mA, and must be observed.

Capacitor  $C_T$  determines the basic circuit timing of the oscillator. If the value shown (10nF) is employed, the charging current of  $25\mu\text{A}$  produces an "on" time of some 200 $\mu\text{s}$  during which the output transistor conducts. Similarly, the discharging current of about  $225\mu\text{A}$  produces an "off" or "non-conducting" time of about 22 $\mu\text{s}$  with this same capacitor value. Although the ratio of the basic "on" time to the "off" time is internally set at 8:1, the user can reduce this ratio by a suitable choice of resistor  $R_{SC}$ , this determines the peak current.

The oscillator timing is fairly critical if optimum performance is to be obtained. If the "on" time is too short, then the peak current through the inductor (L) and hence the maximum output current are reduced. An excessive "on" time can result in high currents and possibly even the destruction of the device and the same effect can be produced by a very short "off" time. A long "off" time can result in a reduced maximum value of the output current—thus one should be wary of altering the component value unless one knows what one is doing!

## Step-up Regulator

The regulator circuit of Fig. 4 provides an output voltage which is greater than the input voltage. In this circuit the output voltage is again equal to:

$$1.3(R1 + R2) \div R2.$$

When an output current of 50mA was taken from this circuit, the overall power efficiency was found to be typically 79% and the output ripple at the oscillator frequency about 30mV. The maximum output current was

about 160mA. As the input supply voltage rose from 5V to 15V, the change in the output voltage was only about 4mV. Load regulation was also very good, an increase in the load current from 5mA to 100mA producing an output voltage change of only approximately 2mV.

## Inverter

A  $\mu\text{A}78\text{S}40$  circuit is shown in Fig. 5 which provides a negative output voltage from a positive input voltage; it is therefore known as an "inverter" circuit. This circuit requires both an external *pn*p power transistor (such as the 2N5003) and an external "catch" diode, D2. Efficiencies as high as 93% at full load and 90% at 10% of full load have been reported for this circuit.

In the inverter mode, the internal op. amp. is used to invert the polarity of the part of the output voltage tapped off by the potential divider circuit so that the resulting positive potential can be compared with the positive reference voltage. This technique is possible only with an op. amp. which can operate with an input down to 0V.

A particularly interesting feature of this inverter circuit is that no part of the  $\mu\text{A}78\text{S}40$  device is connected to the full output voltage. Thus the maximum value of the output voltage is not limited by possible breakdown of the device itself. The readily available 1N4002 is shown for D2, but for maximum circuit efficiency (output power/input power) a fast-switching Schottky diode may be used.

Fig. 6 shows a circuit which will accept any input voltage from +4V to +24V and which will provide outputs of +15V and +12V. Thus the output voltages may be either lower or higher than the input voltage. The basic circuit is essentially similar to that of the step-up circuit of Fig. 4, the basic circuit which provides a 25V output supply. However, the internal op. amp. is also used as a series pass regulator which converts the +15V supply into a +12V output. When the input voltage exceeds +16V, the step-up regulator output of +15V follows the input voltage at approximately  $(V_{in} - 1)$ , but the potential of the +12V line remains virtually constant.

A particular advantage of this circuit is the high ripple rejection provided by the op. amp. This rejection is typically 100dB (minimum 76dB in any  $\mu\text{A}78\text{S}40$  device) and therefore output ripple at the oscillator frequency is virtually non-existent on the +12V line. However, the use of the op. amp. as a series regulator reduces the power efficiency of the circuit somewhat at the higher input voltages; the overall efficiency of this circuit is quoted as about 50% for both the upper (+24V) and lower (+4V) limits of the input voltage range, but increases to a maximum of about 75% for intermediate voltages.

## Inductor

Switching regulator circuits require an inductor and this is always an added complication for the home constructor. The inductor values suggested of 300 $\mu\text{H}$  and 330 $\mu\text{H}$  can be easily made, however, using Mullard RM6 and RM10 cores, which are readily available with an inductance factor ( $A_L$ ) of 250nH in the case of a single-turn coil. As the inductance is proportional to the square of the number of turns it is easy to calculate that 35 turns on one of these cores will produce an inductance of approximately 300 $\mu\text{H}$  and 36 turns about 330 $\mu\text{H}$ .

The RM10 core has larger dimensions than the RM6 core and, although the same number of turns are required with either type of core, the maximum wire diameter which

*continued on page 61* ▶▶▶

NEXT MONTH IN...

**practical**

# WIRELESS

## A Pw Scoop!



## THE Pw 'SHERBORNE' PART 1

### SYNTHESISED AM/FM TUNER

A state-of-the-art design, with microprocessor-controlled coverage of the long- and medium-wave broadcast bands, the 49, 41 and 31 metre short-wave broadcast bands and Band II v.h.f., f.m. Manual tuning and automatic scanning modes are incorporated, plus an 8-station memory. And it doubles as a clock!

### DIRECT CONVERSION RECEIVER

Build this simple receiver and listen to the world. Ideal for the beginner to short-wave listening the prototype picked up stations from all six continents within hours of being completed

### RECHARGEABLE HANDLAMP

Light up your darkest moments with this very useful NiCad powered torch



# TRANSCEIVER POWER UNIT

R.A.Ganderton G8V FH

The modern mobile rig is designed to run from the car's 12 volt supply. This ensures that the transceiver is fed from a low impedance source, as long as the cable used to feed the rig is large enough, but it does give problems when the transceiver is removed from the vehicle and used as a fixed station.

Commercially-built power supplies are available but these tend to be rather expensive if they are conservatively rated. To run a v.h.f. or u.h.f. f.m. transceiver giving around ten to fifteen watts r.f. power output the power unit will need to be able to supply a nominal 13.8V at 5A continuously. The current taken by an f.m. transmitter, unlike an a.m. one, is constant and the unit described here is capable of giving 5A all day, with 6A available but with increased ripple. Short-circuit protection is incorporated together with full over-voltage protection to guard against possible regulator failure.

## Raw Power Supply

The raw d.c. supply is conventional with a high current bridge rectifier feeding into a large reservoir capacitor. This capacitor must be capable of handling very large ripple currents and this unfortunately means that it will not be cheap. The primary of the mains transformer is fused and incorporates a filter built into the mains input plug. The raw d.c. supply is also fused with a 7.5A fast blow fuse which is also part of the overvoltage protection.

## Stabiliser

It is desirable to have a stable output voltage to avoid large fluctuations in the performance of the transceiver. The stabiliser helps with smoothing the supply and also provides a low output impedance.

With high current supplies the choice of stabiliser can

prove to be a problem as there are very few i.c. regulators available capable of handling five or six amps particularly if reasonable cost is of importance. Discrete components can be used but this approach can also prove bulky as well as pricey.


For this unit a 78HG 5A variable regulator i.c. was chosen as this is reasonably priced, provides full overload and thermal protection and allows the output voltage to be adjusted exactly to the 13.8V recommended by the majority of transceiver manufacturers. The 78HG is a four terminal device in a TO3 case and can supply 5A continuously, with current limiting coming in at 7A. The output voltage is controlled by varying the voltage on the control pin of the regulator. Capacitors C2 and C3 prevent the regulator from bursting into high frequency oscillation.

## Overvoltage Crowbar

The regulator will not function unless the input is more than 3V greater than the output required and in this power supply the raw d.c. input to the regulator will be  $1.4 \times V_{r.m.s.}$  or 21V with a 15V transformer. If the regulator chip fails and goes short-circuit then all of the 21V will appear at the output terminals and cause a lot of damage to the expensive transceiver.

Overvoltage protection can be simply added with a cheap overvoltage protection i.c. such as the 3423. This monitors the output of the power supply and when it senses that the output has exceeded a preset value the output of the i.c. triggers a thyristor arranged so as to short-circuit the supply and blow the fuse.

Overvoltage crowbar i.c.s have a reputation for firing at the slightest provocation and this can be very inconvenient, especially if the fuse is blown each time. For this reason the crowbar is arranged to ignore very short duration transients but to fire if the output rises above, say, 15V for longer than 200 $\mu$ s. In practice this has proved to

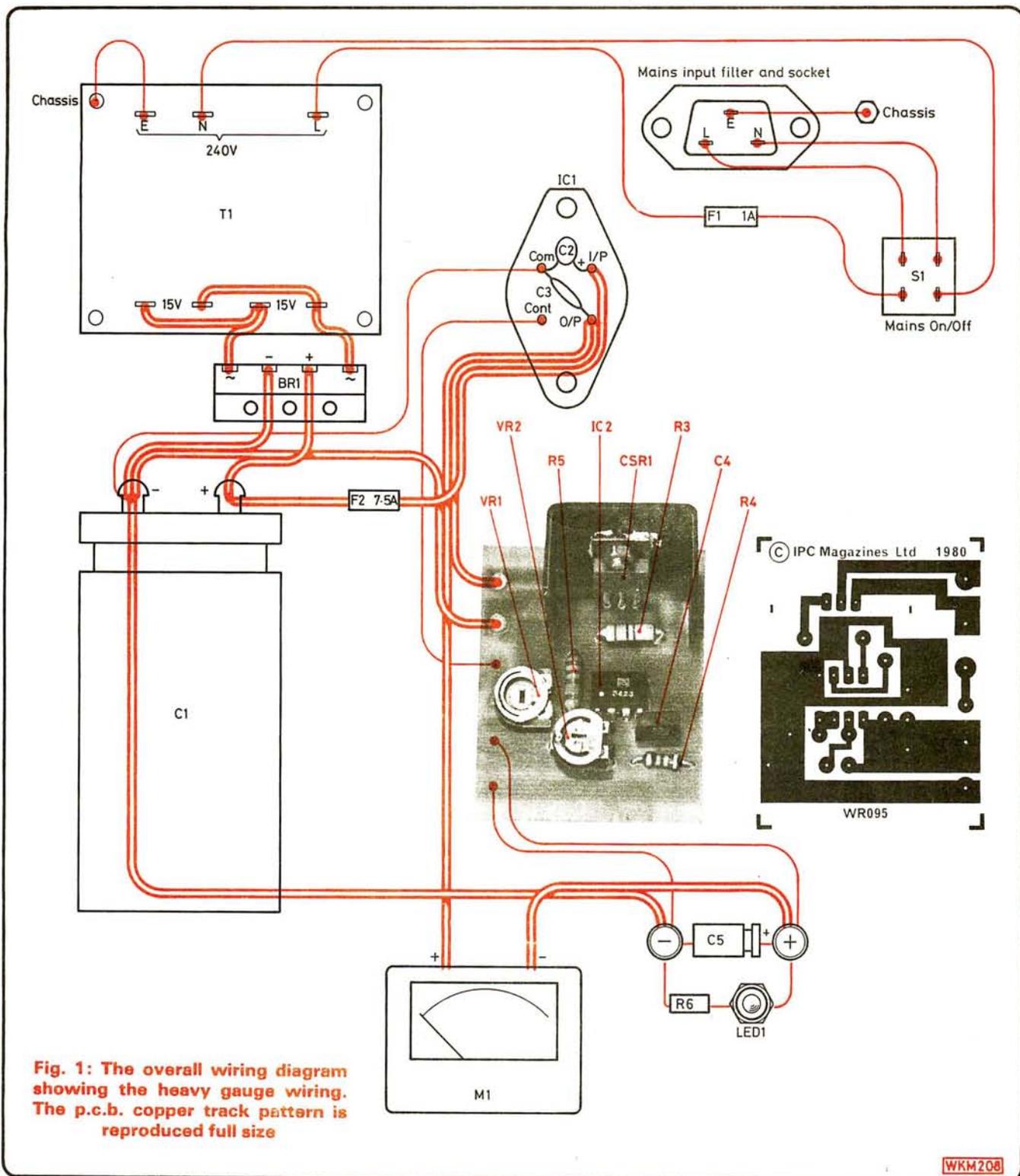

**Fig. 1: The overall wiring diagram showing the heavy gauge wiring. The p.c.b. copper track pattern is reproduced full size**

WKM208


be about right as tripping is very rare. The 1000µF capacitor across the output terminals prevents the output rising faster than the sensing voltages on the i.c. during initial switch on. If this happens the crowbar trips, making it difficult to actually switch the supply on.

The thyristor, which shorts the supply when the crowbar trips, is connected across the output of the regulator rather than the input. This has the advantage of using the current limiting facility of the regulator, limiting at 7A, instead of blowing the fuse. The fuse will still blow however, if the overvoltage condition is caused by regulator failure.

## Construction

As long as a large enough heatsink can be provided for the regulator and bridge rectifier the unit can be built into any case. The prototype was built into a West Hyde Swiftcase which not only gives the supply a professional appearance but has the advantage of providing adequate heatsinking as well.

The regulator has an insulated case so no insulating kit is required when mounting it on the back of the case. However, the holes must be deburred and heatsink compound should be used to ensure good thermal connection.

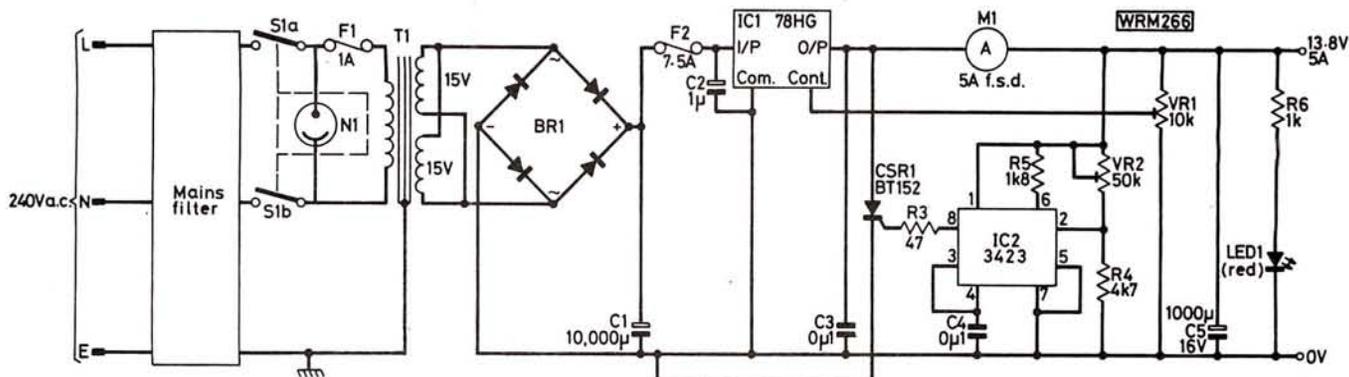


**Fig. 2: The circuit diagram of the 5A power supply**


The transformer, mains filter, plug and fuse are also mounted on the back of the case. The front panel carries the mains switch, ammeter if desired, output terminals and an indicator lamp to show the state of the overvoltage trip.

The thyristor, overvoltage trip i.c. and the presets for overvoltage level and output level are mounted on a small p.c.b. which can be secured to the case bottom by self-adhesive foam pads.

The wiring of the unit is important as the currents involved are very high. All high current paths should be wired using 1.5mm<sup>2</sup> cable. The voltage control and sensing wiring can be carried out in more normal thickness wire. It is advisable to follow the wiring diagram (Fig. 1) even if a different case is used.

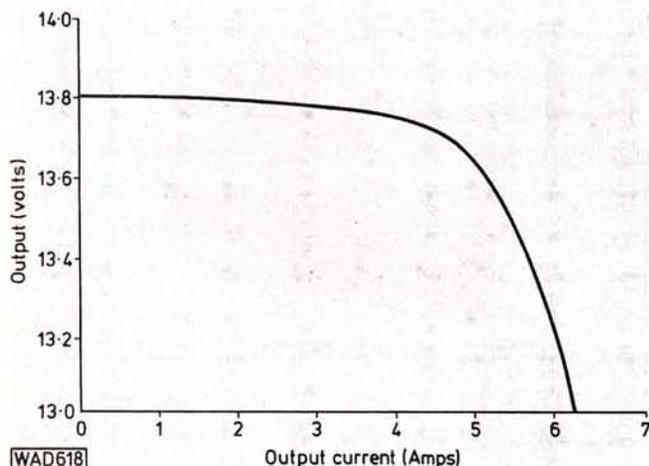

**Fig. 3: The performance of the prototype unit is shown in this graph. The maximum short-circuit current is held at 7A by the regulator itself and up to 5A the regulation is good. The output ripple increases at about 5A as the regulator starts to drop out on the negative going ripple peaks but this could be improved by increasing C1, at greater expense**

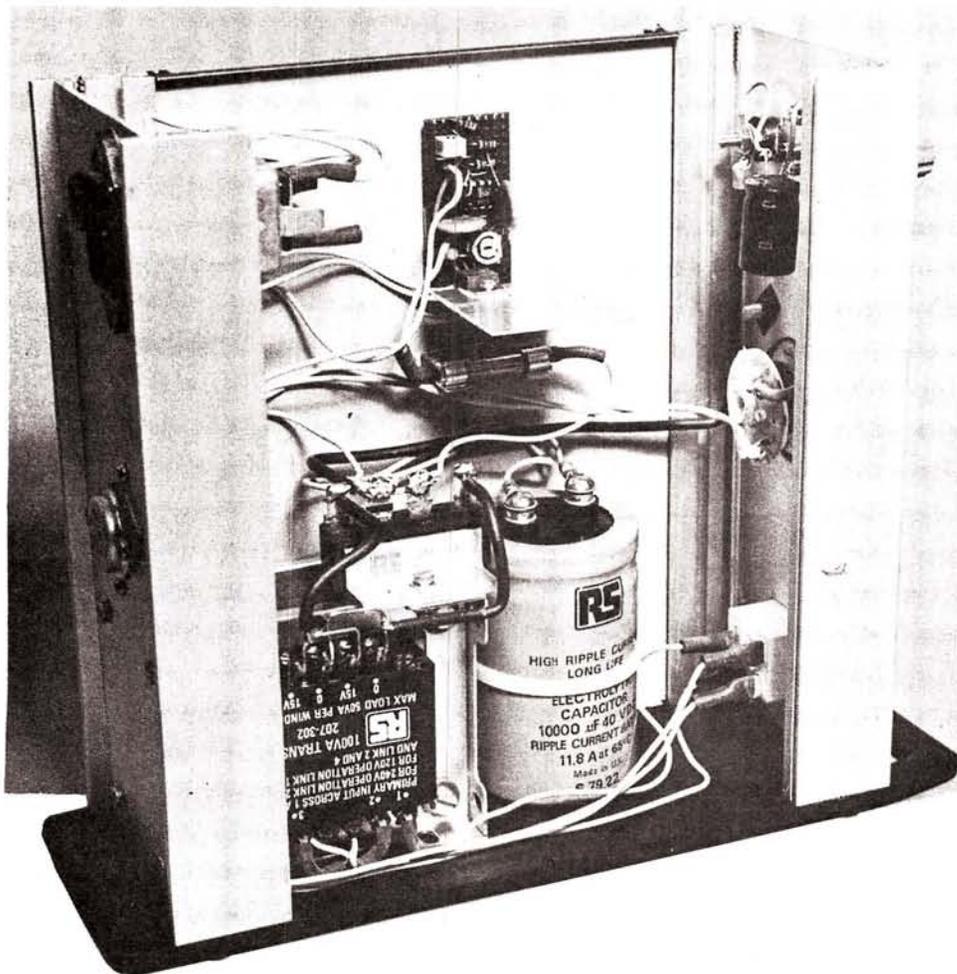

**The interior of the prototype unit. The actual positioning of the components is not critical, but high current paths should be kept as short as possible to prevent excessive voltage drop occurring. The overvoltage crowbar circuit is built here on Veroboard, but the final version uses the p.c.b. shown in Fig. 1**

# LOWE ELECTRONICS LTD.



**TRIO R1000**

**£298** inc VAT

THE FINEST HF COMMUNICATIONS RECEIVER FROM THE LEADING COMPANY IN THE FIELD

## R 1000 BY TRIO

THIS RECEIVER IS SO ADVANCED, IT MAKES ANYTHING ELSE IN ITS PRICE RANGE COMPLETELY OBSOLETE.

And we should know, because we at Lowe Electronics have been firmly committed to Trio ever since we were appointed to be the UK distributors many years ago, and we are your direct contact with the Trio factory if you need advice or information. As the Trio distributors, we maintain the finest amateur radio workshop in the country here at Matlock, and our customers will tell you of our renowned service.

We stock and sell the complete Trio range, and operate a fast, efficient mail order and Securicor delivery service so that you are as close to us as your nearest letter box. We also recently introduced a terrific new credit card scheme which gives you, the customer, real purchasing power with instant credit.

As an example, should you wish to pay £12.50 per month, you have instant credit of £300.00 which is enough to buy your R1000 right away; no hefty deposits, no fuss and as a further bonus, should you need accessories, or even a new transceiver, you can extend the credit on your card to suit. The Lowe blue card is a really powerful purchasing aid and you shouldn't be without it. Why not ask us for details right away and also for full information on all that's good in Amateur radio.



The new digital flight scan receiver from Regency of America is a stunning improvement on any other air band monitor receiver. Utilising its own micro computer system to control an advanced synthesiser, the flight scan allows you to monitor any air band frequency in the range 108-136 MHz and to store up to 16 channels which can then be scanned continuously. Other features include fast keyboard entry of frequency, full band search facilities, channel lockout and much more. For the last word in air band monitors contact us today. Also available - M100 digital FM scanner covering 30-50 MHz, 144-174 MHz and 430-512 MHz.

FLIGHT SCAN £199 inc VAT carr £4.50  
M100 FM SCAN £192 inc VAT carr £4.50



### R820

The ultimate in receiver design. Trio R820. With more features than ever before available in a ham band receiver. This triple-conversion (8-83 MHz, 455 KHz and 50 KHz I.F.s.) receiver, covering all amateur bands from 160 through 10 metres, as well as several short wave broadcast bands, features digital and analog frequency readouts, notch filter, I.F. shift, variable bandwidth tuning, sharp I.F. filters, noise blanker, stepped R.F. attenuator, 25 KHz calibrator, and many other features providing more operating conveniences than any other ham band receiver. Price £690-00, including V.A.T. Carriage £4-50.

### SP820

Matching speaker to fit the R820, with built-in filters, 8 ohms impedance. Price £37-95, including V.A.T. Carriage £1-50.

### SRX30


The SRX-30 represents a new step forward for the keen short wave listener or the radio amateur who needs to tune frequencies outside the amateur bands.

In the past, the performance of general coverage receivers has been limited by the difficulty inherent in setting to a known frequency - OK, so you know that Radio Peaking is on 8547 KHz but how do you set the receiver dial? The SRX-30, due to application of new technology solves the problem by utilising a drift cancelling loop system converting to a very high (40 MHz) first IF so as to remove image interference problems. This is followed by a stable VFO controlled tunable second IF with excellent reset accuracy. The frequency range covered by the SRX-30 is 500 KHz - 30 MHz in thirty bands, each 1 MHz wide. If you wish to tune to say 14250 KHz, simply set the MHz dial to 14, the KHz dial to 250 and there you are, no fuss, no twiddling, no need to use calibrators, etc. (remember the drift cancelling system).

The SRX-30 is housed in a rugged metal case and operates from 240V ac mains or 12V dc supply. Reception modes are USB/LSB/AM/CW to cater for all HF operation and the receiver is equally at home on VHF using an external converter.

This receiver combines small size, accurate readout, ease of use, all mode operation, mains/battery power supply and excellent performance at a remarkably low price. See it, use it and you will like it.

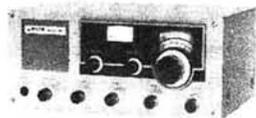Price £178-00 including V.A.T. Carriage £4-50.



### FS10

The FS10 VHF FM monitor receiver is a high performance unit in such a small lightweight package that it will fit into a pocket. The receiver can be aligned for the 2 metre amateur band or the VHF marine band and provides top performance on either band.

The FS10 automatically scans up to ten crystal controlled channels, stopping on any channel where a signal is present. Manual selection of any channel is also provided. Complete with rechargeable battery pack, charger and personal earphone with provision for external antenna. Price £82-00, including V.A.T., crystals extra. (Fitted ten channels £109-25, including V.A.T.) Carriage £1-50.



### AMR217B

The AMR217B VHF FM monitor is an outstanding receiver suitable for either the 2 metre amateur band or the VHF marine FM band and can be supplied for either band on request. The AMR217B has an eight channel scanning facility and can also accommodate up to ten additional switched channels to extend its versatility even further. The receiver is extremely sensitive and is one of the best monitor receivers available to either the amateur or professional user. It is completely self-contained with a built-in speaker and operates from 240V AC mains or 12V DC supplies. A matching mobile mount is supplied to allow easy installation in boat or car. Price £120-75, including V.A.T. (fitted 8 crystals). Carriage £1-50.



### SR9

The SR9 represents the finest value for money ever offered in the FM monitor receiver market. Available in two versions to suit the 2 metre amateur band or the VHF marine FM band the SR9 gives fully tunable coverage of either band and also incorporates the facility for installing optional crystals which will provide up to eleven fixed channels for the most popular frequencies. The SR9 is completely self-contained with built-in speaker and requires only 12V DC at around 200 mA to operate. Mounting hardware is provided for easy installation anywhere.

Price £46-00, including V.A.T. Carriage £1-50.



### AP12

The AP12 is a 12 channel crystal controlled airband monitor receiver covering a frequency range from 108 to 136 MHz which utilises a micro-computer which automatically peaks the R.F. oscillator and mixer stages in accordance with the crystal frequency in use. This means that you can install crystals for any frequency in the entire band without any drop in performance. Supplied complete with rechargeable battery pack, charger and personal earphone. Price £89-70, including V.A.T. Fitted 12 channels: £116-45, including V.A.T. Carriage £1-50.



### R512

The R512 airband receiver is a high performance unit which automatically scans up to eight crystal controlled channels. The receiver will stop on any channel on which there is a transmission, stepping on again at the end of transmission. You may lock the receiver onto any channel of your choice for continuous monitoring and if any channel should be more or less permanently occupied you may also lock out the channel to permit scanning of other channels. These facilities are available on any or all channels. Covering the full band from 108-136 MHz, the R512 is completely self-contained including built-in speaker and is supplied with mains and 12V DC power leads, whip antenna, mobile mounting bracket and personal earphone. Price including five fitted channels is £138-00, including V.A.T. Carriage £1-50.

**PET**  
FULL RANGE OF  
COMPUTERS AND  
PERIPHERALS.  
NEW 16K IN  
STOCK.

For all that's good in Amateur Radio, contact;  
**LOWE ELECTRONICS LTD.,** Chesterfield Road, Matlock, Derbyshire. Tel: 0629 2430 or 2817.  
For full catalogue, simply send 48p in stamps and request catalogue CPW.

# REALLY GREAT ANTENNAS

## THE JOYSTICK VFA

● THE MICROSCOPIC 230cm. GIANT Joystick VFA (Variable Freq. Antenna) ● Simple, rapid erection ● Not only 6-band but CONTINUOUS 0.5 - 30 Mhz., incl BC ● Omnidirectional ● Substantially harmonic-FREE ● 1 million miles per watt, world-record! ● Poor QTH's enhanced! ● QUOTE from RADIO ZS (South Africa) "A remarkable antenna with great possibilities. Its physical size makes confined space operation a practical proposition".

**SYSTEM "A"** For the SWL or 160m. Tx. **£48.55**

## NEW JOYMASTER SYSTEMS

● Amateur Bands 3.5 - 30 Mhz ● System "J" has been superseded by our IMPROVED JOYMASTER SYSTEM "JM2" ● SYSTEM "JM3" is a NEW DEVELOPMENT for the PRISONER OF CIRCUMSTANCE! ● THE HIGH-RISE BLOCK DWELLER'S DREAM!

**SYSTEM "JM2"** 500 w.p.e.p. **£69.00**  
**SYSTEM "JM3"** 500 w.p.e.p. **£90.00\***

\*Does not include 50 ohm. coax. cable where required to feed remotely located JOYSTICK VFA.

JOYSTICK OWNERS - PLEASE NOTE. ● CONVERT YOUR EXISTING SYSTEM "A" OR "J" TO "JM2" (plus £43) or TO "JM3" (plus £61) less UP TO £10.00 TRADE-IN ALLOWANCE on your 111B or Lo-Z-500 ATU subject to condition.

# UNBEATABLE FRG 7/7000 BARGAINS

COMPLETE RECEIVING STATIONS - ASSEMBLED IN SECONDS!

● FRG7 - free wire aerial and purpose-built JOYMATCH ATU ONLY £189.00 ● FRG 7000 - free wire aerial and purpose-built JOYMATCH ATU ONLY £339.00 ● Package "R.1.", (FRG7 + World Record VFA and FREE HEADPHONES) £218.00 ● Package "R.2.", (FRG7000 + World Record VFA and FREE HEADPHONES) £368.00.


We reckon we're offering the

# LOWEST YAESU PRICES

Try phoning us for your *personalised* quote, with or without Partridge antennas. For example:

● FT901DM - ONLY £790!! ● FT101ZD - ONLY £567!! ● FT7B - ONLY £369!! If you take Partridge products as part of a "Package" deal, you'll save even more!

## VHF BUSINESS RADIO

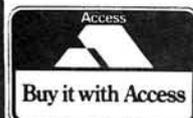

● We can help! Just phone or send stamp.

### JUST TELEPHONE YOUR CARD NUMBER

0843 62535 (ext 5) (62839 after office hours) or send 12p stamp for FREE literature. Prices correct as at press. NOTE our prices are always INCLUSIVE OF VAT, carriage. Prompt service too, goods usually despatched WITHIN 48 HOURS!

5 Partridge House, Prospect Road, Broadstairs, Kent CT10 1LD (Callers by appointment).



THE # WIRE WOUND AND MOST COPIED ANTENNA IN THE WORLD

# 'Firestik' ANTENNAS

CITIZEN BAND FIBREGLASS ANTENNAS AND ACCESSORIES

Call or write for full information:

WINTJOY Ltd.

103 HIGH STREET, SHEPPERTON MIDDX. TW17 9BL.  
 Tel: Walton-on-Thames (STD 09322) 48145



... the sign of fine communications

## SRX30 SWL RECEIVER £178.00

### TRIO EQUIPMENT

	Price inc. VAT
R1000 SWL PLL Receiver 200KHz to 30MHz	287.85
R820 The ultimate SWL receiver	690.00
YG455C CW filter 500Hz	58.65
YG455CN CW filter 250Hz	60.95
SP820 Speaker	37.95
HS5 Communications headphones, tailored response	21.85
HS4 Communications headphones, tailored response	10.35
VHF AMATEUR RECEIVERS	
SR9 Tunable/crystal 2m FM receiver 144-146MHz	46.00
AMR217B Scanner with 8 crystals. Mains/battery	120.75
ROTATORS, TUNERS & SWITCHES	
AR40 (5 core cable required)	54.63
FU200 For lightweight 2m beams	40.39
KX2 AK Antenna Tuner 0.5-30MHz	29.90
CK3 SWL 3-way Antenna Switch	7.20
DAIWA CS201, 2-way Antenna Switch	11.98
KW SWL 3-way Antenna Switch	14.80
AIR BAND RECEIVERS	
SHARP FX-213-AU Air Bands Portable Receiver	18.75
LOWE APT12 Crystal Controlled air band portable receiver c/w ni-cad batteries, charger and fitted 12 crystals	118.45
COPAL-24 Hour Digital Clock Mains Operated	12.95

All prices include new VAT rate

(Securicor carriage available if required)

Buy by post or phone your Barclay Card or Access number.

Alternatively, call in for a chat. The shop is just 10 minutes from Leeds City Station, and there's easy parking if you travel by car ★ Instant H.P. for licenced Amateurs ★ Extended Credit Terms Available ★ Send 50p for Catalogue and Price List.



LEEDS AMATEUR RADIO  
 27 Cookridge Street,  
 Leeds, W. Yorks. Tel. 452657

### LOWE TRIO DISTRIBUTOR



LAR are area distributors for Jay Beams, Antenna Specialists, Hilomast ICOM and Microwave Modules Products.

## ★ components

### Resistors

$\frac{1}{4}$ W 5%

47 $\Omega$	1	R3
1k $\Omega$	1	R6
1.8k $\Omega$	1	R5
4.7k $\Omega$	1	R4

### Potentiometers

Min. horizontal preset

10k $\Omega$	1	VR1
50k $\Omega$	1	VR2

### Capacitors

Ceramic

0.1 $\mu$ F	2	C3,4
-------------	---	------

Electrolytic

1000 $\mu$ F 16V	1	C5
10 000 $\mu$ F 40V	1	C1 (see text)

Tantalum

1 $\mu$ F 35V	1	C2
---------------	---	----

### Semiconductors

Diodes


150V 18A Bridge	1	BR1
BT152	1	CSR1

Integrated circuits

3423	1	IC2
78HG	1	IC1
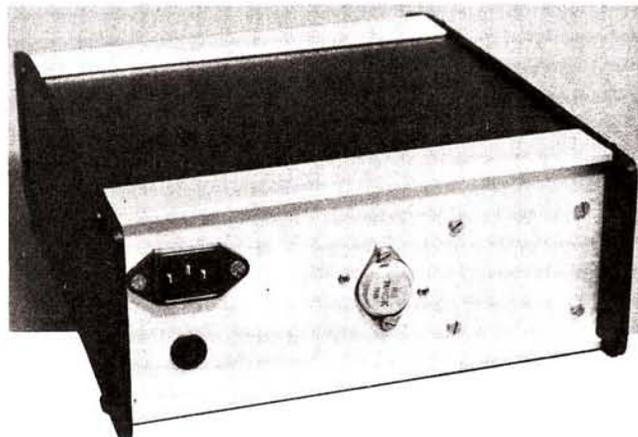
### Miscellaneous

Transformer 15V 100VA; Case, West Hyde Swiftcase SWF222; Illuminated mains switch (S1 and N1); Meter 5A f.s.d.; Mains plug with built-in filter unit; Panel mounting fuse holder; Chassis mounting fuse holder; 4mm insulated terminals, red (1), black (1); p.c.b.; 14-pin d.i.l. socket; Heatsink for CSR1.



The back panel of the West Hyde Brightcase doubles as the heatsink for the regulator. If a different case is used adequate heatsinking must be provided. The integral mains input plug and filter helps to minimise interference being transmitted via the mains wiring

## Testing and Setting-up

The overvoltage control VR2 should be set to maximum voltage (minimum resistance) and the output voltage control VR1 set fully anti-clockwise to give minimum output voltage. Switch on and check for any possible signs of trouble. With a voltmeter across the output terminals set the output to 15V by adjusting VR1. Now carefully adjust VR2 until the crowbar trips and the indicator on the front panel goes out.

The only way to reset the trip is to switch off, but before switching on again reset VR1 to give minimum voltage. After switching on again the output voltage can be set to exactly 13.8V and the output checked on load. A short-circuit across the output terminals should give a current of 7A without blowing fuse F2.

If the unit performs satisfactory it can be put into service powering your transceiver. ●

## KINDLY NOTE!

### Dual Trace Unit, February 1980 and March 1980

There are several minor discrepancies between the circuit diagrams in Part 1 and the p.c.b. layout in Part 2. The p.c.b. layout should be taken to be the definitive version. There are some extra tracks on the p.c.b. track plan which should be removed. These are between the source and gate of Tr603, 604, 605, 606.

### '2BCX 16-element 2-metre beam, February 1980

Quite a number of readers have constructed and are successfully using this aerial. Some, however, have chosen to make the driven elements, reflector and directors etc. of 6mm ( $\frac{1}{4}$ in) aluminium rod or tube instead of 4.76mm ( $\frac{3}{16}$ in) rod as specified, and as a result found it difficult to get an accurate match to 50 ohms and consequently a rather high s.w.r.

Although it is quite in order to use thicker element material, this does necessitate using a slightly longer matching line (Fig. 5 (a) and (c) in the article). This line may be constructed either from rod of the original diameter or from 6mm (0.25in) rod or tube, but must be about 100mm (4in) longer so that the shorting bar as in Fig. 5 (b) and feed tapping points can be moved further out. All other dimensions and materials remain the same.

# introducing

# RTTY

## part 1

### Jeff MAYNARD G4EJA

Telegraphy (of which RTTY is a development) was the first electrical communications technique to gain widespread acceptance. Samuel F. B. Morse brought together a number of then existing technologies and his own invention—Morse code—to provide the first telecommunications system. For many years the hand key, linked to another with copper wire, was the only means of direct remote communication.

Many brains worked through the turn of the century on improving the Morse code system. A cross between typewriter and a telegraph system was invented by Joy Morton and Charles L. Krum and the resulting Morkrum machine adopted by Associated Press in 1915. Concurrently, one Edward Kleinschmidt devised his own similar machine, and in 1925 he merged his company with Morkrum. Five years later this company was absorbed by AT & T and christened The Teletype Corporation. The machine name Teletype was an amalgam of telegraph and typewriter and is, incidentally, still a registered trademark of The Teletype Corporation. The use of the word to describe any mechanical printer is, strictly speaking,

illegal, though like Hoover, it has tended to become part of everyday speech. The pedants amongst us may prefer to use the common abbreviation TTY which is not protected by trademark or copyright legislation.

The developments of remote TTY printing terminals outlined above took place in respect of land-line signalling (Fig. 1) and this should be borne in mind when reading the description of printer interfaces in Part Two of this series.

During World War II, when the modern war machine demanded volumes of textual communications to armies in the field, it became apparent that the land lines hitherto used to link TTY terminals could be replaced by radio transmissions with only minor interface modifications (Fig. 2). Thus RTTY (radio TTY) was born. There then followed parallel developments of RTTY and TTY systems, the latter manifesting itself as the international telex system. The widespread use of TTY machines in commerce and military applications inevitably led to their appearance on the surplus market and hence to their use by amateurs.

## RTTY Code Format


The decoding and coding of Morse traffic by machine is complicated by the variable character length and the use of five different signalling units (dot, dash and three lengths of spaces). TTY on the other hand uses only two signalling elements—mark and space—and, because all characters are the same length, there is no significance to any inter-character spacing (there being no intra-character spacing).

Computer enthusiasts will immediately see the possibilities for processing what is basically a binary system. RTTY was developed before the microprocessor of course, and it is therefore more by good luck that computer techniques can be applied to the system. Such methods will be discussed in the final article of this series.

The two RTTY signalling conditions are known as Mark and Space. Mark is the normal or idle condition of the line (the various methods of representing Mark and Space in RTTY will be outlined later). A character is represented by a combination of marks and spaces and defined in the particular code in use. In order that the start of a character can be correctly identified it is always preceded by a space. Thus from the idle condition there will be mark-to-space transition; the space will last for a defined unit of time (depending on the overall system speed) and be followed by a combination of marks and spaces (each of the same defined unit of time) specifying the particular letter or number being transmitted. The character is finished with a stop pulse—always a mark—which is one-and-a-half units of time. So that is the theory of the code; now let us take a detailed look at the code format and the timing.
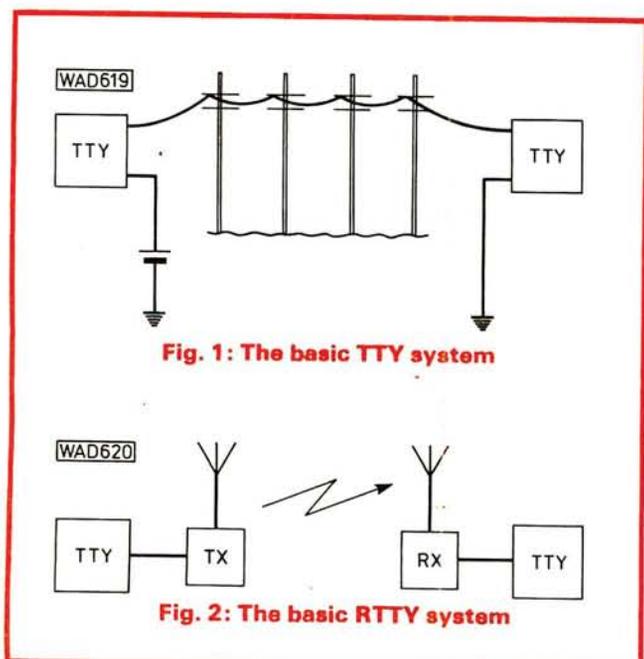
## The Baudot Code

In theory at least, any code could be used to represent characters in RTTY (e.g., ASCII, EBCDIC, ISO and so on). In practice RTTY used the same code as telex—the International Five-Unit Code also known as CCITT No. 2 and Baudot (from the gentleman who devised it). As the name implies, the Five-Unit code uses a combination of five elements (marks and spaces) to represent each character. The total number of combinations available is therefore 32 ( $2^5$ ). It is clear that this is insufficient for normal use, since the alphabet and a few control characters (such as carriage return and line feed) will need 32, leaving no combinations available for figures, punctuation marks and so on.



Character		Signal element				
Letter shift	Figure shift	1	2	3	4	5
A	—	•	•			
B	?	•			•	•
C	:		•	•	•	
D	wru	•			•	
E	3	•				
F	%	•	•	•		
G	@		•	•	•	•
H	£			•	•	•
I	8		•	•		
J	bell	•	•	•		
K	(	•	•	•	•	
L	)	•			•	
M	.			•	•	•
N	,			•	•	
O	9				•	•
P	0		•	•	•	
Q	1	•	•	•	•	
R	4		•	•		
S	'	•	•			
T	5					•
U	7	•	•	•		
V	=	•	•	•	•	•
W	2	•	•			
X	/	•	•	•	•	
Y	6	•	•	•		
Z	+	•			•	
Letters shift		•	•	•	•	
Figures shift		•	•	•		
Space				•		
Carriage-return					•	
Line-feed		•				


**Notes:**

wru means 'who are you and is used in telex. All space is not used.


• = Mark

WAD621


**Fig. 3: The full Baudot International Five-Unit Code (CCITT No. 2)**

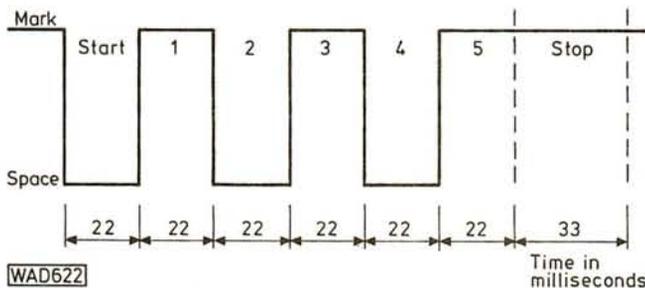

**Fig. 4: Composition of an RTTY character**

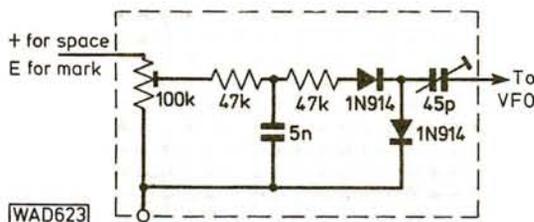

**Fig. 5: A simple circuit to produce FSK on a v.f.o.-controlled transmitter**

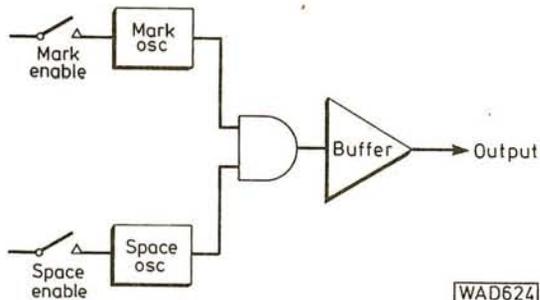

**Fig. 6: General principle of an AFSK generator**

This problem was neatly circumvented by Mr Baudot who introduced shifts. Thus a TTY machine can be in letter shift or figure shift. When in letter shift, any following keys denote their respective letter; when in figure shift, each key denotes a figure or punctuation mark. To change from one shift to another it is necessary to press the appropriate shift key.

The aspiring RTTY enthusiast should bear the shift system in mind; when tuning into an RTTY signal that appears unintelligible it may be that the receiving machine is in the wrong shift. For example a machine in figure shift will print:

:1 :1 :1 :1

when tuned to a station transmitting:

CQ CQ CQ CQ

The full Baudot code is shown in Fig. 3, to which the following comments apply:

1. Some characters (e.g., line feed) are the same in both shifts.
2. The code pattern is the same as the hole pattern across five-unit paper tape.
3. WRU means who are you and is the signal used in telex to request the remote terminal to send its identification (answerback).
4. All space is not a valid code.

## Speeds

The speed of an RTTY signal is expressed in baud, where one baud is equal to one signal element per second. We have already seen that a single RTTY character consists of: a start element; five code elements; 1½ stop elements, giving a total of 7½ elements per character. If then the signal was to be one character per second the RTTY rate would be 7.5 baud.

Most commercial RTTY is at 50 baud (telex being 75 baud) whilst amateur RTTY enthusiasts have standardised at 45.45 baud. Each code element is therefore 22 milliseconds long (60 divided by 45.45) and a complete character is 165 milliseconds long. Fig. 4 illustrates the basic RTTY character timing. From the idle mark state the character always starts with a 22ms space; this is followed by five character elements (10101 in the example) each also 22ms in length; the character is terminated by a stop pulse—always mark—of 33ms (one-and-a-half elements) in length. The amateur RTTY speed corresponds to six characters per second or (for average five-character words plus inter-word spaces) to 60 words per minute; this nomenclature is used by North American amateurs in preference to baud rates.

The timing of RTTY signals is important both in receive and transmit if correct decoding is to be guaranteed. Note that, unlike some modern data transmission codes, Baudot does not contain any mechanism for error checking. Distortion in the received pulse chain can lead to erroneous decoding. The two most common forms of distortion (which can arise from the transmission medium or the originating terminal) are bias and end distortion.

Bias distortion displaces the space-to-mark transition. Lengthening the mark by advancing the transition is called marking bias whilst lengthening the space by delaying the transition is called spacing bias. End distortion displaces the mark-to-space transition. Marking end delays the transition giving a long mark and spacing end advances the transition giving a long space. The RTTY enthusiast will normally have to contend most with characteristic distortion—that is distortion introduced by the transmission medium.

## Converting TTY to RTTY


To achieve a radio TTY link it is necessary to replace the hard-wired d.c. path by some form of coded radio transmission. Two methods of doing this are commonly used:

1. FSK (frequency shift keying) shifts the transmitted carrier frequency for each mark to space transmission.
2. AFSK (audio frequency shift keying) modulates a carrier with two different tones, one each for mark and space. This technique is also known commercially as VFT (voice frequency telegraphy).

The shift between the two frequencies is most important. The receiving unit (discussed next month) will use sharply tuned filters and will not decode for a wrongly spaced shift. The shift also determines the maximum

**Table 1**

Band	Frequency	Modulation
80m	3.60MHz ± 20kHz	
40m	7.04MHz ± 5kHz	
20m	14.09MHz ± 10kHz	
15m	21.10MHz ± 20kHz	
10m	28.10MHz ± 50kHz	
4m	70.56MHz	
2m	144.6MHz	FSK
2m	145.3MHz	AFSK
70cm	432.6MHz	FSK
70cm	433.3MHz	AFSK

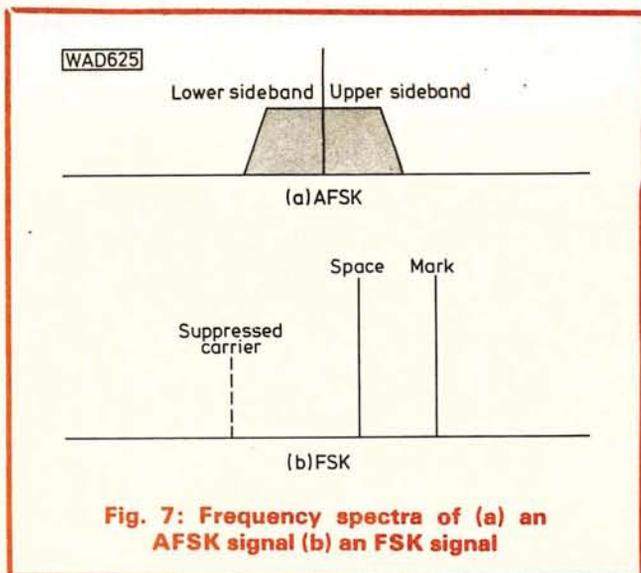

**Fig. 7: Frequency spectra of (a) an AFSK signal (b) an FSK signal**

transmission rate and the bandwidth required, although these are topics beyond the scope of the current article. The shift for amateur RTTY is 170Hz whilst most commercial traffic is at 850Hz.

FSK can be achieved by “pulling” the v.f.o. of a transmitter as shown in Fig. 5. The positive voltage appearing for a space will cause the diodes to forward conduct, placing the capacitor across the v.f.o., thus reducing its frequency (the capacitor being adjusted for the appropriate shift).

AFSK is generated by switching between two audio oscillators (for amateur RTTY of 1275 and 1445Hz), or by pulling a mark oscillator down to the required space frequency. The detailed methods of producing AFSK will be covered in a later article but Fig. 6 shows the general idea. The output of the AFSK oscillator is fed to the microphone input of a transmitter.

The frequency spectra for FSK and AFSK are shown in Fig. 7, which demonstrates clearly that FSK is more efficient (in terms of spectrum utilisation and signal power). However AFSK is much easier to produce. A nice compromise is available, because feeding AFSK to a s.s.b. transmitter will cause a signal closely akin to FSK to be radiated. This is the normal method adopted on the h.f. bands and for v.h.f. DX working. Local RTTY nets on v.h.f. and upwards tend to use AFSK with f.m. transmitters.

## Equipment

Traditionally, the RTTY enthusiast’s shack has been instantly recognisable from the smell of oil and the clanking of gears. Old electro-mechanical machines—such as from Creed, Siemens and Teletype—have been the mainstay for RTTY for years (and can still be bought for £10–£20). Recently RTTY has been invaded by the microprocessor revolution and many more stations are now operational using Pets or Apples or home-brew systems. The use of microprocessors for RTTY will be covered later in this series.

## Where to find RTTY

The IARU band plan recommendations for RTTY are shown in Table 1. Tuning around these frequencies,

*continued on page 61* ▶▶▶

# WATERS & STANTON ELECTRONICS

## FRG7 BY YAESU COMMUNICATIONS RECEIVER

·25 – 30MHz



**SUPER  
DEAL  
PRICE**

**£189** inc. VAT  
Securicor delivery £4.50 extra.

## LARGEST STOCKS IN THE SOUTH

YOU WON'T GET A BETTER  
DEAL OR SERVICE ANYWHERE

### WHERE TO FIND US:-

We are located between Rayleigh and Southend-on-Sea. Approach us from either the A127 or A130 and follow signs to Rayleigh. You'll find us in the quiet country village of Hockley with no parking problems. We've got 4000 square feet packed with electronics items much of which is devoted to Radio Communications. Servicing is carried out on the premises and we are known to Ham Radio operators as the number 1 source for a fair deal – no high power selling, just large stocks at the right prices with back-up after sales service – and that has to be a pretty fair deal.

## YAESU FRG7000 COMMUNICATIONS RECEIVER

0.2 – 30MHz



**SUPER  
DEAL  
PRICE**

**£339** inc. VAT  
Securicor delivery £4.50 extra.

## TRIO R1000 RECEIVER 0.2 – 30MHz



**SUPER  
DEAL  
PRICE**

**£298** inc. VAT  
+ 12v D.C. Kit free  
+ FREE Securicor delivery.

### SHORT WAVE AERIAL PROBLEMS?

We have 2 excellent short wave aerial packages. Both are based on tried and tested communications theory and produced specifically for us by our factory in Japan. That means better value for money – send stamped addressed envelope for details.

**NEW!**

## FM POCKET MONITOR

*Marine or Amateur version  
available.*

**BUILT IN 8 CHANNEL SCANNER  
RECHARGEABLE NI-CADS  
240V AC CHARGER  
MOBILE BRACKET  
FITTED 145.50 or 156.80 xtals.**

This pocket monitor is a brand new VHF monitor receiver that can be supplied for either the 2 metre amateur band or the VHF Marine band. Built into a strong metal case, the unit scans 8 crystal controlled channels with manual override. A telescopic aerial plus "fly lead" aerial are supplied to cater for all portable needs. At this price the stocks will go pretty fast so don't delay.



**SUPER  
DEAL  
PRICE**

**£69** inc. VAT  
Delivery FREE

## HAVE YOU READ THE REVIEW?

Then you'll already know how good it is.

## TRIO TR2400

(144-146.00 or 144-148.00 option)

The TR2400 is without doubt the best synthesized hand portable we have ever seen. We can supply either the 2 or 4MHz coverage models. All units come complete with AC chargers, nicads and flexible antennas. As an authorised Trio dealer we can offer the genuine UK models with full factory back-up. So don't take chances, come to us for a really super deal.

**SUPER  
DEAL  
PRICE**

**£210** inc. VAT  
+ FREE delivery.

## FM VHF MOBILES 144 – 146MHz FDK MULTI-700EX 25 WATTS OUTPUT DIGITAL DISPLAY



**SUPER  
DEAL  
PRICE**

**£199**

The Multi 700EX is specially produced for us in Japan by FDK. FDK are specialists in VHF/UHF communications and are known the World over by Radio Amateurs as manufacturers of the finest equipment available. The 700EX is a mobile FM transceiver with built-in speaker plus microphone and mounting brackets. The power output is variable 1-25 watts and the transceiver tunes in 25kHz or 12½kHz steps from 144-146MHz. Full repeater shifts are built-in including instant reverse repeater operation and also a scanning facility is included. So if you are thinking of buying a mobile unit you won't find a better deal – why not send for a colour brochure.

### ORDER WITH CONFIDENCE . . . OUR REPUTATION IS YOUR GUARANTEE

Callers welcome:- We are open 9am-5.30pm Monday-Saturday, Ex. Wednesday 9am-1.00pm.

Telephone orders:- Simply phone in your Barclaycard or Access number and we will despatch goods within 24 hours.

Mail Orders:- Send cheque or postal order for correct amount printing name and address clearly.

**WARREN HOUSE, 18-20 MAIN ROAD, HOCKLEY, ESSEX. TEL: 03 704 (Hocklet) 6835 TELEX.**



# Lee Electronics Ltd

LEE

AS REVIEWED IN THIS ISSUE

## C7800



The C7800 is one of the most advanced mobile 70cm transceivers available. Features include:- \* Digital Readout \* Five Memories \* Two Speed Scan Rate \* L.E.D.

**£274.85**  
inc. VAT

(C8800 is the matching 2m unit)


Power and S Meter and many more. Why not try one for yourself.

LEE



**NEW LOW PRICE**  
**FRG 7 £199.00**

## TR10 R1000

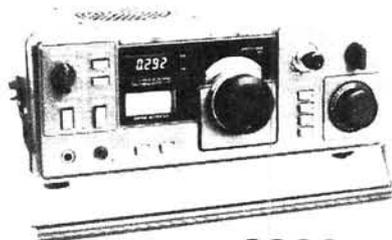

**BEAT THIS PRICE!! £289 inc. VAT**  
**FREE HEADPHONES WITH THIS SET AND WITH FRG7**

## THE NEW C800



This 10 channel scanner out performs many of its rivals due to its highly sensitive front end and excellent filtering. A one channel 50MW transmitter is incorporated and is ideal for local use. Controls include squelch, volume, auto scan and manual channel stepping. The unit comes complete with channels 520, R1, R2, R7, Nicads, charter, helical antenna and wire antenna.

**PRICE £69.95 + VAT**  
**CARRIAGE FREE**


400 EDGWARE ROAD  
LONDON W2  
01-723 5521 Tlx: 298765




INSTANT H.P. & P/EX. WELCOME

Send 25p for full details of our range.

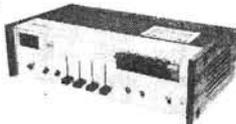**A40 'P.A. CENTRE' 20w.AC/DC** (40w. peak)  
Provides amplification/mixing of mic., T.V. and radio tuner, tape and record player, integral cassette player with quality output to speaker systems. Built in microphone and monitor loudspeaker, level meter.  
price inc. carriage and v.a.t. **£200.0p**



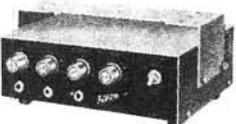**A55 MOBILE P.A. AMPLIFIER AC/DC 20w.**  
Solid state amplifier with chromed mounting bracket for vehicles, boats etc. Takes ceramic/crystal cartridges, radio, tape and mic.  
price inc. carriage and v.a.t. **£66.33p.**



**A60 SHOULDER P.A. SYSTEM 5w.** (7w. peak)  
Powered by internal battery, in carrying case with adjustable shoulder strap. Built in loudspeaker, and 'press to talk' microphone, input socket for mains adaptor.  
price inc. carriage and v.a.t. **£61.20p.**

**L83 10w. MEGAPHONE AND MICROPHONE** (16w. peak)  
Shoulder slung model with communications mic., economical battery operation.  
price inc. carriage and v.a.t. **£66.00p.**

**L81 10w. MEGAPHONE**  
Features on/off switch incorporated in pistol grip and forward facing dynamic microphone.  
price inc. carriage and v.a.t. **£84.65p.**

The above indicates just some of the P.A. equipment in stock. Also available Tannoy Speakers: all types of microphones: microphone stands: audio leads: crossover networks: Vw. meters: soldering irons: millivoltmeters: intercoms: doorphones: cassette and cartridge cases etc. etc.

Phone with your requirements, 9am. to 5.30pm. Mon. to Sat. inclusive.  
*£5 off to personal callers on above items.*



18 Providence Street, North Hill,  
Plymouth PL4 8JG, Devon.

Telephone: Plymouth (0752) 21581-2.

TRADE ENQUIRIES WELCOME

## LISTEN TO THE WORLD

WITH A  
RECEIVER  
FROM



Best Selection  
LOWEST  
PRICES

### MEDIUM WAVE / SHORT WAVE

Trio R300 with dual conversion on higher frequency band (above 18MHz). 170KHz-30MHz coverage. USB/LSB/AM/CW, 120Vac/240Vac/12Vdc supply or internal batteries. **£149**

Low SRX30 as featured in Aug. issue of P.W. Utilises a drift cancelling loop system to give performance plus. 500KHz-30MHz coverage, USB/LSB/AM/CW, 240Vac/12Vdc supply. **£178**

Trio R1000 as featured in May issue of P.W. 200KHz-30MHz. PLL synthesizer. Digital readout plus analog display for easy accurate tuning. 240Vac/12Vdc supply. **£297**

Trio R820, the ultimate in Trio short wave receivers. Covers 160m-10m bands + 4BC bands. Features 1F shift, variable bandwidth & notch tuning. **£690**

### AIRBAND (VHF)

Signal R517 portable, fully tuneable 118 to 143MHz with provision for 3 crystals (extra) 1.8 V Sensitivity, Fine Tuning control, Telescopic aerial. **£49**

Low AP12 portable 12 crystal controlled channels, rechargeable batteries & charger included, Micro-computer tuning, 0.5 V sensitivity **£89** - crystals **£2.80 ea.**

Signal R512 - automatically scans up to 8 crystal controlled channels, lock-out facility. 240Vac/12Vdc supply. **£143.50** inc 8 chs.

Regency Digital Flight Scan - fully synthesised to search 108 to 136MHz + 16 selectable scan channels - 2 priority channels. 240Vac/12Vdc supply. **£230**

### MARINE / AMATEUR (VHF)

Search SR9 - fully tuneable coverage - provision for 11 crystals. Fine tuning and Squelch controls. 12Vdc supply. **£46**

Low FS10 portable, 10 crystal controlled channels automatically scanned. Rechargeable batteries & charger included, Telescopic aerial. **£82** - crystals

Belcom AMR217B - automatically scans up to 7 crystal controlled channels with provision for 10 additional fixed channels. 240Vac/12Vdc supply. **£120** - crystals.

Regency M100 - fully synthesised to search 30-50, 144-174, 440-512MHz + 16 selectable scan channels 240Vac/12Vdc. **£192**

Additional crystals for all above receivers: Airband & Marine, **£2.80**; Amateur, **£2.40**. All prices include VAT but add carriage: S.W. & Regency receivers, **£5.50**; others **£1.50**.

EASY TERMS available. Access and Barclaycard's welcome

**CATRONICS LTD., COMMUNICATIONS HOUSE,**  
**(Dept. 87) 20 WALLINGTON SQUARE,**  
**WALLINGTON, SURREY, SM6 8RG.**

Tel. 01-669 6700 (9 a.m. to 5.30 p.m. Sat 1 p.m.) Closed lunch 12.45-1.45

# Beginners' 2 metre CONVERTER

R.A. Penfold

Most people who become interested in amateur radio do so initially by listening to the s.w. amateur bands. However, the v.h.f. and u.h.f. bands are very popular these days and many short-wave listeners soon wish to explore the bands above 30MHz in particular the 2-metre band, as it carries much local activity and also has interesting DX possibilities.

For the owner of a good s.w. receiver the obvious way to progress to v.h.f. reception is by using a converter ahead of the receiver, thus enabling it to operate on the required band. This is far less expensive than obtaining a separate v.h.f. set, which would result in unnecessary and costly duplication of circuitry.

There are two basic types of converter; the tunable type where the tuning is carried out in the converter and the receiver is used as a fixed i.f. unit, or the type where the converter tuning is fixed and the receiver is used as a tunable i.f. unit. The latter is the more popular method for use in v.h.f. converters where only a relatively small frequency range, e.g., 144–146MHz is to be covered.

The fact that the tuning and therefore the oscillator frequency are fixed, enables a crystal controlled oscillator to be employed, which greatly simplifies the alignment of the converter and gives excellent frequency stability, avoiding the necessity for an expensive tuning drive mechanism like that in the receiver. Even the calibration of the s.w. receiver can be used, as explained later.

## The Circuit

The main design aim was for the simplest possible circuit which would give good results and for a unit which would be easy to set up once completed. The circuit diagram is shown in Fig. 1 and for simplicity no r.f. stage is used. The input signal is coupled direct to a tapping on the mixer input tuned circuit which consists of L1 and VC1, preset tuning only being necessary as its bandwidth is more than adequate to embrace the entire 2-metre band.

In order to compensate as far as possible for the absence of an r.f. amplifier stage, a high gain, low noise mixer stage must be used. A MOSFET mixer, Tr1, is

therefore employed in the unit having a fairly low value source bias resistor, R1, in order to optimise gain. Capacitor C3 is the bypass capacitor and R2 fixes the bias on gate 2 of Tr1. Capacitor C1 and coil L2 form a broadband tuned circuit, tuned to the centre of the i.f. output tuning range, the resultant i.f. signal being coupled to the receiver from a tap on L2 via d.c. blocking capacitor C2.

Transistor Tr1 can be either a MEM616 or a 40673 device, the former giving slightly higher gain and a lower noise level.

## Oscillator

The purpose of the oscillator is to provide a signal which, when heterodyned with the input signal in the mixer, produces the required i.f. output. In this case, the oscillator operates at a frequency of 116MHz producing an i.f. output of 28–30MHz. Heterodyning produces sum and difference signals and it is the difference signal which is required, as shown below:

$$\begin{aligned} 144\text{MHz} - 116\text{MHz} &= 28\text{MHz} \\ 145\text{MHz} - 116\text{MHz} &= 29\text{MHz} \\ 146\text{MHz} - 116\text{MHz} &= 30\text{MHz} \end{aligned}$$

The sum and input frequencies also appear at the mixer output but are removed by the output tuned circuit, L2/C1 and the input tuned circuits of the receiver. It should be apparent that the reception frequency is equal to the frequency indicated on the receiver's tuning dial plus 116MHz. Thus it is an easy matter to convert the indicated reception frequency to the actual frequency of reception, so using the receiver's dial calibration. As the oscillator in the converter is crystal controlled the converter will contribute little to calibration errors.

The choice of an i.f. of 28–30MHz may not appear to be advantageous at first sight as the performance of most s.w. receivers falls off to some degree at high frequencies.

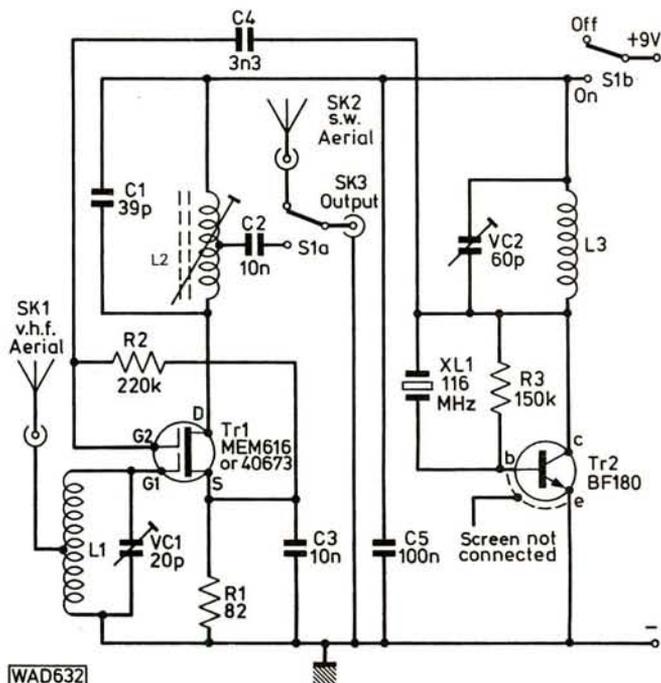


Fig. 1: Circuit diagram of the beginners 2 metre converter

However, this particular i.f. is popular as it is covered by most amateur bands only receivers as well as by most general coverage types. Also, in this instance, it is beneficial to use a high i.f. in order to obtain good image rejection with only the single tuned circuit which is used between the aerial and the mixer stage.

## Oscillator Crystals

Crystals with fundamental frequencies as high as 116MHz are not generally available, but conventional methods of obtaining crystal controlled signals at high frequencies are to use either a low frequency oscillator and multiplier chain, or an overtone oscillator, the latter being the method used in the circuit of Tr2.

With this type of oscillator, the fundamental frequency of the crystal is a fraction of the required output frequency, but the crystal is cut in such a way that it can be made to oscillate at the required frequency determined by VC2 and L3. Crystal XL1 is a fifth overtone type which means that its fundamental frequency is one fifth of its marked frequency.

Transistor Tr2 is used in the common emitter mode and is biased by R3; the screen leadout wire being left unconnected in this circuit. The oscillator output is coupled to gate 2 of Tr1 via C4.

Switch S1b is the on/off switch and S1a disconnects the converter output from SK3 in the "off" position and connects it to SK2 to which a s.w. aerial can be connected, avoiding the need to manually disconnect the converter from the receiver and reconnect the s.w. aerial when using the receiver normally.

The current consumption of the converter is only about 4mA, so a PP3 battery will provide very many hours of operation.

## Construction

With the exception of the sockets, battery and switch, all the circuitry is assembled on a p.c.b. as shown in Fig. 2. The layout of a v.h.f. circuit such as this is highly critical and it is recommended that this board should be used, the component overlay being shown in Fig. 3. The coils must

be made accurately as proper alignment of the finished unit will otherwise be impossible.


Coil L1 is wound using 20 s.w.g. enamelled copper wire and is self-supporting, being wound on an 8mm diameter temporary former such as the shank of a twist drill of appropriate size. This winding consists of precisely 3 turns and is 13mm long. It is left with short, vertical leadout wires which have the enamel insulation scraped off and must be tinned before the coil is soldered into position on the p.c.b., the same treatment being required for the tapping point.

The prototype was used with a telescopic aerial which plugged straight into the front of the converter with the tap at the centre of L1. If the unit is fed from an aerial via a length of coaxial cable, matching will be improved if the tap is placed a little under one turn up from the earthy end of the coil. Coil L3 is identical to L1 except it has no tapping.

A 6mm diameter coil former having a dust iron tuning slug is used for L2. The former is fixed to the p.c.b. using two 8BA bolts and nuts, with a solder tag secured under each mounting nut which act as anchor points for the ends of the winding, which consists of 10 turns of 20 s.w.g. enamelled copper wire, close wound with C1 wired across the two solder tags. The enamel is removed from the coil  $4\frac{1}{2}$  turns down from the positive supply rail end of the winding, this point being tinned and connected to C2. The ends of the winding connect to the p.c.b. conductors via the two mounting bolts.


The specified crystal is a wire-ended type which is soldered direct to the p.c.b., but be careful when soldering as excessive heat could damage the crystal or its mounting. The prototype is housed in an aluminium box which measures approximately 102 x 76 x 51mm. Any similar case should be suitable provided it is of all-metal construction.

The general layout of the front panel can be seen from the photograph. The p.c.b. is mounted on the rear panel of the case using three 6BA mounting bolts about 13mm long, spacers being used to hold the p.c.b. about 6mm clear of the rear panel. However, connect the p.c.b. to the front panel components before finally mounting it, and make sure that it is mounted in a position which does not obstruct S1 when the two parts of the case are fitted together, the battery fitting into the space below SK3.

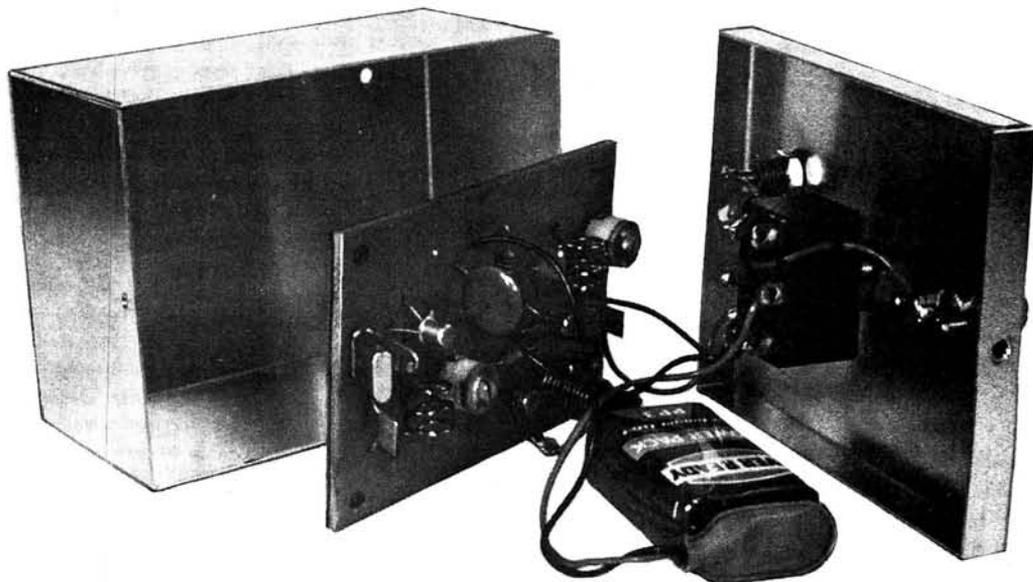


Internal view  
of the converter


# AMATEUR RADIO EXCHANGE

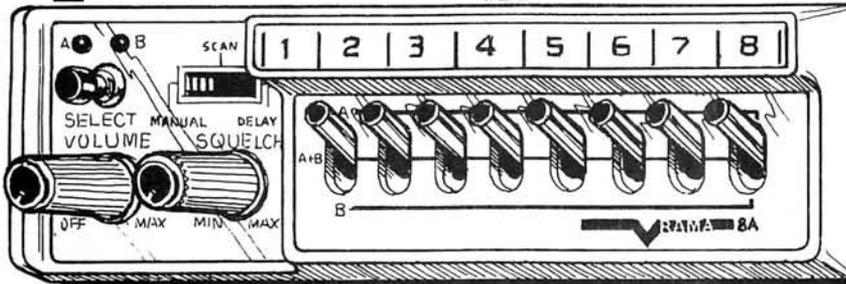


**A RAMA-8A  
AIR-BAND  
SCANNER**

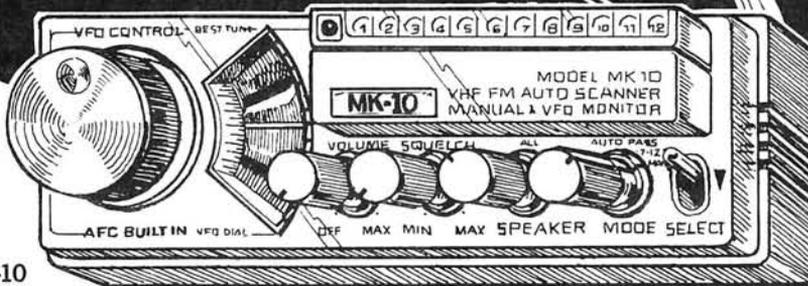

**B MK-10  
AMATEUR-BAND  
RECEIVER**

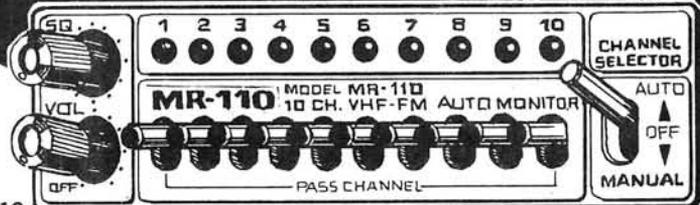

**C MR-110  
AMATEUR-BAND  
RECEIVER**

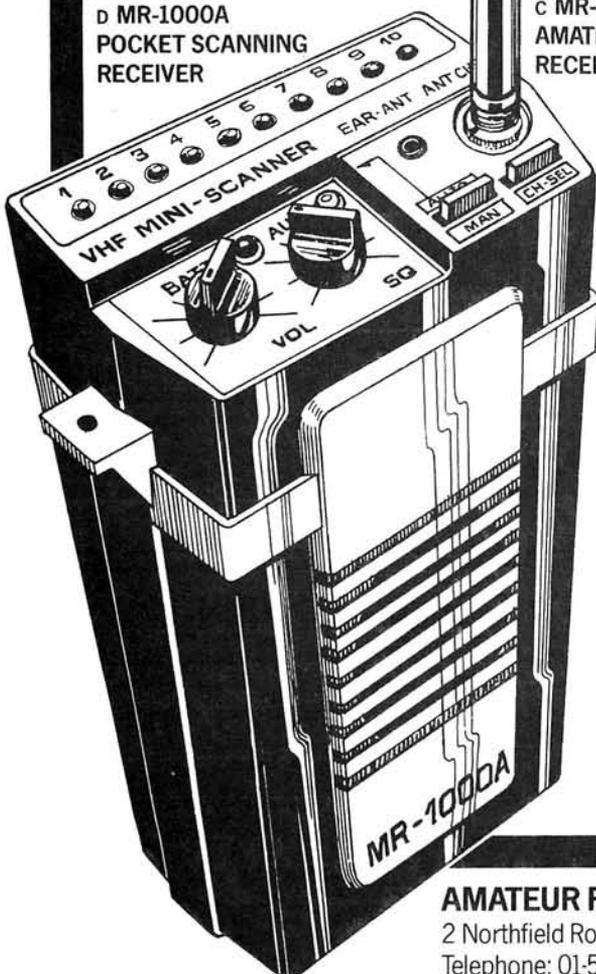

**D MR-1000A  
POCKET SCANNING  
RECEIVER**

## HERE...NOW...

A really competitive range of scanning receivers, all offering top-grade technical specifications and unbelievable value for money. Come and try them in the shop, or phone your orders and enquiries (24-hour answer service when we're closed).

**A RAMA-8A** 16-channel capability crystal-controlled air-band scanning receiver, covering 108–136 MHz. Choose 8 or 16-channel scanning, or manual operation. Sensitivity  $1\mu\text{v}$  (10 db S/N). 12v or mains. **BASIC PRICE £79.**

**B MK-10** VHF FM scanning receiver, covering 144–152 MHz. Scanning or manual tuning through up to 12 crystal-controlled frequencies, **OR** VFO control on main dial. Automatic lock-out facility. Sensitivity  $1\mu\text{v}$  (25 db S/N). 12v or mains. **BASIC PRICE £69.**

**C MR-110** VHF FM scanning receiver. 10-channel capability, with lock-out facility. Sensitivity  $0.8\mu\text{v}$  (20 db S/N). 12v only, ideal for mobile operation. **SPECIAL PRICE JUST £49 FITTED 5 CHANNELS EX-STOCK.**

**D MR-1000A** The finest-value pocket receiver ever offered. VHF FM scanner, 10 channels, and allowing scan or manual tuning across selected crystal-controlled channels. Complete with Nicads and charger. **BASIC PRICE ONLY £39.**

**CRYSTALS: £2 PER CHANNEL FOR ALL MODELS.  
ALL PRICES ARE POST-FREE AND INCLUDE VAT.**

**AMATEUR RADIO EXCHANGE,**  
2 Northfield Road, Ealing, London, W13 9SY.  
Telephone: 01-579 5311.

CREDIT CARD  
SALES BY  
TELEPHONE.



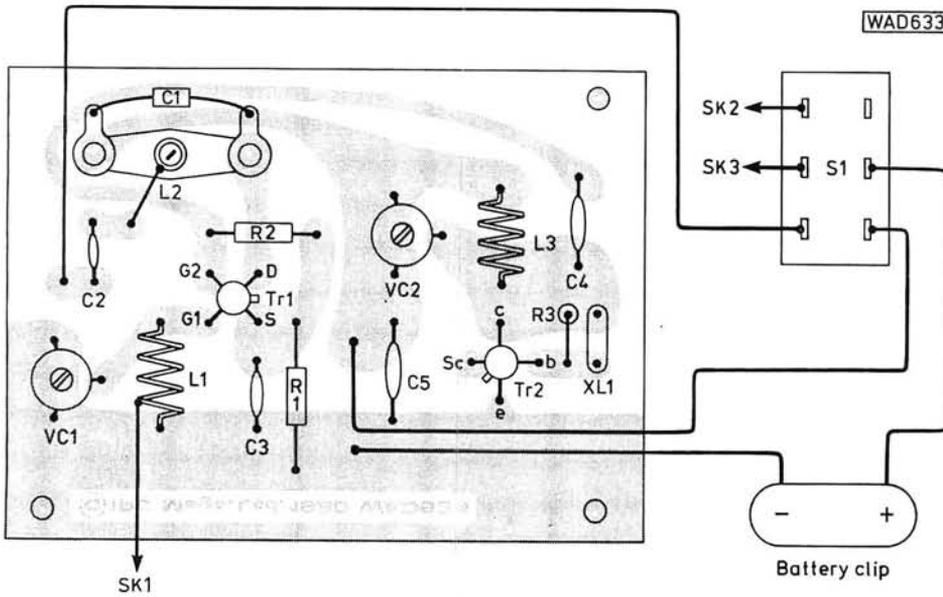
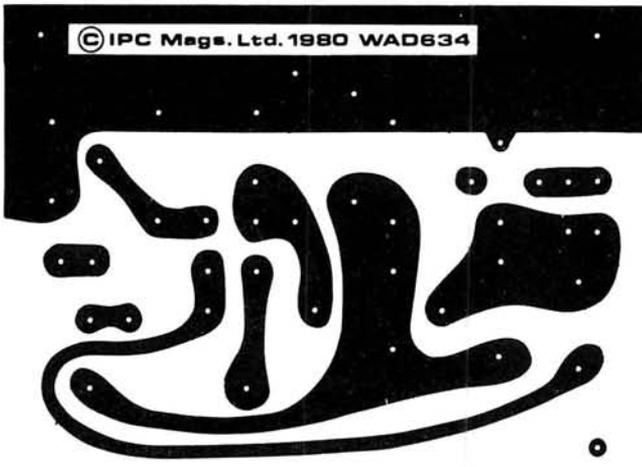


Fig. 2 (Top): The p.c.b. copper track pattern shown full size

Fig. 3 (Left): The component overlay on the p.c.b.

## ★ components

<b>Resistors</b>		<b>Semiconductors</b>	
$\frac{1}{4}$ W 5% carbon		MEM616	
82 $\Omega$	1 R1	or 40673	1 Tr1
150k $\Omega$	1 R3	BF180	1 Tr2
220k $\Omega$	1 R2		
<b>Capacitors</b>		<b>Sockets</b>	
<i>Ceramic</i>		Coaxial	2 SK1,3
3-3nF	1 C4	Wander type	1 SK2
10nF	2 C2,3		
100nF	1 C5	<b>Crystal</b>	
<i>Polystyrene</i>		116MHz	
39pF	1 C1	5th overtone	1 XL1 (see text)
<i>Ceramic Trimmers</i>		<b>Miscellaneous</b>	
4-20pF	1 VC1	Toggle switch d.p.d.t. (S1); 102 x 76 x 51mm aluminium box (1); 20 s.w.g. enamelled copper wire; 6mm coil former with dust core (1); printed circuit board (1); PP3 battery and connector (1).	
10-60pF	1 VC2		

# AMATEUR RADIO EXCHANGE



Brenda (G8SXY) and Bernie (G4AOG) invite you to the only shop in London where you can see and try all the leading makes of Amateur Radio Equipment under one roof . . . YAESU, ICOM, TRIO/KENWOOD, STANDARD . . . and have a cup of Brenda's coffee too! And in the shop NOW, waiting for you to compare it, is the very latest 2m All-mode Mobile . . . the fantastic new **YAESU FT-280/480.**



- Bright green fluorescent display
- Steps FM – 1KHz/12½ or 25KHz/100KHz; SSB and CW – 10Hz/100Hz/1KHz
- Step or scan control from mic
- Scan stops or pauses on signal
- Scans whole band or memories
- Auto tone-burst with repeater shift
- Listen on repeater shift selectable from mic
- Monitors priority channel and locks on when busy
- Digital clarifier plus or minus 10KHz
- Clarifier shift displayed
- LED S-meter true peak reading on SSB
- Semi break-in and sidetone on CW
- "Satellite" mode cancels all shifts and permits tuning during transmission

CLOSED WEDNESDAY, BUT USE OUR 24-HOUR ANSAFONE SERVICE

EASY TERMS UP TO 2 YEARS



CREDIT SALES BY TELEPHONE



INSTANT HP FOR LICENSED AMATEURS

2 NORTHFIELD ROAD, EALING, LONDON W13 9SY.

Tel: 01-579 5311

So easy for Overseas Visitors – Northfields Station is just seven stops from Heathrow on the Piccadilly Line – or phone your order and let us deliver it to you at the Airport.

## Complete Kit of Parts for P.W. NIMBUS

(if all parts purchased)

### TRANSCEIVER

(PCB & all components except channel xrals) **£46.00**

### MODULATOR

(PCB & all components) **£4.50**

### GENERAL ASSEMBLY

(Aerial, mike, box, speakers etc.) **£32.50**

### COMPLETE KIT

(if purchased complete) **£80.00**

## AND

Complete kit for Add-on Base Unit (as featured in June Issue) Price **£38.00.**

We also stock kits for projects published in most magazines.

Personal callers welcome – but please phone first to check availability.


(All prices include post and V.A.T.)

**T. POWELL** 306 St. Paul's Road, Highbury Corner, London N1. Telephone: 01-226 1489.

ACCESS/VISA ACCEPTED

Shop open: Mon. to Fri. 9-5.30. Sat. 9-4.30.

# IT'S AS EASY AS A,B,C...

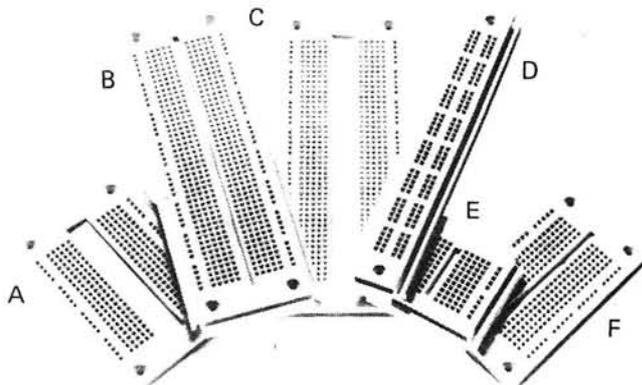

- A EXP 650 For microprocessor chips. **£3.60**
- B EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**
- C EXP 600.6" centre channel makes this the Microprocessor Breadboard. **£6.30**
- D EXP 4B An extra 4 bus-bars in one unit. **£2.30**
- E EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICs. **£1.60**
- F EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. **£3.15**
- G PB6 Professional breadboard in easily assembled kit form. **£9.20** (Not illustrated.)
- H PB 100 Kit form breadboard recommended for students and educational uses. **£11.80** (Not illustrated.)

## & IT'S AS EASY AS 1,2,3 with THE EXPERIMENTOR SYSTEM

SCRATCHBOARD  
-BREADBOARD  
-MATCHBOARD

1. EXP 300PC which includes one item. A matchboard pre-drilled PCB – **£1.32**
2. EXP 302 which includes three items. Three 50-sheet scratchboard workpads – **£1.68**
3. EXP 303 which includes three items. Two matchboards and an EXP 300 solderless breadboard – **£8.60.**
4. EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad – **£9.30**

The above prices do not include P&P and 15% VAT

## TOMORROW'S TOOLS TODAY

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited, Dept. 6H, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Tel: Saffron Walden (0799) 21682 Telex: 817477

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

I enclose cheque/PO for £ \_\_\_\_\_  
or debit my Barclaycard, Access, American Express card  
No. \_\_\_\_\_ Exp. date \_\_\_\_\_  
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

A EXP 650 £5.00	Qty. Reqd.	B EXP 300 £7.76	Qty. Reqd.
C EXP 600 £8.39	Qty. Reqd.	D EXP 4B £3.50	Qty. Reqd.
E EXP 325 £2.70	Qty. Reqd.	F EXP 350 £4.48	Qty. Reqd.
G PB6 £11.73	Qty. Reqd.	H PB 100 £14.72	Qty. Reqd.


### Experimenter System

1 EXP 300 PC £2.38	Qty. Reqd.	2 EXP 302 £2.79	Qty. Reqd.
3 EXP 303 £11.04	Qty. Reqd.	4 EXP 304 £11.85	Qty. Reqd.

Boxed prices include P & P and 15% VAT FREE catalogue tick box

Continental Specialties Corporation, (U.K.) Limited, Dept. 6H Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex. Tel: (0799) 21682
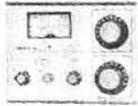
# SMC FOR YAESU MUSEN + STATION ACCESSORIES




## ANTENNA COUPLER

3.5-30MHz. 50/75 ohm Coax (VSWR<5:1) and Single Wire (10-250 ohms) transformed to 50 ohms. To 500W PIP SSB. Watmeter 20 & 250W FSD meter  
**LAC895** (p&p foc) **£105.80**


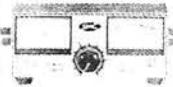
## DIGITAL MULTIMETER

1-10-100-1000 ACV-DCV-ACmA, DCmA, Ohms 10M ohm input impedance on AC & DC Automatic zero and polarity  
**ME52** (p&p free) New Low Price **£44.00**



## HF/VHF SWR METER

Twin Meter. 3.5 to 170MHz Calibrated to 3:1 SWR. 50 ohms Relative Power. SO239 sockets  
**T3-170L** (p&p £0.60) **£12.90**



## MULTIMETERS

(p&p free of charge)  
20K ohms per volt. 1000X overload on ohms Plug in range selection.  
**80** Microtest 40 Ranges **£19.00**  
**680G** Supertest 48 Ranges **£28.15**  
**680R** Supertest 80 Ranges **£36.80**



## WATT METERS

Through line, 1.8-54MHz, SWR scale.  
**LPM885** 20, 200, 1000W FSD (p&p foc) **£58.65**  
Absorption 1.8-500MHz  
**LPM880** 5, 2, 120W FSD (p&p foc) **£90.85**



## HF BALUN TRANSFORMER

1:1 Ratio. 3-40MHz. SO239 (UHF) Socket 5 1/2" x 1 1/2" D. 7 1/2ozs. "Hang up type" High power handling  
**H1Q** (Post free of charge) **£10.00**



## QUARTZ CRYSTALS

(p&p £0.30)  
2m FM Tx: 6, 12, 18MHz Range  
2m FM Rx: (10.7MHz), 14.44, 52MHz Range  
Convertors: (28MHz), 22(6m), 38.66(2m), 50.5 (70cm) **£2.50** each, **£4.60** pair.  
Phone for details  
Spares - Standard units for Yaesu etc P.O.A.



## VHF MONITOR RECEIVERS

12 Chan. FM Monitor. 2 1/2 x 1 1/2 x 4 1/2" 8ozs. 12KHz BW. 130-170MHz  
**HF12** c/w Accessories **£57.50**  
**HF12A12** c/w S(20,23),R(0-7) **£80.50**  
**HF12M9** c/w 16,6,8,10,67,M,12,14 **£77.00**




## DIGITAL FREQUENCY COUNTER

100KHz to 30MHz. 12V DC operation 5.7 segment displays resolves to 10Hz only 6 1/2 x 2 1/2 x 5 1/2"  
**R175D** (p&p free) New Low Price **£44.00**


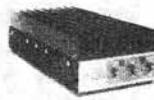
## ANTENNA ROTATORS

(carriage free)  
**AR40** Silent self-calibrating control box to 3sq ft ant wind area **£59.80**  
**BT1** 4 pre set plus manual control to 5 sq ft ant wind area **£90.85**  
Continuous readout on large meter Superior brake mechanism  
**CD45** to 8 1/2 sq ft ant wind area **£113.85**  
**HAM IV** to 15sq ft ant wind area **£166.75**  
**T2X** to 30sq ft ant wind area **£228.85**



## V.H.F. LINEAR AMPLIFIER

80W out for 10W nom drive. 145MHz 12V DC (circa 10A). Switchable; SSB/FM Hang time. RF or man cont. Low noise pre-amp.  
**RC1** Remote control (p&p £0.40) **£17.25**  
**B108** Amplifier (p&p foc) **£113.85**



## V.H.F. LINEAR AMPLIFIER

160W out for 15W maximum drive. 145MHz. 12V dc (circa 18A). RF or manual switching. SSB/FM Excellent heat sink - over temp, trip out/reset.  
**PA 15-160BL** (Post free) **£205.25**



## UHF COAX PLUGS

Post and Packing £0.25 any quantity  
**PL259** Plug **£0.55** **SO239** Socket **£0.48**  
**UG175/U** Reducer **£0.14** **PL258** back/back **£0.90**  
**SO239F** Socket **£0.48** **M359** Elbow **£1.07**




## VHF AND UHF CONVERTORS

50ohm. 9-12V. BNC (p&p free)  
**MMC-28-70-144/IF** **£21.85**  
**MMC-70-144/IF/LO** **£24.15**  
**MMC-432/IF/S** **£29.90**  
**MMC-1296/IF** **£29.90**



## DIP OSCILLATOR

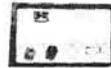1.5-250MHz on fundamental. c/w earphone, battery, 6 plug in coils 1-15MHz crystal test. 2KHz modulation  
**LDM815** (P&P free of charge) **£51.75**



## POWER SUPPLY

12V dc regulated supply. 240V 50/60Hz input 3 Amps cont. 5 Amp peak 3 x 4 1/4 x 6". 3 1/2 lbs  
**ODR123C** (Post free) **£15.50**



## QUARTZ/CERAMIC FILTERS

(p&p £0.30)  
QUARTZ - 3, 18, 9, 10.7MHz Centre frequencies - 350Hz, 600Hz, 2.4KHz, 6KHz, 12KHz, - 20KHz  
CERAMIC - 455KHz (9 and 11 elements) - 2KHz, 4KHz, 6KHz, 12KHz  
Prices; Ceramic **£5-£11** Crystal **£18-£25**



## FM BOOSTER

88-108MHz. (FM BAND 11) pre-amp. Low noise Typ 4.5dB. up to 20dB gain Fitted flying leads (car plugs) 12 volts. LED indicator. 1 1/4 x 3 1/2 x 2 1/4"  
**T203** (p&p free of charge) **£8.90**



## COAX SLIDE SWITCHES

50 ohms impedance SO239 sockets  
**TWS150** 1 in 5 out (p&p £0.30) **£12.10**  
**TWS220** 2 in 4 out (p&p £0.30) **£12.50**



## COAXIAL RELAYS

(p&p free of charge)  
500 series 12VDC. 50ohms. 1KW PEP at 30MHz 50dB isolation at 1 GHz. 0.2dB loss at 0.5GHz.  
**CX540D** 3BNC Sockets **£21.25**  
**CX530D** 3 BNC + 1 'N' **£21.25**  
**CX520D** 3 'N' Sockets **£21.25**  
**CX120A** 50W Cable entry **£10.70**  
**CX120P** 50W Pin connection P/C type **£10.70**



## NEW FIVE BAND HF VERTICAL ANTENNA

SMCHF5. 80,40,20,15,10 metres. 500W PEP 10-20M, 200W 40-80M, 50 ohm coax feed. With/without radials, or use trapped radial kit. Securior Delivery on either or both together £3.00.  
**SMCHF5V** Vertical 2.9Kg about 15 1/2" **£40.25**  
**SMCHF5R** Radial kit 1.8Kg circa 6" **£26.85**

ALL PRICES INCLUDE VAT @ 15%



# SOUTH MIDLANDS COMMUNICATIONS LIMITED

S. M. HOUSE, OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND  
Tel: Totton (0703) 867333, Telex: 477351 SMCOMM G, Telegram: "Aerial" Southampton

## S.M.C. (Jack Tweedy) LTD

Roger Baines, G3YBO  
79 Chatsworth Road,  
Chesterfield, Derbyshire  
Chesterfield (0246) 34982  
9-6: Tuesday-Saturday

## NORTHERN (Leeds) BRANCH

Colin Thomas, G3PSM  
257 Otley Road,  
Leeds 16, Yorkshire.  
Leeds (0532) 782326  
9-5: Mon-Wed & Fri-Sat.

## S.M.C. (Jack Tweedy) LTD

Jack Tweedy, G 3ZY  
150 Horncastle Road,  
Woodhall Spa, Lincolnshire  
Woodhall Spa (0526) 52793  
9-5: Tuesday-Sat (- appointments)



G3ZUL Brian  
GW4GSW Alan

Stourbridge (03843) 5917  
Swansea (0792) 24140

GW3TMP Howarth Pontybockin (035287) 846/324  
GI3KDR John Bangor (0247) 55162

GM8GEC Jack Edinburgh (031665) 2420  
GI3WWY Mervyn Tandragee (0762) 84056

## Alignment

The first step in the alignment procedure is to adjust VC2 to obtain maximum output from the oscillator. If a multimeter set to read 5mA f.s.d. is connected in series with the positive battery lead, VC2 should be adjusted for minimum meter reading which will correspond to maximum oscillator output and give optimum sensitivity. Make sure that this adjustment is done accurately, because if VC2 is maladjusted in the decreased capacitance direction, the oscillator may become unreliable and not always start when the unit is switched on.

Next the core of L2 is adjusted, and this may be easily set for maximum noise output from the receiver which should be tuned to about 29MHz while this adjustment is made.

Assuming a suitable signal generator is not available, VC1 is most easily adjusted by locating a 2-metre transmission and then simply adjusting it for maximum signal strength. If a suitable signal cannot be found, try VC1 at various settings until such a signal is located. Most areas of the country are now served by a repeater, the output from which occupies the high frequency end of the band and provides a suitable tune-up signal.

Note that although the front panel must be detached from the rest of the case while VC1 and L2 are adjusted, the two sections of the case should be maintained in electrical contact, achieved by holding the two parts together while these adjustments are made. The lead between the converter output and the receiver aerial socket must be made by coaxial cable, the outer braiding connected to the

chassis of the converter and the receiver in order to prevent breakthrough of signals on the 10-metre band and must be kept as short as possible.

## Operation

In conjunction with a Trio-Kenwood QR666 receiver the prototype provided excellent results when used in a first-floor room with a telescopic aerial plugged into SK1. This type of aerial should be about 47 inches long for the 2-metre band. Most stations use vertical polarisation and will be received most strongly with the aerial in a vertical position. Some stations, particularly those operating s.s.b. at the low frequency end of the band, use horizontal polarisation, and will be best received with the aerial horizontal and rotated for maximum signal strength. Of course, it is possible to use a more sophisticated aerial system giving a corresponding improvement in results, and suitable designs will be found in "Out of Thin Air", see page 69.

It should perhaps be pointed out that a.m., c.w. and s.s.b. modes are all used on the 2-metre band and can all be received providing the main receiver is equipped to resolve these signals. The most popular form of transmission is f.m. and unless the receiver is fitted with a suitable detector, can best be resolved by switching the receiver to the a.m. mode and slightly offsetting the tuning from the usual maximum signal strength position. This is known as slope detection, usually giving quite good results, and if the receiver has variable selectivity it will almost certainly be best to use the widest available bandwidth. ●

## μA78S40 SWITCHING REGULATOR

▶▶▶ continued from page 42

can be easily accommodated on the RM6 bobbin is about 0.5mm, whereas the RM10 bobbin can accommodate wire of about 0.9mm diameter and should be selected in circuits which may be required to deliver a relatively high output current (above 0.3A).

At lower output currents either type of core is satisfactory, but the RM10 can be wound to have a lower series resistance and this will result in a higher power efficiency.

The μA78S40 is a very versatile switching regulator sub-system which can be used in a wide variety of circuits providing much higher power efficiency than the usual series regulator devices. However, switching regulator circuits do have their disadvantages; in particular, circuits of this type are more complex than simple series regulator circuits and require the use of an inductor. In addition, the circuits generate a switching waveform which, together with its harmonics, can cause radio interference. A further disadvantage is the relatively slow response of a switching regulator to a fast change in the load conditions when compared with a simple series regulator circuit.

In order to minimise electro-magnetic interference, it is important that the output reservoir capacitor ( $C_O$ ) should be placed close to the μA78S40 device and that all wiring should be kept short. In general, it is wise to decouple the input voltage supply with a capacitor soldered directly between pins 13 and 11 (the positive and negative supplies).

The μA78S40 is available from Arrow Electronics Ltd., Leader House, Coptfold Road, Brentwood, Essex CM14 4BN together with RM6 and RM10 cores with the required 250nH inductance factor. ●

## INTRODUCING RTTY

▶▶▶ continued from page 52

particularly on 80m and 20m, will almost always produce the rhythmic "jingle bells" of RTTY (using 170Hz shift and 45.45 baud). The BARTG (British Amateur Radio Teleprinter Group) transmits RTTY news bulletins on 80m on Sunday mornings. An RTTY repeater (GB3PT) transmits on channel RB12 (433.30MHz) from Barkway in Hertfordshire. A German amateur, DL1WX, operates a "store and forward" type of RTTY repeater around 14.075MHz.


Readers interested in copying commercial RTTY transmissions are warned that neither the Broadcast Receiving Licence nor the UK Amateur Licence permit the reception of such signals (a number of successful prosecutions have been brought in the last couple of years). However the Home Office Radio Regulatory Department have indicated that permission can be granted for reception of commercial short-wave RTTY, provided permission is previously obtained from the various press agencies. Interested readers should write to the Home Office at Waterloo Bridge House, Waterloo Bridge Road, London SE1 8UA.

**Part 2 of this series deals with  
RTTY demodulator circuits**

# air test

## USER REPORTS ON SETS AND SUNDRIES

### DATONG UC/1 Up-converter

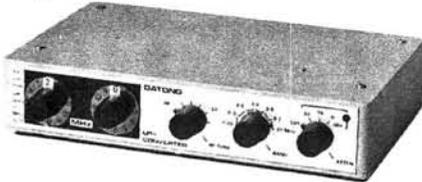

Using a converter is an easy and economical way of adding coverage of an additional band or bands to an existing receiver. Probably the most popular example is a unit converting the 2-metre amateur band down to a frequency covered by an h.f. bands receiver, typically 28–30MHz. If this is done by mixing the 2m signal with the output of a local oscillator running at 116MHz, then 28MHz corresponds to 144MHz, and 30MHz to 146MHz. Other mixing methods could be used, but these could well result in the band being inverted, so that mental arithmetic would be required each time the h.f. receiver was retuned.

A simple constructional design for such a converter appears elsewhere in this issue, but in the Datong UC/1 the same idea is taken and developed to produce a system capable of several different conversions.

The basic unit converts up in frequency any selected 1MHz band in the range 0–30MHz, so that it can be tuned on a 2m receiver covering 144–145MHz. At the same time, a built-in down-converter reconverts the band of frequencies down to the 28–29MHz range, where it can be tuned on receivers designed for the 10m amateur band. It thus gives general coverage of the l.f., m.f. and h.f. bands on a 2m or h.f. amateur bands receiver.

The down-converter is also accessible for use as a conventional 2m converter, as described at the beginning of this article.

When in the up-converter mode, the megahertz portion of the desired frequency is selected digitally by means of two switches on the UC/1, and the kilohertz portion on the tuning scale of the associated receiver. The UC/1

preselector tuned circuits are then peaked by means of a "Band" switch and an "RF Tune" control. A three-position input attenuator (0, 15 and 30dB) is also provided.

The preselector limits the lowest band to frequencies above 90kHz, though reception at reduced sensitivity is possible down to 60kHz (Rugby MSF). Sensitivity is specified at 0.3µV from 0.8–30MHz, 0.6µV from 300–800kHz, 1.2µV from 90–300kHz, and 0.3µV from 144–146MHz, all for 10dB S/N (c.w. or s.s.b. in 2.4kHz bandwidth).

Internally generated spurious occur at harmonics of 1MHz, due to the crystal oscillator, and are typically equivalent to an input signal of 4µV p.d. External spurious responses are typically 60dB below the main response. Input and output impedances are all 50Ω nominal, and the unit is designed to withstand the accidental short-term application of 10W of r.f. to either output terminal.

Power requirements are 120mA at 11.5–13V d.c. The unit measures 272 × 60 × 203mm overall, and weighs 1.75kg.

### Results

Tests of all the modes of operation were carried out in conjunction with the Sugiyama F850, reviewed elsewhere in this issue. The 2m converter was also checked using an FRG-7.


In any converter, and especially one so complex as the UC/1, possible spurious responses, both internal and external, are always one of the fears. Time and facilities did not allow us to carry out any checks with instruments, but listening tests revealed no obvious "nasties", other than the 1MHz crystal harmonics.

The input attenuator is very useful, and at times essential, when converting from h.f. or v.h.f. to 28MHz, to avoid overloading the associated receiver. The UC/1 is specified to have a gain of some 15dB in these modes, whereas the gain when converting up to 144MHz is around 2dB. The "RF Tune" control is very critical to adjust

at l.f. and m.f., and would benefit from the addition of a slow-motion drive.

One feature of the unit that would be of great interest to the broadcast bands DX enthusiast is its fantastic performance on the medium and long wave bands. On the latter, using a 60ft long wire, and up-converting to 28MHz into F850, it outperformed any receiver I've ever heard, in terms of sensitivity and selectivity.

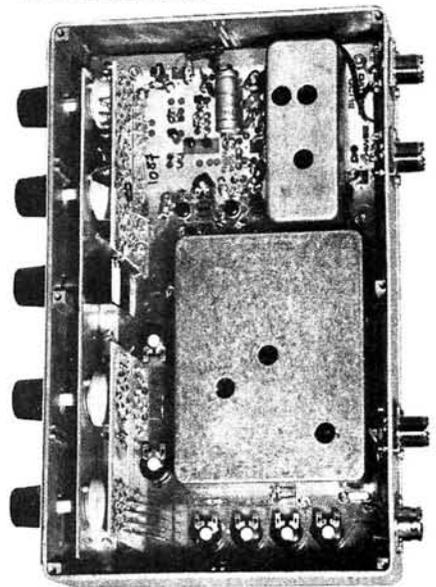The UC/1 costs £136.85, including carriage and VAT, from **Datong Electronics Limited, Spence Mills, Mill Lane, Bramley, Leeds LS13 3HE, telephone Leeds (0532) 552461**, to whom we offer our thanks for the loan of the review unit.



### TRIO TR-2400 Transceiver

The hand-held v.h.f. f.m. transceivers are not only getting smaller in size, they are also improving in performance and the facilities being offered are now rivalling the larger mobile rigs. The Trio TR-2400 is amazing for its size.

It is a fully synthesised transceiver offering 400 channels between 144–145.995MHz together with ten memories and scanning facilities. Repeater shift is built-in together with a tone-burst unit to make repeater operation as simple as possible.



Frequency readout is by four digit l.c.d. with the two lefthand digits of the frequency not shown. Selection of the channel required is by a calculator style keyboard and extra switches provide locks against accidental frequency shift and inadvertent operation of the p.t.t. switch. The other controls, together with the 50Ω b.n.c. aerial socket are on the top of the case.

Rechargeable NiCad batteries are used to power the TR-2400 and these are carried in a compartment at the bottom of the case. Trio reckon that a

fully charged battery pack will provide about 2½ hours of operation based on one minute of transmission followed by three minutes' reception.

The transmission puts out 1.5W of r.f. power and in use this proved just enough to get into GB3SC from some 15 miles away on a very cold night, using the "rubber duck" aerial supplied.


In use the rig proved to be easy to use and fairly comfortable to hold. The l.c.d. readout was easy to read and a backlight enabled it to be read in the dark. However for night time operation it would be advisable to carry a small torch to enable the keyboard controls to be identified.

The only annoying feature was the p.t.t. switch. This took the form of a microswitch operated by a large push-bar on the side of the case. The switch gave very little indication that it had been satisfactorily operated, and a much more positive click action would have been better.

Performance seemed to be good and the construction of the rig was also very good.

The ten memories are useful if you have a choice of repeater and work a lot of simplex as well.

The TR-2400 costs £210.45 inc. VAT.

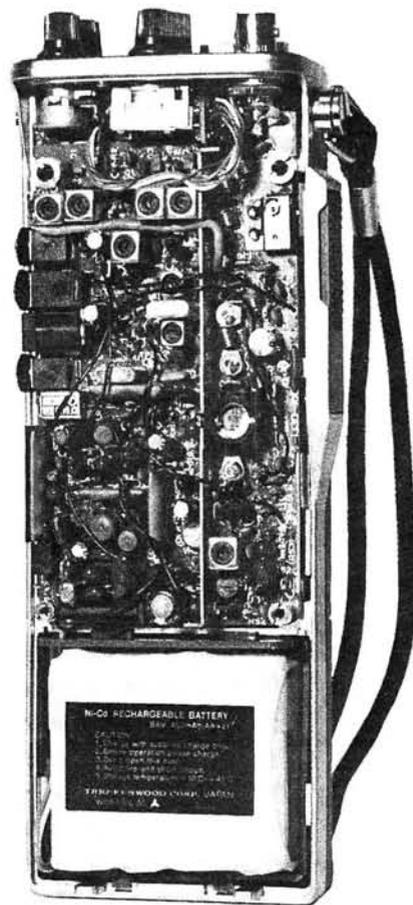

## SUGIYAMA F850


AN all band (160 to 2m including 4m) all mode transceiver, with a specification to suit the most discerning operator.

LIST PRICE:

Fitted 2.4 KHz filter £799.00 inc VAT

Fitted ALL filters £899.00 inc VAT

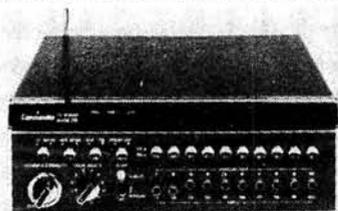432 MHz Transverter (ordered with F850) £100.00 inc VAT



## FM SCANNING MONITORS

318 — Three Band Monitor — allows 20 Channels in 430-470 MHz, 140-175 MHz and 68-88 MHz ranges to be scanned in user programmable order. Mains or battery operation. Vehicle mount supplied. PRICE: £95.00 inc. VAT. Carriage extra on above prices.

Pocket Model — 008 covers 8 Channels in 2m or marine bands. Lockout on all channels. Wide range of accessories supplied PRICE: £59.00 inc. VAT.

Stock Crystals: S20, 21, 22, 23 — RO to 7 — SU 8 and 20 — RBO, 2, 4, 6, 10, 14 — MO, 6, 10, 16. PRICE: £3.00 each inc. VAT.

★  
See the  
SUGIYAMA  
Review in  
This Issue

# Zycomm Electronics Ltd.

G3ZYC G8CNB G3NJK G3ZYD

47/51 Pentrich Rd., Ripley, Derby DE5 3DS Tel Ripley (0773) 44281 Telex 377466

## ZYCOMM Z5800 Hand Portable

A no nonsense synthesised rig free of gimmicks. Covers 144-148 MHz in 5 KHz steps. Simplex or Repeater Operation — High/low power (over 5 watts from internal NiCd pack). PRICE £199.00 inc VAT c/w Desk Charger and Remote Microphone.



## Ci-110 Mk2 POWER AMP

A Solid State, all modes unit covering 1.7 to 38 MHz. Typical power output 130 Watts for 215 watts DC input and 4-7 watts drive (15 watts SSB). RF sensing VOX circuit. Switchable receive pre-amp. Supply requirements: 13.8V at 20A, Negative Earth. Size: 5" w x 7" l x 3" h Weight: 2.5 lbs

PRICE: £95.00 inc VAT

Full range of amateur and commercial antennas and Home Office approved two way radio equipment. SAE for details.



# NIMBUS

## Modular 2m Transceiver System

## Timeburst and Timer Module

### (Part 6)


**Michael TOOLEY BA G8CKT  
&  
David WHITFIELD BA MSc G8FTB**

The module described in this article can be a boon to any serious repeater user and, although designed for use with the *PW* "Nimbus", it can readily be incorporated into almost any v.h.f. f.m. transceiver. The module provides a toneburst for operating a transceiver in conjunction with any 2-metre f.m. repeater in the UK, and also accurately times the transmission, providing both visible and audible warnings at the end of a pre-determined period when the user is about to "time-out" through the repeater. The module is simple to construct and uses readily available components. A full range of adjustments allows the builder to satisfy his own requirements as to time duration, etc.
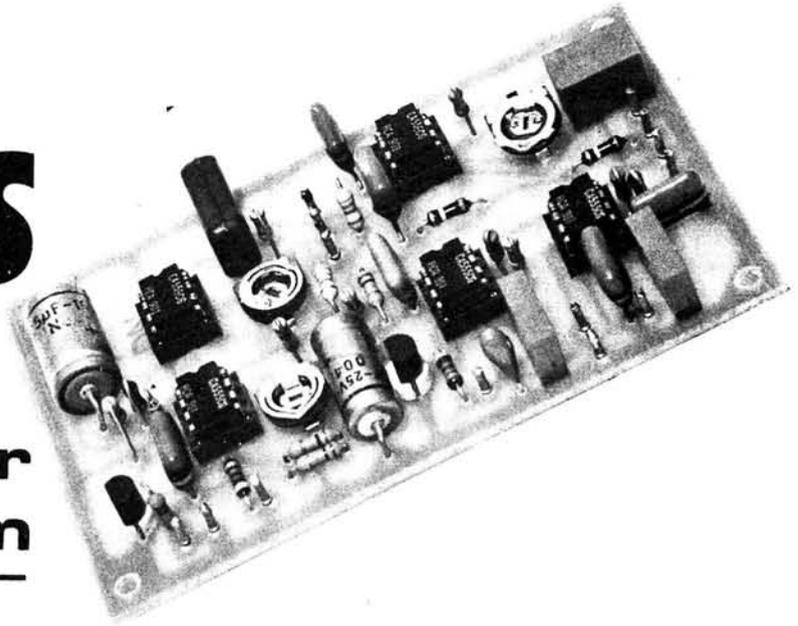
### FM Repeaters

In recent years, one of the major growth areas in amateur radio has been on the repeater front, the number of v.h.f. repeaters in the UK having increased very considerably. In 1974 there were three 2-metre repeaters in operation, in 1976 there were 12 and in 1978 there were 23. Today there are some 37 repeaters operational on 2m, with still more in the pipeline. With such a large number of active repeaters, coverage of the UK is almost complete, the few remaining gaps tending to be in the more remote areas, such as the far north of Scotland. In many of the more populated regions there is even a choice of repeater. London, for example, is well served by four "machines": GB3SL in the south, GB3WL in the west, GB3NL in the north and GB3EL in east London.

Repeaters are primarily intended for mobile and portable use. As such they offer greatly enhanced coverage,




extending the range of a mobile-to-mobile contact from typically 10 miles "direct" to as much as 50 miles via a repeater. Repeaters are usually situated in the most favourable of locations. GB3SL, for example, is sited at the BBC transmitting station at Crystal Palace. Indeed, the repeater is housed in the same building and shares the same aerial mast as the BBC transmitter. Repeaters are built and financed by local groups. The repeater network as a whole is, however, co-ordinated by the Radio Society of Great Britain who, incidentally, are also the licence holders of all of the individual repeaters.

In the UK eight 2-metre channel pairs have been designated specifically for repeater usage. The "input" and "output" frequencies of each pair are spaced by 600kHz and the channels are designated "R0" to "R7", as shown in Table 1. Adjacent channels are spaced by 25kHz and frequencies are allocated on a geographical basis in order to minimise interference. As an example repeaters in West Wales (GB3WW), Aberdeen (GB3GN), Burnley (GB3RF), Tyrone (GB3WT), and North London (GB3NL) all operate on channel "R7". Only under the most exceptional of circumstances are there any problems of overlapping coverage.

The "heart" (or perhaps we should say "brain"! ) of any repeater is its control system. There are, of course, considerable variations in the control systems employed in UK repeaters, since each local group designs its own. However, to ensure compatibility, some common standards have become established. The most important of these is the frequency and duration of the tone signal which is required in order to gain "access" to a repeater. The tone frequency should be 1750Hz (plus or minus 10Hz or so), and its duration should be approximately 500ms. The burst of tone should, of course, occur at the start of the transmission (i.e., as soon as the press-to-talk switch is operated). The tone is detected in the repeater's control system (see Fig. 1), and is used both to reset the timer and also to activate the transmit relay and thus permit "talk-through".

Having sent the necessary tone, the operator is then free to continue with "talk-through" for a period determined by the setting of the timer in the repeater's control system. This is usually set at around 60 seconds after which the repeater will normally either give its call sign and close down or indicate "time-out" whilst at the same time

**Fig. 1: Block diagram of a 2 metre repeater station**

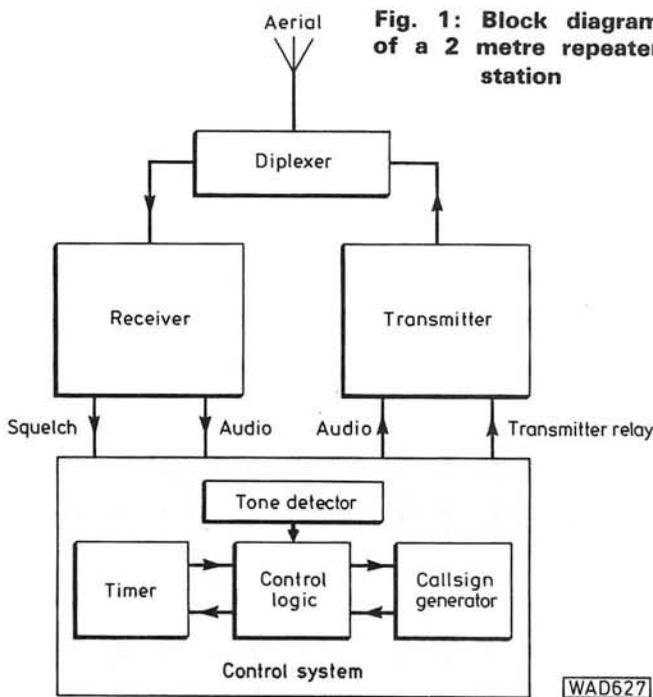


providing for the maximum number of users. Some repeaters do not have a "time-out" limit.

## System Description

The general arrangement of the combined toneburst and timer module is shown in the block schematic of Fig. 2. The toneburst and timer sections are, in fact, quite separate and, should the timing facility not be required, the basic toneburst module may be constructed separately. The input to both the toneburst and the timer is derived from the p.t.t. rail in the transceiver. At the commencement of any transmission, the p.t.t. rail is connected to 0V and stays at 0V for the duration of the transmitting period (see Fig. 3). At the end of a transmission the p.t.t. rail rises again to almost the full value of the positive supply. The negative-going (falling) edge of the p.t.t. voltage which occurs at the start of any period of transmission is used to trigger a monostable with a period of approximately 500ms. The output of this monostable is used to enable an astable oscillator which, as a consequence, provides a 500ms burst of 1750Hz tone at the start of every transmission.

The negative-going edge of the p.t.t. voltage is also used to initiate a monostable with a period of approximately 45 seconds (adjustable to suit the individual user's needs). The monostable output is "high" during the nominal 45s period and a green l.e.d. is used to indicate that normal talk-through may proceed. At the end of the 45s period the monostable output falls (see Fig. 3) and the l.e.d. is extinguished. Furthermore, if the p.t.t. rail is still at 0V (indicating that the transmission is still continuing) a NOR gate is used to set an astable oscillator which has a period of approximately 2s. A red l.e.d. is used to indicate the output state of this astable and, should the period of transmission exceed 45s, this l.e.d. flashes on and off thus providing a visual indication of the fact that "time-out" is about to occur. A further astable oscillator is incorporated in order to provide an audible warning. This astable is set by the output of the previous astable and provides a series of 1s bursts of 1.4kHz tone from the loudspeaker fitted in the transceiver.

inhibiting the "talk-through" audio. The unfortunate operator who continues talking after "time-out" will then only be talking to himself and, furthermore, the repeater will normally not be usable by others until the input frequency becomes clear again. Long-winded "overs" are thus actively discouraged and users are forced to keep it short. Furthermore, regular breaks in transmissions allow others to "break-in" or call others who may be listening on the repeater channel. If a user does wish to talk for more than one minute it is merely necessary for him to momentarily cease transmission, allow the repeater to send an acknowledgment (often given in the form of a "K" (-.-) or "T" (-) in Morse code) and then re-access for another minute's worth. The system may, at first, sound complex but it has proved to be relatively fool-proof whilst

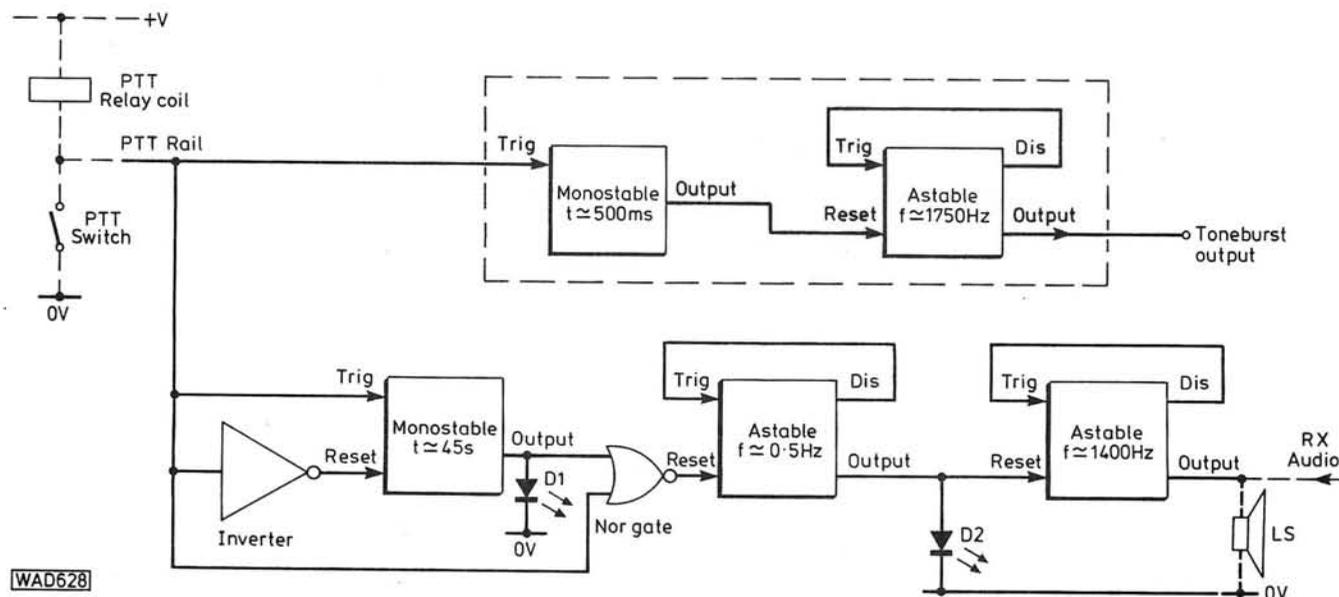

**Fig. 2: Block diagram of the PW "Nimbus" Toneburst and Timer module**

## The 555 Timer

Both the toneburst and the timer circuits make use of the ubiquitous 555 timer i.c., the simplified block diagram of which is shown in Fig. 4. The i.c. can be used in either a monostable or an astable configuration depending upon the external circuitry. The 555 contains two operational amplifiers (both employed as voltage comparators) connected to the "set" and "reset" inputs of a bistable. The inverting input of one operational amplifier and the non-inverting input of the other are supplied from a voltage reference potential divider. An output stage capable of delivering up to 200mA into a non-inductive load buffers the bistable output from the i.c. output at pin 3. A transistor stage is also incorporated and this operates as a saturated switch for the discharge of an external timing capacitor.

In the monostable mode, the trigger input (pin 2) is held at, or near,  $+V_{cc}$  in the quiescent state. The bistable is thus held in the "reset" condition with the  $\bar{Q}$  output at  $+V_{cc}$  which in turn ensures that the transistor is saturated and effectively short-circuiting the timing capacitor C, so inhibiting charge. If a negative-going pulse of sufficient amplitude is applied to the trigger input, the bistable becomes "set" and its output changes state, with the voltage at the  $\bar{Q}$  output falling to zero. The transistor then turns off, allowing the timing capacitor to charge through the series resistor, R. The voltage across the timing capacitor will then rise exponentially to  $\frac{2}{3}V_{cc}$  at which potential the output of the upper operational amplifier will change state resetting the bistable again. This ends the monostable timing period, the time interval for which the output at pin 3 is high after the application of the trigger pulse being given by:

$$t = 1.1 CR$$

In the astable mode, the trigger input pin 2 is connected to pin 6 and an extra resistor is inserted between pin 6 and pin 7. The "reset" input is held at, or near,  $+V_{cc}$  and, as soon as the supply is connected, the timing capacitor (connected at pin 6) starts to charge exponentially. When the capacitor voltage reaches  $\frac{2}{3}V_{cc}$  the initial monostable action ceases and the transistor conducts. The timing capacitor now discharges exponentially through the resistor connected between pins 6 and 7 until the voltage at pin 6 falls to  $\frac{1}{3}V_{cc}$  whereupon the trigger voltage initiates another monostable period. The cycle then repeats itself and the output voltage at pin 3 takes on a square waveform which has a frequency inversely proportional to the CR time constant.

## Circuit Description

The circuit of the basic toneburst module is shown in the top half of Fig. 5. When the transceiver is switched from "receive" to "transmit" the p.t.t. rail voltage falls from approximately 12V to 0V. C1, D1 and R3 produce a short-duration, negative-going pulse from this transition and this triggers the monostable, IC1. The monostable pulse duration is determined by the time constant  $(R5 + VR1) C2$ , and this pulse is used to enable IC2 which is connected in astable mode. The frequency of the astable is set by VR2 and C6, while R7, R8, C4 and R9 provide attenuation and shaping of the output waveform. Since it would be impossible to make any adjustment to VR2 during the 500ms toneburst period, a link, LKB (shown dotted), is incorporated in order to permit continuous operation of the astable oscillator.

## ★ components

### TONEBURST/TIMER MODULE

#### Resistors

$\frac{1}{4}W$  5% carbon

470 $\Omega$	2	R11,16
2.2k $\Omega$	1	R3
3.3k $\Omega$	4	R2,4,6,15
10k $\Omega$	7	R1,8,10,12,13,17,19
100k $\Omega$	3	R7,9,20
220k $\Omega$	2	R5,14
330k $\Omega$	1	R18

#### Potentiometers

Min. preset (horizontal mounting) 0.1W

100k $\Omega$	1	VR2
1M $\Omega$	2	VR1,3

#### Capacitors

Polyester

10nF	2	C6,12
22nF	1	C4
100nF	7	C1,3,5,8,10,11,13
1 $\mu$ F	1	C2

25V Tantalum bead

4.7 $\mu$ F	1	C9
-------------	---	----

25V Electrolytic (tubular)

47 $\mu$ F	1	C7
100 $\mu$ F	1	C14

#### Semiconductors

Transistors

BC548	2	Tr1,2
-------	---	-------

Integrated circuits

555	5	IC1-5
-----	---	-------

Diodes

1N4148	1	D1
--------	---	----

Light-emitting diodes

0.2in green	1	D2
0.2in red	1	D3

#### Miscellaneous

Printed circuit board, p.c.b. pins (12 off)

The circuitry in the bottom half of Fig. 5 provides the timing and warning functions. IC3 is connected in monostable configuration with its period governed by the time constant  $(R14 + VR3) C7$ . When the transceiver is on "receive", the p.t.t. rail is "high" and Tr1 operates as an inverter holding IC3 in the reset condition. When the transition is made from "receive" to "transmit", the p.t.t. rail voltage falls, Tr1 ceases to conduct and IC3 is set and triggered by the negative-going pulse formed by C1, R3 and D1. At the end of the time-out period the output of IC3 falls to 0V.

A warning indication is initiated when the collector of Tr2 goes "high". This only occurs when the output from IC3 has fallen to 0V (at the end of the time-out period) and, at the same time, the p.t.t. rail is still at 0V (indicating that the transceiver is still on "transmit"). IC4 then operates as an astable with a fixed frequency determined



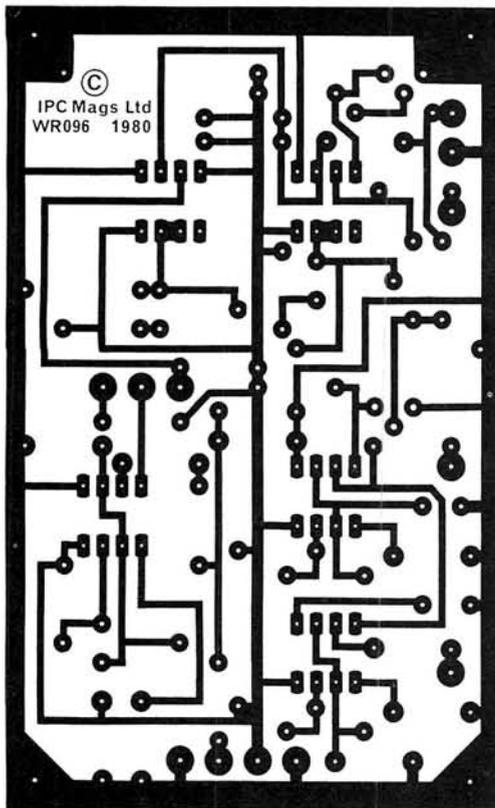


Fig. 6: Track pattern for the p.c.b., shown full size

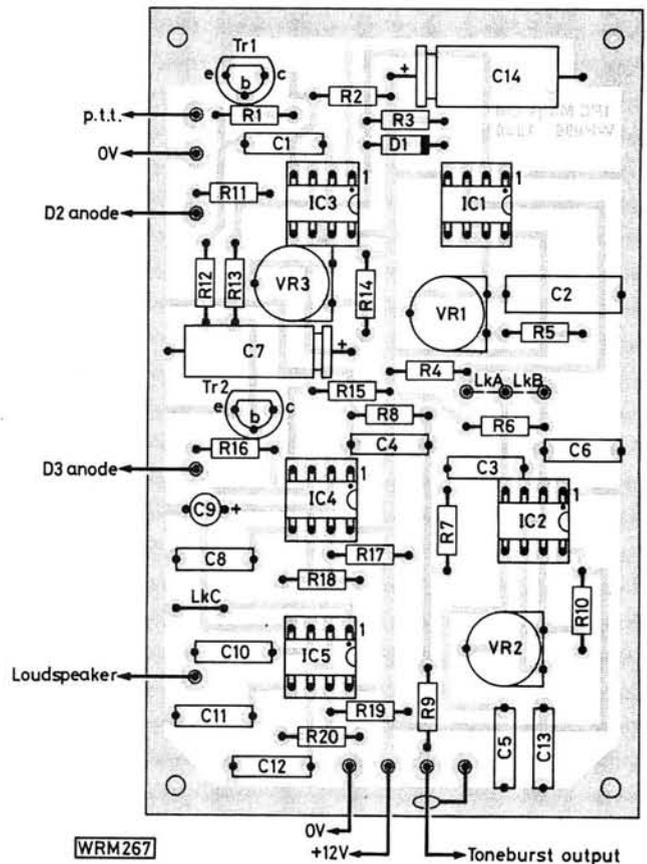


Fig. 7: Component placement and external connections

by R18 and C9. The output from IC4 is used to flash a l.e.d. and also to gate a further astable, IC5, to provide an audio frequency signal suitable for direct connection to the loudspeaker in the transceiver. Link LKC is provided so that the audible warning facility may be disabled when not required.


## Construction and Adjustment

A recommended p.c.b. layout and corresponding component overlay are shown in Figs. 6 and 7. The circuit layout is not critical and builders may, if desired, employ alternative construction techniques such as Veroboard, matrix board, etc.


Alignment of the toneburst oscillator must be carried out accurately, either using a digital frequency meter or by comparison techniques using an accurately calibrated audio frequency signal generator. LKA should be disconnected and LKB connected. VR2 is then adjusted until the correct frequency is achieved (1750Hz will be obtained with VR2 approximately in the centre of its track). It is very anti-social to carry out toneburst adjustments by trial and error with your local repeater and thus "air testing" should not be attempted until after initial bench adjustments have been made. Adjustment of the time-out period, which will depend largely on the requirements of the constructor's local repeater, can be carried out using a stopwatch or wrist-watch. A period of approximately 45 seconds will be obtained with VR3 set to the centre of its track. Similarly, a 500ms burst of tone will be obtained with VR1 in its centre position, and it will not normally be necessary to make any further adjustment to either this pre-set or to VR3. It is recommended that the toneburst frequency be checked periodically after the toneburst module has been fitted to the transceiver. ●

**NEXT MONTH**  
**Battery charger and mains p.s.u. for the**  
**PW "Nimbus" hand-held**

Table 1

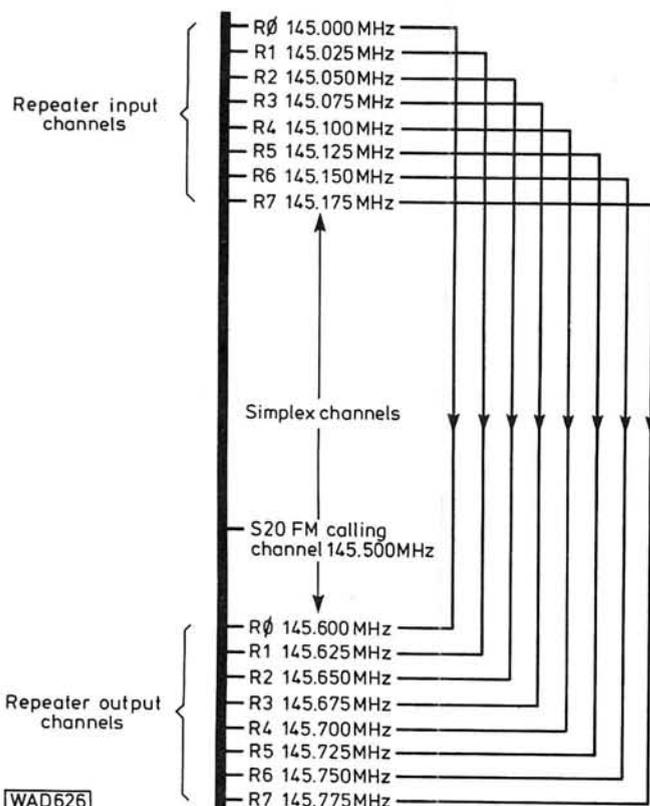

WAD626

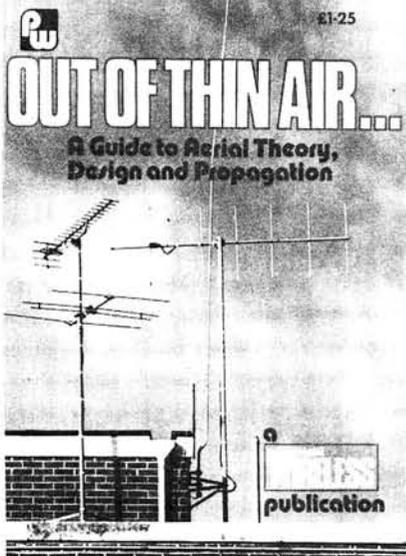

Aerials and aerial accessories are very definitely among the most popular topics covered in *Practical Wireless*. In response to requests from readers, we've reprinted a selection of articles from the past three years, plus two new features—one by Ron Ham on v.h.f. propagation, the other describing the "Ultra-Slim Jim", a new version of that most popular 2-metre aerial design by Fred Judd.

*Out of Thin Air* has 80 pages, 295 x 216mm, and is available from W. H. Smith price £1.25, or by post from Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, price £1.50 including postage and packing to UK addresses, or £1.80 by surface mail overseas. Please ensure that your name and address are clearly legible.

## So You Want to Pass the RAE?



A reprint of the complete series, including details of the new examination format introduced in 1979, is now available. The reprint costs 85p, including postage and packing to addresses within the United Kingdom.

Order your copy by completing and returning the coupon, together with your remittance, to IPC Magazines Ltd., Post Sales Department, Lavington House, 25 Lavington Street, London SE1 0PF. Please ensure that your name and address are clearly legible.

*Practical Wireless*, September 1980

### OUT OF THIN AIR

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,  
Lavington House, 25 Lavington Street,  
London SE1 0PF**

Please send me.....copies at £1.50 each to include postage and packing (£1.80 surface mail overseas)

I enclose P.O./Cheque No.....Value .....

UK remittances must be by crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

**NAME** .....  
(BLOCK LETTERS)

**ADDRESS** .....  
(BLOCK LETTERS)

.....  
.....  
.....Post Code .....

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

— Cut round dotted line —

### PRACTICAL WIRELESS—Radio Amateur Examination Reprint

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,  
Lavington House, 25 Lavington Street,  
London SE1 0PF**

Please send me . . . copies at 85p each to include postage and packing

I enclose P.O./Cheque No..... Value .....

Remittance must be crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

**NAME** .....  
(BLOCK LETTERS)

**ADDRESS** .....  
(BLOCK LETTERS)

.....  
.....  
..... Post Code .....

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

— Cut round dotted line —

# PRODUCTION LINES

alan martin

## Gould DMM


The new Alpha V, the latest and smallest in the comprehensive range of digital multimeters from Gould Instruments Division, is a low-cost hand-held instrument combining versatility and ruggedness. The Alpha V has a 3½-digit liquid-crystal display, and the 25 measuring ranges cover the five basic functions of d.c. voltage, a.c. voltage, d.c. current, a.c. current, and resistance.

The multimeter is powered by a 9V carbon-zinc or alkaline battery (PP3 or equivalent), the latter giving a typical life of 200 hours. Battery-low indication is provided by the multimeter's display, which shows "BAT" when less than 10% of useful battery life remains. Automatic decimal-point, polarity and over-range indication is also provided.

The Gould Alpha V measures only 178 x 76 x 38mm and weighs 282g.

Accessories supplied with the basic instrument include standard red and black test leads, battery and handbook. Other accessories available are a soft protective carrying case, high-voltage probe, r.f. detector, and a special set of test leads rated at 2kV r.m.s. and 20A.

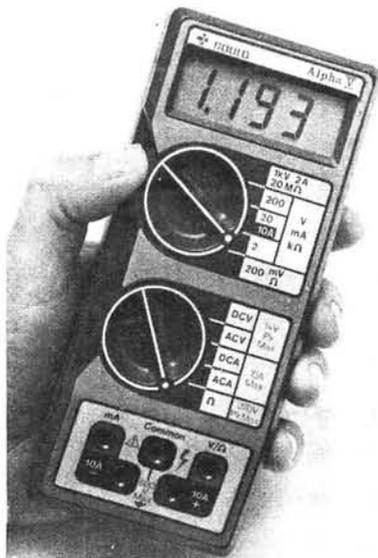Costing £85.00 plus VAT and £3.00 p&p, the Alpha V carries a two-year guarantee and is available from: *Gould Instruments Division, Roebuck Road, Hainault, Essex. Tel: 01-500 1000.*



## UHF Helical Filters

The 7HW series of helical filters for u.h.f. have been designed for various communication applications in u.h.f. radio, s.h.f. i.f. filters, etc. The very small size makes them suitable for replacing all other types of u.h.f. resonator — especially as the first i.f. filter in the booming field of satellite receiving systems.


Although various types are available in the range 300–500MHz, Ambit are stocking units centred on 435MHz, with 1dB bandwidth of 11MHz, and a –50dB bandwidth of only 50MHz (using two blocks coupled together). Temperature coefficients are plotted over the range –10°C to +60°C.

The 7HW costs £1.46 plus VAT and 35p p&p and is available from: *Ambit International, 200 North Service Road, Brentwood, Essex CM14 4SG. Tel: (0277) 230909.*
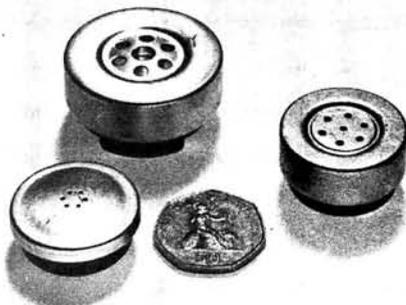
## Telephone Mics

Stolec Ltd. of Rye can now supply a new range of Primo telephone handset cartridges suitable for different applications. The range comprises transmitter and receiver units designed for use with both telephones and radio telephones, and a special feature is the use of a new thin receiver unit providing clear, uniformly high-quality sound.

Various types of cartridges can be supplied to meet a large variety of applications. DM61 and DM76 are dynamic transmitters, the 76 being a low-cost unit, and Model EM 84 is an electret transmitter. The three receivers are dynamic units, suitable as replacements for standard magnetic types.



In addition an electret microphone cartridge with integral amplifier is also available, and this miniature unit is only 10mm in diameter and 9.5mm deep. Prices start from 80p per cartridge.

Further details from: *Stolec Ltd., Eagle Road, Rye, East Sussex. Tel: (079 73) 3725.*

## 2-Chip Synthesizers

A unique range of three 2-chip frequency generating circuits which dramatically simplifies the design of synthesizers for radio applications is announced by Plessey Semiconductors.

The circuits are intended for three types of application—ultra low power for hand-held equipment, general purpose for applications up to 500MHz, and higher frequency for applications up to 1GHz. Each application requires one bipolar high speed divider and one *n*-channel m.o.s. control circuit. As the

typical number of i.c.s is therefore reduced from 12 to 2, this gives a considerable space saving.

Radio synthesizers can take up to a year to design but the new circuits considerably simplify the task of the designer. They are easy to design in and the same circuits can be used for different frequency bands. A typical tuning range would cover 20:1 range of frequencies. Also, the *n*-channel m.o.s. circuits interface directly with memories and microprocessors.

There are considerable financial advantages over conventional solutions as, for example, marine, taxi and police radios can have a choice of channels instead of just one channel for approximately the same cost. In addition, the ultra-low power synthesizer uses less than half the power of alternative solutions, thus prolonging battery life.

The circuits are believed to be the only complete range available in the world from a manufacturer and are the result of a 10 year involvement by Plessey Semiconductors in the development and production of high speed dividers.

*Plessey Semiconductors, Kembrey Street, Crowdy's Hill Estate, Swindon SN2 6BA.*

## Remote Recall Telephone Answering Machine

Storacall, one of the authorised telephone answering machine suppliers, has recently launched its new Ansamaster II Telephone Answering Computer. This revolutionary unit is the first in the world to use a self diagnostic microcomputer that continually monitors each function of the machine and can "Talk" to the user through an alphanumeric digital display. Among other things, the display can indicate how much time has elapsed while recording the outgoing announcement, how many calls have been received, which call is being listened to during playback, whether a call is being taken, and whether the user has misoperated the unit, or if there is a fault with either of the two cassettes.

Among its many features are included fast forward, fast rewind, an answer only facility, variable length outgoing announcement, built-in microphone and call monitor facilities. The most important feature, however, is the remote recall that enables the user to listen to his messages without returning to his home or office. Unlike most other remote controlled answer-

## Cassette Head Demagnetiser

The totally new Bib Electronic Cassette Head Demagnetiser is a completely self-contained and automatic unit. Its use could restore lost output levels, reduce background noise and overall distortion. Removing virtually all residual magnetism, the head demagnetiser is housed in a standard cassette, powered by two internal batteries (supplied) and generates an audible tone when operating.

Available from most hi-fi accessory shops, the unit costs £10.49 inclusive of VAT.

Bib Hi-Fi Accessories Ltd., Kelsey House, Wood Lane End, Hemel Hempstead, Herts HP2 4RQ. Tel: (0442) 61291.



ing machines, the Ansamaster II does not use bulky and expensive pocket activators. Instead a changeable voice code is used, which is programmed by five changeable code switches on the back of the unit. This means that it is easy for more than one person to use the unit and greater security is gained

as the code can be changed at will.

The Ansamaster II from Storacall is available either as an outright purchase or on a rental contract from as little as £3.36 per week.

For further details contact: Storacall Ltd., 28 York Street, Twickenham, Middlesex. Tel: 01-891 3321.

A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA  
 Industrial Sales: 01-328 1009  
 Mail Order: 01-624 8582  
 Also retail shops: 325 Edgware Road, London W2.  
 40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow.  
 108A Stokes Croft, Bristol.

**CAPACITORS:**  
 Mullard Ceramic 63v range  
 1pF to 10,000pF E 24 range  
 all at £0.06 each  
 Siemens Ceramic 63v B37448/9  
 .01: .022: .033: .047mF @ £0.06  
 .068: .1mF @ £0.08: .22mF @  
 £0.11  
 CSF High Voltage Ceramic Discs  
 Prices £0.07 to £0.18 Range  
 100pF to 10,000pF  
 Voltage range up to 6Kv.  
 See catalogue for details.  
 Comprehensive range Siemens  
 Layer Polyester Caps: .001 to  
 3.3mF  
 Prices £0.07 to £0.63.  
 See catalogue for details.  
 Large range of Mullard/Siemens  
 Electrolytic Axial/Radial  
 Capacitance values 1.0mF to  
 10,000mF  
 Voltage ranges 25v: 40v: 63v:  
 100v:  
 Prices and types as catalogue  
 Also Mullard C280; Siemens  
 B32231/4 and B32110. All prices  
 net + VAT and postage/packaging.

**BOXES & CASES**  
 See catalogue for full range.  
 Aluminium boxes 13 sizes.  
 Rexine Covered boxes 7 sizes.  
**NEW RANGE TMEC CASES**  
 Send S.A.E. for details & types  
 Price range. £14.04 to £17.00  
**ABS PLASTIC BOXES**  
 3" x 2 1/4" x 1 3/8"  
 3 3/4" x 2 3/4" x 1 3/8" Prices as  
 4 1/2" x 3 3/4" x 1 1/2" catalogue  
 8" x 4 3/4" x 3"  
**BAZELLI INSTRUMENT CASES**  
 5 sizes.  
 Miscellaneous hardware  
 including  
 Vero Board: Superstrips:  
 Vero Breadboard.  
 Vero boxes (see catalogue for  
 full range).

Card Frames: Fliptop boxes:  
 etc etc.

**TTL see catalogue for full range**

SN7400N	ED.14	SN7491AN	EO.54
SN7401N	EO.14	SN7492N	EO.31
SN7402N	EO.14	SN7493N	EO.32
SN7403N	EO.14	SN7494N	EO.80
SN7404N	EO.14	SN7495N	EO.55
SN7405N	EO.15	SN7496N	EO.34
SN7406N	EO.34	SN7497N	EO.30
SN7407N	EO.26	SN74100N	EO.10
SN7408N	EO.15	SN74107N	EO.21
SN7409N	EO.16	SN74118N	EO.76
SN7410	EO.47	SN74119N	EO.20
SN7411N	EO.15	SN74121N	EO.25
SN7412N	EO.20	SN74122N	EO.48
SN7413N	EO.28	SN74123N	EO.42
SN7414N	EO.47	SN74124N	EO.53
SN7416N	EO.22	SN74125N	EO.40
SN7417N	EO.22	SN74141N	EO.50
SN7420N	EO.15	SN74145N	EO.64
SN7423N	EO.16	SN74148N	EO.05
SN7425N	EO.19	SN74150N	EO.79
SN7426N	EO.19	SN74151N	EO.55
SN7427N	EO.19	SN74153N	EO.55
SN7430N	EO.15	SN74154N	EO.90
SN7432N	EO.17	SN74155N	EO.60
SN7437N	EO.21	SN74157N	EO.59
SN7438N	EO.21	SN74160AN	EO.70
SN7440N	EO.15	SN74161AN	EO.70
SN7441AN	EO.52	SN74162AN	EO.70
SN7442N	EO.40	SN74163AN	EO.70
SN7445N	EO.66	SN74164AN	EO.80
SN7446AN	EO.48	SN74165AN	EO.80
SN7447AN	EO.48	SN74171N	EO.20
SN7448N	EO.45	SN74174N	EO.80
SN7450N	EO.15	SN74175N	EO.63
SN7451N	EO.15	SN74176N	EO.73
SN7453N	EO.15	SN74177N	EO.73
SN7454N	EO.15	SN74180N	EO.70
SN7460N	EO.15	SN74181N	EO.65
SN7470N	EO.26	SN74192N	EO.39
SN7472N	EO.24	SN74184AN	EO.29
SN7473N	EO.25	SN74185AN	EO.10
SN7474N	EO.25	SN74186N	EO.35
SN7475N	EO.31	SN74188AN	EO.84
SN7476N	EO.26	SN74189N	EO.26
SN7480N	EO.39	SN74190N	EO.74
SN7481N	EO.71	SN74191N	EO.79
SN7482N	EO.65	SN74192N	EO.79
SN7483N	EO.60	SN74193N	EO.79
SN7484N	EO.95	SN74196N	EO.74
SN7485N	EO.70	SN74197N	EO.74
SN7486N	EO.25	SN74198N	EO.09
SN7489N	EO.66	SN74199N	EO.09
SN7490AN	EO.33		

**SOLDERING EQUIPMENT**  
**IRONS-ANTEX**  
 15 watt C15 £3.95  
 15 watt CCN £4.20  
 17 watt CX17 £4.20  
 25 watt X25 £4.20  
 Stand £1.50

**DESOLDERING TOOL**  
 Solder £6.50

**SINCLAIR INSTRUMENTS**  
 Digital Multimeter  
 " PDM35 £ 34.50  
 " " DM235 £ 52.50  
 " " DM350 £ 72.50  
 " " DM450 £ 99.00  
 Digital Frequency Meter  
 PFM200 £ 49.80  
 Low Power Oscilloscope  
 SC110 £139.00

**CRIMSON ELEKTRIK HI FI**  
**MODULES**  
 CE608 Power Amp £18.26  
 CE1004 " " £21.30  
 CE1008 " " £23.91  
 CE1704 " " £30.43  
 CE1708 " " £30.43  
 CPS1 Power Unit £16.96  
 CPS3 " " £20.43  
 CPS6 " " £26.09  
 CPR1 Pre Amp £29.57  
 CPR1S Pre Amp £38.70  
 All prices + VAT + postage/  
 packaging

**TOOLS BAHCO**  
 Side Cutter with Bezel.  
 Side Cutter without Bezel.  
 End Cutter without Bezel.  
 Vero Metal Shears.  
 Other items as catalogue.

**1980 CATALOGUE**  
 U.K.: 65p post paid  
 Europe 85p post paid  
 Rest of World £1.25  
 post paid  
 Mail order: 01-624 8582

**KNOBS & SWITCHES**  
 Big selection as catalogue  
 Also Resistors; Presets; Pots;  
 Opto; Semiconductors etc.



## AMATEUR BANDS

by Eric Dowdeswell G4AR

I never miss the opportunity of commenting on the complete inadequacy of the present system for issuing amateur transmitting licences, which enables anyone passing the entirely theoretical Radio Amateurs' Examination to go straight on the air with 150W input on a.m. or 400W p.e.p. of s.s.b. This was underlined this month when I received a letter from a young lad who passed his RAE last December.

He, very wisely, says he doesn't feel that he ought to go on the air yet without spending some time listening "to the technical talk" on the bands to find out "what it's all about", ending by asking me what receiver I would recommend he buy! Now our friend is in an area containing very few radio clubs, so he has probably been studying on his own for the RAE (so all the more credit to him for succeeding), but how is it that he has never got around to listening on the bands, normally the first step on the road to getting a ticket? It is fairly obvious that he will soon be passing his code examination with the same facility that he passed the RAE and yet he appears to have no practical experience whatsoever.

I have frequently come across people capable of constructing, and using, almost any piece of amateur radio gear you care to mention but who are quite incapable of sitting down and passing the examination. They just can't express their thoughts in writing, especially in the atmosphere of an examination room. Perhaps the new multi-choice type of exam, which, in my own view represents yet another lowering of standards, may be more suited to such candidates.

The fact remains, as I have said before, that an entirely theoretical exam is not the best way to ensure that a new licensee does not cause widespread interference with mis-handled high-power transmitting equipment on the v.h.f. and h.f. bands. Of the two types of candidate mentioned, which one deserves to be on the air? Obviously the one with the practical experience, but who, in practice, gets the licence? The theorist.

I repeat my suggestion, for what it is worth, that since the Home Office cannot be expected to set up a practical examination on the subject, it should take advantage of the facilities offered (at no cost) throughout the country, of amateur radio clubs, where potential candidates for the RAE can get a specified number of hours of practical experience

of handling transmitting and receiving equipment under the watchful eye of an appointed licensed amateur, or amateurs.

This, in effect, happens already with the RAE classes held in many clubs, technical colleges and evening classes, although these tend, naturally, to be largely theoretical. There is no reason, however, why they should not become a little more practical, especially in the clubs. Certainly no candidate for the RAE should be allowed to sit until the practical experience has been obtained.

### Here and There

Well, the May RAE has been sat by all and sundry and there will be many anxious eyes cast upon the postman in a couple of month's time, with many candidates wondering why it takes so long to mark a multiple-choice paper. One candidate was **John Dainty** (West Wickham, Kent) who still finds little time for listening. For months past it's been the swotting for the RAE and now its holidaying, but John has persisted with his code, aiming for his G4. He did manage to hear FH8CM on 20m s.s.b. for his 149th country heard.

From Bangor, Co Down, **Sam Mulholland** G18WAZ tells me the other young lads that made the RAE last time were John McBlain G18VTV and Alan Stringer G18VHZ whose father it was who coached the trio to their success, mentioned last month, in the form of G13KDR! All three are hard at it in preparation for their code tests very shortly. Sam is thinking of knocking up a QRP d.s.b. rig for the 80m and 160m bands, an idea I heartily endorse as it will soon lead to more ambitious building projects.

Having acquired an R1968 receiver complete with manual and a spare set of valves for £8, **Keith Taylor** in Camborne, Cornwall, has passed his R1155 onto a friend which is a very thoughtful action and one others might bear in mind in a similar situation.

Although he is 75 now, **Norman Cahill** (Blackley, Manchester) has been dabbling around in radio for the last 40 years. When I suggested he take the RAE, so that he could talk back to the stations instead of just listening to them, he regarded it as "the spark to set me off again", so here's hoping it comes off. In Forest Row, Sussex, **Jonathan Bigwood** is also getting into the act having got hold of a Realistic DX160 but *sans* instruction manual. If anyone can help, and I know many will offer, I suggest first contact him on Forest Row 3085.

### DXing

From 15-year-old **Simon Phillips** in Potters Bar, Herts, comes a first letter on the DX he has been hearing on his FRG-7 and a 110ft long wire, which will shortly be supplemented by an a.t.u. now on the stocks. On 10m Simon found N4ANU (who said he was using just 5W) and HS1WR, with HS1AMT and 4Z6BM on 15m. In Sunderland

**Paul Barker** G4HPS still sends info on his keying activities although, sad to say, the G4MH minibeam bought recently has still not been found a permanent site. He still managed to work FM7BM, HM1JJ, KH6AQ, TZ4AQS, VP2MGQ and ZL2GH on 15m c.w.

In Braintree, Essex, **Richard Guest** has three a.t.u.s and a Codar PR30 pre-selector which links his 60ft wire to his FRG-7. With a set such as this I doubt whether the PR30 is contributing anything at all except more noise! It is always worth switching a pre-selector in and out of circuit on an actual signal, to see if it improves the signal-to-noise ratio rather than just the signal strength. It can be deceptive if one just compares signal strengths.

Monthly report from **Dennis Sheppard** of Minster, Kent, could be the last one for a while as he prepares to move to a new QTH, where he will get his RTTY gear going again. From his past comments let's hope the new place will be a bit freer of local QRM! However, Dennis did copy the following on RTTY: 10m PT2WS, UA0CBO and ZS6ACB, 15m FR7AT, JA3DK, HP1XUL, PY4UP and 9G1JX with JJ1FXD, N4AZB/KP4, PZ1AP, TU2AA, VK2SG, VK5RY, ZS1XR, and a rare one 5T5JD.

Down in Truro, Cornwall, **Bill Rendell** continues to make improvements on his valved AR3 receiver, this time to the i.f. stages to try and improve adjacent-channel selectivity. This did not stop him copying some good DX on 40m in the shape of HK6AQT, VK3XI and 8P6KY. This is a band which is often written off by listeners because of the heavy-weight BC stations to be found there, but a little delving around in between can often prove worthwhile, as exemplified above. Catches for Bill on old favourite 20m included C5ACK, KH6WU, M1D, W6ENK/KH4 on Midway Is, ZK1AC, and 6W8DY who said QSL via VE4SK. Bill was amused at the QTH of HP2XSG given as "Coco Solo" heard on 15m together with HS1AMT (QSL W2TK), J3AH on Grenada, S79MC on Mahe Is in the Seychelles, TJ1BB, TN8MD, VP2MDG (Montserrat), VQ9WE on Diego Garcia (QSL to WA6IJZ), 4S7RS, 8Q7AR (QSL to K2TJ) and 9J2LL, all s.s.b. on all three bands.

During the excitement of the run-up to taking the RAE in May, **Arthur White** of Grantham, Lincs, managed to get hold of an AR88, "almost needing a small crane to get it into the shack" but all well worthwhile he says. Friend G3ZOA has done his best to instill the rudiments of the exam into Arthur but I'm quite sure, from the many letters received from Arthur over the last few months, that he will make it OK. With a 240ft aerial trapeze and a.t.u. in front of the AR88, he found HS1AMR, and AMT, P29JS on Papua New Guinea, 9H4G on Gozo Is, YC3BDL and YBOWR, all on 15m s.s.b.

While "spinning the dial" on his FRG-7, **Dave Coggins** of Knutsford, Cheshire, ran into a rare one in the shape of VR6TC on Pitcairn on the 15m band. With a 66ft inverted Vee aerial, supplemented by dipoles for 10 and 20m, Dave has logged other goodies on 15m such as FP0MD on St Pierre, YJ8YS, and an unusual prefix in 5N9GM who'd like cards through Box 1488 in Kaduna, Nigeria. Similar work on 10m unearthed AH2C on Guam, KG4WM in Guantanamo Bay, VP8QG, and VP8SB on Adelaide Is, 8R1J and 8Q7AR. A look at 20m revealed FK8DH, FO8AK, VP8QI, and extremely desirable ZL2UW/C indicating a QTH on Chatham Is. Forty metres found J3AH, VP2SK and to end with, XT2AW of Upper Volta and please QSL to KN1DPS.

On 10m, **Allan Stevens** (Crowthorne, Berks) went to the trouble of taping the pile-up around what appeared to be SV1DP/P on Mount Athos, but as he was still unable to positively identify the call directly he has not logged it. This is as it should be, of course, as there is no point in deceiving oneself in these matters. Others noted by Allan on 10m were HL9UG and YB0ACL, with 20m producing HC1EE, M1D,

and KB6CC in the Phoenix group, but the precise island is not known, unless some reader can help out on this one.

## Club Time

**Cheshunt & District RC.** Wednesdays at 2000, Church Room, Church Lane, Wormley, Herts. Lectures interspersed with natter-nights and Morse practice and club stations G4ECT and G8KJF on the air. Contact: Bill Pooley G8VBL, 36 Montayne Road, Cheshunt, Herts or ring Waltham Cross 32198.

**Bournemouth RS.** At 1930 in club room of Dolphin Hotel, Holdenhurst Road, B'mouth, first and third Fridays. Contact: G. Freeth G4HFQ, 9 South Avenue, New Milton, Hants or ring New Milton 618092.

**Mid-Warwickshire ARS.** First and third Mondays at 2000, at 61 Emscote Road, Warwick or have a chat with Mary Palmer G8RZR at 12 Edmondes Close, Woodloes Park, Warwick which is Warwick 496453.

**Edgware & District RS.** Second and fourth Thursdays 2000, at the Watling Community Centre, 145 Orange Hill Road, Burnt Oak, Edgware with Morse practice for starters, in both senses! A club net operates on Top Band and slow Morse under the RSGB scheme is transmitted from club station G3ASR on Top Band and on 2m. Publicity bod is Howard Drury G4HMD, 39 Wemborough Road, Stanmore, Middx or 01-952 6462.

**Wirral & District ARC.** Club call is G8WDC with meetings Wednesdays at Concourse Sports Centre, West Kirby at 2000, but check with Sec Ian Brooke G8PMW of 59 Mosslands Drive, Wallasey 'cos club takes time off during summer holidays!

**Dover RC.** At the YMCA, Godwyne Road, Dover, Kent at 1930 hours Wednesdays, with additional outdoor activities during summer. Note special event station will be active all bands at charity fete at Birchington, near Margate, for three days August 20/22, but contact: Peter Chamberlain G8EGT at 59 Capel Street, Capel-le-Ferne, Folkestone or try Folkestone 42387.

**Bolsover ARC.** Every Wednesday 1930 onwards at the Angel Inn. A new rapidly expanding club, with more details from John Lannigan G8TDU, 14 Keelby Road, Gainsborough, Lincs.

**West Kent ARS.** Adult Education Centre, Monson Road, Tunbridge Wells with meetings alternate Tuesdays with July 4 as a reference point. Sec is Brian Castle G4DYF, 6 Pinewood Avenue, Sevenoaks, Kent or 0732 56708.

A special note concerning the **Scottish Amateur Radio Convention** on Saturday, September 13 in the Palace of Arts, Bellahouston Park, Glasgow, organised by the West of Scotland ARS, often mentioned in these columns. Linked will be the RSGB's Region 14 ORM in the afternoon and a dinner and dance in the evening, at the Dean Park Hotel, Rentrew. More details of Scotland's principal amateur radio event of the year from Convener: Tom Hughes GM3EDZ, 38 Ibrox Terrace, Glasgow G51. Thanks to Ian McGarvie GM4JDU for the info.

**Barking Radio & Electronics Society.** With calls G3XBF and G8GPK, club is active every Thursday, with Mondays devoted to constructional work and Tuesdays to Morse sessions. David Couden at 111 Shelley Avenue, Manor Park, London E12 will help with details of the meetings held at the Westbury Recreation Centre, Westbury School, Ripple Road, Barking, Essex where there is a telephone 01-594 4009.

**Cambridge & District ARC.** Fridays at 1930 hours in the Visual Aids Room, Coleridge Community College, Radegund Road, Cambridge. Try David Wilcock G2FKS, the

Publicity Officer, at 19 Cavendish Avenue, Cambridge for more info or ring 0223 47220.

**North Bristol ARC.** RAE and Morse classes plus usual events at the Self-Help Enterprise, 7 Braemar Crescent, Northville, Bristol 7 on Fridays at 1930 hours, but G. E. Taylor G2HDG will be glad to answer questions at 66 Burley Crest, Downend, Bristol.

**St Helens & District ARC.** YMCA, North Road, St Helens at 1945 every Thursday with details of events from Paul Gaskell G8PQD, 131 Greenfield Road, St Helens, Merseyside where there is also a telephone 0744 25472.

**Liverpool & District ARS.** Meets at the Conservative Rooms, Church Road, Wavertree at around 2000 on Tuesdays, catering for beginners and experts alike, while club station G3AHD helps with Morse practice on 144.250MHz every Thursday at 2030. Secretary is Al Neilson G4CVZ, 78 Ackers Hall Avenue, Liverpool L14 2EA.

**Lincoln SW Club.** Can be found at the Lincoln Corporation Social Club, Waterside South, on the second and fourth Wednesdays at 8pm, with current info from Michael Wells G8PNU, 4 Horner Close, Brant Road, Lincoln who is also on 0522 721277.

Afraid this is the end of the line this month with several more clubs unmentioned due to lack of space,

compliment cards. The current QSL from the BBC is a lovely memento for the listener but if you turn it over, you will I think agree that it is useless as a confirmation of reception.

What do you do then to obtain a QSL? If the broadcast is in English and is beamed to this country then take the advice of the mailbag editor of the Voice of Turkey who recently pleaded: "no SINPOs please, tell us something about yourself and what you think of our programmes." It is a programme report that some stations want and if you supply one then you may get a QSL.

## DX Programmes

DX programmes, too, seem to be on the way out. **Jonathan Marks** in his article *Getting the Message Across on Short Wave* in the 1980 *World Radio and TV Handbook*, put the broadcasters' point of view beautifully when he said: "It can be a tough task persuading the finance department that s.w.l.s are interested in a programme which announces times and frequencies of other radio stations."

We live in changing times, but there is compensation on the short waves as programmes too are changing. They are improving no end and are often well worth listening to.

## QSL Cards

"What is a QSL card," asks reader **Frank Edward**. The one illustrated is from HCJB in Ecuador and acknowledges reception of their 100 watt experimental transmission on the 11 metre band. This card is a verification since it specifies

# BROADCAST BANDS

## SHORT-WAVE BROADCASTS

by **Charles Molloy G8BUS**

The recent change in Radio Australia's QSL policy, together with the cancellation of their DX programme a couple of years ago, puts this station among a growing band who are turning away from the DXer to the short-wave listener. How has this come about?

### Reception Reports

Traditionally, a DXer wanting a verification of reception (verie) sent a reception report to the station, who replied with a QSL card. The report gave the date, time and sufficient programme detail to prove that the station really had been picked up, and it continued with detailed information on the quality of reception using one of the reporting codes referred to last month, thus giving an indication how well the transmission was coming through.

This is still the pattern when reporting DX, but modern high-power broadcasters beaming a programme to the UK already know they are getting through. There are monitors, listening agencies and even embassies in the target area to give a continuous check, and a report of a single transmission is of little value. Smaller broadcasters though, still rely on listener reception reports, especially after the introduction of a new schedule.

### Programme Reports

Short-wave listening is a lot easier these days especially if the receiver has digital readout. Broadcasters are now spending their funds on programmes for a growing audience and economies are made at the expense of the DXer. Even if you get a QSL card, it may not be a verie; some are more like

**H**eralding  
**C**hrist  
**J**esus'  
**B**lessings

To: Richard Collins

We wish to thank you for your reception report. We have found it correct and hereby acknowledge with this verification card.

Date of reception 24th Dec 1980  
Time-GMT 0000 GMT  
Transmission was heard on 11.800 kHz

We feel sure that you have heard one of our transmissions, but the information given was not sufficiently complete or correct to receive full confirmation.

We appreciate your interest in our programs and invite you to write again.

Sincerely yours,  
*Robert Anderson*  
Director of Communications


HCJB Casilla 691 Quito, Ecuador South America

(B) Colonial architecture in CUENCA, Ecuador. This country flower market is located at one of the numerous sites in Cuenca where colonial flavor can still be enjoyed. Note the turned columns and the old fountain.

the frequency, date, time (lasting 38 minutes) of reception and gives the name of the DXer. On the reverse side there is a photograph of a local scene in Ecuador but many stations use an artistic design of some sort in place of a photo.
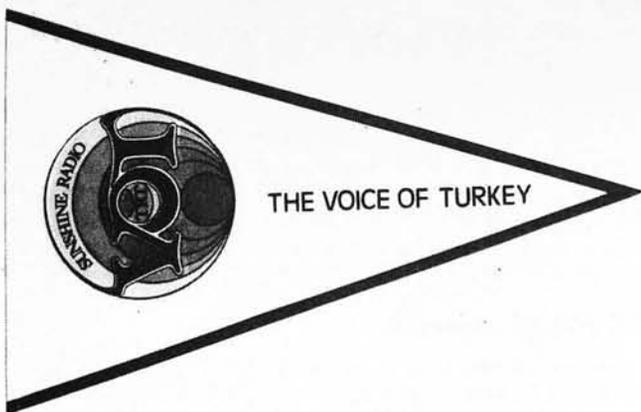
### Pennants

Pennants often come with, or instead of, a QSL. They are usually attractive such as the current one from the Voice of Turkey which is white, black, yellow and orange. While they add colour and atmosphere to the shack or listening area if they are displayed, they are of course no value at all as a confirmation of reception. According to reader **Brian O'Flynn**, pennants are there for the asking from Canada, Peking, HCJB, Budapest, AWR and Vietnam!



## Voices

Regular listeners to Radio Finland will remember Patrick Humphreys who presented their mailbag programme. He is starting a new venture with *Voices* which is an international magazine devoted solely to international broadcasting. This 50-page monthly will include a Feature Programme Guide previewing programmes in English for the coming month, a frequency check list to keep up-to-date with latest changes, and articles about broadcasters and broadcasting. Further information from: *Voices*, Box 226, Helsinki 17, Finland.

*World Radio*, the pre-war BBC weekly which covered programmes from abroad, comes to mind. It came out in pre-TV days when listening to radio programmes from abroad was a popular pastime. Perhaps we have gone round the full circle.

## Sunshine Radio

*DX Corner*, broadcast by the Voice of Turkey, is mentioned by Scottish reader **W. B. Stewart** of Lossiemouth who picked it up on 11 955 at 2045 using his National Panasonic DR28. I often listen to Sunshine Radio as they call themselves. The mailbag programme could really be classed as short talks, which are about various aspects of life in Turkey. A recent one brought back a vivid memory of ferryboat searchlights sweeping across the Bosphorus after dark. Further information about VOT programmes is obtainable from The Voice of Turkey, Mithatpasa Caddesi 37, Ankara, Turkey.

## DX Heard

Radio Free Grenada was picked up on 15 105kHz at 2100 by **Paul Hardy** of Caversham, who says the station announced itself as Radio 535, 535kHz being the m.w. outlet according to the *WRTV Handbook*. The signal was audible for about an hour but was not very strong. Radio Nepal was heard on approx 4.6MHz at 0700 in English by **Nigel Rogerson** of Plymouth, using his Heathkit SW717, homebrewed pre-selector, *PW* audio filter (May 1978 issue) and an inverted "V" aerial installed in the loft.

Reports on the various bands are welcome and should be sent direct, by the 15th of the month, to:

**AMATEUR BANDS** Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

**MEDIUM and SW BANDS** Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG. Reports for both bands **must** be kept separate.


**VHF BANDS** Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

An FRG-7, 100ft long wire and a.t.u. are in use at Bryn near Wigan by **J. Edwards**, who reports hearing Radio Rivadavia in Argentina on 5880 at 0035, La Voz de Cuba on 5315 at 0555, and on the 120m band, China on 2430 and 2600 at 2015.
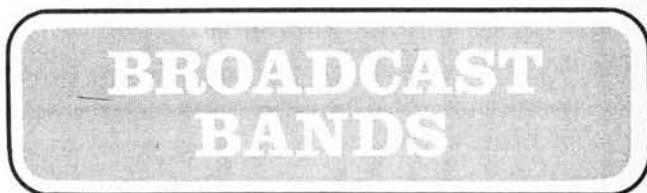
## Readers' Letters

Fifteen-year-old **Ian Smith** of Grimsby is using a Heathkit RA-1 amateur-bands receiver that has had the 20m and 15 bands adjusted to receive the 19m and 13m broadcast bands. When used with a homebrew a.t.u. and 100ft long wire it pulled in 66 stations on 19m and 40 on 21m. Quite an impressive list of DX Ian, sorry there is not room here to reproduce it.

**Tony King** of Radio New Zealand tells me that RNZ is making some major changes this year, starting with a range of new frequencies, to be phased in during the next eight months starting with 15 485 between 1800 and 2150. Tony will front *New Zealand Calling*, a new 30-minute programme which will include DX information.



## MEDIUM WAVE DX

by **Charles Molloy G8BUS**


A number of readers have asked why I made no reference to the differential amplifier in my recent article on loops. Well, the Differential Matching Amplifier (d.m.a.) to give it its full name, is not really part of a loop. It is an additional piece of equipment whose purpose is rather different to what the name would suggest. It is a matching device that enables one to do without the coupling winding and any amplification obtained can be regarded as a bonus.

## Matching Loop to Receiver

Why must a loop have a coupling winding? If you connected the main winding direct to the receiver then it would be loaded by the receiver input impedance which may be as low as 75 ohms. This loading will reduce efficiency *Q* and hence sharpness in tuning, and it may even cause loop detuning as well. The single-turn coupler along with the seven-turn main winding form a 7:1 step-down transformer which gives a better match than would be obtained by direct connection, but there are bound to be losses with such a crude arrangement. What is required is a matching device with a high input impedance and a low output impedance to go between the seven-turn main winding and the receiver. The d.m.a. provides this facility.

## Differential Matching Amplifier

Fig. 1 is the circuit of the *Practical Wireless* d.m.a. which appeared in the April 1973 issue. As a result of some discussion that took place at a DX convention in York at that time, DXer Martin Hall offered to produce several of these d.m.a.s if a number of us chipped in to share the cost. My contribution to the enterprise, I am ashamed to say, consisted of signing a cheque and that is how I became the owner of a d.m.a!

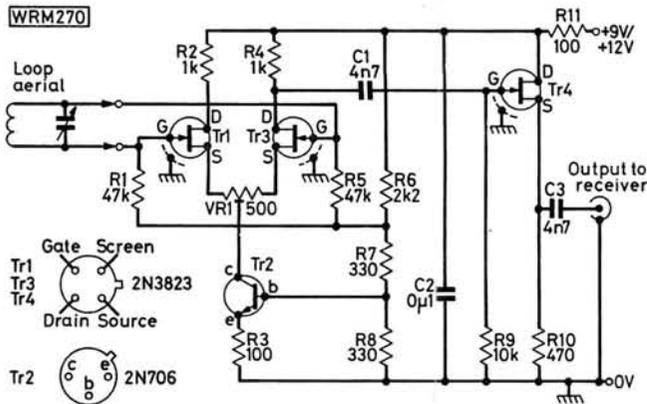

The circuit appears rather complicated because the input is electrically balanced. If you used an ordinary unbalanced amplifier then the loop's figure-of-eight directional pattern would be distorted. The d.m.a. is mounted on the loop, close to and connected across the tuning capacitor, one input to either side. The d.m.a. output is led off to the receiver in the usual way using balanced feeder (lighting flex will do). The d.m.a. ensures that the loop is completely isolated from the receiver and will not be loaded by it. An amplifier used in this way is called a buffer and the d.m.a. quite simply is a buffer amp with a push-pull input.

You can of course insert a d.m.a. between coupling winding and receiver and obtain some amplification this way, but the real point of the device is that it enables one to dispense with the coupling winding altogether and any shortcomings that go with it.

I have not made a great deal of use of my d.m.a. If you are interested in direction finding or if you frequently use a loop for listening to weak signals then a d.m.a. should be of value. A good match between loop and receiver leads to maximum transfer of signal. This will give a boost to a weak signal over and above any gain that is obtained from the amplifier. If you have trouble getting a deep enough null from your loop then a d.m.a. ought to bring an improvement here as well.

Altogether, a loop with differential amplifier should provide material for the experimenter but I feel it would be wise to master the loop on its own before straying into this field.

## Sweden Calling DXers

This is the title of what must be the longest-running DX programme still on the air. It will reach its 1600th weekly edition this year, a span of some 30 years. Started by



QSL card issued by R Sweden in 1969 to mark the 1000th edition of Sweden Calling DXers

veteran DXer Arne Skoog, it is now run by George Wood, which is an appropriate choice since skoog is the Swedish word for wood.

SWCDX consists of tips and news items sent in by listeners. The English edition is aired on a Tuesday and can be picked up on 1179kHz (254m) as part of the half-hour programme starting at 1700, 1830, 2100 or 2300, all times in GMT. The 1700 and 1830 programmes are also transmitted to Europe on 6065kHz in the 49m band.

If you are successful in having one of your "tips" broadcast in the programme then you will go onto the mailing list and receive a copy of the script of the programme each week. The standard is high though, as reports come from all over the world in answer to the various language versions.

## Heard on a Portable

The long-wave band is usually regarded as the home of BBC Radio 4, but there are a number of other interesting broadcasts to be found there after dark.

Start at R4 on 200kHz (1500m), which is transmitted from Droitwich, south-west of Birmingham. Tune up in frequency to 209kHz (1435m). The stronger station is Munich in West Germany but if you null it out by rotating the receiver, you should pick up Azilal in Morocco which carries that country's home service in Arabic. Continue on to 218kHz where once again you will find two stations. The stronger at my QTH is Montecarlo, with programming in French, and the weaker is Oslo in Norway.

Poland is the sole occupant of 227kHz, which is the next channel, though there have been reports of test transmissions from Spain on this frequency. It should be easy to separate the two by rotating the receiver. Luxemburg (home service) is on 236kHz which it shares with stations in four different locations in the USSR. Kalundborg in Denmark puts out a strong signal on 245kHz, while next door on 254kHz the dominant signal is Tipaza in Algeria. It can be nulled out to clear the way for Lahti in Finland.

Try the far end of the band. On 155kHz (1935m) West Germany and Romania fight it out. It is unlikely that you will be able to separate them by rotating the receiver as the two stations lie roughly in the same direction from the UK, but they fade in and out and it is possible at times to hear each of them in the clear for a short period

## Readers' Letters

An old HMV N2-1373 valved receiver with 15ft indoor aerial are in use at Wokingham Berks by reader **K. K. Jones**, who reports hearing Radio Algiers on 254kHz long wave, loud and clear with a daily programme in English from 2000 to 2030. He is surprised just how good this radio performs in spite of its age. Old valved receivers are not to be despised. Many perform very well when they are in good working order, and those that were designed for use with an external aerial can be used with m.w. loop.

My remarks in the July 1979 issue concerning the New Zealand punters loop, have brought a reply from **Tony King**, who assures me that the Punters Dream Aerial Company is still in existence and has sold the astonishing number of well over 1000 antennae. Sounds like something from outer space! Perhaps one of our New Zealand readers would send a photograph or some advertising material to substantiate these strange happenings "down under".

# VHF BANDS

by Ron Ham BRS15744

When the start of the sporadic-E season was accompanied by a solar storm, and a long spell of fine weather, the detailed information in your letters, which arrived from Shetlands to Sussex and Wales to Scandinavia, built up a general picture of events.

## Solar

"Plenty of solar noise and bursts on April 28, 30, and May 1, 2, 5 and 7," writes **John Branegan** GM4IHJ, Saline, Fife, who, like **Cmdr Henry Hatfield**, Sevenoaks, **Reg Taylor**, Shillington, and I, recorded the activity at various frequencies between 136 and 151MHz. Incidentally, Henry is currently testing a solar radio telescope at 550MHz which I hope to hear more about in the future. The consistently fine weather between April 22 and May 19 has enabled both **Ted Waring** (Bristol) and Henry to look at the sun with their optical instruments more frequently than in previous months.

While Ted counted 16 sunspots on the 22nd, 18 on 27th, 33 on 30th, 37 on May 4, 44 on 6th, 46 on 10th, 59 on 11th and 64 on 13th, Henry was looking for active areas on the sun to account for the radio noise, which persisted almost daily from April 26 to May 14. Among the many events he saw were some very angry prominences on the west limb on May 4. On the 11th his radio telescope recorded two five-minute bursts of radio noise at 1455 and 1512, and at 1516, using his spectrohelioscope, he saw two solar flares in progress which no doubt caused the noise. By 1656 one flare had died away and the other had revived. At 1334 on April 26 both Henry and I recorded an eight-minute burst, and a wide variety of much smaller bursts on April 28, 29, 30, May 3 and 7th to 14th inclusive. One burst was so strong at 1244 on the 28th that I heard it at 28MHz. A solar noise storm began at 1311 on May 3 and continued until the 6th, frequently sending our recording pens to f.s.d. on the 4th and 5th.

**Christian Monstein**, Switzerland, has built a radio telescope at the Amateur Observatory of Kreuzlingen. This instrument is part of a group project, and comprises two radio interferometers working at 230MHz and 465MHz on an east-west baseline, with two Yagi aerials spaced 10 metres apart. Christian also built in a helix antenna directed towards the pole star (Polaris) to measure cold sky. The drawings Christian sent look very impressive and I am looking forward to hearing more about the work of this instrument and the observatory in the future.


## The 10 Metre Band

No doubt the solar activity was responsible for the fluctuating conditions on 10m. For instance, at 0904 on April 23 the band was quiet except for one unidentifiable signal and that was subject to a very strong echo, yet during the early morning of May 5, **Sam Faulkner**, Burton-on-Trent, received a 58 signal from H44PT, Solomon Islands, working a G4 which he sorted out from the many s.s.b. signals coming from Japan. The band was dead, except for the odd station which popped up briefly, around 0900 on April 29 and

May 7, 8, 9, 12, 13, 14, and 15 and on some days there were no beacon signals either. During the 28-day period from April 22 to May 19 inclusive, I heard signals from the International Beacon Project stations in Bahrain A9XC, on 11 days, Cyprus 5B4CY, 24 days, and Germany: DL0IGI, 18 days and DK0TE, 11 days. Periodically I heard signals from the beacons in Bermuda VP9BA, Mauritius 3B8MS and South Africa ZS6PW. Ted Waring's beacon report is similar to mine except for the addition of ZS6DN, WD4MSN and YV5AYV which he occasionally heard. **Barry Ainsworth** G4GPW, Lancing, Ted and I all received very strong signals from DL0IGI during the sporadic-E disturbance on May 10, in fact Barry uses this signal as an early warning device for sporadic-E. After May 15, conditions were getting back to normal because during the early mornings of the 16th to 19th inclusive, I received strong signals from stations in Japan and Russia. "SSTV activity on 10m has been very poor," writes Sam Faulkner, having logged only two stations during the period, W6VLH at 1650 on April 23 and ZS6BQT at 1520 on May 5.
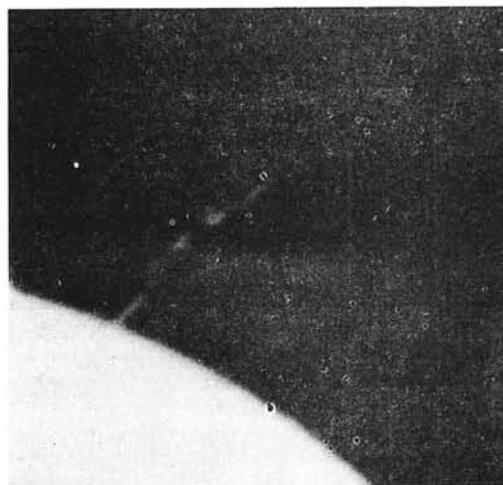
## Sporadic-E

Around 1645 on May 3 I received strong signals from thirteen east-European f.m. broadcast stations between 66MHz and 73MHz, some of which appeared in the 4m amateur band. **Barry Ainsworth**, **Chris Smith** G3UFS, Lancing and **Alec Painter** G4HUJ, Worthing, are operational on 70.26MHz and 70.375MHz, a.m., and are looking for contacts in the hope of renewing interest in this fascinating band. I well remember the excitement in June



A solar event recorded by Henry Hatfield on March 11

**ICELAND** **ISLAND**  
**TF3EA** *VHF BEACON*

Date	GMT	STATION	RST	Mc	Mode
<i>Time for interesting report on TF3VHF</i>					
<i>We hope the beacon will give interesting data.</i>					
Einar Palsson, Lynghaga 15, REYKJAVIK			70.275	CW	2-3-88
Tax		QSL	Report no 13-6-1970	Tax for QSL, 73	
			<i>ES opening,</i>		

1970 when many of us received strong signals from the Icelandic beacon TF3VHF on 70.275MHz and **Constance Hall** G8LY, Lee-on-Solent, working the beacon keeper (the late) Einar Palsson TF3EA. East-European broadcast stations were again heard during sporadic-E events at 0720 and 1234 on May 10, 1812 on the 11th, 1650 on the 16th and 0723 on the 18th. On each occasion the signals were subject to the long deep fading which is characteristic of sporadic-E.

## DXTV

"The number and intensity of sporadic-E openings has increased," writes **Nicholas Brown**, Rugby, who at 1147 on April 29 received the RS-KH electronic test pattern from CST, Czechoslovakia on Ch. R1 (49.75MHz) and RTVE, Spain on Ch. E2 (48.25MHz) around 1600 on May 7. At 1101 on the 10th he received the PM5544 test card from RAI-1, Italy on 1a (53.75MHz) and the same card from Norway, Hemnes, Melhus and Steigen. Between 1225 and 1440 he watched pictures from Bayerischer Rundfunk, West Germany, on both E2 and E3 (55.25MHz), RTVE on E2 and at 1452, a cycle race on R1 from MTV, Hungary, and saw the "Intervision" caption at 1500.

From 0947 to 1130 on the 11th, Nicholas received signals from RTVE on E2, E3 and E4 and the pictures on E4, (62.25MHz), were so strong that they overpowered local electrical interference. During the early afternoon he received pictures from ORF Austria and again from Hungary and Italy. "On the 10th," says Nicholas, "I witnessed a fight between Melhus and Steigen and then another between Bayerischer Rundfunk and Steigen." Nicholas is using an omnidirectional Band I array, a v.h.f./u.h.f. upconverter, a wideband aerial amplifier and a dual-standard monochrome TV receiver used on u.h.f.

"The band remained fairly quiet here until May 4 when I received Scandinavian pictures on both E2 and E3 between 1300 and 1400, a music programme on R1 at 1310 and a magic show from the south at 1450 on E2," writes Sam Faulkner. On May 11 he received a variety programme, news, sport, cartoons and advertisements from RAI on 1a, and around 1435 he saw adverts from MTV-1 and a programme review. At 1610 on the 12th Sam watched a kind of soap opera on R1 and at 1810 a TVP, Poland, caption.

Like Nicholas, **Harold Brodribb**, St Leonards-on-Sea and John Branegan saw pictures from Norway during the morning of the 10th, but Harold watched the pictures from Bergen and Melhus fighting for predominance on E2, as well as brief indications of a German station. Like me, Harold saw the Hungarian test card, MTV-1, Budapest and their caption clock showing a time of two hours ahead of GMT. On the 11th, Harold received a very clear picture from Madrid and saw a news programme, with a map of Spain, showing the

finish of a cycle race followed by pictures of the Pope arriving in Africa. Before 1300 he watched adverts for Coca Cola and "Pronto" furniture polish, at 1320 a part of a nature film on E2 and from about 1405 "a dull film" on R1.

"I have been receiving Band I pictures via sporadic-E for the past four days," wrote **Stephen Scott** G4CKR, Stockport, on May 13 and said that during the morning of the 10th he received programmes on R1 and R2 (59.25MHz), test cards on E3 from Norway-Hemnes and PTT SRG1, Switzerland and a news programme from Italy on 1a. On the 11th, he added Portugal and Spain to the score, and on the 12th, Hungary, along with several unidentifiable stations on each day. Steve uses a Murphy V1913 receiver fed by a rooftop dipole.

John Branegan received pictures from RTVE on E2 around 1400 on April 27, Russia and Poland on R1 on May 3, Austria and West Germany on E2 and Czechoslovakia on R1 on May 4, Portugal and Spain on E2 during the evening of the 5th, Czechoslovakia R1, and Spain E2, on the 6th and RTVE, Spain on both E2 and E4 during the afternoon of the 7th.

**Guy Stanbury**, Chelmsford, has installed a Wolsey Colour King aerial for the u.h.f. section of his JVC 3040 receiver, ready for tropospheric DX. He has also built a new Band II receiver, with a pen recorder output, so that he can monitor 103.9MHz for signals from the low-power RTBF transmitter at Tournai, which are only heard at Chelmsford when some form of atmospheric disturbance is in progress.

At 1400 on May 11, **Andrew Tett**, Surbiton, told Guy that he was receiving a football match on R1 and broadcast signals from Austria, Greece and Yugoslavia in Band II. At midday on the 15th, Guy received a test card from "Telewizja Polska" on R1 and MTV-1 and RAI-1 test cards between 0730 and 1030 on the 16th.

## Meteor Scatter

"Every morning, when at home, I get the dawn chorus of meteors by pointing my aerial due east," says John Branegan, who regularly receives tiny bits of Band I television signals from stations in East and West Germany, Czechoslovakia, Scandinavia and Switzerland. "On an average morning," writes John, "I get a mean rate of 15/20 locked identifiable pictures per hour. When there is a meteor shower, I point my aerial to be at 90° to the expected radiant. In this way I get all the transmitters out to about 1000 miles and in to about 500 miles." John is particularly interested in meteor scatter propagation and is investigating the possibility of a relationship between this and the development of sporadic-E clouds. Readers interested in this line of research should contact John and see if their observations can help.

## Tropospheric

Although conditions were not marvellous for the RSGB 144/432/1296 and SWL contest on May 3 and 4 the atmospheric pressure remained steady at 30.0in (1015mb) and **Pete Hipkin** G8KMG, Stevenage, managed to work 113 stations on 2m s.s.b. spread over G, GW, ON and PAO with a best DX of 350km. Pete used his Multi 2000 and SEM 40 watt linear to a 10-element Yagi, 25ft a.g.l. from his home QTH some 450ft a.s.l. **George Grzebieniak** RS 41733, London, heard three Fs, four GWs, two PAOs and several northern G stations on 2m and an F, three GWs and a PE on 70cm during the event. George wishes that the RSGB would provide more contests on 70cm to increase activity. In readiness for the next event, he has been comparing results, using the signal from GB3WHA, between his 19-

element Tonna and his MBM 48-element Jaybeam aeri- als, both fitted with UR67 coaxial cable. At school, George is making a ZL Special 12-element beam which he intends to test on the signals from GB3VHF.

Another 70cm enthusiast is **Peter Bowyer** G8VPN, Kettering, who uses a Standard C7800 transceiver into a colinear on the chimney at his home QTH some 320ft a.s.l. Under normal conditions, Peter can work through GB3MK RB0, GB3CI RB2, GB3LE RB4, GB3ME RB6, GB3PB and 'DY RB10, GB3HN RB11, and GB3PY and 'NH RB14, but during the tropospheric opening on April 12 he worked through 19 (70cm) repeaters, so there is no wonder that he is looking forward to the next lift when he hopes to use a 88-element multibeam.

Between 1900 and 2000 on May 7, Sam Faulkner, using his amateur TV equipment on 70cm received pictures from G4DYP/T, Chasetown, Staffs, G5KS/T Oldbury, Birmingham, G8DIR/T Shrewsbury and a local G8VBC/T.

## The Shetlands

"I hope more amateurs on the mainland will turn their beams north," writes **Arthur Tait** GM8TLO, Lerwick, Shetland. I wonder if readers fully realise that the Shetland Islands are about 200 miles north of Aberdeen and about the same distance west of Bergen in Norway, which means that for the Shetlanders, any 2m contact outside the Islands is DX. I well remember listening for the signals from the original Lerwick 2m beacon, GB3LER, back in 1964 and the excitement down here in southern England when, because of a big tropospheric opening, we heard it at good strength, and sent our reports to **Ray Flavell** GM3LTP, the beacon keeper.

In 1979 there was an increase in 2m activity when the Lerwick Radio Club GM3ZET, acquired an Icom 2m multi-mode, a 6-element quad and a rotator. The station is mainly operated by GM8SOP, who has made contacts with the mainland of Scotland on s.s.b. and has worked several stations through the Aberdeen and Bergen 2m repeaters. The present v.h.f. enthusiasts include GM3HHT, 'KZH, 'RFR, GM4DQD, 'FNE, GM8HUT, 'MMA and 'RUI. GM4FNE also works through OSCAR from time-to-time.

Arthur was first licensed in September 1979, and during October made contacts through the Aberdeen and Bergen repeaters, but his first real DX came during the evening of April 25 and most of the 26th, when the 2m band opened between Shetland, G, GM and LA. Using his FDK Multi 2700, B108 linear and a 7-element home-brew Yagi, he worked 34 stations, from as far south as G8DVK, Oxford (600 miles) and up north to Caithness, between 1922 on the 25th and 0052 on the 26th. Around 0830 on the 26th, Arthur was again having 5 and 9 QSOs with stations in Yorkshire and, between 1555 and 1739, with a 7/8 whip aerial on his car roof, he worked GM3DZB/M in Macduff, GM8SVB Banff, LA2BR Bergen and LA4EV Askoy, via the Bergen repeater, from outside his home.


GM3DZB/M, operating from a location some 860ft a.s.l. on the Ward of Scousburgh, using a 9-element Tonna, worked ten GMs and two LAs on 2m s.s.b. between 1741 and 1946. After changing to the mobile whip he worked three LAs via the Bergen repeater between 2131 and 2146.

About midnight on May 1, Arthur Tait received an excited phone call from GM8SOP, who, while operating the Lerwick Radio Club station, became the first non-Faroe Island station to access their repeater OY3REA. From about 2142, he had QSOs with OY3H, OY5A, OY9R, OY5NJ and OY5NS. Arthur quickly shoved his rig into his car, put up the 7/8 mobile whip and rushed to a nearby hill with a reasonable take-off to the north-west. He soon heard the OY repeater and made contact with OY5A, OY5SJ and OY5NS. This repeater was

accessed again from Shetland on May 2 and 4, and the same stations were worked again plus OY7ML and OY1VN.
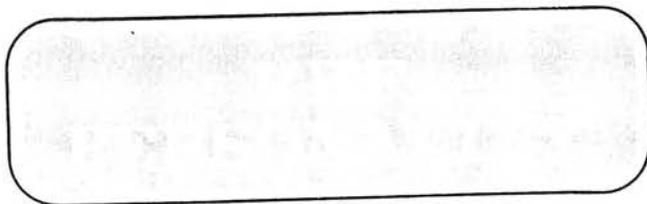
## Sussex Expedition

On Sunday, May 18, the Brownlow family, Gerry G3WMU, XYL Margaret G8TVN, and sons Pete G4ESC and Richard G8VEJ, pitched an open-ended tent by the radio exhibition building at the Chalk Pits Museum, Amberley, Sussex and installed an amateur station so that the museum's visitors could see and hear it working. Contacts were made around the world on the h.f. bands and through the Hampshire repeater, GB3SN on v.h.f. The aeri- als, a ground-plane for 2m and a vertical for 15m and 10m, were attached to their motor caravan alongside the tent. Among the station's visitors were Ron Adams G3YCS, Albert Dymock BRS26593, Dick Farley G3SSJ, Richard McLachlan G3OQT, Sid Talbot G8FCX and Louis Varney G5RV.



## GEORGE GRZEBIENIAK by RON HAM





George Grzebieniak, RS41733, has built a receiving station, covering all the amateur bands from 160m through to 23cm, at his home in London and is a regular contributor to my v.h.f. column.

George remembers playing with wires, "just tying them up", he said, before he was six and a couple of years later he and another boy, also interested in electricity, built simple circuits using batteries and light bulbs. In time his mother bought him a 12 volt mains transformer and George still remembers the electric shocks he had when he used it. His interest in aeri- als began at the age of 11 when his grandfather explained to him why a radio receiver needs an aerial.

Before he was 14, George visited the Science Museum in London and was fascinated with their amateur radio station, GB2SM. On leaving, one of the operators at the station gave George a book about amateur radio, which he read with great interest. In December 1978 his mother bought him a DX160 communications receiver, and very soon young George joined the RSGB and took an interest in the bands above 30MHz. He has gradually installed aeri- als, complete with rotator, and converters for 4m, 2m, 70cm and 23cm.

Although still at school, George has a spare-time job with a local TV dealer, and enjoys listening for the DX during RSGB contests and tropospheric openings. He also has a teleprinter and is preparing a set and aeri- als for DX TV.


# Simply ahead...

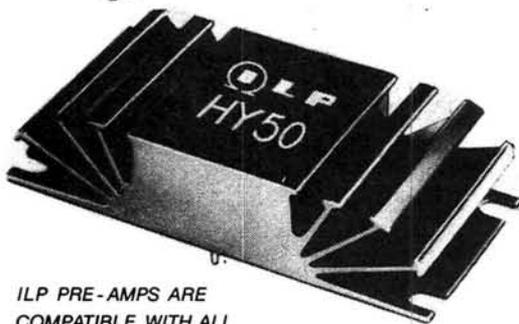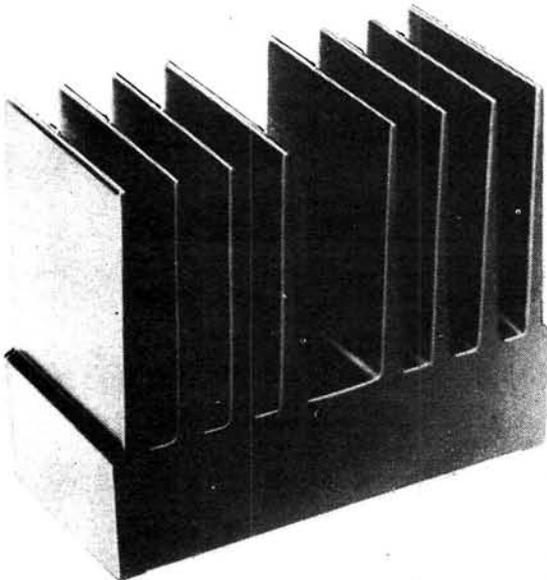

ILP PRE-AMPS ARE  
COMPATIBLE WITH ALL  
ILP POWER AMPS AND PSUs
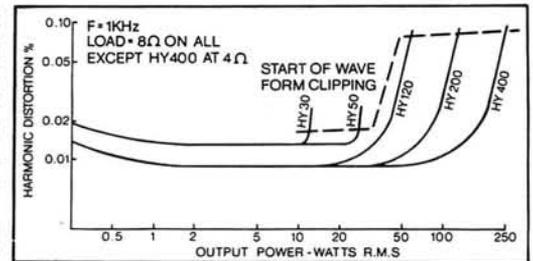
## POWER AMPLIFIERS

ILP Power Amplifiers are encapsulated within heatsinks designed to meet total heat dissipation needs. They are rugged and made to last a lifetime. Advanced circuitry ensures their suitability for use with the finest loudspeakers, pickups, tuners, etc. using digital or analogue sound sources.



Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 $\Omega$	0.02%	100 dB	-20 -0- +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 $\Omega$	0.02%	100 dB	-25 -0- +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 $\Omega$	0.01%	100 dB	-35 -0- +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 $\Omega$	0.01%	100 dB	-45 -0- +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 $\Omega$	0.01%	100 dB	-45 -0- +45	114x100x85	1.15Kg	£27.68 + £4.15

Load impedance - all models 4  $\Omega$  -  $\infty$   
Input sensitivity - all models 500 mV  
Input impedance - all models 100K  $\Omega$   
Frequency response - all models 10Hz - 45 KHz - 3dB

## POWER SUPPLY UNITS



AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS.

ILP Power Supply Units with transformers made in our own factory are designed specifically for use with ILP power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled laminated transformer, for smaller PSU's - in the other, for larger PSU's, ILP toroidal transformers are used which are half the size and weight of laminated equivalents, are more efficient and have greatly reduced radiation.

**PSU 30**  $\pm 15V$  at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + £0.68 VAT

**THE FOLLOWING WILL ALSO DRIVE ILP PRE-AMPS**

**PSU 36** for 1 or 2 HY30's £8.10 + £1.22 VAT

**PSU 50** for 1 or 2 HY50's £8.10 + £1.22 VAT


**PSU 60** with toroidal transformer for 1 HY 120 £9.75 + £1.46 VAT

**PSU 70** with toroidal transformer for 1 or 2 HY120's £13.61 + £2.04 VAT

**PSU 90** with toroidal transformer for 1 HY200 £13.61 + £2.04 VAT

**PSU 180** with toroidal transformer for 1 HY400 or 2 x HY200 £23.02 + £3.45 VAT

# this time with two new pre-amps

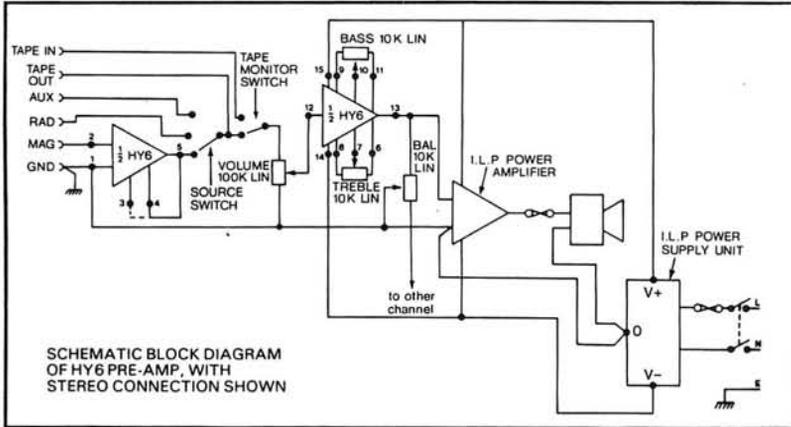

## HY6 mono HY66 stereo

When ILP add a new design to their audio-module range, there have to be very special reasons for doing so. You expect even better results. We have achieved this with two new pre-amplifiers – HY6 for mono operation, HY66 for stereo. We have simplified connections, and improved performance figures all round. Our new pre-amps are short-circuit and polarity protected; mounting boards are available to simplify construction.

Sizes – HY6 – 45 x 20 x 40 mm. HY66 90 x 20 x 40 mm. Active Tone Control circuits provide  $\pm 12$ dB cut and boost. Inputs Sensitivity – Mag. PU. – 3mV; Mic – selectable 1-12mV; All others 100mV; **Tape O/P** – 100mV; **Main O/P** – 500mV; Frequency response – D.C. to 100KHz – 3dB.

### HY6 mono

£5.60  
+ VAT 84p

### HY66 stereo

£10.60  
+ VAT £1 59

Connectors included

B6 Mounting Board  
78p + 12p VAT

B66 Mounting Board  
99p + 15p VAT

- LOW DISTORTION - Typically 0.005%
- S/N RATIO - Typically 90 dB (Mag. P.U. – 68 dB).
- HIGH OVERLOAD FACTOR – 38 dB on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS.
- REQUIRE ONLY POTS, SWITCHES, PLUGS AND SOCKETS.
- COMPATIBLE WITH ALL ILP POWER AMPS AND PSUs.
- NEEDS ONLY UNREGULATED POWER SUPPLY  $\pm 15$ V to  $\pm 50$ V.

NO QUIBBLE  
5 YEAR GUARANTEE  
7-DAY DESPATCH ON ALL ORDERS  
BRITISH DESIGN AND MANUFACTURE  
FREEPOST SERVICE  
– see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

#### HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope – we pay postage on all letters sent to us by readers of this journal.



**ILP**  
**ELECTRONICS LTD.**

FREEPOST 2 Graham Bell House, Roper Close,  
Canterbury, Kent CT2 7EP.  
Telephone (0227) 54778 Telex 965780

Please supply .....

.....Total purchase price £.....

I enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No.....

NAME .....

ADDRESS .....

Signature .....



## Service Sheets

# G.T. THE TECHNICAL INFORMATION SERVICE

## 76 CHURCH ST., LARKHALL, LANARKS ML9 1HE

Any single service sheet for £1 and large S.A.E.

1000's of different service sheets, service manuals and repair manuals always kept in stock for immediate despatch. S.A.E. brings newsletter; pricelist; bargain offers such as service sheets under 40p; quotations for any requested service sheets/manuals without obligation. Phone 0698 883334.

Save time and money - 2 giant catalogues listing thousands of service sheets/manuals plus £4 worth of vouchers free - send £2 + large S.A.E.

**SERVICE SHEETS** from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

**SERVICE SHEETS**, Radio, TV etc., 10,000 models. Catalogue 24p, plus S.A.E. with orders, enquiries. TELRAY, 154 Brook Street, Preston PR1 7HP.

**BELL'S TELEVISION SERVICES** for Service Sheets on Radio, TV etc., £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E., with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

### 30,000 SERVICE SHEETS IN STOCK MANUALS ALSO AVAILABLE

TV Monos Radios Tuners Tape Recorders Transistors all at £1. Car Radios Stereograms/Radiograms £1.25 except Colour TV from £2. State if Circuit will do, if sheets are not in stock. All TV sheets are full length 24" x 12", not in Bits & Pieces. All other Data full lengths. Free Fault Finding Chart or TV Catalogue with order. Crossed P.O.s returned if sheets not in stock.

**C. CARANNA,**  
71 BEaufort Park, London NW11 6BX  
01-458 4882 (Mail Order)

## Aerials

**COPPER AERIAL WIRE** 14swg hard drawn 70' £3.50. 140' £7.00 inc. VAT. Postage & Packing £1.95. T.M.P. Electronics, Supplies, Britannia Stores, Leeswood, Nr. Mold, N. Wales.

### KILL THAT INTERFERENCE

G2DYM ANTI-T.V.I. TRAP DIPOLES:

S.W.L. Indoor models £14.50 & £27.50

S.W.L. Outdoor models £30.00 & £34.50

Tx-ing models £42.50, £52.50 & £59.75

Lists 10 x 8in 17p SAE. Aerial Guide 50p.

Indoor and invisible aerials for S.W.L.'s £3.50.

**G2DYM, Uplowman, Tiverton, Devon.**

## For Sale

**NEW BACK ISSUES OF "PRACTICAL WIRELESS"** available 80p each, post free. Open P.O./Cheque returned if not in stock - BELL'S TELEVISION SERVICE, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

**RECORDING TAPE.** Scotch 150 7" Reel £1.50. 10 1/2" Reel £3.00. R. Southern, 551 Chorley Old Road, Bolton, Lancs.

**PRACTICAL WIRELESS.** February 1973 to January 1977. Reasonable offer accepted. 01-907 6942.

## Situations Vacant

**TESTERS,** Test Technicians, Test Engineers - Earn what you're really worth in London Working for a World Leader in Radio & Telecommunications. Phone Len Porter on 01-874 7281 or write - REDIFON TELECOMMUNICATIONS LTD., Broomhill Road, Wandsworth, London SW18.

**WHETHER** sea-going or shore-based an exciting life awaits you as a Marine Radio Officer. Full details from The Principal, Barking College of Technology, Dagenham Road, Romford, EM7 0XU. (Telephone: Romford 66841).

Practical Wireless, September 1980

## Educational

### TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Y277 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Y277 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

### CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs, Full details from:

**ICS SCHOOL OF ELECTRONICS**  
Dept. Y277 Intertext House, London SW8 4UJ  
Tel. 01-622 9911 (all hours)  
State if under 18

# COMPUTERS

Learn to really understand computers - how they work and how they are programmed. Home study course with skilled Tutor available ensures success. No previous experience needed. Colour brochure from:-Dept. PW.

British National Radio & Electronic School.,  
4 Cleveland Rd, St. Helier,  
Jersey, Channel Islands.

## Miscellaneous

### MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.  
Cassette B: 12-24 w.p.m. for professional examination preparation. Each Cassette are type C90.  
-Morse Key and Buzzer unit for sending practice.  
Price each Cassette (including booklets) £4.75. Morse Key and Buzzer £4.75.  
Prices include postage etc. Overseas Airmail £1.50 extra.

**MHEL ELECTRONICS (Dept. P.W.), 12 Longshore Way, Milton, Portsmouth PO4 8LS.**

**SEEN MY CAT?** 5000 Odds and ends. Mechanical, Electrical. Cat. free. Whiston (Dept. PW) New Mills, Stockport.

## THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4  
Reg. Office 22 Coningsby Gdns

### ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
10 to 29	3.10	1.86	1.10	.80
30 to 34	3.50	2.00	1.15	.80
35 to 39	3.95	2.36	1.34	.98
40 to 43	5.10	2.97	2.28	1.42
44 to 46	6.00	3.60	2.50	1.91
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

### SILVER PLATED COPPER WIRE

14 to 22	5.30	3.03	1.85	1.20
24 to 30	6.50	3.75	2.20	1.40

Prices include P&P and SAT.  
Orders under £2 please add 20p. SAE for list.  
Dealer enquiries welcome.

## LOSING DX?

**UNDER QRM?** DIG IT OUT with a Tunable Audio Notch Filter, between your receiver and speaker. BOOST your DX/QRM ratio, 40dB notch, MORE DX, £13.90.  
**V.L.F. EXPLORE 10-150KHz Receiver, £13.70.**  
**TIME WRONG?** MSF CLOCK is ALWAYS CORRECT - never gains or loses, self setting at switch-on, auto GMT/BSY and leap year. 8 digits show Date, Hours, Minutes and Seconds, larger digit Hours and Minutes for easy QUICK-GLANCE time, also parallel BCD output, receives Rugby time signals, get ABSOLUTE TIME, £54.80.  
**660KHZ RUGBY RECEIVER,** as in MSF Clock, serial data output, built-in antenna, 1000KHz range, £15.70.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, money back assurance so SEND OFF NOW.

## CAMBRIDGE KITS

45 (PJ) Old School Lane, Milton, Cambridge.

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low £1.05. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry and the Trade. BAZELLI, (Dept No.25) St. Wilfreds, Foundry Lane, Halton, Lancaster. LA1 6LT.

## GUITAR/PA/ MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive, 12 month guarantee. Unbeatable at £48; 60 watt £39; 200 watt £65; 100 watt twin channel sep. treble/bass per channel £58; 60 watt £50; 200 watt £72; 100 watt four channel sep. treble/bass per channel £75; 200 watt £98; slavers 100 watt £34; 200 watt £50; fuzz boxes, great sound £10.00; bass fuzz £10.90; overdrive fuzz with treble and bass boosters £20.00; 100 watt combo superb sound overdrive, sturdy construction, castors, unbeatable £98; twin channel £105; bass combo £105; speakers 15in. 100 watt £35; 12in. 100 watt £23; 60 watt £16; microphone Shure Unidyne B £26.

Send cheque or P.O. to:

**WILLIAMSON AMPLIFICATION**

62 Thorncliffe Avenue, Dukinfield, Cheshire.

Tel: 061-308 2064

Dec 79	Radio Control Rx £1.50	Jan 80	Radio Control Encoder £2.00
Jan 80	Radio Control Tx £1.50	Jan 80	Speech Processor £1.80
Jan 80	Wideband Amp £8.70	Feb 80	Servo Amp £0.70
Mar 80	Servo Amp £0.90	Mar 80	Dual Trace Unit £5.70
Apr 80	Signal Generator £2.80	Apr 80	Nimbus Transceiver £4.80
Apr 80	Nimbus Modulator £0.75	Apr 80	Nimbus Relay £0.80
May 80	Photographic Timer £1.30	May 80	NBFM Demodulator £1.30
Jun 80	Audio Limiter Main Board £1.50	Jun 80	Audio Limiter P.S.U. £1.00
Jun 80	VHF/UHF Timer RF Board £1.20	Jun 80	Repeater Timer Main Board £2.70
Jun 80	Nimbus Base Station £2.50	Jun 80	Acoustic Flash Trigger £1.00

**ABOVE P.C.B. PRICES INCLUDE DISPATCH BY FIRST CLASS MAIL**  
We can also supply photo resist copper clad P.C.B. cut to any size 5p per sq. in. + 30p postage. Please send SAE for complete list of P.W. Boards. For P.C.B.s in this issue or those not advertised, take advantage of cheap rate telephone calls by phoning us on Elgin 3227 between 6 pm and 9 pm inc. weekends and we will dispatch board to you next day by first post.

**H.T.E. (ELECTRONICS) DEPT. P.W.**  
50 MILNEFIELD AVE., ELGIN, MORAY 1V30 3EL

## RECHARGEABLE BATTERIES

### TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE SAE FOR LISTS. £1-45 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call, Sandwell Plant Ltd, 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021 354 9764 or see them at TLC, 32 Craven Street, Charing Cross, London WC2.

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolac Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions. £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. 1mm thick £1.70 sq. ft. Post/Packing 60p. White House Electronics, P.O. Box 19, Penzance, Cornwall.

**KEEP ONE HANDY IN THE WORKSHOP**



The unique aerosol treatment for minor burns and scalds. From Boots and other Chemists.

**AVO METER REPAIR SERVICE** For the Amateur. Full avometer repair and calibration service offered. Also large range of spares, service manuals available for AVO'S. Phone Stevenage (0438) 51383.

**MUSICAL MIRACLES**

for the constructor. Build a Synthesiser great or small using Dewtron modules. Mister Bassman Bass Pedal unit etc. Catalogue 35p.

**D.E.W. Ltd,**  
254 Ringwood Rd.  
**FERNDOWN Dorset BH22 9AR.**

**PVC Stickers, nameplates, T-Shirts** designed and printed to your requirements. Reasonable rates. Send stamp for details and quote: Serigraphic Design (P), 4 Bucktons Yard, Darlington, County Durham. DL3 7QL.

**SSB KAYTONE, 1000Hz da-dit-da, £6.00.**  
PT1000, Piptone, 1000Hz for 250 ms, £4.00. AT1750, Toneburst, pos or neg earth, £3.50. RC2-10 Converter, 1dB N.F. 26dB gain, Kit £10.10, Boxed ready built £22.00. RC4-2 Converter, 4 metres input, 2 metre IF, Kit £8.34, ready built £19.00.

**SPECTRUM COMMUNICATIONS**  
12 Weatherbury Way, Dorchester, Dorset DT1 2EF.

**C.W.A.S. ALARM.** Send now for the latest discount catalogue of Professional Burlar Alarm Equipment. C.W.A.S. Alarm, 11 Denbrook Walk, Bradford BD4 0QS, W. Yorks. Phone 0274 682674.

**ORDER FORM PLEASE WRITE IN BLOCK CAPITALS**

Please insert the advertisement below in the next available issue of Practical Wireless for ..... insertions  
I enclose Cheque/P.O. for £.....  
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).


NAME.....

ADDRESS.....

Send to: Classified Advertisement Manager

**PRACTICAL WIRELESS,**  
GMG, Classified Advertisement Dept., Rm. 2337,  
King's Reach Tower, Stamford Street,  
London SE1 9LS Telephone 01-261 5846

Rate  
24p per word, minimum 12 words. Box No. 60p extra.

**3½ DIGIT LCD MULTI-METER KIT**

**NEW**


Build the Practical Electronics handheld DMM. This superb product offers professional precision with extended battery life. Five function operation (AC and DC VOLTS, AC and DC CURRENT, RESISTANCE) with ability to check diodes. 0.5" LCD display with 'Battery Low' warning. Auto-polarity, Auto-zero. Full protection against transients and overloads with ability to withstand mains on any range. 0.5% basic DC accuracy and 15 different ranges. It measures AC/DC voltages from 0.1mV to 500V. AC/DC current from 0.1µA to 2A. Resistance from 0.1Ω to 2MΩ. 200 hour battery life.

The Kit contains all parts needed to construct the multimeter plus assembly instructions, battery and test leads.

We also offer a calibration service (£5.00 + VAT) and a trouble-shooting and calibration service (£7.50 + VAT). Various other component parts are also available as listed.

The multimeter is also available fully assembled and calibrated at a cost of £39.70 + P&P + VAT.

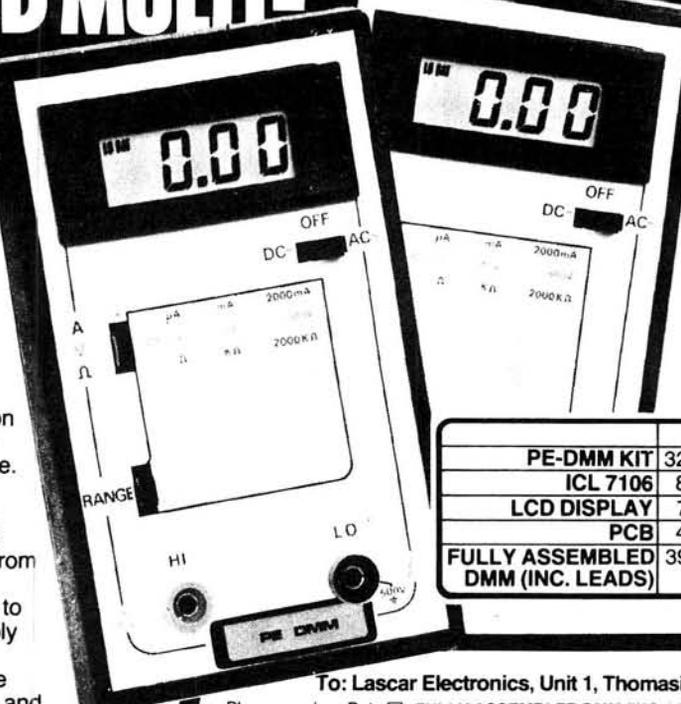Lascar Electronics Ltd., Unit 1, Thomasin Road, Basildon, Essex. Telephone No: Basildon (0268) 727383.



**FEATURED  
ASA  
PROJECT IN  
PRACTICAL  
ELECTRONICS**

	£	P & P	VAT	TOTAL
<b>PE-DMM KIT</b>	32.95	1.00	5.09	<b>39.04</b>
<b>ICL 7106</b>	8.95	0.50	1.42	<b>10.87</b>
<b>LCD DISPLAY</b>	7.95	0.50	1.27	<b>9.72</b>
<b>PCB</b>	4.95	0.50	0.82	<b>6.27</b>
<b>FULLY ASSEMBLED DMM (INC. LEADS)</b>	39.70	1.25	6.14	<b>47.09</b>

To: Lascar Electronics, Unit 1, Thomasin Road, Basildon, Essex.

Please send me Data  FULLY ASSEMBLED DMM (INC. LEADS) £47.09   
PE-DMM KIT £39.04  ICL 7106 £10.87  LCD DISPLAY £9.72  PCB £6.27

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Tel. No. \_\_\_\_\_  
I enclose cheque/P.O. value \_\_\_\_\_

# TRANSFORMERS

**30 VOLT RANGE**  
Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref	Amps	Price	P & P
112	0.5	2.90	0.90
79	1.0	3.93	1.10
3	2.0	6.35	1.10
20	3.0	6.82	1.31
21	4.0	8.79	1.31
51	5.0	10.86	1.52
117	6.0	12.29	1.67
88	8.0	16.45	1.89
89	10.0	18.98	1.89
90	12.0	21.09	2.24
91	15.0	24.18	2.39
92	2.0	32.40	O.A.

**50 VOLT RANGE**  
Sec 50V Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V.

Ref	Amps	Price	P & P
102	0.5	3.75	0.90
103	1.0	4.57	1.10
104	2.0	7.88	1.31
105	3.0	9.42	1.52
106	4.0	12.82	1.73
107	6.0	16.37	1.89
118	8.0	22.29	2.39
119	10.0	27.48	O.A.
109	12.0	32.88	O.A.

**MAINS ISOLATORS (SCREENED)**  
Sec 120/240 Sec 120/240V CT

Ref	VA	Price	P & P
*07	20	4.84	0.91
149	60	7.37	1.10
150	100	8.38	1.31
151	200	12.28	1.31
152	250	14.61	1.73
153	350	18.07	2.12
154	500	22.52	2.47
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

\*Pri 0-220-240V Sec 115 or 240V. State sec. volts required.

**CASED AUTO TRANSFORMERS**  
240V cable in 115V USA flat pin outlet

VA	Price	P & P	Ref
20	6.55	1.03	56W
75	8.50	1.31	64W
150	11.00	1.31	4W
250	13.88	1.67	69W
500	20.13	1.89	67W
1K	30.67	2.65	94W
1500VA	42.82	O.A.	93W
2K	54.97	O.A.	95W

Voltages stated are on full load  
**Continuous Ratings + VAT 15%**

**60 VOLT RANGE**  
Pri 220/240V sec 0-24-30-40-48-60V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V.

Ref	Amps	Price	P & P
124	0.5	4.27	1.10
126	1.0	6.50	1.10
127	2.0	8.36	1.31
125	3.0	12.10	1.31
123	4.0	13.77	2.12
40	5.0	17.42	1.89
120	6.0	19.87	2.12
121	8.0	27.92	O.A.
122	10.0	32.51	O.A.

**Soldering Iron** - 25W to BS spec. £1.75 P&P 30p + VAT  
**Solder Gun** - 100W include bulb for spot on vision and joints £7.50 P&P 70p + VAT  
**De-Solder Pumps** - Spring loaded with quick action button release for one handed working.  
Large £5.10 P&P 35p + VAT  
Small £4.75 P&P 30p + VAT  
Replacement tips Small 65p + VAT. Large 86p + VAT

**ABS Plastic Boxes**: inset brass nuts, slots to take PC cards (boards) flush fitting lid.  
PB1 80mm x 62 x 40 **80p**  
PB2 100mm x 75 x 40 **90p**  
PB3 120mm x 100 x 45 **£1.04**  
PB4 215mm x 130 x 85 **£2.68**  
P&P 33p + VAT.

**Metal Oxide Resistors** 1/4W 5% TR4 (Electrosil)  
390Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2/1K6  
1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K  
110K/120K/130K/180K/220K/270K/300K  
**£1.50/100 + VAT. in 100's only.**

**Antex Soldering Irons** 15W & 25W **£4.58** each  
Safety Stand **£1.75** P & P 52p each  
**P.W. Purbeck** oscilloscope transformer 250-0-250; 6.3V; 12-9V **£8.42** £1.04  
(author approved)

**12 OR 24V OR 12-0-12V**  
Pri 220-240 volts

Ref	12V	24V	P&P
111	0.5	0.25	2.42
213	1.0	0.5	2.90
71	2	1	3.86
18	4	2	4.46
85	0.5	2.5	6.16
70	6	3	6.99
108	8	4	8.16
72	10	5	8.93
116	12	6	9.99
17	16	8	11.79
115	20	10	15.38
187	30	15	19.27
226	60	30	40.41

**SPECIAL OFFER**  
**Multimeter 20KΩ B/V**  
- with combined audio/f.f. test oscillator at 1 KHz and 465 KHz AC/DC to 1000 volts DC current to 500mA resistance to 1KΩ. Size 160x97x40mm  
**£8.50** P & P £1.00 VAT 15%.

**SCREENED MINIATURES**

Ref	mA	Volts	£	P&P
238	200	3-0-3	2.83	0.63
212	1A, 1A	0-6-0-6	3.14	0.90
13	100	9-0-9	2.35	0.44
235	330, 330	0-9-0-9	2.19	0.44
207	500, 500	0-8-9, 0-8-9	3.05	0.85
208	1A, 1A	0-8-9, 0-8-9	3.88	0.90
236	200, 200	0-15-0-15	2.19	0.44
214	300, 300	0-20-0-20	3.08	0.90
221	700 (DC)	20-12-0-12-20	3.75	0.90
206	1A, 1A	0-15-20-0-15-20	5.09	1.10
203	500, 500	0-15-27-0-15-27	4.39	1.10
204	1A, 1A	0-15-27-0-15-27	6.64	1.10
239	50	12-0-12	2.88	0.37

**AVO TEST METERS**  
**AVO 8 MK5** £100.50  
**AVO 71** £40.80  
**AVO 73** £55.40  
**AVO MM5 minor** £35.95  
**AVO Wee Megger** £2.20  
**AVO TT169** in circuit transistor tester £42.60  
**AVO EM272 316K** - Volts £63.40  
**AVO DA116 Digital** £110.90  
**AVO BM7** £55.40  
**AVO Clamp Meter to 300A** £59.10  
All AVO Meggers and accessories available. P & P £1-32 VAT 15%

**20,000 ohm/V Multimeter**, mirror scale Ranges AC DC to 1000V DC current to 250mA Resistance to 3 Mohms  
5" x 3 1/4" x 1 1/4" **£14.36** P&P £1.00 VAT 15%

**U4315 Budget Meter**. 20KΩ/V Ranges to 1000V. 2.5A AC/DC 500KΩ Res. In steel case  
**£15.85**. PP £1.15 VAT 15%

**NEW RANGE TRANSFORMERS**  
2 windings 0-36V-48V/36V-0-36V 48V-0-48V 72V or 96V.

Amps	Ref	Price	P & P
1	430	4.88	0.75
1	431	8.12	0.99
2	432	13.35	1.31
3	433	16.17	1.40
4	434	20.65	2.11
5	435	29.30	2.47
6	436	36.69	O.A.
8	437	40.03	O.A.

**PANEL METERS**

Ref	43mm x 43mm	82mm x 78mm
0 50mA	6.20	6.70
0 500µA	5.95	6.70
0 1mA	5.95	6.70
0 30V	5.95	6.70

VU ind Panel 40mm x 40mm or 48mm x 45mm 250µF fsd  
VU edge SV041 centre zero 250µF **£2.60**  
Carriage 76p VAT 15%

**BRIDGE RECTIFIERS**

100V	25A	£2.40	500V
200V	2A	£0.45	PM7A6
200V	4A	£0.65	12A
400V	4A	£0.85	12A
400V	6A	£1.25	£3.25

**END OF LINE OFFERS**  
**M616** - 0-240V; Screen 1) 13-0-13 1A. 2) 12V 150mA **£1.50** 60p  
**M489** - 0-240V; 1400V - 150mA; 6.3V - 4A **£5.50** £1.04  
- 6K to 3K Ω matching trans. 5 watt **90p** 40p  
**M679** - 240V; 36V 1.6A **£3.00** 78p  
**M865** - 100V Line to 4 0 10 watts **£1.90** 60p  
**M1020** - 0-240V 12-0-12V - 50mA **75p** 30p  
**M1126** - 120/240V; 9-0-9V - 1A **£1.79** 71p

**Split Bobbin Type**  
0-12-15-20-24-30V  
Ref 009 1 Amp **£2.98** P & P £1.10  
Ref 010 2 Amp **£4.62** P & P £1.10

**15V RANGE (7.5-0-7.5V) 0-CT 15V**  
Ref  
1.71 500 mA **2.30** 0.52  
1.72 1A **3.26** 0.90  
1.73 2A **3.95** 0.90  
1.74 3A **4.13** 0.99  
1.75 4A **6.30** 1.10

**MAINS ELIMINATORS**  
Plugs into 13A socket 3V - 100mA or 6, 9, 12V x 300mA **£4.60**. P&P 55p - VAT

**EDUCATIONAL METERS (Moving Coil)**  
0-10A (0-1A), 2A, 0-15V, 0-30V  
Freestanding large scale easy read meters with top screw terminals for quick connections. **£4.50** P&P 66p - VAT

**AUTO TRANSFORMERS**

Ref	VA (Watts)	115V	210V	240V	£	P&P
113	15	0.115	210	240	1.23	0.81
64	75	0.115	210	240	4.41	1.10
4	150	0.115	200	220	5.89	1.10
67	500	0.115	200	220	12.09	1.91
84	1000	0.115	200	220	20.64	2.39
93	1500	0.115	200	220	25.81	0A
95	2000	0.115	200	220	38.31	0A
73	3000	0.115	200	220	65.13	0A
80S	4000	0.115	200	220	84.55	0A
57S	5000	0.115	200	220	98.45	0A

Step up or step down

**Barrie Electronics Ltd.**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS ALD GATE & LIVERPOOL ST

PLEASE MENTION  
**PRACTICAL WIRELESS**  
WHEN  
REPLYING TO  
ADVERTISEMENTS

You don't need to look too closely at the CSC Proto-Clip range of IC test clips to see that they provide instant connection to dual-inline packaged components. Use them on ICs, networks or relays to provide a high-integrity interface for 'hands-off' testing with oscilloscopes, signal sources, logic analysers and other instruments. Contact spacings designed to suit all standard IC packages, CSC Proto-Clips feature a moulded webbing construction, non-corroding nickel-silver contacts, and clip notches to prevent slippage during testing. Make contact with CSC Proto-Clips right away by filling in the coupon.

Continental Specialties Corporation (UK) Limited, Dept. 6QQ, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

**NEEDS NO EXAMINATION**

14 PIN PC14	16 PIN PC16	24 PIN PC24	40 PIN PC40
(£2.60 Nett) £3.85	(£2.75 Nett) £4.02	(£4.90 Nett) £6.49	(£7.90 Nett) £10.23

For larger quantity users, available in custom versions with pre-wired cables

Please deduct £1 from each additional order.

I enclose cheque/PO for £.....  
or debit my Barclaycard, Access, American Express card  
No..... Exp. date.....  
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

NAME.....  
ADDRESS.....  
CONTINENTAL SPECIALTIES CORPORATION

**CSC** FREE catalogue tick box

Continental Specialties Corporation (UK) Limited, Dept. 6QQ, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

**TOMORROW'S TOOLS TODAY**

**L.B. ELECTRONICS LTD.**

**SPECIAL OFFER:** - 5" LED displays. Full spec. 50p each, larger quantities P.O.A. P/P 25p.  
**ASTEC UM1111 E36** Modulators (Pull Outs) 65p each. P/P 25p.  
**JUST ARRIVED:** Battery eliminator 6V 200mA, brand new 95p each. P/P 35p. 5K Multi turn trim pots, PCB Mounting, pack of 14 £2.50. P/P 25p.  
**CAPACITOR SCOOP:** 1600uf at 10V, 160uf at 25V axial lead 24 at £1.00 (mixed). P/P 25p.  
**GIVE AWAY:** 22 pin low profile Dii socket, gold plated 12p each. 10 at £1.00. P/P 25p.  
**PEWEC:** Mini fans 80mm x 80mm approx. 115V £4.50. P/P £1.00.  
**TANTALUM CAPACITORS:** 4.7uf at 25V, 14 for £1.00. P/P 25p.  
**LEDS:** - 2" Red 12p, TIL209 10p, OCP70 25p, 2114 (450NS) £4.50, 2526 (Capacitor Generator) £2.95.

\*ALL I.C.'s POSTAGE AND PACKING 25p\*  
\*ALL PRICES INCLUSIVE OF V.A.T.\*  
\*MANY SURPLUS COMPUTER BARGAINS\*  
ACCESS AND BARCLAYCARD ACCEPTED

**L.B. ELECTRONICS**  
11 Hercies Road, Hillingdon, Middlesex UB10 9LS.  
Telephone: (89) 55399.

# WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TELEPHONE ORDERS BY ACCESS NOW ACCEPTED (Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 30p TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST.

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

**POLYESTER RADIAL LEAD CAPACITORS: 250V;**  
10n, 15n, 22n, 27n 5p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p; 470n 17p; 680n 19p; 1µ 2p; 1.5µ 3p; 2.2µ 3.4p.

**ELECTROLYTIC CAPACITORS (Values are in µF):**  
100V: 10 50p; 47 78p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 4.7, 6.8, 8p; 10, 15, 22, 33, 47, 50, 120p; 63, 100, 270, 50V: 50, 100, 220 25p; 470 32p; 1000 80p; 40V: 22, 33µF 8p; 100 12p; 220, 330 85p; 470 98p; 35V: 10, 33 7p; 330, 470 32p; 25V: 10, 22, 47, 100 8p; 160, 220, 250, 150 12p; 470 25p; 840, 1000 85p; 1500 40p; 2200 52p; 3300 77p; 4700 85p; 16V: 10, 40, 47, 7p; 100, 125 8p; 220, 330 14p; 470 20p; 1000, 1500 30p; 2200 36p; 100V: 100 7p.

**TANTALUM BEAD CAPACITORS**  
35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 1.5, 2.2, 3.3, 4.7, 25V: 0.1, 0.2, 0.3, 0.4, 0.5, 0.68, 1.0, 1.5, 2.2, 3.3, 4.7, 100 50p; 150 50p; 200 50p; 250 50p; 300 50p; 350 50p; 400 50p; 450 50p; 500 50p; 550 50p; 600 50p; 650 50p; 700 50p; 750 50p; 800 50p; 850 50p; 900 50p; 950 50p; 1000 50p; 1050 50p; 1100 50p; 1150 50p; 1200 50p; 1250 50p; 1300 50p; 1350 50p; 1400 50p; 1450 50p; 1500 50p; 1550 50p; 1600 50p; 1650 50p; 1700 50p; 1750 50p; 1800 50p; 1850 50p; 1900 50p; 1950 50p; 2000 50p; 2050 50p; 2100 50p; 2150 50p; 2200 50p; 2250 50p; 2300 50p; 2350 50p; 2400 50p; 2450 50p; 2500 50p; 2550 50p; 2600 50p; 2650 50p; 2700 50p; 2750 50p; 2800 50p; 2850 50p; 2900 50p; 2950 50p; 3000 50p; 3050 50p; 3100 50p; 3150 50p; 3200 50p; 3250 50p; 3300 50p; 3350 50p; 3400 50p; 3450 50p; 3500 50p; 3550 50p; 3600 50p; 3650 50p; 3700 50p; 3750 50p; 3800 50p; 3850 50p; 3900 50p; 3950 50p; 4000 50p; 4050 50p; 4100 50p; 4150 50p; 4200 50p; 4250 50p; 4300 50p; 4350 50p; 4400 50p; 4450 50p; 4500 50p; 4550 50p; 4600 50p; 4650 50p; 4700 50p; 4750 50p; 4800 50p; 4850 50p; 4900 50p; 4950 50p; 5000 50p; 5050 50p; 5100 50p; 5150 50p; 5200 50p; 5250 50p; 5300 50p; 5350 50p; 5400 50p; 5450 50p; 5500 50p; 5550 50p; 5600 50p; 5650 50p; 5700 50p; 5750 50p; 5800 50p; 5850 50p; 5900 50p; 5950 50p; 6000 50p; 6050 50p; 6100 50p; 6150 50p; 6200 50p; 6250 50p; 6300 50p; 6350 50p; 6400 50p; 6450 50p; 6500 50p; 6550 50p; 6600 50p; 6650 50p; 6700 50p; 6750 50p; 6800 50p; 6850 50p; 6900 50p; 6950 50p; 7000 50p; 7050 50p; 7100 50p; 7150 50p; 7200 50p; 7250 50p; 7300 50p; 7350 50p; 7400 50p; 7450 50p; 7500 50p; 7550 50p; 7600 50p; 7650 50p; 7700 50p; 7750 50p; 7800 50p; 7850 50p; 7900 50p; 7950 50p; 8000 50p; 8050 50p; 8100 50p; 8150 50p; 8200 50p; 8250 50p; 8300 50p; 8350 50p; 8400 50p; 8450 50p; 8500 50p; 8550 50p; 8600 50p; 8650 50p; 8700 50p; 8750 50p; 8800 50p; 8850 50p; 8900 50p; 8950 50p; 9000 50p; 9050 50p; 9100 50p; 9150 50p; 9200 50p; 9250 50p; 9300 50p; 9350 50p; 9400 50p; 9450 50p; 9500 50p; 9550 50p; 9600 50p; 9650 50p; 9700 50p; 9750 50p; 9800 50p; 9850 50p; 9900 50p; 9950 50p; 10000 50p; 10050 50p; 10100 50p; 10150 50p; 10200 50p; 10250 50p; 10300 50p; 10350 50p; 10400 50p; 10450 50p; 10500 50p; 10550 50p; 10600 50p; 10650 50p; 10700 50p; 10750 50p; 10800 50p; 10850 50p; 10900 50p; 10950 50p; 11000 50p; 11050 50p; 11100 50p; 11150 50p; 11200 50p; 11250 50p; 11300 50p; 11350 50p; 11400 50p; 11450 50p; 11500 50p; 11550 50p; 11600 50p; 11650 50p; 11700 50p; 11750 50p; 11800 50p; 11850 50p; 11900 50p; 11950 50p; 12000 50p; 12050 50p; 12100 50p; 12150 50p; 12200 50p; 12250 50p; 12300 50p; 12350 50p; 12400 50p; 12450 50p; 12500 50p; 12550 50p; 12600 50p; 12650 50p; 12700 50p; 12750 50p; 12800 50p; 12850 50p; 12900 50p; 12950 50p; 13000 50p; 13050 50p; 13100 50p; 13150 50p; 13200 50p; 13250 50p; 13300 50p; 13350 50p; 13400 50p; 13450 50p; 13500 50p; 13550 50p; 13600 50p; 13650 50p; 13700 50p; 13750 50p; 13800 50p; 13850 50p; 13900 50p; 13950 50p; 14000 50p; 14050 50p; 14100 50p; 14150 50p; 14200 50p; 14250 50p; 14300 50p; 14350 50p; 14400 50p; 14450 50p; 14500 50p; 14550 50p; 14600 50p; 14650 50p; 14700 50p; 14750 50p; 14800 50p; 14850 50p; 14900 50p; 14950 50p; 15000 50p; 15050 50p; 15100 50p; 15150 50p; 15200 50p; 15250 50p; 15300 50p; 15350 50p; 15400 50p; 15450 50p; 15500 50p; 15550 50p; 15600 50p; 15650 50p; 15700 50p; 15750 50p; 15800 50p; 15850 50p; 15900 50p; 15950 50p; 16000 50p; 16050 50p; 16100 50p; 16150 50p; 16200 50p; 16250 50p; 16300 50p; 16350 50p; 16400 50p; 16450 50p; 16500 50p; 16550 50p; 16600 50p; 16650 50p; 16700 50p; 16750 50p; 16800 50p; 16850 50p; 16900 50p; 16950 50p; 17000 50p; 17050 50p; 17100 50p; 17150 50p; 17200 50p; 17250 50p; 17300 50p; 17350 50p; 17400 50p; 17450 50p; 17500 50p; 17550 50p; 17600 50p; 17650 50p; 17700 50p; 17750 50p; 17800 50p; 17850 50p; 17900 50p; 17950 50p; 18000 50p; 18050 50p; 18100 50p; 18150 50p; 18200 50p; 18250 50p; 18300 50p; 18350 50p; 18400 50p; 18450 50p; 18500 50p; 18550 50p; 18600 50p; 18650 50p; 18700 50p; 18750 50p; 18800 50p; 18850 50p; 18900 50p; 18950 50p; 19000 50p; 19050 50p; 19100 50p; 19150 50p; 19200 50p; 19250 50p; 19300 50p; 19350 50p; 19400 50p; 19450 50p; 19500 50p; 19550 50p; 19600 50p; 19650 50p; 19700 50p; 19750 50p; 19800 50p; 19850 50p; 19900 50p; 19950 50p; 20000 50p; 20050 50p; 20100 50p; 20150 50p; 20200 50p; 20250 50p; 20300 50p; 20350 50p; 20400 50p; 20450 50p; 20500 50p; 20550 50p; 20600 50p; 20650 50p; 20700 50p; 20750 50p; 20800 50p; 20850 50p; 20900 50p; 20950 50p; 21000 50p; 21050 50p; 21100 50p; 21150 50p; 21200 50p; 21250 50p; 21300 50p; 21350 50p; 21400 50p; 21450 50p; 21500 50p; 21550 50p; 21600 50p; 21650 50p; 21700 50p; 21750 50p; 21800 50p; 21850 50p; 21900 50p; 21950 50p; 22000 50p; 22050 50p; 22100 50p; 22150 50p; 22200 50p; 22250 50p; 22300 50p; 22350 50p; 22400 50p; 22450 50p; 22500 50p; 22550 50p; 22600 50p; 22650 50p; 22700 50p; 22750 50p; 22800 50p; 22850 50p; 22900 50p; 22950 50p; 23000 50p; 23050 50p; 23100 50p; 23150 50p; 23200 50p; 23250 50p; 23300 50p; 23350 50p; 23400 50p; 23450 50p; 23500 50p; 23550 50p; 23600 50p; 23650 50p; 23700 50p; 23750 50p; 23800 50p; 23850 50p; 23900 50p; 23950 50p; 24000 50p; 24050 50p; 24100 50p; 24150 50p; 24200 50p; 24250 50p; 24300 50p; 24350 50p; 24400 50p; 24450 50p; 24500 50p; 24550 50p; 24600 50p; 24650 50p; 24700 50p; 24750 50p; 24800 50p; 24850 50p; 24900 50p; 24950 50p; 25000 50p; 25050 50p; 25100 50p; 25150 50p; 25200 50p; 25250 50p; 25300 50p; 25350 50p; 25400 50p; 25450 50p; 25500 50p; 25550 50p; 25600 50p; 25650 50p; 25700 50p; 25750 50p; 25800 50p; 25850 50p; 25900 50p; 25950 50p; 26000 50p; 26050 50p; 26100 50p; 26150 50p; 26200 50p; 26250 50p; 26300 50p; 26350 50p; 26400 50p; 26450 50p; 26500 50p; 26550 50p; 26600 50p; 26650 50p; 26700 50p; 26750 50p; 26800 50p; 26850 50p; 26900 50p; 26950 50p; 27000 50p; 27050 50p; 27100 50p; 27150 50p; 27200 50p; 27250 50p; 27300 50p; 27350 50p; 27400 50p; 27450 50p; 27500 50p; 27550 50p; 27600 50p; 27650 50p; 27700 50p; 27750 50p; 27800 50p; 27850 50p; 27900 50p; 27950 50p; 28000 50p; 28050 50p; 28100 50p; 28150 50p; 28200 50p; 28250 50p; 28300 50p; 28350 50p; 28400 50p; 28450 50p; 28500 50p; 28550 50p; 28600 50p; 28650 50p; 28700 50p; 28750 50p; 28800 50p; 28850 50p; 28900 50p; 28950 50p; 29000 50p; 29050 50p; 29100 50p; 29150 50p; 29200 50p; 29250 50p; 29300 50p; 29350 50p; 29400 50p; 29450 50p; 29500 50p; 29550 50p; 29600 50p; 29650 50p; 29700 50p; 29750 50p; 29800 50p; 29850 50p; 29900 50p; 29950 50p; 30000 50p; 30050 50p; 30100 50p; 30150 50p; 30200 50p; 30250 50p; 30300 50p; 30350 50p; 30400 50p; 30450 50p; 30500 50p; 30550 50p; 30600 50p; 30650 50p; 30700 50p; 30750 50p; 30800 50p; 30850 50p; 30900 50p; 30950 50p; 31000 50p; 31050 50p; 31100 50p; 31150 50p; 31200 50p; 31250 50p; 31300 50p; 31350 50p; 31400 50p; 31450 50p; 31500 50p; 31550 50p; 31600 50p; 31650 50p; 31700 50p; 31750 50p; 31800 50p; 31850 50p; 31900 50p; 31950 50p; 32000 50p; 32050 50p; 32100 50p; 32150 50p; 32200 50p; 32250 50p; 32300 50p; 32350 50p; 32400 50p; 32450 50p; 32500 50p; 32550 50p; 32600 50p; 32650 50p; 32700 50p; 32750 50p; 32800 50p; 32850 50p; 32900 50p; 32950 50p; 33000 50p; 33050 50p; 33100 50p; 33150 50p; 33200 50p; 33250 50p; 33300 50p; 33350 50p; 33400 50p; 33450 50p; 33500 50p; 33550 50p; 33600 50p; 33650 50p; 33700 50p; 33750 50p; 33800 50p; 33850 50p; 33900 50p; 33950 50p; 34000 50p; 34050 50p; 34100 50p; 34150 50p; 34200 50p; 34250 50p; 34300 50p; 34350 50p; 34400 50p; 34450 50p; 34500 50p; 34550 50p; 34600 50p; 34650 50p; 34700 50p; 34750 50p; 34800 50p; 34850 50p; 34900 50p; 34950 50p; 35000 50p; 35050 50p; 35100 50p; 35150 50p; 35200 50p; 35250 50p; 35300 50p; 35350 50p; 35400 50p; 35450 50p; 35500 50p; 35550 50p; 35600 50p; 35650 50p; 35700 50p; 35750 50p; 35800 50p; 35850 50p; 35900 50p; 35950 50p; 36000 50p; 36050 50p; 36100 50p; 36150 50p; 36200 50p; 36250 50p; 36300 50p; 36350 50p; 36400 50p; 36450 50p; 36500 50p; 36550 50p; 36600 50p; 36650 50p; 36700 50p; 36750 50p; 36800 50p; 36850 50p; 36900 50p; 36950 50p; 37000 50p; 37050 50p; 37100 50p; 37150 50p; 37200 50p; 37250 50p; 37300 50p; 37350 50p; 37400 50p; 37450 50p; 37500 50p; 37550 50p; 37600 50p; 37650 50p; 37700 50p; 37750 50p; 37800 50p; 37850 50p; 37900 50p; 37950 50p; 38000 50p; 38050 50p; 38100 50p; 38150 50p; 38200 50p; 38250 50p; 38300 50p; 38350 50p; 38400 50p; 38450 50p; 38500 50p; 38550 50p; 38600 50p; 38650 50p; 38700 50p; 38750 50p; 38800 50p; 38850 50p; 38900 50p; 38950 50p; 39000 50p; 39050 50p; 39100 50p; 39150 50p; 39200 50p; 39250 50p; 39300 50p; 39350 50p; 39400 50p; 39450 50p; 39500 50p; 39550 50p; 39600 50p; 39650 50p; 39700 50p; 39750 50p; 39800 50p; 39850 50p; 39900 50p; 39950 50p; 40000 50p; 40050 50p; 40100 50p; 40150 50p; 40200 50p; 40250 50p; 40300 50p; 40350 50p; 40400 50p; 40450 50p; 40500 50p; 40550 50p; 40600 50p; 40650 50p; 40700 50p; 40750 50p; 40800 50p; 40850 50p; 40900 50p; 40950 50p; 41000 50p; 41050 50p; 41100 50p; 41150 50p; 41200 50p; 41250 50p; 41300 50p; 41350 50p; 41400 50p; 41450 50p; 41500 50p; 41550 50p; 41600 50p; 41650 50p; 41700 50p; 41750 50p; 41800 50p; 41850 50p; 41900 50p; 41950 50p; 42000 50p; 42050 50p; 42100 50p; 42150 50p; 42200 50p; 42250 50p; 42300 50p; 42350 50p; 42400 50p; 42450 50p; 42500 50p; 42550 50p; 42600 50p; 42650 50p; 42700 50p; 42750 50p; 42800 50p; 42850 50p; 42900 50p; 42950 50p; 43000 50p; 43050 50p; 43100 50p; 43150 50p; 43200 50p; 43250 50p; 43300 50p; 43350 50p; 43400 50p; 43450 50p; 43500 50p; 43550 50p; 43600 50p; 43650 50p; 43700 50p; 43750 50p; 43800 50p; 43850 50p; 43900 50p; 43950 50p; 44000 50p; 44050 50p; 44100 50p; 44150 50p; 44200 50p; 44250 50p; 44300 50p; 44350 50p; 44400 50p; 44450 50p; 44500 50p; 44550 50p; 44600 50p; 44650 50p; 44700 50p; 44750 50p; 44800 50p; 44850 50p; 44900 50p; 44950 50p; 45000 50p; 45050 50p; 45100 50p; 45150 50p; 45200 50p; 45250 50p; 45300 50p; 45350 50p; 45400 50p; 45450 50p; 45500 50p; 45550 50p; 45600 50p; 45650 50p; 45700 50p; 45750 50p; 45800 50p; 45850 50p; 45900 50p; 45950 50p; 46000 50p; 46050 50p; 46100 50p; 46150 50p; 46200 50p; 46250 50p; 46300 50p; 46350 50p; 46400 50p; 46450 50p; 46500 50p; 46550 50p; 46600 50p; 46650 50p; 46700 50p; 46750 50p; 46800 50p; 46850 50p; 46900 50p; 46950 50p; 47000 50p; 47050 50p; 47100 50p; 47150 50p; 47200 50p; 47250 50p; 47300 50p; 47350 50p; 47400 50p; 47450 50p; 47500 50p; 47550 50p; 47600 50p; 47650 50p; 47700 50p; 47750 50p; 47800 50p; 47850 50p; 47900 50p; 47950 50p; 48000 50p; 48050 50p; 48100 50p; 48150 50p; 48200 50p; 48250 50p; 48300 50p; 48350 50p; 48400 50p; 48450 50p; 48500 50p; 48550 50p; 48600 50p; 48650 50p; 48700 50p; 48750 50p; 48800 50p; 48850 50p; 48900 50p; 48950 50p; 49000 50p; 49050 50p; 49100 50p; 49150 50p; 49200 50p; 49250 50p; 49300 50p; 49350 50p; 49400 50p; 49450 50p; 49500 50p; 49550 50p; 49600 50p; 49650 50p; 49700 50p; 49750 50p; 49800 50p; 49850 50p; 49900 50p; 49950 50p; 50000 50p; 50050 50p; 50100 50p; 50150 50p; 50200 50p; 50250 50p; 50300 50p; 50350 50p; 50400 50p; 50450 50p; 50500 50p; 50550 50p; 50600 50p; 50650 50p; 50700 50p; 50750 50p; 50800 50p; 50850 50p; 50900 50p; 50950 50p; 51000 50p; 51050 50p; 51100 50p; 51150 50p; 51200 50p; 51250 50p; 51300 50p; 51350 50p; 5

# The professional scopes you've always needed.



**Super 6**  
£162.00 plus VAT



**Super 10**  
£219.00 plus VAT

When it comes to oscilloscopes, you'll have to go a long way to equal the reliability and performance of Calscope.

Calscope set new standards in their products, as you'll discover when you compare specification and price against the competition.

The Calscope Super 10, dual trace 10 MHz has probably the highest standard anywhere for a low cost general purpose oscilloscope. A 3% accuracy is obtained by the use of stabilised power supplies which cope with mains fluctuations.

The price £219 plus VAT.

The Super 6 is a portable 6MHz single beam model with easy to use controls and has a time base range of 1µs to 100ms/cm with 10mV sensitivity. Price £162 plus VAT.

Prices correct at time of going to press.

## CALSCOPE DISTRIBUTED BY

**Watford Electronics**  
33-35 Cardiff Road,  
Watford, Herts.  
Tel: 0923 40588

**Audio Electronics,**  
301 Edgware Road, London W.2.  
Tel: 01-724 3564  
Access and Barclay card facilities  
(Personal Shoppers)

**Maplin Electronics Supplies Ltd.**  
P.O. Box 3  
Rayleigh, Essex.  
Tel: 0702 715 155  
Mail Order

# CALSCOPE

## INDEX TO ADVERTISERS

A.D.E. Security Ltd ... ..	88	Felstead Electronics ... ..	82	R.S.T. Valve Mail Order ... ..	14
A.H. Supplies ... ..	10	Flairline ... ..	12	Radio Component Specialists ... ..	88
Acorn ... ..	3	Golledge Electronics P.R. ... ..	82	Radiofon ... ..	54
Amateur Radio Exchange ... ..	57, 59	GMT Electronics ... ..	11	Radio Shack ... ..	35
Ambit International ... ..	13	G T Technical Information Service ... ..	83	R & TV Components ... ..	18
Bamber Electronics ... ..	12	G2 Dym Aerials ... ..	83	Sandwell Plant ... ..	83
Barrie Electronics ... ..	85	HAC Shortwave ... ..	88	Science of Cambridge ... ..	16, 17
Bearman, Phillip ... ..	82	Harversons Surplus Co ... ..	4	Scientific Wire Company ... ..	83
Birkett J ... ..	14	Home Radio (components) Ltd ... ..	12	South Midlands Communications Ltd ... ..	60
Boss Industrial Mouldings Ltd ... ..	5	HTE Electronics ... ..	83	Spectrum Communications ... ..	84
Bowes Electronics, C ... ..	10	ILP Electronics ... ..	80, 81	Stephen-James Ltd ... ..	36
Bredhurst ... ..	Cover II	Intertext I.C.S. ... ..	2, 83	Swanley Electronics ... ..	8
British National Radio & Electronics School ... ..	7, 83	L.B. Electronics ... ..	85	Tandy Corporation (U.K.) Ltd ... ..	9
Bull J ... ..	15	Lascar Electronics ... ..	84	Technomatic Ltd ... ..	8
Burneze ... ..	84	Lee Electronics ... ..	54	Teleradio ... ..	36
Calscope ... ..	87	Leeds Amateur Radio ... ..	48	Tempus ... ..	4
Cambridge Kits ... ..	83	Lowe Electronics ... ..	47	Thanet Electronics ... ..	Cover III
Caranna C ... ..	83	Manor Supplies ... ..	12	Tornel Engineering Co ... ..	4
Catronics Ltd ... ..	54	Maplin Electronic Supplies ... ..	Cover IV	T.T. Electronics ... ..	10
Chromatronics ... ..	6	Marshall A (London) Ltd ... ..	70	V & F Smallcraft ... ..	14
Colomor (Electronics) Ltd ... ..	6	Mhel Electronics ... ..	83	Van Karen Publishing ... ..	82
Continental Specialities Corporation ... ..	59, 87	Monolith Electronics Co Ltd ... ..	2	Waters & Stanton Electronics ... ..	53
Cox Radio (Sussex) Ltd ... ..	82	MRS Communications ... ..	36	Watford Electronics ... ..	86
C.R. Supply Co ... ..	82	Osmabet ... ..	88	Western Electronics ... ..	36
D.E.W. Ltd ... ..	84	Partridge Electronics ... ..	48	Williamson Amplifications ... ..	83
Electrovalue Ltd ... ..	6	Powell T ... ..	59	Wilmslow Audio ... ..	8
Electronic Mail Order ... ..	88	Progressive Radio ... ..	14	Wintjoy Ltd ... ..	48
Envirosystems Ltd ... ..	2			Zycomm Electronics Ltd ... ..	

## BAKER SPEAKERS

### "STAR SOUND"

GROUP 45-12 **£15**

12in. 45 watt  
4, 8 or 16 ohms.

GROUP 75-12

12in. 75W professional  
model. 4, 8 or 16 ohms  
Response 30 - 16,000.  
With aluminium presence dome.

**£22**

DISCO 100/12

12 in 100W model  
8 or 16 ohm

**£26**

DISCO 100-15

15in. 100 watt  
8 or 16 ohms.

**£29**

Send for leaflets on Disco, P.A. and Group Gear.



### E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover.

10W. State 3 or 8 ohm.

Illustrated

ISW model

8 ohms

GOODMANS 20 Watt

Size 12 x 10in. 4 ohms.

Rubber cone surround.

Hi-Fi Bass unit.

GOODMANS TWIN AXIOM 8

8in. 8 ohm Hi-Fi Twin Cone

Special unit 15 watts

**£9.95**

Post £1

**£10.95**

Post £1

**£8.50**

Post £2.00

**£9.95**

Post 95p



### R.C.S. MINI MODULE HI-FI

KIT 15 x 8in 3-way Loud-

speaker System, EMI 5in,

Bass 5in, Middle 3in. Tweeter

with 3-way Crossover

and Ready Cut Baffle.

Full assembly instructions


supplied. Response = 60

to 20,000 cps 12 watt RMS.

8 ohm. £10.95 per kit.

Two kits £20.

Postage £1. Each kit.

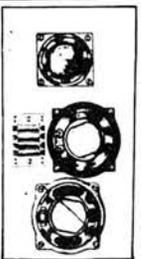

### R.C.S. LOUDSPEAKER BARGAINS

3 ohm. 6 x 4in. £1.50. 7 x 4in. £1.50. 8 x 5in. £2.50. 6 1/2in. £1.80. Bin. £2.60. 10in. £3.50. 12in. £4.50.  
8 ohm. 2 1/2in. £1.50. 3in. £1.50. 5in. £1.50. 10in. £3.50. 12in. £4.50.  
16 ohm. 6 x 4in. £1.50. 7 x 4in. £1.50. 5in. £1.50. Bin. £2.60.  
12in. £4.50. 10 x 6in. £3.50.

### LOW VOLTAGE ELECTROLYTICS

1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
500mF 12V 15p; 25V 20p; 50V 30p;  
1000mF 12V 17p; 25V 35p; 50V 47p; 1200mF/76V 80p.  
2000mF 6V 25p; 25V 42p;  
2500mF 50V 65p; 3000mF 25V 47p; 50V 65p.  
3300mF 63V £1 20; 4700mF 63V £1 20; 2700mF/76V £1.  
5000mF 35V 85p. 5600mF/76V £1 75.

### HIGH VOLTAGE ELECTROLYTICS

8/350V 35p 8+8/450V 75p 50+ 50/300V 50p  
16/350V 45p 8+16/450V 75p 32+32/450V 95p  
32/500V 75p 16+16/450V 75p 100+100/275V 65p  
50/350V 80p 32+32/350V 75p 150+200/275V 70p

### MANY OTHER ELECTROLYTICS IN STOCK

SHORT WAVE 100pf air spaced gangable tuner, 95p.  
TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p.  
CERAMIC, 1pF to 0.01mF, 5p, Silver Mica 2 to 5000pF, 5p.  
PAPER 350V-0.1 7p; 0.5 13p; 1mF 150V 20p; 2mF 150V 20p  
400V-0.001 to 0.05 5p; 0.1 15p; 0.25 25p; 0.47 35p.  
MICRO SWITCH SINGLE POLE CHANGEOVER 20p.  
SUB-MIN MICRO SWITCH, 25p. Single pole change over.  
TWIN GANG, 385 + 385pF 80p; 500pF slow motion 75p.  
385 + 385 + 25 + 25pF. Slow motion drive 85p.  
120pF TWIN GANG, 50p; 355pF TWIN GANG, 75p.  
TWIN GANG 25pF slow motion 95p.  
NEON PANEL INDICATORS 250V. Amber or red 30p.  
ILLUMINATED ROCKER SWITCH. Single pole. Red 65p.  
RESISTORS. 10G to 10M, 1W, 1/2W, 20% 2p; 2W, 10p.  
HIGH STABILITY. 1W 2%, 10 ohms to 1 meg, 12p.  
Ditto 5%. Preferred values 10 ohms to 10 meg, 5p.  
RELAYS. 12V DC 95p. 6V DC 85p. 240V AC 95p.  
BLANK ALUMINIUM CHASSIS. 6 x 4-95p; 8 x 6-  
£1 40; 10 x 7-£1 55; 12 x 8-£1 70; 14 x 9-£1 90; 16 x 6-  
£1 85; 16 x 10-£2 20. ANGLE ALI. 6 x 1/2 x 2in.-20p.  
ALUMINIUM PANELS. 6 x 4-24p; 8 x 6-38p; 14 x  
3-40p; 10 x 7-54p; 12 x 8-70p; 12 x 5-44p; 16 x 6-70p;  
14 x 9-94p; 12 x 12-£1 16; 16 x 10-£1 16.  
PLASTIC AND ALI BOXES IN STOCK. MANY SIZES  
EG Black plastic construction box with brushed aluminium  
facia size 6 1/2 x 4 1/2 x 2 1/2 £1 50  
CASSETTE MECHANISM. Mono heads. No motor. £3.50.  
BRIDGE RECTIFIER 200V PIV 1/2 amp 50p. 2 amp £1.00.  
4 amp £1.50. 8 amp £2.50.  
TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.  
MANY OTHER TOGGLES IN STOCK. Please enquire.  
PICK-UP CARTRIDGES ACOS, GP91 £2.00. GP94 £2.50.  
SONOTONE 9TAHC Diamond £3.75. Magnetic £7  
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p.  
CASSETTE MOTOR. 6 volt £1.00.

### MAINS TRANSFORMERS

6V. 500mA ..... £2.00      6-0-6V 100mA ..... £1.80  
12V, 100mA ..... £1.30      12V, 3 amp ..... £3.50  
12V, 750A ..... £1.75      10V, 30V, 40V, 2 amp ..... £3.50  
10-0-10V 2amp ..... £3.00      40V, 2 amp ..... £3.50  
30V, 5 amp and ..... £3.00      20V, 1 amp ..... £3.00  
17V-0-17V, 2 amp ..... £4.00      20V-0-20V, 1 amp ..... £3.50  
0, 5, 8, 10, 16V, 1/2 amp ..... £2.50      30V-0-30V, 2 amp ..... £8.00  
9V, 3 amp ..... £3.50      2 oi 18V, 6 amp, each ..... £11.00  
15-0-15V 2 amp ..... £3.00      12-0-12V, 2 amp ..... £3.50  
30V, 2 amp ..... £3.50      9V, 1 amp ..... £1.50  
30V, 1 1/2 amp ..... £3.30      28V, 1 amp + 28V 1 amp ..... £5.00  
20V, 40V, 60V, 1 amp ..... £4.00      32-0-32V 6 5A ..... £11.00

Access-Barclay-Visa. Lists 20p. Closed Wed.

### Radio Components Specialists

337 WHITEHORSE ROAD  
CROYDON, SURREY, U.K. TEL. 01-684 1665

## H.A.C. SHORT-WAVE KITS

### WORLD-WIDE RECEPTION

'H.A.C.' well known by amateur constructors for its Short Wave receivers, now offers a complete range of kits and accessories which have been up-dated to suit the novice and the expert.

£12.00 INCLUSIVE - the ever popular and easy to construct DX receiver Mark III; containing all genuine short wave components, drilled chassis, valve, accessories and full instructions.

AT LAST - a battery eliminator kit, which will last you a lifetime - for use in all H.A.C. valve receivers. H.T. batteries are now unobtainable, this will solve your problems for only £8.00.

T TWIN TRANSISTOR RECEIVER, selective, sensitive and with fantastic reception, yet needing only a single PP3 battery, at £14.50 this receiver is outstanding value, and will give you hours of interest and entertainment.

NEW - TRIPLE-T RECEIVER, a more advanced super three transistor receiver, loud, clear reception, value unequalled at bargain introductory price of £20.00.

All orders despatched within 7 days. Send stamped and addressed envelope now for free descriptive catalogue of kits and accessories.

SORRY, NO CATALOGUES WITHOUT S.A.E.

### "H.A.C." SHORT-WAVE PRODUCTS

P.O. Box No. 16, 10 Windmill Lane  
Lewes Road, East Grinstead, West  
Sussex RH19 3SZ

## OSMABET LTD

We make transformers amongst other things.

### TRANSFORMERS TO ORDER

We have capacity for the supply of transformers to specification, either one off, or production runs, your enquiries please.

LOW VOLTAGE TRANSFORMERS: Prim 240V ac.  
6-3V 1.5A £3.00; 3 or 800 £1.75; 8x5" 250 £2.50.  
£3.75; 3A CT £7.90; 6A CT £9.75; 15V 0.5A £3.00; 18V  
1.5A CT £7.90; 24V 1.5A CT £7.90; 30A CT £9.75; 5A CT  
£18.00; 8A CT £29.25; 12A CT £37.50; 40V 3A CT  
£13.50.

MIDGET RECTIFIER TRANSFORMERS: Prim 240V ac.  
6-0-6V 1.5A or 0-0-9V 1A £3.40 each; 12-0-12V 1A or  
20-0-20V 0.75A £4.15 each; 9-0-9V 0.3A or 12V-0-12V  
0.25A or 20V-0-20V 0.15A £3.00 each.

LT TRANSFORMERS TAPPED SEC: Prim 240V ac.  
0-10-12-14-16-18V 2A £7.50; 4A £9.40; 0-12-15-20-  
24-30V 2A £8.25; 4A £12.00; 0-20-30-60V 1A £9.00;  
2A £12.00; 0-40-50-80-100-110V 1A £12.00.  
AUTO & ISOLATION TRANSFORMERS 240/110V ac.  
30 to 4000 watts, many types ex stock. Lists.

MAINS TRANSFORMERS. SPECIAL OFFER. Prim  
240V ac. 300-0-300V 80 Ma: 6.3V 1A CT; 6.3V 1A £5.50;  
250-0-250V 60 Ma: 6.3V 1A £3.00; 250V 100 Ma. 6.3V  
2A £4.00; 9V 3A £2.50; 25V 300 Ma 90p.

### LOUDSPEAKERS

1 1/2" 11" 2 1/2" 2 1/2" 80 £1.25 each; 3" 35Q, 3 1/2" 3,  
8, 16, 80Q, 7 x 4 1/2" 80Q £1.75; 8x5" 250 £2.50.  
Goodman 5" Hi-Fi speaker 5" mid range; C/M 8 2.5 watt  
£6.50. Goodman 3 1/2" Tweeters C/M, 80p for 25W systems,  
£2.50.

"INSTANT" BULK CASSETTE/TAPE ERASER  
Instant erasure of cassettes, and any diameter of tape spools,  
demagnetises tape heads, 200/240V ac. leaflet £8.00.

### EDGWISE LEVEL METER FSD 200/0/A

Size 19 x 18 x 20mm 9000 £1.50.  
CHARGING METERS 1 1/2in diameter  
2A or 3A £1.25 each; 5A or 10A £1.50 each.

SINGLE STRANDED WIRE PVC COVERED  
32/0.2mm (10A) black or blue. £6.50 100m, 0.5mm £2.50  
100m special prices per 1000m and over.

POWER SUPPLY, TWIN OUTPUT Prim 240V ac;  
New, British manufacturer; smoothed d.c. output 20V, 1.5A,  
plus STABILISED output of 15V 100 Ma, plus further 12V  
ac 0.5A, complete with diagram, £4.00.

O/P TRANSFORMERS FOR VALVE AMPLIFIERS  
P.P. sec tapped 3-8-15Q A-A 6KQ, 30W £17.50; A-A 3KQ  
50W £26.00; 100W IEL31, KT88 etc £35.00.

G.E.C. MANUAL OF POWER AMPLIFIERS  
Covers valve amplifiers 30W to 400W £1.25.

MULTIWAY SCREENED CABLE, PVC COVERED  
36 way £1.00; 25 way 75p; 14 way 50p; 6 way 25p.

CONDENSERS AC 50Hz. 4.33/250V; 6/330V. £1.50.  
Electrolytic 400 = 400V 75p; 2000/30V 30p; 2200/40V  
40p; Paper tubular, W/E, 4/160V; 6/160V 30p each, 2mf  
150V 25p, 0.1mf 2KV 50p.

CARRIAGE EXTRA ON ALL ORDERS  
ALL PRICES INCLUDE V.A.T.  
Callers by appointment only. S.A.E. Enquiries, Lists.

46, Kenilworth Road, Edgware, Middx.  
HA8 8YG. Tel: 01-958 9314

### TV VALVES

Any 5-80p, 10-£1.50,  
50-£6.00. Your choice from the  
following - ECC82, EF80, EF183,  
EF184, EH90, PCF80, PCF802,  
PCL82, PCL85/805, PL504,  
PY800, PY88, PFL200.

Colour TV Valves -  
PL508-PL509/519 -  
PY500A-AL802. All tested -  
65p Each.

Signal Injectors with (pre-set) variable AF, which emits RF harmonics  
into the UHF band. Protected up to 300 volts DC. Complete with leads  
£5.70 each.

All Prices Include VAT at 15%. P & P per Order 30p. S.A.E. for Leaflets. Access Cards.

### ELECTRONIC MAILORDER LTD,

62 Bridge St, Ramsbottom, via Bury, Lancs.  
Tel Rams (070 682) 3036.

### AERIAL BOOSTERS

Aerial amplifiers can produce  
remarkable improvement on the  
picture and sound in fringe or difficult  
areas.

B45 - For Mono or Colour this is  
tunable over complete UHF  
television band.

B11 - For stereo or standard  
VHF/FM radio.

Next to the set fitting. Price  
£5.70 each.

## BURGLAR ALARMS

WE HAVE STOCKS OF EVERYTHING YOU NEED.  
CALLERS WELCOME. OPEN 6 DAYS  
EXPRESS POSTAL SERVICE FREE CATALOGUE SEND S.A.E.

### MAXIG SPECIAL OFFER

18 SWG steel plastic coated  
bell box with FREE  
ADE sticker

**£5.00**

Inc. VAT and postage

Mains Battery Control Unit  
with full test facilities

**£23.00**

incl. VAT & P. & P.



### A. D. E. (SECURITY) CO.,

217 WARBRECK MOOR

AINTREE, LIVERPOOL

TEL: 051-525-3440

STOP PRESS! Trade Price List Available  
Applications on Official Stationery only



# FM . . . SSB . . . CW ICOM does it again!

## IC2E

**AT LAST! A two-metre FM handy Talkie from the famous ICOM stable; probably the smallest sized one, too!**

The IC2E looks like being one of the most popular pocket portables on the market – mainly because it is just that – a **pocket** portable. The photograph shows just how small it is. The specification graphs supplied to us by Icom show that its performance is well up to the high standards Icom set themselves, with a clear transmission (all spurious signals are better than -65dB) and a sensitive receiver. The standard battery pack supplied is 9V and this gives 1.5W output. For an even smaller set, one can use the 6V pack for 1W or if you don't mind it being a bit longer there will be a 12V pack available giving 3W for about 150 minutes for 30% TX/RX. The highly competitive price includes helical antenna (with BNC connector), rechargeable battery pack and a battery charger.

### £159 inc. VAT



#### CHECK THESE FEATURES:-

**FULLY SYNTHESIZED** – covering 144-145.995 in 400 5KHz steps.

**POWER OUTPUT** – 1.5W with the 9V rechargeable battery pack as supplied – but lower or higher output available with the optional 6V or 12V packs.

**BNC ANTENNA OUTPUT SOCKET** – 50 ohms for connecting to another antenna or use the rubber duck supplied.

**WEIGHT** – 450 grams with supplied power pack and antenna.

**DIMENSIONS** – height 116 mm (without battery pack), width 65 mm, depth 35 mm.

**SEND/BATTERY INDICATOR** – Lights during transmit – when battery power fails below 6V, it doesn't – indicating the need for a recharge.

**FREQUENCY SELECTION** – By thumbwheel switches indicating the frequency.

**+5kHz SWITCH** – Adds 5kHz to the indicated frequency.

**DUPLEX SIMPLEX SWITCH** – Gives simplex or plus 600kHz or minus 600kHz transmit.

**HI/LOW SWITCH** – Reduces power output from 1.5W to 150mw reducing rapid battery drain.

**EXTERNAL MICROPHONE JACK** – if you do not wish to use the built-in electret condenser mic, an optional microphone/speaker with PTT control can be used. Useful for pocket operation.

**EXTERNAL SPEAKER JACK** – For speaker or earphone.

This little beauty is supplied ready to go complete with nicad battery pack, charger, rubber duck AND the famous THANET WARRANTY.

## THANET ELECTRONICS LTD

143 RECVLVER ROAD, HERNE BAY, KENT, 02273 63859

Phone—or put a message on the ansafone for further details  
ALSO AVAILABLE FROM OUR SHOP IN HERNE BAY

MICROWAVE MODULES  
STANDARD BEARCAT

WESTERN  
G WHIP

ANTENNA SPECIALISTS  
YAESU MUSEN

J-BEAM  
RSGB PUBLICATIONS

HP AND PART EXCHANGE WELCOMED

