

SEPTEMBER 1924

RADIO AGE

The Magazine of the Hour

WITH WHICH IS COMBINED

Radio Topics

Price
25
Cents

In This Issue

REAL BLUEPRINTS

of Baby Heterodyne II and
an Aperiodic Variometer Set

Accurate
Isometric
and Circuit
Diagrams

Latest Hookups
and Studio-Land
Features



Let Our Hook-ups Be Your Guide

MANHATTAN

ELECTRICAL SUPPLY CO., INC.

MAKERS OF THE FAMOUS



MANHATTAN
The
Loud Speaker with
Concert Modulator

*The Manhattan Loud Speaker
with its "concert modulator"
gives real tone quality.*

MANHATTAN

LOUD SPEAKER
AND



RED SEAL
PHONOGRAPH
ATTACHMENT

Oldest and Largest Distributors of



114 SO. WELLS ST., CHICAGO

NEW YORK

ST. LOUIS

SAN FRANCISCO

National Radio Institute Graduates Are "Cashing In" On These Wonderful Opportunities!

Austin Riu, one of our graduates, is now an operator of broadcasting station PWX of Havana, Cuba, and earns \$250 a month. Merle Wetzel, of Chicago Heights, Ill., another graduate, advanced from lineman to Radio Engineer, increasing his salary about 100 per cent. *even while taking his training!* Emmett Welch of Peculiar, Mo., right after graduating started in Radio, earning \$300 a month and expenses as a radio salesman. William West of St. Louis is earning big money as a radio correspondent.

Not a week goes by without our receiving urgent calls for our graduates. "We need the services of a competent Radio Engineer" writes a prominent radio firm, "Would appreciate your recommending any person who could fill position." "We want men with executive ability as well as radio knowledge to become our local managers" writes another firm. "We will require the services of several resident demonstrators"—these are just indications of the great variety of opportunities open to our graduates!

More Money for YOU in Radio

Are you "cashing in" on your Radio Knowledge? If you're not, you are passing up the best bet that has ever come your way. It's entirely up to you. There's nothing impossible in Radio for the man who has nerve enough to try. In a few months at home, you can easily become a *recognized radio expert*—and to these radio specialists, Radio offers remarkable salaries, easy fascinating work, short hours—and a wonderful future!



Earn \$2400 to \$10,000 a Year

You can earn bigger pay than you probably ever dreamed possible. Only don't let yourself stay in a rut. Sit up—look up—make up your mind that if others can make big money and big successes in Radio, so can you. The National Radio Institute has a sound practical radio course that defies comparison. It has a record of successful graduates that is unquestionable evidence of its ability to qualify you quickly for a big money position in Radio.

Our Free Book "Rich Rewards in Radio" tells all about the amazing opportunities Radio offers you, and describes how you can become a recognized radio expert at home in an astonishingly short time. Now—while your ambition is warm—mail the coupon for this big-money Free Book!

National Radio Institute, Dept. 53JA, Washington, D. C.

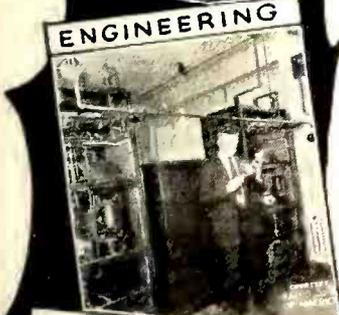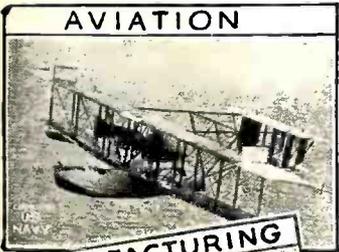**THIS FREE BOOK
Points The Way to
Your Success.**



National Radio Institute, Dept. 53JA
Washington, D. C.

Without obligation send me your book, "Rich Rewards in Radio," which tells all about the opportunities in Radio, how spare time study at home will qualify me quickly as a Certified Radiotrician so I can get one of these splendid positions, and how your Employment Service helps me to secure a big pay position.

Name..... Age.....
Please write plainly.
Street.....
City..... State.....

Always Mention RADIO AGE When Writing to Advertisers

RADIO AGE

The Magazine of the Hour
Established March, 1922

WITH WHICH IS COMBINED

RadioTopics

Volume 3

September, 1924

Number 9

CONTENTS

	Page
How Careful Mounting Will Improve Reception..	5
By Frank D. Pearne	
A Radio Set on a Dial.....	8
The How and Why of Interference.....	9
Hair's Breadth Selectivity With One Tuning Control	11
By Brainard Foote	
Unsnarling Tube Connections.....	15
By Felix Anderson	
A One-Dial "Go-Getter".....	19
By Paul Thorne	
Reminiscences of an Old Operator.....	20
First of a Series by Arthur Lynch	
With the Broadcasters.....	23
The Story of Station WOC.....	24, 25
Studio-Land Features for the Listener-in ..	26, 27, 28
RADIO AGE Blueprint Section.....	29-36
I. An Aperiodic Variometer Set....	29, 30, 35, 36
II. An Improved Baby Heterodyne..	31, 32, 33, 34
By John B. Rathbun	
Radiotorials	37
Radio in Other Lands; In Germany.....	39
Pickups and Hookups by Our Readers.....	41
With the Manufacturers.....	52
The Troubleshooter	46
RADIO AGE Data Sheets.....	48, 50
Corrected List of Broadcasting Stations.....	58

Radio Age is published monthly by
RADIO AGE, Inc.

Member: **Audit Bureau of Circulations.**

Advertising, Editorial and Publication Offices,
500 N. Dearborn St., Chicago

FREDERICK A. SMITH, *Editor*
RUSSELL H. HOPKINS, *Associate Editor*
FRANK D. PEARNE, *Technical Editor*
FELIX ANDERSON, *Technical Assistant*
LOUIS L. LEVY, *Circulation Manager*
M. B. SMITH, *Business Manager*

Advertising Manager

HARRY A. ACKERBURG

Eastern Representative

DAVIDSON & HEVEY, 17 West 42nd Street, New York City

Pacific Coast Representative

BENJAMIN LEVIN, 582 Market St., San Francisco.

Advertising forms close on the 1st of the month
preceding date of issue

Issued monthly. Vol. 3, No. 9. Subscription price, \$2.50 a year.

Entered as second-class matter April 4, 1924, at the post office at Chicago, Illinois, under the act of March 3, 1879, original entry April, 1922.

Copyright, 1924, by RADIO AGE, Inc.

A Chat With the Editor

RADIO AGE is off on its Fall drive. Beginning with this issue we are presenting an excellent group of technical and feature articles that are sure to emphasize this magazine's pre-eminent position as a practical help to constructors of receiving sets.

The first and most important of these consists of the RADIO AGE fac-simile blueprints—printed in blue and presented in such a way that they may be used as actual working drawings the same as any other blueprint.

To make this blueprint feature complete, we asked Mr. Rathbun to draw isometric and hookup diagrams for two world-beating circuits.

He did it with an improved "Baby Heterodyne" and an aperiodic variometer set. Mr. Rathbun's first "Baby Het" took the country by storm. This improved model will be no less popular, for it incorporates the latest ideas in simple and efficient set construction.

The aperiodic variometer hookup will meet the demands of fans who want something a little more complicated and yet easy to construct. These hookups, clearly illustrated with attractive blueprints, will be found in RADIO AGE'S new blueprint section, which begins in this issue on page 29 and runs through to page 36.

Four pages are devoted to the blueprints and four to the explanatory articles. Readers who wish may utilize the center pages consisting of from 29 to 36 and keep them for working aids and ready reference.

This blueprint feature is only a sample of what RADIO AGE has in store for this Fall and Winter. An abundance of the kind of technical articles that made RADIO AGE "The Magazine of the Hour" is in store for fans who are eager to start constructing sets again.

Keep a close watch on RADIO AGE, and if you let our hookups be your guide you will be assured of a successful Radio Winter.

Frederick Smith

—Editor, RADIO AGE



THE GREBE SYNCHROPHASE

TRADE MARK

"It is only when the cold season comes that we know the pine and cypress to be evergreens."

—Confucius

In the coming cold season be not surpassed by thy neighbor—set the pace with your Grebe Synchronphase.

Doctor Mu


A BROADCAST Receiver that marks another long step forward in radio design and establishes a new set of standards in craftsmanship.

Write for literature

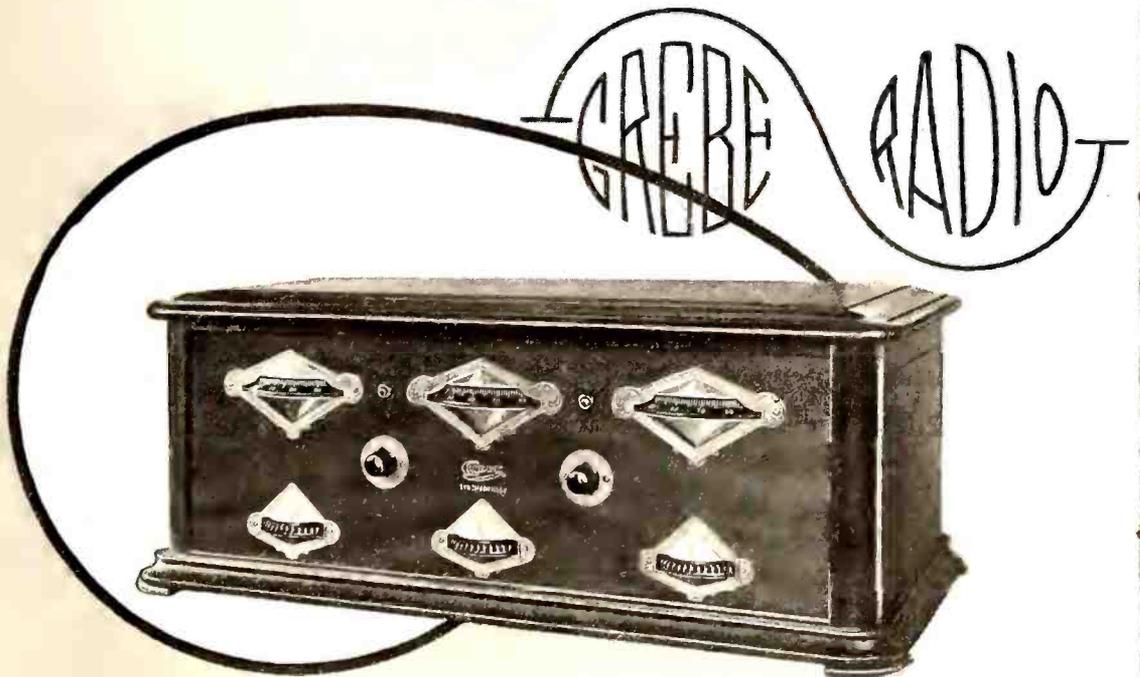A. H. GREBE & COMPANY, INC.

Van Wyck Blvd., Richmond Hill, N. Y.

Western Branch: 451 East 3rd St., Los Angeles, Cal.



ZENITH RADIO

Licensed under Armstrong U. S. Patent No. 1,119,149

TRADE MARK

“Zenith has united the ends of the earth”

—MacMillan



Before Donald B. MacMillan, world-famous Arctic explorer, said good-bye to civilization, his most important task was to choose a radio set.

For he, of all men, could afford to take no chances.

Read now his wireless message from the good ship “Bowdoin,” frozen fast in the ice of Smith Sound, eleven degrees from the North Pole:

“Am very thankful that Arctic Exploring Ship Bowdoin is equipped with complete ZENITH radio apparatus. Here at the top of the world, in darkness of great Arctic night, we have already listened to stations practically all over the United States, from Europe, and even from far-away Honolulu. ZENITH has united the ends of the earth.”
—“MacMillan”

The ZENITH used by Captain MacMillan is one of the earlier models—since improved by the addition of a *third stage of audio frequency*. And you can reach out as far as MacMillan does—even farther—with either Model 3R or Model 4R described just below. The quality, clarity, volume of the new ZENITH is unexcelled.



Super-Portable A six-tube radio set entirely self-contained—tubes, “A” batteries, “B” batteries, loud speaker and loop antenna complete. Highly selective. *Does not need to be opened to operate.* Packed into a small, beautifully finished traveling case—much smaller than the average suitcase—this new Zenith is the most compact set ever made, giving clarity, quality, volume and distance **\$230**

Model 3R (Illustrated above.) A specially designed distortionless *three-stage* amplifier in combination with the new and different Zenith three-circuit regenerative tuner—all in one cabinet. Extreme selectivity. Satisfactory reception over distances of 2,000 to 3,000 miles often accomplished, *using any ordinary loud speaker.* The model 3R is compact, graceful in line, and built in a highly finished mahogany cabinet..... **\$160**

Model 4R A specially designed three-circuit regenerative receiver in combination with an audion detector and *three-stage* audio-frequency amplifier, all in one cabinet. The Zenith 4R may be connected directly to any loud speaker *without* the use of other amplification for full phonograph volume, and reception may be satisfactorily accomplished over distances of more than 2,000 miles..... **\$85**

Write today or send coupon for full particulars and name of nearest dealer

ZENITH RADIO CORPORATION
Dept. 5-F Chicago, Illinois

Gentlemen:
Please send me illustrated literature on Zenith Radio.

Name.....

Address.....

**Zenith Radio Corporation
McCormick Building, Chicago, Ill.**

RADIO AGE

The Magazine of the Hour

M. B. Smith
Business Manager

A Monthly Publication
Devoted to Practical
Radio

Frederick A. Smith
Editor

How Careful Mounting Will Bring IMPROVED RECEPTION

By FRANK D. PEARNE

IN A RECENT issue of RADIO AGE we gave some of the reasons for poor reception, and the object of this article is to make plain to the layman just what takes place in the circuit when the coils and condensers are active, so that he may be better able to decide just how to mount the different parts of his set in such a way as to avoid as much as possible the interference and consequent losses occasioned in many of the sets in use today.

In the first place, it is necessary that he understand perfectly just how energy is passed from one coil to another without any electrical connection between them, or in other words, by induction. As explained before, when a current of electricity flows through a conductor, such a conductor is surrounded by invisible lines of force which are whirling about it either in one direction or the other.

The direction in which they whirl will of course depend upon the direction in which the current is flowing, and the number of lines and the distance they reach from the conductor will depend upon the amount of current flowing. Just how this would look if the lines were visible, is shown at "2" in Figure 1.

IF THE current flows along the conductor in the direction from the observer, then the lines would whirl in the direction in which the hands of a clock would move, and if it was flowing toward the observer, they would whirl in an anti-clockwise direction. Now if this conductor is wound up into a coil as shown at "1" in Figure 3, the lines will

arrange themselves as shown in this diagram. Some of them will continue to whirl about each turn, but most of them will join forces with the adjacent turns, resulting in a magnetic field as shown at "1," Figure 3.

Now as this whirling magnetic field advances in an outward direction and encounters another conductor as shown in Figure 1, and this conductor is forming a complete circuit of some kind, it offers a resistance to the lines passing through it and the lines bend, objecting to passing through it; but nevertheless the lines are forced out by new lines emanating from the original source and regardless of the resistance so offered, they bend around the conductor so far that they finally snap across it on the opposite side as shown at A, B, C and D, in Figure 1.

If the direction in which the lines are whirling is traced as they bend around this conductor, until they eventually snap across on the other side, it will be seen that the lines have been made to whirl in

a complete circle about the conductor resulting in the whirling magnetic field shown at "2" in Figure 1. Thus a magnetic field has been produced around it and a current will flow in this conductor, although it has no electrical connection whatever with the coil or conductor which is producing the magnetic field. This explains the question so often asked as to how the signals can pass from one circuit to another when there is no visible connection between them.

If this conductor is so located that it is out of the range of the advancing lines, then of course no current is set up in it and likewise it will be noted that the closer it is placed to the original source of the lines, the more of them will whirl about it and the more energy will be passed to it.

IF THIS conductor, however, is wound into the form of a coil or loop, as shown in Figure 2, which represents the lines cutting through a loop of a conductor which has been cut in two for simplicity, it will be seen that if this loop is placed at right angles to the loops or

turns which are producing the magnetic field, then the lines cut through both sides of the loop in the same direction, setting up opposing currents in both sides and resulting in one neutralizing the other. No current is produced, so long as the same number of lines cut through each side. Apparently, if one desires to so mount a coil in the receiving set, so that it will not be inductively connected to another coil, the best method is to set it

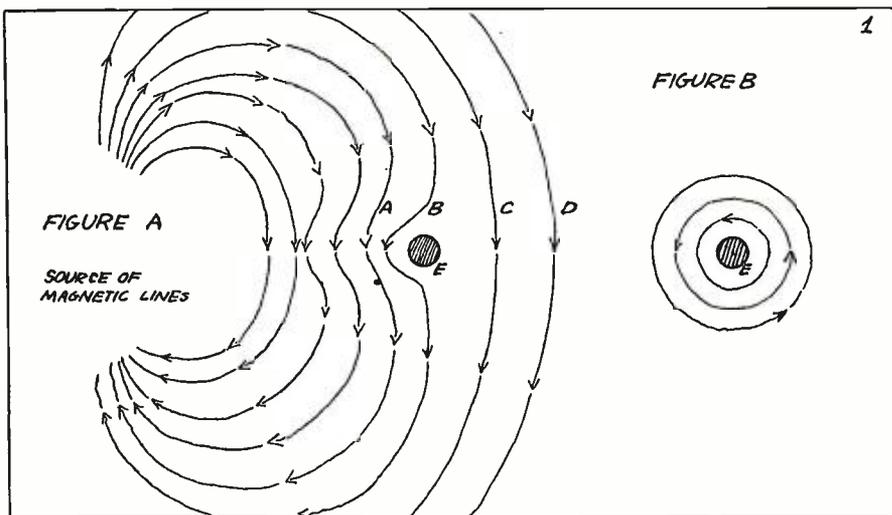


Figure 1. Showing how the whirling lines of magnetic force are made to cut through a conductor.

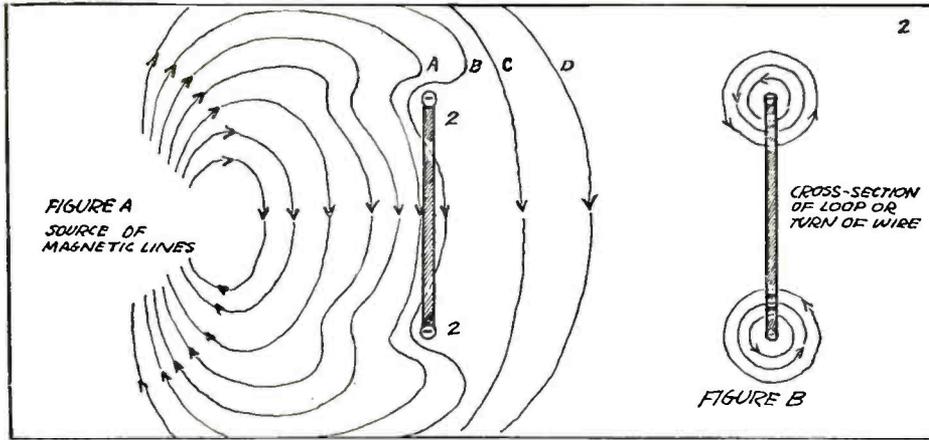


Figure 2. Showing how a loop or coil of wire set at right angles to an excited coil has opposing currents set up in each side, resulting in the neutralization of the current in the loop. This is what happens when your variocoupler is set at zero.

at exact right angles to it, but it must also be remembered that if it is not exactly at right angles, one side will be cut by a few more lines than the other and the result will be that the current in one side will be a little more than that in the other and a current which is equal to the difference between the two will flow.

This naturally will cause interference in the operation of the set which may be very slight, but it is interference just the same and the greater the angle of mounting diverges from an exact right angle, the greater will be the interference. This neutralizing effect is shown at "2" in Figure 2. If two coils which are not intended to be inductively connected are mounted as in Figure 3, care should be taken to mount them far enough apart so that the lines produced in one of them cannot reach the other, or, as shown in the diagram, some of the lines will cut through one side of the coil but will not reach the other side; or some might cut through both sides. But the side nearest the source would be affected more than the distant side, and in either case undesired currents would be produced and interference and losses would occur.

It must be remembered that because of the power required to force these lines past or through a conductor, as is usually stated, much of the energy is used up in this useless and harmful work. The only way to prevent such losses in a case of this type of mounting is to so locate the coils that they are beyond the range of

the magnetic field.

FIGURE 4 shows the ideal method of mounting two coils which are not inductively connected, but because of the danger of not getting them at exact right angles, it is best to keep them separated as far as possible and still consistent with short connecting wires. In this diagram the arrows shown at "2" explain the direction of the opposing currents set up in the two sides of the coil when set at an exact right angle to the coil "1," which is the original source of the magnetic field. Very often, however, it is necessary that certain coils be inductively connected to others and in such a case it is necessary to mount them in such a way that all the lines possible are made to cut through them, in which case they should hear the relationship shown in Figure 5.


Here we have one coil placed in inductive relation to the other. This is usually called a "coupling" of the two. It will be noticed that the winding of one is parallel to the other and a close inspection of this arrangement will show that the lines of force from the original source so cut through the turns of the coil "2" that they apparently whirl around them in opposite directions, but by carefully tracing them out in all positions it will be found that if the wire were laid out straight and parallel to the other, the lines would all be whirling in the same direction and consequently the maximum current would be developed in it. If the coils are separated

some distance, it would be called a loose coupling and if they were close together, or one was wound on top of the other, it would be a tight coupling. If the coil "2" should be tilted slightly with one side higher than the other, more lines would affect one side than the other. This also would tend to give a looser coupling.

This method of changing the coupling is used in the standard variocoupler which is so arranged that coil "2" is mounted on a shaft and is placed inside of coil "1." Then by turning the shaft, the turns of coil "2" may be made to be parallel to those of coil "1" or may be turned at right angles to them. It is obvious that any position between these two extremes may also be obtained. It is this clever idea which makes it possible to get such a fine adjustment when a variocoupler is used in a set.

OTHER methods of producing a variable coupling have been devised, one of the best being the use of two flat coils, such as the honey-comb and spider web type. These are usually mounted in such a way that they are either close together with the turns parallel to each other, or by means of a hinged mounting, one coil may be swung away from the other until the turns are at right angles. Either of these methods is very efficient, so far as efficiency in a radio set is concerned, and it is often a question as to which is the best. Naturally the honey-comb and spider web coils are better than the straight coil wound upon a tube, because they are so designed that their distributed capacity is less than that of the flat straight winding, and their magnetic fields are more concentrated, which would appear to make less danger from stray fields. But it is hard to determine just how far these stray fields will wander.

From this description of the action of the magnetic lines, the reader will observe that the most important thing to remember in the construction of his receiving set is to so arrange the apparatus that he is sure that no interference due to stray magnetic fields is taking place. The visible defects are easily seen and remedied, but the invisible troubles are very seldom corrected, simply because one is not aware of their presence; but if they are recognized and guarded against as carefully as the visible defects, then the results obtained will more than pay for the extra trouble and thought used to

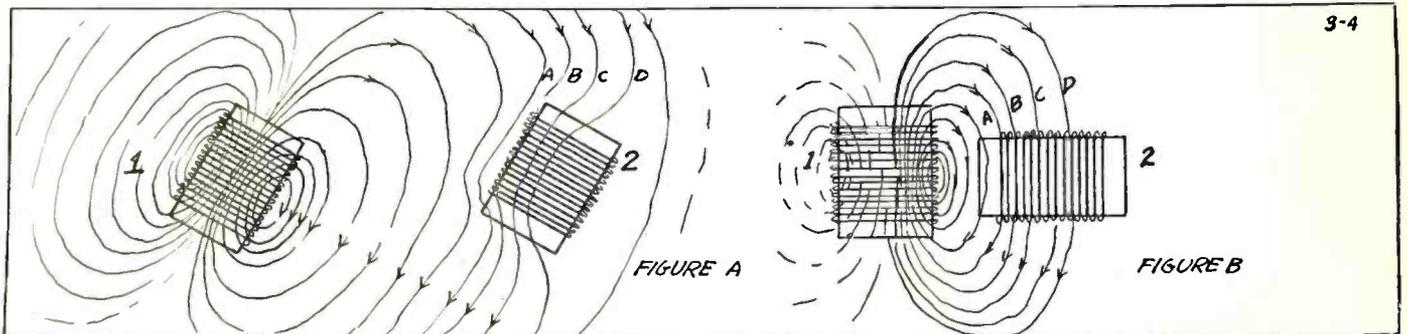

Figures 3 and 4. Figure A shows how magnetic lines from coil 1 cut through turns of coil 2 if they are placed too close together. This is important in neutrodyne and other radio frequency receivers. Figure B shows how losses are brought about when coils are properly placed at right angles. The lines from coil 1 cut through the coil 2 in the same manner as that of Figure 2, and no current is produced in coil 2.

eliminate them.

Now, how about the mounting of condensers in relation to the position of the coils? Here is another invisible problem. As stated in the August issue of RADIO AGE, stray magnetic fields which come in contact with any metal objects will also cause considerable loss of energy. Rapidly alternating currents will send out lines of force from a coil, which whirl first in one direction and then another. When such lines pass through a metal object, such as the plates of a condenser or a shield, they set up eddy currents in them. Just what this means is shown in Figure 6. Eddy currents derive their name from the fact that they arrange themselves in circular form similar to the circles appearing on the surface of the water, when several stones are dropped into it. They are sometimes spoken of as Foucault currents and are a source of loss of energy in any alternating current apparatus.

Naturally, a solid piece of metal is a very good conductor of electricity, and as these currents are set up in the metal itself, the resistance offered to them is very low. It is also known that the pressure which forces the current through the metal is very low, but because of this extremely low resistance, the very feeble pressure generated as the lines cut back and forth through the metal is able to force considerable current around in the circular form shown in Figure 6. In cases where a strong magnetic field cuts through a sheet of metal, it often happens that the current produced in the form of eddies is strong enough to heat the metal so hot that it cannot be touched safely by the hand.

THE currents used in radio reception, however, are not strong enough to produce eddy currents of sufficient strength to heat the metal condenser plates to such a degree that the heat can be noticed, but in a small way the same action takes place with these feeble currents, resulting in a dissipation of much needed energy.

Figure 7 shows how the lines cut through the metal plates of a variable condenser mounted across the end of a coil, which is enough to show that this is not a good method of mounting it. Here the lines naturally have to do considerable work in passing through the metal and in so doing not only do they waste energy in setting up the unnecessary eddy currents, but the resistance of the coil itself to the rapidly alternating current will be considerably increased, which will in turn cut down the current flowing through it. Condensers are not very often mounted in this way, although sometimes in order to save space on the panel, they are mounted inside of the coil. When this is done, the same condition exists and the lines are made to cut through the plates.

If mounted along the side of the coil, it will be seen that the plates will not be directly in the path of the lines, but even then some of them will pass through the plates, and while it is not a good way to mount them, it is better than the method shown in Figure 7. They should

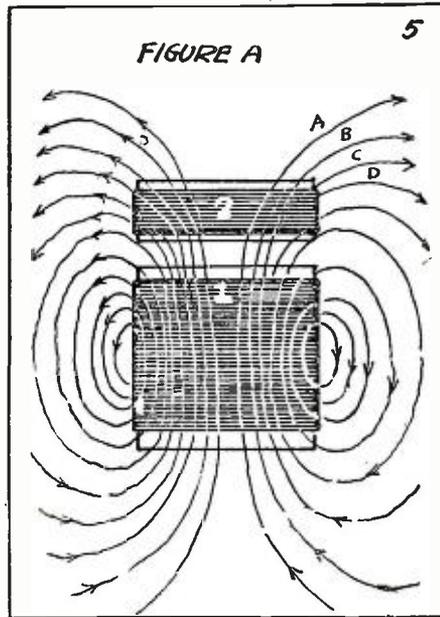


Figure 5. Showing how in this case all lines enter from the inside and pass out, producing maximum current in coil 2 by induction. This is the effect you obtain when your variocoupler is set at maximum.

really be mounted some distance from the coils if the best results are to be expected, and should be so located and in such a position that none of the lines from the stray magnetic fields can cut through the plates.

There are many fans who will dispute this theory in regard to mounting the condenser inside of the coil. They will say that they notice no bad effects from so doing, but it must be remembered that any one of these little things explained herein will not make any great appreciable difference in the action of the set, but a number of them in combination will make the greatest difference in the world. This article is written for the careful fan who wants to get the best possible results from his receiver and is willing to go to a little trouble to carefully lay out his work so as to avoid every unnecessary loss.

There are many sets in use today, the

owners of which very proudly state what marvelous results they are getting, but who do not know that they could far exceed their present reception if they would only pay some attention to the little things which are invisible, but which at the same time are absorbing much of the energy of the set.

A NOTICEABLE improvement in body capacity effects may be made by mounting the coils and condensers a few inches away from the panel. A support may be made on which to brace the apparatus.


However, one should not forget that when a piece of insulation is under the influence of an oscillating current, the molecules moving back and forth tend to absorb the energy with each reversal of the current. As a result, it has been seen—the energy that was absorbed is totally lost, as far as radio reception is concerned. A small extension will be necessary to run the condenser shaft through the panel, the same applying to the rotor of a coil.

This will do away with the popular but not practical method of shielding the entire set by a sheet of copper or tinfoil.

A number of prominent manufacturers ground all the rotors of coils, condensers and switch shafts or any other part of the set that comes in contact with the hand while manipulating the controls. The transformers should be mounted at right angles to each other and not too close together, unless shielded.

Body capacity is usually confined to the tuning controls, the effect being noticed when the hand is removed from the knob of the condenser or coil. Body capacity is usually noticed on distant stations and not so much on local stations. The average listener experiences the most body capacity in the grid circuit. However, it is noticed in many other parts of the circuit exclusive of the grid.

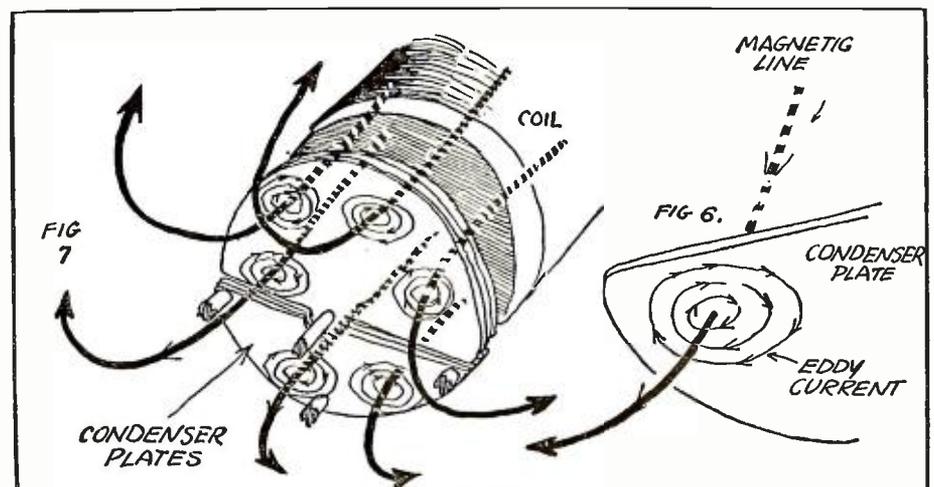On some sets the effect may even be noticed on the phones when the hands are brought in close proximity to them or if your head is near the set. This, however, is not so noticeable on the regular three circuit tuner as on the Ultra-Audion.




Figures 6 and 7. "A" shows the losses by eddy currents when a condenser is mounted on the end of a coil. The lines of force as indicated, in Figure B show the eddy current set up when the line cuts through the plate, which wastes power.

A Complete Radio Set on a Dial

By BERT WHITMAN


THERE are now about seven radio stations in Chicago that broadcast news reports, market reports, musical concerts and operas every day. All of these can be heard by any one who wishes to tune in accordingly.

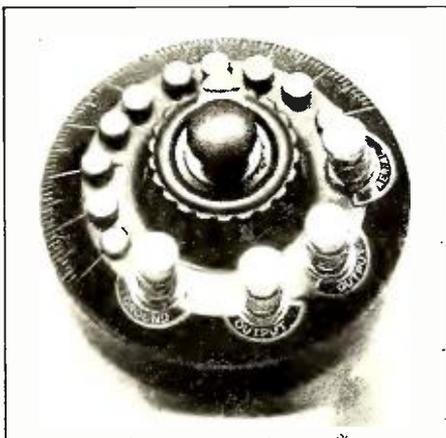Aside from using receivers of standard make, it is possible to home-construct a receiver, the simplicity of which involves only scant knowledge of radio. The set I am going to describe will be very efficient, providing you do not live in Pittsburg or some other point distant from Chicago and expect to hear all the Chicago stations.



A top view of the "Dial Crystal Receiver" showing the arrangement of the taps, binding posts and illustrating the manner in which the vernier knob of the condenser dial is used as the switch knob to vary the inductance.

A radio outfit is usually made up of an aerial to catch the incoming waves and also to catch waves that come in through the ground that are sent out by a broadcasting station. A coil is used so the listener can listen to one station at a time, thus avoiding two or more stations coming in at once, which would only result in a mass of noises. A crystal detector is used to change the waves, thus effecting the magnets in the phones; producing the

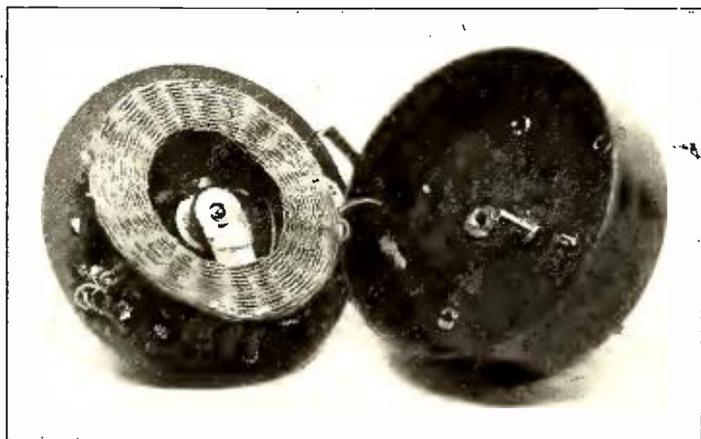

A view of the receiver "exploded" to show the manner in which the inductance is mounted. The crystal detector is mounted on case to the right, the mounting posts being visible in the photo.

sound which reaches the listening fan.

I will now proceed with the details of constructing this odd receiver. The entire set is made on an ordinary three-inch hard rubber dial. For the cabinet for the dial I used a discarded back of a dry cell case from a bicycle light. Where the numerals are marked off, drill a hole large enough for the taps to fit through, at the 10, 20, 30, 40, etc. Where the knob is to turn on a dial, in the middle equal with the shaft, drill a hole clear through. Use this for the switch-arm. The knob on the switch can be easily secured by using the top of a hard rubber binding post; for the shaft, use the shaft of an old rheostat; and for the arm of the switch-lever, you may use the arm of a rheostat. This shaft must go all the way through so it will hold on the crystal detector and the back of the battery case together with the dial. The pointer of this same old rheostat can be used to point out the taps from the switch-lever on the front of the dial.

Also drill four holes opposite of the taps and buy four plates marked aerial, ground phones, and another marked "phones." Place in the binding post where you just drilled the holes and put on the plates wherever desired.

How It's Done

Following are the details for making the coil: Secure a cork $1\frac{1}{2}$ inches at the top. Anchor 19 pins, one-sixteenth of an inch deep, nearly $\frac{1}{4}$ inch apart, in a straight line all around. Proceed by wrapping twice, the end of the wire securely around the pin you wish to start from. Start winding with No. 22 D. C. C. wire over two pins, under two pins, over two, under two, etc., until having gone around six times, and upon coming to the pin you started from, tap it about one-sixteenth of an inch farther from the same. Take these taps off every six turns and stagger it a little farther than the previous one. Continue this until you have as many taps on the coil as you drilled on the dial.


After you have finished this, leave in your pins and give the coil a heavy coat of shellac or any other liquid varnish for coils. After this dries, pull out the pins and slide off the coil. It is advisable to place a small strip of paper on the coil before you place in the pins, so after you shellac the coil and pull out the pins the coil will not stick to the cork. When you have finished this, scrape the insulation off the taps and solder them to the switch points. Solder all connections.

The crystal

detector was purchased at a Woolworth radio counter for ten cents, which serves the purpose very satisfactorily. After doing this, wire the set with the same wire you used to wind the coil with. Cover all the connections with spaghetti so it will make the connections more durable.

When this is finished, tighten up the bolt that holds the cabinet (back of the battery case) and the crystal detector and you have the complete receiver all ready to tune in the nearby stations.

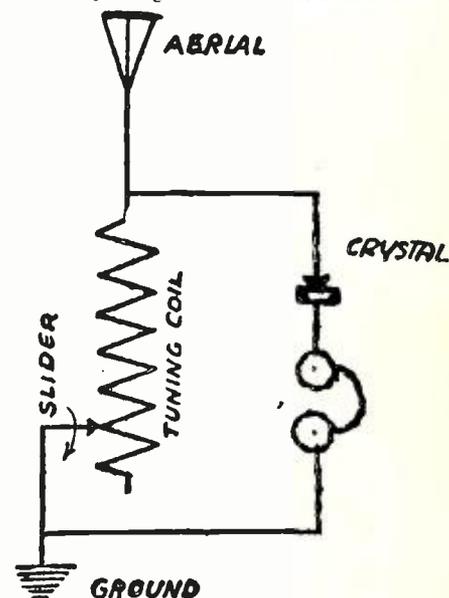To tune and work this set, buy a pair of good phones, about 100 feet of No. 14 copper aerial wire and about 50 feet of No. 14 rubber covered copper wire for your lead in and ground. Rig up your aerial, making it as long as possible. Attach your ground to the radiator. Put



A diagram illustrating the manner of wiring the various parts of the receiver. A .001 Mfd. condenser connected across the phone posts is often an aid to the detector in getting clearer signals.

your aerial to the aerial post on the set, your ground to the ground post on the set and the phones to the two posts marked "phones."

Now you are all ready to tune in. Start by moving the switch lever on the first tap and moving the detector about easily on the crystal to find a good spot. If it does not work on the first tap try the second, third, fourth, fifth and so on until you find the sensitive spot of the crystal. When you hear plainly, lay the set on table sideways to make it stay steady or lay the set in an ordinary glass. It will fit right on the top.

King of Belgium Honors American Citizen

Dr. L. H. Baekeland, of Yonkers, New York, president of the American Chemical Society and honorary professor of chemical engineering in Columbia University, has just been highly honored by King Albert of Belgium, who made him commander of the Order of Leopold. Doctor Baekeland has already received such distinctions as officer of the Legion of Honor of France and officer of the Crown of Belgium.

Interference: the How and Why of It

Why It Is Impossible to Tune Out Local Stations When DX May Be Eliminated

By HENRY A. WORNER

THE average radio fan quite often is confronted with the problem of coping with interference caused by nearby broadcasting stations, while he is engaged in the interesting and absorbing pastime known as "fishing for DX."

What seems to puzzle him especially is the fact that certain stations are apt to interfere more than others. For instance, he knows that one station allows him sufficient latitude for satisfactory tuning of an out-of-town station broadcasting on a wave length which differs from that of the home station by 15 meters, while another local station operating on a different wave length entirely prevents the reception of a moderately distant station, whose wave length differs from that of the interfering station by as much as 17 meters.


To make matters more perplexing, he learns that brother Jim, who lives in Pittsburgh, has on several occasions tuned out powerful KDKA transmitting on 326 meters, and received KGO, at Oakland, California, on the small margin of 14 meters difference in wave length.

Where's the Fault?

It is only natural to suppose that he is peeved over the matter, in view of the fact that Jim happens to be little more than a novice in matters radio, while he has dabbled in radio long enough to consider himself in the light of an expert. The fault cannot be with his set, he argues, for the reason that he built both, Jim's set and his own, and they are as alike as the proverbial peas in the equally proverbial pod, from binding post to phone jack.

IN HUNTING for the cause of the trouble he is apt to put the blame on the offending local station.

"They surely must be off their wave length," he complains, "for the other local station does not interfere to the same extent. The operating personnel must be becoming careless in their adjustments, causing a wave that is far from sharp." You see he has learned a little about such things as decrement, and other equally mysterious things, and comes to the conclusion that he has discovered the cause of it all by accusing the offending station.

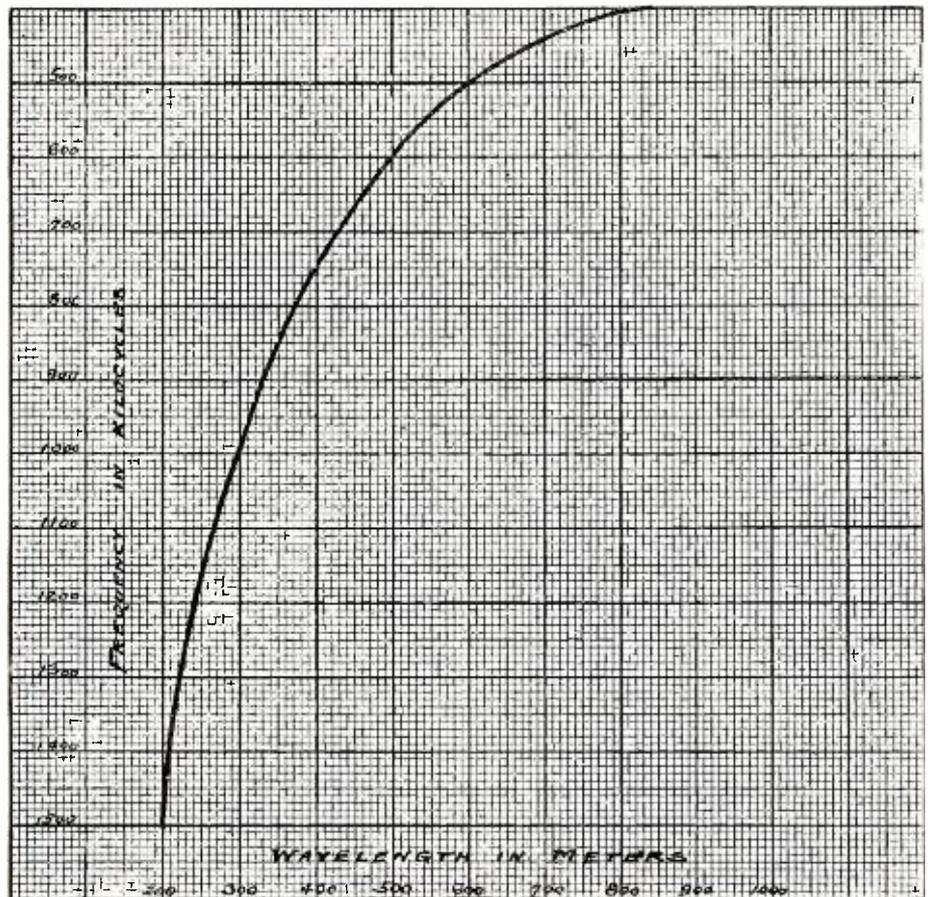

The chart above shows the relation of wave lengths to kilocycles. Notice especially how steep the curve bearing this relationship becomes as it increases in frequency and decreases in wave length.

On the face of it he seems to be right, but nevertheless he is entirely wrong. The cause of complaint is to be found elsewhere, as I shall endeavor to demonstrate. In the first place, it is a mistake to associate broadcasting stations with their wave length assignments, as this practice leads to just such ambiguities as this. One should think in terms of frequencies instead of wave length, in calculating the amount of dial space a certain station ought to occupy.

The relation of wave length to frequency is not, graphically speaking, a straight line, but forms a rather steep curve, as may be observed in Fig. 1. It will be noted that a frequency of 1,500 kilocycles (1,500,000 cycles) produces a radio wave measuring 200 meters from crest to crest, while a wave 300 meters long is created by a frequency of 1,000 kilocycles. The average person is prone to jump at conclusions in a good many things, and radio is no exception. Having discovered at some time that the difference in kilocycles between 200 and 300 meters is 500, he concludes by inference that a hundred meters' difference equal a frequency difference of 500,000 cycles. A second glance at the graph will illustrate to the reader that

such is far from being the case. We find that whereas 300 meters has a frequency of 1,000 kilocycles, the frequency for 400 meters is 750 kilocycles—a difference of 250 kilocycles! We also find that 500 meters equals 600 kilocycles, and 600 meters is the equivalent of 500 kilocycles.

How They Stand

The relationship of wave length to frequency is clearly expressed by the formula:

$$\text{Frequency in kilocycles} = \frac{300,000}{\text{Wave length in meters}}$$

At this juncture, the reader will begin to see a glimmer of light. However, he fails to see the connection between that and the fact that a station like WEA, for instance, transmitting at a frequency of 610kc. (492 meters) is practically annihilated in Philadelphia by WIP or WOO, operating on a frequency of 590 kc. (509 meters)—or a difference of 20,000 cycles.

EVEN the novice in radio knows that in order to hear a station one must adjust the receiver to resonance with the

frequency of the carrier wave on which the station is operating. He is also aware that a nearby station allows him considerable latitude in the matter of accurate dialing, whereas a more distant station requires a little skill in the matter of tuning. Why does a local station "smear" itself over a considerable part of the dial? And why is a margin of 17 meters difference in wave length insufficient to tune in a distant station through local interference, in one instance, and 15 meters or even 14 meters difference, in another instance, plenty leeway to accomplish that very thing? These are questions that not only puzzle the novice but in a great many cases are conundrums to the seasoned fan as well.

The answer lies in the fact that one has to deal not with a single frequency but with a wide band of different frequencies in radiophone transmission and reception. The carrier wave of a broadcasting station upon which the voice and music is carried is the wave length upon which the station is permitted to operate. The wave length is determined by the oscillation constants of the transmitting apparatus, before the voice or music is impressed on it. The peak of this carrier frequency is quite sharply defined even in a local station.

When the carrier wave of a station is being modulated with the frequencies of the speech and music impressed upon the diaphragm of the microphone, the result is a composite wave, which modifies the character of the single carrier frequency to a considerable extent. Let us see just how this is effected. It is customary in music to refer to the oscillation of a musical note by the name of vibration. In effect, a vibration and a cycle of oscillation are identically the same thing.

How Music Vibrates

A musical note is the result of vibrations or oscillations of a known frequency, which remains quite constant. When the pitch of the note is altered, the frequency of vibration is automatically changed. We will say that the musical note, referred to on the piano as Middle-C vibrates about 256 times per second to and fro. (Its actual vibration constant according to the International Standard of Pitch is 258.9.) That is to say, it oscillates at a frequency of 256 cycles per second. Since the frequency of a note doubles with each octave, it follows that the C one octave above Middle-C has an oscillation constant of, say, 512 cycles per second. The next C above would register 1,024 cycles and so forth, until we reach the uppermost C (last white key) on the piano which oscillates at the rate of 4,096 cycles per second.

Some instruments of the orchestra go still higher than that. The piccolo flute can produce notes whose frequencies are more than double that of the uppermost note on the piano, while the violin, when being played in the seventh position, reaches notes that are close to the upper audibility limit of the human ear, which is in the neighborhood of 10,000 cycles.

SO MUCH for the frequencies of fundamental tones. A fundamental tone is

one having practically no harmonics or overtones. A tuning fork is the only device capable of producing a pure note practically free from harmonics. All musical instruments produce notes which have combined with them a certain number of these by-tones, or harmonics. As a matter of fact, were it not for the harmonics, all music would sound dull and there would be no distinction between the various instruments. It is due to the overtones that we are able to distinguish between the various instruments of the orchestra.

These harmonics supply that colorful



Fotograms. N. Y.

NEW YORK STATION OPENS

Mayor John F. Hylan of New York is shown officially opening WNYC, the \$50,000 municipal broadcasting station to be used by New York City.

variety and exquisite shading so much in evidence in the modern orchestra, thereby adding enormously to our enjoyment of symphony concerts, not alone over the radio, but also in the concert hall, auditorium and theater. Thus, by means of these overtones we are enabled to distinguish a violin from a flute, a cornet from a saxophone and a xylophone from a piano. These overtones are therefore vitally necessary to the full enjoyment of music. There are fifteen important harmonics for every principal or fundamental note in music. All of these are not equally prominent. Chimes, carillons and church bells are richer in overtones than any other tone-producing devices.

If we consider the first ten harmonics as of most importance, let us see how they materially affect the music frequencies. High-C is the C situated two octaves above Middle-C on the piano and is the ultimate goal of every ambitious soprano. It is considered the upper limit of the range of the female voice in song and has a vibration constant of 1,024 cycles. The first harmonic has twice the frequency of the fundamental note—in our case 2,048 vibrations. The second harmonic generates frequencies three times that of the principal note, or 3,072 cycles per second—a little more than 3 kilocycles. The tenth harmonic has the enormous frequency of 11,264 cycles, which is over $11\frac{1}{4}$ kilocycles. The lowest note of the Great Organ has a frequency of 32 or less cycles. We must therefore take into account a musical frequency band of over 11 kilocycles.

How Harmonics Function

As there is a plus and minus component in a radio wave, the carrier frequency is therefore modulated by a voice frequency alternately adding and detracting 11 kilocycles. A broadcasting station transmitting on a carrier frequency of 610 kilocycles therefore occupies a frequency band extending between 599 and 621 kilocycles. Expressed in wave length figures, this means that a station operating on 492 meters really covers a wave band lying between 501 and 483 meters. A local station operating on a carrier frequency of 500 kc. (509 meters) causes interference with the station transmitting on 492 meters, by reason of the fact that it blankets a wave band lying between 499 and 518 meters. (601 and 579 kc. respectively.)

A station like WOO occupies a wave-band 19 meters wide, while WEAJ uses one only 18 meters in width. WDAR on a frequency of 760 kilocycles occupies a band of only 11 meters with the same 22 kilocycle variation. It is therefore possible to tune out this station in Philadelphia and tune in WGY in Schenectady on 380 meters.

NOW let us see how much better we fare with a station using a comparatively low wave length. Take KDKA broadcasting on 326 meters (920 kc.). A listener in Pittsburgh desiring to hear KGO in Oakland, California, on 312 meters (960 kc.) has no difficulty in tuning out the Pittsburgh station. 11 kilocycles either side of 920 is the frequency range 909-931 kc. Transposed into wave length this equals a band barely extending 8 meters wide. This goes to show that the lower the wave length, the sharper will be the tuning.

The above covers all cases where the interfering station is a local station. The situation will be improved materially as the distance between the interfering station and the receiver is increased. With the interference located some distance away from the listener, a number of the overtones are lost in transmission, which has the effect of narrowing the operating band of the station, consequently lessening its interference possibilities.

(Continued on page 57)

Using One Tuning Control for Hair's Breadth SELECTIVITY

By BRAINARD FOOTE

Test of Best Circuits Now in Their Simplicity

IT IS a peculiar, yet universally recognized fact, that any single tube regenerative receiver will respond to broadcast signals from stations within the receiving radius of a set employing a radio frequency amplifier. This paradox may perhaps be best explained by the simple statement that a certain amount of signal energy is required to actuate any tube, whether it be the detector or the first tube of a radio frequency amplifier. The use of radio frequency amplification does, however, magnify the weak energy to such an extent that broadcasting from distant points may be more loudly heard with such an amplifier than without one.

The fact remains, nevertheless, that a single detector tube, properly connected and used by a keen-eared listener, will have practically the same receiving range as any other form of receiver with the possible exception of the super-heterodyne. There is little to be said in favor of this or that circuit, providing it is regenerative and the best of apparatus is chosen. The widespread differences of opinion regarding various forms of single tube circuits appear to arise mainly because a highly satisfactory form of one circuit has been compared with but a mediocre representative of some other type. To me it seems that one is as good as another as far as actual distance goes, but that there really is considerable difference in selectivity and ease of operation.

ASSUMING fairly equal sensitivity for all single tube circuits, then, they are not to be compared on this basis, but on

selectiveness and simplicity of operation. Tendency toward radiation is also a most important factor to think about. Most regenerative receivers involve a most "ticklish" control of oscillation in addition to one or two controls for adjusting the set to the various wave lengths. Tickler feedback receivers and those having plate variometers come in this classification and are for that reason rather difficult to operate handily. In addition to these two objections, I might cite the natural tendency of operators of such equipment to permit the tube to oscillate and to hunt for the carrier wave or "whistle" while feeling around in the dark for some distant station.

Back to DeForest

In searching for a circuit which is not only selective and easy to use but which is not critical in its regeneration control also, we must hark back to the early days of radio when Dr. Lee DeForest brought out the Ultra-Audion circuit. Most circuits have a secondary coil with one end connected to the grid condenser and the other end to the filament. The Ultra-Audion, on the other hand, uses the grid condenser connection for one end but connects the other to the plate instead. This normally maintains the circuit in oscillation and depends upon the capacity

of the antenna to absorb energy enough to stop oscillation. Heretofore the circuit has been objected to on the ground that a "hum" was picked up from the electric light line. This was due to the absence of the grid return wire to the filament and to the direct connection of the antenna to the grid coil.

In overcoming the hum and providing means for substituting something else for the antenna's absorption, I found it most satisfactory to use the so-called "aperiodic" or untuned antenna system and to insert a variable condenser as a by-pass across the phones. This eliminates the hum and provides a sure control of regeneration—and a non-critical one. The double circuit plan also increases the selectiveness—something that the Ultra-Audion arrangement has long been famous for, anyway.


In view of the fact that the set is usually oscillating except when the primary and secondary is tuned to the natural period or wave length of the antenna, a condenser, preferably one of .001 mfd., may be inserted in the antenna or ground lead going to the primary of the variocoupler.

When a set is oscillating, the incoming carrier wave will be found to tune very sharp.

As a result it would be advisable to exercise great care in the tuning. This will apply to the tuning condenser.

The Choice of Parts

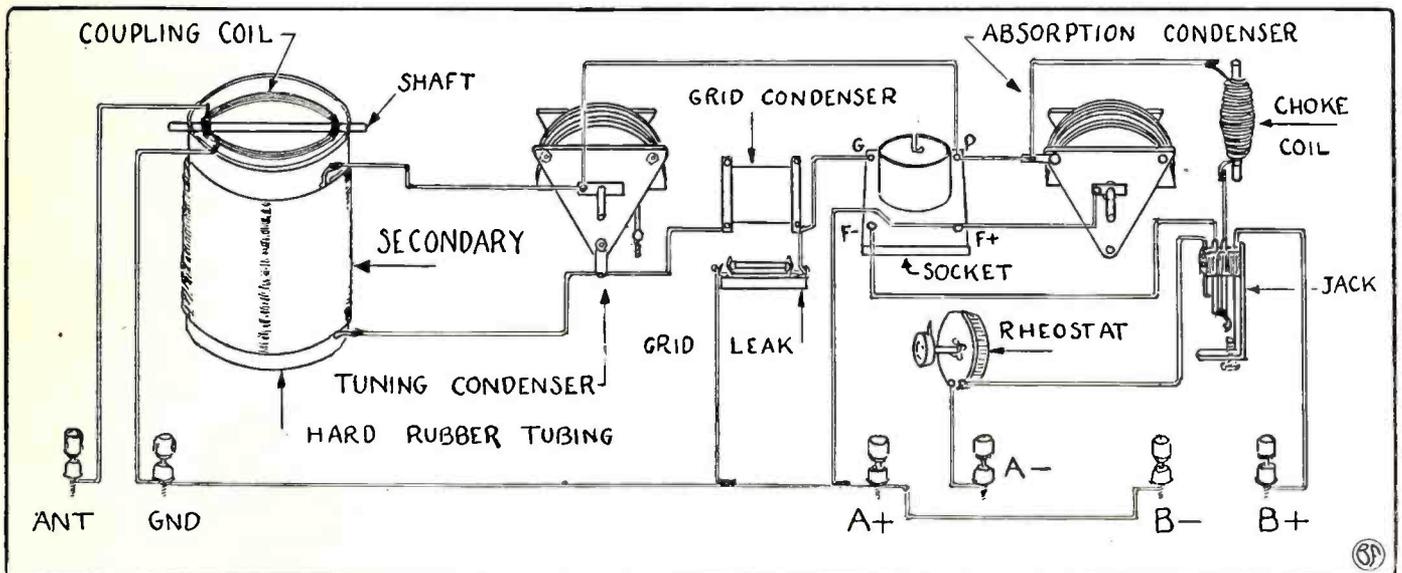I decided to use only the highest grade of apparatus and insulation; to use large wire for the coils, the best kind of grid



Circuit diagram of the Ultra-Audion receiver. There aren't many parts to assemble and the circuit is simple in operation. Special features are the antenna coupling coil, the low capacity grid condenser, the absorption condenser and the R.F. choke coil which keeps radio frequency current out of the phones.

.0005 variable condenser with or without vernier.


The Coils

THE ANTENNA coupling coil consists of 15 turns of the No. 16 wire wound first on a bottle or other cylindrical form about 3 inches in diameter. Two pieces of bicycle tape are used to hold the coil in place as it is slipped off the winding form. The secondary consists of 42 turns of the No. 16 wire wound on the tubing very tightly and smoothly. Two holes through the tubing at each end of the winding serve to hold the ends in place. Mount the coupling coil at one end, and the winding of the secondary should be started right near the other end of the tubing so that there will be room enough for the shaft of the coupling coil. Drill two holes so that the shaft will fit rather snugly and tie the coil to the shaft with small pieces of insulated wire. If the shaft is rather large, it may facilitate matters to divide the coupling coil into two parts and put the shaft in the middle. White thread can be used to fasten the parts together as illustrated. The coil should be held in the center of the tubing by two washers which press tightly against the tube and the coil. These may be sawed from a length of fiber tubing. The coupling coil is adjusted to suit the particular aerial in use and then not touched again. Two short lengths of flexible insulated wire had best be used for connecting the coil to the bus leads to the antenna and ground binding posts. The tubing may be mounted to the sub-panel by two small brass angles with 6-32 machine screws in the panel and tubing for support.

Two aluminum sheets are cut 2x2 inches with a lug about 1/4 inch wide on one corner and extending about 1/2 inch out from the edge. The sheets are hammered flat. Then six strips of 1/16 inch thick hard rubber are cut with a hacksaw 1/4 inch wide and 2 1/2 inches long. Each has a hole made with a No. 27 drill at each end, about 1/8 inch in from the end. Four 6-32 machine screws 1/2 inch long complete the parts and the sketch shows the assembly. The lugs are bent over the end of one strip to make contact underneath the screw head or nut—one lug connected at each side. The bus bar may be soldered directly to the screw heads marked "X" on the sketch. The plates should be parallel and 1/16 inch apart. This form of condenser is simple to make and highly efficient—air is the most perfect dielectric.

The choke coil is made with about 500 turns of the No. 30

wire wound on a short length of dowel stick, hard rubber rod or fiber rod. A convenient way to wind this is to fasten the rod in the chuck of a wheel brace—clamp the wheel brace in a vise, drill two little holes in the rod to fasten the ends of the wire and wind it on. The number of turns is of no importance, the only essential being that it have enough so that the natural wave length of the choke coil is well above the broadcast band. At least 300 turns should be used, and if you wind enough wire so that the coil is about 3/4 inch thick, you'll have plenty.

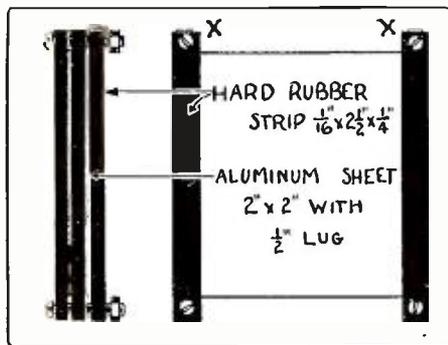

Details of the grid condenser. Two sheets of aluminum and six narrow strips of hard rubber form the condenser, with four screws for the assembly. The most efficient dielectric—air—is employed.

Making the Connections

LITTLE need be said about the method of mounting, as this is shown in the illustrations well enough. In wiring, do not use right-angled bends throughout but run the connecting leads the shortest distance, keeping the following wires at least one inch from all others:

The wire from lower end of secondary to stator connection of condenser;

The wire from stator end of condenser to grid condenser;

The wire from grid condenser to grid;

The wire from the grid condenser to grid leak;

The wire from upper end of secondary to rotor of condenser;

The wire from rotor of condenser to plate;

The wire from plate to stator of absorption condenser;

The wire from stator of absorption condenser to choke coil.

Make these leads short and direct. Some of them need not be made beneath the sub-panel because the points mentioned are nearby above it. The other wires may be run close together, at right angles, or any other way that suits the maker of the outfit.

Use very little soldering flux and wipe off any black deposit after the connections have been soldered. Be careful of the connections to the jack. The frame is joined to the B plus post and the long contact spring to the choke coil. The other two are in the negative filament circuit, for the insertion of the phone plug causes them to come into contact and light the tube.

It is very important that you connect the grid leak to the positive side of the filament, as the tube will not function any other way. Moreover, ground the positive of the filament, as shown in the circuit diagram.

I have found the WD12 to give as good results as any other tube as far as distance is concerned. Just the least bit better volume can be had on the local stations with the UV201A or C301A. The UV199 is also satisfactory, and the rheostat specified will take care of any of them. A single dry cell forms the "A" battery for the WD12 (or C12 or WD11) but with the 201A or 301A tube, four dry cells are needed or else a 6 volt storage battery. The UV200 does not appear to be quite as satisfactory, and inasmuch as the other tubes require only about one-fourth as much current, they are more economical besides being slightly better. Forty-five volts of "B" battery are used for the plate supply.

For local reception, results are quite good with a connection to the electric light line through a .0005 fixed condenser or a plug. The very best aerial is a single straight wire from 75 to 125 feet long, without too long a lead-in. The ground connection is made to a clamp on the radiator or water pipe in the customary manner.

Set the coupling coil at a 45-degree angle to the secondary and the absorption condenser at zero. After making all connections except those to the "B" battery, insert
(Continued on page 55)



Doesn't it look simple? The rheostat's inside and is always set at the right value. The tube lights when the phone plug is pushed in. The left hand condenser has a vernier control and accomplishes the tuning.

Surviving a "Radio Summer"

By J. A. CALLANAN

[As Broadcast for RADIO AGE from Station WTAY.]

For the past few years, ever since the inception of Radio, sales have decreased during the Summer for no reason at all. As a matter of fact, theoretically, trade activities should be greater in the Summer than in the Winter, and undoubtedly during this and ensuing years that condition will prevail.

Heretofore the annual falling off of interest in radio communication has been erroneously ascribed to the belief that seasonal and atmospheric conditions prohibited a full measure of realization of the pleasures attending reception. I have analyzed this subject and have drawn the conclusion that this waning interest is in a much larger measure due to that irresistible call of the Great Out-of-Doors which makes itself felt as the Summer days come on.

But today there is a rival to that call, if we are to discern the signs of the times, from the innumerable inquiries as to the feasibility and the kind of a radio receiver to take on vacations. If it is a truism that a radio set in the home has become an essential of the first order, it is becoming equally a truism that the fan and his receiver are not readily divorced.

Nearly everybody who has a car and goes motoring, camping or touring this year will take along a radio set. No regrets need be experienced for leaving your radio receiver behind you as you journey forth into the open for a day, a week or a month, as the case may be.

Broadcasting will this year, as never before, receive the attention of the fan. All broadcasting stations will be alert for the advantages radio presents as a medium of entertainment through the national interest in vital political events during the Summer. Transmission of such programs is without precedent during the period of time in which radio communication has so gripped the popular mind, as no other one thing has ever done.

Trade has awakened to a new realization that there is to be no interruption. Manufacturers are preparing to supply demands for portable sets. RADIO AGE is deluged with an insistent demand for circuits and data for home construction, and is meeting in current issues these needs by a variety of practical suggestions for making and installing radio receivers in every conceivable way for adaptation to camper, motor and tourist requirements.

Let us consider for a moment the prejudice that admittedly exists in many minds as to the adverse conditions affecting radio reception during the Summer months. Let us admit that radio is variable; that its fascination is in its erratic and elusive characteristics. It unfolds many mysteries, many forces that are not within the ken or control of man. Those much over-worked terms, "Static and Atmospherics," however, carry many burdens which are not their own. While these forces in themselves remain constant in

their seasonal manifestations, the refinements of man-made devices are immeasurable and have minimized the ill effects which hitherto have seemed insurmountable. We may always encounter trouble, more or less, at one time or another and must not be surprised or dismayed at its

In this sketchy little talk I am not forgetting those of my listeners who will not go vacationing. For them I am suggesting the opportunities for fruitful work to be tackled during the Summer, rather than putting your radio set in the cellar for that hot spell when you think that



WHY DO GIRLS LIKE BARBER SHOPS?

Kadel & Herbert.

Surely not because they like the barber's time-worn chatter. Maybe the picture will explain why barber shops are no longer dens of torture for girls getting their hair bobbed. The radio set in the background keeps them occupied while the barber shears their locks. Lunella Young is seated in the chair, being assisted through the clipping ordeal by an ethereal entertainment.

form; but these factors which have seemed a serious deterrent to the uninitiated are to the technical mind a foundation upon which the art is building constantly to embrace larger and larger possibilities. Out of this experience the layman is becoming more and more familiar with underlying principles because he finds it a willing medium of helpfulness in diagnosing and correcting his troubles as they arise.

static is going to be too bothersome. Don't. Rather, work your set for all it is worth and devise ways and means for doing away with that disturber. RADIO AGE will give valuable discussions on remedial measures of proven value. Don't forget that the man who invents a device to overcome any one type of interfering medium will go down in history as one of the outstanding inventors of the age.

FIG 2.

CONNECTION CHART

TUBE	GRID RETURN			PLATE RETURN		
	DETECTOR	RADIO	AUDIO	DETECTOR	RADIO	AUDIO
C-301A UV201A	+ FILAMENT			+ FILAMENT		
DITTO		POTENTIOMETER OR - FILAMENT			+ FILAMENT	
DITTO			-FILAMENT OR - C BATTERY			+ FILAMENT
C-299 UV-199	+ FILAMENT			+ FILAMENT		
DITTO		POTENTIOMETER OR - FILAMENT			+FILAMENT	
DITTO			-FILAMENT OR - C BATTERY			+FILAMENT
WD-11 WD-12 C-11 C-12	+ FILAMENT			+ FILAMENT		
DITTO		POTENTIOMETER OR - FILAMENT			+FILAMENT	
DITTO			-FILAMENT OR - C BATTERY			+ FILAMENT
C-300 UV-200	- FILAMENT			POTENTIOMETER		
RHEOSTAT	- F	- F	- F	- F	- F	- F

the grid and plate return leads, as well as the location of the rheostat.

While these rules apply to most tubes and circuits, there will be exceptions, and the most effective way to find them is to first sketch them out on paper and then work them out in practice. If the chart connections fail to give the expected results, the only certain recourse is experiment and trial. Invariably after one or two trials the proper one will be found.

Detector Tubes

We find in popular demand two types of detector tubes. Recently we mentioned that while we considered the UV200 tube a superior tube than the UV201A from a standpoint of a detector, this was an entirely personal view, and does not in any way mean that the UV201A is worthless in this capacity. In fact, it functions admirably in the detector socket, but to make it do so, we must use an entirely different set of connections than that of the UV200. Figure 3 illustrates the connections for the UV200 when employed as a detector. The UV201A should be connected in the manner shown at Figure 4 when used as detectors, as should all the high vacuum tubes. The UV100, WD11, WD12, C209, C301A, C11 and C12 all are classified as high vacuum tubes, and can all be used as detectors.

The connection of the grid return on a detector tube depends largely upon the type of tube used. Gas tubes work best with the grid return lead connected to

the negative side of the filament. When high vacuum tubes are used as detectors, the general rule is to connect the grid return lead to the positive side of the filament when grid leak and condenser are used. The difference lies in the corresponding characteristics of the tube with regard to their action as amplifiers.

A few words might be said here about the action of the grid condenser and grid leak, and why they are so important in getting the proper quality of signal at the output end of the circuit. Referring to Figure 3, we have a circuit designed to give the greatest possible output to the amplifier circuit. To effect this condition, the grid leak resistance should be high compared with the input resistance of the tube; that is, about two megohms or more.

When a signal voltage is applied to the input terminals (in this case the secondary of the tuner), a voltage is built up across the resistance R, by the action of the rectifying characteristics of the grid circuit. This voltage is alternating in nature according to the modulation frequency. The condenser C bypasses the radio signal around the grid leak. When the voltage across R rises, this condenser becomes charged and after the wave has passed this charge must leak off by the way of the grid leak, so that the grid of the tube will be restored to its original potential.

Now if the grid leak and condenser are not properly proportioned, so that the charging current can leak off at the proper instant, we have distortion. The

rate of discharge of the radio frequency signal which has been impressed upon the grid of the tube depends upon the proper choice of the grid leak and condenser. The customary way to obtain this proper action is to purchase a grid condenser having as the lowest consistent reactance with respect to the operating range of radio frequencies, and then make the grid leak have as high a resistance as we can without introducing distortion.

If static is strong, or you are near a strong local station, this idea does not work out very well, as the charges are excessive, and will not leak off fast enough when a high resistance leak is used. The high grid leak value should be used only on weak signals.

Many people question why a low resistance leak should be used with the gas content tubes, and this can be explained by saying that the gas which is allowed to remain in the tube during the process of manufacture furnishes in connection with irregularities in the plate and grid characteristics a conducting path for the charges to leak off. When the action described fails to accomplish this important leakage path, we use an additional grid leak to help it along.


In some circuits, especially radio frequency amplifying, we find that there are connections (usually when impedances are used) which do not provide a direct current path through to the ground, and in such cases we connect the grid leak from the grid post to the positive filament. The Ultra-Audion circuit is another example of this case.

Radio Frequency


The grid return connection of the tube, when used as a radio frequency amplifier, is entirely dependent upon the nature of the circuit used. When potentiometers are used to suppress oscillations by varying the polarity impressed upon the grid, the grid return connection usually is made to the movable arm of the potentiometer, as shown in Figure 5. The action of the potentiometer in the circuit is to increase very finely the negative or positive charges on the grid.

When the movable arm is advanced toward the positive filament side of the resistance segment, the losses of the grid are increased, and the objectionable oscillations are suppressed. When the arm is moved toward the negative side, the grid losses are decreased, and full amplification value is had of the tube; but usually this state is not entirely possible, for as soon as the plate circuit comes into resonance with the grid circuit of the tube, oscillations start and we encounter distortion and radiation.

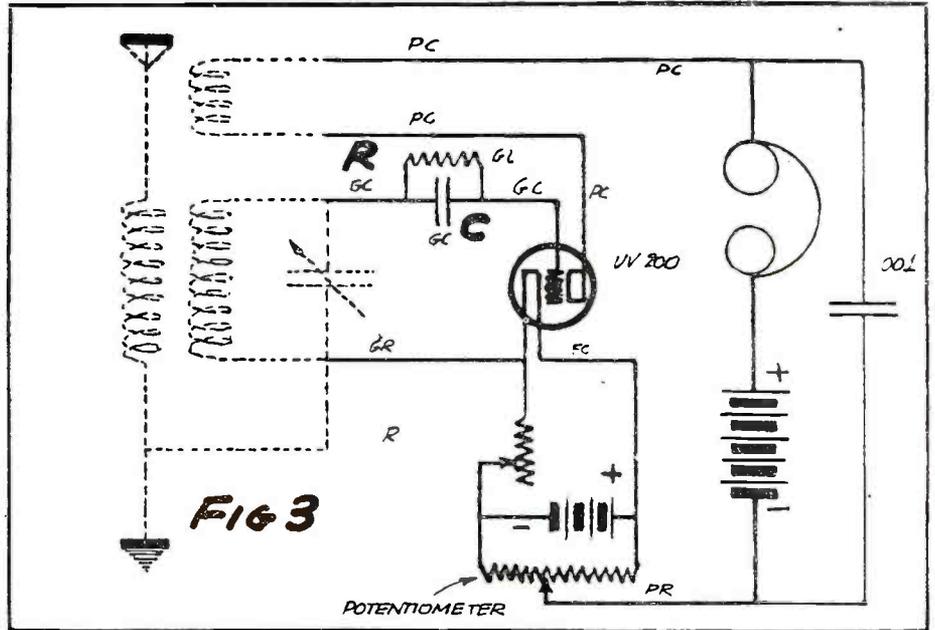
When some other means of stabilization is used, as an example the Neutro-



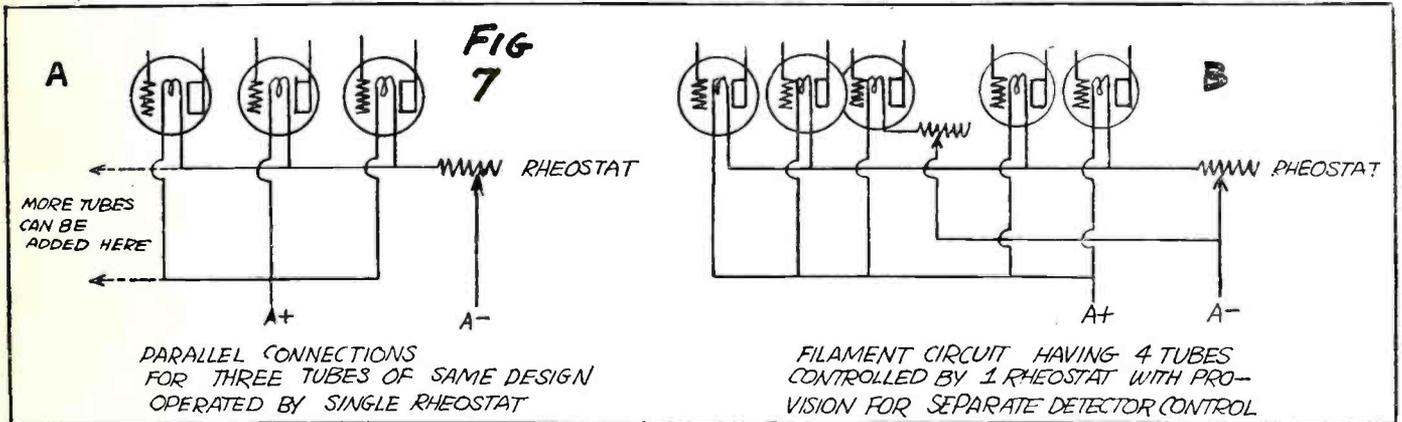These are the connections you should use when you employ a UV200 or other soft tube as a detector.



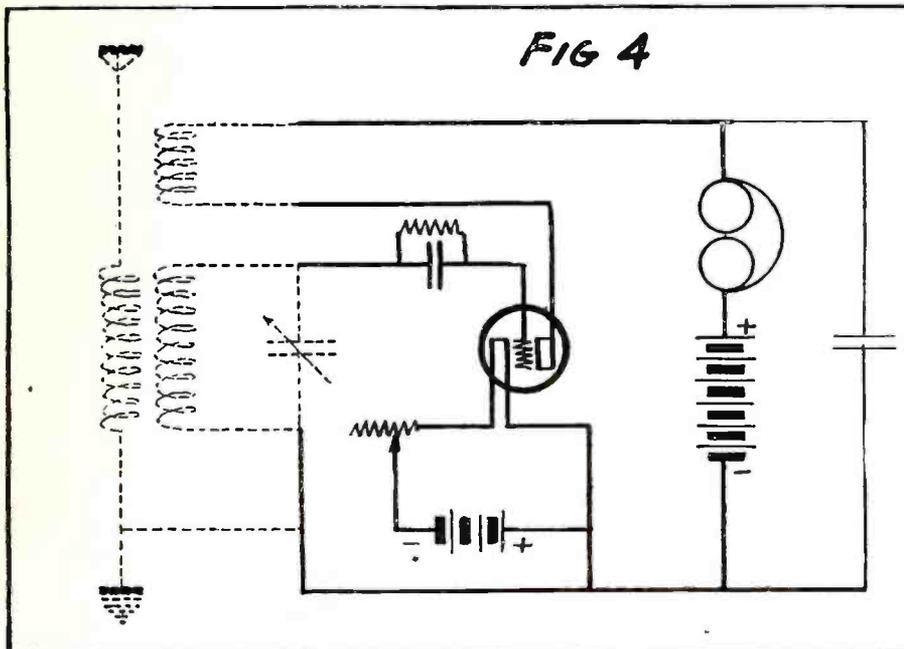The filament circuits of several vacuum tubes may be controlled simultaneously with a single rheostat as shown on the wiring diagram above. This type of filament control is especially useful in multitube sets such as the super-heterodyne.




When a UV or WD tube is employed as a detector, the connections illustrated above should be used for the most effective results.

dyne, Rice and other circuits which balance off the plate and grid condenser action and oscillations, the grid return leads of these amplifiers should be connected to the negative filament. This gives full amplification efficiency, the obnoxious oscillations having been suppressed by or rather prevented by the neutralization of the plate and grid circuits.

Potentiometer Losses

In radio frequency circuits, where a potentiometer is used to effect this stabilization, we introduce a great deal of losses, and as a consequence the strength of the signals suffer. It is therefore best when making any type of radio frequency amplifier which uses a potentiometer to first try the circuit with the grid return of the first radio frequency amplifier connected to the movable arm of the potentiometer, connecting the remaining stages to the negative side. In this way only the first tube operates at reduced amplification, while the remaining radio amplifiers work at full efficiency. The idea just described is shown in Figure 6.

For reasons that are quite evident, it

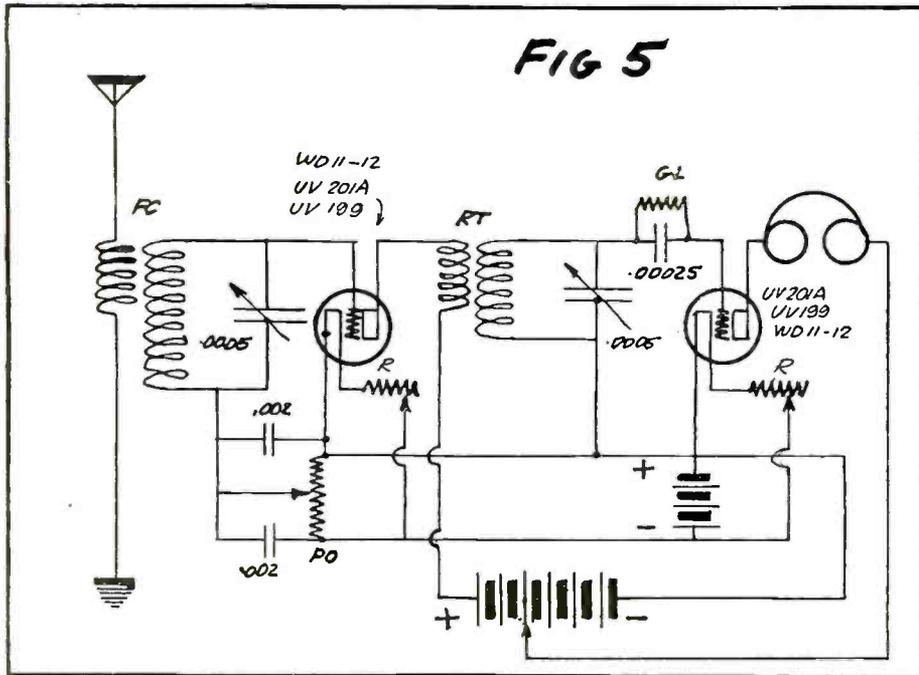

is not advisable to use more than normal voltages on the plates of tubes when they are used as radio frequency amplifiers. If more than 60 volts are used, it is advisable to use a grid biasing battery in order to offset an excessive drain on the plate battery. Usually it is only possible to make use of the grid biasing scheme when some other means of suppressing oscillations than a potentiometer is used. In other words, only such circuits as the Neutrodyne, Rice circuit and Superdyne or Teledyne is this grid bias idea practical.

The normal voltage for the standard tubes on the market as radio frequency amplifiers is 45, and it should be remembered that the little gain in amplification obtained when a higher plate voltage is applied does not compensate insofar as the drain on the B battery is concerned.

Other Radio Frequency Connections

Individual peculiarities of circuits and characteristics of the tubes themselves are often evident in radio frequency circuits, but this matter lies entirely within the scope of experimentation. If it is found that the circuit refuses to give the results expected, the proper recourse is as before mentioned—experiment. Peculiarities of this nature are really so different in nature that it is quite impossible to classify them under any definite head.

We have still another use for the potentiometer in the circuit, in this case controlling the plate return of the detector tube. It is especially advisable with gas content tubes to use a potentiometer with its outer or resistance segment terminals connected to the positive and negative filament battery, and the movable center arm connected to the negative B battery.

This arrangement of the potentiometer affords a very delicate control of the plate battery current, and inasmuch as gas content tubes such as the UV200 are very critical with respect to plate current, it becomes a matter of much importance.

The A. C. and UV, as well as the WD tubes, are not critical to either filament or plate current, and therefore do not require the potentiometer in this capacity.

The Technical Office of RADIO AGE is frequently asked to settle disputes as to whether the filament rheostats should be placed in the negative or positive leads of the circuit. In some cases, as in the UV200 detector tube, the position of the rheostat is not important, but it does make a difference in other cases. Specifically, this is the audio frequency amplifier, and for the sake of uniformity and consistency in wiring, it is always advisable to connect the rheostat in the negative filament lead.

Incidentally, many of our readers request that we designate for them the


polarity of the tube socket connections with respect to the posts marked F and F. Often they ask us if the tubes have polarity action within the filament of the tube, because the sockets are marked F positive and F negative. The entire mystery is explained by saying that the filament connections are marked negative or positive for convenience in wiring, and it does not make any difference with regard to tube performance whether either end of the filament is made positive or negative.

It is often desirable where space is valuable to use as few controls as possible, and the filament circuits, especially in the amplifier components, offer a chance to save panel space. Two or three amplifier tubes can be controlled effectively with one rheostat, and if desired both radio frequency and audio frequency amplifiers can be manually operated by the same resistance. The diagram shown in Figure 7 shows how additional tube may be added. It should be remembered, however, that as you add tubes, the resistance of the rheostat decreases.

Audio Frequency Amplifiers

The connections for audio frequency amplifiers of the cascade type are as old as the hills, and nearly every radio man can draw them from memory. However, many of them vary in design with respect as to how all connections are made, so for those who have any doubt as to the connections, I am showing in Figure 8 a diagram of a standard amplifier which can be added to any receiver without much trouble. It is considered good practice to omit the jack from the first stage, but if it is desired, follow out the dotted lines and the circuit will function just as well.

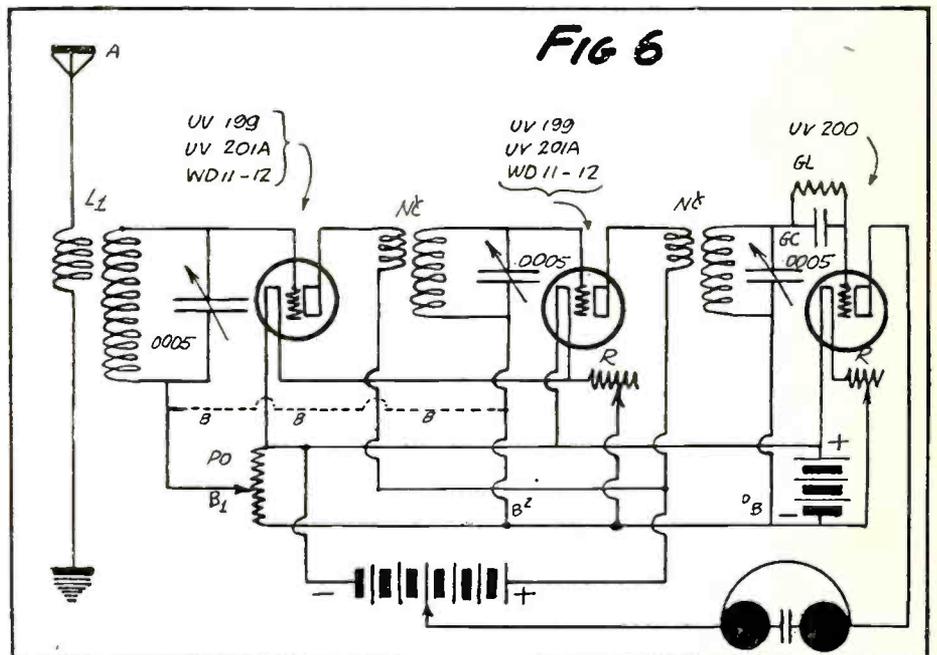That leaves us with only one more
(Continued on page 51)



It is often necessary to connect the grid return of the second stage of RF to the potentiometer arm as shown, but should be avoided if possible. With a straight negative bias on the grid of the second RF tube, the circuit gives the greatest amplification.

DX With a Single-Dial

GO-GETTER

By PAUL THORNE

IN THE overwhelming excitement over supers and super-supers, and the ever-increasing members of the Dyne family, we seem of late to have largely overlooked several very important factors in radio development. What of the beginners—thousands of whom appear every day—or the old hands who have tired of many knobs and dials, and now want something that they can just turn on and listen? What of the modest experimenter who likes to tinker, but stands aghast at the multiplicity of controls and the network of wiring that makes even an old timer scratch his head? And what of that growing army of ladies who want to listen in on radio programs, yet are frightened away by “all those things you have to turn?”

These folks may all look far these days without finding any of the comparatively simple but effective hookups that used to appear regularly. Of course, the newcomers can go back and dig up some of the old stuff, but they feel that radio is advancing, and they are expecting something new. And even the old so-called simple hookups had their numerous taps and dials, so the ladies at least would be no better off.

While the engineers and experts are discussing their dynes and supers, here's something for the folks I've mentioned.

Are Supers Superior?

WHEN one compares the DX records sent to the various radio publications, the doubt often arises as to whether the newer super-circuits are really so superior to the simple circuits as we are sometimes led to believe. Looking over the records sent in by the proud and boastful owners of intricate sets, I find that I have had practically all of the stations listed on one or two tubes, using the hookup presented here.

For simplicity combined with effectiveness, this one-control hookup is hard to beat. It is very compact (note that, you portable set builders); it eliminates taps, operating on a minimum of fixed coupled inductance;

uses spider web coils, and has only one tuning control—the variable plate condenser. Regeneration is controlled by the rheostat, but as the tube shows little inclination to “spill,” it is seldom necessary to touch the rheostat again after the first station has been brought in with satisfactory volume and clearness.

It enables the beginner to experience the thrill of building his own set, and obtain really wonderful results right from the start, something which the average beginner often finds hard to accomplish. It offers the old hand who has tired of many controls an opportunity to get similar results with less effort. It is a set that the ladies will appreciate, for while the man of the house is away, they can easily tune in. To operate, they merely turn on the tube, and then turn the condenser dial to the station wanted, or if they don't know where to find the station, they simply turn the dial and some station will quickly come in. There is only ONE record to make when logging stations, and as they always come in at exactly the same point, it is easy to pick them up again if the station is on the air and weather conditions are right.


The set is easy and simple to build, and quite inexpensive. The circuit diagram gives all the necessary information except the preparing of the coils. This part is explained in detail further on.

Occasionally, coils wound on a tube, with a tapped primary, have been used. What I have accomplished is the eliminating of dead end losses, and useless work in building and tuning, by doing away with taps. At the same time I have made the circuit more selective. I have also greatly improved the volume and clearness by changing the rheostat to the negative side of the filament, and the addition of the ground connection from A—, and the lead containing a fixed condenser around the batteries. The increase in volume is considerable, especially on DX reception. The clarity of the reproduction is not excelled by any circuit, and is favorably commented upon by almost everyone who hears my sets.

The size of the cabinet and panel is left to the builder's individual requirements. He may want to start with a one-tube set, and add amplification in a separate unit later, or he may wish to combine one or two steps of audio amplification in the set at once. While the diagram shows only the detector circuit, audio amplification can easily be added in the usual way. And in connection with this matter of size, let me say here that by using a compact plate condenser, and a UV199 tube, the set can be built into surprisingly small space, making a very efficient and convenient portable set.

An effective arrangement of parts is to place the antenna and ground binding posts in the upper left-hand corner of panel (looking at the front), and the phone and battery binding posts up and down the right-hand side.

The plate condenser is put on the left, and the rheostat on the right, with the inductance coils behind the condenser and the tube back of the rheostat. If a variable grid leak is used it can be placed in the center of the panel. If a fixed leak is preferred, two megohms will be about right. I prefer the pencil type grid leak, as one can obtain very fine adjustment with it, which is highly important for good DX work.

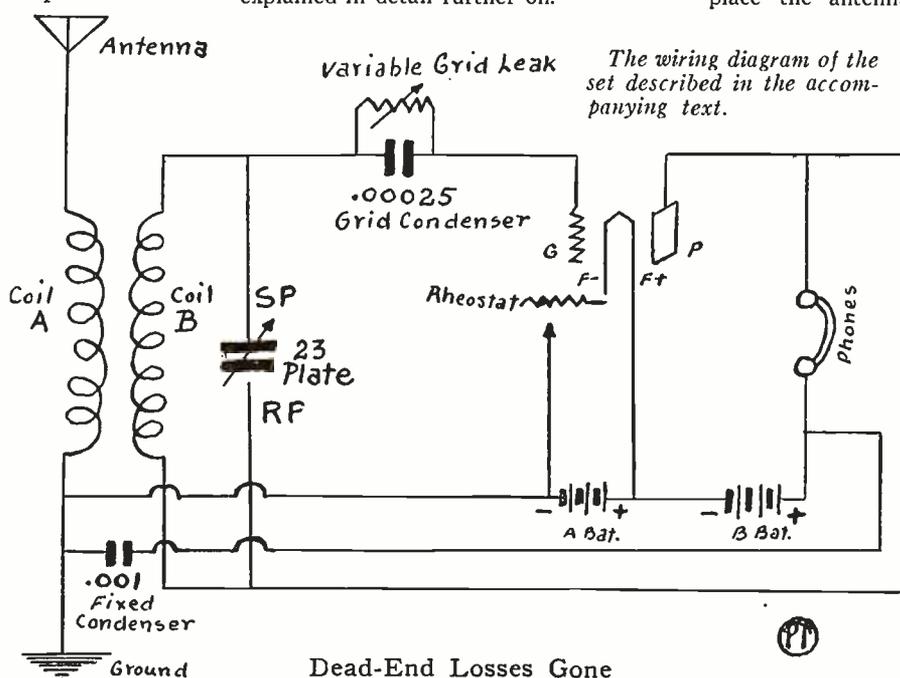

Dead-End Losses Gone

AS USUALLY hooked up, however, a variocoupler is employed for induct-

In winding the secondary (B) coil, the
(Continued on page 53)

Reminiscences of an Old OPERATOR

Part One:

"My Amateur Days"

¶ A Vivid Retrospection of the Days
When a Radio "Bug" Who
Claimed to Extract Mes-
sages From the Ether
Was Declared
Mentally
Unsound.

Thru some misunderstanding the youngster let go at the critical moment; the mast fell toward the white-faced and helpless group of would-be engineers, and shot through a skylight into a barber shop below.

Illustration by
GEO. B. DENNIS

By
ARTHUR LYNCH

MY EARLIEST remembrance of wireless dates back to the latter part of 1906, or the early part of 1907, I am not quite sure which. The excitement started with my discovery in a current boys' magazine of a diagram for "a wireless receiving set which any boy can make," over which fortunate experimenters had heard stations "five miles distant." The diagram of this wondrous creation as it appears on a tattered piece of school drawing paper is now among my prized possessions in case some intrepid experimenter might desire to try it out alongside his super-heterodyne.

The slogan "make it out of the junk you have" would hardly apply to a masterpiece of this magnitude, as few if any would find their shop stocked with the necessary apparatus. The list of materials was impressive, containing such highly scientific items as "200 feet of annunciator wire, one 75-ohm bi-polar tele-


THIS article is the first of an interesting series by a veteran commercial operator, who describes the facts and thrills of his rise from an awe-inspired experimenter, back in 1907, to a full-fledged radio expert. Don't fail to miss a single installment, you amateurs!

phone receiver," and again "one carbon rod from a common dry battery."

Among the concluding items stands out in my memory a shining item—"one brass head upholsterer's tack with head between $3/16$ " and $1/4$ " in diameter." How I did sweat over that item! With foot rule in hand I visited some fifteen upholstery shops in my own and neighboring cities in search for this elusive item. Upholsterers' tacks by the bucketful, yea, by the wagon load, were to be found in profusion, but not one could I locate that fell exactly within the limits specified by my guiding genius.

Early in my search I found little interest in my micrometer standards as to tack head sizes, the dealers visited feeling that I should somehow squeeze in a tack $9/32$ " or worry along with one about $5/32$ ". With scorn I rejected their counsel! What could a mere upholsterer understand of the niceties of science!

That was the trouble with the non-scientific gentry of those days. They looked askance at we youngsters' experiments in the mystic sport—wireless. They thought we were tinkering with instruments of the devil—to put it mildly. They offered us absolutely no co-operation at all, which made our efforts all the more difficult. But it was such dogged determination that finally overcame early obstacles and made radio what it is today. And now those same skeptics are our staunchest admirers and the first to say: "I told you so! I knew he'd make good!" But let us proceed.

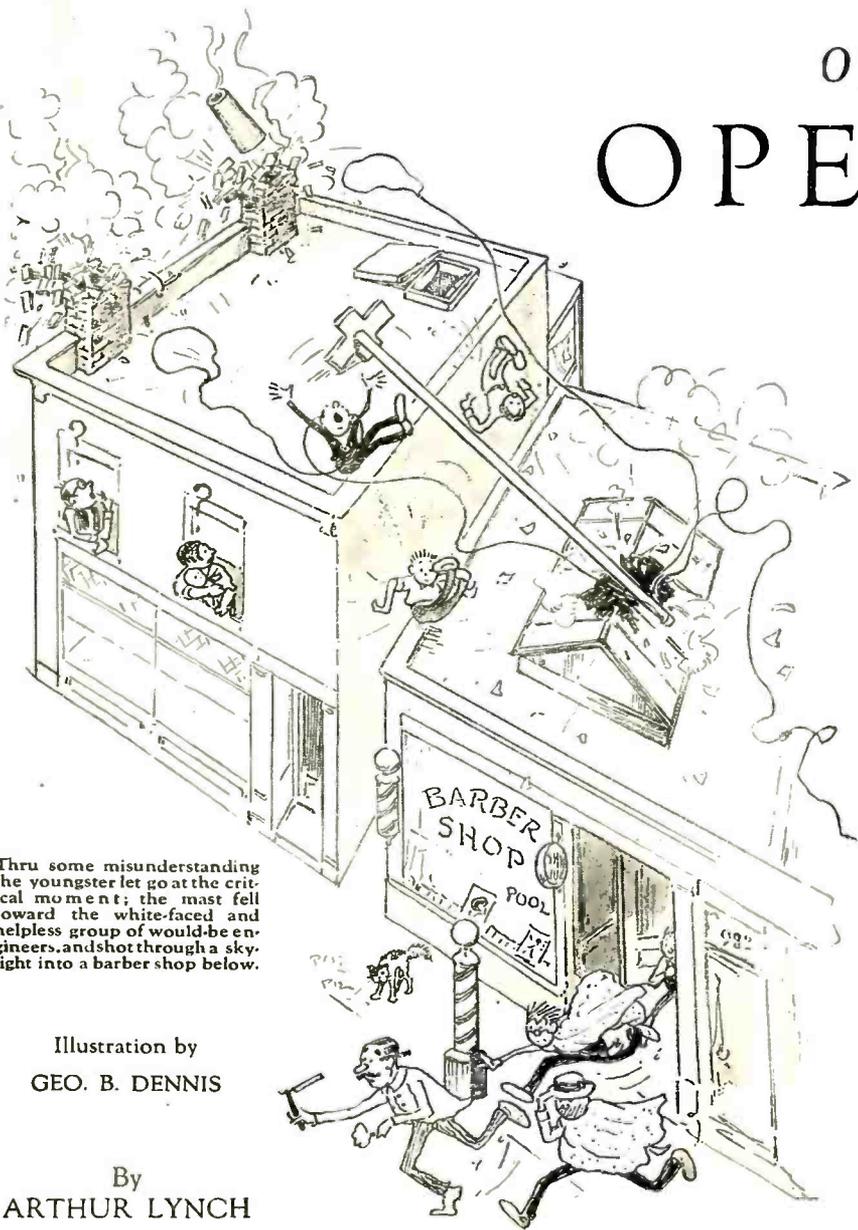

While searching for new stores to enter I concluded to take the next shopkeeper into my confidence, but after three trials I concluded that this would not do at all. In no case did I get beyond a third explanation of my purpose in procuring an upholsterer's tack with head between $\frac{3}{16}$ " and $\frac{1}{4}$ ". The first fellow was merely dumfounded. "Wireless telegraph!" he kept exclaiming. He HAD heard that it was possible to telegraph and talk with wires, but a wireless telegraph was absolutely beyond him.

All "Unbelievers"

HE HAD to call Lena, his wife, who came with two babies in arms and several afoot to hear me tell it all over again, which story was no sooner complete than friend Otto, from the bakery, happened in with his Meerschaum for a chat with his good friends. A third telling was finished amid an accompaniment of wondering exclamations from all but Otto. This sturdy German struck a jarring note in the symphony by expressing entire disbelief in the whole project.

In the argument which followed the object of my quest was entirely forgotten and I finally extricated myself, followed by thunderous advice against my foolhardiness from the now thoroughly aroused Otto.

My next conferee quickly became bored at my insistence upon such close dimensions and returned to his bench with the darkness dense and unpunctured by my careful explanations of the wonders of the new science.

The third auditor listened to my opening text, but as I began on the sermon itself he laid his tools down, came closer and started to scowl ominously. Then he interrupted and roughly informed me that I was crazy. Telegraph without wires! Any time a freckled, lanky, short-panted kid armed with a smudged foot ruler laid off in eighths tried to tell him he was going to hear some messages coming through the air without any wires—well, he was too dash-blamed, gad-swoked wise for that. I was some young Edison, I was, etc.

In despair I returned to my room and viewed the lavish outlay spread before me. Everything was there, right down to the "two blocks of soft wood $1\frac{1}{4}$ " x 3 " x 1 " thick" which were supposed to support the tuning coil on the base " 3 " x $3\frac{1}{2}$ " long by 1 " thick," all shaved down to the hair—but no upholsterer's tack with head between $\frac{3}{16}$ " and $\frac{1}{4}$ ". I almost gave up making the set because to my mind it never could work with an upholsterer's tack over $\frac{3}{4}$ "; and at night I had dreams of Hertzian waves, little purple glowing rings something under $\frac{1}{4}$ " in diameter, dying by the millions, hanging in festoons on my wires with their leader stuck fast on the brass head tack some thirty-second of an inch too large.


Finally, with much care I filed down the circumference of a large tack to just a trifle under one and three-quarters of the eighth-inch spaces on my foot rule, and after polishing off the rough file marks, tried to convince myself that it would work.

With the set assembled, the first of

many vigils at the one phone of the outfit began under awesome circumstances. My skeptical upholsterer friends had somewhat cooled my own ardor, and with my confidence further shaken by dissenting voices among my friends, I became chary of confiding my plans to anyone. Only my mother knew what I was doing and on the night of the first trans-continental tests she was in collusion with me falsely to announce that I had gone out for the evening.

In the darkness of my room I lay in hiding until quiet reigned in the household and mother's whisper at the door assured me that all was well. With curtains drawn and light turned low I made a final inspection of my connections from lead-in to gaspipe and found everything as per drawing.

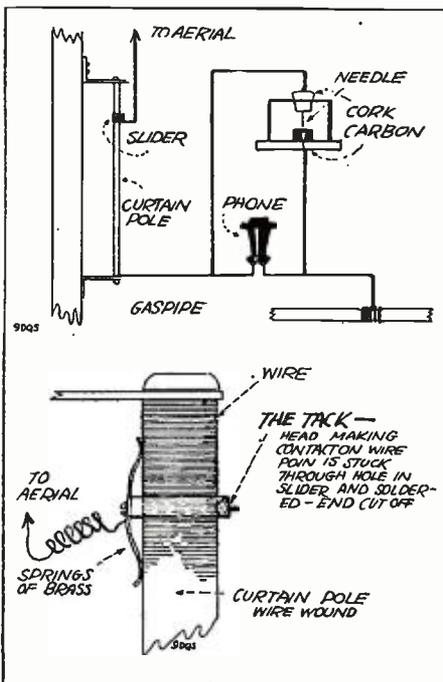THEN with a firm gulp swallowing my heart for the fifth time, I grasped the



This is the kind of "long distance Carbon receiver" that was in vogue back in the infant days of radio.

receiver and—witness the birth of the loud speaker idea—placed it within a close foot of my ear! Of course it was foolish of me to expect to hear the distant (four miles) station without radio frequency amplification, but remember that I was brand new at the game.

Suffice to say that I heard nothing from that receiver, even with it only an inch from my ear. Gaining courage I pressed it lightly to my ear, then, not suffering any ruptured eardrum, I squeezed it tightly, but no amount of grinding of receiver into ear produced anything but a dead silence. Right ear or left ear made no difference; light pressure or heavy pressure of needle on carbon block; brass curtain ring at top, center or bottom of tuning coil. all was silent as the grave.

Wrathfully I eyed the offending upholsterer's tack which, you recall, I had doctored into a semblance of proper

dimensions. There, undoubtedly, was the trouble. However, I decided I would look over my aerial and outside connections on the morrow.

My aerial consisted of a brass rod stuck about four feet above the third story roof. Quite an antenna, at that, when a fellow can get Cuba on a loop—and six or eight tubes. Passing up the good or bad qualities, for I knew naught of either then, my daylight inspection showed everything shipshape, so I decided to give the outfit another tryout that night. Possibly, I thought, there were no messages being sent the night before.

But there was nothing doing that night or for several succeeding nights. Then as I was pondering one day I was chilled by a horrible thought. Possibly our only local station, "CG," Collingswood, N. J., was farther away than the four miles I had always believed lay between our house in Camden, N. J., and the suburb. The article regarding the set only claimed five miles for it, you will recall. Maybe the station was five and a quarter miles!

At first opportunity nothing would do but for me to pedal on my bike to Collingswood, watching the odometer tick off the tenths. 4.3 it registered from my house to Collingswood by road. In an air line it was no doubt much closer.

Now, absolutely stuck, I started doggedly listening, listening. In the morning before breakfast, at noon as soon as I was home from school, night after night, and still not a sound until—

One noon, as usual rushing up to my room, I was arrested at the doorway by a prodigious clicking coming from the general direction of my set. With heart standing still I breathlessly approached and soon traced the wild racket to the seventy-five ohm phone lying on the table. No need to put the receiver to ear—the clicking was of goodly bulk and strong and could be heard perfectly well with the phone where it was.

His Dreams Blasted

ON THE point of tearing madly through the house shouting the tidings to all, I paused. Somehow it struck me that something was irregular about all this. Picking up the receiver and placing it near my ear I immediately noted that the loud clickety-clicks emanating therefrom had little in them of a far off nature. They sounded more like good, healthy battery juice being fed directly into the coils of that phone. We had often used this very hook-up as a variation of our key and sounder circuits.

Hastily I examined my wiring. Sure enough, there were signs aplenty of dirty work at the cross roads. Hooked to my aerial and ground was an extra pair of wires leading over the window sill and down the outside of the house. Tiptoeing softly downstairs and down cellar, I came upon my Uncle Joe, a dabbler in electricity but a skeptic as to wireless, with a key, two dry cells and the other ends of two wires which I could gamble were furnishing sigs to my third floor "wireless" set.

Now that I am more or less grown up

What the Broadcasters are Doing

Radio Station WIP Broadcasts From Bottom of Atlantic

Since radio broadcasting took this country by storm, many strange things and many strange sounds have been broadcast. The roar of the mighty Atlantic's waves, the rattle of a rattlesnake, the voice of an aviator high in the heavens.

And now, the marvels of the deep sea have been broadcast to the entire world. On Thursday, July 31, at 3 p. m. and 8 p. m. the Atlantic City Control Station of Radio Broadcasting Station WIP, of Gimbel Brothers, Philadelphia, broadcast from the bottom of the Atlantic Ocean.

Not satisfied with the new and novel idea of broadcasting the surf noises of the mighty Atlantic, Station WIP's engineers looked for a stunt that would be even more thrilling.

So a deep sea diver dropped over the side of a boat, to the floor of the Atlantic Ocean, fifty feet or so below. In his diving helmet, he had a special radio microphone, connected by lead cable to the boat and from there to the Remote Control Station of Station WIP, on the Steel Pier, Atlantic City, N. J.

C. O. Jackson, expert diver of the Philadelphia Derrick and Salvage Corporation, was the first man to talk over radio from the bottom of the sea.

Through the heavy glass windows of his diving suit, Mr. Johnson has seen many strange and wonderful sights of under-sea life. The special microphone, which was attached inside his helmet, enabled him to describe to the radio public, exactly what was going on at the bottom of the mighty Atlantic.

The strange fish, and other sea creatures living at the bottom of the sea were described. The appearance of the sub-sea foliage and mineral formations were broadcast in full detail.

This was the first time that any broadcasting station has sent a microphone to the bottom of the sea. Special cable, waterproof and flexible, is necessary to connect the diver to the boat. The voice originates from the helmet of the diver, thence to the boat floating on the surface of the water above. The boat, in turn, is connected by wire to the Remote Control Station on the Steel Pier. Here the voice from under the ocean is amplified many thousands of times, then transmitted over special telephone lines to the main station, located on the Gimbel Brothers store in Philadelphia, more than thirty miles away.

Movie Talks On WGY

WGY, the Schenectady broadcasting station, introduced a new weekly feature last month which is sure to be of interest to a great majority of the station's listeners. Quinn Martin of the New York World delivered the first of a series of "Movie Notions." Mr. Martin, who has made a study of the movie industry for years and has visited most of the large studios, told about the best pictures produced and took his listeners back of the silver sheet into the producing studios and explained how some of the stunts are done. He gives intimate pictures of some of the leading figures in the motion picture industry. In his first talk he discussed the slow but sure tendency of the producer to artistic production.



BURTON THATCHER

has gained considerable fame and following for his method of teaching vocal lessons over station WLS of Chicago. His listening clientele consists of hundreds of men, women and children who have profited by his instructions broadcast over the air in the past few months.

Musical Rehearsal Held by Telephone

One of the most unique musical performances in this age of startling achievements was accomplished when a musical rehearsal was successfully completed by means of long distance telephone.

Miss Wellman, who is one of the youngest vocal artists engaged in concert work, was invited by Victor Saudek, director of the KDKA Little Symphony Orchestra, to appear on the broadcasting program of station KDKA and render a few musical numbers. Miss Wellman gladly accepted the invitation and arranged to come to Pittsburgh before the date scheduled for her appearance for the purpose of rehearsing her numbers with the KDKA Little Symphony Orchestra.

A few days later Mr. Saudek received a telephone call at the East Pittsburgh broadcasting studio from Miss Wellman in New York stating she would be unable to leave New York in time for her rehearsal, and so she decided that it would be better to cancel her engagement. Mr. Saudek, however, suggested that she conduct the rehearsal by means of the long distance telephone over which they were conversing. She agreed.

The orchestra was soon in readiness, and with the telephone receiver to his ear listening to Miss Wellman singing, Victor Saudek was able to direct the Little Symphony Orchestra at the East Pittsburgh studio and thus conduct the rehearsal. "The Spring Song" from the opera "Samson and Delilah" by Saint Saens, and "Oh Rest in the Lord" from the oratorio "Elijah" by Mendelssohn, the two numbers which Miss Wellman sang at the concert, were played until the orchestration was satisfactory.

Radio Brings Help for Tornado- Stricken

At the time of the appalling Lorain tornado disaster some weeks ago, various Chicago stations co-operated in many ways toward bringing relief to the stricken areas.


Every one of the local broadcasting stations of the city read off regular announcements from the Chicago Herald-Examiner, soliciting the aid of doctors and nurses to aid and give medical attention to the sufferers of the terrible storm which struck the Ohio towns.

The value of this service can never be computed, but it is a convincing argument in favor of the use of radio broadcasting in times of disaster and danger.


"OUT WHERE THE TALL CORN GROWS".



FRANK W. ELLIOTT
"FWE"

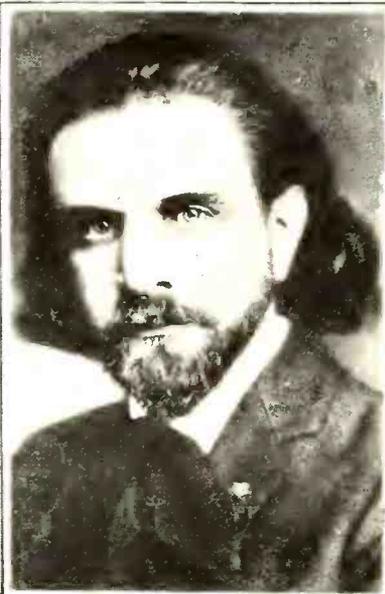

B. J. PALMER, D.C., Ph. C.
"BJP"

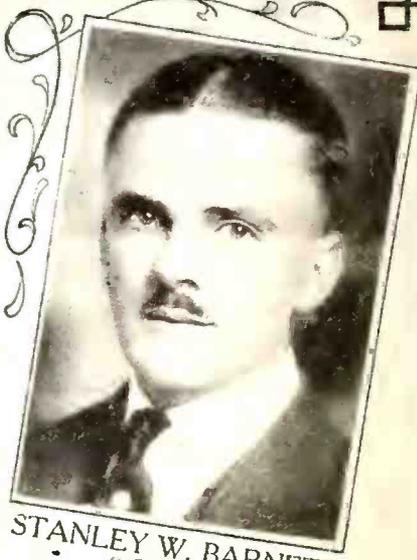

STANLEY W. BARNETT
"BWS"



FRANKLIN W. PIERCE
"ANR"

PERSONNEL
of
RADIOPHONE
WOC

DAVENPORT
IOWA




GILSON V. WILLETS
"GWW"



ERWIN SWINDELL
Musical Director

"Where the West Begins"

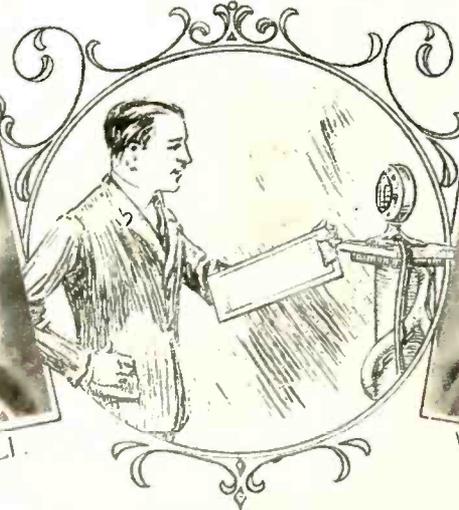

VAL McLAUGHLIN
"The Sandman"

Here are some of the folks you are sure to hear when you tune in on the Palmer School of Chiropractic station, WOC, at Davenport, Ia., "out where the tall corn grows." WOC recently celebrated its second birthday and for a "two-year-old" it is quite a husky youngster, as radio stations are rated.

THE radio broadcasting apparatus installed at WOC, the station of the Palmer School of Chiropractic at Davenport, Ia., puts its facilities for broadcasting on a favorable footing with those of the most powerful stations anywhere in the country.

Housed in specially fitted rooms on Up-E-Nuf, the roof auditorium of the school, are the broadcasting apparatus and the studio equipment, each the last word in modernity.

The studio is one of the most efficient in the Middle West. In the first place, the altitude is sufficient to eliminate street noises which might interfere with perfect broadcasting, and secondly, there is genuine beauty of surroundings as well as picturesqueness of furnishings.

Solidly constructed is the room in which the actual broadcasting is done, and the studio and reception room afford ample accommodations for any number of artists that could possibly be used on a single program.

Pipe Organ Programs

THE installation in the B. J. Palmer residence of the pipe organ gives another unique and unusual form of radio-phone music. The organ is one of the finest in the country. The console is located at the east end of the music room and the main organ is located in a chamber especially built for it directly overhead.

The Echo organ is placed in a similar chamber at the extreme west end of the porch, and on account of its relative location to that of the main organ, the most charming and enchanting effects are possible.

The outlay of money entailed by WOC's broadcasting service approximates \$60,000 annually, indicating the faith the owners of the station have in the permanency of radio as a public necessity. Other organizations in the country are convinced of the place of radio in the American scheme of things, and likewise have invested materially, although few have striven for the complete-

A Radio Station That Receives 12,000 APPLAUSE CARDS WEEKLY!

THE "INSIDE STORY" OF WOC

ness of facilities which now characterizes WOC. The most vacillating of doubting Thomases must concede that the step taken by WOC has reacted to the satisfaction and entertainment of the school's friends and has brought the name of Davenport before the country as it could be brought in no other way.

That it has proven a boon to the thousands of receiving stations in Iowa and surrounding states is certain. WOC was planned by and manufactured under the supervision of the same engineers who startled the world in 1915 by establishing vocal contact between Arlington, Va., and Paris, Colon, Honolulu and San Diego, and who during the war contributed materially to radio telephonic developments undertaken by the Army and Navy.

Distance Tests Held

THE Palmer School of Chiropractic broadcasting station is unique in many respects. Designed to cover a region of from 100 to 150 miles from Davenport, and to deliver 500 watts of radio frequency power to the antenna system under all conditions, under favorable conditions it can be heard at very

entire United States had been reached, with the exception of the New England states and the country west of the Rockies.


At the end of the first month's test broadcasting, in spite of severe summer weather, the remaining states had dwindled to three in number, with the record air line distance at 1,765 miles.

Shortly afterward was established the enviable record of being heard in every civilized state and province in the North American Continent on one single program.

To obtain ideal operating conditions for WOC, a special suite of rooms has been prepared, every means having been taken to insure suitable acoustic properties. The chamber that houses the microphone and forms the headquarters for the speakers, vocalists and musicians secured to conduct the broadcast programs is a mysterious compartment with walls shrouded beneath layers of draperies and a floor buried beneath the heaviest of carpets. Constant study has proved that to prevent the reflection of sound and to prevent the impairment of the quality of vocal and instrumental music such precautions are necessary.

WOC has received in one week as many as 12,000 applause cards from "listeners-in" within a radius of 4,000 miles. Acknowledgment cards, form letters, and circular letters are made to cover as much of this work as possible, but there are in addition an endless amount of requests for individual numbers, repeat numbers, replies to police reports, requests by speakers, requests for acknowledgment, etc., which require individual attention.

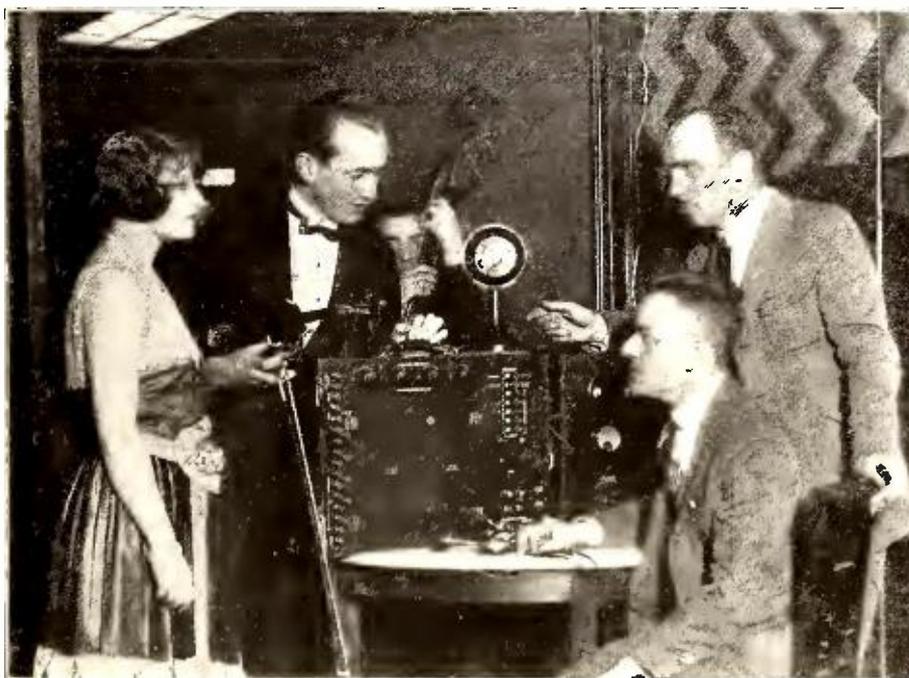WOC operates on a 484 meter wave length. Tune in tonight and get acquainted with its peppy staff.



LITTLE LESSONS IN BROADCASTING

George Frenger, better known to WJZ-WGY listeners as "A. F. N.," is giving a few hints on broadcasting to Paul Specht, while the latter is waiting for his orchestra to "take the air" at the Alamac, N. Y. At the left Mlle. Sascha Beumont, dancer, is listening to George's warnings on how to speak to a microphone.



Usually it's hard to smile in the presence of an unresponsive microphone. But Howard I. Milholland, announcer of the Pacific Coast Station KGO, likes to announce. He is shown above at his favorite indoor sport.

How Would You Say 'Good Night'?

WHAT 'GOOD NIGHT' MEANS AT KGO

AS HE left the home of the Rev. Milholland in Roodhouse, Illinois, 39 years ago, how was the good old country doctor to know that his cheery "good night" would be echoed years later so significantly by the new voice he had just ushered into the world?

If KGO, the General Electric Pacific Coast Station, had then been in existence, "Daddy" Milholland surely would have preceded his son as announcer and broadcast the glad news to the world. Being of a humorous turn of mind, he perhaps imagined himself, megaphone in

hand, on a steep, snowy roof, announcing to the sleeping world, "It's a boy!"

The following Sunday the Rev. Milholland blushed a little (he was only 22 at the time) announcing to his congregation, "God has been good to me and has given me a son; we shall christen him 'Howard'."

Howard weighed 10 pounds when he was born, and in less than three years he was big enough to say "good night" plainly. When he was 21, he graduated from the Eastern Illinois State Normal School. He then began writing his name

"Howard I. Milholland," and decided to go West. After sizing up the Rocky Mountains in the distance, he settled in Denver, engaging in the photographic supply business.

BEING married now, and with a growing sense of his responsibilities, Howard I. Milholland is next found growing a mustache. "Straightaway," said "HM," when telling the story of his life recently, "I got the idea of being an impersonator."

A minister's son does not always stay out of church activities even when he fails to follow his father into the pulpit. So for the next few years it's natural that we should learn of "HM" singing in various churches and directing choirs. Meanwhile he also traveled considerably as a reader and impersonator.

"When I first stepped before a microphone on the evening of January 8, this year, at the opening of KGO," said "HM," "I naturally felt a little nervous, but my platform experience helped a lot. With the coaching given me by Mr. Hager of WGY, I saw that announcing required a technique, based upon the ability to enunciate clearly. I also found the routine of announcing very much different than the routine of platform work."

"HM's" ambition is to learn how to say "good night." He believes that much of an announcer's work is so cut and dried that he should give a lot of thought to the way he says "good night." With "HM" the phrase "good night" can mean many things. If your day has been a hard one, "HM" simply wishes you a "good night" or a "better night." Should you have taken a little step aside during the day, "good night" for you means—do a little better tonight. If you are grouchy or unsociable, "good night" is simply a friendly suggestion which might help you. If you have the spirit of malice in your heart, "HM's" "good night" may tell you that by kindness and love we fulfill our mission here.

Or you might just happen to be listening in on KGO for the first time. "Good night" then is meant to convey to you the hope that you have enjoyed the program and will listen again.

"Perhaps I take my job too seriously," said Howard I. Milholland. "I think I must have inherited a desire to preach from my father. And the best sermon I can think of is simply 'good night'."

N. Y. Philharmonic Orchestra on WGY

During the months of July and August, WGY gave a special musical treat for its audiences. A series of eleven concerts by the New York Philharmonic Orchestra and a series of eight concerts by Goldman's Band were broadcast.

Programs of both organizations, the New York Philharmonic Orchestra and Goldman's Band, were presented in New York, the former at Lewisohn Stadium, College of the City of New York, and the latter at The Mall, Central Park. WGY was connected to New York by wire and presented the concerts in co-operation with WJZ.

Broadcasting From Portable Station to Be Tested to Find WJAZ Location

Many Illinois Cities to Compete to Win Zenith Station

AN unusual occurrence took place when a metropolitan broadcasting station was recently disposed of by one of the pioneer radio corporations in broadcasting, because the station dominated the air to such an extent as to prevent radio listeners within its immediate scope from hearing any other stations. It probably began the movement of broadcasting stations having their ultimate location away from the thickly populated areas of the country.

This unexpected stroke of policy was announced by the Zenith Radio Corporation when it sold Station WJAZ, then located on the Edgewater Beach Hotel. Because of the uncontrollable interference caused by this station throughout the entire north shore of Chicago, the company decided to erect a new station far enough away from the city so as to be no longer an interference to the three million of people who live in the city.

A "Portable Test"

On the heels of this announcement, the Zenith Radio Corporation was deluged with letters from the Chambers of Commerce of many of the small communities in the outlying districts of Chicago. Some letters came from places two hundred miles away.

So urgent were many of the invitations from these smaller towns that it was decided to conduct a series of tests to ascertain the best locality for broadcasting and to determine at the same time the place offering the least opportunity for interference. The best working plan which suggested itself was to erect temporary broadcasting stations in all the towns selected for test. For a time it looked as though the plan of making tests would have to be abandoned because the attendant obstacles seemed to be insurmountable. But after planning and experimenting in the company's laboratories a way out was discovered.

The company is now building a complete broadcasting unit mounted on a one-ton truck. There have been portable transmitting stations for code work, but from all available information, this is the first portable broadcasting station in history. It will be equipped with a 100-watt transmitter. It will have the unusual setting of a glass-enclosed truck, so that the public may witness the operation of



Kadel & Heibert.

EVEN THE INDIANS HAVE THE RADIO "BUG"

Radio is becoming the most popular entertainment of all among the Indians on the reservations in Wyoming, where thousands are encamped. The big chiefs and their families are showing a decided preference for radio in place of the traditional Indian tom-tom music. Here you see two Indian chiefs "listening in" on a set donated by a nearby Chamber of Commerce interested in Indian welfare.

the station wherever it is taken. It will be operated entirely from storage batteries. Part of the truck equipment will be a motor generator for recharging the batteries. The aerial will be supported above the truck by means of telescoping masts. Gold plated antenna wire will be used, as gold reduces surface resistance and greatly increases efficiency in an antenna of this size.

Arrangements are under way with towns favorably disposed to receive the new broadcasting station. Tests will be arranged in each case for a definite night and the officials of these municipalities will be invited to extend the greetings of their respective communities to the world by themselves speaking into the microphone of the portable broadcasting sta-

tion. Already programs with two towns provide for the local band taking part in the broadcasting.

To Award Prizes

In every town prizes will be awarded for the longest distance reception. The data gathered through these tests will be especially valuable to radio technicians and engineers. For, as is generally known, it is impossible for radio experts, with all their theory and practice, to predetermine the broadcasting value of any given locality without actual tests.

For this series of experiments the call letters 9XN will be used. They will be remembered as the call letters that played so important a part in the radio communication with the MacMillan Arctic expedition.

Strictly Personal

Harry Aldyne Answers Some Pertinent Questions for Radio Fans

1. Dear Mr. Aldyne:

Is Jack Nelson of Station WGN married?

—L. R. T., Des Moines, Ia.

Yes, Lois, our good friend Jack is very happily married. More than that, his romance was one of the first to have its origin through a radio courtship. Jack is well satisfied that it pays to broadcast. Come again.

2. My Dear Mr. Aldyne:

Are the "Duncan Sisters" that I hear on Wednesday and Friday nights over KYW really sisters, or have they assumed that relationship merely

for publicity purposes?

—B. R. S., St. Louis, Mo.

You bet your sweet life they are sisters, and they have a brother and another married sister, too. We wish there were more of them. No trouble at all.

3. Dear Mr. Aldyne:

How is it the announcer of WLAG has such a high pitched voice?

—A. B. L., San Antonio, Tex.

We agree with you that the announcer of WLAG has a woman's voice. The announcer happens to be a woman. Don't shoot.

Popularity Contest Waxes Warm

Here Are the Ten Leading Candidates

By Harry Aldyne

They're off! The Radio Favorite Popularity Contest conducted by RADIO AGE has rapidly accelerated in momentum until definite indications of interest have come in from all four corners of the earth. Individuals make this contest a success, all with the one hope of making an impartial test of leadership in the great field of the radio industry.

It must be particularly noted that votes may be cast for any one connected with the radio industry; announcers, individual entertainers, orchestra, manufacturers, inventors, etc. One ballot counts only one vote.

To date the choices have been so widely scattered that it is hardly fair to say any group has a particular lead, and any one of five hundred or so stands a good chance

Name	Classification	Where Heard
Bill Hay	Announcer	KFKX—Hastings, Nehr.
Lamkin Kay	Announcer	WSB—Atlanta, Ga.
Duncan Sisters	Entertainers	KYW—Chicago
Husk O'Hare's Orchestra	Orchestra	WLS—Chicago
E. W. Tyson	Announcer	WWJ—Detroit
Jack Nelson	Announcer-Entertainer	WGN—Chicago
H. W. Arlin	Announcer	KDKA—E. Pittsburgh
Karl Bonawitz	Organist	WIP—Philadelphia
Fred Smith	Announcer	WLW—Cincinnati
Edward H. Smith	Director and Player	WGY—Schenectady

of heading the list when the first of a series of monthly semi-final contests is held.

However, that you may know which direction the wind is blowing, there are listed above the names of the first ten who have a slight advantage over the field.

Get in your votes, and if there are any suggestions or questions bearing on the contest, entertainers or broadcasting stations in general, send your letters for the attention of the Contest Editor.

The first contest closes on September 12, so that results may be announced in the October RADIO AGE. Get busy and send in the coupon on this page NOW!

POPULARITY CONTEST COUPON

Harry Aldyne,
Contest Editor,
RADIO AGE,
500 N. Dearborn St., Chicago.

I wish to cast my vote for:

Name of favorite

Classification

Station Date heard

Name [optional]


Address [optional]



RADIO INSTALLED IN SOCIETY SWIMMING POOL

P. and A. Photo

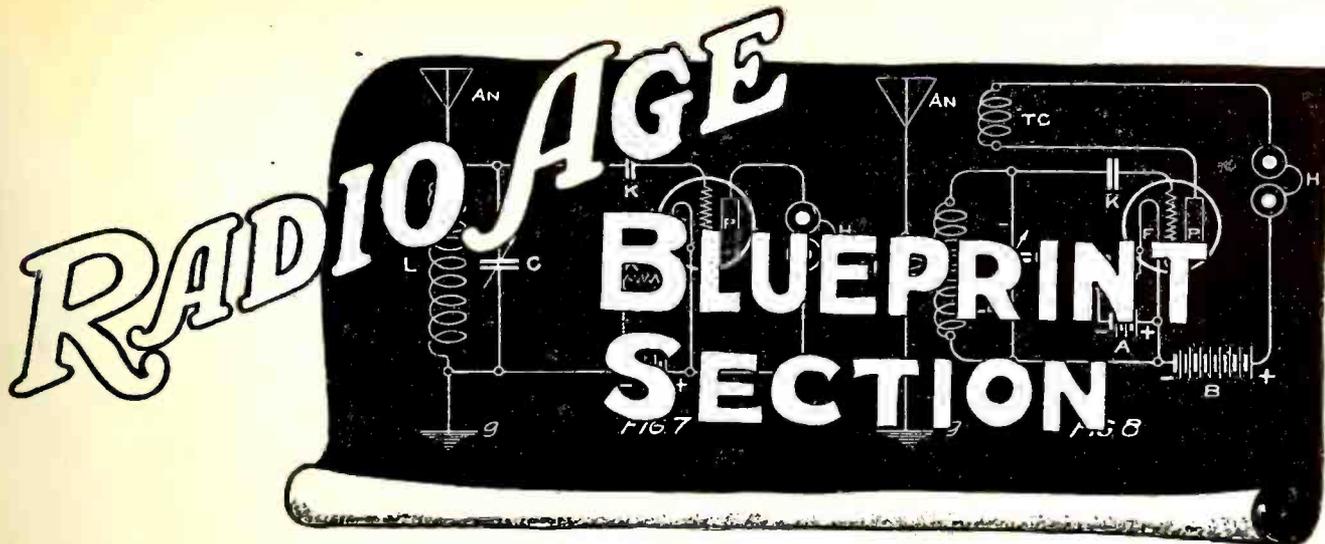Even swimmers like radio entertainment between dives and crawls. Here a group of swimmers, all members of Washington's "400," are paying rapt attention to a concert from New York. The set is installed in the Wardman Park Pool, one of the capital's most exclusive play spots.



For More Efficiency Try

An Aperiodic Variometer Set

By JOHN B. RATHBUN

Copyright: 1924

Applying a Variometer Idea to a Wizard Circuit

TUNING the grid circuit inductively by means of a variometer is nothing new in radio. In fact, this is practically as old as the use of the fixed inductance tuned by a condenser, but the idea has considerable merit owing to the fact that it is possible to establish higher potentials on the grid of the tube in this way. Thus, the incoming signal has more effect on the tube grid when capacity is lacking in this circuit than when a variable condenser is used for tuning the circuit to wave length. Better results are therefore obtained.

In the older circuits, the grid variometer was used as a tuning agent for single circuit sets or else it was used in connection with the standard type of tapped variocoupler where the additional losses introduced rather offset the inherent advantages of the variometer inductance. Used in a single circuit set, there was a loss of selectivity. Used with a standard variocoupler, the losses in the taps and tap switches often offset the increased efficiency of the variometer. In other words, the variometer was never used so that it was allowed to develop its full possibilities in the grid circuit.

Variometer "Switched"

After carefully going over this matter and experimenting with various combinations of variometers, it was finally decided to make the variometer an integral part of the primary and secondary tuning circuits so that the variometer formed the secondary winding of the coupler, while a few turns of wire at one end of the variometer acted as an "aperiodic" primary coil. No condenser was needed, and the full selectivity of the variocoupler was attained without losses in the tapped coils and rotor. The construction is simplicity itself and lives up to expectations in every way.

HAVING progressed this far, the next thing was to apply the idea to some specific circuit where its full possibilities could be developed without complicating the controls. Various circuits were investigated and finally it was decided that the Rathbun Wizard circuit offered an excellent opportunity for the application when the plate circuit was tuned by a second variometer. While the original Wizard circuit worked very well without the plate variometer and with direct inductive feed-back, yet the addition of the plate variometer made the set even more

selective than before and greatly increased the signal strength. Regeneration is more easily controlled without accurate filament current adjustment, and by the combined effects of the feed-back coil and the tuned plate circuit, a condition of resonance is more accurately approached in both circuits and the impedance of the circuit can be made more nearly the theoretical zero necessary for the establishment of maximum voltages.

In Fig. 1 on page 30 we show a picture circuit of the set called the "Aperiodic Variometer Set" with the two variometers used for the grid and the plate respectively. For maximum results and for loud speaker operation at fair distances, one stage of audio amplification has been added permanently which gives an excellent two-tube set with great volume and a very considerable range. Of course, the detector tube can be used alone or else another stage of audio amplification can be added, but for the best results for a given investment, I believe that the circuit is at its best the way that it is shown in the figures. It is certain that the addition of radio frequency steps only slightly increases its range and that the expense and trouble of adding the radio stages is not justified by the slight increase in performance.

Variometer as Secondary Coil

In Fig. 1, page 30, is the grid variometer marked (VI) which is used for tuning the set to wave length, this variometer acting as the secondary circuit coil of a two-circuit receiver. At the left is the aperiodic primary coil (L) consisting of about 25 turns of No. 26 D. S. C. wire wound on a four-inch diameter bakelite or cardboard tube. In addition to acting as the primary of the


(Continued on page 36)

HOW TO USE RADIO AGE BLUEPRINTS

The blueprints printed in this section are so arranged as to form a complete unit with the explanatory articles when desired by the reader. For example, the center sheet consisting of pages 31, 32, 33 and 34 contains two blueprints and two pages about the Baby Heterodyne. Just follow this four-page sheet at the center and you will have a complete section to follow when you make the Baby Het. Likewise the second center sheet, which also can be followed as one unit, is devoted to the aperiodic variometer set. The blueprints for this hookup are on pages 30 and 35, and the article on pages 29 and 36.

Blueprints appearing in future issues will be arranged in the same manner.

—The Editors.

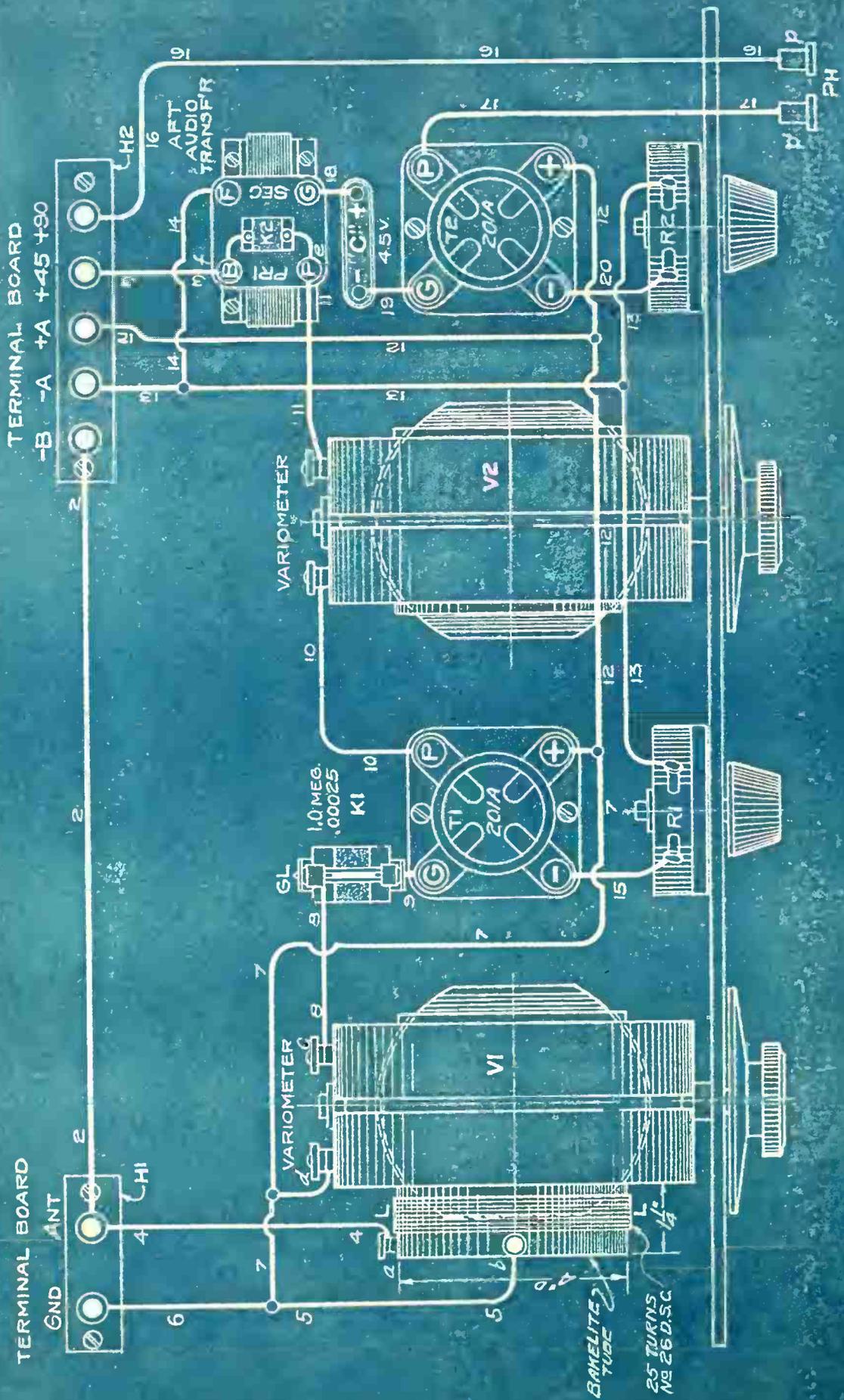

TERMINAL BOARD
-B -A +A +45 +90

TERMINAL BOARD
ANT
GND
HI

AN APERIODIC VARIOMETER SET

WITH TWO STAGES OF AUDIO AMPLIF.

FIG. 1

PAT. PENDING

COPYRIGHT 1924
RADIO AGE, INC.
CHICAGO ILL.

J.B.R.

Radio Age Offers An Improved Baby Heterodyne

By JOHN B. RATHBUN

Copyright: 1924

A New 'Baby Het' that Has Proved to Be One of Year's Most Stable and Sensitive Receivers

OWING to the enthusiastic reception which greeted the first single tube "Baby Heterodyne" published in the February issue of RADIO AGE, it was thought advisable to make further experiments with this circuit with a view to improving its stability and reducing its rather critical adjustment. The result of this investigation is the "Baby Heterodyne II," which is a marked advance over the older circuit in a number of respects.

There have been no radical changes in the principles, but small refinements made here and there which will make the set easier to handle and much more compact. Those of you who are familiar with the original circuit will quickly note the changes that have been made by consulting the schematic diagram in Fig. 3, and the wiring diagram layout of Fig. 1, shown in the actual RADIO AGE blueprints in this issue.

For the assistance of our readers who are not familiar with conventional circuit diagrams, we have shown the wiring diagram in picture form in Fig. 1, where all the apparatus is drawn out in detail. This is further assisted by the isometric view of Fig. 2, which shows the installation of the apparatus in its proper relative positions, together with such of the wiring that can be seen from the back of the panel. All of the parts in the three illustrations are given the same letters and figures so that the parts can easily be traced from one drawing to the others. The schematic drawing of Fig. 3 is for the use of the more advanced students who wish to see clearly the functioning of the circuit, and to whom a drawing of this sort means more than the isometric and picture diagrams. The isometric is useful for the layout of parts, but in making the actual wiring connections we advise the use of either Fig. 1 or Fig. 3.

As a further help, these diagrams are printed as real blueprints to aid the "fans" when actually working on the set.

As with the old circuit, we still use the aperiodic type of coupler (L1-L2) which has proved so selective and effective, but to conserve space and simplify connections, the oscillator coil (L3) has been wound directly on the same tube with the primary and secondary coils. In the old circuit the oscillator coil and feed-back were wound on a separate form which gave the beginners considerable trouble when it came to making the winding. On the present winding (L1) is the primary, (L2) is the secondary and (L3) is the combined oscillator pickup and feed-back coil. The secondary (L2) is tuned to wave length by the vernier variable condenser (C1) and is the only wave length aerial control used.

Windings Without Shellac

ALL COILS are wound in the same direction with No. 26 D.S.C. wire

the coils being separated by the distances shown in the coil detail of Fig. 1. The diameter of the tube is 3 inches and the length is about 5 inches, either a cardboard or Bakelite tube being allowed. The windings are dry wound without shellac, paraffin or other energy-absorbing materials. Ten turns are used for the primary (L1), 60 turns for the secondary (L2), and 25 turns for the oscillator pickup (L3). It should be remembered that the number of turns on the secondary (L2) is somewhat affected by the length of the aerial and that this number of turns is correct only for aeriels running from 50 to 60 feet in length. Longer aeriels require fewer turns, shorter aeriels require more turns, but for the lengths given the set will easily tune within the ordinary broadcasting limits.

In making connections of the condenser (C1) we must connect the stator or stationary plates (S1) to the wire (8) which runs to the grid of the tube and "C" battery, and the rotor or moving plates must be connected to the line (12). This is necessary to avoid the effects of body capacity. Performance is very much improved and stabilized by the addition of the fixed condenser (K1) of 0.002 mf. capacity which connects the grid return line to the primary by capacity effect. This also reduces body capacity or the tendency toward body capacity.

One of the most important improvements is the use of the biasing or "C" battery placed in the grid circuit with its negative pole (—) to the grid of the tube. With hard amplifier tubes this increases the sensitivity and on local stations greatly increases the signal strength. It is a substitute for the more usual grid condenser and grid leak, and the grid leak and grid leak condenser can be used of course if preferred. By maintaining the grid at a fixed negative potential, the tube works on the most advantageous point in its characteristic curve and in most all cases will give far better results than the usual condenser and leak. A three cell, 4.5 volt flashlight or standard "C" battery is used with plate voltages of from 67.5 to 90 volts, but with lower "B" battery voltages the voltage of the "C" battery is correspondingly reduced. The bypass condenser (K2) is advisable in some cases, while it does no good in others. The necessity for this condenser

can only be tried by experiment in the circuit used, for the units adopted may or may not require this part.

Variometer Less Critical

AFTER much experimental work conducted on plate inductances, I came to the conclusion that a variometer (VA) was less critical and gave better control of the oscillations than the condenser tuned impedance used in the first circuit. The variometer gives more latitude in the range of wave lengths than the former honeycomb coil and there is less tendency toward whistling than before. A very small fixed condenser (K4) is connected across the variometer and establishes the oscillations necessary for this type of circuit. With the apparatus used in the experimental outfit, a condenser of 0.0001 mf. capacity was found sufficient, although 0.00025 mf. might perform better with some classes of variometers. Any standard molded type or self-supporting winding type of variometer can be used at (VA), but we do not recommend wooden variometers as they seldom have sufficient inductance for this purpose.

Some improvement can be had when (K4) is made a variable instead of a fixed condenser, but of course this includes the expense and complication of the circuit at a very little increase in effectiveness. In this case an 11 plate 0.00025 mf. variable condenser is sufficient for the purpose. However, a fixed condenser will perform very nicely, conserving space and simplifying tuning.

At (K3) is a 0.006 mf. fixed bypass condenser which is very effective in stabilizing the circuit and in reducing the resistance to the radio frequency current in the plate circuit. Again, it forms a capacious feed-back from the plate to the grid which materially increases the range and signal strength of the circuit. By examining Fig. 3 it will be seen that some plate energy passes to the primary through (K1) and therefore aids sharp tuning in the plate circuit. The phones (PH) are fitted with the 0.001 mf. bypass condenser (K5) which usually is of value in obtaining clear reception.

For the best results hard amplifying tubes must be used such as the UV201A, C301A, UV199 or C299. Detector tubes of the UV200 type cannot be used, and the WD11 or WD12 do not give very good selectivity or amplification. As a rule, a 67.5 volt "B" battery is the best, although 90 volts can be used with a little increase in volume. With 45 volts on the plate we do not get the proper signal strength, while with 90 volts we generally get noise and distortion. The voltage of the filament battery "A" and the resistance of the rheostat (R) of course depend upon the type of tube used.

(Continued on page 34)

Blueprints of the "Baby-Het" on Two Pages Following.

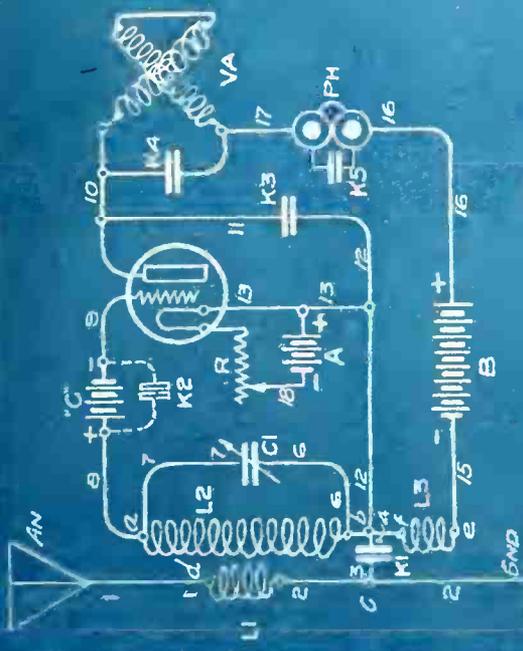


FIG. 3
SCHEMATIC DIAGRAM

NOTE
OUTDOOR AERIAL BEST AT
50 FT. TO 60 FT. LONG. MUST
NOT EXCEED 50 FT. UNDER
ANY CONDITIONS.
LOOP AERIAL CANNOT BE
USED SUCCESSFULLY.

USE ANY HARD AMPLIFYING
TUBES SUCH AS W-201A, C-30A
UV-199, C-299, WITH FROM 67
TO 90 VOLTS ON THE PLATE
AND A C BATTERY OF 4.5 WRT

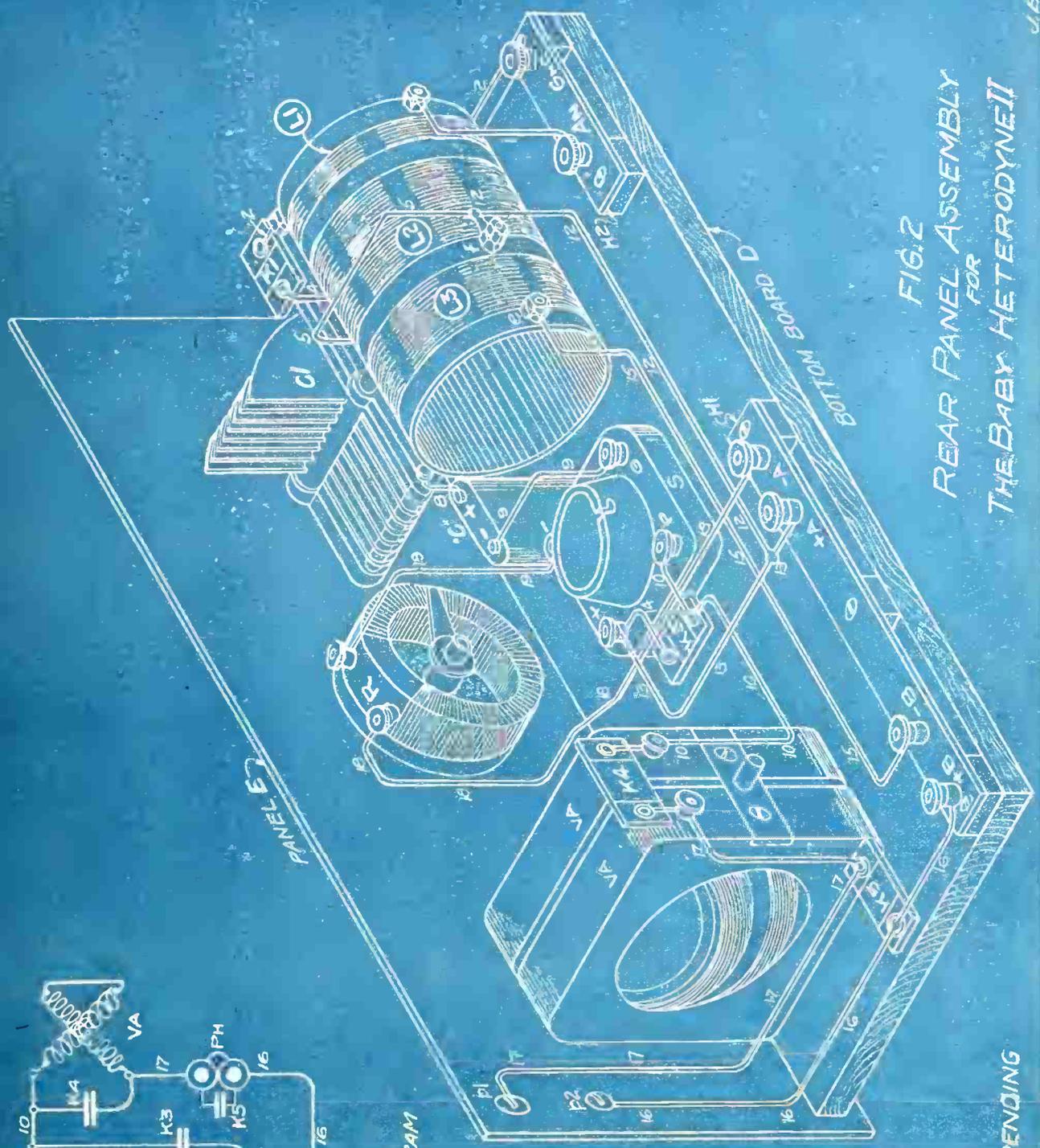


FIG. 2
REAR PANEL ASSEMBLY
FOR
THE BABY HETERODYNE II

An Improved Baby Heterodyne

(Continued from page 31)

Notes on Controls

THERE are two tuning controls, the variable condenser (C1) and the variometer (VA), both of which are very sharp and somewhat critical. This means that both controls should be of the vernier type, particularly (C1), since the latter brings in or drops a station completely on a very few divisions of the dial. Condenser (C1) is a 23 plate, (0.0005 mf.) variable condenser of the vernier type, and preferably should be of the so called "low loss" variety. The variometer (VA) can be the special vernier type of variometer now found on the market or else it can be made into a vernier type by the addition of the small knobs which act on the edge of the dial. Careful adjustment is needed at this point.

Filament control is also of the greatest importance and requires a rheostat which can be closely adjusted. With the proper rheostat the tube can be kept right on the edge of the "spilling point" where the amplification is at a maximum. One of the most important features of this circuit is its ability to work without distortion when the tube is being pushed hard, but to develop this properly requires accurate control of the filament current.

This receiving set will assemble nicely on a 7-inch x 14-inch x $\frac{3}{16}$ -inch panel as shown by (E) in the isometric view of Fig. 2. The panel should be of the hard rubber or bakelite type and is fastened to the baseboard (D) by wood screws which pass through the panel and attach to the front edge of the baseboard. The only wire connections carried by the main panel are the phone binding posts (p1) and (p2).

All battery binding posts and the posts for the connection of the aerial and ground wires are "back connected": that is, are carried by the hard rubber or bakelite terminal strips (H1-H2) located near the rear edge of the baseboard. This arrangement does away with the unsightly wires and connections that are always in view in the front of a front connected panel. The terminal strips are about $1\frac{1}{4}$ inches wide and $\frac{1}{8}$ or $\frac{3}{16}$ inch thick, and are raised above the baseboard so that the bottom screws of the posts do not come into contact with the wood baseboard.

Careful attention should be paid to the wiring and wiring connections. All joints should be carefully soldered where possible, and at points where connections are made to binding posts solder lugs should be used to insure good contact. Ordinary No. 14 tinned square bus wire is best for the purpose as it is stiff enough to hold its shape and is easy to solder. While the wire should be covered with spaghetti at points where one wire passes over another, it is bad practice to cover the whole length of the wire as this increases the capacity without correspondingly increasing the insulation resistance.

SOCKETS are of prime importance in the successful operation of a receiving set and not enough attention is given to this point by the average builder. The best bakelite sockets are none too good for this job, for we must be sure that there is no leaking of the precious energy between the socket springs and prongs, and again there must be no unnecessary resistance between the prongs of the tube and the springs. The cheap "tar paper" sockets made of soft compositions are actually fairly good conductors for radio frequency currents and generally leak enough current to considerably reduce the range and signal strength. Some sockets I have tested leak more current than a 0.5 grid leak, and when the tubes were placed in these sockets no grid leak was necessary. However, this is a mighty expensive means of doing away with a grid leak and most certainly is not recommended.

In buying sockets, see that the springs are stiff and that they make the proper contact with the prongs of the tubes. A socket may carry the filament current so that the filament lights, but this is no guarantee that the grid prong conveys the radio impulse to the grid of the tube or that the plate prong is making sufficient contact to close the plate circuit. There have been all sorts of woe at this point and tubes and hookups have been unjustly accused for what is properly the fault of the socket.

Before wiring up the set, test each piece of apparatus separately so that you will not have to dismantle the whole thing later on in order to remove some faulty member. Scrape off the springs in the socket to a bright surface and then insert a tube to make sure that the springs are making uniform contact with the tube lugs before you screw the socket down to the baseboard. If the tubes are making proper contact, the springs will all move when the tube is pulled in and out.

Secondly, test out the coils (L1-L2-L3) to determine whether there are any broken wires or open circuits in the coils. Very often a wire is broken in winding, or the end of the wire does not make perfect electrical contact at the connection screws. It is not easy to see a broken wire, as it is covered by insulation; hence the only sure test is to connect the coil, a battery and the phones all in series. If the circuit is perfect, there will be a sharp click every time the circuit is closed. If there is no noise when the battery is connected, then the wire is broken or there is a poor connection at some point.

Both batteries should be tested at frequent intervals, particular attention being paid to the "B" battery. We can generally tell whether the "A" battery is working by the way it lights up the filament, but the "B" battery requires a voltmeter. Voltmeters for testing "B" batteries can be obtained at a very reasonable price and are the only insurance against the dead "B" batteries that so often are the cause of trouble. Just the other day I was called in to service a stubborn set which would not operate above a whisper, and found that the "B" battery which should have applied 90 volts on the plate

only developed 16 volts when the voltmeter was applied. The owner was loud in his condemnation of the set until he saw where the trouble lay.

VACUUM tubes of the present day are rushed through the factory at such a rate that they are not properly tested and hence are a source of trouble when we have no means of making a proper test. Wherever possible, it is a good plan to make a trial of the tube in a set that you know is in proper operating order. Try it in a friend's set and compare it with the tube that he is using.

Next, connect a couple of dry cells in series and connect the end wires to the terminals of the variable condensers. If the sparks fly when you turn the rotor in the dark, it is sufficient evidence that the condenser is short circuited. This, if done before the condenser is mounted in place, may save you from burning out a tube, and at the least will save you a lot of trouble in the future. The fixed condensers should be tested in the same way, touching the battery terminals at each end of the condenser terminals. If you see a spark, throw the condenser away; it is short circuited. Unfortunately, a fixed condenser may have only a partial short circuit that is sufficient to cause trouble but not conductive enough to show a spark. This is not easily discovered without the proper instruments and the amateur is not usually able to determine the fault.

After going over all of the parts in this way before they are screwed into place and wired up, we will save ourselves a lot of trouble. The variometer, like the coils, should be tested for open circuits, due to broken wires and loose contacts at the rotor. The rheostat should also be tested for open circuits and also to see if the contact finger touches the wire coil at all points with equal tension or pressure. Much trouble is had with rheostats that "run off center," since the finger will not make contact at certain points and will open the circuit or dim the tube.

It is generally easier to hook up the filament circuit first—that is, connect all wires of the filament and "A" battery to the rheostat and socket before anything else is done. Then we can follow up with the plate circuit and then the tuning circuit.

In case the circuit tunes broad or the necessary selectivity is not obtained, reverse the aerial and ground connections at (d) and (c). If the variometer seems to have no effect on the control of the circuit, reverse the connections of the coil (L3) at the connections (b) and (e).

If the circuit does not tune down to low enough wave lengths, remove a few turns of wire on (L2). If it does not reach the higher wave lengths, a few turns can be added to (L2).

[*"Baby Heterodyne Notes," containing answers to questions regarding Mr. Rathbun's first "Baby Hel" hookup will be published in October RADIO AGE.*]

FIG. 2
REAR PANEL ASSEMBLY
FOR
APERIODIC VARIOMETER


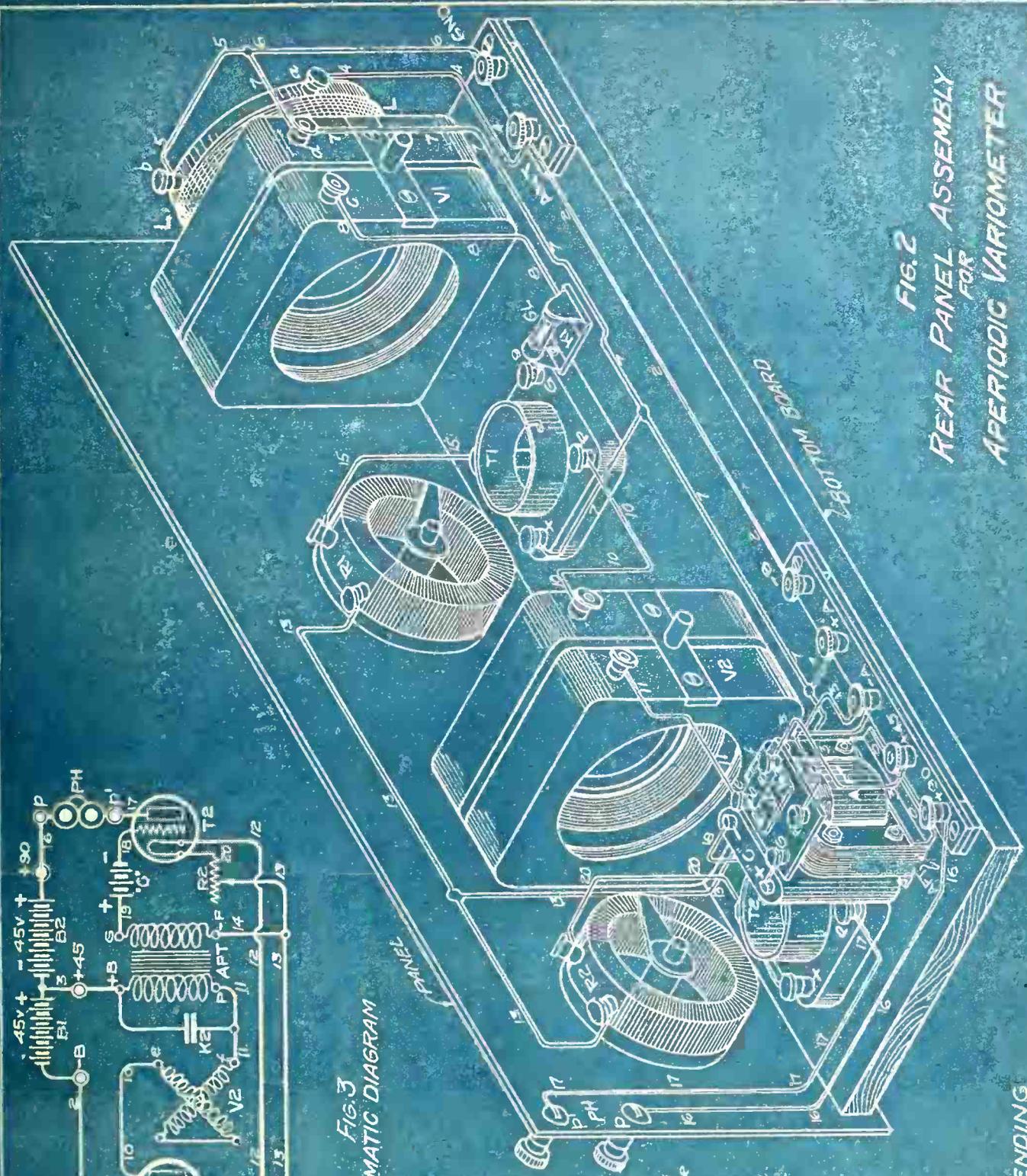


FIG. 3
SCHEMATIC DIAGRAM

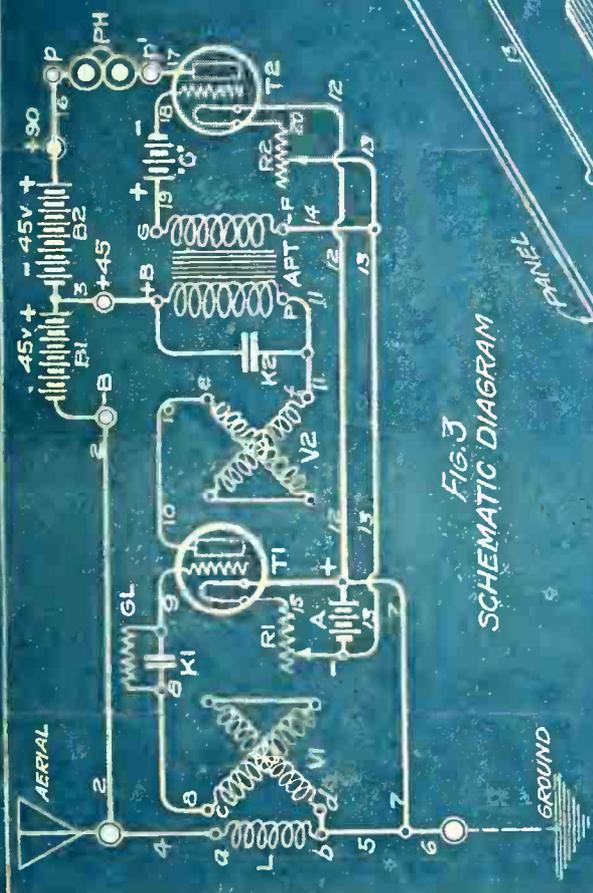

OUTPUT OF SET TO BE CON-
NECTED TO PHONES OR LOW
SPEAKER AT POINTS P-P.

NOTE!
USE ONLY AMPLIFYING TUBES
SUCH AS 6X4, 6X5, 6X6, 6X7, 6X8, 6X9, 6X10, 6X11, 6X12, 6X13, 6X14, 6X15, 6X16, 6X17, 6X18, 6X19, 6X20, 6X21, 6X22, 6X23, 6X24, 6X25, 6X26, 6X27, 6X28, 6X29, 6X30, 6X31, 6X32, 6X33, 6X34, 6X35, 6X36, 6X37, 6X38, 6X39, 6X40, 6X41, 6X42, 6X43, 6X44, 6X45, 6X46, 6X47, 6X48, 6X49, 6X50, 6X51, 6X52, 6X53, 6X54, 6X55, 6X56, 6X57, 6X58, 6X59, 6X60, 6X61, 6X62, 6X63, 6X64, 6X65, 6X66, 6X67, 6X68, 6X69, 6X70, 6X71, 6X72, 6X73, 6X74, 6X75, 6X76, 6X77, 6X78, 6X79, 6X80, 6X81, 6X82, 6X83, 6X84, 6X85, 6X86, 6X87, 6X88, 6X89, 6X90, 6X91, 6X92, 6X93, 6X94, 6X95, 6X96, 6X97, 6X98, 6X99, 6X100.

PLATE VOLTAGE ON DETECTOR
TUBE = 45 VOLTS. PLATE VOLT-
AGE ON AMPLIFIER TUBE = 90
VOLTS. USE TWO BLOCOS OF 45
VOLT "B" BATTERIES.

COPYRIGHT 1924
RADIO AGE, INC.
CHICAGO, ILL.

PAT. PENDING

An Aperiodic Variometer Set for Efficiency

(Continued from page 29)

circuit, the coil (L) also acts as the tickler or feed-back coil which induces additional impulses into the secondary by connections with the plate circuit. The tube of (L) is fastened to the side of a standard molded variometer in any way that may be convenient with the instrument used. The distance between the coil and variometer is not critical and can be made as shown. Any type of molded or honeycomb variometer can be used, but a wooden variometer is not usually practical owing to the great clearance space ordinarily found between the rotor and stator of the wooden variometers.

AT (V2) we have the standard plate variometer used for controlling regeneration and for varying the inductance of the plate circuit. This can also be any standard type of molded or honeycomb variometer but usually the inductance value must be greater than can be attained with the ordinary wooden variometer. Very frequently the inductance of wooden variometers is so low that they have absolutely no effect on the regeneration when turned in any direction, and this fact is emphasized for the benefit of those of our readers who may attempt the building of the circuit with this type of variometer. The tuning is exceedingly sharp and fairly critical so that the addition of a "Tiny Turn" vernier button to the dials of the variometers will be of importance, or any other type of geared vernier adjustment which can be conveniently attached to the dials.

At (K1) we have the usual type of grid condenser with a capacity of from 0.00025 to 0.0005 mf. the former value usually proving best for the UV201A and UV199 tubes. Tube (T1) is the detector tube which is controlled by the filament rheostat (R1). Of course maximum results are obtained with the power tubes operated by a storage battery such as the UV201A, but very good results can also be obtained by the small dry cell tube known as the UV199. The WD11 and WD12 are not so selective but can be used if the other tubes are not practical under the given operating conditions. The soft detector tubes such as the UV200 will not give as much volume on strong signals as the UV201A or the UV199 for the reason that we cannot carry such high plate voltages on the soft detector tubes.

Distortion Eliminated

As shown in the diagram, 45 volts are used on the detector tube (T1) and 90 volts on the audio amplifier tube (T2). This gives the maximum results without distortion when the UV201A and UV199 are used. Using a higher voltage on the detector tube (T1) gives a somewhat greater signal strength on local stations but it also introduces undesirable tube

noises and distortion. Lower voltages than those specified naturally give weaker signals, and the weaker voltages on the plate also reduce the selectivity of the circuit.

The grid leak (GL) is of the pencil mark or other variable leak. Its value is to be adjusted until the signals are strongest and clearest. If the resistance is too high, then there will be noises and the reception will have a whiney tone. If the resistance is too low, then too much radio frequency current will be bypassed and the signal strength will be reduced. The proper value for any one tube can only be tried by direct experiment.

THE aerial connection at (ANT) together with the ground (GND) and battery connections are placed at the rear of the set, thus allowing all wires to enter the rear of the cabinet and improve the appearance of the receiver. The binding posts at the rear are mounted on two strips of bakelite or hard rubber about 1" to 1 1/4" wide and about 3/16" thick. The strips are raised above the surface of the

**USE THE ORIGINAL
RADIO AGE
BLUEPRINTS
On Pages 30 and 35
to Make This
Aperiodic Variometer Set.**

**Another Group of Unrivaled
Blueprints in October RADIO AGE.**

bottom board, so that no metal parts or wires will come into contact with the wood. This construction is clearly shown in both Fig. 1 and Fig. 3, page 35, the latter being the isometric view of the set.

Audio Amplification

For aid in picking up distant stations at good volume and for loud speaker operation on local and at moderate distances, one stage of audio frequency amplification has been added. Stations 200 miles away have been picked up with good volume on the loud speaker with the single amplifying stage, and local comes in with terrific volume. In fact, local stations can be had on the loud speaker with the detector tube (T1) alone, but as will be explained, it is considered desirable to have the detector and the amplifier connected in one permanent unit.

A five-to-one ratio audio frequency transformer is shown at (AFT). The primary of the transformer is connected at the posts (P) and (B) to the detector circuit at the output wires (e) and (f).

The secondary of the transformer is at (G) and (F), and is connected into the circuit of the amplifier tube (T2). A three cell, 4.5 volt "C" battery is connected in the grid circuit of the amplifier tube for biasing the grid and is of great assistance in clearing up the reception and for obtaining maximum amplification. In

all cases, the negative (—) terminal of the "C" battery should go to the grid (G) of the tube, so that the grid will receive a negative charge or bias. The output or plate (P) of the tube (T2) goes to the phones or loud speaker (PH).

In laying out this circuit, it was considered advisable to omit the usual jack between the detector tube and amplifying stage, both on the score of simplicity and effective operation. While both tubes must be used at all times with the present arrangement, yet it has certain advantages which are lacking when intermediate jacks are installed. For example, there are no losses or noises due to imperfect contacts in the jacks, and, further, as the audio stage is always in circuit, there is no danger of detuning a distant station when the audio stage is plugged in. When a jack is installed after the detector, and when one picks up a faint signal, it often happens that this station is lost when a stage or two of audio is plugged in at the jacks.

In this arrangement, this cannot happen, and when the reception becomes too strong, we have merely to turn down the rheostats.

DeForest Films Sound and Action Miles Apart

Dr. Lee DeForest, inventor of the Audion, which makes possible radio broadcasting and receiving, as well as talking motion pictures, has just achieved another triumph. He has invented a long-distance synchronizing device by which two cameras, one photographing sound and the other action, may be operated simultaneously, and the resultant product afterwards amalgamated in perfect synchronization.

The Democratic National Convention in Madison Square Garden in New York City afforded the opportunity for Doctor DeForest to test out his new invention. A regulation motion picture camera was set up in Madison Square Garden, where the wild scenes of the convention were photographed. At the same time a DeForest Phonofilm camera was in action in the studio of Doctor DeForest on East Forty-eighth Street. These two cameras were connected by radio, the one in the Garden photographing the action and the one in the studio the sound. From the two negatives thus produced, positive prints were made which contain both the sound and the action. The result was a photographic reproduction of the convention that is absolutely startling in its realism.

The possibilities of this latest invention of Doctor DeForest are almost incomprehensible. As an illustration, a great naval battle might be fought off the Pacific Coast, with a news reel photographer on the spot. He would communicate with DeForest at his studio in New York, for instance, and announce that fact. Then he would proceed with photographing the action of the battle, while in New York the sounds of the cannonading would be recorded, in perfect synchronization with the photographed action, and the two amalgamated later on a standard motion picture film.

RADIOTORIALS

EIGHT of the largest radio manufacturing corporations in the United States were named recently as defendants in a complaint filed by the Federal Trade Commission, charging the use of "unfair methods of competition in commerce in violation of Federal Act."

The complaint alleges that the defendants have combined and conspired to create a monopoly in the manufacture, purchase and sale of radio devices and apparatus and other electrical articles. An attempt to monopolize domestic and trans-oceanic radio communication and broadcasting is also charged.

The Government's charges are the natural outcome of the recent trend in the progress of radio. Little manufacturers have been squeezed out of business, while the big corporations continue to absorb their weaker competitors and take over as many radio patents as they can buy.

If such wholesale absorption continues, radio will soon be in the tentacles of a one-man corporation operating only for profit and with no regard for the common good. The Government of the United States has shown wise foresight in investigating these alleged attempts at monopoly and to nip in the bud any effort to take radio out of the hands of the independent broadcaster, listener and manufacturer.

Of course the eight defendants will reply and deny the charges. But their alleged unfair activities have at least been restricted by the bulldog watchfulness of the Federal Trade Commission.

Regardless of who these corporations are, they are attempting to control the radio industry, as big corporations will. If they buy up all the patents of any importance, it is easy to foresee what will happen to the small but efficient manufacturer whose products are now the pride of the radio industry and whose inventions are helping to develop radio so rapidly. Monopoly of radio patents will drive independent incentive to the wall. Radio will become stabilized to the point of stagnancy.

The Federal Trade Commission's complaint also charges attempted monopoly over domestic and trans-oceanic broadcasting. Here the listener is affected. If broadcasting is monopolized, you can imagine the kind of cut-and-dried, political programs that will be served to the listening public in the not too distant future. The listeners will tire of censored programs and interest will drop off as a result.

The amateur operator will also be affected. He will be restricted because his devices are controlled by the big corporations. The corporations will tell him just what he can do and what he must not do. Domestic broadcasting, both in code and programs, will become a joke and the toy of a mercenary trust.

The foregoing examples of what *might* happen do not mean they *will* happen. In fact, the Government's action indefinitely forestalls any chance these corporations might have had to further their alleged monopolistic ideas. But this action should arouse the listeners, the amateurs and the independent broadcasters and manufacturers to such a stage of enthusiastic protest that any plans for a "Radio Trust" will disappear before they are well under way.

Here is a chance for the amateurs to get busy and render another service like that which characterized their fight against the proposed radio tax. The life of

the amateur and the small broadcaster is at stake. It will be a fight extending over a period of years, and upon it will depend whether radio is to continue to be a public utility for public good or just another means for personal publicity.

A CONVICT in a Middle Western state penitentiary wrote to a storage battery dealer in his home town and asked for a second-hand radio battery to attach to a receiver that he had built and set up in his cell. He paid for it out of his meager earnings of a dollar and a half a month, saved during the four years of his imprisonment. The convict related his life as a shut-in and how the little radio set brought him his first touch with the outside world. He told how the set had cheered him and built hope in his heart that he will be able to live a straight life when his release comes. It was a human letter and touched the heart of the battery dealer, who decided to send the convict a brand new battery instead of a second-hand one. But before doing so he asked the warden of the penitentiary for his consent. The warden refused, explaining that "radio within prison walls has not yet been put through the experimental stage." So the convict didn't get his battery and the world beyond has been cruelly cut off. We believe radio in the future will do more than endless preaching, bullying and solitary confinement to reform prisoners in our jails. That warden would have been doing a public service toward reducing criminal tendencies if he had not only permitted that one convict to have his radio set, but had ordered sets installed in every cell. Some day we hope such a liberal and humane measure will be taken by forward-looking states.

RADIO FANS like nothing better than to make their own sets and be assured that they are making them correctly. The chief fault with thousands of home-made radio sets is that they are the result of wholesale guesswork and not of careful following of specified plans. In printing four pages of real blueprints in this and succeeding issues, RADIO AGE believes it is helping the exasperated radio fan to get down to a working basis and build his sets *right*. The building season is about to start, and there is no better insurance for successful reception than clear, accurate and authentic blueprints for working drawings. The blueprints in this issue are the last word in reliability—as are the hook-ups they portray.

WE NOTE with interest that a group of manufacturers has organized a Radio Manufacturers' Association for the general improvement and stabilization of the radio industry. This is only another indication that the big men in radio are realizing that the best sets and accessories can be made only by individual incentive and not by the hired talent of grasping corporations. The men who make up the Radio Manufacturers' Association are leaders in their respective radio fields and they know that their mutual co-operation will make radio safe for the listener, the amateur and the independent broadcaster who wants to give the public what it wants—not what the broadcaster wants.

You Cannot Afford to Miss the Priceless Hookup Ideas in the 'Annual'

The profound technical problems to be encountered in the study of Radio are all very interesting to the expert, but the great majority of "fans" are vitally concerned in the building of simple sets that really will work and produce effective results.

To supply this demand for practical, simple and efficient sets, RADIO AGE compiled THE RADIO AGE ANNUAL for 1924 in the belief that it contains more real help and meaty material than any other book on this subject ever published.

THOUSANDS have been sold at \$1 each since they were first offered to fans early this year. The supply is rapidly becoming exhausted, so we are making this last appeal to the fans to order their ANNUAL now if they have not already done so.

Full of Hookups That Are Guaranteed to Work!

here!

This Coupon, Pinned to a Dollar Bill, Will Bring the ANNUAL to You by Return Mail!

(If by Check, Add 5c for Exchange.)

RADIO AGE, Inc., 500 N. Dearborn St., Chicago, Ill.

Gentlemen: Attached find One Dollar (\$1) for which kindly forward me by return mail one copy of RADIO AGE ANNUAL FOR 1924. If not satisfied with it I will return it to you within three days and you will refund my money.

Name.....

Address.....

City.....State.....

This Book Is Endorsed by Expert and Novice Alike


The principal articles are illustrated with the well-known RADIO AGE isometric drawings, reputed by countless experts as the clearest construction diagrams ever put on the market.

The construction of every standard set and essential accessories is described in detail in the ANNUAL. Each tuner and each accessory was built in the RADIO AGE laboratories and tested and proved before it was awarded space in the ANNUAL.

You cannot afford to be without this wonderful radio "guide book." Send your dollar today for this gold-mine of radio ideas.

A Few of the Features

- | | |
|----------------------------------|------------------------|
| Simple Crystal Set | Reinartz |
| Long Distance Crystal Set | Haynes |
| Your First Tube Set | Hopwood |
| Erla Reflex | Cockaday |
| Kaufman Tuner | Neurodyne |
| Grimes Inverse Duplex | 3-Circuit Tuner |
| Two Stage Amplifier | Super-Heterodyne |
| Baby Heterodyne I | Simple Radio Frequency |
| One Tube Loop Aerial | Ultra Audion |
| Wave Trap, Filter and Eliminator | Rosenbloom |
| Loading Coils | Push-Pull Amplifier |
| Transformers | Portable Reinartz |
| Battery Charger | Wave Meters |
| | Two-Circuit Crystal |

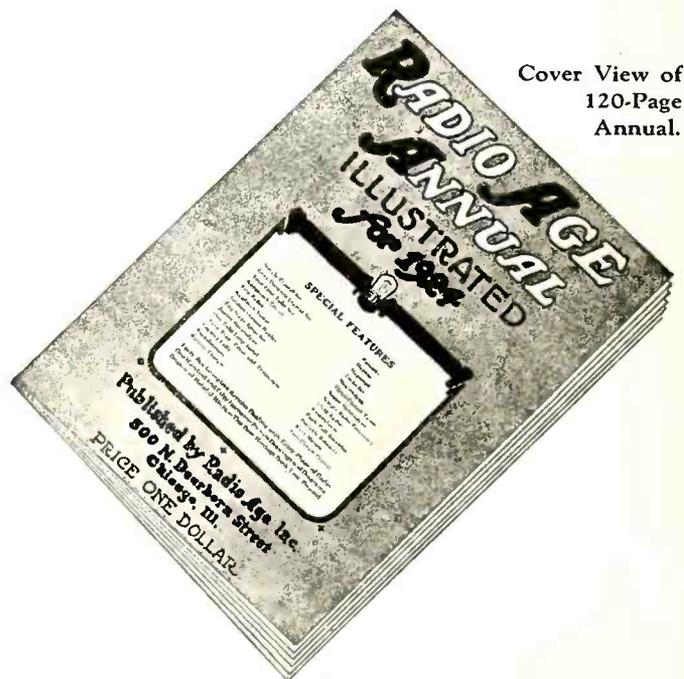

Radio In Other Lands



Lack of Vision Prevents Germany From Taking Her Place in Radio Progress

BERLIN:—If the visitor to Germany were to judge by the number of aerials seen above the roofs of dwellings, he would make the error of assuming that popular use of radio receiving sets in the republic was in a flourishing state. It should interest every American lover of radio and every American official who has to deal with regulation of radio transmission and reception to read the following facts about the collapse of popular radio in Germany after a few months of feverish enthusiasm. By observing the errors other governments and peoples have made in connection with radio development, the United States may avoid committing similar disastrous mistakes.

One reason for the astonishing decline in home radio activities in Germany is perhaps to be found in the fact that Germany failed to perceive the vast possibilities in the new art, either as a social factor or as a richly profitable industry, until long after the people of the United States had made great strides toward developing and stabilizing radio.

Radio a "Toy"

An American in Berlin told me that no longer than a year ago he was requested by New York people to inquire as to the possibility of obtaining twenty thousand complete radio sets from German manufacturers. The Berlin interests to whom the American carried this proposal greeted it with derision.

"Why!" they exclaimed, "the German people are a serious minded people. They would not consider going so extensively into the business of producing such a toy as the radio set."

THAT ended the negotiations. Since then the same German manufacturers have seen the light and are desperately trying to make up for lost time and neglected opportunities.

With characteristic alertness in finding markets abroad for German products, the manufacturers there are constantly pushing out into new fields, offering credits and prices that sometimes are the despair of competitors in other countries. One important radio manufacturing concern in Germany is doing an extensive business and there are scores

By FREDERICK A. SMITH

of smaller establishments that are capable of producing equipment in quantities. But the fact remains that Germany has not been able to make the same popular success with home radio that has been achieved in the United States. England also has far out-raced Germany in the development of radio in and for the home.

RADIO TRAVELOGS

Frederick A. Smith, editor of RADIO AGE and author of the series on foreign radio beginning in this issue, has just completed a tour of eight European countries observing radio conditions and practices. He was correspondent on the West Front during the World War for the Chicago Tribune and flew into



Frederick A. Smith

Berlin a few days after the armistice in 1918. On returning to the American lines he filed a single cablegram of 17,000 words which was published in all the leading papers of the United States. These experiences equip him with the ability to travel intelligently and accurately observe conditions.

After looking over the situation in Germany, I would say that the almost tragic suspension of radio interest among the people is due to the following conditions, some of which are being corrected:

The Causes

Limitation of adjustment of receiving sets to 700 meter wave length.

Failure of German manufacturers to standardize standard parts such as bulbs, sockets, head phones and plugs. Fans who sought to replace parts in their sets had great difficulty in finding parts that would fit their sets.

Programs of an unsatisfactory character.

Taxes imposed on manufacturers, dealers and users of sets.

Sale of inferior tubes and insufficient production of tubes.

German broadcasting, manufacturers and use of receiving sets are under supervision of the Reichs Telegraph, which corresponds to the Post Office supervision in England and to the Department of the Interior supervision in the United States. But the paternalism of the German government's attitude is in striking contrast to the rather liberal methods employed by the American authorities. So far as radio is concerned, the German government officials attempted to do all the thinking for the people who might be interested in radio. In the end it was the people who did the thinking and the government is now left with a deflated bubble on its hands.

One of the restrictions placed upon radio operation in the German homes was that which prohibited the use of circuits which might reradiate. The wisdom of any arbitrary exclusion of a radio circuit may well be doubted at any time. In a case where an apparently flourishing home industry fell afoul of evil times, such exclusion must be considered as significant as a possible contributing cause of the collapse of radio interest.

In the next place, the manufacturers of radio sets in Germany were forbidden to make any sets that would pick up broadcasting on other than the 700 meter wave lengths. The manufacturer was compelled to submit a sample of the set he proposed to produce.

THE main telegraph office examined the set and either approved or condemned it. In case the set met with the approval of the telegraph office, the manufacturer was permitted to make sets, always with the provision that each set should be sealed by the government and have upon the seal the initials, "R. T. V." For each set thus made the manufacturer was compelled to pay seven marks (about \$1.75) to the Reichs Telegraph. On June 1 of this year this tax was reduced to three and one-half marks per set. It is necessary to stamp each tube produced by a German manufacturer and to pay a government fee of one-half a mark for producing it. It

should be remembered that the mark mentioned herein is the new German mark which appears to have a stabilized value of about twenty-five cents in American money.

Factories which made bulb sets had to pay 2,500 marks to the government.

Retail dealers in radio sets and equipment formerly paid 800 marks to the government each year. It is interesting to note that 300 marks of this sum was for the privilege granted to the dealer to demonstrate receiving sets for customers who came to his shop. The total tax on retail dealers has now been reduced to 30 marks each month.

All Sets Taxed

Now for the tax on the broadcast listener. It appears that the burden placed upon the German radio lover was sufficient without adding a financial weight to it; but Germany insisted that the user of a set should pay 60 marks per year as a penalty for enjoying (?) those programs which might be available on the 700 meter wave length. This tax included the modest crystal set as well as the more expensive tube sets.

The tax on the listener-in produced much the same situation that England faced when it sought to make the receiving set owner pay a fee. Thousands upon thousands of users of sets ignored the tax and went on their way trying to make radio function without benefit of legal rights. The German government very sternly called attention to these delinquencies and serious punishment was prescribed for those who evaded the tax. But the radio fans apparently felt that the government's radio bark was worse than its bite and the tax evasion continued placidly. Nobody went to jail.

It was then decided to reduce the fee to only two marks the month. Immediately there was a substantial increase in the number of permits applied for. Whereas only 20,000 fans had declared themselves as such under the higher tax and obtained the ostensibly necessary government permission to use a set, one hundred thousand persons in Berlin alone now have government license to "listen in." Seven per cent of the proceeds of all these taxes was and is devoted to assisting the financing of broadcasting from the various public stations in Germany. This method of aiding broadcasters is followed in England and the situation there will be described in another article of this series.

There is no estimate available of the number of sets in use in Germany at the present time. Radio in the home was forbidden by the government up to October 3, 1923. There was a small exporting business and a few amateurs were trying out circuits of their own production in secret. On October 3 the government announced that use of home radio sets would be permitted. It was fondly hoped that a revenue could be obtained from the enthusiastic members of the radio fraternity that had refused to be suppressed by a frowning government. The first broadcasting station was established in Berlin, practically financed by the government.

Enthusiasm Grows

THE rush for receiving sets was enormous. The industry had had no chance to develop normally or effectively and there was a consequent rush of manufacturers into the business of making sets and parts. There was absolutely no uniformity of size of parts and the confusion of the fan who wanted to replace any accessory of his outfit may be imagined. He rushed from shop to shop in pursuit of tubes that would fit the peculiar sockets in his set, or went feverishly about looking for plugs that would fit the holes in his panel. Material was put on the market by inexperienced manufacturers who fell far short of excellent production. There was a famine in bulbs and radio folks know how aggravating it is to have a set for which no tubes are available.

Despite all these difficulties, fans bought outfits at prices ranging from 400 to 600 marks. German enthusiasts at first were not aware of the fact that crystal sets could be used and when they learned that this inexpensive form of radio fun had been withheld from them, with the consequent necessity of paying good sums for tube sets, many of them complained that they had been imposed upon.

In addition to all this the requirement that all sets should be sealed by the government and kept sealed caused confusion. If a fan wanted to open his cabinet to replace a worthless tube or other part he was forced to break the seal. Then who was to replace the seal?

Broadcasting stations were apparently unable to meet the varied tastes of German listeners-in. Many wanted jazz music instead of classic numbers, and vice versa. The merest suggestion of political flavor in a broadcast talk caused a whirlwind of protest from fans throughout the republic. And then there was the monotony of that 700 meter wave length. This restriction made it impos-

sible for the Germans to pick up the stations that might have entertained them from England, France, Holland and other adjacent countries.

Radio Suffers Set Back

Then along came more serious financial difficulties in the German business world. In March of this year the radio business suffered a violent slump. Many manufacturers went out of business and sets that formerly had sold for 300 marks are now being offered at 100 marks, and this price is not a sufficient temptation to keep the fan in the game. German landlords appeared to have a strong objection to the erection of aerials on roofs and this led to legal complications, many suits having been brought by radio enthusiasts and by landlords.

I found radio manufacturers and dealers in Germany somewhat doubtful of the possibility of bringing the industry back to a flourishing condition. But

I formed the opinion that it will not be long before the government and the business interests will find a readjustment of conditions that will yet put radio back on the map in music-loving Germany. I predict that Berlin one day will be one of the great radio centers, just as it is now one of the most important capitals of the continent.

When the day comes that all the world will be linked in a chain of radio stations and all peoples will be aerial neighbors, it is to be hoped that Germany will have solved her radio difficulties and be a part of the great international game whose brilliant future we in the United States so confidently anticipate.



Keystone View.

GERMAN BROADCASTING STATION READY SOON

The largest broadcasting station in Germany is shown in the picture. It is located at Konigswusterhausen and is to be used, when completed, for broadcasting as well as code purposes. Its radius will be 4,000 meters. The entire plant will operate on three 350 H. P. Diesel engines.



Pick-ups and Hook-ups by our Readers



The material appearing under the title "Pickups and Hookups by Our Readers" in RADIO AGE, is contributed by our readers. It is a department wherein our readers exchange views on various circuits and the construction and operation thereof. Many times our readers disagree on technical points, and it should be understood that RADIO AGE is not responsible for the views presented herein by contributors, but publishes the letters and drawings merely as a means of permitting the fans to know what the other fellow is doing and thinking.

YOU remember the way old WDAP used to come on the air? All you old timer Dial Twisters do, I'm sure. They used to have a wonderful song that made you jerk your shoulders and sway when Jack Nelson sang "WDAP." Here's a little parody on his song that opens up this month's Pickups Section:

*Hello John,
Are you on
To the good old Pickups Page?
If you haven't tuned in,
You've missed a bet;
It's the best in RADIO AGE.
Now I don't know where you
Happen to be,
But there's one thing sure
That is easy to see:
The contributions snappy,
Will make you happy
As a radio bug should be.*

CHORUS

*Oh, you ought to read the letters,
And the diagrams so clear;
Learn what the bugs are doing,
Though they live both far and near;
Now if you want to be a member
Of this Dial Twister rage,
You've got to learn to tune, so
You'll get a button soon
From*

—The Editor of the Pickups Page.

CONTRIBUTORS

J. H. Fargnahr A. J. Secor J. J. Drey P. Edward Chapman

DIAL TWISTERS

Name	Address	Circuit
Ralph Mellon	25 King Street, Pottstown, Pa.	Regenerative
Ray Hahn	3517 Chestnut Street, Milwaukee, Wis.	Three Circuit
P. L. Hartnett	316 Henderson Avenue, Tampa, Fla.	Single Circuit ES Crosley
Robert M. Hillis	1462 Belle Avenue, Lakewood, Ohio	Ultra-Audion
Clair McCormick	Ewen, Mich.	Crosley Trirdyn
Franklin Troutman	11304 Coates Avenue, Cleveland, Ohio	Single Circuit

J. H. Fargnahr, of 3974 Olive Street, St. Louis, Mo., says that he is just "oscillating" with information on a new transformer for a neutrodyne receiver that he thinks is the stuff to neutralize easily. The following tells the story:

**RADIO AGE,
Gentlemen:**

Experiencing quite a bit of difficulty in neutralizing a neutrodyne receiver, I hit upon quite an idea, which, while it gives complete magnetic coupling between primary and secondary, it magnetically isolates each transformer, which in turn prevents magnetic coupling between RF transformers, and also saves consid-


erable space behind the panel in shortening leads.


In this "doughnut transformer" the wire to be used for the primary and secondary is wrapped with felt in addition to double covered insulation (to get around the inter-turn capacity effects) in such a manner that the closed magnetic path is run directly through the center of the core. This doughnut core (having practically the same permeability as air) is used as a form only, and any other non-magnetic material would do just as well, as it serves only to guide the transformer windings. It should have an inside diameter, just roughly one-third of the outside diameter.

The primary is wound on the "doughnut" core (threading each turn through the hole in the doughnut) in such a manner that one or more complete layers are obtained. Fractional layers unbalance the magnetic field and defeat the original purpose of the transformer.

A thin layer of felt is wound on covering the primary, and the secondary is then wound, care being taken to obtain complete layers in the same manner as the primary.

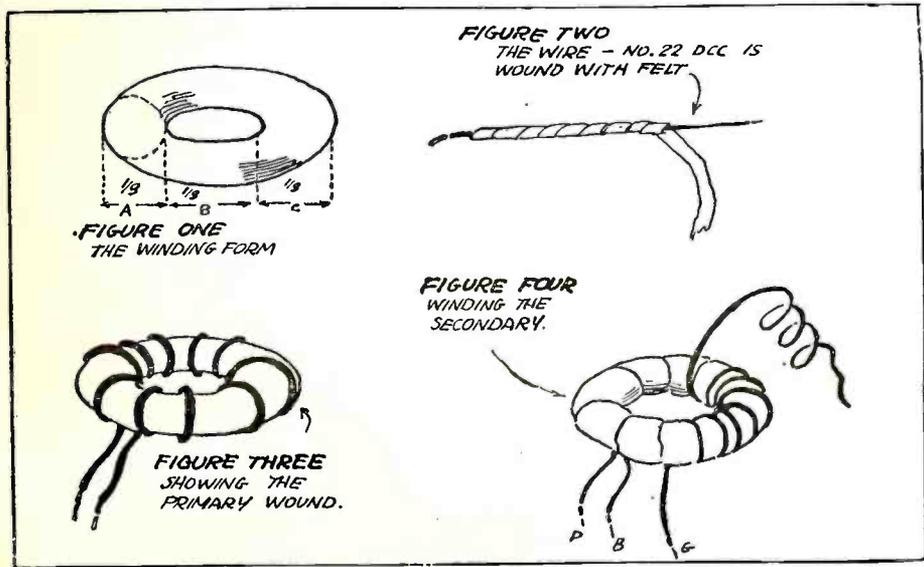Five holes are drilled in the lid of a metal box (obtained in most any drug store) in order to bring out the transformer leads and the neutralizing tap. (Note—If a straight RF transformer is made in this fashion, the neutralizing tap can be omitted. This would make only four leads—two primary and two secondary.) Holes are drilled in the bottom of



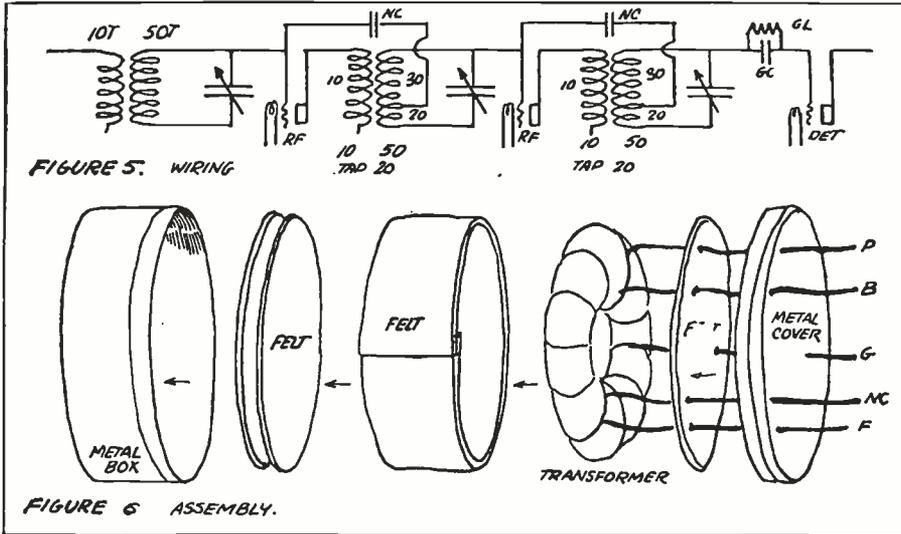

out of this circuit if possible, as they are "lossers."

Yours very truly,
A. J. SECOR.

228 Laurel Ave.,
Bridgeport, Conn.
July 19, 1924.

This is just the type of letter and report we are looking for; concise and to the point with a report of results, type of apparatus and modifications used. Some of the experimenters who read this department might use Mr. Secor's form of giving the results with various circuits. Your suggestions are certainly appreciated, and we'll bet they will make a good many reflex fans change wires in their receivers.

And now we've got to devote some space to our friend, J. J. Drey, of Iron River, Michigan; who still continues to be flooded with mail. Evidently there is some question as to how he winds his coils, and he has kindly consented to tell the many Twisters just how he does it. Right here I might ask the fellows to be a little judicious about asking other Dial Twisters for information. Remember some of them are busy men; they have other things to do, and while they would be glad to help you out, they really have to devote some attention to private interests. If you really *must* ask questions of these generous radio men, make your questions to the point; ask only what you really need.

the metal box so that the unit may be fastened to the end plate of the tuning condenser. The bottom and sides are lined with felt (be generous) and the transformer windings are put into place.

The boxes should not be connected together, nor should they be grounded. The tube may be mounted directly behind this metal box-condenser unit, and much space may be saved in this manner.

In closing, I sincerely hope that this little suggestion may help some of the fellow DT's out of the neutralizing troubles.

Most oscillatingly yours,
J. H. FARGNAHR.

3974 Olive St.,
St. Louis, Mo.

although I suppose Mr. Robbins would not approve.

I enclose hook-up as modified. You will note that I am not partial to potentiometers or the untuned primary.

I have also built the tuned impedance reflex as shown in the July number and had good results with that hook-up also, and then I modified it to better advantage. I enclose modified hook-up of that circuit.

Values for fixed condensers are not given because they are dependent on transformers and other apparatus used, and values are best determined by experiment.

On hook-up No. 1 a .005 MFD was used across the phones, while

RADIO AGE,
Gentlemen:

In your June issue of RADIO AGE you have published my hook-


You have no doubt seen shielded transformers before—but nearly all of them were of the fixed type. We don't know how the above idea works out, but it certainly looks good, and we're giving it to you just as our St. Louis friend gave it to us. If any of the readers of this department try it out, let us know how it works out. The sketches submitted by the contributor are given in Figures 1, 2, 3, 4 and 5.

Old readers of RADIO TOPICS and those readers of RADIO AGE who are interested in reflex stunts will like this next contribution. RADIO TOPICS readers will recall that Tri-Coil circuit, and RADIO AGE addicts have in mind the Sure-Fire circuit. The following is a contribution that can be applied to either of them:

RADIO AGE,
Gentlemen:

Just a few lines in appreciation of a good radio magazine and equally good hook-ups.

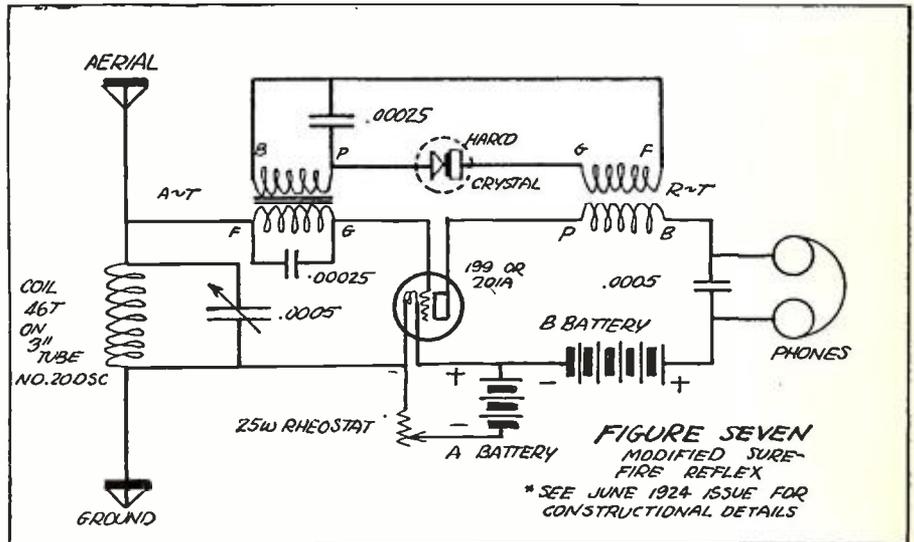I try out all of the reflex layouts, as reflex is my hobby. I built the Sure-Fire reflex as shown in the June number and had very good results with it. I then rebuilt it in accordance with some ideas that I had and increased the volume considerably, without any sacrifice of selectivity,



for No. 2 a .0015 was used.

The R. F. T. in No. 1 is a Tri-Coil type 9.

The variometer in No. 2 is a Raven.

The variable condenser in both hook-ups is of brass milled and turned from the solid block. (I used to be a tool-maker).

I can get WJZ and WOR on a table talker with both of these hook-ups.


Once more, keep potentiometers

up, as I have found, through experiment, to give exceptionally good results and through my experiments I have found the correct winding of a coil, that covers the general broadcasting waves, which is submitted in the sketch. To date I have received many letters requesting further information on the winding of the coil. You neglected to state the number of wire. It should be a 24 or 26 single cover cotton. Either one will do, but louder and clearer signals I have

found better with number 24 gauge.

There seems to be also a misunderstanding by the Reinartz fans in regard to the winding of the coil. I am herewith submitting to you a new sketch clearly illustrating the numbers on the taps. Will you kindly publish this as clearly as possible to enlighten numerous Reinartz fans. I am a very busy man with store duties and have not the time to answer each one personally in detail, but will always welcome any information, should one be in difficulty regarding the hook-up.

The instructions for widening the coil are as follows: Procure an ordinary spider frame which may be purchased at any radio shop. It has a wooden center of about 1 3/4 or 2 inches in diameter, with 17 spokes. Start winding the plate coil, which is on the inside of the frame. The starting end of the wire is the first tap. Wind 15 turns around in spider web form in weaving every second spoke in each one. This will form a Duo-Lateral air winding. Wind for 15 turns, make the second tap. Wind 15 more turns. This will be the fourth tap or the end of the plate coil. Cut the wire off, twist around the spoke. Now start your grid coil, which is wound right next to the plate coil, the end being about a quarter of the diameter away from the forty-fifth or end tap of the plate coil. The starting point of the grid coil is the first tap. Wind one turn, make the second tap. Wind two more turns, make the third tap. Wind two more turns, make the fourth tap. Wind one more turn, make the fifth tap. Wind one more turn, make the sixth tap. Wind one more turn, make the seventh tap. Wind one more turn, make the ninth tap. Wind two more turns, making the tap which goes to the ground. Wind eight more turns which will be the twentieth turn on the first tap for the grid switch. Wind seven more turns, make the second tap. Wind seven more turns, making the third tap. Wind three more turns, make the fifth tap. Wind three more turns, make the sixth tap, or the end of the outside coil. This end should

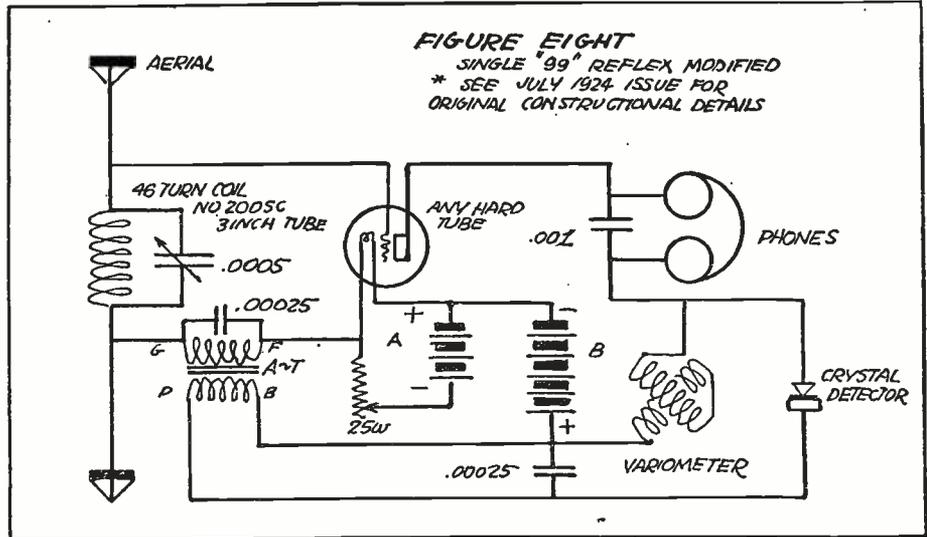

be the forty-third turn from the end of the grid starting coil.

The other parts are to be connected as shown in the hook-up of the June issue of RADIO AGE.

I also wish to call attention to the fact that the second or third stage radio frequency transformer cannot be used in this hook-up. It must be a first stage radio frequency trans-

former that the readers have confined themselves to a good magazine.

Thanking you to please publish the instructions of the coil in full detail so that all Reinartz fans will know how to construct it. If this is done correctly, according to my specifications, and according to the publication of your June issue, they will have a hook-up that will give remarkable results. I remain,

Yours very truly,
J. J. DREY.


Iron River, Mich.

Mr. Drey's procedure for winding the coil for this Reinartz circuit is illustrated in Figure 8.

P. Edward Chapman, of 805 North Preston Street, Philadelphia, Pa., is prompted by the article of the June issue Pick-ups Section on the Improved Superdyne, by M. C. Williams, to submit a few of the results he obtained with his four-tube "Selectdyne." Here they are; the hookup will be printed in our next issue.

Calls Heard By
P. E. Chapman,
805 N. Preston St.
Philadelphia, Pa.

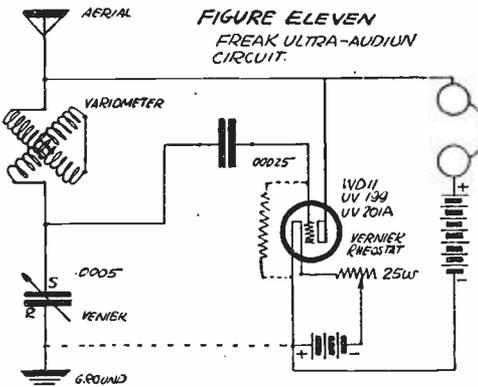WOR, WJZ, WEA, WJY, WDT,
WGI, WHAZ, WCAE, KDKA, WOC,
KYW, WDAP, WNAJ, WSB, KSD,
WGY, WRL, WRR, WFAA, WLW,
WAAD, WSAI, CKY, WGR, WWJ,
WOP, WRAX, WDAF, KFAW, WMAF,



former. I have had many requests for this information.

I did not realize that your RADIO AGE was so popular, but by the numerous letters the writer has received from practically every state in the union, requesting further information regarding the Reinartz hook-up, and from this fact it is evi-

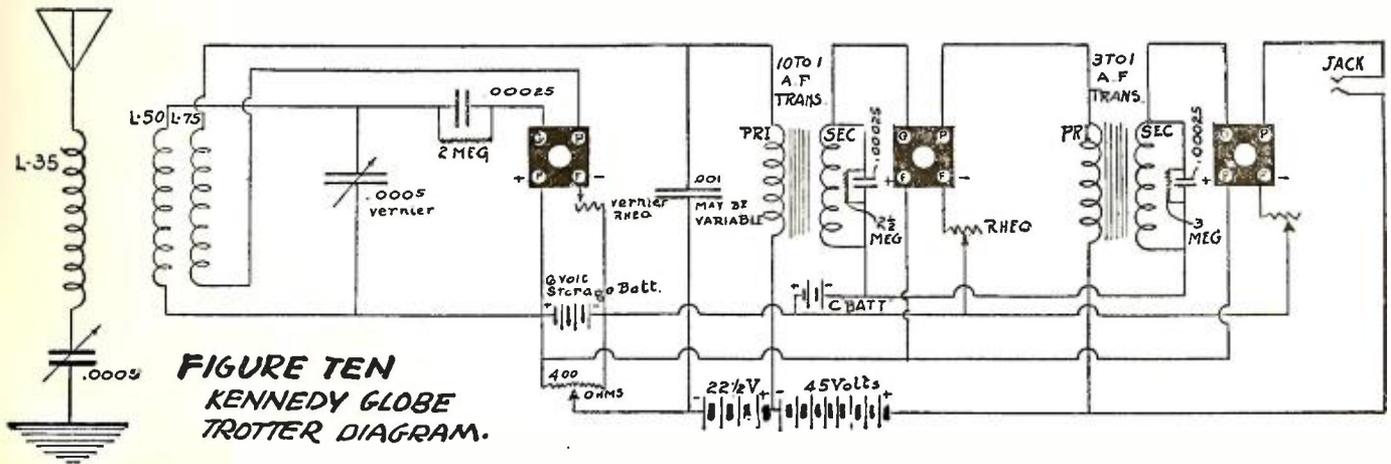


FIGURE TEN
KENNEDY GLOBE
TROTTER DIAGRAM.

WSAQ, WCAP, WRC, WCAW, WOAW, WPO, PWN, 6KW, WMAQ, WJAX, WTAM, WIAF, WBZ, WLAG, WBAB, KHJ, KDYO, KZK, KFIO, CFCA, WIAD, WCB, WEAH, KFAS, WSAL, WCAH, WBT, WILAS, WHAA, KFI, WCAT and verified receptions of 2ZY, Manchester, England, and 2LO London, England.

From England to California—that's some receiver if you think it over. And only four tubes, too! (At this point the owners of super-heterodynes will plug in another stage in the tooth gnashing-hair pulling act.) Some of the fellows who felt that the six tube affair of Mr. Williams printed in the June issue is just a trifle too large will without question seriously consider this little four tube "Selectdyne" of Mr. Chapman's. In the popular vernacular, it's what you would dub "the berries."

Two Dial Twisters have called our attention to the fact that in our diagram of the Kennedy "Globe Trotter" hook-up,

go on to the DX lists, we want to say that we are still open to suggestions, and more contributions. The Summer has run us a little short of our supply of available contributions for the first part of the Pickups Pages, so if you fellows want to read more of them, you've got to loosen up and let us hear from you.

The response to the Static Puncturing Contest was not as great as we would have expected it to be, but nevertheless when one considers that the idea of listening in through static is not one to be relished, we can hardly blame the boys. At any rate, here are the results for June and July.

First Prize List

RADIO AGE,
Gentlemen:

As I would like to enter your

mer time is a good list. Last Winter we used to make a fellow a Dial Twister for a list like that. So Ralph Mellon's name goes down on the subscription list for one year—FREE!

Second Prize—June

RADIO AGE,
Gentlemen:

Ever since reading about your Dial Twisters, I have had a desire to become one of them, so I looked over my log book to see if my list might entitle me to admittance. In the past three months I have heard the following (excepting all local) DX stations:

Calls Heard

WLW, WBZ, WGY, WHAZ, KHJ, PWN, WLAG, WDAF, WSB, WOS, WIP, WOAW, KFKX, KGO, WGR, KDKA, WEAH, WGI, WHB, WJZ, WSAL, WTAY, WOR.

I am using the old two-variometer-variocoupler hook-up, slightly modified as per the enclosed diagram. This change makes the set oscillate more freely and gives slightly more volume. (Editor's Note: The above list is not the prize winner; the one following did the trick).

Using this set on June 12th, from 9 to 10 p. m., I heard the following:

Calls Heard


KYW, KSD, WLS, KDKA, WTAS, WMC, WCB, WOC, WBAP, WDAF, WEBH, WQJ.

A curious thing was noticed about WOC. They were transmitting on two wave lengths; one their regular wave, and the other one right among the "hams." (A harmonic.)

I hope that this at least makes me a Dial Twister.

Yours truly,
RAY HAHN.

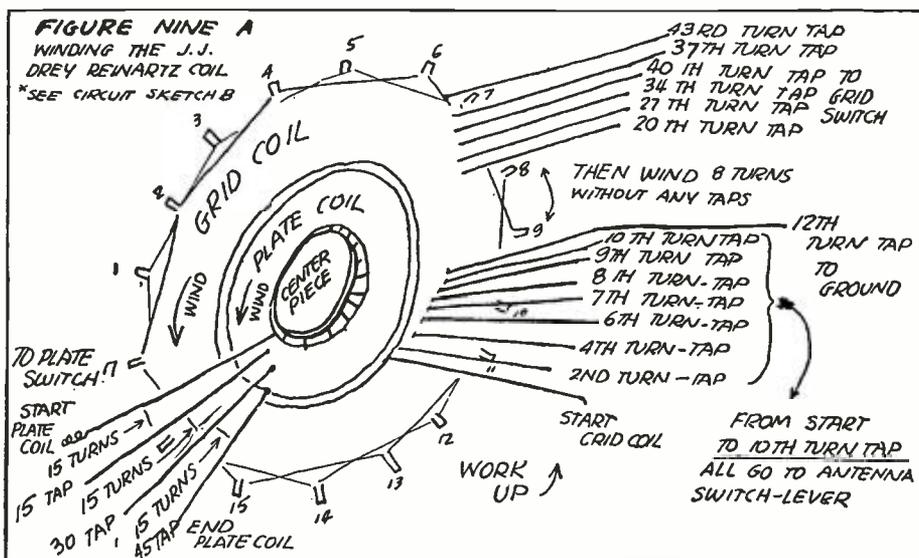1517 Chestnut St.,
Milwaukee, Wis.
(Continued on page 54)



published in our June, 1924, Troubleshooter Section, there are several inconsistencies which would confuse the average beginner. Louis A. Cass of Chicago, and T. J. Kennedy, the designer of the circuit, are the watchful bugs who are responsible for the corrected diagram shown in Figure 10.

A Prize Offer

We would like to mention the fact that the idea of giving a free copy of RADIO AGE to each fellow who points out an error in the Corrected List of United States, Canadian and Cuban Broadcasting Stations works out fine; so far we have had to give out only a few copies. But don't let that keep you from helping us to make that list just as up-to-date as possible.

Incidentally, does anyone happen to have a complete, reliable list of British and French broadcasting stations that they would like to have added to our regular monthly list?

September means the commencement of the DX season, and we are sure to have reports of more and more fellows hearing foreign broadcasting, so the list will be handy.

Before we leave the contributions and

"Static Puncturing Contest," I enclose the list of stations I have heard during the month of June. The receiver I used in getting this list was a single tube portable set, using a regenerative circuit. The list of stations is as follows:

Calls Heard


WTAR, KDKA, WBZ, WHN, WGY, WTAM, WFI, WEAH, WJZ, WRC, WOR, WCAP, WJY, WGN, WJAR, WBBR, WSAN, WTAT, WLW, WJP, WBAR, WOO, WCB, WHAZ, KFKX, WTAS, WDAF, WLS, WHAM, WPAB, WGR, WEAN, WANC, WSAL, CKAC, WEAP, WAAL, WSB, WJAX, KFNG, WCAE, WWAP, WBS, WJAS, WRAX, WCAU, WEAM, KQV, 2XR, 2XI, and WNAT.


I will leave it to you whether this is a good DX record or not. What little DX I do get, your magazine helps me to make it possible. Last Summer I did not read your magazine and the best I could do with a three tube set was WGY.

I think that speaks for itself.
Yours truly,
RALPH MELLON.

25 King St.,
Pottstown, Pa.

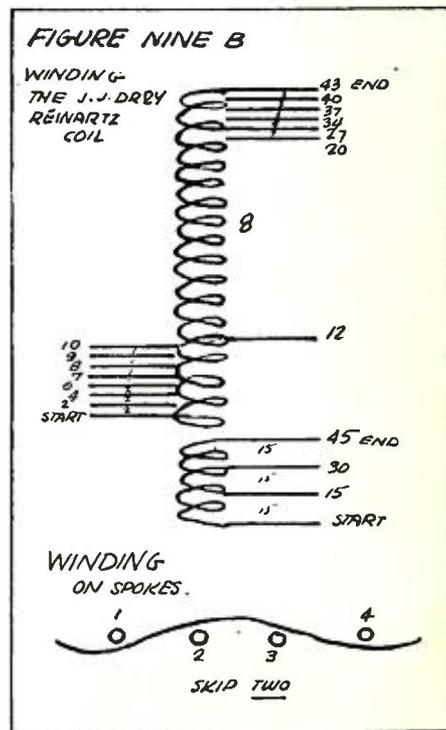Ralph is mighty modest about that list. Fifty-one stations in Sum-



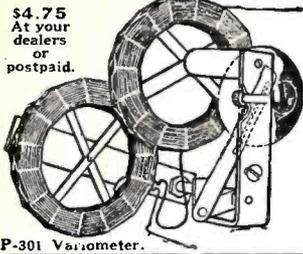

\$4.75
At your
dealers
or
postpaid.

P-301 Variometer.


With two 50-turn untapped coils as a variometer with PERFECT RATIO OF INDUCTANCE.

Other Pfanstiehl Pure Inductances.

	Turns	List Price	Wave Length
P-201	25	\$0.55	100-340
P-202	35	.59	125-470
P-203	50	.65	170-650
P-204	75	.74	220-960
P-205	100	.90	300-1300
P-206	150	1.10	470-1980
Pfanstiehl Ultra Audion			\$.95
Pfanstiehl Reinartz			1.75


\$6.00

At your
dealers
or
postpaid.

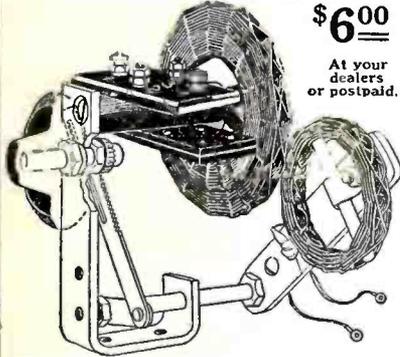

P-600 Oscillator for Superheterodyne. Oscillates sharply and steadily and improves the hook-up.

TRY THE NEW Pfanstiehl PURE INDUCTANCES

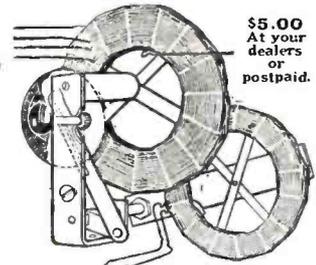

\$5.00
At your
dealers
or
postpaid.

P-300 Variocoupler.

Using this Unit in our Efficiency hook-up (furnished with Unit) a Wisconsin fan picked up Hawaii.

FOR LOW LOSS RECEIVERS

"Pfans:" You have been trying out all kinds of circuits. You know those you like best. Let us suggest that you now endeavor to improve these favorite circuits to their highest efficiency.

Much has been said recently about the necessity of good parts. Inductances are of extreme importance for efficiency. Pfanstiehl Pure Inductances are good because:

1. Air-cored means no absorption of signal strength;
2. Stagger-wound means no appreciable distributed capacity;
3. Vernier control of adjustment means distance-getting.

Manufactured by

Pfanstiehl Radio Co.

Highland Park, Ill.

Chicago Office: 1001 W. Washington Blvd.

(Haymarket 8010)

TOWER'S

TOWER'S Scientific
WEIGHS ONLY 80Z
Perfect Tone Mates

\$2.95
plus a few cents postage



Buy a Headset you'll be proud of

RADIO TOWER'S SCIENTIFIC HEADSETS
Money Back Guarantee

OUR \$200,000.00 COMPANY STANDS SQUARELY BACK OF EVERY HEADSET

WORLD'S GREATEST HEADSET VALUE

Longer Cord (full 5 feet). Stronger Magnets, Higher Resistance, Increase of Sensitivity, Perfect Tone Mates
EVERY SET TESTED BY LICENSED RADIO OPERATORS

Send no money - Order on a Post-Card

THE TOWER MFG. CO. : 98T BROOKLINE AVENUE, BOSTON, MASS.

Scientific

Trouble



Shooter

E. K., New London, Conn.

Question: I am constructing the four tube neutrodyne receiver as described in the RADIO AGE ANNUAL. May I use a 5:1 ratio transformer instead of a 4:1 with equal results? I am going to use UV199 tubes. If not, please name a good 4:1 transformer. What is the use of the C battery? Where should this C battery be connected? What is the correct voltage of such a battery when using about 75 volts on the plate?

Answer: You may use a 5:1 ratio audio frequency transformer without impairing the results of the set. The UV199 tubes are good for the circuit you are building. Use the 5:1 transformer you have on hand, and save yourself the price of another one of 4:1 ratio, which is not absolutely necessary. Don't forget that we cannot answer questions which relate to comparison of manufactured and advertised apparatus. It is the purpose of the C battery to place a strong negative charge of the grid of the

tube when excessive plate voltages are used. This lowers the drain on the battery and makes it last longer. The proper voltage of the C battery with UV199 tube 75 volts plate potential would be from three to four volts. The negative of the C battery is connected to the F post on the audio transformer (the grid return post), while the positive of the C battery is connected to the negative A battery.

C. P. J., St. Louis, Mo.

Question: I have a radio receiving set using the Reinartz hookup. I am not getting any results with respect to long distance stations. If I get any distant stations, there is a howl or whistle in the coil or tube all the time. If I put my hand near the dials or tuning switches, it makes the noise worse. Sometimes I can put my hand in a certain place and if I hold it there, I can tune the station in, but as soon as I move my hand it will start to whistle. I have a two-strand aerial about 30 feet long. I have the 23-plate condenser connected with the rotary

plates to the ground, and I have the 43-plate rotary plates to the aerial side. Have a .0005 MF condenser hooked between the grid and the coil and I am using a UV200 detector tube. I am not using any amplification at all. Could this be my trouble? If I use a crystal coil in series with the aerial to the tube set, I can get pretty good results. If I do not use this coil, there is a howling noise all the time. I get KSD loud enough to hear all over the room with the phones, without the crystal coil. The crystal coil just works good on long distance stations.

Answer: The howl or whistle can be due to several causes. First it may be due to improper tuning, inasmuch as the set may be oscillating at the time you are receiving, which is not correct. The set should be so adjusted that it is just at the spill-over point, which is just below the point of regeneration, where the maximum amplification effects are obtained without distortion. The second possibility lies in the grid leak. Make or buy one that is variable, and adjust it. I find that many of the sets now in use are hampered in not using a leak that is adjustable in some way or other. Noises are common from poorly adjusted grid leaks. The hand capacity you mention may be due to the fact that your grid and plate wiring comes too close to the panel or mounting board, and it would be a wise move to rewire the set, and keep the leads short and direct, at the same time running them high in the air and at right angles to other wiring. Your trouble might also be due to a set of poor variable condensers. Get yourself a set of the new low loss type of condenser which is now being sold everywhere, and you will note a difference in both tuning and results. Adjust the plate battery voltage carefully; to do this it is wise to use a potentiometer connected across the A battery, with the center arm connected to the negative B battery lead. The B battery in addition should be tapped. The crystal coil in the aerial circuit is an indication that your antenna is too short. Thirty feet is ideal for 150 to 200 meter reception, but not for 300 to 400 meter work. If you can't lengthen your antenna, add a few more turns (about 15 or 20) to the antenna coil (the one with the 10 single turns), which is connected to the switch and the 43-plate condenser, and about 10 more turns on the grid coil. A local station of any appreciable strength will break through the tuning of a receiver (especially if the condensers are poor), even though the set may be way off resonance, and for local reception tuning does not have to be so accurate.

Monumental Achievements

The New Bremer-Tully Low Loss Tuner



The New "Lifetime" Condenser

B-T Spaced series bank winding on coil frame of Bureau of Standards type, gives remarkable selectivity and volume.

Adjustable untuned primary solves the problem of adapting a tuner to the various types of antennae, circuit requirements, and local receiving conditions without taps.

Adjustable lubricated cone bearing.

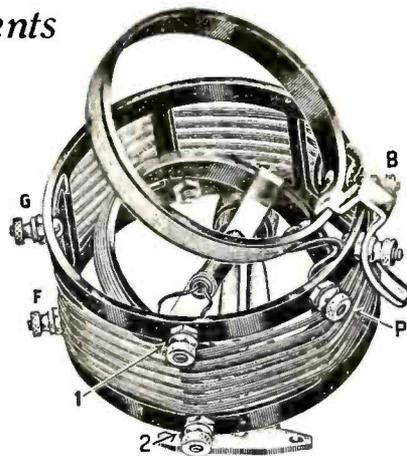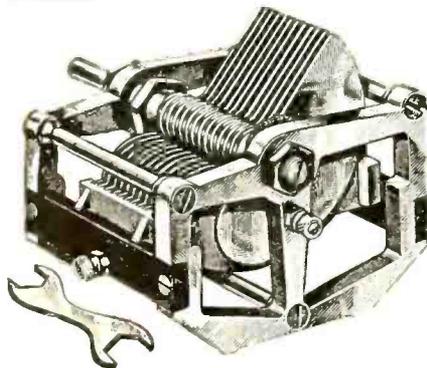Adaptable to any circuit requiring a tuner.



\$5.00

TWO TYPES

Short wave, 50 to 150 meters,
Broadcasting, 200 to 565 meters,
\$5.00

These ranges covered with B-T 11-plate "Lifetime Laboratory Condenser."

Bremer-Tully Laboratory Type Condenser at a commercial price.
Light Weight—Compact Size—Lowest Loss. This condenser is the only Low Loss straight line wave length condenser. Adjustable, lubricated bearings, pig-tail connections. It is Electrically perfect and Mechanically beyond comparison.

Write for "20 point" folder. It gives you the details.

"Better Tuning" (now in 6th Edition) tells you why and shows you how. Send ten cents for copy.

Bremer-Tully Mfg. Co., 532 S. Canal St., Chicago

The De Luxe NEUTRODYNE

BUILD THIS FAMOUS 5 TUBE KIT

Complete Quick Assembly Outfit of Synchronized Receiving Set to Reach From Coast to Coast With Amazing Selectivity and Clarity

WRITTEN Money-Back Guarantee. This is the amazing set selling by thousands all over America. No radio knowledge needed, no skill with tools, no experience. Every one instantly understands our extra complete instructions and simple, clear blueprint diagram. Just 2 or 3 hours fascinating fun builds your set. You can't go wrong. You get the big broadcasting stations. Extraordinary long distance from Coast to Coast is easy. Only the best in this set—ALL genuine STANDARD NEUTRODYNE parts LICENSED under the original HAZELTINE patents and guaranteed to give perfect results and satisfaction. Also all parts are MATCHED for beautiful appearance. The front is the handsomest ever made, reproducing fine mahogany, with every marking engraved in GOLD. A magnificent ornament. A perfect, highest grade, efficient, powerful instrument that you cannot duplicate for THREE TIMES THE PRICE.

WHAT THIS GENUINE STANDARD SET CONSISTS OF—

1 Drilled Radion Mahogany Panel, like mahogany, engraved in gold; 3 4-inch Radion Mahogany Dials, gold engraved; 2 gold-plated Jacks; 3 genuine Hazeltine Neutroformers mounted on the famous Comsco Bakelite End Condensers (positively the only Neutrodyne Kit including these famous Comsco Condensers); 2 Hazeltine Neutrodons; 5 Bakelite Sockets; 1 6-ohm Rheostat and 1 30-ohm Rheostat with gold-plated knobs to match panel; 2 genuine Killark completely shielded Audio Transformers; 1 Baseboard; 20 feet Tinned Bus-Bar; 1 .00025 Freshman Grid Condenser; 1 Tubular Glass Grid Leak; 1 Set Engraved Bindings Posts; 1 .002 Micon Condenser; 1 .006 Micon Condenser; Exact Size Special Panel; Instructions and Blue Print, all packed in large handsome partitioned box, \$34.49 complete.

ACCESSORIES TO PUT SET IN OPERATION

Everything needed to operate set after building—5 Tested Tubes (Type 201A), \$19.50; 2 45-volt extra large Variable "B" Batteries for Neutrodyne, \$6.50; 1 60-ampere Hour Storage Battery (guaranteed 2 years), \$11.25; 1 pair 3,000-ohm Phones, \$3.75; Double Plug, 90c; 1 Antenna Equipment, \$1.50; COMPLETE OUTFIT, \$43.40. (Accessories also sold separately.) If you order Building Outfit and Operating Outfit both together we will include fine Mahogany Finish.

CABINET FREE

SEND NO MONEY. We ship C. O. D. Pay your postman. Then build and enjoy your set under our WRITTEN Money-Back Guarantee sent with equipment. We acknowledge all orders by return mail. Ship same or following day. We answer every letter we get on same day. The Radio Shack are the largest Radio Dealers in America. No inferior goods. Only the best and most reliable. You buy in safety. Send your C. O. D. order today. This present low price cannot continue. Act NOW. Circular FREE, with Broadcast List and Map.

THE RADIO SHACK

Dept. RA9, 55 Vesey Street, New York, N. Y.


GENUINE, STANDARD, SYNCHRONIZED LICENSED HAZELTINE

WRITTEN MONEY-BACK GUARANTEE

SEND NO MONEY WE SHIP C. O. D.

\$34⁴⁹

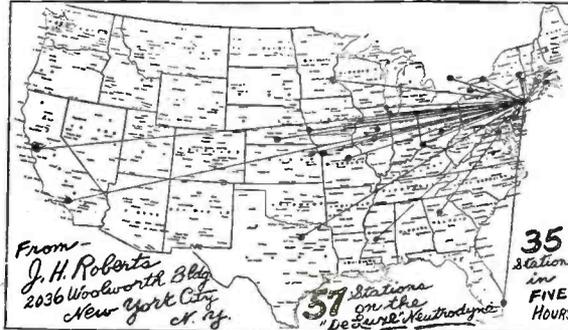Read These Letters From Enthusiastic Fans



LOOK AT THIS MAP SENT IN

"From Clawson, Michigan, I get from Coast to Coast on my horn, including HONOLULU, HAWAII, on the night of March 21, at 2:05 A. M."
—Dale Jenkins, Clawson, Mich.

"I congratulate you on giving the radio fans these wonderful bargains."
—A. J. Toll, 742 Nelson St., London, Ont., Can.

"I would have had to pay three times your price out here for the same parts I bought so low from you."
—Stephen Vandrey, 529 16th Ave. N., Nampa, Idaho.

"Enclosed find map I made for you in appreciation of your De Luxe Neutrodyne. This map shows results I obtained on Thursday evening, March 27, 1924—a total of 35 stations from Canada to Texas and Florida, and from Massachusetts to California, all in 5 hours—as far north as Toronto, and south to Miami and Dallas. To date I have listened to a grand total of 57 stations—8 in New York; 4 in Newark; 3 in Chicago and Philadelphia; 2 in Pittsburgh, Davenport, Hastings, Kansas City, Providence, Omaha, Cincinnati and Los Angeles; and 1 each in Columbus, Toronto, Washington, Zion City, Plainfield, Schenectady, Rochester, Topeka, Jackson, Minneapolis, Lockport, Boston, Dallas, Jefferson City, Urbana, Mattapoisett, Tarrytown, Elgin, Oak Park, Cleveland, Atlanta, Oakland and Miami."
—J. H. Roberts, 2036 Woolworth Bldg., New York City.

(These are from hundreds of letters constantly coming in with high praise.)



KGO, OAKLAND, CAL., RECEIVED IN SUMMERTIME!

2,090 Miles From Cleveland, Ohio

2,620 Miles From New York, N. Y.

WITH A KENNEDY TUNER

Per Unsolicited Testimonials

I am so greatly interested in your TUNER and the RESULTS I AM GETTING THIS POOR RECEIVING WEATHER that I just must write you. I am glad my veracity seems to be in pretty good standing here; otherwise your TUNER sure would make me out a prevaricator. KGO FOUR TIMES WITHIN EIGHT DAYS not so bad, eh? This morning about 12:30 on LOUD SPEAKER WITH WSAI GOING JUST THREE METERS AWAY.

YOUR TUNER sure is creating interest among my friends, as of late I seem to be the only one who has had real DX. Even my friends who are using SUPER SETS have not pulled CALIFORNIA in for weeks, let alone those using other units. I wish to remain,

Very sincerely yours,
E. R. ANDREWS, Attorney at Law,
304 Ulmer Bldg., Cleveland, Ohio.

I am getting such WONDERFUL results WITH YOUR KENNEDY TUNER that I must let you in on what I received the past seven days. KGO, Oakland, CALIFORNIA THREE NIGHTS OUT OF SEVEN! Wishing you all the success in the world with your tuner. I remain, a WD12 ONE TUBE DX GETTER.

VINCENT T. KENNEY,
124 W. 96th St., New York City.

July 30, 1924.

July 31, 1924.

DX FANS! If you want real results, get a KENNEDY TUNER AND HAVE THE WHOLE U. S. A. AT YOUR FINGERTIPS.

Only one dial to get stations and the other to increase or decrease volume. Kennedy Tuner is used in place of variocoupler, variometer and honeycomb coils, saving the cost of over \$9.00 worth of unnecessary junk that is in most receiving sets, and no dead end losses.

KENNEDY TUNER
\$5.00
INCLUDING GLOBE
TROTTER DIAGRAM

Send for Free Diagram
T. J. KENNEDY
Radio Globe Trotter
1360 University Ave.,
New York, N. Y.

GUARANTEE:
If not satisfied after
30 days, we will cheer-
fully return your money.

The Traffic Cop of the Air

FERBEND Wave Trap

Add a Ferbend Wave Trap to your set and "Police" your reception. Regulate the Traffic Guaranteed to tune out any interfering station. Sent postpaid on receipt of \$8.50, or C. O. D. plus postage.

Send for free booklet, Ferbend Electric Co., 16 E. South Water St., Chicago

HUDSON-ROSS

Sells only nationally advertised radio apparatus.

Send for discounts.

123 W. Madison St. Chicago

YOUR SUBSCRIPTION

—should be renewed as soon as it expires, so you won't miss a single issue of RADIO AGE. Order your October copy in advance if you buy from a news-stand, or you may miss a number full of technical and feature articles on up-to-date radio. Another batch of attractive and instructive blueprints in October RADIO AGE. Watch for it.

**VACUUM TUBES (JJ-9-26)
OPERATING CHARACTERISTICS**

BIASED AUDIO FREQUENCY AMPLIFICATION. High vacuum tubes used for audio amplification circuits should always be given a negative bias when the plate voltage of these tubes exceeds 45 volts, and even at 45 volts a saving is shown in the plate current and hence in the life of the "B" batteries. Greater amplification, greater freedom from distortion and a smaller demand on the "B" batteries are obtained by proper biasing voltages on the grids of the tubes.

Biasing the audio stage tubes is generally performed by placing a "C" battery in the grid line or return grid line with the negative post of the battery next to the grid post (G) of the socket. Potentiometers are seldom used because of the comparatively high plate voltages used with the amplifying tubes. As the "C" batteries supply only a very small amount of current during the operation of the set, and are automatically placed on an open circuit when the tubes are turned out, a small flash-light battery will last a long time on this service without the necessity of switches or special attention. The small special "C" batteries now on the market are excellent for this purpose, and after installing will last for more than a year without replacement or attention.

Fig. 1 on the adjacent data sheet shows the biasing battery "C" in the grid line of a single stage audio circuit. It will be seen that the negative of the "C" battery is placed toward the grid, and in addition to the negative pole of the "A" battery maintains a negative potential on the tube. That is all the secondary in circuit (SEC) of the audio frequency transformer (AT).

Fig. 2 shows the same effect obtained by placing the biasing battery in the grid return line, but it is likely that this is not so effective as the direct connected battery shown in Fig. 1. While the current drawn from the battery is so small that there cannot be much resistance loss, due to the resistance of the secondary winding of the transformer, yet there is an impedance loss which is likely to pull down the voltage slightly on extremely loud signals, and which would therefore tend to reduce the bias at the time when biasing was most needed. However, this system works very well and is used extensively.

Fig. 3 shows a two stage audio amplifying circuit in which a single "C" battery biases the grids of both tubes by a connection of the negative of the "C" battery to the secondaries of both transformers. The battery is therefore in the grid lines. The same results could of course be obtained by the use of two "C" batteries, one battery being placed directly in the grid line of each tube as in Fig. 1. The system outlined in Fig. 3, however, saves one battery and simplifies construction. The audio frequency transformers are shown at (AT-1) and (AT-2). Two "B" batteries (B1-B2) give minimum distortion but only (B1) need be used.

At voltages of approximately 40, biasing has not much effect on reducing distortion, nor does it noticeably increase the volume. It does, however, reduce the demand for current on the "B" batteries and in this way prolongs the life of the "B" batteries. At about 60 volts, the effect of biasing becomes very noticeable with a considerable increase in volume and less distortion when the tubes are being pushed hard. At 90 volts the volume depends very greatly upon the degree of bias and the proper bias voltage eliminates the mush and distortion that would otherwise be present without the "C" battery.

The biasing voltage must be increased as the plate voltage is increased. The proper biasing voltage varies with different tubes, and is given in the tables in the next data sheet.

**VACUUM TUBES (JJ-9-25)
OPERATING CHARACTERISTICS**

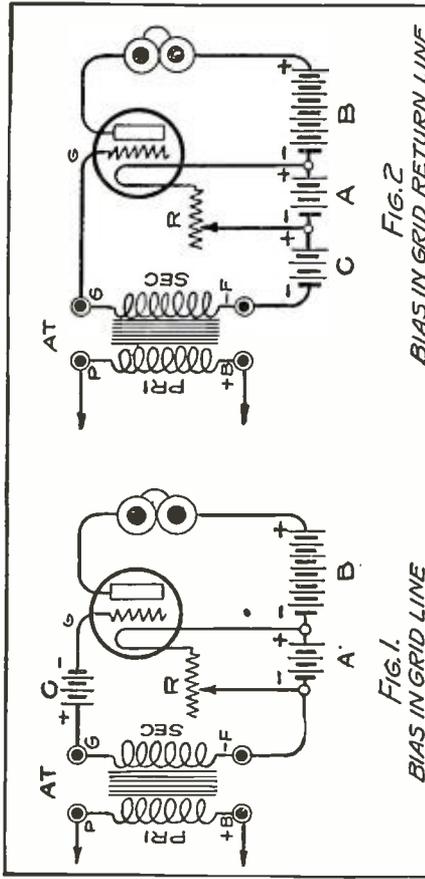


FIG. 1.
BIAS IN GRID LINE

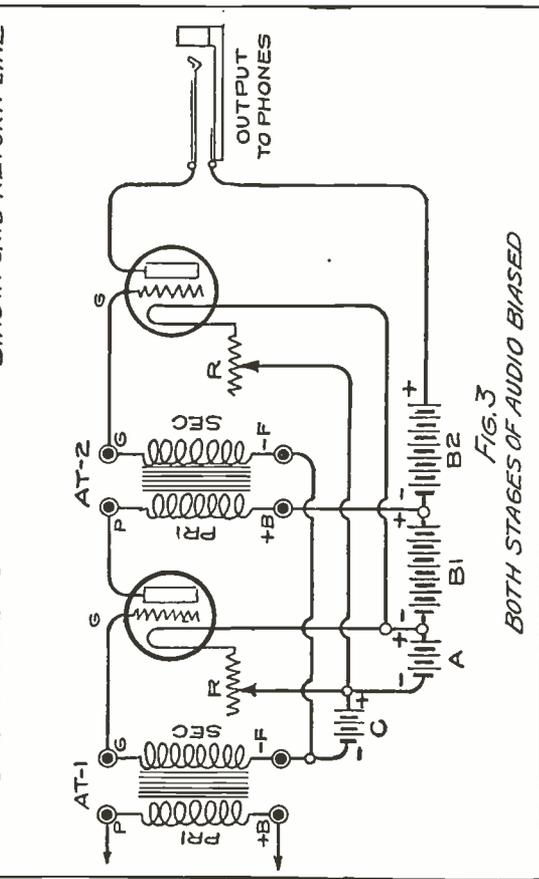


FIG. 2
BIAS IN GRID RETURN LINE

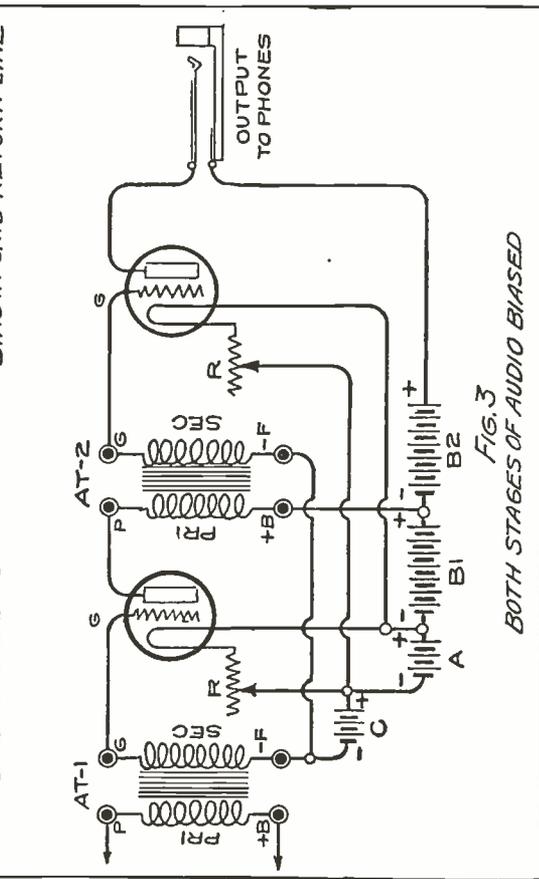


FIG. 3
BOTH STAGES OF AUDIO BIASED

Reminiscences of an Old Operator

(Continued from page 22)

at something above fifteen hundred and we positively did not get over it for weeks. The sound of that marvelous Fessenden synchronous rotary, with its pure soft whistle, will live with me forever.

And then—Shep went to sea. Which marked the turning of my footsteps toward the commercial game, and, incidentally, nearly marked the head of my grave with the usual inscription. It happened like this:


Shep, being away on the ships, had commissioned me to dismantle his set, for which I was to receive most of the equipment. The ten-wire flat top had been replaced by an enormous two-wire triangle extending along two sides of a city block and diagonally from one corner to the other, this last side being about 500 feet long.

In taking this long stretch down, I was standing on a tin roof, grounded through the rain spout, heaving away on these two long strands when they swung low onto some old 4,600-volt power lines in the alley on which the insulation was hanging in shreds. There was a tremendous report and a great flash and I found myself sitting on the roof with the ends of the wires dangling over the roof—absolutely untouched and without having felt a slightest tingle.

Very quietly I sat while the neighbors returned, one by one, indoors, figuring how in Sam Hill I was still there, absolutely as green and uncooked as if I had not just a moment before shorted, or grounded, or in some way run counter to a lot of volts on the wrong side of the transformer. Cautiously investigating, picking up a couple of handfuls of perfectly rounded copper marbles in the alley under the power lines, where some six feet of aerial wire had been melted, I found a perfectly satisfactory explanation. It was a nicely fused ground switch from which I had "neglected" to disconnect the lead before trying to pull the wires over to my roof. That was all—but that was enough.

My amateur days overlap into my commercial with my first trip to "BX" station and my adoption by Dave Heilig as one of the men "posting up" for a ship job. But more of that in the next issue, if the good editor will let my sigs get through.

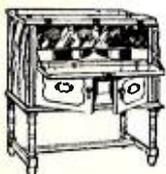(In an early issue of RADIO AGE Mr. Lynch will write on "My Initiation Into the Commercial Game," in which he experiences some hazardous adventures while serving as operator on the S. S. Seminole to Haiti. Watch for it.)



CABINETS

If you are interested in a radio cabinet in which is combined both beauty and practicability, just write

LAKESIDE SUPPLY CO.,
Dept. R
73 West Van Buren St.
CHICAGO, ILL.
Telephone, Harrison 3840



Write for your free copy of

Ward's Radio Catalogue



A Valuable 68-Page Reference Book on Radio—a Market Place for the Best in Sets and Parts

We want you to have a copy of Ward's new Radio Catalogue. You will find it to be an encyclopedia of information on Radio, the liveliest topic of the day. It contains a new Radio map—diagrams of the best hook-ups—descriptions of complete sets, and standard parts for building sets.

Headquarters for Radio

Montgomery Ward offers you all types

Montgomery Ward & Co.

The Oldest Mail Order House is Today the Most Progressive

Chicago Kansas City St. Paul Portland, Ore. Oakland, Cal. Ft. Worth

of Radio Equipment at a saving. We sell direct to you only merchandise of highest quality. Everything you buy from us, carries our 52-year-old guarantee—"Your money back if you are not satisfied."

Enjoy the Long Winter Evenings

Every form of entertainment can be brought into your home by Radio. Keep in touch with the world—Sports—Election Returns—Dance Music—Speeches—Sermons—Current Events—you can enjoy them all by Radio.

Write today for your copy of this complete Radio Catalogue. Address our house nearest you: Dept. 43-R



SPIDERWEB COILS

Use low loss inductance coated with Waterproof Anti-Capacity Cement, Rubber Plugs for mountings, all types wound to specifications. No order too small or too large, quantity production solicited. Send BLUE PRINTS for quotations. Try a set of our Spiderweb Air Core Harkness Coils, list \$2.00. Special prices to Dealers and Jobbers.

Make Money

as a

RADIO

Demonstrator

Big Opportunity now to everyone who knows how to set up and operate a radio set—also to take orders on a price and term basis more favorable than regular dealers can offer. Your chance to get into the Radio business. Own a set or not, as you choose. Give all or part time to this work.

Write at Once

Give us this information: Age; Business; Do you own a Radio Set?; What kind?; How much time do you want to spend in this work?

Marshall Radio Products, Inc.
Marshall Blvd. & 19th St., Dept. 98-96 Chicago, Ill.

HUDSON-ROSS

Largest exclusive Radio Jobbers in middle West.

Write for discounts.

123 W. Madison St. Chicago

600 MILE RADIO SETS \$4.95
Notubes or batteries. Copyrighted construction plans \$1.00
Satisfied customers everywhere.
Particulars free.
LEON LAMBERT
642 Kaufman Bldg., Wichita, Kansas

BUYERS' AND SELLERS' SERVICE SHEETS

TUBE SOCKETS No. 3-A-24

1. **Spring Contacts.** Design:—Double contact springs or the new "side swipe" springs are desirable, since single contact springs are apt to bend out of contact and stay bent. Note that springs are so designed and fastened that they will not work loose.

Material:—Phosphor bronze, not too thin, is the best material, and gives longest life. It should be punched with the grain lengthwise with the spring not cross-wise, or the springiness will be diminished.

German silver is more apt to bend out of contact, and its resistance is higher. Test the springs by plucking them to ascertain that the material is springy and strong.

2. **Insulation.** **Material:**—Bakelite, hard rubber or porcelain. The latter when thoroughly glazed has low specific inductive capacity and high insulating qualities, but cannot be so well designed, and is more easily broken.

Soft compositions called "moulded mud" and used in cheap sockets, are partial conductors and to a large degree short-circuit signals to be detected or amplified. Such material is easily cut with a knife. Felt, and fibre are apt to gather moisture and are not first choice.

3. **Connections.** Design:—Lugs for soldering are desirable since contact must be perfect. If you are going to solder, be sure the insulation is good and will not soften under heat, as melting is not only unsightly but metal parts may be disarranged and open-circuited.

4. **Cleanliness.** Do not accept socket which has dirt, pencil marks or grease on the base.

5. **Shock-absorbers.** Design:—For tubes which are microphonic, such as U. V. 199 and C. 209, supports made from strips of rubber or a cushion of sponge rubber are desirable. Some cushioned tubes are fastened to the base by a screw through the socket. Such a method of connection does away with the effect of the cushion.

6. **Finish.** Style:—Metal posts should be nickle-plated and polished in order that they may not tarnish.

7. **Socket must be so designed** that there is no possibility of the tube prongs touching any of the springs unless the guide pin on the tube base is in the corresponding slot on the socket. Some sockets are so made that when the tube is put into the socket and rotated until the guide pin drops into the socket, the prongs will often make contact so that B-battery will burn out the filament.



BUYERS' AND SELLERS' SERVICE SHEETS

JACKS No. 4-A-24

1. **Springs.** **Material:**—Phosphor bronze or German silver. Former has lower resistance and greater elasticity; latter matches other metal parts and its appearance may be preferred.

Length:—Longer the better to insure long life, constant tension; short springs crystallize and break. **Thickness:** Heavy springs preferred for long life and to eliminate complication of booster springs. **Design:** If tip or short spring is placed next to frame with an insulation between spring and frame, plug may sometimes cause spring to touch frame and short circuit, especially after thimble wears a little.

2. **Terminals.** Design:—For convenience in soldering spread lugs preferred, and should be well tinned; to accommodate wires, holes of sufficient wire up to No. 12 B. & S., or whatever is to be used, needed for security and neatness in soldering.

3. **Contacts.** **Material:**—Pure silver will not oxidize, turn black or corrode, and therefore insures a clean and satisfactory contact; be sure contact points are clean.


4. **Insulation.** **Material:**—Such special composites as Bakelite, Formica, or Micarta preferred, since these do not expand, contract, or absorb moisture. Design:—Insulation if attached to springs prevents slipping of springs from one side of frame to the other. An insulating sleeve or tube should extend for the full length of the screws which pass through the ends of the springs when held by lock washers; the screws are more secure.

5. **Frame.** **Material:**—Brass or heavy iron, nickel-plated; may be polished (there is little to be said in favor of an argument sometimes advanced that iron frame may become magnetized except that in certain positions iron may encourage flow of stray lines of force). Design:—Straight or tapered; width of latter type is such that greatest strength of frame is located where greatest strain occurs, at the bend; also bent frame eliminates insulation stack-up between frame and springs and makes for more solid mounting for the springs. Straight jacks may be turned upside down and make mounting for a subpanel. Special mounting screws and washers for tapered jacks make same thing possible with them; also this type permits wires to be run beneath it.

6. **Jack Thimble.** Design:—To compensate for varying panel thicknesses washers are supplied; stationary thimble riveted to frame with adjustable lock-nut preferred, since this insures against incorrect mounting and makes for plug entering correct distance and consequent wood connection. If plug enters too far, it may reach cut-off springs; if not far enough, may rest on insulator of plug. Size:—Test with plug if possible; standard diameter is 1/4 inch; some jacks and plugs are made oversized; a loose plug may fail to lift springs high enough to make contact in a filament control jack; or it may short-circuit against a misshaped frame; therefore be sure to make test, at least, before making radio assembly. Heavy thimble preferred to light one because threaded part may be twisted off.

7. **Capacity.** The capacity of standard jacks is negligible as compared with the capacity of the two lead wires to the phones or loud-speaker, and moreover you generally use a condenser across the phones anyway. On a few circuits using very short waves, a so-called low-capacity jack may be needed.

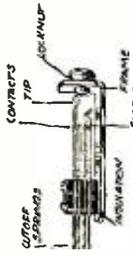8. **Soldering.** Beware of a jack with soldering flux on it. Most soldering fluxes are corrosive and contain zinc chloride, a conductor of electricity which will short-circuit the jack.



Unsnarling Vacuum Tube Connections Every Question

(Continued from page 18)

problem to cope with: namely, the filament and plate batteries. Not infrequently we receive questions asking how long a battery will last with a certain tube. It is impossible to answer this; unless one knows how long you listen, an accurate record of the current used and the tube or number of tubes used.

About the best answer I can give to a question like that is to say that to obtain the greatest life and efficiency with dry cells, never let the drain per cell exceed one-quarter ampere, and it is decidedly wiser to connect batteries in series parallel so that the current rate of discharge is in the neighborhood of one-eighth ampere. Have a voltmeter handy, and never discard the cell until it falls below 1.0 volt.

A standard 6-inch, 1½-volt cell used for two hours per day at a discharge rate of six hundredths of an ampere will last a good deal more than 300 hours. At a discharge rate of one-eighth ampere, under the same conditions, it will last somewhat over 200 hours; at .18 of an ampere discharge, the cell will last about 125 hours, and with a quarter ampere discharge rate, under the conditions as above mentioned, it has a life in hours of about 100 or slightly more. This also assumes that the battery is useless after the voltage has fallen to 1.0.

Knowing the amount of current it takes to operate your tube, and knowing the voltage, it is a comparatively easy matter to figure out from the above scale the number of batteries you will need.

Tapped B batteries are always advis-

able, especially in detector circuits. I have found that many times I could bring in five or six stations which I had never heard before by simply varying the plate battery voltage of the detector tube. It is decidedly wise to run up and down the scale of these taps in the course of long distance listening, for I am sure that you will discover its worth.


In conclusion, I would like to bring up the subject of poor tubes. Not infrequently do I run on to these "duds," and if I find a circuit properly connected and not giving the best results or none at all, I immediately suspect a "dud" tube. The only real way to determine this is to substitute it for one that you know is good.

In adjusting any receiver, it is a good plan if more than one tube is used to try changing the tubes around in the sockets, as often it will be found that a tube will work more effectively in one socket than in another.

Editor's Note: This is the second and last article on vacuum tube efficiency. The first part dealing with the choice of apparatus was published in the July issue of RADIO AGE, which is available at the customary price of 30 cents in stamps. Brainard Foote gave a discussion of detector tubes with grid bias battery, in the July issue. Further information on vacuum tube efficiency appears in the DATA SHEETS of the months of June and July. Readers who have not read these articles, on operating efficiency, should, by all means do so.

ANSWERED for only \$1

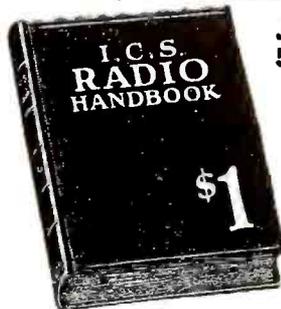At last you have under one cover a Complete Radio Handbook



JUST OUT 514 PAGES

Compiled by HARRY F. DART, E.E.

Formerly with the Western Electric Co., and U. S. Army Instructor of Radio. Technically edited by F. H. Doane.

No more need you turn from book to book, hoping to find what you want. It is all here, in 514 pages crammed full of every possible radio detail. Written in plain language, by engineers for laymen. Clears up the mysteries, tells you what you want to know. A complete index puts everything within your reach in a few seconds.

IT EXPLAINS: Electrical terms and circuits, antennas, batteries, generators and motors, electron (vacuum) tubes, every receiving hook-up, radio and audio frequency amplification, broadcast and commercial transmitters and receivers, super-regeneration, codes, license rules. Many other features.

Under one cover. Yes, it is all in one volume of 514 pages of clear type with hundreds of diagrams and illustrations. Takes the place of eleven or more specialized texts, each costing from two to ten times the dollar you pay for this single book. Belongs in every radio-equipped home, on every amateur's table.

Send \$1 to-day and get this 514-page I. C. S. Radio Handbook—the biggest value in radio to-day. Money back if not satisfied.

TEAR OUT HERE


INTERNATIONAL CORRESPONDENCE SCHOOLS
Box 8783-B Scranton, Penna.

I enclose One Dollar. Please send me—post-paid—the 514-page I. C. S. Radio Handbook. It is understood that if I am not entirely satisfied I may return this book within five days and you will refund my money.

Name.....
Address.....

AUDIO AMPLIFIER CIRCUIT FOR ANY DETECTOR OUTPUT

FIG 8

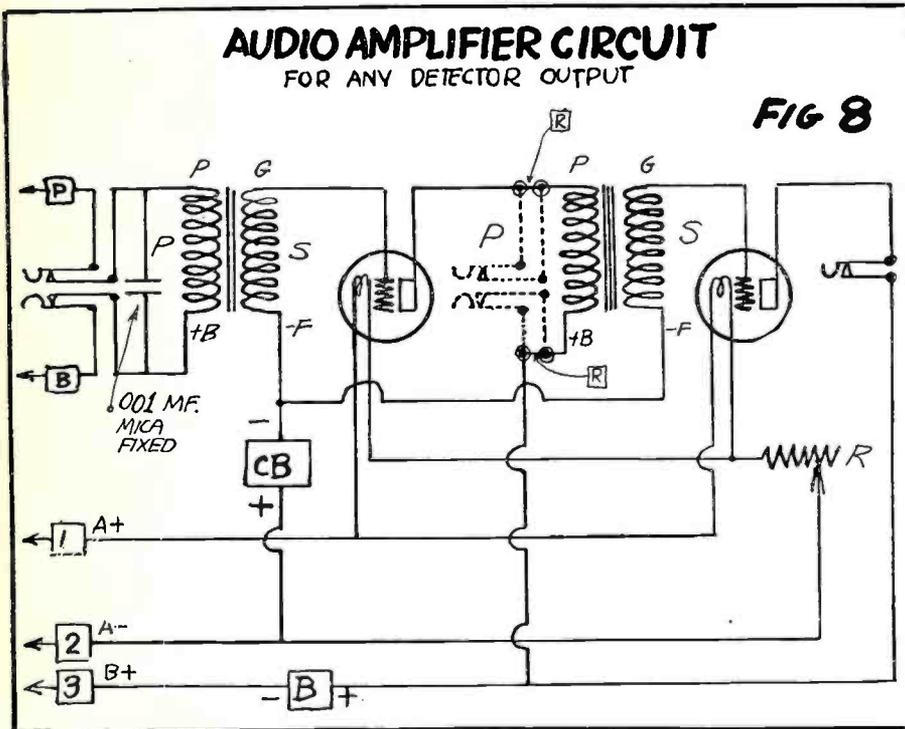

“Reminiscences of an Old Operator,” the True Story of an Amateur’s Early Struggles, Begins in This Issue.

ASK US!

Don't waste money trying this, that and something else in an effort to get the results you want. We know radio conditions in every section of the U. S. and Canada. Tell us the results you want and we will tell you the receiver to buy or build that will get you those results. We also furnish plans, instructions, precautions, etc. You get impartial advice from us, as we are not interested in the sale of any kind of equipment. Send stamped, self-addressed envelope for questionnaire and particulars. No obligation.

KUSTER & PHELPS,
Radio Counsellors and Technicians.
646 N. Michigan Blvd., Suite 325, Chicago

WITH THE MANUFACTURERS



Deresnadyne Receivers Give Clear Tones

The Deresnadyne Receiver introduces a new principle in radio reception, which seems to possess decided possibilities. It is the invention of E. A. Beane and E. F. Andrews of Chicago. The circuit itself is similar to that of standard tuned radio frequency hookups, differing in the omission of certain parts heretofore considered necessary and in the proportioning and placing of the parts. Its performance is different from previous types. Its most impressive feature is its clear reproduction. This tone quality is, however, attained without the slightest sacrifice of volume or distance. On these points, the Deresnadyne is easily the equal of the best present-day receivers. It is extremely selective, tuning sharply enough to eliminate any ordinary interference, even in congested areas, and at the same time avoiding the critical sharpness which makes tuning difficult. Another feature is its freedom from undesired oscillations that produce whistling and distortion. No setting of the controls will cause the set to whistle. Tuning is still further simplified by the fact that each station will always be found at a particular setting of the dials and can be logged.


Liberty Electric Corp. Moves

The Liberty Electric Corporation moved recently to a new factory at Stamford, Conn. The factory is of the modern type, with more than 35,000 square feet of floor space to accommodate the need for increased manufacturing facilities.

The principal Liberty product is the Liberty Super-Heterodyne Kit No. R-40. Liberty intermediate wave transformers have been especially designed for perfection with super-het reception. These transformers are shielded to prevent interstage couplings and may be placed close together. Liberty units are also known for their selec-


The Bradleyleak

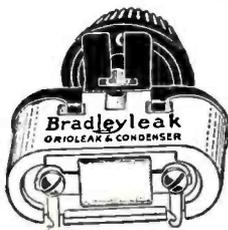The Bradleyleak, manufactured by the Allen-Bradley Company of Milwaukee, Wis., is one of the very finest type of variable grid leaks on the market.



The accompanying cuts illustrate its appearance, which is very much like the familiar Bradleyleak filament control. The leak is variable continuously from about one-quarter to ten megohms of resistance, and can be used with any type of tube now on the market with perfect satisfaction.

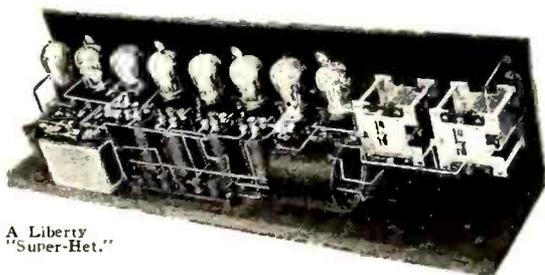A special provision is made for the grid condenser connections, in the form of a sunken bed in the porcelain itself to accommodate the small size fixed condensers now in vogue. Screws are provided for the mounting of this condenser and short grid leads are effected by its use.



tivity. Three stations operating on 455, 462 and 469 meters—one of them a 1,000-watt station near by—were completely separated with Liberty units. The Liberty super-het kit comes complete.

New Electrad Products

Several new and improved radio products have been placed on the market recently by Electrad, Inc., New York City.

Among them are the Electric Certified Grid Leak, which is accurately calibrated and fixed, having permanent resistance; the Electrad "Hydrogrounds," made in the temporary drive type for campers; disc permanent type, and drive type—permanent. The hydroscopic element in the Hydroground has an affinity for moisture and holds it permanently in suspension.

Other new Electrad products include lightning arresters, indoor and outdoor types; vernier dial; lamp socket antenna, Electrad Diode tube, grid leak mountings, resistance coupled amplifier kits, etc.

Reichmann Designs "Thorola"

Frank Reichmann, inventor of the thortite horn and the thorphone loud speaker, has just designed a new reproducing unit known as the Thorola, which is being manufactured by the Reichmann Company of Chicago.

"The Thorola has proven its superiority in direct competition with other amplifying and reproducing devices in the \$25 class," says Mr. Reichmann. "It reproduces the highest violin notes and the lowest drum beats without distortion and with great volume."

This design uses for the first time the push and pull principle with a permanent adjustment. The horn is one piece thortite and cannot be thrown into resonance with any audible sound wave frequency.

Franklin a Freshman Stockholder

Albert W. Franklin, chief engineer of the Charles Freshman Co., manufacturers of radio apparatus, of New York City, has just been made a stockholder in the concern.

Mr. Franklin is the inventor of the Freshman Variable Grid Leak and many other popular radio items.

Marshall-stat for All Tubes

The Marshall-stat, known as the "Universal Rheostat," is a smooth accurate-adjustment rheostat. Specially treated Marshall resistance discs enable the operator to obtain any resistance down to the finest vernier adjustment for any tube or combination of tubes. Breakage impossible. Only one hole required in panel.



The New Liberty Electric Corp. Factory at Stamford, Conn.

A One-Control "Go Getter"

(Continued from page 19)

builder may have to be governed somewhat by the plate condenser used. I find that different makes of condensers of the same rated capacity actually gives varying results, calling for from 48 to 55 turns. Therefore, while I give 48 turns as standard (and this will usually be satisfactory), the builder may find that it will be best to wind on about 55 turns at first, and then remove one or two turns at a time, if necessary, until the correct number for the condenser being used is found. This is easily done without disturbing the coils or any other part of the completed set. To get correct dial reading and number of turns, select, say, a 360-meter station. When this station tunes in at approximately 30 on the dial, you have the right number of turns on your secondary, and will then be able to cover all the broadcast wave lengths.

Get Correct Spacing

COIL "A," the primary, consists of six turns of No. 18 DCC wire. Coil "B," the secondary, has 48 turns (see suggestion above) of No. 22 DCC. Be sure to wind the wire on both coils in the same direction, and leave the ends of the wire of sufficient length to make your connections. For winding these coils use the wooden type of spider web form, with a center approximately 2½ inches in diameter. This type has thin round spokes, and in winding you pass the wire under two and over two, and so on until required number of turns is completed.

When completed, place the centers of the two coils evenly together, which automatically gives correct spacing between coils, and securely fasten together with a small brass machine bolt and nut. A neat effect can be obtained by cutting off the unused ends of the spokes down to the wire on both forms. On the secondary, which is toward back of set when set up, leave one spoke untouched. Drill a hole of proper size in baseboard and insert this long spoke. This gives an easy and secure mounting for coils.

The set as described will cover the entire band of broadcast wave lengths with an average-size outside antenna, and under favorable local and weather conditions will give the fan all the DX records he wants.

Magnavox Produces a Tube

The engineers who developed the Magnavox line of reproducing and amplifying equipment have now produced a vacuum tube which has been placed on the market at a price of \$5.00. The Magnavox tube, Type A, is a storage battery tube for use as audio frequency and radio frequency amplifier in all standard circuits. Also recommended for detector use. It is not critical of adjustment either as to plate or filament. Filament consumption is one-quarter of an ampere. Its principal feature consists in its capacity for eliminating the grid.

New Models Bristol Radio Receivers

Incorporating the Patented Grimes Inverse Duplex System

Watch for further announcements in all leading radio publications.

Grimes' System Insures National Tone Quality

Improved Bristol Audiophone Loud Speakers—give greater volume, are more sensitive and still maintain their round, full tone and their distinctive freedom from distortion.

Ask for Bulletin No. 3017-P.

Manufactured by

The Bristol Company


Waterbury Conn.



SENIOR AUDIOPHONE
15 inch Bell
Price.....\$30.00



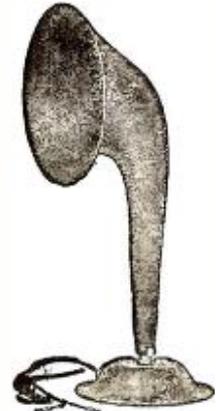JUNIOR AUDIOPHONE
11 inch Bell
Price.....\$22.50



BABY AUDIOPHONE
With Fibre Horn
Price.....\$12.50

HOWARD PARTS

No. 1001 Rheostat, \$1.10
No. 1003 Potentiometer, \$1.50
No. 1002 Micrometer, \$1.50
At All Dealers.



Dept. A

4248 N. Western Ave.

Build a Super-Het PRECEL Super Kit

Including fixed coupler, oscillator coil, filter, three intermediate wave R. F. Transformers, blue print, panel layout, etc. Complete Kit list \$25.00 each.

It Works and Can't Be Beat!
Order now, as supply is limited.

Electrical Manufacturer's Agency, Inc.
25 N. Dearborn St. CHICAGO
COMET BATTERIES

First of a Series of Technical Radio Articles by Armstrong Perry
Begins in October RADIO AGE

Always Mention RADIO AGE When Writing to Advertisers

FREE



To Each Purchaser of a World Battery

A 24-Volt "B" Storage Battery positively given FREE with each purchase of a WORLD "A" Storage Battery. The WORLD Battery is famous for its guaranteed quality and service. Backed by years of Successful Manufacture and Thousands of Satisfied Users. You save 60%.

Prices That Save and Satisfy

Auto Batteries		Radio Batteries	
6-Volt, 11 Plate \$12.25	6-Volt, 100 Amps. 12.50	6-Volt, 126 Amps. 12.50	6-Volt, 140 Amps. 15.00
6-Volt, 13 Plate 14.25			
12-Volt, 7 Plate 17.00			

Shipment Express C. O. D. subject to examination. 5 per cent discount for cash in full with order.

2-Yr. Guarantee Bond in Writing With Each World Storage Battery

proves satisfactory World performance. Mail this ad with your name and address—we will ship battery day order is received; and give you your choice of "B" Storage Battery or a handsome nickel finish Auto Spottie. FREE. Write TODAY.

WORLD BATTERY COMPANY
1219 So. Wabash Ave. Dept. 36, CHICAGO, ILL.

This FREE "B" Storage Battery takes the place of dry cell "B" batteries. Can be recharged and will last indefinitely. To be sold retail for \$6.00. It is the only battery of its kind equipped with solid rubber case—and insurance against acid and leaks. Take advantage of this remarkable introductory offer NOW. (To those who prefer it, we will send FREE a handsome nickel finish Auto Spottie, instead of the "B" Battery. Be sure to specify which is wanted.)

GIVEN FREE

To introduce this new and superior World "B" Storage Battery to the Public.



Pickups by Our Readers

(Continued from page 44)

I think Mr. Hahn's letter is a good one, and I think he will be glad to receive RADIO AGE for one year FREE. You fellows who missed out on that contest—MISSED SOMETHING!

I feel that this fellow deserves some recognition at least, for his good work. His listening is done in static the year around, far away from broadcasting stations, and his perseverance gets him a RADIO AGE ANNUAL.

RADIO AGE,
Gentlemen:

I have been getting your magazine from newsstands ever since you published your first number. I have every issue. I would sooner lose my tuning arm than to miss a number. I think that RADIO AGE is the biggest and best publication on the market.

I am a ham (my call being 4VA) but I would rather mix in with this bunch of Pick-up Birds of RADIO AGE than anything else. I have a single tube single circuit, and a Crosley Model X. I understand that the Crosley won't count in the lists, will it? Do I have to use one tube? I want to be a Dial Twister—I think it is more fun to be a BCL with the RADIO AGE bunch than getting a glass arm from poking at a key.

Here is a list I got on my one tube set:

KDKA, KJS, WBAP, WSY, WSAI, WOC, WSB, WWI, WLW, WMC, WGY, WOO, WJAX, WTAM, WCAI, WEAH, WDAR, WEAO, WOR, WMAJ, WFI, WDAT, WOAL, PWX, 6KW, WHAS, WSAF, WWJ, KSD, CYL, WGY, WSI, KVG, 2BY, WIAS, KGO and one in Porto Rico, the call of which I missed in tuning.

Now I don't think this is so bad, because all you fellows are up there amongst all the stations; where I am, way down here, there aren't many stations. To get any, you've got to reach out a long way first.

I want to wish you all the success in the world with your "million dollar RADIO AGE."

Yours truly,
P. L. HARTNETT.

316 Henderson Ave.,
Tampa, Florida.

Yessir! That letter deserves third prize. Down in the land of everlasting Summer, you do have static. I've had some of the radio bugs tell me that if it ever gets much worse, it would be fatal to listen. HI!

Score so far, by the courtesy of the Pick-ups Station of RADIO AGE is as follows:

June Game:						Prizes
	1	2	3	4	5	Total
Dial Twisters...	1	1	1			3
Old Man Static...	0	0	0			0

Always Mention RADIO AGE When Writing to Advertisers

Here's another live wire:

RADIO AGE,
Gentlemen:

I am sending the following article for the Pick-ups Page in RADIO AGE. (He's quite a poet, and doesn't know it—makes 'em rhyme any time).

I am using the following hook-up employing a UV200 tube and have an antenna 40 feet long and 25 feet high. I have received as far as 200 miles with a wire 20 feet long and 10 feet high. My list of stations is as follows:

Calls Heard

KGO, KLZ, WCAP, WRC, WDAE, WSB, KFAU, KYW, WLS, WEBH, WGN, WMAQ, WJQ, WTAS, WTAY, WCBQ, WGAZ, KFLZ, WOC, WHAA, KFKB, WEAH, WEAR, WNAC, WGI, WBZ, WDS, KOP, WCX, WWJ, WBAH, WLAG, KFAX, WCAL, WOS, WDAF, WHB, WOO, KFEZ, KSD, WCK, WEB, KFKX, WAAW, WQAW, WCAJ, WOR, WEXM, WOB, WGR, WSAW, WCAP, WMAC, WMAK, WFAF, WHN, WLY, WJZ, WHAM, WGY, WHAZ, WBT, WABW, WLW, WSAI, WTAM, WJAX, WHK, WBAV, WEAO, WABD, KGW, KDKA, WDAR, WOO, WIP, WIP, KQV, WCAE, WIAS, WPAW, WEAN, WJAR, KFDY, WNAV, WMC, WCM, WFAA, WBAP, WEAV, WCAR, KTW, WHA, WCAV, WHAD, CFCN, CKAC, CKCK, CFCA, CKY, PWX.

This makes 94 stations in all, in 30 different states, 5 in Canada and 1 in Cuba. A good part of this list was made during June and July.

ROBERT M. HILLIS.

1462 Belle Ave.,
Lakewood, Ohio.

Some time ago, a fellow, when subscribing, wrote in and told us that our magazine was not filled with a lot of crazy DON'TS—so we are going to spoil his perfectly good opinion of RADIO AGE by printing the following:

Don't forget to point out errors in the broadcast line.

Don't forget to renew your subscription.

Don't fail to read the October issue of RADIO AGE containing the story of the August Static Puncturing Contest.

New Lego Detector

A new fixed detector, The Lego Wonder, is being put out on the market by the Lego Corporation, of 225 West 77th Street. The engineers of this concern, after months of experimentation, maintain that the Lego Detector is ideal for Reflex and Crystal sets. Among the features of the Lego Wonder are the following:

No parts to replace or wear out; the use of a new material that effectively eliminates distorted and interrupted reception, and substitutes clarity and increases volume; 100 per cent sensitive; no searching for sensitive spot; glass encased, is immune from sun and dust.

RADIO PAYS BIG

EARN \$3000 to \$9000 a Year

Enter fast growing radio field, thousands of big pay jobs waiting for you. U. S. Gov't., Steamships, R. R's., Corporations eagerly seek Radio trained men. Advancement rapid, earn from \$3000 to \$9000 yearly.



Prepare for Big Pay in Spare Time

My reputation as Radio Engineer and instructor insures you complete, speedy success, at home in spare time; **earn while you learn.** I make you expert in radio designing, building, repairing and operating and teach you only practical "inside" dope. You quickly complete my course and step out into Big Pay. No experience required.

FREE RADIO OUTFIT 1000 MILE TUBE SET

For a short time I will give tube radio set in handsome cabinet to men who enroll now, absolutely FREE. Send at once for my FREE wonder-book of inside Radio "dope."



A. G. MOHAUPT, Radio Engineer,
RADIO ASS'N OF AMERICA,
4513 Ravenswood Avenue, Dept. 29, CHICAGO
Dear Sir: Send me your FREE Radio Book and your limited plan without cost or obligation.

Name.....
Address..... City.....

HUDSON-ROSS
Sells only Guaranteed Radio Apparatus.
Send for discounts.
123 W. Madison St. Chicago

Attaining Hair's Breadth Selectivity with One Control

(Continued from page 13)

the tube and put the phone plug in the jack. The tube should then be illuminated and the rheostat knob turned until the brilliancy is in accordance with directions accompanying the tube. Then connect the "B" battery and a sharp click should be heard. The tube should respond with a bell-like note when it is jarred slightly. Rotate the tuning condenser dial until a bird-like whistle is picked up—signifying the "carrier wave" of a broadcasting station. Increase the absorption condenser to about 70, when the whistle should cease and voice or music be heard.

IF THE absorption condenser does not stop the oscillation, increase the coupling between the antenna coil and the secondary until the oscillation does stop. The proper degree of coupling will be such that oscillation may be started and stopped by a movement of the absorption condenser at any point on the tuning condenser's dial. In the case of a small aerial, it may not be possible to stop oscillation, and in that case, wind about five more turns on the coupling coil.

Without oscillation, and with the absorption condenser at 100, tune in a local station on the tuning condenser and adjust the rheostat for best reception, using no more brilliancy than is necessary for loud and clear signals. Then decrease the absorption condenser to a point near oscillation, when the volume will be several times as great.


It is important to note that the circuit may be quite close to the point of oscillation over a wide range on the tuning dial. In searching for DX stations, the best and most thoughtful practice is to keep the reading of the absorption condenser slightly higher than is needed to produce oscillation, and at that point there will be sufficient regeneration to bring in the stations well. The presence of a DX station, or in fact any station, is indicated by a swishing sound caused by the contacts of the high voltage generator at the station. This slight swishing noise is very sharp in tuning, and if the station is weak it is utterly impossible to get it without the use of the vernier control.

How the Scale Should Read

Users of some condensers (.0005 in size, however) may find that the condenser scale isn't just right as regards its tuning range. To be sure of getting 546 meters (KSD), the highest broadcast wave length, WIP or WOO should come in at about 84 on the tuning condenser. The accompanying "curve" will show plainly about where the various stations may come in and will also give the reader an idea of the appearance of a "DX List." Anyone can make up such a curve

BAKELITE

TRADE MARK REG. U. S. PAT. OFF.

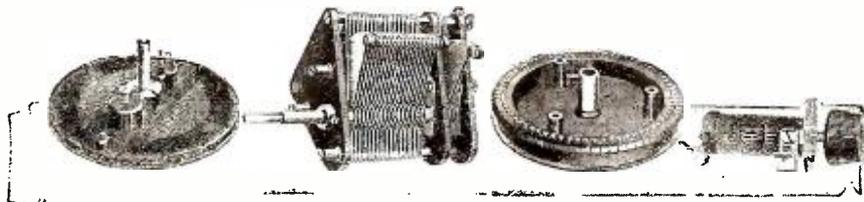

Standard Insulation —wherever Dials turn

With every facility for testing materials used in radio work, the United States Signal Corps chose Bakelite for the potentiometer base here shown. We also illustrate a Rogers Radiometer, Kellogg Condenser and Fil-Ko-Stat, all of which are Bakelite Insulated.

These critical radio experts, as well as the most inexperienced amateur, have come to recognize the phrase "Made of Bakelite" as a guaranty of excellence in radio insulation.

Bakelite enhances the value of any radio set. Its high electrical resistance, stability and beauty of finish have led to its adoption as standard insulation by the large majority of radio manufacturers.

Send for a copy of our Radio Booklet H



Send for our Radio Map

The Bakelite Radio Map lists the call letters, wave length and location of every broadcasting station in the world. Enclose 10 cents to cover the cost and we will send you this map. Address Map Department.

BAKELITE CORPORATION

247 Park Avenue, New York, N. Y.
Chicago Office: 636 West 22d Street

THE MATERIAL OF A THOUSAND USES

Latest Development In
RADIO
The New Pfanstiehl
Non-Oscillating
Principle
Complete Outfits
\$5 DOWN
Easy Monthly Payments

The season's biggest sensation. Carl Pfanstiehl's improvement over Neutrodyne, Spurr, Reflex, etc. Positively non-regenerative. Brings a new degree of musical quality, selectivity, and simple operation. Solid mahogany cabinets. Accessories included.


Write Today for FREE Trial Offer! Write quick and get our special price offer with 2 week's FREE Trial, and easy payments, 3, 4 or 5 tube sets. Write: MARSHALL RADIO PRODUCTS, Inc., Dept. 58-96, Marshall Blvd. and 19th Street, Chicago, Ill.

all free! **RADIO LIBRARY**

JUST SEND A POSTCARD YOU GET "Library of Latest Radio Literature," written by foremost radio authorities. Contains HUNDREDS of valuable wiring diagrams, HOOK-UPS, illustrations, articles, data, etc.

EXPLAINS in clear, understandable language the popular new circuit: reflex, neutrodyne, phisiform, "nameless" super-heterodyne, etc., and how to build sets. Covers long and short wave amplification, push-pull and audio amplifiers. Latest information on multi-tube and other radio subjects. LOG BOOK INCLUDED FREE. Also our latest Radio Catalog featuring NATIONALLY ADVERTISED lines at attractive savings. Write today — offer limited. Address: ATWOOD-KING, Inc., Dept. P-9, 163 W. Washington St., Chicago

ATWOOD KING INC.

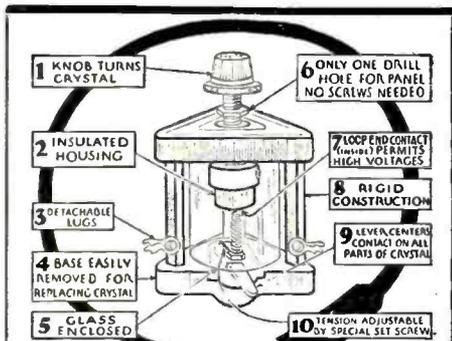

Best Crystal Ever Designed!

FRESHMAN

Double Adjustable Crystal Detector

At last the experimenter who has searched for the ideal crystal can now depend upon a perfect detector. The new Freshman Double Adjustable Crystal Detector has met every requirement of the ideal unit. It affords uninterrupted, noiseless, distortionless reception, yielding extraordinary volume with entire absence of squeals and howls often introduced by vacuum tube detectors.

The World's Best for Crystal or Reflex Sets

No more searching for the sensitive spot—merely turn the knob as you would a dial. Freshman Double Adjustable Crystal Detector for panel or base use, complete..... **\$1.50**

Freshman Super-Crystal with Non-Metallic Housing. Fits any standard detector unit..... 50c

At your dealer's or send purchase price and you will be supplied postpaid.

FREE! Write for building plans and hookups of Super-Heterodyne, Reflex and other popular circuits.

Chas. Freshman Co. Inc.
Radio Condenser Products
106 Seventh Ave., New York

CLASSIFIED ADVERTISEMENTS

Ten cents per word per insertion, in advance. Name and address must be counted. Each initial counts as one word. Copy must be received by the 10th of month for succeeding month's issue.

RADIO CIRCUITS

SPECIAL FOR SEPTEMBER

The Reinartz Radio Booklet, by Frank D. Pearne, fully illustrated, and RADIO AGE, for \$2.50. Price of booklet alone is 50c. Send check, currency or money order to RADIO AGE, 500 N. Dearborn Street, Chicago.

RADIO EQUIPMENT

WHOLESALE PRICES ON STANDARD RECEIVERS. 25% discount; list for stamp. LIVE PROPOSITION TO DEALERS. Thomas Radio Co., 111a Dix St., Muncie, Ind.

RADIO BATTERIES

Super Radio A and B Circuit Batteries, which bring in long distance reception. Sold for cash or on payment plan. Write for prices and details Radio Battery Corporation, 501-B Industrial Bank Bldg., Flint, Mich.

MISCELLANEOUS

158 GENUINE Foreign Stamps. Mexico War Issues, Venezuela, Salvador and India Service, Guatemala, China, etc., only 5c. Finest approval sheets 50 to 60% Agent Wanted. Big 72-p. Lists Free. We Buy Stamps. Established 20 Years. Hussman Stamp Co., Dept. 152, St. Louis, Mo.

QUALITY PRINTING—200 bond letter heads, \$1.50; 250 envelopes, \$1.50; 250 cards, \$1.25. Samples. Midland Press, 543 West Hickory, Kankakee, Ill.

after he has listed the tuning dial numbers for a dozen stations or so. all that is required being a sheet of plain graph paper. Divide the lower line into tens for the dial numbers and the left vertical margin into tens for wave lengths between 200 and 550 meters.

The selectivity of the circuit will be sufficient to bring in WKAQ, Porto Rico, without a whisper from WDAP (now WGN) or WJAR—both 360 meter stations also. The fact is that WKAQ is a bit higher than 360 meters. The selectivity will also be sufficient to tune out WLW of Cincinnati (309 meters) and bring in KGO, Oakland, California (312). Of course, such long distance as KGO cannot be accomplished every night or even every week, but there are dozens and dozens of stations within the reach of this Ultra-Audion receiver. All that is necessary to get them is patience with the vernier "knob," as this is the heart of the control. Keep the regeneration up near the oscillation point, but be careful not to let it "spill over" and whistle very often as this will interfere with other listeners within a quarter of a mile or so. The circuit is not nearly as serious an interferer as a regenerative circuit where the aerial circuit is tuned, but it can radiate to some extent. The beauty of the arrangement shown is that the tendency is to tune the set without allowing it to oscillate whereas in other forms of regenerative circuit users are naturally more prone to use oscillation as a means of picking up DX stations.

The little "swishing" sound mentioned is your guiding notice and you can turn the vernier from 15 to 25 past eight or ten easily receivable broadcasting stations without having to touch the absorption condenser at all.

RADIO AGE
The Magazine of the Hour

RADIO AGE is a monthly periodical published on the 25th of each preceding month. There are 12 volumes, per number, constituting a volume. The subscription price for RADIO AGE in United States, its possessions and Canada is \$2.50 per year; foreign, \$3.00 per year. Single copies in United States, 25 cents each. Sample copy will be sent upon request. United States postage stamps in good condition, United States coin, money orders and personal checks accepted. No foreign stamps or coin will be honored. Checks and money orders should be drawn to the order of RADIO AGE, Inc.

All contributions should be addressed to R. H. Hopkins, Associate Editor, Suite 730, 500 N. Dearborn St., Chicago, Illinois. Contributions such as are not available will not be returned unless full return postage is enclosed. Remuneration for contributions printed in RADIO AGE is made upon publication, the word rate and amount being decided at the judgment of the Editor. Rates differ for various subjects. Good glossy photographic prints or other illustrations are solicited.

Other communications should be addressed to various departments as follows: Technical, Felix Anderson; Advertising, H. A. Ackerburg, advertising manager, Davidson & Hevey, Eastern representatives, 17 West 42d St., New York City; business and magazine returns, A. M. Leeb. All departments, excepting New York agency, are located at 500 N. Dearborn St., Chicago, Illinois, in care of RADIO AGE.

RADIO AGE, Monthly. Established March, 1922. Entered as second class matter at the Post Office at Chicago, Illinois, under the act of March 3, 1879, April 4th, 1924. Title Registered in U. S. Patent Office. Copyright, 1924: By RADIO AGE, Inc., 500 N. Dearborn St., Chicago, Illinois. The contents of this magazine are copyrighted, and must not be reproduced in part or in full without permission.

RADIO AGE is on sale on or about the 26th of each month on various news-stands and magazine agencies in the United States, Mexico, South America, England and Canada.

TO SUBSCRIBE, use the blank provided for in the magazine on one of the pages herein. Write plainly. Avoid sending coins in plain envelopes. We will not be responsible for loss of money or other communications in the mails. Subscription price per year (12 numbers) is \$2.50 in the United States and Canada. Subscriptions for less than one year not accepted. Subscription may be made in combination with QST or RADIO AGE ANNUAL if so desired.

Always Mention RADIO AGE When Writing to Advertisers



12 Cells 24 Volts Solid Rubber Case

\$4.00 COB SPECIAL

INTRODUCTORY PRICE
For a limited time only, and to introduce this new and superior Storage "B" Radio Battery to the Public, we are selling it for \$4.00. Regular Retail Price is \$5.00. You save \$2.00 by ordering NOW. A finer battery cannot be built than the World Storage "B" Battery

(12 CELLS—24 VOLTS)
To ten million homes with Radio Sets—and to countless millions of prospective buyers—this WORLD Storage "B" Battery brings a new conception of battery economy and performance. Here is a battery that pays for itself in a few weeks—will last for years and can be recharged at a negligible cost. And you save \$2.00 by ordering now.

A Superior Battery Equipped With Solid Rubber Case
Has heavy duty 2 1/8 in. x 1 in. x 1 1/4 in. plates and plenty of acid circulation. Extra heavy glass jars allow ready observation of charge and prevent leakage and seepage of current. It holds its charge, while idle, at constant voltage. You will find this battery a boon to long distance reception. It does away with a great many notes so often placed on "static. Mail your order today."

SEND NO MONEY

Just state number of batteries wanted and we will ship day order is received. EXTRA OFFER: 4 batteries in series (96 volts), \$16.00. Pay Expressman after examining batteries, 5 per cent discount for cash in full with order. Send your order NOW and save \$2.00.

WORLD BATTERY COMPANY
Makers of the famous World Radio "A" Storage Battery
1219 S. Wabash Ave., Dept. 81, Chicago, Ill.

SAVE \$2.00 BY ORDERING NOW!

You are Missing Lots of Signals Without a—

Jiffy RIBBON ANTENNA

No set is at its best without a "Jiffy."

Jiffy Ribbon Antenna will work wonders for you. It is light in weight, yet has exceptionally high tensile strength. It is non-corrosive and cannot rust!

Supplied in 100 foot lengths, complete with two insulators—ready to install. (Works as either in-door or out-side aerial.)



At your dealer's or direct

\$1.50

Apex Stamping Company
Dept. 12 Riverdale, Ill.

HUDSON-ROSS

RADIO HEADQUARTERS
sells to dealers only.

Write for discounts.

123 W. Madison St. Chicago



B-METAL quality warrants the 90% discard. Only 10% marketed, but it pays us. Your dealer will get you one.

B-METAL REFINING CO.
5th Floor, 525 Woodward Ave. DETROIT, MICH.

The How and Why of Interference

(Continued from page 10)

Distinguishing Instruments

How often have you found that, were it not for the announcer telling you that such and such a composition was a violin solo, you would be unable to tell whether it was played by a violin or a flute? Having been told that it was a violin playing the piece, your imagination comes into play and you believe that you are listening to a violin.

The above explanation also accounts for the fact that one can separate equally distant stations operating on nearly the same wave length, within less than the space of one degree on the tuning dial, while with the case of a comparatively near station and an extremely distant one, a goodly number of harmonics have to be reckoned with in the music from the near station, which are entirely absent in the distant one.

So, don't tear your hair in exasperation when your receiver fails to obliterate that local interference sufficiently to allow you to bring in that coveted DX. No wave trap or filter is of any help in this case, for its use would also eliminate the signal itself. And, above all, do not blame the offending station.

The fault lies in the proximity of your receiver to the local station and the obvious remedy is—remove your receiver to a more advantageous location with respect to the home station or wait until local stations get "off the air" before you attempt to tune in DX.

New Ray-dio "B" Battery

The famous Lavier Formula, a new method for making batteries, has just been applied to radio batteries by the Jordan Battery Company, Ypsilanti, Michigan, manufacturers of Ray batteries.


This battery is called the Ray-dio "B" Storage Battery and is said to be a revolution in radio battery construction.

Among the many unusual features of this battery is the fact that no separators are used, giving free, unobstructed passage of the current, thus eliminating the hissing and sizzling that are often laid to static.

Ray-dio "B" Storage Batteries, it is said, respond instantly to atmospheric variations, and eliminate the annoyance of constant tuning.

"Babydyne" Latest in One-Tube Reception

The latest marvel in the radio world is the International Babydyne Radio Receiver, made by the A. and T. Radio Co. of Danvers, Mass. It owes its efficiency to a well-balanced hookup and to the newest radio improvements it incorporates. The Babydyne is compact, durable and easy to handle. It can be placed easily in a handbag, can be coupled to two stages of amplification and will tune in distant stations 1,500 miles away with ease. Static is reduced to a minimum.

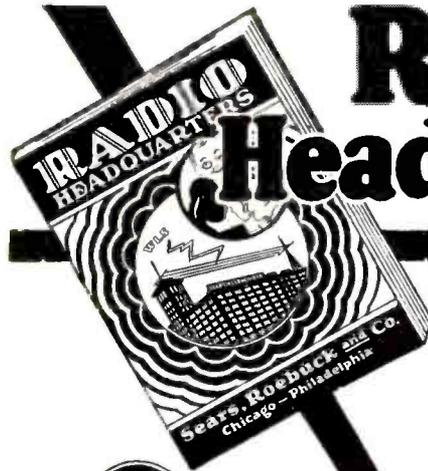


Radio Headquarters

Everybody is interested in Radio. If you would keep in step with the progress that has been made in this greatest of all discoveries, you should have our NEW RADIO Catalog just now off the press.

You can get the latest and best equipment from RADIO HEAD-QUARTERS. We have everything that anybody needs to enjoy the entertainment, news and education that are waiting to be brought right into your home.

Don't be without the comfort of Radio this fall and winter when reception is so fine.

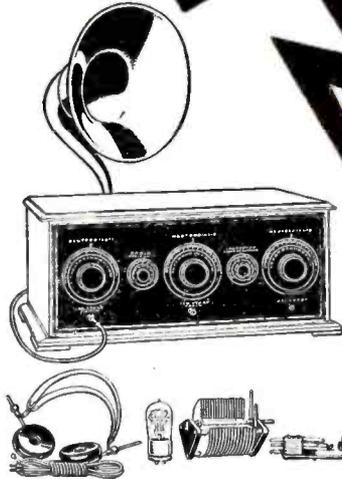The World's Largest Store—RADIO HEADQUARTERS—can save you money on everything you need.



The World's Largest Store is RADIO HEADQUARTERS. Here you can get the famous SILVERTONE neurodyne receiving set or the smallest radio part—at the lowest prices in America.

Mail the coupon TODAY to the store nearest you. 99R7L.

Sears, Roebuck and Co.
Chicago Philadelphia Dallas Seattle

Send New Radio Catalog.

Name

Postoffice State

Rural Route Box No.....

Street and No.

Sears Roebuck and Co.

The World's Largest Store owns and operates Station W.L.S. Wavelength 345 Meters. Tune in

"ROLLS ROYCE" RADIO TUBES



Like their name, significant of quality. Durable and powerful. Bring in distance with a maximum of volume and clearness.

- Type 200...5 Volts, 1 Ampere Detector Tube.
- Type 201A...5 Volts, .25 Ampere Amplifier and Detector.
- Type 199...3-4 Volts, .06 Ampere Amplifier and Detector.
- Type 199...3-4 Volts, .06 Ampere With Standard Base.
- Type 12...1½ Volts, .25 Ampere Platinum Filament Amplifier and Detector.
- "THE ROLLS ROYCE OF RADIO TUBES" ALL TYPES\$2.50
- Type 202...5 Watt Transmitters\$3.00

ALL TUBES GUARANTEED to work in Radio Frequency. Especially adapted for Neurodyne, Reflex and Super-Heterodyne Sets.

SHIPPED PARCEL POST C. O. D. WHEN ORDERING MENTION TYPE.
ROLLS ROYCE TUBE CO.
21 Norwood St. (Dept. A) Newark, N.J.



Are you getting DX?

This book will show you how to get more!

It tells all about vacuum tubes and how to control them so as to get greatest DX, most volume and longest life from tubes and batteries. How to get maximum regeneration, clearest signals. Tells how vacuum tubes work.

IT'S FREE! WRITE FOR IT TO



Dept. R. A. 824 Harrisburg, Penna.

Have You Seen the Real Blueprints in This Issue?

Corrected List of U. S., Cuban, Canadian, British and French Broadcasting Stations

Complete Each Issue

THE list of broadcasting stations on these pages is brought up to date each month by additions of new stations and deletion of those which have suspended operation. The list is the product of a vast volume of correspondence and its completeness is due in large measure to the assistance of our special news service in Washington, D. C. Suggestions, corrections and additional data will be welcomed from readers and broadcasters.

KDKA	Westinghouse Electric & Mfg. Co.	East Pittsburgh	326	KFNL	Radio Broadcast Ass'n.	Paso Robles, Calif.	240
KDPM	Westinghouse Electric & Mfg. Co.	Cleveland, Ohio	270	KFNV	L. A. Drake Battery and Radio Supply Shop	Santa Rosa, Calif.	234
KDPT	Southern Electrical Co.	San Diego, Calif.	244	KFNX	Peabody Radio Service	Peabody, Kansas	240
KDYL	Telegram Publishing Co.	Salt Lake City, Utah	360	KFNY	Montana Phonograph Co.	Helena, Montana	261
KDYM	Savoy Theatre	San Diego, Calif.	244	KFNZ	Royal Radio Company	Burlingame, Calif.	231
KDYO	Oregon Institute of Technology	Portland, Ore.	360	KFOC	First Christian Church	Whittier, Calif.	236
KDZE	Frank E. Siefert	Bakersfield, Calif.	240	KFOD	Vern Peters	Wallace, Idaho	224
KDZE	Rhodes Department Store	Seattle, Wash.	360	KFOJ	Moberly High School Radio Club	Moberly, Missouri	246
KDZI	Electric Supply Co.	Wenatchee Wash.	360	KFOL	Carte A. Ross Motor Service Co.	Casper, Wyo.	242
KDZR	Bellingham Publishing Co.	Bellingham, Wash.	361	KFON	Epoch Radio Shop	Long Beach, Calif.	242
KFAD	McArthur Bros. Mercantile Co.	Phoenix, Ariz.	260	KFOO	Latter Day Saints University	Salt Lake City, Utah	261
KFAE	State College of Washington	Pullman, Wash.	330	KFOQ	Ora William Chancellor	Galveston, Texas	240
KFAF	Western Radio Corporation	Denver, Colo.	278	KFOR	David City Tire & Electric Co	David City, Nebraska	226
KFAR	Studio Lighting Service Co. (O. K. Olsen)	Hollywood, Calif.	280	KFOT	College Hill Radio Club	Wichita, Kansas	241
KFAW	The Radio Den (W. B. Ashford)	Santa Ana, Calif.	280	KFOY	Board of Education, Technical High School	Omaha, Nebraska	238
KFAY	W. J. Virgin	Medford, Ore.	283	KFOZ	Beacon Radio Service	St. Paul, Minn.	234
KFBB	F. A. Buttrey & Co.	Havre, Mont.	360	KFPB	Leon Hudson Real Estate Co.	Fort Smith, Ark.	233
KFBC	W. K. Azbill	San Diego, Calif.	278	KFPD	Edwin J. Brown	Seattle, Wash.	224
KFBE	Reuben H. Horn	San Luis Obispo, Calif.	242	KFPF	Garretson and Dennis	Los Angeles, Calif.	238
KFBG	First Presbyterian Church	Tacoma, Wash.	360	KFPH	Harold Chas. Mailander	Salt Lake City, Utah	242
KFBK	Kimball-Upson Co.	Sacramento, Calif.	283	KFPL	C. C. Baxter	Dublin, Texas	242
KFBL	Leese Bros.	Everett, Wash.	224	KFPM	The New Furniture Co.	Jefferson City, Mo.	242
KFBS	Trinidad Gas & Electric Supply Co. and the Chronicle News	Trinidad, Colo.	360	KFPN	Missouri National Guard	Denver, Colo.	231
KFBU	The Cathedral (Bishop N. S. Thomas)	Laramie, Wyo.	283	KFPO	Colorado National Guard	Denver, Colo.	231
KFCB	Nielson Radio Supply Co.	Phoenix, Ariz.	238	KFPF	G. & G. Radio & Electric Shop	Olympia, Washington	236
KFCF	Frank A. Moore	Wall, W. Va.	360	KFPQ	Clifford M. Esler	Denison, Texas	231
KFCH	Electric Service Station (Inc.)	Billings, Mont.	360	KFPR	Los Angeles Co. Forestry Dept	Los Angeles, Calif.	231
KFCL	Leslie E. Rice	Los Angeles, Cal.	336	KFPS	Carl A. Ross Motor Service Co.	San Francisco, Calif.	236
KFCP	Ralph W. Flygare	Ogden, Utah	260	KFPV	Heintz & Kohlmoos, Inc.	San Francisco, Calif.	236
KFCV	Fred Mahaffey, Jr.	Houston, Texas	360	KFPW	St. Johns M. E. Church, S.	Carterville, Mo.	268
KFCZ	Omaha Central High School	Omaha, Nebr.	258	KFPY	Symons Investment Co.	Spokane, Wash.	283
KFDD	St. Michaels Cathedral	Boise, Idaho	252	KFPX	First Presbyterian Church	Pine Bluff, Ark.	242
KFDH	University of Arizona	Tucson, Ariz.	368	KFOA	The Principia	St. Louis, Mo.	261
KFDJ	Oregon Agricultural College	Corvallis, Ore.	360	KFOB	The Searchlight Publishing Co	Fort Worth, Tex.	254
KFDR	Bullocks' Hardware & Sporting Goods (Rob. G. Bullock)	York, Nebr.	360	KFOC	Kidd Brothers Radio Shop	Taft, Calif.	227
KFDX	First Baptist Church	Shreveport, La.	360	KFOE	Chickin Supply Co.	Anchorage, Alaska	280
KFDY	South Dakota State College of Agriculture and Mechanics Arts	Brookings, S. Dak.	360	KFOE	Dickenson-Henry Radio Laboratories	Colorado Springs, Colo.	224
KFDZ	Harry O. Iverson	Minneapolis, Minn.	231	KFOG	Southern Calif. Radio Ass'n	Los Angeles, Calif.	226
KFEC	Meier & Frank Co.	Minneapolis, Minn.	231	KFOH	Albert Sherman	Hillshough, Cal.	231
KFEL	Winner Radio Corp.	Denver, Colo.	254	KFOI	The Thos. H. Rice Corp	Silver City, Calif.	234
KFEQ	Scraggin & Company Bank	Oak, Nebr.	268	KFOJ	Harbour Longmire Company	Oklahoma City, Okla.	236
KFER	Auto Electric Service Co.	Fort Dodge, Iowa	231	KFOK	Democrat Leader	Fayette, Mo.	236
KFEV	Radio Electric Shop	Douglas, Wyo.	263	KFOL	Oklahoma Free State Fair Assn	Muskogee, Okla.	252
KFEX	Augsburg Seminary	Minneapolis, Minn.	263	KFOR	Walter LaFayette Ellis	Oklahoma City, Okla.	250
KFEY	Bunker Hill & Sullivan Mining and Concentrating Co.	Kellogg, Idaho	360	KFOS	Dickenson-Henry Radio Laboratories	Manitou, Colo.	246
KFEZ	Asso. Eng. Societies of St. Louis	St. Louis, Mo.	248	KFOU	Texas National Guard	Denison, Texas	252
KFFB	Jenkins Furniture Co.	Boise, Idaho	240	KFOV	W. Riker	Holy City, W. Va.	234
KFFE	Eastern Oregon Radio Co.	Pendleton, Ore.	360	KFOW	Omaha Grain Exchange (Portable)	Omaha, Nebr.	231
KFFP	First Baptist Church	Moberly, Mo.	278	KFOX	C. F. Krier	North Bend, Wash.	248
KFFR	Nevada State Journal (Jim Kirk)	Sparks, Nev.	226	KFOY	Alfred M. Hubbard	Seattle, Wash.	233
KFFS	Graceland College	London, Iowa	263	KFSG	Angelus Temple	Los Angeles, Calif.	278
KFFY	McGraw	Omaha, Nebr.	278	KGK	Tacoma Daily Ledger	Tacoma, Wash.	252
KFFZ	Pincus & Murphy	Alexandria, La.	275	KGB	Hollock & Hunt Radio Service	Tacoma, Wash.	252
KFGC	Louisiana State University	Baton Rouge, La.	254	KGO	General Electric Co.	Oakland, Calif.	312
KFGD	Chickasha Radio & Electric Co.	Chickasha, Okla.	244	KGU	Marion A. Mulrony	Honolulu, Hawaii	Waikiki Beach 360
KFGH	Leland Stanford University	Stanford, Calif.	273	KGW	Portland Morning Oregonian	Portland, Ore.	492
KFGL	Arlington Garage	Arlington, Ore.	226	KGY	St. Martins College (Reb. Sebastian Ruth)	Lacy, Wash.	258
KFGL	Crane	Clatskanie, Ore.	226	KHJ	Times-Mirror Co.	Los Angeles, Calif.	395
KFGX	First Presbyterian Church	Orange, Tex.	226	KHO	Louis Wasmer	Seattle, Wash.	360
KFGZ	Emmanuel Missionary College	Berrien Springs, Mich.	268	KJQ	C. O. Goulter	Stockton, Calif.	360
KFHA	Western State College of Colorado	Gunnison, Colo.	252	KJR	Northwest Radio Service Co.	Seattle, Wash.	270
KFHD	Utz Electric Shop Co.	St. Joseph, Mo.	226	KJS	Bible Institute of Los Angeles	Los Angeles, Calif.	360
KFHH	Amhrose A. McCue	Neah Bay, Wash.	283	KJL	Warner Brothers Radio Supplies Co.	Oakland, Calif.	360
KFHJ	Fallon & Co.	Santa Ana, Calif.	278	KKL	Triune Publishing Co.	Oakland, Calif.	509
KFHR	Rita Electric & Radio Co.	Seattle, Wash.	270	KKZ	Reynolds Radio Co.	Denver, Colo.	283
KFI	Earle C. Anthony (Inc.)	Los Angeles, Calif.	469	KKMJ	San Joaquin Light & Power Corp.	Stockton, Calif.	273
KFID	Ross Arhuckle's Garage	Iola, Kans.	246	KMO	Love Electric Co.	Tacoma, Wash.	360
KFIF	Benson Polytechnic Institute	Portland, Oregon	360	KNT	Grays Harbor Radio Co. (Walter Hemrich)	Aberdeen, Wash.	263
KFIL	Windisch Electric Farm Equipment Co.	Louisburg, Kans.	234	KNX	Electric Lighting Supply Co.	Los Angeles, Calif.	360
KFIO	North Central High School	Spokane, Wash.	242	KOB	New Mexico College of Agriculture & Mechanic Arts	State College, N. Mex.	360
KFIQ	First Methodist Church	Bakings, Wash.	242	KOP	Detroit Police Department	Detroit, Mich.	286
KFIU	Alaska Electric Light & Power Co.	Juneau, Alaska	226	KPO	Hale Bros.	San Francisco, Calif.	360
KFIV	V. H. Broyles	Pittsburg, Kans.	240	KQP	Apple City Radio Club	Hood River, Ore.	360
KFIX	Reorganized Church of Jesus Christ of Latter Day Saints	Independence, Mo.	240	KQV	Doubleday-Hill Electric Co	Pittsburg, Pa.	360
KFIZ	Daily Commonwealth and Oscar A. Huelsman	Fon Du Lac, Wis.	248	KQW	Charles D. Herrold	San Jose, Calif.	370
KFJB	Marjorie B. Electrical Co.	Marquette, Iowa	248	KRE	V. C. Battery & Electric Co.	Berkeley, Calif.	288
KFJC	Seattle Post-Intelligencer	Seattle, Wash.	233	KRW	Post Dispatch (Pulitzer Pub. Co.)	St. Louis, Mo.	546
KFJD	National Radio Manufacturing Co.	Oklahoma City, Okla.	252	KTW	First Presbyterian Church	Seattle, Wash.	360
KFJE	Liberty Theatre (E. E. Marsh)	Astoria, Ore.	252	KUO	Examiner Printing Co.	San Francisco, Calif.	360
KFJK	Delano Radio and Electric Co.	Bristow, Okla.	233	KUY	Coast Radio Co.	El Monte, Calif.	256
KFJL	Hardsacg Manufacturing Co.	Ottumwa, Iowa	242	KWG	Portable Wireless Telephone Co.	Stockton, Calif.	360
KFJM	University of North Dakota	Grand Forks, N. Dak.	229	KYO	Electric Shop	Honolulu, Hawaii	570
KFJQ	Valley Radio Div. of Elec. Constr. Co.	Grand Forks, N. Dak.	229	KYW	Westinghouse Electric & Mfg. Co.	Chicago, Ill.	236
KFJR	Ashley C. Dixon & Son	Stevensville, Mont. (near)	258	KZM	Westinghouse Electric & Mfg. Co.	Oakland, Calif.	360
KFJX	Iowa State Teachers' College	Cedar Falls, Iowa	229	KZN	Cope and Johnson Co.	Salt Lake City, Utah	268
KFJY	Tunwall Radio Co.	Fort Dodge, Iowa	248	WAAB	Valdemar Jensen	New Orleans, La.	268
KFJZ	Texas National Guard, One hundred and twelfth Cavalry	Fort Worth, Texas	254	WAAC	Tulane University	New Orleans, La.	360
KKFA	Colorado State Teachers College	Fort, Greeley, Colo.	248	WAAD	Ohio Mechanics Institute	Cincinnati, Ohio	360
KKFB	Brinkley-Jones Hospital Association	Milford, Kans.	286	WAAG	Chicago Daily Drivers Journal	Chicago, Ill.	286
KKFC	Conway Radio Laboratories (Ben H. Woodruff)	Conway, Ark.	224	WAAL	San Joaquin Light & Power Corp.	Milwaukee, Wis.	280
KKFD	F. F. Gray	Butte, Mont.	283	WAAM	I. R. Nelson Co.	Newark, N. J.	283
KKFE	Westinghouse Electric & Manufacturing Co.	Hastings, Nebr.	286	WAAN	University of Missouri	Columbia, Mo.	254
KKFG	Nassour Bros. Radio Co.	Colorado Springs, Colo.	283	WAAP	Omaha Grain Exchange	Omaha, Nebr.	284
KKFL	Asher H. Frank	Menominee, Mich.	281	WAAR	Harrisburg Sporting Goods Co.	Harrisburg, Pa.	266
KKFL	Paul E. Greenlaw	Frankinton, La.	234	WABD	Parker High School	Dayton, Ohio	283
KKLE	National Educational Service	Denver, Colo.	268	WABE	Young Men's Christian Association	Washington, D. C.	283
KKLO	Bizzell Radio Shop	Little Rock, Ark.	261	WABG	Arnold Edwards Piano Co.	Jacksonville, Fla.	248
KKLR	University of New Mexico	Albuquerque, New Mexico	236	WABH	Lake Shore Tire Co.	Sandusky, Ohio	240
KKLU	Rin Grande Radio Supply House	San Benito, Texas	236	WABI	Bangor Railway & Electric Co.	Bangor, Me.	240
KKLV	Rev. A. T. Brinkman	Rockford, Ill.	229	WABL	Connecticut Agricultural College	Storrs, Conn.	283
KKFW	Missoula Electric Supply Co.	Missoula, Mont.	234	WABM	F. E. Doherty Automotive and Radio Equipment Co.	Saginaw, Mich.	254
KKFX	George Roy Clough	Galveston, Tex.	240	WABN	Ottumwa, Inc.	Washington, D. C.	283
KKFL	Fargo Radio Supply Co.	Fargo, N. Dak.	231	WABO	Lake Avenue Baptist Church	Rochester, N. Y.	252
KKFLZ	Atlantic Automobile Co.	Fayetteville, Ark.	273	WABP	Robert F. Weinig	Dover, Ohio	266
KKFM	University of Arkansas	Fayetteville, Ark.	236	WABQ	Haverford College Radio Club	Haverford, Pa.	261
KKFMW	M. G. Sateren	Sioux City, Iowa	261	WABR	Scott High School, N. W. B. Foley	Toledo, Ohio	270
KKFMX	Carleton College	Northfield, Minn.	283	WABT	Holiday-Hal Radio Engineers	Washington, Pa.	252
KKFN	Henry Field Seed Co.	Shenandoah, Iowa	268	WABU	Victor Talcott Machine Co.	Camden, N. J.	226
KKFN	Wooten's Radio Shop	Warrensburg, Mo.	234	WABV	College of Wooster	Wooster, Ohio	270
KKFNJ	Warrensburg Electric Shop	Warrensburg, Mo.	234	WABX	Henry B. Joy	Mt. Clemens, Mich.	286
				WABY	John Mazaldi, Jr.	Philadelphia, Pa.	242
				WABZ	Coliseum Place Baptist Church	New Orleans, La.	263
				WBAW	Purdue University	W. Lafayette, Ind.	283
				WBAA	The Dayton Co.	Minneapolis, Minn.	417
				WBAB	Wireless Phone Corp.	Minneapolis, Minn.	244
				WBAC	James Millikin University	Decatur, Ill.	360

Results

Speak louder than words

Get the fullest enjoyment out of your radio. Pick up the messages

From **ANYWHERE**
ANYPLACE
ANYTIME



Non Directional Aerial

successfully used on all makes of sets.

As the name indicates the Portable Globe Aerial is shaped like a Globe and can be moved from place to place. It is also collapsible, ornamental and, above all, mechanically perfect, for whatever position a wire has to be in to pick up wave lengths the best, this Aerial has one in that position and several more similar. It is

Absolutely Non Directional

The Portable Globe Aerial works on the roof, in the house, on trains or ships or out in the woods.

In its operation it is more selective, and tunes much sharper and clearer with less static.

It is the greatest Radio Value of the day—featured at a price within the range of everyone.

Send money order or will ship C. O. D. **\$10.00** Parcel post prepaid in United States

THE PORTABLE GLOBE AERIAL CO.

1600 Locust St. St. Louis

DEALERS—We have an interesting proposition for dealers and jobbers. You can greatly increase your radio sales with the use of the Globe Aerial.



WANTED

OPPORTUNITY to become associated with livest radio sales organization in the west. Must be financially able to pay for sample line. Opportunity to make real money. First replies will be given preference. Address

WELBAR MFG. CO.

53 W. Jackson Blvd. Chicago

HUDSON-ROSS

Wholesale radio only.

One of the first and still in the lead. Write for discounts.

123 W. Madison St. Chicago



The Jewell Radio Test Set

¶ This is the most complete Radio Test set on the market.

¶ Manufacturers, Experimenters, Jobbers and Dealers all over the world are using it. This set is Jewell's outstanding contribution to Radio.

Price **\$75⁰⁰**

Send for Complete Circular

No. 95



Order from Dealer

Jewell Electrical Instrument Co.

1650 Walnut St. Chicago

"25 Years Making Good Instruments"

INTERNATIONAL BABYDYNE RECEIVER

The last word in simplified radio! This set will tune in over 1,000 miles.

LIST PRICE: \$10 (Without the tube).
(Discount to dealers and distributors.)

SET COMPLETE **\$15**

With tube, phones, batteries, etc.

(No discount on complete set.)



This offer bears a real money-giving value, for we include in it only guaranteed articles!

Whether you are at home, in the camp, automobile, boat or railroad riding, the Babydyne will meet your requirements. Our present model is eight inches long by six wide and weighs one pound. It can be advantageously coupled with two stages of amplification.

RADIO TUBES

WRITE to-day for descriptive literature and low prices of our guaranteed tubes.

**INTERNATIONAL
BABYDYNE
RADIO RECEIVER**

TRADE MARK

Manufactured by

A. @ T. RADIO COMPANY

Dept. B, DANVERS, MASS.

Corrected List of Broadcasting Stations

Table listing broadcasting stations with columns for call letters, station name, and location. Includes stations like WBAP, WBAX, WBAY, etc., and their respective locations such as Fort Worth, Tex., Columbus, Ohio, etc.

U.S. Gives Amateurs New Wave Lengths.

WASHINGTON. — Practically 15,545 amateurs will rejoice over the news that Secretary Hoover's radio aides have opened four new short wave bands for their exclusive use.

Nine district radio supervisors have received orders from Commissioner of Navigation D. B. Carson, under whose direction the Radio Section operates, to issue general and restricted amateur radio station licenses permitting the use of the wave lengths between 75 and 80 meters; 40 and 43 meters; 20 and 22 meters; and 4 to 5 meters, for pure CW telegraphy, 24 hours a day.

COMING IN OCTOBER RADIO AGE

Just to show you RADIO AGE has a bag of surprises for its readers in the October issue, we are giving you an inkling of some of the features. Look these over:

First of a Series of Technical Hookup articles by **ARMSTRONG PERRY**

TWO More Unique Hookups illustrated with Four Pages of **REAL BLUEPRINTS**

By John B. Rathbun

The Latest in **SIMPLE, EFFICIENT HOOKUPS**

for Beginners, by **FRANK D. PEARNE ROSCOE BUNDY BRAINARD FOOTE FELIX ANDERSON** And others.

Also, all the latest studio features for some entertaining reading between work on RADIO AGE hookups—including:

The Sunny Side of Running a Broadcasting Station

Being The "Inside" of WGN.

The **WINNERS** of the First **RADIO POPULARITY CONTEST** and all about them.

Handling Temperamental Movie Stars With Radio

A Unique Dispatch from Hollywood.

Second article on "Reminiscences of an Old Operator."

And a Choice Portion of "PICKUPS BY OUR READERS" **MORE FEATURES—MORE PAGES**

ON THE STANDS SEPT. 22

Telmaco Acme Receiver
The Ideal Receiver for all Seasons



The Telmaco Acme Receiver is truly portable. Entirely contained in beautiful traveling case. Tubes, batteries, loop, loud speaker, everything built into set. No outside loop, no aerial, no ground required.

Size of Case 8" x 10" x 18". Weighs only 27 pounds complete. Easily Carried.



Acme 4-Tube Reflex Circuit Used securing selectivity, distance and volume with minimum battery consumption.

Complete in itself. Easily carried from room to room in your home or to office, neighbors, etc. Take it along and have music, entertainment, speeches, news, market reports wherever you happen to be.

Instantly ready for use as it is. You can use external antenna and ground, loop and loud speaker if desired. 4 tubes (fully protected by shock absorber sockets)—equal to 7 tubes, due to reflexing and use of crystal detector.

Reasonably Priced Write for Free illustrated circular fully describing Telmaco Acme Receiver.

Complete Telmaco 64 page catalog containing 20 circuits in blue and describing the best in radio sent postpaid for 10c.

Dealers! Catalog and Price List furnished to all bona fide dealers making request on their business stationery.

Radio Division


TELEPHONE MAINTENANCE CO.

20 South Wells Street

Dept. C

Chicago, Illinois

T-100 Battery Charger

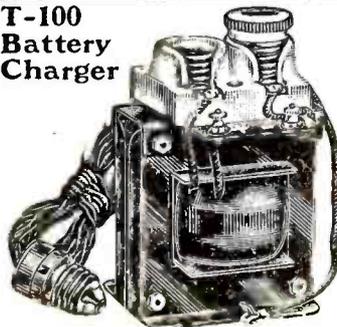

The Best and Lowest Priced on the Market

This battery charger operates on 110 volt, 60 cycle, A. C. circuit, charging a 6 volt battery at a 2 ampere rate. Standard 2 ampere charging tube is used. The T-100 is the lowest priced first-class charger on the market. Large numbers now in use have proved entirely satisfactory. No vibrating parts to get out of order. Absolutely noiseless in operation. Furnished with plug and cord for lamp socket. Battery leads marked. Fuse protects charger from accidental short circuit of 110 volt leads. Fully guaranteed.

Price complete, with 2 ampere tube, \$12.00

Radio Division

TELMACO
Quality Radio Exclusively

TELEPHONE MAINTENANCE CO.

20 So. Wells St., Dept. C, Chicago, Ill.

5000 RADIO DEALERS buy from **HUDSON-ROSS**
123 W. Madison St. Chicago
Send for dealers discount.

Free Mailing Lists
Will help you increase sales send for FREE catalog giving counts and prices on thousands of classified names of your best prospective customers—National, State and Local, Individuals, Professions, Business Concerns.
99% Guaranteed 5¢ each
ROSS-Gould Co. 313 N. 10th St. St. Louis

LEGO WONDER
FIXED DETECTOR
for **REFLEX & CRYSTAL SETS**
Something entirely new
100% SENSITIVE.
No parts to wear out; practically everlasting.
Unconditionally Guaranteed.
Designed to withstand high Plate Voltage.
For Sale by All Dealers or Sent Postpaid. Insured \$1.00.
Lego Corp., 225 W. 77th St., N. Y. C.

Corrected List of Broadcasting Stations

WQAN	Scranton Times	Scranton, Pa.	280	WSAZ	Chas. Electric Shop	Pomeroy, Ohio	258
WQAO	Calvary Baptist Church	New York, N. Y.	360	WSB	Atlanta Journal	Atlanta, Ga.	429
WQAO	Abilene Daily Reporter (West Texas Radio Co.)	Abilene, Texas	360	WSL	J. & M Electric Co.	Utica, N. Y.	273
WQAS	Prince Valter Co.	Lowell, Mass.	266	WSY	Alabama Power Co.	Birmingham, Ala.	360
WQAX	Radio Equipment Company	Peoria, Ill.	248	WTAB	Fall River Daily Herald Publishing Co.	Fall River, Mass.	248
WQJ	Calumet Baking Powder—Rainbow Gardens Station	Chicago, Ill.	448	WTAC	Penn Traffic Co.	Johnstown, Pa.	360
WRAF	The Radio Club (Inc.)	Laporte, Ind.	224	WTAF	Louis J. Gallo	New Orleans, La.	242
WRAL	Northern States Power Co.	St. Croix Falls, Wis.	248	WTAG	Kern Music Co.	Providence, R. I.	258
WRAM	Lombard College	Galesburg, Ill.	244	WTAH	Carmen Ferro	Belvedere, Ill.	236
WRAN	Black Hawk Electrical Co.	Waterloo, Iowa	236	WTAJ	The Radio Shop	Portland, Me.	230
WRAO	Radio Service Co.	St. Louis, Mo.	360	WTAL	Toledo Radio & Electric Co.	Toledo, Ohio	252
WRAY	Antioch College	Yellow Springs, Ohio	242	WTAM	Willard Storage Battery Co.	Cleveland, Ohio	390
WRAW	Avenue Radio Shop (Horace D. Good)	Reading, Pa.	238	WTAP	Cambridge Radio & Electric Co.	Cambridge, Ill.	242
WRAX	Flaxon's Garage	Gloicester City, N. Y.	268	WTAQ	S. H. Van Gordon & Son	Osseo, Wis.	220
WRBC	Immanuel Lutheran Church	Valparaiso, Ind.	278	WTAR	Reliance Electric Co.	Norfolk, Va.	280
WRC	Radio Corporation of America	Washington, D. C.	469	WTAS	Charles E. Erbstein	Elgin, Ill.	286
WRH	Chicago Herald & Examiner	Chicago, Ill.	536	WTAT	Edison Electric Illuminating Co.	Boston, Mass. (portable)	244
WRK	Doron Bros. Electric Co.	Hamilton, Ohio	360	WTAU	Ruegg Battery & Electric Co.	Tecumseh, Nebr.	360
WRL	Union College	Schenectady, N. Y.	360	WTAU	Ruegg Battery & Electric Co.	Tecumseh, Nebr.	242
WRM	University of Illinois	Urbana, Ill.	360	WTAU	Agricultural & Mechanical College of Texas	College Station, Tex.	290
WRR	City of Dallas (police and fire signal department)	Dallas, Texas	360	WTAX	Williams Hardware Co.	Streator, Ill.	231
WRW	Tarrytown Radio Research Laboratory (Koenig Bros.)	Tarrytown, N. Y.	273	WTAY	Oak Leaves Broadcasting Station	Oak Park, Ill.	283
WSAB	Southeast Missouri State Teachers College	Cape Girardeau, Mo.	360	WTAZ	Thomas J. McGuire	Lambertville, N. J.	283
WSAC	Clemson Agricultural College	Clemson, S. C.	360	WTBE	Illinois State Agricultural College	Manhattan, Kans.	273
WSAD	J. A. Foster Co.	Providence, R. I.	261	WWAB	Hoenic, Swern & Co. (John Rasmussen)	Trenton, N. J.	230
WSAI	United States Playing Cards Co.	Cincinnati, Ohio	309	WWAD	Wright & Wright (Inc.)	Philadelphia, Pa.	360
WSAJ	Grove City College	Grove City, Pa.	259	WWAE	Alamo Dance Hall, L. J. Crowley	Joliet, Ill.	227
WSAN	Allentown Radio Club	Allentown, Pa.	229	WWAO	Michigan College of Mines	Houghton, Mich.	244
WSAP	Seventh Day Adventist Church	New York, N. Y.	263	WWI	Ford Motor Co.	Dearborn, Mich.	273
WSAR	Doughry & Welch Electrical Co.	Fall River, Mass.	254	WWJ	Detroit News (Evening News Assn.)	Detroit, Mich.	517
WSAU	Camp Marietta	Chesham, N. H.	229	WWL	Electrical Equipment Co.	New Orleans, La.	266
WSAX	Chicago Radio Laboratory	Chicago, Ill.	268	WYAM	Catholic University	Miami, Fla.	283
WSAY	Irving Austin (Port Chester Chamber of Commerce)	Port Chester, N. Y.	233	WYAW	Catholic University	Washington, D. C.	236

Canadian Stations

CFAC	Calgary Herald	Calgary, Alberta	430	CHCM	Riley & McCornack	Calgary, Alberta	415
CFCA	Star Print. Prtg. Co.	Toronto, Ontario	400	CHCS	The Hamilton Spectator	Hamilton, Ont.	420
CFCH	Marconi Wireless Teleg. Co. of Canada	Montreal, Quebec	440	CHYC	Northern Electric Co.	Montreal, Quebec	410
CFCH	Abitibi Power & Paper Co.	Iroquois Falls, Ont.	400	CJCA	Edmonton Journal	Edmonton, Alberta	450
CFCK	La Cie de L'Evenement	Quebec, Quebec	410	CJCC	London Free Press Prtg. Co.	London, Ont.	430
CFCK	Radio Supply Co.	Edmonton, Alberta	410	CJCD	T. Eaton Co.	Toronto, Ont.	410
CFCL	Centennial Methodist Church	Victoria, British Col.	400	CJCE	Sprott-Shaw Radio Co.	Vancouver, B. C.	420
CFCN	W. W. Grant Radio (Ltd.)	Calgary, Alberta	440	CJCI	Maritime Radio Corp.	St. John, New Brunswick	400
CFCC	Radio Specialties (Ltd.)	Vancouver, B. C.	450	CJCM	J. L. Phillippe	Mont Joli, Quebec	430
CFCR	Laurentide Air Service	Sudbury, Ont.	410	CJCN	Simons Agnew & Co.	Toronto, Ont.	410
CFCW	The Radio Shop	London, Ont.	420	CJCS	Evening Telegram	Toronto, Ont.	430
CFDC	Sparks Co.	Nanaimo, B. C.	430	CKAC	La Presse Pub. Co.	Montreal, Quebec	430
CFQC	The Electric Shop (Ltd.)	Saskatoon, Saskatchewan	400	CKCD	Vancouver Daily Province	Vancouver, B. C.	410
CFRC	Queens University	Kingston, Ontario	450	CKCE	Canadian Independent Telephone Co.	Toronto, Ont.	450
CFUC	University of Montreal	Montreal, Quebec	400	CKCK	Lester Pub. Co.	Regina, Saskatchewan	420
CHAC	Radio Engineers	Halifax, Nova Scotia	400	CKCO	Ottawa Radio Association	Ottawa, Ont.	440
CHBC	Albertan Publishing Co.	Calgary, Alberta	410	CKCX	P. Burns & Co.	Calgary, Alberta	445
CHCB	Marconi Company	Toronto, Ont.	410	CKCL	Wilkinson Electric Company	Calgary, Alberta	400
CHCD	Canadian Wireless & Elec. Co.	Quebec, Quebec	410	CKOC	Wentworth Radio Supply Co.	Hamilton, Ont.	410
CHCE	Western Canada Radio Sup. (Ltd.)	Victoria, B. C.	400	CKV	Manitoba Telephone System	Winnipeg, Manitoba	450
CHCL	Vancouver Merchants Exchange	Vancouver, B. C.	440	CNRO	Canadian National Railways	Ottawa, Ont.	435

Cuban Stations

PWX	Cuban Telephone Co.	Habana	400	2K	Alvara Daza	Habana	200
2DW	Pedro Zayas	Habana	300	2HS	Julio Power	Habana	180
2AB	Alberto S. de Bustamante	Habana	240	2OL	Oscar Collado	Habana	290
20K	Mario Garcia Velez	Habana	360	2WW	Amadeo Saenz	Habana	210
2BY	Frederick W. Borton	Habana	260	SEW	Leopoldo V. Figueroa	Colon	360
2CX	Frederick W. Borton	Habana	320	6K W	Frank H. Jones	Tuinucu	340
2EV	Westinghouse Elec. Co.	Habana	220	6K X	Frank H. Jones	Tuinucu	275
2TW	Roberto E. Ramires	Habana	230	6CX	Antonio T. Figueroa	Cienfuegos	170
2HC	Heraldo de Cuba	Habana	275	6DW	Eduardo Terry	Cienfuegos	225
2LC	Luis Casas	Habana	250	6BY	Jose Ganduxe	Cienfuegos	300
2KD	E. Sanchez de Fuentes	Habana	350	6AZ	Valentin Ullivarri	Cienfuegos	200
2MN	Fausto Simon	Habana	270	8BY	Alberto Lovelo	Stgo. de Cuba	250
2MG	Manuel G. Salas	Habana	280	8FV	Andres Finnet	Stgo. de Cuba	225
2JD	Raul Perez Falcon	Habana	150	8DW	Pedro C. Anduz	Stgo. de Cuba	275

British Stations

2LO	London	365	5NO	Newcastle	400
51T	Birmingham	475	5SC	Glasgow	420
5WA	Cardiff	355	2BD	Aberdeen	495
6BM	Bournemouth	385	6SL	Sheffield (relay station)	303
2ZY	Manchester	375			

French Stations

YN	Lyon	740	8AJ	Paris	1,780
FL	Paris (Eiffel Tower)	2,600	ESP	Paris	459

Do You Want More Information About Up-to-Date and Reliable Radio Products ?

RADIO AGE is full of advertisements and articles about the latest and most dependable radio products. Usually, when a fan is interested in a particular article, he wants all the information and descriptions he can get.

To accommodate its readers, RADIO AGE is offering to save them effort and expense by notifying advertisers and non-advertising manufacturers to mail specified literature.

Just clip the coupon at the right and mail it to RADIO AGE, with stamps to cover cost of catalogs or other literature desired from advertiser. We will write the letters for you, thus assuring you of prompt attention from the manufacturer.

There is no charge to readers for this service.

CLIP THIS COUPON

Mfgs'. Information Dept.

RADIO AGE,

506 N. Dearborn St., Chicago.

Please send me literature and information regarding (product)

.....made by (mfr.)

.....for which I

enclose.....in stamps to cover mailing.

Name

Address

Is Manufacturer advertiser in RADIO AGE?.....



FREE THIS GENUINE A. R. E. TWIN SUPERDON



No matter what your present occupation is, I can qualify you in a few weeks time to write your own income ticket in the fascinating, fast-growing, big-pay, long-profit field of Radio! And not only am I able to give you a better, more complete knowledge of Radio itself, but I will show you how to apply your knowledge to turn it into big money quickly. \$2,000 to \$10,000 a Year!

Millions of dollars a year are now being divided among radio men not so well trained as I propose to train you. You will command \$2,000 to \$10,000 a year salary or you can take it in profits from a real business all your own. I will show you.

- **I. J. MENDELS**
- In my 16 yrs. experience, I have met and coped with every electrical and radio problem.
- I have educated thousands for the better paying positions in radio manufacturing and have taught in one of the world's largest technical schools.
- **Fascinating New Profession**
- I am not going to make you a mere radio mechanic. I will train you to handle the big problems of Radio as well, because that's where the big money lies. You will be qualified in every branch of radio.
- **Learn Quickly—At Home**
- Under my personal direction you will learn quickly at home—in spare time. Don't wait to think this over. Mail in the coupon at once—and when you have all the facts before you, then give serious thought to my offer and your future.
- **The Wonderful SUPERDON**
- A high powered advanced design broadcast receiver. Gets all stations within 3000 mile circle. Mail the coupon Now for full details of this wonderful instrument and how to get it FREE. Mail the coupon Now! Today! © 1924 A. R. E.
- **IRWIN J. MENDELS** Director, AMERICAN Radio Engineers 646 N. Michigan Ave., Dept. 65, Chicago

MAIL THIS COUPON

IRWIN J. MENDELS, Director, AMERICAN Radio Engineers 646 N. Michigan Ave., Dept. 65, Chicago
Send me your big catalog and full particulars of your complete course of training. Also tell me more about the A. R. E. Twin Superdon Long Distance Receiver and how I can get it FREE.

Name.....
Address.....
City..... State.....

A Manufacturers' International Exposition
Under the Direction of James F. Kerr
A MAMMOTH SPECTACLE OF SCIENTIFIC ACHIEVEMENT

The FIRST
RADIO WORLD'S FAIR
Madison Square Garden
SEPT. 22 to 28 Monday to Sunday Night
INCLUSIVE
1 P.M. UNTIL 11 P.M.

Extraordinary Features Daily!

A Manufacturers' Exposition

WHICH WILL BE ATTENDED BY THE PRINCIPAL RADIO JOBBERS AND DEALERS OF THE UNIVERSE

De Luxe Exhibits By Nationally Known American Manufacturers

Representative Displays By The Famous Manufacturers Of
ENGLAND ☞ FRANCE ☞ BELGIUM
ITALY ☞ SWITZERLAND & AUSTRIA

Blanks For The Big Amateur Set Builder's Contest Are Now Ready
Six Silver Trophies and Twenty-five Cash Prizes.
No Entry Fee.

Send in your name without delay.

Business Office
Hotel Prince George
New York City.

Direction of
U. J. HERRMANN
and
JAMES F. KERR

PATENTS

To the Man with an Idea

I offer a comprehensive, experienced, efficient service for his prompt, legal protection and the development of his proposition.

Send sketch of model and description, for advice as to cost, search through prior United States patents, etc. Preliminary advice gladly furnished without charge.

My experience and familiarity with various arts frequently enable me to accurately advise clients as to probable patentability before they go to any expense.

Booklet of valuable information and form for properly disclosing your idea free on request. Write today.

RICHARD B. OWEN, Patent Lawyer
81 Owen Bldg., Washington, D. C.
2278-M Woolworth Bldg., N. Y. City

IF YOU WANT REAL RADIO ADVICE—

Radio Age Annual, the best hookup book, and one year's subscription—\$3. If you want this double bargain sign the coupon and mail at once. Send price by check, currency or money order. If by check add five cents for exchange. Clip the coupon at the right.

Radio Age, Inc.,
500 North Dearborn Street
Chicago

Gentlemen: Please send me by return mail your illustrated Radio Age Annual, containing more than 100 big pages of hookups and instructions and also send me Radio Age, The Magazine of the Hour, for one year. I enclose \$3. This will give me a one dollar book and a \$2.50 subscription at a saving of fifty cents. Please start my subscription with the.....number.

Name.....
Street Address.....
City.....
State.....

If book alone is desired, mark cross here and enclose \$1.00. If subscription only, mark cross here and enclose \$2.50.

Department of RADIO ENGINEERING

Radio Age Institute Tests




Look for the Approval Seal


The above approval seal will be furnished free of charge by RADIO AGE, and any article bearing this seal has been approved by the Institute Laboratory.

We will be pleased to receive and test any materials that are offered on the market and give them our endorsement where they meet all Institute tests. Send materials to RADIO AGE INSTITUTE, 504 N. Dearborn St., Chicago.

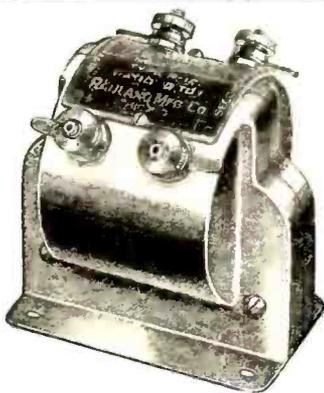
The following radio accessories have successfully passed RADIO AGE INSTITUTE tests for awards in September, 1924.



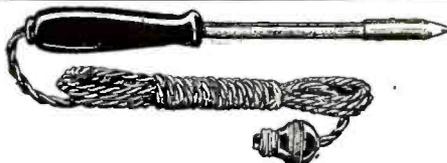Test No. 1. All American Transformers. More than 750,000 now in use. Include audio frequency transformers, power amplifying transformer, long wave radio frequency transformers. Made by Rauland Mfg. Co., Chicago. Tested and approved by RADIO AGE Institute.



Test No. 3. Security electrical soldering iron No. 25. Made especially for radio work. Designed to reach heretofore inaccessible points of complex sets. A $\frac{3}{8}$ " rod 5" long and with $\frac{1}{2}$ " removable copper tie 2" long. Heating element of nichrome wire at tip where heat is needed. Flows solder freely. Guaranteed for one year and passed by Radio Age Institute Tests. Made by Security Electric Mfg. Co., Chicago, Ill.

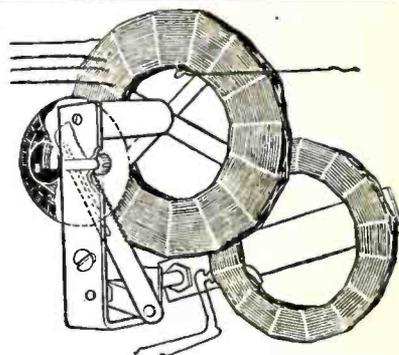

Pfanstiehl tuning unit—above.




Test No. 2. Radolene, flexible radio insulator. Known as the "liquid spaghetti" and something new in the field of radio and electrical insulation. A liquid to be applied with a brush; dries at once. Has withstood voltage puncture tests under severe conditions up to 800 volts. Passed by Radio Age Institute Tests. Made by Neumade Products Corp., 249 W. Forty-seventh St., New York.



Test No. 4. Allen Special Radio Soldering Paste. Manufacturers' tests with this item permanently eliminated 122 potential noise centers. Allen soldering paste is non-corrosive, acidless and protective. Guaranteed to eliminate noises, squeals and whistlings caused by loose connections. Volume increased and greater reception gained. Passed by Radio Age Institute Tests. Made by L. B. Allen Co., 4519 N. Lincoln St., Chicago.

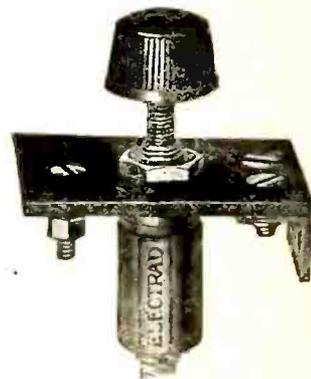Test No. 5. Pfanstiehl tuning unit—a variocoupler. Same advantages offered as variometer. Inductance tapped for 200 to 600 meters with ample overlap. Tested with unusually satisfactory results by Radio Age Institute. Made by Pfanstiehl Radio Co., Highland Park, Ill.



Test No. 6. Electrad Variable Grid Leak and condenser combined. A novel instrument that is attracting wide attention of fans who want compact parts. A perfect variable pressure Grid Leak, $\frac{1}{4}$ to 30 megohms, together with special .00025 mfd. condenser. Practically no hysteresis losses noticed in special Radio Age Institute tests. Metal parts gold plated. Mounted on a bakelite panel. Made by Electrad, Inc., 428 Broadway, New York.

RADIO AGE INSTITUTE will not place its approval on any radio set or accessory which will not meet the most exacting tests. A gummed stamp bearing the test number will be sent to all inventors or manufacturers whose products pass Institute tests.



Your Radio Troubles Ended for 30 Cents in Stamps

HOW LONG have you postponed making that favorite hookup of yours because you couldn't find reliable and clear diagrams? Too many sets have been spoiled and dispositions ruined because fans have followed inaccurate diagrams. If you are constructing a receiving set and need diagrams that will produce perfect results, RADIO AGE can help you by return mail.

We have laid aside a limited number of back issues of RADIO AGE for your use. Below are listed hookups and diagrams to be found in these issues. Select the ones you want and enclose 30 cents in stamps for each one desired.

An Index to the Best in Radio Hookups !

May, 1922

—How to make a simple Crystal Set for \$6.

September, 1922

—How to make a Regenerative Set at a low cost.
—Getting good results from Armstrong Super-Regenerative Set.

October, 1922

—How to make a Tube Unit for \$23 to \$37.
—How to make an Audio Frequency Amplifying Transformer.

November, 1922

—Photo-electric Detector Tubes.
—Design of a portable short-wave radio wavemeter.

May, 1923

—How to make the Erla single-tube reflex receiver.
—How to make a portable Reinartz set for summer use.

June, 1923

—How to build the new Kaufman receiver.
—What about your antenna?

December, 1923

—Building the Haynes Receiver.
—Combined Amplifier and Loud Speaker.
—A selective Crystal Receiver.

January, 1924

—Tuning Out Interference—Wave Traps—Eliminators—Filters.

The article which was announced from stations WJAZ, WOC and WOAW.

—A Junior Super-Heterodyne.
—Push-Pull Amplifier.
—Rosenbloom Circuit.

February, 1924

—How to make a battery charger.
—Improved Reinartz Circuit.
—Interference rejectors.
—Single Tube Heterodyne.
—How antenna functions.
—Adding two audio stages to selective receiver which began as a crystal set.
—Superdyne receiver.

March, 1924

—An Eight-Tube Super-Heterodyne.
—A simple, low loss tuner.
—Junior Heterodyne Transformers.
—A Tuned Radio Frequency Amplifier.
—How to make the Kopprasch Receiver.
—Adding Radio Frequency to the Variometer Set.
—Simple Reflex Set.

April, 1924

—An Efficient Super-Heterodyne (fully illustrated).
—Selecting the Right Receiver.
—A Ten-Dollar Receiver.
—Anti-Body Capacity Hookups.
—Radio Frequency Amplification.
—Reflexing the Three-Circuit Tuner.
—Index and first two instalments of Radio Age Data Sheets.

May, 1924

—Construction of a Simple Portable Set.
—An Ideal Set for the Summer Camper.
—A Traveling Man's Receiver.
—Radio Panels.
—Making a Basket-Weave Tuner.
—Third Instalment of Radio Age Data Sheets.

June, 1924

—Important Factors in the Construction of a Super-Heterodyne.
—A Universal Amplifier.
—A Sure Fire Reflex Set.
—Adding Radio and Audio to Baby Heterodyne.

July, 1924

—A Portable Tuned Impedance Reflex.
—Operating Detector Tube by Grid Bias.
—Getting the Most Out of Vacuum Tubes.
—A Three-Tube Wizard Circuit.
—Recharging Storage Batteries From a 32-Volt Lighting System.

August, 1924

—The Invisible Circuit.
—Breaking Into Radio Without a Diagram.
—The English 4-Element Tube.
—Filtered Heterodyne Audio Stages.
—An Audio Amplifier Without an "A" Battery.

RADIO AGE, Inc.

500-510 North Dearborn Street, Dept. 730, CHICAGO, ILL.

The PAUL REVERE of TODAY

TWENTY MILES in a single night. That was the wonderful broadcasting achievement of Paul Revere as he galloped from village to village, waking the countryside with the cry "the British are coming."

Just one-hundred and fifty years ago he made that broadcasting record. Today news flashed in any part of the country is heard almost instantly, not a mere twenty miles but thousands of miles away.

In every part of the United States Crosley Radio Receivers are bringing in far distant stations clearly and distinctly. Up to the minute news, concerts, music, lectures, are yours to enjoy right in your home when and from where you choose if you own a Crosley.

Keeping always at the head of the procession in improvements and innovations, the Crosley Radio Corporation has made it possible for every one to possess the maximum efficiency in radio reception at the minimum cost.

The Crosley Trirdyn 3R3 illustrated below is, in the opinion of many experts, the best radio receiver ever offered to the public at any price. The experiments of over 200 experts have shown that in ease of tuning, sharpness of signals and nicety of calibration, the Trirdyn cannot be excelled. Local stations may be easily tuned out even if very close to you, and far distant reception almost instantly brought in.

The Trirdyn 3R3 illustrated below is a three tube set incorporating tuned radio frequency amplification, regeneration and reflex. It has been proven to give the efficiency of a four or five tube set. And yet it is priced at only \$65 without batteries, tubes and headphones. The Trirdyn Special, set in a special solid mahogany cabinet which is made to house all the necessary accessories, may be had for only \$75.

Before you purchase a radio receiver, listen in on a Crosley Trirdyn.

For Sale by Good Dealers Everywhere.



Crosley Trirdyn, 3R3 \$65.00

Other Crosley Models

- Crosley 50** A one tube Armstrong Regenerative Receiver. Price, less accessories, \$14.00. A two stage amplifier, Crosley 50-A, may be added to it for only \$18.00, thus making a three tube set.
- Crosley 51** The two tube Armstrong Regenerative set that became the biggest selling receiver in the world in just 24 days. Price, less accessories, \$18.50. By adding the Crosley 51-A, a one stage amplifier at \$14.00, a three tube set may be formed.
- Crosley 50-P** The Crosley 50 in neat, strong, portable quartered oak cabinet for only \$18.00.
- Crosley 51-P** The Crosley 51 in compact leatherette portable case, completely self containing, at \$25.00.
- Crosley 52** A new Armstrong Regenerative three tube set assuring loud speaker volume on distant stations under almost any conditions. Price, without accessories, \$30.00.
- Crosley X-J** One of the best known and most popular four tube receivers on the market. A radio frequency set at \$55.00, without accessories.
- Crosley X-L** A rearrangement of the four tube Crosley X-J set in a beautiful mahogany console cabinet. Price, without accessories, \$120.00.

The Crosley Radio Corporation

Powel Crosley, Jr., President

963 Alfred Street,

Cincinnati, Ohio



All Crosley Regenerative Receivers licensed under Armstrong U. S. Pat. 1,113,149

CROSLEY
Better - Cost Less
Radio Products

The Crosley Radio Corporation owns and operates Broadcasting Station W. L. W.

MAIL THIS COUPON TODAY

The Crosley Radio Corporation,
963 Alfred St., Cincinnati, O.

Gentlemen: Please mail me free of charge your complete catalog of Crosley instruments and parts together with booklet entitled "The Simplicity of Radio"

Name _____

Address _____