

THE

# RADIO CONSTRUCTOR


Vol 21 No 4

**NOVEMBER 1967**  
**2/6**

A DATA PUBLICATION

RADIO . TELEVISION  
ELECTRONICS . AUDIO

## TRANSISTORISED TELEPHONE

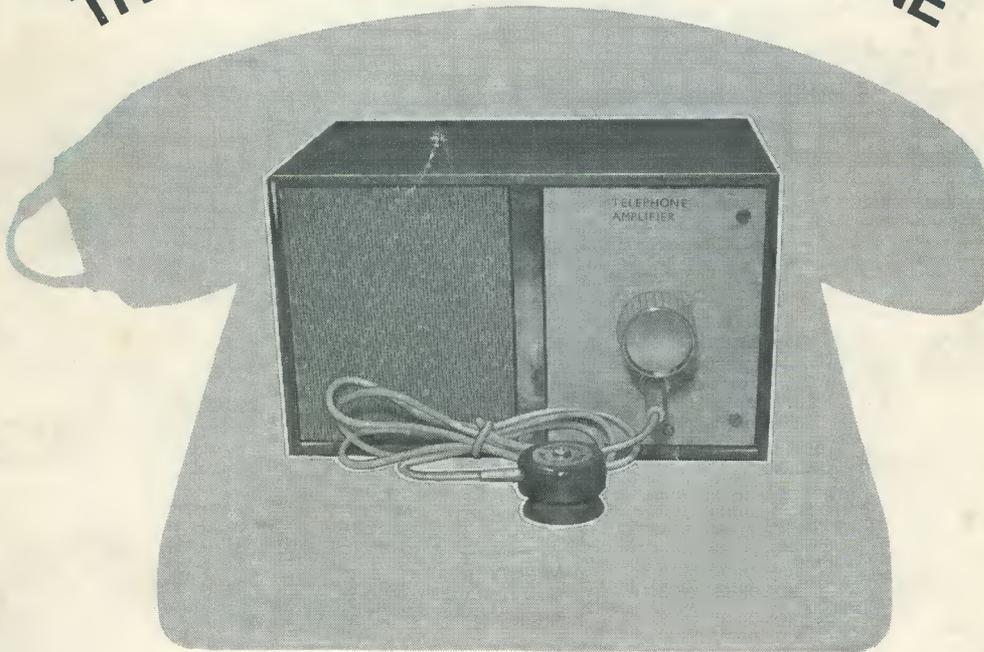

## AMPLIFIER

*Also featured*

Simple product  
Computer



Automatic Radio  
Control Keying Unit



F.W. Pre-amplifier  
converter

# Scottish Insurance Corporation Ltd

66-67 CORNHILL · LONDON · EC3



## TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) (i) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you write to the Corporation's Office a proposal will be submitted for completion.

---

Write for full details, quoting reference 5304, to:—

**THE MANAGER**  
**SCOTTISH INSURANCE CORPORATION LTD.,**  
**66-67 CORNHILL, LONDON E.C.2**

---



**Bargains  
for  
Autumn  
Building**

**TAPE WITH FREE TAPE WALLETS FROM TRS**

With each reel of this tape by an internationally famous manufacturer we give you a beautifully made wallet strongly made in simulated leather with space for a reel of tape each side. This is professional quality full frequency tape with metallised leader/stop foils. These library wallets solve once and for all the problems of storing tapes efficiently and tidily.

7in. reel,  
1800ft. with  
wallet  
**22/6**

5 1/2 in. reel,  
1200ft. or  
7in. reel  
1200ft. with  
wallet  
**17/6**


5in. reel,  
900ft. with  
wallet  
**12/6**

p. & p. 1/6 per reel

**TRS MULLARD AMPLIFIERS**

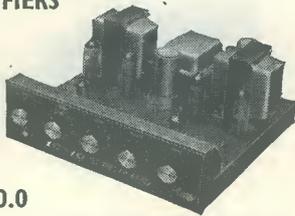**STEREO 10-10**

Valve amplifier to exact Mullard spec. With pre-amp tapped off transformer 3 and 15Ω, all controls, H.T. and L.T. outlet, mono, stereo and speaker phase switching. Complete with escutcheon, knobs, plugs, etc., Ready built.



**£20.00**

Kit form due shortly **£17.10.0**

**3-3 MONO**

3 valve 3W amplifier with controls, absolutely complete kit including panel, knobs, etc. **£7.10.0**

**5-10 MONO**

5 valve, 10W basic amplifier kit complete. **£9.19.6**  
(p. & p. 7/6)  
with passive control network and panel £11.19.6  
2 valve pre-amp kit **£6.12.6**

**GARRARD PLAYERS AND PLINTHS**

**LM.3000** Record Player with 9 T.A. Stereo Cartridge. **8 Gns.**  
Brand new as from factory.

**AT.60 Mk.II Deluxe** Auto-changer. **£11.19.6**  
Die-cast T/Table. Less cartridge.

**AT.60 Mk. I** with die-cast T/Table **£10.19.6**

**SP.25 De-luxe** single record player, less cartridge. Die cast. **9 1/2 Gns.**  
T/Table. Packing and carr. on any one of above, 7/6 extra.

Plinths. The ideal mounting for Units offered here. Will readily suit any hi-fi set-up. Teak finish with soft plastic dust cover. Packing and carriage 5/-.  
Clear-view rigid plastic cover 5/6 (p. & p. 3/6).

Garrard Cartridges. Hi-fi quality turnover mono and stereo cartridges. Mono from 15/- Stereo from **25/-**  
All post free.

**VEROBOARD**—All standard sizes including 2 1/2 in. x 5 in. 3/8; 2 1/2 in. x 3 1/2 in. 3/4; 3 1/2 in. x 5 in. 5/2; 3 1/2 in. x 3 1/2 in. 3/9; 2 1/2 in. x 1 1/2 in. 12/6. All accessories and tools in stock.

**RESISTORS**—Modern ratings, full range 10 ohms to 10 meg-ohms. 10% ± 1W, 4d. each; 20% 1W, 6d. each; 2W, 9d. each; 5% Hi-stab. 1/2W, 5d. each; 1W, 6d. each; 1.2-10 meg. 10% 1/2W, 4d. each; 1/2W, 5d. each. 1% Hi-stab. 1/2W, 1/6 each (below 100Ω, 2/- each).

**WIREWOUND RESISTORS**—25Ω to 10kΩ 5W, 1/6 each; 10W, 1/9 each; 15W, 2/3 each.

**CONDENSERS**—Silver Mica. All values 2pF to 1,000 pF, 6d. each. Dico ceramics 9d. Tub. 450V T.C.C., etc. 0.001-0.01mF, 10d. each; 0.1-350V, 10d. each; 0.02-0.1mF, 500V, 1/- each. T.C.C. 350V 0-25, 1/9 each; 0.5, 2/- each.

**CLOSE TOL. S/MICAS**—10% 5-500pF, 9d.; 600-5,000pF, 1/-; 1% 2-100pF, 11d.; 100-250pF, 1/2; 270-800pF, 1/-; 800-5,000pF, 2/-.

**ALUMIN. CHASSIS**—18g. Plain undrilled, folded four sides, 2in. deep, 6in. x 4in., 4/6; 8in. x 6in., 5/9; 10in. x 7in., 6/9; 12in. x 6in., 7/6; 12in. x 8in. 8/-, etc.

**ALL SINCLAIR PRODUCTS STOCKED AS ADVERTISED**

**7 VALVE AM/FM RG REPLACEMENT CHASSIS**

A superbly powerful high performance instrument for the keenest enthusiasts. Provides tuning on long, medium and F.M. wavebands. Excellent sensitivity. Permeability tuning on F.M. Large clear dial, A.V.C., good neg. feedback, Magic eye, 3W output. A.C. 200/250V. Circuit diagrams available. Aligned, tested and ready for use (Carr. and insurance 7/6). **£13.19.6**

**OUR NEW  
LISTS**

feature more lines than ever at money saving prices. For latest issue please send 6d.

Please include S.A.E. with all enquiries.

**TRS RADIO COMPONENT SPECIALISTS** Established 1946

70 Brigstock Road, Thornton Heath, Surrey

01-684 2188. Hours 9 a.m.—6 p.m. 1 p.m. Wednesdays  
A few doors from Thornton Heath Stn. (S.R. Victoria section).

**BI-PAK SEMICONDUCTORS 8 RADNOR HOUSE 93/97 REGENT ST., LONDON W.1.**

**NEW AND TESTED VALUE PACKS**  
One 10/- pack of your own choice free with orders valued £4 or over.

- 2 Drift Trans. 2N1225 Germ. PNP 100 Mc/s. 10/-
- 6 Matched Trans. OC44/45/81/81D 10/-
- 16 Red Spot AF Trans. PNP 10/-
- 16 White Spot RF Trans. PNP 10/-
- 5 Silicon Rects. 3A 100-400 PIV 10/-
- 2 10A Silicon Rects. 100 PIV 10/-
- 2 OC139 Trans. NPN Switching 10/-
- 1 12A SCR 100 PIV 10/-
- 3 Sil. Trans. 28303 PNP 10/-
- 12 Assorted Computer Diodes 10/-
- 4 NPN Med. Speed Switching Trans. 10/-
- 4 Zener Diodes 250mV 3-12V 10/-
- 5 2G417 Trans. Eqvt. AF117 10/-
- 3 200 Mc/s Sil. Trans. NPN BS726/27 10/-
- 2 Bi-directional Trans. ASY66 PNP 10/-
- 3 Zener Diodes 400mV 33V 5% Tol. 10/-
- 4 High Current Trans. OC42 Eqvt. 10/-
- 2 Power Transistors I OC26 I OC35 10/-
- 5 Silicon Rects. 400 PIV 250mA 10/-
- 4 OC75 Transistors Mullard Type 10/-
- 3 NPN Silicon Trans. 70 Mc/s 10/-
- 1 Power Trans. OC22 100V 10/-
- 4 OA202 Sil. Diodes Sub-min. 10/-
- 2 Low Noise Trans. NPN 2N929/30 10/-
- 1 Sil. Trans. NPN VCB 100 ZT86 10/-
- 8 OA81 Diodes (CV448) 10/-
- 4 OC72 Transistors Mullard Type 10/-
- 4 OC77 Transistors Mullard Type 10/-
- 5 Metal Alloy Transistors Mat Type 10/-
- 4 Sil. Rects. 400 PIV 500mA 10/-
- 5 GET884 Trans. Eqvt. OC44 10/-
- 5 GET883 Trans. Eqvt. OC45 10/-
- 2 GET20 Germ. PNP Trans. with Heat-sink 10/-
- 3 VHF Sil. Epoxy Trans. NPN 100 Mc/s 10/-
- 2 2N708 Sil. Trans. 300 Mc/s NPN 10/-
- 5 GT41/45 Germ. Trans. PNP Eqvt. OC71 10/-
- 3 GT31 LF Low Noise Germ. Trans. PNP 10/-
- 6 IN914 Sil. Diodes 75 PIV 75mA 10/-
- 8 OA95 Germ. Diodes Sub-min. IN69 10/-
- 3 NPN Germ. Trans. NK1773 Eqvt. AC130 10/-
- 2 OC22 Power Trans. Germ. 10/-
- 2 OC25 Power Trans. Germ. 10/-
- 2 OC73 Mullard Trans. 10/-
- 4 AC128 Trans. PNP High Gain 10/-
- 2 AC127/128 Comp. pair PNP/NPN 10/-
- 10 Assorted Gold Bonded Diodes 10/-
- 6 TK22C Germ. Switching Trans. 10/-
- 3 2N1307 PNP Switching Trans. 10/-

- 20 Germ. Diodes General Purpose 10/-
- 7 CG62H Germ. Diodes Eqvt. OA71 10/-
- 3 AF116 Mullard Type Trans. 10/-
- 12 Assorted Germ. Diodes Marked 10/-
- 130 Amp Power Rectifier 100 PIV 10/-
- 4 AC126 Germ. PNP Trans. 10/-
- 5 1 Amp. Germ. Rect. 200 PIV 10/-
- 1 ORP61 Photo-conductive cell 10/-
- 4 Silicon Rects. 100 PIV 750mA 10/-
- 3 AF117 Trans. Mullard Type 10/-
- 7 OC81 Type Trans. 10/-
- 3 OC171 Trans. Mullard Type 10/-
- 3 2N2926 Sil. Epoxy Trans. 10/-
- 7 OC71 Type Trans. 10/-
- 2 GET9 Power Trans. 60VcB. 8A 10/-
- 25 Trans. Heatsinks fit TO18, SO12, etc. 10/-
- 1 TK400A Power Germ. Trans. ADY22 10/-
- 2 28701 Sil. Trans. Texas 10/-
- 2 BFY16 Sil. Trans. STC 10/-
- 2 Zener SZ2A150F, 15V 1W 10/-
- 3 BCY43 Sil. Trans. 100 Mc/s 10/-
- 3 12 Volt Zeners 400mV 10/-
- 2 GET571 Germ. Trans. OC28 10/-
- 3 BSY95A Sil. Trans. NPN 200 Mc/s 10/-
- 3 BC108 Sil. NPN High Gain Trans. 15/-
- 1 Zener Diode 25W 18 and 22V 15/-
- 2 2N910 NPN Sil. Trans. VCB100 Mc/s 15/-
- 2 1000 PIV Sil. Rect. 1.5A RS310 AF 15/-
- 3 High Volt AF Trans. PNP ACY17 15/-
- 3 BSY95A Sil. Trans. NPN 200 Mc/s 15/-
- 3 OC200 Sil. Trans. Mullard 15/-
- 2 Sil. Power Rects. BYZ13 15/-
- 1 Sil. Power Trans. NPN 100 Mc/s TK201A 15/-
- 6 Zener Diodes 3-15V Sub-min. 15/-
- 1 2N1132 PNP Epitaxial Planar Sil. Trans. 15/-
- 2 2N697 Epitaxial Planar Trans. Sil. 15/-
- 4 Germ. Power Trans. Eqvt. OC16/Mullard 15/-
- 1 Injunction Trans. 2N2646 Eqvt. D5E29 15/-
- 2 Sil. Trans. 200 Mc/s 60VcB ZT83/84 15/-
- 1 Sil. Planar Trans. NPN 100 Mc/s BSY25 15/-
- 1 Sil. Trans. IS104 150 Mc/s HFE 200 NPN 15/-
- 2 SCR 50 PIV IA TO-5 can 15/-
- 1 Tunnel Diode IN3720 (TDS) G.E. 15/-
- 1 Unijunction Trans. 2N2160 TO-5 can G.E. 15/-
- 2 Sil. Rects. 5A 400 PIV Stud Type 15/-
- 2 Mullard Trans. OC28/29 15/-
- 1 10A Sil. Stud Rect. 800 PIV 15/-
- 1 Tunnel Diode AEV11 1050 Mc/s STC 15/-
- 2 2N2712 Sil. Epoxy Planar HFE225 max. 15/-
- 1 2N1257 PNP Sil. Planar TO-5 can 15/-
- 6 BY100 Type Sil. Rects. 20/-

Minimum Order 10/- CASH WITH ORDER PLEASE. Add 1/- postage and packing per Order. GUARANTEED by return postal service. Overseas add extra for Airmail.

Our vast stocks change daily with hundreds of semiconductor bargains becoming available. Just send 2p to cover 3 months mailing of our latest stock lists, eqvt. charts, circuits, etc.

**BI-PAK EXCLUSIVE-SILICON TRANS.**

300 Mc/s NPN Planar Sim. 2N706

Price	2/-	1/9	1/6	1/3	1/9
Qty.	1-24	25-99	99-499	500-999	1000 up

**SILICON PLANAR DIODES.** 1/- (1-99); 10d. (100-499) 60 PIV 200mA, Sub-min. 9d. (500-999); 7d. (1000 up). ALL BRAND NEW—TESTED AND GUARANTEED. Full Data and List of possible Replacements available.

AF17	3/6	M	D	OA91	1/3
AF139	10/-	U	L	OA182	1/6
AFZ12	10/-	U	L	OA200	3/-
BC107	6/-	L	V	OA202	3/6
BC108	5/-	L	L	OC44	1/9
BFY50	10/-	L	I	OC45	1/9
BFY51	7/6	A	C	OC71	2/3
BFY52	10/-	R	C	OC73	3/-
OA5	10/-	A	E	OC76	3/-
OA10	1/9	D	S	OC81D	2/3
OA47	2/-	D	S	OC82D	2/3
OA70	1/9	O	S	OC170	2/6
OA79	1/3	BRAND	NEW	OC200	4/-
OA81	1/6			OC201	7/6
OA85	1/6			ORP12	8/6

**NEW—UNTESTED DEVICES—NEW**

120 Glass Sub-Min.	GERM. DIODES	10/-
50 Mixed Germ.	TRANSISTORS	10/-
20 Mixed Volts	ZENERS	10/-
30 NPN, PNP, MIXED	SILICON TRANS.	10/-
60 200mA Sub-Min.	SILICON DIODES	10/-
20 Germ. I Amp.	RECTIFIERS	10/-
40 Like OC81 AC 128	TRANSISTORS	10/-
10 2 Amp. Stud	SIL. RECTIFIERS	10/-
25 Sil. NPN, 200 Mc/s	TRANSISTORS	10/-
16 Top-Hat 750mA	SILICON RECT.	10/-
75 Germ. Diodes	GOLD BONDED	10/-
10 1 Amp. 50-400 PIV	SCR's	20/-

## AN EXCELLENT STEREO SYSTEM

A "Package Deal" saves you money



**GARRARD  
PLAYER  
AT-60**



**20+20W  
STEREO  
AMP.  
AA-22U**

**20+20W TRANSISTOR STEREO AMPLIFIER, Model AA-22U.** Outstanding performance and appearance. Kit **£39.10.0** (less cabinet).. Assembled **£57.10.0** Attractive walnut veneered cabinet **£25.0** extra.

**GARRARD AUTO/RECORD PLAYER, Model AT-60.** less cartridge **£14.12.10** With Decca Deram pick-up **£19.7.4** incl. P.T. Many other Garrard models available, ask for Lists.

**TRANSISTOR FM STEREO/MONO TUNER, TFM-IS** Styled to match amplifier above. Comprises TFM-T1 Tuning Heart **£5.16.0** incl. P.T. TFM-IS I.F. Amp. P.S. etc. **£19.2.0** Total Price Kit **£24.18.0** (less cabinet). Cabinet **£2.5.0** extra.

**COTSWOLD SPEAKER SYSTEMS.** Standard or M.F.S. cover 30 c/s - 20,000 c/s. 3 loudspeakers. Kit **£25.12.0**. Assembled and Finished **£33.4.0**.

## NEW! PORTABLE STEREO RECORD PLAYER, SRP-1

Kit **£27.15.0**

Assembled price on request



Automatic playing of 16, 33, 45 and 78 rpm records. All transistor—cool instant operation. Dual LP/78 stylus. Plays mono or stereo records. Suitcase portability. Detachable speaker enclosure for best stereo effect. Two 8in x 5in. special loudspeakers. For 220-250V a.c. mains operation. Overall cabinet size 15 $\frac{1}{2}$  x 3 $\frac{1}{2}$  x 10 $\frac{1}{2}$ in.

Compact, economical stereo and mono record playing for the whole Family—plays anything from the Beatles to Bartok. All solid-state circuitry gives room filling volume.



## ENJOY YOURSELF AND SAVE MONEY

Finished models provide years of superlative performances

### INSTRUMENTS

**3" LOW-PRICED SERVICE OSCILLOSCOPE, Model OS-2.** Compact size 5" x 7 $\frac{1}{2}$ " x 12" deep. Wt. only 9 $\frac{1}{2}$ lb. "Y" bandwidth 2 c/s-3 Mc/s  $\pm$ 3dB. Sensitivity 100mV/cm. T/B 20 c/s-200 kc/s in four ranges; fitted mu-metal CRT Shield. Modern functional styling.


Kit **£23.18.0** Assembled **£31.18.0**



OS-2


**5" GEN-PURPOSE OSCILLOSCOPE, Model 10-12U.** An outstanding model with professional specification and styling. "Y" bandwidth 3 c/s-4.5 Mc/s  $\pm$ 3dB. T/B 10 c/s-500 kc/s.

Kit **£35.17.6** Assembled **£45.15.0**

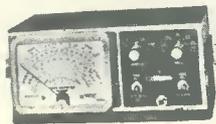

IM-13U

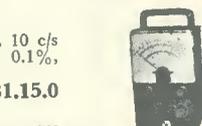**DE LUXE LARGE-SCALE VALVE VOLT-METER, Model IM-13U.** Circuit and specification based on the well-known model V-7A but with many worth-while refinements. 6" Ernest Turner meter. Unique gimbal bracket allows operation of instrument in many positions. Modern styling. Kit **£18.18.0** Assembled **£26.18.0**




V-7A

**AUDIO SIGNAL GENERATOR, Model AG-9U.** 10 c/s to 100 kc/s, switch selected. Distortion less than 0.1%, 10V sine wave output metered in volts and dB's.

Kit **£23.15.0** Assembled **£31.15.0**

**VALVE VOLTMETER, Model V-7A.** 7 voltage ranges d.c. volts to 1,500. A.c. to 1,500 r.m.s. and 4,000 peak to peak. Resistance 0.1  $\Omega$  to 1,000M  $\Omega$  with internal battery. D.c. input resistance 11M  $\Omega$ . dB measurement, has centre-zero scale. Complete with test prods, leads and standardising battery.

Kit **£13.18.6** Assembled **£19.18.6**

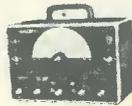

RF-1U

**MULTIMETER, Model MM-1U.** Ranges 0-1.5V to 1,500V a.c. and d.c.; 150 $\mu$ A to 15A d.c.; 0.2  $\Omega$  to 20M  $\Omega$ . 4 $\frac{1}{2}$ " 50 $\mu$ A meter. Kit **£12.18.0** Assembled **£18.11.6**

**R.F. SIGNAL GENERATOR, Model RF-1U.** Up to 100 Mc/s fundamental and 200 Mc/s on harmonics. Up to 100mV output. Kit **£13.18.0** Assembled **£20.8.0**

**SINE/SQUARE GENERATOR, Model IG-82U.** Freq. range 20 c/s-1 Mc/s in 5 bands less than 0.5% sine wave dist. less than 0.15 $\mu$  sec. sq. wave rise time.

Kit **£25.15.0** Assembled **£37.15.0**

VISIT THE HEATHKIT CENTRE Telephone No. 01-636 7349  
233 TOTTENHAM COURT ROAD, LONDON W.1  
Open Monday to Friday 9 a.m.-5.30 p.m. Saturday 9 a.m.-1 p.m.

OPENING 24th October, 1967— THE HEATHKIT CENTRE  
17-18 ST. MARTIN'S-HOUSE, BULL RING, BIRMINGHAM

### Complete your motoring pleasure with this outstanding CAR RADIO, Model CR-1



Will give you superb LW and MW entertainment wherever you drive. Tastefully styled to harmonise with any car colour scheme. Available for your convenience in two separate parts, RF Amp. Kit **£1.13.6** incl. P.T. IF/AF Amp. Kit **£11.3.6**

Total Price Kit (excl. Loudspeaker) **£12.17.0** incl. P.T.  
8" x 5" Loudspeaker **£1.16.1** incl. P.T.

### TRANSISTOR RADIOS

**"OXFORD" LUXURY PORTABLE, Model UXR-2.** Specially designed for use as a domestic, car or personal portable receiver. Many features, including solid leather case. Kit **£14.18.0** incl. P.T.



UXR-2

**TRANSISTOR PORTABLE, Model UXR-1.** Pre-aligned I.F. transformers, printed circuit. Covers L.W. and M.W. Has 7" x 4" loudspeaker. Real hide case. Kit **£12.11.0** incl. P.T.



UXR-1

**JUNIOR EXPERIMENTAL WORKSHOP Model EW-1.** More than a toy! Will make over 20 exciting electronic devices, incl: Radios, Burglar Alarms, etc. 72 page Manual. The ideal present! Kit **£7.13.6** incl. P.T.

### STEREO TRANSISTOR FM TUNER

(Mono version also available)

14 transistor, 5 diode circuit. Tuning range 88-108 Mc/s. Designed to match the AA-22U Amplifier. Available in separate units, can be built for a total price.

TFM-IS Kit (Stereo) **£24.18.0** incl. P.T.

TFM-IM Kit (Mono) **£20.19.0** incl. P.T.

Cabinet extra **£2.5.0**.



FM Tuner

### SEE HOW EASY-IT-IS TO BUILD ANY HEATHKIT MODEL YOURSELF

Full details of manual only purchase scheme in latest catalogue. Remember all Heathkit models are fully guaranteed.

## NEW! STEREO AMPLIFIER, TSA-12

12 x 12 watts output.

Kit £30.10.0 less cabinet

Assembled £42.10.0

Cabinet £2.5.0 extra



### FOR THIS SPECIFICATION

• 17 transistors, 6 diode circuit •  $\pm 1$ dB, 16 to 50,000 c/s at 12 watts per channel into 8 ohms • Output suitable for 8 or 15 ohm loudspeakers • 3 stereo inputs for Gram, Radio and Aux. • Modern low silhouette styling • Attractive aluminium, golden anodised front panel • Handsome assembled and finished walnut veneered cabinet available • Matches Heathkit models TFM-1 and AFM-2 transistor tuners.

Full range power . . . over extremely wide frequency range. Special transformerless output circuitry. Adequately heat-sunk power transistors for cool operation—long life. 6 position source switch.

FULL SPECIFICATION SHEET AVAILABLE

## NEW! STEREO TAPE RECORDER, STR-1

Fully portable—own speakers

Kit £45.18.0

Assembled price on request

### FOR THIS SPECIFICATION

channel • 18 transistor circuit for cool, instant and dependable operation • Moving coil record level indicator • Digital counter with thumbwheel zero reset • Stereo microphone and auxiliary inputs and controls, speaker/headphone and external amplifier outputs . . . front panel mounted for easy access • Push-button controls for operational modes • Built-in stereo power amplifier giving 4 watts rms per channel • Two high efficiency 8" x 5" speakers • Operates on 230V a.c. supply.

Versatile recording facilities. So easy to build—so easy to use.

FULL SPECIFICATION SHEET AVAILABLE



## Build Britain's Best Electronic Kits

No special Kit-building skills or Electronic Knowledge required



### Low-priced STEREO FM RADIO



FM  
TUNER  
FM-4U



STEREO  
DECODER  
SD-1

**HI-FI FM TUNER. Model FM-4U.** Available in two units. R.F. tuning unit (£2.15.0 incl. P.T.) with I.F. output of 10.7 Mc/s, and I.F. amplifier unit, with power supply and valves (£13.13.0). May be used free standing or in a cabinet. Total Kit £16.8.0 (Multiplex adapter available. as extra.)

**STEREO DECODER. Model SD-1.** Converts FM Mono receivers to stereo at low-cost. Styled to match Heathkit models FM-4U and AFM-1 Tuners. Kit £8.10.0 Assembled £12.5.0



SSU-1

### SPEAKER SYSTEMS

**HI-FI SPEAKER SYSTEM, Model SSU-1**  
Ducted-port bass reflex cabinet in the white: Two speakers, vertical or horizontal models with legs. KIT £12.12.0, without legs, KIT £11.17.6 incl. PT.



**AVON MINI SPEAKER SYSTEM**  
6 1/2" Bass, 3 1/2" Treble speakers and crossover unit. Kit £4.18.0 incl. PT. Beautiful. Walnut veneered fully-finished cabinet, £8.18.0, Total price Kit £13.16.0 incl. PT.

### "AMATEUR" EQUIPMENT

**THE "MOHICAN" GENERAL COVERAGE RECEIVER. Model GC-1U.** With 4 piezo-electric transmitters, variable tuned B.F.O. and Zener diode stabiliser, this is an excellent fully transistorised general purpose receiver for Amateur and Short wave listeners. Printed circuits, telescopic aerial, tuning meter and large slide-rule dial. Kit £37.17.6 Assembled £45.17.6


**AMATEUR BANDS RECEIVER. Model RA-1.** To cover all the Amateur Bands from 160-10 metres. Many special features, including: half-lattice crystal filter; 8 valves; signal strength "S" meter; tuned R.F. Amp. stage. Kit £39.6.6 Assembled £52.10.0

**160-10M TRANSMITTER. Model DX-100U.** Careful design has achieved high performance and stability. Completely self-contained. Kit £81.10.0 Assembled £106.15.0

**COMMUNICATIONS TYPE RECEIVER. Model RG-1.** A high performance, low cost receiver for the discriminating listener. Frequency coverage: 600 kc/s-1.5 Mc/s and 1.7 Mc/s-32 Mc/s. Kit £39.16.0 Assembled £53.0.0



GC-1U

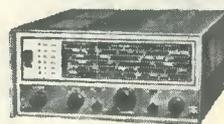

RG-1

### Low-cost 3 + 3W Transistor Stereo Amplifier, TS-23



Incorporating all the essential features for good quality sound reproduction from record, radio and other sources. 16 Transistor, 4 diode circuit. Good frequency response 6 position selector switch. Modern slim line styling.

Kit (less cabinet) £17.15.0

Kit (with handsome finished cabinet) £18.19.0



Send for this Catalogue . . .

. . . it's FREE!

36 pages packed with Britain's largest selection of electronic Kits. Mail coupon or write:

**DAYSTROM LTD., Dept. RC-11 GLOUCESTER. Tel. 20217.**

To DAYSTROM LTD., GLOUCESTER

Please send me FREE BRITISH CATALOGUE   
Please send me details of models

Please send a FREE Catalogue to my friend

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

Name \_\_\_\_\_  
Address \_\_\_\_\_

RC-11

RC-11

# REGULATED SUPPLY FOR TRANSISTOR CIRCUIT ASSEMBLY AND TEST

- All solid-state construction
- 0-25V DC. 0-0.5 A. 0.7 A. Limiter
- Just £19.18.6 in kit form

Another fine example from the professional looking Knight-kit range of test equipment—the KG-661 regulated power supply for low-voltage, low-current transistor testing and servicing.

Both line and load variations are regulated for constant voltage and the ripple output is only 7 mV r.m.s. at full rated load. Silicon transistors are used throughout for temperature stability with generous heat sinks for long life. An automatic current limiter operates at 0.7 A (short circuited) to provide complete burnout protection.

Knight-kits are new to the U.K. and available from Electroniques. Full specifications on all the test equipment, which includes 'scopes, multimeters, signal generators and a vacuum tube voltmeter can be found in our FREE 64-page brochure. And there's also a wide range of Hi-Fi and general interest kits.

Knight-kits not only save you money but are fun and instructive to build. Performance specifications are fully guaranteed and for any problem, however small, our Service Department is ready to advise and assist. Credit terms are available if required.

Electroniques also stock a comprehensive range of technical publications, many of which are detailed in your brochure. The knowledge gained from circuit construction can thus be complemented with theory and operating principles in order to get the very best results from your equipment.



Please send me your FREE brochure K24 giving full details on the complete range of Knight-kits.

Send to ELECTRONIQUES (Prop. STC) Limited, Edinburgh Way, Harlow, Essex.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_



**knight-kit** by  
Quality Built-in, Built-up by you



electroniques

## THE MODERN BOOK CO

**The Practical Aerial Handbook.** By G. J. King. 35s. Postage 1s. 6d.

**Basic Theory and Application of Transistors.** U.S. Dept. Army. 10s. Postage 1s.

**Radio and Audio Servicing Handbook.** By G. J. King. 30s. Postage 1s. 6d.

**Colour Television Explained.** By W. A. Holm. 21s. Postage 1s.

**A Beginner's Guide to Television.** A Newnes Pub. 8s. 6d. Postage 6d.

**Transistors for Technical Colleges.** By L. Barnes. 25s. Postage 1s.

**101 Questions and Answers About Transistors.** By L. G. Sands. 21s. Postage 1s.

**Transistor Pocket Book.** By R. G. Hibberd. 25s. Postage 1s.

**Tape Recorder Servicing Manual.** By H. W. Hellyer. 63s. Postage 2s.

**Inter: GEC Transistor Manual.** 18s. Postage 2s.

**Inter: S.C.R. Manual 4th ed.** 25s. Postage 2s.

**Questions and Answers Electronics.** By C. Brown. 8s. 6d. Postage 6d.

**The Electronic Musical Instrument Manual.** By A. Douglas. 37s. 6d. Postage 1s.

**Multi-Channel Radio Control A Map.** Tech. Pub. 12s. 6d. Postage 9d.

**Transistor Electronic Organs for the Amateur.** By A. Douglas and S. Astley. 18s. Postage 1s.

**TV Fault Finding 405 625 Lines.** A Data Pub. 8s. 6d. Postage 6d.

**Questions and Answers Radio and Television.** By H. W. Hellyer. 8s. 6d. Postage 6d.

**Radio Valve Data 8th ed.** Compiled by "WW". 9s. 6d. Postage 1s.

We have the Finest Selection of English and American Radio Books in the Country

**19-21 PRAED STREET (Dept RC) LONDON W2**

Telephone PADdington 4185



# A NO-COMPROMISE HIGH-FIDELITY LOUDSPEAKER

Listen to a Q.14. Hear it in your own home. It is the result of long and thorough investigation into speaker design in order to produce one which would out-perform anything within pounds of its price. How far we have succeeded can be seen from the independently taken test report which compares excellently with loudspeakers over four times the price. The Sinclair Q.14 is uncommonly versatile, too. It can serve as a free-standing unit for bookshelf, etc., as a corner radiator, or be flush mounted in a multi-unit assembly. Power handling capacity is in excess of 14 Watts with remarkably smooth response between 60 and 16,000 c/s. Size  $9\frac{3}{4}$ " square x  $4\frac{3}{4}$ " deep, in black matt finish with solid aluminium bar embellishment and detachable plinth base.

SINCLAIR

# Q14

# £6.19.6

TRY IT IN YOUR OWN HOME—MONEY (INC. POSTAGE) REFUNDED IF NOT SATISFIED



## SINCLAIR MICROMATIC PRICE REDUCED

With sales and export orders for the Sinclair Micromatic breaking all records, we have changed over to new production methods to meet the ever-increasing demand for the world's smallest radio set. This has enabled us to effect dramatic economies in production costs. At the same time, we have appreciably improved the set's quality by supplying a magnetic earpiece with it, and what was superb performance before, now sounds better than ever. At the new prices, everyone is going to want the Micromatic. Order yours now for prompt delivery.

Kit complete with magnetic earpiece, solder and instructions, originally 59/6, now

# 49'6

Post Paid

Ready built with magnetic earpiece, originally 79/6 now

# 59'6

Post Paid

2 Mercury Cell long life batteries for either of above, each, 1/10d.


## SINCLAIR Z.12 12 WATT INTEGRATED HI-FI AMPLIFIER AND PRE-AMP

- Size  $3" \times 1\frac{3}{4}" \times 1\frac{1}{4}"$ .
- 8 special HF transistors.
- Ultra-linear class B output and generous neg. feedback.
- Response—15 to 50,000 c/s  $\pm 1$ dB.
- Output suitable for 3, 7.5 and 15 ohm loads. Two 3 ohm speakers may be used in parallel.
- Input—2mV into 2K ohms.
- Signal to noise ratio—better than 60dB.

USE IT FOR HI-FI, RADIO, MUSICAL INSTRUMENTS, INTERCOM, P.A., etc.



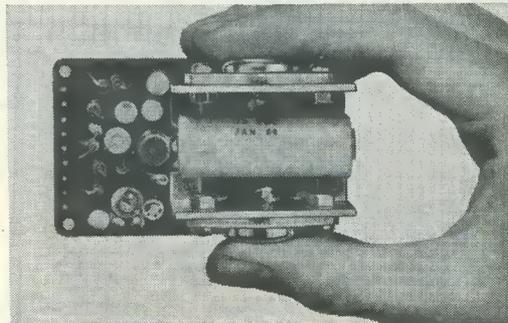**SINCLAIR RADIONICS LIMITED**  
22 NEWMARKET RD., CAMBRIDGE  
Telephone OCA3 52996



Ready built, tested & guaranteed with Z.12 manual

# 89'6

- 12 watt RMS continuous sine wave
- Ideal for battery operation

SINCLAIR MICRO-FM

7 Transistor Tuner/ Pocket Receiver. Needs no aligning when built. Complete kit.

# £5.19.6

STEREO 25

Pre-amp/Control Unit for two Z.12s in stereo, built.

# £9.19.6

PZ.3 Mains Power Unit.

# 79/6

**GUARANTEE** If you are not completely satisfied when you receive your purchase from us, your money will be refunded at once, in full and without question.

SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send

NAME


ADDRESS

for which I enclose cash/cheque/money order value £.....s.....d.....

RC11

NOW AVAILABLE . . .
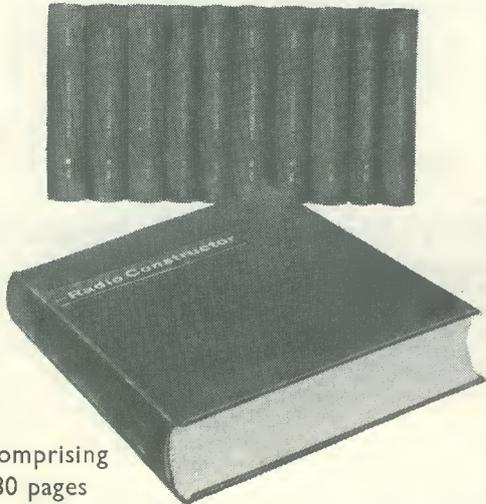
## BOUND VOLUME No. 20 of "The Radio Constructor" FOR YOUR LIBRARY



Comprising  
780 pages  
plus index

Volume 20 August 1966 to July 1967

**PRICE 32/6 Postage 4/6**

**Special discount of 10/- for regular readers**


Where the 12 monthly issues making up the volume are returned, the price is only 22/6 plus 4/6 postage

**BOUND VOLUME No. 19**  
August 1965 to July 1966  
*Limited number still available  
same prices as above*

Available only from:—

**Data Publications Ltd.**  
57 Maida Vale London W9

## BUILD THIS LOW-COST HI-FI

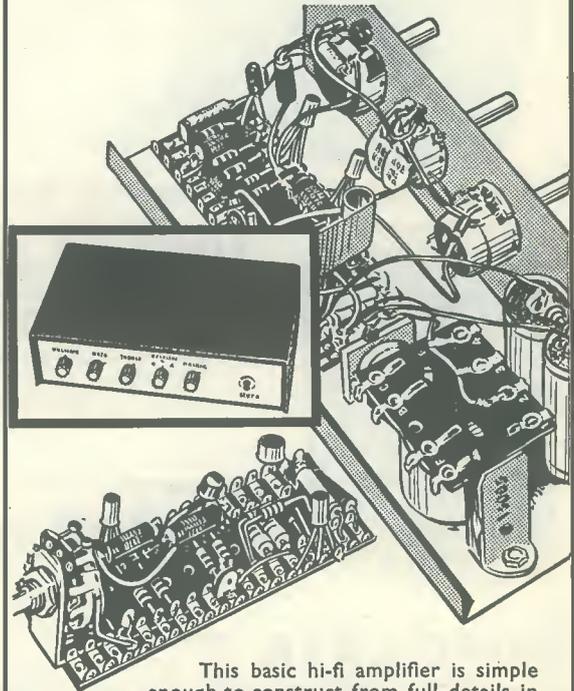

This basic hi-fi amplifier is simple enough to construct from full details in this issue of **PRACTICAL WIRELESS**. Input sensitivity 3mV; output 1 watt 30–50,000 c/s. A suitable pre-amp and a companion power amplifier, giving 5 or 15 watts into 15 or 3 ohms respectively, will follow on in this series.

— Also in this issue —

**I.C. F.M. TUNER** built on a printed circuit board.  
**MIDGET TRANSISTOR TRANSMITTER** using only two silicon planar transistors.  
**REPAIRING MOVING COIL METERS**—typical faults and their remedies.

# PRACTICAL WIRELESS

DECEMBER ISSUE OUT 3rd NOVEMBER. 2/6

# Fast Mail Order for the Amateur Radio Enthusiast!

## AERIAL EQUIPMENT

**TWIN FEEDER.** 300 ohm twin ribbon feeder similar K25, 8d. per yard. 75 ohm twin feeder, 6d. per yard. Post on above feeders and cable, 2/- any length.

**COPPER WIRE.** 14G, H/D, 140 ft., 30/-; 70ft., 16/- . Post and packing 3/3. Other lengths pro rata.

**FEEDER SPREADERS.** 6" Ceramic type F.S., 10d. each. Postage 2/6 up to 12.

**CERAMIC CENTRE PIECE** for dipoles, Type AT, 1/6 each. P. & P. 1/-.

**2 METRE BEAM, 5 ELEMENT W.S. YAGI.** Complete in box with 1" to 2 1/2" masthead bracket. Price 56/- . P. & P. 4/-.

**SUPER AERAXIAL.** 70/80 ohm coax. 300 watt very low loss, 2/3 per yard. 50 ohm 300 watt, 2/6 per yard. P. & P. 2/6.

**TOUGH POLYTHENE LINE,** type ML1 (100lb.), 2d. per yd. or 12/6 per 100 yds. Type ML2 (220lb.), 4d. per yd. or 25/- per 100 yds., ML4 (400lb.), 6d. per yd. ideal for Guys, L.W. Supports, Halyards, etc. Postage 1/6 on all line.

## MIDLAND AGENTS FOR

# EDDYSTONE

Receivers & Components

Transmitters, Receivers and

Sundry Equipment by

- KW ELECTRONICS
- HALSON
- T.W. ELECTRONICS
- CODAR RADIO
- PARTRIDGE

## NEW BOXED VALVES

3/6 each, 4 for 10/- . P. & P. 2/-.

TYPES		
6N7GT	6SF7	6AB7
6AC7	6F7	6SK7
6K7	U.10	6MSP4
Z21	Z22	KT41

**ABSORPTION WAVEMETERS,** 3.00 to 35.00 Mc/s in 3 Switched Bands. 3.5, 7, 14, 21 and 28 Mc/s. Ham Bands marked on scale. Complete with indicator bulb. A MUST for any Ham Shack. ONLY 25/- EACH. Post free.

**SHORT WAVE KIT,** 1 valve only, 45/- . Phones, Ant. and Batteries 40/- extra if required. Ideal for junior operator.

**VARIABLE CONDENSERS.** All brass with ceramic end plates and ball race bearings. 50pF, 5/9; 100, 6/6; 160, 7/6; 240, 8/6. Extension for ganging. P. & P. 2/-.

**SEALED RELAYS,** 12v. 105Ω Coil Type A. 4 Pole, C.O. 15/- . Type B.2 Pole, C.O. + 2 Pole Norm. on, 12/6. P. & P. 1/6.



At your service **G2AK, G3LAY, G3VVF**  
Please print your address. No. C.O.D. under £1.

The Widest Range in the Midlands

- ★ HIRE PURCHASE
- ★ PART EXCHANGE

## Chas. H. YOUNG Ltd.

170-172 Corporation Street,  
Birmingham 4

'phone 021-236 1635



SEMICONDUCTORS DISTRIBUTED EXCLUSIVELY BY

BI-PRE-PAK LTD., DEPT. E.  
222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
PHONE: SOUTHEAD (0702) 46344

## NEW FROM THE U.S.A. "TEXAS" Integrated Circuits

SN7360	Quadruple 2 Input Nand/Nor Gate	19/6
SN7430	8 Input positive Nand Gate	21/6
SN7302	Dual J-K Flip-Flop with pre-set	35/-
F.E.T'S.	Field Effect Transistors	
2N3822	'N' Channel 4-lead	15/-

No.	DESCRIPTION	PRICE
A1.	6—Silicon rectifiers BY100 type	20/-
A2.	10—Relays mixed types and voltages	20/-
A3.	20—Mixed marked and tested trans.	20/-
A9.	1—2N 174 real power trans. 80V 150W	20/-
A15.	2—Power Comp. Pair. AD161/2	20/-
B1.	50—Unmarked untested, trans., new	10/-
B2.	4—Solar cells, inc. Book of instructions	10/-
B3.	4—OAS gold bonded, diodes Mul-lard	10/-
B5.	7—Matched set, OC44, 45/81D/81 + diode	10/-
B6.	15—Red spot AF. trans. or white spot RF	10/-
B8.	2—Power trans. OC25/35 type	10/-
B9.	1—Light sensitive cell, ORP12 type	9/-
B10.	1—50V trans. germ. PNP latest type	10/-
B41.	1—Tunnel diode, AEY11, 1050 Mc/s	10/-
B24.	2—Sil. recs. 10 amp., 50-100 PIV	10/-
B42.	5—Switching trans. TK22C 3TC	10/-
C2.	1—Uni junction, 2N2160 or 2N2646	15/-
C4.	2—RF power trans., OC22 and BUY11	15/-
C31.	4—Sil. recs. 800 PIV 1/2 amp. top hat	15/-
C32.	2—Power trans. TK400A/NKT404 VCB64 IC 8 amp.	15/-
D18.	1—ORP60 type light sensitive cell	5/-

## WHY WASTE MONEY ON UNTESTED PACKS? OF SEMICONDUCTORS!

ALL THESE PRE-PAKS ARE TESTED AND GUARANTEED

40	PNP-NPN Silicon	TRANSISTORS 10/-	25	NPN 400 Mcs. Silicon	TRANSISTORS 10/-
40	Silicon Sub. Min.	DIODES 10/-	10	Silicon 750 mA Top Hat	RECTIFIERS 10/-
40	NPN Silicon	TRANSISTORS 10/-	40	NPN Silicon TO. 5. CAN	TRANSISTORS 10/-
75	Germanium Min.	DIODES 10/-	5	3 amp. Silicon 50-800 PIV.	STUD RECS. 10/-

GENUINE TRANSISTORS NOT REMARKS					
OC45	IF transistor	1/9	OA9	Equal to OAS	2/-
OC44	Osc. transistor	1/11	OC36	Power transistor (better than OC35)	7/6

TRANSISTORS	PRICE	TRANSISTORS	PRICE
AC107	6/-	BSY25	10/-
AC126	2/6	BSY26	5/-
AC127	2/6	BSY27	5/-
AC128	3/-	BSY28	5/-
ACY17	5/-	BSY29	5/-
AF14	3/-	OC41	2/6
AF115	3/-	OC71	2/6
AF117	4/-	OC72	2/6
AF118	3/6	OC73	5/-
AF119	3/6	OC81	2/6
AF178	10/-	OC83	4/-
ASY66	2/-	OC139	2/6
BC211	7/6	OC140	5/-
BFY50	15/-		

OC170...	2/6	2N1309	7/6
OC171...	4/-	25303	2/6
OC200...	5/-	POWER TRANSISTORS	
OC201...	8/-	OC20	10/-
2G301...	2/6	OC23	10/-
2G303...	2/6	OC25	8/-
2N697...	5/-	OC26	5/-
2N706...	5/-	OC28	5/-
2N711...	10/-	OC35	5/-
2N1302	4/-	DIODES	
2N1303	4/-	AA42	2/-
2N1304	5/-	OA10	2/-
2N1305	5/-	OA70	1/9
2N1306	6/-	OA79	1/9
2N1307	6/-	OAB1	1/9
2N1308	8/-	OAB2	2/-
		IN914	1/6

## FREE ★ ★

Packs of your own choice to the value of 10/- with all orders over £4.

SEND FOR OUR FREE LISTS AND CATALOGUE OF ALL OUR PRODUCTS. CHECK YOUR OWN EQUIVALENTS WITH OUR FREE SUBSTITUTION CHART.

NO CONNECTION WITH ANY OTHER FIRM  
MINIMUM ORDER 10/- CASH WITH ORDER  
PLEASE. Add 1/- post and packing per order.  
OVERSEAS ADD EXTRA FOR AIRMAIL.

## Great News ★

We now give a written guarantee with all our semi-conductors.



For the benefit of our customers who have catalogues dated earlier than February 1967 we set out below the new items that have been added.

	Price
<b>Books</b>	
B135A Fault Location Exercises in Radio and T.V. Servicing Vol. 2 ...	8/6
B31B Radio Circuits by Miller/Spreadbury ...	25/-
B31C "Reed Switches" F. R. Industrial Electronics ...	3/6
B78B Radio and T.V. Servicing—Electronics Servicing. (Specimen Answers to Intermediate Papers 1961-64) ...	8/6
<b>Capacitors. Metallized polyester 5% tolerance.</b>	
C77A 0.47µF 400V 31 x 15 mm ...	5/6
C77B 0.22µF 400V 26 x 12 mm ...	3/3
C77C 0.1µF 400V 19 x 11 mm ...	2/3
C77D 0.047µF 400V 16 x 10 mm ...	2/-
C77E 0.033µF 400V 16 x 8 mm ...	1/9
C77F 0.022µF 400V 14 x 7 mm ...	1/9
C77G 0.01µF 400V 14 x 5.5 mm ...	1/6
<b>Capacitors. Increased range of Cydon compression trimmers.</b>	
VC29LA MT31A/3 3-40pF ...	1/-
VC29LB MT31A/5 30-140pF ...	1/3
VC29LC MT31A/12 7-60pF 1 mm ...	1/5
VC29MA MT25/1 2.5-40pF ...	1/6
VC29MB MT25/2 3.5-70pF ...	1/6
VC29SA TP10 400-1250pF ...	2/6
VC29SB TP29 500-2000pF ...	2/10
<b>Kits</b>	
KT206A Printed Circuit Kit for photoelectric projects ...	39/6
KT206B Optical parts for use with above kit ...	19/6
<b>Rectifier</b>	
MR19A Contact-cooled rectifier 250V 100mA (bridge). 46 x 35 x 8 mm	15/-
<b>Sockets. Metal sockets to take coil pins.</b>	
ZA38A 4-mm sockets ...	6d.
ZA38B Standard pin sockets ...	6d.
<b>Soldering Irons</b>	
ES25A Weller "Marksman" soldering iron, 25 watt model SP25 ...	29/-
ES25B Kit containing the above iron, solder, 2 spare bits and soldering aid ...	38/-
ES25C Spare screw-in bits ...	3/-
ES25H Spare element ...	11/-
<b>Switches</b>	
WS152 Bulgin S319/D. SPST key switch with key removable in both positions ...	8/-
WS126 Bulgin SM357 SPCO "Push" switch ...	5/6
<b>Tape. Synchrotape, inexpensive British-made recording tape, complete with metallic stop-foils, coloured leaders and trailers (except for some 3in. sizes).</b>	
PAT33A 3in. 150ft. ... 4/9 PAT33J 5in. 900ft. ... 18/6	
PAT33B 3in. 225ft. ... 6/3 PAT33K 5in. 1200ft. ... 28/6	
PAT33C 3in. 300ft. ... 8/9 PAT33L 5 1/2in. 900ft. ... 18/6	
PAT33D 3in. 450ft. ... 13/9 PAT33M 5 1/2in. 1200ft. ... 22/6	
PAT33E 4in. 450ft. ... 12/- PAT33N 5 1/2in. 1800ft. ... 36/-	
PAT33F 4in. 600ft. ... 18/- PAT33P 7in. 1200ft. ... 22/6	
PAT33G 4in. 900ft. ... 27/6 PAT33Q 7in. 1800ft. ... 28/6	
PAT33H 5in. 600ft. ... 15/- PAT33R 7in. 2400ft. ... 48/-	
<b>Testgear</b>	
TG29 Signal tracer ...	26/3
TG30 Signal injector ...	26/3
<b>Thermistor</b>	
VA1077 Mullard ...	2/6
<b>Thyristors</b>	
SD33A SCRO5 4 amp 400-volt PIV (240-volt RMS) ...	45/-
SD33B SCRO6 10 amp 400-volt PIV (240-volt RMS) ...	70/-
<b>Transformer. Midget for transistor power supplies.</b>	
TM25A Osmor MT9. 9-0-9 volts at 80mA. 30 x 40 x 30 mm ...	10/9
<b>Transistor Mounting Kits.</b>	
TR47A Mullard 56239 insulating kit for AD161-AD162 etc. ...	8d.
<b>Twist Drills. High-speed twist drills for BA sizes; tapping and clearing.</b>	
TL47A No. 10 2 BA clear ...	2/2
TL47B No. 24 4 BA clear 2 BA tap ...	1/6
TL47C No. 31 6 BA clear 4 BA tap ...	1/3
TL47D No. 42 8 BA clear 6 BA tap ...	1/-
TL47E No. 50 8 BA tap ...	11d.
<b>Volume Controls. Our moulded track range VR18B have proved to be so superior to the ordinary carbon track types we have now greatly extended this range.</b>	
VR18B LOG. 5 K, 10 K, 25 K, 50 K, 100 K, 250 K, 500 K, 1 meg. ...	5/-
VR18C LIN. 100 ohms, 500 ohms ...	6/-
VR18D LIN. 5 K, 10 K, 25 K, 50 K, 100 K, 250 K, 500 K, 1 meg. ...	5/-
VR18E Ganged LOG. 1 K, 5 K, 10 K, 100 K, 500 K, 1 meg. ...	10/6
VR18F Ganged/DP, LOG. 1 K, 5 K, 10 K, 100 K, 500 K, 1 meg. ...	13/-

Now what of the future? Set out below are new items, already in stock, that will be going into the next reprint of the catalogue. We would particularly like to draw your attention to the first item (large value 1% tolerance capacitors) which we believe are rare.

Cat. No.	Capacity	D.C. Working Voltage	Tolerance	Price
2FG 25	.001	100	1%	1/3
2FG 27	.005	100	1%	1/9
2FG 29	.01	100	1%	2/3
2FG 31	.05	100	1%	2/6
2FG 33	.1	100	1%	3/-
2FG 35	.5	100	1%	6/-
2FG 37	1.0	63	1%	11/6

Cat. No.	Description	Price
E966	Pyrex Glass strain insulators, ...	5/6
VC40 D	Dilemin 2 gang 192 + 78 + 15pF trimmers 1/8 x 1/8 x 1/8	12/6
DL 53 B	Spindle Lock for pin. spindle ...	1/6
PK 78	5 amp 3 pin non reverse flex connector ...	2/6
PL 36	Sub miniature filament lamp 6V. 70mA. ...	7/9

Cat. No.	Makers No.	Coil	Resistance	Switching	Contacts	Price
WS153	CRI/A	18-30V	2.6K	S.P. normally open	200V .5A 10V	15/-
WS154	CRI/B	12-18V	560 ohms	"	"	15/-
WS155	CRI/C	9-12V	400 ohms	"	"	13/6
WS156	CRI/D	6-9 V	190 ohms	"	"	12/6

Relays (Keyswitch)	Cat. No.	Makers No.	Voltage	Switching	Price
WS159	MH2	1	6	2PDT ...	12/9
WS160	1051	6	6	5PDT ...	12/-
WS161	MH4	6	6	4PDT ...	16/-
WS162	MH2	12	12	2PDT ...	12/9
WS163	1051	12	12	5PDT ...	12/-
WS164	MH4	12	12	4PDT ...	16/-
WS165	Mk2	24	24	2PDT ...	17/9
WS166	Mk3	24	24	3PDT ...	19/3
ES20N	240V	Desoldering tool for printed circuit ...			84/-
WS133	Miniature toggle 25/64 x 5/16 x 1/4 SPDT ...				13/9
WS134	Miniature toggle 25/64 x 5/16 x 1/4 DPDT ...				27/3
WS174	Push Button switches Bank of 3 D.P. change over each button				11/-
WS175	Push Button switches Bank of 4 D.P. change over each button				13/6
TG39	V-T2 Meter Movement	50 microamps	2 1/2 scale		75/-
TG40	V-T2	100	"		75/-
TG41	V-T2	500	"		75/-
TG42	V-T2	1 milliamp	"		60/-
TG43	V-T2	5	"		67/6

All this will not interest you much of course if you do not possess a Home Radio Catalogue. But this can easily be remedied. Just fill in the coupon and send it to us with your cheque or p.o. for 9/6 (7/6 plus 2/- p. & p.) May we add that for good measure each catalogue contains 5 vouchers, each worth 1/- when used as directed.

Name..... BLOCK CAPS

Address.....

.....

.....

Home Radio Ltd., Dept. RC, 187 London Road, Mitcham, CR4 2YQ

# THE Radio Constructor



Incorporating THE RADIO AMATEUR

NOVEMBER 1967

Vol. 21 No. 4

Published Monthly (1st of Month)  
First Published 1947

Editorial and Advertising Offices  
57 MAIDA VALE LONDON W9

Telephone CUNningham 6141  
Telegrams Databux, London

© Data Publications Ltd., 1967. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

**Annual Subscription** 36s. (U.S.A. and Canada \$5) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

**Queries.** We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. Queries should be submitted in writing and accompanied by a stamped addressed envelope for reply.

**Correspondence** should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

**Opinions** expressed by contributors are not necessarily those of the Editor or proprietors.

**Production.**—Letterpress/contact litho.

Published in Great Britain by the Proprietors and Publishers  
Data Publications Ltd. 57 Maida Vale London W9  
Produced by Quicks the Printers,  
Clacton-on-Sea, England

Short Wave Pre-Amplifier Converter Unit <i>by G. A. Stanton, G3SCV</i>	202
Simple Product Computer (Suggested Circuit No. 204) <i>by G. A. French</i>	210
News and Comment	214
Automatic Radio Control Keying Unit <i>by M. W. Shores, N.Z.I.S.T.</i>	216
Trade News	219
Electronic Oscilloscope Switch <i>by L. J. Aston</i>	220
Scintillation Detectors and Photomultiplier Tubes <i>by M. J. Darby</i>	223
Transistorised Telephone Amplifier <i>by B. T. Hathaway</i>	224
Lightweight Whip Aerial for 160-Metres Mobile <i>by W. E. Thompson, G3MQT</i>	231
Can Anyone Help?	233
Understanding Radio (Phase-Splitter Circuits) <i>by W. G. Morley</i>	234
In Your Workshop	238
Stabilised Variable Mains Supply Unit <i>by F. Neville Hart</i>	244
Radio Topics <i>by Recorder</i>	247

# Short Wave Converter

This simple unit operates both as a pre-amplifier from 1.6 to 5.3 Mc/s, and as a converter from 10.5 to 31.5 Mc/s. A neat circuit technique enables either function to be selected without complex switching. The output for the main receiver is at low impedance and is given by a cathode follower.

THE SIMPLER TYPES OF SHORT-WAVE RECEIVER—including many commercial broadcast sets—suffer from a variety of shortcomings. These include lack of sensitivity and selectivity on the lower ranges, and a proneness to image interference on the higher ranges. Tuning is often extremely critical and on the higher ranges almost impossible. The unit to be described has been designed to overcome these failings, and is both relatively simple to construct and low in cost.

The unit is in fact a dual purpose one. On the lower short waves (i.e. 1.6 Mc/s to 5.3 Mc/s) it functions as a pre-amplifier and gives a useful boost to signals received on these frequencies. On the higher range (10.5 to 31.5 Mc/s) it functions as a converter. Signals on this range are converted to 1.6 Mc/s, to which frequency the main receiver is then tuned. In this mode of operation the main receiver becomes an "i.f. strip" and the whole arrangement works as a double superhet with all the

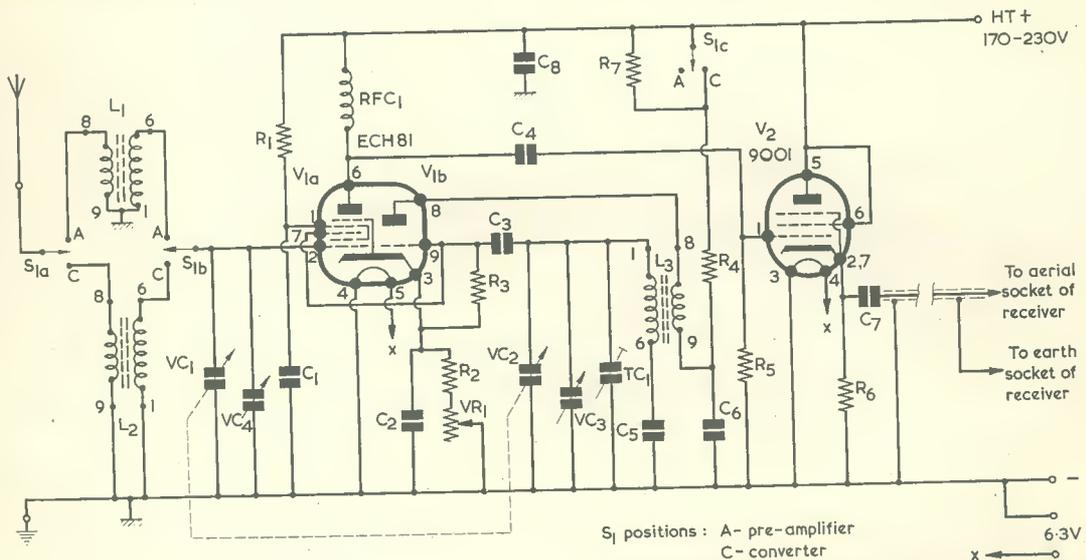


Fig. 1. The circuit of the Pre-Amplifier/Converter Unit. In some instances, this may obtain heater and h.t. power from the main receiver to which its output connects

# Pre-amplifier

## Unit

by

G. A. Stanton G3SCV

advantages that this implies. On the higher band, tuning is entirely carried out on the converter, and as this includes band-spread facilities, becomes much more easy.

### Circuit Operation

The circuit of the unit is given in Fig. 1. When functioning as a pre-amplifier, switch  $S_{1(a)(b)(c)}$  is set to position A, whereupon signals are fed from the aerial to the grid of  $V_{1(a)}$  via the coupling and tuned windings of coil  $L_1$ . This coil, in conjunction with  $VC_1$  and  $VC_4$ , covers 1.6 to 5.3 Mc/s.  $V_1$ , it will be seen, is a triode heptode. On the range under

consideration however, the heptode alone operates, the full h.t. supply being disconnected from the triode section by  $S_{1(c)}$ . The signals presented to the heptode grid are amplified and appear across the r.f. choke in its anode circuit. The signals could be taken direct from the anode to the main receiver, but this would present certain difficulties. For one thing the anode circuit is at a fairly high impedance, whereas most receivers will have a much lower input impedance at their aerial terminals. To connect directly from the one to the other will cause at least moderate, and probably severe, losses. Also, the output is best taken via a length of screened

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{2}$  watt 10%, unless otherwise stated)

$R_1$	15k $\Omega$
$R_2$	150 $\Omega$
$R_3$	47k $\Omega$
$R_4$	27k $\Omega$
$R_5$	470k $\Omega$
$R_6$	1k $\Omega$
$R_7$	2.2M $\Omega$ 20%
$VR_1$	20k $\Omega$ potentiometer, linear

### Capacitors

$C_1$	0.01 $\mu$ F ceramic, 250V wkg.
$C_2$	0.01 $\mu$ F ceramic
$C_3$	100pF silver-mica
$C_4$	220pF ceramic or silver-mica, 250V wkg.
$C_5$	2,000pF ceramic or polystyrene
$C_6$	0.01 $\mu$ F ceramic, 250V wkg.
$C_7$	1,000pF ceramic
$C_8$	0.01 $\mu$ F ceramic, 250V wkg.
$VC_{1,2}$	300 + 300pF (or 310 + 310pF) 2-gang air-spaced variable
$VC_3$	15pF air-spaced variable
$VC_4$	25pF air-spaced variable
$TC_1$	3-30pF trimmer, Mullard concentric

### Inductors

$L_1$	Miniature Dual-Purpose Coil Range 3, Blue (Denco)
$L_2$	Miniature Dual-Purpose Coil Range 5, Blue (Denco)
$L_3$	Miniature Dual-Purpose Coil Range 5, White (Denco)
$RFC_1$	R.F. choke, 2.6mH, type RFC5 (Denco)

### Valves

$V_1$	ECH81
$V_2$	9001 (see text)

### Switch

$S_{1(a)(b)(c)}$  3-pole 2-way rotary

### Miscellaneous

2 epicyclic slow motion drives with flanges, Cat. No. 4511/F (Jackson Bros)

Spindle coupler

1 B7G valveholder

1 B9A valveholder

Knobs

Set No. 5 (Dials: control panels on clear background) or Set No. 6 (Dials: control panels on black background) Panel-Sign Transfers. (Data Publications, Ltd.)

Chassis materials, connecting wire, etc.

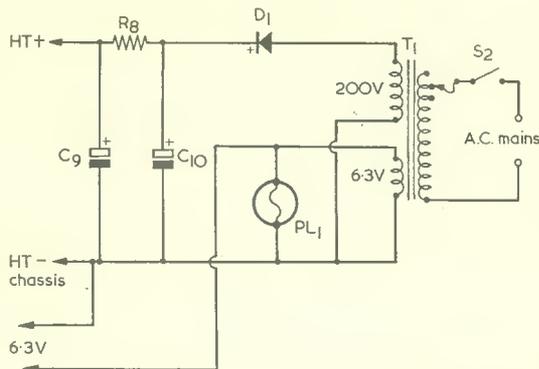


Fig. 2. If the unit is to be completely self-contained it may have its own power supply, as shown here

cable. If this were directly connected to the anode circuit of  $V_{1(a)}$  the self-capacitance of the cable would add to the losses just mentioned. To overcome these difficulties the signal is fed from the anode of  $V_{1(a)}$  to the grid of  $V_2$ , the latter functioning as a cathode follower.  $V_2$  gives no voltage amplification. Instead, it serves as an impedance matching device and enables almost all the output of  $V_{1(a)}$  to be fed to the main receiver.

When the unit is operated as a converter, signals are switched by  $S_{1(a)}$  and  $S_{1(b)}$  to the grid of  $V_{1(a)}$  via  $L_2$ , this coil covering 10.5 to 31.5 Mc/s. At the same time the triode section of  $V_1$  is brought into operation by  $S_{1(c)}$ .  $V_{1(b)}$  functions as an oscillator, and the oscillations are mixed with the signal in the heptode section in the normal manner. The oscillator tuning is trimmed to produce an "i.f." of 1.6 Mc/s at the heptode anode.  $VC_2$  (together with  $VC_1$ , to which it is ganged) provides the main bandset tuning.  $VC_3$ —a small variable capacitor in parallel with  $VC_2$ —enables the oscillator frequency to be varied slightly and provides bandspread. It will be noted that no switching appears in the oscillator tuned circuit itself. This not only greatly simplifies construction but also reduces losses and obviates r.f. switch wiring in a critical section of the unit.

The "i.f." signal appearing at the anode of  $V_{1(a)}$  is passed to the grid of  $V_2$  in the same manner as occurs when the unit is employed as a pre-amplifier. A low impedance output is then available at the cathode of  $V_2$  for application to the main receiver.

When the unit is employed as a pre-amplifier for 1.6 to 5.3 Mc/s, signals are tuned in on the main receiver, being brought up to full strength by adjusting  $VC_1$  in the unit. When the unit is used as a converter for 10.5 to 31.5 Mc/s, the main receiver is set to 1.6 Mc/s and remains tuned at that frequency. Tuning is then carried out by  $VC_1$  and  $VC_2$  in the unit, with  $VC_3$  giving bandspread.

The screened cable coupling the unit to the receiver can conveniently be TV coaxial cable.

It will be noted that a  $2.2M\Omega$  resistor,  $R_7$ , is inserted in series with the h.t. supply to  $V_{1(b)}$  when  $S_{1(c)}$  is set to position A. This resistor prevents

## COMPONENTS

Fig. 2 Power Supply

$R_8$  1k $\Omega$  1 watt

### Capacitors

$C_9, 10$  16 + 16 $\mu$ F electrolytic, 300V wkg.

### Transformer

$T_1$  Mains transformer. Secondaries, 200V at 20mA, 6.3V at 1A.

### Rectifier

$D_1$  BY100

### Switch

$S_2$  On-off toggle

### Pilot Lamp

$PL_1$  6.3V 0.3A pilot lamp

Panel-mounting pilot lamp assembly

cathode poisoning in  $V_{1(b)}$ , which might otherwise occur if the unit were employed as a pre-amplifier for long periods of time. The value of  $R_7$  is too high to allow  $V_{1(b)}$  to oscillate when  $S_{1(c)}$  is in position A.

$VC_4$ , a small variable capacitor across the aerial tuned circuit, allows for different types of aerial and enables the input circuit to be correctly adjusted when the unit is used as a converter.  $VR_1$ , in the cathode circuit of  $V_1$ , controls the bias of the heptode section and acts as a gain control.

In the original,  $V_2$  is a 9001 pentode connected as a triode (i.e. with the anode and screen-grid strapped). The only reason for using this particular valve was that it happened to be available in the spares box. A 6C4 will function just as effectively, as also will a triode connected EF91. The base connections shown in Fig. 1 are for a 9001.

### Power Supply

Power requirements for the unit are very modest. For the h.t. supply a mere 15mA at 200 volts is ample, while a 6.3 volt 1 amp source will supply both valve heaters and a pilot light, with a fair margin to spare. Actual heater consumption for  $V_1$  and  $V_2$  is 0.45 amp when a 9001 or a 6C4 is used for  $V_2$ , and 0.6 amp when an EF91 is used for  $V_2$ . The prototype was self-contained and Fig. 2 gives the circuit of the power supply section. The mains transformer is a "converter" type.\* The suggested rectifier is a BY100 silicon diode. The latter is capable of supplying current far in excess of that required here but, being available for a few shillings, it is an obvious choice. (Continued on page 207)

\*A suitable transformer is available from G. W. Smith & Co. (Radio) Ltd., 3 Lisle Street, London, W.C.2. This is listed as a "converter transformer" and has secondaries of 200 volts at 25mA, and 6.3 volts at 1 amp.—Editor.

# Denco (Clacton) Limited

357-9 OLD ROAD CLACTON-ON-SEA ESSEX

---

## AN APOLOGY

In the interest of our Home Constructor friends and the Component Retailers who supply their requirements, we have endeavoured with great success to maintain our selling prices for very many years. We have now reached the stage where we have just got to increase our prices or go out of business if we wish to maintain our high standard of quality and also continue to support articles published in Technical Magazines.

On January 1st 1968 all of our catalogued prices will be increased by approximately 10%; we have done our very best for all concerned and trust to receive your continued support.

Ask your Retail Component Stockist, or if in difficulty write to us direct, for a copy of our General Catalogue price 2/6d.

---

**DENCO (CLACTON) LIMITED 357-9 OLD ROAD CLACTON-ON-SEA ESSEX**

---



IF YOU'RE BUYING A HOUSE

# Mortgage Protection

is the best Policy for you

If you're buying your house with the help of a Building Society or a private loan, a "Yorkshire" Mortgage Protection Policy will take care of your outstanding payment in the event of your premature death. And, if you wish, you can arrange a Protection "Plus" Policy, which gives you a substantial cash return at the end of the mortgage term. It costs so little yet means so much to your dependants. Leave them a home not a mortgage!

Please send for further details, without any obligation, of course.

## THE YORKSHIRE INSURANCE COMPANY LTD

Chief Offices: Rougier Street, YORK  
and Becket House, 36-37 Old Jewry, LONDON E.C.2

Please send me further particulars of the  
"Yorkshire" Mortgage Protection Policy

Name .....

Address .....

.....

J/B

# RADIO CONSTRUCTOR

## BUILD SOME OF THE FASCINATING DESIGNS FEATURED EACH MONTH



NEXT MONTH'S  
SPECIAL FEATURES

- 3-STAGE PRESELECTOR
- ELECTRONIC SIREN
- SOLID-STATE TIME DELAY UNIT

### MAKE SURE OF YOUR COPY!

To .....

NEWSAGENT

Please reserve/deliver **RADIO CONSTRUCTOR** (2/6), dated December, on sale 1st December and continue every month until further notice.

Name .....

Address .....

.....

.....

## Short Wave Pre-amplifier Converter Unit

(Continued from page 204)

If the main receiver is an a.c. mains type incorporating an isolating mains transformer, it is quite likely capable of supplying the little extra power required for the unit, whereupon the components shown in Fig. 2 are not required. If this course is adopted it is suggested that a  $2k\Omega$  1 watt resistor be included in the h.t. positive feed from the receiver. This will decouple the supply and will prevent the possibility of instability due to interaction between the unit and the receiver front end. *On no account should h.t. or heater supplies be obtained from a receiver whose chassis connects to one side of the mains.*

### Construction

Construction is quite straightforward but the exact details will depend, of course, upon the components used. Standard types were used in the original and a chassis-plus-panel arrangement made for convenient assembly. The general layout is given in Figs. 3, 4 and 5.

The critical part of the circuit is that around  $V_1$ . Short direct connections are necessary here if best results are to be obtained, and most of the smaller components associated with this section should be mounted directly to the valveholder. In the interests of short leads, the valveholders should be oriented

as shown in Fig. 4. (If a 6C4 is used for  $V_2$ , however, its valveholder should have pin 6 closest to  $V_1$  valveholder). Especial care should be taken in wiring the oscillator section for, at the higher frequency end of the range covered, an extra half inch of wire or a "wobbly" component can make all the difference between success and failure. In order to keep the oscillator leads short the bandspread capacitor ( $VC_3$ ) is mounted directly under the oscillator section of the main tuning capacitor ( $VC_2$ ). In the layout  $VC_3$  is shown as a chassis mounting type. Panel mounting types are cheaper to buy and one of these could be substituted, in which case it must be mounted on a small substantial metal bracket in the same position. A spindle coupler and a length of  $\frac{1}{4}$ in spindle couple  $VC_3$  to its slow motion drive.

Outside dimensions for the prototype chassis and panel are given in Figs. 4 and 5, but these are intended merely as a guide. Constructors should first obtain the components they intend to use and then make up a chassis which can accommodate them comfortably. Chassis depth should be such as to give adequate clearance for the aerial and oscillator coils and  $VC_3$ . Solder connections to these coils should, incidentally, be made quickly, as excessive heat may cause the plastic mounting to distort. The coils are fitted to  $\frac{1}{4}$ in holes in the chassis and secured with the plastic nuts provided. Holes are also drilled for the connecting wires to the fixed vanes of  $VC_1$ ,  $VC_2$  and  $VC_4$ , the holes being positioned so that these wires follow the shortest possible route. Further holes will be required for other leads passing through the chassis, and all holes should be

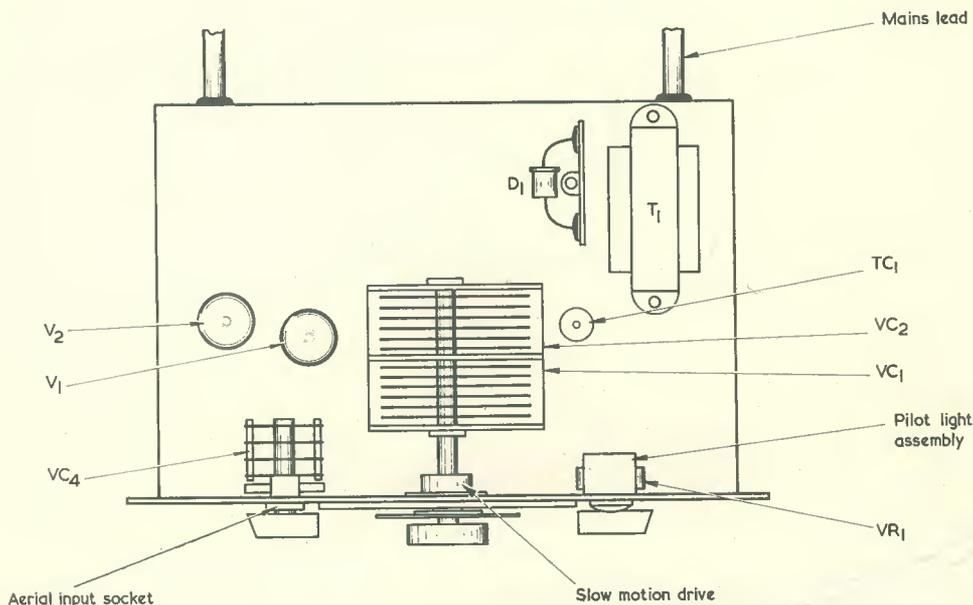


Fig. 3. Top view of the prototype unit, showing the positions taken up by the main components.  $TC_1$  is soldered directly to the adjacent fixed vane tag of  $VC_2$

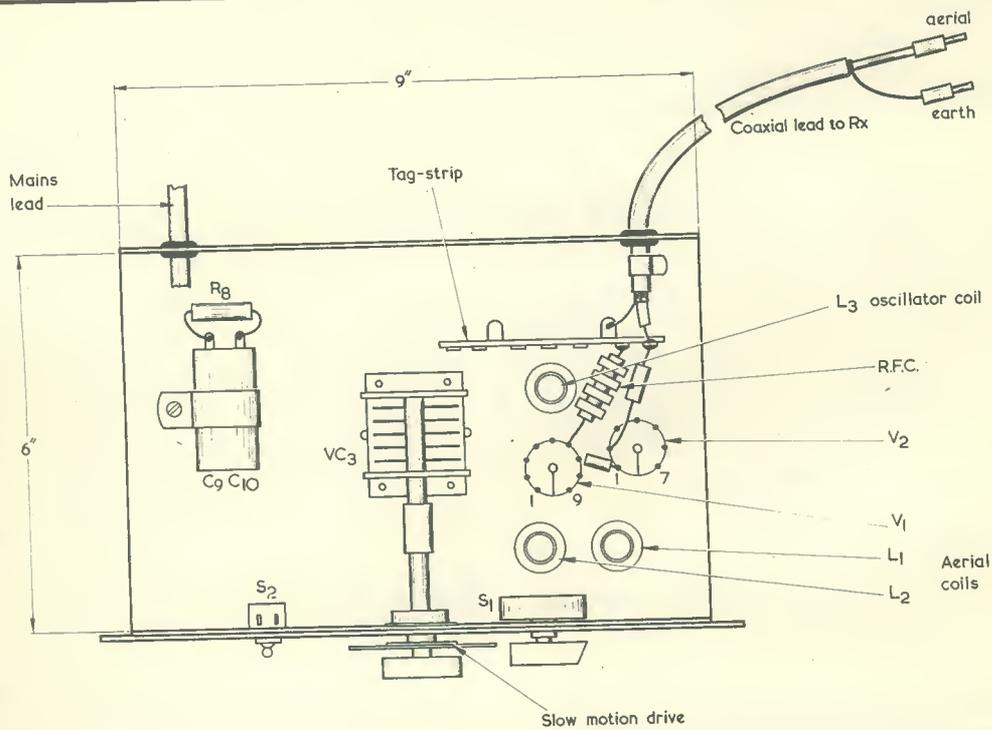


Fig. 4. Under-chassis view of the prototype, indicating the basic layout. Chassis dimensions are intended as a guide only

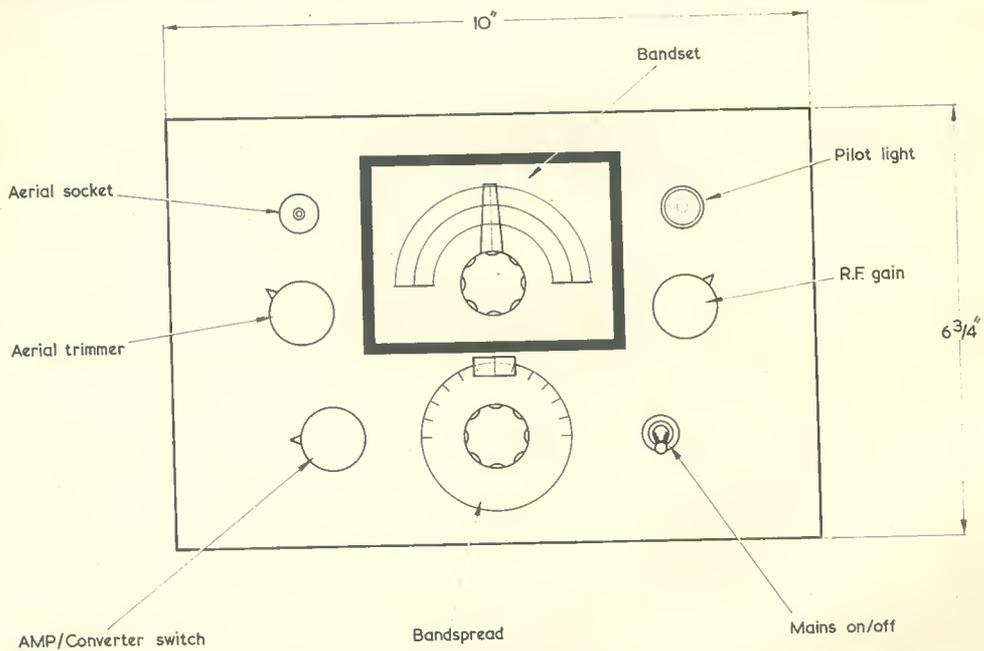


Fig. 5. The front panel layout of the unit. Panel material is aluminium sheet. The bandset cursor may be made from a small piece of Perspex, this being fixed to the flange of the slow motion drive

fitted with grommets. The moving vane connections to the variable capacitors may be taken via the chassis, one or more solder tags under the securing nuts for  $V_1$  and  $V_2$  valveholders providing the chassis connection for the coils.

Fig. 5 shows the panel layout, giving the positions of the various controls. Both the bandset and bandspread controls utilise flange-type epicyclic slow motion drives. A medium size dial taken from the Data "Panel-Signs" range is used for the bandset control. A small circular ivory dial, or similar, mounted directly on the lower drive flange is used for the bandspread control.

#### Alignment and Calibration

Alignment and calibration of the unit is most easily carried out with the aid of a signal generator, standard practice being followed. The unit and its parent receiver are connected as for normal use, with the latter tuned to a point at or near 1.6 Mc/s. In practice the exact frequency is unimportant but should be carefully noted for future reference, for this is in effect the "first i.f.". The unit is switched to the converter position with the bandspread control and the aerial trimmer at their mid-points, and the r.f. gain control at maximum. With the bandset control at maximum capacitance a modulated signal of 10.5 Mc/s is injected into the aerial input of the unit and the core of  $L_3$  is adjusted until the signal is heard. The core of  $L_2$  is then adjusted for maximum response. With the bandset at minimum capacitance a signal of 31.5 Mc/s is injected and  $TC_1$  is adjusted until this also, is heard. If two positions of the trimmer produce the signal, that with the lowest capacitance is the correct one. The aerial trimmer,  $VC_1$ , is next adjusted for maximum signal. The whole process is then repeated in order to take up any small final adjustments that may be necessary. The cores and  $TC_1$  should then be fixed with a spot of wax and the converter range can be calibrated.

If a signal generator is not available alignment will be more tricky and will require rather more patience, for broadcast signals will have to be used. One of the difficulties in aligning without instruments is knowing where to expect the various bands to appear on the dial. As a rough guide the following were logged on the prototype using the "Panel-Signs" dial.

25 metre broadcast band — 80  
19 metre broadcast band — 55  
16 metre broadcast band — 40  
13 metre broadcast band — 20

If the bandset dial is set at 80 the core of  $L_3$  should be carefully adjusted until a broadcast signal in the 25 metre band is heard. This is then brought to maximum by adjusting the core of  $L_2$ . With the bandset dial at 20,  $TC_1$  should be adjusted until a signal is heard in the 13 metre band. This is then brought to maximum by adjusting the aerial trimmer. This procedure will bring the circuits roughly into line and the dial can then be calibrated against known signals.

Alignment of the unit as a pre-amplifier is a simple matter with or without a signal generator. All that is necessary is the correct positioning of the core of  $L_1$ . The main receiver is set at 1.6 Mc/s and, with the bandset control at maximum capacitance, the core of  $L_1$  is adjusted for maximum "noise". Signals on this range are tuned on the main receiver and "peaked" by the unit tuning control.

When used as a pre-amplifier it may be found that, with certain types of aerial, oscillation occurs. All that is necessary to prevent this is to adjust the r.f. gain until the oscillations cease. At this point the unit will be functioning in its most sensitive state. On many signals the r.f. gain will have to be reduced below this point to prevent overloading of the main receiver.



## New Components for Colour TV


### *Plessey Voltage Multiplier for High Tension Supply*

An alternative to the use of two valves in a colour television receiver is provided by a Voltage Multiplier Assembly developed by the Wound Components Division at the Titchfield, Hampshire, factory of the Plessey Components Group. Additionally, the assembly enables the line output transformer to be rendered far more simple and reliable.

By eliminating two rectifier valves an important source of unreliability is removed. This is of particular interest to rental companies whose financial success depends entirely upon keeping down maintenance costs.

The Voltage Multiplier has been designed around selenium rectifiers which, it is considered, provides the most economical method of extra high tension generation, and will do so for some time to come.

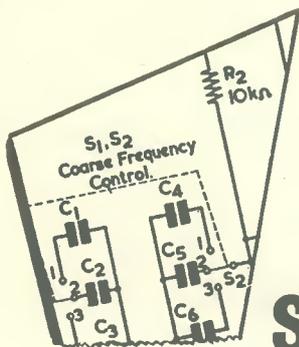The more expensive silicon rectifiers, however, will be incorporated in an alternative version of the Voltage Multiplier which will shortly be available.



# Simple Product Computer

## SUGGESTED CIRCUIT No. 204

by G. A. FRENCH

IN LAST MONTH'S "SUGGESTED Circuit" article the author described a computer which, with the aid of a few electronic components, was capable of calculating the total resistance of two resistors in parallel or the total capacitance of two capacitors in series. Simple computers of this nature form interesting and instructive constructional projects and, provided that only a few components are required and that assembly can be carried out in a short time, are capable of offering quite useful facilities when they are completed.

The product computer described this month employs only a small number of standard components, and is capable of solving the equations

$$x \times y = z, \quad x = \frac{z}{y} \quad \text{or} \quad y = \frac{z}{x}.$$

A particularly useful feature is that it can be used to find square roots. The basic principles employed have been described in an earlier issue of this journal\* but the previous article did not provide specific details for a suitable d.c. null indicating device, as are given here. The null indicating circuit described in the present article may prove to be of assistance also to readers carrying out general work on d.c. operated measuring bridges.

### The Computer

The product computer employs the basic circuitry illustrated in Fig. 1, in which we see three linear track potentiometers,  $R_1$ ,  $R_2$ , and  $R_3$ , a centre-zero current reading meter and a d.c. supply. It will be noted that  $R_1$  and  $R_3$  connect directly across the

d.c. supply lines whilst the track of  $R_2$  connects between the slider of  $R_1$  and the lower supply line.

Let us now assume that  $R_2$  has a high value compared with  $R_1$ , with the result that the current it draws through the upper section of  $R_1$  is negligible compared with the current flowing through  $R_1$  itself. Let us assume also that the d.c. supply offers  $E$  volts.

If the resistance between the slider of  $R_1$  and the lower supply line is  $x$  times the total resistance of  $R_1$ , then the voltage appearing between  $R_1$  slider and the lower supply line becomes  $xE$  volts. This voltage is applied to the track of  $R_2$ . If, in its turn, the resistance between the slider of  $R_2$  and the lower supply line is  $y$  times the total resistance of  $R_2$ , then the voltage between  $R_2$  slider and the lower supply line is  $y$  times the voltage given by  $R_1$ . In other words, the voltage at  $R_2$  slider is  $y \cdot xE$ . At the same time, if the resistance between the slider of  $R_3$  and the lower supply line is  $z$  times the total resistance of  $R_3$ , then the voltage between the slider of  $R_3$  and the lower supply line is  $zE$  volts.

When the potentiometers are adjusted such that the centre-zero meter suffers no deflection, the voltage at the slider of  $R_2$  relative to the lower supply line is equal to the voltage at the slider of  $R_3$ . Under these conditions,  $y \cdot xE = zE$ , which simplifies to  $y \cdot x = z$ , or  $xy = z$ . If the three potentiometers were fitted with scales calibrated in terms of  $x$ ,  $y$  and  $z$ , we could then find from the scale of  $R_3$  the product of  $x$  and  $y$  on the scales of  $R_1$  and  $R_2$ .

A numerical example may help to illustrate this relationship. Let us

assume that each potentiometer has a scale calibrated in fractions from 0 to 1, with 0 corresponding to the lower end of the track. If we adjust  $R_1$  so that its slider is  $\frac{1}{3}$  of the way up its track then the voltage at the slider (relative to the lower supply line) is  $\frac{1}{3}E$ , and the  $R_1$  scale will indicate  $\frac{1}{3}$ . If we similarly adjust  $R_2$  so that its slider is  $\frac{1}{3}$  of the way up its track, the voltage on  $R_2$  slider is  $\frac{1}{3}$  of that applied to  $R_2$ . This is  $\frac{1}{3} \times \frac{1}{3}$  of  $E$ , or  $\frac{1}{9}E$ . We next adjust  $R_3$  so that the meter indicates zero, whereupon the slider of  $R_3$  must offer a voltage of  $\frac{1}{9}E$ , corresponding to the slider of  $R_3$  being  $\frac{1}{9}$  of the way up its track. The scales fitted to the potentiometers will then indicate that  $\frac{1}{3} \times \frac{1}{3} = \frac{1}{9}$ , which is of course correct.

### Practical Scales

To introduce the operation of the computer we have employed the terms  $x$ ,  $y$  and  $z$ , these representing fractions of the total resistance of each potentiometer. It is, however, difficult to read scales calibrated in fractions and a practical version of the circuit requires potentiometer scales which are calibrated in terms of numbers above unity. A very useful set of scales is shown in Fig. 2, this diagram also including the centre-zero null indicating meter and an on-off switch in series with the d.c. supply.  $R_1$  and  $R_2$  are calibrated from 0 to 10, the calibration being equal to 10 times  $x$  or  $y$ , as applicable. The scale for  $R_3$  is calibrated from 0 to 100, the calibration being equal to 100 times  $z$  (or  $10x$  multiplied by  $10y$ , which equals  $100xy$ ). The three potentiometers have linear tracks and are connected into the basic

\*"In Your Workshop", *The Radio Constructor*, March 1963.

circuit of Fig. 1. Also, the zero point on each potentiometer scale corresponds to the slider being at the end of the track which connects to the lower supply line.

Several further examples will illustrate how the scales of Fig. 2 may be used. Let us set  $R_1$  to 5, and  $R_2$  to 7, then adjust  $R_3$  so that the meter reads zero.  $R_3$  will indicate 35. This is, of course, obvious from our previous discussion, because  $R_1$  is giving five-tenths of  $E$ , and so on.

If we have an Ohms Law problem, in which we want to find the resistance when, say, a potential of 6 volts causes 3 amps to flow, we may use the  $x = \frac{z}{y}$  relationship offered by

the computer, substituting for  $R = \frac{E}{I}$ .

We set  $R_3$  to 6 and  $R_2$  to 3, after which we adjust  $R_1$  for zero indication in the meter.  $R_1$  will indicate 2, which tells us that the resistance is  $2\Omega$ .

To find square roots we set  $R_3$  to the square and adjust  $R_1$  and  $R_2$  in step for zero deflection in the meter. If, for instance, we set  $R_3$  to 81, then the meter will indicate zero when both  $R_1$  and  $R_2$  are adjusted to 9.

We have used whole numbers in these numerical examples for simplicity of illustration but, with careful calibration, it will be possible to obtain readings which include fractions of whole numbers as well. With good calibration we should be able to find, for instance, that the square root of 72 is 8.5 to two significant figures.

To obtain increased utility from the computer it is desirable to add a second scale to each potentiometer, as in Fig. 3. In these second scales,  $R_3$  is calibrated from 0 to 10 and  $R_1$  and  $R_2$  from 0 to 3.16, which is the square root of 10. (Details of carrying out the calibration are given later in this article). This second set of scales will be particularly useful for square root calculations. The first set of scales may be used where the squares are 10 to 100, 1,000 to 10,000 and so on, whilst the second set of scales is used for squares from 1 to 10, and 100 to 1,000, etc. The second set of scales also "expands" the  $R_3$  scale over the 0—10 range for normal multiplication.

#### Working Circuit

To convert the basic circuit of Fig. 1 into a usable form, it is necessary to add a few extra components. A full practical circuit is illustrated in Fig. 4, and it may be noted that the added components all appear around the null indicating meter. Their function is to maintain

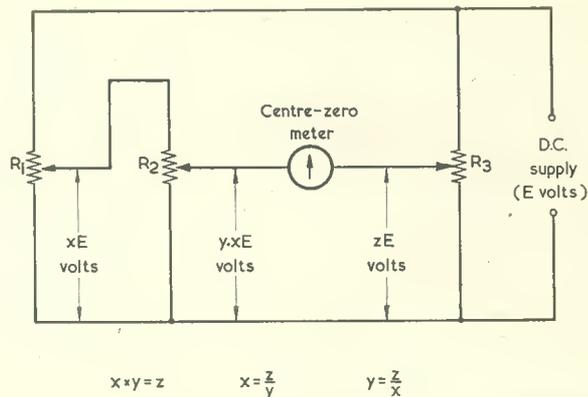


Fig. 1. The basic circuit of the product computer. The three potentiometers have linear tracks

the sensitivity of the meter as the null is approached whilst ensuring that excessive current does not pass through the meter when the sliders of  $R_2$  and  $R_3$  are a long way from the balance positions. Inspection of the circuit will show that it is possible to set up the potentiometers so that the full supply voltage appears between the sliders of  $R_2$  and  $R_3$ .

The normal approach to a problem of this nature is to connect two diodes across the meter in the manner shown in Fig. 5. If these were silicon diodes they would conduct when the forward voltage applied to them was of the order of 0.6 volts, and the series resistor shown in the diagram would be given a value which ensured that the meter read full-scale deflection under this condition. The limiting resistor shown in Fig. 5 ensures that excessive current does not flow through the diodes when the applied voltage across the two end terminals increases further.

The writer initially checked results with two silicon diodes, using a

centre-zero 1—0—1mA meter having a coil resistance of  $100\Omega$ , and a limiting resistor of  $200\Omega$ . He found in practice that the meter series resistance had to be well in excess of  $1k\Omega$  if excessive current was not to pass through the meter. Making the assumption that the meter reads voltage changes only as the sliders of  $R_2$  and  $R_3$  in Fig. 4 approach the null point, this meant that the meter would be worse than 10 times less sensitive than it need be for settings of  $R_2$  and  $R_3$  near the null. Germanium diodes, which pass forward current at a lower voltage than silicon diodes, were next tried, and these enabled the series resistance to be significantly reduced. But by far the best results were given with two germanium transistors type ACY19 connected as shown in Fig. 4 with the base-emitter and base-collector junctions of each transistor in parallel. These enabled the series resistance to be reduced to  $300\Omega$  in the author's experimental circuit, and had the advantage of becoming

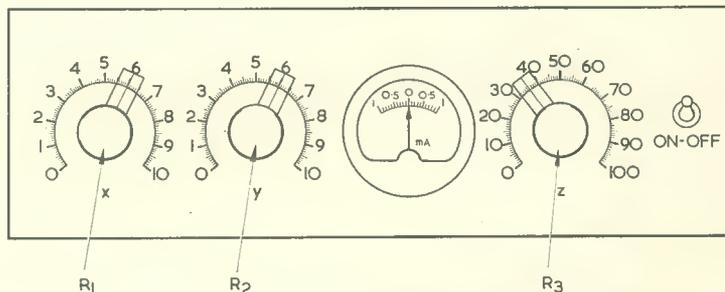


Fig. 2. How scales may be fitted to the three potentiometers to enable them to be used in a practical computer. The panel layout shown here is suitable for the working circuit of Fig. 4

conductive much more abruptly as forward voltage increased than did the germanium diodes. The two transistors were, in consequence, employed in the prototype circuit. The 200Ω limiting resistor, R<sub>5</sub>, limits the current in the transistors to 45mA and the power to 18mW, both these figures being well within the ratings for the types used. It is very probable that other transistors in the ACY17 to ACY22 (inclusive) range will offer similar results in the present application, but these were not checked by the writer.

In Fig. 4 the series meter resistance is given by the preset variable resistor R<sub>4</sub>. After construction of the computer, this resistor is set to insert full resistance into circuit, after which R<sub>1</sub> and R<sub>2</sub> sliders are set to the top ends of their tracks and R<sub>3</sub> to the bottom end. R<sub>4</sub> is then adjusted to give full-scale deflection in the meter. R<sub>2</sub> slider is then set to the bottom end of its track and R<sub>3</sub> slider to the top end. If the meter reading is now in excess of f.s.d. R<sub>4</sub> is readjusted to bring it to f.s.d. The writer found that, with the transistors employed by himself, the setting for R<sub>4</sub> was about the same for either transistor in the conducting state. If desired, R<sub>4</sub> can be replaced by a fixed resistor of the same value after this setting-up procedure.

The three potentiometers in Fig. 4

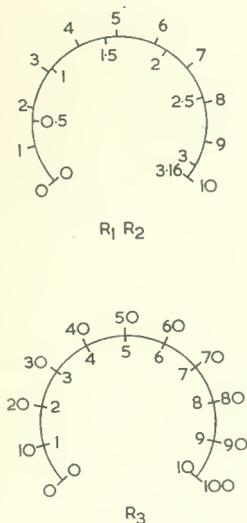


Fig. 3. For increased utility, a 0 to 3.16 range is added to the scales of R<sub>1</sub> and R<sub>2</sub>, and a 0 to 10 range to the scale of R<sub>3</sub>. For simplicity, inter-number graduations are not shown here, although they should appear in the actual scales made up

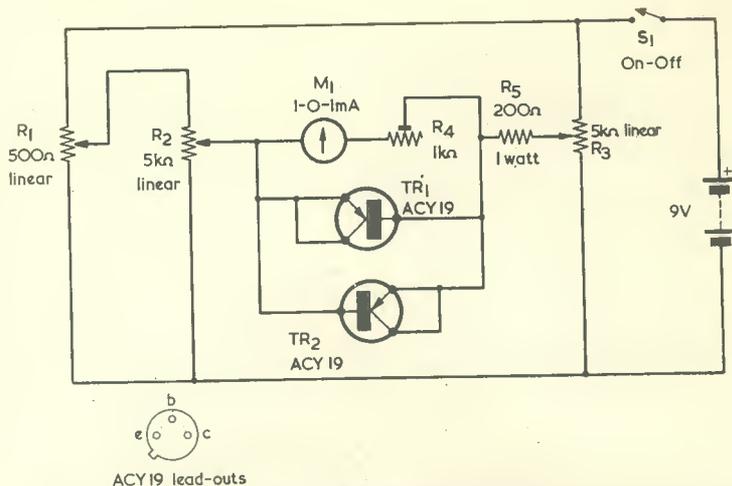


Fig. 4. A practical product computer circuit. R<sub>1</sub>, R<sub>2</sub> and R<sub>3</sub> are the similarly numbered potentiometers of Fig. 1, and the circuit functions in the same basic manner

are given values which reflect a compromise between resolution of readings and battery current consumption. At normal potentiometer settings battery consumption will be of the order of 22mA. If desired, increased resolution would be given if the three potentiometers were reduced to about half of the values shown in Fig. 3, this being at the cost of a doubled battery current consumption. The three potentiometers should, preferably, be large wirewound types. When the potentiometers are set close to the positions which cause maximum current to flow via the limiting resistor R<sub>5</sub>, the current drawn by the meter circuit will approach 45mA. This factor also argues the desirability of using wirewound potentiometers. In practice, care should be taken to ensure that the potentiometers are not left in the positions which cause this high current to flow for very long periods as, apart from battery drain, overheating of the end sections of the

potentiometer tracks could result. Again with economy in mind, it was decided to employ a 1-0-1mA centre-zero meter for the unit, and the protection circuit given by the two transistors is intended for a meter of this sensitivity only. The battery may be any 9-volt type capable of providing the required current. Since the circuit functions in the manner of a bridge, accuracy is maintained despite reductions in voltage as the battery ages.

### Calibration

After construction has been completed and R<sub>4</sub> set to its final resistance, calibration may be carried out. The first potentiometer to be calibrated is R<sub>3</sub>. Since some potentiometers have small sections at the ends of the track which offer zero resistance over a small angle of rotation, it is first of all necessary to find the angular settings of the slider which correspond to the start of the track proper. Switch on S<sub>1</sub>, connect a

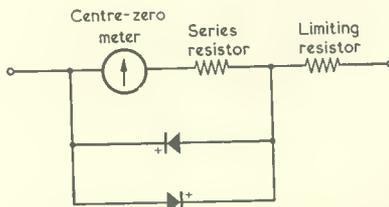


Fig. 5. The usual approach to giving a centre-zero meter a high sensitivity when low voltages are applied to the terminal points, whilst preventing excess meter current when high voltages are applied

voltmeter between the slider of  $R_3$  and the lower supply line and, with its aid, mark off the points where the actual track commences. Calibrate these as 0 (lower end of track) and 100 (upper end of track) respectively. The voltmeter is now no longer required, and the intervening points for the  $R_3$  scale may all be calibrated as a linear scale.

Next, set the slider of  $R_1$  to the top of its track and, using the null indicator, calibrate  $R_2$  from the corresponding calibration points for  $R_3$  (i.e. 90 corresponds to 9, 80 to 8, and so on). Then, set  $R_2$  slider to the top of its track and similarly calibrate  $R_1$  from 0 to 10, also working from the  $R_3$  calibration. It will be recalled that an initial assumption was made that  $R_2$  draws negligible current through  $R_1$ . In fact, of course,  $R_2$  draws a significant current, and this point is taken up in the manner in which  $R_1$  (which has a slightly non-linear scale) is calibrated.

Next, add the 0-10 scale to  $R_3$  and the 0-3.16 scales to  $R_1$  and  $R_2$ . The latter two scales may be made up by following Fig. 6, which shows the

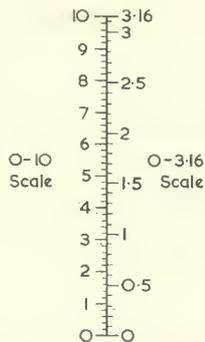


Fig. 6. As stated in the text,  $R_1$  and  $R_2$  require a 0-3.16 scale in addition to a 0-10 scale. After the 0-10 scale has been calibrated, the 0-3.16 scale may be added by following this diagram, which shows the corresponding figures of the two scales alongside each other.

figures of each scale alongside each other.

The computer is then ready for use.



## New Approach to D.I.Y.

### 'MIDIEX '68' AT BIRMINGHAM NEXT MAY

A new twist to "do-it-yourself" exhibitions is announced by Gordon Saville Exhibitions (1967) Ltd. Believing that there is an increasing public interest in leisure and sporting pastimes, Mr. Gordon Saville is to stage a "make-it and do-it" exhibition at Bingley Hall, Birmingham.

"Despite the television age which makes vast numbers of the public stick to the TV sets like limpets", claims Mr. Saville, "there is a definite trend towards spare time occupations that develop the creative instincts in a person. There is a great thirst for knowledge on all manner of hobbies amongst all ages."

Mr. Saville adds, "More and more people are carrying out their own home repairs, making everything from furniture to boats, collecting all manner of items from stamps to national costumed dolls, assembling kits ranging from model railways to single seater aircraft, and a host of other pastimes which test both the mental and physical capabilities of the individual".

The exhibition, "MIDIEX '68", will take place from the 8th - 18th May, 1968. A plan drawing giving the stand areas and rents is available on request from Gordon Saville Exhibitions (1967) Ltd., 21 Victoria Road, Surbiton, Surrey (Tel: 01-399 3232) or from Sales Publicity Management (Midlands) Ltd., Northampton House, Poplar Road, Solihull, Warwickshire (Tel: 021-705 8302).

## SWINGEING PRICE REDUCTIONS

### IN INTEGRATED CIRCUITS

For the second time in nine months, S.T.C. Semiconductors Limited has made substantial cuts in its UK prices of diode-transistor logic (DLT) integrated circuits.

Some sixty flatpack and dual-in-line devices have been reduced: all are ceramic-packaged units in the company's internationally known MIC 930 series.

The cuts, described by a company official as "swingeing" have been particularly dramatic in the case of dual-in-line circuits, many of which have been reduced by over 50%.

For example, the price of the industrial MIC 946 Quad 2-input gate, which was 37s. each for 100-up quantities, is now 15s. 9d. each: equivalent to a gate function of less than 4s.

These considerable reductions in price have been made possible by continuous improvement in manufacturing techniques and the rapid expansion of manufacturing volume. The additional reductions on the dual-in-line circuits following the recent commencement of quantity production at the company's Footscray, Sidcup, Kent, plant.

The manufacturing unit has the advantage of being equipped with the latest production equipment available, including automated test equipment for both production and quality assurance testing.

Commenting on the reductions, Mr. P. A. L. Harris, Marketing Manager of S.T.C. Semiconductors said "In the majority of applications, where higher speeds of operation are not required, our DTL provides technical advantages for the user, including absence of current-spiking problems, availability of the direct wired-OR function, plus a fully proven hermetic package at a cost only marginally above that of plastic encapsulated circuits."

"Despite the claims now being made for TTL integrated circuits, it remains a fact that the 930 DTL series is in use in far greater numbers throughout the world, is available from more suppliers and above all is cheaper than any TTL family."

### That Term 'Ham' Again

We were very intrigued to see a letter in a recent issue of the R.S.G.B. *Bulletin* pointing out, once again, the undesirability of using the term "ham" with reference to those participating in amateur radio.

This term has always been one of this magazine's pet aversions, and in any reference to amateur radio we have always taken care to avoid its use.

There seems to be some doubt as to how the word originated and why it became particularly associated with amateur radio. The phrase "ham actor" seems fairly well authenticated, and was a derogatory term for an actor who was not particularly outstanding in his profession. We are not aware that it was ever used to identify a person who engaged in amateur dramatics or acting "just for the fun of the thing". However, whatever its origin, it conveys a sense of derogation to the man in the street.

Every group these days is concerned with keeping its "image" in the public eye as favourable as possible, and this is particularly important for amateur radio as its facilities are much coveted by commercial interests.

We would like to see "ham" dropped entirely where amateur radio is concerned.

### Ultra Sensitive TV Camera

In his "Industrial Newsletter" in the BBC World Service programme "Science and Industry", Denis Desoutter reported on a television camera that is extremely sensitive to ordinary wavelengths of light. In fact it is sensitive to light so dim that it would be difficult or impossible for a human eye to notice. The heart of the device is a new camera tube, developed by the English Electric Valve Company and called the Isocon.

The Isocon, said Desoutter, could be used to take cine film or still pictures in the dark, and after amplification give a high quality television picture of either 625 lines or 1,025 lines. He anticipated that it would have many industrial and military uses but one special application would be in astronomy, where the light of distant stars is very faint. In the past huge telescopes like the 200in one at Mount Palomar had to be built to collect enough of this dim light to make a good picture. The Isocon camera is about 100 times more sensitive which means that it can do the same job as an ordinary 200in telescope with only a 24in aperture.

### Out For the Count

When reading comments by sports writers it sometimes seems almost unnecessary to play off the event as, according to the journalists, it is only bad luck, or injury, or something of that nature which can prevent the favoured one from winning, defeat from such a cause being unfair and not proving the winner to be the better man. It all seems pointless and one wonders whether the relevant information could be fed into a computer, which could then work out the winner with all chance and bad luck being eliminated.

We have recently learned, with some surprise, that something like the foregoing has actually happened in the States.

Someone had the idea of finding out who was the greatest boxer ever. Boxing experts fed information such as punching power, stamina, intelligence, etc. into a computer in respect of several boxers past and present. "Fixtures" were arranged, the first being between Jack Dempsey and "Gentleman Jim" Corbett.

The computer produced a round by round commentary and Jack Dempsey was computed to have won by a knock-out in the seventh round.

Perhaps a computer will one day work out which came first, the chicken or the egg, and why it really did cross the road!

## Free Sample Offer — New Instrument Cleaner

This new instrument cleaner consists of two blocks which are soft, rather like plasticine to the touch, and which do not injure the skin or corrode metal.

"Rodico" is not intended to usurp the use of normal cleaners, but is especially provided to remove dirt and contamination from specific surface areas such as those found in watches, precision instruments, etc.

Send to Southern Watch & Clock Supplies Ltd., 48-56 High Street, Orpington, Kent, mentioning this magazine, for a free sample.

*This is "Rodico", a revolution in the cleaning of specific areas on small parts. A touch with "Rodico" removes the loose dirt; if the dirt is fixed then rub until removed — miniature tools too, may be cleaned with "Rodico" before they are used.*



# COMMENT

## Electronics for Everyone

Do-it-yourself kits which enable anyone, regardless of their technical knowledge, to assemble radio/electronic apparatus for use in the home, have been announced by Electroniques, STC's retail distribution organisation.

An agreement has been concluded between STC and Allied Radio Corporation, America's largest retail electronic distributor, whereby Electroniques (proprietors STC Ltd.) will exclusively manufacture and market, in the UK and Europe, the complete range of Knight-Kit construction kits for electronic apparatus.

Knight-Kits are designed to provide everyone of average intelligence with hours of enjoyment which is both instructional and materially beneficial. They enable anyone to assemble useful radio tuners and hi-fi amplifiers, which have a professional finish, will work first-time, and have a high performance.


All the preparational chores normally associated with this work have been eliminated: all parts are ready for assembly and are accompanied by very clear and easy-to-follow instructions.

The areas of interest covered by Knight-Kits are quite wide. In addition to stereo radios and amplifiers, the range includes car engine testers—believed to be the first of their kind available in the UK—electronic test equipment, a photographic exposure meter and electronic instructional apparatus for children.

All these kits will be manufactured at Harlow, but initially, kits are being imported and are available completely adapted to British power supplies and standards.

A full technical advisory service, staffed by STC engineers, trained by Knight-Kit, has been set-up at Harlow to provide full technical support.

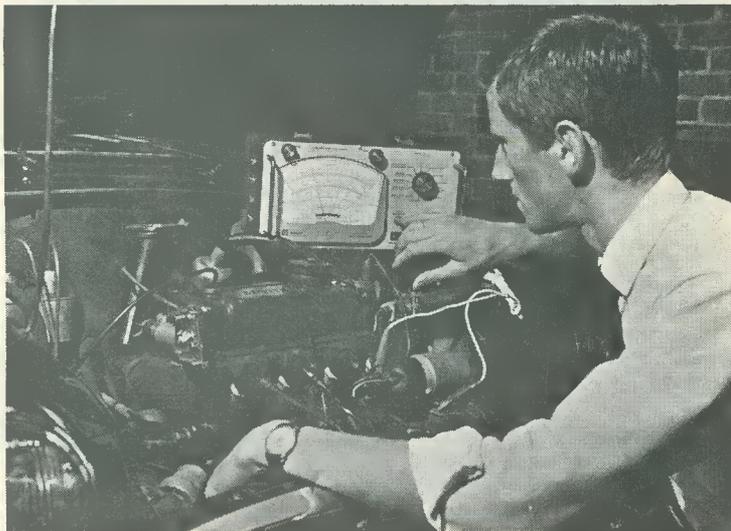Announcing the new move, Mr. Jack Evans, Manager of STC Electronic Services Division, the parent organisation of Electroniques, said—"The availability of Knight-Kits in the UK and Europe is further proof of Electroniques policy in providing a comprehensive service in electronics to the Public."



*Measuring engine speed with the Knight KG-375A Auto Analyser. The KG-375A is one of the many "Knight-Kit" construction kits now being marketed exclusively in the UK and Europe by Electroniques (prop STC Ltd.). "Knight-Kits" are easy to assemble kits which enable anyone regardless of their technical knowledge to assemble professional standard apparatus. Believed to be the only instrument of its kind available in kit form in the UK, the KG-375A checks engine speed, contact dwell-angle, charge rate, and the operation of generator automatic voltage control systems*



*Using the Knight "100 in 1" Electronic Laboratory, one of the many instructional devices which can be easily assembled from the "Knight-Kit" range of construction kits now being marketed in the UK and Europe exclusively by Electroniques (prop STC Ltd.). Capable of being assembled by anyone, regardless of their technical knowledge, the "100 in 1" Electronic Laboratory enables children in the 8 to 16 age group to carry out over 100 interesting and instructive experiments in radio and electronics*

# Automatic Radio Control Keying Unit

M. W. SHORES N.Z.I.S.T.

Intended for the more experienced radio control enthusiast, this article describes a transmitter attachment which provides automatic control of two escapements.

THE SIMPLE SYSTEM TO BE DESCRIBED IS DESIGNED for use with an already established single channel transmitter-receiver combination. This radio link may either be tone modulated, or straight carrier wave. The important requirement is that the receiver switches a relay in its final stage; the relay in turn controlling a separate rubber driven escapement circuit.

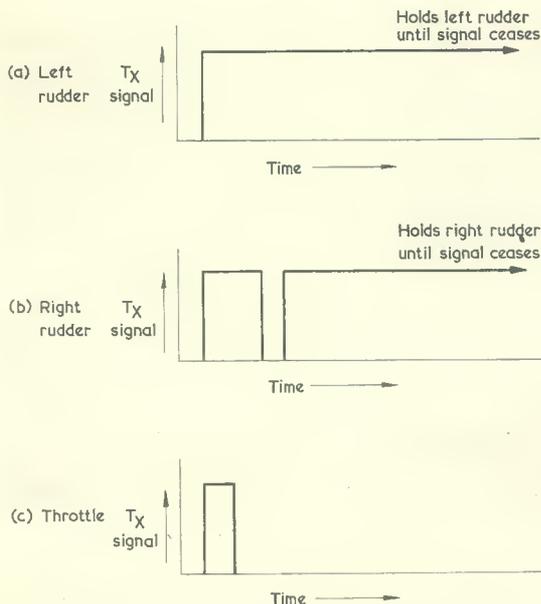


Fig. 1. The transmitted control signals employed in the author's system

Escapements are of two basic types, known as "simple" and "compound" respectively, and they find use mainly in model aircraft to move the control flying surfaces, or actuate an engine throttle control. In the writer's model a Japanese O.S. K1 compound escapement is used for rudder control, with a simple two-pawl escapement linked to it electrically to provide throttle control on "quick blip" (a very short transmitted pulse).\* This latter function is made possible through a circuit which includes the "back contact" of the relay. A full description of escapements may be found in model control literature.

## Keying Sequences

The transmitter keying sequences required for the respective control positions are shown in Fig. 1. Escapement wiring and connections to the receiver relay appear in Fig. 2. Usually the transmitted signals represented in Fig. 1 are keyed manually, using a micro-switch or similar, but this presupposes a certain amount of concentration on the part of the controller which is often better applied to the behaviour of the model itself. The truth in this statement becomes obvious when we consider that the average radio control model aircraft covers a distance of perhaps 50ft. each second.

The keying unit of Fig. 3 is able to "think" for the controller, and provides selective left/right rudder plus engine control at will in the shortest possible time; and all from single channel! In the absence of a signal, the K1 escapement automatically returns to neutral rudder.

In Fig. 3, a P.O. self-centring key switch with two sets of changeover contacts each side is used for rudder operation. For left rudder the key is pushed to the left and held there. The normally open contacts of  $S_{1(a)}$  close, completing the transmitter output circuit via the keying leads. A continuous signal is transmitted, and left rudder holds on until the key is released, breaking the transmitter circuits.

\*The O.S. K1 compound escapement is available from E. Keil & Co. Ltd., Russell Gardens, Wick Lane, Wickford, Essex. E. Keil & Co. are the sole agents in the U.K. for O.S. products.—Editor.


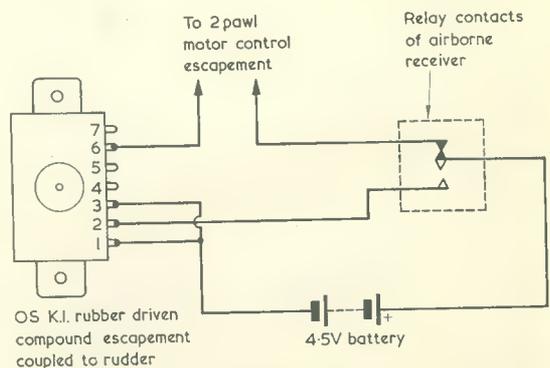


Fig. 2. The escapement wiring in the airborne equipment

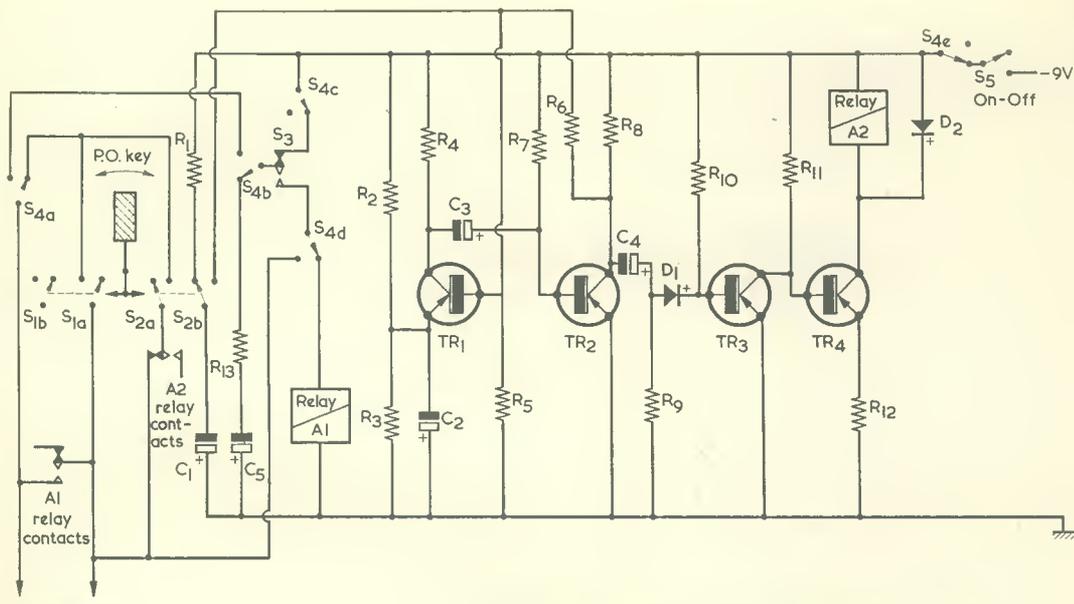

Keying leads to transmitter

S<sub>4a</sub>-S<sub>4e</sub> ganged. (All sections shown in normal operating position)

Fig. 3. Full circuit of the automatic keying unit

**Resistors**

(All resistors 1/4 watt 10% unless otherwise stated)

- R<sub>1</sub> 50Ω 1 watt
- R<sub>2</sub> 1kΩ
- R<sub>3</sub> 330Ω
- R<sub>4</sub> 10kΩ
- R<sub>5</sub> 20kΩ
- R<sub>6</sub> 180kΩ
- R<sub>7</sub> 220kΩ
- R<sub>8</sub> 10kΩ
- R<sub>9</sub> 33kΩ
- R<sub>10</sub> 47kΩ
- R<sub>11</sub> 2.2kΩ
- R<sub>12</sub> 100Ω
- R<sub>13</sub> 68Ω 1/2 watt

**Capacitors**

(All capacitors electrolytic)

- C<sub>1</sub> 30μF, 12V wkg.
- C<sub>2</sub> 100μF, 6V wkg.
- C<sub>3</sub> 5μF, 12V wkg.
- C<sub>4</sub> 8μF, 12V wkg.
- C<sub>5</sub> 100μF, 12V wkg.

**Semiconductors**

- TR<sub>1</sub> OC71
- TR<sub>2</sub> OC71
- TR<sub>3</sub> OC71
- TR<sub>4</sub> OC72 (with heat sink)
- D<sub>1</sub> OA81 or similar
- D<sub>2</sub> OA81 or similar

**Switches**

- S<sub>1</sub>, S<sub>2</sub> P.O. self-centring key switch; 2 sets changeover contacts each side
- S<sub>3</sub> Microswitch, s.p.d.t.
- S<sub>4</sub> 5-pole, 2-way, miniature wafer switch (optional)
- S<sub>5</sub> s.p.s.t., toggle

**Relays**

A1, A2 Relays with single set of changeover contacts; or make contacts (A1) and break contacts (A2). Coil resistance 100Ω or greater

**Batteries**

Two 4.5V batteries type 1289 (Ever Ready)

COMPONENTS

If the key is pushed to the right and held, S<sub>2(a)</sub> and S<sub>2(b)</sub> change over their contacts. Now, before this change, C<sub>1</sub> was fully charged to -9V through R<sub>1</sub>; this resistor merely limits the charging current to a safe value. Because of the change-over of

S<sub>2(b)</sub>, the charged capacitor is immediately connected to the base of TR<sub>1</sub> where it discharges rapidly, delivering a sharp negative pulse. TR<sub>1</sub> and TR<sub>2</sub> form a monostable multivibrator where, in the stable state, TR<sub>1</sub> is off and TR<sub>2</sub> conducting.

The negative spike from  $C_1$  now turns  $TR_1$  on and  $TR_2$  off. This switching action is regenerative and very sharp. A negative square-edged voltage results at the collector of  $TR_2$  which is differentiated by  $C_4$  and  $R_9$  to a sharp negative-going pulse at the anode of  $D_1$ . The polarity of this diode is such that it will not conduct this pulse, and any vestige that did get through would only try to switch  $TR_3$  on harder, for this transistor is already conducting. This condition exists because  $R_{10}$  provides a path for base current to  $TR_3$ . Since  $TR_3$  is on,  $TR_4$  is biased off by the potential developed across  $R_{11}$ , which very nearly equals the supply voltage.

Meanwhile,  $S_{2(a)}$  has also been changed over by the key switch, and the transmitter circuit is completed through its contacts and the normally closed contacts of relay A2. The transmitter therefore radiates a signal until this circuit is broken.

The monostable is now in its unstable state, and will remain so until  $C_3$  has discharged through  $R_7$  and the bottomed transistor,  $TR_1$ .  $C_3$  begins to discharge immediately after the unstable state has been reached. After a finite time (approximately 0.7 times the time constant of  $C_3$  and  $R_7$ ) the stable state is resumed, whereupon  $TR_1$  cuts off, and  $TR_2$  conducts and bottoms. The consequent positive voltage step occurring at the collector of  $TR_2$  is differentiated, and this time  $D_1$  conducts. The resultant positive spike is passed to the base of  $TR_3$  which is driven beyond cutoff, producing a square topped negative pulse at its collector. The width of this pulse is proportional to the time constant of  $C_4$  and  $R_9$ .  $TR_4$  amplifies the pulse current and briefly energises relay A2, whose contacts interrupt the circuit to the final of the transmitter. Having quickly passed through the left rudder position, the escapement will now have reached right rudder and will remain there until the P.O. key is allowed to return to neutral. At this neutral position  $C_1$  is reconnected to the negative rail and rapidly recharged, ready for the next command. By altering the values of  $C_3$  and  $C_4$ , the time delay and duration of signal interruption are easily adjusted.

The values shown in Fig. 3 are those found to be satisfactory in the original unit. Diode  $D_2$  protects  $TR_4$  from the high back e.m.f. in the relay coil when this transistor ceases to conduct. The relays used in the prototype were fairly small 100 $\Omega$  types salvaged from defunct weather balloon transmitters, but any small relays of the same or greater d.c. resistance should suffice.

### Quick Blip

Now we come to quick blip. This is given very

simply by the charging of  $C_5$  through  $R_{13}$ , and its subsequent discharge through  $R_{13}$  and relay A1 when  $S_3$  is pressed; no originality is claimed. The normally open contacts of relay A1 are wired across the keying leads and briefly complete the transmitter circuit until the charge in  $C_5$  is exhausted.

$S_3$  requires a little explanation. In the writer's original a microswitch was used for reliability, but ordinary push button or key types may be preferred. A toggle switch is not suitable, as one has to remember to switch back to the 'charge' position each time. Also, hand keying with a toggle switch becomes almost impossible when  $S_4$  is switched to the fail-safe position. Relay A1 will always pull in for the same length of time, regardless of how long  $S_3$  is pressed.

### Fail-Safe

A fail-safe circuit is incorporated in the original, but is not absolutely necessary. It is provided by  $S_4$ , which cancels all the circuitry and returns all keying functions to manual, using  $S_3$  only.

The unit as described has been fully flight tested and has been in use for over a year.  $S_4$  has only ever been used during ground tests, in order to conserve battery power. Two flat 4.5V torch batteries have proved a most satisfactory and lasting power source, these being wired in series.

The prototype is housed in an aluminium case measuring 8 x 5 x 2½ in, which is held quite comfortably at waist level, connected via twin flex to a ground based transmitter. The quiescent current from the 9V supply is in the order of 12mA rising to 50mA when either relay pulls in, which is for comparatively short periods.

It might appear possible to use the rudder circuitry for control of a model equipped with the most simple system, where a two-pawl escapement is connected directly to the rudder proper. In such a case, however, there are two neutral rudder positions, unlike the single neutral of a compound escapement. This means that a pulse of interference moves the escapement from one neutral to the other. A left rudder signal then gives right rudder, and vice versa. The resultant confusion could quickly write off many hours of painstaking work. The present system is therefore recommended only for use with the types of escapement referred to at the beginning of this article.

Finally, it can be stated that the construction of the original proved very worthwhile and that the resultant saving in mental strain has been considerable.



---

## Micro-Power Amplifier

Quite a few readers have reported good results with the Micro-Power Amplifier described in our last September issue. Some who have used the modification shown in Fig. 4 of the article concerned have found the control of gain to be somewhat cramped at the low resistance end of the potentiometer travel. A smoother control of gain is given if the potentiometer is reduced in value, a suitable alternative value being 50k $\Omega$ .

## TRADE NEWS

### Eagle Products' New Multimeter


Special features designed to achieve greater accuracy are incorporated in the new Multimeter EP.50LN illustrated here—the most advanced model in the new range of Eagle Products' precision test instruments.

The features include 50,000 $\Omega$ /V d.c. for greater accuracy on high resistance circuits and a specially mirrored and expanded two-colour scale eliminating parallax in reading. Additionally the facility of an "Off" position locks the movement thus protecting against shock and possible damage whilst in transit, etc.

The EP.50LN incorporates an overload protection circuit, a special 0 to 3V d.c. range for transistor circuit tests and a polarity reversing switch.

Front panel markings are in two colours for simplified operation, and the new Multimeter is supplied complete with fitted leather case, test leads, batteries and instruction manual.

Specification is as follows: Volts d.c. 0 to 0.3; 0 to 3; 0 to 12; 0 to 60; 0 to 120; 0 to 300, 0 to 600 and 0 to 1,200V. Volts a.c. 0 to 6; 0 to 30; 0 to 120; 0 to 300; 0 to 600 and 0 to 1,200V. Current d.c. 0 to 30 $\mu$ A, 0 to 6mA; 0 to 300mA and 0 to 12A. Resistance 0 to 10k $\Omega$ ; 0 to 1M $\Omega$ , 0 to 10M $\Omega$  and 0 to 100M $\Omega$ . Decibels—20 to +17dB (0dB 1 milliwatt in 600 $\Omega$ ). Output—capacitor in series with a.c. voltage ranges. Size 6 $\frac{1}{2}$  x 4 $\frac{1}{4}$  x  $\frac{3}{8}$ in. Retail price (approx.) £11.11.0d.

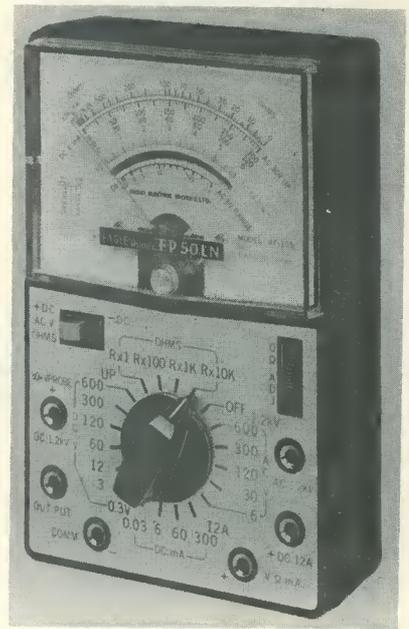

### Knight-Kit Star Roamer Receiver

The Knight "Star Roamer" communications receiver, one of the many useful devices which can be easily constructed from the range of "Knight-Kits" now being marketed in the UK and Europe by Electroniques (prop STC Ltd.). Capable of being assembled in an evening by anyone, regardless of their technical knowledge, the "Star Roamer" is an ideal "starter" receiver for short-wave listening. It covers the frequency range 300 kc/s to 30 Mc/s in 5 bands.



### STC Logic Modules

STC's low-cost logic modules, the Series 40, now includes a Schmitt Trigger module (Type 43E) which facilitates system operation from transducers.

The Series 40 are discrete-component germanium modules of a robust fully encapsulated construction which enable solid state logic systems to be devised at a cost comparable to relay logic.

The Type 43E converts transducer analogue outputs into a two-state form. Its basic upper and lower trigger levels are 0.4V and 0.35V respectively, and can be increased by an external resistive divider.

Input signals can be from photo-electric, magnetic, ultrasonic, capacitive and semiconductor transducers.

Its fan-out capability is three; the outputs are suitable for driving a Series 40 system.

The new module is expected to have wide application in logic systems involving the measurement or control of temperature, quantity, flow, and speed of materials, liquids and gases throughout industry and science.

# Electronic Oscilloscope Switch

by L. J. Aston

Using readily available transistors and components, this electronic switch enables an oscilloscope to display two traces at the same time. The unit may be built in a small case or, even, fitted inside the oscilloscope case.

QUITE A NUMBER OF ELECTRONIC "trace doublers" have been described in various technical magazines. These have been very useful in their way, but all have employed valves. The oscilloscope switch presented here employs eight inexpensive transistors together with standard miniature parts, these giving an instrument which is small and light and which requires only 6 volts at some 3 to 5mA for power.

## Circuit Description

Consider TR<sub>1</sub> and TR<sub>2</sub> in the circuit, which appears in Fig. 1. These two transistors conduct alternately at a rate determined by the frequency control switch S<sub>1(b)</sub>. First TR<sub>1</sub> conducts, the signal applied to its base being amplified and fed to the oscilloscope input, whilst TR<sub>2</sub> is cut off. Then, after a period, selected by S<sub>1(b)</sub>, TR<sub>2</sub> conducts and TR<sub>1</sub> is cut off. It is the signal fed to TR<sub>2</sub> base

which is then applied to the oscilloscope. The switching speed is too fast to be seen and the result is that two traces are displayed on the screen.

TR<sub>7</sub> and TR<sub>8</sub> form a multivibrator which generates the switching frequency. S<sub>1(b)</sub> changes the timing capacitor, giving switch frequencies of about 1, 2.5, 4 and 15 kc/s. It is found that TR<sub>7</sub> and TR<sub>8</sub> give a reasonably 50:50 output at all the frequencies selected by S<sub>1(b)</sub>. The

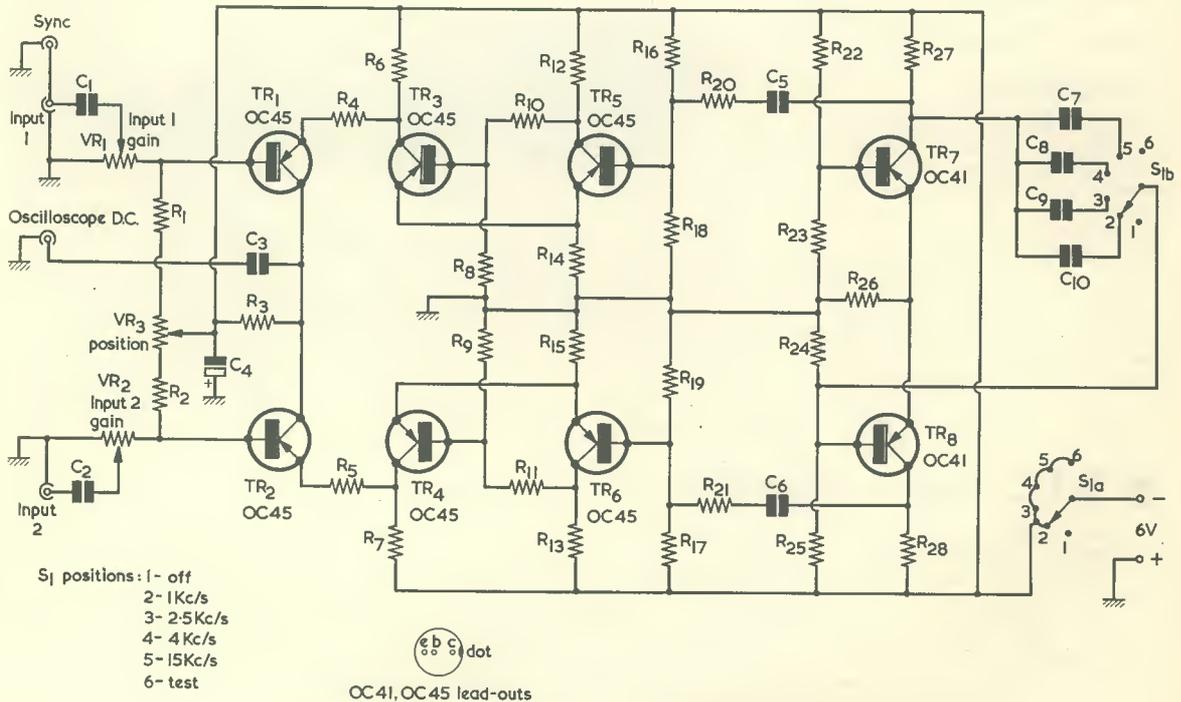


Fig. 1. The circuit diagram of the electronic oscilloscope switch

### Resistors

(All fixed valued  $\frac{1}{4}$  watt 5%)

R <sub>1</sub>	10k $\Omega$
R <sub>2</sub>	10k $\Omega$
R <sub>3</sub>	3.3k $\Omega$
R <sub>4</sub>	3.3k $\Omega$
R <sub>5</sub>	3.3k $\Omega$
R <sub>6</sub>	10k $\Omega$
R <sub>7</sub>	10k $\Omega$
R <sub>8</sub>	3.3k $\Omega$
R <sub>9</sub>	3.3k $\Omega$
R <sub>10</sub>	10k $\Omega$
R <sub>11</sub>	10k $\Omega$
R <sub>12</sub>	3.3k $\Omega$
R <sub>13</sub>	3.3k $\Omega$
R <sub>14</sub>	470 $\Omega$
R <sub>15</sub>	470 $\Omega$
R <sub>16</sub>	100k $\Omega$
R <sub>17</sub>	100k $\Omega$
R <sub>18</sub>	10k $\Omega$
R <sub>19</sub>	10k $\Omega$
R <sub>20</sub>	1k $\Omega$
R <sub>21</sub>	1k $\Omega$
R <sub>22</sub>	5.6k $\Omega$
R <sub>23</sub>	4.7k $\Omega$
R <sub>24</sub>	560k $\Omega$
R <sub>25</sub>	470k $\Omega$
R <sub>26</sub>	10k $\Omega$
R <sub>27</sub>	10k $\Omega$
R <sub>28</sub>	10k $\Omega$
VR <sub>1</sub>	10k $\Omega$ potentiometer, carbon, linear
VR <sub>2</sub>	10k $\Omega$ potentiometer, carbon, linear
VR <sub>3</sub>	25k $\Omega$ potentiometer, carbon, linear

### COMPONENTS

### Capacitors

C <sub>1</sub>	0.1 $\mu$ F
C <sub>2</sub>	0.1 $\mu$ F
C <sub>3</sub>	0.1 $\mu$ F
C <sub>4</sub>	10 $\mu$ F electrolytic, 9V wkg.
C <sub>5</sub>	0.1 $\mu$ F
C <sub>6</sub>	0.1 $\mu$ F
C <sub>7</sub>	200pF silver-mica or ceramic
C <sub>8</sub>	400pF silver-mica or ceramic
C <sub>9</sub>	680pF silver-mica or ceramic
C <sub>10</sub>	800 pF silver-mica ceramic

### Transistors

TR <sub>1</sub>	OC45
TR <sub>2</sub>	OC45
TR <sub>3</sub>	OC45
TR <sub>4</sub>	OC45
TR <sub>5</sub>	OC45
TR <sub>6</sub>	OC45
TR <sub>7</sub>	OC41
TR <sub>8</sub>	OC41

### Switch

S<sub>1</sub> 2-pole 6-way rotary switch

### Miscellaneous

6-volt battery  
4 coaxial sockets  
4 knobs  
Connecting wire, case, panel, etc.

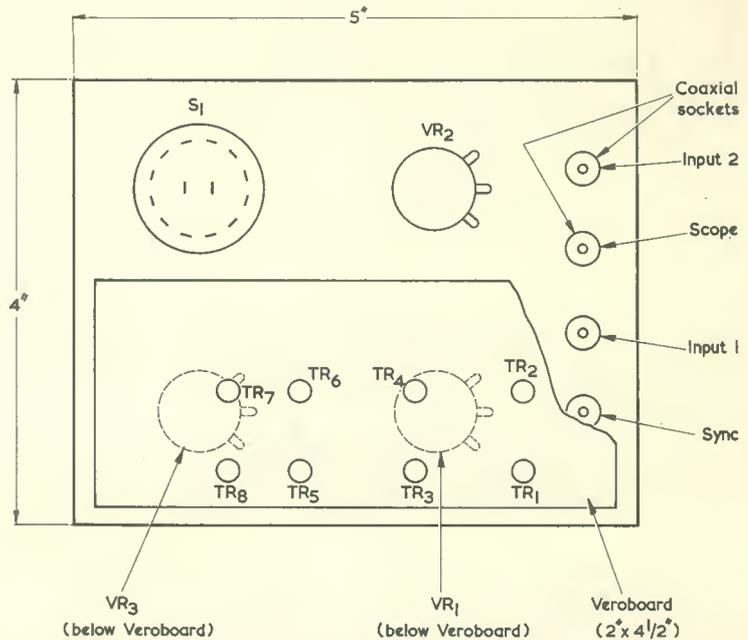


Fig. 2. The layout is not critical, and that used for the prototype is shown here to provide an idea of what is required. All components are mounted on a 4 x 5 in panel which fits to a box having a depth of 2 $\frac{1}{2}$  in. There is room behind VR<sub>2</sub> for a small 6 volt battery

output pulse at TR<sub>7</sub> collector is 180° out of phase with that at TR<sub>8</sub> collector. During one half-cycle TR<sub>5</sub> base receives a positive pulse from TR<sub>7</sub> and TR<sub>6</sub> base receives a negative pulse from TR<sub>8</sub>. In the next half-cycle the pulse polarities reverse.

TR<sub>4</sub>, TR<sub>5</sub>, and TR<sub>3</sub>, TR<sub>6</sub> are squaring circuits which convert the multivibrator pulses to fast-rising square waves to drive the emitters of TR<sub>1</sub> and TR<sub>2</sub>. A positive pulse fed to the base of TR<sub>5</sub> produces a positive square wave at TR<sub>3</sub> collector which drives TR<sub>1</sub> into conduction; at the same time a negative pulse fed to the base of TR<sub>6</sub> produces a negative square wave at TR<sub>4</sub> collector, driving TR<sub>2</sub> into cut-off. Any signals fed into the base circuits of TR<sub>1</sub> and TR<sub>2</sub> are thereby passed on to the oscilloscope on alternate half-cycles, and appear as two separate waveforms.

The test position on S<sub>1(b)</sub> disables the multivibrator by removing the timing capacitor and only one trace is displayed. This is an amplified version of whatever is being fed into the input sockets, and its existence proves that the battery supply for the switch is usable. The writer employs a battery of five 225mA/H DEAC cells which lasts a long time between

charges, but it is still useful to know that all is well before settling down to test, for example, the frequency response of an amplifier.

It will be noted that S<sub>1(a)</sub>, which is ganged with S<sub>1(b)</sub>, functions as the on-off switch.

The position control moves the two traces relative to one another. When the slider of this control is at one end of the track, one trace is displayed at the top of the screen with the other below it. Turning the control causes the two traces to approach each other until they become superimposed, after which they separate again with the trace previously at the top being below. The inputs to the two channels are controlled by the two 10k $\Omega$  gain potentiometers. The input impedances are relatively low, but this fact has given no difficulties with the writer's activities which have consisted of testing radios and amplifiers. If a high impedance source is used, it may be connected via a suitable pad to avoid loading it excessively, but this has not been found necessary in the writer's case.

The prototype unit was assembled in a box measuring 5 x 4 x 2 $\frac{1}{2}$  in, which is about the minimum useful size for easy operation. The circuit

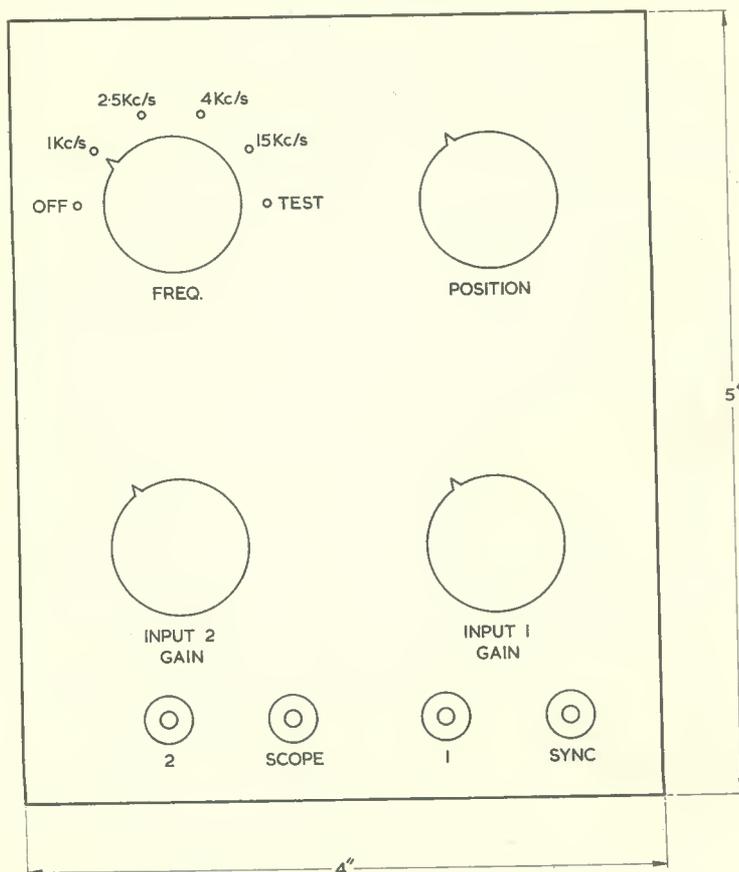


Fig. 3. Front view of the panel

was made up on Veroboard with flying leads to the potentiometers, switches and sockets, these being mounted on a front panel to which the Veroboard was secured with spacing pillars. The general layout is given in Fig. 2. Component positioning is not critical, however, and constructors building the unit may employ any reasonable layout they wish. Miniature coaxial sockets should be used for the inputs, the sync socket and the output socket. There is no reason why the whole unit could not be built inside an oscilloscope, providing there is sufficient space on the front panel to

accommodate the extra controls and sockets.

#### Setting Up

Insert a milliammeter in series with one of the battery leads, switch on and check that the current is between 3 and 5mA. If all is well, remove the milliammeter and connect a lead from the "Oscilloscope" socket to the d.c. input of the oscilloscope. With the internal sync of the oscilloscope on, a square wave will appear on the screen. Next, connect a lead from the "Sync" socket of the unit to the oscilloscope external sync, and switch the latter

to external sync. Connect an audio frequency generator to the "Input 1" socket and adjust Input 1 gain to display a sine wave. Run another lead from the generator to the "Input 2" socket and set the Input 2 gain control to give a sine wave on the other trace. Adjusting the position potentiometer will move the traces as previously described.

Next, adjust the position control until the two traces are superimposed. Perfect meshing of the waveforms indicates that the phase shifts in the switch amplifiers are identical. This condition, it may be added, is easily obtained without matching transistors although, if a transistor tester should be available, it is worthwhile matching TR<sub>3</sub> to TR<sub>4</sub> and TR<sub>5</sub> to TR<sub>6</sub>.

Useful sync should be given even when the Input 1 gain control is close to, or at, zero level.

The best switching frequency depends on the ranges in the oscilloscope being used and the frequencies being examined. It is, of course, a simple matter to adjust S<sub>1</sub> whilst a particular waveform is being checked to find the best frequency.

#### Practical Uses

Having become familiar with the controls, let us test a valve or transistor a.f. amplifier. Connect an audio frequency generator to the "Input 1" socket of the switch unit, and to the input of the amplifier. Connect the output of the amplifier to the "Input 2" socket of the unit. With the unit coupled to the oscilloscope as already described, adjust the gain controls for equal amplitude on both traces. The signals can now be compared for distortion, and the result of any alterations made to the amplifier under test can be directly observed on the screen. Varying the frequency of the audio generator will indicate the high and low frequency cut-off points in the amplifier.

In company with all other electronic oscilloscope switches, this unit cannot give results equal to those obtainable with a double beam oscilloscope. Nevertheless, it will be possible in many cases to build it from the "spares box", and it is a very useful accessory. \*

## Anglia Prepares for Colour

Anglia Television's preparations for the start of their colour television service in 1970 has begun with an order for seven of EMI's highly successful Type 2001 colour camera channels. Vertical aperture correctors and encoders are also being supplied by EMI Electronics.

The latest contract, part of an extensive colour television expansion programme, brings the total value of orders received by EMI Electronics from Anglia to £190,000. Earlier contracts have covered sound and vision switching for a new Master Control, a vision mixer and remotely-controlled cameras for Presentation, a telecine chain and an eight-channel studio sound control desk.

**A** SCINTILLATION DETECTOR OR SCINTILLATION counter is one of the most important types of apparatus used for the detection of nuclear radiation.

### History

In the early years of this century a great deal of fundamental work on radioactivity and atomic structure was carried out by Rutherford and others using a very simple form of scintillation detector. Alpha particles from a radioactive source were allowed to strike a screen coated with phosphorescent zinc sulphide so that the energy of each alpha particle was converted into a minute flash of light (or scintillation). These flashes of light were counted visually in a dark room. Anyone who has attempted to count scintillations will appreciate how tedious and time consuming this experimental work is. It is necessary for a person to wait about ten minutes in a dark room for his eyes to become fully adapted to the dark before he can even see the scintillations. It was mainly for these reasons that interest in scintillation detectors declined when gas filled detectors (especially Geiger-Müller tubes) became available and were used with electronic counting equipment.

However, interest in scintillation detectors greatly increased when S. C. Curran and W. Baker used a phosphorescent material (or phosphor) in combination with a photomultiplier tube for the automatic counting of the scintillations (about 1944). The method was developed by H. Kallmann of Germany in 1947. Only alpha particles can be counted visually, because the flashes of light emitted when beta particles or gamma photons strike a phosphor are too weak to be detected by the eye. However, any type of nuclear radiation can be detected by the use of a suitable phosphor with a photomultiplier tube.

### Photomultiplier tubes

All conventional types of photomultiplier tube consist of a photocathode deposited on one end of the tube and a system of electrodes known as "dynodes". Two common types of tube are shown in Fig. 1.

When a very small amount of light strikes the specially prepared photocathode surface, electrons are emitted from the latter and are attracted to the first dynode by the applied potential. The dynode surfaces are also specially prepared so that each electron which strikes the surface will cause an average of about four electrons to be emitted ("secondary emission"). These secondary electrons are attracted to the next dynode and further multiplication takes place at this dynode surface. A typical photomultiplier tube contains about 10 to 12 dynodes and provides an overall amplification of perhaps one million. This amplification by secondary emission is, however, very dependent on the overall potential applied to the tube.

The photomultiplier tubes are constructed so that each electron emitted by any one dynode must strike the next dynode. This may be effected by the

# Scintillation Detectors and Photomultiplier Tubes

by M. J. Darby

Electronics covers a wide range, a not unimportant section of which is devoted to radiation detection. This short article offers a simple description of the operation of scintillation radiation detectors, these being devices which have important advantages when compared with Geiger-Müller tubes.

venetian blind or the box and grid structures shown in Fig. 1, but other types of photomultiplier tube employing focussing devices are also available. Special types of electron multipliers have recently been manufactured<sup>1,2,3</sup>, but so far as is known these have not yet been used for scintillation counting.

Photomultiplier tubes must always be used in a light-proof enclosure. They have a sensitivity which may exceed 10,000 amps per lumen and the photocathode will be damaged if any appreciable amount of light falls on it whilst potentials are applied to the tube. The tubes should be used only to detect light of extremely low intensity.

(Continued on page 230)

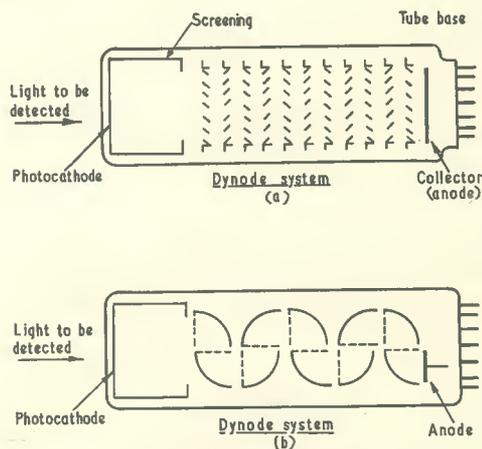


Fig. 1 (a). Scintillation photomultiplier using the venetian blind system  
(b). The alternative box and grid system



# Transistorised Telephone Amplifier

by B. T. H.

A simple high-gain telephone amplifier which amplifies all telephone conversations.

**T**HIS SIMPLE DEVICE ENABLES THE RECEIVED SIGNAL from a telephone to be reproduced at good volume from a loudspeaker. The amplifier pick-up signal is derived from an induction coil that is simply attached to the side of the telephone with a rubber sucker. The Telephone Amplifier can be of particular value in the following typical situations.

(1). Taking notes dictated over the telephone, in which case the Telephone Amplifier eliminates the need to hold the hand-set, and both hands are left free.

(2). Waiting while a secretary at the other end of the line spends half an hour trying to locate the party to whom one wishes to speak. In this case the Telephone Amplifier allows one to carry on working or relaxing some distance from the instrument, without fear of missing the connection when it is finally made.

(3). Receiving a call from a long-lost friend or relative in the presence of the whole family. In this instance the Telephone Amplifier allows the conversation to be shared by the entire family, thereby eliminating the constant shouts of "What's he saying? What's he saying?" that usually occur in such situations.

The unit described on these pages employs a five transistor circuit, has a built-in speaker, incorporates provision for volume adjustment, and costs about £3.10.0 to build.

## System Operation

The basic principle of operation of the Telephone Amplifier is illustrated in block diagram form in Fig. 1. Here, the communication signals flowing in the telephone lines pass through a coil in the body of

the telephone instrument, and in so doing create a magnetic field that fluctuates in sympathy with the speech signals; this coil is usually situated in the right-hand rear of a standard telephone instrument.

If a second coil is now placed in the fluctuating field of the telephone coil, electrical signals corresponding to the original speech signals are induced into this second coil, which thus functions as an inductive pick-up unit. The pick-up signals can then be amplified and fed to a loudspeaker or some other device, as required.

In practice, the pick-up signals from the inductive unit are very weak, and must be subjected to considerable amplification before they can be fed to a loudspeaker. In the Telephone Amplifier described here, the pick-up signals are first fed to a high-gain pre-amplifier and then on to a power-amplifier stage before finally reaching the loudspeaker.

The actual inductive pick-up coils used in a system of this type are available, ready-built, at moderate cost from most component suppliers. In consequence so far as the amateur electronics enthusiast is concerned, the construction of the Telephone Amplifier system is mainly concerned with electronic amplifier assembly, and a practical circuit is shown in Fig. 2.

Here, the pick-up coil is connected, via a jack plug and socket, across VR<sub>1</sub> which functions as a volume control. A portion of the pick-up signal is then taken from VR<sub>1</sub> slider and fed, via C<sub>1</sub>, to the pre-amplifier stage given by TR<sub>1</sub> and TR<sub>2</sub>.

In the pre-amplifier stage TR<sub>1</sub> is wired as a common emitter amplifier, with bias network R<sub>1</sub>, R<sub>2</sub>, R<sub>5</sub> and C<sub>2</sub>, and having a split collector load comprising R<sub>3</sub> and R<sub>4</sub>. TR<sub>1</sub> collector is direct coupled to the

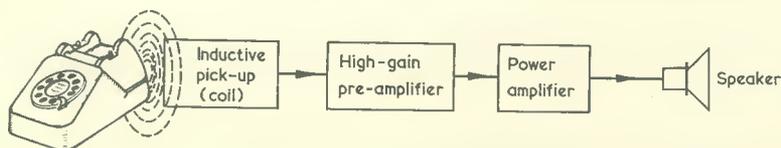


Fig. 1. Block diagram illustrating the functioning of the Telephone Amplifier

# Telephone Amplifier



Cover Feature

Hathaway

which gives loudspeaker reproduction of conversations.

base of TR<sub>2</sub>, which is wired as an emitter follower. TR<sub>2</sub> has a high input impedance and a low output impedance, and gives near-unity voltage gain with zero phase shift between input and output. Thus, the signal appearing at TR<sub>2</sub> emitter is virtually identical with that at TR<sub>1</sub> collector and is at a low impedance level. This output signal is fed, via C<sub>3</sub>, to the junction of R<sub>3</sub> and R<sub>4</sub> in the collector load of TR<sub>1</sub>; consequently, almost identical a.c. signals appear at both ends of R<sub>4</sub> when the circuit is operating, and very little alternating current flows in this resistor, which therefore behaves as if its a.c. resistance were far greater than its d.c. resistance. In other words, the feedback signal to the junction of R<sub>3</sub> and R<sub>4</sub> causes TR<sub>1</sub> to behave as if it had an

exceedingly large value of collector load; the voltage gain of the circuit is consequently very high.

This technique of increasing the effective a.c. resistance of a component by the use of signal feedback is known as bootstrapping, and is widely used in modern transistor circuitry.

The greatly amplified pre-amplifier signal is taken, at low impedance, from the emitter of TR<sub>2</sub> and is fed, via C<sub>5</sub>, to the power amplifier stage incorporating TR<sub>3</sub>, TR<sub>4</sub> and TR<sub>5</sub>.

TR<sub>3</sub> is wired as a common emitter amplifier, with collector load R<sub>8</sub> and VR<sub>2</sub>. Also, the collector of TR<sub>3</sub> is d.c. coupled to the bases of TR<sub>4</sub> and TR<sub>5</sub> which are wired as complementary emitter followers, giving a very low impedance output signal at the

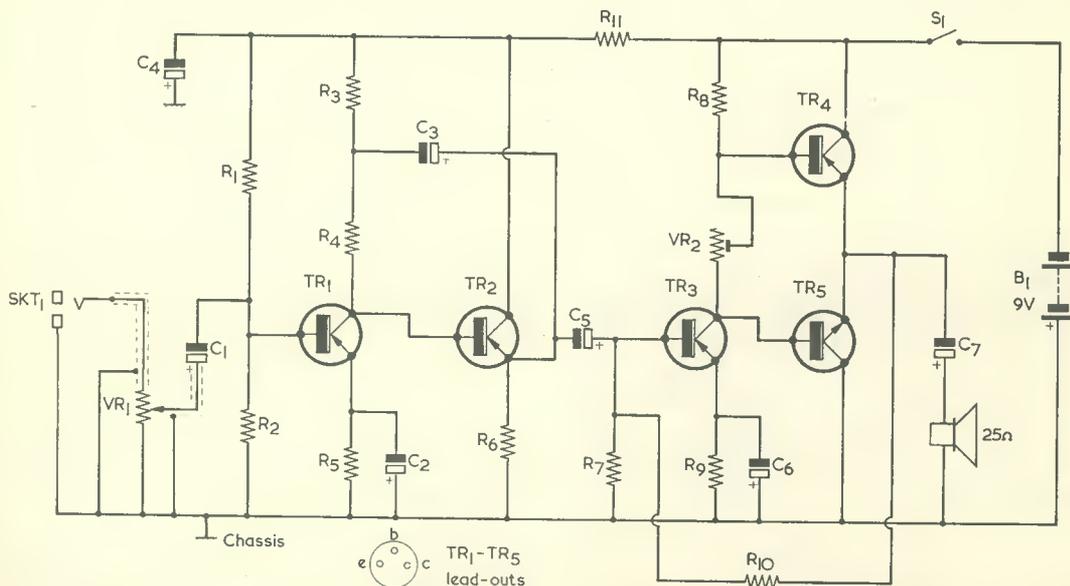


Fig. 2. Circuit diagram of the Telephone Amplifier. The pick-up coil (not shown here) couples into SKT<sub>1</sub> via a suitable plug and lead. S<sub>1</sub> is ganged with VR<sub>1</sub>

A - mounting holes; 6BA clear

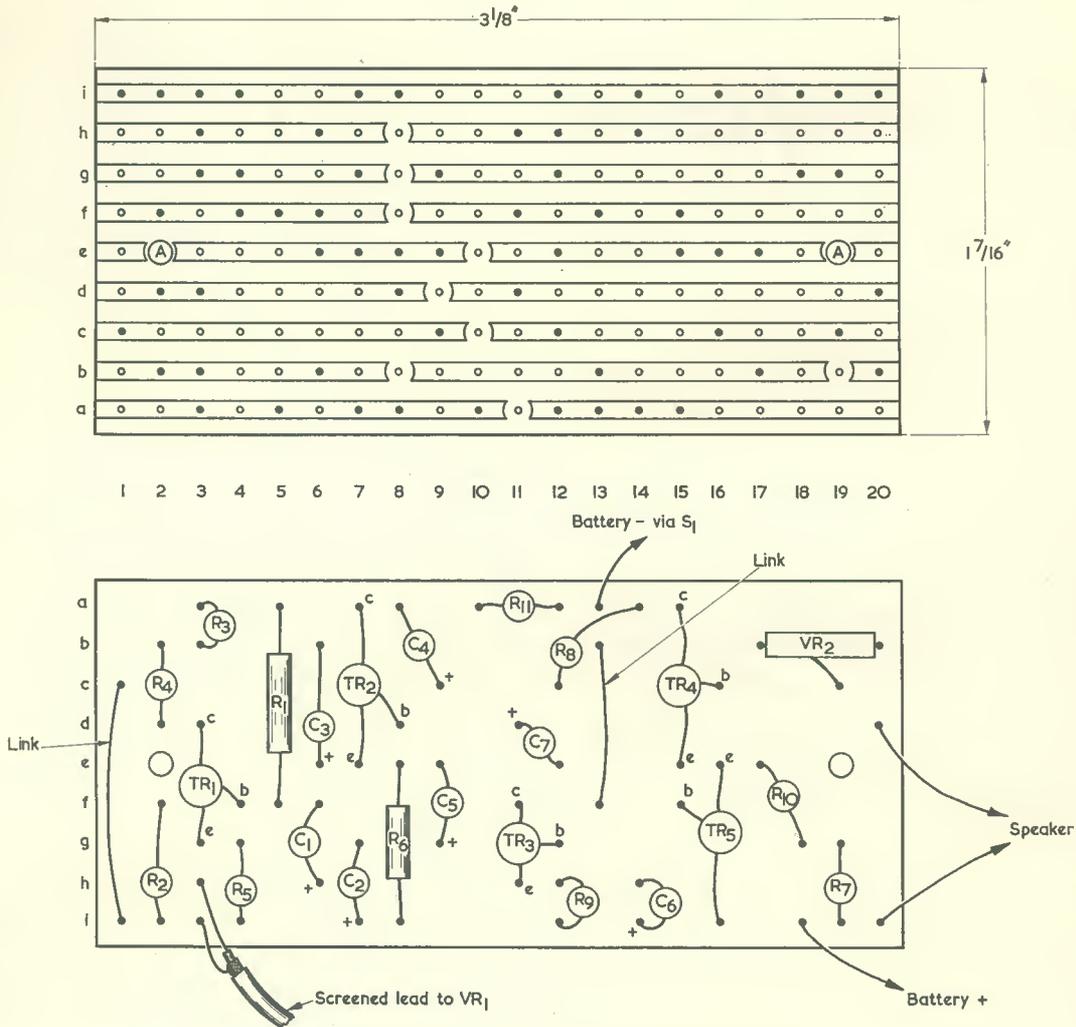


Fig. 3. The copper and component sides of the Veroboard panel

junction of TR<sub>4</sub> emitter and TR<sub>5</sub> emitter which is virtually identical in form to that at TR<sub>3</sub> collector. This low impedance output signal is coupled to the 25Ω speaker via C<sub>7</sub>. VR<sub>2</sub> enables the quiescent bias currents of TR<sub>4</sub> and TR<sub>5</sub> to be set to the correct operating levels. Base-bias for TR<sub>3</sub> is provided by R<sub>7</sub> and R<sub>10</sub>. These resistors also form a direct coupled negative feedback loop which helps to stabilise the bias levels and improve the fidelity of the power amplifier stages.

The power amplifier is decoupled from the pre-amplifier by C<sub>4</sub> and R<sub>11</sub>, the latter component being inserted in the negative supply line. The unit is powered by a 9 volt battery, and consumes a total current of approximately 6.5mA under quiescent conditions.

### Construction

The major part of the electronic circuitry is wired up on a small piece of Veroboard panel with 0.15in hole spacing, and construction should be started by cutting this panel to size and drilling the two small mounting holes, to clear 6BA screws, as shown in Fig. 3. Cut back the copper from the two mounting holes to prevent possible short-circuits, later, to the mounting screws. Next, break the copper strips, with the aid of a small drill or the special cutting tool that is available, as indicated.

Component assembly details, on the non-copper side of the panel, are also shown in Fig. 3. Note that all components other than R<sub>1</sub> and R<sub>6</sub> are mounted vertically on the panel, and that insulated sleeving should be used where there is any danger of com-

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{2}$  watt 10%)

R <sub>1</sub>	82k $\Omega$
R <sub>2</sub>	10k $\Omega$
R <sub>3</sub>	1.8k $\Omega$
R <sub>4</sub>	4.7k $\Omega$
R <sub>5</sub>	1k $\Omega$
R <sub>6</sub>	4.7k $\Omega$
R <sub>7</sub>	1.8k $\Omega$
R <sub>8</sub>	680 $\Omega$
R <sub>9</sub>	100 $\Omega$
R <sub>10</sub>	12k $\Omega$
R <sub>11</sub>	560 $\Omega$
VR <sub>1</sub>	5k- $\Omega$ potentiometer, log track, with on-off switch S <sub>1</sub>
VR <sub>2</sub>	100 $\Omega$ potentiometer, skeleton preset, vertical

### Capacitors

(All capacitors miniature electrolytic)

C <sub>1</sub>	16 $\mu$ F 12V wkg.
C <sub>2</sub>	30 $\mu$ F 6V wkg.
C <sub>3</sub>	16 $\mu$ F 12V wkg.
C <sub>4</sub>	50 $\mu$ F 12V wkg.
C <sub>5</sub>	16 $\mu$ F 12V wkg.
C <sub>6</sub>	50 $\mu$ F 6V wkg.
C <sub>7</sub>	160 $\mu$ F 10V wkg.

### Transistors

TR <sub>1</sub>	2G374 (Texas)
TR <sub>2</sub>	2G374 (Texas)
TR <sub>3</sub>	2G374 (Texas)
TR <sub>4</sub>	2N1307 (Texas)
TR <sub>5</sub>	2N1306 (Texas)

(N.B. In case of difficulty, the transistors may be obtained from L.S.T. Components, 23 New Road, Brentwood, Essex.)

### Switch

S<sub>1</sub> s.p.s.t., part of VR<sub>1</sub>

### Battery

B<sub>1</sub> 9-volt battery type DT7 (Exide)

### Pick-up Coil

Telephone pick-up coil (recording adaptor) with lead and jack plug. (Henry's Radio)

### Socket

SKT<sub>1</sub> Jack socket, to suit pick-up coil plug

### Speaker

25 $\Omega$  speaker, 3in

### Miscellaneous

Veroboard with 0.15in hole spacing,  $3\frac{1}{2}$  x  $1\frac{1}{8}$ in (see Fig. 3)  
Sheet aluminium, grommets, connecting wire, insulated sleeving, screened lead, etc.

ponents short-circuiting against one another. The mounting legs of VR<sub>2</sub> should be reduced in diameter with the aid of a small file, so that they fit easily in the holes in the Veroboard, before attempting to solder this component in place. Particular care should be taken to ensure that all transistors and electrolytic capacitors are correctly orientated when they are soldered in place.


Once component assembly on the Veroboard panel is complete the unit can be given a simple functional check in the following manner. Set VR<sub>2</sub> for zero resistance (slider at TR<sub>4</sub> end of the track), short-circuit the screened input leads together and connect up the speaker. Also, connect up the battery with a meter in series and check that the total current of the unit is less than 7mA. Then check that TR<sub>1</sub> collector, TR<sub>2</sub> emitter, TR<sub>3</sub> collector, and the emitters of TR<sub>4</sub> and TR<sub>5</sub> are all at a potential of  $4.5V \pm 1V$  with respect to either supply line.

If satisfactory, the rest of the unit can now be made up. Bend, cut, and drill the chassis, battery holder, and front panel, as shown in Fig. 4.

Fig. 4(a) gives a front view of the front panel, which is made from aluminium sheet. Holes A are 6BA clear and are used for securing the main chassis to the panel. Holes B are for fixing the front panel to the cabinet and are drilled as required. Hole C is  $\frac{3}{8}$ in diameter and takes VR<sub>1</sub>, whilst hole D has a diameter to suit the input jack socket SKT<sub>1</sub>. In the prototype the speaker was fixed to

the back of the front panel by impact adhesive, this being found quite satisfactory in practice, but if the constructor prefers to bolt or clamp the speaker to the panel, suitable holes may also be drilled at this stage.

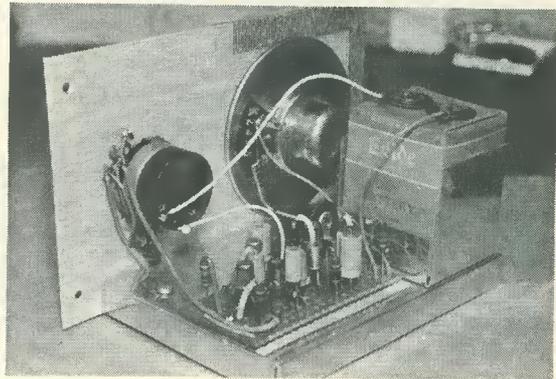A top view of the chassis, also made from aluminium sheet, is given in Fig. 4(b). The four aprons are bent down, away from the reader. The battery holder is shown in Fig. 4(c) and is made from light aluminium. In the prototype the holder was secured to the main chassis with impact adhesive at the position indicated in Fig. 4(b)



Rear view of the amplifier outside its cabinet

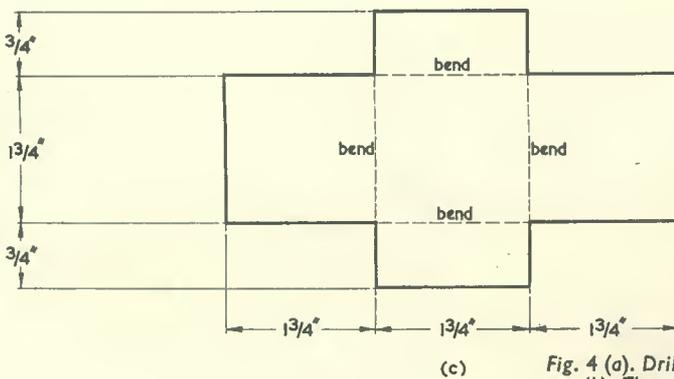
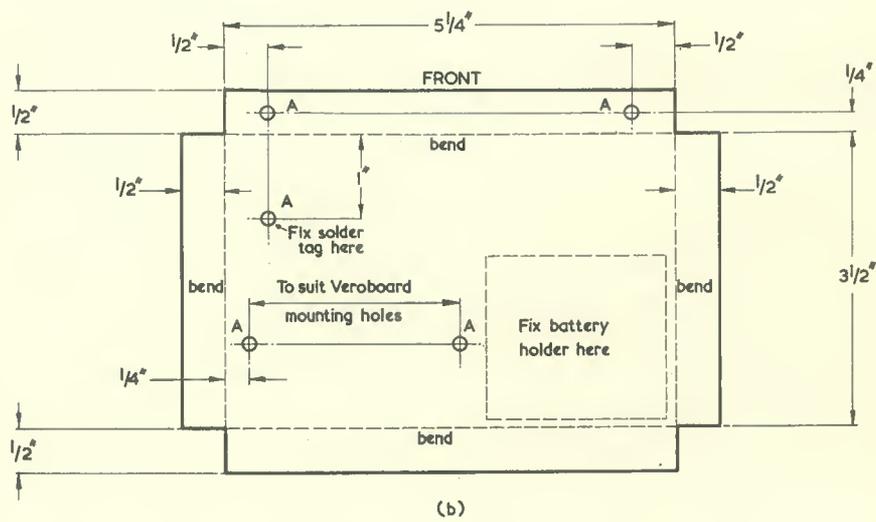
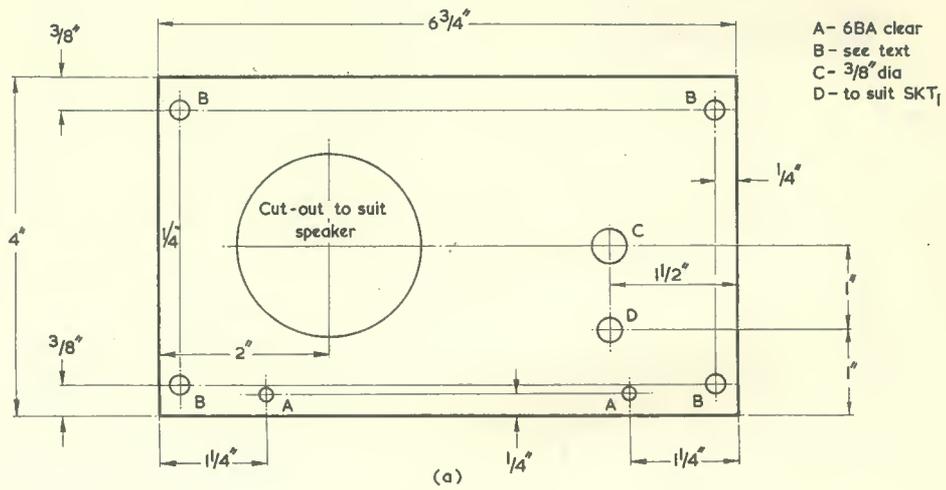


Fig. 4 (a). Drilling details for the front panel  
(b). The main chassis before bending  
(c). The battery holder

but it can alternatively be bolted in position, where-upon suitable holes may now be drilled in both parts.

The three parts of Fig. 4 should be made up as illustrated. Next, cover the front panel with a self-adhesive decorative plastic and speaker fabric, if required, and fix the speaker to the front panel with an impact adhesive (or by any other mounting method preferred). Fit  $VR_1$  and socket  $SKT_1$  to the front panel.

Now bolt the main chassis to the front panel, and mount the battery holder in position, using impact adhesive or bolts, as desired. Next secure the Veroboard panel to the main chassis, taking care to interpose two small rubber or p.v.c. grommets between the underside of the Veroboard and the chassis to act as spacer-insulators. A spare piece of self-adhesive plastic can be secured to the chassis below the Veroboard to act as an additional insulator if required.

Fix a solder tag to the main chassis as shown in Fig. 4(b), and wire up the final circuit in the following manner. Connect the negative Veroboard lead to the negative battery terminal via  $S_1$ , connect the positive Veroboard lead to the positive battery terminal, and wire up the speaker. Connect the screened lead from the Veroboard panel to  $VR_1$  and a second screened lead from  $VR_1$  to socket  $SKT_1$ . Connect the earthy tag of  $VR_1$  to the solder tag fitted to the main chassis. The braiding of both screened leads connects to the earthy tag of  $VR_1$ .

The unit is now complete and ready for use, and can be fitted in a suitable cabinet.

#### Using The Unit

Before putting the amplifier to permanent use, it must be set up in the following manner.

Plug the inductive pick-up coil into  $SKT_1$ , connect a current meter in series with the battery, move the telephone hand-set well away from the amplifier, and switch on. Now, after dialing "TIM" or a similar service, move the pick-up head around the telephone instrument until a position of



A closer view of the assembled Veroboard panel. Transistor  $TR_1$  is to the left

maximum signal strength is found, and then fix the pick-up head in place with the rubber sucker. Adjust the volume control as necessary.

Once a good signal has been obtained in the above manner, adjust  $VR_1$  for low volume and then adjust  $VR_2$  for minimum current reading in the meter consistent with low cross-over distortion. This will normally be obtained with a quiescent current of about 6.5mA. Once set as above, the unit is ready for permanent use.

It should be noted that if the volume of the amplifier is set too high or the telephone hand-set is placed too close to the speaker, acoustic feedback will result and the system will "howl". This occurrence should be guarded against when fixing the equipment in position. If the inductive pick-up is to be semi-permanently fixed to the telephone body, it is recommended that the rubber sucker be lubricated with brake fluid or a similar oil rather than water, since the oil has a low rate of evaporation and will therefore retain the necessary vacuum for very long periods of time.



## EMI U.H.F. Aerials

Contracts totalling £400,000 have been awarded to EMI Electronics by the BBC and ITA for the supply and erection of UHF transmitting aerials. These will extend the range of current BBC-2 colour programmes and provide the facilities for the UHF duplication of existing VHF transmissions.

The new aerials, consisting of Emislot panels and varying in aperture from 20 feet to 72 feet, will be cantilever-mounted on existing masts and towers and enclosed in 5ft. diameter fibreglass cylinders. The cylinders reduce the wind-loading effect by one-third and provide protection against the weather for both aerials and maintenance staff.

The sites involved are the BBC structures at Crystal Palace, Cotingtons Hill in Hampshire and Waltham-on-the-Wolds, Leicestershire, and the ITA installations at Caradon Hill, Cornwall, Sandy Heath, Bedfordshire, Moel-y-Parc, Flintshire, and Angus near Dundee. Under the co-siting agreement UHF aerials are used by both broadcasting organisations. The 650ft. Crystal Palace tower will carry two co-linear aerials, each of 27ft. aperture, which replace the original aerial supplied by EMI for experimental purposes.

The sub-contractors for the erection work are the B.I.C.C. Company Ltd. and J. L. Eve Company Ltd.

## Scintillation Detectors and Photomultiplier Tubes

(Continued from page 223)

The photocathode material must, as in a photocell, be chosen according to the wavelength of the light which is to be detected. Antimony-caesium are often employed. Even in the absence of light a few electrons will be emitted from the cathode, since they will gain enough heat energy to leave the cathode. They give rise to spurious or background counts. The background counting rate can be reduced by cooling the photomultiplier tube in a refrigerator, since this will reduce the number of electrons leaving the cathode when the latter is in complete darkness.

### Typical Circuit

A typical circuit for a photomultiplier tube is shown in Fig. 2. A potential divider chain is required to enable appropriate potentials to be applied to each of the dynodes, so that the electrons are suitably accelerated. When photons of light fall on the photocathode, the emitted electrons are multiplied in the dynode chain and a pulse of current flows in the anode circuit. This pulse is coupled to the first amplifier valve via the capacitor  $C_2$ . After suitable amplification the pulses are counted electronically.

The e.h.t. potential is normally in the range 700 to 1,800 volts, depending on the amplification required. Pulse output voltages of somewhat over 1 volt can be obtained when high potentials are

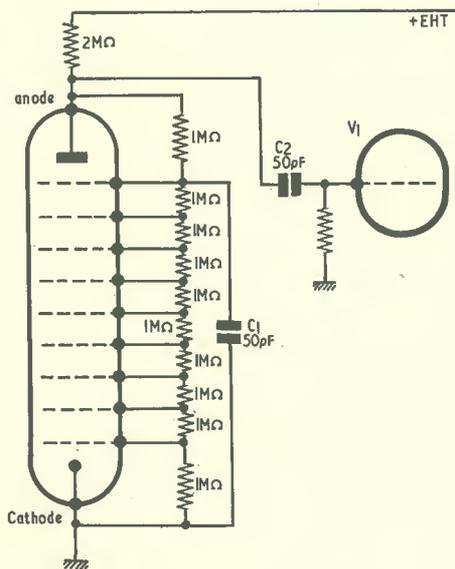


Fig. 2. A typical circuit for a photomultiplier tube.

applied to the tube, but optimum noise performance is obtained at smaller applied voltages.

The output pulses produced by a Geiger counter are all of the same amplitude if the potential applied to the tube is kept constant. In the case of a scintillation counter, however, the number of photons produced in the phosphor is (under certain conditions) proportional to the energy of the particle of radiation being detected. After photoemission and amplification has taken place, the anode current (and hence the output pulse voltage) will also be proportional to the energy of the incident particle which gave rise to the pulse. Thus if the pulses are sorted into various channels according to the amplitude of each individual pulse, it is possible to count the pulses due to particles of each energy separately.

### Phosphors

The phosphor used to convert the energy of the nuclear radiation into light must be chosen according to the type of radiation which is to be detected. A screen coated with impure zinc sulphide can be used to detect alpha radiation. The alpha particles reach the phosphor via a very thin aluminium window. Phosphors of naphthalene may be used for beta detection, whilst a large crystal of sodium iodide containing a trace of thallium iodide can be used as a gamma detector. The efficiency of the latter is much greater than the efficiency of a Geiger tube for gamma detection. Potassium iodide is not suitable for use as a phosphor, since potassium is weakly radioactive and would give rise to a steady background count.

Very low energy particles (such as those from tritium) are often counted by a liquid scintillation technique, since they do not have enough energy to penetrate even a thin window. In liquid scintillation counting the specimen of the radioisotope is mixed with an organic phosphor dissolved in a solvent. The resulting liquid is placed inside the dark enclosure in front of the photomultiplier tube cathode.

### Cerenkov Detectors

Photomultiplier tubes are also used in Cerenkov detectors. P.A. Cerenkov discovered in 1934 that a weak bluish-white light is emitted from transparent materials when high energy radiation passes through them. This phenomenon was explained in 1937 as being due to a kind of electromagnetic shock wave which arises when a charged particle at nearly the velocity of light enters an optically denser medium. The velocity of light itself is lower in the second medium and the particle velocity therefore quickly falls, so that the particle is not travelling at a velocity exceeding that of light in the second medium. Light is emitted in this process. The phenomenon is somewhat analogous to the sound shock wave produced when an aircraft breaks the "sound barrier".

A Cerenkov counter is very similar to a scintillation counter, but a transparent medium such as glass or water is used instead of a phosphor. The

light emitted by a single particle of radiation is much weaker in intensity than that emitted in normal scintillation counting. (However, those who have seen a really large source of radiation of about one million curies shielded beneath water cannot fail to be impressed by the beautiful bluish-white Cerenkov light which is emitted.)

#### Other Uses

Photomultiplier tubes are used in various types of optical equipment. For example, they often find application in flying spot scanners, in equipment for counting and sizing microscopic particles, in photometry, and in spectroscopy, etc.

#### References

1. G. W. Goodrich and W. C. Wiley. "Resistance Strip Magnetic Multiplier", *Rev. Sci. Instr.*, Vol. 32, p. 846 (1961).
2. J. Adams and B. W. Manley. "The Channel Electron Multiplier", *Electronic Engineering*, Vol. 37, p. 180 (1965).
3. J. B. Dance. "Resistive Film Electron Multipliers", *The Radio Constructor* July 1966.

#### Suggestions for Further Reading

- J. Sharpe and E. E. Thomson. "Photomultiplier Tubes and Scintillation Counters", E.M.I. Document No. CP154 (1958).
- J. Sharpe. "Dark Current in Photomultiplier Tubes", E.M.I. Document No. CP5475 (1964).
- "Mullard Photomultiplier Tubes", Mullard Publication 23/007/D/E-4-'63.
- S. C. Curran. "Luminescence and the Scintillation Counter" Butterworth, 1953.
- J. B. Birks. "Scintillation Counters", Pergamon, 1954.
- C. C. Bell Jr. F. Newton Hayes. "Liquid Scintillation Counting" Pergamon, 1958.



## Lightweight Whip Aerial for 160-metres Mobile

by W. E. Thompson G3MQT

**Details of a simple base-loaded whip which, using a 64in telescopic aerial, resonates satisfactorily from 1,920 to 2,000 kc/s. An advantage of the design is that the parts may be readily obtained through normal home-constructor channels.**

**T**HIS SIMPLE BASE-LOADED WHIP WAS DESIGNED to be cheap and easy to make from readily procurable parts, to be weatherproof, and to be capable of being quickly erected or removed when necessary. It weighs no more than 9 ounces, and the cost to the author was only 30s. Performance is quite satisfactory so far as can be expected with aerials of this type on Top Band.


Once the design was formulated the aerial was made in a few hours, using only the usual tools to be found in most amateur workshops. Access to a lathe would have been of help, but not possessing one the writer managed with a file and a hand drill clamped in the bench vice for the small amount of turning necessary.

#### Construction

The accompanying diagram, which shows a sectional view of the assembly, will reveal the method of construction readily enough. The coil assembly is made up from three 6in lengths of Paxolin tubing obtained from Home Radio

(Mitcham) Ltd. One piece is  $1\frac{1}{2}$ in outside diameter, on which the coil is wound. Another piece is  $1\frac{3}{8}$ in outside diameter, from which two pieces  $\frac{3}{8}$ in long are cut from each end. This ensures getting two square ends! The rest of the  $1\frac{3}{8}$ in tubing is not required. The two short pieces are fitted to the ends of the  $1\frac{1}{2}$ in tube to serve as spacers for locating the outer cover, and to contain the coil ends. Two small holes in the coil former alongside the inside edges of the spacer are needed to secure the ends of the winding. The coil is close-wound with 24 s.w.g. enamelled wire to occupy the  $5\frac{1}{4}$ in length between the two spacers. This will take about 216 turns, using just over 2oz of wire, and will produce a coil of about  $440\mu\text{H}$ . The third length of tubing is  $1\frac{3}{8}$ in outside diameter, and this fits over the two end spacers so that it totally encloses the coil to keep it weatherproof, and to protect the winding from damage. As these Paxolin tubes have  $\frac{1}{16}$ in walls, they will be found to interfit closely.<sup>1</sup>
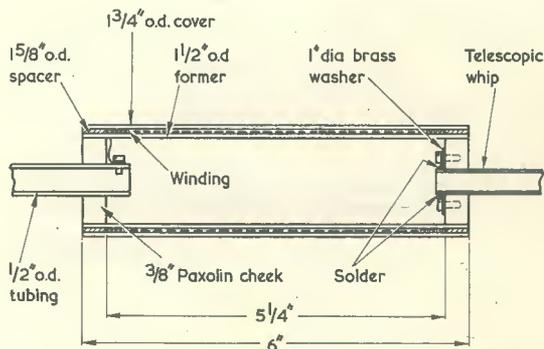
<sup>1</sup>The three Paxolin tubes are available in 6in lengths from Home Radio (Mitcham) Ltd. under Cat. Nos. ZA25 ( $1\frac{1}{2}$ in O.D.), ZA25A ( $1\frac{3}{8}$ in O.D.) and ZA25B ( $1\frac{3}{8}$ in O.D.). Wall thickness in these sizes is  $\frac{1}{16}$ in.—Editor.



Sectional detail showing the construction of the base-loading coil assembly. In the author's installation the  $\frac{3}{8}$ in tubing at the left is passed over an existing car radio aerial in the partially retracted position, thus enabling the 160 metre aerial to be quickly fitted and removed



*The whip aerial mounted on the existing car aerial*

Two end cheeks are required. These can be made from  $\frac{3}{8}$ in thick Paxolin, turned so that they fit reasonably tightly into the inside ends of the coil former. Those who possess a lathe might well use thicker material so that a lip can be formed to cover the edges of the Paxolin tubes.

A  $\frac{3}{8}$ in hole is made centrally in one cheek to take the bottom end of the telescopic whip. This whip is 8in closed, and 64in fully extended. It is obtained from Henry's Radio, Ltd.<sup>2</sup> The whip should be a tight fit in the cheek, but for additional strength it can be soldered to a 1in diameter washer made from thin sheet brass which is fixed to the inside of the cheek by two short 6BA screws. The tapped holes for these screws should be "blind" so that they do not pierce the surface of the cheek. One end of the coil can be connected to the whip by clamping the wire under one of the 6BA screws.

The other cheek has a hole drilled centrally to take the end of a 9in length of stout (17 s.w.g. wall) aluminium tubing,  $\frac{1}{2}$ in outside diameter. A slightly undersize hole, and some careful dressing of the tubing with fine abrasive paper, will ensure a force fit which should be quite secure. If necessary, the tube could be clamped to the cheek by some means (by pinning, or a grub screw, for example). It should protrude above the inside surface of the cheek sufficiently to take a small 6BA screw in its wall, to which the other end of the coil is connected.

At this stage of construction the coil ends may be finally connected to the telescopic whip and to the 9in aluminium tubing, keeping the wire lengths as short as possible. The end cheeks are then secured to the coil former. The faces of the cheeks should be level with the ends of the Paxolin tubes. Three holes are needed at each end, spaced 120 degrees circumferentially, drilled and tapped 6BA to a depth of about  $\frac{1}{2}$ in. Countersunk screws should be used. If the whole coil assembly is now sprayed with three or four coats of Holt's "Dampstart",

<sup>2</sup>The 8in x 64in telescopic aerial used by the author was listed as Type D in pre-1967 Henry's Radio catalogues. The current 8in x 64in aerial available from Henry's Radio is listed as Type TA13. To ensure a tight fit, check the diameter at the base of the TA13 aerial before drilling the hole in the Paxolin cheek.—Editor.

which can be obtained in aerosol cans from a garage or a motor accessory shop, the aerial will be rendered quite weatherproof. Several thin coats are better than fewer thick ones, but each coat should be allowed to dry off before applying another.

### Fitting To The Car

Readers will probably have their own ideas of where and how to fix the whip to a car, but the method adopted by the writer may be of interest. His car already had a car radio aerial mounted on the off-side front wing. This aerial retracts into the wing and locks in the closed position when not in use. When it is unlocked it springs up, revealing some 4 to 5in of the bottom section with the other sections still retracted in it. This seemed the obvious place to mount the 160 metre whip, since the coaxial feeder would serve for both aeriels.

The inside of the aluminium tube at the base of the 160 metre whip was carefully enlarged with fine abrasive paper wrapped around a rat-tail file until a smooth sliding fit was obtained on the car radio aerial. It is now only a moment's task to erect or to dismount the mobile whip and, when mounted, it is quite secure and safe. Being very light and thin it offers little wind resistance, and the telescopic top bends only slightly at speeds up to the legal maximum of 70 m.p.h. The writer has no idea what it would do at higher speeds because he has no desire to get pinched for speeding.



*The neat appearance of the 160 metre whip when mounted in position*

### Tuning

The aerial is tuned in the usual way by adjusting the length of the telescopic top section and noting the effect on a field-strength meter. When resonated at a particular frequency, the setting holds good for about 10kc/s each side of resonance. It has been found that the aerial performs best from about 1,920 to 2,000kc/s. At lower frequencies it is admittedly somewhat temperamental. This suggests that a coil slightly higher in inductance would cover the lower frequency range better, but this has not been investigated in practice as the writer rarely uses Top Band frequencies below 1,900kc/s when mobile.

### Some Results

The best contact made when mobile with this aerial was on the A.13 travelling from the exit of the Dartford Tunnel towards Dagenham, when a satisfactory two-way contact was established near West Thurrock with G3SZC/A in Whitstable, Kent, and held until signing out near Dagenham, about 36 miles from Whitstable along the Thames

Estuary. The topography and propagation conditions at the time were favourable factors, but mobile contacts made at other times show that ranges of 15 to 20 miles are often achieved.

When the aerial was in its infancy on G3MQT/M a contact was made one evening at Pembury, Kent, with G6TQ at Tonbridge some 4 miles away when driving in pouring rain. This contact was held while travelling down the A.21 towards Hastings until near Whatlington, some 18 miles from G6TQ. Even though the rain was bucketing down the aerial held its tune.

### Conclusion

This aerial has been in use for over a year, has been out in all weathers, and has stood the test of time and many miles of motoring. It has attracted favourable comment at mobile rallies, such as Pegwell Bay, Longleat, South Shields, and others. Taking all things into consideration the design fills the writer's needs quite adequately, and it is thought to be of sufficient interest for the information to be passed on to others.



---

## CAN ANYONE HELP ?

*Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time*

**Pye V.H.F. Transmitter & Receiver Units, Type PTC113.**—N. T. Shepherd, 10 Worth Park Avenue, Pound Hill, Crawley, Sussex,—borrow or purchase any information.

6V6, 2 x 6SL7, with variable tape speed. Circuit diagram, manual or any information.

**ARC-5 Command Receiver.**—H. A. Kemp, Lower Cliff Farm, Strines, Stockport, Cheshire,—designated R-27/ARC-5, any information.

**V.H.F. Receiver Unit 62A.**—F. Shacklock, 3 Sycamore Road, Nottingham,—serial No. AP67590 (1957), circuit, manual or any information.

**Minimitter MR44 Receiver.**—S. Smith, 19 Hyde Road, Kenilworth, Warks,—loan of circuit or handbook.

**Equipment Required.**—I. M. Jiggins, 12 Field End, Cheltenham Road East, Gloucester,—has undertaken to rebuild a Halifax Bomber for the Skyfame Museum at Staverton Airport. The project is greatly in need of the outer cases of the following equipment—ARI 5085 receiver, ARI 5153 indicator, ARI 5085 indicator and Mk XIV computer. Also required is a set of valves for the R1155 receiver.


**Reflectograph Tape Recorder.**—A. Nichols, 1 South Avenue, Swanton Morley, East Dereham, Norfolk,—model and type unknown, valve line-up is 2 x

**Philips BG290U/15 Receiver.**—D. Jones, 70 Gloucester Avenue, London, N.W.1.—purchase or borrow circuit diagram.

# UNDERSTANDING RADIO

## Phase-splitter Circuits

$$f = \frac{1}{2\pi\sqrt{LC}}$$

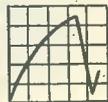

by W. G. Morley

IN LAST MONTH'S CONTRIBUTION TO THIS SERIES we commenced an examination of valve phase-splitter circuits suitable for providing out-of-phase a.f. voltages for application to the control grids of two output valves in push-pull. We then examined the split-load phase-splitter, this consisting of a single triode having equal values of resistance in its anode and cathode circuits. The out-of-phase voltages then appear at the anode and cathode of the triode.

We now carry on to further types of phase-splitter.

### The "Paraphase Amplifier"

A very simple phase-splitter circuit is illustrated in Fig. 1. In this diagram the input a.f. signal is applied, by way of  $C_1$  and grid resistor  $R_1$ , to  $V_1$ , which functions as a normal voltage amplifier. An amplified version of the input signal appears at the anode of  $V_1$ ,  $R_2$  being the anode load.

The anode signal from  $V_1$  is fed, via  $C_3$ , to the potentiometer given by  $R_4$  and  $R_5$ , the signal voltage

at the junction of these two resistors being passed to the grid of  $V_2$ .  $V_2$  is similar to  $V_1$ , and the two triodes could consist, in practice, of a double-triode valve.  $V_1$  anode load,  $R_2$ , is equal in value to  $R_6$ . Similarly, cathode resistor  $R_3$  is equal in value to  $R_7$ .  $C_2$  and  $C_4$  are electrolytic cathode bypass capacitors, and  $C_1$ ,  $C_3$  and  $C_5$  are a.f. coupling capacitors.

The signals for the control grids of the following push-pull stage are taken from the anodes of  $V_1$  and  $V_2$  via  $C_3$  and  $C_5$  respectively. The output via  $C_3$  is merely the input signal amplified by  $V_1$  whilst the output via  $C_5$  is the same signal after further amplification by  $V_2$ .  $V_2$  provides  $180^\circ$  phase reversal, with the result that the two signals are  $180^\circ$  out of phase, as is required of the circuit.

The input signal to  $V_2$  grid is attenuated by  $R_4$  and  $R_5$ , the attenuation being such that the output via  $C_5$  is equal in amplitude to the output via  $C_3$ , as is also required of the circuit. To see how the desired amount of attenuation is achieved, let us assume that  $V_2$  offers a voltage gain of 40.  $R_4$

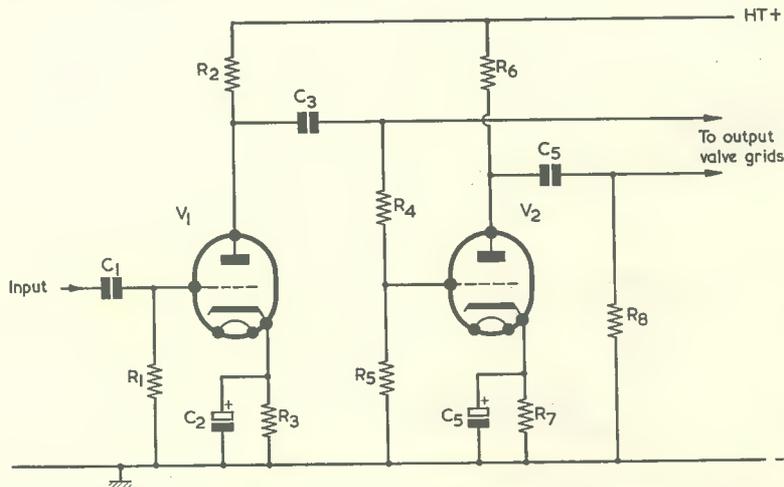


Fig. 1. The "paraphase amplifier" phase-splitter.  $V_2$  provides the requisite phase reversal

and  $R_5$  are then given values which ensure that  $\frac{R_4}{R_4 + R_5}$  of the signal voltage from  $C_3$  is passed to  $V_2$  grid. In general,  $\frac{R_4 + R_5}{R_5}$

gain of  $V_2$ .

$R_4$  plus  $R_5$  are equal to  $R_8$ , and it will be noted that  $R_4$  plus  $R_5$  can be used as the grid resistor for one of the push-pull output valves whilst  $R_8$  can be used as the grid resistor for the other push-pull output valve. Each output voltage is an amplified version of the input voltage, the amplification being that provided by  $V_1$ .

The cathodes of  $V_1$  and  $V_2$  may share a common cathode resistor and bypass capacitor, as in Fig. 2 (a). The single resistor should have half the value of either  $R_3$  or  $R_7$  in Fig. 1, since it is required to drop the same cathode bias voltage at twice the current. Since the a.f. currents passed by the cathodes of  $V_1$  and  $V_2$  are assumed to be equal and opposite, the bypass capacitor may be dispensed with, as in Fig. 2 (b). In practice, however, omitting the common cathode bypass capacitor may result in some unbalance at extreme high and low frequencies.

An advantage of the phase-splitter circuit under discussion is that both the triode cathodes couple to chassis via a low value resistor, with the result that there is less likelihood of hum pick-up from the heater supply than with the split-load phase-splitter we discussed last month. On the other hand the circuit suffers from the disadvantage that, for good balance,  $R_4$  and  $R_5$  have to be adjusted to cater for the actual voltage gain provided by  $V_2$ . Thus,  $R_4$  and  $R_5$  may need to be altered if a new valve is fitted in the  $V_2$  position or if the voltage gain offered by the existing valve varies as it ages. The changes in value could be conveniently made, incidentally, by replacing  $R_4$  and  $R_5$  by a preset potentiometer, as in Fig. 2 (c). A further disadvantage is that the output signal obtained from  $V_2$  has undergone an extra stage of amplification, and may in consequence be a slightly distorted version of that obtained from  $V_1$ . Also, the signal obtained from  $V_2$  passes through an extra capacitor,  $C_5$ , whereupon some unbalance at the lower audio frequencies, where the reactance of  $C_5$  becomes appreciable, may occur. This last point can be of importance in high quality or high fidelity applications.

The phase-splitter of Fig. 1 is sometimes described as a "pharaphase amplifier". However, the word "paraphase" tends to be applied to other amplifying circuits which offer two push-pull outputs for a single input, and this fact should be borne in mind when references to the term are encountered.

### See-Saw Phase Inverter

Fig. 3 shows a phase-splitter circuit which is known as a "see-saw phase inverter". For the circuit to function correctly,  $R_4$ ,  $R_5$  and  $R_6$  are closely matched in value, which can be typically  $1M\Omega$ . Also, capacitor  $C_2$  should have negligible reactance at the audio frequencies it is intended to handle.  $R_2$  and  $R_7$  are merely anode load resistors. Both have the same value, which is that normally em-

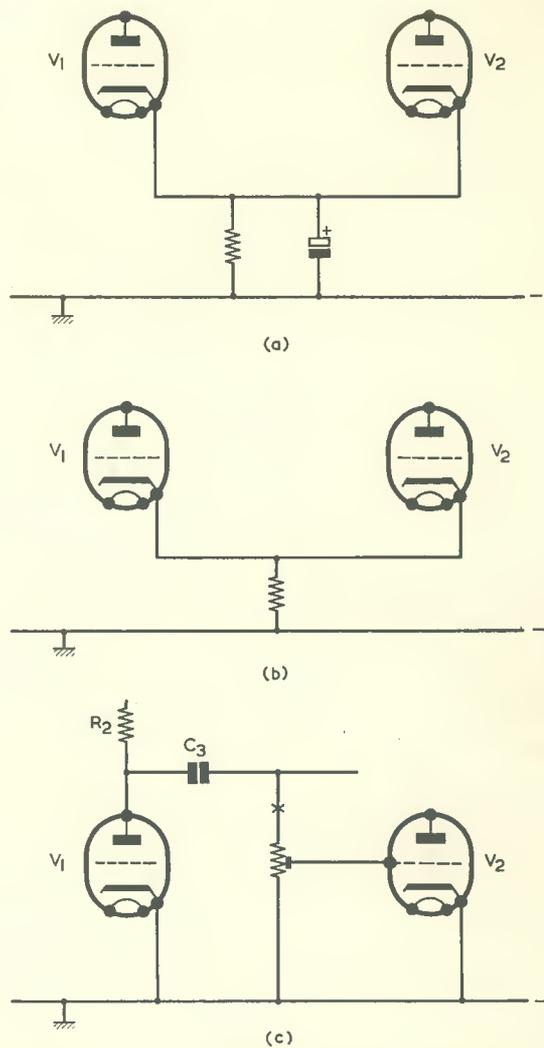


Fig. 2 (a). The separate cathode resistors and bypass capacitors in Fig. 1 may be replaced by a single cathode resistor and bypass capacitor, as shown here  
 (b). The bypass capacitor may also be omitted, and a single cathode resistor employed on its own  
 (c). For convenience of adjustment,  $R_4$  and  $R_5$  of Fig. 1 can be replaced by a preset potentiometer. A fixed resistor inserted at the point marked with a cross could be added to limit the range offered by the potentiometer and make its setting-up easier to carry out

ployed by either triode when used as a voltage amplifier. The two cathodes of the double-triode are connected together and couple to chassis via cathode bias resistor  $R_3$ . As we shall see shortly, there is no necessity for a cathode bypass capacitor. Capacitors  $C_1$ ,  $C_3$  and  $C_4$  are a.f. coupling capacitors, and  $R_1$  is the grid resistor for  $V_1$ . The two outputs provide out-of-phase signals for the grids of a following push-pull output stage.

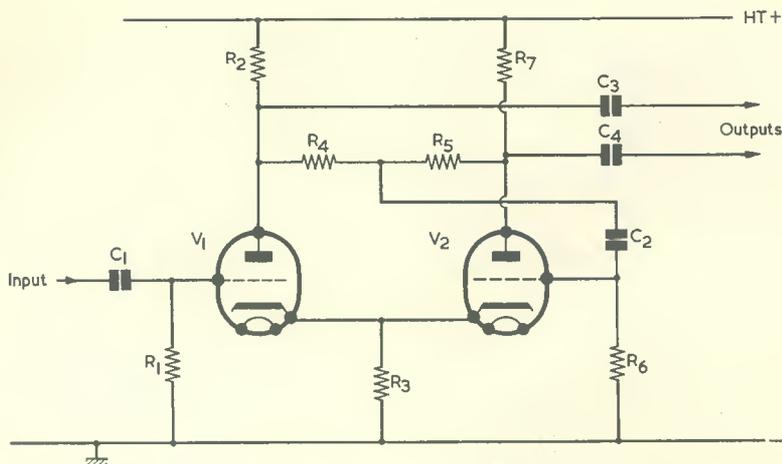


Fig. 3. The "see saw phase inverter". In this circuit  $R_4$ ,  $R_5$  and  $R_6$  are closely matched in value.

When an a.f. input is applied to the grid of  $V_1$  an amplified signal appears at its anode. Ignoring the action of  $V_2$  for the moment, this signal is applied to the potentiometer given by  $R_4$  and  $R_6$  ( $C_2$  has negligible reactance) and a portion is applied to the grid of  $V_2$ . Thus, the grid of  $V_2$  has applied to it a signal of the same phase as that at the anode of  $V_1$ .  $V_2$ , whose action we have ignored up to now, amplifies this signal and an amplified version,  $180^\circ$  out of phase with that at  $V_1$  anode, appears at the right-hand end of  $R_5$ . In consequence, when the operation of  $V_2$  is considered we find that amplified signals of opposite phase appear at the outside ends of  $R_4$  and  $R_5$ , the signal at their junction being fed to the grid of  $V_2$ .

Because the values of  $R_4$ ,  $R_5$  and  $R_6$  are equal,

the circuit has an automatic tendency to give output signals of nearly equal voltage amplitude. If, for some reason, the amplitude of the signal at the anode of  $V_2$  were to decrease, the signal at the junction of  $R_4$  and  $R_5$  would contain a higher proportion of the  $V_1$  anode signal. This higher proportion would be applied to the grid of  $V_2$ , resulting in an increase in signal amplitude at  $V_2$  anode which would counteract the previous decrease. Put another way, the circuit stabilises because the amplitudes of the signals at  $V_2$  anode and grid are interdependent; the anode signal amplitude must always be that which causes the corresponding signal amplitude to appear at the grid. The equilibrium taken up by the circuit is such that the signal at the junction of  $R_4$  and  $R_5$  always contains

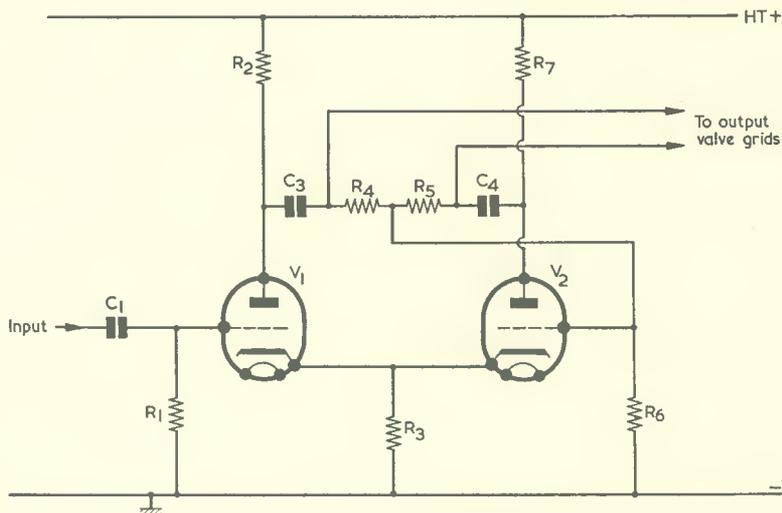


Fig. 4. A slight rearrangement of the circuit of Fig. 3 gives this "floating paraphase" phase-splitter, in which  $C_2$  is not required. Some "floating paraphase" phase-splitters have separate cathode bias resistors, with parallel bypass capacitors, for the two triodes

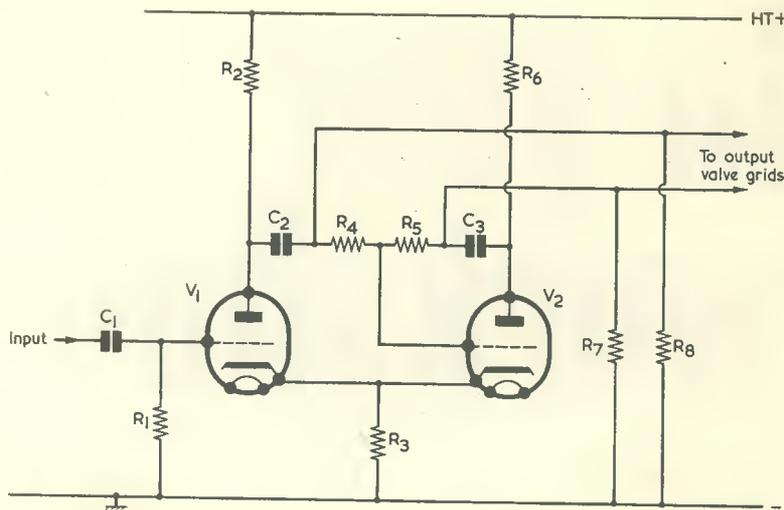


Fig. 5. A development from the circuits of Figs. 3 and 4. Only two closely matched resistors,  $R_4$  and  $R_5$ , are required here

a small proportion of the signal at the anode of  $V_1$ . To obtain output voltages in practice which are closely equal in amplitude,  $R_4$ ,  $R_5$  and  $R_6$  should be components having a tolerance of  $\pm 5\%$  or better, selecting  $R_5$  to have a slightly higher value than  $R_4$ . Also  $V_2$  should be a type offering a high degree of voltage amplification.

The "see-saw phase inverter" provides amplification, this being given by  $V_1$ . Each output has very nearly the same amplitude as would appear at the anode of  $V_1$  if this triode operated on its own as a normal voltage amplifier. Both output impedances are the same, and the two outputs in Fig. 4 may connect direct to the push-pull output grids. Also, the valve cathodes connect to chassis via a low-value resistor, with the result that hum pick-up from the heater supply is liable to be low.  $R_3$  has a value equal to half that of a normal cathode bias resistor for either triode on its own. There is no necessity to connect a bypass capacitor across  $R_3$  because it carries both anode currents, these being opposite in phase and (very nearly) equal. The phase splitter derives its name from the fact that the outer ends of  $R_4$  and  $R_5$  swing in the manner of the ends of a see-saw about a fulcrum, the latter being slightly to the right of their junction.  $V_1$  and  $V_2$  may, in practice, consist of a double-triode valve.

There are a number of phase splitter circuits which operate in a similar manner to that of Fig. 3. These can all be identified by the fact that they have two valves whose anodes feed into the distinctive pattern of three closely matched resistors (with the junction coupling to the grid of the second valve) given in Fig. 3 by  $R_4$ ,  $R_5$  and  $R_6$ . In some versions  $R_4$  and  $R_5$  may be grid resistors for the push-pull output valves, the anodes being coupled to them via coupling capacitors (see Fig. 4). Such circuits are generally described as "floating paraphase" phase splitters, the term "floating" deriving from the fact that the grid of the second valve is

connected to a "floating" point in the circuit. As was mentioned earlier, the term "paraphase" applies to an amplifier which converts a single input into two push-pull outputs.

If, with the circuit of Fig. 3,  $C_2$  presents appreciable reactance at the lower audio frequencies, some unbalance at such frequencies is possible. Unbalance of this nature is less liable to occur with the somewhat more symmetrical circuit of Fig. 4, where both anodes couple into  $R_4$  and  $R_5$  by way of coupling capacitors  $C_3$  and  $C_4$ , these having equal values.

A development of the circuits of Figs. 3 and 4 is given in Fig. 5, in which there are only two closely matched resistors,  $R_4$  and  $R_5$ . These resistors may similarly be of the order of  $1M\Omega$  in value.  $R_2$  and  $R_6$  are normal anode load resistors having equal values, whilst  $C_2$  and  $C_3$  are equal value a.f. coupling capacitors. The same self-balancing action occurs as with the previous circuits, the signal at the anode of  $V_2$  having an amplitude which causes the corresponding signal amplitude to be applied to its grid. This circuit provides slightly better balance than do those of Figs. 3 and 4. It will be seen that the grid of  $V_2$  is maintained at chassis potential so far as bias is concerned by way of  $R_4$ ,  $R_5$ ,  $R_7$  and  $R_8$ .  $R_7$  and  $R_8$  are the grid resistors for the output valves.


In the three circuits just discussed balance improves, in all cases, as the voltage gain offered by  $V_2$  increases. In consequence it is desirable to use a high gain valve here, and a suitable choice would be one section of an ECC83 double-triode. The other section of this valve can then be employed as  $V_1$ .

#### Next Month

In next month's issue we shall complete our examination of phase-splitters by discussing the Schmitt phase inverter, after which we shall introduce the subject of negative feedback.



# In your workshop

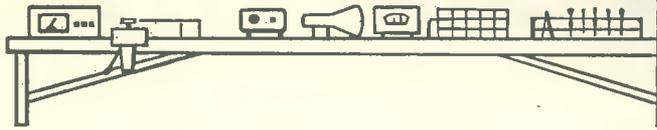

**Microphony is not a common trouble in transistor radios, but it still crops up every now and again. In this month's episode Dick has his first encounter with the fault, but he is soon shown how to clear it by Smithy.**

**W**ITH A GRUNT OF SATISFACTION, Dick fitted into place the last screw which secured the little printed circuit board of the medium and long wave transistor portable.

It had had an interesting fault: the  $0.01\mu\text{F}$  i.f. bypass capacitor immediately following the detector had decided to change its function in life from that of merely holding a charge to the more exciting exercise of passing current, and it had passed a wide variety of currents modulated by a.f. ranging from the Beatles to Tchaikowsky ever since it had arrived at this decision. Eventually, it passed the current from Dick's testmeter switched to an ohms range, whereupon its guilty secret was laid bare. As so frequently happens to those of us who have lost the capacity to meet our obligations, the capacitor was then forcibly removed from its fellows and thrown into the wretched company of the broken-down (i.e. Dick's waste bin), its place in the receiver being taken by a more disciplined brother of equal potential value.

After fitting the new capacitor, Dick had ensured that the receiver was working correctly in its disas-

sembled state, including a full volume check on what was now his favourite test transmission—Radio 1 on 247 metres. He had then applied his signal generator and carefully aligned the i.f. transformers. And, now, he was cheerfully turning home the last screw which held the printed circuit board in place in the cabinet.

## Microphony

Dick next fitted and connected the battery, closed the cabinet and switched on the receiver for its final check-out. An exploratory turn of the controls showed that the set had excellent sensitivity and selectivity on both medium and long waves. Dick finally switched to medium waves and once more selected Radio 1 on 247 metres. He turned the volume to its full setting and slightly adjusted the tuning. At once the receiver broke into a loud discordant howl. Startled, Dick reduced the volume level, whereupon the howl disappeared.

Dick cautiously advanced the volume control again, with the result that the howl became audible once more. He readjusted the tuning control and the howl disappeared. After further investigation Dick

discovered that the howl only occurred at a tuning point very close to the central position for the Radio 1 transmission and that it did not appear at any other setting of the tuning capacitor on either the medium wave band or the long wave band. He scratched his head and gazed despondently at the receiver which had developed this unexpected last-minute fault.

"Hey, Smithy!"

There was silence for a moment. Smithy the Serviceman, at his bench on the other side of the Workshop, was obviously fully preoccupied.

"Yes?" he replied eventually, and with manifest reluctance.

"I've got a real weirdie here," called out Dick to Smithy's back. "I'm getting a howl on just one station only."

"I know," said Smithy laconically. "I heard it over here."

"But what would cause a fault like that?"

"Is it a transistor set?" queried Smithy in return.

"Yes," replied Dick, puzzled at this reaction on Smithy's part, "as a matter of fact, it is."

"Then," stated Smithy firmly, "you've very probably got a microphonic tuning capacitor."

After which pronouncement Smithy, presumably satisfied that he had completely cleared up Dick's problem, once more proceeded to lose himself in the receiver he was repairing.

Dick glared furiously at the Serviceman's back, and returned to the attack.

"How," he persisted, "can you say it's the tuning capacitor if you haven't even *seen* the set?"

Warily, Smithy laid his test prods on his bench. He switched off the set on which he had been working, stood up and walked over to Dick's bench.

"I can see," he remarked resignedly, "that the quickest way of getting your troubles sorted out is to come over here and tackle them directly. What have you done with that set up to now?"

"To start off with," said Dick in reply, "I found the fault, which was a shorted i.f. bypass capacitor after the detector. I put in a new capacitor and, since there was just a slight possibility that changing it might have had an effect on the alignment of the last i.f., I gave the i.f. transformers a touch-up and put the printed board back into the case. After which, blow me if the set doesn't start to howl like a banshee every time I tune slightly to one side of Radio 1!"

"I think," said Smithy thought-

fully, "I can see what's happened here. Incidentally, there wasn't any real necessity to align the i.f.'s although it was a reasonable thing to do, I suppose. Did you line them up as recommended in the service sheet?"

"Oh, definitely," replied Dick promptly, picking up a service manual and passing it over to Smithy. "As you can see, the manual says the i.f. is 470 kc/s. I tuned the set to the high frequency end of the medium wave band, applied the signal generator via a 0.01 $\mu$ F capacitor to the fixed vanes of the signal frequency section of the 2-gang and set the genny up to 470 kc/s." (Fig. 1).

### I.F. Alignment

"Well," commented Smithy, "that's a pretty good start at any rate. When you're lining up the i.f.'s of a medium and long wave transistor radio you have to apply the i.f. signal to the base of the mixer-oscillator, and the method of coupling you've just described is as good as any. Also, it has the advantage that the fixed vane tag of the aerial tuning capacitor is easy to get at. By the way, some manufacturers state that the set should be tuned to the low frequency end of the medium wave band instead of the high frequency end before you line up the i.f.'s. So, for the very best results, you should really check the service literature before commencing the alignment. Still, your approach is good enough for general work."

Smithy looked briefly at the manual Dick had given him.

"After connecting up the signal generator," he continued, "what did you do next?"

"I lined up the i.f. transformers," said Dick simply.

"To 470 kc/s?"

"To 470 kc/s."

"All of them?"

"Of course."

"In," asked Smithy gently, "a set with staggered i.f.'s?"

"Who says this set has staggered i.f.'s?"

"I do, you steaming great nit," snorted Smithy wrathfully, returning the service sheet to Dick. "And so does this service manual! If you'd taken the trouble to read it more fully instead of merely glancing at the figure for the intermediate frequency, you'd have seen that the third i.f. transformer should be aligned to 470 kc/s, the second to 468 kc/s and the first to 472 kc/s!"

The Serviceman pointed an accusing finger at the section of the manual devoted to i.f. alignment.

"Well, stap me," said Dick, crestfallen, "I must have missed that bit!"

"I'll say you did," growled Smithy. "Anyway, you might as well line the i.f.'s up properly, now I'm over here. If we're fortunate, that's all that will be needed to get rid of that howl of yours. You can get at the i.f. cores quite easily whilst the set is in its case. You can also get at the injection point for the signal generator and the speaker tags as well."

"Why should I want to get at the speaker tags?"

"Because," replied Smithy, "I want to see the i.f.'s aligned correctly this time, and the best way of doing this is to either replace the speaker with an output meter switched to the speaker impedance or to connect a high resistance a.c. voltmeter across the speaker terminals. (Fig.2). You'll get much more accurate results using a meter to indicate the output level than by relying on your ears. I see that this set has got a 15 $\Omega$  speaker so you want to keep your signal generator at a level which causes the a.c. voltmeter to read about 0.9 volts."

Dick looked puzzled.

"Why 0.9 volts?" he asked.

"That voltage," explained Smithy, "corresponds to approximately 50mW in 15 $\Omega$ , and 50mW is the generally accepted standard output to be used when lining up loudspeaker radios, unless the makers state otherwise. With a 10 $\Omega$  speaker 50mW

corresponds to 0.7 volts, by the way, and with a 20 $\Omega$  speaker it corresponds to 1 volt. I should add that 50mW is a fairly low output power and the corresponding i.f. input is usually too small to allow the results of alignment to be heavily masked by a.g.c. The receiver volume control is, of course, turned to full whilst you do the alignment, and the a.c. voltmeter you connect across the speaker must present a resistance considerably higher than the speaker impedance."

"Fair enough," said Dick, as he reached for his testmeter, and switched it to a low a.c. volts range.

It did not take Dick long to make the requisite connections to the receiver.

"Here we are," he called out cheerfully, as he switched on the set. "All systems go! I'll start off with the third i.f. transformer at 470 kc/s."

Carefully, Dick adjusted the signal generator to this frequency and set its output level to give approximately 0.9 volts in his meter. He aligned the core of the third i.f. transformer.

"What did you say the frequency for the middle one was?"

"468 kc/s," replied Smithy.

Dick readjusted the signal generator frequency and aligned the second i.f. transformer, also adjusting the signal generator output for the required reading in his testmeter.

"The first one," he asked, "is 472 kc/s, isn't it?"

"That's right," confirmed Smithy.

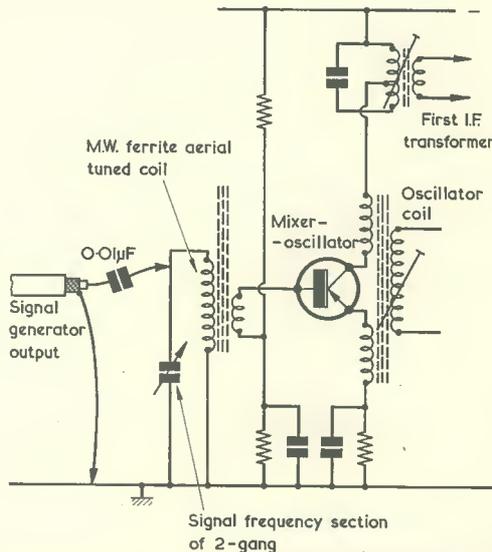


Fig. 1. The basic signal frequency circuit of a typical mixer-oscillator stage switched to medium waves. A convenient method of injecting an i.f. signal for alignment consists of applying the signal generator output, via a 0.01 $\mu$ F capacitor, to the signal frequency section of the 2-gang tuning capacitor

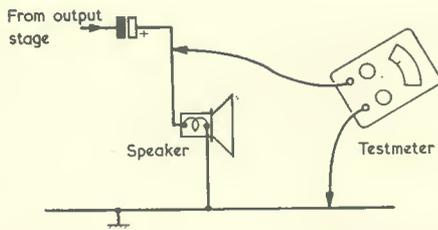


Fig. 2. Most transistor receiver manufacturers specify that the i.f. stages should be aligned with the receiver providing an a.f. output of 50mW. When the coupling from the output stages to the speaker is via an electrolytic capacitor, instead of via a transformer, the speaker impedance will be high enough to enable 50mW to correspond to a useful deflection in a testmeter connected across the speaker and switched to a low a.c. volts range

The alignment of the first i.f. transformer was soon completed, whereupon Dick switched off the receiver and disconnected the test equipment leads.

"I must admit," he remarked, "that it's a jolly sight easier to line up these i.f. transformers with a meter than it is by ear, because you get such a definite indication that you're at the peak."

"True enough," agreed Smithy. "I know there are a lot of service engineers who line up the i.f.'s of a radio by ear, thinking that it's a waste of time to connect up an output meter or, even, to clip a test-meter switched to an a.c. volts range across the speaker. In general, though, it's best to use the meter and it can often cause the actual alignment to be carried out more quickly, too. A further point is that the alignment will almost certainly be more accurate. Anyway, let's see if we've cleared that howl out of your receiver."

Dick switched on the receiver and tuned in the 247 metre Radio 1 signal.

"I get the impression," he remarked, "that the a.f. quality is a bit better. There seems to be more top."

"There should be," stated Smithy. "You've now got the i.f. response that the manufacturers intended, instead of the much narrower response which you introduced."

Dick turned the volume to full and tuned carefully through the Radio 1 signal. There was no trace whatsoever of any howl.

#### Acoustic Feedback

"Smithy," said Dick admiringly, "you're a genius."

The Serviceman breathed on the fingernails of his right hand and polished them nonchalantly on his lapel.

"I suppose," he remarked modes-

tly, "that I do have my occasional little successes."

"This is certainly one of them," said Dick jubilantly. "First of all, you make a correct diagnosis without even seeing the set, after which you get me to do the exact thing which is needed to cure the fault."

"I was a bit lucky there," confessed Smithy. "I was banking on the fact that your original i.f. alignment had made the skirts of the i.f. response a lot steeper than they should have been."

Dick's mood of elation at having successfully cured the fault changed to one of gloom as he considered the nature of the fault itself.

"So far as I'm concerned," he stated morosely, "this whole business is a complete mystery. You said at the beginning that the howl was very probably due to a microphonic tuning capacitor and I then cleared the fault just by realigning the i.f.'s. I'm baffled!"

"Don't let it worry you," said Smithy soothingly. "Everything is really quite simple, as I'll show you. The best way to explain what happens will be to start right at the beginning with this microphony

business. Have you ever bumped into a microphonic howl with an a.f. amplifier?"

Dick scratched his head for a moment, then his face brightened.

"Yes I have," he said. "Some years ago I had a valve tape recorder in for repair which howled like billy-oh on playback if you turned the volume up above a certain level. That was a dead easy snag, too. All I had to do was to replace the valve immediately following the playback head, which had gone microphonic. You could tell the valve was microphonic because, if you tapped it at a volume setting which was too low to bring on the howl, it sounded from the speaker as if you were bashing a Chinese gong!"

"Right," said Smithy. "Well, that situation represents about the simplest sort of acoustic feedback you can have. (Fig. 3). In this case you have a microphonic valve in an early stage of an a.f. amplifier, and it develops a signal voltage corresponding to any noise or vibration that impinges on it. If the sound from the speaker reaches the valve, either via the air or the hardware of the cabinet and chassis, or via a combination of the two, you have a positive feedback loop set up and the whole thing is capable of breaking into oscillation, resulting in what we often call an 'acoustic howl'. The usual reason for a valve going microphonic is that a mechanical fault has caused the control grid to lose its rigidity and to flap around. The valve offers the greatest microphonic effect at the mechanical resonant frequency or frequencies exhibited by the grid. In the howl which is then set up these frequencies tend to predominate and this factor gives the acoustic howl a distinctive quality that I can best describe as being 'mechanical' in nature."

"That effect," remarked Dick, "is similar to what you get when a

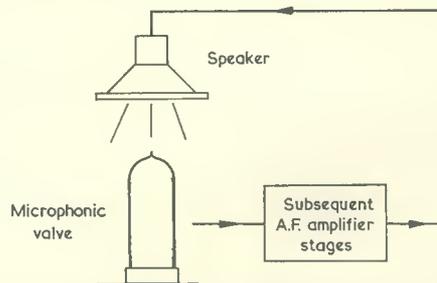


Fig. 3. If a microphonic valve in an early stage of an a.f. amplifier is subjected to sound from the speaker, a positive feedback loop is set up. If there is sufficient overall gain in the loop the system breaks into oscillation, causing an acoustic howl to be given by the speaker

public address microphone picks up too much signal from the speaker."

"True enough," confirmed Smithy. "In the public address case, though, the coupling back from the speaker to the microphone is via sound waves in the air only. When the loudspeaker is in the same cabinet as a microphonic valve, as occurred in your tape recorder, you get coupling by way of the hardware as well, as I mentioned just now. Anyway, let's press on! Now, a valve is a component which is well-known for becoming microphonic. Another component which is also well-known for microphony is an air-spaced tuning capacitor. As you can readily imagine, if the vanes of an air-spaced tuning capacitor are subjected to sufficient vibration, the capacitance it offers will vary at the frequency of the vibration. This is especially true if the capacitor vanes are thin and are very closely enmeshed, as occurs in the types which are used in medium and long wave radio receivers. In receivers of this type, the capacitor is also in the same cabinet as the speaker, whereupon an acoustic feedback path can exist between the two."

#### Feedback Path

"I can understand all that," said Dick, "but what puzzles me is how varying capacitance in a tuning capacitor can cause an a.f. signal to be fed to the speaker and allow an acoustic howl to be given. The effect *can't* be as direct as with a wobbly control grid in an a.f. amplifier valve."

"It isn't," agreed Smithy. "Nevertheless, the varying capacitance can be changed to a.f. if the capacitor in question tunes the oscillator of a superhet. Let's assume that we have an a.m. superhet, and we tune it to a signal. An i.f. signal equal to the difference between the signal carrier frequency and the oscillator frequency is then fed to the i.f. amplifier. If we cause the vanes of the oscillator section of the tuning capacitor to vibrate at an audio frequency and thereby change in capacitance, we are varying the oscillator frequency at the same rate. This means that the intermediate frequency fed into the i.f. amplifier is also varying at the same rate."

"But that," interrupted Dick excitedly, "is a frequency variation! If the set's an a.m. superhet, its detector won't respond to a frequency variation."

"It won't," confirmed Smithy, "but if the frequency variation is applied to the sloping skirt of the i.f. response due, perhaps, to slight detuning of the receiver, it becomes

converted to an *amplitude* variation, and the detector *can* respond to that. The overall feedback loop then includes the following processes. (Fig. 4). Mechanical vibration of the oscillator tuning capacitor vanes due to sound from the speaker produces an oscillator frequency varying at a.f., and the mixer then changes this to a varying intermediate frequency. If this varying i.f. is applied to a sloping part of the i.f. response, it becomes converted to an amplitude variation. The amplitude variation is then detected by the detector and passed on to the a.f. stages of the set. These amplify it and feed it to the speaker. So, provided there is sufficient gain in the loop, everything is set up for oscillation to occur and an acoustic howl to be given. This loop is more complicated than the microphonic valve one, because one of the processes in the loop is the conversion of frequency variation in the i.f. amplifier to amplitude variation. Also, feedback cannot take place unless a carrier is tuned in on the receiver and applied to the mixer in order that an i.f. can be formed. But the tendency to oscillate is still there, and if there is sufficient gain and the sound from the speaker can cause sufficiently high vibration in the tuning capacitor, the whole thing breaks into oscillation at the mechanical resonant frequency, or frequencies, of the vibrating parts of the capacitor. The resultant howl has the same distinctive 'metallic' character as with a microphonic valve, which is why I recognised that howl from your set as microphony when I first heard it."

A sudden gleam of enlightenment appeared in Dick's eyes.

"I'm just beginning to realise," he remarked, "what you meant when you said that my i.f. alignment may have brought on the howl because it could have made the i.f. response have a steeper skirt. I suppose that, if the skirt is steeper, the amplitude variation becomes bigger."

"Exactly," confirmed Smithy. "It would appear that the tuning capacitor in your particular receiver is fairly close to the acoustic howl condition, but that actual oscillation doesn't occur when the i.f. response curve has a nice symmetrical shape with fairly evenly sloping skirts, because the amplitude variation resulting from frequency variation is too small. (Fig. 5 (a)). I would guess that your first alignment caused the skirts to be much steeper than they should have been with, probably, one side steeper than the other. (Fig. 5 (b)). The steeper the slope the greater the i.f. amplitude variation resulting from frequency variation and, hence, the greater the overall gain in the oscillation feedback loop. The fact that the howl occurred only when you tuned to one side of the signal would also argue that the i.f. response was asymmetric, there being just sufficient change from frequency to amplitude variation on the steeper slope to allow the howl to appear."

"Why," asked Dick, "did the howl only occur on one station?"

"That," replied Smithy, "is just the luck of the draw, as there are a lot of fortuitous factors involved. In medium and long wave transistor

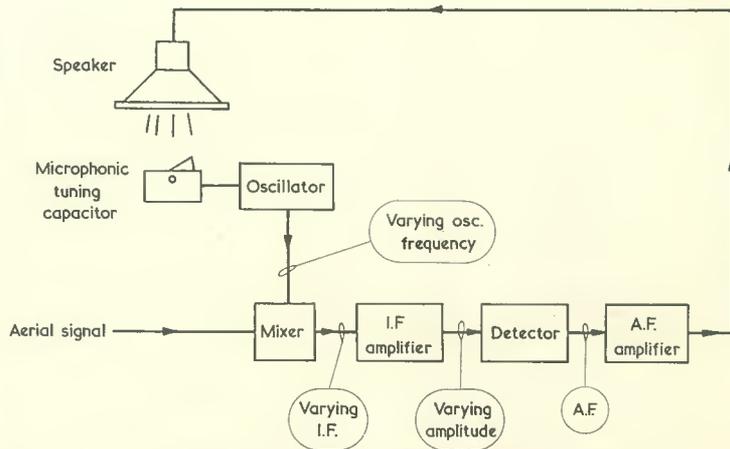


Fig. 4. When a microphonic oscillator tuning capacitor in an a.m. receiver causes the appearance of an acoustic howl, the feedback loop takes up the form shown here. The manner in which a varying i.f. is converted to a varying signal amplitude is illustrated in Fig. 5

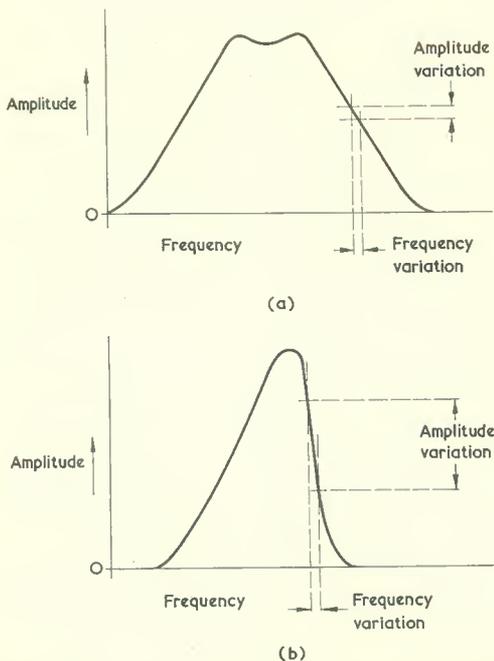


Fig. 5 (a). If the i.f. corresponding to the carrier of a received signal is applied to the skirt of an i.f. response and is then varied slightly, an amplitude variation results  
 (b). Due to Dick's careless alignment, the i.f. amplifier in his receiver was given an asymmetric response curve similar to that shown here. A frequency variation applied to the steep side of the response results in a much greater amplitude variation

sets acoustic howls usually turn up near the high frequency end of the medium wave band where the tuning capacitor vanes are slightly meshed, as occurred, in your case, on 247 metres. This will be the condition which corresponds to maximum oscillator frequency variation for a given level of mechanical vibration in the capacitor. In your set, the maximum oscillator frequency variation just happened to occur around 247 metres. You don't normally get acoustic howls on long waves because the lower oscillator frequency means that the frequency variation will also be lower."

#### Howl On Short Waves

Dick absorbed this information. "If that's the case," he remarked after a moment's thought, "the situation must become worse with sets which cover short waves."  
 "That's very true," agreed Smithy. "Because the oscillator frequency is higher again. In practice, though, acoustic howls don't seem to be too troublesome in the fairly small proportion of transistor radios made

in this country which cover short waves. This will be, of course, because the manufacturers have taken the appropriate precautions against it. In earlier years, by the way, acoustic howl on the short wave bands of three-band mains valve radios used to be a great problem both to manufacturers and to service engineers. This was due to the fact that these sets had output valves giving a good 3 or 4 watts and the oscillator tuning capacitor used to have the relatively high value of 500pF instead of the lower capacitance that appears in more modern tuned circuit designs. To prevent acoustic coupling from the speaker, the tuning capacitors in those older radios were frequently mounted on very soft rubber grommets, or on a sub-chassis which was similarly mounted on very soft grommets. You could bring on an acoustic howl with some of these sets by merely fitting a replacement dial cord too tightly! If the replacement cord pulled the tuning capacitor out of position and made it exert too much pressure on its rubber grommets, the

acoustic isolation provided by the latter would be reduced and the set would then start howling as you tuned in stations on the short wave band. Some of those old sets were real shockers in that respect. Alternatively, the howl could be caused by a microphonic oscillator section in the frequency-changer and all that was then required was the fitting of a new valve. Transistors don't go microphonic, which was why I asked you at the beginning whether your set was a transistor type. If it was, your acoustic howl would have almost certainly been due to tuning capacitor microphony, as that was about the only possible culprit left."

"Well, I'm darned," said Dick admiringly. "You really *did* use a crafty bit of reasoning there!"

"Oh, I'm like that," grinned Smithy. "Anyway, so far as medium and long wave transistor radios are concerned, the precautions against acoustic feedback to the variable capacitor don't have to be so stringent as for the short wave bands of those earlier valve radios. In some transistor sets the tuning capacitor is mounted on small rubber grommets, whilst in others it's just bolted straight down. Incidentally, if you ever get another set with the same sort of acoustic howl, you want to check that the i.f. alignment is as the manufacturer intended and that the effect of any resilient mounting provided for the tuning capacitor hasn't been upset in any way. If the worst comes to the worst and both these points prove to be satisfactory, then you just have to fit a new tuning capacitor. Cheerio!"

#### F.M. Receivers

With which unexpected parting shot, Smithy turned abruptly and made his way back to his own bench.

"Hey, hang on a minute!" called out Dick. "What about f.m. radios? Won't acoustic howl be more liable to occur in these than in a.m. receivers? The oscillator frequency in f.m. sets is higher than on short waves and the frequency variation caused by a vibrating tuning capacitor will be detected directly by the discriminator."

"Good point," commended Smithy, who was now back at his own bench. "But don't forget that the frequency variation will have to be pretty wide to give an appreciable audio frequency after the discriminator. The range of the discriminator in an f.m. sound radio is plus or minus 75 kc/s, whereas quite efficient frequency discrimination via the skirts of a 470 kc/s i.f. amplifier can take place over plus or minus 1 kc/s only. Again, a variable capacitor

which has to tune the oscillator frequencies for Band II requires only a few vanes and these can be quite widely spaced. Such a capacitor will give less microphony than one of about the same dimensions with a greater number of vanes that are more closely spaced. With f.m. sets the possibility of acoustic feedback is *there*, but the risk of its occurring is not so great as might at first sight appear. A simple resilient mounting for the tuning capacitor using rubber or p.v.c. grommets is normally all that is necessary to

avoid it. Toodle-pip!"

After this final farewell, Smithy turned his back very firmly on his protesting assistant and proceeded to devote his full attention to the receiver he had been investigating before Dick's acoustic howl had made itself evident.

In point of fact, that howl from Dick's bench had raised in Smithy's mind many nostalgic memories of his earlier struggles to clear acoustic feedback on the short wave bands of those old valve radios he had referred to. So vivid were his recollections,

indeed, that his fingers had been itching to get to grips once more with one of the oldest of his electronic adversaries, and he had secretly been highly relieved when Dick called for his assistance.

Perhaps it was for the better, then, that the Serviceman was not capable of reading the thoughts which were passing through Dick's mind at that moment. As that percipient young man put it to himself: old Smithy always makes a fuss when you ask him for a bit of help, but he loves doing it nevertheless!



## EMI Colour TV

EMI announced in April of this year that they had passed the million pounds mark for colour television equipment orders. Since then they have received further substantial orders bringing the present total value to £2,000,000 in less than five months. These orders have been received mainly from Europe and the United Kingdom and customers include A.B.C. TV, Anglia TV, B.B.C. and Yorkshire TV.

EMI's colour experience over the last 20 years has been incorporated in a very comprehensive range of colour television equipment. Designed for both the American and European television standards, using solid-state techniques throughout, the range includes the colour camera channel, slide scanner, vision mixing and switching equipment, encoders, decoders, vertical aperture correctors, and other ancillary equipment.

The four lead-oxide vidicon colour camera Type 2001 has continued to impress customers particularly in respect of stability and ease of operation. The camera's remarkable stability, both electrical and mechanical, results from the use of a direct imaging optical system together with the "capstan" arrangement of pick-up tubes and the unique lens mounting. The camera takes a range of zoom lenses each of which can quickly and simply be replaced.


## New Sample Changer

A new automatic gamma sample changer has been developed by EMI Electronics specifically for use with a wide variety of different nucleonic counting systems. The user is thus able to adapt the unit to his particular application using existing ancillary equipment. The sample changer (Type ASC 1) accommodates up to 50 samples, has an integral solid state programme unit and employs a highly stable, low noise EMI photomultiplier.

The unique design of the heavily shielded crystal/photomultiplier assembly ensures high efficiency independent of sample volume and a low background level, unaffected by local highly active sources.

### CARTOON

H  
U  
C  
K  
L  
E

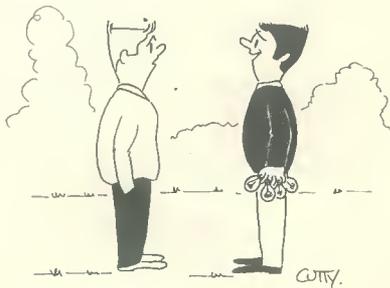

"I'm gonna plant these old light bulbs and grow some electric currants"

# Stabilised Variable Mains Supply Unit

by F. Neville Hart

A simple low-cost unit offering output voltages from 0 to 17 at currents up to 500mA.

NOW THAT IT IS POSSIBLE TO OBTAIN OR BUILD really high quality transistor amplifiers, many giving outputs of well over 5 watts, it is essential to provide a fully stabilised power supply offering anything from 9 to 17 volts or so.

In the case of amplifiers with push-pull output stages, a voltmeter will show considerable supply voltage variations, even across a battery, on loud passages, and to a musical ear distortion is quite obvious in such instances.

The writer uses the unit described in this article to supply a 5 watt amplifier and radio at a voltage of 12 to 15. Only on a particularly high input does the voltmeter needle budge, and then only for a quarter of a volt or so. It is also useful to be able to vary the output voltage so that small radios, etc., can be supplied. The present unit provides a variable output from 0 to 17 volts.

## Power Unit Circuit

In the circuit, shown in Fig. 1, it will be seen that the ACY18 controls the voltage by regulating the current to the base of the large OC35. The base current required by the ACY18 is only of low value, and the potentiometer does not have to handle a heavy current. It can, in consequence, be an ordinary carbon type. It was found in practice that the value chosen for this component, 20kΩ, gave good calibration spacing for a dial mounted behind its control knob.

The two zener diodes can be type OAZ207, whereupon slightly greater than 18 volts (assuming diodes in the centre of tolerance) appears across them, this voltage then being applied to the track of the potentiometer. The zener diodes are clamped to a small aluminium heat sink measuring 1½ x 1½ in, plus a flange for mounting, which also enables them to be supported mechanically. The heat sink is not entirely necessary, but the writer considered it worthwhile as there appeared to be some warming up of the diodes with the prototype.

Other combinations of zener diodes, with a total zener voltage adding up to about 18, could also be used. If desired, the diodes could be chosen to offer a total zener voltage up to about 21 volts (corresponding to a maximum output voltage from the unit of approximately 20 volts) but regulation may be poorer at output voltages above about 17. With the original, it was found that capacitor C<sub>2</sub>, across the diodes, eliminated a ripple which was otherwise present on the output.

As will be seen from Fig. 2 (a), the OC35 is directly secured to a heat sink, this being made of aluminium sheet and measuring 2½ x 1½ in excluding the mounting flange. This sheet is at the full rectified negative potential, so care must be taken to see that it is well insulated from other components and wiring.

The function of resistor R<sub>3</sub> is to ensure that C<sub>3</sub> discharges rapidly when switching off without a load, this being a useful facility for some applications.

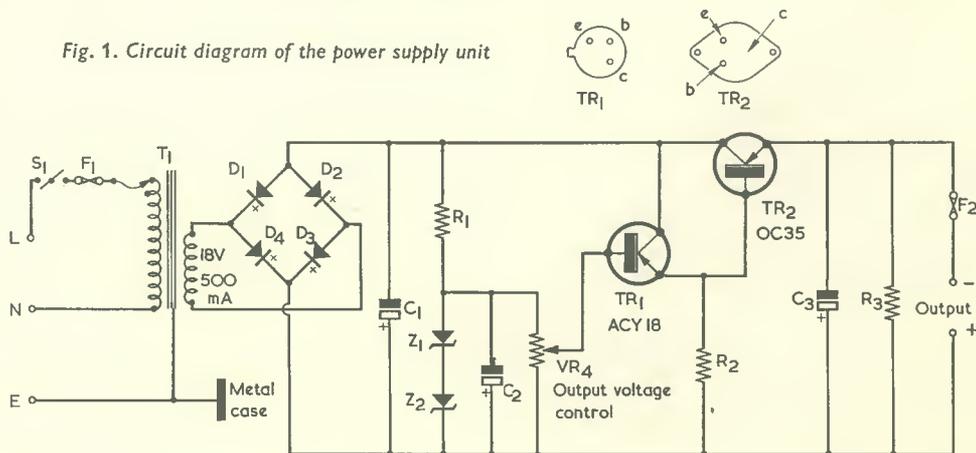


Fig. 1. Circuit diagram of the power supply unit

The power unit is built into an aluminium case to assist in the elimination of mains hum, a 2-way output lead passing out of this to the radio or amplifier being supplied. In any event, however, negligible hum is present, since large value smoothing capacitors are used.

### Fuses

Fuses are advisable. One-hole-fixing fuse holders are available, and both fuses should be rated at 1 amp.

With 3-way mains sockets the earth connection may be taken to the power supply case, as shown in the circuit diagram. If desired, the positive output of the power supply may be made common to the metal case.

For safety reasons, a piece of Paxolin is attached over the mains terminals of the transformer. In addition, the inside of the metal case is covered with Fablon as insulation against any accidental contact with a "live" wire or connection. It must be remembered that the inside of the case cannot be seen when the top half is fitted and all precautions *must* be taken to ensure that there is no risk of any

## COMPONENTS

### Resistors

(All fixed resistors 10%)

- R<sub>1</sub> 1k $\Omega$   $\frac{1}{2}$  watt
- R<sub>2</sub> 1k $\Omega$  1 watt
- R<sub>3</sub> 2k $\Omega$   $\frac{1}{2}$  watt
- VR<sub>4</sub> 20k $\Omega$  variable, linear

### Capacitors

- C<sub>1,2,3</sub> 500 $\mu$ F electrolytic, 30V wkg.

### Transformer

- T<sub>1</sub> Mains transformer, secondary 18V 500mA, type PS245 (Henry's Radio Ltd.)

### Semiconductors

- TR<sub>1</sub> ACY18
- TR<sub>2</sub> OC35
- D<sub>1,2,3,4</sub> Germanium rectifier type GJ3M (Henry's Radio Ltd.)
- Z<sub>1,2</sub> Zener diode type OAZ207 (see text)

### Fuses


- F<sub>1,2</sub> 1A fuse, with fuse holder

### Switch


- S<sub>1</sub> on-off toggle
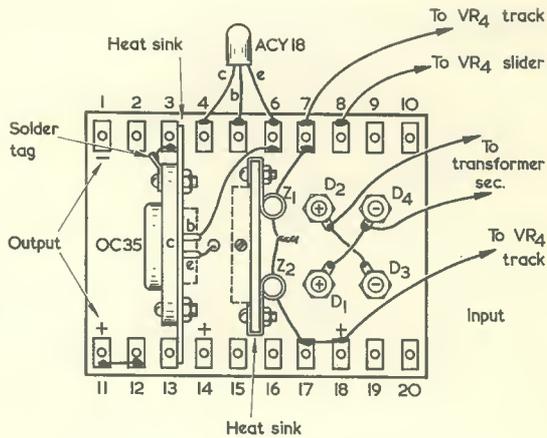
### Miscellaneous

- Heat sink clips
- Pointer knob
- Tagboard
- Aluminium sheet, spacing washers, grommets, etc.



(a)

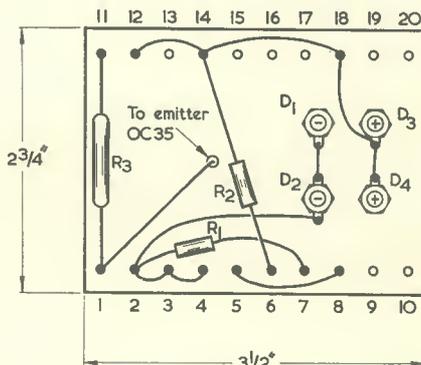

(b)

Fig. 2 (a). The upper side of the tagboard  
(b). The wiring on the underside of the tagboard

connection touching the internal surface of the case. Do *not* rely on the Fablon for this, as it is merely intended as an additional safeguard.

The potentiometer can be calibrated with a good voltmeter and the reading will be little affected by variations of the current taken. For evenly spaced readings around the dial, the potentiometer must have a linear track.

The usual care in soldering the leads of the transistors should be observed and this point also applies to the zener diodes and the germanium rectifiers, as the transference of excess heat to any of these would affect performance.

The metal case is made of two pieces of aluminium bent to fit into one another, one piece forming the ends and bottom, and the other the sides and top. They should be held together with self-tapping screws. See Fig. 3.

The transformer is secured to the bottom half direct, but the main part of the unit is built on to a Paxolin double tagboard obtainable generally and cut to approximately 3 $\frac{1}{2}$  x 2 $\frac{3}{4}$ in, with 10 tags on each side. The wiring layout before the capacitors

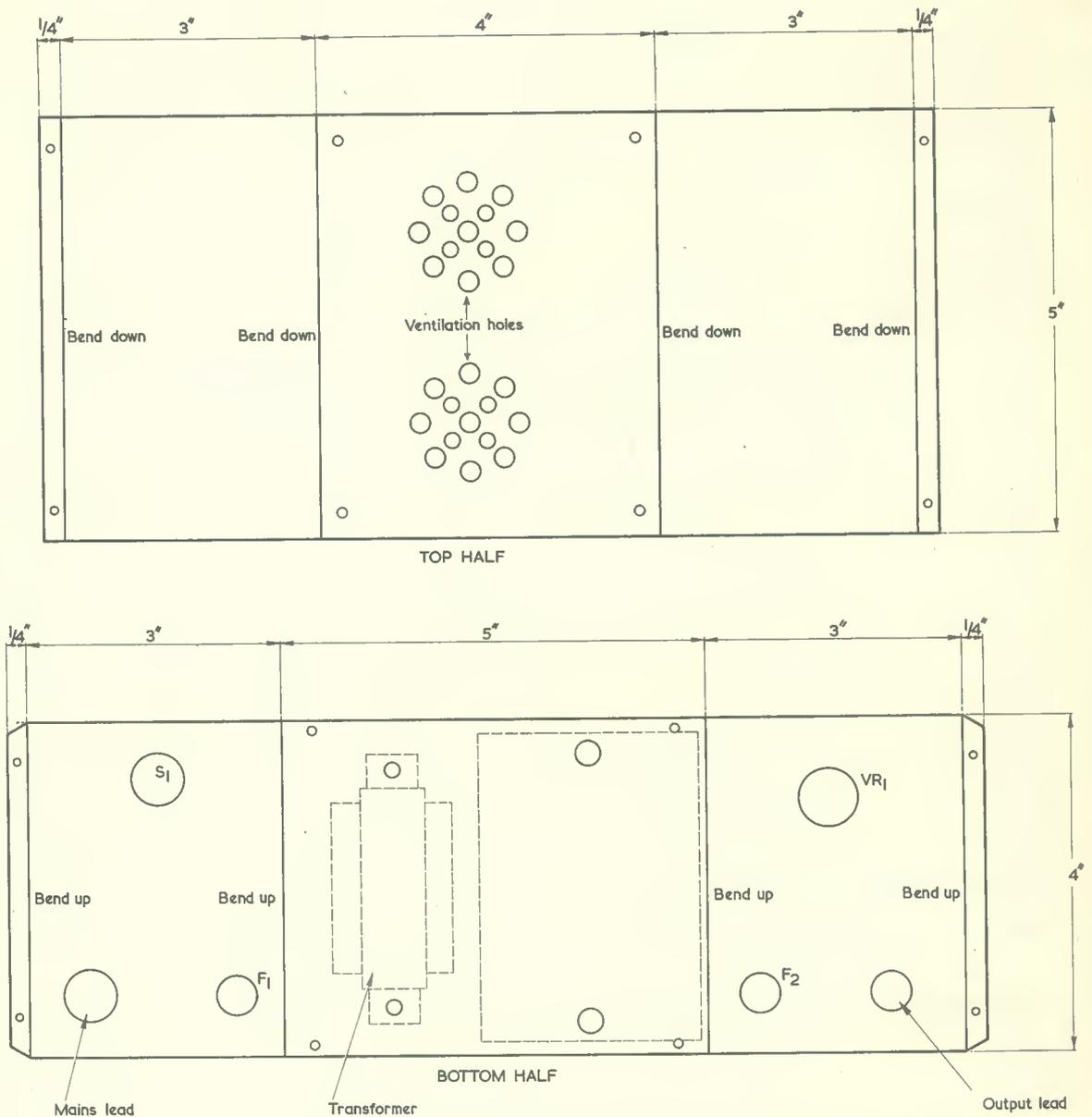


Fig. 3. Details of the two halves of the metal case before bending. The material is aluminium sheet

are fitted is shown in Figs. 2 (a) and (b). After the wiring steps shown are completed the capacitors are added in the following manner, carefully observing polarity. C<sub>1</sub> between tag 18 (positive) and tag 4; C<sub>2</sub> between tag 17 (positive) and tag 7; C<sub>3</sub> between tag 12 (positive) and tag 1. Fit sleeving over all wires where any risk of short-circuit exists. When soldered up, the tagboard is secured to the bottom half of the metal case by means of long screws with spacing washers.

The rectifiers are mounted on to the Paxolin of the tagboard at suitably drilled holes. Connections are made by way of solder tags, as this type does not have wire ends, only fixing nuts. The larger end of each rectifier is positive (+) and the transparent end is negative (-).

The power unit should not, of course, be used at a higher voltage for any radio or amplifier than that specified by their manufacturers. \*

# Radio Topics

## By Recorder

ONE OF THE MAIN DIFFICULTIES with building small computers for industrial, educational and experimental applications is the large number of connections which have to be made. For instance even the humble bistable which is needed to divide by 2 has some 14 two-terminal components (resistors, capacitors and diodes) and 2 transistors, whereupon the total number of connections it needs is of the order of 20. Thus, to set up a counter capable of dividing only by 8, you have to sit down and make no less than 60 connections. The problem involved is not so much the cost of components required for the computer—it is the amount of time which has to be spent in wiring it up.

### Logic Modules

A neat answer to this problem is provided by West Hyde Developments Ltd., who manufacture a wide range of plug-in logic modules under the name "Pidam", each module consisting of a complete logic element capable of performing a basic function in logic circuitry. The modules may be plugged into B9A valveholders, and are designed so that the wiring between valveholders is kept to a minimum. In consequence, the Pidam system considerably eases the problems of initial design and assembly of small computers because it reduces wiring time and offers the further advantages of versatility and flexibility.

The supply voltages required are +7.5, 0 and -7.5 and the modules are standardised so that pin 7 is always OV, pin 8 is always -7.5V and pin 9 is always +7.5V. A layout

intended for experimental work may, therefore, have pins 7, 8 and 9 of the B9A valveholders permanently wired up to the supply source. If relay operation is required, a -24V supply is also needed. Suitable power packs capable of offering the required voltages can be obtained from West Hyde Developments, as may other ancillary equipment including reed switch relays, an electromagnetic counter and an oscilloscope. Apart from their use for experimental and educational purposes, Pidam modules can, of course, appear in finalised equipment intended for industrial control functions.

There are 16 logic modules in the Pidam range, these including AND and OR gates, a linear amplifier, a Schmitt trigger, a bistable and a shift register. The accompanying photograph illustrates the Pidam bistable with its cover removed. As may be seen, standard components are used inside the module.

An illustrated booklet describing the Pidam system and its applications has now been published. Readers of *The Radio Constructor* may obtain copies free of charge by writing to West Hyde Developments Ltd., 30 High Street, Northwood, Middx. I should add that many of the Pidam assemblies may be obtained in kit form, as is made clear in the booklet.

### Printed Circuit Hotel

One of our contributors, Mr. C. P. Finn (his last article, "S.W.G. Measurement", appeared in the December 1966 issue), reports an unconventional use for printed circuit boards at Atherstone, Warwick-

## Your Local Supplier

LONDON

Established 1910

### H. L. SMITH & CO. LTD.

Comprehensive stocks of components  
by all leading makers.

287-9 EDGWARE ROAD  
LONDON W.2

Tel: 01-723 5891

### TELERADIO ELECTRONICS

For Radio Control Devices, Miniature  
components, Special Transistors,  
Circuits and data on boat and  
aircraft control.

QUOTATIONS GLADLY FOR PARTS USED IN  
MAGAZINE ARTICLES

(S.A.E. Enquiries REF. D/P)

325/7 FORE STREET,  
EDMONTON (3719)  
LONDON, N.9.

### WHY BI-PAK? FOR SEMICONDUCTORS

- ★ Fastest by return mail service
- ★ Lowest possible prices
- ★ Largest range available
- ★ Satisfaction guaranteed
- ★ For further proof see page 193

BI-PAK SEMICONDUCTORS  
8 Radnor House,  
93/97 Regent St., London W.1

### G. W. SMITH & Co (Radio) Ltd.

3-34 LISLE STREET,  
LONDON, W.C.1.  
Tel. GERrard 8204/9155  
Open 6 days a week

#### CATALOGUE

Over 150 pages of electronic  
components, test, communi-  
cation and Hi Fi Equipment.  
Fully illustrated. 5/- p & p 1/-

## Your Local Supplier

LONDON

### ELECTRONICS GALORE!

in the NEW  
**dca CATALOGUE**

Send 1/6 now for your copy  
to: DEPT. R/C

**dca ELECTRONICS  
LIMITED**

28 UXBRIDGE ROAD,  
EALING, W.5

### THE MODERN BOOK CO.

Largest selection of English and  
American radio and technical books  
in the country.

19-21 PRAED STREET,  
LONDON, W.2

Tel: PADdington 4185/2926

ESSEX

### ELECTRONIC COMPONENTS

Valves, transistors, capacitors,  
transformers, amplifiers,  
tuners, etc., etc.

765 HIGH ROAD,  
SEVEN KINGS  
(opp. Seven Kings Hotel)  
ILFORD, ESSEX

Telephone: GOOdmayes 1826

### MARKET CENTRE For Semiconductors

Prompt, efficient mail order service  
for Mullard, Newmarket, Texas,  
Sinclair, S.T.C., Fairchild Semi-  
conductors. We also offer a com-  
prehensive selection of miniature  
components for transistor circuitry.  
Catalogue 1s.

**L.S.T COMPONENTS**  
23 New Rd., Brentwood, Essex

shire. In the White Hart Hotel at Atherstone printed circuit boards measuring 6 x 4in are screwed to some of the doors to act as rather intriguing finger-plates. These were originally intended for industrial use, possibly computing, since they have tab areas on the edge for plug-in connections. Other points of interest are that they are "imperforate" (that is, the holes have not been pierced for the components) and they have never seen solder in their lives. As a result, the copper parts have acquired quite a lustre from the polishing action of many fingers, although they are not deliberately polished.

Mr. R. Packer, the present landlord of the White Hart Hotel, says the printed circuit boards were there when he took over, and has no idea of their past history or who made them.

A well-designed printed circuit board immediately after etching is, of course, quite a decorative thing, and is certainly attractive enough in appearance to be used as an unconventional finger-plate on a door. Some of the bright plastic housings used for present-day capacitors and other components are similarly pleasant to look at. Perhaps we are approaching the time when our wives, instead of fussing because electronic bits and pieces find their way into the house, will actually start raiding our spares boxes for components with which to embellish the place!

#### A Theremin For Christmas

It won't be long before the party season commences and the more electronically minded amongst us are called upon to produce gadgets for the amusement of guests.

One of the simplest gadgets to make for a party is based on the principle of the theremin, and can be easily knocked up by the more experienced short-wave enthusiast. For those who haven't heard of it before, I should mention that the theremin is a pre-war electronic musical instrument which is still mentioned in the radio press every now and again. Basically, it consists of two r.f. oscillators beating with each other, the resultant a.f. note being fed to an amplifier and loudspeaker. A vertical metal rod several feet long is connected to the hot end of the tuned circuit in one oscillator, with the consequence that the resonant frequency of that tuned circuit varies as the theremin player's hand approaches the rod.

If the oscillators are set up so that a zero beat note is given when the player's hand is well away from the

rod, a continually rising note is given as the player's hand comes closer to it. Quite interesting and amusing effects can be obtained with practice. It is desirable to give some tremolo to the tone by waggling the hand or fingers, as otherwise the sine wave beat note tends to become monotonous. It is, of course, the body capacitance of the theremin player which causes the change in oscillator frequency, and it is necessary to ensure that the earthy end of the tuned circuit coupled to the rod is connected to a reasonably good earth.

The party variation on the theremin consists of replacing the metal rod with a piece of thin wire some four or five feet long fixed to one side of a doorway. The hot end of the tuned circuit of an r.f. oscillator is coupled to this, and the oscillator output is fed to any short-wave receiver fitted with a b.f.o. and capable of feeding a speaker at good volume. Best results will normally be given at a frequency in the order of 5 to 10 Mc/s. The oscillator and receiver are set up to zero beat before the party starts, and guests are invited to try and pass through the doorway without causing the "radar sentry" (or whatever fanciful name you care to give the gadget) to sound a warning. Non-technical people find it quite fascinating to observe that a siren-like tone which gradually increases in pitch is heard as they approach the door, and to find that the "sentry" cannot be "beaten" however carefully they try to sidle through.

The oscillator coupled to the pick-up wire at the door may be mounted unobtrusively on the skirting board near the bottom of the wire, and it could employ a single transistor and its own small battery. It should have a pre-set variable capacitor across the tuned coil to which the pick-up wire connects, the capacitor being adjusted to a value which gives the pick-up wire just sufficient sensitivity. As can be readily imagined, the pick-up wire will have greater sensitivity as the value of the pre-set capacitor decreases, since it will then be capable of altering a greater proportion of the total tuning capacitance. The short-wave receiver is tuned to whatever oscillator frequency is given at the desired frequency. Sufficient sensitivity is given when the beat note approaches the upper audible limit in frequency when someone is very close to the wire.

#### Car Radio Supply

To finish this month, I pass on



A Pidam bistable module, manufactured by West Hyde Developments, Ltd.  
This may be plugged into a B9A valveholder

an idea to those readers who employ 9-volt transistor portables in their cars from time to time, and who feel that it might be economical to run these from the 12-volt battery fitted in the car. I haven't tried this idea myself, and I merely put it forward as a suggestion. It should be quite easy to put into operation provided that care is taken to prevent short-circuits between the car body and any metalwork of the radio which is at the potential of the radio chassis. Similarly, care must be taken to ensure that there is no risk of damage due to short-circuits between the car body and any aerial system external to the radio cabinet. The idea should only be tried out by those who fully understand the principles involved.

Now that high-wattage zener diodes are readily available it becomes a simple matter to obtain a well regulated 9-volt supply from a 12-volt car battery. To take very extreme figures, the car battery voltage may vary between 11 and 15 volts. If a car battery exhibiting such voltages is connected to a 9-volt zener diode by way of a 20Ω resistor the following figures apply.

At 11 volts battery potential, 2 volts are dropped in the 20Ω resistor, resulting in a current of 100mA in this resistor and, with no load across the zener diode, in the diode as well. The resistor dissipates 0.2 watt and the diode 0.9 watt.

At 15 volts battery potential, 6 volts are dropped in the 20Ω resistor, with a consequent current

of 300mA in the resistor and, assuming no load, in the zener diode. Resistor dissipation is 1.8 watt and zener diode dissipation is 2.7 watt.

I see that the ZS9.1 zener diode listed in the Henry's Radio catalogue is rated at 9.1 volts  $\pm 5\%$  and 7 watts, so this would be eminently satisfactory for the zener diode. And the 20Ω resistor could be any 3 watt or 4 watt component.

By using the zener diode and resistor in series, a well regulated 9.1 volts becomes available across the zener diode and, provided that the short-circuit risks I mentioned just now are carefully avoided, should offer adequate current availability for a normal 9-volt transistor portable. In cars with a positive earth, the zener diode should be at the positive end of the series combination. With a negative earth, the zener diode should be at the negative end.

The zener diode and resistor offer a very simple 9-volt supply but they do not provide any noise suppression. It should be found that the large-value electrolytic capacitor fitted across the supply lines in a conventional transistor portable should filter out any noise that is present. And, of course, the radio *must* be connected with correct polarity across the zener diode or, apart from any other damage that might occur, that large-value electrolytic will cease to take any further interest in life!



## Your Local Supplier

HAMPSHIRE

### BOURNEMOUTH

LARGEST HI-FI AND  
RADIO COMPONENT  
STORE IN THE SOUTH

FORRESTERS NATIONAL  
RADIO SUPPLIES LTD.  
70-72 Holdenhurst Road  
Bournemouth  
Telephone 25232

LANCASHIRE

### NEW CROSS RADIO

Electronic components and  
Equipment,  
Transistor Panels,  
all at competitive prices

6 Oldam Road, Newcross  
Manchester 4  
Telephone CEN 1541

SURREY



SMITHS PRECISION  
6 MINUTE DELAY  
ACTION SWITCH

Clockwork actuated

10/6 EACH

Post 2/6  
(3 or more post free)

Separate switching up to 6 mins. Each action for loading up to 15 amps. 250 volts. For photographic timer, sequence switching operations, etc., etc. Brand new units at a fraction of their value. Connection sheet supplied.

Radio Component Specialists  
337, WHITEHORSE ROAD,  
WEST CROYDON, SURREY  
Phone 01-684-1665 FULL LIST 1/-

SUSSEX

### E. JEFFERIES

For your new television set,  
tape recorder, transistor radio,  
and hi-fi equipment.

PHILIPS, ULTRA, INVICTA, DANSETTE,  
MASTERADIO, PERDIO, MARCONI,  
PHILCO, FIDELITY.

6A Albert Parade,  
Victoria Drive,  
EASTBOURNE SUSSEX

# Value in the Shops 80'9

THE RADIO CONSTRUCTOR  
SPECIAL PRIVILEGE PRICE OF

THE *NEW*  
TOLTEC  
HAIR DRYER



### SPECIFICATION

Moulded in beautiful symmetrical pastel blue impact resisting thermoplastic casing.  
Quiet in operation.  
Hot or cold air.  
No radio or T.V. Interference—meets British standard specification.

Fitted with safety cut-out.  
12 months & money refund guarantee. 230-250 volts A.C. only.  
**Value 80'9 in the shops**

Send the coupon below with the sum of only 57'— (this includes 4/6d to cover postage, packing and insurance, unless you are collecting personally).

Please send me one Toltec Hair Dryer at the special privilege price as advertised in *The Radio Constructor*.

I enclose cheque/postal order value .....

Name.....

Address.....

(Block Capitals please)

To: Toltec Electronic & Trading Co. Ltd.  
Hatton House, Hurst Green, Etchingam, Sussex

## AMATRONIX LTD. (DEPT. RC 11)

396 SELSDON ROAD, CROYDON, SURREY, CR2 0DE

We sell the latest transistors at the lowest prices. All goods are new, first grade and guaranteed to makers' specification. Quantity prices for 5 or more of one type. List 3d. with data and useful circuits: free with all orders.

### ★ 2N2926 SPECIAL OFFER

ALL beta groups (55-110, 90-180, 150-300, 235-470) 3/- (5+, 2/6)  
Any 5, one group or mixed, 12/6.

### 9V BATTERY ELIMINATOR KIT 17/6

Submin. mains trans, 0-230-250V, 9-0-9V 80mA, submin bridge rectifier, min. 1000uF, 16V electrolytic, with circuits and hints on constructing a 9V eliminator which will fit into the space of a PP6, etc., battery.

### SIMPLE TRF PACKAGE 11/-

Matched set of 4 silicon transistors plus circuit and notes on a sensitive MW or LW T.R.F. for 3V operation. Very economical in components.

### MICRO-POWER AMPLIFIER KIT 15/-

All components for the 1.5V amplifier described in the September "RC", plus notes on construction and circuit of a radio "front end".

### MINIATURE AMPLIFIER KIT 13/-

Three transistors and all passive components for a miniature transformerless single-ended push-pull class B amplifier. Operation from 3V to 12V. Maximum power 600mW at 12V. Data for various loads included. State voltage when ordering.

SEE OUR PREVIOUS ADVERTISEMENTS FOR OTHER BARGAINS.  
Mail order only. Cash with order. U.K. post free on orders over 10/- (otherwise add 6d.) Discounts: 10% over £5, 15% over £10. Special quotations for large quantities.

# NEW BOOKS

### SEPTEMBER

BASIC ELECTRICITY and an Introduction to Electronics .....	30/-
ELECTRONIC GADGETS FOR YOUR CAR .....	22/-
T.V. SERVICING MADE EASY .....	24/-
ELECTRONICS IN OCEANOGRAPHY .....	35/-
101 MORE WAYS TO USE YOUR SCOPE IN TV SECOND EDITION .....	24/-

### OCTOBER

COLOUR T.V. TRAINING MANUAL .....	40/-
SYNCHROS AND SERVOS .....	35/-
101 WAYS TO USE YOUR SQUARE WAVE AND PULSE GENERATOR .....	22/-
PROJECT IN BASIC MAGNETISM .....	25/-
SLIDE RULE IN ELECTRONICS .....	30/-
TROUBLESHOOTING AUDIO EQUIPMENT .....	25/-
COMPUTER DICTIONARY AND HANDBOOK .....	90/-

### NOVEMBER

AUDIO AMPLIFIER DESIGN .....	25/-
TRANSISTOR SUBSTITUTION HANDBOOK (7th EDITION).....	15/-
PRACTICAL HAM RADIO PROJECTS .....	20/-
ROCKET AND SPACE SCIENCE SERIES— VOLUME 2 PROPELLANTS .....	30/-
UNDERSTANDING UHF EQUIPMENT .....	25/-

Please send for a complete catalogue of over 100 titles dealing with Electronics and allied subjects.

## W. FOULSHAM & CO. LTD.

YEovil ROAD SLOUGH BUCKS ENGLAND

# FREE TO AMBITIOUS ENGINEERS

—THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 132-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronic Courses, administered by our Specialist Electronics Training Division—explains the benefits of our Appointments Dept. and shows you how to qualify for five years promotion in one year.

## SATISFACTION OR REFUND OF FEE

Whatever your age or experience you cannot afford to miss reading this famous book. If you are earning less than £30 a week send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

### WHICH IS YOUR PET SUBJECT

RADIO  
TELEVISION  
ELECTRONICS  
ELECTRICAL  
MECHANICAL  
CIVIL  
PRODUCTION  
AUTOMOBILE  
AERONAUTICAL  
PLASTICS  
BUILDING  
DRAUGHTMANSHIP  
B.SC.  
CITY & GUILDS  
GENERAL CERTIFICATE  
OF EDUCATION  
ETC., ETC.

### PRACTICAL EQUIPMENT

Basic Practice and Theoretical Courses for beginners in Radio T.V. Electronics Etc. A.M.I.E.R.E. City & Guilds  
Radio Amateur's Exam. R.T.E.B. Certificate. P.M.G. Certificate. Practical Radio, Radio & Television Servicing  
Practical Electronics  
Electronics  
Engineering  
Automation

### INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T.

NOW offers you a real laboratory training at home with practical equipment.

Ask for details.



### POST COUPON NOW!

■ Please send me your FREE 132-page "ENGINEERING OPPORTUNITIES"  
■ (Write if you prefer not to cut page)

■ NAME .....

■ ADDRESS .....

■ .....

■ .....

■ SUBJECT OR EXAM THAT INTERESTS ME .....

409B

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

(Dept. 409B), Aldermaston Court, Aldermaston, Berkshire

THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD

## YOUR SOURCE

FOR RELIABLE COMPONENTS & RAPID MAIL SERVICE

2N3819 FET	15/-
BC107/8	5/-
2N2646 UJT	12/-
TD716 Tunnel diode incl. data sheet	12/-
OC71 equiv.	9/6
ORP12	9/6

"X" Line MODULES	
Ready built solid state circuits	
X-161 2 Watt Amplifier	35/-
X-191 Guitar Amplifier	35/-
X-141 Record Player Amp.	35/-
X-151 Intercom.	35/-
X-481 Audio Booster	30/-
X-461 Siren	35/-
X-471 Burglar Alarm	35/-
X-661 Metronome	30/-
X-761 Morse Oscillator	20/-
X-671 Lamp Flasher	32/6
X-691 Lamp Flasher (Double)	30/-
X-261 Mic. FM Transmitter	35/-
X-271 Telephone Transmitter	35/-
X-241 R/Player Transmitter	35/-
X-291 Guitar Transmitter	35/-
X-371 Wireless Sentry	35/-

AC126	6/-	OA200	4/-	OC140	9/6
AC128	4/-	OA202	4/-	OC170	4/-
AC176	6/-	OC20	22/6*	OC171	6/-
ADT140	12/6*	OC22	13/-	OC200	6/-*
AF114	4/9*	OC23	25/-*	OC202	13/-*
AF115	4/9*	OC25	9/6*	OC203	8/6*
AF116	4/9*	OC26	12/-*	OC204	11/-*
AF117	4/9*	OC28	15/-*	OC205	10/6*
AF118	9/-	OC29	15/-*	OC71	19/6
AF139	12/-	OC35	12/-	ORP12	9/6
ACY17	5/-*	OC36	14/-*	2G381	5/-
ACY20	3/6*	OC41	3/6	2N385A	15/-
ADY21	4/-*	OC42	4/-	2N696	7/-*
ADY49	10/-*	OC44	3/-	2N706	4/-
BAY31	4/-*	OC45	3/-	2N1302	5/-
BAY38	6/-*	OC71	3/6	2N1303	5/-
BC108	5/-	OC72	4/6	2N1304	6/-
BC107	5/-	OC73	3/3	2N1305	6/-
BC109	6/-	OC75	5/-*	2N1306	8/-
BCY40	16/-	OC76	4/-	2N1307	8/-
BCY31	13/6*	OC81	3/-	2N2147	17/-
BCZ11	10/-	OC81D	3/-	2N2160	14/9
BFY50	6/-*	OC81Z	9/-	2N2926	3/9
BFY51	6/-*	OC82	4/6	R53	23/-
BFY52	6/-*	OC82D	4/6	ST140	3/-*
BSY95A	4/9*	OC83	4/-	ST141	5/-*
BY100	5/-	OC84	6/-	V405A	13/-
OA5	2/6*	OC139	12/-	XA102	3/-*
OA10	2/6*	Items starred-* are price reductions			
OA70	1/6	Mullard output set 2 x OC81 + OC81D	7/-		
OA79	1/6	Mullard RF set 2 x OX45 + OC44	8/6		
OA81	1/6				
OA85	2/-*				
OA90	3/-				
OA91	1/6				

SUPER SAVE PACKS	
1 Pair 2N1304/5 NPN/PNP	10/-
3 BC109 High gain NPN	15/-
3 2N2926 Planar any gain	10/-
4 BC113 Fairchild planar	10/-
10 D1476 (OC71 equiv) New	10/-
20 Mixed New transistors Germanium & Silicon Marked	20/-
20 Mixed New Diodes Germanium & Silicon Marked	15/-
16 Red & White spot New (8 red—8 white RF)	10/-
4 OC16 equiv. (V30/30P)	10/-
2 OC19 Mullard New	10/-
2 25722 Texas 100W Silicon	15/-
4 BY100 Brimar 800piv 750mA	13/6
4 OA210 Mullard 400piv 550mA	12/-
12 OA200 equivalent (1S130)	6/-
12 OA202 equivalent (1S132)	9/-
4 SL103K 100piv 10A Stud Rects	15/-
4 SL103E 100piv 2A Stud Rects	10/-
2 SCR's one at 400v 3Amp one at 50v 1Amp (Seconds for turn-on time OK 50c/s)	10/-
2 12volt 1Watt Zeners IN202	10/-
36 Square inches Verboard .15"	10/-
2 120volt 1.5Amp Avalanche Rect 5Amp surge by S.T.C.	12/-
150 Assorted ceramic capacitors mainly colour coded exceptional value—guaranteed satisfaction	10/-

ALL PACKS ARE POST FREE!!!

These modules are not moulded in plastic and can be opened for servicing etc. S.A.E. for details.

#### NOTICE

We do not offer for sale semi-conductors of the "Re-marked" type. (for example our listing of Mullard transistors all bear the Mullard brand name) Furthermore all goods offered are subject to our normal money-back guarantee.

TRADE SUPPLIED—EXPORT ENQUIRIES WELCOME P. & P. PLEASE ADD 9d.

QUOTATIONS BY RETURN FOR QUANTITY 24 hour Postal Service


TELEPHONE 7904

L.S.T. COMPONENTS 23 New Rd. Brentwood. Essex.

PRINTED CIRCUIT BOARDS with two OC 35's on heat sinks and 6 other transistors plus diodes etc., per board.....	18/6
Minimum of six M.A.T. Transistors on Printed Panel with Zeners, silicon diodes etc. ....	14/-
Airsaced Transistor Tuning Condensers 365 pF .....	4/6
100 + 100 pF with SM drive .....	5/-
208 + 176 pF with SM drive .....	7/6
Loudspeakers 2" 80 ohm 2½" 35 ohm .....	5/6
Driver Transformer for above Loudspeakers .....	2/9
Toggle Switches single pole .....	2/-
D.P.D.T. ....	2/6
1 mA 2" square Moving Coil Meters .....	17/6
Stud Mounting Rectifiers 200 P.I.V. 2 Amps .....	2/-
200 P.I.V. 6 Amps .....	2/6
Wire-ended plastic encapsulated 400 P.I.V. 500 mA .....	1/-
800 P.I.V. 500 mA .....	2/6
Power Transistor Holders .....	1/-
Electrolytic Condensers 1µF 12 v.w., 2µF 12 v.w., 8µF 30 v.w., 50µF 12 v.w., 100µF 12 v.w., all 1/- each 9/- dozen	
Silicon General Purpose NPN Transistors (300 Mc/s) .....	2/6
F.E.T. MPF105 .....	8/6
AD161/162 matched pairs .....	12/6
AFZ12 .....	4/6
2N502 .....	8/6
BCY34 .....	4/-
2N706 .....	3/6
BCY38 .....	4/-
2N706A .....	4/6
BC150 .....	5/6
2N708 .....	5/6
BCZ11 .....	7/6
2N1305 .....	3/-
BFY50 .....	4/6
2N2926 .....	3/6
BFY51 .....	4/6
2N3663 .....	8/6
BFY52 .....	4/6
BFY53 .....	4/6
Single M.A.T. Transistor on P.C. Board plus other components per panel .....	2/6

**J. Birkett, 25 The Strait, Lincoln**  
TELEPHONE: 20767

### BE TRANSISTOR-WISE!

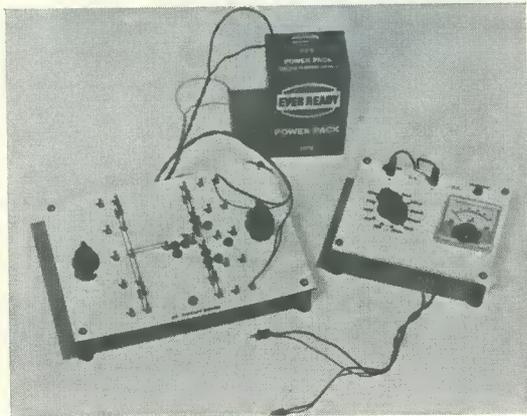

Our course of 21 practical lessons on diodes and transistors imparts perfect understanding! No theory! Easy-to-follow instructions! Common emitter, common base, emitter follower operations; current, voltage and power amplifications; switching transistors; temperature effects; leakage currents, etc., etc. Germanium and silicon pnp and npn transistors.

**TRANSISTOR COURSE TCI** £7.10.0  
Complete course, but less  
9 volt battery . . . .

**METER KIT:** 50µA—50mA. 50mV—50V. 20,000 o.p.v. 69/6  
Also **BASIC TRANSISTOR CIRCUITS KIT** 85/-

Write for **FREE DETAILS** to:

**Electronic Experiments**  
Brinklow, RUGBY.

### RADIO CONTROL FOR MODELS



# RADIO CONTROL FOR MODELS

SHIPS, BOATS and AIRCRAFT  
By **F. C. JUDD**

With sections on servo-mechanisms by  
**RAYMOND F. STOCK**

*More than 200 illustrations—circuits, working diagrams, photographs & tables. Each page is packed with information.*

## 192 Pages

# 15s.

Postage 9d.

This book is basically an amalgamation of "Radio Control for Model Ships, Boats and Aircraft" and "Radio Control Mechanisms". Additional material has been added on Multi-Channel Operation; Transistorised Radio Control Receivers—Simple and Three-Channel; A Compact Efficiency Aerial; Deac Battery Information; Licence Conditions, etc.

To Data Publication Ltd., 57 Maida Vale, London, W.9

Please supply.....copy(ies) of your publication "RADIO CONTROL FOR MODELS" DATA BOOK No. 16.

I enclose cheque/crossed postal order for.....

NAME.....

ADDRESS.....

BLOCK LETTERS PLEASE

## SMALL ADVERTISEMENTS

Rate: 9d. per word. Minimum charge 12/-.  
Box No. 2/- extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box numbers should be addressed to: Box No.—, *The Radio Constructor*, 57 Maida Vale, London, W.9.)

**SERVICE SHEETS, 1925-1967.** From 1s. Catalogue 6,000 models, 2s. 6d. S.A.E. enquiries.—Hamilton Radio, 54 London Road, Bexhill, Sussex.

**100 PAGE ILLUSTRATED CATALOGUE NO. 17** of Government and manufacturers' electronic and mechanical surplus, also a complete new section of the latest semi-conductors and miniature components, includes a credit voucher for 2s. 6d. Send for your copy now. Price 3s. post free. Arthur Sallis (Radio Control) Ltd., 93 North Road, Brighton, Sussex.

**FOR SALE.** Oscilloscopes—Galvanometers—Evershed & Vignolles Meggers—Relays—Uniselector Switches—Solenoids. Also other items and components. Free list. Stamp please.—R. & E. Mart, Box 9 G.P.O., Tunbridge Wells, Kent.

**TORIOD COILS** for sale. Suitable RTTY, etc. Mostly 88mH but some values above and below. S.A.E. for details. 7s. 6d. each. Box No. F289.

**RESISTORS.**  $\frac{1}{2}$  watt carbon film 5%. All preferred values in stock from 10 ohms to 10 megohms. 2d. each. Send s.a.e. for free sample. **CAPACITORS:** Mullard miniature metallised polyester PC mounting all 250V d.c. working. 0.01mF, 0.022mF, 0.047mF, 0.1mF, 0.22mF, all at 6d. each. Hunts tubular 0.1mF, 200V working at 3d. each. Send 6d. stamp for extensive list of low priced Electronic Components, Instruments and Equipment. Please include 1/- postage and packing on all orders under £1.—Dept. R.C.3, BRENSAL ELECTRONICS LIMITED, CHARLES STREET, BRISTOL 1.

**5 TON FACTORY CLEARANCE.** Radio, TV, elec. components in 15s. and 27s. 6d. mixed parcels. Post free. Example: resistors, condensers, pots., speakers, coax, coils, fibre washers, valves, over a dozen different types, tuning knobs, grommets, sleeving, IFS, Paxalin, wire, rectifiers. Lots of other items. Pot luck. Postal orders to: P. L. Newton, 10 Cecil Road, Muswell Hill, London N.10.

**BRIGHTEN UP YOUR ADVERTISING!** Break the ice with a cartoon, "tailor made" for your product. Reasonable charges. Box No. F294.

**BOOKS FOR SALE.** *Hi-Fi Projects for the Hobbyist*, Fieldman, 10s. *Electronic Valves in A.F. Amplifiers*, Rodenhuis, 3s. 6d. *Tubes for Computers*, Philips, 5s. 6d. *Industrial Rectifying Tubes*, Philips, 5s. 6d. *U.H.F. Tubes for Communication and Measuring Equipment* 5s. 6d. *Instructions to Radio Constructors*, Warring, 7s. 6d. All post free. Box No. F297.

**WIRELESS-MICROPHONE TRANSMITTERS.** From 25s. each. Send s.a.e. for details. Also 1 x 1 x 1in transmitters (including built-in microphone) available in kit form or ready made.—Mr. Bobker, 64 Choir Street, Salford 7, Lancs.

continued on page 254

## BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcot Road, Chalk Farm,  
LONDON, N.W.1.

47 Norfolk Road,  
LITTLEHAMPTON, Sussex  
Littlehampton 2043

Please forward all mail orders to Littlehampton


5Z4	7/6	EBF89	5/9	EY86	5/9	PY800	6/-	AF114	4/-	GET897	4/6
6AT6	3/9	EC92	6/6	EY88	7/6	PY801	6/-	AF115	3/-	GET898	4/6
6AU6	5/6	ECC81	3/6	EZ40	6/-	U25	12/6	AF116	3/-	OA81	1/9
6BV6	7/-	ECC82	4/6	EZ41	6/6	U26	11/-	AF117	3/4	OA95	1/9
6L6	7/6	ECC83	4/6	EZ80	3/9	U191	12/-	AF118	3/-	OA182	2/-
6LD20	6/6	ECC84	5/6	EZ81	4/3	U301	12/6	AF119	3/-	OA200	3/-
6V6G	3/6	ECC85	5/-	KT66	16/6	UACB80	5/3	AF125	3/6	OC19	25/-
6J30L2	12/6	ECC88	7/-	PC86	8/6	UAF42	7/9	AF127	3/6	OC22	5/-
12AT6	4/6	ECC189	9/-	PC88	8/6	UBC41	6/6	AF180	9/6	OC23	7/-
12AU6	4/9	ECF80	7/-	PC95	6/9	UBC81	6/6	AFZ12	5/-	OC25	5/-
19AQ5	5/-	ECF82	6/9	PC97	5/9	UBF80	5/6	BA115	2/8	OC26	5/9
20D1	13/-	ECF86	8/6	PC900	8/6	UBF89	5/9	BA129	2/6	OC28	5/-
20P4	17/6	ECH42	8/9	PCC84	5/6	UC92	5/6	BA130	2/-	OC30	7/-
30C15	12/-	ECH81	5/-	PCC85	6/9	UCB84	8/-	BCY10	5/-	OC35	10/-
30C17	13/-	ECH83	7/-	PCC88	10/6	UCB85	6/6	BCY12	5/-	OC36	7/6
30C18	9/6	ECH84	6/6	PCC89	9/9	UCF80	8/3	BCY33	5/-	OC38	11/6
30F5	11/6	ECL80	6/-	PCC189	8/3	UCH21	9/-	BCY34	4/-	OC44	2/-
30FL1	15/-	ECL82	6/3	PCF80	6/3	UCH42	8/6	BCY38	5/-	OC45	1/9
30FL12	15/-	ECL83	9/-	PCF82	6/-	UCH81	6/-	BCY39	5/-	OC46	3/6
30FL14	12/6	ECL86	7/9	PCF84	8/-	UCL82	7/-	BFY50	5/0	OC70	2/3
30L15	14/-	EF41	9/-	PCF86	8/-	UCL83	8/9	BFY51	4/6	OC71	2/-
30L17	13/-	EF80	4/6	PCF801	8/6	UF41	7/9	BFY52	5/-	OC72	2/-
30P4	11/6	EF85	4/6	PCF802	9/6	UF42	4/9	BF163	4/-	OC75	2/-
30P4MR	13/-	EF86	6/3	PCL82	6/3	UF80	6/9	BY100	3/6	OC76	3/-
30P12	11/-	EF89	4/9	PCL83	8/6	UF85	7/3	BY234	4/-	OC77	3/4
30P19	11/-	EF183	6/3	PCL84	7/-	UF86	9/-	BY238	4/-	OC78	3/-
30PL1	15/-	EF184	5/9	PCL85	8/3	UF89	5/6	BY212	5/-	OC78D	3/-
30PL13	15/-	EH90	7/6	PCL86	8/-	UL41	8/9	BY213	5/-	OC81	2/-
30PL14	15/-	EL33	12/-	PFL200	13/6	UL84	5/6	GET103	4/-	OC81D	2/-
30PL15	15/-	EL41	8/-	PL36	9/-	UM80	6/6	GET113	4/-	OC82	2/3
DM70	6/-	EL42	7/6	PL81	6/9	UY41	5/9	GET116	7/6	OC83	2/-
DY87	5/9	EL84	4/6	PL82	5/9	UY85	4/9	GET118	4/6	OC84	3/6
E88CC	12/-	EL95	5/-	PL83	6/-	2N404	6/6	GET119	4/6	OC123	4/6
EABC80	5/9	ELL80	13/-	PL84	6/3	AC107	3/6	GET573	8/6	OC169	3/9
EAF42	7/6	EM80	5/9	PL500	13/6	AC126	2/-	GET597	8/6	OC170	6/6
EB91	2/3	EM81	6/9	PY33	10/6	AC127	2/-	GET873	4/-	OC171	3/4
EBC41	7/3	EM84	6/-	PY81	5/-	AC128	2/-	GET887	4/6	OC172	4/-
EBC81	6/3	EM85	11/-	PY82	5/-	AC156	4/-	GET889	4/6	OC200	6/6
EBF80	5/9	EM87	6/6	PY83	5/6	AD140	8/-	GET890	4/6	OC202	5/6
EBF83	7/-	EY51	5/6	PY88	7/3	AD149	8/-	GET896	4/6	OC203	5/6

Terms of business: Cash with order only. No C.O.D. Post/Packing 6d. per item. Orders over £5 post free. All orders despatched same day as received. Complete catalogue including transistor section and components with terms of business 6d. Any parcel insured against damage in transit for 6d. extra. We are open for personal shoppers 9 a.m.-5 p.m. Saturdays 9 a.m.-1 p.m.
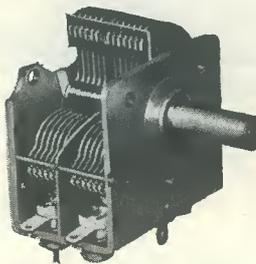
# JACKSON

the big name in **PRECISION** components

Precision built radio components are an important contribution to the radio and communications industry. Be sure of the best and buy Jackson Precision Built Components.



"00" Twin Condenser  
12/6 each

Designed for use in miniature transistor receivers. The front (aerial) section is 208pF to provide coverage for medium waves, and the rear section is 176pF, which may be padded to match the oscillator—very robust yet lightweight. Front area  $1\frac{3}{8}$ in. x  $1\frac{1}{8}$ in. x 1in. deep.

*It's reliable if it's made by JACKSON!*

**JACKSON BROS. (LONDON) LTD.**

(DEPT. R.C.), KINGSWAY-WADDON, CROYDON, CR9 4 DG  
Phone: Croydon 2754-5 (01-688). Grams: Walfilco, Croydon

# NEW STYLE SELF-BINDER for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check-device is fitted to each.



PRICE **15/-** Post Free  
PLAIN BACKED 14/6 Post Free

Available only from:—

**Data Publications Ltd.**  
**57 Maida Vale London W9**

## SMALL ADVERTISEMENTS

*continued from page 253*

**BARGAIN PARCELS!** 120 (minimum) radio parts, etc., mostly new, 12s. 6d. a parcel. G. Hart, Lings Lane, Chelmondiston, Ipswich, Suffolk.

**TECHNICAL DRAWINGS, Artwork, etc.** Electronic and Radio Circuits a speciality. Moderate charges.—B. P. Meaney, 43 Forest Road, Worthing, Sussex.

**LIMITED QUANTITY PCF80, PCC84, EF80, EBF80, ECL80; 6V6, 6Q7, 6K7.** All 5s. Tested. C.W.O. Webberley, 19 Baring Road, New Barnet, Herts.

**"MEDIUM WAVE NEWS"** Monthly during DX season—Details from: K. Brownleff, 7, The Avenue, Clifton, York.

**CHATTERBOX RECORDING CLUB.** Free membership, news tapes, badges, stickers, news sheets, etc. 368 Rush Green Road, Romford, Essex.

**INNOVATION IN DX CLUBS ANNOUNCED!** Formed in October, 1965, the Radio New York Worldwide Listeners Club now has 3,600 members in 86 countries! A unique club offering shortwave listeners monthly magazines containing listening tips and technical features, numbered wallet-sized membership cards and gold 8½in. by 11in. membership certificates. Multi-lingual report forms available for cost of postage. "We must be doing something right!" Find out . . . join now! Send 7s. 2d. (crossed domestic money order) for one year's membership to:—The Radio New York Worldwide Listeners Club, 485 Madison Avenue, New York 10022, U.S.A.

**FOR SALE.** Complete 2 metre station. Rx is that described in the March 1966 issue of *The Radio Constructor*. Companion Tx, QVO 4/7 p.a.; pp 6BQ5's modulator; with power supply and aerial changeover relay all on one chassis. Complete with xtal mic. and speaker. £20. G2UK, "East Keal," Romany Road, Oulton Broad, Lowestoft, Suffolk.

**19 SET FOR SALE.** New condition, with a metered mains power unit, £12.—Rolls, 23 Brandreth Avenue, Dunstable, Beds.

**PRINTED CIRCUIT BOARDS MADE AND DRILLED** Send full scale drawing and 5d. per square inch. Prompt service. Minimum charge 3s. S.A.E. enquiries. R. D. Crabtree, 213 Hyde Park Road, Leeds 6, Yorks.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free Services to members including Q.S.L. Bureau. Amateur and Broadcast Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine, etc., 35s. per annum.—Secretary, ISWL, 60 White Street, Derby.

**WANTED.** Ships Chronometer and Sextant; pay cash, or preferably exchange radio gear. Box No. F310.

**ARE YOU A MOTORING ENTHUSIAST?** The Seven Fifty Motor Club caters for all types of motor sport—racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancer's End," St. Winifred's Road, Biggin Hill, Kent.

*continued on page 255*

## SMALL ADVERTISEMENTS

continued from page 254

**FOR SALE.** 8-day clock by Waltham Watch Co.  $3\frac{1}{4}$ " diam. panel mounting, with second hand and date dial, £5. Deck watch by Jolay,  $2\frac{1}{2}$ " diam., rotatable navigational ring graduated to  $360^\circ$  in fitted wooden case. £10, p.p. paid.—Box No. F311.

**MARCONI No. 9 RECEIVER.** Complete with crystal calibrator, meter. 1.8 – 5.00 Mc/s Perfect. £5. Suitable power pack £3. Also CR100 receiver, requires attention, £3.10.0d. Collection advised or carriage extra.—Phone 01-440-3569 after 6 p.m.

**MICROPHONES.** Crystal, stick, with anodised keyhole stand, outside customers' limits but guaranteed working order, from known manufacturer, 10s. 6d. each, p. & p. paid.—Box No. F313.

**METAL LOCATOR.** As per January 1967 *Wireless World* design. Lightweight, professionally constructed. 70s., postage 5s. Details:—Box No. F314.

**RECITALS OF RECORDED MUSIC.** The second Saturday evening of each winter month. Next recital: 11th November, 1967, 8 p.m. Woodford Green United Free Church, Woodford Green, Essex. Bus routes 20, 20A, 38A and 179—alight at "The Castle" stop. Works by Bach, Handel and Dvorak.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service campaign planning, design and artwork, printing and stationery. Please ask for price list.—The Holborn Direct Mail Company, 2 Mount Pleasant, London, W.C.1. Telephone: TERminus 0588.

**BOOKS FOR SALE:** "Alfred Nobel" E. Bergengren, £1. "Black Sailed Traders" R. Clark, 7s. 6d. "Radioisotope Laboratory Techniques" R. A. Faires, 10s. "Optical Microscope Technique" D. Birchon, 10s. "Atomic Medicine" Behrens, £1. "Medical Radiation Biology" Ellinger, 30s. "Effects of Atomic Weapons" U.S.A. Atomic Energy Commission, £1. "Physics in Medical Radiology" Russ, Clark & Pelc, 7s. 6d. "Disease & its Conquest" Hollis 7s. 6d. "Earth's Envelope" T. Lobsack, 15s. "The Atomic Submarine" C. Blair, 7s. 6d. "Astronautics in the Sixties" K. W. Gatland, 30s. "Space Research and Exploration" D. R. Bates, £1. "Once Round the Sun" Story of the I.G.Y., Fraser, 10s. "Earth Satellite" P. Moore, 7s. 6d. "Frontier to Space" E. Burgess, 5s.—Box No. F316

**THE WORLD'S SMALLEST BUG** (Wireless microphone). Rifle bullet size. £7.10.0. Post free. Shirt button size microphone 12/6.—Box No. F317.

**ESSEX GARDENERS.** Buy your bedding and rock plants, shrubs, etc., also cacti, from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only, Monday to Saturday.

**PROPERTIES** for sale and to let in London and suburbs. Apply to Maggs & Stephens, Estate Agents, 229 Maida Vale, London, W.9. MAIda Vale 8123.


**QUALIFY** as a technician, to service COMPUTERS, COLOUR TELEVISION, AUTOMATIC CONTROL SYSTEMS. Day or evening courses, includes extensive practical work, using modern equipment.

Also special course (2 days per week) enabling beginners to reach City and Guilds Intermediate level in six months. Full details from: Section 47/48, Southall College of Technology, Beaconsfield Road, SOUTHALL Middlesex.
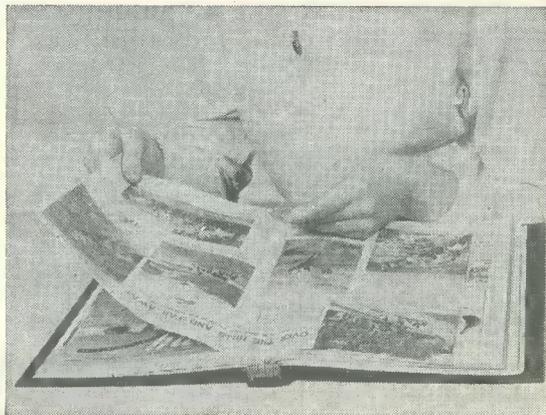
# PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines

(max. format  $7\frac{1}{2}$ "  $\times$   $9\frac{1}{2}$ " )



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Rich maroon finish. Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check-device is fitted to each.

PRICE **14'6** Post Free

Available only from:—

**Data Publications Ltd.**  
57 Maida Vale London W9

# CHASSIS and CASES by



**H. L. SMITH & CO. LTD.**  
287/9 Edgware Road  
London W2  
TEL: 01-723 5891

## BLANK CHASSIS—Same Day Service

Of over 20 different forms made up to YOUR SIZE.  
(Maximum length 35", depth 4".)

SEND FOR ILLUSTRATED LEAFLETS or order straight away, working out total area of material required (including waste) and referring to table below which is for four-sided chassis in 16 s.w.g. aluminium.

48 sq. in.	4/6	176 sq. in.	9/10	304 sq. in.	15/2
80 sq. in.	5/10	208 sq. in.	11/2	336 sq. in.	16/6
112 sq. in.	7/2	240 sq. in.	12/6	368 sq. in.	17/10
144 sq. in.	8/6	272 sq. in.	13/10	and pro rata	
P. & P. 3/-		P. & P. 3/6		P. & P. 4/6	

Discounts for quantities. More than 20 different sizes kept in stock for callers.


**FLANGES** (1" or 1 1/2"), 6d. per bend.  
**STRENGTHENED CORNERS**, 1/- each corner.  
**PANELS**

Any size up to 3ft at 6/- sq. ft. 16 s.w.g. (18 s.w.g. 5/3).  
Plus postage and packing

## CASES

### ALUMINIUM, SILVER HAMMERED FINISH

Type	Size	Price	Type	Size	Price
U	4 x 4 x 4"	10/-	W	15 x 9 x 8"	44/-
U	5 1/2 x 4 1/2 x 4 1/2"	15/6	Y	8 x 6 x 6"	26/6
U	8 x 6 x 6"	21/-	Y	12 x 7 x 7"	41/-
U	9 1/2 x 7 1/2 x 3 1/2"	22/-	Y	13 x 7 x 9"	46/-
U	15 x 9 x 9"	44/6	Y	15 x 9 x 7"	48/6
W	8 x 6 x 6"	21/-	Z	17 x 10 x 9"	66/-
W	12 x 7 x 7"	34/-	Z	19 x 10 x 8 1/2"	71/-

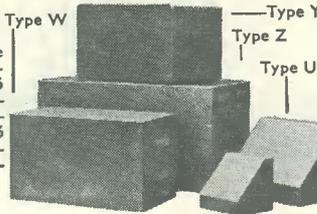

\* Height  
Type Z has removable back and front panels.  
Type Y all-screwed construction.

## HAMMERITE HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK, ETC.

**TRIAL TIN** (Covers 5 sq. ft.) only 3/9 + 9d post.

State colour: Blue, Silver, Black or Bronze (Air Drying) 2 1/2 oz. tins 3/9, 1/2 pint 8/-, 1 pint 16/- CARR. up to 5/-, 9d, up to 10/-, 1/9, over 10/-, 3/- VERY SPECIAL PRICES FOR LARGER SIZES.  
**AMAZING RESULTS, JUST TRY IT.**  
FIREPROOF THINNERS, PANEL TRANSFERS, TINTERS, ETC. LIST FREE.  
FINNIGAN SPECIALITY PAINTS (RC) Mickley Square, Stocksfield, Northumberland. Telephone: Stocksfield 2280



## WANTED

Contact springs as shown

BEST PRICES PAID

S.a.e. to "Lanco", 76 Sedgemore Road, Willenhall, Coventry, Warwickshire

## BULK COMPONENT BARGAINS

★ ASSORTED RESISTORS—Hi-Stab (5% 1/10 to 1/2 watt, worth £3) 300 off ..... 15/-

★ ASSORTED CAPACITORS—New Ceramic, Polyester, Electrolytic, Paper, 100 off ..... 10/6

(P. & P. 1s. 6d. per order, C.W.O.)

**Elmbridge Instruments Ltd.** Island Farm Avenue, West Molesey Surrey

## ARDEEN (RADIO)

EVERY TRANSISTOR WE SELL IS COMPREHENSIVELY GUARANTEED (12 MONTHS) TOP MANUFACTURER'S NEW, TESTED PRODUCTS ONLY:—  
2N2926, AC126, 128; OC44, 45, 71, 81, 81D 4/-  
OC170, 171, BC108, 109; AF126, 127, 2N706 4/6.  
BC107—(Replaces 50 other N.P.N.s—Details supplied)  
5/- each, 3 for 13/6. AD161, 162 12/- each.  
Bridge Rectifiers—30V 150mA 4/-; 300mA 5/-; 700mA 9/-

Return Post Service, Mail Order Only. Lists 6d.

280 CROXTED ROAD, LONDON SE.24.

## YUKAN SO PROFESSIONAL THE YUKAN SELF-SPRAY AEROSOL WAY —

Get these AIR DRYING GREY HAMMER or BLACK WRINKLE (CRACKLE) Finishes


Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/11 at our counter or 15/11, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 5/-) for 18/11, carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or P.O. for total amount to: YUKAN, Dept. RC/11, 307a Edgware Rd., London W.2

Closed December 1st to December 31st for Annual Holidays

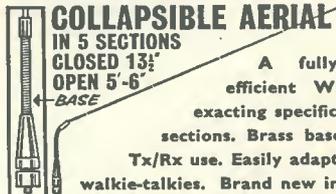Other Yukan Air Drying Aerosols include:  
Zinc Chromate Primer.  
Clear Lacquer.  
Anti-Tarnish Gold and Metallic Finishes.



## COLLAPSIBLE AERIAL IN 5 SECTIONS CLOSED 13 1/2" OPEN 5'-6"

A fully adjustable highly efficient Whip aerial made to exacting specifications. Copper plated sections. Brass base. An ideal aerial for Tx/Rx use. Easily adaptable for cars, scooters, walkie-talkies. Brand new in makers boxes. Only 17/6 each, p. & p. 2/6. Two aerials for 30/- post 2/6.

Available from **S. & R. SUPPLIES, Dept. RC1**  
24 Cawoods Yard, Mill St., Marsh Lane, LEEDS 9

# THE RADIO CONSTRUCTOR

## ANNUAL SUBSCRIPTIONS to this magazine may be obtained direct from the publishers ONLY 36/- per year, post free

Please send remittance with name and address and commencing issue required to:

**DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9**

Please mention **THE RADIO CONSTRUCTOR** when writing to advertisers

## THE RADIO CONSTRUCTOR

Price 2/6 each, postage 6d.

Annual Subscription 36/—, post free.

Bound Volumes Vol. 19 August 1965 to July 1966 32/6, postage 4/6.

Vol. 20 August 1966 to July 1967 32/6, postage 4/6.

Cordex Self-Binders With title "The Radio Constructor" on spine, 15/—, post free.  
With no title on spine 14/6, post free.

## DATA BOOK SERIES

**DB5 TV FAULT FINDING**

124 pages. Price 8/6, postage 8d.

**DB6 THE RADIO AMATEUR OPERATOR'S HANDBOOK**

64 pages. Price 5/—, postage 5d.

**DB14 SHORT WAVE RECEIVERS FOR THE BEGINNER**

72 pages. Price 6/—, postage 6d.

**DB15 TWENTY SUGGESTED CIRCUITS**

48 pages. Price 3/6, postage 5d.

**DB16 RADIO CONTROL FOR MODELS**

192 pages. Price 15/—, postage 9d.

**DB17 UNDERSTANDING TELEVISION**

512 pages. Price 37/6, postage 3/—

## PANEL-SIGNS TRANSFERS

Six sheets in each set

**Set 3: WORDING—White**

**Set 4: WORDING—Black**

**Set 5: DIALS—Control Panels have no background**

**Set 6: DIALS—Control Panels have a black background**

Price per set 4/6, postage 4d.

I enclose Postal Order/Cheque for.....in payment for.....

NAME .....

ADDRESS .....

*(Please use Block Capitals for both name and address)*

*Postal Orders should be crossed and made payable to Data Publications Ltd.*

*Overseas customers please pay by International Money Order*

*All publications are obtainable from your local bookseller*

**Data Publications Ltd., 57 Maida Vale, London W.9**



# NEW SOLID STATE HIGH FIDELITY EQUIPMENT

Power Amplifiers—Pre Amplifiers—Power Supplies

(British made)

WE PROUDLY PRESENT THIS NEW RANGE OF AUDIO EQUIPMENT

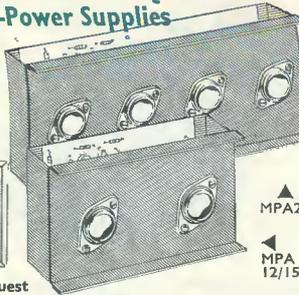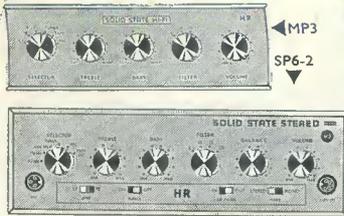developed from DINSDALE Mk. II—each unit or system will compare favourably with other professional equipment selling at much higher prices. Brief details are below



SYSTEM	COMPRISING	SYSTEM PRICE
★A	5 watt mono for 3/5 ohm speakers.	<b>£10.3.0</b>
★1	12 watt mono for 3 to 5 ohm speakers.	<b>£13.17.6</b>
★2	12 watt mono for 12 to 16 ohm speakers.	<b>£14.12.6</b>
★4	24 watt mono two channel for 12 to 16 ohm speakers.	<b>£20.15.0</b>
★8	20 watt mono/stereo for 12 to 16 ohm speakers.	<b>£24.0.0</b>
★9	24 watt mono/stereo for 3 to 5 ohm speakers.	<b>£26.15.0</b>
★14	40 watt mono/stereo for 7½ to 16 ohm speakers.	<b>£29.10.0</b>

Complete fully illustrated brochure free on request

**THE FINEST VALUE IN HIGH FIDELITY — CHOOSE A SYSTEM TO SUIT YOUR NEEDS AND SAVE POUNDS**

**SEND FOR FULL DETAILS ON ALL ADVERTISED PRODUCTS. FREE ON REQUEST**


### VHF FM TUNER



87/105 Mc/s Transistor Superhet. Gearing tuning. Terrific quality and sensitivity. For valve or transistor amplifiers. 4 x 3½ x 2½in. Complete with dial plate. 5 Mullard Transistors, Plus 4 Diodes. (Cabinet Assembly 20/- extra).

**TOTAL COST £6.19.6**  
TO BUILD P.P. 2/6

### FM STEREO DECODER

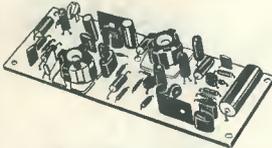

7 Mullard Transistors. Printed Circuit Design with Stereo Indicator. For use with any valve or transistor FM. Uses pot cores to Mullard design and ger. and silicon transistors. As used by B.B.C. and G.P.O.

**COMPLETE KIT PRICE £5.19.6**  
P.P. 2/-

### BUILD A QUALITY TAPE RECORDER



3-speed version using '363' decks  
★TWO-TRACK. Deck £10.10.0. Martin Amplifier. £14.19.6. Cabinet and speaker 7gns. Complete kits with FREE 7in. 1,200ft. tape, spare spool. Today's Value £45. **27 gns.** P.P. 15/-

★FOUR-TRACK. Deck £13.10.0. Martin Amplifier £15.19.6. Cabinet and speaker 7gns. Complete kits with FREE 7in. 1,200ft. tape, spare spool. Today's Value £50. **30 gns.** P.P. 15/-

### MW/LW QUALITY TRANSISTOR RADIO TUNER



Fully tunable superhet with excellent sensitivity and selectivity. Output up to ½ volt peak. Complete with front panel, etc. 9 volt operated. For use with any amplifier or tape recorder.

**TOTAL COST £3.19.6**  
TO BUILD P.P. 2/6



### REGENT-6 MW/LW POCKET RADIO TO BUILD

6-Transistor superhet. Gearing tuning. Push-pull speaker output. Moulded Cabinet 5 x 3 x 1½in. Phone socket.

**TOTAL COST £3.9.6**  
TO BUILD P.P. 2/-


Full tuning on both bands.
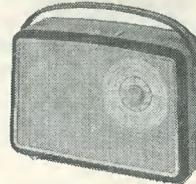
### TOURMASTER TRANSISTOR CAR RADIO British Made



7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wavechange. RF stage. Supplied built, boxed, ready to use with Speaker and Baffle. Car fixing kit and manufacturers' current guarantee. Special Bargain Offer. Positive earth.

**LIST PRICE 15 GNS.**  
Push-button version **£7.19.6** P.P. 4/6  
£11.19.6. P.P. 4/6




### 7-TRANSISTOR MW/LW SUPERHET NEW! PORTABLE

New printed circuit design with full power output. Fully tunable on both mw/lw bands. 7 Transistors plus diode, push-pull circuit. Fitted 5 inch speaker, large ferrite aerial and Mullard transistors. Easy to build with terrific results. All local, and continental stations.

**TOTAL COST £6.19.6** P.P. 4/-  
TO BUILD

### GLOBEMASTER

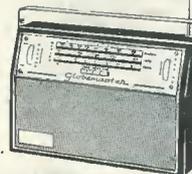

6-Mullard Transistors 7 x 4 speaker very sensitive excellent coverage Full 3-waveband tuning. Pushbutton wavechange. Superhet printed circuit. Black-chromed cabinet 11 x 7½ x 3½in. (SW 17-50 metres). Ear/Record sockets. 1 watt push-pull output.

**TOTAL COST £8.19.6** P.P. 4/-  
TO BUILD

### MAYFAIR PORTABLE

Designed by L. W. ROCHE



### Electronic Organ

Total Cost **99 GNS.**

- ★Build this superb Instrument STAGE BY STAGE in your own home.
- ★A truly portable instrument for all enthusiasts.
- ★Fully Transistorised POLYPHONIC British design.
- ★Call in for a DEMONSTRATION—full details on request.

### ORGAN COMPONENTS

We carry a comprehensive stock of organ components for TRANSISTOR and VALVE FREE PHASE designs: complete details, on request.

### CATALOGUE

The most COMPREHENSIVE — CONCISE — CLEAR — COMPONENTS CATALOGUE. Complete with 10/- worth discount vouchers FREE WITH EVERY COPY.

- ★20 pages of transistors and semi-conductor devices, valves and crystals.
- ★150 pages of components and equipment.
- ★50 pages of microphones, decks and Hi-Fi equipment.

**SEND TODAY 8/6 POST PAID**

### 1967 EDITION

225 pages, 6000 items  
1000 illustrations



# HENRY'S RADIO LTD

Telephone (01) 723-1008/9  
OPEN MON.—SAT. 9 a.m.—6 p.m. THURS. 9 a.m.—1 p.m.



303 EDGWARE ROAD LONDON W2

### Transistors & Semi-Conductor Devices

We have the LARGEST RANGE OVER 650 TYPES  
★COMPETITIVE PRICES ★FULLY GUARANTEED  
★1st GRADE STOCKS. SEND FOR FREE LIST No. 36  
Also 24-PAGE ILLUSTRATED BROCHURE LISTING 2000 DEVICES with data and circuits, including VALVES and QUARTZ CRYSTALS 1/- Post paid