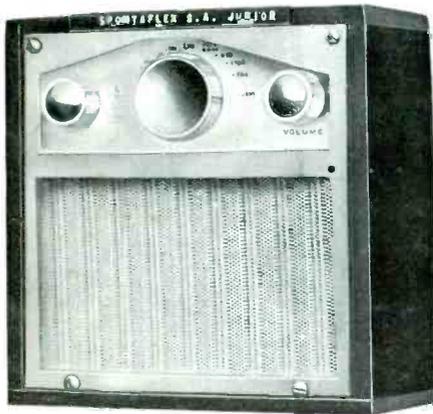


RADIO & ELECTRONICS CONSTRUCTOR

Vol. 26 No. 4

NOVEMBER 1972

20p



FEATURE 1

THE
'S·A·JUNIOR'
PORTABLE
RECEIVER



FEATURE 2

THE 'WYVERN'
160m
SOLIDSTATE
TRANSMITTER

**ALSO
FEATURED**

LOW VOLTAGE TIMER



Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or ¼ units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances. And remember - as you buy more possessions just add more Home Units at any time.

THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

COMPONENTS

HOBBYIST - AMATEUR - DOMESTIC SURPLUS -
INDUSTRIAL - BULK OFFERS

JUST A FEW OF OUR BARGAINS ARE LISTED BELOW - PAY US A VISIT
OR SEND STAMPED ADDRESSED ENVELOPE FOR A QUOTE ON YOUR REQUIREMENTS

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AF116	15p	BFY52	10p	in Heat Sink	15p
AC127	12p	ORP12	43p	T.O.3 Mica	
AC188	22p	2N3055	40p	washers	2p
AD149	30p	2N2401	15p	UNMARKED TESTED	
AD161	30p	Centercel Diodes	5p	BY127	8p
AD162	30p	6-110 volt, 0.6 amp.		BC179	10p
Matched pair	50p	encapsulated with built		2N2926	5p
BCY40	45p				

1/4 glass fuses— 250 m/a or 3 amp (box of 12)	6p
3" tape spools	4p
FX2236 Ferrox Cores	5p
PVC or metal clip on M.E.S. bulb holder	3p
All metal equipment Phono plug	2p
Bulgin, 5mm Jack plug and switched socket (pair)	20p
12 volt solenoid and plunger	25p
250 RPM 50 c/s locked frequency miniature mains motor	50p
200 OHM coil, 1 1/4" long, hollow centre	10p
Relay, P.O. 3000 type, 1,000 OHM coil, 4 pole c/o	60p
R.S. 12 way standard plug and shell	50p

SWITCHES

Pole	Way	Type	
4	2	Sub. Min. Slide	10p
6	4	} Wafer Rotary	12p each
1	11		
4	3		
3	7		
2	5		
1	3	+ off Sub. min. edge	10p
1	3	13 amp small rotary	12p
2	2	Locking with 2 to 3 keys	£1.50
2	1	2 Amp 250V A.C. rotary	20p

RESISTORS

1/8 - 1/4 watt	1p
1 watt	1 1/2p
Up to 10 watt wire	8p
15 watt wire wound	10p

SKELETON PRESETS

5K or 500K	3p
------------	----

SAFETY PINS

Standard size, 10 for 4p	
--------------------------	--

VALVES - NEW AND BOXED

DY86	44p	EM87	90p	PL84	46p
EB91	26p	EL84	36p	PY81	40p
ECC82	36p	EY86	46p	PY82	42p
ECC83	36p	EZ80	30p	PY88	52p
ECH81	44p	PCC84	50p	UABC80	58p
EABC80	46p	PCC89	62p	UCL82	50p
EBF89	44p	PCF80	38p	UL84	50p
ECL82	44p	PCF82	50p	UY85	42p
ECL86	56p	PCL82	38p	UM84	32p
EF80	36p	PCL84	50p	UCH81	44p
EF85	44p	PCL85	64p	6BA6	26p
EF86	44p	PCL86	56p		
EF91	52p	PL36	78p		
EF183	40p	PL81	72p		
EF184	44p	PL83	56p		

MANY OTHERS

DIE CAST ALLY BOX

4 5/8 x 3 5/8 x 2 5/8 with lid	50p
--------------------------------	-----

5K switched volume control	15p
5K Log Pot	10p
1meg Tandem Pot	15p

BSR TD2 TAPE TRANSPORTER

With record-playback-erase heads	£2.50
----------------------------------	-------

STEEL BOX WITH LID

10 x 5 1/2 x 3" grey hammer finish	£1
------------------------------------	----

RELAY

6 volt, 2 pole c/o heavy duty contacts	50p
--	-----

RESETTABLE COUNTER

English Numbering Machines LTD.
MODEL 4436-159-989

6-14 volt, 6 digit, illuminated, fully enclosed. £2.50

ELECTROLYTICS

Mullard C426, TCC, CRL, CCL, HUNTS, STC SUB MINIATURE, ETC.

MFD	Volt	MFD	Volt	
16	50	20	12	} 4p each
260	12	500	6	
50	50	100	25	} 2p each
100	18	100	6	
125	10	6	3	} 3p
8	50	8	6	
12	20	25	6.4	} 7p
10	20	250	18	
8.2	20	400	16	} 6p
50	25	400	40	
2.5	64	8	500	} 9p
25	25	100	200	

CONDENSERS

MFD	Volt	
0.005	500	} 2p each
0.001	1,250	
3.3PF	500	} 2p each
500 PF	500	
2,200PF	500	} 3p each
3,300PF	500	
0.1	350	} 5%
0.1	500	
0.25	150	} 350V
0.056		
0.061		} 4p each
0.066		
0.069		} 5p
0.075		
0.08		} 5p
0.1	1,500	
0.25	350	} 5p
0.5	350	
0.22	250	} 5p
0.25	500	

TUNING GANG

100PF, 50PF, 33PF
20p each

TRIMMERS

30 PF Beehive }
12PF P.T.F.E. } 10p each
2,500PF 750V }

WIREWOUND SLIDER

150 OHM, 250 OHM
5K 4p each

INDICATORS

12 volt red or mains neon amber, push fit round, chrome bezel
15p each

Rotor with neon indicator, as used in Seafarer, Pacific, Fairway depth finders
20p each

WIREWOUND POTS

250, 350 OHM, 1K, 4 watt, 10K, 20K, 50K, all at 10p each

RECORD PLAYER CARTRIDGE

ER.5XME Mono, with turn over stylii, single hole fixing 35p

GREEN INDICATOR

Takes M.E.S bulb 10p

CONNECTOR STRIP

Belling Lee L1469, 12 way polythene. 5p each

CAN CLIPS

1" or 1 3/8" or 3/4" 2p

T.O.5 HEATSINKS

Style 154 high conductivity 5p

PAXOLINE

2 3/4 x 4 3/4 x 1 1/8" or 3 x 2 1/2 x 1 1/8" 2p

4 3/8 x 1 1/2 x 1 1/8" 2 for 1p

220K 3 watt resistors 2p

VALVE RETAINER CLIP, adjustable 2p

OUTPUT TRANSFORMERS

Sub-miniature Transistor Type 20p

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE
LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11
Open 10 a.m. till 8 p.m. Monday to Saturday Phone 01-223 5016

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way*.

Learn basic Radio and Electronics at home – the fast, modern way. Give yourself essential technical 'know-how' – like reading circuits, assembling standard components, experimenting, building – quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors – even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN – but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build – and it's a good one – is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course – but it teaches the real thing. The easy to understand, practical projects – from a burglar-alarm to a sophisticated Radio set – help you master basic Radio and Electronics – even if you are a 'non-technical' type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of "NEW OPPORTUNITIES". This brand new booklet – just out – tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B9, ALDERMASTON COURT, READING RG7 4PF
Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

B9

NAME..... AGE.....
(BLOCK CAPITALS)

ADDRESS.....

.....

SUBJECT OF INTEREST.....

NOW AVAILABLE . . . LATEST BOUND VOLUME No. 25 of "The Radio Constructor" FOR YOUR LIBRARY



Comprising
768 pages
plus index

AUGUST 1971
to JULY 1972

PRICE £2.00 Postage 29p

BOUND VOLUME NO. 23
(August 1969 to July 1970)

BOUND VOLUME NO. 24
(August 1970 to July 1971)

Limited number of these volumes still available.

PRICES

Volume 23 £1.88 Postage 29p

Volume 24 £2.00 Postage 29p

We regret all earlier volumes are now completely sold out.

Available only from

DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC 107	20p AD 149	50p BC 143	30p BD 131	50p BF 179	30p C 444	35p 2G 301	2N 1613	20p 2N 2926(R)	10p 2N 3906	27p
AC 113	20p AD 161	33p BC 145	45p BD 132	60p BF 180	30p C 450	22p 2G 302	2N 1711	20p 2N 2926(B)	10p 2N 4058	12p
AC 115	23p AD 162	33p BC 147	10p BD 133	65p BF 181	30p MAT 100	19p 2G 303	2N 1889	32p 2N 3010	70p 2N 4059	10p
AC 117K	20p AD 161 and	30p BC 148	10p BD 135	40p BF 182	40p MAT 101	19p 2G 304	2N 1893	37p 2N 3053	17p 2N 4061	12p
AC 122	12p AD 162(MP)	55p BC 149	12p BD 136	40p BF 183	40p MAT 120	19p 2G 306	2N 2148	57p 2N 3055	50p 2N 4284	17p
AC 125	17p ADT 140	50p BC 150	18p BD 137	45p BF 184	25p MAT 121	20p 2G 308	2N 2160	60p 2N 3391	14p 2N 4285	17p
AC 126	17p AF 114	24p BC 151	20p BD 138	50p BF 185	30p MPF 102	42p 2G 309	2N 2192	35p 2N 3391A	14p 2N 4286	17p
AC 127	17p AF 115	24p BC 152	17p BD 139	55p BF 188	40p MPF 104	37p 2G 339	2N 2193	35p 2N 3392	14p 2N 4287	17p
AC 128	17p AF 116	24p BC 153	28p BD 140	60p BF 194	12p MPF 105	37p 2G 339A	2N 2194	35p 2N 3395	14p 2N 4288	17p
AC 132	14p AF 117	24p BC 154	30p BD 155	80p BF 195	12p OC 19	25p 2G 344	2N 2217	22p 2N 339A	14p 2N 4289	17p
AC 134	14p AF 118	25p BC 157	18p BD 125	60p BF 196	14p OC 20	43p 2G 345	2N 2218	20p 2N 3395	17p 2N 4290	17p
AC 137	14p AF 124	30p BC 158	12p BD 176	60p BF 197	14p OC 22	38p 2G 371	2N 2219	20p 2N 3402	21p 2N 4291	17p
AC 141	14p AF 125	25p BC 159	12p BD 177	65p BF 200	45p OC 23	42p 2G 371B	2N 2220	22p 2N 3403	21p 2N 4292	17p
AC 142	14p AF 126	28p BC 160	45p BD 178	75p BF 222	95p OC 24	56p 2G 373	2N 2221	20p 2N 3404	28p 2N 4293	17p
AC 142K	14p AF 127	28p BC 161	50p BD 179	70p BF 257	45p OC 25	38p 2G 374	2N 2222	20p 2N 3405	42p 2N 5172	12p
AC 151	15p AF 178	50p BC 168	12p BD 185	65p BF 259	85p OC 28	50p 2G 378	2N 2268	17p 2N 3414	15p 2N 5457	32p
AC 154	20p AF 179	50p BC 169	12p BD 186	65p BF 262	55p OC 29	50p 2G 381	2N 2369	14p 2N 3415	15p 2N 5458	32p
AC 155	20p AF 180	50p BC 170	12p BD 187	70p BF 263	55p OC 35	42p 2G 382	2N 2369A	14p 2N 3416	28p 2N 5459	40p
AC 156	20p AF 181	45p BC 171	14p BD 188	70p BF 270	35p OC 36	50p 2G 401	2N 2411	24p 2N 3417	28p 2N 5460	50p
AC 157	24p AF 186	45p BC 172	14p BD 190	75p BF 271	30p OC 41	20p 2G 414	2N 2412	24p 2N 3525	42p 2N 5461	42p
AC 165	20p AF 239	37p BC 173	14p BD 195	85p BF 273	35p OC 44	15p 2N 388	2N 2711	21p 2N 3702	10p 2N 5303	55p
AC 166	20p AL 102	65p BC 174	14p BD 196	90p BF 274	35p OC 45	12p 2N 388A	2N 2712	21p 2N 3703	10p 2N 5304	70p
AC 167	20p AL 103	25p BC 175	19p BD 197	90p BF 275	60p OC 70	10p 2N 404	2N 2713	21p 2N 3704	11p 2N 5305	84p
AC 168	24p ASY 26	25p BC 177	19p BD 198	90p BF 276	27p OC 71	10p 2N 404A	2N 2714	17p 2N 3705	10p 2N 5306	84p
AC 169	14p ASY 27	30p BC 178	19p BD 199	95p BF 277	22p OC 72	14p 2N 524	2N 2904A	21p 2N 3706	9p 2N 5307	84p
AC 176	20p ASY 28	25p BC 179	19p BD 200	95p BF 278	30p OC 74	42p 2N 527	2N 2905	21p 2N 3707	11p 2N 5321	56p
AC 177	24p ASY 29	25p BC 180	24p BD 205	80p BF 86	22p OC 75	15p 2N 598	42p 2N 2906	15p 2N 3709	9p 2N 5322A	52p
AC 178	28p ASY 50	25p BC 181	24p BD 206	80p BF 87	24p OC 76	15p 2N 599	42p 2N 2906A	18p 2N 3710	9p 2N 5323	46p
AC 179	28p ASY 51	25p BC 182	10p BD 207	95p BF 88	22p OC 77	25p 2N 696	15p 2N 2907	20p 2N 3711	9p 2N 5324	70p
AC 180	17p ASY 52	25p BC 182L	10p BD 208	95p BF 50	20p OC 81	15p 2N 697	13p 2N 2914	22p 2N 3818	28p 2N 5325	70p
AC 180K	20p ASY 54	25p BC 183	10p BDY 20	£1.00 BF 51	20p OC 82	15p 2N 698	13p 2N 2923	14p 2N 3820	50p 2N 5326	70p
AC 181	17p ASY 55	25p BC 184	12p BF 115	24p BF 52	20p OC 82D	15p 2N 699	24p 2N 2924	14p 2N 3821	35p 2N 5327	70p
AC 181K	20p ASY 56	25p BC 184L	12p BF 117	25p BF 53	17p OC 82D	15p 2N 706	8p 2N 2925	14p 2N 3822	28p 2N 5328	42p
AC 187	23p ASY 57	25p BC 186	28p BF 118	70p BPX 25	85p OC 83	20p 2N 706A	2N 2926(G)	12p 2N 3903	30p 40361	40p
AC 187K	20p ASY 58	25p BC 187	28p BF 119	70p BSX 19	15p OC 84	20p 2N 708	12p 2N 2926(H)	11p 2N 3904	30p 40362	40p
AC 188	22p ASZ 21	20p BC 188	11p BF 121	45p BSX 20	15p OC 139	20p 2N 711	30p 2N 2926(I)	10p 2N 3905	28p	
AC 188K	20p BC 107	9p BC 207	11p BF 122	50p BSX 25	15p OC 140	20p 2N 717	30p	28p		
ACY 17	25p BC 108	7p BC 208	11p BF 123	45p BSX 26	15p OC 169	25p 2N 718	24p			
ACY 18	20p BC 109	10p BC 209	12p BF 125	45p BSX 27	15p OC 170	25p 2N 718A	50p AA 119	8p BY 130	16p OA 47	7p
ACY 19	20p BC 113	10p BC 212L	11p BF 127	55p BSX 28	15p OC 171	25p 2N 726	28p AA 120	8p BY 133	21p OA 70	7p
ACY 20	20p BC 114	10p BC 213L	11p BF 152	45p BSX 29	15p OC 201	25p 2N 727	28p AA 129	8p BY 164	50p OA 79	7p
ACY 21	20p BC 115	15p BC 214L	14p BF 153	45p BSX 38	18p OC 202	28p 2N 743	20p AA 30	9p BYX 38 30	42p OA 81	7p
ACY 22	18p BC 116	15p BC 225	25p BF 154	70p BSX 39	18p OC 203	28p 2N 744	20p AAZ 13	10p BYZ 10	35p OA 85	9p
ACY 27	18p BC 117	15p BC 226	35p BF 155	48p BSX 40	28p OC 204	25p 2N 914	14p BA 100	10p BYZ 11	30p OA 90	6p
ACY 28	19p BC 118	10p BCY 30	24p BF 156	55p BSX 41	12p OC 205	25p 2N 918	30p BA 116	21p BYZ 12	30p OA 91	6p
ACY 29	35p BC 119	30p BCY 31	24p BF 157	55p BSX 95A	12p OC 209	35p 2N 929	21p BA 126	22p BYZ 13	25p OA 95	7p
ACY 30	28p BC 120	80p BCY 32	30p BF 158	40p Bu 105	£2.00 P 06A	40p 2N 930	21p BA 148	14p BYZ 16	40p OA 200	6p
ACY 31	28p BC 125	12p BCY 33	22p BF 159	40p C 110	30p P 06A	20p 2N 1131	20p BA 154	12p BYZ 17	35p OA 202	3p
ACY 34	21p BC 126	18p BCZ 11	25p BF 160	40p C 111E	35p ST 140	43p 2N 1132	22p BA 155	14p BYZ 18	35p SD 10	5p
ACY 35	21p BC 132	12p BCY 70	14p BF 162	40p C 400	30p OCP 71	43p 2N 1302	14p BA 156	13p BYZ 19	28p SD 19	5p
ACY 36	28p BC 134	18p BCY 71	18p BF 163	40p C 407	25p ORP 12	43p 2N 1303	14p BY 100	15p CG 62	IN 34	7p
ACY 40	17p BC 135	12p BCY 72	14p BF 164	40p C 424	20p ORP 60	40p 2N 1304	17p BY 101	12p CG (Eq) OA 91	5p IN 34A	7p
ACY 41	18p BC 136	15p BCZ 10	20p BF 165	22p C 425	50p ORP 61	40p 2N 1305	17p BY 105	17p CG 651 (Eq)	IN 914	6p
ACY 44	35p BC 137	15p BCZ 11	25p BF 173	22p C 426	35p ST 141	12p 2N 1306	21p BY 114	12p OA 70-0A79	6p IN 916	6p
AD 130	38p BC 139	40p BCZ 12	25p BF 174	35p C 428	20p ST 41	17p 2N 1307	21p BY 126	14p OA 5	35p IN 414B	6p
AD 140	48p BC 140	30p BD 121	60p BF 176	35p C 441	30p T15 43	30p 2N 1308	23p BY 127	15p OA 55L	21p OS 1021	10p
AD 142	48p BC 141	30p BD 123	65p BF 177	35p C 442	30p T15 46	27p 2N 1309	23p BY 128	15p OA 10	35p OS 951	6p
AD 143	38p BC 142	30p BD 124	60p BF 178							

DIODES & RECTIFIERS

50p AA 119	8p BY 130	16p OA 47	7p
8p BY 133	21p OA 70		
8p BY 164	50p OA 79		
9p BYX 38 30	42p OA 81		
10p BYZ 10	35p OA 85		
10p BYZ 11	30p OA 90		
21p BYZ 12	30p OA 91		
22p BYZ 13	25p OA 95		
14p BYZ 16	40p OA 200		
12p BYZ 17	35p OA 202		
14p BYZ 18	35p SD 10		
13p BYZ 19	28p SD 19		
15p CG 62	IN 34		
12p CG (Eq) OA 91	5p IN 34A		
17p CG 651 (Eq)	IN 914		
12p OA 70-0A79	6p IN 916		
14p OA 5	35p IN 414B		
15p OA 55L	21p OS 1021		
15p OA 10	35p OS 951		

Cut these 3 pages out and keep for reference

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. count by weight	0.50
C 2	200	Capacitors mixed values approx. count by weight	0.50
C 3	50	Precision Resistors .1%, .01% mixed values	0.50
C 4	75	1/4 W Resistors mixed preferred values	0.50
C 5	5	Pieces assorted Ferrite Rods	0.50
C 6	2	Tuning Gangs, MW/LW VHF	0.50
C 7	1	Pack Wire 50 meters assorted colours	0.50
C 8	10	Reed Switches	0.50
C 9	3	Micro Switches	0.50
C 10	15	Assorted Pots & Pre-Sets	0.50
C 11	5	Jack Sockets 3—3.5m 2 — Standard Switch Types	0.50
C 12	40	Paper Condensers preferred types mixed values	0.50
C 13	20	Electrolytics Trans. types	0.50
C 14	1	Pack assorted Hardware — Nuts/Bolts, Gromets, etc.	0.50
C 15	4	Mains Toggle Switches, 2 Amp D/P	0.50
C 16	20	Assorted Tag Strips & Panels	0.50
C 17	10	Assorted Control Knobs	0.50
C 18	4	Rotary Wave Change Switches	0.50
C 19	3	Relays 6 — 24V Operating	0.50
C 20	4	Sheets Copper Laminate approx. 10" x 7" 0.50	

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19, C20. Component Lists for mail order available on request.

JUMBO COMPONENT PAKS

MIXED ELECTRONIC COMPONENTS Exceptionally good value

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price incl. P & P. £1.50 only


BRAND NEW POST OFFICE TYPE TELEPHONE DIALS

ONLY 35p each

THE NEW S.G.S. EA 1000 AUDIO AMP MODULE

Guar. 3 Watts RMS. Module Tested and Guaranteed.

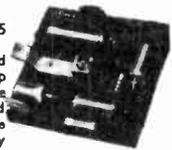Qty. 1—9 £2.63; 10—25 £2.28. Price each. Larger quantities quoted on request. Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.



SYSTEM 12 STEREO

Each kit contains two amplifier modules, 3 Watts RMS, two loudspeakers, 15 OHMS, The pre-amplifier, transformer, power supply module, front panel and other accessories as well as an illustrated stage-by-stage instruction booklet designed for the beginner. Further details available on request.



ONLY £16.95 FREE P & P

NOW-TURN OVER FOR MORE FANTASTIC OFFERS

The largest selection

NEW LOW PRICE TESTED S.C.R.'S.

PIV	1A	3A	5A	6A	7A	10A	16A	30A	30A
T05	T066	T066	T064	T048	T048	T048	T048	T048	
50	0.23	0.25	0.35	0.35	0.47	0.50	0.58	0.63	£1.15
100	0.25	0.33	0.47	0.47	0.50	0.58	0.63	0.63	£1.40
200	0.35	0.37	0.49	0.49	0.57	0.61	0.75	0.75	£1.60
400	0.43	0.47	0.56	0.56	0.67	0.75	0.93	0.93	£1.75
600	0.53	0.57	0.68	0.68	0.77	0.97	1.25	1.25	£1.90
800	0.63	0.70	0.80	0.80	0.90	1.30	1.50	1.50	£4.00

SILICON RECTIFIERS—TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0.04	0.05	0.05	0.07	0.14	0.21	0.30
100	0.04	0.06	0.05	0.13	0.16	0.23	0.75
200	0.05	0.09	0.06	0.14	0.20	0.24	1.00
400	0.06	0.13	0.07	0.20	0.27	0.37	1.25
600	0.07	0.16	0.10	0.23	0.34	0.45	1.88
800	0.10	0.17	0.11	0.25	0.37	0.58	2.00
1000	0.11	0.25	0.14	0.30	0.46	0.63	2.50
1200	0.11	0.33	0.18	0.38	0.47	0.75	

TRIACS

VBMOM	2A	6A	10A
TO-1	TO-45	TO-88	
5p	5p	5p	
100	30	50	76
200	50	60	90
400	70	75	110

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE
 2.5-37 400mW (100-7)
 (Case) 13p ea. 1W (Top-Hat) 18p ea. 10W (80-10 Hat) 25p ea. All fully tested 5% tol. and marked. State voltage required.

DIACS

FOR USE WITH TRIACS
 BR100 (D32) 87p each

10amp POTTED BRIDGE RECTIFIER

on heat sink
 100 PIV 90p each

FREE

One 50p Pak of your own choice free with orders valued £5 or over.

NEW LINE

Plastic encapsulated 2 amp Bridge Rects.
 50 v RMS 32p each
 100 v RMS 37p each
 400 v RMS 46p each

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed

Pak No.	EQVT
T1	8 2i3713
T2	8 1i1374
T3	8 1i1216
T4	8 2i3817
T5	8 2i3827
T6	8 2i3448
T7	8 2i3458
T8	8 2i3478
T9	8 2i3399A
T10	8 2i3417

All 50p each pak

UMJUNCTION

UT44, EQVT 2N2646.
 EQVT 8143, BF3900
 87p each, 25-99 25p
 100 UP 80p.

CADMIUM CELLS

ORP12 43p
 ORP60, ORP61 40p each

2N2060 NPN SIL. DUAL TRANS. CODE D1899 TEXAS.

Our price 25p each.

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706 B, BSY27 2N35A.

All available devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2060, BCY70. When ordering please state preference NPN or PNP.

180 VCB MIXIE DRIVER TRANSISTOR

8mm. BEX31 & C407, 2N1893 FULLY TESTED AND CODED ND 120, 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

SIL. G.P. DIODES 5p

300mW	30	0.50
40PIV (Min.)	100	1.50
80v 8mm.	500	5.00

Full Tested 1,000, 9.00
 Ideal for Organ Builders.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACE. OC25-28-29-30-35-36. NKT 401-402-404-405-406-451-402-453. T1307-307A, 2N250A, 2N456A-457A-458A, 2N511 A & B, 2N220-222, PTC VCO 80V VCEO 50V IC 6A/30 WATTS HTE 30-170.

F.E.T.'S

2N3819	40p
2N3820	50p
2N3821	35p
2N3823	40p
2N5458	40p
2N5459	40p
BFV10	40p
MPF105	40p

PRICE

1-24	25-99	100 up
43p each	46p each	50p each

NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each. Red cover edition.

SILICON High Voltage 500V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand New Coded R 2400 VCEO 250V VCEO 100V IC 6A/30 WATTS. HFE type 200T 5MBZ.

OUR PRICE EACH

1-24	25-99	100 up
50p	45p	40p

2N3055

115 WATT SIL POWER NPN 50p EACH

AD161/AD162 NPN

M/P COMP GERM TRANS. OUR LOWEST PRICE OF 55p PER PAIR

SILICON 50 WATTS MATCHED NPN/PNP BIP 19 NPN TO-3 PAIR.

BIP 20 PNP. Brand new.

1-24	25-99	100 up
80p	75p	65p

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS

NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Contents	Price
U1	120 Glass Sub-Min. General Purpose Germanium Diodes	50p
U2	60 Mixed Germanium Transistors AF/RF	50p
U3	76 Germanium Gold Bonded Sub-Min. like OA5, OA47	50p
U4	40 Germanium Transistors like OC81, AC128	50p
U5	60 200mA Sub-Min. Silicon Diodes	50p
U6	30 Sil. Planar Trans. NPN like BSY96A, 2N706	50p
U7	16 Sil. Rectifiers Top-Hat 750mA Vltg. Range up to 1,000	50p
U8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	50p
U9	20 Mixed Voltages, 1 Watt Zener Diodes	50p
U10	20 BA76 charge storage Diodes DO-7 Glass	50p
U11	25 PNP Sil. Planar Trans. TO-5 like 2N132, 2N2904	50p
U12	12 Silicon Rectifiers Epoxy 500 mA up to 800 PIV	50p
U13	30 PNP NPN Sil. Transistors OC200 and 2S 104	50p
U14	150 Mixed Silicon and Germanium Diodes	50p
U15	26 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	50p
U16	10 3Amp Silicon Rectifiers Stud Type up to 1,000 PIV	50p
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	50p
U18	8 6Amp Silicon Rectifiers BZY13 Type up to 800 PIV	50p
U19	26 Silicon NPN Transistors like BC108	50p
U20	12 1.5Amp Silicon Rectifiers Top-Hat up to 1,000 PIV	50p
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	50p
U22	30 MADT's like Mini Series PNP Transistors	50p
U23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	50p
U24	25 300 MHz NPN Silicon Transistors 2N708, BSY27	50p
U25	30 Fast Switching Silicon Diodes like IN914 Micro-Min	50p
U26	10 PNP Germanium AF Transistors TO-18 like AC127	50p
U27	10 1Amp SCR's TO-5 case up to 500 PIV CR51/25-600	£1.00
U28	15 Plastic Silicon Planar Trans. NPN 2N2926	50p
U29	20 Sil. Planar Plastic NPN Trans. Low Noise Amp 2N3707	50p
U30	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	50p
U31	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	50p
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	50p
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	50p
U34	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	50p
U35	26 Silicon Planar Transistors PNP TO-18 2N2806	50p
U36	26 Silicon Planar NPN Transistors TO-18 BFY50/61/52	50p
U37	30 Silicon Alloy Transistors 80-2 PNP OC200, 2S322	50p
U38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N8011	50p
U39	30 RF Germ. PNP Transistors 2N1308/5 TO-5	50p
U40	10 Dual Transistors 6 lead TO-5 2N2060	50p
U41	25 RF Germanium Transistors TO-5 OC45, NKT77	50p
U42	10 PNP Germanium PNP Transistors TO-18 NKT867, AF117	50p
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	50p
U44	20 Sil. Trans. Plastic TO-3 BC115/NPN	50p
U45	7 3A SCR. T066 up to 800 PIV	£1.00

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR TO-18

Let's and NPN Biot. to BP 25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 50p 55p

DTL & TTL INTEGRATED CIRCUITS

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Out" which include Functional and part Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	12 > 7400	50p	UIC46	5 > 7446	50p	UIC86	5 > 7486	50p
UIC01	12 > 7401	50p	UIC47	5 > 7447	50p	UIC87	5 > 7487	50p
UIC02	12 > 7402	50p	UIC48	5 > 7448	50p	UIC88	5 > 7488	50p
UIC03	12 > 7403	50p	UIC49	12 > 7450	50p	UIC89	5 > 7489	50p
UIC04	12 > 7404	50p	UIC50	12 > 7451	50p	UIC90	5 > 7490	50p
UIC05	12 > 7405	50p	UIC51	12 > 7452	50p	UIC91	5 > 7491	50p
UIC06	8 > 7406	50p	UIC52	12 > 7453	50p	UIC92	5 > 7492	50p
UIC07	8 > 7407	50p	UIC53	12 > 7454	50p	UIC93	5 > 7493	50p
UIC08	12 > 7410	50p	UIC54	12 > 7455	50p	UIC94	5 > 7494	50p
UIC09	12 > 7413	50p	UIC55	12 > 7456	50p	UIC95	5 > 7495	50p
UIC10	12 > 7420	50p	UIC56	12 > 7457	50p	UIC96	5 > 7496	50p
UIC11	12 > 7430	50p	UIC57	8 > 7458	50p	UIC97	5 > 7497	50p
UIC12	12 > 7440	50p	UIC58	8 > 7459	50p	UIC98	5 > 7498	50p
UIC13	8 > 7413	50p	UIC59	8 > 7460	50p	UIC99	5 > 7499	50p
UIC14	8 > 7414	50p	UIC60	12 > 7460	50p	UIC100	5 > 74100	50p
UIC15	12 > 7420	50p	UIC61	8 > 7470	50p	UIC101	5 > 74101	50p
UIC16	12 > 7430	50p	UIC62	8 > 7472	50p	UIC102	5 > 74102	50p
UIC17	12 > 7440	50p	UIC63	8 > 7473	50p	UIC103	5 > 74103	50p
UIC18	5 > 7443	50p	UIC64	12 > 7460	50p	UIC104	5 > 74104	50p
UIC19	5 > 7444	50p	UIC65	8 > 7470	50p	UIC105	5 > 74105	50p
UIC20	5 > 7445	50p	UIC66	8 > 7472	50p	UIC106	5 > 74106	50p
UIC21	5 > 7446	50p	UIC67	8 > 7473	50p	UIC107	5 > 74107	50p
UIC22	5 > 7447	50p	UIC68	8 > 7475	50p	UIC108	5 > 74108	50p
UIC23	5 > 7448	50p	UIC69	8 > 7476	50p	UIC109	5 > 74109	50p
UIC24	5 > 7449	50p	UIC70	8 > 7477	50p	UIC110	5 > 74110	50p
UIC25	5 > 7450	50p	UIC71	8 > 7478	50p	UIC111	5 > 74111	50p
UIC26	5 > 7451	50p	UIC72	8 > 7479	50p	UIC112	5 > 74112	50p
UIC27	5 > 7452	50p	UIC73	8 > 7480	50p	UIC113	5 > 74113	50p
UIC28	5 > 7453	50p	UIC74	8 > 7481	50p	UIC114	5 > 74114	50p
UIC29	5 > 7454	50p	UIC75	8 > 7482	50p	UIC115	5 > 74115	50p
UIC30	5 > 7455	50p	UIC76	8 > 7483	50p	UIC116	5 > 74116	50p
UIC31	5 > 7456	50p	UIC77	8 > 7484	50p	UIC117	5 > 74117	50p
UIC32	5 > 7457	50p	UIC78	8 > 7485	50p	UIC118	5 > 74118	50p
UIC33	5 > 7458	50p	UIC79	8 > 7486	50p	UIC119	5 > 74119	50p
UIC34	5 > 7459	50p	UIC80	5 > 7487	50p	UIC120	25 Asst.	50p
UIC35	5 > 7460	50p	UIC81	5 > 7488	50p	UIC121	74's	£1.50

Packs cannot be split, but 25 a.sorted pieces (our mix) is available as PAK UIC X1.

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES

18, BALDOCK STREET (A10), WARE, HERTS. TEL: 61593.
 OPEN MON. - SAT. 9.15 a.m. to 6 p.m. FRIDAY UNTIL 8 p.m.

All Mail Orders please add 10p post and packing. Send all Orders to Bi-Pak P.O. Box 6, Ware, Herts.

-the lowest prices!

74 Series T.T.L. I.C.'s

Bi-Pak Still Lowest In Price.
Full Specification Guaranteed.
All Famous Manufacturers.



	1	25	100+		1	25	100+
SN7400	0.15	0.14	0.12	SN7480	0.67	0.64	0.56
SN7401	0.15	0.14	0.12	SN7481	£1.00	0.90	0.90
SN7402	0.15	0.14	0.12	SN7482	0.67	0.64	0.56
SN7403	0.15	0.14	0.12	SN7483	0.67	0.64	0.56
SN7404	0.15	0.14	0.12	SN7484	0.77	0.74	0.68
SN7405	0.15	0.14	0.12	SN7485	0.77	0.74	0.68
SN7406	0.35	0.31	0.28	SN7486	£1.66	£1.80	£1.55
SN7407	0.35	0.31	0.28	SN74100	0.97	0.94	0.88
SN7408	0.18	0.17	0.16				
SN7409	0.18	0.17	0.16	SN74106	0.97	0.94	0.88
SN7410	0.15	0.14	0.12	SN74107	0.40	0.38	0.36
SN7411	0.28	0.24	0.23	SN74110	0.45	0.53	0.50
SN7412	0.35	0.31	0.28	SN74111	£1.25	£1.15	£1.10
SN7413	0.29	0.26	0.24	SN74118	£1.00	0.95	0.90
SN7416	0.43	0.40	0.38	SN74119	£1.35	£1.25	£1.10
SN7417	0.43	0.40	0.38	SN74121	0.40	0.37	0.34
SN7420	0.15	0.14	0.12				
SN7422	0.50	0.48	0.45	SN74122	£1.40	£1.30	£1.10
SN7423	0.50	0.48	0.45	SN74123	£2.80	£2.70	£2.60
SN7425	0.50	0.48	0.45	SN74141	0.67	0.64	0.58
SN7427	0.65	0.62	0.60	SN74145	£1.50	£1.40	£1.30
SN7428	0.70	0.65	0.60	SN74150	£3.00	£2.70	£2.50
SN7430	0.15	0.14	0.12	SN74151	£1.00	0.95	0.90
SN7432	0.60	0.52	0.40	SN74153	£1.30	£1.10	0.95
SN7433	0.80	0.75	0.70	SN74154	£1.90	£1.70	£1.60
SN7437	0.64	0.62	0.60				
SN7438	0.15	0.14	0.12	SN74155	£1.40	£1.30	£1.20
SN7440	0.15	0.14	0.12	SN74156	£1.40	£1.30	£1.20
SN7441	0.67	0.64	0.58	SN74157	£1.80	£1.70	£1.60
SN7442	0.67	0.64	0.58	SN74161	£1.80	£1.70	£1.60
SN7443	£1.30	£1.25	£1.20				
SN7444	£1.20	£1.20	£1.20	SN74162	£4.00	£3.75	£3.50
SN7445	£1.80	£1.77	£1.75	SN74163	£4.00	£3.75	£3.50
SN7446	0.97	0.94	0.88	SN74164	£2.25	£2.15	£2.10
SN7447	£1.00	0.97	0.95	SN74165	£2.25	£2.20	£2.15
SN7448	£1.00	0.97	0.95	SN74166	£3.50	£3.25	£3.10
SN7450	0.15	0.14	0.12	SN74174	£2.50	£2.30	£2.10
SN7451	0.15	0.14	0.12	SN74175	£1.80	£1.50	£1.40
SN7453	0.15	0.14	0.12	SN74176	£2.50	£2.40	£2.30
SN7454	0.15	0.14	0.12				
SN7455	0.15	0.14	0.12	SN74177	£2.50	£2.40	£2.30
SN7470	0.29	0.26	0.24	SN74180	£2.00	£1.90	£1.80
SN7472	0.29	0.26	0.24	SN74181	£2.50	£2.00	£1.75
SN7473	0.27	0.26	0.24	SN74182	£3.00	£1.90	£1.80
SN7474	0.37	0.35	0.32	SN74184	£3.50	£3.20	£3.00
SN7475	0.48	0.43	0.42	SN74190	£1.95	£1.90	£1.85
SN7476	0.40	0.39	0.36	SN74191	£1.80	£1.85	£1.80
SN7480	0.67	0.64	0.58	SN74192	£1.90	£1.90	£1.85
SN7481	£1.20	£1.15	£1.10	SN74193	£2.00	£1.90	£1.75
SN7482	0.67	0.66	0.60	SN74194	£2.70	£2.60	£2.50
SN7483	£1.10	£1.05	£0.95	SN74195	£2.00	£1.90	£1.80
SN7484	£1.00	0.95	0.90	SN74196	£1.80	£1.70	£1.60
SN7485	£1.00	£2.50	£2.40	SN74197	£1.80	£1.70	£1.60
SN7486	0.32	0.31	0.30	SN74198	£2.50	£2.00	£1.70
SN7489	£2.50	£2.25	£2.00	SN74199	£2.50	£2.00	£1.70

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0.1% DISTORTION
HI-FI AUDIO AMPLIFIER
THE AL50



- ★ Frequency response 15Hz to 100,000 - 1dB. **ONLY**
- ★ Load - 3, 4, 8 or 16 ohms. **£3.25p each**
- ★ Distortion - better than 0.1% at 1KHz.
- ★ Signal to noise ratio 80dB.
- ★ Supply voltage 10 - 35 Volts.
- ★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.



STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (rms) per channel, simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MTS0, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 62mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disco Systems, Public Address, Intercom Units etc. Handbook available 10p. PRICE £3.95

TRANSFORMER BMT80 £1.95 p. & p. 25p.

STEREO PRE-AMPLIFIER, TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable base and treble controls.



SPECIFICATION
 Frequency Response 20Hz - 20KHz ± 1dB
 Harmonic Distortion better than 0.1%
 Inputs: 1. Tape Head 1.25 mV into 60KΩ
 2. Radio, Tuner 35 mV into 60KΩ
 3. Magnetic P.U. 1.5 mV into 60KΩ
 All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB, from 20Hz to 20KHz.
 Base Control ± 15dB @ 20Hz Treble Control ± 15dB @ 20KHz
 Filters: Rumble (High Pass) 100Hz
 Scratch (Low Pass) 8KHz
 Signal/Noise Ratio better than - 65dB
 Input overload + 25dB Supply + 35 volts @ 30mA
 Dimensions 292mm x 82mm x 36mm Price £11.00

SPECIAL COMPLETE KIT COMPRISING 3 AL50's, 1 SPM80, 1 BMT80 and 1 PA100 ONLY £23.00 FREE p & p.

All prices quoted in new pence Gird No. 338-7006
 Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE, HERTS
 Postage and packing add 10p. Overseas add extra for airmail
 Minimum order 50p. Cash with order please.
 Guaranteed Satisfaction or Money Back

LOGIC DTL 930 SERIES

LINEAR I.C.'s— FULL SPEC.

ROCK BOTTOM PRICES

Type No.	1-24	25-99	100 up
BP 201C—SL201C	63p	63p	45p
BP 701C—SL701C	63p	60p	45p
BP 702C—SL702C	63p	60p	45p
BP 702—72702			
BP 708—72708	53p	45p	40p
BP 709P—µA709C	36p	34p	30p
BP 710—72710	36p	34p	30p
BP 711—µA711	44p	43p	40p
BP 741—72741	45p	45p	40p
µA 705C—µA705C	75p	60p	50p
TA A263	25p	25p	55p
TA A293	70p	70p	70p
TA A360	170p	160p	160p

Type No.	1-24	25-99	100 up
BP930	15p	11p	10p
BP932	15p	11p	11p
BP933	15p	11p	11p
BP935	15p	11p	11p
BP936	15p	11p	11p
BP944			
BP945	15p	12p	11p
BP946	15p	11p	10p
BP948	25p	24p	20p
BP961	65p	60p	45p
BP962	11p	11p	10p
BP963	65p	60p	45p
BP969A	40p	25p	25p
BP969B	40p	25p	25p
BP969C	40p	25p	25p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

NUMERICAL INDICATOR TUBES

MODEL	CD68	GR 116	3015F
Anode voltage (Vdc)	170 min	175 min	5
Cathode cur'nt(mA)	2.3	14	
Numeral h'ght (mm)	16	13	9
Tube height (mm)	47	32	22
Tube diameter (mm)	19	13	12
I.C. driver rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0.9 + Decimal point: All side viewing: Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

	Price each
Epoxy TO-5 case	1-24 25-99 100 up
uL900 Buffer	85p 85p 77p
uL914 Dual 2 1/2 p	
uL915	85p 85p 87p
uL923 J-K Flip-Flop	85p 85p 87p
Date and Circuits Booklet for I.C.'s	
Price 7p.	

DUAL IN LINE SOCKETS

	1-24	25-99	100 up
Prof. Type No			
TSO14 pin type	30p	27p	25p
TSO16 pin type	35p	32p	30p
Low Cost No.			
BPS 1	15p	13p	11p
BPS 16	16p	14p	12p

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	..	18p
DTB4 Transistor & Valve circuitry for D.P. Coils	..	18p
DTB9 Valve Type Coil Pack Application circuitry	..	18p
MD.1 Decoder Circuitry for Stereo Reception	..	21p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers

Have fun with electronics...



Radionic Construction Kits

NO SOLDERING BATTERY OPERATED

Build your own radio receiver and many exciting experiments with the unique printed circuit board and mounted components. Easy to build, no soldering, battery operated, plus a fully illustrated instruction manual giving precise directions for each experiment. Ideally suitable for both the experimenter and beginner.

Radionic Products Limited

St. Lawrence House, Broad Street, Bristol BS1 2HF.
Tel: 0272 25351

Member of the ESL BRISTOL Group of Companies



Please send me literature on Radionic radio and electronics construction kits.

NAME _____
ADDRESS _____

RC

BI-PRE-PAK



COMPLETE TELEPHONES
Normal household type as supplied to the Post Office, ex. G.P.O. Only **95p** each, p. & p. 35p each.



TELEPHONE DIALS
Standard Post Office type. Guaranteed in working order.
ONLY 50p
p. & p. 15p.

TESTED AND GUARANTEED PAKS

H2	4	Photo Cells, Sun Batteries, 0.3 to 0.5V, 0.5 to 2mA.	50p
H79	4	1N4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
H81	10	Reed Switches, mixed types large and small	50p
H99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H30	20	1 Watt Zener Diodes, 6.8 - 43V	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon Planar types	50p
H39	10	Integrated Circuits: 6 Gates, BMC 962, 4 Flip Flops, BMC 945.	50p
H40	20	BFY507, 2N696, 2N1613, NPN Silicon uncodded TO-5	50p

UNMARKED UNTESTED PAKS

H4	150	Germanium Diodes Min. gas type	50p
H3	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
H4	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
H4	50	Sil. Diodes sub. min. 1N914 and 1N916 types	50p
H4	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
E1	50	Germanium Transistors PNP, P, F, & R, F	50p
H4	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H14	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	50p
H17	20	3 amp Silicon Stud rectifiers, mixed volts	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic Mixed volts	50p

MAKE A REV. COUNTER FOR YOUR CAR

The TACHO BLOCK This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

4p		4p	
AC107	0-15	OC170	0-23
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-15	OC201	0-25
AC176	0-20	2G301	0-13
ACY17	0-20	2G303	0-13
AF239	0-30	2N711	0-15
AF186	0-20	2N1302-3	0-17
AF139	0-30	2N1304-5	0-20
BC154	0-20	2N1306-7	0-22
BC107	0-10	2N1308-9	0-20
BC108	0-10	2N3819FET	0-40
BF194	0-15	2N4416FET	0-50
BC109	0-10	Transistors	0-40
BF274	0-20	OC20	0-25
BFY50	0-15	OC23	0-25
BSY25	0-13	OC25	0-25
BSY26	0-13	OC28	0-30
BSY27	0-13	OC35	0-30
BSY28	0-13	OC36	0-37
BSY29	0-10	AD149	0-30
BSY95A	0-10	AU110	0-75
OC41	0-15	25034	0-25
OC44	0-10	2N3055	0-50
OC45	0-10	Diodes	0-10
OC71	0-10	AA42	0-07
OC72	0-13	OA95	0-07
OC81	0-13	OA79	0-07
OC81D	0-18	OA81	0-07
OC83	0-13	IN914	0-06
OC139	0-15		
OC140			

POWER TRANSISTOR PRICE BREAKTHROUGH!

PLASTIC CASED SILICON POWER TRANSISTORS OF LATEST DESIGN. 40 WATTS and 90 WATTS. PNP & NPN TYPES.

ALL TYPES AVAILABLE AT THE MOST SHATTERINGLY LOW PRICES OF ALL TIME. ALL ARE FULLY TESTED, MARKED AND GUARANTEED!

	40W	NPN	1-12	13-25	26-50
PAK	40W	NPN	20p	48p	44p
MP 40	40W	PNP	21p	19p	17p
MP 90	90W	NPN	24p	22p	20p
	90W	PNP	25p	23p	21p

A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs **£3.50**, post paid.

A MUST for Colour T.V. Alignment.

Our famous P1 Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels Identification Chart supplied to give some information on the Transistor.

Please ask for Pak P1; only 50p 1cp P & P on this Pak.

FREE CATALOGUE

FOR TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS.



8 RELAYS FOR £1

VARIOUS TYPES POST & PACKING 25p.

VARIOUS TYPES POST & PACKING 25p INTEGRATED CIRCUITS

THE LOWEST PRICES OF ALL FOR YOUR DTL LOGIC

		1-12	13-25	26-50
Clocked Flip Flop	BMC931	20p	18p	16p
Ex. 2/4-input Buffer	BMC932	12p	11p	10p
2/4-input Expander	BMC933	12p	11p	10p
Hex. Inverter	BMC934	12p	11p	10p
Hex. Inverter	BMC935	12p	11p	10p
Hex. Inverter	BMC936	12p	11p	10p
Hex. Inverter	BMC937	12p	11p	10p
Decade Counter	BMC938	25p	23p	21p
Div. by 16 Counter	BMC939	25p	23p	21p
Hex. Inverter	BMC940	12p	11p	10p
Hex. Inverter	BMC941	12p	11p	10p
Type D Flip Flop	BMC942	20p	18p	16p
Ex. 2/4-input Power	BMC944	12p	11p	10p
Clocked Flip Flop	BMC945	20p	18p	16p
Quad Inverter	BMC946	11p	10p	9p
Clocked Flip Flop	BMC948	20p	18p	16p
Quad Inverter	BMC949	12p	11p	10p
Pulsed Trig. Binary	BMC950	20p	18p	16p
Monostable Multivib.	BMC951	25p	23p	21p
Dual J/K Flip Flop	BMC953	20p	18p	16p
Dual J/K Flip Flop	BMC955	20p	18p	16p
Quad. 2-input Power	BMC956	20p	18p	16p
2-input Gate	BMC958	12p	11p	10p
3-input NAND Gate	BMC961	12p	11p	10p
3-input NAND Gate	BMC962	11p	10p	9p
Audio Amp. 3-watts	SL403D	£1.50	£1.40	£1.36
Linear Op. Amp	709C	25p	20p	15p
Decade Counter	SN7490	65p	60p	55p

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each. Now new low profile type. 16 pin type at 19p each.

BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines: **B.P.I. Transistor Equivalents and Substitutes;** 40p

This includes many thousands of British U.S.A., European and C.V. equivalents. **The Iltiff Radio Valve & Transistor Data Book** 9th Edition P & P 21p 75p

Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER. PLEASE Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD


DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX, SSO 9DF
TELEPHONE: SOUTHEND (C702) 46344

PROFESSIONALS



For the construction of your circuits the following items and free literature are available from your local retailer.

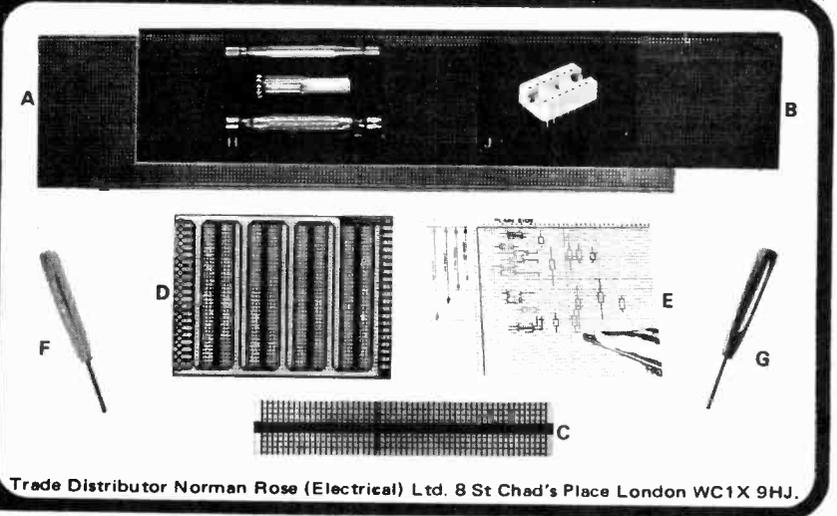- A VEROBOARD
- B PLAIN BOARD
- C GROUP BOARD
- D D.I.P. BREAD BOARD
- E DESIGN SHEET
- F SPOT FACE CUTTER
- G PIN INSERTION TOOL
- H TERMINAL PINS
- J D.I.P. SOCKET




Trade Distributor Norman Rose (Electrical) Ltd. 8 St Chad's Place London WC1X 9HJ.

USE VERO CIRCUIT BOARDS AND ACCESSORIES

AND NOW TO HOUSE YOUR CIRCUITRY

Verobox ALUMINIUM ENCLOSURES

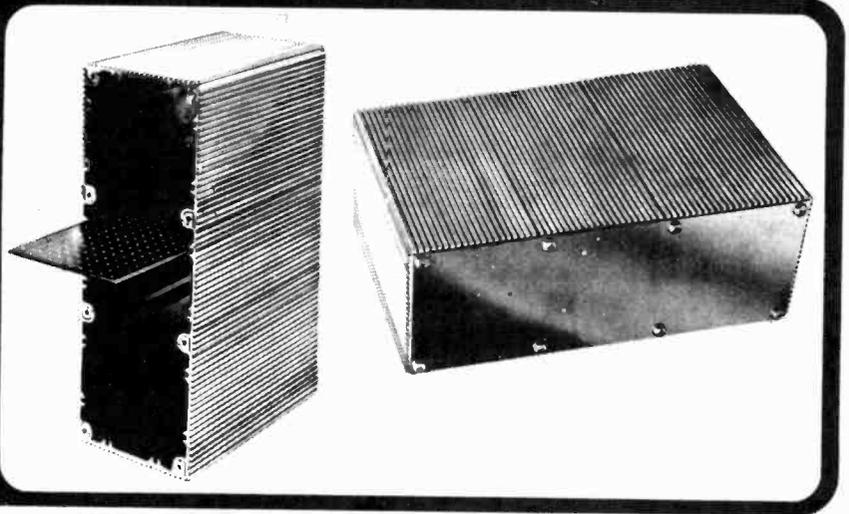- ★ 6 standard sizes available from your retailer.
- ★ Made from precision extrusions with integral board guide slots.
- ★ Finned sides improve appearance and radiate heat.
- ★ Parallel sides for ease of component mounting.



VERO ELECTRONICS LTD.,

Industrial Estate, Chandler's Ford, Eastleigh, Hants SO5 3ZR Tele Chandler's Ford 2952 Telex 47551
 RADIO & ELECTRONICS CONSTRUCTOR

THE MODERN BOOK CO

AMATEUR RADIO TECHNIQUES

by Pat Hawker G3VA AN RSGB PUBLICATION

£1.60

Postage 10p

Transistor Substitution Handbook No. 12
by The Howard W. Sams Engineering Staff

£1.40 Postage 10p

A Guide to Amateur Radio
by Pat Hawker G3VA 40p Postage 6p

RCA Solid State Hobby Circuits Manual

by RCA £1.05 Postage 12p

Beginner's Guide to Practical Electronics
by R. H. Warring £1.25 Postage 10p

Hi-Fi in the Home
by John Crabbe £2 Postage 12p

Beginner's Guide to Television
by Gordon J. King £1.60 Postage 10p

Electronics Pocket Book
by J. P. Hawker £1.60 Postage 12p

Servicing with the Oscilloscope
by Gordon J. King £1.80 Postage 12p

The Mazda Book of Pal Receiver Servicing
by D. J. Seal £3.50 Postage 20p

VHF-UHF Manual

by Jessop £1.60 Postage 12p

SCR Manual
by General Electric £1.55 Postage 10p

20 Solid State Projects for the Car & Garage
by R. M. Marston £1.20 Postage 70p

Electronics Experimenters Circuit Manual
by General Electric £1 Postage 7p

110 Semiconductor Projects for the
Home Constructor

by R. M. Marston £1.20 Postage 7p

38 Practical Tested Diode Circuits for the
Home Constructor

by B. B. Babani 35p Postage 5p

T.V. Fault Finding 405/625 Lines
by J. R. Davies 50p Postage 7p

Colour Television with Particular
Reference to the Pal System
by Patchett £3 Postage 10p

Radio Valve & Transistor Data
by A. M. Ball 75p Postage 10p

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

SAVE TIME AND MONEY

LIST PRICE **£6.25**

OUR PRICE **£4.84**



As supplied by us to **SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY.** Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21½" x 11½" x 6½". Size of drawers 6¼" x 2¼" x 1¼". Other sizes available. Callers welcome Mon-Sat. 9 a.m.-1 p.m. 2 p.m.-6 p.m. **NEW** as illustrated **OUR PRICE ONLY £4.84** plus 35p carriage on orders less than £10. Money back guarantee. **SEND FOR FREE COLOUR BROCHURE.**

TRADE AIDS

(DEPT. RC2) 11 CHILTERN DRIVE,
BERRYLANDS, SURBITON, SURREY

01-399 4383

100 yds. Berrylands Railway Station

The New Styled "MULTI-MINI" TWIN VICES



An extra "Pair of Hands" for those tricky jobs

ASSEMBLY - SOLDERING - GLUING - WIRING - DRILLING ETC.

- ★ INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- ★ JAWS WILL FIRMLY GRIP ROUND, FLAT, SQUARE OR HEXAGONAL PARTS.

TWIN VICE: £8.95 (25p - p&p)

ALSO AVAILABLE

SINGLE VICE: £5.45 (21p - p&p)

CANLEY ENGINEERING (SALES) LTD.

Dept. C/RC1
OSBORNE ROAD, COVENTRY CV5 6EA
Tel. (0203) 77163/4



LOUDSPEAKER BARGAINS

Fane Pop 100 watt 18" 8/15 ohm	£19.50
Fane Pop 50 watt 15" 8/15 ohm	£11.15
Fane Pop 50 watt 12" 8/15 ohm	£ 9.25
Fane Pop 25/212 25 watt 8/15 ohm	£5.40
Fane Pop 15 12" 10 watt 8/15 ohm	£4.00
Baker Group 25 12" 3.8 or 15 ohm	£8.60
Baker Group 35 12" 3.8 or 15 ohm	£8.00
Celestion PS8 for Unilux	£2.35
EMI 13 x 8, 3.8 or 15 ohm	£2.50
EMI 13 x 8, 3.8 or 15 ohm	£2.60
EMI 13 x 8 twin/tw, 3.8 or 15 ohm	£3.60
EMI 13 x 8 type 350 15 watt 8 ohm	£8.00
Richard Allan 8" 3.8, or 15 ohm	£2.35
Richard Allan 12" dual cone 3 or 15 ohm	£2.50
Fane 8" d/cone 808T 8 or 15 ohm	£2.85
Fane 8" d/cone, roll surround, 807T 8 or 15 ohm	£3.50
Elac 9 x 5, 59RM109 15 ohm	£2.70
Elac 9 x 5, 59RM114 8 ohm	£2.70
Elac 6½" dual cone 8 ohm	£2.25
Elac 6½" d/cone, roll surround 8 ohm	£3.50
Elac 4" tweeter 8 ohm	£1.50
Crossover for above (p & p free)	£1.50
Goodmans 8P 8 or 15 ohm	£4.75
Goodmans 10P 8 or 15 ohm	£5.25
Goodmans 12P 8 or 15 ohm	£10.50
Goodmans 15P 8 or 15 ohm	£17.00
Goodmans 18P 8 or 15 ohm	£27.00
2" 2¼" or 3" 80 ohm	.65
Philips 5" 8 ohm	£1.95
7 x 4 or 8" x 5", 3 or 8 ohm	£1.50
10" x 6" 3.8 or 15 ohm	£2.00

FREE with orders over £5.00 "HiFi loudspeaker enclosures" book.

All units guaranteed new and perfect.

Prompt despatch. P & P 25p per speaker.

Send for our free booklet "Choosing a speaker".

WILMSLOW AUDIO (Dept. RC)

10 Swan St., Wilmslow,
SK9 1HF, Cheshire



Christmas Presents a Problem!

We can take it for granted that she will be buying you the very thing you've set your heart on, so let's concentrate on that superb present you are so generously thinking of buying her! Simple - as everybody knows, today's finest range of radio and electronic components is to be found in the Home Radio Components Catalogue. You could buy her a copy, so that she can pick out just what she wants. On second thoughts, that might complicate matters. Better make the choice yourself. After all, you want it to be a surprise for her on Christmas morn! Moreover, you'll both have the Home Radio Components Catalogue and can spend many hours together, browsing through it. The Catalogue is crammed full with details of 8,000 items, of which about 1,500 are illustrated. It costs

only 70 pence, including post and packing, and each copy contains 10 vouchers worth 5p each.

Of course, you can call at our shop (we're open 9 to 5.30 Monday to Saturday, except Wednesday 9 to 1) and get just what you want straight off the shelf. Incidentally, a catalogue bought this way will cost you only 50 pence. Whether you order by post or buy over the counter you should join our Credit Account Service. It's the simple and convenient way of buying all your radio and electronic components. We supply pre-paid envelopes and order forms, and no matter how many orders you send us you make only one payment per month. Full details and entry forms are in the catalogue.



The price of 70p applies only to catalogues purchased by customers in the UK and to BFPO addresses.

218



POST THIS COUPON with your cheque or postal order for 70 pence.

Name

Address



Home Radio (Components) Ltd.
Dept. RC, 234-240 London Road, Mitcham CR4 3HD.

RADIO & ELECTRONICS CONSTRUCTOR

RADIO & ELECTRONICS CONSTRUCTOR

NOVEMBER 1972

CONTENTS

Vol. 26 No. 4

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 *Telegrams*
Databux, London

© Data Publications Ltd., 1972. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £2.70 (U.S.A. and Canada \$7.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

LOW VOLTAGE TIMER by R. L. Graper	220
NEW PRODUCTS	225
THE 'S.A. JUNIOR' PORTABLE RECEIVER by Sir Douglas Hall, K.C.M.G., M.A.(Oxon)	226
NEWS AND COMMENT	232
PHOTOGRAPHER'S METRONOME (Suggested Circuit 264) by G. A. French	234
50 YEARS 'ON THE AIR'	236
CYCLOPS (Electronic Robot) – Part 5 by L. C. Galitz	237
'LASER-LINE'	241
SHORT WAVE NEWS by Frank A. Baldwin	242
THE 'WYVERN' 160 METRE SOLID STATE TRANSMITTER by John R. Green, B.Sc., G3WVR	244
MULTIMETER INPUT RESISTANCE BOOSTER by M. N. Pointing and G. A. Miller	252
RECENT PUBLICATIONS	255
UNUSUAL TRANSFORMER EFFECT by A. L. Chivers	256
QSX by Frank A. Baldwin	258
TRADE NEWS	259
HIGH-SPEED TRAIN COMMUNICATIONS	260
IN YOUR WORKSHOP	261
RADIO TOPICS by Recorder	268
RADIO CONSTRUCTOR'S DATA SHEET No. 68 (Coil Data 1)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

Radio & Electronics Constructor is printed by Carlisle Web Offset.

DECEMBER ISSUE WILL BE
PUBLISHED ON DECEMBER 1st

LOW VOLTAGE

This mechanically operated timing unit switches off a transistor radio after any preset period up to an hour.

THE DEVICE TO BE DESCRIBED CONSISTS OF A LOW voltage time switch and it is intended for use with transistor radio receivers. It must *not* be used to switch voltages or currents in excess of those employed for small battery-operated transistor radios.

The basis of the device is a Smiths 'Ringer', this being a clockwork timer manufactured by Smiths Industries Limited which, after the completion of a preset timing period, causes a bell to sound. The timer is suitable for domestic use and offers timing periods up to 1 hour. It has a disc on the front panel calibrated in minutes and this is rotated clockwise by means of an integral handle to the delay period required, as indicated by an arrow on the casing. The timer commences operation as soon as the disc is released; the disc rotates slowly anti-clockwise until its zero mark appears at the arrow on the casing. A bell then rings and the timing period is completed. The particular Smiths 'Ringer' employed by the author has a case diameter of approximately 2½ in.

SWITCHING OPERATION

In order that the 'Ringer' may be employed for switching purposes, a small wedge-shaped cam is mounted on the front panel disc at or near the zero mark. This cam causes a moving contact to lift from a fixed contact when, at the end of a timing period, the disc returns to the zero position. It is necessary for the 'Ringer' to be securely fitted inside a suitable housing in order that the contacts may be mounted adjacent to the disc. The author's design is such that the 'Ringer' can be readily removed from the housing at any time. Similarly, the cam may easily be removed from the disc, allowing the 'Ringer' to be returned to normal usage.

An idea of the overall construction may be obtained from Fig. 1. It will be seen that there is a small adjusting screw on the contact which is raised by the cam at the end of the timing period. The timing unit couples to the receiver being switched by way of a length of twin flex

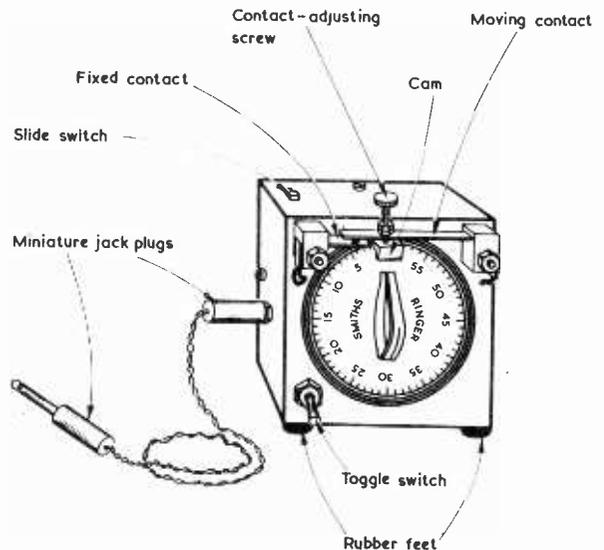



Fig. 1 The appearance of the completed timing unit. The front disc is calibrated in minutes from zero to 60 and rotates anti-clockwise as the timing period proceeds. At the end of the period the cam appears under the contact-adjusting screw and raises the moving contact

terminated in jack plugs. In addition to the timer-actuated contacts, two miniature switches, one slide and one toggle, are fitted to the housing, as also is a miniature jack socket. However, the miniature slide switch is only required if an additional contact, to be discussed later, is to be incorporated.

The main sections of the housing are illustrated in Fig. 2. The dimensions shown in this diagram exactly

RADIO & ELECTRONICS CONSTRUCTOR

TIMER

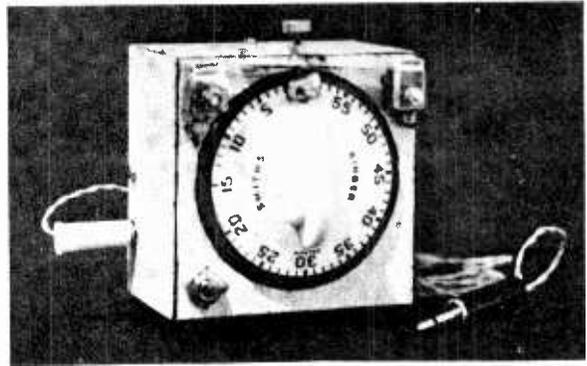

The prototype timing unit. This photograph was taken before the addition of the 'switch-on' contact.

by
R.L. Graper

A holes 6BA clear
B holes $1/16''$ dia
C holes see text

$1/4'' \times 1/4''$ wooden dowel
4 off


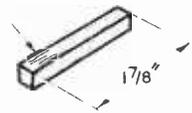


Fig. 2 The parts which are required for the timing unit housing

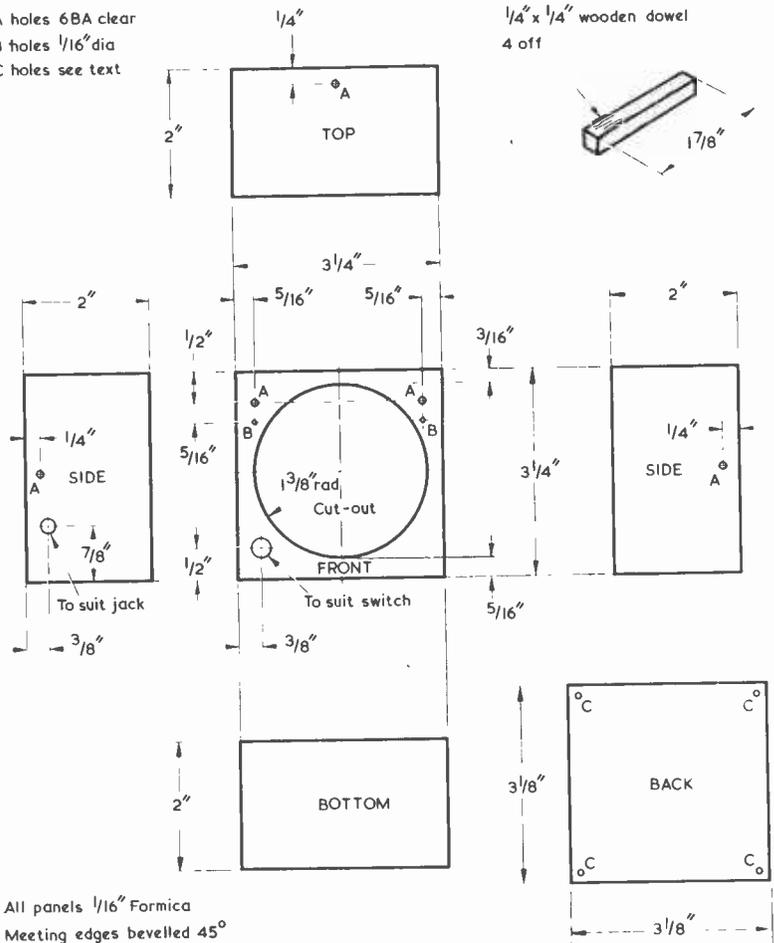

suited the 'Ringer' employed by the author, but readers are advised to measure up the particular timer to be used before constructing the case to ensure that it will fit comfortably. If necessary, the dimensions may be modified to suit.

All the panels shown in Fig. 2 are $\frac{1}{16}$ in. Formica. The meeting edges are bevelled at 45° to give a neat finish. There are two pairs of panels having the same outside dimensions, these being the top and bottom and the two sides. These pairs should be matched together during construction. If it is found difficult to obtain a miniature toggle switch sufficiently small to fit into the position allocated for it on the front panel it may alternatively be mounted on the top panel with its body behind the 'Ringer' after the latter has been inserted.

Apart from the back, all the parts of the box are glued together with Evo-Stik contact adhesive, the corners being strengthened with the four lengths of dowel shown in Fig. 2. The assembly of the housing requires some patience and the Evo-Stik instructions should be strictly followed. If desired, the four dowels may be glued to the sides first, being just clear of the edge bevelling. When the glue has set, the top, bottom and front may be added. After assembly a length of nylon cord should be wound tightly a number of times round the box and the whole set aside for complete drying. All holes should, of course, be cut out before assembly. The back is fitted after the whole unit has been assembled and wired up. It is secured by short pins passing through holes 'C' in the back panel and thence into the ends of the four dowels.

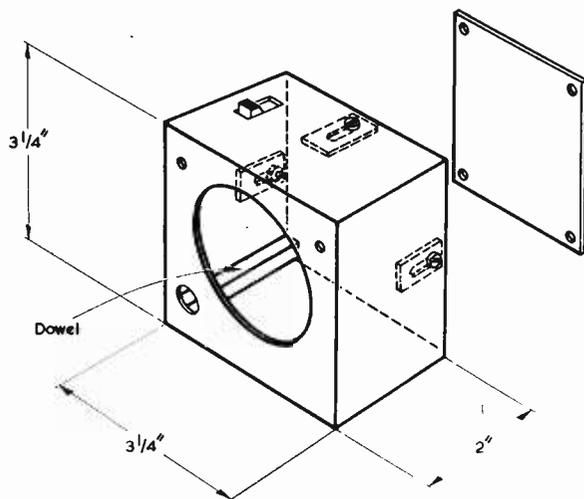


Fig. 3 The completed housing. The slide switch shown here is only needed if an extra 'switch-on' contact is added

When completed, the box has the appearance shown in Fig. 3. (This diagram also shows the slide switch, which as just stated may not be needed, and three Formica pieces which hold the 'Ringer' in position and which will shortly be described.)

The 'Ringer', in normal use, has a shape which causes its front panel to slope backwards slightly. In order that its front panel may be brought into the same plane as the front of the housing a wedge is inserted, inside the housing, beneath the bottom rear of the

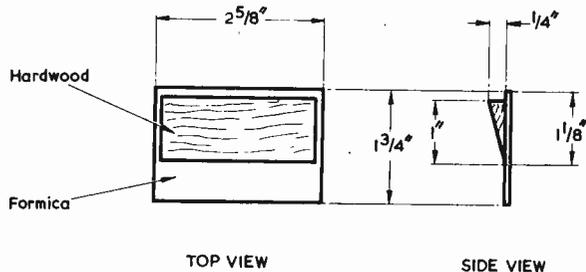


Fig. 4 The wedge assembly. This tilts the 'Ringer' slightly forwards so that its front is in the same plane as the front panel of the housing

'Ringer'. The wedge assembly is made up as shown in Fig. 4, and it consists of a piece of Formica with the wedge glued to it. After the 'Ringer' has been inserted in the housing the piece of Formica is slid underneath it, whereupon the wedge provides the requisite tilting forwards of the 'Ringer'. The wedge assembly is not fastened permanently inside the housing; it may be removed at any time, thereby allowing the 'Ringer' to be taken out again. The width shown for the Formica piece, $2\frac{5}{8}$ in., assumes exact dimensioning of the housing and dowels. If the width available in the housing is fractionally smaller than $2\frac{5}{8}$ in., the width of the Formica piece in the wedge assembly should be reduced accordingly.

Also holding the 'Ringer' in position are three Formica strips having the dimensions shown in Fig. 5. These are mounted by means of 6BA nuts and bolts to the 'A' holes in the top and two sides, as indicated in Fig. 3. A plain 6BA washer is included under each nut. After the 'Ringer' has been inserted these three pieces are secured in place, being pushed forward until they bear against the rear top and side edges of the 'Ringer', whereupon the 6BA bolts are finally tightened. The slots in the three pieces have a width which allows a 6BA bolt to pass through. It may be necessary to add a spacing washer between any of the three pieces and the panel to which it is secured if it is found that the piece does not butt reliably against the rear surface of the 'Ringer'.

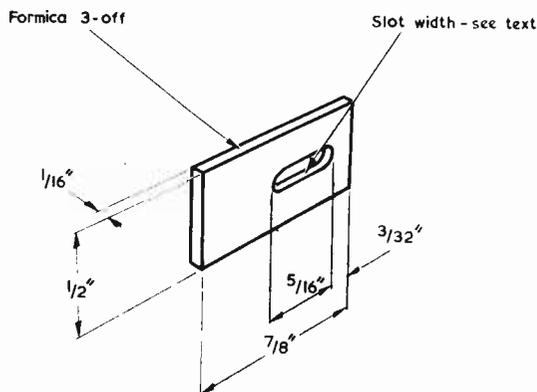


Fig. 5 One of three Formica pieces which assist in holding the 'Ringer' in position

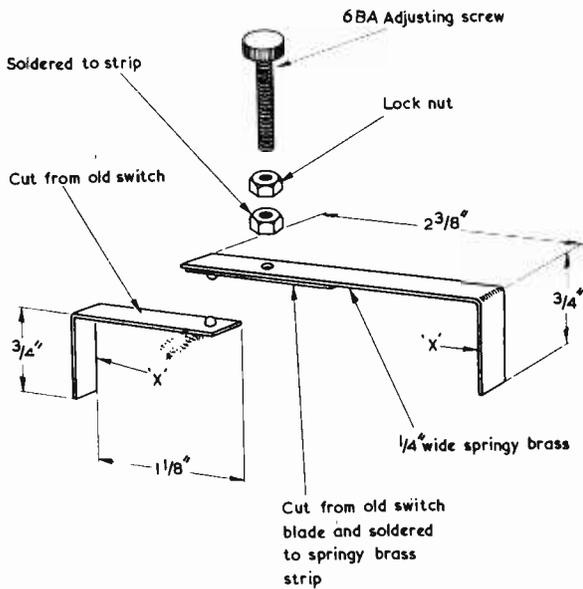


Fig. 6 Details of the contacts and their construction

CONTACTS

The construction of the contacts operated by the 'Ringer' depends to some extent upon the materials available to the reader. The author's method of construction is illustrated in Fig. 6, in which it will be seen that contacts cut from a discarded switch of the lever-operated type are employed, one of these being soldered to a length of springy brass strip. The width of the contacts and the strip is $\frac{1}{4}$ in. Also shown are the 6BA adjusting screw and two 6BA nuts. The lower of these is brass and is soldered to the brass strip (this may be achieved by holding it temporarily in position with a steel screw, which will not solder readily), whilst the upper nut is threaded onto the adjusting screw and acts, later, as a lock-nut.

The two contact mountings are made as illustrated in Fig. 7. Each mounting consists of two halves of

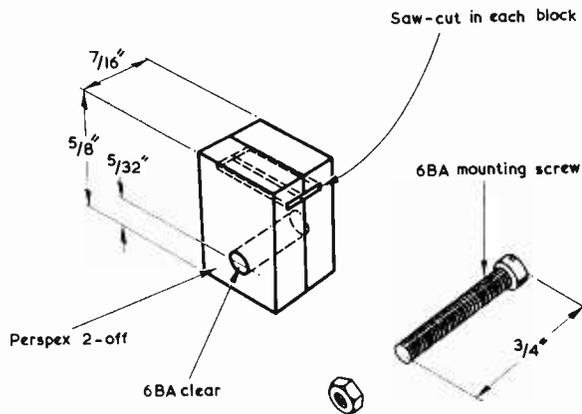


Fig. 7 The contact mountings are made up as shown here

Perspex which, when bolted together, give overall dimensions of $\frac{3}{8}$ by $\frac{7}{8}$ in. There is a saw-cut on the inside edge of each half which, when the pair are assembled, takes the contact strip. The distance of the saw-cut from the top of the mounting is best judged individually; that for the springy brass strip should be a little higher than that for the fixed contact.

Referring back to Figs. 1 and 2, the contact mountings are secured with $\frac{3}{8}$ in. 6BA bolts and nuts at holes 'A' of the front panel with the saw-cuts horizontal and above the securing bolts. The contacts are held in the saw-cuts with their ends 'X' (see Fig. 6) on the outside and pointing downwards. Thin p.v.c. insulated wires are soldered to the ends 'X' and are passed through holes 'B' in the front panel to the inside of the housing.

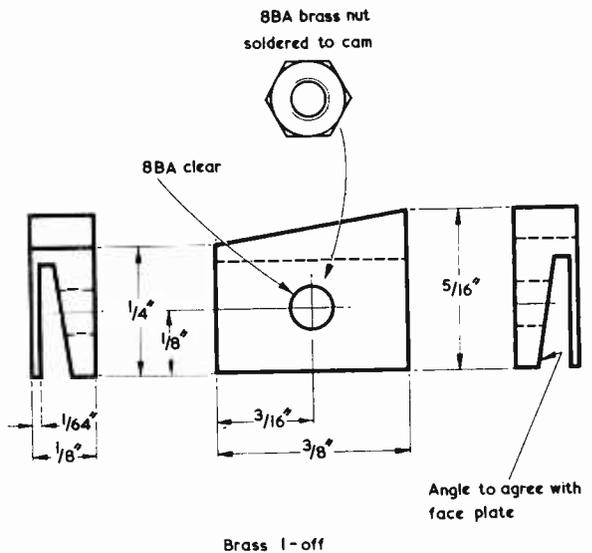


Fig. 8 Dimensions of the cam. This is secured to the front disc of the 'Ringer'

The cam has the dimensions given in Fig. 8. This is made of brass and has a wedge shape at its upper end which causes the moving contact to be raised when the front disc, or face plate, of the 'Ringer' approaches the zero setting. The slot in the cam passes over the edge of the front disc of the 'Ringer' and should be cut so that it is very nearly $\frac{1}{4}$ in. deep. The cam is secured to the front disc by an 8BA nut soldered to the front surface of the cam. It is important for the upper surface of the cam to be as smooth as possible, in order to ensure minimum friction with the lower end of the contact adjusting screw. A little light lubricant, such as molybdenum disulphide, can be helpful here.

As a final operation, four rubber feet are added at the corners of the bottom panel of the housing. These may consist of four rubber grommets secured with adhesive.

When the construction of the timing unit has been completed, the moving contact is adjusted for the desired pressure on the fixed contact. The distance over which the moving contact is displaced upward at the end of the timing cycle is then preset by means of the 6BA screw which passes through it.

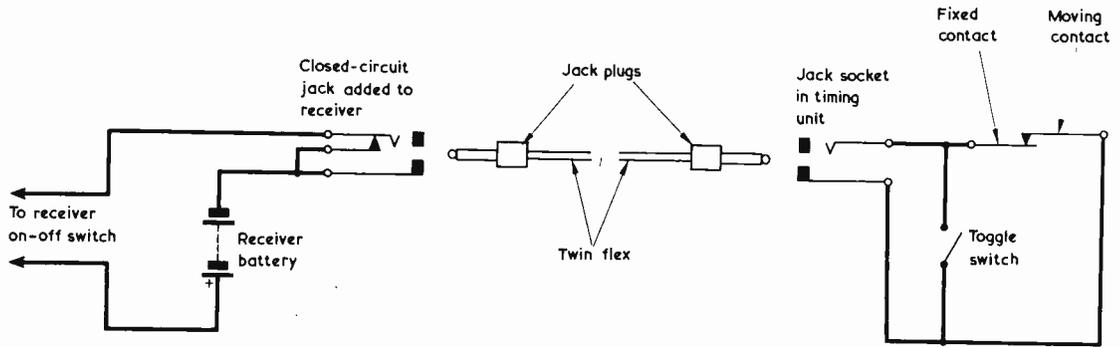


Fig. 9 The circuit of the timing unit and the manner in which it is coupled to the receiver. The closed-circuit jack may be inserted in the positive lead from the battery instead of the negative lead if desired

CIRCUIT

The timing unit connects to the receiver in the manner shown in Fig. 9. A miniature closed-circuit jack socket is added to the receiver, this being inserted in series with one of the battery leads. A closed-circuit jack socket is employed because this enables the receiver to function normally when the jack plug is removed. Since it is a little difficult to visually trace the appropriate tags of a closed-circuit jack socket, it will probably be best to identify them by a continuity test before installing and wiring in the socket.

The wire coupling the timing unit to the receiver consists of twin flex having a miniature jack plug at each end. One jack plug fits into the jack socket at the receiver whilst the other fits into a jack socket on the side panel of the timing unit. The twin flex can have any convenient length.

The internal wiring in the housing follows the circuit of Fig. 9. The timing contacts can be overridden by the miniature toggle switch, should this be desired.

EXTRA CONTACT

As so far described, the timing unit enables a circuit to be broken after any period up to an hour. A particularly useful application is the switching off of a bedside transistor radio. The radio can be tuned to any transmission and the timing unit set up. If the listener falls asleep during the timing period the receiver is automatically switched off at its end.

The writer felt it would be of value if the timing unit could also switch a transistor radio *on* after the timing

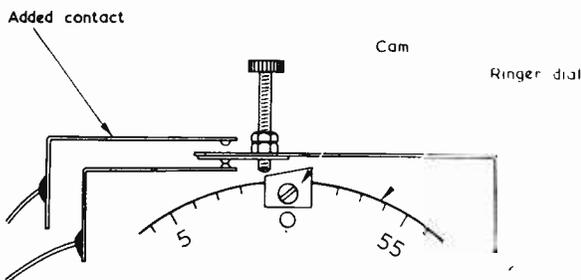


Fig. 10 Adding an extra contact to provide a 'switch-on' facility

period, rather than off, and he later added a second contact which achieved this requirement. Since most readers will only require the switching off facility the addition of the second contact will be dealt with only briefly.

The second contact is added in the manner shown in Fig. 10. Its method of operation is quite obvious: as the front disc of the 'Ringer' approaches the zero position the cam causes the moving contact to be raised, whereupon it connects to the added contact.

When the added contact is employed, it is necessary to alter the design of the left-hand contact mounting from that shown in Fig. 7. It needs to be made longer and have an extra saw-cut to take the upper contact.

Adding the extra contact necessitates the addition of the miniature slide switch referred to earlier and shown in Figs. 1 and 3. Also, the toggle switch requires to be a changeover type. The circuit employed is shown in Fig. 11 and it will be seen that the slide switch selects

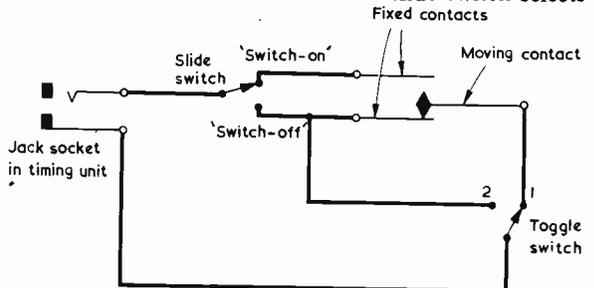


Fig. 11 The circuit employed with the extra contact

either the switch-off or switch-on facility. The toggle switch now overrides either of the contact operations. On Position 1 it enables both contacts to carry out their required operation. On Position 2 it both short-circuits the switch-off contacts and open-circuits the switch-on contacts.


EDITOR'S NOTE

It must be pointed out that the manufacturers of the 'Ringer' Timer, Smiths Industries Limited, state that, whilst they have no objection to the publication of details of the timing unit described here, it must be made clear that a Smiths timer so modified would not, normally, be covered by any guarantee given with their products.

New Products



DUAL-IN-LINE I.C. SOCKETS

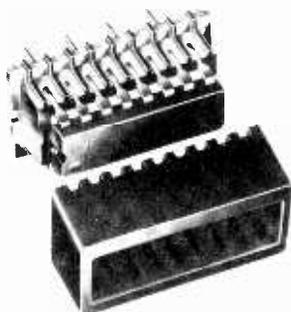

Just introduced by Jermyn's Manufacturing Division, is an entirely new d.i.l. i.c. socket that represents a revolutionary concept in such socket design. In this product (the A23-2055 series), the separate contacts normally employed in conventional socket construction have been eliminated. Instead, contact between the i.c. legs and the pins connecting the socket to a p.c.b. is effected by means of gold or tin-plated copper areas, which are deposited on the plastic body of the socket using a special new plating technique. The plated body is in the form of a saddle, over which the i.c. legs are slipped to make a complete surface rather than the conventional point contact. The i.c. is located in open-sided slots, and is held in position by a plastic retainer, which presses the i.c. legs inwards to make perfect contact with the plated areas.

Further information from: Jermyn Industries, Manufacturing Division, Vestry Estate, Sevenoaks, Kent.

PRINTED-CIRCUIT-BASED LOUDSPEAKERS

What is believed to be the world's first ever printed-circuit-based loudspeaker has been successfully developed by Fane Acoustics Ltd., following over three years of laboratory work. This development consolidates Britain's position as world leaders in loudspeaker design and manufacture, and gives Fane a major export potential. Fane's development engineers, have now perfected the first unit, the 'Fane 910', and this has now entered full-scale production at the company's Batley, Yorkshire factory. The 'Fane 910' is a robust, high power tweeter horn unit for a 25 watt input. Typical applications include guitar, discotheque, organ and public address systems where improved high frequency reproduction - up to 15 KHz - is required. A major benefit of the printed circuitry employed is the resulting uniformity of the speakers. Furthermore, simplified assembly procedures have made possible a list price of £12.40, which is comparable with conventionally wired units. A dowelled assembly in the 'Fane 910' permits the components to



Picture shows: TOP, a fully assembled "Fane 910" printed-circuit loudspeaker. A major advantage of the printed circuit is uniformity. BELOW, the unit is shown in component form. When required, component replacement can be undertaken quite simply by the user himself

be assembled only in the correct way. It can therefore be dismantled and re-assembled by the user, should a maintenance requirement ever result from damage, and the problems usually associated with sending goods away for repair are thus avoided. All Fane's dealers at home and abroad, will supply spares, and the amateur can replace any item in a minute or so. The export potential for such a loudspeaker in the booming world of 'pop' groups, discotheques etc. is enormous and Fane is currently planning a major assault on the Continent. The 'Fane 910s' exponential, die-cast aluminium horn section has a mouth opening measuring 6½in x 3½in (16.8cm x 9.1 cm) and the speaker employs a latest type high efficiency one-inch pole magnet with a 16,000 Gauss rating. Overall depth of the speaker - which is available initially in a black crackle finish - is 6½in (16.5cm). Fane Acoustics Ltd. - a member of the Audio Fidelity Group - is based at Hick Lane, Batley, Yorkshire.

STEREO DECODER


A new stereo decoder from Tolliday-George-Ellam Ltd. of 37 City Road, Cambridge, brings to thousands of VHF receiver and tuner owners the chance to receive stereo broadcasts.

The ISA stereo decoder is being marketed exclusively by TGE for the makers, their associated company, Industrial Sub-Assemblies Limited of Cottenham, Cambridge.

The launch coincides with the build-up of interest in the forthcoming Radio 2 stereo broadcasts to complement those already being transmitted on Radio 3.

Enthusiasts wanting stereo listening will be able to buy for their mono VHF equipment the bolt-on decoder, which incorporates a phase-locked loop stereo demodulator, for £16.50, to get the same results from existing equipment as from costly new stereo receivers or turners.

NOVEMBER 1972

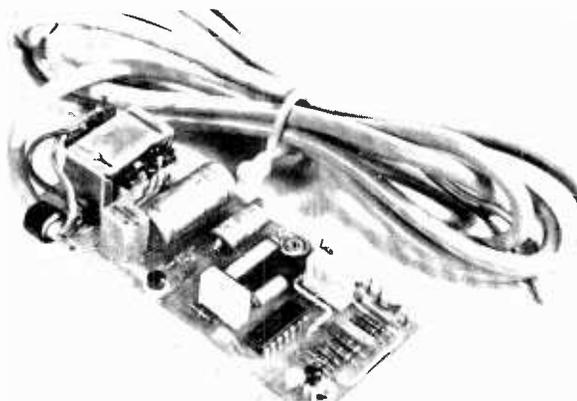




Cover Feature


- 1

THE 'S.A. JUNIOR' PORTABLE RECEIVER

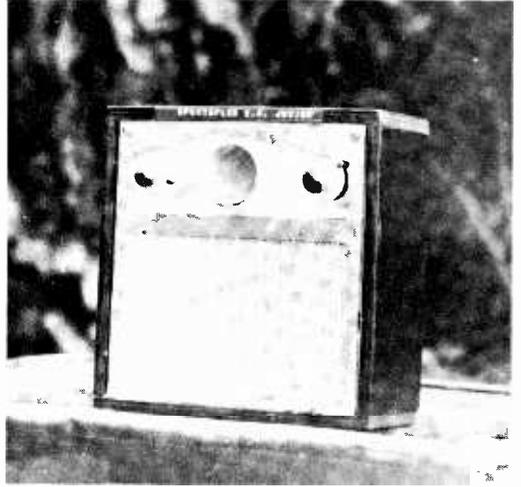

by

Sir Douglas Hall, K.C.M.G., M.A. (Oxon)

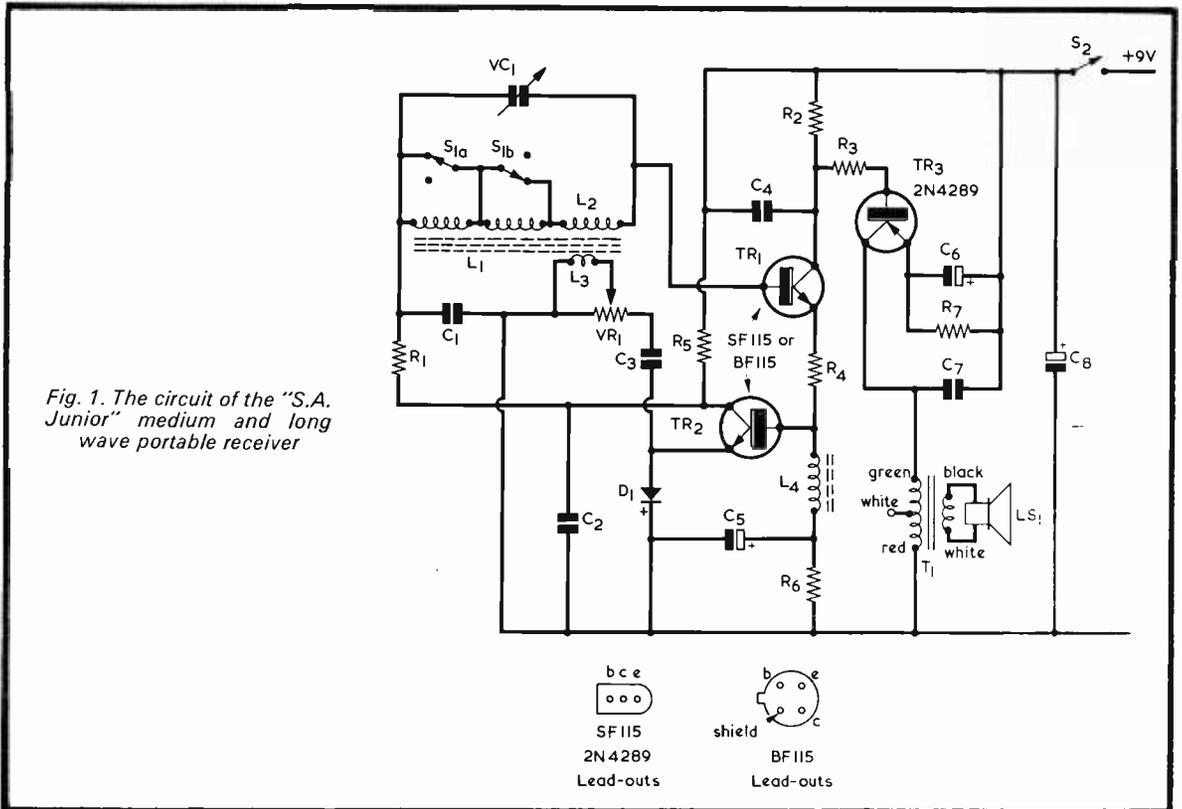

Using reflexing over two transistor stages, this receiver offers a high level of selectivity and sensitivity both on medium and on long waves.

THE AUTHOR HAS PUBLISHED THREE PORTABLE receiver designs using a 'Super Alpha' variant of his 'Spontaflex' circuit.*

He described the 'S.A.5' as the best medium and long wave design he has as yet published in this journal, and this opinion still holds good. The present design, whilst not possessing the output power nor the remarkable consistency of reaction setting which was given by the 'S.A.5', still offers the excellent sensitivity and selectivity inherent in the circuit. It is small (the case measures about 5½ in. square by 2½ in. deep) and employs only three transistors. It provides, on both medium and long waves, many alternative stations at good strength on a speaker after dark, and several during the hours of daylight in most places. Unlike the 'S.A.5', the long wave band is continuously tunable. Four programmes on each waveband are available at the author's home in South Devon.

Although the circuit used is basically similar to previous 'Super Alpha Spontaflex' circuits, certain modifications have been made which result in simplification and economy in the use of components and, in some cases, increased efficiency. The current taken from the PP6 battery is only about 7 to 8mA.

*The "Spontaflex" S.A.4 Transistor Portable', *The Radio Constructor*, May 1968; 'The "Spontaflex" Silicon S.A.3 Portable', *The Radio Constructor*, December 1969; 'The "Spontaflex" S.A.5 M. and L.W. Portable', *The Radio Constructor*, June 1971.

THE CIRCUIT

The circuit is given in Fig.1. In this diagram, wave-change switch S1(a) (b) is in the position which selects medium waves. It will be seen that TR1 and TR2 form the 'Super Alpha' pair at radio frequencies. The signal is picked up by L2, on a ferrite rod, this being tuned by VC1 which has a maximum capacitance of only 100pF. The whole of the tuned circuit is across the input to TR1. Because of the 'Super Alpha' arrangement, the input impedance of TR1 is extremely high and very little damping is offered to the tuned circuit. The signal at the output of TR1 appears across R4 and L4, the greater part being across L4, and is then applied to the input of TR2. This transistor acts as the second half of the 'Super Alpha' pair, and the amplified radio frequency signal is passed to the diode D1, which acts both as a load and as a demodulator.

The resulting audio frequency at D1 is returned to TR2, which now functions as a common base amplifier. In order to ensure that the radio frequency output from TR2 is not at an impedance that is too low for the desired operation of the diode, it is necessary for the tuned circuit to have extremely high impedance. This is achieved by employing an unusually large inductance-to-capacitance ratio and by the use of reaction, which will be found to be exceptionally beneficial with this circuit. As can be seen from Fig.1, reaction is obtained by coupling back from the emitter of TR1, and it is

COMPONENTS

Resistors

(All fixed values ½ watt 10%)

R1	10kΩ
R2	2.7kΩ
R3	1kΩ
R4	220Ω
R5	100kΩ
R6	1kΩ
R7	180Ω (see text)
VR1	5kΩ potentiometer, linear, with S2.

Capacitors

C1	1,000pF silvered mica
C2	1,000pF silvered mica
C3	0.01μF paper or plastic foil
C4	0.01μF paper or plastic foil
C5	100μF electrolytic, 2.5 V.Wkg.
C6	640μF electrolytic, 2.5 V.Wkg.
C7	0.1μF paper or plastic foil
C8	1,000μF electrolytic, 10 V.Wkg.
VC1	100pF variable, 'Dilecon' (Jackson Bros.)

Inductors

L1,2,3	Ferrite aerial assembly (see text)
L4	2.5mH r.f. choke type CH1 (Repanco)
T1	Output transformer type LT700 (Eagle)

Semiconductors

TR1	SF115 or BF115
TR2	SF115 or BF115
TR3	2N4289
D1	OA5

Switches

S1	2-pole 2-way rotary (see text)
S2	s.p.s.t. (with VR1)

Speaker


LS1	3Ω speaker, 5in. by 3in. (see text for magnet size)
-----	---

Battery

9 volt battery type PP6 (Ever Ready)

Miscellaneous

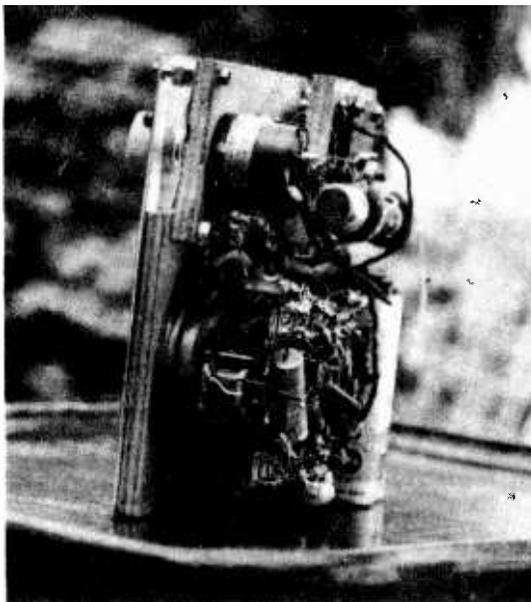Ferrite rod, 4½ in. by ½ in. dia
 18-way R.S. Components Standard tagboard (Home Radio Cat. No. BTS10)
 Epicyclic drive with flange type 4511/F (Jackson Bros.)
 1 large knob
 2 small knobs
 Battery connectors
 Speaker gauze
 Plywood, Perspex, Fablon or Contact, etc.



A side view of the receiver "chassis"

consequently effective over both radio frequency stages.

If the tuning arrangements are compared with the variable inductance tuner used in the 'S.A.5' receiver, it will be found that the present receiver offers an even better inductance-to-capacitance ratio over the lower wavelength half of the medium wave band, whilst there is a somewhat inferior ratio from about 350 metres upwards. Indeed, at around 200 to 250 metres the ratio is so high that the increased amplitude of all signals, wanted or not, could in certain circumstances (e.g. if the tuner section were used with a powerful amplifier without a volume control) overcome the superior selectivity which is obtained as a result of the high inductance of the coil. At this part of the scale the present tuner is more sensitive than the 'S.A.5' but a little less selective.

When S1(a)(b) is switched to long waves, L1 comes into circuit. L1 had to be carefully designed. There is not very much room for it on the ferrite rod and it was found that a single pile-wound coil proved to have sufficient self-capacitance to allow medium wave breakthrough of strong stations and to restrict the coverage given on the long wave band with only 100pF as a variable tuning capacitance. On the other hand, a low capacitance high inductance coil, while satisfactory on the long wave band, caused trouble on the medium wave band due to damping of the medium wave coil when the long wave coil was short-circuited by the wavechange switch. Finally, a two-pie coil, with each pie individually short-circuited when listening to medium waves, proved satisfactory.

We left the demodulated signal passing through TR2. It emerges, in much amplified form, across R5, whence it is fed to the base of TR1 via the ferrite rod tuned windings. R1, C2 and C1 filter out the radio frequency component. From here the circuit differs from all the previous 'S.A.' designs, in which the first transistor acted as a common collector current amplifier at audio frequencies. In this case the amplified signal is taken from the collector of TR1, with R2 as collector a.f. load, and TR1 acts as a common emitter amplifier. Resistor R4, which is not bypassed, introduces a large amount of negative feedback. This is essential in order that the input impedance of TR1 be kept high at audio fre-

quencies and consequently not damp the signal across R5, an occurrence which would drastically reduce the amplification given by TR2. But because the load resistance in the collector circuit of TR1 is higher in value than that in its emitter circuit, TR1 is able to give some voltage amplification while still maintaining its input impedance at a sufficiently high level. Extra gain is therefore given by this stage, as compared with that given in the earlier circuits. Remembering that the input impedance of TR3 (say 2k Ω) in series with R3, is in parallel with R2, it will be seen that the effective collector load is roughly 7 times the value of R4. A voltage gain of about 17dB may be expected.

TR3 functions as a normal high amplification common emitter output stage. C4 and C7 provide further radio frequency filtering.

It will be seen that TR1 obtains base bias from the collector circuit of TR2 which, in turn, obtains its base bias from the emitter circuit of TR1. This arrangement involves heavy negative feedback of direct current and results in good stability.

A warning is given not to use a separate battery switch rather than one combined with VR1. If the receiver is switched on with reaction adjusted to a critical setting, or to a setting providing oscillation, it is possible for the circuit to be shock-excited into parasitic oscillation. No harm is done, but no signals will be heard until the reaction control is backed right down and brought up again. The possibility of this nuisance is ruled out if S2 is combined with VR1, as specified.


It is important to use the specified semiconductors. There may be others that would work as well, but the chances are that several modifications would be involved for best results. Those specified are readily obtainable. If a BF115 is used for TR1 or TR2, no connection is made to its shield lead-out.

Before proceeding to details of construction, reference should be made to the switch employed for S1(a)(b). This should have a construction which ensures that it projects backwards from the panel on which it is mounted by a small amount only. The type may be recognised from the outline given in Figs. 2(b) and 4, and it is available from Henry's Radio as 'Type B'. Another point is that the magnet of the speaker should, preferably, not have a diameter greater than 1 $\frac{1}{2}$ in.


CONSTRUCTION

The first constructional step is to take a piece of $\frac{1}{2}$ in. plywood and cut out three sections, one measuring 5in. by 3 $\frac{1}{2}$ in., one 5in. by 2in. and one 3 $\frac{1}{2}$ in. by 2in. A hole for the speaker is cut in the 5in. by 3 $\frac{1}{2}$ in. piece such that the speaker will lie close to one 5in. edge, leaving a $\frac{1}{2}$ in. strip of wood free at the other 5in. edge.

Place the 3 $\frac{1}{2}$ in. by 2in. piece over the 5in. by 2in. piece so that the long edges and the 2in. edges at one end are together. Clamp the pieces together when so positioned. Mark out the exact centre of the larger piece and drill a $\frac{1}{8}$ in. hole through both pieces at this point. Drill two further $\frac{1}{8}$ in. holes to take VR1 and S1 in the positions shown in Fig. 2(b). One of these holes will pass through the 5in. by 2in. piece only, and this is the hole that will later take VR1. Also drill two 4BA clear holes through both pieces, as indicated in Fig. 2(b). Unclamp the two pieces of plywood and put the 3 $\frac{1}{2}$ in. by 2in. piece to one side. Enlarge the centre hole in the 5in. by 2in. piece to $\frac{3}{4}$ in. diameter and fit a flange type epicyclic drive to it, as illustrated in Fig. 2(b). Also fit VR1 and S1. Bolt or screw this panel to the free $\frac{1}{2}$ in. strip on

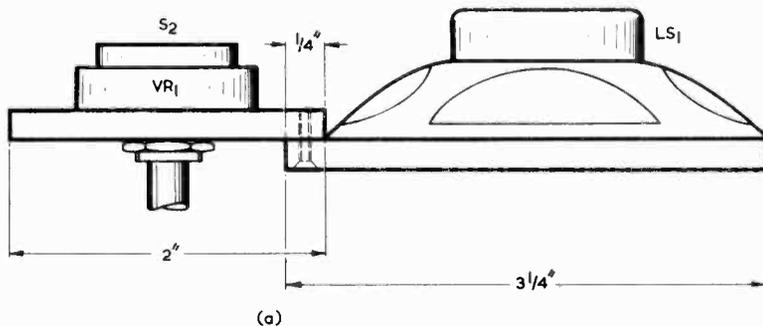

(a)

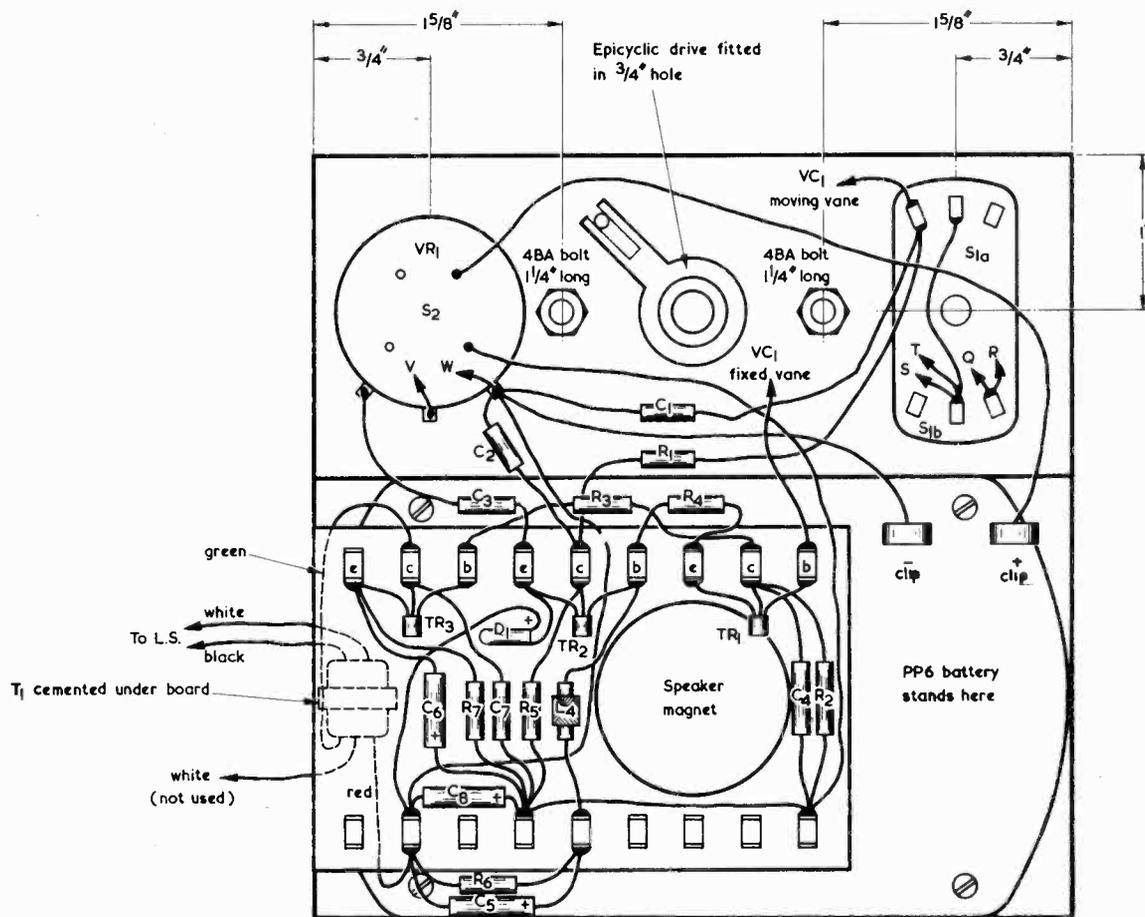

(b)

Fig. 2 (a). The two panels which form the "chassis" of the receiver
 (b). Major wiring details. The tagboard fits over the speaker magnet. Tag positioning in S2 may vary from that shown here, and the required tags for connection should be identified with a continuity tester

the loudspeaker panel, as shown in Fig. 2(a).

Cut a section with 9 pairs of tags on it from a 16-way Standard size R.S. Components tagboard. Cut a hole in this 9-way tagboard to take the magnet of the speaker. See Fig. 2(b). As mentioned earlier, the speaker employed should have a magnet with a diameter not

greater than 1 1/4 in., or else a special tagboard will have to be made up by the constructor using a piece of Paxolin and 6BA bolts, nuts and solder tags, and providing room for the larger hole required.

The hole in the tagboard should be made very slightly larger than the diameter of the speaker magnet. A turn

or two of Sellotape around the magnet will then ensure a tight fit later on. A piece of Fablon or Contact should be stuck to the underside of the tagboard to prevent the possibility of short-circuits to the speaker frame. Note also that transformer T1 is affixed, under the board, with a suitable adhesive.

Secure T1 in place and connect its white and black secondary leads to the speaker. Then fit the board over the speaker magnet, fit small components and complete the wiring shown in Fig. 2(b). Note the two lengths of wire from TR1 and S1 which will subsequently be connected to VC1. Fit two 1½ in. countersunk 4BA bolts to the 5 in by 2 in. panel, as indicated. The bolt heads are away from the reader.

L2 and L3 should now be wound on a tube which is free to slide on the ferrite rod. It is useful to employ a piece of Fablon or Contact about 2½ in. square here, leaving on all the protecting paper except for a strip about ½ in. wide. The piece of Fablon or Contact is wrapped round the rod, not too tightly, and made into a secure tube by means of the unprotected strip at one end. L2 consists of 130 turns of 32 s.w.g. enamelled wire close-wound, and L3, spaced ¼ in. from L2, has 10 turns of the same wire close-wound in the same direction. The completed coil is then placed on the rod, which is fitted with rubber grommets as shown in Fig. 3. VC1 has its spindle cut down to ¼ in. and is then fitted to the appropriate hole in the 3½ in. by 2 in. piece of plywood. The ferrite rod is also fixed to this piece of plywood by means of cord (*not* wire) passed through four suitably placed small holes. It will probably be necessary to place a ¼ in. thick strip of plywood or similar non-conducting material under the grommets to prevent the coils fouling the moving vane of VC1.

VR1/S2 will appear here when assembled

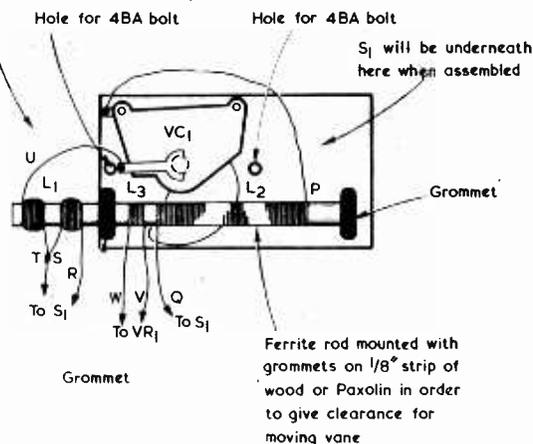


Fig. 3. The ferrite rod assembly and the sub-panel on which this and VC1 are mounted. Winding details are given in the text.

L1 should now be made and fitted to the rod, also as shown in Fig. 3. It consists of two pieces of 200 turns each of 38 s.w.g. enamelled wire. Each piece is pile-wound to a width of about ¼ in., the two pieces being separated from each other by ¼ in. They are wound on a 1½ in. long tube of Fablon or Contact made up as described for L2 and L3. The two centre leads are soldered together to make a continuous coil. L1 is wound in the same sense as L2 and L3.

Fit the two assemblies together by means of spacing nuts on the 4BA bolts under the VC1 panel. Tighten the grub screws of the drive to the spindle of VC1 and connect the two relevant leads to the tags of VC1. Connect up coil leads as indicated in Fig. 3. Provided the two sections are correctly assembled together, S1 will be out of sight, but VR1/S2 will be visible. There will be an unused ¼ in. hole in the VC1 panel over S1; this is not shown in Fig. 3.

It will be found that the two 4BA bolts do not protrude through the small 3½ in. by 2 in. panel, and that it is impossible to fit nuts. In all probability the combined assembly will be found perfectly firm when the epicyclic drive grub screws have been tightened, but if this should not prove to be the case, VC1 should be temporarily removed and the holes in the small panel countersunk so that locking nuts can be fitted to the 4BA bolts. Bolts longer than 1½ in. are not used as they could foul VC1.

CHECKING PERFORMANCE

At this stage a PP6 battery may be fitted in the position indicated in Fig. 2(b) and the receiver tried out. It may prove helpful to contrive a temporary clip to hold the battery in position, though this is not essential. It should be found on medium waves that oscillation starts with the slider of VR1 advanced about one third of the way along its track when VC1 is at minimum capacitance, gradual further advancement in VR1 being required as the capacitance of VC1 is increased. The position for oscillation in VR1 will be fairly constant throughout the long wave band, where it should need to be advanced about half-way along its track. Reaction will be found to be beautifully smooth. There is no suspicion of backlash and a weak signal can be held with great sensitivity when the receiver is on the verge of oscillation. This condition does not produce the best quality, but on more powerful stations reaction will be turned back to some extent and quality will be found to be quite good for a small receiver. The reaction control acts as a true volume control since it damps the tuned circuit when it is at a low setting.

If the current drawn from the battery is less than 7mA the value of R7 may be reduced until this current is taken.

Medium wave coverage should be from about 190 to 540 metres, but it may be necessary to vary the number of turns from the 130 specified to suit some ferrite rods. The prototype uses a rod obtained from Amatronix Ltd., 396 Selsdon Road, South Croydon, Surrey, CR2 0DE. On the long wave band, coverage will be from about 1,000 to 1,900 metres.

Paxolin or aluminium panel with cut-outs for scale, controls and speaker aperture


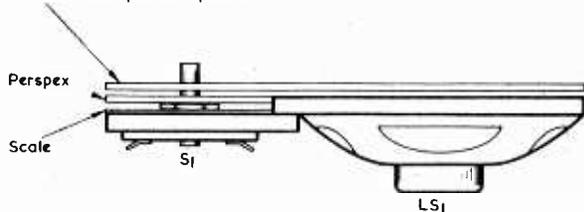


Fig. 4. Adding a tuning scale, Perspex panel and final "tidying-up" panel. For simplicity the tag-board fitted over the speaker magnet is omitted here.

A scale may be made using a piece of card measuring 5in. by 1½in. This is fitted as shown in Fig. 4, where the 'chassis' will be seen to be lying on its back. A wire pointer is fitted to the flange of the epicyclic drive, and the scale calibrated – an easy task if carried out after dark owing to the large number of stations which will be received. Next a piece of ¼in. thick Perspex is cut to measure 5in. by 1½in., after which three ⅜in. holes are cut out in it for the spindles. This is placed over the spindles, the locking nuts of which will space the Perspex away sufficiently far to leave room for the scale pointer. Finally, a 'tidying-up' frame is cut from Paxolin or aluminium to cover the whole of the 'chassis' front. The exact design of this frame is left to the constructor but Fig. 5(b) shows a suggestion. This frame is screwed to the front of the 'chassis' with a piece of speaker gauze held over the speaker aperture.

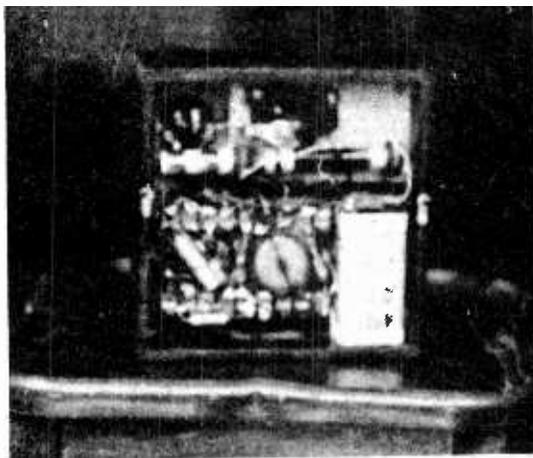

Rear view of the receiver with the back removed

CABINET

A suggestion for a simple case is illustrated in Fig. 5(a). Two pieces of ¼in. plywood are cut measuring 5in. by 2½in., and two pieces 5½in. by 2½in. These pieces are screwed together as shown. Before cutting out the pieces it is advisable to measure the actual 'chassis', in case this has not been made quite accurately in terms of dimensions. The dimensions of the pieces of plywood in Fig. 5(a) may then be modified accordingly. With the prototype it was found an easy matter to make the case a sufficiently tight fit for the chassis to be held securely in it without the need to use screws. One approach to this end consists of making the pieces for the case slightly oversize and then trimming them down with a file.


A back, 5in. square, is cut from ¼in. peg-board or similar material with holes in it. This is pushed into the back of the case and is held by small solder tags which are screwed to the backs of the case sides and are free to swivel.

When completed, the case may be varnished in any colour favoured by the constructor.


A LARGER VERSION

If size is not a problem, better quality and greater output can be obtained by using a larger speaker. As a matter of interest, the author has rebuilt the prototype of the 'S.A.3' receiver mentioned at the beginning of this article to the circuit described here. The 'S.A.3' receiver is in a larger cabinet and has an 8in. by 5in. elliptical speaker. The original speaker, ferrite rod assembly, output transformer, reaction control, wave-change switch, battery and groupboard were retained, these all being wired up to the new circuit. The groupboard was rewired with the new components needed.

The instability problem when first switching on with a switch not combined with the reaction control did not appear, this being due, no doubt, to the less crowded layout of the larger receiver. R7 may be reduced in value to obtain a greater undistorted output, the extra current passed by TR3 being well within the capacity of the PP9 battery used with the 'S.A.3'. Various values for R7 between 180Ω and 47Ω can be tried in this larger version of the circuit, a meter being inserted in one of the battery leads to monitor the current drawn for the different values. A good compromise is a value in R7 which causes a total current of about 14 to 15mA to be drawn. The final value of R7 which will produce this figure depends upon the characteristics of some of the components used.

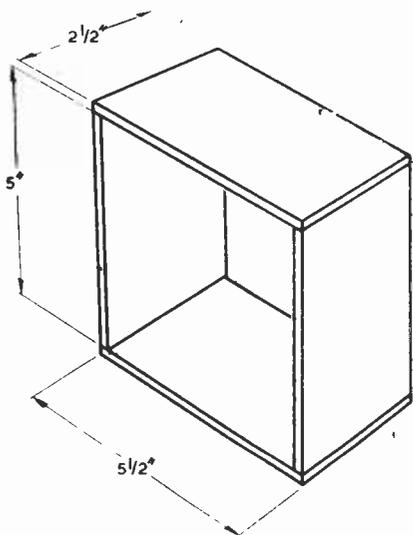

(a)

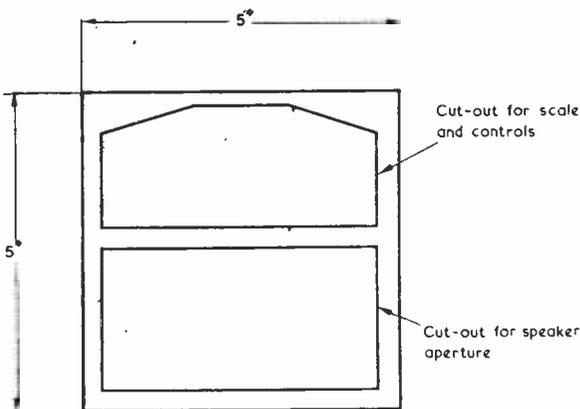


(b)

Fig. 5 (a). The cabinet may have the simple construction illustrated here
(b). Suggested design for the front covering panel

NEWS . . . AND .

D.J. DISCMAJOR DISCOTHEQUE PRE-AMP

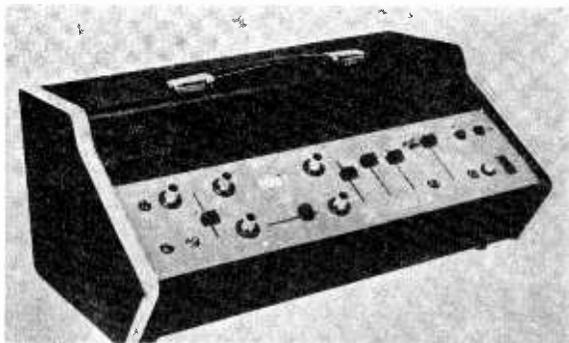

The D.J. Discmajor Discotheque Pre-Amp will be of prime interest to the professional D.J., Clubs and organisations who demand first class sound quality. Slider controls are used for all of the main functions which facilitate ease of operation for the user. Added to this is a mic input with its own volume and tone controls, mic over-ride with a variable level control, tape input with its own volume control and a visual cue meter which in conjunction with the P.F.L. gives complete visual and audible control over all input channels. A single slider 'cross-fade' controls the two magnetic inputs, for total flexibility.

The Discmajor is also available complete with a 100 watt Power Amplifier. The complete power section will cut out instantly if the unit is misused or shorted and will only come on again when the fault has been cleared and the fault warning lamp on the front panel re-set.

VINTAGE RADIO MUSEUM

Crystal-sets with cats-whiskers, antique receivers with bright-emitter valves and plug-in coils, horn speakers half of wood and half of metal. All are on show – many are working – at the new Vintage Wireless Museum in Lincolnshire. Admission is free, and at any convenient time.

The Museum is supervised by the Wireless Preservation Society, a non-profit-making organisation, the objects of which are the preservation and restoration of vintage wireless and electronic equipment for purely cultural, educational and historical purposes.

President is Mr. W. K. E. Geddes, who is in charge of the Radio Section at the Science Museum in South Kensington. Vice-President is Mr. F. Ward, G2CVV, the Immediate Past-President of the Radio Society of Great Britain. The Chairman is Mr. D. Hoults, G400 and the Vice-Chairman Mr. N. Carter, G2NJ.

Hon. Secretary and Curator is Mr. D. Byrne, G3KPO, of Homa House, Quadring, near Spalding, who should be contacted at STD. 077-584-485 by readers wishing to look around the Museum.

It is interesting to note that it is probably the only museum in the world where visitors can actually handle the exhibits, but this makes it of particular value to research workers.

MIRACLE OF BROADCASTING

British religious dignitaries were among those initially suspicious of the apparently miraculous wireless devices in the 1920s.

In 1923, the then Dean of Westminster refused to allow the wedding service of the Duke of York to be broadcast from Westminster Abbey. It might be received, he said, by 'a considerable number of persons in an irreverent manner, and might even be heard by persons in public houses with their hats on.'

NEW SERVICE FOR THE HANDICAPPED

A National library has been established to help the many disabled people who are unable to read books in the normal manner. It is a library of 'Talking Books', and it will provide a wide variety of titles, all on purpose-made Tape-Cartridge, which contains up to thirteen hours of reading.

The National Library of Talking Books for the Handicapped is a registered charity and the Chairman of the Council, Major Frank Clarke, in announcing its foundation, said, 'The people we aim to serve fall into the category of severely disabled persons, many of whom are elderly.' The Chairman added, 'It is hoped that Local Authorities and organisations for the handicapped will co-operate with us so that "Talking Books" and Play-back Machines may be made freely available to those in need.'



RADIO & ELECTRONICS CONSTRUCTOR

COMMENT

EMI MARINE INTRODUCES HIGH-PERFORMING, SOLID-STATE 12 CHANNEL RADIO-TELEPHONE



A self-contained, solid-state, 12 channel VHF/FM radio-telephone introduced by EMI Marine of Sevenoaks, Kent, combines high performance and straightforward operation in a package especially designed to withstand marine use.

Costing £310, the 'Mariner' uses the latest, fully-proven solid-state circuit techniques, and corrosion resistant materials, to ensure reliability and interference-free communication. It incorporates advanced design features to provide protection against accidental misuse, to enhance performance, and simplify maintenance and servicing.

The transistorised power amplifier has a unique safeguard so that even if inadvertently loaded with an open- or short-circuited aerial connection no damage will result to the amplifier. The circuitry of the 'Mariner' uses

silicon integrated circuits, FET components, diodes and transistors. This gives excellent high-temperature performance and low power consumption.

The circuits provide full performance over the ambient temperature range -30°C. to $+60^{\circ}\text{C.}$ They have a rated capacity of double their working load, providing a wide safety margin.

The extremely low current drain (less than 0.15 amps.) allows continuous receiver operation in the standby mode, with only a single 12V to 14V wet-cell battery as the power source. The transmitter provides 1W or 25W RF output. In the transmit mode, on 25W output, d.c. current consumption is 3.5 amps.

The equipment conforms to the latest Post Office specification, incorporating 25 kHz channel spacing.

GOLDEN JUBILEE FOR RADIO APPRENTICE TRAINING

The BBC is not the only organisation celebrating a Golden Jubilee connected with radio.

Half a century of training RAF apprentices in the radio trades was marked by celebrations on Friday, October 13, at the No. 1 Radio School, RAF Locking, near Weston-super-Mare, Somerset.

It was in 1922 that the training of apprentices was first started at the Electrical and Wireless School, Flowerdown, near Winchester, Hampshire. From then on right up to the present day the training of radio and electronic apprentices has been of prime importance to the RAF.

The development of radar during World War II

greatly increased the scope of radio trades. After the war, radio mechanics concentrated on servicing and ceased to be trained in operating skills. In 1948 the first of the apprentices to be trained specifically as ground or air radio mechanics graduated from Cranwell, to where the school had moved in 1929.

Since the apprentice training started in 1922, more than 9,750 radio apprentices have been trained. Over 2,000, more than one-fifth, have been commissioned and 13 have reached Air Rank.

As part of the Golden Jubilee celebrations, an Old Boys' Day was held at No. 1 Radio School, RAF Locking on Friday, October 13.

IN BRIEF

● A leaflet available from Coutant Electronics Ltd., of 3 Trafford Road, Reading, Berkshire, gives details of a range of high quality potted e.h.t. converters. The leaflet provides full mechanical and electrical details.

● To broadcast abroad today the BBC uses a total of 70 transmitters - 44 of them at sites in the United Kingdom and 26 of them at strategically placed relay bases overseas.

● A new version of its well-proven infra-red detector, the AFA Infrascan, has been introduced by AFA-Minerva (EMI) Ltd., Twickenham, Middlesex, an EMI company, for operation on 24 volt battery power supplies. The latest version of this scanning detector ensures continuous fire surveillance of installations even during periods of mains power failure - the detector automatically switching to battery supply in emergency situations.

● Any member of World Radio Club who reports accurately on reception of NOVEMBER 1972

the Anniversary Edition on November 9th, 10th or 12th, will receive a special QSL card. Membership is free, and the address is: World Radio Club, BBC, Bush House, London.

● SGS (United Kingdom) Limited, the first UK semiconductor manufacturer to gain a British Post Office D3000 Grade 1 Approval, is now under contract to supply DTL Integrated Circuits under this Approval to STC Limited for use in TXE4 Electronic Telephone Exchanges.


● The third edition of a handbook 'Noise measurement techniques', written by W. V. Richings Technical Director of Dawe Instruments Limited, specialists in the manufacture of sound level measuring equipment and internationally known makers of electronic and ultrasonic equipment, is available free on request from Dawe Instruments Limited, Concord Road, Western Avenue, London, W3 0SD.



Stick 'em up or I'll drill yer!

PHOTOGRAPHER'S METRONOME

by G. A. FRENCH

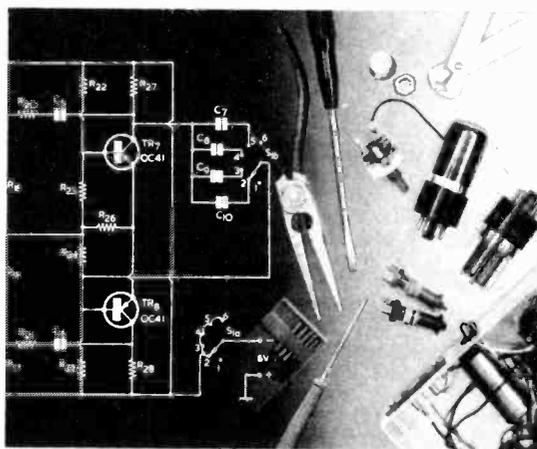


THIS MONTH'S 'SUGGESTED CIRCUIT' IS the outcome of a suggestion made by a friend who is a professional photographer. Certain processes in the printing of photographs need to be timed accurately, the timing periods often varying from one photograph to the next. A common approach consists of counting seconds orally. Since it is difficult to assess the length of a second precisely, each number is preceded by a word which will bring the total uttered length up to approxi-

mately one second, whereupon a spoken succession such as 'Kodak one, Kodak two, Kodak three', and so on, is employed.

As was explained to the author, the printing processes could be carried out much more easily and reliably if some form of metronome could be devised which would produce 'clicks' or pulses of sound at intervals of exactly one second. Seconds could then be counted off accurately by counting in time with the metronome.

The production of an electronic metronome is not, of course, a particularly difficult requirement to meet, and a simple solution to the problem is given in the accompanying circuit diagram. This gives short bursts of an audio tone around 700Hz, the burst starts being spaced at one second intervals. The writer felt that a unit giving tone bursts was preferable to a device which merely produced 'clicks', as the latter would not be so readily audible.

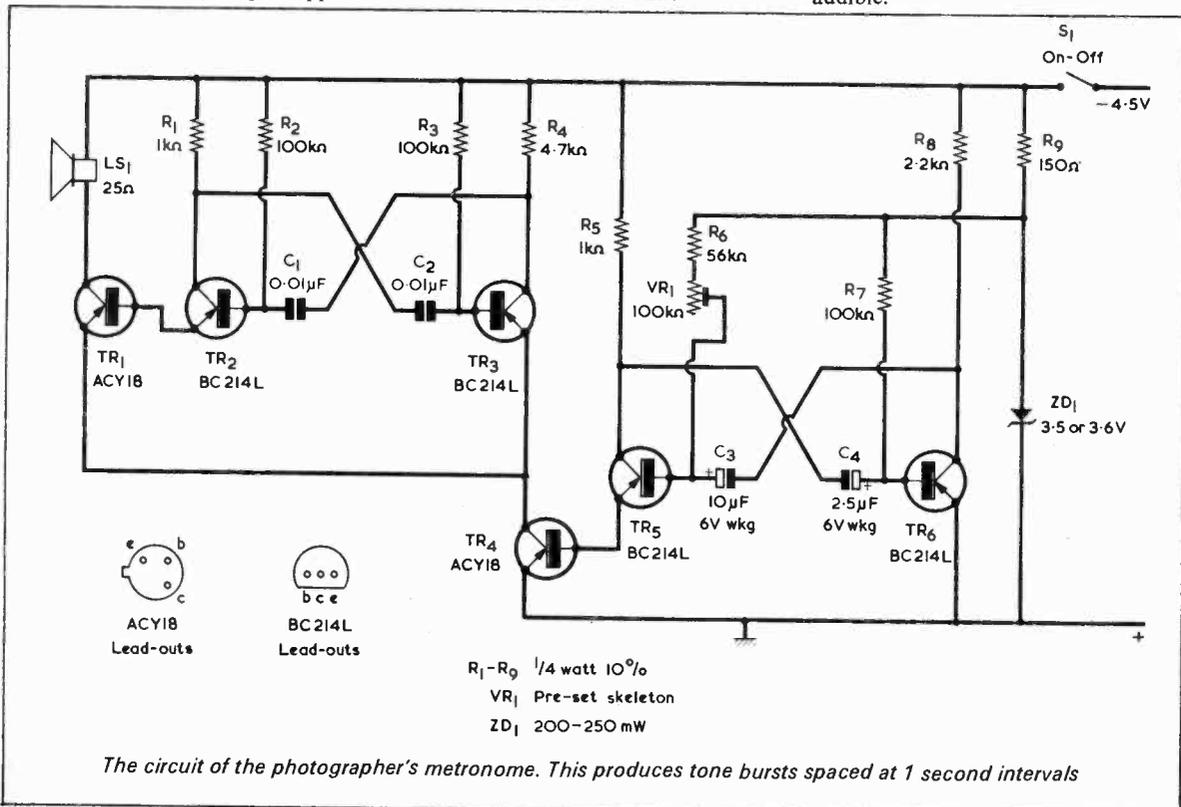

CIRCUIT OPERATION

The circuit consists of two multivibrators. The multivibrator around TR2 and TR3 produces the 700Hz tone, and it is switched on and off by the multivibrator around TR5 and TR6 which operates at a speed of one cycle per second.

Dealing first with the 700Hz multivibrator, we may examine its functioning when transistor TR4 is turned hard on, thereby allowing the positive supply to be applied to the lower supply line of the multivibrator. TR2 and TR3 form a 50:50 multivibrator, the running frequency of which is governed by the values of R2, R3, C1 and C2. The emitter of TR2 is returned to the lower supply line via the base-emitter junction of TR1, with the result that when, during the multivibrator cycle, TR2 is conducting TR1 is turned hard on. The collector of TR1 couples to the negative supply rail via the 25Ω loudspeaker LS1, and this consequently reproduces the multivibrator frequency. The audio output level is more than adequate for normal dark-room requirements.

R1, in TR2 collector circuit, is given the relatively low value of 1kΩ, and it ensures that sufficient current flows in TR1 base to bring it hard on when TR2 is conducting. There is no necessity for the collector load of TR3 to have a value as low as this, and a small saving in average battery current is achieved by giving R4 a value of 4.7kΩ.

The second multivibrator turns TR4 on and off (thereby turning the first multivibrator on and off) in the same manner that the first multivibrator controls TR1. This second multivibrator is, however, asymmetric and capacitor C3, coupling to the base of TR5, has a larger value than capacitor C4, which couples to the base of TR6. Also, the final setting in VR1 will probably cause the total resistance inserted by this component and R6 to be greater than that of R7. Thus, TR5 is turned off during the multivibrator cycle for a period that is at least 4 times that during which TR6 is turned off. In practice, it is turned off for about 7 times as long, and the result is a series of tone bursts from the speaker which have a comfortably audible length in relation to the silent periods between them.

As with the collector load of TR1, TR5 collector load, R5, is given a value of 1kΩ to ensure that TR4 is turned hard on when TR5 conducts. Again in the interests of economy in battery current, R8 is given a value which is higher than that of R5. The value of R8 is not critical, but it was found empirically that the value specified, 2.2kΩ, offered the best performance.

It is necessary for the frequency of operation of the TR5, TR6 multivibrator to be as accurate as possible. This frequency is controlled by R6, VR1, R7, C3 and C4, and a measure of

stabilization is obtained by returning R6 and R7 to the regulated voltage across zener diode ZD1. Even with this zener diode in circuit, however, it is desirable to discard the battery when its potential falls below some 4 volts. The length of the multivibrator cycle is set by means of the pre-set potentiometer VR1.

COMPONENTS

None of the components are critical or difficult to obtain. Loudspeaker LS1 can be a small inexpensive component with a nominal impedance of 25Ω and having a cone diameter of some 3 to 4 in. Transistors TR1 and TR4 are shown as ACY18, but any other transistors in the ACY17 to ACY22 'family' could be employed instead, as also could the ACY39, ACY40, ACY41 or ACY44. These all have the same lead-out disposition as the ACY18.


Capacitors C3 and C4 are shown as electrolytic, and these should be adequate for normal requirements. It is desirable to employ new capacitors here, rather than components which have seen a lot of service in other circuits. If a high degree of long-term accuracy is desired, plastic foil capacitors may be used instead of electrolytic components, in which case the value of C4 may be changed to 2.2μF. High value polycarbonate capacitors in 2.2μF and 10μF are available from V. Attwood, P.O. Box 8, Alresford, Hants. There is no necessity for C3 and C4 to be close-tolerance types as variances from nominal capacitance are taken up in the adjustment of VR1.

After the circuit has been assembled and constructed it is necessary for VR1 to be set up such that the tone bursts from the speaker appear at intervals of exactly one second. This process can be carried out with the aid of a watch having a sweep second hand. The unit is switched on and the number of tone bursts counted whilst observing the second hand of the watch. VR1 is then adjusted experimentally until 15 bursts are reproduced in quarter of a minute. An electrolytic capacitor in the C3 position which is at the extreme of its tolerance range could conceivably result in the required frequency being outside the range of adjustment offered by VR1. Should this occur, the value of R6 should be adjusted accordingly. The length of the multivibrator cycle increases as the sum of the resistance inserted by R6 and VR1 increases, and vice versa. If electrolytic capacitors which have been in store for a considerable period are used for C3 and C4, the unit should be run for several minutes or so to allow them to settle down to their final capacitance before setting up VR1.

The current drawn from the 4.5 volt battery by the prototype unit was 11mA between tone bursts and 80mA when tone bursts were generated. This corresponds to an average battery current of approximately 20mA. ■

BUY THIS BEST SELLER

T.V. FAULT FINDING 405/625 LINES

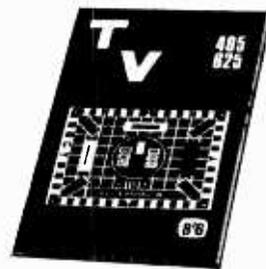

REVISED & ENLARGED

Edited by J. R. Davies

124 pages Only 50p

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price 50p from your
Bookseller

or post this Coupon together
with remittance for 56p
(to include postage) to

DATA PUBLICATIONS LTD.
57 Malda Vale, London, W.9

Please send me the 4th revised edition of TV Fault Finding, Data Book No. 5

I enclose cheque/crossed postal order for.....

NAME

ADDRESS

.....

.....

R.C. Block Letters Please

'50 years on the air'

The BBC celebrates 50 years "on the air" this month. We give some of the background to the origins from which public broadcasting began.

FIFTY YEARS AGO BRITISH BROADCASTING WAS BORN in an ex-army hut near Chelmsford in Essex, when on 14th February 1922 a group of Marconi engineers began a series of regular experimental transmissions. Every Tuesday evening from a rigged-up transmitter, call sign 2MT Writtle, or more affectionately to its listeners, Two Emma Tock, transmitted programmes whose original purpose was entirely technical. Shortly afterwards, in May, another transmitter, later to be even better known, was opened up at Marconi House in the Strand in London. This was the famous 2LO station that provided the foundation from which the British Broadcasting Company grew after its formation on 14th November of the same year.

Two Emma Tock provided the first regular broadcast service in this country, and incidentally broadcasting's first audience, an audience which in its enthusiasm for the pioneering programmes, generated the original demand for public service broadcasting. The 2MT transmitter was set up for use in a series of experiments designed to establish the effective range of a wireless telephony transmitter. At the same time a number of radio amateurs were appearing, largely young ex-service men who had learnt about radio during the 1914-18 war, who had put together their own receiving sets, and who wanted transmissions to receive. Earlier experiments with entertainment, as when Dame Nellie Melba and later Lauritz Melchior, the Danish tenor, had broadcast from a makeshift studio in Chelmsford in 1920, had shown that there was a potential for wireless telephony outside official communication and navigation usage, but the official attitude had been discouraging, and the duty of granting licences for transmitters was the preserve of the Postmaster General. Government was unwilling to consider licences for more than a token number of even technical transmissions.

2MT was finally granted an experimental licence to transmit early in 1922, though the permission was hedged about with many restrictions. But for half an hour on Tuesday evenings, experiments were to be allowed, though even then with three-minute breaks in every ten, to ensure that no interference with "legitimate services" was being perpetrated.

2MT opened regular broadcasts officially on behalf of the amateurs who needed a source against which they could calibrate their receivers, and to begin with its programmes were not very much more interesting than early 1920 transmissions made before the government clamp-down, when W. T. Ditcham read from Bradshaw's railway timetable, but the enthusiasm and gaiety of the young Marconi engineers who ran it very soon turned it into a half-hour's entertainment in its own right. The names of those men read like a roll-call of some of the great names in Broadcasting. In charge of the project was Captain P. P. Eckersley, who later went to the new British Broadcasting Company as its first Chief Engineer. It was his infectious and spontaneous humour

which gave 2MT its unique flavour; he was not only the first engineer in charge, he was also the first of the true radio entertainers, with a gift for ad-libbing that constantly alarmed those of a less adventurous disposition who worked with and around him. Others in the team were Noel Ashbridge, later Sir Noel, who was the BBC's first technical director, till his retirement in 1952, R. T. B. Wynn, a later Chief Engineer of the BBC and B. N. MacLarty, who became Head of the BBC's Design and Installation team before he returned to Marconi's in 1947 as Engineer in Chief.

By contrast, Marconi's 2LO station, granted its licence in May, began a rather staid existence, a happy coincidence for the pioneers of 2MT, as it gave them an opportunity to provide skits and lampoons which were much appreciated by their listeners. 2LO operated on conditions of restricted timing, at first even no music, and low power, beginning with 100 watts, later raised to 1½kW. Its programmes had each to be individually licensed by the PMG, and were limited to private occasions often for charity, at which Marconi engineers installed the receiving apparatus and operated it. Each programme was notified to listeners by postcard by means of a special mailing list kept by The Marconi Company, and most of them consisted of light music.

The 2LO station transmitter was designed by Captain H. J. Round, installed by C. S. Franklin and run by A. R. Burrows who eventually became the much-loved Uncle Arthur of the BBC. Among the many papers in the Marconi archives which tell the story of the birth of British Broadcasting, not the least interesting is Arthur Burrows' letter requesting permission to recruit a young man of particular quality to compeer the station's programmes, a young man with "technical tendencies . . . grace of manner . . . and an excellent telephone voice". Many of Burrows' requirements were couched in terser terms and it was his organisational skill and foresight that shaped the studio techniques which are still the basis of modern broadcasting.


By this time many wireless societies had been formed and more and more the demand for radio receivers was being felt. In the United States since 1919 'wireless' had become fashionable, but with no constitutional control of the use of wavelengths, chaos reigned in a commercially sponsored free-for-all. The British Government, seeking a way from the dilemma posed by popular demand on the one hand and a justifiable reluctance to allow free access to the air on the other, set up the Wireless Sub-Committee of the Imperial Communications Committee in April of 1922. After consideration, their recommendation to set up a single broadcasting company was accepted and in November 1922 the British Broadcasting Company was formed from six commercially interested companies with £100,000 share capital.



This is the fifth article in the series concerning robots and cybernetic devices, and it continues with the construction of Cyclops.

PART FIVE

by
L. C. Galitz

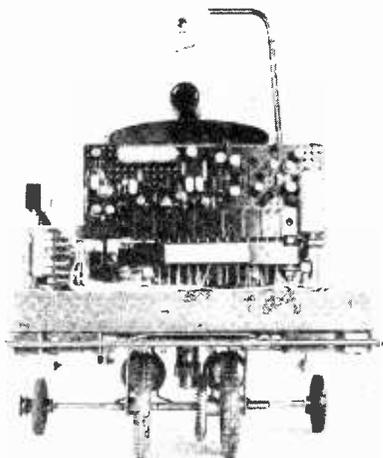

IN THE LAST ARTICLE, CONSTRUCTION of the basic reflexes – reflexes that are instinctive and innate – was discussed. In this article, another type of reflexive response is dealt with; one which is not inborn but is conditioned by the environment – the conditioned reflex.

The first person to study the realms of the conditioned reflex in great detail was Pavlov. In his experiments he would firstly show food to a hungry dog, and measure the amount of saliva produced. Here we have an innate reflex. There is a specific stimulus, which we shall designate Ss, evoking a specific effect, which we shall call Es. After measuring the extent of Es, on the second and subsequent times of feeding, just prior to showing the hungry animal the food Pavlov would present to the animal another stimulus. This second stimulus was a neutral stimulus, having no relevance to the specific stimulus. To the neutral stimulus we shall designate the symbol Sn, and to the effect it evokes we shall designate the symbol En. In Pavlov's experiments, this second stimulus was the ringing of a bell, producing say a pricking up of the dog's ears. Thus the animal would hear a bell and, immediately after this, would be given some food. After about twenty of these coincidences, Pavlov found that on hearing the bell, the animal commenced salivating. In other words, the animal had been conditioned to associate the bell with food.

Pavlov found that in order to build the conditioned reflex quickly, Sn had to be presented a very short time before Ss. He also found that the animal did not produce the conditioned reflex if the bell was rung after the food, or if the bell was rung a long time before the food. He also discovered that in order to maintain the conditioned reflex, the association had to be continually reinforced. It was no use ringing the bell without giving the animal the food; and if the conditioned response was produced it would fade away just as surely if the coincidence of signals never again occurred. Furthermore, if the food was presented without previously ringing the bell, the conditioned response would also fade away, but not as quickly as with the case where the bell is rung without the food.

The conditioned reflex is used with animals extensively today. One often sees an animal at a circus performing a trick and then getting a lump of sugar as a reward. He has been conditioned to associate a correct performance

with food. However, we have also seen that some animals go through trick routines without getting a reward. This is accomplished by having two inter-linked conditioned reflexes. The animal is given a pat and then receives some food. Hence, it associates a pat with food. Then after performing the trick successfully, it gets a pat, and begins to associate that a good performance means a pat. Thus we now have trick means pat means food, and in order that the animal performs his routine correctly without having to feed it in the circus ring, all the trainer has to do is pat the animal after the trick. This process is known as establishing a second-order-conditioned-reflex.

So far, we have dealt with conditioned reflexes where success means reward. There is another variety where failure means punishment. An example of the latter variety is where a crack of the whip follows an animal's misbehaviour, and all reflexes built up where the second stimulus is painful are known as defensive reflexes. With these defensive reflexes, often one association where the second stimulus is more than just discomfort is sufficient to establish a conditioned response, and it often never needs reinforcing.

BLACK BOX ANALYSIS

We can imagine the conditioned reflex unit in animals as a little black box with two inputs, Ss and Sn, and two outputs, Es and En. Normally there are two transmission lines inside; one joins Ss to Es, and the other joins Sn to En. After conditioning, the second transmission line breaks, and reforms to connect Ss to Es. The main problem in synthesizing a conditioned reflex black box is designing the 'bookmaker' which decides when two inputs are associated or not. The way in which our 'bookmaker' works will be described next. (The term 'bookmaker', employed by Dr. W. Grey Walter in his book 'The Living Brain', is applied here to a circuit which tries to work out whether conditioning is profitable or not).

Firstly, we must differentiate Ss and contract it. When our animal is feeding, there is a long output from its food detectors to the input of the black box, and this must be made of short duration. Contrary to this, the second step is to extend Sn from the short period the bell rings, to a much longer period, for it must be 'remembered' for a while. The third stage compares the differentiated Ss and the extended Sn. If there is any overlap, the overlap areas are fed to a summer, which

executes the fourth stage of conditioning. The summer thus sums the coincidences between S_s and S_n , and it's also designed to 'leak' its output away very gradually, so that the summer level will fall if S_s and S_n never again coincide. Incorporated in the summer is a device which gives an output once the summer level has reached a critical level - the threshold of learning. It is this output which operates the switching of the transmission lines, and in Fig.24, details of the operations involved are given pictorially. The sections in Fig.24(c) go through a period of conditioning, which then finally becomes inhibited through lack of reinforcement.

BLOCK DIAGRAM

The operations just described must now be converted into electronic circuitry for it to be incorporated into Cyclops, and the block diagram equivalent is given in Fig.25. It will be noticed that both differentiation and extension are carried out by monostables. This is due to the fact that in order to give a sufficiently long pulse to the summer, a capacitor used in a differentiating circuit would have to be of gargantuan proportions. The differential monostable has a quasi-stable time of one second and the extension monostable has a quasi-stable period of seven seconds. The output of each is fed to one input of a 2-input And-gate. Thus, there will only be an output from this coincidence gate when both monostables are in their quasi-stable period. This will only happen if S_n is given within a period seven seconds before S_s , and the gate will not give an output if S_n is given more than seven seconds before S_s , or if it is given after S_s . The output will also be of reduced duration if S_n is given between six and seven seconds before S_s , because the extension monostable will cut off during the period that the differential monostable is in its quasi-stable state.

The output of the coincidence gate goes to a summer which sums the outputs of the gate, and also 'leaks' slightly during the periods that the gate is not giving an output, so that if reinforcement does not occur the summer level drops. The output of the summer is monitored by a Schmitt trigger whose output is normally at logic nought.

It can be seen from Fig.25 that, whenever S_s is applied, the stimulus also travels down the transmission line to an Or-gate which subsequently gives an output to the E_s terminal. Thus S_s evokes E_s . Similarly, S_n travels down the transmission line to a gate, but this time it is an And-gate. The other input of this And-gate comes from the Schmitt trigger via an inverter, so that when the Schmitt trigger is off, there is a logic one on the upper input of the And-gate, and thus the S_n pulse goes through the gate to the E_n terminal. At the same time, the

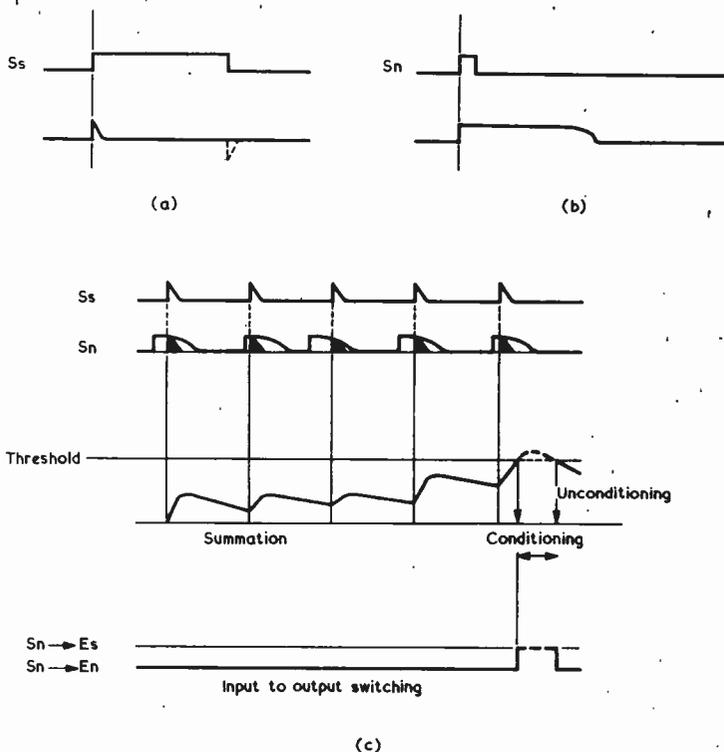


Fig. 24 (a). How S_s is differentiated
 (b). The extension of S_n
 (c). The creation of the conditioned reflex. S_s and S_n coincide a number of times, causing the summation which appears below them. When the summation characteristic exceeds the threshold level conditioning takes place, with the consequent input to output switching shown at the bottom

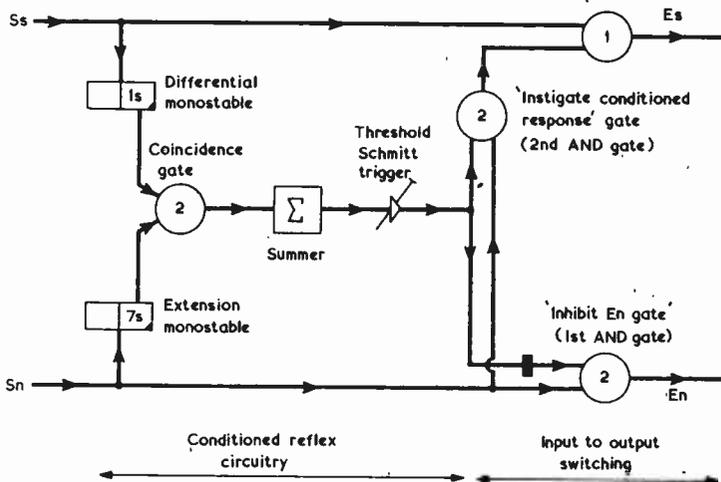


Fig. 25. Theoretical version of the conditioned reflex circuits

Sn pulse goes to another And-gate, whose other input goes directly to the Schmitt trigger; and so when the latter has not fired there will be a logic nought on the And-gate's input, and the second And-gate will not fire.

When the summer level reaches the input threshold of the Schmitt trigger, the trigger fires, making its output change to logic one. Once this happens, there will be a logic nought on the upper input of the first Sn And-gate, and therefore the Sn pulse coming along the lower transmission line will not get through this gate. On the other hand, there will now be a logic one input on the second gate, and when a pulse from Sn comes along the transmission line, there will be an output from this gate which leads to the other input of the Or-gate. Thus, after conditioning, instead of Sn evoking En, it now evokes Es.

THE PRACTICAL BLOCK DIAGRAM

The block diagram employed for the practical model differs from the theoretical diagram of Fig.25, the differences being mainly in the input and output stages rather than with the 'bookmaker'.

Firstly, the conditioned reflex in Cyclops is made to do two jobs. In one mode, the inputs and outputs are switched so that it is allowed to associate magnetism with touch, and

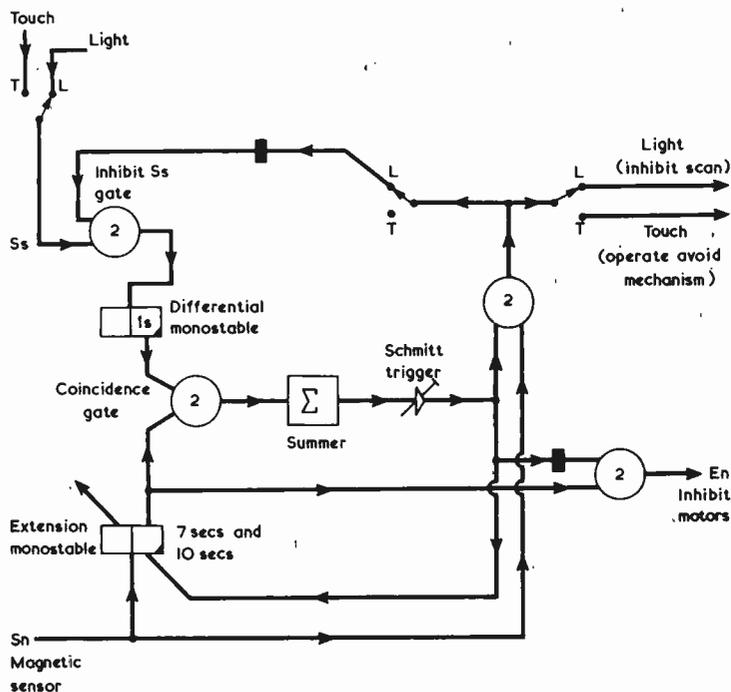


Fig. 26. Practical conditioned reflex unit. Note that the Ss to Es transmission line already exists in the basic circuitry.

COMPONENTS

Resistors

(All fixed values ½ watt 10%)

R23	1kΩ
R24	2.2kΩ
R25	2.7kΩ
R26	2.2kΩ (see text)
R27	6.8kΩ
R28	100kΩ
R29	2.7kΩ
R30	1kΩ
R31	1kΩ (see text)
R32	2.7kΩ
R33	100kΩ
R34	15kΩ
R35	15kΩ
R36	2.7kΩ
R37	1kΩ
R38	4.7kΩ
R39	22kΩ
R40	10kΩ
R41	470Ω
R42	4.7kΩ
R43	56kΩ
R44	1kΩ
R45	1kΩ
R46	56kΩ
VR4	10kΩ potentiometer, preset skeleton

Capacitors

C6	0.05μF
C7	125μF electrolytic, 10 V.Wkg.
C8	0.05μF
C9	400μF electrolytic, 10 V.Wkg.
C10	1,000μF electrolytic, 10 V.Wkg.

Semiconductors

TR15-TR18	Any p.n.p. transistor, e.g. OC71
TR19, TR20	2N2926
TR21, TR22	As TR15-TR18
TR23	Any p.n.p. transistor with low leakage
TR24, TR25	As TR15-TR18
TR26, TR27	Any n.p.n. transistor, e.g. AC127
TR28	Any p.n.p. transistor capable of driving relay, e.g. OC81
TR29, TR30	As TR15-TR18
TR31	As TR28
D4	Any silicon diode, e.g. OA200
D5	Silicon diode with high reverse resistance
D6-D9	As D4

Magnetic Sensor

X2	Dry reed switch, R.S. Components type 7RSR (Home Radio Cat No. WS121)
----	---

Battery

BY3	6V 225mA/H Deac rechargeable battery (Ripmax Ltd.)
-----	--

Veroboard, Connector

Veroboard:	0.15in. matrix, 2 × 5in., 13 strips × 33 holes
Connector:	Painton 15 pin in-line connector (see text)

Miscellaneous

Tank clip (for securing BY3)	(Ripmax Ltd.)
2-off Meccano double brackets,	part 11 (see text)
1-off Meccano rod and strip connector,	part 212a
1-off Meccano rod,	3½in., part 16.

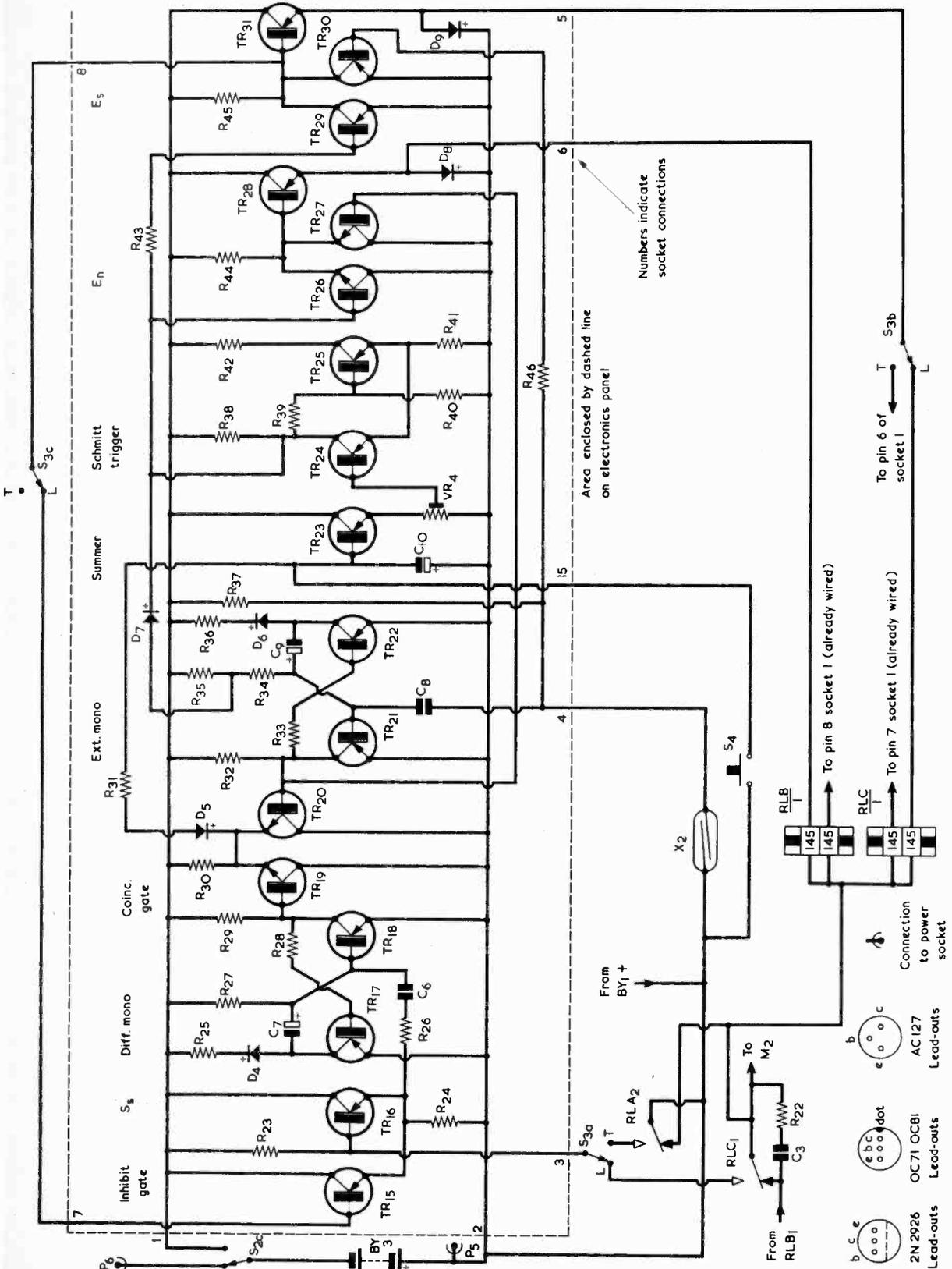


Fig. 27. Circuit diagram for the conditioned reflex unit

in the other mode, the inputs and outputs are switched so that Cyclops has the ability to associate magnetism with light.

An extra gate had to be included because of this since it was found that, when Cyclops was conditioned, giving Sn evoked Es, but in both cases, the action of Es was to produce Ss. Due to the fact that touch means pain in Cyclops, in the 'magnetism means touch' mode, this automatic reinforcement of the coincidence between Sn and Ss is desirable. The conditioning does not need to be reinforced — this being found in real life with defensive reflexes. However, the effect is undesirable with 'magnetism means light' conditioning, and the extra gate temporarily disconnects Ss whilst Es is being evoked in the 'magnetism means light' mode. In the other mode, there is no feedback supplied to the new And-gate via the inverter, and thus Ss is never inhibited, and automatic reinforcement is allowed to take place.

Another modification used concerns what is known as the trace reflex. After conditioning, an animal can allow Ss to occur after a longer period after Sn than before conditioning. Accordingly, the output of the Schmitt trigger alters the time constant of the extension monostable from seven seconds before conditioning to ten seconds after conditioning.

In Cyclops, Sn is always the output from a magnetism sensor. It will be

appreciated that strong magnetic fields could upset the operation of Cyclops' circuitry by inducing unwanted voltages in the circuit whilst Cyclops roams around. (In actual fact, extremely powerful fields not normally encountered outside the research laboratory would be required to do this, but Cyclops is only demonstrating the principle involved.) To prevent this, whenever Cyclops encounters a strong enough magnetic field he stops dead to prevent these voltages being induced, and he 'plays possum' for a short while; after a few seconds, he slowly creeps off again. Thus, En is to stop the motors for a while. In the interests of economy, therefore, instead of having a third monostable to do this after the En And-gate, Cyclops uses his extension monostable instead, and the input of the En gate goes to the output of this monostable instead of directly to Sn. The altering of this monostable's time constant bears no relevance, because En is inhibited whenever the monostable runs with a ten second time constant. Fig.26 gives details of the modifications.

Therefore, when Cyclops operates in the 'magnetism means light' mode, in order to establish the conditioned reflex one must apply a magnet to his magnetic sensor, and then shine a light into his eye. After several such coincidences, instead of stopping when one applies the magnet he will con-

tinue in the direction he was going when the magnet was applied. He has thus built up the association that magnet means light which is food, and so keep going in the same direction in order to home into the magnet.

When Cyclops operates in the 'magnetism means touch' mode, to set up the conditioned response one must apply the magnet, which makes Cyclops stop in his tracks for a short while, and then jar his touch sensor, which makes him go through his avoid reflex. After a few coincidences, upon applying the magnet he will immediately start twisting and turning in an attempt to avoid the magnet, because the association that 'magnet means touch' which is pain, and so has to be avoided, has been set up.

CIRCUIT

The circuit for the conditioned reflex unit is given in Fig.27. This will be discussed in the next issue, in which the concluding article in the present series on Cyclops will be given. Also given this month is a Components List showing the additional parts required. Some of these are discussed in detail next month and readers are advised to wait until the appearance of the next article before obtaining any components over which they may have any doubt.

(To be concluded)


'LASER-LINE'

The accompanying photograph illustrates the Marconi-Elliott 'Laserline' in operation at the British Steel Corporation plant in Ebbw Vale, South Wales. The 'Laserline', is produced by Marconi-Elliott Avionic Systems Ltd., a member of GEC-Marconi Electronics Limited.

At the Ebbw Vale works B.S.C. surveyors have, with the aid of the 'Laserline', cut by 80% the time spent in checking the alignment of overhead crane rails. The first survey incorporating the 'Laserline' was of the 700 ft. rails in the No. 2 galvanising line, where 25 ton loads of steel strip are handled by an overhead crane with a span of 90 ft. The rails are 60 ft. above floor level and heat haze makes visual sighting difficult, whereupon survey work could only be carried out previously during the few hours when the plant was not fully operating. There are a score of overhead crane rails in the Ebbw Vale works.

The beam of the 'Laserline' penetrates haze and enables more accurate measurements to be obtained. It can be set up very quickly, so that a survey at Ebbw Vale can now be completed in three hours at any time of the year instead of over several days during the annual shut down period."

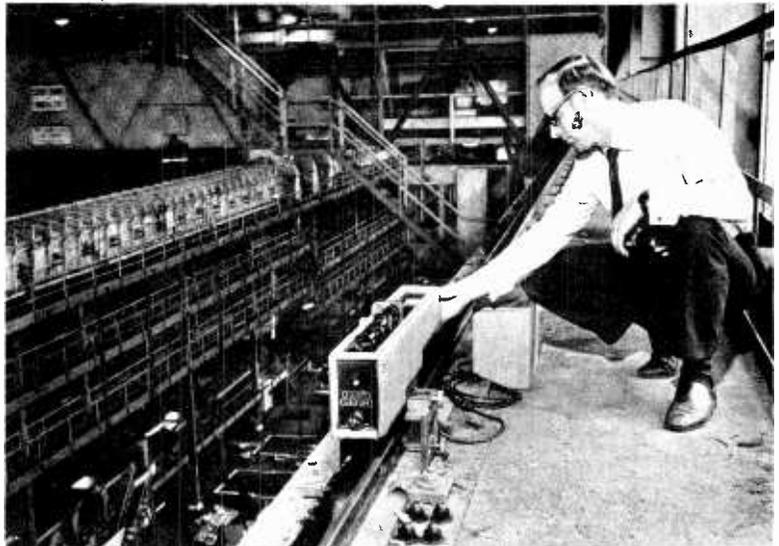The 'Laserline' is a portable laser beam projector designed specifically



for field operation, and it provides an accurate linear reference in pipe-laying, tunnel guidance and other civil engineering applications. It is rugged and waterproof, is fitted with a sighting telescope and levelling bubble and operates from a 12 volt battery. The advantages of a laser beam are that,

once aligned, it operates unmanned and is not disturbed by people or vehicles passing through the reference line. The 'Laserline' is manufactured by the Neutron Division of Marconi-Elliott Avionic Systems Ltd. at Elstree Way, Borehamwood, Herts. ■

SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

The lead story this month concerns the appearance of Radio Conakry, Guinea Republic, on a measured 4903 (61.18 metres) where it was first heard by us in early September at 1930 with identification in French followed by African music. This represents a shift in frequency from 4910. The published evening schedule is from 1600 to 2400 and the address is - Radiodiffusion Nationale, B.P. 617, Conakry.

NOW HEAR THESE

Asian stations are being heard here in the U.K. somewhat earlier this year than is normal, during afternoon sessions Indian stations on the low frequency bands have been coming through at quite good signal strengths.

AIR Delhi on 4760 (63.03m) at 1659, Hyderabad on 4800 (62.50m) at 1700 and Madras on 4920 (60.98m) at 1720 (under Moscow) have all been logged according to the British Association of Dicers (BADX).

Other Asian stations that have been heard are - Radio Ceylon on 4870 (61.60m) at 1724; Radio Nepal on 5000 (60.00m) at 1615 to 1620 sign-off and Radio Singapore on 5010 (59.88m) and on 5052 (59.38m) with Asian music, identification, National Anthem and sign-off at 1627.

During late night sessions, the following Asian stations have been logged - Radio Bangkok on 4830 (62.11m) at 2257 with 14 or 15 note chime interval signal, anthem, more chimes, man speaking in Thai and then into Asian 'pops'; Radio Malaysia, Kajang, on 4845 (61.92m) at 2315 with Indian music and Tamil announcements; Lan-Chou in Kansu province of China on 4864 (61.67m) at 2252 with talk in Chinese; Radio Phonm-Penh on 4907 (61.14m) at 2226 with music and talk in Khmere; Radio Malaysia, Penang, on 4985 (60.18m) at 2316 with announcements in English, advert for ground coffee and western 'pops' and Radio Singapore around 2310 with Chinese songs on 4845 (61.92m), 4985 (60.18m), 5010 (59.88m) and on 5052 (59.38m).

We have recently logged Radio Phonm-Penh at 2215 on 4907 when continuous Buddhist chants were being radiated. Radio Singapore on 5052 was also logged during the same evening at 2255, a programme of dance music being marred by CW interference on the channel.

● IRAQ

Radio Baghdad, which was reported to have vacated 7240 for 7210 has in fact been using 7227 (41.51m). Following a lead from BADX, we heard it at 1920 with a programme of Arabic music and songs.

● PAKISTAN

Radio Pakistan has been logged on 11650 (25.75m), an experimental channel, at 1600 with opening melody, and news in dialect followed by local music. ●

● SEYCHELLES

FEBA may often be heard around 1745 on 11955

(25.09m), at which time we listened to a religious programme in English.

● CLANDESTINE

The Voice of the Malayan Revolution was recently logged by us on 15789 (19.00m) at 1347 when a talk in a Chinese vernacular was heard followed by a choral marching song at 1350, this pattern being followed until 1400 when identification (?) was made. Faded out by 1410.

● SRI LANKA

Colombo has been heard with a programme of dance music records and announcements in English at 1645 on 15120 (19.84m). The channel is subject to splatter from an adjacent jamming station, only brief 'snatches' of the programme being heard.

● ETHIOPIA

ETLF Addis-Ababa has been heard (following a lead from BADX) on 7145 (41.99m) with the news in English after station identification at 1900. BADX reports that the station is asking for reports on this channel.

● INDIA

AIR Delhi can be heard with news of Indian affairs in English at 1900 onwards on 7215 (41.58m), the channel being subject to QRM from an adjacent jamming station.

● EGYPT

For an evening newscast giving the Arabic view of world affairs, tune to 9805 (30.59m) where Cairo broadcasts the news in English at 2215.

● CHINA

Peking broadcasts on many differing channels, 15030 (19.96m) and 15060 (19.92m) being regularly heard during the evenings around 1915 but there are Chinese regional stations that can be heard if conditions are right and a little patience exercised. Of these, the Fukien Front transmitters on 3200 (93.75m), 3400 (88.23m) and 3900 (76.92m) are most often reported, usually around 2015 to 2045 or so - but what about listening for Kueiyang, Kweichow, on 3260 (92.02m) when signing-on at 2158; Hupeh, Wuhan, on 3940 (76.14m) after sign-on at 2130; Hsi-ning, Tsinghai, on 3950 (75.95m) with gym exercises at 2245; Urumchi, Sinkiang, on 4110 (72.99m) at 2304 with talk in Uighur; Urumchi on 4500 (66.66m) at 2307 with talk in Chinese dialect or K'un-ming, Yunnan, on 4760 (63.02m) at 2205 with songs in Chinese - the latter station also being reported, in parallel, on 4785 (62.69m) and 6935 (43.29m). Information on Chinese local stations has been kindly provided by BADX.

● BRAZIL

ZYN32 Radio Nacional Brasilia may be heard, according to BADX, on 15448 (19.42m) at 2230 with a talk in English, request for reports and tapes.

RADIO & ELECTRONICS CONSTRUCTOR

TIME-CHECK

The stations mentioned in the foregoing paragraphs are listed here on a time-check basis for the convenience of readers.

GMT	Freq.	Stn.	Revd.
1347	15789	Voice Malayan Revolution	
1600	11650	R. Pakistan	
1615	5000	R. Nepal	
1645	15120	Colombo	
1659	4760	AIR Delhi	
1720	4920	AIR Madras	
1724	4870	Colombo	
1745	11955	Seychelles	
1900	7145	Addis-Ababa	
1900	7215	AIR Delhi	
1915	15030	Peking	
1915	15060	Peking	
1920	7227	R. Baghdad	
1930	4903	R. Conakry	
2015	3200	Fukien Front	
2015	3400	Fukien Front	
2015	3900	Fukien Front	
2130	3940	Hupeh	
2158	3260	Kuei-yang	
2205	4760	K'un-ming	
2215	9805	Cairo	
2226	4907	R. Phonm-Penh	
2230	15448	ZYN32 R.N. Brasilia	
2245	3950	Hsi-ning	
2252	4864	Lan-Chou	
2257	4830	R. Bangkok	
2304	4110	Urumchi	
2307	4500	Urumchi	
2310	4845	R. Singapore	
2310	5010	R. Singapore	
2310	5052	R. Singapore	
2316	4985	Penang	

CURRENT SCHEDULES

● HOLLAND

Radio Nederland broadcasts in English to Europe as follows - weekdays from 0930 to 1050 on **6020** (49.83m)

and on **7275** (41.24m); from 1400 to 1520 on **6020**; from 1830 to 1950 on **6020** and **15375** (19.51m). On Sundays from 0930 to 1050 on **6020**, **6140** (48.86m) and on **7275**; from 1400 to 1520 on **6020** and from 1830 to 1950 on **6020** and on **15375**.

● KUWAIT

Radio Kuwait has replaced the **11825** channel with that of **15415** (19.46m) for the English transmission from 1730 to 1900.

● THAILAND

Bangkok has an external service in English from 1025 to 1117 and from 0415 to 0530 on **9655** (31.07m) and on **11905** (25.20m) the latter transmission being intended for North America.

● TURKEY

Radio Ankara broadcasts to the U.K. and N. Africa in English from 2200 to 2230 on **9515** (31.53m) and on **15195** (19.74m).

● NORWAY

Radio Norway, Oslo, broadcasts in English on Sundays as follows - from 1200 to 1230 on **6130** (48.94m), **15175** (19.77m), **21655** (13.85m), **21730** (13.80m) and on **25900** (11.58m). From 1600 to 1630 on **15345** (19.55m), **21655**, **21730**, **25730** and on **25900**. From 1800 to 1830 on **6130**, **17825** (16.83m), **21655**, **21730** and on **25900**. From 2000 to 2030 on **6130**, **17825**, **21655** and on **21730**. From 2200 to 2230 on **11850** (25.31m), **15175** and on **15345**. On Mondays from 0001 to 0030 on **9610** (31.22m), **11735** (25.56m) and on **11850**.

● LEBANON

Radio Lebanon, Beirut, radiates a programme in English from 1830 to 1900 on **15170** (19.77m), for Europe and from 0230 to 0300 on **9550** (31.41m) for North and Central America.

● PAKISTAN

Radio Pakistan, Karachi, broadcasts in English to Europe as follows - from 2000 to 2010 and from 2035 to 2040 on **7095** (42.28m) **9460** (31.71m) and on **15520** (19.33m).

AROUND THE DIAL

● GABON

Franceville is currently reported using **4830** (62.11m) by BADX, being heard from 2000 until 2200 sign-off. Identification "Ici Franceville, station Nationale, la Voix de la Renovation" being heard at 2115. Not in parallel on **4777**, so presumably a shift from that channel.

● SENEGAL

Dakar can often be heard on the regular **4890** (61.34m) channel around 1915, usually with local music and songs with announcements in French.

● GHANA

Accra has been heard often around 2110 with local news in English followed by station announcements on the normal **4980** (60.24m) channel.

● SOUTH AFRICA

Johannesburg, with 'pops' and announcements in English at 2133 on **4945** (60.66m).

● CEYLON

Radio Ceylon, logged often from 1700 until sign-off at 1730 with "All Asia Service of Radio Ceylon from Republic of Sri Lanka", on **9719** (30.86m).




Cover Feature - 2

The 'WYVERN' 160

Solid State

by

John R. Green, B.Sc., G3WVR

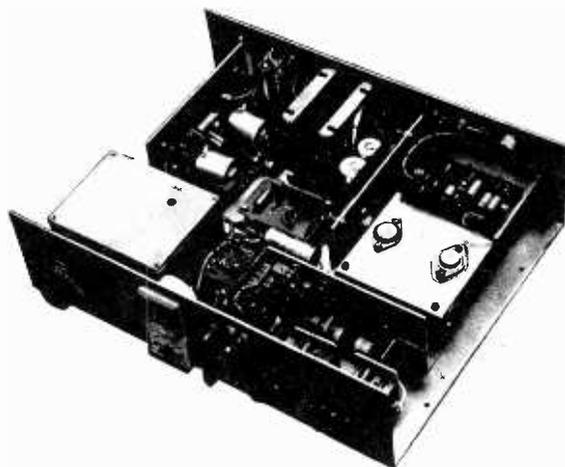

This view inside the transmitter illustrates the manner in which the circuit modules are assembled on the main chassis

THIS ARTICLE REPRESENTS THE AUTHOR'S DEVELOPMENT of a solid state transmitter which has been in use for some two years.

Initial development of p.a. and modulation techniques began earlier, however, and the design presented is a v.f.o. controlled version of an earlier, simpler, crystal controlled transmitter. The design will appeal to those who are eager to experiment with the constructional challenge of an all-transistor transmitter, and good results should be obtained without difficulty.

The design is capable of running at least 10 watts input and provides excellent quality of modulation, good frequency stability and negligible frequency modulation. Although the overall system is quite large and complex in terms of component quantities, the modular construction simplifies the building and testing programme to a step-by-step process.

In this month's issue the v.f.o., wideband driver stage and frequency doubler and driver section are described, whilst the subsequent two articles will deal with the power amplifier stage, modulator, power supply and VU meter driver. Chassis assembly and the building and testing procedure will be discussed in the third article.

The overall system block diagram is shown in Fig.1, which is self-explanatory. The detailed operation of each section will be covered in the constructional information.



Metre

Transmitter

This 3-part series deals with a comprehensive transmitter design which incorporates semiconductors throughout. The description of its construction is continued in Parts 2 and 3, which will be published in the next two issues.


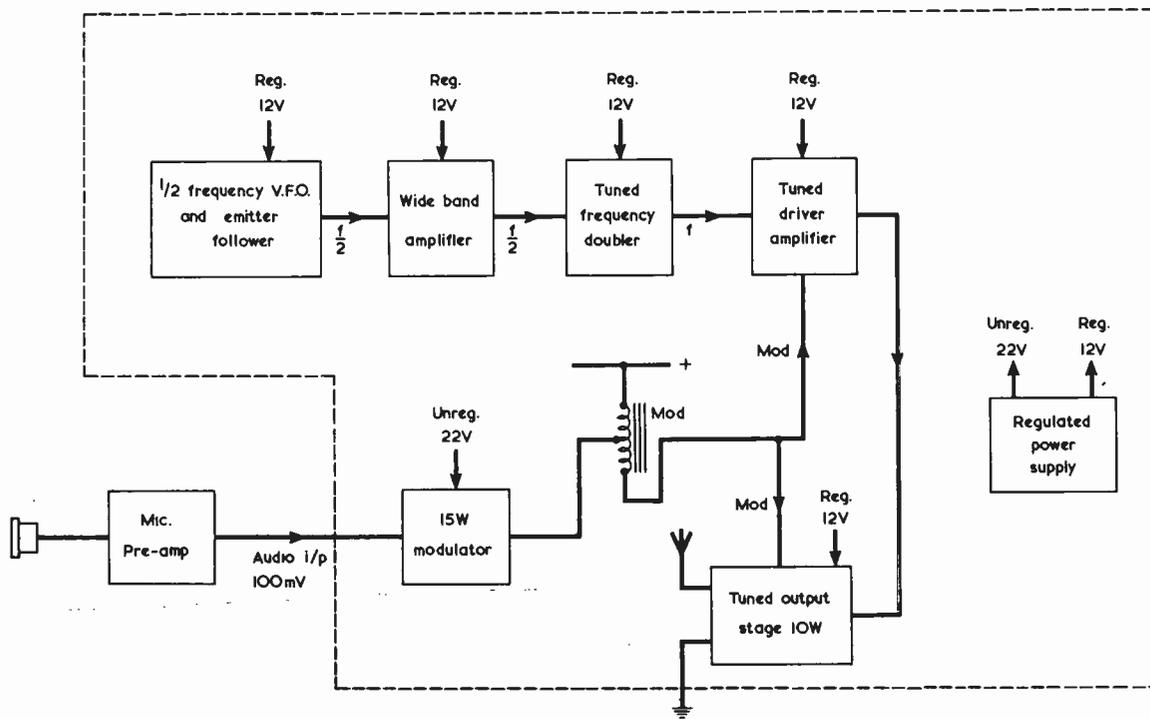


Fig. 1. Block diagram showing the sections of the all-transistor 160 metre transmitter

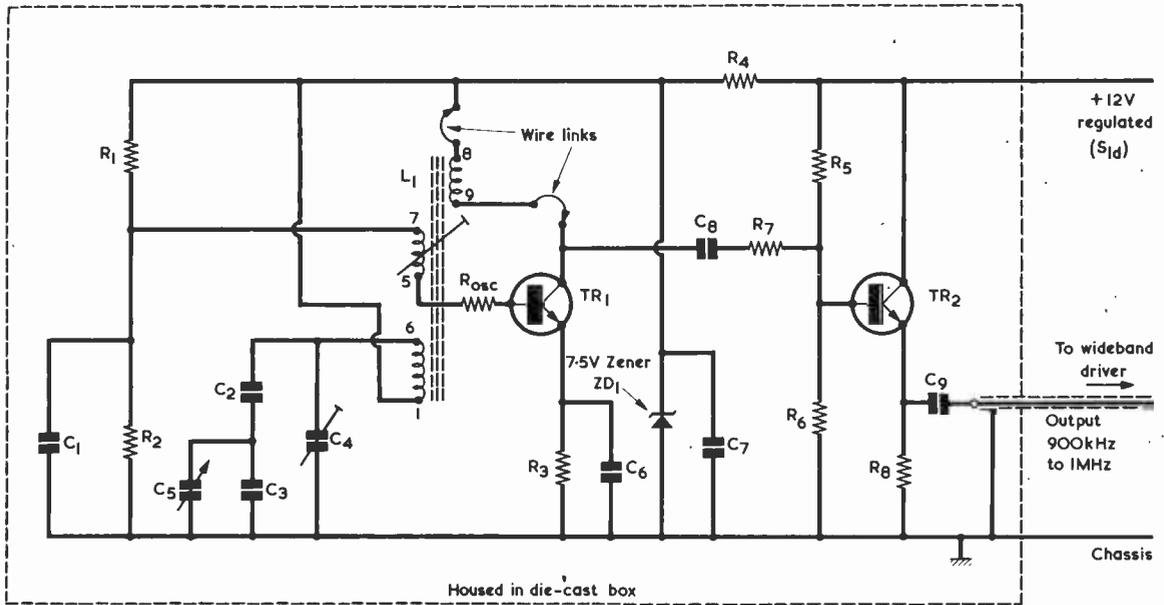

TR₁ 2N2484/BC109/2N930
TR₂ BFY50/2N3053

2N2484, BC109, 2N930,
BFY50, 2N3053
Lead-outs

Fig. 2. Circuit diagram for the v.f.o. stage

THE V.F.O. STAGE

The circuit diagram of the v.f.o. stage is shown in Fig.2. The frequency range covered is 900kHz to 1MHz, i.e. half the output frequency, since during development it was found impractical to run the oscillator at the fundamental frequency due to serious 'f.m. pulling' and asymmetric modulation which this produced.

Oscillation is achieved with the Denco coil L1 (Yellow, Range 2T, Transistor) wired in a positive feedback mode. Frequency stability is maintained by:


- (a) using a 7.5 volt zener stabilized supply;
- (b) coupling the coil to TR1 as 'loosely' as possible (which maintains a high Q and also, incidentally, improves the output waveform and helps to prevent parasitic oscillations) by selecting Rosc;
- (c) running TR1 at low power to prevent heating.

Oscillation can only occur if the coil is wired for positive feedback so connections 8 and 9 may have to be reversed if the circuit will not oscillate. Pin 1 of the coil is returned to the positive supply rail as this simplifies the printed circuit layout.

When testing, start with Rosc as a short-circuit link. When oscillation is obtained in the correct frequency band (by adjustment of the coil core) begin increasing the value of Rosc, starting at say 2.2k Ω , and go on increasing until oscillation stops. Finally, reduce Rosc to the highest preferred value which still permits reliable oscillation.

The emitter follower, TR2, presents a high impedance to the oscillator, buffers it from the next stage and provides a low impedance output.

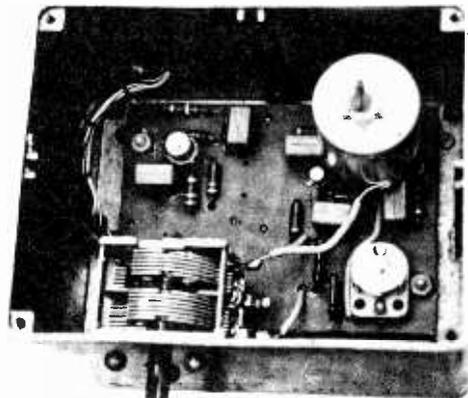The regulated 12 volt supply is obtained from switch S1(d), which will be described in Part 2.



A view inside the v.f.o. box. Note the manner in which the coil can connect to chassis via the tuning capacitor frame.

Resistors

(All 1/2 watt 10%)

- Rosc See text
- R1 18kΩ
- R2 8.2kΩ
- R3 1kΩ
- R4 390Ω
- R5 10kΩ
- R6 10kΩ
- R7 100Ω
- R8 470Ω
- R9 18kΩ
- R10 5.6kΩ
- R11 680Ω
- R12 390Ω

COMPONENTS

- R13 220Ω
- R14 4.7kΩ
- R15 1kΩ
- R16 47Ω
- R17 4.7kΩ
- R18 47Ω
- R19 47Ω
- R20 47Ω
- R21 See text
- R22 47Ω
- R23 47Ω
- R24 22Ω
- R25 See text

- C16 0.1μF plastic foil
- C17 240pF silvered mica
- C18 68pF silvered mica
- C19 0.1μF plastic foil
- C20 240pF silvered mica
- C21 0.1μF plastic foil
- C22 0.1μF plastic foil

Inductors

- L1 Denco Miniature Dual Purpose Coil, Yellow, Range 2T, transistor usage
- L2, 3 Denco Miniature Dual Purpose Coil, Yellow, Range 3T, transistor usage

Semiconductors

- TR1 2N2486/BC109/2N930
- TR2 BFY50/2N3053
- TR3 2N2484/BC109/2N930
- TR4 BFX88
- TR5, 6 2N3053
- ZD1 7.5V, 200mW, zener diode

Miscellaneous

- Die-cast box, 4 3/8 ins. by 3 3/8 ins. by 3 1/8 ins.
- 3 B9A valveholders, printed circuit type (for L1, L2 and L3)
- 2 TO5 heat sinks (for TR5 and TR6)
- Slow-motion drive, Eagle T502 or similar
- Printed circuit board
- 16 s.w.g. aluminium
- Coaxial cable

Capacitors

- C1 0.1μF plastic foil
- C2 390pF silvered mica
- C3 200pF silvered mica
- C4 30pF trimmer, air-spaced
- C5 300pF variable
- C6 0.1μF plastic foil
- C7 0.1μF plastic foil
- C8 0.1μF plastic foil
- C9 0.1μF plastic foil
- C10 25μF electrolytic, 25 V.Wkg.
- C11 0.1μF plastic foil
- C12 0.1μF plastic foil
- C13 0.1μF plastic foil
- C14 25μF electrolytic, 25 V.Wkg.
- C15 68pF silvered mica

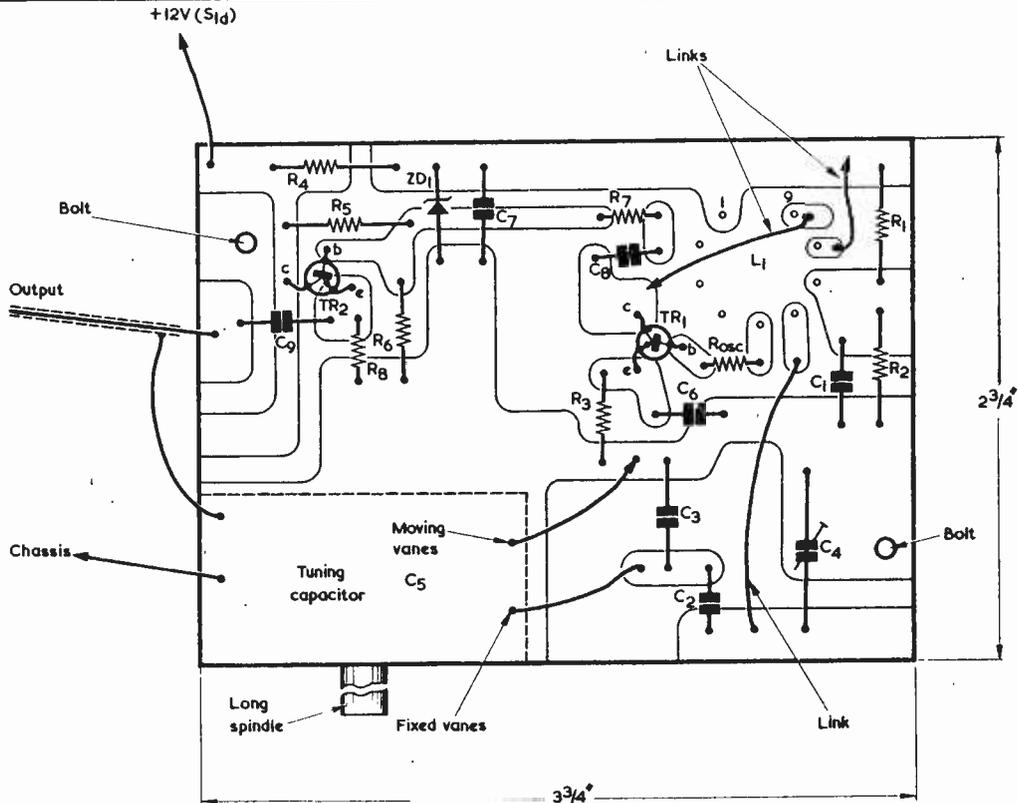


Fig. 3. The layout of the v.f.o. printed circuit board. This view is with the components towards the reader

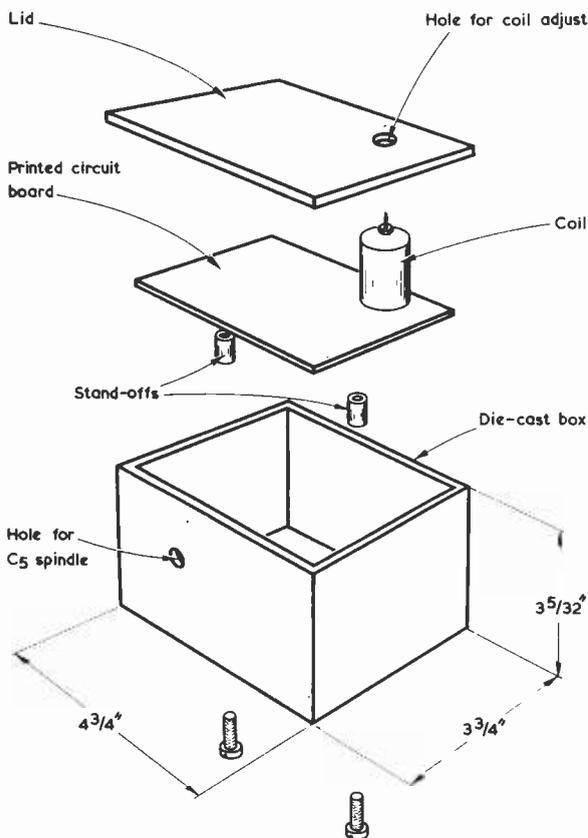


Fig. 4. How the v.f.o. printed circuit board is fitted in the die-cast box

The printed circuit layout is given in Fig. 3 and the housing details in Fig. 4. It is necessary for the v.f.o. to be screened and it is fitted in a die-cast box having the dimensions shown. The author obtained this box from G. W. Smith & Co. (Radio) Ltd., 3 Lisle St., London, W.C.2.

The printed circuit is shown full-size in Fig. 3, and the diagram may be traced, if desired. The view is of the component side of the board. The tags of a printed circuit type B9A valveholder (in which the coil is fitted) pass through the board at the holes indicated and these holes should be marked out from the valveholder itself as the hole positioning in the diagram is approximate only. Since Fig. 3 shows the component side of the board, the valveholder tags are numbered from 1 to 9 in an *anti-clockwise* direction. As may be seen from the photograph of the v.f.o. circuit, the coil is fitted with a screening can. This is made from the can in which the coil is supplied, it being cut down to clear components adjacent to the coil. The can has a solder tag at its lower end and is earthed to the frame of the tuning capacitor. The latter requires a long spindle (or needs to be fitted with a spindle extender) to enable it to couple to the slow-motion drive on the front panel of the complete transmitter. The tuning capacitor is bolted to the front of the die-cast box and is not mounted on the printed circuit.

Although printed circuit construction is neat and reliable, some constructors may prefer to use plain Veroboard and 'Cir-Kit'. This is, of course, quite permissible although it is wise to stick to a similar layout.

The use of Veroboard with copper strips is not recommended due to the multiple feedback capacitance paths this offers, which could produce instability.

Note the wire links between tags 8 and 9 of L1 and the remainder of the circuit. These enable the connections to these tags to be reversed, if necessary, to obtain positive feedback.

The printed circuit board is spaced off from the bottom of the die-cast box by means of suitable stand-off spacing washers. A hole in the lid provides access to the adjusting screw of the coil core. The supply and output leads are taken out in a laced-up harness through a hole in the rear of the die-cast box. This hole is not shown in Fig. 4, but it may be seen in the photograph of the v.f.o. unit. The output, taken via coaxial cable, connects to the input of the wideband driver section.


WIDEBAND DRIVER SECTION

This second section, whose circuit is given in Fig. 5, uses a conventional amplifier stage (TR3) to raise the signal from the v.f.o. to a level which causes TR4 to be switched on and off. TR4 then provides pulses of current to drive the frequency doubler.



The printed circuit layout is shown in Fig. 6. Again, the view is from the component side of the board, and as the board is reproduced full-size, the diagram may be traced. The board is mounted on Chassis Bracket No. 1, which is illustrated in Fig. 7. Four spacing washers stand the board off the bracket surface. As will be seen later, when the overall chassis assembly is dealt with, the board is mounted with its input end close to the v.f.o. box.

FREQUENCY DOUBLER AND DRIVER

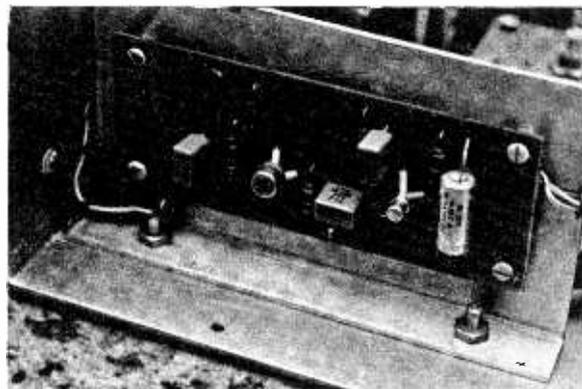The frequency doubler and driver section incorporates higher power transistors (2N3053) which are biased to be cut off and switched on only by incoming positive-going r.f. pulses. These pulses are obtained from the wideband driver. The circuit of the doubler and driver



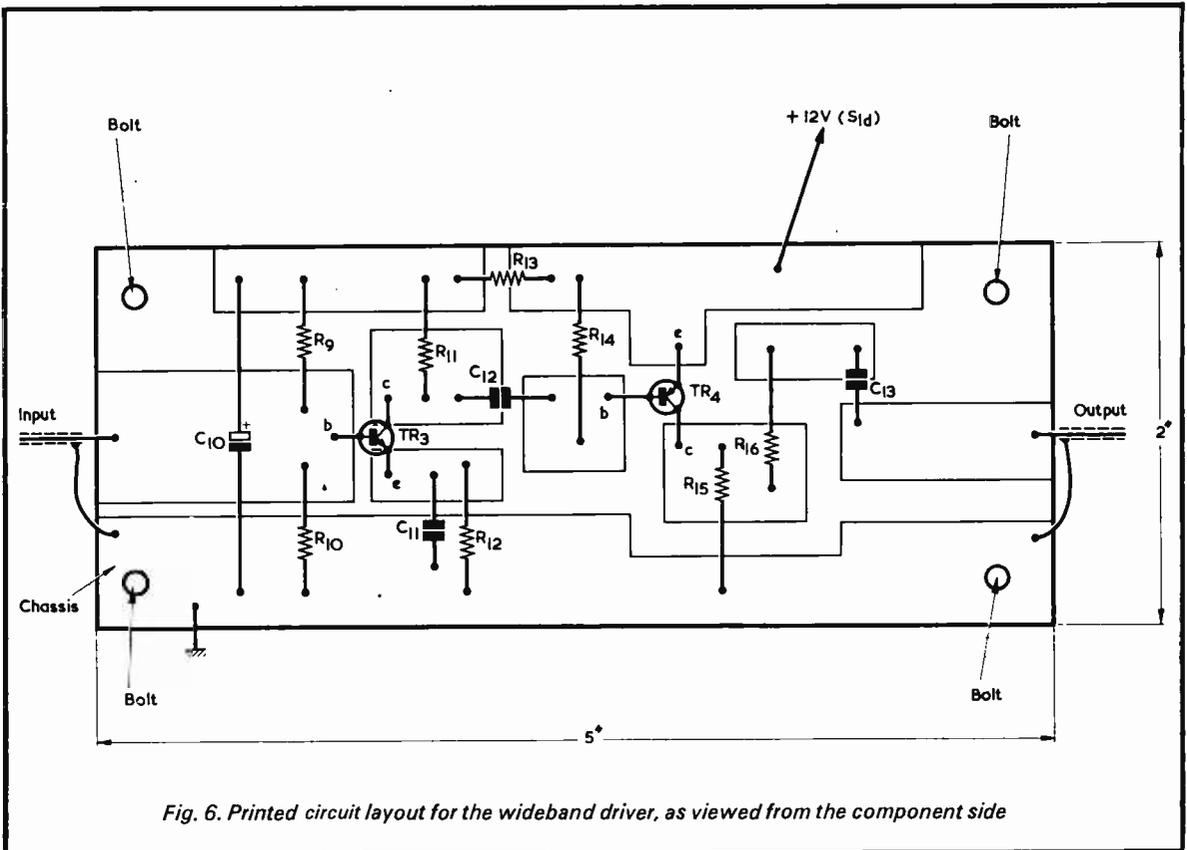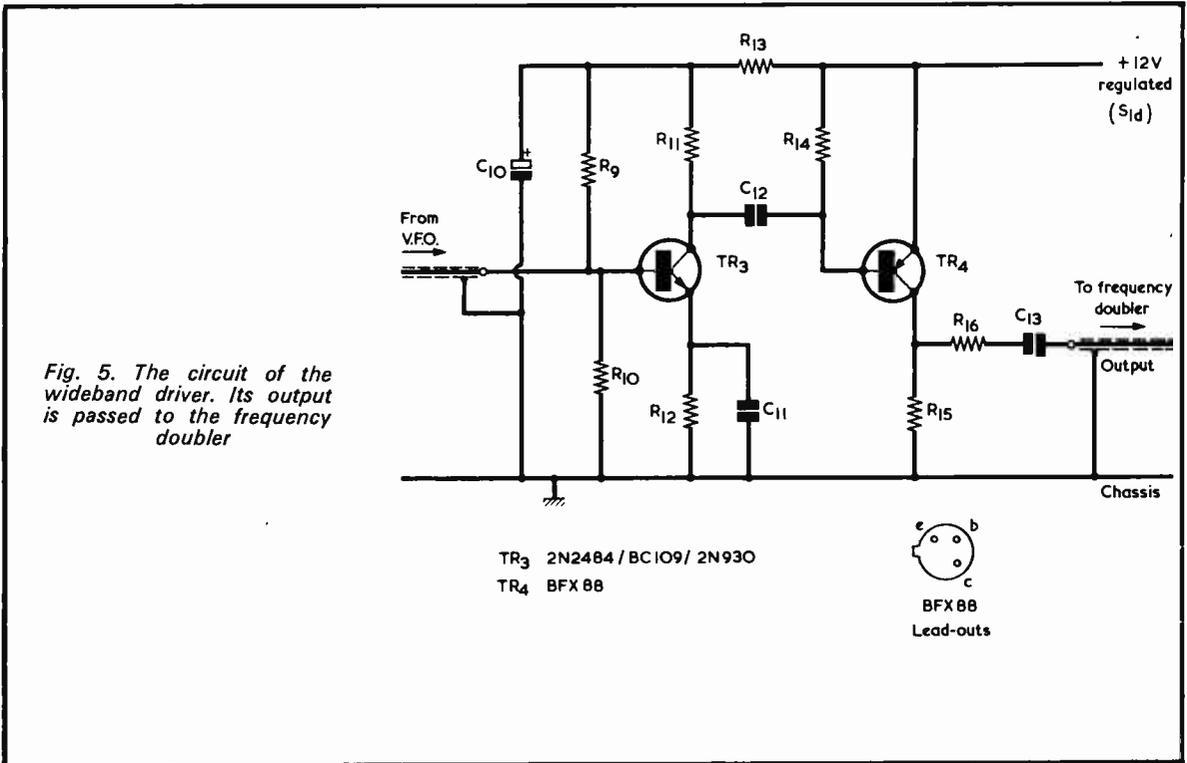The wideband driver board in position on Chassis Bracket No. 1



RADIO & ELECTRONICS CONSTRUCTOR

OUR NEXT ISSUE FEATURES TRANSISTORISED OSCILLOSCOPE



The article describes the mechanical construction of the instrument, the power supply and display section, and the X amplifier module. The only thermionic device is the cathode ray tube. The remainder of the circuit will be covered in the concluding article, which will be published next month.

(Pt. 1 of a 2 Part article)
by R. A. Penfold

ALSO
HIGH-GAIN SILICON REFLEX
RECEIVER

* * *
USING THE F.E.T.

PLUS

MANY OTHER ARTICLES

PRICE 20p

ON SALE 1st DECEMBER

ORDER YOUR COPY **NOW**

Copies may also be obtained direct from the Publishers, 26p. including postage. Published by Data Publications Ltd. 57 Maida Vale, London W9

Chassis bracket No.1
(16 swg aluminium)


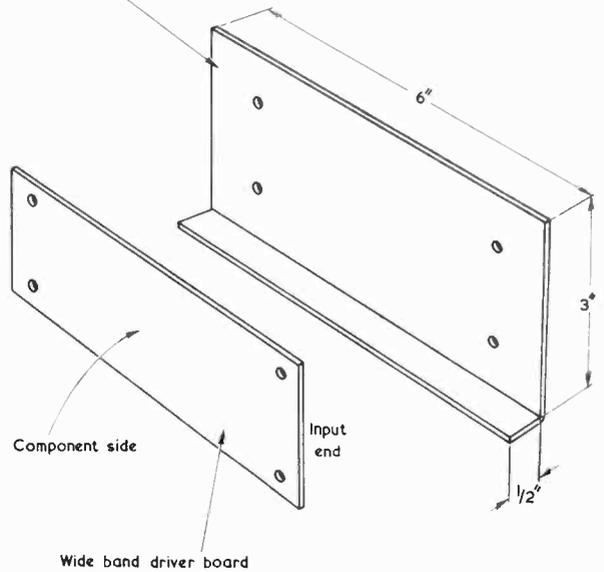


Fig. 7. The board is mounted on Chassis Bracket No. 1

section appears in Fig. 8. The references, at the supply input points, to S1(c) and S1(d) will be explained when the power amplifier stage is described.

Both the coils, L2 and L3, are Denco Yellow, Range 3T, transistor usage types, and they are tuned, by their cores, to approximately 1.9MHz. For optimum band coverage they should be stagger-tuned, say to 1.86MHz and 1.94MHz. Damping resistors R21 and R25 present a method of lowering the Q of the coils, but at the expense of drive. Their values are selected as necessary for the desired band coverage.

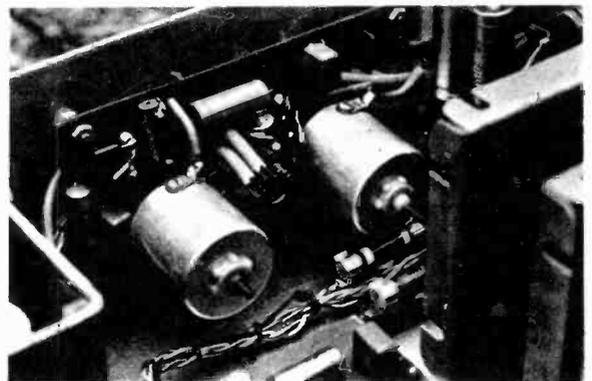

The frequency doubler and driver board. This is also mounted on Chassis Bracket No. 1

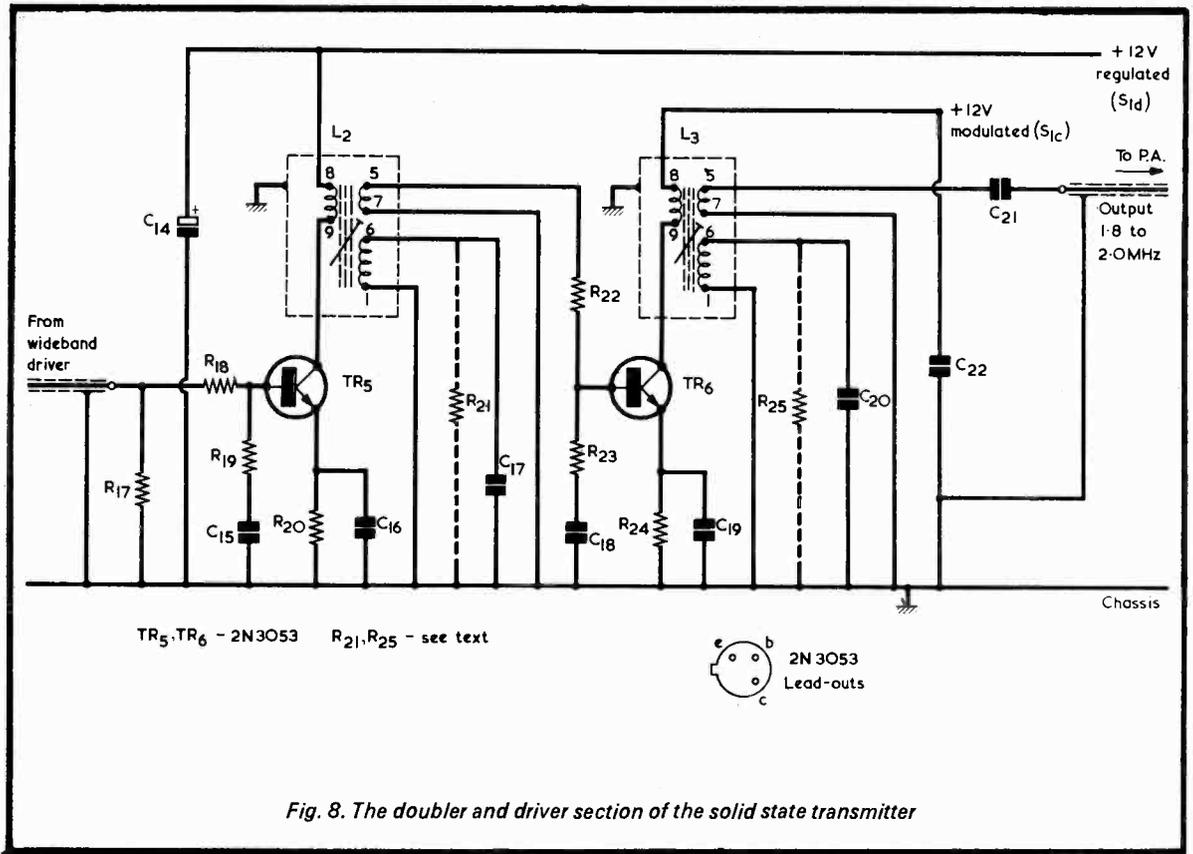


Fig. 8. The doubler and driver section of the solid state transmitter

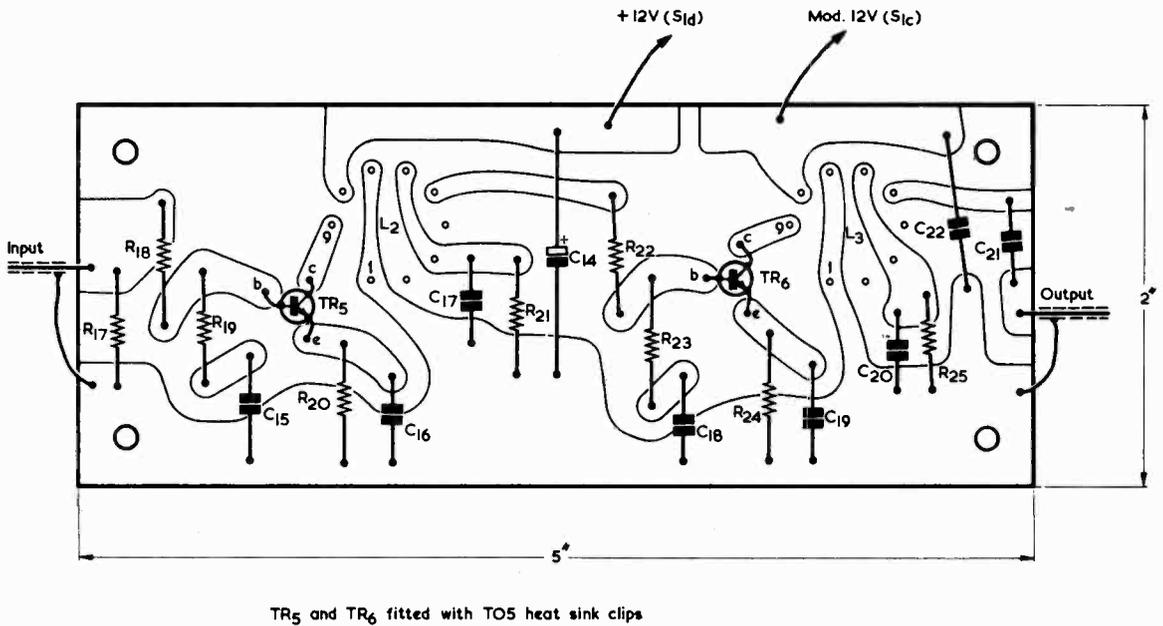


Fig. 9. Component side of the printed circuit board for the doubler and driver section

Multimeter Resistance

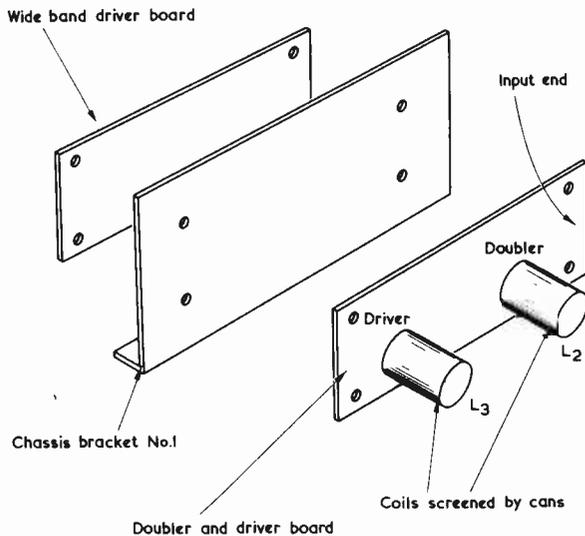


Fig. 10. The doubler and driver board is mounted on Chassis Bracket No. 1 on the opposite side to the wideband driver board

The pulses of current from TR4 in the wideband driver stage therefore switch TR5 at 900kHz to 1MHz, and this frequency is doubled by the tuning of L2. The pulses of current from L2 in turn switch TR6, which pulses L3 at 1.8 to 2.0MHz. The stage should provide approximately 500mW to 1W of drive.

The components R18, R19, C15, R22, R23 and C18 are included for stability. They prevent self-oscillation or the generation of parasitic oscillations.

Should the stage fail to provide sufficient drive, this may be increased by using two transistors in parallel for TR5 and TR6 and halving the value of resistors R20 and R24.

The printed circuit layout is shown in Fig.9, where it is reproduced full size and may be traced. The holes for the B9A coilholder tags are positioned only approximately in this diagram and they should be marked out on the board with the aid of the valveholders themselves. The view in Fig.9 is of the component side of the board. This results in the valveholder tags proceeding from 1 to 9 in an anti-clockwise direction.

A TO5 heat sink clip should be fitted to both TR5 and TR6.

The two coils are screened (as an additional precaution against instability) the screening cans being made from the cans in which the coils are supplied. Each can is cut down so that it does not foul components near the coils, and is fitted with a solder tag to enable it to connect to the copper section which is at chassis potential.

When completed, the board is fitted, using stand-off spacing washers, to the Chassis Bracket No.1 on the opposite side to the wideband driver board. The input end of the doubler board is at the rear of the bracket, adjacent to the output end of the wideband driver board. See Fig.10. The output of the wideband driver board is wired to the input of the doubler board.

(To be continued)

THE CIRCUIT TO BE DESCRIBED IS A SIMPLE EXTRA THAT can be added to a multi-testmeter having a 50 μ A direct current range. The circuit causes the input resistance to be boosted to valve voltmeter standards.

It must be pointed out that, since the two transistors employed in the circuit have a relatively wide gain spread and are operated at a low voltage, and since the testmeter input resistance may vary for different models of meter, the circuit has to be classed as experimental. It is possible that resistor values other than those specified here may be required in other units built up to the circuit, and construction should only be attempted

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt 5%)

R1	2M Ω
R2	5M Ω
R3	3M Ω
R4	10M Ω
R5	1M Ω
R6	1k Ω
R7	39k Ω
VR1	1.5k Ω potentiometer, skeleton
VR2	10k Ω potentiometer, wire-wound.

Transistors

TR1	BC169C
TR2	BC169C

Switches

S1(a)(b)	2 pole 3 way, rotary
S2(a)(b)	d.p.s.t., toggle

Batteries

B1	1.5 volt cell type HP7 (Ever Ready)
B2	1.5 volt cell type HP7 (Ever Ready)

Miscellaneous

4 insulated sockets
2 pointer knobs
Twin battery holder
Groupboard, case, etc.,

Input Booster

by M. N. Pointing and G. A. Miller

A simple experimental circuit which can enable a 20,000 ohms per volt testmeter to present a very high resistance to the circuit being checked.


by readers who appreciate the principles involved and are capable of making any adjustments to resistor values that may be required. The values quoted in the Components List are those used in the prototype. This was employed in conjunction with a 10,000 ohms per volt Japanese-made testmeter having the type number TE-200.

RANGES

The ranges offered by the prototype unit are 1 volt d.c. at 2M Ω input resistance, 2 volts d.c. at 7M Ω and

5 volts d.c. at 20M Ω input resistance. These were the ranges required by the authors but there is no reason why other higher voltage ranges could not be added by suitable alteration of the input resistors. The accuracy of the unit was found to be adequate for normal circuit checks.

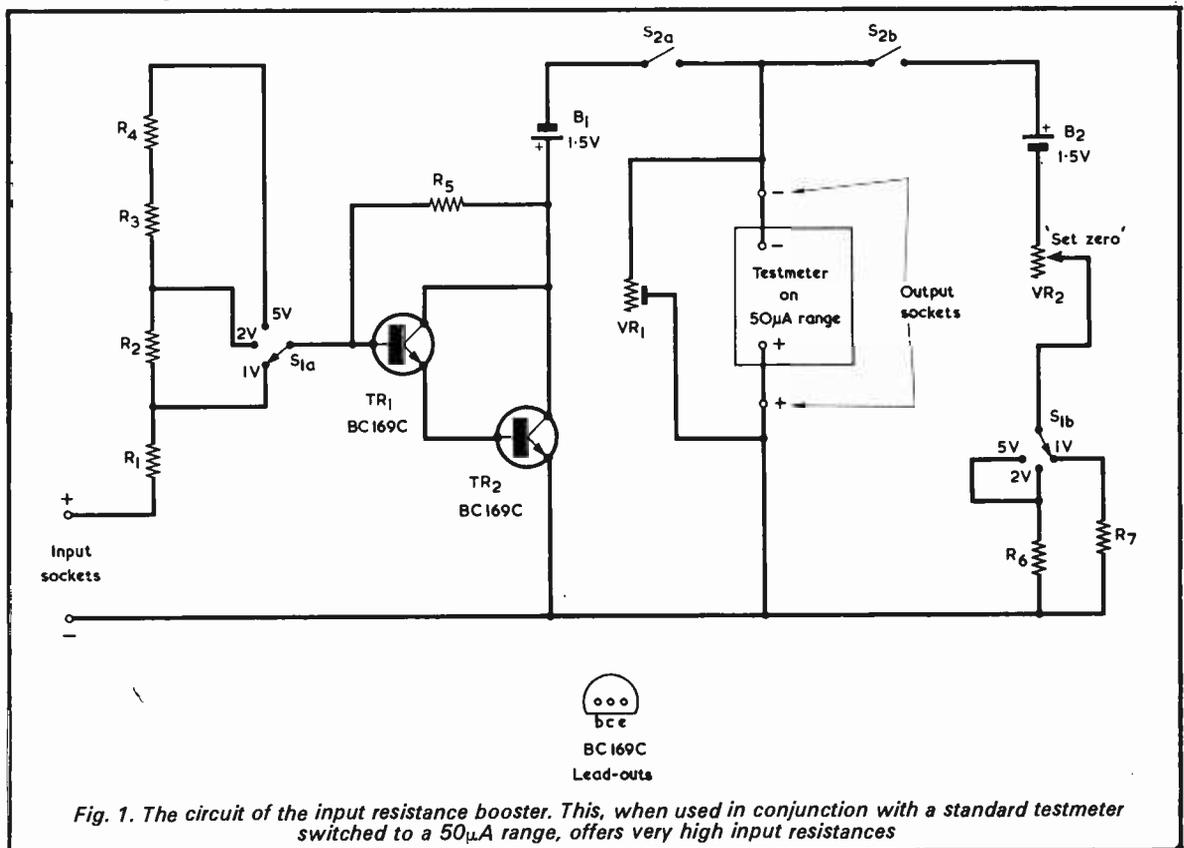The circuit is a greatly simplified version of that found in many commercial transistor voltmeters, and is shown in Fig. 1. Basically the meter, which is the multi-testmeter switched to read 50 μ A full-scale deflection and connected by its test leads to the unit, is driven by the high gain amplifier given by TR1 and TR2.



When a voltage is applied to the input sockets it causes a small current to flow through the input resistor and the base emitter circuits of TR1 and TR2. TR1 and TR2 are connected to form a Darlington pair, the gain of which is approximately equal to the product of the individual gains of the two transistors. As the maximum gain for a BC169C transistor is 900 it can be seen that the gain of the Darlington pair can be very high indeed. An amplified version of the current in the input circuit of the Darlington pair flows through the collector circuit and causes a corresponding deflection of the meter needle.

R5 is included to keep the transistors conducting as, otherwise, the input voltage would have to exceed that at which forward current flowed in the base-emitter junctions of the two transistors. Low input voltages, particularly on the 1 volt range, cause a reduction of the bias current available from R5. In practice, this effect is allowed for by zeroing the meter on each range with the input terminals short-circuited.

VR1 shunts the meter and is adjusted such that 1 volt, 2 volts and 5 volts cause full-scale deflection on the respective ranges. In the prototype, VR1 was a 1.5kΩ skeleton preset potentiometer. A 2kΩ or 2.5kΩ potentiometer could be employed instead if the 1.5kΩ value is difficult to obtain.

The transistor circuit is powered by the 1.5 volt cell, B1. A second 1.5 volt cell, B2, in company with VR2 and R6 or R7, supplies a current which cancels out the standing transistor current due to R5. VR2 is a panel-mounting wire-wound potentiometer and is adjusted for

a zero reading in the meter. R6 and R7 have values which assist in the accurate setting of VR2.

Resistors R1 to R4 are specified as 5% in the Components List. This tolerance should be close enough for most requirements and it may, in any case, be necessary to slightly adjust the values of one or more of the resistors during setting up. Small increases in value can be achieved by inserting lower value resistors in series.

CONSTRUCTION

Many of the components in the prototype were wired up on a small groupboard in the manner shown in Fig. 2. However, layout is not important and any other method of wiring could be employed. The groupboard was fitted in a small metal case, on the front panel of which were mounted S1, S2, VR2 and two pairs of insulated sockets. One pair of sockets provides the input connections and the other pair of sockets the output connections to the testmeter. The cells were fitted in a small twin battery holder.

SETTING UP

Setting up consists of adjusting VR1 so that the test meter gives the desired reading on each range. The 5 volt range can be set up with the aid of a 4.5 volt battery which has been previously checked by the testmeter. The 2 volt range may be similarly set up with the aid of a 1.5 volt cell. A setting up voltage for the 1 volt range can be obtained by connecting a potentiometer having

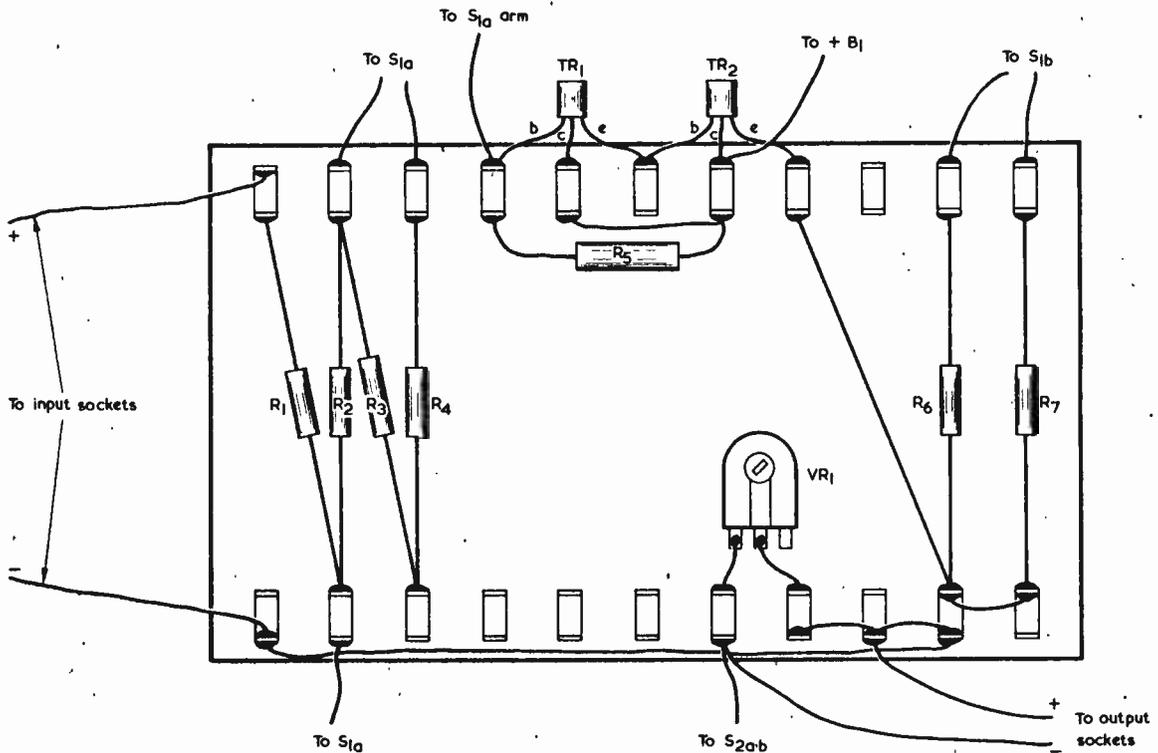


Fig. 2. In the prototype, some of the components were wired up on a groupboard, as shown here

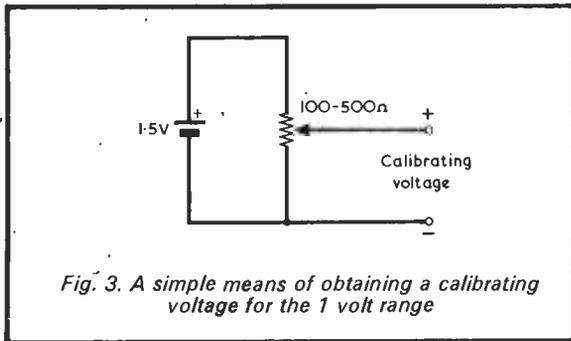


Fig. 3. A simple means of obtaining a calibrating voltage for the 1 volt range

a value between 100Ω and 500Ω across a 1.5 volt cell, as shown in Fig. 3. The potentiometer is previously set up so that 1 volt becomes available between the slider and one end, as measured with the testmeter.

Other sources of known voltage can also, of course, be used for setting up.

The guard against damage to the testmeter, when setting up, due to excessive current in the B1 or B2 circuits, the testmeter should be initially switched to a high current range, say 0-10mA, before turning the

unit on. The meter can then be subsequently set to the $50\mu\text{A}$ range if the current indication is sufficiently low. On each range the unit is zeroed by adjusting VR2 for a zero current indication with the input sockets short-circuited.

If it is found that a single setting of VR1 cannot be obtained for all three ranges, the values of R1 to R4 may be slightly adjusted as required.

USE

The unit is simple to use and is not dependent on any external power supply. The current drawn from the cells is low and these should have a long life.

To measure a voltage, the testmeter, switched to read $50\mu\text{A}$ f.s.d., is plugged into the two output terminals. The range selector switch, S1, is set to the appropriate range. Two test leads connected to the input terminals are then short-circuited together and VR2 is adjusted for a zero reading. The test leads are next applied to the points at which the voltage to be measured appears, and this voltage is read from the appropriate scale of the testmeter.

The unit must be zeroed by means of VR2 each time it is used and each time the range is changed. ■



THE WAY THINGS WORK.

591 pages, $5\frac{1}{2} \times 8\frac{1}{2}$ ins. Published by George Allen & Unwin Ltd. Price £3.65.

"The Way Things Work" is a follow-up of a volume which appeared in this country as "The Universal Encyclopedia of Machines", and it is stated to contain twice as many subjects as the previous work.

The method of presentation is unique. Wherever possible each subject dealt with is presented on a double-page of the book, diagrams being printed on the right-hand page and a concise text discussing the subject on the left-hand page. In most instances, single subjects are dealt with in their entirety on a double-page, but in some cases they have to be carried over from one double-page to the next. The diagrams are detailed and excellently drawn, and they are reproduced in black and red. For the section on colour television a full colour range is used.

The matters illustrated cover a fantastically wide range and include such diverse subjects as nuclear reactors, prospecting for minerals, road intersections and junctions, cartography, artificial hearts, vertical-take-off-and-landing aircraft, liquid-propellant rocket systems and many, many more. The majority fall into the mechanical category but enough subjects are of an electronic nature to justify a review on these pages. The electronic items include high fidelity, electronic music, wave guides, v.h.f. stereo broadcasting and video tape recording. Obviously, the matters dealt with cannot be given a full treatment, but the potted descriptions are extremely concise and accurate. They give more than adequate background to enable the reader to grasp how the device or function dealt with works, and thereby justify the title of the book. There are, also, no "simplifications" in the descriptions.

The book provides fascinating reading and instruction for anyone who is interested in the chemical, mechanical and electrical world around him, and it will in particular prove to be an excellent and educational present for a youngster in his teens.



INTRODUCTION TO SEMICONDUCTOR DEVICES. By F. J. Bailey, C.Eng., M.I.E.R.E.

238 pages, $5\frac{1}{2} \times 8\frac{1}{2}$ ins. Published by George Allen & Unwin Ltd. Price £3.95.

This book is intended to provide sufficient basic information on semiconductor devices to enable the student, engineer or technician to understand their operation and the manner in which they may be used. The approach is non-mathematical, although simple equations are given when these are essential.

The first chapter discusses basic semiconductor theory, and is followed by chapters on diodes and bipolar transistors. Next to be dealt with are junction field effect transistors, insulated gate field effect transistors and thyristors. The final chapter is devoted to integrated circuits, and this is succeeded by a glossary of the more important terms and the index.

Illustrations are clear and the text is concise and lucid. It is obvious that care has been taken to see that description of devices and their functioning are precise. The volume forms a good standard text-book and it can be read with profit by anyone who is embarking on the subject of semiconductors. The price quoted at the head of this notice is for the hard-back issue. A paperback version at lower cost is also available.

UNUSUAL TRANSFORMER EFFECT

by
A. L. Chivers

How to make a step-down transformer step up a voltage!

THERE ARE QUITE A FEW LITTLE MYSTERIES IN electronics and the author discussed one of these in this journal some time ago.* At that time, an experiment was described which demonstrated that the brilliance of an electric light bulb could vary by quite a considerable factor despite the fact that a moving-coil voltmeter connected across it showed no change in indication.

TRANSFORMER EXPERIMENT

Here's another experiment which the author recently carried out. He connected a $1,750\Omega$ 40 watt wire-wound resistor (actually a valve heater dropper resistor) in series with an m.e.s. pilot lamp having a nominal rating of 6.5 volts 0.15 amp. Connected across the lamp was an a.c. voltmeter with an f.s.d. of 10 volts, and the zero and 220 volt taps of the primary of a large mains transformer. The set-up is shown in Fig. 1 (a).

Next, the on-off switch was closed, whereupon the 240 volt a.c. mains was applied to the series combination of the bulb, with its parallel voltmeter and mains transformer winding, and the resistor. Now, a $1,750\Omega$ resistor passes 137mA when 240 volts is applied across it. In Fig. 1 (a) a current of slightly less than 137mA will flow, because of the voltage dropped across the lamp. In practice, when the on-off switch was closed the lamp became illuminated and the a.c. voltmeter indicated 4.7 volts.

So far, so good. These are reasonable results to expect in a circuit of this nature. The lamp and meter

were next disconnected from the 220 volt tap in the mains transformer primary and were then connected to the 240 volt tap, as in Fig. 1 (b). When the on-off switch was closed the lamp shone at *reduced* brilliance and the a.c. voltmeter indicated 3.9 volts only.

After this, the bulb and the a.c. voltmeter were transferred to the 200 volt tap, as illustrated in Fig. 1 (c). This time, when the on-off switch was closed the lamp shone much more brightly than on the two previous occasions and the a.c. voltmeter indicated 6 volts!


Pilot lamps are notorious for offering non-linear resistance, since the resistance of their filaments increases markedly with temperature. To ensure that this non-linear resistance was not confusing the issue, it was decided to repeat the experiment using a 30Ω 2 watt wire-wound resistor in place of the lamp. When the resistor was connected up to the 220 volt tap, as in the manner shown, with the bulb, in Fig. 1 (a), the a.c. voltmeter indicated 3.6 volts. The 30Ω resistor and meter were next connected to the 240 volt tap, following Fig. 1 (b), whereupon the meter reading dropped to 3.3 volts. Finally, the 30Ω resistor and meter were, as shown (with the bulb) in Fig. 1 (c), transferred to the 200 volt tap. The meter indication then rose to 4.3 volts.

EXPLANATION

This experiment can easily be repeated by readers, provided that the mains transformer employed has a primary whose wire is capable of passing 0.15 amp. The transformer used by the author had an h.t. secondary rated at 250-0-250 volts at 120mA, plus several 6.3 volt heater secondaries, and so the wire in its primary winding could well carry 0.15 amp. Due to auto-transformer action the wire between the zero and 220

RADIO & ELECTRONICS CONSTRUCTOR

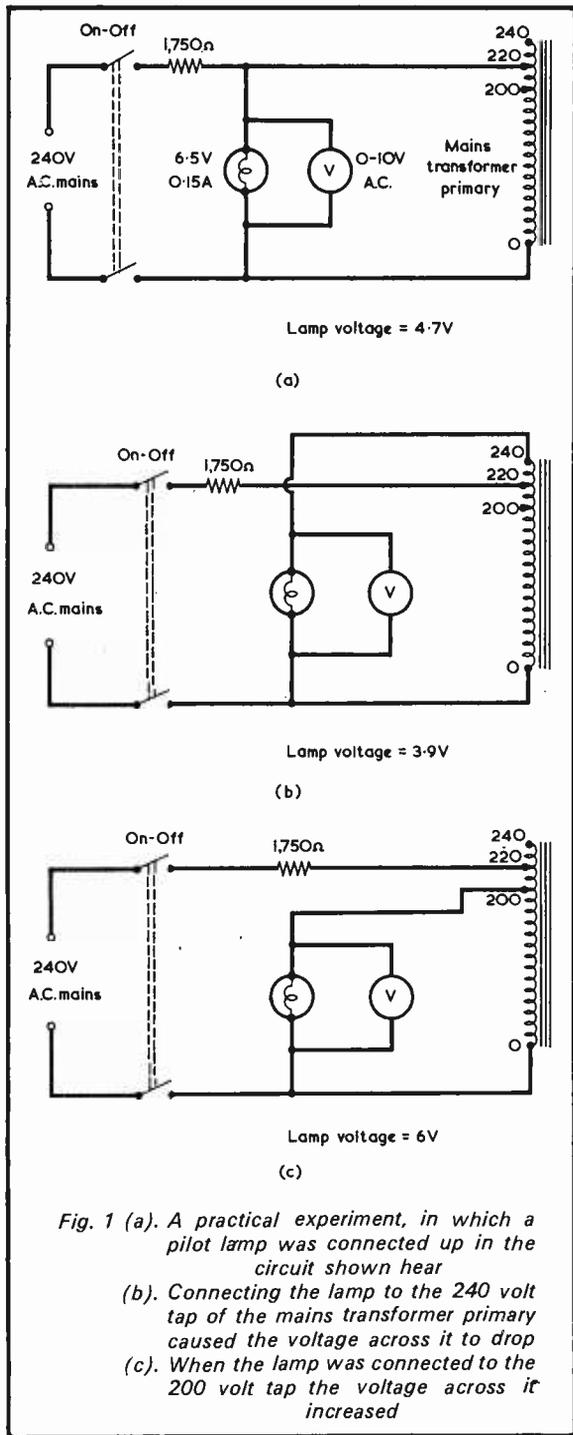*A. L. Chivers, 'A.C./D.C. Mystery Bulb', 'The Radio Constructor', August 1971.




volt taps in Fig. 1 (b), and between the zero and 200 volt taps in Fig. 1 (c), actually has to carry much less than 0.15 amp, but that's another story.

The experiment proves conclusively that it is possible to have both a step-up autotransformer which provides a step-down in voltage and a step-down autotransformer which provides a step-up in voltage! What is the cause of this unexpected behaviour?

The answer lies in the fact that the current available to the transformer winding in the experiment is limited to what is virtually a constant current by the 1,750 Ω series resistor. For small voltage changes at the transformer winding the current remains almost completely unaltered. When, in Fig. 1 (b), the bulb was connected to the 240 volt tap, the constant current still had to flow between the zero and 220 volt taps of the transformer primary. There was in consequence a step-down in current to the pilot lamp, whereupon less voltage appeared across it. In Fig. 1 (c) the bulb was connected to the 200 volt tap. The constant current once more flowed between the zero and 220 volt taps of the transformer winding, with a current step-up between the zero and 200 volt taps. The flow of increased current through the bulb resulted in an increased voltage across it. There were similar results with the 30 Ω resistor but, since this offers a resistance which does not alter with current, the changes in voltage were not so dramatic.

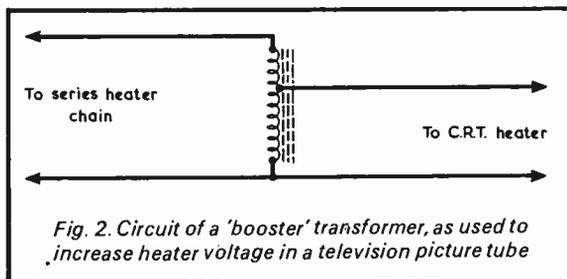Remember, a step-up transformer offers both a step-up in voltage and a step-down in current. And a step-down transformer offers both a step-down in voltage and a step-up in current. With the present experiment the current, being virtually constant, was the deciding factor and the small voltages which appeared at the transformer winding were of secondary performance.



This effect can be put to practical use in any a.c. circuit having a high value of series resistance, and it enables a greater current to flow in a low voltage resistive component than is actually passed by the series resistance. A typical example is given by the TV c.r.t. filament 'booster' transformers that are used to increase the heater voltage of ailing picture tubes when these are connected in a series heater chain. Such transformers are autotransformers and have the voltage step-down, current step-up, circuit shown in Fig. 2. ■

'Jubilee' 8-Watt Amplifier

In Fig. 1 of the above article, published in the August 1972 issue, the non-earthly end of R17 should connect to the upper terminal of the 6.3 volt 3.5 amp winding of the mains transformer. The correct connection is specified in the circuit and constructional descriptions.



Q

S

X

By
FRANK A. BALDWIN

(All Times GMT)

The reception of a rarely reported station on a new channel is always an event of some importance to the SWL, particularly when the channel in question is an 'out of band' frequency. Such an event occurred during early September when the writer was searching the area of the dial around the 4600 mark.

On the 9th of September, at 1930, on a measured 4627, a station was heard using Spanish announcements in addition to those in the Arabic language. Musical and song programmes of the Arabic type were featured. Reception conditions however were very poor, signal strength was low and utility QRM abounded, these precluding any definite and positive identification. Similar conditions prevailed for the next few evenings, although it was established that three separate trumpet fanfares were often used between programme items.

On the 13th September however, conditions were good and the clear identification "Radio Sahara" was taped. Previously, a landline contact with Alan B. Thompson of Neath had resulted in his equipment being brought into use on the channel – the result was therefore doubly confirmed at one and the same time.

Radio Sahara previously operated on the crowded 7MHz band and was only rarely heard here in the U.K. and even then only for very brief periods. It was known that the station was looking for a clear channel but nobody in the SWL world thought it would suddenly appear on 4627, least of all the writer.

At 2000 there is a newscast in vernacular, probably Hassania; into Spanish at 2010; identification at 2015 then Arabic style music. Three fanfares are heard prior to the news at 2000. At 2110 there is a news review in Spanish to 2130. Prior to the 2158 sign-off, there is a four-note interval signal, identification in Spanish, 'Muy buenos noches' and a short National Anthem. The address for reports is – Radio Sahara, Apartado 7, El Aaiun, Spanish Sahara – although I think you will be rather lucky if any reply is received! The Hassania language, according to my information, is a mixture of Spanish and Arabic.

258

● THE CUROM AFFAIR

Earlier this year (May) reports appeared in the SWL press of Radio Curom in the Netherlands Antilles broadcasting on 20778 and later on 17513 (on the latter channel from 1500 to 0400 over a period of some days, although the frequency was said to vary at times).

A regular reader of this feature, E. Sloan of Belfast, logged the transmission on 20779 and duly reported this fact to R. Curom. In the reply, a station official confirmed that the reception details were correct but then added 'we never broadcast on short waves but on 855kHz only.' It transpires, from the information provided by reader E.S., that Curom rent a transmitter from the Government and 20634 is the frequency of their direct link to Holland via a three-channel telephone transmission. The letter added 'The last stage is modulating the signal on 1000kHz with an oscillator on 21634. Due to false tuning of the modulation stage we got a mixing of 21634 and 855, giving 20779 of sufficient strength to be heard in Europe'. What about the 17513 however?

● UNIDENTIFIED

Always of interest to many SWL's, perhaps some readers may care to tune to 4220 around 2030 or so. The channel is a difficult one with a continuous unmodulated carrier often on the air and marring reception. Recently at 2040 we heard a programme of music and songs in the Russian language. One well-known SWL has suggested that this might be Peking using the Urumchi transmitter for the Russian Service but, according to BADX, an unidentified Russian station, Peking and Urumchi are listed as occupying the channel with the latter transmitter signing-on in Kazakh at 2340. Tune your dial and take your choice!

● ANGOLA

Angolan stations are always of interest and the low-powered (1kW) CR6RB Radio Ecclesia can be heard, if conditions are right, on 4985, where we recently logged it at 1925 with a talk in Portuguese. Based in Luanda, the station radiates programmes having a mainly religious content.

● SUPER DX

Reportedly one of the best Papua/New Guinea outlets for signal strength is Radio Milne Bay on 3360 with a 10kW transmitter (ex-3235). Sign-on with morning service is at 1945 and the channel is usually a clear one, all according to BADX. Listen out for VL8AS and that super Dx!

● LATIN AMERICA

Latin American stations are always of interest and in any list the Venezuelans usually predominate – ours is no exception.


- 4765 0020 ZYN37 Feira de Santana, Brazil, with station identification and LA music. Schedule from 0730 to 0400, 1kW (62.96m).
- 4790 0018 YVON Ondas Portenas, Puerto La Cruz, Venezuela, programme of local music and songs. Schedule from 1000 to 0300, 1kW (62.63m).
- 4825 2250 HIFA Voz de la Fuerzas Armadas, Santo Domingo, Dominican Republic, with local guitar music and songs. Schedule 1200 to 0500, 3kW (62.17m).
- 4870 0010 YVKP Radio Tropical, Caracas, Venezuela, with a newscast in Spanish. Schedule 1000 to 0400, 5kW (61.60m).
- 4890 0100 YVKB Radio Dif, Caracas, Venezuela, identification followed by the inevitable LA music. Schedule 1000 to 0400, 5kW (61.35m).
- 4905 2125 ZYZ20 Radio Relogio, Rio, Brazil, talk in Portuguese, time checks of 3 'pips' every minute, short musical interludes. Schedule 24 hours, 5kW (61.16m).
- 4940 0010 YVPA Radio Yaracuy, San Felipe, Venezuela, Organ music and commercials with echo-effect. Schedule 1000 to 0400, 10kW (60.72m).
- 4980 0102 YVOC Ecos del Torbes, San Cristobal, Venezuela, announcements in Spanish after identification. Schedule not published, 10kW (60.24m).
- 5010 0030 HIMI Radio Cristal, Santo Domingo, Dominican Republic, with LA songs rendered by young lady with a most charming voice. Schedule 24 hour, 1kW (59.88m).
- 15155 2242 ZYB9 Radio Dif. de Sao Paulo, Brazil, with station identification, announcements with echo-effect followed by LA music (without echo-effect). Schedule 1500 to 0300, 10kW (19.79m). ■

RADIO & ELECTRONICS CONSTRUCTOR

NEW RS303 TUNER AMPLIFIER AND RW346PE STEREO RECORD PLAYER FROM SIEMENS

The combination of the new RS303 four band tuner amplifier and the RW346PE Stereo record player from Siemens is launched by Interconti Electronics Ltd., Albany House, Petty France, London SW1. Shown here with two spherical and two cubic loudspeakers this unit provides the discerning hi-fi enthusiast with a truly advanced sound system.

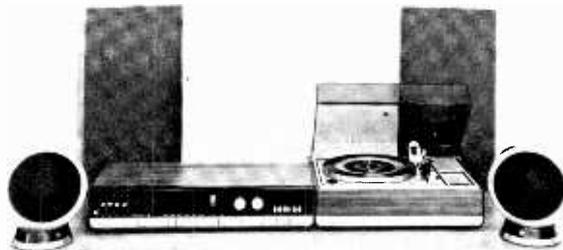Also available within the Siemens range is a wide selection of alternative speakers matched for this system.



PRECISION FLEXIBLE COAXIAL CABLE



The Solidev Ltd. Plaxial coaxial cable showing the stranded centre conductor, the helical grooved dielectric, the electro-deposited outer conductor, the jacket and the braided protective sleeving.


Plaxial coaxial cable is claimed by Solidev Ltd. to be the only precision flexible coaxial cable that provides 100% r.f. shielding with no degradation of attenuation

of v.s.w.r. even with minimum radius bends of $\frac{1}{8}$ in. The manufacturing method provides the inherent flexibility advantages because the dielectric material covering the inner conductor is formed with a continuous helical groove. The outer conductor is electrodeposited copper (0.001 in) which follows the contours of the helical groove. This is covered by an irradiated polythene jacket; with an extra braided protective sleeving over a t.f.e./f.e.p. jacket. The centre conductor is formed in stranded copper wire. This method of construction enables cable harnesses to be made with constant, reproducible, electrical characteristics and permits interchanging of harness between systems without mismatch. The cable has a mechanical performance equivalent to semi-rigid cables but can, in addition, withstand many thousand of flexures without breaking. The cable can be used with either straight through or right angle connectors, without degradation of v.s.w.r. because the cable itself is flexed to provide even a $\frac{1}{8}$ in minimum bend radius right angle without using separately machined parts. The shielding is effective up to 18GHz, and the attenuation is less than 2dB/100ft at 10MHz and less than 90dB/100ft at 100GHz. The temperature limits for the RG371 are -55°C . to $+90^{\circ}\text{C}$. and for the type RG398 they are -65°C . to $+125^{\circ}\text{C}$. For further information: Solidev Ltd., Tubs Hill House, North Entrance, London Road, Sevenoaks, Kent.


PRACTICAL LOW-COST POCKET MULTIMETER

A new pocket multimeter, the MX001A, has been introduced by ITT Metrix and is available in Britain from ITT Components Group Europe. Priced at £12.75 the MX001A is attractively styled with a shock-resistant plastic case. The MX001A can measure voltages up to 160 V d.c. and 500 V and 160 CV on separate sockets with a sensitivity of 20,000 ohm/V; up to 500 V a.c. with 1600 V on a separate socket; and currents up to 500 mA d.c. (5A on separate socket) and 1.6 A a.c. Resistances up to 5 megohm can also be measured. Weighing only 400 g, the MX001A is fully protected against overload by both fuse and diodes. It employs a moving coil movement with a high flux central magnet with minimal flux leakage. Range selection is by a thumbwheel switch, with the range selected being shown at a window below the scale. A full range of accessories is available including a filter probe for t.v. line voltage measurements, 15 kV a.c./d.c. probe, 30 kV d.c. probe, range multiplier resistor box (3000 to 6000 V a.c./d.c.) and an adaptor for resistance measurements from 20 kilohm to 50 megohm. In addition a carrying case and rubber shock protector are available. For further information contact ITT Components Group Europe, Instrument Sales, Edinburgh Way, Harlow, Essex.

NOVEMBER 1972

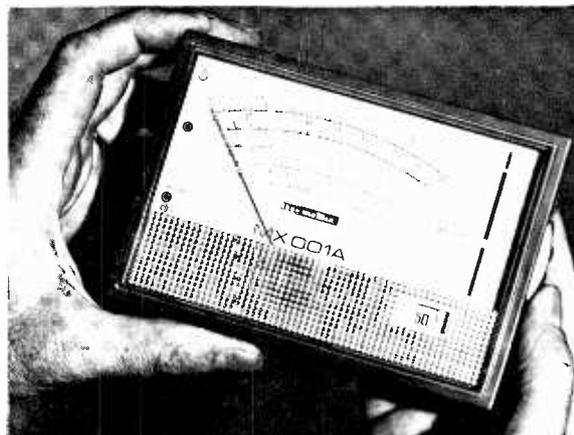

HIGH-SPEED TRAIN COMMUNICATIONS

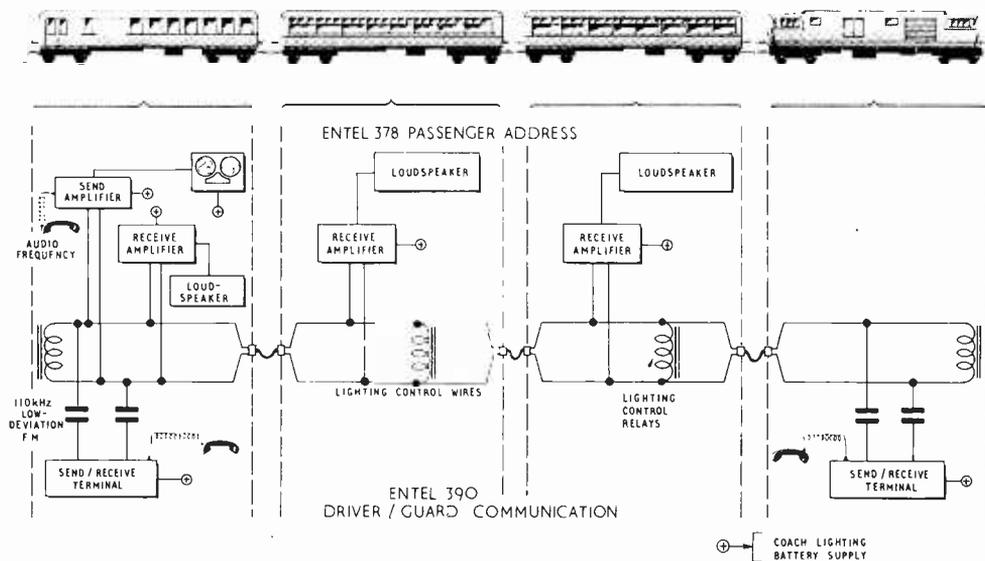

The plans of the British Rail Board for high-speed trains travelling at up to 150 m.p.h. have raised the acute necessity of improving communications between drivers and guards. There is, additionally, a demand for passengers to be kept informed of the progress of the journey, times of meal sittings and the like.

With this in mind, Nelson Tansley Limited, of 10 Shepherds Bush Road, London, W.6., who have already built up an excellent reputation in railway communications, have produced a range of equipment under the generic name "ENTEL" to fulfil the new requirements. Driver-guard communication sets and passenger address equipment are two separate systems designated ENTEL 390 and ENTEL 378 respectively. The accompanying diagram illustrates both systems, the top section being concerned with passenger address equipment, while the lower section shows the ENTEL 390 driver-guard communication system.

The main problem that Nelson Tansley engineers had to overcome in the development of the systems was the impossibility of providing a special cable, running the length of the train, on which the signals could be carried. The equipment was therefore designed to take advantage of any continuous circuit already in existence. Since the control wires for the lighting relays are, in British Rail, the only conductors which are always coupled throughout a passenger train, these were employed for the communications systems. In this case, departure from the ideal of a 600Ω noise-free line is caused chiefly by the connection across the wires of a large number of relay solenoids, the impedance of which is not only complex, but variable.

ENTEL 378

The passenger address system, ENTEL 378, consists of a "Send" amplifier driving "Receive" amplifiers and loudspeakers in each coach. The terminal impedances of the amplifiers are tailored to suit the complex impedance of the line, and the audio frequency signal is transmitted at a high level (10 volts at 1 kHz for a rated 10 watts output to the loudspeakers) to reduce the effects of superimposed noise. Further noise reduction is obtained by the use of a curtailed bandwidth of 300 to 5,000 Hz. The system is operated by the guard, who is provided with a telephone hand-set. Announcements recorded on tape may also be made.

ENTEL 390

Designed solely for two-way voice communication between driver and guard, ENTEL 390 is capacitively coupled to the same pair of wires as the passenger address system, but the signal is transmitted on a low-deviation frequency-modulated carrier at around 110 kHz. Although well above frequencies used for train-control signals, this frequency is not yet so high as to require excessive attention to matching and attenuation problems. A "Send-Receive" terminal is located in the driver's cab (or cabs, if more than one locomotive is in use) and in as many guard's compartments of the train as required. Each terminal is provided with a hand-set having a "Press-to-Talk" button and a bulkhead-mounted electronics panel. The hand-set emits a call tone when a remote call button is pressed, the call being acknowledged by lifting the hand-set and pressing the "Talk" button. Simultaneous operation of "Talk" buttons gives duplex operation of the system, with a side tone caused by the heterodyne beat between the two carriers, which differs in frequency by a few hundred hertz. The tone helps to discourage indiscriminate talking-through which, it is felt, could result in vital information being misheard.

Solid-state electronics are used in all control and signal circuits of both ENTEL 378 and ENTEL 390, and all equipment has been thoroughly tested and approved by the British Rail Board for incorporation in the modern stock now coming into operation.

In your Workshop -shop

WITH THE PROFESSIONAL AIR OF A Cordon Bleu master-chef putting the final touch to his *potage a la tortue*, Dick carefully inserted two tea-bags into the Workshop tea-pot. The battered kettle alongside the sink had just commenced to sing and Dick waited expectantly for it to burst into full voice. After a short period, steam started to jet from the kettle whistle, which spluttered into a series of intermittent high pitched chirps. These soon merged into a continuous note until, eventually, the kettle was producing its full shrill pipe. Satisfied that the water in the kettle had reached an acceptable 100°C, Dick picked it up, removed its whistle, and poured its contents into the tea-pot.

He next put milk into his cup and into Smithy's disreputable tin mug then, after allowing a decent interval for the brewing of the tea, filled both these vessels with the health-giving infusion. Walking over to Smithy's bench he placed the Serviceman's mug alongside him then retired to his own bench with the cup.

A cold and blustery November wind blew flurries of rain against the windows. It was, that afternoon, very cosy inside the Workshop.

A TO Z

Smithy sipped his tea approvingly. "These tea-bags," he remarked, "aren't too bad after all, are they?"

"They're just the job," affirmed Dick warmly. "There's no more bother with the sink getting blocked up now, not since we changed over to using them instead of ordinary tea. We hardly ever have to use the plunger at all these days."

NOVEMBER 1972

A quiet spell in the Workshop enables both Dick and Smithy to enjoy an elongated tea-break. It also allows them to test each other's knowledge (and the reader's) over a wide range of electronic topics having initial letters which cover the alphabet from A to Z.

"Good, good."

The atmosphere, was redolent with the self-satisfaction of practical men who have, at a stroke, eradicated a problem of exceptionally long standing.

Dick drank quickly at his cup.

"You've no need to hurry," remarked Smithy comfortably. "There's hardly any work left to do today, and so we can have a good long tea-break."

"Fair enough," said Dick carelessly. "Still we ought to do *something* with the time."

An idea struck him.

"I tell you what," he continued keenly. "Let's have another go at the A to Z game! It must be more than a year since we last played it!"

"D'you mean the game where we go through the alphabet alternately?"

"That's right. We think of something in electronics which starts with each letter in order and then ask the other one what it is. The idea is to get a subject which catches the other one out. I'll start off with A."

"Very well then" replied Smithy indulgently. "You ask me something which begins with A."

"Right," said Dick briskly, as he creased his brow in concentration. "Now here's a good one to begin with. What does the word 'aperiodic' mean?"

"It's a rather loose term," replied Smithy promptly, "which is applied to untuned amplifiers or to the couplings between stages in such amplifiers. An ordinary a.f. amplifier does not have any resonant circuits which would cause it to offer a peak at a particular frequency, and so you can refer to it as being an aperiodic amplifier or as being an amplifier having aperiodic couplings between its stages. You very often have aperiodic r.f. amplifiers, too. For instance, the first stage in a radio receiver can be untuned, whereupon it amplifies all the signals picked up by the aerial and passes these on to the next stage, which is tuned. This first stage is called an aperiodic r.f. amplifier."

"Blow me," remarked Dick, somewhat crestfallen, "you certainly had your answer pat on that one."

"Not to worry, lad," replied Smithy comfortingly. "It's my go now, with B. Tell me, Dick, what is a biradial tip?"

"A biradial tip? Blimey, I've never heard of it before. Can you give me a clue?"

"You encounter it," Smithy prompted him, "in record player pick-ups."

"Do you?" said Dick slowly. "Then I suppose it must have something to do with the stylus. Would it be the same as an elliptical stylus tip?"

"You've got it right first go," commended Smithy. "A biradial or elliptical stylus tip has an outline which isn't round but which is in the form of an ellipse. The major axis of the ellipse, that is to say the longer axis, goes across the record groove and is sufficiently wide to prevent the stylus descending to the groove bottom, where ingrained particles of dirt are liable to introduce noise in the pick-up output. The minor axis of the ellipse is in line with the record groove and it allows the tip to present an arc of a circle of relatively small radius to the groove walls, whereupon the stylus is more readily capable of following high frequency modulation in the groove. Typical dimensions for a biradial stylus tip are 0.0007 inch radius for the curvature across the record groove and 0.0003 inch radius for the curvature against the groove wall." (Fig. 1).

"Well," said Dick complacently. "I gave you the right answer, didn't I?"

"You did, indeed," affirmed Smithy. "It's your turn now, with C."

"All right," replied Dick. "What's 'cryogenics'?"

"Cryogenics?" repeated Smithy. "Blimey, where did you dig that one out of?"

"I read about it in a science journal."

"It looks," stated Smithy thoughtfully, "as though I'll have to do a bit of guesswork here. Now, the prefix 'cryo' seems to be applied to things concerned with low temperatures, and

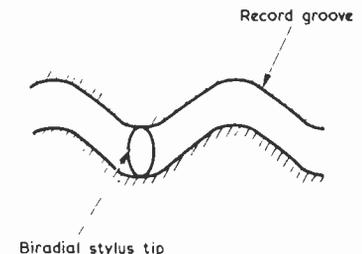


Fig. 1. Illustrating, in simplified form, the operation of a biradial or elliptical pick-up stylus tip

Your Local Supplier

LONDON

Established 1910

H. L. SMITH & CO. LTD.

Comprehensive stocks of
components by
all leading makers

287-9 EDGWARE ROAD
LONDON W2 1BE

Tel: 01-723 5891

THE MODERN BOOK CO.

Largest selection of English &
American radio and technical
books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP

Tel: 01-723 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS

LONDON, W.10

Tel: 01-969 3657

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.

70-72 Holdenhurst Road

Bournemouth

Telephone 25232

particularly with temperatures near absolute zero. I'll make a guess and say that 'cryogenics' is a science which has to do with materials maintained at temperatures near absolute zero."

"Darn it," said Dick irritably, "you're dead right, too."

"Good show," commented Smithy, cheerfully. "Now it's my turn. What's a decade?"

"That one's easy," replied Dick confidently. "In electronics it's the spacing between two frequencies which have a ratio of 10 to 1. The term is used also for the case where resistance and capacitance values go up in multiples of 10. Right, it's me now. What's an Esaki diode?"

"It's the same as a tunnel diode. What's 'fan-out'?"

"I think I know that one," replied Dick hesitantly. "Do you get it in logic circuits?"

"You do," confirmed Smithy.

"Then," replied Dick, emboldened, "it's the number of following gate inputs that a gate output can drive."

"That's correct," confirmed Smithy. "If a gate is said to have a fan-out of 10, that means it can drive up to 10 subsequent gates but no more."

GROUND WAVE

"Fair enough," commented Dick. "Well, we're now up to G, and it's my turn."

There was silence for some moments. "Come on," grumbled Smithy impatiently. "I can think of lots of things beginning with G."

"That's the trouble," wailed Dick. "So can I! But they're all simple things like 'grid' and 'gain' and 'ground'. Hang on a jiff though, that gives me an idea! What's a ground wave?"

"That is a good one," said Smithy. "If you did but know it, ground waves represent one of the most complicated subjects going in electronics, and that's despite the fact that they were known about from the early days of broadcasting. When a transmitter sends out a signal, this can pass to the receiver over a number of routes. The signals in the different routes are referred to as tropospheric waves, ionospheric waves and ground waves. Tropospheric waves appear above 50MHz or so and are carried around the curvature of the earth due to refraction in the atmosphere. Ionospheric waves are those which are reflected back to the earth again by the ionosphere, and these fall within the frequencies from just below 1MHz up to around 60MHz or more. The ground wave comes into play at frequencies below some 2.5MHz and it consists mainly of a wave which follows the curvature of the earth, thereby allowing the signal to be taken some way beyond the transmitter aerial horizon. The ground wave can be split up into two components, one being the surface wave,

which tends to hug the earth's curvature, and the other being the space wave. The space wave can, in turn, itself be subdivided into the direct wave and the reflected wave. The first of these is a direct wave from the transmitter aerial to the receiver aerial and the second is a wave reflected from the surface of the earth. Some of the complications I mentioned just now are caused by the fact that surface wave dissemination varies according to the nature of the surface over which it passes, conditions being best over sea water and worst over land with low electrical conductivity." (Fig. 2).

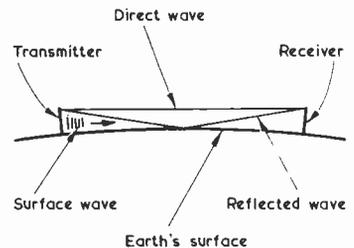


Fig. 2. The component parts of a ground wave. Only the start of the surface wave is shown; this extends to the receiver and beyond

"Well, that explains ground waves well enough for me," commented Dick. "Also, they've got me safely past the letter G! It's your turn now, Smithy, with H."

"I've got a good one here," said Smithy. "What's Hartley's Law?"

"Is it anything to do with oscillators?"

"Nothing whatever."

"Or jamming?"

Smithy threw an irritated glance at his assistant.

"Hartley's Law," he pronounced firmly, "is a fundamental law of communications and it states that the product of the time and bandwidth necessary for the transmission of a given amount of information is a constant. This assumes that the information is sent in a form which utilises bandwidth in the most economical manner possible."

"That sounds interesting," said Dick. "What it means, then, is that bandwidth goes up as the quantity of information rises. There's far more information in a television signal than there is in an a.m. sound signal, which explains why a television channel is about 8MHz wide whilst an a.m. sound broadcasting channel need only be, say, 8kHz wide."

"Exactly," confirmed Smithy. "It's almost always desirable to keep bandwidth down and in radio transmission this can be done by making economical use of the sidebands involved. A simple illustration of bandwidth reduc-

tion is given by the use in TV transmissions of a system in which nearly all of one sideband is suppressed."

"It's nice," commented Dick, "to hear of one law that's being obeyed. What's the next letter?"

"It's I," stated Smithy, "and it's you to go."

"That sounds a bit Irish to me," grinned Dick, "but I get your meaning. Okay then, what's an igfet?"

"It's an insulated gate field effect transistor," said Smithy. "The gate is insulated from the channel between the source and the drain by a very thin layer of silicon oxide and it has an extremely high input resistance. Right now! J is next, so let's see what I can dream up for you."

Smithy took a large draught of tea from his mug and thought for a moment.

"Ah, yes," he remarked. "I'll return the compliment to you and ask you what a jugfet is."

"That's easy," replied Dick. "That's a junction gate f.e.t. It's the more common type which doesn't have an insulated gate."

Smithy's assistant pondered for a moment.

"And now let me ask you one beginning with K. What's 'keystone distortion'?"

"It's distortion of the picture shape on a TV tube screen," said Smithy. "And it describes the case where the top is wider than the bottom, as occurs in the keystone of an arch. It's a form of trapezium distortion and the latter term applies to any case where two sides of the picture are parallel and two are not. Picture distortion of this nature is normally caused by short-comings in deflector coil performance." (Figs. 3(a) and (b).)

LOAD LINE

Smithy took a further large draught from his mug.

"The letter L is next," he remarked. "So you tell me what you know about load lines."

Dick's face fell.


"I thought things were getting a bit too easy," he sighed. "All I know about load lines is that you use them in some mysterious way with the characteristic curves for valves or transistors. But as to how exactly they are used, I just haven't got a clue."

"It's quite easy to employ load lines," replied Smithy. "I think you'd better come over here and I'll give you an example of how you draw up a load line for a resistive load."


As Dick walked over to Smithy's bench, that worthy proceeded to take a book of valve data from a drawer.

"I'll show you how to draw a load line on top of a family of valve characteristic curves," resumed the Serviceman.

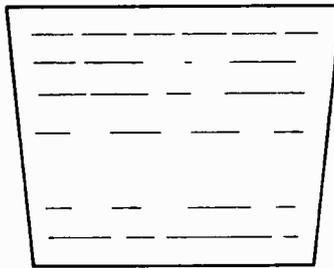"I'm using valve characteristics because the technique can be demonstrated a



(a)

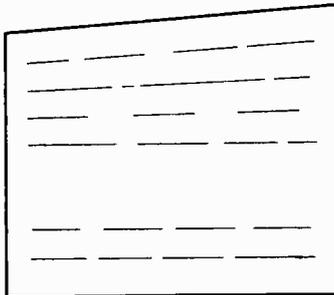

(b)

Fig. 3(a). Keystone picture shape distortion
(b) Trapezium distortion applies to any case where two sides of the television picture are not parallel

little more easily with these than with transistor curves."

Smithy opened the valve book and selected a page which illustrated the Ia/Va curves for one section of the double-triode type 12AX7. (Fig. 4(a).)

"As you can see," he went on, "I've chosen a 12AX7 triode for this little exercise, but any other amplifier valve would have done just as well. The characteristic curves we work with are those for anode current against anode voltage. As you can see, each of the curves corresponds to a particular grid voltage, this being with respect to the cathode of the triode."

Smithy indicated the individual curves to his assistant.

"This is all okay up to now," put in Dick. "Keep on, Smithy!"

"Right-ho," said Smithy. "Now, the function of the load line we are going to add is to define the performance of the valve when it has a particular value of anode load resistor and there is a particular value of h.t. voltage. Let's say that we're going to use an anode load resistor of 100kΩ and that the h.t. supply voltage is 250. After we have drawn the load line, this will indicate the anode voltage at any anode current under these conditions. There

Your Local Supplier

SURREY

WITWORTH TRANSFORMERS

TV Line out-put transformers

Manufacturers of the largest range in the country. All makes supplied.

Free catalogue.

Modern

BAIRD, BUSH, GEC, PHILIPS

Replacement types ex-stock.

For "By-return" service, contact London 01-948 3702

Tidman Mail Order Ltd., Dept. R.C.

236 Sandycroft Road,

Richmond, Surrey TW9 2EQ

Valves, Tubes, Condensers, Resistors, Rectifiers and Frame out-put Transformers.

Mains Transformers also stocked.

Callers welcome.

SUSSEX

E. JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

YORKSHIRE

WILSIC ELECTRONICS LTD.

Your local supplier for
EAGLE PRODUCTS,
CYBERNAT MOTORING AIDS
WILSIC HI-FI, MUSICAL
EQUIPMENT, KITS, AND
COMPONENTS

OUR CATALOGUE FREE

Postage 5p

Eagle Products Catalogue

Postage 5p

6 COPLEY ROAD

DONCASTER

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS
RADIO & TELEVISION

For the convenience of Irish
enthusiasts we supply

The Radio Constructor

Data Books and

Panel-Signs Transfers

Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

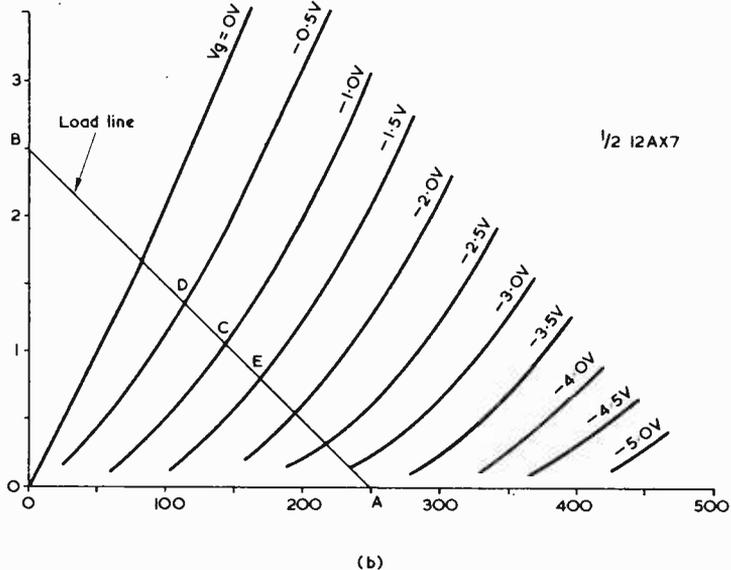
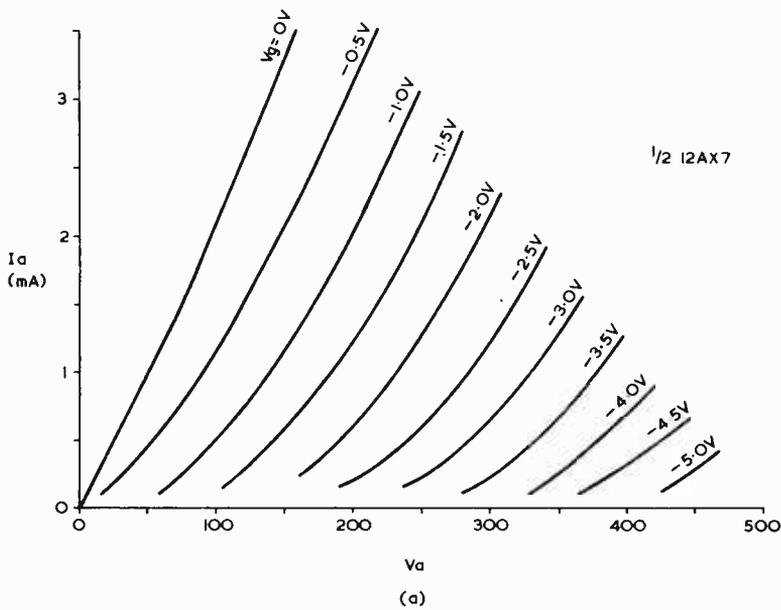


Fig. 4(a). Anode current-anode voltage curves for one section of a valve type 12AX7
 (b). Adding a load line corresponding to an anode load resistor of 100kΩ and an h.t. voltage of 250 volts

are two points for the load line which we can mark in straight away, these corresponding to zero anode current and to zero anode voltage."

"You can't," interrupted Dick, "have zero anode voltage in a triode. There's bound to be some voltage between the anode and the cathode."

"I know there is," retorted Smithy, a little testily. "If you'd let me continue my explanation I would have been able to say that the zero anode voltage

point was a theoretical one. Now, let's get on. When the anode current is zero the anode voltage becomes 250, because no voltage is dropped across the 100kΩ resistor. We can mark in the corresponding point on the curves graph as point A. If the anode voltage is zero then the full 250 volts is dropped across the 100kΩ resistor, resulting in an anode current of 2.5mA. This gives us point B. All that we now have to do is to draw a straight line between

the two points. That straight line is the load line for 100kΩ anode load and 250 volts h.t., and it defines the anode voltage for any anode current.

Working from the line you can see, for example, that 1mA of anode current corresponds to an anode voltage of 150. This ties in with fact, because an anode current of 1mA would cause 100 volts to be dropped in the load resistor."

Smithy showed Dick the graph, complete with its load line. (Fig. 4(b).) Dick looked at it blankly.

"So where do we go from here?" "Dash it all, boy, can't you see?" said Smithy irritably. "With 250 volts h.t. and an anode load of 100kΩ, the anode voltage must *always* fall on the load line at the point which corresponds to the anode current it passes. What we are now also capable of finding is the anode voltage at different grid voltages. These are the points where the grid voltage curves cut the load line. For instance, the 1 volt negative grid voltage curve cuts the load line at point C, and those for 0.5 volt and 1.5 volts negative at D and E."

Smithy inserted the letters. "Point C," he went on, "corresponds to 140 volts on the anode, point D to 115 volts on the anode, and point E to 165 volts on the anode. This means that if we bias the valve at 1 volt negative and then apply a signal with a value of 0.5 volt peak, or 1 volt peak-to-peak, the anode voltage will swing down to 115 volts on one set of half-cycles and swing up to 165 volts on the other set of half-cycles. Thus, we find that the output signal has a peak-to-peak value of 50 volts, which means that the valve offers a voltage gain, under the conditions which the load line represents, of 50 times. Also since, in this instance, the swings of anode voltage on either side of the central figure are equal, we can assume that any distortion introduced in the process of amplification should be quite low."

"Stap me," exclaimed Dick. "I can see what you're getting at now! With this load line idea you can find the performance of the valve for *any* value of anode load resistor and for *any* h.t. voltage."

"Exactly," agreed Smithy. "To draw the load line you first of all mark off the h.t. voltage at the zero current point. You then mark off the anode current point at the current which would flow if the full h.t. voltage were applied across the anode load resistor. Join the two points with a straight line and you've got the load line. This will tell you the anode voltage at any of the grid voltages for which curves have been drawn in. You can do just the same thing with a family of transistor collector current and collector voltage curves representing operation in common emitter. With transistors, V_{cc} takes the place of the h.t. voltage. Anyway, that's enough of load lines, so let's get on to the letter M. And it's

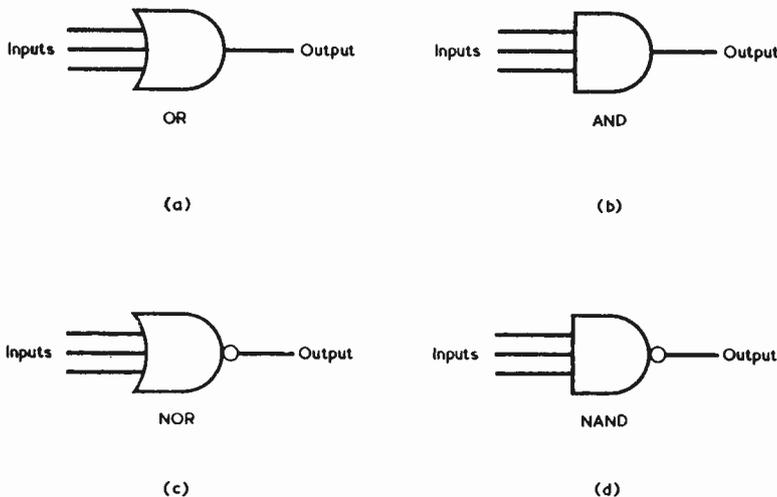


Fig. 5. Circuit symbol for (a) an OR gate, (b) an AND gate, (c) a NOR gate and (d) a NAND gate. Three inputs are shown, but the gates may alternatively have two inputs or more than three inputs

your turn."

Dick turned his thoughts away from load lines and concentrated.

"All right," he said, "what's a myriawatt?"

Myria, myria," repeated Smithy reflectively. "Let's just think a moment. Oh yes, I remember now! 'Myria' is the metric prefix for 10,000. A myriawatt is 10,000 watts. Okay?"

"Yep," said Dick. "I thought for a moment then that you were going to break into a 'myria, myria, on the wall' routine!"

"I'll do a metric one on you now," said Smithy, ignoring Dick's comments. "What's a nanosecond?"

"That's another easy one," replied Dick. "I always remember 'nano' by saying it comes between 'micro' and 'pico'. A nanosecond is one-thousand-millionth of a second, or a thousandth of a microsecond."

"Good," said Smithy. "What's the next letter?"

"O," replied Dick, "and it's me to go. I'll give you an easy one, too. What's an OR gate?"

"It's a gate which gives an output 1 when one or more of its inputs is 1," replied Smithy. "The common circuit symbol for it is a sort of elongated semicircle with a curved edge where the inputs go, as opposed to the straight edge at the input side that you have with an AND gate symbol. If a small circle is added at the output end, this represents an inverter and the gate becomes a NOR gate. Here, the output is 0 when one or more of the inputs is 1." (Figs. 5(a), (b) and (c).)

"A little circle at the output end of an AND gate makes that a NAND gate, too, doesn't it?" (Fig. 5(d).)

"It does," confirmed Smithy. "As I understand it, the official symbol now-

adays for all gates is simply a rectangle with the gate function written inside, but the symbols I've just described are those that are commonly used throughout industry. It's me next with P. What do I mean by 'pre-emphasis'?"

"Pre-emphasis?" repeated Dick frowning. "Blimey, I should know that."

He scratched his head helplessly. "No," he said eventually, "I give up. What is 'pre-emphasis'?"

"It's the process of increasing the amplitude of a band of frequencies in a signal relative to the other frequencies," explained Smithy. "We get it for instance in the transmission of f.m. sound, in which the higher audio frequencies are pre-emphasised at the transmitter and are then de-emphasised at the receiver. This results in a higher signal-to-noise ratio. With British f.m. transmissions the pre-emphasis is 50 microseconds."

"How d'you mean, 50 microseconds?"

"The 'pre-emphasis,'" explained Smithy, "can be carried out by a simple filter incorporating inductance and resistance in series and the de-emphasis by another signal filter incorporating resistance followed by shunt capacitance. The 50 microsecond figure then applies to their time constant. Provided the time constant is correct, the right amount of pre-emphasis or de-emphasis will always be given by either filter. With the inductive pre-emphasis circuit the time constant is L in henrys divided by R in ohms, and suitable values would be 1 henry and 20k Ω . The time constant for the capacitive filter is the familiar C times R , and typical values for a 50 microsecond de-emphasis filter would be 100k Ω and 500pF." (Figs.

6(a) and (b).)

QUASAR

"Well now, that's something I've definitely learned today," stated Dick cheerfully. "I've got a smasher for the next letter, which is Q. What's a quasar?"

"A what?"

"A quasar."

"Spell it."

"Q-U-A-S-A-R."

Smithy looked at his assistant suspiciously.

"You wouldn't be trying to take the Michael, would you?"

"Of course not."

"I don't believe there is such a word," stated Smith with conviction.

"You've just made it up."

"No, I haven't"

"Oh all right," said Smithy bad temperedly. "You tell me what it is then."

"It's a source of radio signals from outer space," explained Dick. "Quasars can be located by radio astronomy and have rather the same behaviour, from the radio signal point of view, as have stars."

"Humph," grunted Smithy grudgingly. "All I can say is that I didn't know *that* before. Very well then, I'll try an awkward one out on you for R. What's 'radiation resistance'?"

"Of an aerial?"

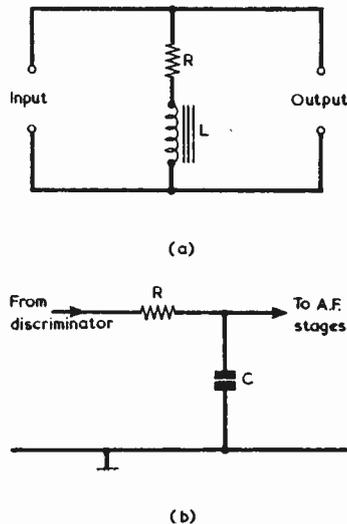


Fig. 6(a). A pre-emphasis filter. The input source should have an internal resistance much higher than the value of R

(b). A de-emphasis filter, as incorporated in an f.m. receiver. The filter can perform the secondary function of i.f. filtering

"Yes," said Smithy shortly, "of an aerial."

"It's the effective resistance presented by an aerial when it's used for transmitting," replied Dick confidently. "Since the aerial is dissipating energy in the form of radio signals it can be looked upon, so far as the power going into it is concerned, as a resistance, and this is the radiation resistance. As power is equal to I^2R , the radiation resistance of the aerial is equal to the power going into it divided by the square of the aerial current."

Dick smiled sweetly at the obviously nonplussed Serviceman. He forebore to mention that he had just happened to be reading about radiation resistance in a radio magazine during lunch-time.

"Shall I give you one for S?"

Ungraciously, Smithy grunted an assent.

"What," asked Dick, "is a see-saw circuit?"

A gleam of satisfaction came into Smithy's eyes.

"Ah now," he remarked, obviously pleased, "this is a question that's a bit

more down to earth. The see-saw circuit first came into being in the earlier days of hi-fi valve amplifiers, in which it was used as a phase-splitter. It employed a double-triode in an arrangement where there were two equal value resistors between the anodes, with their junction coupled to the grid of the second triode." (Fig. 7(a).)

Smithy sipped for a moment at his mug.

"But it is easier nowadays to demonstrate see-saw operation with the aid of an operational amplifier," he went on. "If an input from a source which is assumed to have no internal resistance is fed via a resistor to the inverting input of an op-amp and a resistor of the same value is connected between the output and the inverting input, you get a set-up where the output is equal in amplitude but of opposite phase to the input." (Fig. 7(b).)

"I see," said Dick. "As the input goes one way the output goes the other way. Is that why it's called a see-saw circuit?"

"That's right," replied Smithy. "Another point is that, because of the very high gain of an op-amp the voltage at its inverting input terminal hardly varies at all, which is why the terminal can be looked upon as being a virtual earth. You still get the see-saw effect if the two resistors have different values but the output amplitude isn't then equal to the input amplitude. Which brings me up to T."

"Letter T or liquid tea?"

"Both," replied Smithy, draining his mug and handing it over to his assistant. "It's a good thing you reminded me!"

Smithy waited 'as Dick busied himself at the Workshop sink with the task of replenishing his mug.

"I'll give you a nice simple one now," he remarked as Dick returned. "What's a thermistor?"

"It's a device," said Dick without hesitation, "whose resistance goes down as its temperature goes up. What's 'unilateralisation'?"

"Dear me," chuckled Smithy. "You're going back a bit here.

'Unilateralisation' is the rather posh name given to the neutralising arrangements which were employed in the earlier medium and long wave transistor radios, particularly when these had OC45's and similar transistors in the i.f. stages. The output of each i.f. amplifier transistor was coupled back to the input via a capacitor on its own or via a capacitor in series with a resistor." (Fig. 8.)

Smithy drank from his recharged mug.

"Well now," he said musingly, "what shall I do about V? Ah, I know. Tell me what 'vertical blanking' is."

"That's the process," said Dick, "of cutting off the cathode ray tube beam in a TV receiver during vertical retrace at the end of each field. If you didn't do this the spot would trace out a pattern on the screen as it returned to the top to start another field."

"True," assented Smithy. "The blanking level is also, incidentally, automatically provided by the transmitted signal."


"Blow me," remarked Dick. "It's W next and we've nearly come to the end of the alphabet already. Anyway, what's a wave trap?"

"It's a tuned circuit," replied Smithy, "whose function is to reject an unwanted signal. You most often find it in the form of a parallel tuned circuit inserted in series with the aerial connection to a receiver. Since a parallel tuned circuit offers a maximum impedance at its resonant frequency, the wave trap is set up to be resonant at the frequency of the unwanted signal." (Fig. 9.)

X-RAYS


Smithy frowned.

"There's only X, Y and Z left now,"

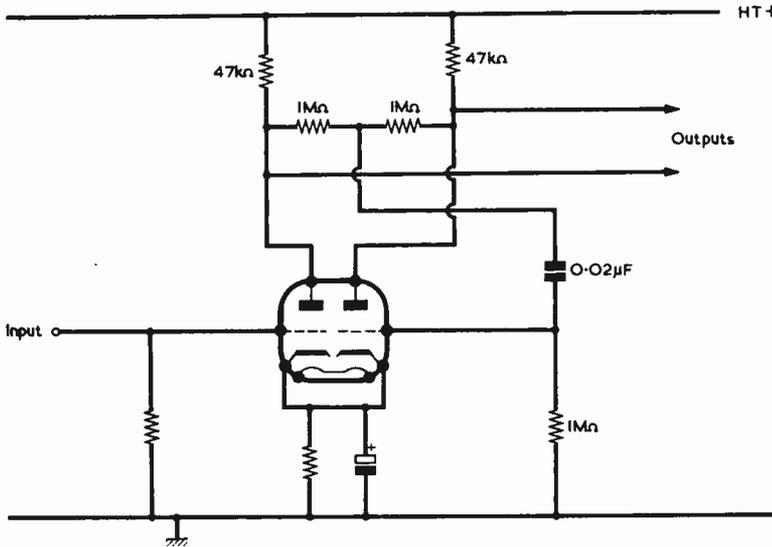

(a)

Fig. 7 (a). The original see-saw valve phase splitter, with suitable component values in the anode and second grid circuits
(b). A see-saw circuit employing an operational amplifier. When R_1 is equal to R_2 the output amplitude equals the input amplitude. See-saw operation is still given if the resistors are unequal

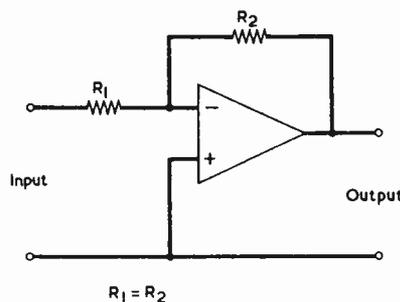

(b)

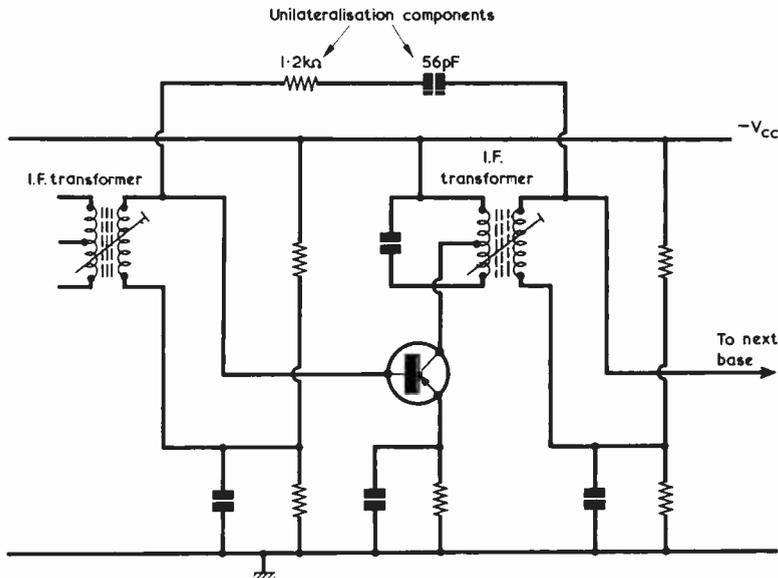


Fig. 8. An example of unilaterisation in a receiver i.f. amplifier, with typical component values. In some cases the resistor may be omitted

he commented, "and these are always difficult letters to deal with. I think I'd better ask you about X-rays."

"Well," said Dick, "X-rays are the invisible rays which pass through you and enable your innards to be photographed."

"An excellent and highly scientific description," stated Smyth. "It's worth adding, perhaps, that X-rays are in the electromagnetic family and that they cover higher frequencies than those of visible light, these frequencies starting at around the point where the ultra-violet band ceases."

"There's Y next," commented Dick. "I've got a good one here. What's a 'Y-cut crystal'?"

"It's a quartz crystal segment," replied Smyth, "which has been cut along a particular axis of the parent crystal. You don't normally encounter

Y-cut crystals, the more common types being AT and BT cuts. These letters indicate planes inside the parent crystal before it's cut, and each of the cuts are at different angles inside the crystal. Blimey, I'm stuck with Z now! Ah, I know. Tell me what 'zero-beat' is."

"That's a good one to finish off with," said Dick. "If you tune an a.m. superhet with a b.f.o., or a t.r.f. receiver whose reaction is advanced beyond oscillation point, through a signal, you get the well-known heterodyne whistle with the carrier of the signal. You can tune the receiver so that the frequency of the heterodyne beat note becomes so low that it is inaudible. If you keep tuning, the beat note becomes audible again at a very low frequency, which then rises. The tuning point at the middle of the two points where the signal becomes inaudible is known as zero-beat."

"Very good," remarked Smyth, pleased. "The term also applies to any other case where two separate signals which heterodyne together have virtually equal frequencies. Well, we seem to have successfully made our way once more through the alphabet."

"What's more," chimed in Dick, "we've managed to find a subject for each letter, too. And that just can't be bad."

Whereupon, after having passed the letter Z, we must now take our leave of the pair, enconced as they are in the warm comfortable Workshop with an unusually small amount of work in front of them and the consequent ability to take things nice and easy. Circumstances such as these can hardly be bad, either.

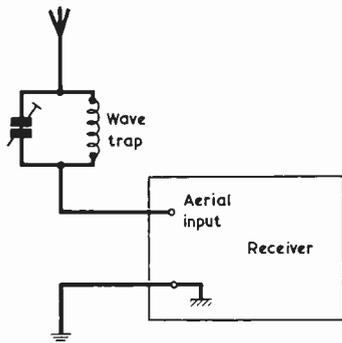


Fig. 9. A wave trap inserted in the aerial feed to a receiver

COMPUTER PANELS

Panel contains 2 x Mullard OC23 Transistors and 5 other Transistors etc. 2 panels 50p p.p. 15p. Panel contains 2 x Mullard OC28 Transistors 2 XBCY34, etc. 2 panels 50p p.p. 15p. Assorted Computer Panels contains many useful Transistors, Diodes, Trim Pots, etc. 4 panels for £1 post free. Assorted Panels contains minimum of 10 integrated circuits, also Transistors, Diodes etc. £1 p.p. 15p. Electrolytic Capacitors UF/V. 2000/35, 10,000/15, 10,000/25, 12,500/35. All 30p each p.p. 6p. 2,000/50, 2,500/50, 5,000/50, 10,000/50, 12,500/50, 50,000/15 all at 40p each p.p. 10p. Also available wide range motor start capacitors also block paper, etc. Send our exact requirements.

Send your exact requirements

XEROZA RADIO

1, East Street, Bishops Tawton, Devon

DE-SOLDERING

Made Easy

UNSOLDERING BITS - release component leads in one operation. $\frac{1}{8}$ " diam, shanks.
Dual-in-line (0.3"), I.C. 85p.
Long line of leads 75p.
T 0.5 outline 55p.
Finepoint non-seize 30p.
MATCHING SOLDERING
IRON £1.80
SOLDER-ABSORBING WICK 40p.

ORIENTATION LTD.

Mayfield, Coverack, Cornwall

RADIO & ELECTRONICS CONSTRUCTOR

ANNUAL SUBSCRIPTIONS
to this magazine may be obtained through your newsagent or direct from the publishers **ONLY £2.70** per year, post free

Please send remittance with name and address and commencing issue required to:

DATA PUBLICATIONS LTD
57 Maids Vale London W9 1SN

Radio Topics

By Recorder

ALTHOUGH NOISE IS LOOKED UPON as one of the factors which pollute our environment there are times when, properly controlled, it has a level of usefulness. This is particularly true of white noise. White noise consists of random noise containing a wide band of frequencies without any peaks in the frequency response, and it is analogous to white light, which includes all the frequencies of the visual spectrum. It is common to refer to white noise as covering the audio frequencies only but the term nowadays seems to be applied to noise bands at radio frequencies as well.

White noise is of particular value in the testing and evaluation of high fidelity equipment since it enables any abnormalities in the frequency response of such equipment to be revealed under operating conditions. If white noise with a flat frequency response is fed into the input of the equipment then white noise with a similarly flat response should appear at the output. If it doesn't then there's something wrong with the equipment.

In the higher frequency ranges there are many applications for flat white noise in radar and communications systems. Here, it may be used for signal path verification and as a carrier for secure line operation.

NOISE GENERATORS

A company which specialises in the production of noise generators is Solidev Ltd., Tubs Hill House, North Entrance, London Road, Sevenoaks, Kent, who now announce the Solidev SD series of noise diode sources. These are available with or without their energising circuits in an eight frequency band range of between 5Hz to 20kHz and 1MHz to 500MHz. When the energising circuit is included, the diode, the current limiting resistor and the d.c. blocking capacitor in the output are encapsulated in one pack-

age designed for printed circuit mounting. All these units can be selected for response flatness, and they operate into a load impedance of 50Ω.

Other devices produced by Solidev Ltd. include noise reference test sets; units with extremely high levels of flat noise for use in band rejection noise calibration systems; panel mounted noise sources for incorporation into test equipment; and a range of custom built modules for a variety of electrical and physical conditions to MIL specifications.

Professional readers will be interested to learn about the wide range of noise generating equipment that is currently being manufactured. And the non-professional amateur may be impressed, also, to learn that a humble quantity such as noise can attract to itself such a diverse field in design and development.

TELEPHONE AMPLIFIER

All sorts of odd jobs tend to come my way these days, and a recent one consisted of the repair of a home-built telephone amplifier which had developed a nasty attack of distortion. It was simply a sensitive transistor a.f. amplifier complete with speaker, to the input of which was coupled a telephone pick-up coil. A telephone pick-up coil consists, as you will almost certainly already know, of a coil mounted in a small plastic moulding having a rubber sucker at one end. You simply affix this by means of the sucker to the base of the telephone instrument, choosing a position which offers optimum coupling to the internal transformer inside. Thus, there are no direct connections to Post Office lines and the operation of the telephone is unimpaired. These pick-up coils can be obtained, incidentally, from Henry's Radio, Ltd. The type sold by Henry's Radio has an impedance of about 2kΩ, is referred to as a 'telephone recording adaptor', and appears in the Henry's Radio catalogue in the section devoted to microphones.

My problem, whilst fixing the amplifier, was to find a source of signal which could be fed into the amplifier, via the telephone pick-up coil, for a length of about fifteen minutes or so whilst I chased the cause of the distortion.

The obvious approach here is to dial the time number and use the continual time announcements as a source of signal. However, I rejected this idea for two reasons. First, it seemed to me to be morally wrong to tie up a line to a public service number for as long a period of time as I would require. Second, I haven't got a telephone in my workroom.

The solution proved to be remarkably simple. The transistor radio I use in my workroom for news bulletins and the like has its output stage fed by a driver transformer. All I had to do was to tune in a station, set the

volume of the radio to a low level and place the pick-up coil on top of that driver transformer. The coil picked up the field from the transformer at just the same level as it would have done from a telephone, and it enabled me to trace the fault in the amplifier without any difficulty. The fault, by the way, was simply a cold joint at one of the transistor bias resistors, and it required nothing more technical than a gentle prod with a screwdriver to reveal itself.

BEFORE THE WAR THOSE OF US IN THE radio game used to complain bitterly about what we considered to be the unnecessary multiplicity of valve types. There were certainly plenty of valves around in those days, and one of the complicating factors was the large quantity of different valve bases which were employed. These included the British 4-pin, the British 5-pin, the British 7-pin, the Mazda Octal, the International Octal and the Philips side-contact bases. From the States there were also the UX4, UX5, UX6 and UX7 bases. Later to descend on us were the B7G, B8A and B9A bases.

Even with this multiplicity of valve types, we would have held up our hands in horror could we have foreseen the myriad hordes of transistor types beneath which we are now being swamped. The home-constructor may imagine, from the lists of transistors published by component retailers, that the situation is not all that bad. But there are many more transistor types than those which find their way into the amateur market. If, for instance, the constructor ventures into the servicing field he will soon encounter receivers having transistors whose type numbers seem to have no relationship whatsoever with the more familiar ones we play around with at home. There is, one begins to suspect, just one copy of the specifications for each of these outlandish transistors, and this is locked firmly away in the safe of the receiver manufacturing company which employs them in its wares.

INTEGRATED CIRCUITS

It is with something of a surprise, then, that I find that a degree of rationalisation has become evident in the world of integrated circuits. So far as operational amplifiers are concerned, the 709 and 741 appear to have carved out their own highly stable niche. And in logic i.c.'s the well-known 74 series of TTL packages seems to be meeting most of the general requirements that are apparent in this field. There are, admittedly, sub-divisions within the type numbers, these defining whether the devices in question are, say, dual-in-line or in flat package, and also their temperature limits. But these sub-divisions should not at any event trouble the home-constructor to any great extent, apart from the fact that


he will probably find that the dual-in-line versions are the most easy to work with.

There are, of course, still a great many i.c. types other than the ones I've just mentioned. But the latter presumably represent the ultimate in performance for their particular applications and, since they are more than good enough for common-or-garden op-amp and logic functions, have become standardised types. And a jolly good thing, too.

An unusual development is that components other than semiconductor devices are now being designed to fit into the integrated circuit format! The two d.i.l. packages you see in the accompanying photograph are not semiconductor integrated circuits at all; they are, instead, resistor networks.

These new units are made by ITT Components Group Europe and are part of a range of standard resistor networks in 14 pin dual-in-line packages which are known as 'Key' resistor modules.

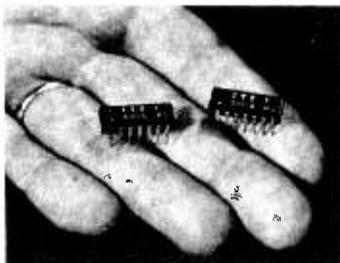These networks offer groups of resistors connected in various patterns to meet circuit functions that repeat themselves many times in equipment assemblies. As such, they are capable of reducing costs by simplifying component ordering, inspection and storage and of easing assembly and inspection during equipment production.



Resistor networks are now being produced, by ITT Components Group Europe, in the d.i.l. package formerly assigned to integrated circuits. A range of modules with different internal circuits and varying resistance values is available

The networks include the following packages.

A module with seven different resistors, all of equal value, suitable for l.e.d. (light-emitting diode) current limiting.

A module with thirteen resistors, all of equal value in any one unit, and all commoned at one end to pin 14.

A module with twelve resistors, all of equal value in any one unit and commoned at one end to pin 14, plus a

capacitor for decoupling connected between pins 7 and 14.

A module having two groups each of six resistors. Within each group the resistors are commoned at one end and brought out to pin 14 for one group and to pin 7 for the other group. These networks are available with resistors all of equal value in any one unit, or a single fixed ratio between the two groups of resistors in any one unit.

(Further information on these packages can, incidentally, be obtained from ITT Components Group Europe, Film Circuit Operation, Brixham Road, Paignton, Devon.)

The idea of multiple resistor packs is not new, of course, and these have been used quite a lot in the past. But it is interesting, to say the least, to see them now turning up in the d.i.l. style which has been brought about by the advent of the integrated circuit.

CONTRA ENTRY


A disturbing feature of the computer is that, so far as time is concerned, it is strictly a one-way device. No allegation written out by a computer can be expunged. The only rectification possible is the issuing of a balancing counter-allegation later.

This was brought home to me when I was checking a recent bank statement, which had been made up by the bank's central computer. There, in the 'Receipts' column, was an entry for £11 marked against 'Sundry Credit', but there was no corresponding record of this in my paying-in book. It looked as though I had become £11 richer through divine intervention via the bank central computer and that I'd be able to pay off the rent after all. But such was not to be the case. An entry 24 days later described as 'Contra Entry' put that £11 firmly in the 'Payments' column and I was back to square one once again.

Presumably it was a human agency that credited me with the money in the first place, and a second human agency that had initiated the 'Contra Entry' bit to correct the error after it had been found that the bank's central resources were light of £11. Or, spine-chilling thought, had the computer itself detected the error and then taken it upon itself to put it right before anyone found out? Perhaps, even more frightening, that computer is trying out its skill at embezzlement on a small scale. When it becomes sufficiently proficient, it will then salt away small sums from individual accounts into a private numbered account in Switzerland, this being done with the aid of an accomplice computer situated in that country.

Perhaps the most annoying thing about this story is that I didn't know I was the possessor of an illicit £11 until after the money had been debited back again.

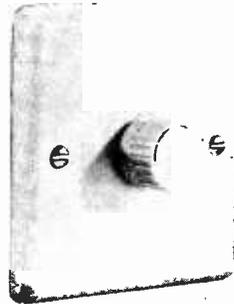Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt £3.20. Kit Form £2.70
300 Watt £2.70. Kit Form £2.20

All plus 10p post and packing.
Please send C.W.O. to:

DEXTER & COMPANY
7 ULVER HOUSE, 19, KING STREET,
CHESTER CH1 2AH. Tel: 0244-25883.
As supplied to H.M. Government Departments.

BURNS ELECTRONICS

TEST EQUIPMENT:

Crystal Calibrator CC-10 £25.60
Wavemeter TC-101 £18.30
Frequency Standard SD-11 £78.00

COMMUNICATIONS ACCESSORIES:

FET Converter FC2/FC4 £16.20
FET Converter FS2/FS4 £18.00
FM Detector FMD-1 kit £6.70
tested £8.20
Tone Burst Generator TBG-1
kit £4.70
tested £5.70

Full details of equipments on request. We also stock a wide range of Semiconductors, Integrated Circuits, Coil Assemblies, Capacitors, Resistors, Nuts and Bolts, Packs of Ferric Chloride etc. Send 10p. for equipment and component Catalogues or CWO to:

THE COTTAGE,
35 BEULAH HILL,
LONDON,
SE19 3LR

B. H. COMPONENT FACTORS LTD.

**BARGAIN PRICES
MONEY BACK GUARANTEE**

<p>SPECIAL RESISTOR KITS 1W 5% carbon film</p> <p>10E12 KIT - 10 of each E12 value 10 ohms - 1M. £2.80 A TOTAL OF 610 RESISTORS net.</p> <p>25E12 KIT - 25 of each E12 value 10 ohms - 1M. £6.50 A TOTAL OF 1525 RESISTORS net.</p> <p>ROTARY SWITCHES 1P 4W, 1P 12W, 2P 2W, 2P 4W, 2P 5W, 3P 3W, 3P 4W, 4P 2W, 4P 3W. 24p</p> <p>BARGAIN PACKS</p> <p>PVC WIRE 7/0076, 5 x 10 yds. 5 colours... 30p PVC WIRE 14/0076, 5 x 10 yds. 5 colours... 30p SMALL 4 WAY CABLE, 10 yds... 50p SMALL SCREENED WIRE, 10 yds. 3" DIA... 50p MIN. GEN. PURPOSE SWITCHING DIODE... 25 for 25p NEON BULB, 80V, WIRE ENDED... 5 for 20p RESISTORS ASSORTED 1W and 1/2W... 100 for 40p ELECTROLYTICS TRANSISTOR TYPE... 25 for 50p POLYESTER CAPACITOR 10µF 100V... 50p MINIATURE PUSH BUTTON, push to make... 10p TRANSFORMER (MAINS) 32 - 0 - 32 at 150 mA... 50p SYNCHRONOUS MOTOR 240V 3W ex. equip... 75p POTS, ASSORTED, SOME EX. EQUIP... 5 for 25p SILICON DIODE 400V 3A (TOP HAT)... 4 for 25p SILICON DIODE 100V 20A (PLASTIC CASE) 2 for 70p OAB ex equip. TESTED... 4 for 20p OC83 ex equip. TESTED... 6 for 25p Electrolytic 2.5µF 50V... 25 for 80p ACY17 ex equip. TESTED... 5 for 20p</p>	<p>CERAMIC PLATE CAPACITORS 750V. (pF) 5, 10, 25, 40, 70, 220. 2 1/2p 225V, 100PF, 50V, 2 1/2p. (µF/V) 0.001/350, 2p 0.0047/30, 2p. 0.01/50, 2p. 0.01/350, 2p 0.022/50, 2 1/2p. 0.047/30, 3p. 0.1/30, 4p 0.1/100, 5p</p> <p>VEROBOARD 0.1" MATRIX</p> <p>2.5" x 5" ... 25p 2.5" x 3.75" ... 23p 3.75" x 5" ... 28p 3.75" x 3.75" ... 25p 2.5" x 1" 2 for 12p</p> <p>0.15" MATRIX</p> <p>2.5" x 5" ... 25p 2.5" x 3.75" ... 17p 3.75" x 5" ... 30p 3.75" x 3.75" ... 25p 2.5" x 1" 2 for 12p</p> <p>0.15" MATRIX PLAIN</p> <p>2.5" x 5" ... 12p 2.5" x 3.75" ... 11p 5" x 3.75" ... 20p</p> <p>PINS (STATE SIZE) 10 - 4p, 25 - 8p, 100 - 30p</p> <p>INSERTION TOOLS (STATE SIZE) 54p TRACK CUTTER 40p</p> <p>QIN PLUGS</p> <p>2 pin 12p SOCKET 10p 3 pin 13p SOCKET 10p 5 pin 180° 15p SOCKET 12p</p>	<p>RESISTORS 1/2W 5% CARBON FILM 1p each 10 ohms - 1M 100 for 55p</p> <p>1N 4001 8p 2N706 10p AC127 18p 1N 4002 7p 2N708 13p AC128 20p 1N 4003 8p 2N1303 17p BC108 11p 1N 4004 9p 2N3055 60p 8EY51 20p 1N914 6p 2N3866 80p OC71 12p 7400N 15p 7440N 25p OC75 15p 7401N 15p 7470N 30p OC83 18p 7410N 15p 7483N 120p OC84 15p 7430N 15p 7493N 80p uL914 30p</p> <p>TUNNEL DIODES 1N3717 ET, TD715, TD716, 50p</p> <p>PANEL NEON 240V, TAG ENDED... 15p R.F. CHOKES, 0.22uH, 2.2uH, 12uH, 22uH... 8p TRANSISTOR EQUIVALENTS BOOK 40p ELECTRONICS DATA BOOK... 25p LIGHT EMITTING DIODE... 50p MINITRON 3015F... £1.80p</p> <p>ZENER DIODES BZY88 TYPE, UNMARKED, BUT TESTED AND POLARITY MARKED, ALL VALUES</p> <p>2 - 13 volts... 5p BRIDGE RECTIFIER, PLASTIC, 100V 1A... 40p</p>	<p>POLYESTER CAPACITORS C280 SERIES 250V. 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3p, 0.088µF, 0.1µF, 0.15µF, 4p, 0.22µF, 5p, 0.33µF, 7p, 0.47µF, 8p, 0.68µF, 10p, 1µF, 13p, 1.5µF, 20p, 2.2µF, 23p.</p> <p>POLYESTER CAPACITORS C296 SERIES (TUBULAR) 180V, 0.01µF, 0.015µF, 0.022µF, 2p, 0.047µF, 0.088µF, 3p, 0.15µF, 0.22µF, 4p, 0.33µF, 5p, 0.47µF, 8p, 0.68µF, 1µF, 10p.</p> <p>400V, 0.001µF, 0.0012µF, 0.0015µF, 0.0018µF, 0.0022µF, 0.0033µF, 0.01µF, 2p, 0.015µF, 0.033µF, 3p, 0.088µF, 4p.</p> <p>MINIATURE ELECTROLYTIC MULLARD C428 SERIES 5p each</p> <p>(µF/V) 0.64/64, 1.6/25, 4/40, 5/64, 8/40, 10/16, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 84/10, 80/16, 80/25, 100/64, 125/16, 200/64, 200/10, 320/64.</p> <p>MULLARD C437 SERIES 64/64, 8p, 160/25, 9p, 180/40, 11p, 640/64, 9p, 1600/64, 14p.</p> <p>ELECTROLYTIC CAPACITORS (µF/V.) 2.5/50, 3p, 4/10, 10/15, 16/15, 20/25, 25/15, 25/25, 40/8, 64/10, 200/6, 250/10, 4p, 10/6, 10/50, 25/50, 32/50, 50/10, 64/25, 100/25, 6p, 50/60, 64/40, 250/15, 1000/3, 8p, 100/50, 250/25, 400/10, 500/10, 500/12, 640/10, 1000/6, 8p, 500/25, 10p, 500/50, 12p, 1000/12, 10p, 1000/25, 2000/12, 2500/12, 15p, 1000/50, 35p, 2000/25, 25p, 2500/25, 30p, 3000/50, 65p, 5000/50, 85p.</p>
---	---	--	--

C.W.O. ONLY. P & P 10p ON ORDERS BELOW £5. DISCOUNT: ABOVE £10 - 10%, £20 - 15%
DEPT. RC. 61 CHEDDINGTON ROAD, PITSTONE, LEIGHTON BUZZARD, BEDS, LUT 9AQ TEL. CHEDDINGTON
(0296) 668446. Callers by appointment only. ENQUIRIES - S.A.E., LIST 5p. EXPORT WELCOME. POST AT COST.



UNDERSTANDING TELEVISION

by
J. R. DAVIES

Over 500 pages
300 diagrams

£2-10

POSTAGE
20p

UNDERSTANDING TELEVISION deals with:

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Colour television
- **COLOUR TELEVISION - 80 page section deals comprehensively with this subject**

The reader is required to have only a basic knowledge of elementary radio principles. The treatment is non-mathematical throughout, and there is no necessity for any previous experience in television whatsoever. At the same time UNDERSTANDING TELEVISION is of equal value to the established engineer because of the very extensive range it covers and the factual information it provides.

Please supply UNDERSTANDING TELEVISION, Data Book No. 17.

I enclose cheque/crossed postal order for.....

NAME.....

ADDRESS.....

(BLOCK LETTERS PLEASE)

To Data Publications Ltd., 57 Maida Vale, London, W9 1SN

SMALL ADVERTISEMENTS

Rate: 4p (9d) per word. Minimum charge 60p (12/-).
Box No. 10p (2/-) extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W9 1SN

FOR SALE: VHF KIT, 80 - 180 MHz. Receiver, tuner, converter. World wide sales. Incomparable. £4.00 or s.a.e. for literature. Johnsons (Radio C), Worcester WR1 2DT.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p. with free Fault Finding Guide. Catalogue 15p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p. post free.

CATALOGUE NO. 18, containing credit vouchers value 50p, now available. Manufacturers new and surplus electronic and mechanical components, price 23p post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex.

FOR SALE: Widescreen Cine Outfit. 9.5mm Prince cine camera fitted with Zenoscope Anamorphic lens, 9.5mm Specte projector with adaptor for Zenoscopic lens, widescreen 60 in. by 30 in., six 9.5mm cassettes for camera. £50, Box No. G192.

BUILD IT in a **DEWBOX** robust quality plastic cabinet 2 in. x 2½ in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now - right now.

MECCANO FOR "CYCLOPS" - Special Pack of all Meccano parts required - £3.39 including postage. Send off today to *The Meccano Spare Parts Specialists* and start building! "Everything Meccano" at M. W. MODELS, 165 Reading Road, Henley-on-Thames, Oxon. Telephone 3342.

FOR SALE: Pye Cambridge transmitter/receiver. Modified for 2 metres. Excellent condition. £30. Box No. G193.

VERNITRON CERAMIC RESONATORS for i.f. filtering. FM4, 10.7MHz (bandwidth 235kHz), matched pair £1.50. 455kHz types: TF-01A, 38p; TO-02A, 45p; TF-04 442, 40p; TFN-3A kit, £1.50; TFN-3ADX, £1.50; TF-2D5, 40p. Data supplied with orders. Mail order only. U.K. post 5p. **AMATRONIX LTD.**, 396 Selsdon Road, South Croydon, Surrey, CR2 0DE.

BUILD THE MULLARD C.C. TV CAMERA. Complete kits now available from Crofton Electronics. Send large s.a.e. for details to: 15-17 Cambridge Road, Kingston-Upon-Thames, Surrey. Reply by post. No callers please.

FOR SALE: 2 metre converter, 24-26MHz I.F., built in a.c. 230V power supply. £10. Box No. G194.

"HOW TO LISTEN TO THE WORLD" 1973, £1.90. "WORLD RADIO TV HANDBOOK", published December, £2.80. "SWL ADDRESS BOOK", station's QSL policies, £1.45. Post (first class) 10p each. David McGarva, Box 114G, Edinburgh EH1 1HP.

Q MULTIPLIER COILS. High efficiency pot core assemblies for use in the range 50kHz - 2MHz. Other frequencies to order. 50p. each plus 5p. p. & p. State frequency required and whether p.c. or single hole mounting. Overseas enquiries invited. Storey, 145 The Knares, Basildon, Essex.

(Continued on page 273)

NOVEMBER 1972

IN THIS CATALOGUE



10p
post paid
in U.K.

- 96 Pages
- Transistors, with technical specs.
- I.Cs with working diagrams
- Resistors, capacitors, components
- Diagrams, tables, information
- GENUINE DISCOUNTS

ELECTROVALUE LTD. Dept.
28 St. Judes Rd., Englefield Green, Egham, TW20 0HB R.C.6
9-6 daily: 1.0 p.m. Sat. Telephone Egham 3603

TECHNICAL TRAINING in Radio, Television and Electronic Engineering

Let ICS train You for a well-paid post in this expanding field. ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma Courses in Radio, TV Engineering and Servicing, Colour TV Servicing, Electronics, Computers, etc. Expert coaching for:

- * C&G. TELECOMMUNICATION TECHNICIANS CERTS
- * RADIO AMATEURS EXAMINATION
- * GENERAL RADIOCOMMUNICATIONS CERTIFICATES
- * C&G. RADIO SERVICING THEORY

CONSTRUCTOR COURSES

Build your own transistor portable, signal generator, multi-test meter—all under expert guidance. **POST THIS COUPON TODAY** and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

Member of the ABCC.

Accredited by the C.A.C.C.

Name _____ Age _____
BLOCK CAPITALS PLEASE

Address _____

INTERNATIONAL CORRESPONDENCE SCHOOLS

WA 33

INTERTEXT House,
Stewarts Road,
London SW8 4UJ

ICS
Gets you there.

RSGB BOOKS FOR YOU

New (fourth) edition of the ever-popular **AMATEUR RADIO TECHNIQUES**

by Pat Hawker, G3VA

Aimed at extending the reader's awareness of new devices and techniques. Provides a source book for many useful circuits and aeriels. An *ideas* book rather than a constructional manual, but an ideas book that will prove its value time and time again.

Substantially enlarged edition comprising 256 pages with over 600 diagrams. New material and features include more emphasis on integrated circuits, a quick guide to digital electronics, and much additional information on the cure of TV interference and on aeriels.

£1.80 including postage and packing

RAE MANUAL

by G. L. Benbow, G3HB *Sixth (1972) edition*
The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. A completely re-written edition brought fully up to date to meet the present examination syllabus requirements.

96 pages

90p post paid

These are two of a complete range of technical publications, log books and maps, all obtainable from:

RADIO SOCIETY OF GREAT BRITAIN
35 DOUGHTY STREET, LONDON, WC1N 2AE

POTENTIOMETERS Lin or Log, 12p; with DP Switch, 23p; Dual Ganged, 36p; Special Offer, 5K with DP switch, 15p; WAVECHANGE SWITCHES, 22p; Special Offer, Miniature, 4p, 3W, 16p; AMPLIFIERS: 1 Valve (EL84), £3; $\frac{1}{2}$ W Transistorised £1; 10W Transistorised, £3-75. JB3 Junction Box, £1-20. 5" Plastic Library Cases, 10p. 500uA TUNING METERS, 50p. CARTRIDGES: Compatible ACOS GP91-35C, 90p; Stereo GP93-1, £1-15; Ceramic with Diamond Stylus, £1-80. CAPACITORS 100mF 25V, 5p; 220mF 25V, 5p; 400-200-50-16mF 300V, 30p; 0.1 500VDC, 300VAC, 3 $\frac{1}{2}$ p. MINIATURE INDICATOR LAMPS (5 colours), 11p; 6 or 12V Bulbs for above, 4p. MAINS NEONS panel mounting (red, green, clear), 15p. 100 MIXED RESISTORS, 45p. ROTARY SWITCHES (on/off) 250V 2A, 10p. PLUGS: Jack Standard, 10p; Screened, 13p; 2.5mm and 3.5mm, 6p; Screened, 8p. HEADPHONES: High Impedance (2,000 ohm), 90p; STEREO 8 ohm, £1-95; STEREO 8/16 ohm, £2-10. MICROPHONES: Lapel, 28p; ACOS MIC. 45, 90p; Dual Impedance Dynamic 600 ohm and 50k, £4-50. RECORDING TAPE: 5" LP 900ft., 45p; 5 $\frac{1}{2}$ " LP 1,200ft., 60p; 7" LP 1,800ft., 81p. RESISTORS: carbon film 5%, 1 $\frac{1}{2}$ p. ALUMINIUM CHASSIS from 6" x 3" to 16" x 10", all 2 $\frac{1}{2}$ " deep. Transistors, Rectifiers, etc.
Large S.A.E. for list No. 4. Special Prices for quantity quoted on request. Add 10p for P&P on orders under £5.

M. DZIUBAS


158 Bradshawgate, Bolton, BL2 1BA. Lancs.

NEW STYLE SELF-BINDER

for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

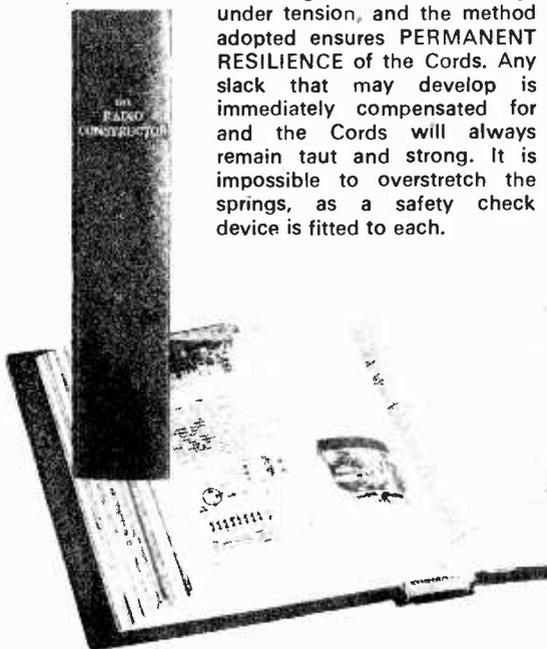

PRICE **75p** P. & P. 14p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 ISN

SMALL ADVERTISEMENTS

(Continued from page 271)

FOR SALE: "Jane's Fighting Ships" 1965/66 edition. £5.00. Box No. G195.

UNTESTED GOLD BONDED DIODES: BA144 type Germanium OA91 type 200 for 50p, Zeners BZY88 type 100 for 50p. Post free. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

COMPONENTS TO CLEAR: Woden Mic. transformer, M.T.101, £1.50. E.C.C. Miniature relay type 2,5A, £1.00. 8 in. speaker, 30p. Eddystone 5 pin coil formers, 10p. Metal rectifiers, type SETT 2 W.B., 30p. Capacitors: 5mfd 3000V d.c., 30p. 2mfd 1000V d.c., 20. 1mfd 1000V d.c., 15p. 4mfd 500V d.c., 10p. Box No. G196.

"MEDIUM WAVE NEWS" Monthly during Dx season - Details from: K. Brownless, 7 The Avenue, Clifton, York.

VALVES TO CLEAR: VR91, 171DDP, 801, U14, HP4106, 6B4-G, 6AG5. A11 at 20p each. Box No. G197.

FOR SALE: Advance constant voltage transformer, input 190/260V, output 240V 500W. As new. £20. Edwards, 2 Newlands Lane, Culverstone, Gravesend, DA13 ORD. Telephone: Fairseat 822503.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £2.00 per annum. (U.K. and British Commonwealth), overseas 6 Dollars or £2.50. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

WANTED: Early books on wireless, pre-1925. Details to Box No. G198.

WANTED: *Wireless World* issues wanted July 1971 to April 1972 inclusive, together with June 1972. Also *Radio Constructor* Volume 16. J. R. Ault, 23 Newton Street, West Bromwich, Staffs.

WANTED: Advertiser has built a sky survey camera for use by members of an Astronomical Society. It uses whole plate size photographic plates. Has anyone got any double-sided whole plate holders please? Box No. G.199.

TELSEN, LISSEN, GRAHAM FARISH bakelite phenolic components with terminals required. Birkinshaw, 219 Teagues Crescent, Telford, Salop., TF2 6RA.

AERIAL BOOSTERS. L45 - 625 UHF Television, L12 - 405 Television, L11 - VHF Radio, Price £2.95. Resistors, capacitors and television valves sold in bargain parcels. S.A.E. for free leaflets. VELCO ELECTRONICS, Bridge Street, Ramsbottom, Bury, Lancs.

FOR CONSTRUCTORS, Inventors and Small Manufacturers. A self-employed precision instrument maker can undertake development/prototype work. 'Specials' and small batch production of machined components. Box No. G201.

WORLD DX CLUB covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.38 a year. Enquiries to Secretary, WDXC, 11 Wesley Grove, Portsmouth, Hants., PO3 5ER.

MULLARD MODULE LP1153 ½ watt output into 8 ohms 9 volt supply, brand new with data 70p. post paid. Transistor ignition £9.50; kit £7.50. S.A.E. lists. C. & W. Electronics, Unit 4, Meadow Road Industrial Estate, Worthing, Sussex.

(Continued on page 275)

NOVEMBER 1972

PRECISION

POLYCARBONATE CAPACITORS

Fresh Stock - Fully Tested and Guaranteed

Close tolerance professional capacitors by well-known manufacturer. Excellent stability and extremely low leakage. All 63V D.C.

0.47 µF:	±5% 30p;	±2% 40p;	±1% 50p
1.0 µF:	±5% 40p;	±2% 50p;	±1% 60p
2.2 µF:	±5% 50p;	±2% 60p;	±1% 75p
4.7 µF:	±5% 70p;	±2% 90p;	±1% 115p
6.8 µF:	±5% 95p;	±2% 115p;	±1% 150p
10.0 µF:	±5% 110p;	±2% 140p;	±1% 180p
15.0 µF:	±5% 160p;	±2% 210p;	±1% 270p

NEW! - TANTALUM BEAD CAPACITORS

Values available .22, .47, 1.0, 2.2, 4.7, 6.8 µF at 35V, 10 µF 25V, 15 µF 20V, 22 µF 15V, 33 µF 10V, 47 µF 6V, 100 µF 3V. All at 9p each; 6 for 50p; 14 for £1.00. Special pack, 6 off each value (72 capacitors) for £5.00.

TRANSISTORS: BC107; BC108; BC109 (please state which), all at 9p each. 6 for 50p; 14 for £1.00; May be mixed to qualify for lower price. All brand new to full manufacturer's specification.

POPULAR DIODES: IN914 - 7p each; 8 for 50p; 18 for £1.00. IN916 - 9p each; 6 for 50p; 14 for £1.00. IS44 - 5p each; 11 for 50p; 24 for £1.00. All brand new and marked.

400mW ZENER DIODES: Values available 4.7, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15 volts. All new and marked. All at 10p each; 6 for 50p; 14 for £1.00.

RESISTORS: Carbon film ½ watt 5%. Range 2.2Ω-2.2MΩ E12. Series i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades. All at 1p each. 8p for 10 of any one value; 70p for 100 of any one value. Special development pack 10 off each value 2.2Ω to 2.2MΩ (730 resistors) for £5.00.

440V A.C. CAPACITORS: 0.1 µF: Size 1¼" x ½", 25p each
0.25 µF: Size 1½" x ¾", 30p each 0.5 µF: Size 1¾" x ¾", 35p each
1.0 µF: Size 2" x ¾", 45p each 2.0 µF: Size 2" x 1", 75p each
Suitable for use on C.D. ignition, 250V A.C. motors, etc.

5p post and packing on all orders below £5

V.ATTWOOD, Dept C.5., P.O. Box 8, Alresford, Hants.

FREE TO AMBITIOUS ENGINEERS

- THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

SEND FOR YOUR FREE COPY TO-DAY

NEW OPPORTUNITIES is a highly informative 76 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern home study courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics courses administered by our Specialist Electronics Training Division - explains the benefits of our free Appointments and Advisory service and shows you how to qualify for five years promotion in one year.

PRACTICAL EQUIPMENT INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with all the practical equipment you need, plus basic practice and theoretical courses for beginners in Radio, TV, Electronics, etc.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. (B10), Aldermaston Court, Reading RG7 4PF

SEND OFF THIS COUPON TO-DAY!

Tick subjects that interest you:

AMSE (Elec) City & Guilds Certificate RTEB Certificate
Radio Amateurs' Exam DMG Certificate Colour TV
Electronic Engineering Computer Electronics Radio and TV
Servicing Practical Electronics Practical TV and Radio
Please send booklets & full information without cost or obligation.

NAME..... AGE.....

(BLOCK CAPITALS PLEASE)

ADDRESS



OCCUPATION.....

To: BIET Dept. B10, Aldermaston Court, Reading RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges

RADIO MODELLER

ELECTRONIC BOOKS



● MODEL RADIO CONTROL

Detailing both Theory and Practice, this book, by leading authority Paul Newell, will become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system. 134 pages. Price £2-25 U.K. Postage 13p

● SINGLET SET

The Singlet Transmitter, Superhet and Super-regen receivers, are now all three available in one book. Complete construction details with full size p.c. layout, components list etc. Ideal introduction to the hobby for the home constructor. 20 pages. Price 30p. U.K. Postage 3p

● LOW COST PROPORTIONAL

Modellers who want to save money buy this volume when converting single channel equipment to simple proportional. They find a wealth of really up to date information in the clear descriptions, full size practical and working drawings, plus over a dozen circuit modules for pulse proportional units. 118 pages. Price £1-05 U.K. Postage 11p




ON SALE NOW at all leading shops or direct from:-

RADIO MODELLER, BOOK SALES, 64 Wellington Road, Hampton Hill, Middx.

PLAIN-BACKED NEW STYLE SELF-BINDERS

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

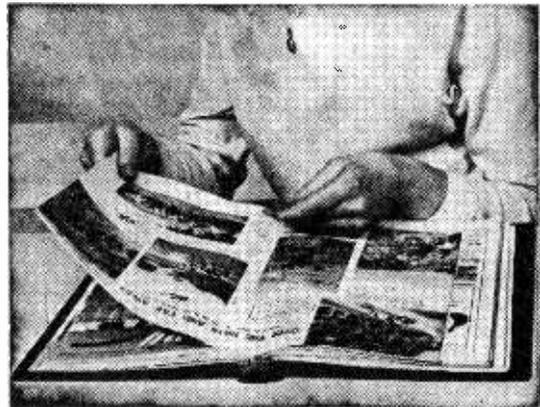for your other magazines
(max. format 7½" x 9½")



PRICE **70p** P. & P. 14p

Available only from:—

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

Data Publications Ltd. 57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 273)

TELEPRINTER EQUIPMENT FOR SALE: A 5ft. high cabinet, containing a 'teleprinter terminal', consisting of an AR88D receiver, three chassis above containing equipment, a main power unit below the receiver and three spare chassis below that. One chassis contains an 1800 cycle filter. Whole unit looks very smart. Each chassis comes out on runners. £65. S.A.E. for details. Box No. G202.

THE BRITISH AMATEUR ELECTRONICS CLUB. A club for all who are interested in electronics as a hobby. Quarterly Newsletter sent free to members. Subscription 50p per year. Details from Hon. Secretary, J. G. Margetts, 17 St. Francis Close, Abergavenny, Mon.

FOR SALE: Teleprinter 75R, £17.00. S.A.E. for all details. Box No. G203.

COMPONENTS GALORE. Pack of 500 mixed components, manufacturer's surplus plus once used. Pack includes resistors, capacitors, transistors, I.C., gang pots., etc. Tremendous value. Send £1 inc. postage. C.W.O. To: Caledonian Components, Fosterton Firs, Strathmore Road, Thornton, Fife.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

RECITALS OF RECORDED MUSIC. The second Saturday evening of each winter month. Next recital: November 11th, 1972, 8 p.m. at Woodford Green United Free Church Woodford Green, Essex. Bus routes 20, 20A, 179 and 275 - alight at "The Castle" stop. Programme consists of works by Mendelssohn, Richard Strauss, Poulenc & Brahms.

TWIN LEAD. 7A. 250V. White sheath. May be used as 50Ω feeder. Approx. 1dB loss per 100 feet at 30MHz. Easily split apart. 30m. - £1.00, 100m. - £2.50. Messrs. Burns Electronics, The Cottage, 35 Beulah Hill, London SE19 3LR.

FIBREGLASS CIRCUIT BOARD. 5p.-12 square ins., 50p. square foot. Double 8p. - 12 square ins., 70p. square foot. Post 10p. BRB, 17 Southbreck Rise, Worksop, Notts., S80 2UP.

FOR SALE: Ex-Government miniature oscilloscope. General purpose type with optical magnifier. Working order. £18 o.n.o. Carriage extra or collect Middlesex. Box No. G204.

SITUATIONS VACANT

BBC requires Monitor for the Special Listening Section of its Monitoring Service at Caversham, near Reading, Berks. Duties include checking of voice transmissions, compiling schedules and writing short listening observations and, at times, to ensure that Language Monitors obtain the best possible reception of foreign broadcasts covered. Some shift work involved and possibility of tours of duty overseas. An interest in international broadcasting, ability to operate communications receivers and other monitoring equipment, and to identify the main languages is essential, and knowledge of at least one foreign language an advantage. Shortlisted candidates may be required to undergo tests. Starting salary £2,100 p.a. rising by annual increments of £117 to £2,685 p.a. plus 15% irregular hour working allowance. Write for application form to Personnel Assistant, BBC, Caversham Park, Reading RG4 8TZ.

REVERBERATION UNIT KIT Mk III

6 transistor reverberation chamber to which microphones, instruments, etc., may be connected for added dimensional effect. The output is suitable for most amplifiers and the unit is especially suitable for use with electronic organs. A ready-built spring and transducer assembly is used. Complete easy-to-build kit, with constructional notes and circuits £7.50. Pre-drilled and printed case £2.00 extra. All parts available separately.




WAH-WAH PEDAL KIT Mk III



The Wilsic Wah-Wah pedal comprises a SELECTIVE AMPLIFIER MODULE KIT, containing all the components to build a two transistor circuit module, which may be used by the constructor for his own design or fitted to the FOOT VOLUME CONTROL PEDAL (as photo) converting it to Wah-Wah operation. This pedal is in strong fawn plastic and fitted with output lead and screened plug. Selective amplifier module kit £1.75. Foot Volume control pedal £5.13. COMPLETE KIT £6.50. Add 38p for assembly of module.

WILSIC VIBRATO UNIT

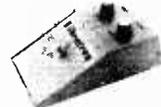A new kit to build a self-contained vibrato foot switch unit. 4-silicon transistor circuit in tough grey hammered finish metal cabinet. Variable speed and depth controls and on-off foot switch. Ideal for guitars but unsuitable for high level inputs. COMPLETE KIT £5.25, all parts available separately.



THE WILSIC BOOK OF CIRCUITS contains the full instructions for the Reverb unit, Wah-Wah pedal and our Vibrato unit. PRICE ONLY 15p

SEND 5p in stamps for latest catalogue (Spring 1972) of Hi-Fi, components, guitars, etc., etc. Friendly, high-speed service.



WILSIC ELECTRONICS LTD.

6 COPLEY ROAD, DONCASTER, YORKS

ESSENTIAL BOOKS

MOBILE RADIO TELEPHONES. Important reference book for users of commercial mobile communications equipment. Includes chapters on installation, operation & maintenance. Contains photos and diagrams etc. Price £2.60 incl. postage.

GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Contains circuits, data, illustrations and valuable information for British/USA receivers, transmitters, trans/receivers. With modifications to sets and test equipment. Latest impression £3.25 including postage.

WORLDS SHORT WAVE MEDIUM & LONG WAVE RADIO STATIONS & FM & TV LISTING. Only 40p incl. postage.

HANDBOOK OF TRANSISTOR SUBSTITUTES AND EQUIVALENTS by B. B. Babani. Includes many thousands of British, USA and Japanese Transistors. 78 pages. Only 40p., post & packing 5p. Available from GERALD MYERS (RC), 18, Shaftesbury Street, Leeds LS12 3BT. Please include extra postage for abroad.

MORSE MADE EASY!!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.) Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without transmitting. You can't help it, it's as easy as learning a tune. 18-W.P.M. In 4 weeks guaranteed. Beginner's Section only £3.50. Complete course £4.50 (Overseas £1 extra). Details only, 4p stamp. 01-660 2896

G3HSC/Box 38, 45 GREEN LANE, PURLEY, SURREY.

SYNTHESISER MODULES

Voltage-controlled modules for synthesiser construction and other musical MIRACLES! Catalogue 15p. D.E.W. Ltd., 264 Ringwood Road, Ferndown, Dorset.

INTERNATIONAL SHORT WAVE LEAGUE



Membership £2.00 per annum (U.S.A. \$6.00) including 12 monthly issues of "Monitor" – the League journal. Including free use of all Services, QSL Bureau etc.

THE LARGEST S.W.L. ORGANISATION IN THE WORLD

For full details write to:
The Secretary, I.S.W.L., 1 GROVE ROAD, LYDNEY, GLOS. GL15 5JE.

YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY -
 Get these air drying GREY HAMMER BLACK WRINKLE OR (CRACKLE) finishes NOW!

Yukan Aerosol spraykit contains 453g. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey and blue. 90p cart. pd. Modern Eggshell Black Wrinkle (Crackle) producing a 3D textured finish. 90p cart. pd. all at 85p per push-button self-spray can at our counter. Also durable, heat and water resistant Black Matt finish (339g. self-spray cans only) 75p cart. pd.
 SPECIAL OFFER: One can plus optional transferable snap-on trigger handle (value 25p) for 95p cart. pd. Choice of 13 self-spray plain colours and primer (motor car quality) also available.
 Please enclose cheque or crossed P.O. for total amount direct to:
DEPT: RC/11 YUKAN, 307a EDGWARE ROAD, LONDON W21 1BN
 We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too. Now British—Open all day Saturday. Closed Thursday afternoons. *Now British—even better*

Other Yukan Air Drying Aerosols. 453g. at 90p cart. pd. Includes: Zinc Chromate, Clean Lacquer, Metallic: Grey, Blue.

Closed ALL DECEMBER for annual holiday

BRAND NEW MAINS INTERCOM. British made ideal for home/office/factory/shop or baby alarm. Plugs in to ANY power or light socket. No long trailing wires to fix, fully transistorised, the unit is housed in a two-tone brown colour case. The Intercom includes 1 master and 1 slave. It will make a very appreciative Xmas gift and it is offered at a fraction of the cost of some imported sets.

£9.50 + 25p post.

SOKSOL DE-SOLDER KIT. Here is a kit that is a must for every service engineer and electronic project constructor. You make it up to your own exacting requirements. It de-solders transistors, I.C.'s, those wrap-round solder joints on switches, potentiometers, transformers, etc., etc. Simple to use. You just drop special braid in the supplied chemical solution, pull out and allow to dry. When ready to use just simply place braid on device to be de-soldered, apply soldering iron to braid and the rest is sheer magic as all solder is soaked up in seconds. The kit includes 20 feet of special braid, Chemical solution and full instructions. £1.00, post 15p. Money back guarantee if dissatisfied.

ELEKON ENTERPRISES, 224A ST. PAUL'S ROAD, HIGHBURY CORNER, LONDON N.1

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
124 pages. Price 50p, postage 6p.
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**
80 pages. Price 45p, postage 6p.
- DB16 RADIO CONTROL FOR MODELS**
192 pages. Price 75p, postage 8p.
- DB17 UNDERSTANDING TELEVISION**
512 pages. Price £2.10, postage 25p.
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 53p, postage 6p.
- DB19 SIMPLE SHORT WAVE RECEIVERS**
140 pages. Price 80p, postage 6p.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable from your local bookseller.

Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please mention **THE RADIO CONSTRUCTOR** when writing to advertisers

U.K.'s LARGEST ELECTRONICS CENTRES!

HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.



NOW OPEN!

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381
 354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736
 309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963
 303 BARGAIN STORE SPECIAL OFFERS All Mail to: 303, Edgware Rd., London, W2 1BW

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

BUILD THE TEAKAN

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER



FREE TEAK CABINET with complete kits
FEATURES New slim design with 6 I.C.s, IC sockets, 10 silicon transformers, 4 rectifiers, 2 zeners, Special Gardeners low field slim line transformer Fibreglass P.C. panel. Complete chassis work
HIGH QUALITY AND STABILITY ARE PREDOMINANT FEATURES DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.
FACILITIES On/off switch indicator, headphone socket, separate treble bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector, Mag P.U. Radio Tuner, Aux. Can be altered for (i/c, Tape, Tape head etc. (Plans list Ref. 20 on request)
 (Plans list Ref. 20 on request)
 Constructional details Ref. No. 21 30p
 Design approved kits distributed by Henry's Radio Ltd.

(As featured in "Practical Wireless" May to August 1972)

SPECIAL KIT PRICE
£28.50 P&P 45p

SLIM DESIGN WITH SILVER TRIM
 Overall chassis size 14½" x 6" x 2" high

(Complete with FREE TEAK CABINET)

RECORD DECKS CHASSIS

SP25/3	£10.25	H770	£14.50
MP60	£9.95	MP610	£12.95
AP76	£17.95	GL75	£28.50
P.L.I.N.T.H. COVERS (State Model)			
SP25/MP60/610	£3.30 (Post 40p)		
AP76	£4.50 (Post 40p)		
CART/P.L.I.N.T.H. COVER (Post 70p)			
(HL) MP60/G800/PC	£18.50		
MP610/SC5MD/TPD2/PC	£19.95		
AP76/M7565M/PC	£32.50		
AP76/M7565M/PC	£38.95		
(HL) AP76/G800/PC	£28.50		
(HL) SP25/G800/PC	£18.95		
HT70/G800/TPD1/PC	£24.50		
(HL) 2025/9TANCD/PC	£13.95		
MP60/SC5MD/PC	£17.25		
(HL) GL75/G800/PC	£41.95		
(HL) GL75/G800/PC	£38.95		

ULTRASONIC TRANSDUCERS

Operate at 40Kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.
PRICE PER PAIR £3.90 Post 10p

POWER INTEGRATED CIRCUITS

Plessey SL403D - 3 watt with 8 page data, layouts and circuits £1.50 P.C. Board 60p.
 Mean Sink 14p.
 Sinclair IC12 - 6 watt with data and circuits £1.80.
 TH5013P - 20 watt Power Amp Module £4.57.
 TH5014P - IC Preamp 10W £1.50.
 Data/Circuits for above No. 42 10p.

MARRIOTT TAPE HEADS 4 TRACK MONO OR 2 TRACK STEREO

'17 High Impedance	£2.00
'18 Med Impedance	£2.00
'36 Med Low Imp	£3.50
Eraser Heads for above	75p
'63' 2 track mono - Hi Imp.	£1.75
'43' Erase Head for above	75p

7 SEG & NIXIE TUBES

(Post 15p per 100)
 NX3 NX13 GN40 - 9 Side view with data 85p
 GNP 7 GNP 8 0-9 Side view with decimal points and data 95p
 3015P 7-segment LED each £7 per 4 with data.
 12 and 24 hour clock circuits for above. Ref. No. 31 15p.

MINIATURE AMPLIFIER

5 transistor, 300mW o/p. Fitted volume and sensitivity control. 9 volt operated.
£1.75 each P/P 15p

QUALITY SLIDER CONTROLS

60mm stroke sliders and ganged. Complete with knobs 5K, 10K, 25K, 100K, 250K, 500K, 1 meg. Log and Lin. 45p each. 10K, 25K, 50K, 100K, 250K Log and Lin. ganged. 75p each.

HI-FI & TAPE EQUIPMENT

Acknowledged as UK's largest stockists with lowest prices plus 12 months guarantee. Write or call for FREE 16 page lists (Ref 17)

TRANSISTORS IC'S RECTIFIERS SCR'S TRIACS etc.

LATEST BROCHURE Ref. No. 36 on request

LOW COST HI-FI SPEAKERS

E.M.I. Size 13½" x 8½". Large Ceramic Magnet.
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20, Post 22p.
TYPE 150TC Twin cone version £2.75, Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms £3.85, Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms £7.70, Post 28p.



POLISHED CABINETS 150 150TC 450 £4.60 Post 30p
 ASSEMBLED IN POLISHED CABINET 15 (8 ohm)
 Simul 4 (Assembled 150TC) per pair £16.50 post 70p
 Series 8 (Assembled 450) per pair £18.95 post 70p



NEW MW/LW TUNER TO BUILD ML-3

Uses Mullard Module. Slow motion tuning.
 Built in battery. Ferrite aerial. Overall size 7" x 2½" x 3½".
TOTAL COST TO BUILD £4.85 Post 15p. All parts sold separate y - Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF IF. Medium, Medium and Long Wave bands plus Medium Wave Bandspread for extra sensitivity. Also slow motion geared tuning, 600mV push pull output, fibre glass PVC covering cabinet for aerial socket. Attractive appearance and performance. **TOTAL COST TO BUILD £7.98** p.p. 15p. (Battery 72p). All parts sold separately. Leaflet No. 2



CATALOGUE

Fully detailed and illustrated covering every aspect of Elec.ronics. Plus data, circuits and information.

10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p Post Paid (40p FOR CALLERS)
PLUS! FIVE 10p VOUCHERS

Send to this address - Henry's Radio Ltd. (Dept. RC), 3 Albemarle Way, London, E.C1 - for catalogue by post only. All other mail and callers to '303' see above.

TEST EQUIPMENT

JUST A SELECTION

SE2508	Pocket Pencil Signal Injector	£1.90
SE500	Pocket Pentol Signal Tracer	£1.50
1HL330	Reinust 2K Volt	£4.55
TE115	Grid Dip Meter 440 KHz, 280 mHz	£13.45
500	20 K Volt Multimeter £9.25	With leather case £10.50
200H	20K Volt Multimeter £4.20	With case £4.95
AF105	50K Volt Multimeter £8.50	With case £9.50
U4311	AC DC Multimeter with transistor tester	£10.50
TE120	RT Generator 120KHz, 500Mhz Car 35p	£15.95
TE22D	Audio Generator 20Hz, 200KHz Car 35p	£17.50
U15	3 Pulse Scope 10Hz, 10mHz Car 50p	£39.00
TE65	Valve Voltmeter 28 ranges Car 40p	£17.50

ALL NOMBREX MODELS IN STOCK



BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BAND-WIDTH PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO.

A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. **TOTAL £6.97**, p.p. 20p. Decoder Kit £5.97. Tuning meter unit £1.75. Mains unit (optional) Model PS900 £2.47. Post 20p. Mains unit for Tuner and Decoder PS1200 £2.62. Post 20p.



PA-DISCO-LIGHTING

UK's Largest Range. Write phone or call in. Details and demonstrations on request.

DJ30L	3 Channel sound to light unit 3Kw	£29.75
DJ40L	3 Channel Mic (built in) to light 3 Kw	£38.75
DJ705	70 watt Disco amp/mixer	£49.95
DISCOAMP	100 watt Disco amp/mixer	£67.95
DJ105S	30 watt Disco amp/mixer	£32.75
Anti-Feedback Quality Mic		£11.50
DJ500	50 watt P.A. Amp	£56.25
DJ300	150 watt rms Group Valve Amp	£99.50

Everything for PA Disco Lighting FREE Sineck List Ref. No. 18



SINCLAIR PROJECT 60 MODULES

- SAVE POUNDS

Z30 £3.57	Z50 £4.37
STEREO 60 £7.97	P25 £3.97
P26 £6.37	P28 £4.77
Transformer for P28 £2.95	
Active Filter Unit £4.45	
Stereo FM Tuner £16.95	
IC12 £1.80	Q16's £15 pr

Post etc 20p per item

PACKAGE DEALS Post 25p.
 2 x Z30 Stereo 60 P25 £15.95
 2 x Z30 Stereo 60 P26 £18.00
 2 x Z50 Stereo 60 P28 £20.25
 Transformer for P28 £2.95
 PROJECT 605 KIT £19.95



MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

All the parts you need plus Data and Circuits. Get a Catalogue - it's all in there!

Pages subject to change without notice. £ 60 F. 309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday

H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H