


# RADIO & ELECTRONICS CONSTRUCTOR

NOVEMBER 1974

25p



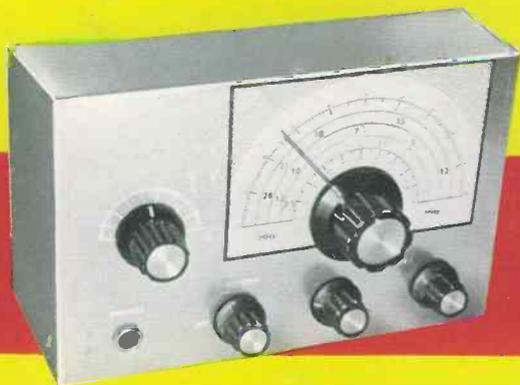
**DIRECT  
READING  
CAPACITANCE  
METER**



**REFLEX SHORT WAVE RECEIVER**

**ALSO  
FEATURED**

**BATTERY MISER**

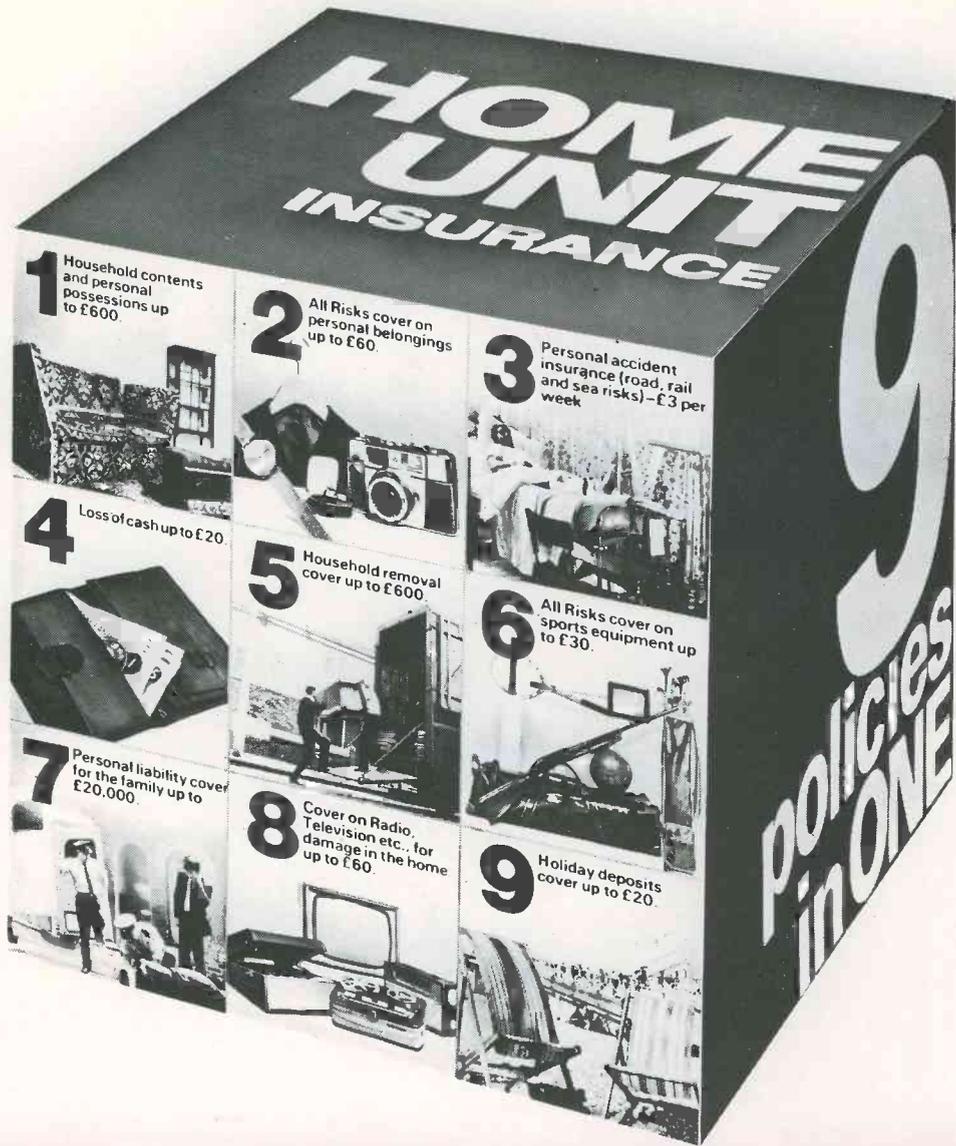

## Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. **And it's how we save you so much money: just ONE policy to issue instead of nine!** You can build up to the cover you need by additional units

(or  $\frac{1}{2}$  units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company.

The Home Unit Policy can replace your existing insurances. And remember - as you buy more possessions just add more Home Units at any time. *Quote Ref. 20/9468*

## THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,  
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

20/9468

# DENCO (CLACTON) LIMITED

## 355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX


Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	..	24p
DTB4 Transistor & Valve circuitry for D.P. Coils	..	24p
DTB9 Valve Type Coil Pack Application circuitry	..	24p
MD 1 Decoder Circuitry for Stereo Reception	..	24p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers
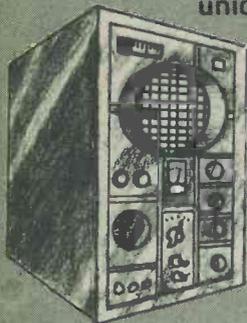
## 1. Understand electronics.

Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

## 2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



WAA

**Free!**

Brochure, without obligation to:  
**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept AX 1174**  
P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Block caps please

# The Largest Selection

BRAND NEW FULLY GUARANTEED DEVICES

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	0.22	AD181	0.22	BD131	0.22	BF182	0.44	MJE2955	0.95	2C308	0.39	2N2192	0.39	2N3381	0.16	2N4060	0.13
AC113	0.20	AD182(MP)	0.75	BD132	0.66	BF183	0.44	MJE2956	0.62	2C309	0.39	2N2193	0.39	2N3381A	0.18	2N4061	0.13
AC115	0.22	AD1740	0.55	BD133	0.72	BF184	0.28	MJE3440	0.55	2C339	0.22	2N2194	0.39	2N3382	0.16	2N4062	0.13
AC128	0.20	AF124	0.93	BD135	0.44	BF185	0.44	MPE102	0.46	2C338A	0.18	2N2217	0.24	2N3383	0.16	2N4284	0.19
AC127K	0.13	AF116	0.27	BD136	0.44	BF187	0.30	MPE105	0.41	2C344	0.18	2N2218	0.22	2N3384	0.16	2N4285	0.19
AC125	0.19	AF116	0.27	BD137	0.50	BF188	0.44	MPE105	0.41	2C345	0.18	2N2219	0.22	2N3385	0.19	2N4286	0.19
AC126	0.19	AF117	0.27	BD138	0.55	BF194	0.13	OC20	0.39	2C371	0.18	2N2220	0.24	2N3402	0.23	2N4287	0.19
AC127	0.20	AF118	0.39	BD139	0.61	BF195	0.13	OC212	0.70	2C371B	0.13	2N2221	0.22	2N3403	0.23	2N4288	0.19
AC128	0.20	AF124	0.93	BD140	0.66	BF196	0.16	OC22	0.52	2C373	0.19	2N2222	0.22	2N3404	0.21	2N4289	0.19
AC132	0.16	AF125	0.33	BD145	0.88	BF197	0.16	OC23	0.54	2C374	0.19	2N2268	0.19	2N3405	0.46	2N4290	0.19
AC134	0.16	AF128	0.31	BD175	0.66	BF200	0.50	OC24	0.62	2C377	0.33	2N2369	0.16	2N3414	0.17	2N4291	0.19
AC137	0.16	AF127	0.31	BD176	0.66	BF222	1.05	OC26	0.42	2C378	0.18	2N2369A	0.16	2N3415	0.17	2N4292	0.19
AC141	0.20	AF139	0.53	BD177	0.72	BF257	0.50	OC28	0.23	2C381	0.18	2N2413	0.27	2N3416	0.21	2N4293	0.19
AC141K	0.32	AF178	0.53	BD178	0.72	BF258	0.66	OC28	0.55	2C382	0.18	2N2412	0.27	2N3417	0.21	2N4294	0.19
AC142	0.20	AF179	0.55	BD179	0.77	BF259	0.94	OC29	0.55	2C401	0.33	2N2646	0.52	2N3525	0.83	2N5294	0.60
AC142K	0.28	AF180	0.55	BD180	0.77	BF262	0.61	OC35	0.46	2G414	0.33	2N2711	0.23	2N3614	0.74	2N5457	0.35
AC151	0.17	AF181	0.55	BD185	0.72	BF263	0.61	OC36	0.55	2G417	0.28	2N2712	0.23	2N3615	0.52	2N5458	0.35
AC154	0.22	AF186	0.55	BD186	0.72	BF270	0.39	OC41	0.22	2N388	0.39	2N2714	0.23	2N3616	0.82	2N5459	0.44
AC155	0.22	AF239	0.41	BD187	0.77	BF271	0.33	OC42	0.27	2N388A	0.61	2N2904	0.19	2N3644	0.10	2N6221	0.75
AC156	0.22	AL102	0.72	BD188	0.77	BF272	0.88	OC44	0.17	2N404	0.22	2N2904A	0.23	2N3702	0.13	2S301	0.55
AC157	0.27	AL103	0.72	BD189	0.83	BF273	0.39	OC45	0.14	2N404A	0.31	2N2905	0.23	2N3703	0.13	2S302A	0.46
AC165	0.22	ASV26	0.28	BD190	0.83	BF274	0.39	OC70	0.11	2N624	0.46	2N2905A	0.23	2N3704	0.14	2S303	0.46
AC166	0.22	ASV27	0.33	BD195	0.61	BF280	1.05	OC71	0.56	2N698	0.46	2N2906	0.17	2N3705	0.13	2S304	0.62
AC167	0.22	ASV28	0.28	BD196	0.94	BFX29	0.30	OC72	0.16	2N598	0.46	2N2906A	0.20	2N3706	0.13	2S304	0.77
AC168	0.27	ASV29	0.28	BD197	0.99	BFX84	0.24	OC74	0.16	2N599	0.50	2N2907	0.22	2N3707	0.14	2S305	0.86
AC169	0.18	ASV50	0.28	BD198	0.99	BFX85	0.33	OC75	0.17	2N598	0.14	2N2907A	0.24	2N3708	0.09	2S306	0.86
AC176	0.22	ASV71	0.28	BD199	1.05	BFX86	0.24	OC76	0.12	2N598	0.14	2N2908	0.15	2N3709	0.10	2S307	0.86
AC177	0.27	ASV72	0.28	BD200	1.05	BFX87	0.27	OC77	0.28	2N598	0.57	2N2924	0.16	2N3710	0.10	2S321	0.62
AC178	0.31	ASV54	0.28	BD205	0.88	BFX88	0.24	OC81	0.17	2N699	0.39	2N2925	0.16	2N3711	0.10	2S322	0.46
AC179	0.31	ASV55	0.28	BD206	0.88	BFY50	0.22	OC81D	0.17	2N706	0.09	2N2926(G)	0.14	2N3819	0.31	2S322A	0.46
AC180	0.22	ASV56	0.28	BD207	1.05	BFY51	0.22	OC82	0.17	2N706A	0.10	2N2926(R)	0.12	2N3820	0.55	2S323	0.62
AC180K	0.32	ASV57	0.28	BD208	1.05	BFY52	0.22	OC82D	0.20	2N708	0.33	2N2926(O)	0.17	2N3821	0.39	2S324	0.77
AC181	0.22	ASV58	0.28	BDY20	1.10	BFY53	0.18	OC83	0.22	2N711	0.33	2N2926(R)	0.11	2N3823	0.31	2S325	0.62
AC181K	0.32	ASV73	0.28	BF115	0.27	BSX19	0.17	OC39	0.22	2N717	0.39	2N2926(B)	0.11	2N3903	0.31	2S326	0.77
AC187	0.24	ASZ21	0.44	BF117	0.50	BSX20	0.17	OC40	0.22	2N718	0.27	2N3910	0.77	2N3904	0.33	2S327	0.77
AC187K	0.25	BC107	0.14	BF118	0.77	BSY25	0.17	OC69	0.28	2N718A	0.55	2N3905	0.11	2N3905	0.31	2S328	0.77
AC188	0.25	BC108	0.14	BF119	0.77	BSY26	0.17	OC70	0.28	2N718A	0.55	2N3906	0.11	2N3906	0.31	2S329	0.77
AC188K	0.25	BC109	0.15	BF121	0.50	BSY27	0.17	OC71	0.28	2N727	0.31	2N3905A	0.19	2N4058	0.10	40381	0.44
AC171	0.28	BC113	0.11	BF122	0.55	BSY28	0.17	OC200	0.28	2N743	0.22	2N3905A	0.55	2N4059	0.11	40362	0.50
AC187	0.25	BC107	0.14	BF125	0.50	BSY29	0.17	OC201	0.31	2N744	0.22	OC202	0.31	2N814	0.18		
AC187K	0.25	BC108	0.14	BF126	0.50	BSY30	0.17	OC203	0.31	2N814	0.18	OC204	0.28	2N929	0.23	AA119	0.09
AC188K	0.25	BC109	0.15	BF127	0.55	BSY31	0.17	OC205	0.39	2N930	0.23	AA120	0.09	BY133	0.23	OA10	0.15
AC171	0.28	BC113	0.11	BF128	0.55	BSY32	0.17	OC206	0.39	2N930	0.23	AA121	0.09	BY130	0.18	OA47	0.08
AC187	0.25	BC107	0.14	BF129	0.55	BSY33	0.17	OC207	0.39	2N930	0.23	AA122	0.09	BY133	0.23	OA70	0.08
AC187K	0.25	BC108	0.14	BF130	0.55	BSY34	0.17	OC208	0.39	2N930	0.23	AA123	0.09	BY133	0.23	OA70	0.08
AC188K	0.25	BC109	0.15	BF131	0.55	BSY35	0.17	OC209	0.39	2N930	0.23	AA124	0.09	BY133	0.23	OA70	0.08
AC171	0.28	BC113	0.11	BF132	0.55	BSY36	0.17	OC210	0.39	2N930	0.23	AA125	0.09	BY133	0.23	OA70	0.08
AC187	0.25	BC107	0.14	BF133	0.55	BSY37	0.17	OC211	0.39	2N930	0.23	AA126	0.09	BY133	0.23	OA70	0.08
AC187K	0.25	BC108	0.14	BF134	0.55	BSY38	0.17	OC212	0.39	2N930	0.23	AA127	0.09	BY133	0.23	OA70	0.08
AC188K	0.25	BC109	0.15	BF135	0.55	BSY39	0.17	OC213	0.39	2N930	0.23	AA128	0.09	BY133	0.23	OA70	0.08
AC171	0.28	BC113	0.11	BF136	0.55	BSY40	0.17	OC214	0.39	2N930	0.23	AA129	0.09	BY133	0.23	OA70	0.08
AC187	0.25	BC107	0.14	BF137	0.55	BSY41	0.17	OC215	0.39	2N930	0.23	AA130	0.09	BY133	0.23	OA70	0.08
AC187K	0.25	BC108	0.14	BF138	0.55	BSY42	0.17	OC216	0.39	2N930	0.23	AA131	0.09	BY133	0.23	OA70	0.08
AC188K	0.25	BC109	0.15	BF139	0.55	BSY43	0.17	OC217	0.39	2N930	0.23	AA132	0.09	BY133	0.23	OA70	0.08
AC171	0.28	BC113	0.11	BF140	0.55	BSY44	0.17	OC218	0.39	2N930	0.23	AA133	0.09	BY133	0.23	OA70	0.08
AC187	0.25	BC107	0.14	BF141	0.55	BSY45	0.17	OC219	0.39	2N930	0.23	AA134	0.09	BY133	0.23	OA70	0.08
AC187K	0.25	BC108	0.14	BF142	0.55	BSY46	0.17	OC220	0.39	2N930	0.23	AA135	0.09	BY133	0.23	OA70	0.08
AC188K	0.25	BC109	0.15	BF143	0.55	BSY47	0.17	OC221	0.39	2N930	0.23	AA136	0.09	BY133	0.23	OA70	0.08
AC171	0.28	BC113	0.11	BF144	0.55	BSY48	0.17	OC222	0.39	2N930	0.23	AA137	0.09	BY133	0.23	OA70	0.08
AC187	0.25	BC107	0.14	BF145	0.55	BSY49	0.17	OC223	0.39	2N930	0.23	AA138	0.09	BY133	0.23	OA70	0.08
AC187K	0.25	BC108	0.14	BF146	0.55	BSY50	0.17	OC224	0.39	2N930	0.23	AA139	0.09	BY133	0.23	OA70	0.08
AC188K	0.25	BC109	0.15	BF147	0.55	BSY51	0.17	OC225	0.39	2N930	0.23	AA140	0.09	BY133	0.23	OA70	0.08
AC171	0.28	BC113	0.11	BF148	0.55	BSY52	0.17	OC226	0.39	2N930	0.23	AA141	0.09	BY133	0.23	OA70	0.08
AC187	0.25	BC107	0.14	BF149	0.55	BSY53	0.										

# -the lowest prices!

## P.W. TELE-TENNIS KIT OF PARTS

Including all resistors, capacitors, semi-conductors, I.C. sockets, switches and transformer

Our Usual Price £27.50

**SPECIAL OFFER**  
**£23.50** incl. V.A.T. and P. & P.

We regret free pack not applicable to this offer

**ND 120 MIXIE DRIVER TRANSISTOR**  
Suitable replacement for BSX 21, C 407, 2N 1893 120evb.  
1 25 100+  
0.19 0.17 0.16

Sil. trans. suitable for PE Organ. Metal To-18 Eqty. ZTX300 6p each. Any Qty.

**GP 100 TOS METAL CASE GERMANIUM**  
V<sub>beo</sub> = 80V. V<sub>ceo</sub> = 50V. I<sub>C</sub> = 10 amps. P<sub>tot</sub> = 30 W. h<sub>fe</sub> = 30-170.  
Replaces the majority of Germanium power transistors in the OC, AD and NKT range.  
1 25 100+  
0.47 0.44 0.40

**GP 300 TOS METAL CASE SILICON**  
V<sub>beo</sub> = 100V. V<sub>ceo</sub> = 60V. I<sub>C</sub> = 15 amps. P<sub>tot</sub> = 115W. h<sub>fe</sub> = 20, 100FT.  
1MHz. Suitable replacement for 2N 3055, BLY 11 or BDY 20.  
1 25 100+  
0.53 0.53 0.51

### NEW 8th EDITION

250 pages  
**TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to B.I. PAK £1.85 each.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX. STOCK. SEND FOR FREE LIST.

### INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	12 x 7400	0.55	UIC46	5 x 7446	0.55	UIC90	5 x 7490	0.55
UIC01	12 x 7401	0.55	UIC48	5 x 7448	0.55	UIC91	5 x 7491	0.55
UIC02	12 x 7402	0.55	UIC50	12 x 7450	0.55	UIC92	5 x 7492	0.55
UIC03	12 x 7403	0.55	UIC51	12 x 7451	0.55	UIC93	5 x 7493	0.55
UIC04	12 x 7404	0.55	UIC53	12 x 7453	0.55	UIC94	5 x 7494	0.55
UIC05	12 x 7405	0.55	UIC54	12 x 7454	0.55	UIC95	5 x 7495	0.55
UIC06	8 x 7406	0.55	UIC60	12 x 7460	0.55	UIC96	5 x 7496	0.55
UIC07	8 x 7407	0.55	UIC70	8 x 7470	0.55	UIC100	5 x 74100	0.55
UIC10	12 x 7410	0.55	UIC72	8 x 7472	0.55	UIC121	5 x 74121	0.55
UIC20	12 x 7420	0.55	UIC73	8 x 7473	0.55	UIC141	5 x 74141	0.55
UIC30	12 x 7430	0.55	UIC74	8 x 7474	0.55	UIC151	5 x 74151	0.55
UIC40	12 x 7440	0.55	UIC76	8 x 7476	0.55	UIC154	5 x 74154	0.55
UIC41	5 x 7441	0.55	UIC80	5 x 7480	0.55	UIC193	5 x 74193	0.55
UIC42	5 x 7442	0.55	UIC81	5 x 7481	0.55	UIC199	5 x 74199	0.55
UIC43	5 x 7443	0.55	UIC82	5 x 7482	0.55			
UIC44	5 x 7444	0.55	UIC83	5 x 7483	0.55	UICX25	25 assorted	74's £1.65
UIC45	5 x 7445	0.55	UIC86	5 x 7486	0.55			

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

2 Amp. BRIDGE RECTS.	D1699 NPN SILICON	LINEAR INTEGRATED CIRCUIT PAKS
50 v RMS 35p each	DUAL TRANSISTOR	ULIC700 10 - 709 . . . . . 0.55
100 v RMS 41p . . . . .	(Similar to 2N2060)	ULIC710 7 - 710 . . . . . 0.55
200 v RMS 45p . . . . .		ULIC741 7 - 741 . . . . . 0.55
400 v RMS 50p . . . . .		ULIC747 5 - 747 . . . . . 0.55
1000 v RMS 55p . . . . .		ULIC748 7 - 748 . . . . . 0.55
Size 16 mm x 16 mm.		

### QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price 5p
Q 1 20	Red spot transistor PNP	0.55
Q 2 16	White spot R.F. transistors PNP	0.55
Q 3 4	OC71 type transistors	0.55
Q 4 6	Matched transistors OC44/45/81/81D	0.55
Q 5 4	OC75 transistors	0.55
Q 6 5	OC72 transistors	0.55
Q 7 4	AC128 transistors PNP high gain	0.55
Q 8 4	AC128 transistors PNP	0.55
Q 9 7	OC81 type transistors	0.55
Q 10 7	OC71 type transistors	0.55
Q 11 2	AC127/128 Complementary pairs PNP/NPN	0.55
Q 12 3	AF116 type transistors	0.55
Q 13 3	AF117 type transistors	0.55
Q 14 3	OC171 H.F. type transistors	0.55
Q 15 7	2N2928 Sil. Epoxy transistors mixed color resistors BVZ13	0.55
Q 17 5	NPN 2 x ST.148 & 3 x ST.140	0.55
Q 18 4	MADT's 2 x MAT 100 & 2 x MAT 120	0.55
Q 19 3	MADT's 2 x MAT 101 & 1 x MAT 121	0.55
Q 20 4	OC44 Germanium transistors A.F.	0.55
Q 21 4	AC127 NPN Germanium transistors	0.55
Q 22 20	NKT transistors A.F. R.F. coded	0.55
Q 23 10	OA202 Silicon diodes sub-min.	0.55
Q 24 8	OA81 diodes	0.55
Q 25 15	IN914 Silicon diodes 75PIV 75mA	0.55
Q 26 8	OA95 Germanium diodes sub-min IN69	0.55
Q 27 2	10A PIV Silicon rectifiers BS425R	0.55
Q 28 2	Silicon power rectifiers BVZ13	0.55
Q 29 4	Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.55
Q 30 7	Silicon switch transistors SN706 NPN	0.55
Q 31 6	Silicon switch transistors 2N708, NPN	0.55
Q 32 3	PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0.55
Q 33 3	Silicon NPN transistors 2N1711	0.55
Q 34 7	Silicon NPN transistors 2N2369, 500MHz (code P307)	0.55
Q 35 3	Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0.55
Q 36 7	2N3946 TO-18 plastic 300MHz NPN	0.55
Q 37 3	2N3953 NPN Silicon transistors	0.55
Q 38 7	PNP transistors 3 x 2N3703, 2 x 2N3702	0.55

**555 I.C. 65p each**

## MAMMOTH I.C. PACK

APPROXIMATELY 200 PIECES ASSORTED MANUFACTURERS FALL-OUT INTEGRATED CIRCUITS INCLUDING LOGIC 74 SERIES LINEAR and AUDIO AMPLIFIERS

MY CODED also SOME UNKNOWN TYPES - YOU TO IDENTIFY

PAK NO. M.I.C. 200

PRICE £1.25 per PAK including p & p & V.A.T.

1974 CATALOGUE NOW READY 10p

### NEW LOW PRICED TESTED S.C.R.'S

PIV	1A	3A	5A	7A	10A	16A	30A
T05T066	T066	T066	T064	T048	T048	T048	T048
50	0.28	0.28	0.39	0.39	0.52	0.55	0.59
100	0.28	0.37	0.62	0.62	0.52	0.64	0.70
200	0.39	0.41	0.54	0.54	0.63	0.67	0.63
400	0.48	0.52	0.62	0.62	0.74	0.83	1.03
600	0.59	0.63	0.75	0.75	0.85	1.07	1.38
800	0.70	0.77	0.88	0.88	0.99	1.32	1.65

### 2N3055

115 WATT SIL POWER NPN 55p EACH

## KING OF THE PAKS Unequaled Value and Quality

### SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Money back refund if not satisfied

Pak No.	Description	Price 5p
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.55
U 2	Mixed Germanium Transistors AF/RF	0.55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.55
U 4	Germanium Transistors like OC81, AC128	0.55
U 5	60 200mA Sub-Min. Silicon Diodes	0.55
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	0.55
U 7	18 Sil. Rectifiers TOP-HAT 750mA VLTR. RANGE up to 1000	0.55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.55
U 10	20 BAY50 charge storage Diodes DO-7 Glass	0.55
U 11	PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0.55
U 13	30 PNP-NPN Sil. Transistors OC200 & 25 104	0.55
U 14	150 Mixed Silicon and Germanium Diodes	0.55
U 15	NPN Sil. Planar Trans. TO-5 like BFY61, 2N697	0.55
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.55
U 17	30 Germanium PNP AF Transistors TO-5 like ACT 17-22	0.55
U 18	8 Amp Silicon Rectifiers BVZ13 Type up to 600 PIV	0.55
U 19	Silicon NPN Transistors like BC108	0.55
U 20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.55
U 21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0.55
U 23	MADT's like MHz Series PNP Transistors	0.55
U 24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.55
U 25	25 300MHz NPN Silicon Transistors 2N708, BSY27	0.55
U 26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.55
U 29	10 1 Amp SCR's TO-5 can, up to 600 PIV CRS1/25-800	1.10
U 32	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	0.55
U 33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.55
U 34	30 Silicon PNP Alloy Trans. TO-5 BCY28 2S302/4	0.55
U 35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.55
U 36	Silicon Planar NPN Transistors TO-5 BFY60/51/52	0.55
U 37	30 Silicon Alloy Transistors SO-2 PNP OC90, 2S322	0.55
U 38	20 Fast Switching Silicon Trans. NPN 400MHz 2N3011	0.55
U 39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0.55
U 40	10 Dual Transistors 8 lead TO-5 2N2060	0.55
U 43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.55
U 44	20 Sil. Trans. Plastic TO-5 BC116/116	0.55
U 45	7 3A SCR. T066 up to 600PIV	1.10
U 46	20 Unijunction transistors similar to TS143	0.55
U 47	10 TO220AB plastic triacs 50V 6A	0.55
U 48	9 NPN Sil. power transistors like 2N3055	1.10
U 49	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	1.10

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

### FREE

One 55p Pak of your own choice free with orders valued £4 or over.

### SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0.05	0.06	IN4001	0.05	0.08	0.15	0.21
100	0.05	0.07	IN4002	0.06	0.10	0.17	0.23
200	0.06	0.10	IN4003	0.07	0.12	0.22	0.25
400	0.08	0.15	IN4004	0.08	0.15	0.30	0.38
600	0.09	0.17	IN4005	0.10	0.18	0.38	0.45
800	0.12	0.19	IN4006	0.11	0.20	0.38	0.55
1000	0.14	0.30	IN4007	0.12	0.25	0.48	0.65
1200	—	0.35	—	0.30	0.58	0.75	0.90

### CADMIUM CELLS

ORP12 48p

### DIACS

FOR USE WITH TRIACS	VBOM 2A	6A	10A
BR100 (D32) 25p each	TO-5	TO-6	TO-48
10 amp POTTED BRIDGE RECTIFIER on heat sink	100	0.33	0.55
100PIV, 99p each	200	0.55	0.86
	400	0.77	0.83

All prices quoted in new pence Giro No. 388-7006 Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE - HERTS

Postage and packing add 10p Overseas add extra for airmail Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back



**"I MADE IT MYSELF"**

*Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.*

**Now! Learn the secrets of radio and electronics by building your own modern transistor radio!**

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn - and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy - making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

**No soldering - yet you learn faster than you ever dreamed possible.**

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits - assemble components - build things - experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

**So fast, so easy, this personalised course will teach you even if you don't know a thing today!**

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

**Send now for FREE 76 page book - see how easy it is - read what others say!**

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

**NOW AVAILABLE . . .  
LATEST  
BOUND VOLUME  
No. 27  
of  
"Radio & Electronics  
Constructor"**



AUGUST 1973 to JULY 1974

Comprising **PRICE £2.20 P&P 33p**  
772 pages inc. index

**BOUND VOLUME No. 24  
(August 1970 to July 1971)**

**BOUND VOLUME No. 25  
(August 1971 to July 1972)**

**BOUND VOLUME No. 26  
(August 1972 to July 1973)**

**PRICES**

**VOLS. 24 & 25  
£2.00 per volume. P&P 33p**

**VOL. 26  
£2.10 per volume. P&P 33p**

Limited number of these volumes still available.

We regret all earlier volumes are now completely sold out.

Available only from  
**DATA PUBLICATIONS LTD.,  
57 MAIDA VALE, LONDON, W9 1SN**

**POST  
TODAY FOR  
FREE BOOK**

To: ALDERMASTON COLLEGE  
DEPT. BRE 85  
READING RG7 4PF

BRE 85

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



# WILMSLOW AUDIO

## THE Firm for speakers!

### SPEAKERS

Baker Group 25, 3, 8 or 15 ohm £7.75  
 Baker Group 35, 3, 8 or 15 ohm £8.50  
 Baker Group 50/12, 8 or 15 ohm £12.50  
 Baker Deluxe 12", 8 or 15 ohm £10.75  
 Baker Major 3, 8 or 15 ohm £8.50  
 Baker Superb 8 or 15 ohm £14.50  
 Baker Regent 8 or 15 ohm £7.75  
 Baker Auditorium 12" £12.50  
 Celestion PST8 (for Unilex) £2.55  
 Celestion G12H 8 or 15 ohm £15.00  
 Celestion G12M 8 or 15 ohm £12.00  
 Celestion G15C 8 or 15 ohm £24.00  
 Celestion G18C 8 or 15 ohm £33.00  
 Celestion MH1000 8 or 15 ohm £10.95  
 Coral 6 1/2" d/cone roll/surr. 8 ohm £2.50  
 Coral 6 1/2" (larger magnet) 8 ohm £3.15  
 Coral 8" d/cone, roll/surr. 8 ohm £3.25  
 EMI 13 x 8, 3, 8 or 15 ohm £2.25  
 EMI 13 x 8, d/cone 3, 8 or 15 ohm £2.50  
 EMI 13 x 8 t/w. 3, 8 or 15 ohm £3.75  
 EMI 13 x 8 type 350, 8 or 15 ohm £8.25  
 EMI 13 x 8 20 watt bass £6.60  
 EMI 5" 98132CP 8 ohm £2.50  
 EMI 6 1/2" 98350 4 or 8 ohm £3.00  
 EMI 8 x 5, cer. mag. 8 ohm £1.65  
 EMI 8 x 5, 10 watt, d/c roll/s 8 ohm £2.50  
 EMI 10 x 6 93870 8 ohm £2.25  
 EMI 2 1/2" tweeter 8 ohm .65  
 Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm £2.80  
 Elac 6 1/2" d/cone, roll surr. 8 ohm £3.50  
 Elac 6 1/2" d/cone 8 ohm £2.65  
 Elac TW4 4" tweeter £1.21  
 Elac 10" 10RM239 d/c 8 ohm £2.65  
 Elac 8" 3 ohm £2.50  
 Eagle Crossover 3, 8 or 16 ohm £1.50  
 Eagle CT5 cone tweeter 8 ohm £1.75  
 Eagle CT10 tweeter 8 or 16 ohm £2.55  
 Eagle DT33 dome tweeter 8 ohm £5.45  
 Eagle FF5 3 way crossover £3.15  
 Eagle SN75 crossover with tw. control £4.00  
 Eagle FF28 multicell, horn £7.75  
 Eagle HT15 horn tw. 16 ohm £3.80  
 Eagle HT21 horn tw. 8 ohm £5.88  
 Eagle MHT10 horn tw. 8 ohm £3.80  
 Eagle FR4 4" full range £5.30  
 Eagle FR65 6 1/2" full range £8.35  
 Eagle FR8 8" full range £10.65  
 Fane Pop 15 watt 12" £4.80  
 Fane Pop 25/2 25 watt 12" £6.95  
 Fane Pop 50 watt 12" £11.00  
 Fane Pop 55 12" 60 watt £12.50  
 Fane Pop 60 watt 15" £13.00

### SPEAKERS

Fane Pop 100 watt 18" £22.50  
 Fane Crescendo 12A 8 or 15 ohm £29.00  
 Fane Crescendo 12B 8 or 15 ohm £30.00  
 Fane Crescendo 15, 8 or 15 ohm £36.00  
 Fane Crescendo 18, 8 or 15 ohm £49.95  
 Fane 701 twin ribbon horn £35.00  
 Fane 910 horn £12.75  
 Fane 920 horn £33.00  
 Fane 152/12a 15" 15 ohm £16.00  
 Fane 801T 8" d/cone roll surr. £7.00  
 Fane 803T 8" d/cone roll surr. £5.25  
 Fane 805T 8" d/cone roll surr. £3.50  
 Fane 808T 8" d/cone £2.75  
 Fane 807T 8" d/cone roll surr. £3.85  
 Goodmans 8P 8 or 15 ohm £5.00  
 Goodmans 10P 8 or 15 ohm £5.30  
 Goodmans 12P 8 or 15 ohm £12.95  
 Goodmans 12P-D 8 or 15 ohm £16.75  
 Goodmans 12P-G 8 or 15 ohm £15.75  
 Goodmans 12AX 100 watt 8 or 15 ohm £36.50  
 Goodmans 15AX 100 watt 8 or 15 ohm £40.25  
 Goodmans 15P 8 or 15 ohm £21.00  
 Goodmans 18P 8 or 15 ohm £36.00  
 Goodmans Midax 750 £16.00  
 Goodmans Axent 100 tweeter & crossover £7.25  
 Goodmans Audiom 100, 8 or 15 ohm £12.00  
 Goodmans Axiom 401, 8 or 15 ohm £17.25  
 Goodmans Twinaxiom 8" 8 or 15 ohm £8.25  
 Goodmans Twinaxiom 10" 8 or 15 ohm £9.00  
 Gauss 12" full range 8 ohm £69.50  
 Gauss 12" Bass 8 ohm £69.50  
 Gauss 15" full range 8 ohm £75.00  
 Gauss 15" Bass 8 ohm £75.00  
 Gauss 18" full range 8 ohm £80.00  
 Gauss 18" Bass 8 ohm £80.00  
 All the above Gauss (American) speakers are fitted with 4 1/2" voice coils and can handle 200 watts RMS.  
 Kef T27 £5.25  
 Kef T15 £6.00  
 Kef B110 £7.25  
 Kef B200 £8.25  
 Kef B139 £14.25  
 Kef DN8 £2.00  
 Kef DN12 £4.95  
 Kef DN13 £3.30  
 Richard Allan 12" d/cone 3 or 15 ohm £2.75  
 Richard Allan CG8T 8" d/c roll surr. 8 ohm £6.35  
 STC 4001G super tweeter £6.19  
 Wharfedale Super 1ORS/DD 8 ohm £9.80  
 2 1/2" 64 ohm, 70mm 8 ohm, 70mm 80 ohm .65  
 2 1/2" 75 ohm .50  
 7" x 4" 3, 8 or 15 ohm £1.40  
 8" x 5" 3, 8 or 15 ohm £1.50  
 10" x 6" 3, 8 or 15 ohm £2.30

### SPEAKER KITS (Carr. 75p each. £1.50 pair)

Baker Major Module 3, 8 or 15 ohm each £10.75  
 Fane Mode One each £9.90  
 Goodmans DIN 20 4 ohm each £9.75  
 Helme XLK25 pair £22.00  
 Helme XLK30 pair £14.95  
 Helme XLK50 pair £39.95  
 Kefkit 2 each £24.75  
 Kefkit 3 each £36.75  
 Peerless 3-15 (3 sp. system) each £15.00  
 Richard Allan Twinkit each £8.95  
 Richard Allan Triple 8 each £13.75  
 Richard Allan Triple each £19.95  
 Richard Allan Super Triple each £23.75  
 Wharfedale Linton 2 kit pair £19.25  
 Wharfedale Glendale 3 kit pair £34.50  
 Wharfedale Dovedale 3 kit pair £52.50

### PA/DISCO AMPLIFIERS (Carr. and ins. £1)

Baker Major 100 watt £49.75  
 Linear 30/40 £30.00  
 Linear 40/60 £35.00  
 Linear 80/100 £58.95  
 Linear 100 watt slave £44.00  
 Eagle PRO A120, 120 watts RMS £129.00  
 Eagle PRO A65, 65 watts RMS £98.50  
 Eagle PRO A35, 35 watts RMS £77.00  
 Eagle TPA40 mains/12v mobile £50.00  
 Eagle HH5 36 watts mobile 12v. £37.50  
 Eagle TPA20 paging amplifier £45.00  
 Eagle RA859 Reverb (p. & p. 75p) £18.25  
 Eagle RA856 Reverb (p. & p. 75p) £12.50

### MICROPHONES (p. & p. 50p)

Shure 515 SB £14.95  
 Shure 515 SA £15.75  
 Shure 545 £29.95

FREE with loudspeaker orders over £7 - "HiFi Loudspeaker Enclosures" book

All items guaranteed new and perfect

Prompt despatch

Carriage: 38p per speaker, 20p per tweeter, crossover or 2 1/2"/70mm speaker, kits 75p each (£1.50 pair)

ALL PRICES QUOTED INCLUDE VAT.

Send stamp for free booklet 'Choosing a speaker'

Big discounts on Grundig, ITT, Koyo, etc. Send stamp for list

# WILMSLOW AUDIO

DEPT RC

LOUDSPEAKERS: SWAN WORKS  
 BANK SQUARE, WILMSLOW, CHESHIRE

AMPLIFIERS, RADIO ETC.  
 10 SWAN ST., WILMSLOW, CHESHIRE



## Agfa Cassettes

Agfa Low Noise Cassettes  
 AT LESS THAN HALF PRICE!

AGFA HIGH DYNAMIC SUPER

AGFA STEREO-CHROM  
 CHROMIUM DIOXIDE

	The best buy		
C60	1	5	10
C90	37p	£1.80	£3.50
C120	50p	£2.48	£4.95
	63p	£3.10	£6.20
	1	5	10
C60+6	50p	£2.40	£4.70
C90+6	68p	£3.35	£6.60
C120	99p	£4.90	£9.90
	1	5	10
C60	85p	£4.20	£8.30
C90	£1.08	£5.35	£10.60

SAME DAY DESPATCH  
 WILMSLOW AUDIO

Dept. RC

10 Swan Street, Wilmslow, Cheshire.

SK9 1HF

P. & P. 15p per order Cut-price prerecorded cassettes - send stamp for list

# COMPONENTS

HOBBYIST - AMATEUR - DOMESTIC - SURPLUS - INDUSTRIAL - JUST A FEW OF OUR BARGAINS ARE LISTED BELOW - SEND STAMPED ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS. THESE OFFERS APPLY ONLY TO MAIL ORDER AND NOT SHOP SALES.

GOODS SENT AT CUSTOMER'S RISK, UNLESS SUFFICIENT PAYMENT FOR INSURANCE INCLUDED

## VALVE BASES

Printed circuit B9A - B7G	4p
Chassis B7 - B9G - B7G	4p
Shrouded chassis B7G - B9A	6p
B8A - B9A chassis - B12A tube	6p

## TAG STRIP

6 way 4p Single 1p

## WRIST COMPASS

20p with Needle Lock

1 1/4 glass fuses - 250 m/a or 3 amp (box of 12)

3" tape spools

10K + 10K Log Switched Pot

PVC or metal clip on M.E.S. bulb holder

All metal equipment Phono plug

Bulgin, 5mm Jack plug and switched socket (pair)

12 volt solenoid and plunger

250 RPM 50 c/s locked frequency miniature mains motor

200 OHM coil, 2 1/4" long, hollow centre

Belling Lee white plastic surface coax outlet Box

R.S. 12 way standard plug and shell

TO3 Mica Washer 2p

18 volt 4 amp charger,

bridge rectifies 60p

GC10/4B Cold

Cathode £5.00

Brand New Boxed

6K7G 25p

## ELECTROLYTICS MFD/VOLT. Many others in stock

5p. 1/75, 2/75, 2.5/64,	30, 260/12, 330/10
4/60, 5/50, 6/3, 6/25,	9p. 400/16, 550/12,
8/6, 8/40, 8/50, 8/150,	20p. 8/500, 16/450,
12/50, 15/35, 16/40,	100/200, 100/250-
16/50, 20/12, 25/3,	275, 16-32/275, 32-
25/6, 25/12, 25/25,	32/275, 100-100/150,
25/30, 50/10, 50/12,	100-100/275, 50-50/
50/25, 50/50, 64/10,	300: Solid Tantalum,
100/6, 100/12, 100/	8/20, 10/20, 12/20,
15, 100/18, 100/25,	50p. 8/800, 2000/50,
125/10, 150/12, 150/	12,000/12, 32-32-50/
25, 200/3, 250/6, 200/	350.
12, 500/6,	£1.100-100-100-150
6p. 1/350, 2/350,	-150/320.
150/40, 250/18, 250/	

## INDICATORS

Arcoelectric green, takes M.E.S. bulb	15p
Bulgin D676 red, takes M.E.S. bulb	15p
12 volt red, small pushfit	20p
Mains neon, red, pushfit	20p

## CAPACITORS

Mixed type PFDS, 2p. 1, 3.3, 4.7, 5.6, 10, 12, 15, 16, 18, 20, 22, 24, 25, 27, 30, 33, 37, 39, 47, 50, 56, 68, 88, 100, 110, 120, 150, 200, 220, 250, 300, 330, 470, 500, 600, 680, 800, 1000, 2200, 3000, 3300, 5000.

Poly, met., film, paper, etc. MFD/Volt, 3p. .001/1250, .005/250, .03/350, .03/12, .03/200, .033/100, .0068/70, .056/350, .061/035, .069/350, .075/350, .08/350, .1/350, .1/500, .13/350, .25/150.

4p. 1500, 1800, 2200, 3000, 3300, 6800, 8200 PFD. .01/350, .013/350, .05/125, .05/250, .068/200, .25/350.

5p. .033/100, .1/250, .5/350.

6p. .1/600, .1/1500, .22/250, .5/250

10p. .01/1000, 1/350, 2/150, 2/200, 8/20, .1/900, .22/900, 4/16, .25/250 AC (600VDC)

40p. 5/150, 9/275AC, 10/150, 15/150, 40/150.

## TRIMMERS, 15p each

100PF. Ceramic, 30PF Beehive, 12PF PTFE 2500PF 750 volt, 33PF MIN. AIR SPACED 5PF, MIN. AIR SPACED, 50PF CERAMIC.

## CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 3p each

## CAN CLIPS

1" or 1 3/8" or 3/4" 2p

## LABGEAR MAINS DROPPER

36 ohm 25 watt + 79 ohm 9 watt 25p

TUNING CONDENSERS 50PF, 25p

2 Amp Suppression Choke 5p

## PAXOLINE

3 x 2 1/2 x 1 1/8" 2p

4 1/2 x 1/2 x 1 1/8" 2 for 1p

220K 3 watt resistors 2p

100 ohm 3 watt resistor 4p

VALVE RETAINER CLIP, adjustable 2p

## OUTPUT TRANSFORMERS

Sub-miniature Transistor Type 25p

Valve type, centre tapped or straight 40p

3 pin din to open end, 1 1/2yd twin screened lead 35p

Whiteley Stentorian 3 ohm constant impedance volume control way below trade at £1

## SWITCHES

Pole	Way	Type	
4	2	Sub. Min. Slide	18p
6	2	Slide	20p
4	2	Lever Slide	15p
6	4	Wafer Rotary	30p each
4	3		
3	7		
2	5		
1	3		
1	3	13 amp small rotary	12p
2	2	Locking with 2 to 3 keys	£1.50
2	1	2 Amp 250V A.C. rotary	20p
1	2	Toggle	10p

## RESISTORS

1/4 - 1/2 watt 1p

1 watt 2p

Up to 5 watt wire 10p

10 watt wire

wound 12p

15 watt 14p

## SKELETON PRESETS

5K or 500K 4p

5K wirewound 5p

500k Dual Concentric

Potentiometer 40p

## WIREWOUND POTS

250, 300 OHM, 1K, 4

watt, 5K, 10K, 11K, 20K,

50K, all at 20p each

Philips transformer,

safety fused. In 200-

220-240v. Out 240v

60ma + 6.3v 1a approx

2" x 2 1/2" x 2 1/2" £1.50

5K, 20K, Log Pot 15p

1meg Tandem Pot 25p

2M, 5M, Log Switch-

ed pot 25p

## THERMISTORS

VA1008, VA1034,

VA1040, VA1055,

VA1066, VA1100

VA1077, 15p

VA1005, VA1026 25p

## PARMEKO P480

6000/55, 20 Henry

12A, potted choke £1

## RELAYS

12 volt S.P.C.O octal

mercury wetted high

speed 75p

P.O. 3000 type, 1,000

OHM coil, 4 pole c/o

60p

## COMPUTER AND AUDIO BOARDS

HOT OF QUALITY, REASONABLE LEAD TRANSISTORS, SOME POWER. SILICON, GERMANIUM, ZENER DIODES, POT CORES HI-STAB RESISTORS, SOME WIREWOUND, CONDENSERS, CHOKES, TRIMPOTS, ELECTROLYTICS, ETC.

3lb. for 75p + 30p post and packing

7lb. for £1.50 + 50p post and packing

## SUBMIN VERTICAL SKELETON PRESET

50, 100, 220, 470, 680 OHM 1, 2.2, 4.7,

6.8, 15, 22, 47, 68, 100, 220 K OHM.

ONLY 4p EACH

## KNOBS

SILVER METAL PUSH ON WITH POINTER, OR WHITE PLASTIC, GRUB SCREW WITH POINTER AND SILVER CENTRE 10p EACH.

## ZM1162A INDICATOR TUBE

0-9 Inline End View. Rectangular Envelope 170V

2.5M/A £3.60

## RESETTABLE COUNTER

English Numbering Machines LTD.

MODEL 4436-159-989

6-14 volt, 6 digit, illuminated, fully enclosed. £2.50

# THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 7 p.m. Monday to Saturday also most Sundays.

Phone 01-223 5016

### SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AC107 .. 17p	BC148A/B, 9B/C 13p	BF115 .. 20p
AC127/8 .. 10p	BC157/8/9 .. 9p	BF167/173 .. 25p
AC188 .. 10p	BC158A/B .. 15p	BF178 .. 31p
ACY28 .. 20p	BC159C, 157A .. 15p	BF179/181 .. 33p
AD149 .. 43p	BC178 .. 15p	BF180 .. 25p
AD162 .. 33p	BC186/7 .. 25p	BF182/3 .. 40p
AF116/7 .. 14p	BC213L .. 11p	BF184 .. 17p
AF124/6 .. 20p	BC337 .. 19p	BF185 .. 26p
AF127 .. 28p	BC547 .. 12p	BF194/5 .. 10p
AF139 .. 33p	BC558A .. 12p	BF196/7 .. 13p
AF178 .. 30p	BCY40 .. 87p	BF200 .. 32p
AF180/1 .. 50p	BCY70/1/2 .. 11p	BF262/3 .. 70p
AF239 .. 36p	BD112/3 .. 63p	BF336 .. 35p
ASY27 .. 30p	BD116 .. 75p	BFX29 .. 28p
ASY73 .. 26p	BD115 .. 65p	BFX30 .. 29p
BC107A or B .. 15p	BD131/2 .. 35p	BFX84/88 .. 24p
BC107/8/9 .. 8½p	BD135 .. 37p	BFY50 .. 17p
BC108A/B .. 14p	BD203 .. £1.41	BFY51/2 .. 12p
BC109B .. 14p	BD232 .. 75p	BR101 .. 35p
BC147/8/9 .. 7p	BD234/5 .. 75p	BSV64 .. 50p

### BRIDGE RECTIFIERS

Amp	Volt RMS		Amp	Volt RMS	
½	1,600	BYX10 30p	2	30	LT120 30p
1	140	OSH01-200 38p	0.6	6-110	EC433
1.4	42	BY164 35p	Encapsulated with built-in heat sink .. 15p		

### 1 AMP RECTIFIERS

IN4003 200 volt .. 5p
IN4004 400 volt .. 5½p
IN4005 600 volt .. 5½p
IN4006 800 volt .. 7½p
IN4007 1,000 volt .. 7½p

### HIGH POWER RECTIFIERS

	Amp	Volt	
SR100	1.5	100	6½p
SR400	1.5	400	7½p
LT102	2	30	10p
BYX38-600	2.5	600	34p
BYX38-300R	2.5	300	26p
BYX38-900	2.5	900	40p
BYX38-1200	2.5	1,200	52p
BYX49-600	2.5	600	34p
BYX49-300	2.5	300	26p
BYX49-900	2.5	900	40p
BYX49-1200	2.5	1,200	52p
BYX48-300	6	300	40p
BYX48-600	6	600	50p
BYX48-900	6	900	60p
BYX48-1200	6	1,200	80p
BYX72-150R	10	150	35p
BYX72-300R	10	300	45p
BYX72-500R	10	500	55p
BYX42-300	10	300	45p
BYX42-600	10	600	65p
BYX42-900	10	900	80p
BYX42-1200	10	1,200	95p
BYX46-300*	15	300	£2.90
BYX46-400*	15	400	£3.20
BYX46-500*	15	500	£3.60
BYX46-600*	15	600	£3.90
BYX20-200	25	200	60p
BYX52-300	40	300	£1.75
BYX52-1200	40	1,200	£3.00

\*Avalanche type

RG4-1250 Mercury vapour rectifier	£8.00
1" Terryclips chrome finish	4p
Cinch 10-way terminal block	15p
Pair of LA2407 Ferroxc cores with adjuster	25p
Chrome Car Radio fascia	15p
Rubber Car Radio gasket	10p
DLI Pal Delayline	£1.40
Relay socket	12p
Take miniature 2PCO relay	
B7G or B9A valve can	2p
0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive, 4½" dia.	15p

### OPTO ELECTRONICS

ORP12 50p	Photo transistor
BPX40 65p	BPX29 £1.40
BPX42 £2.48	OCF71 42p
BPY10 £1.50	

### RED L.E.D.

BPY68 £1.60	2v 50mA max.
BPY69 £2.60	4½ mm diam. 18p
BPY77 £2.60	

### PNPN PROGRAMMABLE UNIJUNCTION BRY39 23p

BFW10 .. 55p
BSV79 .. £1.30
BSV80 .. £1.10

### N. Channel BSV81 M.O.S.T. £1.56 BFS28 Dual M.O.S.T. 92p

Plastic, Transistor or Diode Holder 1p  
Transistor or Diode Pad 1p  
Holders or pads 50pper100

Philips Iron Thermostat 15p  
Bulgin 2-pin flat plug and socket 10p  
McMurdo PP108 8 way edge plug 15p

### TO3 HEATSINK

Europlec HP1 TO3B individual 'curly' power transistor type. Ready drilled 20p

Tested unmarked or marked ample lead ex new equipment

ACY17-20 8p	OC71/2 6p
ASZ20 8p	OC200-5 15p
ASZ21 15p	TIC44 29p
BC186 11p	2G240 2-50
BCY30-34 10p	2G302 6p
BCY70/1/2 8p	2G401 10p
BF115 10p	2N711 25p
BY127 8p	2N2926 5p
BZY88 series 5p	2N598/9 6p
HG1005 4p	2N1091 8p
HG5009 4p	2N1302 8p
HG5079 4p	2N1907 2-50
L78/9 4p	Germ. diode 2p
M3 10p	GET120 (AC128 in 1" sq. heat sink)
OA81 4p	20p
OA47 4p	20p
OA200-2 4p	GET872 12p
OC23 20p	

BSX21 .. 20p	2N393 .. 50p
BU105/01 .. £1.95	2N706 .. 10p
CA3001 .. £2.50	2N987 .. 42p
CV7042 (OC41 OC44, ASY63) 12p	2N1091 .. 55p
GET111 .. 72p	2N1302 .. 16p
MA393 .. 50p	2N2219 .. 25p
OC35 .. 33p	2N2401 (ASY26-27) 25p
TAA570 .. £1.39	2N2904/5/7 .. 18p
TAD100 .. £1.42	2N2906 .. 15p
2G302 .. 19p	2N3053 .. 13p
	2N3055 (992) .. 33p

### THYRISTORS

1 240 BTX18-200 .. 75p
1 400 BTX18-300 .. 85p
1 240 BTX30-200 .. 40p
6.5 300 BT102-300R .. 68p
6.5 500 BT102-500R .. 75p
10 700 BT106 .. 99p
15 500 BT107 .. 90p
6.5 500 BT101-500R .. 83p
6.5 500 BT109-500R .. 90p
20 600 BTW92-600RM .. £3.90
15 800 BTX95-800R Pulse Modulated .. £18.00

### OTHER DIODES

Centercel .. 10p	BZY88 Up to 15 volt 7p
IN916 .. 4p	BZX61 11 volt 20p
IN4148 .. 4p	
BA145 .. 15p	51b New Mixed Components £2 plus 40p p & p
BA182 .. 24p	
OA5/7/10 .. 20p	

### TRIACS

Amp	Volt		DIAC	BR100 20p
25	900	BTX94-900 .. £7.50		
25	1200	BTX94-1200 .. £10.20		

### CQY11B

infra red transmitter £1 WESTINGHOUSE 28TIO 30 AMP 1000VOLT THYRISTOR WITHOUT NUT £5

### PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp £1.50

### PAPER BLOCK CONDENSER

0.25MFD 800 volt .. 30p
1MFD 400 volt .. 15p
2MFD 250 volt .. 20p
2MFD 1.5 kv .. 50p
4MFD 250 volt .. 20p
15MFD 150 volt .. 50p

### METAL CHASSIS SOCKETS

Car Aerial .. 5p
Coax .. 6p
5 or 6 pin 240° din .. 6p
Speaker din switched .. 6p

### ZN 414 AM RADIO IC £1.10p

8 way Cinch standard 0.15 pitch edge socket 20p

U.E.C.L. 10 way pin connector 2B6000 OA1P10 20p

U.E.C.L. 20 way pin connector 2A60000A1P20 30p

U.E.C.L. 10 way pin socket 2B606001R10 20p

U.E.C.L. 20 way pin socket 2B60800A1R20 30p

BELLING LEE L1354 TV Aerial diplexer 10p

Philips electronic engineer kits add on series A20, E1004, E1005 £1.00 each (parts worth more)

TAA300 T0-74 1 Watt A.F. AMPLIFIER I.C. 4-5 to 9v £1.46

WIREWOUND SLIDER 150 Ohm, 250 Ohm 5K 4p each

HANDLES Rigid light blue nylon 6½" with secret fitting screws 5p

Rotor with neon indicator, as used in Seafarer, Pacific, Fairway depth finders 20p each

Miniature Axial Lead Ferrite Choke formers 2p

DEE PLUG McMurdo DA15P 15 way chassis plug 20p

Fairway 18009 Coax. socket 5p

TIE CLIPS Nylon self locking 7" 2p

CINCH 150 12 way edge socket 10p

11b Mixed nuts, bolts, washers etc. 35p

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE  
LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.  
TOTAL GOODS PLUS CARRIAGE, ADD 8% V.A.T.

# THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11  
Open 10 a.m. till 7 p.m. Monday to Saturday also most Sundays  
Phone 01-223 5016

# Goodbye to the long wait



# for electronic components.

## Now there's Doram— a completely professional electronics service for the amateur.



### 7-day service.

If you've been buying electronic components long you'll know all about the long wait.

Somehow the things you really need never turn up on time.

Well, OK, now things have changed. Now there's Doram.

Doram is a brand-new deal for serious amateurs. It's a complete door-to-door components service operated by mail order.

### Millions of components.

You just buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint of lager!) and then you order from it.

We can offer you stocks of millions of components. With a choice of over 4,000 different lines.

And we're so confident of our service that if we can't supply the part you want within 7 days of receiving your order, we'll give you your money back. Immediately.

So you know just where you stand. You'll never waste time hanging around while we re-order.

### No-quibble guarantee.

It's just about impossible to buy a defective part from us. Because our checking is so pains-taking.

But even if the unthinkable does happen—and you're unlucky—then

**I ENCLOSE 25p\*. PLEASE SEND  
ME THE NEW DORAM  
CATALOGUE.**

\*This will be refunded on orders of £5 (less VAT) or more received by us before 31st March, 1975.

Name \_\_\_\_\_  
\_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

REC/11/74

**Doram Electronics Ltd.,**  
PO Box TR8,  
Wellington Road Industrial Estate,  
Wellington Bridge, Leeds LS12 2UF.

# DORAM

we'll still make you happy quickly.

Because we offer a no-quibble replacement part service.

And our guarantee is guaranteed by the fact that we belong to the biggest electronics distribution Group in Britain.

All the goods supplied are branded goods. Produced by big-name manufacturers like RS, Mullard, SGS-ATES, Ferranti, Siemens etc.

# NEW STYLE SELF-BINDER

for  
"Radio & Electronics  
Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

PRICE  
**90p**  
including V.A.T.

P. & P. 18p

Available only from:—

**Data Publications Ltd.** 57 Maida Vale London W9 1SN

## THE MODERN BOOK CO

### RECEIVING PAL COLOUR TELEVISION

By A. G. Priestley Price £5.25

#### SERVICING ELECTRONIC ORGANS

By M. H. Applebaum PRICE £2.05

STEREO F.M. RADIO HANDBOOK

By Harvey PRICE £2.60

DIGITAL LOGIC BASIC THEORY AND

PRACTICE By J. H. Smith PRICE £1.50

110 SEMICONDUCTOR PROJECTS

By R. M. Marston PRICE £1.30

HOW TO USE INTEGRATED CIRCUIT

LOGIC ELEMENTS

By W. Streater PRICE £1.60

HOW TO SOLVE SOLID-STATE

CIRCUIT TROUBLES

By Lemons PRICE £1.95

RAPID SERVICES OF TRANSISTOR

EQUIPMENT By J. King PRICE £2.05

THE MAZDA BOOK OF PAL RECEIVER

SERVICING By D. J. Seal PRICE £4.00

THE RADIO AMATEUR'S HANDBOOK

By ARRL PRICE £2.95

#### ELECTRONIC SECURITY SYSTEMS

By L. G. Sands PRICE £3.35

INTEGRATED CIRCUIT POCKET BOOK

By R. G. Hibberd PRICE £2.70

TELEVISION ENGINEERS' POCKET BOOK

By P. J. McGoldrick PRICE £2.70

99 WAYS TO USE YOUR OSCILLOSCOPE

By A. Saunders PRICE £1.65

SIMPLE SINGLE CHANNEL RADIO

CONTROL By R. H. Warring PRICE £1.65

IMPROVING YOUR HI-FI

By J. Earl PRICE £3.20

HANDBOOK OF IC CIRCUIT PROJECTS

By J. Ashe PRICE £1.60

TEST EQUIPMENT FOR THE RADIO

AMATEUR By H. L. Gibson PRICE £2.00

ELECTRONIC ORGAN SERVICING GUIDE

By R. Middleton PRICE £2.45

ALL PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

**19-21 PRAED STREET (Dept RC) LONDON W2 1NP**

Telephone 01-723 4185

# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



## Telephone Corner

COMPLETE TELEPHONES  
EX. G.P.O. NORMAL  
HOUSEHOLD TYPE

Only 99p

POST & PACKING 45p EACH  
TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only 25p

POST & PACKING 16p each

## Tested and Guaranteed Paks



### TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, 1" long, 3/4" dia. High speed P.O. type	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short Lead Transistors, NPN Silicon Planar types.	50p
H39	6	Integrated Circuits, 4 Gates BMC 962, 2 Flip Flops BMC 945	50p
H41	2	Sil Power transistors comp pair BD131/132	50p
H63	4	2N3055 Type NPN Sil. power transistors. Below spec. devices	50p
H64	4	3B19 N Channel F.E.T.'s ZN3B19 in plastic case	50p
H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66	50p
H66	4	40362 Type PNP Sil. transistors TO-5 can comp. to H65	50p



## Unmarked Untested Paks

### UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	50p
B66	150	Germanium Diodes Min. glass type	50p
B83	200	Transistors, manufacturers rejects, AF, RF, Silicon and Germanium	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
H34	15	Power Transistors, PNP, Germ NPN Silicon TO-3 Can.	50p
H67	10	3B19 N Channel F.E.T.'s plastic case type	50p

## Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.00 each

## EXTENSION TELEPHONES

Ideal for childrens toys ONLY 70p p.p. 25p

## ELECTRONIC TRANSISTOR IGNITION £6.00

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

## NEW X HATCH

Our new vastly improved Mark Two Cross Hatch Generator is now available

Essential for alignment of colour guns on all colour T.V. receivers. Featuring plug-in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable - ideal for the engineer's tool box - and only measures 3" x 5 1/2" x 3".

Ready built unit only **£9.95** Complete Kit **£7.95**  
(and p&p but no batteries)



## LM 380 AUDIO IC

We have just received a large consignment of LM380 IC's. These are specially selected to a higher grade and are marked with the number SL 60745. This fantastic little 3watt audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special price **£1.00 ea** complete with data and projects book

## Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

## Our very popular 4p Transistors

TYPE "A" PNP Silicon alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.  
TYPE "G" NPN Silicon similar ZTX 300 range.  
TYPE "H" PNP Silicon similar ZTX 500 range.

8 RELAYS FOR **£1.00** p. & p. 27p.

## UHF TV Tuner Units

Brand new by a famous manufacturer

Data supplied **£2.50**

## Plastic Power Transistors



### NOW IN TWO RANGES

There are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms. Range 1. VCE. Min. 15. HFE Min 15.

40 Watt	1-12	13-25	26-50
90 Watt	20p	18p	16p
	24p	22p	20p
Range 2. VCE. Min 40. HFE Min 40.			
40 Watt	1-12	13-25	26-50
90 Watt	30p	28p	26p
	35p	33p	30p

Please state NPN or PNP on order.

HIGH SPEED MAGNETIC COUNTERS EX GPO  
4 digit (non reset) 4 x 1 x 1 in. 30p

### INTEGRATED CIRCUITS

We stock a large range of I.C.s at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

### METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 15p Wall Chart 18p

### LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each  
16 pin type at 17p each } Now new low profile type

### BOOKS

We have a large selection of Reference and Technical Books in stock.

## Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. only **50p**

Please send me the FREE BI-Pre-Pak Catalogue

I enclose large SAE with 5p stamp

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Please add V.A.T. at current rate

MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 15p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

# BI-PRE-PAK LTD

Co Reg No B20919

Dept C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.

TELEPHONE: SOUTHEND (0702) 46344.



*I've often wondered -  
How CAN you compare  
one catalogue with  
another?*

After all, few firms can give you more than a brief description. Take the *Home Radio Components Catalogue* for instance. They could have said that the cover is in full colour and shows Barbara Hepworth's beautiful "Theme on Electronics". Or that it consists of no less than 240 pages of quality art paper, has over 1,700 illustrations, and lists about 6,800 different items.

What really counts however, is *the organisation behind the catalogue*, and in this connection I give full marks to Home Radio Components, because from my experience they really *care* about helping their customers. But don't merely take my word for it - find out for yourself. The best way to do that is to get a copy of their catalogue right away. Just send them a cheque or postal order for 98 pence (65p for the catalogue and 33p for postage, packing and insurance). By the way, they include 14 coupons in the catalogue, each worth 5 pence if used as directed, so you can get not only the cost of the catalogue back, but 5p towards the postage as well. If that's not philanthropy I don't know what is! It's just one of the ways Home Radio Components think of their customers. *Send for your catalogue today - you'll never regret it.*



**65p. plus 33p** POST AND PACKING

**Send off the coupon to-day. It's your first step to solving your component buying problems.**

The price of 98p applies only to customers in the U.K. and to BFPO addresses.

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....

.....

.....

HOME RADIO (Components) LTD., Dept. RC,  
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No.  
912956, London



# RADIO & ELECTRONICS CONSTRUCTOR

NOVEMBER 1974

Vol. 28 No. 4

Published Monthly (1st of Month)  
First Published 1947

*Incorporating The Radio Amateur*

*Editorial and Advertising Offices*  
57 MAIDA VALE LONDON W9 1SN

Telephone  
01-286 6141

Telegrams  
Databux, London

© Data Publications Ltd., 1974. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

*Annual Subscription:* £3.30 (U.S.A. and Canada \$8.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

*Technical Queries.* We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

*Correspondence* should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

*Opinions* expressed by contributors are not necessarily those of the Editor or proprietors.

*Production.*—Web Offset.


## CONTENTS

REFLEX SHORT WAVE RECEIVER by R. A. Penfold	206
NEWS AND COMMENT	212
BATTERY MISER by V. S. Evans	214
ZENER DIODE CHECKING UNIT (Suggested Circuit 288) by G. A. French	216
TRANSISTOR LEAD-OUT LOCATER – Part 2 by J. R. Davies	218
CAN ANYONE HELP?	222
NEW PRODUCTS	223
DIRECT READING CAPACITANCE METER by Alan C. Ainslie	224
SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin	230
SELECTIVE RECEIVER FOR THE L.F. BANDS – Part 3 by F. G. Rayer	232
TRANSFORMER RATIO ANALYSER by S. L. Martin	235
THREE TRANSISTOR REGENERATIVE RECEIVER by A. P. Roberts	238
IN YOUR WORKSHOP Transformer Secondary Currents	243
ELECTRONIC ODDITIES by R. River	249
CONSTRUCTOR'S DATA SHEET No. 92 (Enamelled Wire Coil Lengths)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

The Radio & Electronics Constructor is printed by Carlisle Web Offset.

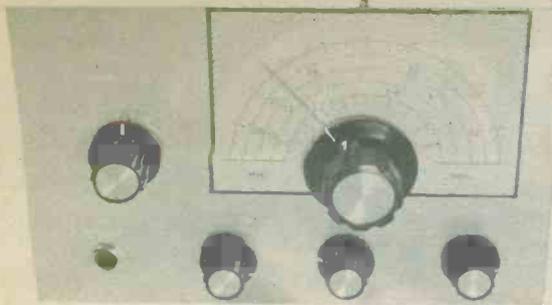DECEMBER ISSUE WILL BE  
PUBLISHED ON 2nd DECEMBER



# REFLEX

By R. A. Penfold

**Intended for a crystal earphone or crystal headphones, this simple receiver can be initially constructed in the form of a single transistor circuit. If desired, a 1-transistor a.f. amplifier may then be added on the same chassis.**

**T**HIS LITTLE RECEIVER HAS A FREQUENCY COVERAGE extending from around 1.5 to 36MHz in three bands, and it thus covers virtually the complete short wave frequency spectrum. The approximate coverage for Range 3 is 1.5 to 5.5MHz (200 to 54.5 metres), for Range 4 5.0 to 17MHz (60 to 17.5 metres), and for Range 5 10 to 36MHz (30 to 8.5 metres). These Range numbers correspond to the Denco Blue plug-in coils type 3T, 4T and 5T respectively, and the band required is selected by merely plugging the appropriate Denco coil into its holder. The complications which would arise if bandswitching were used are thus avoided.

The basic receiver employs only a single transistor in a reflex circuit having controlled regeneration. An optional single transistor a.f. amplifier can be added to give the set a degree of extra gain. The output, either with or without the a.f. amplifier, is intended for a crystal earphone or crystal headphones. As with any small short wave receiver, an efficient outdoor aerial is required to obtain good results.

## THE CIRCUIT

The circuit diagram for the basic single transistor version of the receiver is shown in Fig. 1. Signals received by the aerial are coupled via L1 to the tuned winding, L2. This is tuned by VC1 and VC2 and selects signals at the desired frequency, these being coupled to the base of the transistor by way of coupling winding L3. C2 bypasses the earthy end of L3 to chassis for r.f. signals. Of the two tuning capacitors, VC1 is the main tuning control, whilst the lower value VC2 is the band-spread control.

TR1 operates as an r.f. amplifier, and the amplified r.f. signals appear at its collector. The r.f. choke, L4,

presents a high impedance to r.f. signals whilst C4 offers a low impedance at these frequencies. In consequence, the r.f. signals pass via C4 and D1 back to the base coupling winding, L3. Although it has no d.c. return, diode D1 functions in practice as a non-linear device and the signal now passed to L3 consists of the detected r.f. signal.

TR1 functions this time as an a.f. amplifier. L4 offers a low impedance at audio frequencies and the amplified a.f. signal passes through this choke and the d.c. blocking capacitor to the volume control, VR3. The signal from this control is then fed to the jack socket SK4 and thence to the earphone or headphones. C5 filters out any residual r.f. component in the output signal which is still present after the r.f. choke. R2 is the collector load for the transistor, both at r.f. and at a.f., and R1 is the base bias resistor.


Two aerial sockets are provided, one coupling direct to L1, and the other coupling to that winding via C1. The aerial is normally plugged into SK2, but it can be plugged into SK1 under conditions of high signal strength which could cause overloading of the receiver.

In order to increase gain and selectivity, regeneration, or r.f. positive feedback, is incorporated in the circuit. The signals at the collector of the transistor and the non-earthly end of L2 are in phase, whereupon C3 and VR1 are employed to provide a controllable level of r.f. feedback. VR1 functions as a coarse control of regeneration, fine control being given by VR2 which varies the supply voltage applied to the transistor. This arrangement enables an extremely smooth control of regeneration to be provided.

It will be noted that the ends of winding L3 are designated '5 or 7' and '7 or 5'. This is because it was found that the coils for Ranges 3 and 4 had this winding

RADIO & ELECTRONICS CONSTRUCTOR

# SHORT WAVE RECEIVER

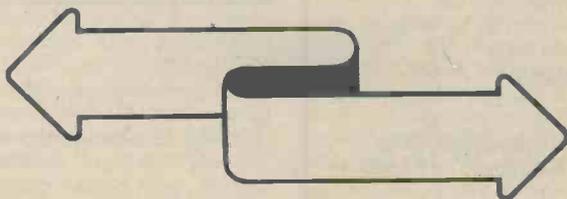

connected one way round to its pins in relation to L2, whilst the Range 5 coil had the winding connected the other way round. The two methods of connection are accommodated by providing two coil holders, one for the Ranges 3 and 4 coils, and the other for the Range 5 coil.

Of the components, the only ones that require special comment are VC1 and VC2. VC1 can be any small air-spaced capacitor having a maximum capacitance of around 365pF and a Jackson type '0' or '00' would be

suitable. VC2 requires a maximum capacitance of 50pF and can be a Jackson type C804. VC1 is provided with a scale taken from 'Panel Signs' Set No. 5, and this causes its spindle to be 2½ in. from the top of the front panel. Before cutting out the front panel ascertain that there will be sufficient space above the chassis to accommodate the body of the particular component used for VC1. If not, the height of the panel should be increased or a capacitor of smaller size employed. 'Panel Signs' are available from the publishers of this journal.

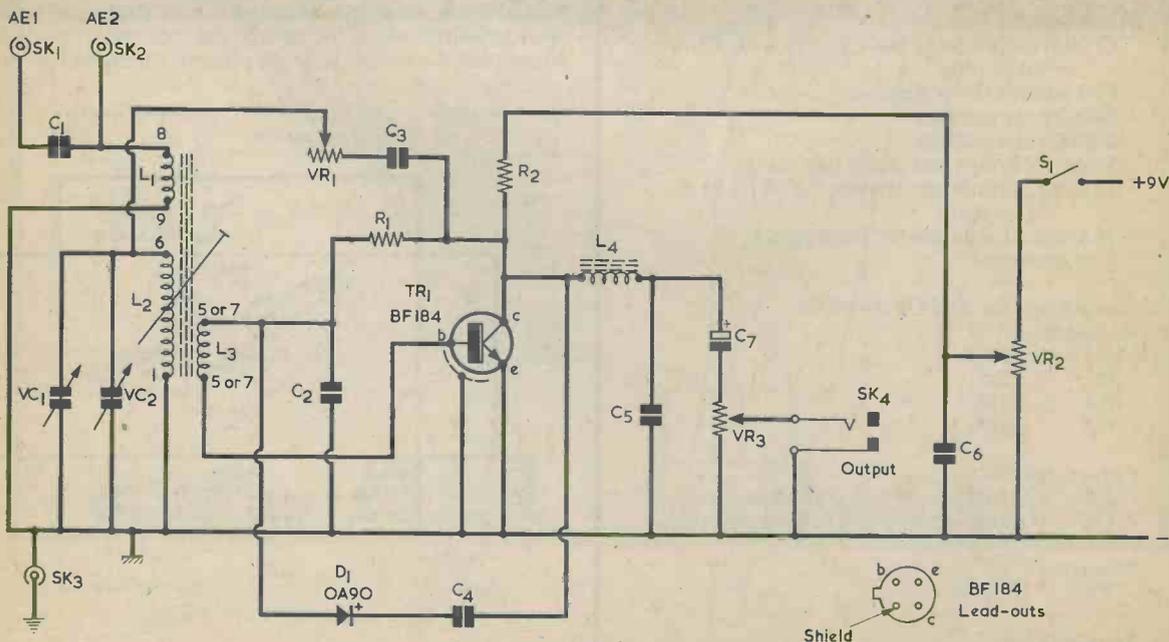


Fig. 1. The circuit of the single transistor reflex short wave receiver

## COMPONENTS

### Resistors

- R1 470k $\Omega$ ,  $\frac{1}{4}$  watt 10%  
 R2 4.7k $\Omega$ ,  $\frac{1}{4}$  watt 10%  
 VR1 100k $\Omega$  potentiometer, linear  
 VR2 25k $\Omega$  potentiometer, linear  
 VR3 25k $\Omega$  potentiometer, log, with switch S1

### Capacitors

- C1 10pF ceramic or silvered mica  
 C2 0.01 $\mu$ F plastic foil  
 C3 8.2pF ceramic or silvered mica  
 C4 0.022 $\mu$ F plastic foil  
 C5 0.01 $\mu$ F plastic foil  
 C6 0.01 $\mu$ F ceramic or plastic foil  
 C7 2 or 2.2 $\mu$ F electrolytic, 16 V. Wkg.  
 VC1 365pF variable (see text)  
 VC2 50pF variable (see text)

### Inductors

- L1, 2, 3 Miniature Dual Purpose coils, Blue, transistor usage, Ranges 3T, 4T and 5T (Denco)  
 L4 2.5mH r.f. choke, type CH1 (Repanco)

### Semiconductors

- TR1 BF184  
 D1 0A90

### Switch

- S1 s.p.s.t., part of VR3

### Sockets

- SK1 Wander plug socket, red  
 SK2 Wander plug socket, red  
 SK3 Wander plug socket, black  
 SK4 3.5mm jack socket

### Miscellaneous

- Crystal earphone or headphones with 3.5mm jack plug  
 PP3 battery (Ever Ready)  
 Battery connector  
 2 B9A valveholders  
 5 control knobs and scales (see text)  
 16 s.w.g. aluminium chassis, 7 by 4 by  $1\frac{1}{2}$  in. (see text)  
 18 s.w.g. aluminium for front panel  
 $\frac{1}{4}$  in. grommet

### Components for Add-On Amplifier

#### Resistors

- (All  $\frac{1}{4}$  watt 10%)  
 R3 2.2k $\Omega$   
 R4 3.3M $\Omega$   
 R5 6.8k $\Omega$

#### Capacitors

- C8 0.1 $\mu$ F plastic foil, side wires  
 C9 150pF polystyrene or silvered mica

#### Transistor

- TR2 BC169C

#### Miscellaneous

- 0.1 in. matrix Veroboard.

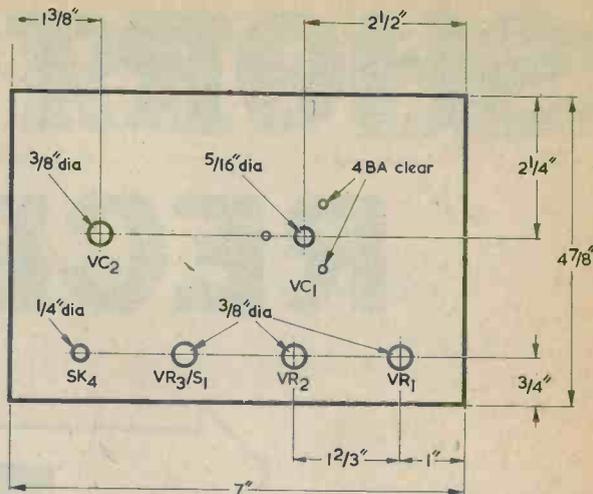


Fig. 2. Dimensions and drilling details for the front panel

## CHASSIS AND PANEL

The front panel is home-made from 18 s.w.g. aluminium sheet and it has the dimensions shown in Fig. 2. This diagram also gives drilling details.

If the capacitor employed for VC1 is a Jackson type '0' or '00' component, it is mounted to the front panel by three 4BA countersunk bolts which pass into tapped holes in the front plate of the capacitor. Spacing washers, which could consist of 2BA nuts, are fitted between the panel and the capacitor front plate to provide clearance for the raised centre section. The bolts must be short and their ends must not pass beyond the inside surface of the capacitor front plate or they may damage the fixed or moving vanes. The capacitor is mounted so that its fixed vanes are towards VC2, as illustrated in the photograph showing the rear of the receiver. A piece of paper placed against the front plate of the capacitor can


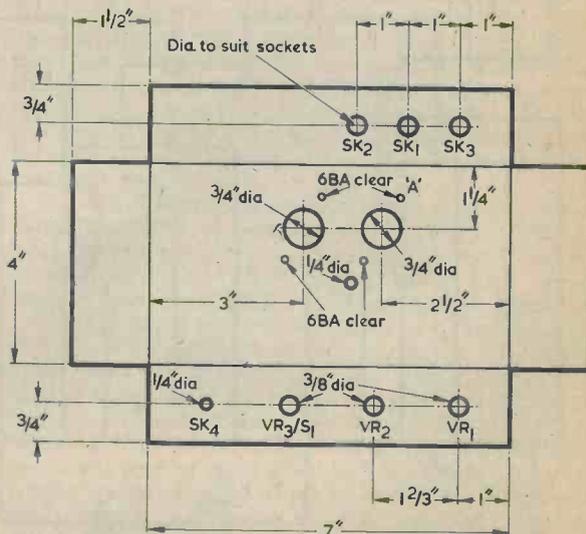


Fig. 3. Top view of the chassis. The flanges are shown opened out for clarity

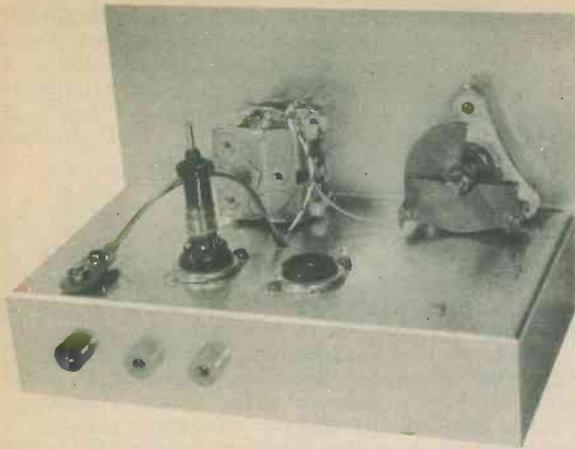



*Rear view of the receiver with a coil inserted*

occupies the holder on the right and the Range 5 coil occupies the holder on the left-hand side. It should be mentioned that the regeneration circuit used in this receiver is not one for which the coils are specifically designed, and it is possible that the connections to pins 5 and 7 may differ in some coils. Whilst this would not upset operation when the coil is used in its normal circuit application it could prevent regeneration taking place in the present receiver. The coils should be initially fitted to the valveholders in the manner just described. Should it be found that a coil does not allow regeneration to take place, the effect of fitting it to the other valveholder should be checked.

### AERIAL AND EARTH

A long wire aerial is required, and this should be a proper outdoor type as very few stations will be received under average conditions when using a short indoor aerial. For best results the aerial should consist of 50 feet or more of wire strung between any two convenient points which place the aerial at a reasonable height, and preferably clear of buildings or other large obstructions. The wire should be reliably insulated at its securing points in order to prevent received signals from being earthed.

Normally, the aerial will be plugged into socket SK2. When using a very long aerial, however, or when conditions are very good, the receiver may be over-

loaded. Overloading will result in stations in parts of the band being inseparable, together with a loud hissing sound in the background. This is due to cross-modulation.

Under these conditions it is necessary to reduce the signal input from the aerial, and this is achieved by plugging the aerial into SK1.


An earth connection can be plugged into SK3, but this will probably have little effect on the performance of the set except, perhaps, on the 80 metre and, more particularly, on the 160 metre amateur bands.

An earth can consist of a length of metal pipe with a lead connected to it. The pipe is buried in moist earth, and the lead taken to the receiver. The earth lead-in should be as short as possible. The effectiveness of the earth is largely dependent upon the area of metal which is in contact with the ground, and therefore the larger the pipe the better.
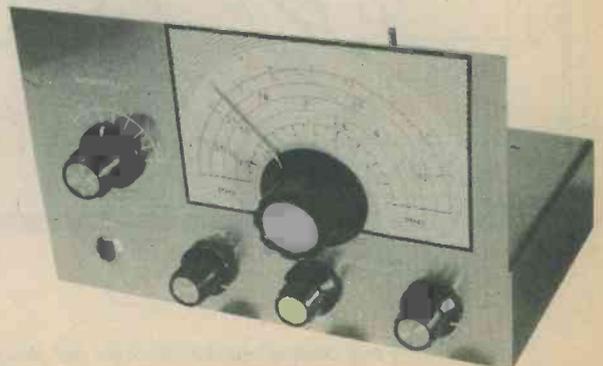
### USING THE RECEIVER

The set is very simple to operate, although a little experience with the regeneration controls may need to be gained before optimum results are obtained. VC1 is the main tuning control, but as each coil covers a wide range of frequencies, tuning is likely to prove rather difficult using this on its own, especially on Ranges 4 and 5. Therefore VC1 is set to the part of the band which is to be covered, and the tuning is carried out by the

*Another view of the receiver as seen from the front*



bandsread control, VC2. This has a much lower value than VC1, and so covers only a small portion of the band.

VR3 is the combined a.f. volume control and on-off switch, and in the single transistor version of the receiver will need to be kept at maximum all the time.

The settings of VR1 and VR2 are very critical if maximum sensitivity is to be obtained. Start with VR1 adjusted fully anti-clockwise, and VR2 advanced about two-thirds to three-quarters of full travel in the clockwise direction. If VR1 is now advanced there should be a small increase in sensitivity. Continuing to advance VR1 will cause the sensitivity to steadily increase until a point is reached where the set breaks into oscillation. This will be heard as a reduction in background hiss and as whistles when the set is tuned across transmissions.

VR1 should be backed off to a point just below that at which oscillation occurs. VR2 is then advanced in a clockwise direction as far as is possible without the set oscillating. It is at the setting just below the oscillation point that the sensitivity and selectivity of the receiver are at their greatest. In order to obtain good results it is important to ensure that the regeneration controls are adjusted accurately to this setting.

Do not try to obtain fine adjustment of regeneration by means of VR1 as this is only the coarse control. A much more precise setting can be obtained by using VR2. Always ensure that VR2 is well advanced in a clockwise direction, as if this control is advanced less than about half-way a serious loss of gain may result. The required settings for VR1 and VR2 will vary with the settings of the tuning controls and the coil which is in use.

The specific coverage of each coil depends upon the position of its adjustable core, and this should be set so that about  $\frac{3}{8}$  in. of its metal thread protrudes from the top of the coil former. The Range 4 coil is likely to prove of most use since this range contains most of the popular broadcast bands. It also contains the 40 metre amateur band. The Range 5 coil gives coverage of the h.f. broadcast bands and amateur bands. Coverage with the Range 3 coil includes the 80 and 160 metre bands, as well as numerous maritime transmissions.

The front panel has one of the medium size tuning scales in 'Panel Signs' Set No. 5 affixed to it, and this appears behind VC1 control knob. It may be marked up in terms of the main frequency bands after these have been located and identified. A home-made cursor is fitted to the control knob by means of adhesive. A small scale, also taken from 'Panel Signs' Set No. 5, is positioned behind the knob for VC2. With the prototype, white wording, taken from 'Panel Signs' Set No. 3, was positioned alongside the controls to indicate their functions.

### ADD-ON STAGE

The maximum volume and gain of the basic receiver are not very high, and results are considerably enhanced by the addition of an a.f. amplifier stage. The circuit of a suitable amplifier is shown in Fig. 5. This is a straightforward high gain common emitter stage.

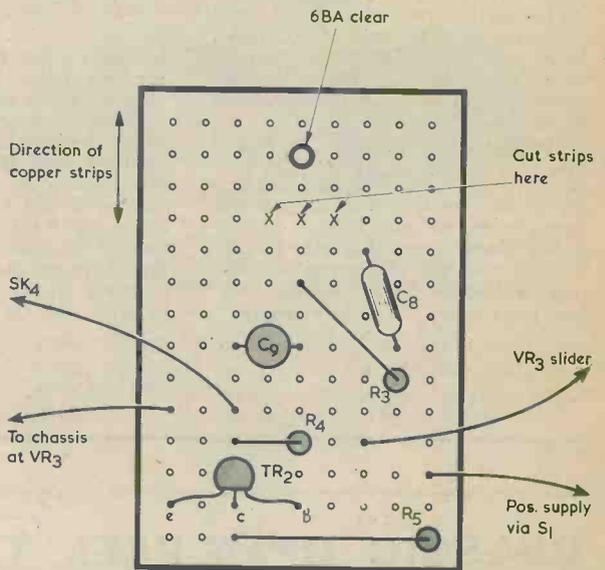


Fig. 6. Component side of the Veroboard panel on which the amplifier stage is assembled

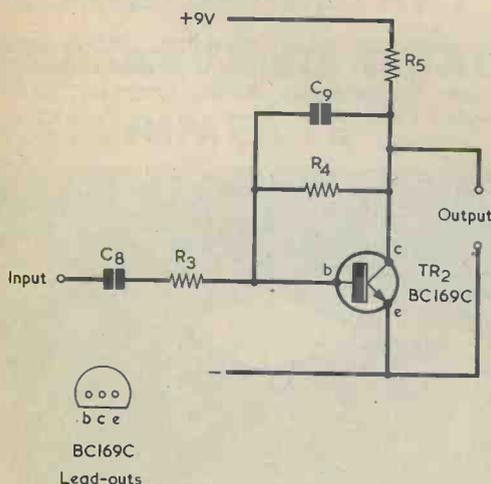


Fig. 5. Circuit of the add-on amplifier stage

It is assembled on a 0.1 in. matrix Veroboard panel having 9 by 14 holes. Fig. 6 shows the layout on this panel as viewed from the component side. The copper strips have to be cut at three points, as indicated in the diagram. The only major wiring modifications required to the single transistor version consist of disconnecting the lead from VR3 slider to SK4 and of making the alternative connections between these circuit points and the amplifier which are shown in Fig. 6. A 6BA clear hole has also to be drilled in the chassis to take a bolt for mounting the amplifier board. Its position, under the chassis, is indicated in Fig. 4. The board is mounted by means of a single 6BA bolt  $\frac{1}{2}$  in. long, an insulated spacing washer about  $\frac{1}{4}$  in. thick being placed over this between the chassis and the board.

As a final point, the current consumption of the receiver is very low. It is approximately 2mA for the single transistor version, and 2.6mA for the two transistor version.

## DE LUXE DIGITAL ELECTRONIC ALARM CLOCK

Like any dependable alarm clock, the new Heathkit GC-1092AE keeps accurate time and wakes you up in the morning. But that's where its similarity to conventional clocks end. For instance, when the distinctive intermittent electronic "beep" wakes you in the morning, there are no switches or buttons to fumble for. Instead, the slightest touch of the Heathkit "logo" on top of the case, turns off the alarm . . . electronically. And, if you like a lie-in you may activate the "snooze cycle" the night before to give yourself another 7 minutes catnap (repeatable up to an hour).

**Emergency Power Supply:** If you've ever been late for work because your alarm woke you an hour late due to a power-cut, you'll appreciate this feature: it has its own built-in battery power supply that takes over in case of power failure - keeping accurate time (without the lighted display, however) and wakes you in the morning . . .



on time! When AC power is restored the correct time is once again displayed eliminating the need to reset the clock.

**Deluxe Features:** Switch-selection of 12 or 24-hour time format; on an indicator-light that lets you set the alarm in correct 24-hour cycle so you can go to bed at 9 p.m. and set the alarm for 10 a.m. without being awakened in an hour; an automatic light sensor control that gives a consistently readable display - bright in brightly lit areas, dim in dark areas - and a

battery-saver switch that keeps batteries from discharging when the clock is unplugged for extended periods of time.

**Big Orange Digits:** Hours, minutes and seconds are displayed on the front panel with big  $\frac{1}{2}$  in-high 7-segment Beckman Planar gas discharge tubes for easy, across-the-room viewing. Switches on the bottom panel make setting the time and alarm quick and easy - allow you to hold seconds for correction to a time standard or time an interval and hold the final displayed time. Plug-in IC's and colour coded wiring make the GC-1092AE an enjoyable and rewarding kit building experience.

Kit K/GC-1092AE £50.80. Assembled A/GC-1092AE £72.40 (including 8% VAT and delivery within United Kingdom).

FREE Catalogue available from: Heath (Gloucester) Ltd., Gloucester, GL2 6EE.

## CLASSIC OPEN-REEL TAPE FROM 3M

Hi-fi enthusiasts preferring the open-reel format are promised tape performance with more brilliant high frequencies, according to 3M, which has just introduced its new range of Scotch Classic tapes.

Classic tapes use a new proprietary low-noise ferric oxide, giving them a high-frequency performance 3 db higher than Scotch high output low-noise professional tape (206 and 207). Classic tape's signal-to-noise ratio is 8 db higher than standard recording tape.

It is available on 7 inch plastic reels in standard-play (1,200 ft.) long-play (1,800 ft.) and double-play (2,400 ft.) lengths and on reels with NAB-type hubs in 2,400, 3,600- and 4,800 foot lengths. The box for both reel sizes is an innovative book style with a padded front. It has attractive point-of-sale black and silver embossed lettering. The technical and performance data information on the removable sleeve is repeated inside for permanent reference, and the tape is protected in a poly bag cradled in a premoulded plastic tray. Pressure sensitive index and spine labels are also provided.

Suggested list prices for 7 inch reels, excluding VAT,

212

are: standard-play, £4.02; long-play, £5.00; double-play, £6.78. On 10 $\frac{1}{2}$  inch reels, the recommended retail prices are: standard-play, £9.63; long-play, £11.58; double-play, £15.23.




# COMMENT

## SANKEN HYBRID AUDIO AMPLIFIERS LAUNCHED IN U.K.

The appointment of Armon Products Ltd. of 54 George Street, London W1, as U.K. agents for Sanken Electric Company of Tokyo means that the range of Sanken hybrid audio amplifiers is now available to U.K. electronics hobbyists and hi-fi enthusiasts. Four models are offered, all at short delivery times: S1-1010G (10 watts max, r.m.s.), S1-1020G (20 W), S1-1030G (30 W) and S1-1050G (50 W). All are of compact flat unitary construction, and all have quasi-complementary Class B outputs.

These easy-to-use self-contained hybrid power amplifiers have been designed for use in high-fidelity equipment, musical instruments, public address and other audio applications. Sanken claim  $\pm\frac{1}{2}$  dB response from 20 to 100,000 Hz, and less than 0.5% harmonic distortion at full power. Passivated chip transistors are used at the power output end; all others are flip-chip high-reliability types.

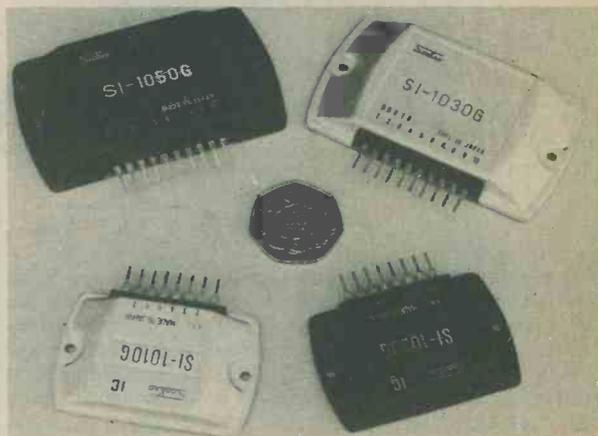The two larger circuits have built-in current limiting and differential input stages, and will feed out into 4 or 8 $\Omega$  loads. The two smaller do not have differential input, and are for a 8 $\Omega$  loads only. All four can operate from single or dual (split) power supplies, and all have 40,000 $\Omega$  input impedance, typically. Design input



Armon Products are offering four new hybrid audio amplifiers from 10 to 50 watts r.m.s., made by the Japanese Sanken Electric Company.

voltages vary from 0.3 to 0.7, throughout the range. Retail prices of these units are: 10 W, £3.30 each; 20 W, £6.60; 30 W £8.40; and 50 W, £13.00 (all prices subject to VAT). Delivery within 10 to 14 days.

## HOME SECRETARY APPROVES CEEFAX AND ORACLE EXPERIMENTS

The Home Secretary has approved the introduction for a two year experimental period, of the broadcasting of live information on television by means of the technique known as CEEFAX (BBC) and ORACLE (IBA).

The purpose of the experiment, whereby those in possession of the necessary receivers will be able to receive printed up-to-date information over a wide range of topics on their television screens, is to enable an assessment to be made of the demand for the service, to determine what form it should take and to estimate the scope for the manufacture of the equipment. It is assumed that the Annan Committee on the Future of Broadcasting will consider the technique involved against its review of broadcasting policy as a whole.

The regular transmission of live broadcasts by the BBC started in September, when the equipment was shown at the opening conference of the International Broadcasting Convention by both the BBC and IBA.

The United Kingdom leads the field in the development both of the technique and the hardware, and there are good prospects for industrial production both for home and overseas, if the service becomes established.



"Sorry, Doctor. We do not stock your sort of transformer"

# BATTERY MISER

By V. S. Evans, G4AVT

An unusual and individual approach to the problem of battery economy

**B**ATTERIES FOR DOMESTIC PORTABLE RADIOS ARE NOW expensive items, which brings very much to the fore the question of battery life and current drain. Unfortunately this aspect of economics is not always given the importance we should like by commercial designers and manufacturers. As a consequence, there are transistor portables on the market which are quite ravenous in consumption of replacement batteries.

## CURRENT DRAIN

It is fairly usual for the current consumption of a portable radio to be expressed as a 'no signal' current and as a current figure 'at average volume, rising on peaks'. Specifications of this nature may appear reasonable but the reality can be very different as there are other important data relative to battery life which must be considered.

Current consumption at 'average volume' may be doubled or even more at three-quarters to full volume. Also, assuming the portable works on a 9 volt battery, the drain is less as the voltage drops so that the quoted figures may be based on something less than 9 volts, e.g. the average voltage for the battery's working life of say 8.5 volts. A further wasteful factor occurs with a new battery which can be well in excess of 9.5 volts. This means that the current drain can be really high for the first part of the battery's life. Another relevant aspect is the lowest voltage the battery can reach before distortion or other shortcomings in receiver performance become unacceptable. This voltage can be higher than one would expect, resulting in early discard of the battery.

## VOLTAGE REGULATION

Providing the basic 'no signal' current is reasonable, a solution to the wide variables can be found in a simple voltage regulator. This is the purpose of the Battery Miser described in this article. The Miser is placed in circuit between the receiver and the battery. It receives the battery voltage (which is varying with age and use) but puts out a steady fixed voltage to the radio. This fixed voltage is designed to be the minimum voltage at which the radio will work efficiently. Ideally for this purpose the optimum working voltage of the radio should be 2 or 3 volts below the nominal rated voltage

of the battery. Thus a radio can be designed to give its best performance at a voltage of 6 volts. The 6 volt supply will be supplied and maintained via the Miser from a 9 volt battery throughout that battery's working life, and that life should be longer than we are accustomed to. The longer life is due to the fixed receiver voltage confining the current drain to fixed designed limits.

A 'hungry' commercial 6 volt portable could be powered in this manner, provided there is room in the case for the 9 volt battery and the Miser.

A 9 volt portable which is heavy on batteries can also be helped by the Miser, providing the minimum voltage at which it will work efficiently is 8 volts or less. This can be ascertained either by observation, i.e. by checking the battery voltage at the first sign of fall off in performance or, better, with the aid of a variable voltage power supply. It is important that the voltage checking should be carried out under load conditions with the receiver switched on.

## CIRCUIT DIAGRAM

The Battery Miser has only three components and its layout is unimportant. The circuit is shown in Fig. 1, and it will be seen that it is simply a standard zener regulated emitter follower. The zener diode should have a voltage rating slightly in excess of the voltage it is intended to apply to the receiver. It should be a 5% component with a dissipation rating between 200 and 250mW. Resistor R1 should have a value which causes about 0.5 to 1mA to flow in the zener diode when the

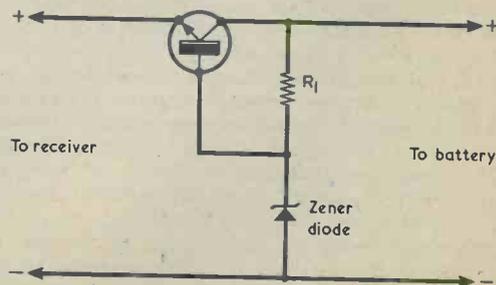


Fig. 1. The Battery Miser is essentially an emitter follower voltage regulator

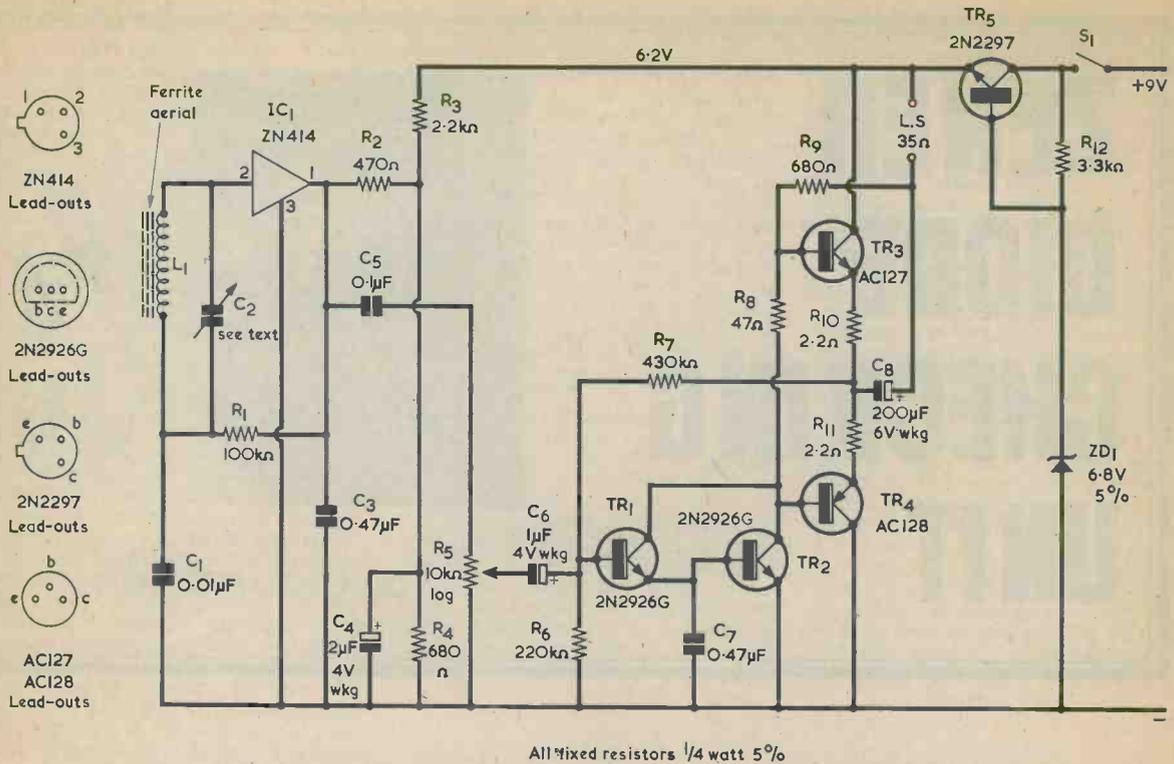


Fig. 2. A simple medium wave portable receiver incorporating the Battery Miser. Current consumption is virtually unchanged throughout the useful life of the 9 volt battery

battery is at its nominal voltage. The transistor may be any small power transistor having a wattage rating in excess of the maximum power it is required to dissipate. If, for instance, it is required to give a 6 volt output from a 9 volt battery then it will have to drop 3 volts. Should the peak current of the receiver be 50mA, then the dissipation in the transistor is 3 times 50, or 150mW. The author uses a silicon transistor type 2N2297 in his version of the circuit. This is in a TO-5 can and has a maximum power rating of 800mW. A slight disadvantage with a silicon transistor is that the 0.6 volt drop between its base and emitter means that the battery voltage, near the end of battery life, has to be at least 0.6 volt higher than the receiver voltage for the circuit to function as intended. A small germanium power transistor, with a base to emitter voltage drop of about 0.15 volt, would allow the battery voltage to fall a little further than does a silicon transistor.

## DESIGN PROJECT

To demonstrate the usefulness of the Battery Miser, the author constructed a small portable receiver based on the Ferranti ZN414 integrated circuit. The circuit of the receiver is shown in Fig. 2. The provision of a stabilized supply voltage, given here at the emitter of the 2N2297, is particularly desirable both for the ZN414 and for the following a.f. amplifier. The simple potential divider consisting of R3 and R4 is all that is required for supplying the ZN414, and the potential at the junction of these two resistors does not alter despite widely varying battery voltage. Also, the two output transistors can be set up for optimum operating con-

NOVEMBER 1974

ditions with respect to both quiescent current value and the obtaining of half-supply voltage at the output emitters.


So far as operation of the ZN414 is concerned, it is particularly important to ensure that C3 connects to lead-outs 1 and 3 of the i.c. by short leads. L1 is a medium wave ferrite rod aerial coil and is tuned by a suitable value of tuning capacitance in the C2 position. In general, a value around 300pF should give more than adequate coverage.

The AC127 and AC128 output transistors should be matched if a low value of R8 is to be achieved with minimal distortion. They are available as a matched pair from Home Radio. Mis-match can be compensated to some extent by increasing the value of R8, but at the expense of increased current drain. If desired, R8 may be replaced by a pre-set 200Ω potentiometer, this being adjusted for minimum quiescent current consistent with crossover distortion. Such a potentiometer should be set initially to insert zero resistance into circuit. The resistance should then be gradually increased until the desired setting is obtained. The quiescent current may be measured by inserting a current-reading meter in the collector circuit of the AC127.

R7 fixes the standing voltage at the junction of R10 and R11, which should be approximately half the regulated voltage. If the voltage at the junction of these resistors is a little too high, slightly reduce the value of R7, and vice versa.

As a guide, the quiescent current of the amplifier should be about 10mA. This rises to 15mA with speech, and to 20 to 25mA with loud music, peaking at 30mA. These current figures will, of course, remain constant throughout the useful life of the 9 volt battery. ■


# ZENER DIODE CHECKING UNIT

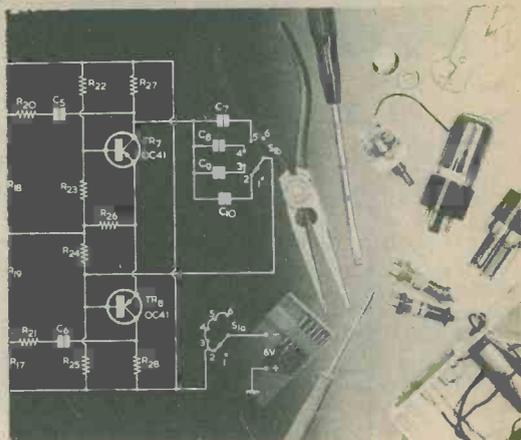

by G. A. FRENCH

Zener diodes are nowadays obtainable with voltage ratings ranging from 2.4 to no less than 100 volts. A large proportion of the diodes available consists of manufacturers' surplus. Zener diodes in this class tend to appear in a variety of shapes and sizes, and are liable to have defaced or confusing type numbers and markings. In addition, it is not always an easy matter to determine the polarity of the diode leads, and some devices have actual zener voltages which do not conform with those indicated on their cases.

THIS MONTH'S ARTICLE IN THE 'Suggested Circuit' series is devoted to a simple piece of test equipment for checking zener diodes. The unit may readily be home-constructed and, since it will in most cases be used only occasionally, particular emphasis has been placed on economy. There is only one expensive component, this being a mains transformer having a secondary voltage lying between 125 and 250 volts. It is anticipated that many constructors will be able to salvage a suitable transformer from an old valve radio receiver or that they may have such a component in stock from their earlier valve days. A voltmeter is also needed, but this is merely a multimeter coupled to a pair of terminals mounted on the unit. The only requirement here is that the meter should have a sensitivity of 10kΩ per volt, or better, on its voltage ranges.

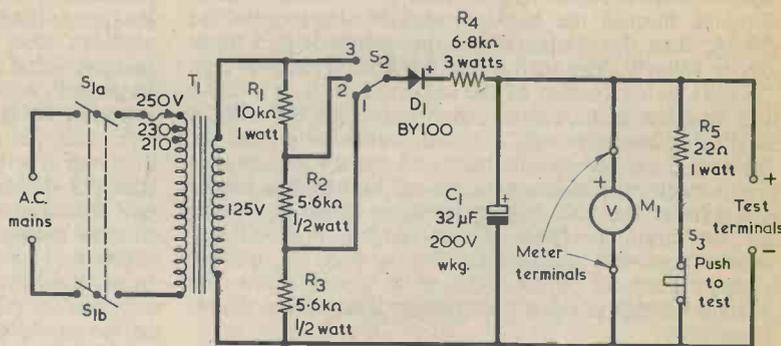

S<sub>2</sub> positions : 1 0 - 20V  
 2 0 - 40V  
 3 0 - 100V  
 M<sub>1</sub> : see text

Fig. 1. The circuit of the zener diode checking unit. When push-button S<sub>3</sub> is pressed the voltage across C<sub>1</sub> rises to the zener value of the test diode

## THE CIRCUIT

The circuit of the zener diode checking unit appears in Fig. 1. Here, the a.c. mains supply is applied, via on-off switch S1(a)(b), to the primary of transformer T1. The transformer shown in the diagram has a 125 volt secondary and this couples to the potential divider given by R1, R2 and R3. The standing current flowing through these resistors is approximately 6mA, and a voltage of about 66 volts with respect to the lower rail appears at the junction of R1 and R2, and a voltage of about 33 volts at the junction of R2 and R3. Thus, switch S2 can select either of these voltages or the full 125 volts which is available from the secondary.

The voltage selected by S2 is rectified by D1 and is then passed to current limiting resistor R4. Normally, push-button S3 is closed, but when it is pressed (and assuming that no component is connected across the test terminals) its contacts take the short-circuit off C1 and allow this capacitor to charge up to the peak value of the alternating voltage selected by S2. When S3 is released, capacitor C1 is quickly discharged again by way of the low value resistor R5, this last component being included to limit the capacitor discharge current and prevent sparking at the push-button contacts. It is quite in order for S3 to be in the closed condition when the mains supply is switched on, as all that happens is that a limited rectified current flows through R4.

It will be seen that the three positions of S2 correspond to diodes having zener voltages of 0 to 20, 0 to 40 and 0 to 100 respectively.

When the unit is used to check a zener diode a multimeter switched to a voltage range is connected to the meter terminals, S2 is set to position 1 and the test zener diode is connected to the test terminals with its cathode to the positive terminal. S3 is then pressed, whereupon C1 charges at once to a voltage which is limited by the zener diode. This voltage will be the zener voltage of the diode and will be indicated by the multimeter. If the voltage is in excess of 20 volts, S3 is released, S2 is set to position 2 and the process repeated. Should the zener voltage be higher than 40 volts S3 is released, S2 set to position 3 and S3 pressed once more. At each check, the multimeter should be initially set to a voltage range higher than the maximum figure in the range selected by S2, to guard against the case where the test diode is a high voltage device. This precaution ensures that voltages considerably in excess of f.s.d. value are not passed to the meter.

*It is possible to obtain unpleasant shocks from both the test and the meter terminals, particularly when S2 is set to position 3. The operator's hands must be kept away from both sets of terminals whenever S3 is pressed.*

If the test diode is connected to the test terminals wrong way round it will function as an ordinary silicon diode, and the voltage reading given when S3 is pressed will be about 0.6 volt only. This factor is useful in determining the polarity of an unmarked diode.

The maximum possible dissipation in the test diode is of the order of 15mW, when S2 is in position 1, 60mW for position 2 and 300mW for position 3. Diodes with zener voltages of 6 volts or less may read a little low on the unit because these low voltage diodes have a much greater initial slope in their characteristic. All other diodes should be brought well on to the flat part of their characteristic.

## COMPONENTS


The components employed in the unit are all quite standard items. The four terminals should be of the insulated type in order to reduce the risk of accidental shock.

Switch S2 should, ideally, be of the break-before-make type. In practice, however, it will be quite in order to employ an inexpensive make-before-break switch here. This will allow two of the fixed contacts to be momentarily short-circuited together as the switch

than 3 watts if it is found difficult to obtain a 6.8kΩ component with that rating. All the resistors may be 5% or 10% components.

Diode D1 can be any silicon rectifier having a p.i.v. of 350 volts or more. (This figure applies to a capacitor and not a resistor input circuit but, although D1 works into R1, it is still possible for C1 to charge to peak level.) The author used a BY100, which happened to be on hand.

The transformer employed by the author was an R.S. Components 'Midget Mains 250 Volt' transformer. This has a 125-0-125 volt 50mA secondary, of which one 125 volt section was employed in the circuit. Any other mains transformer offering a secondary voltage in excess of 125 volts and, preferably, not greater than 250 volts can also be used, but it is necessary to insert an additional resistor between one end of the secondary and the potential divider given by R1, R2 and R3 to ensure that the voltage across these three resistors is maintained at approximately 125 volts. Three of the most common secondary voltages likely to be encountered are 200, 230 and 250 volts, and Fig. 2 gives details of the

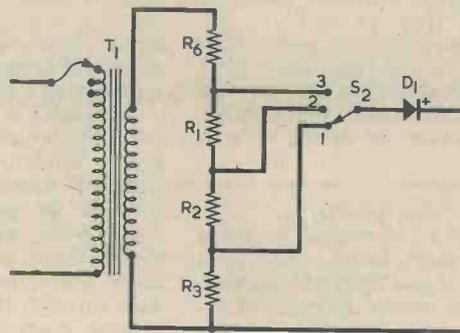

Secondary voltage	R6
200V	12kΩ 1 watt
230V	18kΩ 2 watts
250V	22kΩ 2 watts

Fig. 2. If a mains transformer having a secondary voltage higher than 125 volts is used an additional resistor, R6, is inserted into circuit in the manner shown here

is changed from one position to the next, but the result will only be a relatively small increase in the current drawn from the mains transformer secondary. Switch S3 is a push-button whose contacts break when it is pressed.

It is essential that capacitor C1 should have a low leakage current. Any good quality modern component will be satisfactory here. Its working voltage can, of course, be higher than the figure indicated in Fig. 1. The wattage ratings of the resistors are shown in the diagram. R4 may have a higher rating

manner of connection and the value of the additional resistor, which is shown as R6. In most cases, the transformers will be valve receiver types having centre-tapped h.t. secondaries of 200-0-200 volts, 230-0-230 volts and 250-0-250 volts. One half of any of these secondaries is used in the present application. The current requirement of the circuit is less than 20mA, and this should be readily available from transformers of this type. Such transformers will also have low voltage heater secondaries, to which no connections are made.

# TRANSISTOR LEAD-OUT LOCATER

## Part 2

This concluding article describes the construction and setting up of the transistor lead locator. The locator is capable of identifying the lead-outs of any normal bipolar transistor, and also of indicating whether it is p.n.p. or n.p.n.

IN LAST MONTH'S ISSUE WE EXAMINED THE CIRCUIT AND operation of the transistor lead locator. We carry on, in this month's concluding article, to details of construction and setting up.


### COMPONENTS

The layout of the unit is not at all critical provided that wiring is kept reasonably short. Some constructors may prefer to assemble the unit in a case of their own choice, working only from the circuit diagram. However, it is probable that most readers intending to make up the unit would prefer to use the case and follow the layout employed in the author's prototype, whereupon details of these are given in the present article.

The case employed by the author is an aluminium box type AB10, and can be obtained from Home Radio or Electrovalue. The dimensions of the box are 5½ by 4 by 1½ in., and it is provided with a lid. This lid forms the front panel of the unit, and all the small components are mounted on tagstrips fitted on its inside surface. The 3 volt battery is external to the case, connection to it being made by way of two flexible leads terminated in crocodile clips. An excellent choice for the 3 volt supply is the Ever Ready No. 800 cycle lamp battery, and it is an easy matter to connect the unit to such a battery whenever it is required.

Constructors who prefer to have the battery self-contained inside the unit case will need to employ a box that is sufficiently deep to accommodate it. If the front panel of such a box measures 5½ by 4 in., the same front panel layout as is employed in the prototype can be followed. The alternative case could be home-made and it is necessary for it to be made of metal and not an insulating material.

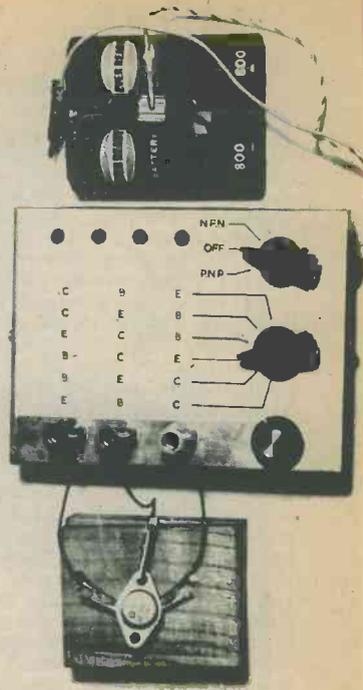S1 is a 4-pole 3-way rotary switch, and the component



By J. R. Davies

employed here should be of the 'miniature wavechange' type having a body diameter of about 1½ in.

Switch S2 is 3-pole 6-way rotary, and it is made up from Miniature Maka-Switch parts. The parts required are a Miniature Maka-Switch shafting assembly, a packet of ten miniature spacers (of which only four are used in the present application) and two miniature 2-pole 6-way wafers. When assembled, this constitutes a 4-pole 6-way switch in which only 3 of the poles are used. Miniature Maka-Switch kits are generally available through the larger home constructor mail order houses. Potentiometer VR1 needs to be a small component and it should have a body diameter of approximately ¾ in. The potentiometer used by the author was a type P20, less switch, available from Electrovalue Ltd., and having a value of 22kΩ. The two switches will be fitted with small pointer knobs, and the potentiometer with a small round knob having a skirt diameter of around ¾ in.

The spindles of all three controls should be cut to a length suitable for the knobs to be employed. The spindle of the Maka-Switch shafting assembly obtained by the author did not have a flat on it. A flat is essential here to ensure that the knob cannot rotate on the spindle, and a flat was in consequence filed out on the spindle. The flat can have any angular position on the spindle. If S1 also does not have a flat, one should be filed out on it.

The three terminals can be any insulated types which give reliable and robust connections. The appearance of the unit is enhanced if terminals of different colours are employed, but this is not, of course, essential. Final items in the 'hardware' category are the six 5-way tagstrips on which the smaller components are wired. The tagstrips used in the prototype were Lektrokit type LK-2231.

## FRONT PANEL DRILLING

As was explained in the preceding article, a piece of stiff card is affixed to the front panel of the unit and it provides a scale which denotes switch functions. The scale is shown full size in Fig. 8, and this diagram may be traced directly. It is necessary to draw up and cut out at least a rough copy of the scale before drilling the front panel, this copy having marked on it the three radial lines from switch S1, the six radial lines from switch S2, and the centres of the holes in which the l.e.d.'s will appear.

Drilling details for the front panel are given in Fig. 9. All the holes shown here may be drilled out with the exception of the four  $\frac{1}{4}$  in. holes for the l.e.d.'s. The six 6BA clear countersunk holes will later take countersunk 6BA bolts which secure the six tagstrips on the inside of the panel. The scale which has been copied from Fig. 8 is positioned on the panel in such a manner that its top edge is just below the top edge of the panel and the holes for S1 and S2 are centralised in the U-cuts at the right of the scale. Using the Fig. 8 scale as a template, mark out the centres of the four  $\frac{1}{4}$  in. holes and then drill out these holes.

Next, assemble the Maka-Switch assembly to provide S2. This requires one spacer on each length of studding between the indent plate and the first wafer, and another spacer between the first wafer and the second. Make certain that the wafers are fitted such that they function correctly as the switch spindle is rotated. Excess studding and actuating shaft at the rear is cut off.

The indent plate of the shafting assembly has a locating lug at the front which is intended to pass through a corresponding anchor hole drilled in the front panel. This ensures that the body of the switch cannot rotate even if the mounting bush nut becomes loose.

## COMPONENTS

Aluminium box type AB10,  $5\frac{1}{4}$  by 4 by  $1\frac{1}{2}$  in.  
 6-off 5-way tagstrips, Lektrokit type LK-2231  
 3 insulated terminals  
 2 pointer knobs  
 Round knob  
 2 crocodile clips  
 Sleeving  
 $\frac{3}{8}$  in. grommet  
 Miniature Maka-Switch assembly for S2  
 (see text)

Remove the bush mounting nut and washer, pass the switch bush through the panel and temporarily fit the pointer knob to it. With the aid of the Fig. 8 scale, find the orientation of S2 body which is required to ensure that its knob is correctly aligned with the six radial lines on the scale. Carefully mark out the point required for the anchor hole in the front panel, remove the switch and then drill out the anchor hole. Switch S1 will also have a locating lug. Repeat the process with this switch to ensure that its pointer knob is correctly aligned with the three radial lines on the Fig. 8 scale and then drill the anchor hole in the appropriate position.

The final piece of metalwork consists of cutting and filing out a U-cut on the side of the aluminium box near the point where S1 will appear, in the manner shown in Fig. 10. This will later take a  $\frac{3}{8}$  in. grommet through which pass the two battery leads, the grommet being held in position when the front panel is secured in place.

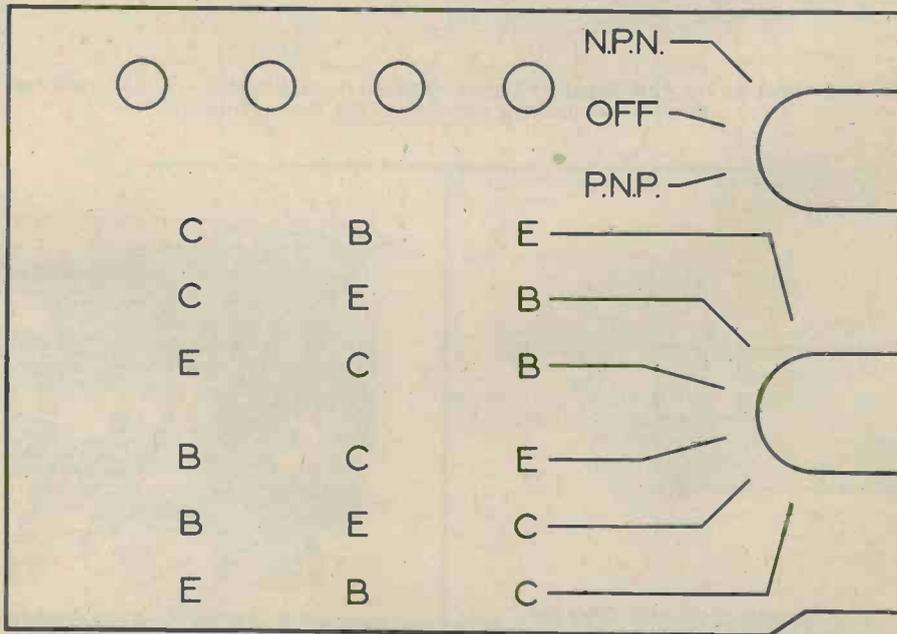


Fig. 8. The scale which is affixed to the front panel of the transistor lead locator. The mounting bush nuts of S1 and S2 fit into the two cut-outs at the right. The scale is reproduced full size and the diagram may be traced

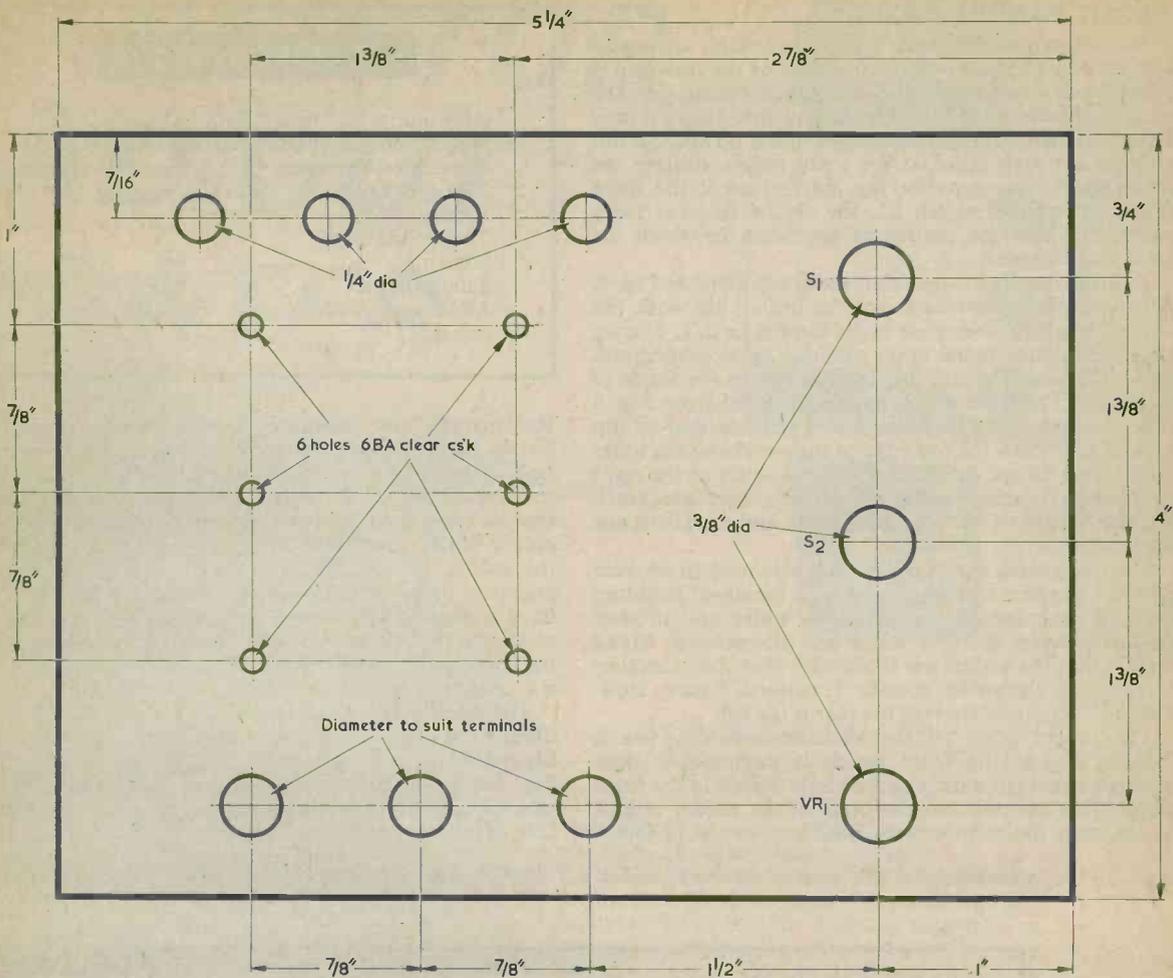


Fig. 9. Drilling details for the front panel. To ensure optimum registration, the four  $\frac{1}{4}$  in. holes at the top are marked out by using the scale of Fig. 8 as a template


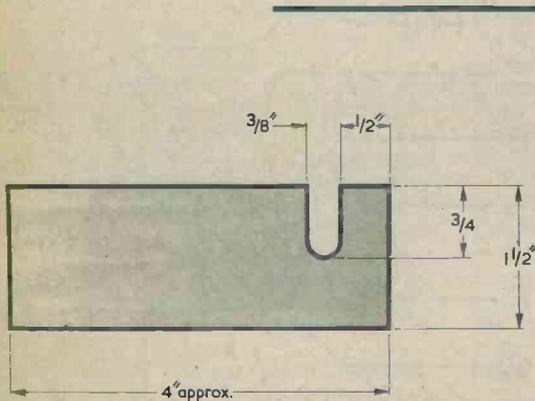


Fig. 10. A U-cut at one side of the case takes the grommet through which the battery leads pass. The grommet slides out when the front panel is removed, enabling the panel to be positioned clear of the case, when required, without any difficulty

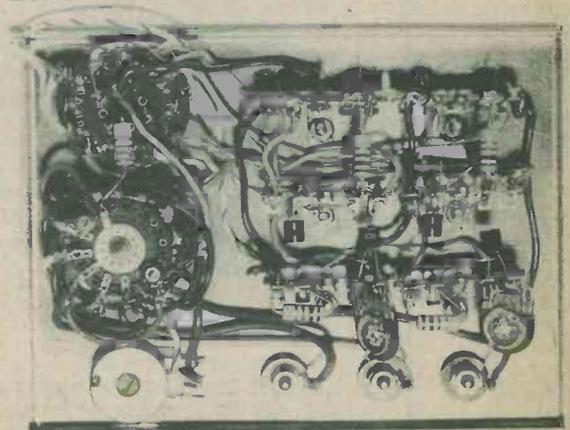

All the small components are fitted to tagstrips mounted on the rear of the front panel. This enables a compact layout to be achieved without cramping of parts

WIF  
Ne  
point  
S2, b  
in the  
work  
wirin  
last m  
switch  
tinit  
up.  
First  
switch  
may b  
point  
switch  
arm of  
pole of  
with th  
connec  
Wor  
to mak  
wire u  
the arr  
switch  
wiring  
that g  
fully c  
1, 2 a

Batt  
  
Batt

## WIRING

Next mount VR1, S2 and the three terminals, fitting a pointer knob to S2. The first component to wire up is S2, but details of the wiring required here are not shown in the wiring diagram of Fig. 11, because it is easier to work from the circuit than from a wiring diagram. The wiring circuit for S2 is given in Fig. 7, which appeared in the last month's issue. It is unimportant which poles of the switch are employed for S2(a), (b) and (c). A continuity tester is virtually essential when it is being wired up.

First connect a wire to the arm of one pole of the switch, baring its other end so that a continuity tester may be connected to it. This is the arm of S2(a), or point 'X'. Connect the arm of another pole of the switch to the centre tag of VR1. This is point 'Y', the arm of S2(b). Finally, connect R4 to the arm of a third pole of the switch, to give point 'Z', which corresponds with the arm of S2(c). The other end of R4 will later connect to a tag on S1.

Working from Fig. 7, and using the continuity tester to make certain of identifying the correct switch tags, wire up S2(a). Fig. 7 has purposely been drawn so that the arms move in the same direction as they do when the switch is viewed from the rear, and this should assist in wiring up. The position of the switch arms in Fig. 7 is that given when the knob, as viewed from the front, is fully clockwise. Three wires, corresponding to terminals 1, 2 and 3, should now be available from S2(a). Trans-

ferring the continuity tester to the arm of S2(b), proceed to wire this section of the switch, taking up the wires 1, 2 and 3 from S2(a). When S2(b) has been wired up a further three wires, 1, 2 and 3, should be available from this for S2(c). The continuity tester is then transferred to the arm of S2(c), and this is then wired up, taking in the wires 1, 2 and 3 from S2(b). The three wires 1, 2 and 3 from S2(c) are then taken to the correspondingly numbered terminals.

The writer must apologise to the more experienced constructor for putting what is, perhaps, excessive emphasis on the procedure required for wiring up S2. However, it is extremely easy to make a mistake here and an error in wiring can cause mysterious shortcomings in performance which are very difficult to remedy later. Indeed, to make quite sure that all is well, the constructor is advised to check the switch wiring with the aid of the continuity tester and Fig. 7 after wiring has been completed. If the continuity tester is connected to the arm of S2(a) there should be continuity to terminal 1 only on the first two positions of the switch, to terminal 2 only on the next two positions, and to terminal 3 only on the final two positions. The continuity tester should then be transferred to the arm of S2(b), which should connect to the terminals indicated in Fig. 7, and then finally to the arm of S2(c) and the process repeated.

General wiring up may then follow, as illustrated in Fig. 11. S1 and the six tagstrips are mounted, the central mounting lug of each of the latter being below


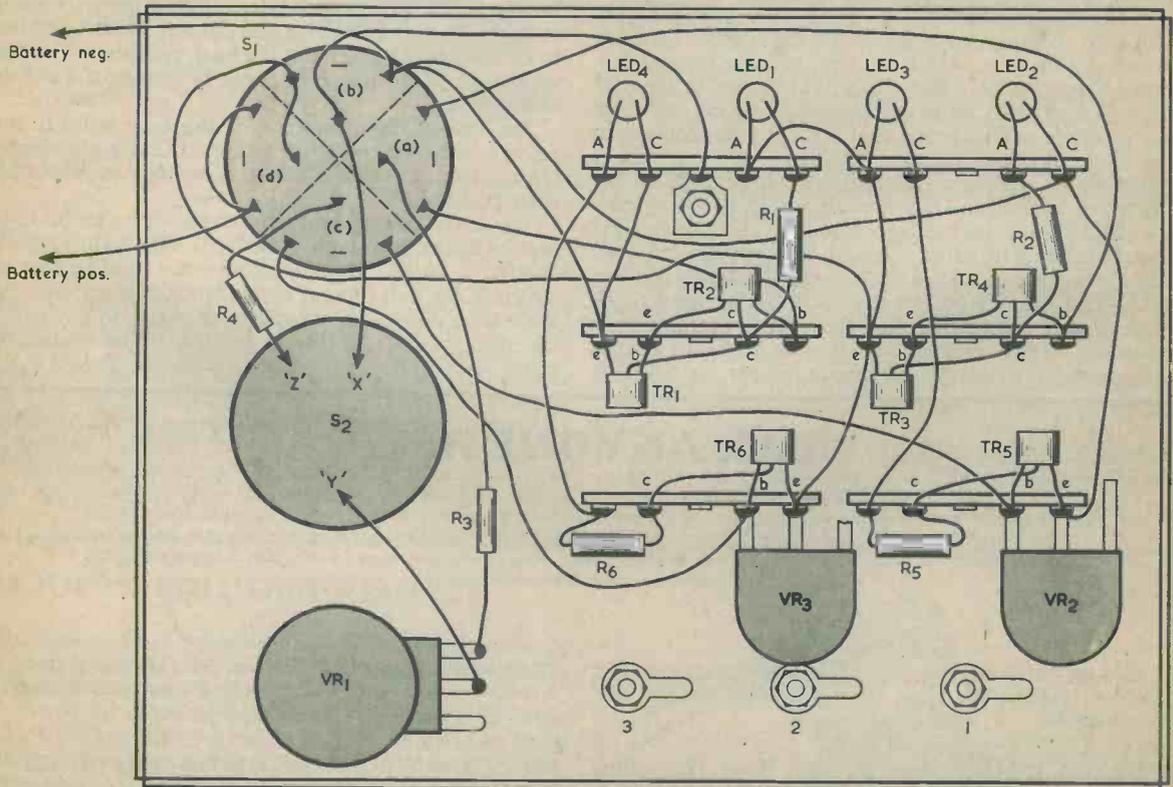


Fig. 11. Wiring diagram for the components mounted behind the front panel. The wiring at switch S2 is carried out with the aid of the circuit diagram which was published last month

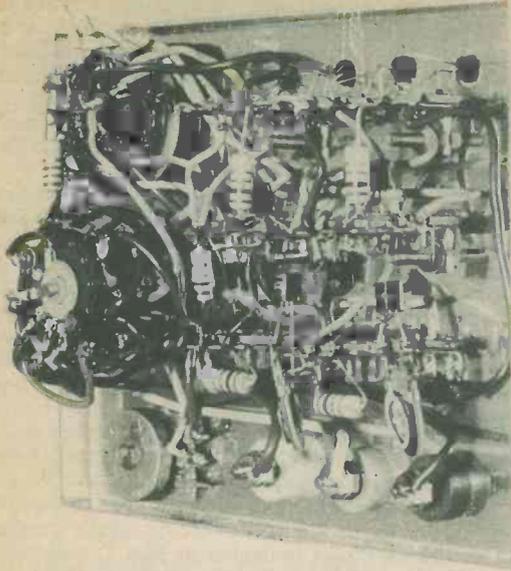

Another view of the components mounted on the rear of the front panel

the strip as indicated in the diagram. Note that the four sections of S1 do not appear, round the switch, in alphabetical order. Although less essential than when S2 was wired, a continuity tester will still be found helpful when making connections to S1. It is quite possible with some components that the centre contact for each switch section may have a position, relative to the three outside tags, which differs from that shown in the diagram. A continuity tester eliminates any wiring errors on this score. It will be noted that there is a connection to chassis from the centre tag of S1(b).

The four l.e.d.'s are soldered to the lower tags on the Lektrokit tagstrips. They are supported by their lead-outs and should be positioned so that their bodies are central in the ¼ in. holes in which they appear. 'Mid-air joints' may be needed for the collector lead-outs of TR1, TR3, TR5 and TR6. The lead-outs of R3 need to be covered with sleeving. It may be necessary to solder an extension lead to this resistor if its own lead-outs are not long enough to reach the circuit points to which it

connects. The two skeleton potentiometers, VR2 and VR3, each have two tags soldered to the adjacent tagstrips. No connection is made to the third tag of each potentiometer.

## SETTING UP

When construction is completed it is necessary to set up VR2 and VR3. First set these two potentiometers to insert maximum resistance into circuit, adjust VR1 to insert minimum resistance into circuit (i.e. fully anti-clockwise), then connect a known p.n.p. *silicon* transistor to the test terminals. Put S1 to 'PNP' and adjust S2 to the setting which corresponds to the transistor lead-outs. Both LED1 and LED4 should light up. Slowly decrease the resistance inserted into circuit by VR3 until the brightness of LED4 *just* commences to reduce.

Next connect a known n.p.n. *silicon* transistor to the test terminals and adjust S2 accordingly. Put S1 to 'NPN' and gradually reduce the resistance inserted into circuit by VR2 until the brightness of LED3 *just* starts to reduce. Both VR2 and VR3 are then set up and the unit is ready for use.

When employing the unit, remember that VR1 knob must always be initially set fully anti-clockwise. If a test transistor causes S2 to give two positions where two l.e.d.'s are illuminated, VR1 is then advanced clockwise until the incorrect reading is eradicated. This adjustment of VR1 will be occasioned mainly by germanium transistors. The required setting in VR1 is normally not at all critical and can be found very quickly.

When the unit is completed and has been checked for satisfactory operation a final version of the scale shown in Fig. 8 may be drawn up and cut out. Four holes need to be cut out in the scale at the l.e.d. positions. The scale is then affixed to the front panel by means of a suitable adhesive.

The current consumption of the unit is fairly low, being of the order of 20mA with two l.e.d.'s illuminated. On no account should a battery voltage in excess of 3 volts be used.

The circuit is earthed by the chassis connection to the arm of S2(a). Although some fairly high gain amplifier chains, in which the test transistor can itself appear, are set up in the unit there is no evidence of instability, and there is no necessity for bypass capacitors in any part of the circuit. The prototype proved to be completely stable with all transistors which were checked on it. ■

## CAN ANYONE HELP?

*Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received for to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.*

**Trio 9R-59DS Receiver** – T. C. Falconer, 112 Parkhead Drive, Edinburgh, 11 – Details of modifications and re-aligning.

**Ex W.D. 2 Valve (Mark II) Short Wave Transmitter/Receiver W 17/11/219** – A. Willis, 9 Victoria Street, Cornholme, Todmorton, Lancs, OL14 8LR – Any data, circuit or wiring diagrams.

**R109 at RX** – R. L. Morrison, 58 Derryboye Road, Crossgar, Co. Down, N. Ireland – Power pack Voltage/Current Outputs, also alignment data required.

**C.T. 373 Test Set-Oscillator/Distortion Meter** – D. Kerr, 9 Mckellar Avenue, Ardrossan, Ayrshire KA22 7AS – Handbook, Service Manual or Diagram required. Purchase or borrow.

# New Products




## BATTERY STATUS INDICATOR

New from Litronix is the RLC-400 battery status indicator, a T1 miniature-sized LED lamp with red diffused lens, incorporating a voltage-sensing integrated circuit.

Designed to indicate battery status in small portable equipment, such as calculators and cameras, the RLC-400 features a sharp turn-on characteristic, having zero luminous intensity at 2.0V and better than 0.2 mcd at 3.0V. Maximum forward voltage is 5.0Vdc. Development quantities are available now at unit prices ranging from 30p, according to volume. For further information contact: Watts, Steadman & Partners, 34 High Street, Saffron Walden, Essex, CB10 1EP.


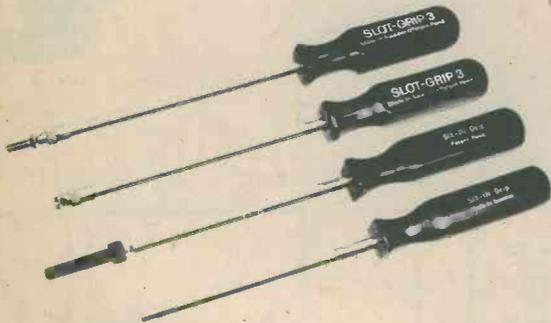
## SLOT-GRIP SCREWDRIVERS FOR EASY POSITIONING



firmly in place without the risk of dropping, regardless of the difficulties of the mounting position.

Made of highest quality non magnetic Swedish steel, these new products carry a twelve month manufacturing guarantee. The Allen and Phillips screwdrivers have one face of the tip sprung to provide a tight fit into the screw, whilst the slot head driver employs a split tip which serves the same purpose.

Known as Six-in Grip, the Allen type screwdrivers are available in eleven combinations of length and tip width, including five with insulated handles intended for use in the electric and electronic industries.

The Star-Grip Phillips range is made in five lengths covering point sizes 1, 2 and 3, whilst the standard Slot Grip is sold in two blade lengths of 150mm and 175mm, having tips of 6mm and 8mm wide respectively.

All these screwdrivers have the same turning power as ordinary drivers the Six-in Grip being provided with flats at the top of the blade, enabling a spanner to be used to give additional leverage. The Slot Grip is held in place by a sliding sleeve which enables the tip to be replaced if it should be damaged, instead of replacing the whole tool.

Prices range from 97p up to £1.68 dependent upon size, and further details may be obtained from Compass Electronics, 150 Tooley Street, London SE1 2XE.

At Internecon/UK 74, the international micro electronics exhibition held in Brighton from 15th-17th October 1974, Compass Electronics introduced a patented new range of Swedish screwdrivers, designed to end the time wasting and frustration involved in locating screws in assemblies where access is restricted. Available in three patterns to cater for Allen and Phillips-type heads as well as conventional slot head screws, the tips of these screwdrivers will hold the screw

## MODERN SOLDERING IRONS

A unique range of Soldering Irons is being introduced by Colstar Limited, who have just announced the Single-Handed Soldering Pistol type KL 3000.

The solder is fed through a reel direct to the tip of the pistol, so that soldering can be carried out with one hand, leaving the second hand free to hold components, wires, etc.

This system is widely used by major manufacturers on the Continent, and is patented in most countries.

Further information may be obtained from Colstar Limited, 233/243 Wimbledon Park Road, London SW18.



# DIRECT READING

Employing three integrated circuits, this instrument measures the values of both non-electrolytic and electrolytic capacitors up to 10 $\mu$ F. A built-in meter gives direct indication of the capacitor values.

By Alan C. Ainslie

CONSTRUCTORS OFTEN NEED TO MEASURE THE VALUES of capacitors; for example in fault finding or as a check during construction. Also one needs to find 'matched pairs' for such circuits as 'Twin Tee' or to evaluate a component for a precise application. The latter can be especially important if small electrolytic capacitors are used in critical circuits as the actual capacitance can vary considerably from that marked on the component. Large electrolytic capacitors (say over 25 $\mu$ F) are rarely used in critical circuits as they are not as stable as the smaller values.

Traditionally capacitors have been measured using bridge techniques to cover a wide range of values. However, to construct a wide range bridge is difficult, the calibration is awkward and, as it is not usually direct reading, it can be slow to use.

The instrument to be described measures from 100pF to 10 $\mu$ F f.s.d. (with useful indications at 10pF) in 6 ranges. The capacitance value is directly displayed on a panel meter with a ' $\div 2$ ' facility for small deflections.

## CIRCUIT OPERATION

The full circuit of the capacitance meter is shown in Fig. 1.

The capacitor under test is connected to pins 10 and 11 of the SN74121 monostable. The output of the monostable will be low (about 0.3 volt) normally until a negative-going pulse is applied to pins 3 and 4. The output then goes high for a period solely dependent on the value of the capacitor and the resistance, between pin 11 and the 5 volt positive rail, which is selected by S3(b).

The high output level of the 74121 is clamped to 3.3 volts by zener diode D3. R7 ensures a satisfactory zener current in the high state. Thus the output at pin 6 of the 74121 is a pulse of defined height whose duration is controlled by the unknown capacitor.

A repetitive pulse train (clock) is fed to pins 3 and 4 of the monostable. As this pulse train has a constant period for each range the mark-space ratio or duty cycle of the monostable output is governed solely by the unknown capacitor.

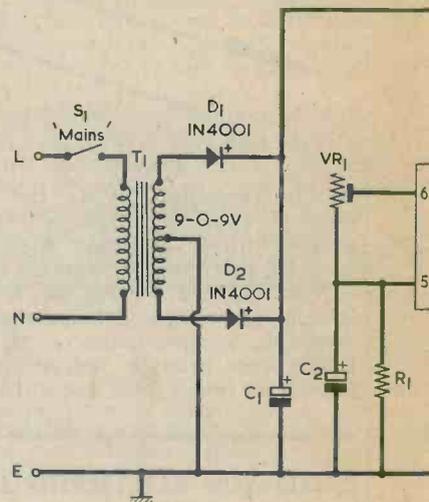


Fig. 1. The

# DIRECT READING CAPACITANCE METER

By Alan C. Ainslie

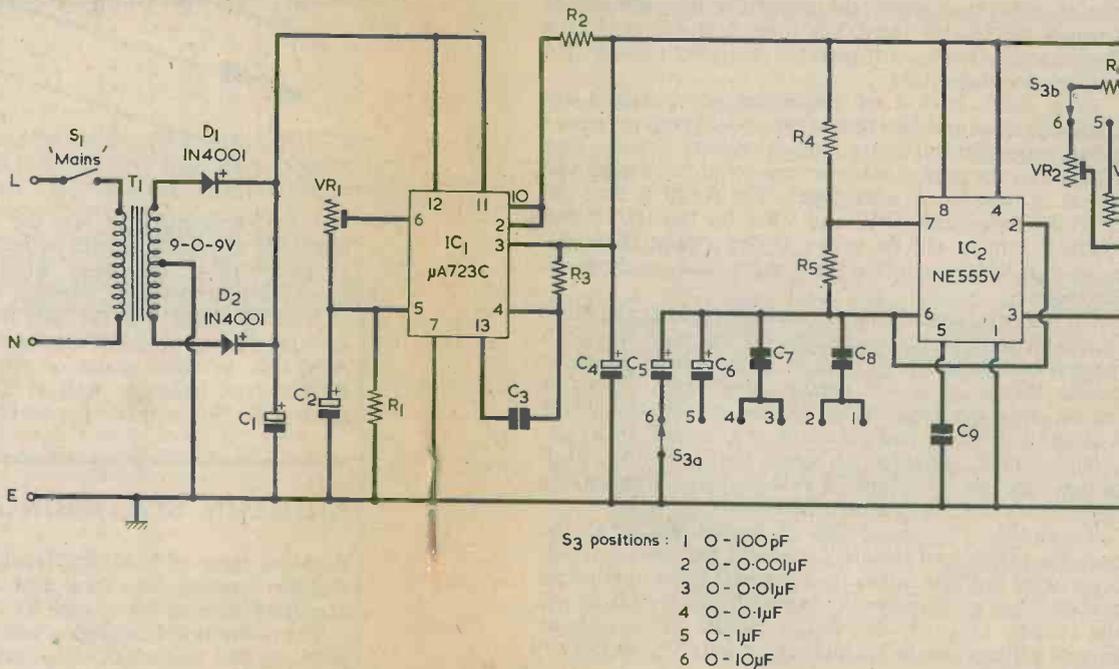


Fig. 1. The circuit diagram of the direct reading capacitance meter. This is capable of measuring values up to 10 $\mu$ F



A simple voltmeter connected to the output pulse train takes the average of the waveform and gives a deflection proportional to the mark-space ratio, i.e. proportional to the capacitance.

Fig. 2 shows the principle of operation diagrammatically. The range under consideration is the  $1\mu\text{F}$  f.s.d. range. With a  $1\mu\text{F}$  external capacitor the mark period is shown as half the clock period. This corresponds to a mark-space ratio of 1:1. The mean of a 1:1 pulse train is one half of the peak value, i.e. 1.5 volt. Thus the voltmeter would read 1.5 volt f.s.d.

With a  $0.5\mu\text{F}$  external meter the mark-space ratio is reduced to 1:3, i.e. the mark is one quarter of the whole period. The mean voltage is now 0.75 volt, giving a meter deflection of 0.5 f.s.d. Similarly with an external capacitor of  $0.25\mu\text{F}$  we find that the mean would be 0.375 volt, corresponding to 0.25 f.s.d.

From these examples it is quite obvious that the scale is perfectly linear.

The voltmeter multiplier resistance is made up of R8 and VR9. Switch S2 short-circuits VR9 to halve the multiplier resistance and double the deflection when the meter reads below half full scale. This helps to improve the accuracy of the readings.

In order to offset the 0.3 volt that exists at the monostable output when it is low (and which would cause a zero error) the negative end of the voltmeter is returned to a potential developed across the potential divider, R10, VR8, the latter being the 'set zero' pre-set control.

The clock is formed by an astable 555 oscillator which offers the high stability required. The 555 output is t.t.l. compatible when the device is powered from a positive 5 volt rail as in this application.

C5, C6, C7 and C8 form the charge capacitors selected by S3(a). R4 and R5 form the charge resistors and R5 is the discharge resistor. C9 decouples the control voltage point, which is unused.

## CALCULATIONS

To cover the six decade ranges it may be thought that six different clock rates would be required. However the 74121 accepts timing resistors from  $1.4\text{k}\Omega$  to  $40\text{k}\Omega$ . As this is a range of over 10:1 the switching between adjacent pairs of ranges can be accomplished merely by

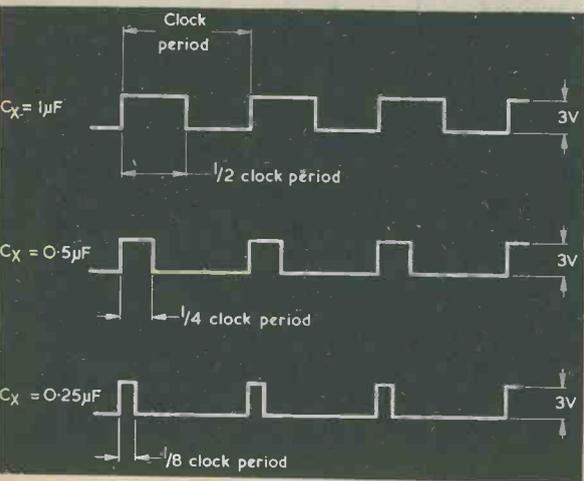


Fig. 2. The length of the positive pulse at the output of the SN74121N varies in linear fashion with the value of the test capacitance

changing the 74121 timing resistors, which have to be switched anyway to allow calibration of each individual range. Thus the expense of a couple of capacitors can be saved.

Choosing the 74121 timing resistors to be pre-set at about  $1.75\text{k}\Omega$  and  $17.5\text{k}\Omega$  gives ranges separated by a factor of 10. The period of the monostable is given by

$$T = 0.7Ct.Rt,$$

and so the period will be  $1.2 \times 1,000Ct$  and  $12 \times 1,000Ct$  for the  $1.75\text{k}\Omega$  and  $17.5\text{k}\Omega$  values of  $Rt$  respectively.

Thus for the  $0.01\mu\text{F}$  range the period will be  $120\mu\text{S}$  with  $Rt$  at  $17.5\text{k}\Omega$  and for the  $0.1\mu\text{F}$  range the period will again be  $120\mu\text{S}$  with  $Rt$  at  $1.75\text{k}\Omega$ . The one clock period to cover both these ranges should be twice the monostable period, i.e. about  $240\mu\text{S}$ .

The 555 timer has two separate timing equations, one for charge through R4 and R5 and another for discharge through R5 only. These equations are:

$$T1 = 0.7Cc(R4 + R5)$$

$$\text{and } T2 = 0.7Cc(R5).$$

The total period is  $T1 + T2$  and

$$T1 + T2 = 0.7Cc(R4 + 2R5).$$

With R4 and R5 equal,

$$T1 + T2 = 0.7Cc(3R).$$

The value of  $T1 + T2$  that we require is  $240\mu\text{S}$ . With  $Cc$  at  $0.1\mu\text{F}$  this period is given when  $3R$  is  $3.3\text{k}\Omega$ , so both R4 and R5 could be  $1\text{k}\Omega$ .

For the  $100\text{pF}$  range the monostable period is  $1.2\mu\text{S}$  with  $Rt$  at  $17.5\text{k}\Omega$  and for the  $1,000\text{pF}$  range a  $1.2\mu\text{S}$  monostable period is obtained with  $Rt$  at  $1.75\text{k}\Omega$ . With a  $Cc$  of  $1,000\text{pF}$  timing, the clock period is calculated to be the required  $2.4\mu\text{S}$ .

The operation of the 555 timer is such that pins 6 and 2 are comparator inputs which cause  $Cc$  to discharge when pins 6 and 2 are at a voltage slightly more than two thirds  $V_{CC}$ . When the capacitor has discharged through R5 to one third  $V_{CC}$  pins 6 and 2 cause the discharge process to stop and the charging through R4 and R5 to commence.

At a clock period of  $2.4\mu\text{S}$  the comparators are relatively slow and the discharge and charge processes extend considerably past the calculated limits. This means that the period is longer than that calculated and comes in practice to about  $4\mu\text{S}$ . The result is that the calibration resistors, VR7 and VR6, for the  $100\text{pF}$  and  $1,000\text{pF}$  ranges will be set to higher values than calculated in order to obtain the correct f.s.d. readings on the meter.

On the two largest ranges the clock period calculated to enable one timing capacitor to be used for both ranges would be  $24\text{mS}$ . This is long enough to cause needle flicker in a few meter movements. For this reason only the  $10\mu\text{F}$  range is used at this clock rate with the  $1\mu\text{F}$  range being clocked at a faster  $2.4\text{mS}$  rate.

The timing resistors on both the  $1\mu\text{F}$  and  $10\mu\text{F}$  ranges are set at about  $1.8\text{k}\Omega$  to give monostable periods of  $1.2\text{mS}$  and  $12\text{mS}$  respectively.

To reduce the possibility of needle flutter at the possible expense of linearity the discharge resistor, R5, is specified as  $820\Omega$  rather than the  $1\text{k}\Omega$  value mentioned earlier. This gives generally higher clock speeds on all the ranges. Linearity difficulties should not intrude as even at a duty cycle of 3:2 an error of only 5% maximum is introduced.

The combinations of clock speeds and full scale monostable periods are summarised in the accompanying table. The values given should be taken as a nominal guide only, as component tolerances can cause significant changes to the calculated values.

**TABLE**  
*Clock and Monostable Periods*

Range	Clock Period	Monostable Timing Resistor (Non-adjusted Value)	Monostable Period at Full Scale
100pF	4μS	50kΩ (VR7)	1.5μS
0.001μF	4μS	5kΩ (VR6)	1.5μS
0.01μF	240μS	50kΩ (VR5)	120μS
0.1μF	240μS	5kΩ (VR4)	120μS
1μF	2.4mS	5kΩ (VR3)	1.2mS
10μF	24mS	5kΩ (VR2)	12mS

### POWER SUPPLY

The 555 and 74121 both give timing periods which are reasonably independent of the power supply voltage, but to ensure good short and long term stability a power supply regulator is incorporated for the positive 5 volt rail.

The current required by the unit is about 50mA or so and a μA723 regulator chip is able to supply this current without an external emitter follower.

At pin 6 a stable reference of just over 7 volts is produced. This is divided by R1 and VR1 and fed to pin 5, the non-inverting input of the comparator. The inverting input, pin 4, is connected to the output of the device via R3 to equalise the differential input resistance and reduce thermal effects. R2 produces a voltage drop which, when it exceeds 0.6 volts, causes the regulator overcurrent limit to function, thereby protecting the devices in the event of a fault. C3 is necessary to provide frequency compensation.

The μA723 is fed by about 11 volts or so from a centre tapped 9-0-9 volt transformer, with D1 and D2 as rectifiers.

### COMPONENTS

The timer and monostable integrated circuits are available from most mail order suppliers dealing in components of this type. The regulator is a type μA723C in 14 pin d.i.l., and an equivalent is the Texas SN72723N. Another equivalent is listed by Electrovalue Ltd., as LIC723C14.

The mains transformer employed in the author's unit was a small component offering 9-0-9 volts at 100mA, and having fixing centres at approximately 1½ in. This is not listed by the larger mail-order houses and a suitable, but somewhat bigger, alternative is the Osmabet transformer retailed by Home Radio under Cat. No. TMM9. The Osmabet transformer secondary current rating is 0.3 amp. Any other small 9-0-9 volt transformer with a current rating of 100mA or more can also be used.

The holes in the author's printed circuit board for the tags of VR2 to VR8 inclusive are intended for miniature horizontal mounting skeleton pre-set potentiometers. Components having the requisite tag spacing are potentiometers type PN, horizontal mounting, obtainable from Electrovalue Ltd. VR1 and VR9 may similarly be Electrovalue type PN, vertical mounting.

NOVEMBER 1974

## COMPONENTS

### Resistors

(All fixed values ¼ watt 10%)

R1	4.7kΩ
R2	4.7Ω
R3	2.2kΩ
R4	1kΩ
R5	820Ω
R6	1kΩ
R7	680Ω
R8	4.7kΩ
R9	10Ω
VR1	5kΩ
VR2	5kΩ
VR3	5kΩ
VR4	5kΩ
VR5	50kΩ
VR6	5kΩ
VR7	50kΩ
VR8	1kΩ
VR9	10kΩ

### Capacitors

C1	640μF electrolytic, 16 V. Wkg.
C2	10μF electrolytic, 12 V. Wkg.
C3	100pF
C4	10μF electrolytic, 12 V. Wkg.
C5	10μF electrolytic, 12 V. Wkg.
C6	1μF plastic foil or electrolytic, 12 V. Wkg.
C7	0.1μF
C8	0.001μF
C9	0.047μF

### Integrated Circuits

IC1	μA723 or equivalent
IC2	NE555V or equivalent
IC3	SN74121N

### Diodes

D1	1N4001
D2	1N4001
D3	3.3 volt zener diode, 400mW

### Transformer

T1	Mains transformer, secondary 9-0-9V (see text)
----	--

### Meter

M1	Moving-coil meter, 0-100μA
----	----------------------------

### Switches

S1	s.p.s.t. toggle
S2	single pole push-button, press to close
S3	2-pole 6-way rotary

### Miscellaneous

1 red socket
1 black socket
1 knob
Printed circuit board
Materials for case and panel

## CONSTRUCTION

The electronics can be built on a small printed circuit board. In the prototype the board was secured to the two terminals of the meter, this being a Japanese model MR-65P having the same outside dimensions as The Henelec 65 Series retailed by Henry's Radio Ltd. The mains transformer was also mounted on this board. The component and copper sides of the board are illustrated in Figs. 3 and 4, the latter being reproduced full size. In Fig. 4, the two holes 'X' are for the meter

terminals and the two holes 'Y' are mounting holes for the mains transformer. The positions of these holes will vary for different meters and transformers and should be marked out with the aid of the components themselves. It will also probably be necessary to make the board slightly larger than is shown in Fig. 4 to take alternative transformers, and the board should not be cut out until the transformer has been obtained and the modified dimensions determined. It will merely be necessary to make the board a little wider and longer.

Fig. 3. The component side of the printed circuit board


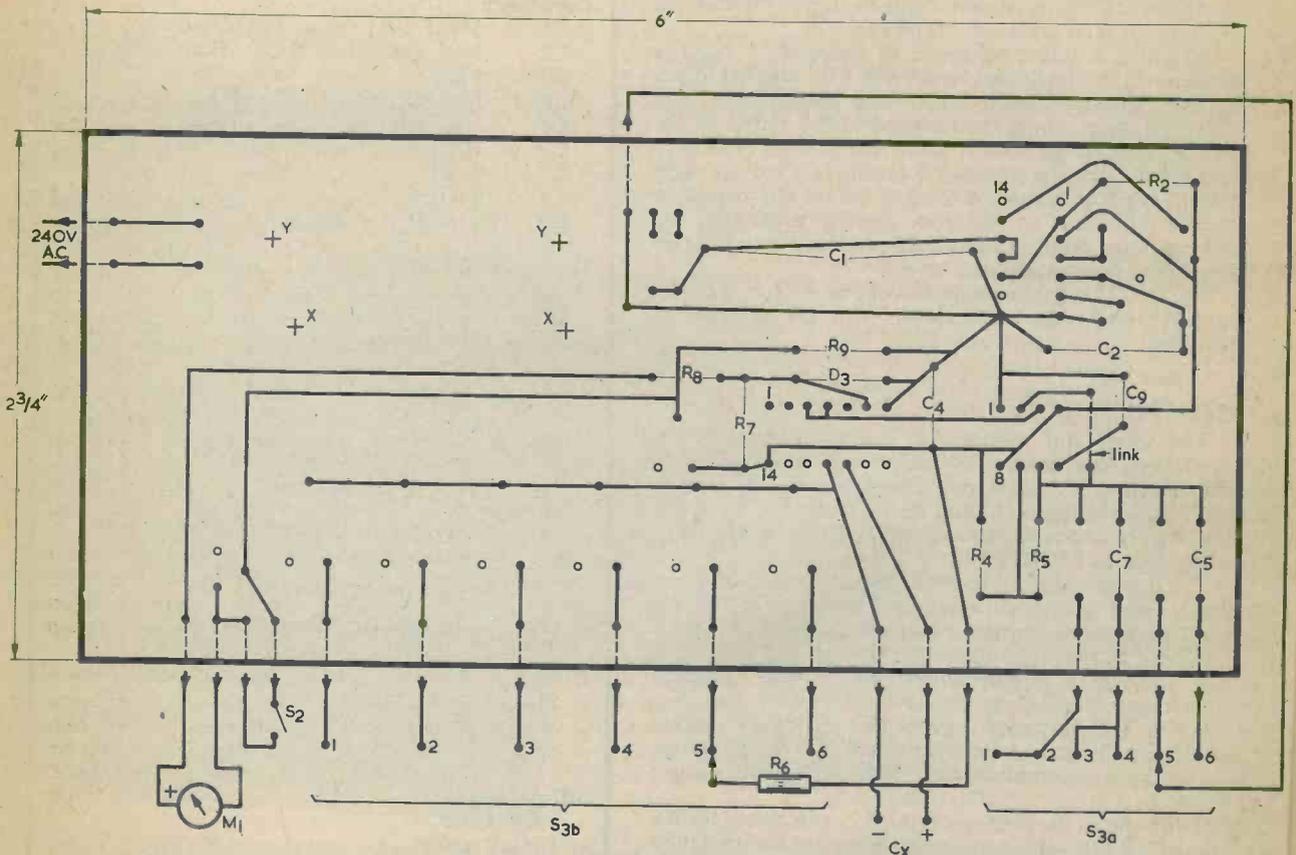
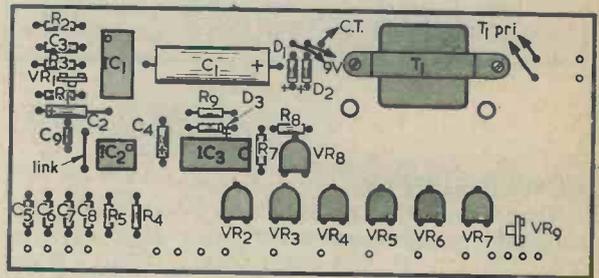


Fig. 4. The copper side of the board. To assist in positioning components, the end pins of the integrated circuits are indicated as also are some of the capacitors and resistors. The negative rail connection to pin 8 of IC1 is in order as this is an 'NC' pin. The board dimensions, but not the basic copper pattern, may need to be modified for different mains transformers and meters

The copper pattern for all the remaining components remains unaltered and can be traced from Fig. 4.

The design can be marked out onto the clean copper board with one of the many p.c.b. resist pens now available. There is no location for R6, which can be mounted on the range switch.

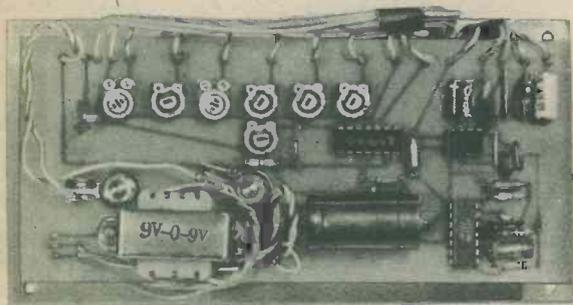
The author recommends that the project be constructed on fibre glass board for stability. This is available from Home Radio Ltd., in varying sizes, including 4 by 16 in. under Cat. No. BTS53. To ensure even



etching of the panel it can be floated copper side down on top of the etchant. In this way the copper removal is more even and etching is quicker.

The etched board can now be drilled. A No. 60 drill (0.040 in.) is suitable for most of the component leads, although the pre-set potentiometers will require slightly larger holes. The components are inserted on the board as in Fig. 3, taking particular note of diode polarities and i.c. orientation.

The next stage is to prepare the cabinet and front panel, and the photographs should give a guide as to a suitable panel layout. The dimensions of the panel and case should suit the particular meter employed and allow the printed circuit assembly to be comfortably housed. A number of commercial cabinets of about the required size are available. On the front panel one of the sockets for the test capacitor should be red to indicate the positive connection and the other black. The author employed a mains on-off push-button switch whose contacts close and then open on successive pushes, but a normal toggle switch could also of course be used.

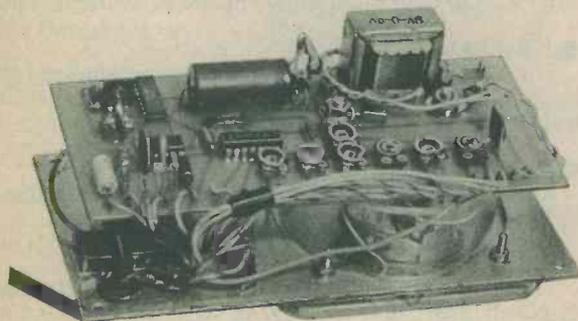

*The printed circuit board is mounted by the two connecting bolts of the meter movement*

As already mentioned, the completed printed circuit board is supported at the two holes marked 'X' through which pass the terminals of the meter. The wiring from the controls to the board can now be completed using neat short leads as this is in fact a fairly high frequency circuit. It was found with the prototype that the stray capacitances in the 'Cx' leads was of the order of 6 to 7pF. This small capacitance could be reduced slightly, if desired, by spacing the leads to the test sockets away from other wiring.

*The printed panel with the components mounted. This corresponds to Fig. 3*

The author also fitted a small bulb inside the meter to illuminate its scale, the bulb being powered from one half of the mains transformer secondary. The bulb is not included in the Components List.

## CALIBRATION

The completed unit is now ready for testing and calibration. VR1 is set to maximum resistance and the mains supply switched on. VR1 is then adjusted to give a reading of 5 volts on pin 8 of the 555.

With S2 closed, a high capacitance range selected and no external capacitor connected, VR8 is adjusted to bring the meter pointer exactly to zero.

A capacitor of about 0.047 $\mu$ F is next connected to the test terminals. With the range switch at the 0.1 $\mu$ F position VR4 is adjusted so that with S2 closed the meter reads full scale. S2 is then opened and VR9 adjusted so that the meter reads exactly half full scale.

The voltmeter part of the instrument is now set up and the ranges can next be set for full scale deflection, starting with the 100pF range and adjusting VR7, and finishing with the 10 $\mu$ F range and adjusting VR2. Obviously, good 'standard' capacitors should be used but the average of a batch of reputable capacitors should not be too far off.


As explained earlier the 10 $\mu$ F range may be subject to needle flutter. If this is the case then R5 can be reduced, say to 680 $\Omega$ . However, the circuit has been used with several meter movements and all have shown less than 1% flutter.

If an oscilloscope is available the waveform at pin 6 of the 74121 can be checked. The mark-space ratio at f.s.d. should not be significantly in excess of 1:1 otherwise linearity may suffer. Poor linearity with the correct waveform can be directly attributable to the 74121. Checking with a digital period meter shows very good linearity with the majority of devices.

All components in the Components List are rated for continuous operation and, with reasonable care in assembly and calibration, the constructor will have a reliable capacitance meter of high accuracy and good stability.

# SHORT WAVE NEWS

## FOR DX LISTENERS

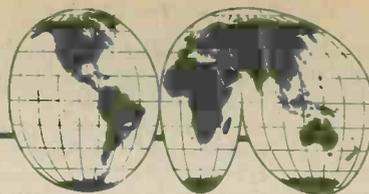

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

Stepping off once again on the left foot (like all exercise types) we commence with the subject of clandestines – and why not, the vast majority of them are left anyway, and extremely left at that!

On 9422.5 one afternoon at 1543 we had the pleasure of hearing one of our old friends, none other than "Voice of the Thai People". This one had previously been reported inactive but has obviously now been reactivated. Programme format is the usual OM and YL alternate harangue in Thai until 1600 when there is a marching song by male chorus, military music at 1608, slogans and off at 1610. The transmission is thought to be a Chinese operation from Yunnan Province.

A little earlier in the afternoons, if you are around, set the dial on 9988.5 from 1400 onwards and you may log the Voice of the United National Front of Cambodia. Logged several times recently, the last entry shows that signal strength peaked from 1420 onwards when the usual format emerged. Yes, you guessed aright, OM and YL in Cambodian (Khmer) alternately, each vying to out-harangue the other apparently. Sign-off was at 1432, suddenly and without any military music etc.

For listeners here in the U.K. the best chances of hearing VUNFC would be from 1330 sign-on to 1430 sign-off and from 2300 sign-on to 2400 sign-off on 9988, 10080, 10120 and on 12005 (all variable by plus or minus 5kHz). They also transmit on 4675 and 7015 as above but these channels are unlikely to be heard here.

### CURRENT SCHEDULES

#### ● TANZANIA

Radio Tanzania, Dar es-Salaam, operates an External Service mainly in English from 0330 to 0530 on 6105; from 0900 to 1600 on 9750 and from 1600 to 2015 on 15435 and 4785. R. Tanzania can also be currently heard, in Swahili and English, on 4825 and on 5050 during the early evenings. For 90 metre band hunters, listen on 3339 around 1700 for Zanzibar (See Around the Dial).

#### ● SPAIN

Spanish National Radio (RNE), Madrid, has an External Service to Europe, Africa, North and South America. English is only used in the North American Service from 0100 to 0345 on 6065 and 11925.

#### ● AUSTRALIA

Radio Australia currently offers a programme in English to the U.K. from 0645 on 7280 and 9570 and an evening transmission to the U.K. from 1800 to 2100 on 7270, 9745 and on 9755. When checked by us at 1900

(newscast) only the latter channel was audible and even that was marred by co-channel QRM.

#### ● NETHERLAND

Radio Nederland, Hilversum, presents an External Service in English to Europe from 0930 to 1050 on 6045 and 7210; from 1400 to 1520 on 6045, 11740 (Madagascar relay), 15415, 15425 and 21570 (both transmissions also on 6020 on Sundays only). From 1830 to 1950 on 6020, 6085 and 11950; from 2000 to 2120 on 11730 (Madagascan relay).

#### ● BELGIUM

An External Service from Brussels in English is directed to the Americas from 2255 to 2315 and to the Americas and Far East from 0040 to 0100 on 6055, 9655 and on 11855.

#### ● PAKISTAN

Radio Pakistan has a World Service directed to the U.K. from 0830 to 1100 in Urdu on 15115 and 17910 and from 1915 to 2115 in Urdu, Sylheti and English on 7085 and on 9463.

#### ● SOUTH AFRICA

Radio RSA, Johannesburg, currently directs a programme in English to Europe and West Africa from 2100 to 2150 on 5980, 7270, 9525 and on 11900.

#### ● MEXICO

Radio Mexico operates an External Service in Spanish but identification is sometimes given in both French and English. The transmissions are from 1325 to 1535 and from 2255 to 0305 on 9705, 11770, 15125 and on 21705.

#### ● NIGERIA

The Voice of Nigeria, Lagos, beams a programme in English to Europe from 0555 to 0735 on 7275, 11770 and on 15185.

#### ● BANGLADESH

Radio Bangladesh, Dacca, now broadcasts in English to Europe from 1230 to 1300 on 17680.

#### ● EGYPT

The Overseas Service from Cairo radiates in English to North America from 0200 to 0330 on 9475; from 1315 to 1430 to South Asia on 17920 and from 2145 to 2300 to Europe (newscast at 2200) on 9805.

Broadcasts to Africa ("Voice of Africa") in English to West Africa is from 2030 to 2200 on 17725.

RADIO & ELECTRONICS CONSTRUCTOR

## AROUND THE DIAL

On the higher frequency bands we have -

### ● EGYPT

Cairo at 0942 on 17745 with a programme of Arabic music and songs by both male and female singers.

### ● PAKISTAN

Radio Pakistan at 1615 on 9460 when presenting a programme in English about recent events in Mozambique. Sign-off without National Anthem at 1619.

### ● MONACO

Trans World Radio at 1520 on Sundays with a religious programme. Identification at 1530 then news of church affairs here in the U.K. Listen on 9685.

### ● CHINA

Radio Peking at 1239 on 11650 when featuring a programme in English describing the Chinese industrial scene and achievements, future plans and endeavours.

### ● FINLAND

Helsinki at 1424 on 9550 with an informative presentation of Finnish theatre history and recent productions.

### ● TANZANIA

Radio Tanzania, Dar es-Salaam, at 1800 on 15435 when we heard the 6 pips time signal, identification "Radio Tanzania, Dar es-Salaam", the world news in English with a further identification at 1804.

### ● CONGO

R.TV Congolaise, Brazzaville, at 2301 on 4765 when signing-off after the National Anthem, revealing two Latin American stations on the same channel.

### ● INDIA-1

All India Radio, Delhi, at 1000 on 17775, with a newscast of local events in English until 1010 when a pleasant-voiced YL presented news of recent proceedings within the Indian parliament. Very informative.

On the LF bands a whole host of stations have been logged and we first present a few which could be heard by the beginner listener, leaving the Dx till last.

### ● IRAQ

Baghdad at 2021 on 3240, Arabic music and songs, OM announcer.

### ● GHANA

Accra at 2002 on 4915 with a newscast in English read by OM announcer.

### ● MALAWI

Blantyre at 2139 on 3380 religious programme in English. Also at 1810 with world news in English, time check at 1815 and into vernacular programme.

### ● TANZANIA

Zanzibar at 1721 on 3339 with a programme in Swahili to 1733 sign-off, heard often.

### ● BURUNDI

Bujumbura at 1827 on 3300, African music, drums, chants, channel suffers from heavy QRM at times.

### ● ANGOLA

CR6RZ Emisora Official, Luanda, with a programme of dance music records at 2005 on 3375

### ● INDIA-2

AIR Delhi at 1820 on 3905 YL with song in Hindi, local music.

For the Dxer, the following may be of some interest.

### ● PERU

OAX8F Radio Atlantida at 0452 on 4788 station identification and Euro-style dance music records, announcements in Spanish, sign-off 0601.

OAX8X Radio Samaren at 0315 on 4815, identification, local pops, ads. At 0330 after identification, programme of Andean flute and drum music with 'noticias'.

OAZ4C Radio Andina at 0410 on 4995, plaintive Andean songs and music by OM, identification at 0414.

OAX8V Radio Eco at 0423 on 5010, songs in Spanish, LA music with frequent identifications preceded by two chimes.

### ● COLOMBIA

HJLZ La Voz del Cinaruco at 0436 on 4865, OM in Spanish, local music, identification 0437, newscast.

HJKC Em. Nuevo Mundo at 0500 on 4755 OM with identification then local news in Spanish.

### ● ECUADOR

HCRQI Radio Quito at 0323 on 4923 local music, guitar, OM with song, announcements with identification at 0326.

HCAJ2 C.R.E. Guayaquil at 0347 on 4765, OM with song and guitar, hetro QRM.

### ● SRI LANKA

Colombo at 1703 on 4902, commencement of Buddhist chants on full moon day.

Colombo at 1705 on 4870, OM and YL with duet in vernacular, local music, off with choral National Anthem at 1731.

### ● INDIA

AIR Delhi at 1653 on 4800, OM with song in Hindi, local music, sign-off without National Anthem after announcements by YL at 1700.

### ● PAKISTAN

Peshewar at 1749 on 3330, YL's in chorus with local song, 6 pips at 1800 and identification in English.

Radio Pakistan on 4835 at 1611, YL with talk in Urdu, sign-off at 1628 with National Anthem after identification in English.

R. Pakistan at 2027 on 4734 YL with song in Urdu, local music, announcements in French.

### ● SINGAPORE

R. Singapore at 1603 on 5010 with Euro-style dance music records and announcements in English, also in parallel on 5052. Sign-off at 1628 with National Anthem after series of announcements in English.

### ● MALAYSIA

Kuching at 2235 on 5005, YL with announcements in vernacular, light music local style.

### ● HONDURAS

HRPL3 Radio Progreso, LA music at 0358 on 4920, OM with identification then sign-off without National Anthem at 0400.

### ● S. YEMEN

Aden at 1719 on 5060, OM with songs in Arabic, local music, hetro QRM.

# SELECTIVE

## Part 3

In this final article of our 3-part series, details are given of three optional stages which may be added to the basic receiver.

THE FIRST TWO ARTICLES IN THIS SERIES DESCRIBED THE basic receiver. This concluding section will deal with three additional optional stages which may be installed in the receiver after it has been completed. Any one of these can be used, and they all require the fitting of a B7G valveholder to the chassis hole which was marked 'For Extra Stage' in Fig. 4.

### PRE-AMPLIFIER

The pre-amplifier is an untuned r.f. booster stage designed to raise the signal level when a telescopic aerial fitted to the cabinet is relied upon for reception, or

when a *very short* aerial is in use. The circuit for this stage is shown in Fig. 7.

Wiring should be short and direct, with grid and anode leads kept well separated. The primary of L1, originally used for aerial coupling, is disconnected from the chassis and its pin 9 is taken to the h.t. positive line via R4, with C4 functioning as an r.f. bypass capacitor. The valve should be fitted in a skirted valveholder with screening can, and the central spigot of this valveholder is earthed to the chassis.

This stage will give a substantial increase in signal strength. It is *not* suitable for use with a long aerial, and will only introduce cross-modulation and other troubles if such an aerial is connected.

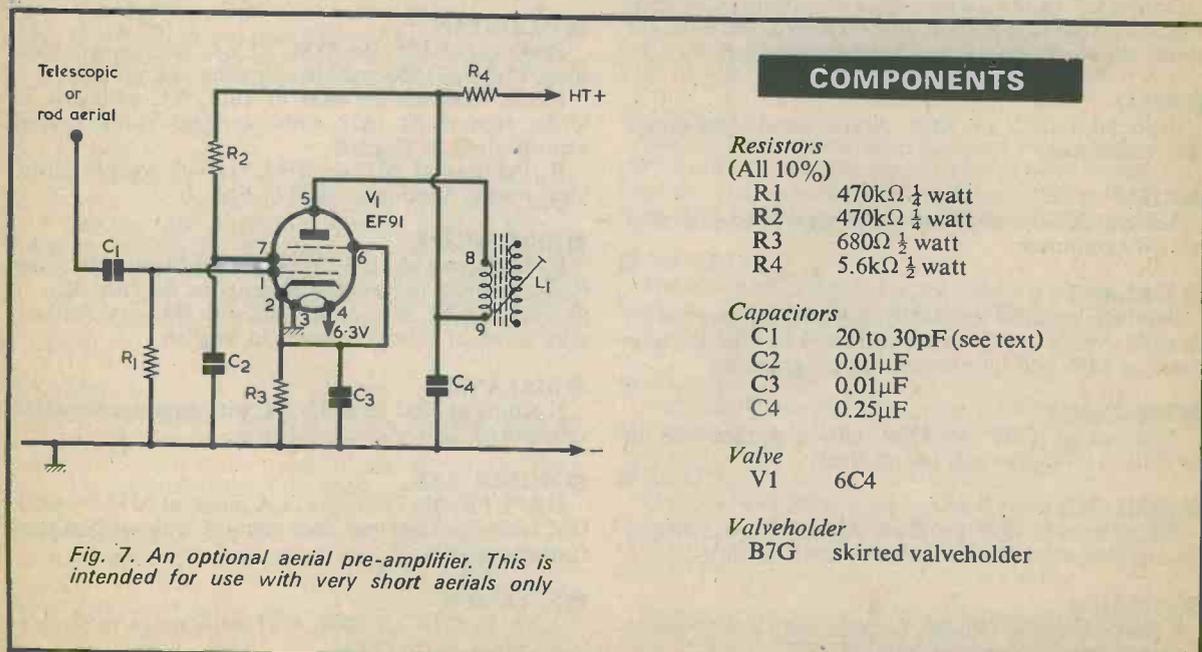


Fig. 7. An optional aerial pre-amplifier. This is intended for use with very short aerials only

# RECEIVER FOR THE L. F. BANDS

By F. G. Rayer, T.Eng. (C.E.I.) Assoc. I.E.R.E.

## CRYSTAL MARKER

The circuit of the crystal marker is given in Fig. 8. It employs a 100kHz crystal, giving harmonic 'pips' at 100kHz or 0.1MHz points. Its primary use is to provide exact calibration of Amateur bands. As an example, it will give marker 'pips' at 1.8, 1.9 and 2.0MHz in the 160 metre band, and at 3.5, 3.6, 3.7 and 3.8MHz in the 80 metre band.

For the low frequency short wave range, one frequency can be established by tuning in the standard frequency transmission from MSF on 2.5MHz. All the other 0.1MHz points can then be marked by counting up and down from this known frequency.

TC1 allows the crystal frequency to be varied slightly to permit zero beating with the 2.5MHz transmission, or with the B.B.C. Radio 2 200kHz signal tuned in on

the long wave band of another receiver. An error in crystal frequency will be heard as a very low audio tone or as a flutter on reception, but even if this is not corrected the accuracy will be far higher than is usually needed for the present purpose. Suitable 0.1MHz crystals are available from many suppliers of short wave components.

The crystal harmonic will operate the tuning indicator or may be heard when the b.f.o. is switched on. The oscillator valve is not screened and the location of this stage should give sufficient stray coupling into the receiver r.f. circuits. If it is wished to increase the coupling for higher frequency bands, run an inch or so of insulated wire from tag 5 of the oscillator valveholder close to VC7.

The oscillator is controlled by a rotary on-off switch mounted between VR1 and VR2, and the crystal is positioned below the chassis.

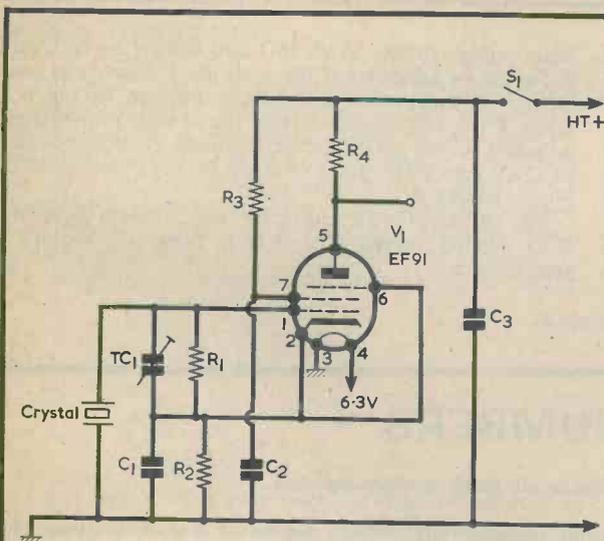


Fig. 8. The 0.1MHz crystal marker. This provides harmonics of crystal frequency over all the ranges covered

## COMPONENTS

### Resistors (All 10%)

R1	470k $\Omega$ $\frac{1}{4}$ watt
R2	10k $\Omega$ $\frac{1}{2}$ watt
R3	100k $\Omega$ $\frac{1}{2}$ watt
R4	22k $\Omega$ $\frac{1}{2}$ watt

### Capacitors

C1	1,000pF silvered mica
C2	0.01 $\mu$ F
C3	0.01 $\mu$ F
TC1	100pF trimmer

### Valve

V1	EF91
----	------

### Switch

S1	s.p.s.t. rotary
----	-----------------

### Crystal

	0.1MHz quartz crystal with holder
--	-----------------------------------

### Valveholder

B7G	plain valveholder
-----	-------------------


## ELECTRONIC MUTING

When the receiver is used in conjunction with a transmitter, some means of change-over is necessary when the transmitter is turned on. This frequently consists of transferring the aerial from the receiver to the transmitter, and of muting the receiver to avoid acoustic feedback from its loudspeaker to the microphone.

The circuit in Fig. 9 causes the change-over to be

depends on the aerial impedance and transmitter power, but can be expected to be of the order of 30 to 100 volts. C26 and R22 in Fig. 9 are the existing capacitor and resistor in the receiver a.f. stages.

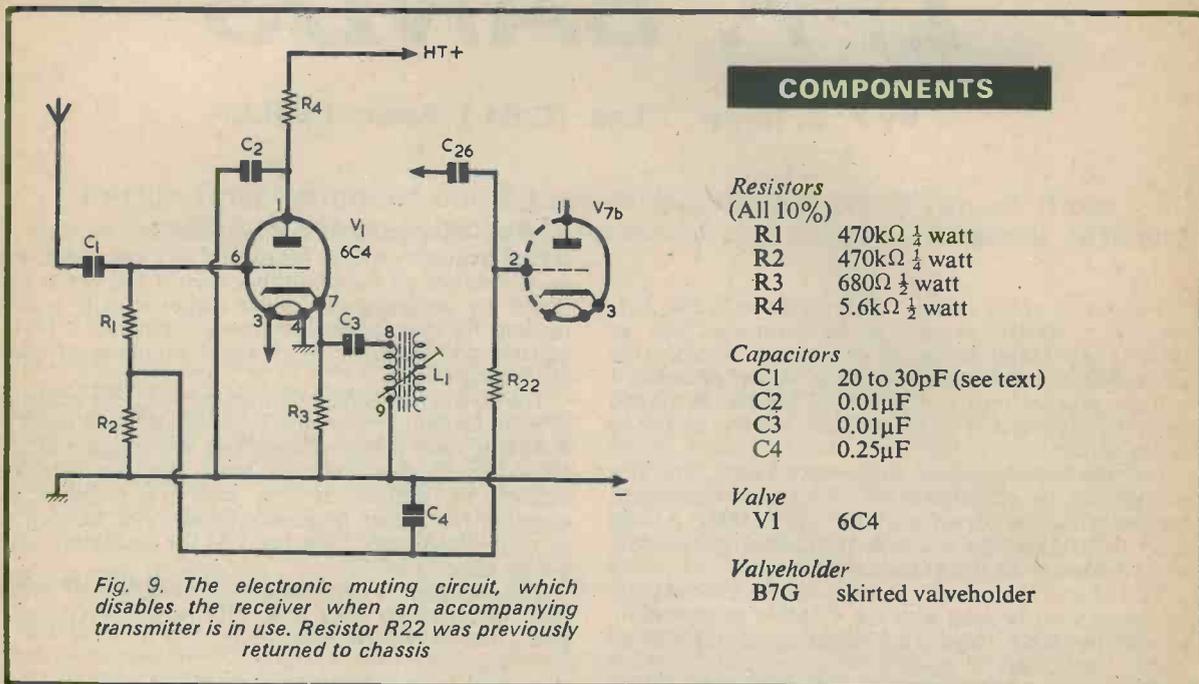Should the receiver be used with a transmitter without the muting stage, the usual care must be taken to avoid a high level of r.f. reaching L1, whose windings may be destroyed. A relay or switch may be needed to short-circuit the primary of L1, unless only low power is run. C1 in Fig. 9 may be 20pF to 30pF, and needs to be of



accomplished automatically. Capacitor C1 is connected to the transmitting aerial circuit. During reception the 6C4 acts as a cathode follower, and signals across R3 are coupled to L1 in the receiver via C3.

During transmission, the large r.f. signal voltage applied to C1 develops a high negative voltage at the valve grid due to grid rectification. This negative voltage cuts off the stage, preventing the high level r.f. from reaching L1. A high negative bias is also applied to the a.f. output stage, cutting this off. The actual bias

high voltage rating. With 75Ω and similar aerial loads, it should be adequate if the working voltage is at least twice the transmitter h.t. supply voltage to the p.a. stage. C1 is positioned outside the chassis immediately adjacent to the aerial socket. Ceramic capacitors rated at 12kV and with values of 22pF or 27pF are listed by Home Radio.

The valve in the electronic muting circuit is fitted in a B7G skirted valveholder, but it does not require a screening can. ■

(Concluded)

## BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two year old. The cost is the cover price stated on the issue, plus 6p postage.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available. Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

# TRANSFORMER RATIO ANALYSER

By S. L. Martin

An inexpensive item of test gear which measures the turns ratios of small a.f. transformers

SADDLED RECENTLY WITH A LARGE BATCH OF SMALL unmarked transistor a.f. amplifier transformers, the writer devised the item of test equipment described here to sort them out in terms of turns ratio. The circuit to be described has its limitations and would not qualify as an item of laboratory equipment. On the other hand it gives reasonably accurate measurements of turns ratio as well as determining the phase relationship between two windings on a transformer. The components needed are standard types and the more experienced constructor may well have all that is required already to hand in his spares box. A 0-50 $\mu$ A meter movement is employed, and this is provided by a multi-testmeter switched to read this range of current.

## BASIC OPERATION


The basic mode of operation is illustrated by the circuit given in Fig. 1. Here, an a.c. supply is applied to the primary of a step-down transformer. Also connected across the supply is a potentiometer, the slider of which connects via an a.c. voltmeter to the upper end of the secondary. The two large dots alongside the upper ends of the primary and secondary indicate similar winding ends. That is to say, the two ends indicated by the dots could both be winding 'starts' or could both be

winding 'finishes'. In consequence the induced alternating voltage at the upper end of the secondary is in phase with the applied alternating voltage at the upper end of the primary.

The potentiometer is adjusted for a null, or zero, reading in the a.c. voltmeter. The voltage tapped off by the potentiometer slider will also be in phase with that at the upper end of the primary so that, when the voltage at the potentiometer slider is equal to that at the upper end of the secondary winding, the a.c. voltmeter gives the null reading. At all other settings of the potentiometer there will be an alternating voltage difference between the potentiometer slider and the upper end of the secondary winding, and this will be indicated by the a.c. voltmeter. As may be seen, the circuit is one step removed from the familiar Wheatstone bridge.

The alternating voltages across the primary and secondary windings are proportional to the turns ratio. If the transformer has a turns ratio of 2:1 the alternating voltage at the upper end of the secondary, with respect to the lower circuit rail, will be half that at the upper end of the primary. The voltage at the slider will similarly be half that at the upper end of the primary when the potentiometer slider is half-way up the track. So, a 2:1 transformer ratio will be indicated, after

Fig. 1. Illustrating the basic mode of operation of the transformer ratio analyser

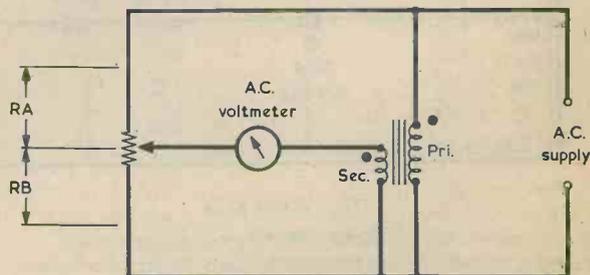

$$\frac{\text{Pri. turns}}{\text{Sec. turns}} = \frac{RA + RB}{RB}$$

adjustment for a null reading in the a.c. voltmeter, by a 2:1 ratio between the total track resistance and the track resistance below the potentiometer slider.

If the transformer has a turns ratio of 4:1, then the null indication will be given when the potentiometer slider is quarter-way up the track. Other turns ratios will have corresponding track resistance ratios in the potentiometer, and the overall situation is indicated by the equation which appears below the circuit in Fig. 1. It is an easy matter to provide the potentiometer with a scale calibrated in terms of turns ratio, whereupon the circuit becomes suitable for measuring this property of an a.f. transformer.

Finally, it should be noted that the circuit will not give a null reading if the secondary of the transformer is connected with opposite phase to that shown in Fig. 1, or if it is connected as a step-up transformer. Also, the potentiometer slider can only approach, but not pass through, a null indication if the transformer has a turns ratio of 1:1.

### WORKING CIRCUIT

A practical working circuit is shown in Fig. 2. Comparing this with Fig. 1, the primary of the transformer being checked connects to terminals B and C, and the secondary to terminals D and E. This method of connection is illustrated in Fig. 3(a). The a.c. supply of Fig. 1 is now the alternating voltage appearing across the  $10\Omega$  resistor, R3, in Fig. 2. Due to the presence of R2, this voltage is approximately one-tenth of the 6.3 volts obtained from transformer T1, which is a standard 6.3 volt heater transformer. Thus, the alternating frequency applied to the transformer being checked is that of the a.c. mains supply, i.e. 50Hz. The voltage across R3 is only 0.63, whereupon there is little risk of damage to a small transistor a.f. transformer.

The a.c. voltmeter incorporates the rectifying and smoothing circuit given by D1 and C1, whilst the meter proper is the 0-50 $\mu$ A movement shown as M1. In practice this is a multimeter switched to read 50 $\mu$ A f.s.d., and connected to the circuit by way of two suitably positioned terminals. The limited capabilities of the circuit do not really warrant the expense of a permanently installed panel-mounting meter. Normally S1, a push-to-close press button, is left in the open condition. This allows R1 to remain in series with the meter, whereupon it limits the current input which can flow when VR1 slider is away from the zero voltage setting. VR1 is initially adjusted to give a rough zero indication, after which S1 is pressed and a final fine setting in VR1 can then be achieved.

To use the device, the transformer being checked is connected to terminals B, C, D and E with on-off switch S2 open. S2 is then closed and VR1 adjusted for a null reading in the meter, remembering that meter indication is a little sluggish due to the presence of C1. If a null indication cannot be obtained, the connections to the transformer are changed to obtain correct phasing or to ensure that it is functioning as a step-down instead of a step-up component. As soon as a rough null indication is obtained in the meter, S1 is pressed and a final null setting obtained in VR1. The transformer turns ratio is then read from a scale fitted to VR1.

The circuit will also check tapped transformer windings, these being connected to terminals B, C and D as shown in Fig. 3(b). The turns ratio found is then the ratio between the turns in the total winding and the turns in the section connected to terminals D and C. This facility is helpful when dealing with components such as driver transformers which may have a centre-tapped winding and an overall 1:1 ratio. The presence of the centre-tap may be found with the circuit of Fig. 3(b), and the overall ratio determined by checking the

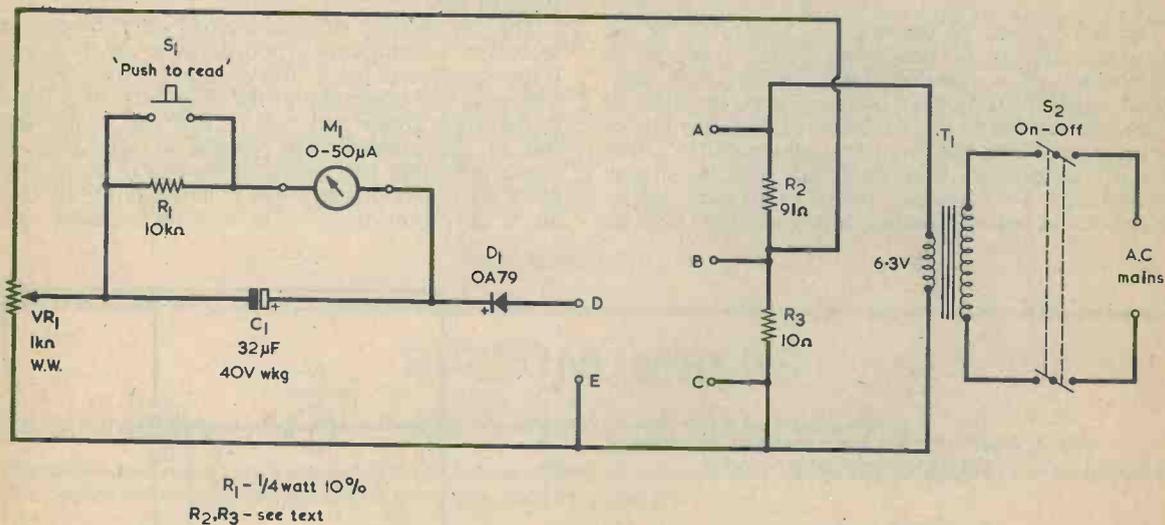


Fig. 2. The practical circuit of the ratio analyser


0-1mA, or similar. This gives an additional protection against possible excess current in the meter.

## COMPONENTS

As mentioned, the components are all standard types. T1 is any 6.3 volt heater transformer having a secondary current rating of 0.5 amp or more. R2 and R3 may have ratings of  $\frac{1}{2}$  watt or more. For precise readings with valve output transformers, R2 should be exactly 9 times the value of R3, but in practice the nearest preferred value of 91 $\Omega$  will be satisfactory. Both R2 and R3 should, preferably, be 2% or 1% in tolerance on value. Incidentally, the combined value of R3 and VR1 in parallel is only marginally lower than the value of R3 on its own.

D1 is specified as an OA79, but most germanium diodes of similar type could be employed in its place. A 0-100 $\mu$ A meter could be used, if desired, for M1, but the null sensitivity will, of course, be somewhat lower. Since D1 becomes nearly non-conductive at forward voltages below about 0.1 volt, the null obtained when checking efficient transformers which give a true null zero may be determined by swinging VR1 slightly on either side of the central null position.

VR1 is wire-wound since components of this type are normally capable of a high level of resolution. An important point here is to ensure that when the slider is at the end-stops there is very little resistance between the slider and the adjacent end-of-track terminal. This is a function of potentiometer mechanical design and the ideal condition is given when there is very nearly zero resistance at the track ends. A few wire-wound potentiometers, particularly in the lower resistance values, have quite high 'end-hop' resistances, and a potentiometer of this type would not enable the higher turns ratios to be indicated. It is for this reason that the potentiometer consists of VR1 connected across R3, instead of using a 10 $\Omega$  potentiometer to carry out the function of both components.

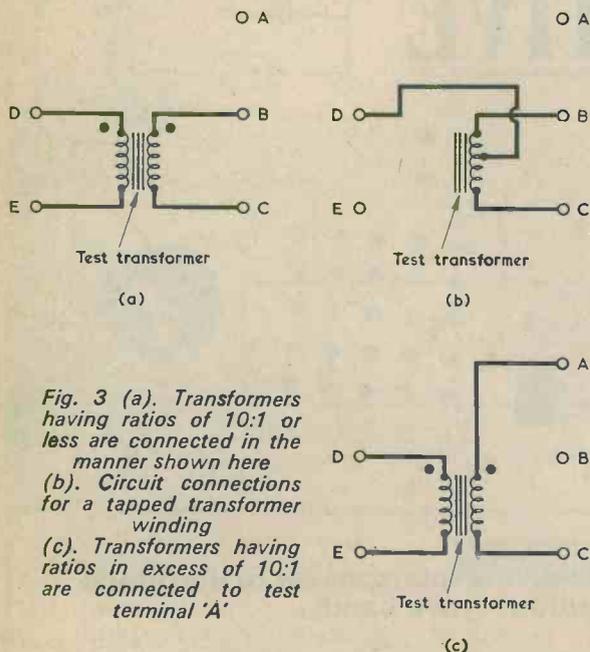

remaining winding against half the centre-tapped winding. During checks, any windings which are not connected to the test terminals are left open-circuit.

In Fig. 1 reference was made to the 'primary' and 'secondary' of the transformer. This was for convenience in explanation and, so far as using the test device is concerned, the 'primary' is the winding having the greater number of turns. A few small transistor transformers may give a balance null reading which is not zero but is a little above zero. This is due to losses in the transformer which result in a small phase shift at 50Hz, and the effect is not important.

Valve speaker transformers having step-down ratios from some 30:1 to 90:1 can also be checked, and they are connected to terminals A, C, D and E, as illustrated in Fig. 3(c). The alternating voltage across terminals A and C is about 10 times that across terminals B and C, and the ratio indicated at the null setting of VR1 is then multiplied by 10. Thus, a ratio of 4:1 on VR1 scale corresponds to a transformer ratio of 40:1. Before checking, the primary of the valve speaker transformer can be identified by an ohmmeter, and it will have much higher resistance than the secondary. It is this high resistance winding which connects to terminals A and C.

When checking any unknown transformer which may have a high turns ratio, initially set the testmeter to read


TABLE

RB ( $\Omega$ )	Turns Ratio
100	10:1
125	8:1
167	6:1
200	5:1
250	4:1
333	3:1
500	2:1
667	1.5:1
833	1.2:1
1,000	1:1

The potentiometer is calibrated by disconnecting the lower end of its track from the rest of the circuit, and then connecting an ohmmeter between the track lower end and the slider. Calibration in terms of turns ratio may then be carried out with the aid of the accompanying Table.

# THREE TRANSISTOR REGENERATIVE RECEIVER

By  
A. P. Roberts

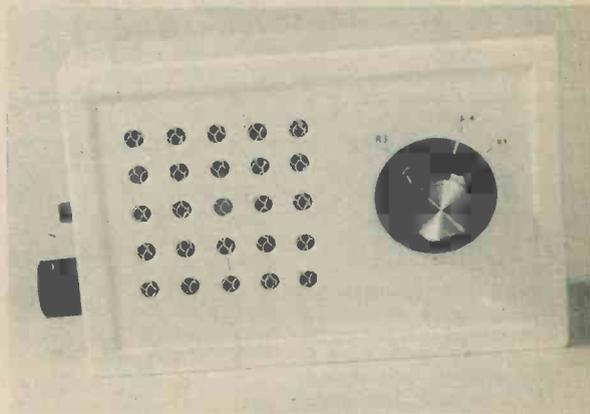

**A self-contained transistor portable giving loudspeaker or earphone reception on the medium wave band.**

**T**HIS IS A SIMPLE PORTABLE 3-TRANSISTOR RECEIVER covering the medium wave band, and providing loudspeaker reception. Due to the simplicity of the circuit the available volume is not great, but the set makes a good bedside receiver. An output socket is provided for a magnetic earphone.

## CLASS A OUTPUT

A Class A output stage is used, and the total current consumption of the receiver is approximately 12mA. This is economically provided by four 1.5 volt cells connected in series to give 6 volts. The set is completely self-contained, having an internal ferrite aerial, and it can be made up in reasonably compact form. The author's receiver was housed in a case measuring approximately 6 by 4 by 2 in.

With the prototype a number of stations can be received at a reasonable volume level, including B.B.C. Radios 1, 3 and 4 during daylight. Additionally, Radio Luxembourg and several other Continental stations can be received after dark.

The circuit diagram of the receiver is shown in Fig. 1. The circuit consists of a single transistor regenerative detector, TR1, feeding a 2-stage audio amplifier incorporating TR2 and TR3.

VC1 is the tuning capacitor and L1 is the tuned winding on the ferrite aerial. L2 is a coupling winding, and it couples the received signals into the low input impedance of TR1 base via the d.c. blocking capacitor, C1. TR1 is biased by R1, and has L3 and VR1 as its collector load for r.f., whilst R2 acts as its a.f. collector load. C2 is an r.f. bypass capacitor.

The way in which this type of circuit detects the signal is quite simple. The transistor is biased so that it is conducting only a low current between its emitter and collector. Negative r.f. half-cycles at the base cause a larger collector current to flow. The gain of the transistor increases with increasing collector current, and so these half-cycles receive a higher degree of amplification.

Positive r.f. half-cycles have the opposite effect, and cause a smaller collector current to flow with, in consequence, a lower degree of amplification. The overall non-linear amplification thus given by the transistor results in detection of the received signal.

The use of controllable regeneration, or positive feedback, increases the level of the input r.f. signal, and also the difference in the amplification which is given to half-cycles of opposite polarity. Detection is therefore more efficient as also is the amplification provided by the transistor.

In Fig. 1, L3 is the regenerative feedback winding, and it couples the amplified r.f. signal at TR1 collector back to its base by way of L2. Potentiometer VR1 controls the level of feedback. If VR1 is set to insert minimum resistance into circuit, L3 on its own forms the r.f. collector load for TR1. There will be a relatively high r.f. current in this winding and a similarly high r.f. signal fed back via L2 to the base. The feedback, under these conditions, will be such as to cause the stage to oscillate. If VR1 is next adjusted to insert an increasing resistance into circuit, there will be a lower r.f. current flowing in L3 and the level of feedback will reduce. At a certain setting of VR1 the feedback will be insufficient to maintain oscillation in TR1, although the feedback

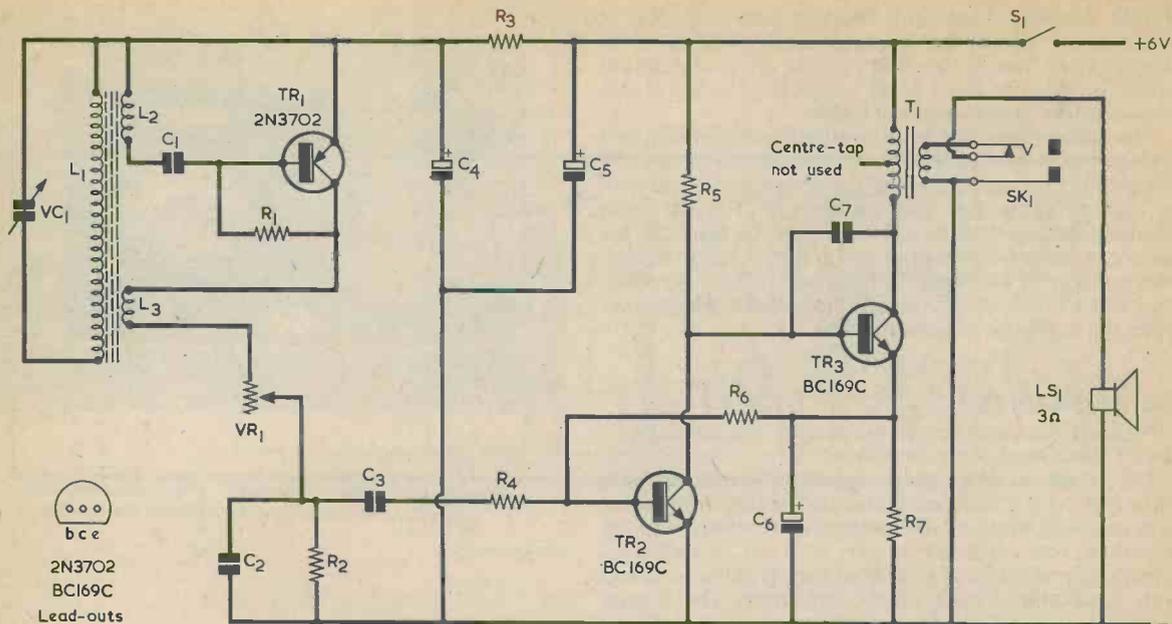


Fig. 1. The circuit of the 3-transistor regenerative receiver

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{4}$  watt 10%)

R1	1.5M $\Omega$ (see text)
R2	5.6k $\Omega$
R3	1k $\Omega$
R4	2.7k $\Omega$
R5	4.7k $\Omega$
R6	150k $\Omega$
R7	82 $\Omega$
VR1	5k $\Omega$ potentiometer, linear

### Capacitors

C1	0.022 $\mu$ F plastic foil
C2	0.015 $\mu$ F plastic foil
C3	0.22 $\mu$ F plastic foil, side wires
C4	100 $\mu$ F electrolytic, 10 V. Wkg.
C5	100 $\mu$ F electrolytic, 10 V. Wkg.
C6	400 $\mu$ F electrolytic, 4 V. Wkg.
C7	1,000pF disc ceramic
VC1	Value to suit ferrite aerial (see text)

### Inductors

L1, 2, 3	Medium wave ferrite aerial (see text)
T1	Output transformer type LT700 (Eagle)

### Transistors

TR1	2N3702
TR2	BC169C
TR3	BC169C

### Switch

S1	Slide switch
----	--------------

### Socket

SK1	3.5mm jack socket with break contact
-----	--------------------------------------

### Speaker

LS1	3 $\Omega$ speaker, 3 in. square
-----	----------------------------------

### Miscellaneous

8 $\Omega$  magnetic earphone with 3.5mm jack plug (if required)  
 Plain Veroboard, 0.15 in. matrix  
 4 cells, 1.5 volt type HP7 or equivalent (Ever Ready)  
 Battery holder (see text)  
 PP3 connector clip for battery holder  
 Case (see text)  
 Speaker mesh material  
 2 knobs

will still boost the signal applied to TR1 base. The feedback reduces further as VR1 inserts yet more resistance into circuit. Normally, VR1 is adjusted such that the feedback is just below the point at which oscillation takes place.

C2 has a low impedance at r.f. and a high impedance at audio frequencies. In consequence it bypasses the r.f. signal at the junction of VR1 and R2 but allows the

appearance of the detected a.f. signal across R2.

The value of bias resistor R1 is a little critical as it has to enable TR1 to have a collector current which is sufficiently low to allow non-linear amplification, and hence detection, to take place, but which is not so low as to give too small an overall amplification. Some transistors of the type specified may function better with a slightly different value in the R1 position. The receiver

should be assembled and checked out with R1 at  $1.5M\Omega$ , as specified. Experimentally-minded constructors can then, if they wish, try the effect of different values in place of the  $1.5M\Omega$  component to see if any improvement in performance results.

The audio stages are quite straightforward, using two high gain silicon transistors in a d.c. coupled circuit. C7 is a stabilizing capacitor which gives negative feedback at higher frequencies and prevents the circuit from breaking into oscillation. Transformer T1 provides the necessary impedance step down to allow a low impedance speaker or earphone to be driven from the output. SK1 has a break contact which disconnects the speaker when the earphone plug is inserted.


## COMPONENTS

Most of the components are readily available, but a few of these need some comment.

The ferrite aerial can be any ready-made medium wave type with a 5 in. ferrite rod and having a transistor base coupling winding. The component employed in the prototype was obtained as part of a set of inductors intended for a medium wave superhet. It came complete with a suitable 2-gang tuning capacitor. The 2-gang capacitor is used in the present receiver, connection being made to the aerial section of the capacitor only. The author tried other ready-made medium wave ferrite aerials with complete success, these including the Denco ferrite aerial type MW/5FR. If the Denco ferrite aerial is employed, VC1 should have a value of 208pF. A single gang 208pF capacitor (Jackson type O1), or the 208pF section of a  $208 + 176pF$  2-gang capacitor can be used. In some cases, and particularly if a 2-gang component is employed, the tuning capacitor may be fitted with an integral trimmer. This trimmer is initially left at about half maximum capacitance.

It is important to ensure that the lead-outs of the aerial are connected properly, and Fig. 2 shows the correct connections. It also gives details of the additional winding, L3, which is made from a length of thin p.v.c. insulated single core wire. L3 is positioned away from L1 and L2, as illustrated.

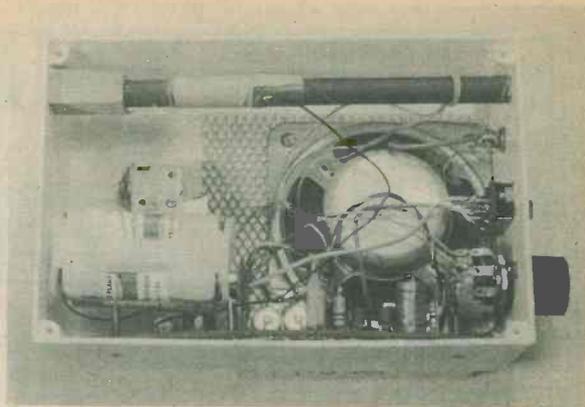Most ready-made aerials have a base coupling winding consisting of about four or five turns of wire. Ideally, this receiver should have a coupling winding with about ten turns. It is an easy matter to use one of the lead-outs of the coil (the one furthest from the tuned winding) to add another five or six turns to the winding, the extra turns being taped to the coil former. A piece of thin



*The layout inside the case. There is adequate space for the components without crowding*

insulated wire is then used to extend the lead-out back to its original length.

It is by no means essential to alter the ferrite aerial in this way, but the modification will give a worth-while increase in sensitivity.

The speaker in the prototype was a 3 in. square type with an impedance of  $3\Omega$ . Smaller speakers of the same impedance could be used, but these will probably have a lower efficiency.

The four 1.5 volt cells are fitted in a battery holder of the type illustrated in the photograph of the interior. This is an Eagle type BH4N or, alternatively, the Bulgin type 2/CB/4U7 can be used.


The author's receiver was housed in a plastic case measuring 6 by 4 by 2 in. Any non-metallic case of similar dimensions may be used, or could be constructed from plywood, but first make sure that it will be large enough to take the particular speaker and variable capacitor employed, in company with the Veroboard assembly and the other components. The space needed by the Veroboard assembly will be apparent from Fig. 3 and the photograph of the case interior.

## CONSTRUCTION

Construction starts with the preparation of the main component panel. This is a piece of plain Veroboard (i.e. without copper strips) having a matrix of 0.15 in. and 33 by 10 holes. This takes all the small components, and a component layout and wiring diagram is given in Fig. 3.

First drill out the two 6BA clear mounting holes in the positions shown. Next drill out two  $\frac{3}{16}$  in. holes to take the mounting lugs of T1. In Fig. 3 these holes appear in the first and fifth row of holes from the top. If the transformer does not fit comfortably into holes with this spacing, drill out the lower hole in the sixth row of holes from the top.

The components are then mounted in the positions indicated in the diagram, which shows the board from the component side. The underside wiring is illustrated in broken line. In many instances, the component lead-

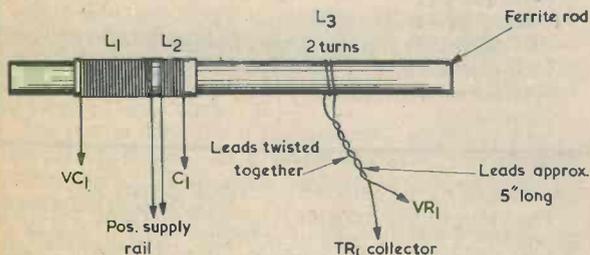

*Fig. 2. Illustrating how the ferrite rod aerial windings are connected into circuit*

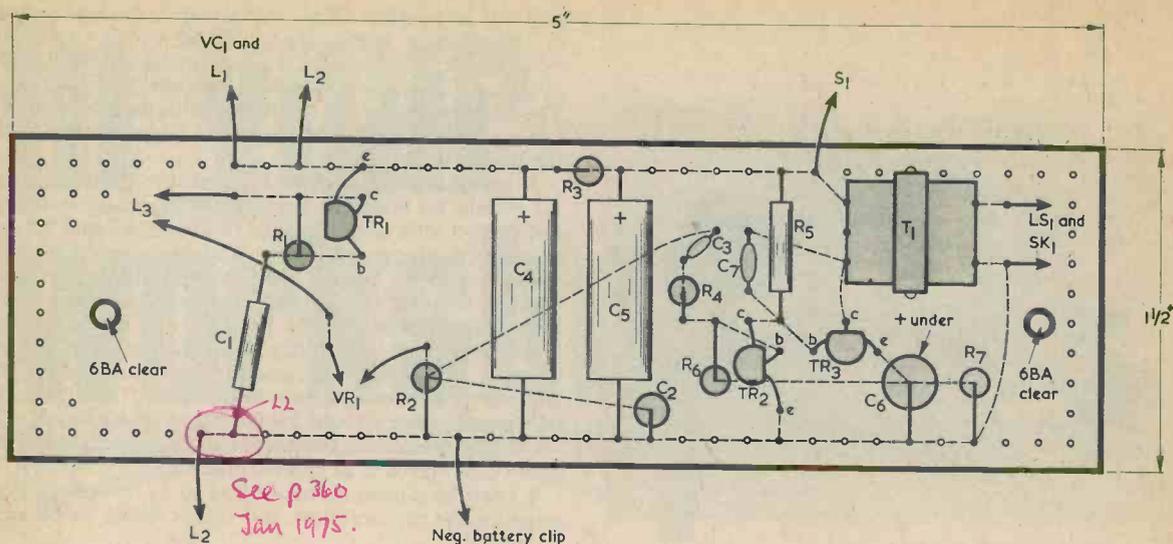


Fig. 3. The smaller components are assembled on a plain Veroboard panel, shown here as viewed from the component side

outs will be long enough to reach their connection points. Additional lengths of wire carry the positive and negative supply connections, and it will be found helpful to carry out this part of the wiring first. Where adjacent leads pass very close to one another, one of these is insulated with sleeving. When connecting L3 to the board it should be borne in mind that its connections may have to be transposed during the setting up procedure.

The finished panel is later mounted on the inside bottom of the case by means of two 1 in. 6BA countersunk screws, with suitable spacing washers between the underside of the board and the inside surface of the case. T1 is near the left hand end of the case, as seen from the front. The board may be used as a template to mark out the positions of the two countersunk holes required in the case. The panel will be mounted when the connections between it and the other components have been made.

The general layout inside the case can be seen from the photographs. With the author's receiver, a matrix of 25 1/4 in. diameter holes, with 1/2 in. spacing, was drilled on the left front side of the case, after which a square of speaker mesh material was glued behind this. The speaker was, in turn, glued to the mesh. Alternatively, the speaker could be mounted to the front panel by four bolts and nuts, with the mesh sandwiched in between. The ferrite aerial is mounted at the top of the case, as far away from metal objects such as the speaker, VC1 and the battery, as possible. A piece of 3/8 in. square wood was glued to one end of the rod to give a total length equal to the inside width of the case, and both were then glued in position in the case.

VC1 is mounted on the front panel next to the speaker, whilst VR1, S1 and SK1 are mounted on the left

hand side of the case, as seen from the front. VR1 is at the bottom, S1 in the centre and SK1 at the top. Ensure that clearance exists between VR1 and the Veroboard panel. VC1 will probably have a construction which allows it to be mounted by three 4BA bolts passing through tapped holes in its front plate. A piece of paper can be used as a template for marking out these holes on the front panel by initially pressing it against the capacitor front plate. The 4BA bolts used to secure the capacitor must be short. If their ends pass beyond the inside surface of the capacitor front plate they can damage the fixed or moving vanes.


When all these parts have been mounted, the remaining wiring can be completed. Most of the wiring is illustrated in Figs. 2 and 3, and the few connections which are not shown in the circuit diagram. VR1 is wired so that the resistance it inserts into circuit decreases as it is turned clockwise. (When the photographs were taken it was wired to insert increasing resistance.) All the interconnecting leads must be insulated.

The battery holder fits behind VC1 and can be held in position by a piece of foam rubber or plastic glued to the inside of the cabinet back.
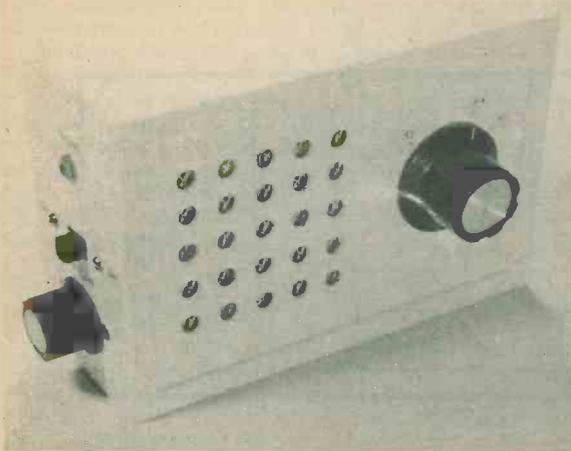
### SETTING UP AND USE

Before switching on the completed receiver, set L1 and L2 towards one end of the ferrite rod, and L3 at about the centre. VR1 should be adjusted to insert maximum resistance into circuit.

Upon switching on the set, a rushing sound should be heard from the speaker. Adjusting VC1 will probably not cause any stations to be received until VR1 is advanced clockwise. If VR1 should be advanced too far the set will break into oscillation, and proper reception



*This view shows the regeneration control, the on-off switch and the earphone socket, all of which are mounted on the left side of the case*

will not be possible. The most sensitive setting for VR1 is immediately below the point at which oscillation occurs, and not when it is fully advanced. For all but the strongest signals VR1 will need very careful adjustment. The best setting for VR1 will vary with the setting of the tuning control, and it will need readjustment each time the tuning is altered.

If oscillation cannot be obtained, the connections to L3 should be reversed. Should the frequency coverage not extend fully to the ends of the band, L1 and L2 can be moved along the ferrite rod to alter the range covered and so correct this. If VC1 has an integral trimmer this can be adjusted to control coverage at the high frequency end of the band. In the unlikely event that there is any tendency towards instability at the extreme high frequency end of the range when the trimmer is set for minimum capacitance, then the trimmer capacitance should be increased to avoid this. If VC1 does not have a trimmer, a 10pF capacitor may be connected across it in this eventuality.

L3 can be moved along the rod so as to find the best position for regeneration, but this is likely to be very uncritical.

As a finishing touch, legends from 'Panel Signs' Set No. 4 can be added at VR1, S1 and SK1, together with suitable indications of station positions behind the control knob of VC1. ■

## NEXT MONTH'S ATTRACTIVE ISSUE

### Features

#### PULSE COUNTING F. M. TUNER

By employing the pulse counting method of discrimination, this f.m. tuner performs as a superhet receiver having an i.f. amplifier which requires no tuned circuits at all. The tuner may be powered by a 9 volt power supply unit.

The following month's concluding article will give details of construction and of setting up.

#### OSCILLOSCOPE AMPLITUDE CALIBRATOR

This unit provides a.c. or d.c. voltages from 10mV to 10 volts for calibration or test purposes, and consists of a multivibrator followed by an accurate attenuator.

\* \* \*

**PLUS**


**MANY OTHER ARTICLES**

ON SALE 2nd DECEMBER PRICE 25p

**RADIO & ELECTRONICS  
CONSTRUCTOR**

Copies may also be obtained direct from the Publishers, 30p including postage. Published by Data Publications Ltd., 57 Maida Vale, London W9 1SN.

# In your workshop

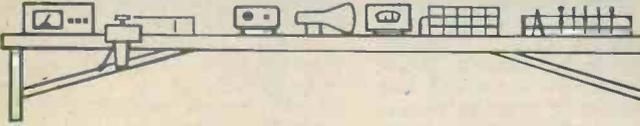

This month Smithy the Serviceman ostensibly sets out to explain to Dick how simple a matter electronics really is. But he ends by having his assistant far more confused than he had been at the start.

DICK SCRATCHED HIS HEAD, THEN turned back the volume control knob on the medium and long wave transistor radio on his bench.

The radio reproduced the music from the local station at reasonable quality level. Once more Dick slowly advanced the gain control. The sound from the receiver increased in amplitude until it filled the Workshop. The music suddenly reached a peak, the receiver became momentarily silent, and then it commenced to play once more. There was another peak in the music, followed by a further momentary silence from the receiver.

The irritated clattering of a soldering iron on its rest became audible from Smithy's side of the Workshop.

Dick turned down the volume and scowled at the receiver. Then he turned up the volume again.

## LOW BATTERY

"Ye gods," yelled out Smithy irately. "Am I going to be subjected to that racket all morning?"

"I'm *trying*," retorted Dick in a pained tone, "to find out what's wrong with this set. Every time there's a loud sound from the speaker it cuts out."

"You don't need to tell me that," snorted Smithy. "I've been hearing nothing else but that set cutting out on loud sounds for the last quarter of an hour. For goodness' sake put a new battery in it and get on with some useful work."

"The very first thing I did was to check battery voltage."

Smithy's reply was short and to the point.

"Put in a new battery."

Shrugging his shoulders, Dick switched off the receiver and walked

over to the spares cupboard. Returning he peeled off the cardboard which covered the battery terminals, removed the existing battery and fitted the new one to the set. He switched on and listened to the receiver.

It gave a perfect performance at all volume levels.

Perplexed, Dick stared at the old battery then applied the test prods of his meter to its connectors. The meter registered 8.5 volts.

"How the heck," he called out, "did you know that this set wanted a new battery, Smithy? Why, you haven't even looked at it."

"I didn't need to," replied the Serviceman over his shoulder. "It was sufficient just to hear it. I was almost 100% certain that the battery was causing the trouble."

"But it couldn't have been," persisted Dick. "It's only half a volt below its proper voltage of 9 volts."

Smithy sighed, rose from his stool and walked over to his assistant.

"Show me."

Obligingly, Dick connected his testmeter to the battery and indicated the reading of 8.5 volts.

"Now connect it to the set and measure its voltage whilst the set is playing."

Dick removed the new battery, reconnected the old one and clipped on the testmeter leads. He switched on the receiver. The battery voltage at once dropped to less than 8 volts. Dick turned the volume up, whereupon the meter needle danced in sympathy with the level of the reproduced music. The music rose to a crescendo, the meter reading dropped to 5 volts, and the receiver became silent for a short period until the battery voltage rose and it resumed working. Hastily, Dick switched the set off.

"There you are," pronounced Smithy. "That battery had developed a high internal resistance. The Class B output stage of the set draws increased current as the volume level goes up, and loud sounds were causing so much current to be drawn that there wasn't enough battery voltage to keep the oscillator running. So the set ceased to work for a very short period after the start of a loud sound until the voltage on its supply rails increased to a level which allowed the oscillator to come on again." (Fig. 1).

Ruefully, Dick took out the faulty battery and put back the new one.

"Stap me," he remarked forlornly. "I certainly made a mess of this job. I remember now that I measured the voltage of the old battery with the set switched off."

"You should never do that," advised Smithy sternly. "Always measure battery voltage on load."

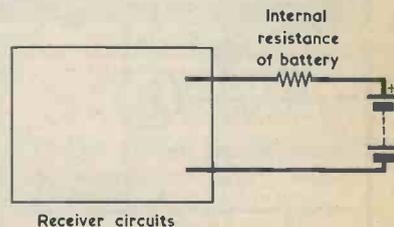


Fig. 1. The internal resistance of a battery may be represented as a physical resistor in series with it. In the instance shown here, the voltage applied to the receiver circuits drops as the receiver current increases

"There are times," stated Dick desolately, "when I think I'm not cut out for this servicing lark. That's the second silly mistake I've made this morning."

"Go on," said Smyth, intrigued. "What else have you done?"

"I wasted nearly half an hour with another set replacing a transistor base bias resistor that I thought had gone low in value. After I'd put the new one in I found it showed the same low resistance as the old one did."

"How was the resistor connected?"

"Between the collector and base of the transistor." (Fig. 2(a)).

"I can guess what happened here," commented Smyth. "You connected the testmeter so that it passed forward current through the base-collector junction of the transistor." (Fig. 2(b)).

"That's what I must have done," agreed Dick dejectedly. "Anyway, I next checked the new resistor with the testmeter leads the other way round and it showed the correct resistance. If I'd thought of doing that with the first one I needn't have gone to the bother of changing it." (Fig. 2(c)).

#### METER POLARITY.

"Well, you know now," pronounced Smyth heavily, "As a matter of principle, whenever you're checking the value of a resistor which is connected in a transistor circuit it's often a good plan to apply the meter leads one way round and then the other way round. There are so many effective diodes given in transistor circuits, due to base-emitter and base-collector junctions, that it's quite easy to obtain a low resistance reading by mistake. Another thing to remember when using a testmeter switched to an ohms range is that the positive test lead in most cases carries the negative voltage from the testmeter battery whilst the negative test lead carries the positive voltage.

That's because nearly all testmeter resistance reading circuits rely on an internal series battery in the meter. This is a useful thing to remember when checking electrolytics for leakage and things like that."

"I tell you, Smyth," said Dick morosely. "This electronics business is really getting too much for me. This positive is negative and negative is positive thing is just the final sting in the tail so far as I'm concerned."

"Do you mean," queried the startled Serviceman, "that you're actually thinking of giving up servicing? Of leaving the Workshop and going for another job?"

"Well, yes," confessed Dick. "Something in the open air for a change. Like on the milk round, for instance."

"If you're going to deliver milk you've got to get up . . ." started Smyth, then checked himself. Dick's passing reference to a "sting" had caused memories of a recent cinema visit to suddenly flood his mind. He abruptly turned his head away so that his assistant could not see the expression of almost Stygian cunning that was now emblazoned across his face.

"Hey, what's up with you?" asked Dick. "What are you looking away like that for?"

With an effort, Smyth composed his features, then faced his assistant.

"It's nothing," he stated bravely.

"Just a tic I'm afflicted with."

"Humph," grunted Dick suspiciously. "I thought it was only cattle that had ticks."

"I didn't mean that sort of tick," grated Smyth. "Let's get back to this electronics business which, you say, is getting too much for you."

"So it is, too," repeated Dick. "I reckon I'm going to find myself a job where things are a lot simpler."

"Now I'm certain you don't mean that," commented Smyth reprovingly. "Tell you what, let's take a bit of time

off so that I can show you how simple, basically, electronics is."

He walked over to the spares cupboard, then returned with a small mains transformer.

"Here we are," he said comfortingly. "This is a nice simple mains transformer with a 240 volt primary which has a 220 volt tap in it. We shan't worry about the secondary windings. Now, take up your soldering iron, connect a bit of 2-core flex to the zero and 240 volt tags, then connect the other end of the flex to the mains. Okay?"

"Fair enough," said Dick reluctantly. "But I don't quite see what this is leading up to."

Dick quickly wired up the transformer, then looked up at Smyth enquiringly. (Fig. 3(a)).

"Right," said that worthy. "Set up your testmeter to a high a.c. volts range, switch on the mains to that transformer and measure the voltage across the primary. As I said just now, we won't worry about the transformer secondaries."

"I'm switching on the mains now," announced Dick, "and I'll see what voltage we've got between the zero and 240 volt tags on the primary. Here we are, it's spot on at 240 volts." (Fig. 3(b).)

"Good. Now check the voltage between the zero volt point and the 220 volt tap."

"This is just a waste of time," grumbled Dick. "It's bound to be 220 volts. And so it is!" (Fig. 3(c).)

"Fair enough," continued Smyth. "Next check the voltage between the 240 and the 220 volt taps."

"Blimey, Smyth," complained Dick. "This has just got to be 20 volts. And - let's see now - that's exactly what it is." (Fig. 3(d).)

"Very good," commended Smyth. "Now did you find that at all hard to understand?"

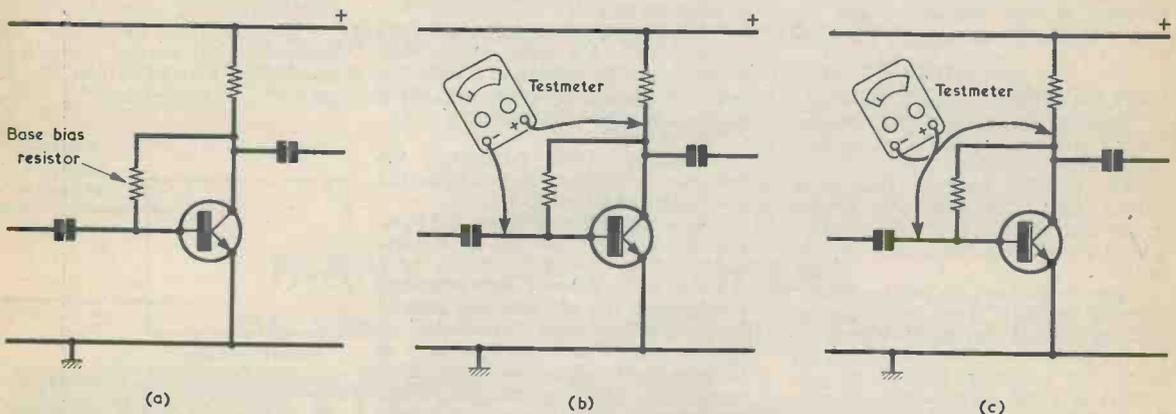


Fig. 2(a). A typical amplifier stage with a base bias resistor between collector and base. An n.p.n. transistor is assumed  
 (b). Applying a testmeter switched to an ohms range to the bias resistor can cause the base-collector junction of the transistor to be forward biased. The meter then gives a false low resistance reading  
 (c). If the testmeter leads are transposed the base-collector junction is reverse biased and a reasonably accurate resistance measurement can be made

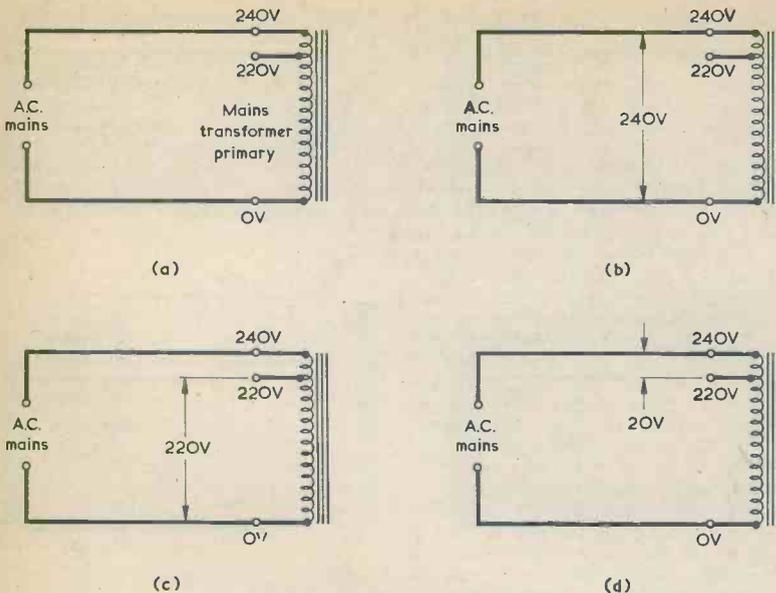


Fig. 3(a). Applying the a.c. mains to the primary of a standard 240 volt transformer having a tap at 220 volts. No connections are made to the secondary or secondaries  
 (b). The applied voltage is 240 volts  
 (c). As is to be expected, a voltage of 220 volts is given at the tap  
 (d). A voltage of 20 volts appears between the 220 and 240 volt points

"It was dead easy," replied Dick scornfully. "We just had what was, in effect, a 240 volt autotransformer with a tap at 220 volts."

"And could we assume," queried Smithy, "that the current in the 240 to 220 volt part of the transformer winding was flowing in the same direction as the current in the 220 to zero volt section?"

"Of course we could assume that. It must be."

"Excellent," said Smithy, rubbing his hands together. "Switch off the mains and remove the lead from the 240 volt point and connect it to the 220 volt tap."

Dick picked up his soldering iron and carried out the Serviceman's instructions. (Fig. 4(a).)

"All finished, lad?" asked Smithy heartily. "That's fine. Will you now measure the a.c. voltage between the zero volt point and the 220 volt tap?"

"Dear, oh dear," muttered Dick rebelliously. "Talk about wasting time. Well, the voltage is 240 volts, which is what you'd expect it to be." (Fig. 4(b).)

"Good," commented Smithy. "And now the voltage between the zero and 240 volt points."

Dick carried out the voltage test. (Fig. 4(c).)

"It's just above 260 volts," he announced. "It's bound to be higher than the mains voltage at the 220 volt tap because the transformer is now

acting as a step-up autotransformer."

"Good, good," purred Smithy. "Could you next check the voltage between the 220 volt tap and the 240 volt point?"

"Corluvaduk," said the mutinous Dick. "I've done some daft things in my time but this is plain ridiculous. Anyway, the voltage is round about 22 volts." (Fig. 4(d).)

"Excellent," said Smithy. "It's slightly more than the 20 volts we had previously because we're applying the mains voltage to a lower tap in the winding."

#### WINDING CURRENTS

"What," asked Dick, "comes next?"

"We start to think," replied Smithy, "about current in the transformer as it's now connected. Would you say that the current induced in the section of the winding between the 240 volt point and the 220 volt tap is flowing in the same direction as the current in the 220 volt to zero volt section?"

"Oh, definitely," stated Dick emphatically. "We've got the same voltage polarities that we had in the previous case, so the current in the top part must be flowing in the same direction as the current in the lower section. In terms of voltage this means that during half-cycles when the 220 volt tap is positive the 240 volt point is positive also, but more so because of the autotransformer step-up effect."

## Your Local Supplier

LONDON

### THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,  
LONDON, W2 1NP  
Tel: 01-723 4185/2926

## ST. HELEN'S RADIO

Hi-Fi Equipment  
Tape Recorders  
Radio Receivers  
Television

SPECIALISTS IN RADIO  
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS  
LONDON, W.10  
Tel: 01-969 3657

HAMPSHIRE

## BOURNEMOUTH

LARGEST HI-FI AND  
RADIO COMPONENT  
STORE IN THE SOUTH

FORRESTERS NATIONAL  
RADIO SUPPLIES LTD.

70-72 Holdenhurst Road  
Bournemouth  
Telephone 25232

SURREY

## WITWORTH TRANSFORMERS

TV Line out-put transformers

Manufacturers of the largest range in the country. All makes supplied.

Modern

BAIRD, BUSH, GEC, PHILIPS  
Replacement types ex-stock.

For "By-return" service, contact  
London 01-948 3702

Tidmah Mail Order Ltd., Dept. R.C.

236 Sandycombe Road,  
Richmond, Surrey TW9 2EQ

Callers welcome.

## Your Local Supplier

SUSSEX

### E. JEFFRIES

For your new television set  
tape recorder, transistor radio  
and hi-fi equipment

PHILIPS, ULTRA, INVICTA  
DANSETTE, MASTERADIO, PERDIO,  
MARCONI, PHILCO FIDELITY

6A Albert Parade  
Victoria Drive,  
EASTBOURNE SUSSEX

EIRE

### PEATS for PARTS


ELECTRONIC COMPONENTS  
RADIO & TELEVISION

For the convenience of Irish  
enthusiasts we supply  
Radio & Electronics  
Constructor  
Data Books and  
Panel Signs Transfers  
Also a postal service

Wm. B. PEAT & Co. Ltd.  
28 PARNELL STREET  
DUBLIN 1

### H.A.C. SHORT-WAVE KITS

WORLD-WIDE RECEPTION

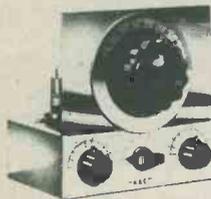

Famous for over 35 years for Short-Wave  
Equipment of quality, "H.A.C." were the  
Original suppliers of Short-Wave Receiver  
Kits for the amateur constructor. Over  
10,000 satisfied customers—including  
Technical Colleges, Hospitals, Public  
Schools, R.A.F., Army, Hams, etc.

1974 "DX" RECEIVER  
Complete kit—price £4.30 (incl. p. & p.  
& V.A.T.)

Customer writes: "Australia, India and  
America at loud volume."—"I have now  
heard over 300 stations including many  
amateurs. I have received 32 Q.S.L. ver-  
ified reports—from all continents. An am-  
azing one-valver.

This kit contains all genuine short-wave  
components, drilled chassis, valve, ac-  
cessories and full instructions. Ready to  
assemble, and of course, as all our  
products—fully guaranteed. Full range of  
other S.W. kits, including the famous  
model "K plus" (illustrated above). All  
orders despatched by return. Stamped  
envelope for free catalogue of kits & com-  
ponents. Test Report available.

"H.A.C." SHORT-WAVE PRODUCTS  
(Dept. RC.) P.O. Box 16  
East Grinstead, Sussex RH19 3SN

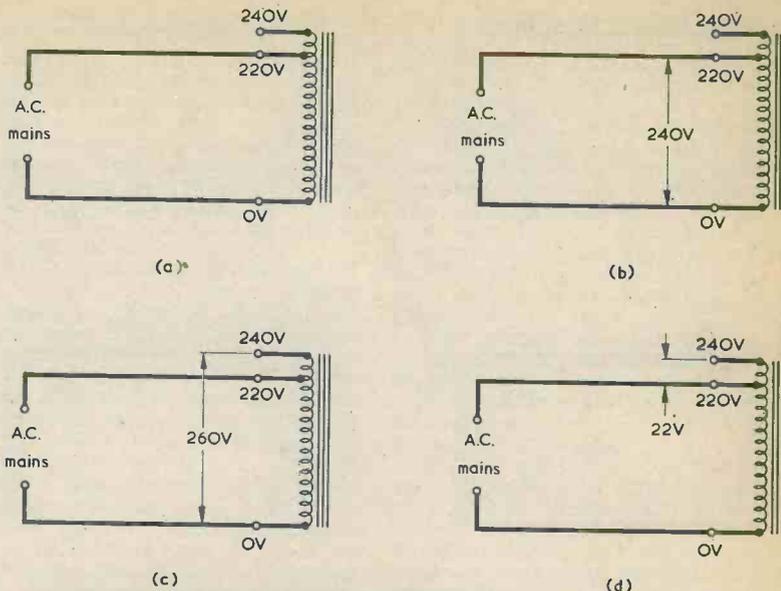


Fig. 4(a). This time the a.c. mains is applied to the zero and 220 volt points  
(b). Once again the input voltage is 240 volts  
(c). Due to step-up effect, the voltage at the 240 volt point is in excess of 240 volts  
(d). A slightly increased voltage is also given between the 220 and 240 volt points

"Very good," said Smithy silkily. "Now switch the mains off from that transformer and let's draw its symbol on some paper. Have you got a piece of paper anywhere?"

Dick reached forward and produced a grubby note-pad from the back of his bench. Smithy fastidiously tore off several sheets until he encountered one which was reasonably free of the patina of sticky grime which, mysteriously, clung to all of the more permanent items on his assistant's bench.

"I will now," announced Smithy, as he took out his ball-point pen, "draw out the circuit of our mains transformer primary. I'll use larger loops than usual for the winding symbol so that I can add little arrows to indicate current flow. And I'll also add a resistor across the 220 and 240 volt points to act as a load. If there wasn't a load here there wouldn't, in practice, be any current in this part of the winding. All right?" (Fig. 5(a).)

"Sure."

"Will you," continued Smithy, "be happy if I refer to 'conventional current', which is assumed to flow from positive to negative?"

"Suits me," replied Dick carelessly.

"Right," said Smithy briskly. "Then I'll start off with the mains half-cycle you referred to just now where the 220 volt tap is positive and where the zero volt point is, consequently, negative. Our conventional current flows from positive to negative down the winding, so I'll add some arrows to show this." (Fig. 5(b).)

"That seems all right to me," com-

mented Dick. "Now add the arrows to the top part of the winding."

"In the same direction?"

"In the same direction."

Carefully, Smithy added the arrows. (Fig. 5(c).)

"There we are," he pronounced. "Now what could you have simpler than that?"

With a gesture of finality, Smithy put the cap on his pen and returned it to his pocket. Dick gazed at the circuit on his note-pad.

"It could be I was wrong about this electronics scene after all," he commented after a moment's thought. "Perhaps I was letting myself get put down too much just because I flumped a few simple faults."

His countenance brightened.

"I think," he continued, "I'll stay on in the servicing game after all."

Smithy looked at him amiably.

"I'm glad to hear it," he stated warmly. "I was certain you'd realise that things aren't as difficult as you've been making out."

The Serviceman walked over to his bench, leaving his assistant gazing raptly at the diagram on his note-pad.

#### A MATTER OF POLARITY

The Serviceman waited a little, then glanced round. His assistant was still engrossed with the diagram.

The time, Smithy decided, was just right. He cleared his throat.

"Ahem."

Dick continued to look at the diagram.

RADIO & ELECTRONICS CONSTRUCTOR

"Ahem," said Smithy, in a louder tone.

Surprised, Dick turned round.

"What did you say?"

"I said 'ahem'."

"What on earth did you say that for? I've never heard you say 'ahem' before."

"People say 'ahem,'" explained Smithy tetchily, "when they want to

catch other people's attention. I was trying to catch your attention."

"Well, I don't dig this 'ahem' bit. You're really *weird* this morning, Smithy. First of all, you've been all kind and considerate towards me, and now you've started saying 'ahem'."

"For the love of Pete," exploded Smithy furiously, "just forget I darned well said 'ahem'. All I want to do is flaming well say something to you, you steaming great hairy-nostrilled nit."

"Ah now," said Dick in a relieved tone of voice, "that's more like it. I was getting quite worried about you. What did you want to talk about?"

"That transformer we've just been discussing," replied Smithy, forcing himself into a calmer state. "I've just remembered that we haven't *quite* finished our examination of it."

"Haven't we?"

"There's one final thing outstanding," stated Smithy. "We forgot to look at the current which flows in the load resistor connected across the top part of the transformer winding."

"Fair enough," said Dick equably. "Let's press on and do that right now."

Smithy walked back to Dick's bench and pulled out his pen once more.

"When we left this transformer," he said, "it was receiving a half-cycle from the mains which caused the 220 volt tap to be positive. We then added the arrows which indicate the flow of conventional current."

"Agreed."

"So let's next look at the top part of the winding on its own."

Smithy pulled Dick's pad towards him and drew out a further diagram. (Fig. 6(a).)

"We now," he continued, "have the top winding feeding conventional current into the load resistor. We already know the current direction in the winding and this current obviously flows through the resistor. In consequence, we can add a further arrow alongside the resistor to indicate the current direction inside it."

Smithy added the arrow. (Fig. 6(b).)


"This seems reasonable enough," commented Dick assuredly. "The conventional current follows the same direction through the resistor as it did in the transformer winding, and so it goes from the bottom of the resistor up to the top."

"As you say," concurred Smithy gently. "Now, conventional current flows from positive to negative. The result, so far as the resistor is concerned, is that the voltage from the transformer winding is such that the bottom of the resistor is positive and the top of the resistor is negative."


Smithy added a positive and a negative sign to his sketch. (Fig. 6(c).) He glanced expectantly at his assistant.

Dick looked worried.

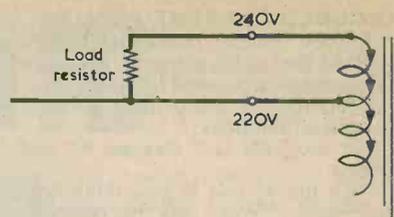
"Just a minute," he said unhappily. "Let's get this straight. We're examining the transformer during the half-cycle when the 220 volt tap is positive. But what we've now found out is that



(a)

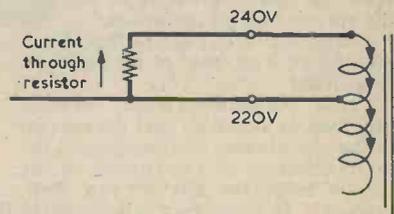

(b)

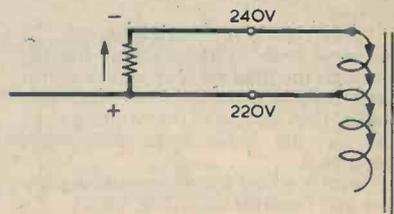

(c)

Fig. 6(a). The situation at the upper section of the transformer winding of Fig. 5(c) is shown in detail here

(b). The direction of the current in the load resistor (c). the consequent polarity of the voltage across the resistor

this causes the 240 volt point to go *negative* of the 220 volt tap."

His brow creased in anguish.


"But that *can't* be true," he wailed. "We know that the 240 volt point goes *positive* of the 220 volt tap. Blimey; we've just *measured* the voltages and we've found that the 240 volt point has a higher voltage than the 220 volt tap, which means that when the 220 volt tap goes positive the 240 volt point goes more positive. And yet when you look at the circuit in basic form this tells us that the 240 volt point goes *negative* of the 220 volt tap!"

He glowered at the diagram, then gave a gesture of utter despair.


"That's it," he remarked with certitude. "Milk round, here I come!"

"Come, come," remonstrated Smithy. "You mustn't be too hasty."

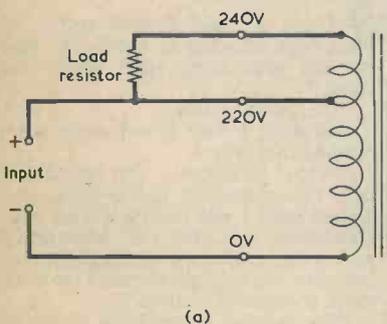
"Too hasty? Who's being too hasty when he's leaving a job where, before your very eyes, positive becomes negative and negative becomes positive? From now on, all I'm going to worry about is how to keep the gold tops separate from the silver tops."



(a)

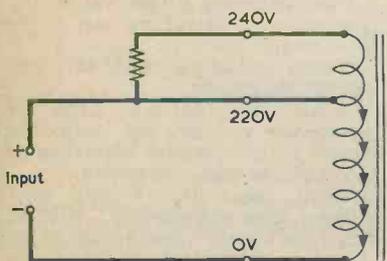

(b)

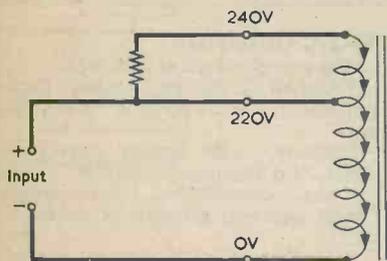

(c)

Fig. 5(a). The circuit situation which exists on half-cycles when the upper input terminal is positive

(b). The arrows indicate the direction of current flow in the lower section of the winding

(c). Current in the upper section of the winding if it is assumed that this flows in the same direction. In practice a load resistance is required across the upper section to allow the current to flow

## INDUCED CURRENT

Smithy glanced down at the anguished face of his assistant. A tremor of compassion touched his heart.

"Perhaps," he murmured, "I should get you off this hook."

He took the last diagram he had drawn.

"It's not as bad as you think," he continued. "What has happened is that we made an error in the steps which led to this conclusion. Let me draw the last diagram again and put the correct current arrows in."


Smithy scribbled out a further sketch and placed it in front of his assistant. (Fig. 7(a).)

"Now, the error we made," he went on, "was in assuming that the current in the top winding section flows in the same direction as the current in the section below the 220 volt tap. Well, it doesn't. In actual fact, it flows in the opposite direction, as I've shown by the arrows in this new diagram."

"Ye gods," groaned Dick. "Now he's changing the direction of the current."

"And rightly so," stated Smithy. "If we now look at the current flowing through the load resistor we see that it goes from top to bottom. And that means that the top of the winding is, so far as the resistor is concerned, positive."

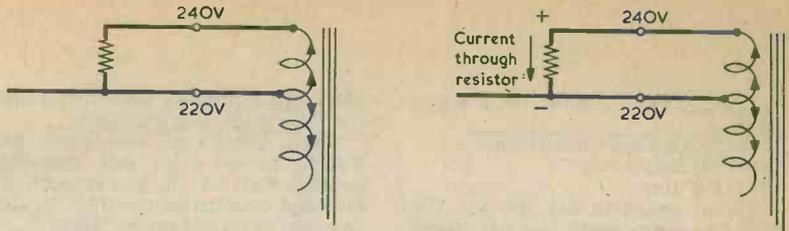Smithy added the arrow and a positive and negative sign. (Fig. 7(b).)



(a) Fig. 7(a). Fig. 6(a) re-drawn, with the current arrows pointing upwards  
(b). The current through the load resistor and the voltage polarity is then as shown here

"Well," remarked Dick doubtfully. "That does at least tie in with the observed facts about the winding voltages. When the 220 volt tap goes positive, the 240 volt point goes more positive."

He examined the sketch again.

"But this means," he went on, "that the current induced in the winding between the 220 and 240 volt points flows in the opposite direction to that which flows in the 220 to zero volt section. Can that be true, Smithy?"

"It is," confirmed Smithy. "In fact, the current has to flow in the opposite direction if only to satisfy the known facts about voltage addition which are given when you connect one winding of a transformer in series with another winding. The current induced in the upper section of our transformer winding or in the secondary of any transformer flows, inside the winding, in the opposite direction to the current which flows in the primary winding."

"But how can this be possible?"

"It arises," said Smithy, "from the basic property of an inductor, which is to oppose any change in the current which flows through it. Say we have an iron-cored smoothing choke and we start to pass a current through it. The current causes an expanding magnetic field to be set up, and that expanding field in turn produces a back e.m.f. in the choke winding which opposes the flow of the current. If we add another winding to the choke and connect a resistor across that winding so that current can flow in it, the winding will function like the secondary in a transformer, and it will have induced in it a current which flows in the same direction as that corresponding to the back e.m.f. produced in the original winding."

"Stap me," said Dick. "That idea takes a bit of getting used to."

"I'll agree," said Smithy, "that it's a bit of a pill to swallow, but it makes sense when you give it some consideration. What I've said about current direction in primary and secondary windings applies to all transformers, and it must obviously be true because of the readily measurable voltages which are obtained when we connect transformer windings in series."

There was silence for some moments as Dick absorbed this information.

"Do you know, Smithy," he said eventually, "the trouble with electronics is that it's so darned interesting. Perhaps I won't give up servicing after all."

"There is," said Smithy softly, "a milk float standing at the dairy. And it's got your name right across the front."

"Oh, I don't know."

Suddenly, a flash of comprehension crossed Dick's face.

"Why," he gasped, "you set all this up! You conniving old twister, you waited until I was feeling fed up with electronics, and then you deliberately set up this business about transformer currents and voltages to make me even more cheesed off with it."

Dick pointed a trembling finger at the Serviceman.

"You're trying to get rid of me. You're trying to get me out of the Workshop!"

Smithy spread his hands in a self-deprecating gesture.

"Dick, lad," he said. "I'm not getting any younger, you know. The idea of a quiet peaceful Workshop all to myself has many attractions."

"Well, that's nice, I must say," retorted Dick indignantly. "After all these years you're now trying to get shot of me. Casting me out like a worn-out glove or a sucked-out orange. And after all I've done for you!"

"You've never done anything for me, ever. All you do is impede things."

## BASIC QUESTION

The pair glowered at each other.

"And if I do go," asked Dick ominously, "who's going to make your tea?"

"Blimey," said Smithy apprehensively, "I'd forgotten about that."

"Aha," crowed Dick triumphantly. "Who wants to get shot of me now, eh?"

"I never said I wanted to get shot of you," replied Smithy hastily. "At least not in so many words. Besides, it was you who started off all this talk about the milk round."

They faced each other belligerently. The ridiculous aspect of the situation suddenly occurred to Dick and he grinned. It was not long before Smithy joined him and the Workshop was soon filled with howls of laughter.

And so, disapprovingly, we must take our leave of Smithy and his assistant as they fall about with most unseemly hilarity, when they should have been engaged in the serious pursuits that are becoming to a professional servicing establishment.

Still, you've got to have a chuckle now and again.

RADIO & ELECTRONICS CONSTRUCTOR

**RADIO & ELECTRONICS  
CONSTRUCTOR**

**ANNUAL  
SUBSCRIPTIONS  
to this magazine  
may be obtained  
through your  
newsagent  
or direct from the  
publishers  
ONLY £3.30  
per year, post free**

Please send remittance with name and address and commencing issue required to:







**DATA PUBLICATIONS LTD  
57 Malda Vale London W9 1SN**

# ELECTRONIC ODDITIES

By R. River

Not all electronics is to be found in the  
text-books.

## LOGIC

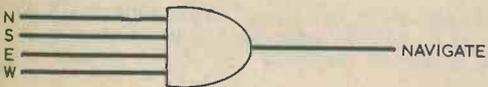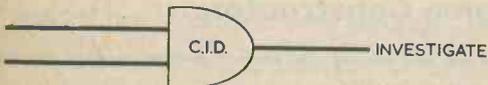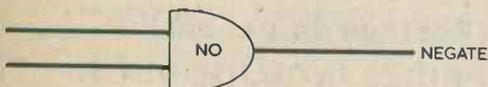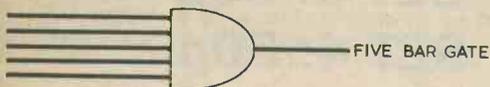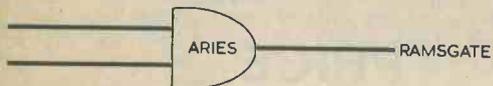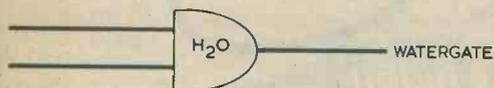

- Q. Is this the sync circuit?  
A. Yes, you can tell because it's got two taps.

Watching horse racing on colour TV is a completely new experience.  
The horses stay still and the colours run.

- Q. What do you get if you split integrated circuits in two?  
A. Fission chips.

- A. This is a genius coil.  
B. Genius coil?  
C. Yes, it's got a high Q of 300.

- Q. What can you catch with a mag-net?  
A. A tuner fish?

- A. Why are you laughing? What's so funny about an inductance capacitance smoothing circuit?  
B. Of course it's funny, don't you see the choke?

- Q. What will write but won't make a torch light?  
A. A lead pen-cell.

- A. Our cat's swallowed a frame-frig valve!  
B. Did it do him any harm?  
A. No, now he's got a bigger  $\mu$ .

- Q. Where does a volt have its ohm?  
A. 'Ampshire.

The introduction of the pilot-tone multiplex system on Radio 3 was a great idea. Now when you listen to a concert you can hear the audience cough in stereo.

- Q. What do you get if a resistor overheats?  
A. Ohm cooking.

Hi-Fi loudspeaker units use woofers and tweeters. What do pocket transistor radios use? Loudspeakers?

- Q. Why are you chewing resistors?  
A. I'm an ohmmeter.

And now for further news of the threatened TV engineers' and technicians' stri . . . .

# Use the **NEW Strip-fix Plastic** **PANEL SIGNS**

★ **SET 3 - Wording - WHITE**

★ **SET 4 - Wording - BLACK**


Over 1,000 words and symbols, covering more than 300 terms, in each set

Illustration of actual size = RADIO

★ **SET 5 - DIALS**

6 sheets containing one Large and two Medium scales, Large Horizontal Tuning scale, Frequencies, 12 Control Panels

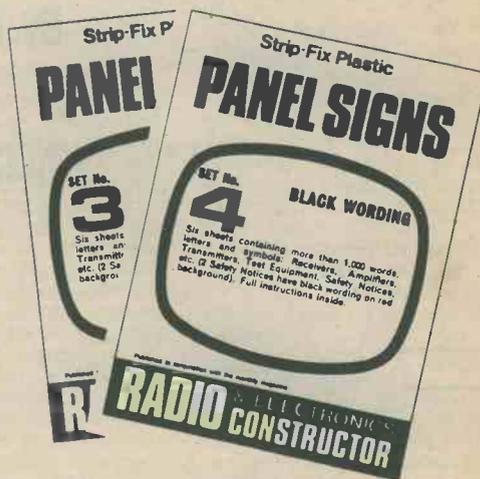- Easy to fix
- Stapled in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish



## PRICE

SET 3: 38p

SET 4: 50p

SET 5: 38p

(Postage 4p per set)

ALL PRICES INCLUDE V.A.T.

The Perfect Transfer for the Home Constructor

**To Data Publications Ltd., 57 Maida Vale, London, W.9 1SN**

Please supply Panel Signs as follows: Set 3 ..... Set 4 ..... Set 5 .....

I enclose cheque / crossed postal order for ..... (Tick which set is required)

NAME .....

ADDRESS .....

(BLOCK LETTERS PLEASE)

# SMALL ADVERTISEMENTS

Rate: 5p per word. Minimum charge 75p  
Box No. 10p extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN

**SERVICE SHEETS** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault Finding Guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex. Telephone Hastings 429066

**CHROMASONIC ELECTRONICS.** New list 10p. post free. Data Dept., 56 Fortis Green Road, London, N10 3HN.

**FOR SALE:** Polarised relays, suitable for RTTY terminal units. £1.00. Box No. G235.

**RADIO, TV AND OTHER VALVES.** Large stocks 1930-1974. S.A.E. for quotations. Price list 15p. Also available transistors and stylii. Cox Radio, 19 The Parade, East Wittering, Sussex. Telephone: West Wittering 2023.

**FM RADIO Transmitter Modules** complete with microphone and battery. Four simple connections only required. Return of post delivery. £4.50. E.E.S. Ltd., The Airport, Exeter, Devon.

**WANTED.** Early radio books, prior to 1925. Box No. G236.

**BUILD THE MULLARD C.C. TV CAMERA.** Complete kits now available from Crofton Electronics. Send large s.a.e. for details to:- 124 Colne Road, Twickenham, Middlesex, TW2 6QS. Telephone: 01-898-1569.

**MINI MAINS TRANSFORMERS.** 30 x 30 x 37mm. Cool, quiet, British. Pri: 220/250V. Type MT3, 3-0-3V rms, 300mA, £1. MT7, 7-0-7V, 120mA, £1. VAT included. Use MT3 for 3V or 6V rectified d.c., MT7 for 9V or 18V. Circuits supplied. Mail order only. U.K. post 5p per order. Amatronix Ltd., 396 Selsdon Road, South Croydon, Surrey, CR2 0DE.

**SUPER CONSTRUCTORS PACK** containing 50 assorted spacers 4 and 6BA clearance and threaded types. Two 6" extension shafts, Two couplers, Two 2" extension shafts with couplers attached, 1 foot each of 2-4 and 6BA brass studding (3ft.), 20 tag strips, 2 trimmer converters, 100 mixed self-tapping screws, plus free gift. Bargain at £1.65p inclusive of postage. Electro-Mech Products, 7 Chantry Avenue, Bideford, Devon. Telephone: 6820.

**HARDWARE SUPPLIES.** Sheet aluminium, screws, nuts, washers, etc. Fascia panels in aluminium, individual requirements. Printed circuit boards, one-off or small runs, individual and for patterns published in this magazine. Send 10p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford-upon-Avon, Warwicks. CV37 9JP.

**UNIQUE VHF KITS,** 80 - 180 MHz. Receiver, tuner, converter. World wide sales. £4.50p. S.W. Kits also available. S.A.E. for literature. Johnsons (Radio C), Worcester, WR1 3QQ.

**FOR SALE:** 1000 mixed resistors £1.00, postage 25p. 10 mixed 3-5-7-10W resistors 25p. 10 untested unijunction transistors 50p. 10 mixed crystals 50p. Sinclair digital multimeter DMI £47.50. Digital multimeter kit £80.00; S.A.E. for details. Panel mounting neon 15p. 6V 5W soldering iron 1/16" bit £2.00. ZN414 i.c. £1.00. Box No. G243.

(Continued on page 252)

## BENTLEY ACOUSTIC CORPORATION LTD.

All prices inclusive of V.A.T.

The Old Police Station, Gloucester Road, LITTLEHAMPTON Sussex. PHONE 6743

OB2 .40	9D7 .65	E88CC .75	EL41 .90	PCL84 .45	UL41 .75
ZD21 .45	10E1 .75	E180F 1.00	EL84 .31	PCL805 .55	UL84 .42
3V4 .70	10F18 .55	EA50 .27	EL91 .50	PCL86 .47	UM80 .44
3R4GY .80	12A6 1.00	EABC80	EL506 .90	PEN45 .80	UY41 .45
5U4G .40	12AC5 .70	EAF42 .75	ELL80 1.25	PEN46 .50	UY85 .35
3V4G .50	12AD5 .65	EAF80 .60	EM80 .45	PL81 .60	X41 1.00
5Y30T .45	12AE6 .65	EAF801.75	EM81 .65	PL81 .50	X66 1.25
3Z4G .45	12AT6 .40	EB91 .20	EM83 .55	PL82 .37	AC165 .28
6J0L2 .80	12AU6 .45	EB91 .20	EM84 .40	PL83 .45	AD140 .40
6BH6 .60	12AV6 .50	EB8C1 .35	EM87 .70	PL84 .40	AD149 .55
6A05 .45	12BA6 .45	EBF80 .39	EY51 .40	PL504 .75	AD161 .50
6AT6 .45	12BE6 .50	EBF83 .43	EY83 .34	PL508 .90	AD162 .50
6AU6 .30	12BH7 .50	EBF89 .32	EY87/6 .33	PL511 .45	AD164 .28
6AV6 .45	12K5 1.00	EC92 .45	EY88 .40	PL802 .95	AF115 .17
6BA6 .28	14S7 .80	ECC331.50	EZ40 .50	PY33/2 .50	AF121 .33
6BE6 .35	19A05 .50	ECC35 .95	EZ41 .55	PY81 .35	AF126 .20
6BH6 .60	20P4 1.00	ECC401.00	EZ80 .28	PY82 .35	BC107 .14
6B16 .55	30C15 .80	ECC81 .34	EZ81 .29	PY83 .38	BC108 .14
6BQ7A .55	30C17 .80	ECC82 .33	EY501 .70	PY88 .40	BC109 .11
6BR7 1.00	30F5 .80	ECC83 .33	GZ32 .50	PY500 .95	BC113 .28
6BR8 1.50	30FL1 .67	ECC84 .30	GZ34 .60	PY300A	BC118 .25
6BW6 .80	30FL2 .67	ECC85 .40	HVR2A	.95	BC211 .42
6BW7 .70	30FL14 .78	ECC28 .44	PCW8 1.00	PY800 .40	BF159 .28
6BZ6 .49	30L15 .75	EFC80 .34	KTW61 .50	PY801 .40	BF163 .22
6C4 .35	30L17 .70	EFC82 .38	KTW62 1.50	QVQV3/	BF180 .33
6C6 .40	30P12 .80	ECF86 .75	KTW62 1.50	10 1.75	BY100 .20
6C9 1.00	30P19 .75	ECH351.25	U25 .85	R19 .60	BY126 .17
6CL6 .65	30PL1 .85	ECH42 .70	U26 .66	U25 .85	BY127 .20
6C15 .75	30PL13 .95	ECH81 .33	U191 .75	U26 .66	OA91 .10
6E5 1.00	30PL14	ECH83 .44	PABCB0	U191 .75	OA95 .10
6F1G .75	35L6GT.75	ECH84 .44	PC86 .60	U201 .85	OC23 .42
6F6G .50	35W4 .50	ECL82 .34	PC88 .60	UACB80	OC24 .42
6F1H .55	35W4 .50	ECL83 .70	PC89 .60	UAF42 .60	OC44 .11
6F23 .80	35Z4GT.70	ECL86 .40	PC90 .48	UBC81 .45	OC45 .12
6G2Z .67	50B5 .95	EFC22 1.50	PC90 .48	UBC81 .45	OC46 .17
6HG6T 25	50C5 .60	EF20 1.50	PC94 .40	UBF80 .40	OC70 .14
6J5GT .45	50L6GT.65	EF40 1.50	PC98 .60	UBF89 .40	OC71 .12
6J6 .30	85A .60	EF41 .50	PC98 .60	UC29 .45	OC72 .12
6K7G .30	AT14 .50	EF80 .26	PC98 .60	UC84 .75	OC74 .25
6K8G .45	AZ31 .60	EF83 1.00	PC98 .60	UC85 .45	OC75 .12
6L6G .58	DAF91 .30	EF85 .34	PC98 .60	UC85 .45	OC75 .12
6O7 .50	DAF90 .50	EF86 .30	PC98 .60	UC85 .45	OC75 .12
6O7GT .50	DF91 .30	EF89 .27	PC98 .60	UC85 .45	OC75 .12
6SG7 .44	DF96 .50	EF91 .37	PCF84 .59	UC81 .40	OC81 .12
6S17 .55	DK91 .45	EF92 .50	PCF86 .60	UC82 .38	OC81D .12
6V17 .17	DK92 .70	EF93 .60	PCF81 .50	UC83 .35	OC82 .12
6V6GT .45	DK96 .60	EF183 .30	PCF802 .50	UF41 .70	OC82D .12
6X4 .40	DL92 .40	EF184 .35	PCF805 .80	UF80 .35	OC83 .22
6X5GT .45	DL96 .55	EFH95 .55	PCF806 .50	UF80 .35	OC84 .26
7B6 .75	DY87/6 .38	EL32 .50	PCF82 .38	UF81 .40	OC202 .47
7Y4 .75	DY802 .35	EL34 .66	PCL83 .50	UF89 .40	OC205 .47

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. Despatch charges: Orders below £5, add 10p per order up to three items, each additional item 3p extra. Orders between £5 and £10 add 25p total. Orders over £10 post free. Same day despatch. Terms of business available on request. Any parcel insured against damage in transit for only 3p extra per parcel. Please enclose S.A.E. with any enquiries.

## ENGINEERS

# FREE



YOURSELF FOR A

# BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through our low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer.

Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

**CUT OUT THIS COUPON**  
**CHOOSE A BRAND NEW FUTURE HERE!**  
Tick or state subject of interest. Post to the address below.

**POST NOW**

Build-As-You-Learn  Electronic Engineering  CITY & GUILDS Installations and Wiring

PRACTICAL RADIO AND ELECTRONICS (with kit)  Computer Electronics  CITY & GUILDS Electrical Technicians

Electrical Engineering  Computer Programming  CITY & GUILDS Telecommunications

Electrical Installations and Wiring  General Radio and TV Engineering  Radio Amateurs' Exam etc. etc.

Electrical Draughtsmanship  Radio Servicing, Maintenance and Repairs  G.C.E. 5th O' & 'A' LEVELS

Electrical Mathematics  Transistor Technology  Coaching for many major examinations

To ALDERMASTON COLLEGE, Dept BRE 95, READING RG7 4PF **BRE 06**

NAME (Block Capitals Please)

ADDRESS

Other subjects

Accredited by C.A.C.C.

Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# Why go hunting for components when there's CATALOGUE 7



- 112 pages
- Transistors, I.C.s, Thyristors, etc.
- Rs and Cs of all kinds
- Pots

**GENUINE DISCOUNTS  
COMPUTERISED  
HIGH-SPEED SERVICE**

**25p**  
Post free  
including  
25p refund  
voucher

Look it up in Catalogue 7 first. Packed with components, attractively priced, brand new and guaranteed to spec. You are more likely to get the things you want from ELECTROVALUE and there are excellent discounts too.

Anything over £2 (except Baxandall speaker) send carriage paid—in U.K. And with Catalogue 7 you get a 25p Refund Voucher usable on orders for £5 or more list value. Catalogue 7 also includes useful diagrams and data.

## ELECTROVALUE LTD.

(Dept. RC.11) 28 St. Judes Road, Englefield Green, Egham, Surrey  
TW20 0HB (Telephone: Egham 3603)  
Northern Branch, (Personal callers) 680 Burnage Lane, Manchester  
(Telephone: 061-432 4945)

# RADIO MODELLER ELECTRONIC BOOKS

### ● MODEL RADIO CONTROL


Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.  
134 pages.

Price £2.25

U.K. Packing  
& Postage 32p

**ON SALE NOW**  
at all leading shops  
or direct from:—

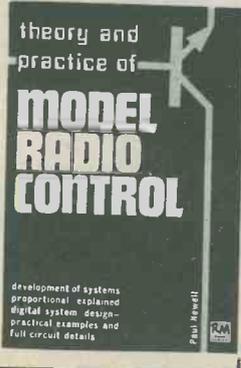**RADIO MODELLER  
BOOKS DIVISION,**  
64 Wellington Road,  
Hampton Hill, Middx.



## SMALL ADVERTISEMENTS

(Continued from page 251)

**RADIO & TELEVISION AERIAL BOOSTERS.** Improve weak reception. £3.10. 5 television valves, 45p. S.A.E. leaflets. Lancashire Mail Order (R), 6 William Street, Stubbins, Ramsbottom, Bury, Lancs.

**MAGNIFIERS**, ideal for wiring printed circuit boards, etc. 4" dia. lens on flexible arm and heavy base £6.00, also Binomag headband magnifier — £5.70. Available by post from Revor Optical & Technical, 36 Baker Street, London W.1. Telephone: 01-836 4536.

**COMPONENTS GALORE.** Manufacturers' surplus plus fall-out. Pack of 500 mixed components includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers, coils and formers, etc. Send £1.00 plus 15p p. & p. C.W.O. to Cascade Components Company, Dept. R. & E., Bankhead Farm, South Queensferry, West Lothian.

**FOR SALE:** Pye pocketphones, untested, £20.00. Pair infra-red monoculars, untested, £2.00. Binatone stereo cassette deck, £50.00. Venner type 8-day reconditioned time switch, £2.50. Box No. G244.

**FOR SALE:** Sinclair scientific calculator, duplicated present, £36. Exponent, trigonometric, logarithms, unused, perfect (List £52.92) 1 year guarantee. Box No. G245.

**MULLARD 10W RMS AMPLIFIER MODULES.** Brand new for 24 volt 4 ohm operation. Tremendous offer, absolutely no extra components or hardware required. Supplied with circuit and full data for simple operation. £2.65 inclusive. LTE, 46 Minehead Road, South Harrow, Middlesex. Mail order only please.

**FOR SALE:** 2 low-band Pye Rangers and pair untested Pye pocketphones. Or exchange for AU08 and 35mm camera. Box No. G246.

**FOR SALE:** Enamelled copper wire 2½ oz. reels 30 s.w.g. only, 30p each. 250MΩ 1 in. pots, 5p each. Post and packing 10p. Daniel Collier, Sturtsbury Farm, Bumbles Green, Nazeing, Essex.

**WANTED:** Stroboscope tuning forks. Teletype No's. 103628 for 60 w.p.m. and 104984 for 66 w.p.m. Box No. G247.

**ANTIQUÉ WIRELESS ENTHUSIASTS.** For all your requirements in radio pre-1945 contact: Tudor Rees's Antique Wireless Service. Retail shop now open at 64 Broad Street, Staple Hill, Bristol. Telephone: 0272-565472.

**WANTED:** Service manual for Hallicrafter's Sky rider communications receiver. Box No. G248.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £2.00 per annum. (U.K. and British Commonwealth), overseas 6 Dollars or £2.50. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

**FOR SALE:** Germanium point contact diodes, equivalent OA91. Branded. 5 for 25p inclusive. T.A.C., 59 Luckwell Road, Bristol, BS3 3ES.

(Continued on page 253)

RADIO & ELECTRONICS CONSTRUCTOR

## SMALL ADVERTISEMENTS

(Continued from page 252)

**FOR SALE:** Handbook of satellites and space vehicles £7.00. Self-sealing plastic bags 2½" x 2½", 100-30p, s.a.e. for sample. 5lbs mixed components £2.50. Avo 8 £20.00. Battery operated door chimes (need repair) 75p. Servisol switch cleaner 70p, 2 tins £1.00. 10 mixed LED'S £1.50. Valve tester £20.00. 2-speed drill with 'hammer' action, ¾" chuck, £12.50. 75 yds x 2" Sellotape roll £1.00. Freezing spray aerosol £1.30. Bush CTU25 colour TV, serviced with new tuners, £125.00. 10" 8Ω speaker £2.75. 100mW walkie-talkies £27.00. 147kHz-220MHz signal generator £38.00. Reconditioned adjustable arm bench lamp £5.00. 24V input 500W 240V inverter £30.00. 50W hi-fi amplifier kit £12.50. Manufacturer's reject (repairable) walkie-talkies (retail £59.95) £30.00. Minifon pocket wire recorder, new condition, £8.00. S.A.E. for lists. Box No. G249.

**QUARTZ CRYSTALS.** 5675 kc/s to 8650kc/s in steps of 25kc/s. ½" pin spacing. £2 for 20 our selection. 7000 to 7175 £1.00 each. E.E.S. Ltd., The Airport, Exeter, Devon. Telephone 66523.

**TRANSISTOR RADIOS.** Completely wired, M/L PCB, speaker, cabinet, leatherette case, earpiece. Sample £3. TEN for £25. M/W £2, TEN for £15. Post extra. Cook, 90 Ewhurst Road, Crawley, Sussex. Telephone: Crawley 23885.

**FOR SALE:** 5 new Pop-8-track cartridges £6.00. 50 ex-juke box records £3.50. Cassettes C60 40p, C90 50p, C120 60p. Cassette cube case MOC236 £4.50. Head cleaners cassette 50p, 8-track 75p. Adaptor to play cassettes through car radio £12.00. Miniature radio, rechargeable batteries and recharger, £4.50. Box No. G250.

**WORLD DX CLUB** covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.60 a year. Enquiries to John Rush, 12 Northfield Road, Thatcham, Berks.

**FOR SALE:** Selenium solar cells 15p. 30W fluorescent chokes 30p. 3015F minitrons £1.15. ZN414 i.c. £1.00. NE555 75p. Pocket a.m./f.m. radios £5.50. 200 mixed transistors 80p. C60 blank cassettes 35p. Insulated 1/16" test sockets, 10 - 50p. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, Ireland.

**SUPERB INSTRUMENT CASES** by Bazelli. manufactured from heavy duty PVC faced steel. choice of 174 types. send for free list. Bazelli Instrument Cases. Dept. 26. St. Wilfrid's. Foundry Lane. Halton. Nr. Lancaster. LA2 6LT.

**FOR SALE:** Electronic circuits manual £4.50. Also back numbers of *Radio Constructor* and *Wireless World*. Send for list. Box No. G251.

**WANTED:** Pye Bantam radio telephones. Any band or condition. Jefferies, 105 Cloudhill Road, St. George, Bristol.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.

**TELEVISION VALVES** 10p each: ECC82, ECH84, EF80, EF183, EF184, DY86/7, PC86, PC88, PCF80, PCF801, PCF802, PCC84, PCC189, PY33, PY800, PY88, PCL82, PCL84, PCL85/805, PL36, PL504. P. & P. 10p. Electronic Mailorder, Ramsbottom, Bury, Lancs.

(Continued on page 255)

## PRECISION

### POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

440V AC (+/-10%)	50p	63V Range	+1%	+2%	+5%
0.1µF (1½" x ½")	50p	0.47µF	56p	46p	36p
0.22µF (1½" x ½")	59p	1.0µF	66p	56p	46p
0.25µF (1½" x ½")	62p	2.2µF	80p	65p	55p
0.47µF (1½" x ½")	71p	4.7µF	£1.30	£1.05	85p
0.5µF (1½" x ½")	75p	6.8µF	£1.64	£1.29	£1.09
0.68µF (2" x ½")	80p	10.0µF	£2.00	£1.60	£1.40
1.0µF (2" x ½")	91p	15.0µF	£2.75	£2.15	£1.90
2.0µF (2" x 1")	£1.22	22.0µF	£3.50	£2.70	£2.55

**TANTALUM BEAD CAPACITORS** - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL AT 10p EACH; 10 for 95p; 50 for £4.00.

### TRANSISTORS:

BC107/8/9	9p	BC183/183L	11p	BF194	12p	BFY51	20p
BC114	12p	BC184/184L	12p	BF196	13p	BFY52	20p
BC147/8/9	10p	BC212/212L	14p	BF197	13p	OC71	12p
BC153/7/8	12p	BC547	12p	AF178	30p	2N3055	50p
BC182/182L	11p	BC558A	12p	BFY50	20p	2N3702/4	11p
1N914	6p; 8 for 45p; 18 for 90p.	1N916	8p; 6 for 45p; 14 for 41p.	IS44	5p; 11 for 59p; 24 for £1.00.	IN4148	5p; 6 for 27p; 12 for 48p.

**LOW PRICE ZENER DIODES:** 400mW; Tol. +5% at 5mA. Values available: 3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.5V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each; 6 for 39p; 14 for 84p. SPECIAL: 100 Zeners for £5.50.

**RESISTORS:** High stability low noise carbon film 5%, ½ W at 40°C; ¼ W at 70°C. E12 series only - from 2.2Ω to 2.2MΩ ALL AT 1p EACH; 8p for 10 of any one value; 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

**SILICON PLASTIC RECTIFIERS** - 1.5 Amp - Brand new wire ended D027: 100 P.I.V. - 7p (4/26p); 400 P.I.V. - 8p (4/30p); 800 P.I.V. - 11p (4/42p). **BRIDGE RECTIFIERS:** 2½ Amp. 200V - 40p; 350V - 45p; 600V - 55p.

**SUBMINIATURE VERTICAL PRESETS** - 0.1W only: ALL AT 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω 1K, 2.2K, 4.7K, 6.8K, 10K, 15K, 22K, 47K, 100K, 250K, 680K, 1M, 2.5M, & 5M.

**TRANSFORMERS:** Primary 220-240V, 12V @ 2A & 24V @ 1A. £2.00 plus 22p post.

**PLEASE ADD 8% V.A.T. TO ORDERS. PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5.00.** Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona-fide companies. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

## MARCO TRADING

Dept. C9, The Old School, Edstaston, NR. WEM, Salop.  
Tel: WHIXALL (Salop) 464 (STD 094872) (Props: Minicost Trading Ltd.)

## ENGINEERS

# FREE

## YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through our low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer.

Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

**CUT OUT THIS COUPON**  
**CHOOSE A BRAND NEW FUTURE HERE!**

Tick or state subject of interest. Post to the address below.

<input type="checkbox"/> Computer	<input type="checkbox"/> Building	<input type="checkbox"/> RADIO/TELECOMMS.	<input type="checkbox"/> Garage Man.
<input type="checkbox"/> Elec.	<input type="checkbox"/> Carpentry	<input type="checkbox"/> C & G	<input type="checkbox"/> MAA/IMI Dip
<input type="checkbox"/> Electronic Eng.	<input type="checkbox"/> Civil Eng.	<input type="checkbox"/> Radio TV	<input type="checkbox"/> GENERAL
<input type="checkbox"/> Eng.	<input type="checkbox"/> Const. Eng.	<input type="checkbox"/> C & G	<input type="checkbox"/> Agric. Eng.
<input type="checkbox"/> Elec. Eng.	<input type="checkbox"/> Heat & Vent.	<input type="checkbox"/> Inst. of Builders	<input type="checkbox"/> Telecomms.
<input type="checkbox"/> Mech. Eng.	<input type="checkbox"/> Inst. of Mgt. & Works	<input type="checkbox"/> Inst. of Highways and Supers.	<input type="checkbox"/> Gen. Educ.
<input type="checkbox"/> A.M.S.E. (Mech)	<input type="checkbox"/> <b>MANAGEMENT</b>	<input type="checkbox"/> Painting & Dec.	<input type="checkbox"/> Slide Rule
<input type="checkbox"/> Diesel Eng.	<input type="checkbox"/> Computer	<input type="checkbox"/> Surveying	<input type="checkbox"/> Refrigeratn.
<input type="checkbox"/> Inst. Motor Ind.	<input type="checkbox"/> Prog.	<input type="checkbox"/> <b>DRAUGHTSMANSHIP</b>	<input type="checkbox"/> G.C.E. '80 '80's & 'A' LEVELS
<input type="checkbox"/> Maintenance	<input type="checkbox"/> Management	<input type="checkbox"/> A.M.I.E.D.	<input type="checkbox"/> Coaching for many major examinations
<input type="checkbox"/> Mech. Eng.	<input type="checkbox"/> Prod. Eng.	<input type="checkbox"/> A.E.C. Cert.	
<input type="checkbox"/> Welding	<input type="checkbox"/> Qual. Control	<input type="checkbox"/> Auto Eng.	
<input type="checkbox"/> <b>ELECTRICAL &amp; ELECTRONIC</b>	<input type="checkbox"/> Storekeeping	<input type="checkbox"/> C & G Auto	
<input type="checkbox"/> A.M.S.E. (Elec)	<input type="checkbox"/> Work Study	<input type="checkbox"/> Eng.	
<input type="checkbox"/> C & G Elec. Eng.	<input type="checkbox"/> Works Man.		
<input type="checkbox"/> Eng.	<input type="checkbox"/> <b>CONSTRUCTIONAL</b>		
	<input type="checkbox"/> A.M.S.E. (Civil)		
	<input type="checkbox"/> Archtecture		
	<input type="checkbox"/> Drawing		

To ALDERMASTON COLLEGE, Dept BRE 90 READING RG7 4PF **BRE 90**

NAME (Block Capitals Please)

ADDRESS

Other subjects

Accredited by C.A.C.C.

Age

Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

**MASSIVE CLEARANCE BARGAINS**

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Rotary, Slide, Switches, IF's, Tag Strips, Drive Drums, Springs, Coil Formers, Wire, Grommets, Relays, Pulley Wheels, Magnets, Transistor Panels etc., etc. Save yourself £5 on these well selected parcels 6lbs net weight £1.00, p. p. 50p.

Brand new Wire-wound Resistors. 1-7 Watts. Good Selection. 100 for £1 p. p. 20p.

Mullard Ferrite Cores LA3 100 to 500KHz, 50p. LA4 10 to 30KHz. 75p. LA2100 3 to 200 KHz. 50p.

P.V.C. Flexible Connecting Wire Assorted Colours 100 yards for £1.00 p.p. 20p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection. 300 for £1. p. p. 20p.

Special Offer Electrolytic Capacitors Reversible 3600uF 70 volts H.D. Terminals 60p, p.p. 20p.


Please include 8% V.A.T. to total cost of goods.

**MAIL ORDER ONLY  
XEROZA RADIO**

1, EAST STREET,  
BISHOPS TAWTON,  
DEVON
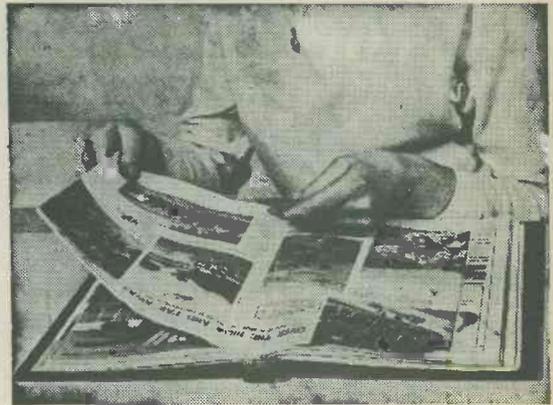
# PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines  
(max. format 7½" x 9½")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

**COLOURS: MAROON OR GREEN**  
(If choice not stated, colour available will be sent)

**PRICE 85p** P. & P. 18p

including V.A.T.

Available only from:—

**Data Publications Ltd.**  
57 Maida Vale London W9 1SN

**MICROJET WELDER**  
A TINY FLAME UP TO  
**5000°F!**  
WELDS-BRAZES  
SOLDERS **£13.95**

**INC. FLAME TIPS**

A precision tool using a combination of butane and compressed oxygen or micronox. U.S.A. manufactured. Gives a flame of pencil lead thickness. Adjustable temperatures up to 5,000°F.

Lights instantly. No priming. Cuts metals, welds, brazes and solders etc., gold and silver. Ideal for electronic construction and all fine precision work, clock makers, silver-smiths, etc. Up to 40 minutes operation using fuel supplied. Replacement set of 2 micronox and 1 butane cylinders £1.50 inc. post. Complete with detailed instructions. Only £13.95 plus 40p p. & p. Send £14.35.

**JOHN DUDLEY & CO. LTD.**, (Dept. RC.6), 301 Cricklewood Lane London, N.W.2. Tel.: 01-458 5917 (Callers welcome - Easy Parking)

## INTERNATIONAL



## SHORT WAVE LEAGUE

Membership £2.00 per annum (U.S.A. \$6.00) including 12 monthly issues of *Monitor* — the League journal. Including free use of all Services, QSL Bureau etc.

**THE LARGEST S.W.L. ORGANISATION  
IN THE WORLD**

For full details write to:

**The Secretary,  
I.S.W.L.,  
1, GROVE ROAD, LYDNEY,  
GLOS. GL15 5JE.**

## SMALL ADVERTISEMENTS

(Continued from page 253)

**EXPERIMENTERS!** Hundreds of unusual items cheap. List No. 9, 6p. Grimsby Electronics, Lambert Road, Grimsby, Lincs. (Callers Saturdays only).

**150 RESISTORS** (Hi-stabs etc.) 50p. 20 1½" fuses (many anti-surge) 50p. 50 Mullard Z700U 75p. Add 15p postage. C. W. O. Hughes, 1 Quarry Green, Liverpool L33 8XY.

**FOR SALE:** Heathkit HW32A 20 meter TX/RX, HP23 power supply and loudspeaker in matching cabinet. GH12 microphone. Factory aligned and tested. Used twice. Complete rig £75. Abbott, 48 Cornmill Drive, Liversedge, Yorkshire.

**SEMICONDUCTORS.** Unused, tested. BC108, OC81, 6p each. OA202, 3p each. Postage and packing 10p. Hoggarth 8A Ghyll Beck Drive, Otley, West Yorkshire.

**FREQUENCY LIST TRANSFERS.** We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p. Five sheets for 10p. postage 3p. Data Publications Ltd., 57 Maida Vale, London W9 1SN.

### PERSONAL

**JANE SCOTT FOR GENUINE FRIENDS.** Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

**ELECTRONICS MEN.** You are worth more than a measly £40 or £50 a week. Much more. And you do not need to be highly qualified. Last year I earned £3,600 for six months work. The other six months I had off. My booklet will tell you how I started and how you too could do similar if not better. No selling and no capital outlay except the price of the booklet. It's 43p from Alben, Mill Lane, Acle, Norwich, Norfolk, NOR 6OZ.

**MAKE NEW FRIENDS!** The exciting reliable way. All areas, all ages. Write: S.I.M. Computer Dating (REC), 109 Queens Road, Reading, Berks.

**SPONSORS** required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, The Manse, Back Lane, Wymondham, Norfolk.

**YOUNG MAN DISABLED** needs work at home. Electronic/wire assembly. Would collect and deliver. Mr. B. Grimes, Llainwen, Glanrhyd, Cardigan, Wales, SA43 3PE.

**ESSEX GARDENERS.** Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

**INCOME TAX** and Business Accounting. Stop worrying and let us cope. Call Walton-on-Thames 28080.

**IF YOU HAVE ENJOYED A HOLIDAY** on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:—The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

## ESSENTIAL BOOKS!

**HOW TO MAKE 2M & 4M CONVERTORS FOR AMATEUR USE.** Available at last after many delays. Fully comprehensive. Contains circuits, lay-outs, component lists, diagrams and full instructional notes. Price 60p, p.p. 15p.

**HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION.** 40p, p.p. 15p.

**THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK.** Gives circuits, data and illustrations plus valuable information for British/USA receivers, transmitters, trans/receivers. Available later October. £4 including postage.

**DIRECTORY OF GOVERNMENT SURPLUS WIRELESS EQUIPMENT DEALERS.** Gives details of surplus wireless equipment stores and dealers including addresses plus equipment and spares that they are likely to have available. A valuable book only 50p, p.p. 10p.

**GETTING THE BEST FROM YOUR COLOUR TV.** R. Maude, Essential advice for colour TV engineers and owners. Could save you pounds. 50p, p.p. 15p.

**THE THEORY OF GUIDED ELECTROMAGNETIC WAVES.** The most comprehensive book yet written about waveguides, transmission lines, cavity resonators. Over 500 pages. Ideal for anyone interested in Radar and UHF. Published at £11.50. Special offer £4.50, p.p. 50p.

**MOBILE RADIOTELEPHONE EQUIPMENT HANDBOOK.** Gives circuits, data and illustrations plus some valuable modifications for amateur use for commercial radiotelephone equipment including PYE and other popular makes. Available early November. £4.75, p.p. 35p.

**HANDBOOK OF FIXINGS & FASTENINGS.** B. Launchbury. Covers all aspects of fixings & fastenings. Includes characteristics and range of sizes, types and applications of nails, wood screws, light plugs, heavy masonry fixings, rivets, screws, washers, bolts etc. Essential for the do-it-yourself enthusiasts. Profusely illustrated. Published at £1. Special offer 50p per copy, p.p. 25p.



Send for this fully comprehensive catalogue of radio books. Free.

**THE BARGAIN BOOK GAZETTE.** Contains thousands of interesting new and out of print books at bargain prices. Subjects include all types of hobbies, collecting, 1001 interests. Published regularly and sent free on request.

Dept. R. C. GERALD MYERS (Publisher & Bookseller), 138 Cardigan Rd., Headingley, Leeds 6, Yorks. (Callers Welcome).

### C AND G EXAM

Make sure you succeed with an ICS home study course for C and E Electrical Installation Work & Technicians Radio/TV/Electronics Technicians. Telecommus Technicians and Radio Amateurs.

### COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

### TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits.

Get the qualifications you need to succeed. Free details from:

### INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 233B Intertext House, London SW8 4UJ.

Or phone 01-622 9911

## MORSE MADE EASY!!!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.) Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. IN 4 WEEKS GUARANTEED. Complete course, 3 Records and Books, £4.95 incl. P.P.I. etc. (Overseas £1 extra). Or details only, 4p stamp. Or phone S. Bennett, G3HSC, 01-660 2896.

Box 38, 45 GREEN LANE, PURLEY, SURREY.

# SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the .....issue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 5p  
= 75p.

**ALL WORDING  
IN  
BLOCK LETTERS  
PLEASE**

I enclose remittance of.....being payment at 5p a word. MINIMUM 75p.  
Box Number, if required, 10p extra.

NAME.....  
ADDRESS.....

*Copy to be received four weeks prior to publication. Published on the 1st of every month.*

## DATA BOOK SERIES

- DB5 TV FAULT FINDING**  
New edition in course of preparation.
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**  
88 pages. Price 70p, postage 7p.
- DB16 RADIO CONTROL FOR MODELS**  
192 pages. Price 75p, postage 13p.
- DB17 UNDERSTANDING TELEVISION**  
512 pages. Price £2.10, postage 25p.
- DB18 AUDIO AMPLIFIERS**  
128 pages. Price 53p, postage 9p.
- DB19 SIMPLE SHORT WAVE RECEIVERS**  
140 pages. Price 80p, postage 9p.

I enclose Postal Order/Cheque for.....in payment for.....

NAME.....

ADDRESS.....

(BLOCK LETTERS PLEASE)

*Postal Orders should be crossed and made payable to Data Publications Ltd.  
Overseas customers please pay by International Money Order.  
All publications are obtainable from your local bookseller.  
Data Publications Ltd., 57 Maida Vale, London W9 1SN*

**PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS**