

JOB

RADIO & ELECTRONICS CONSTRUCTOR


DECEMBER 1974

25p

P U L S E




COUNTING
F.M.
TUNER

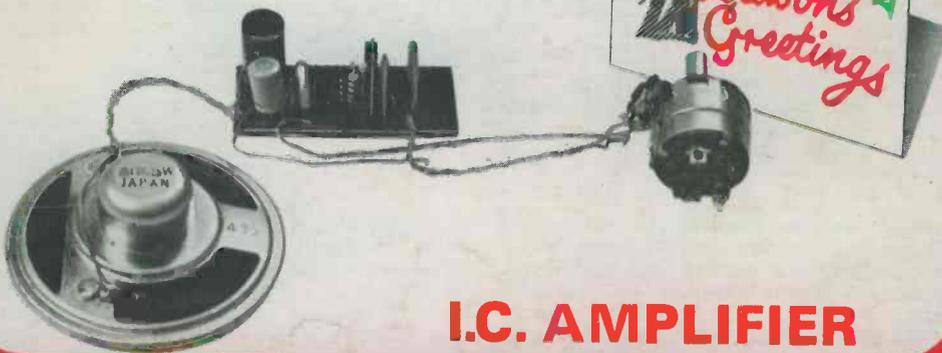

I.C. AMPLIFIER

ALSO
FEATURED

OSCILLOSCOPE
AMPLITUDE CALIBRATOR

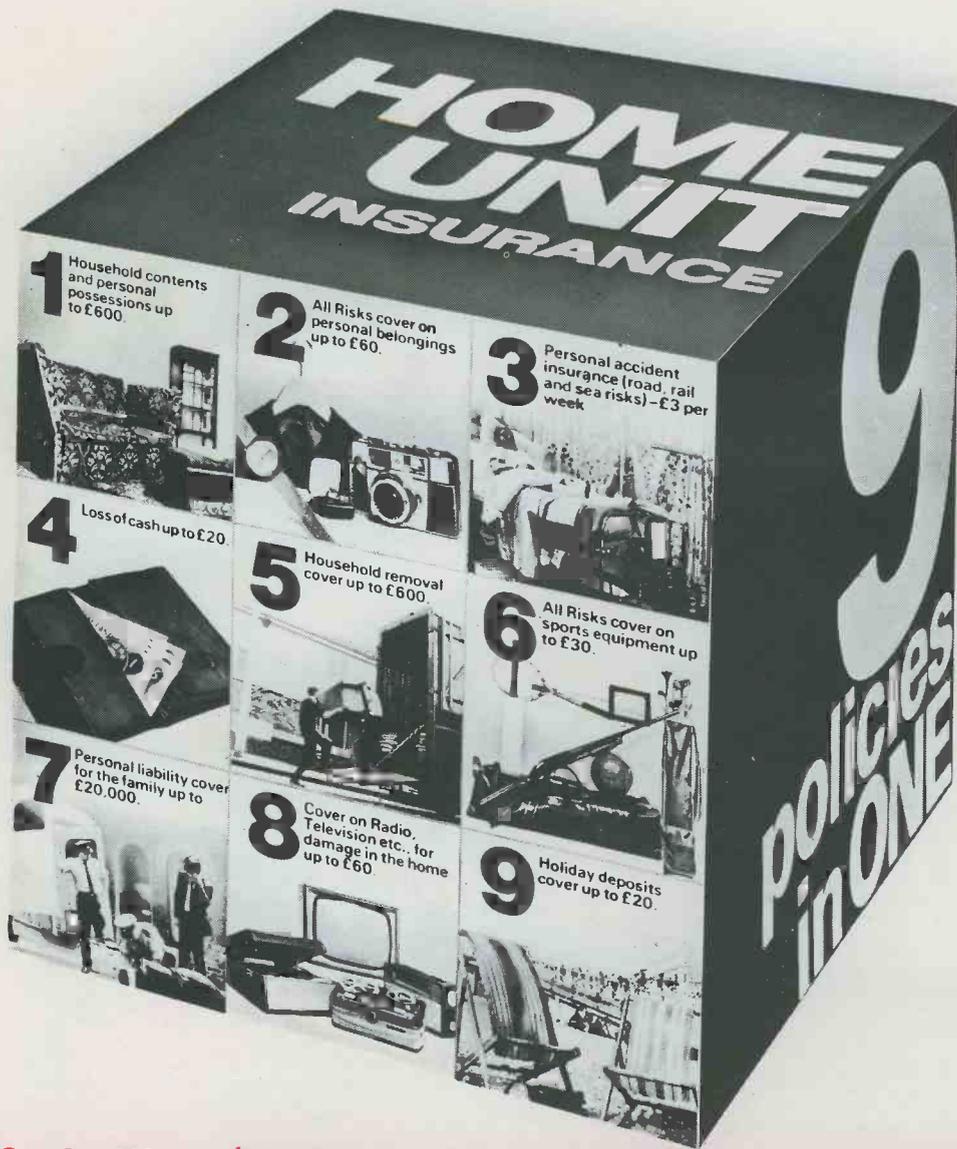

Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or 1/2 units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances And remember - as you buy more possessions just add more Home Units at any time. *Quote Ref. 20/9468*

THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....


.....

.....

.....

20/9468

ELECTROVALUE CATALOGUE 7

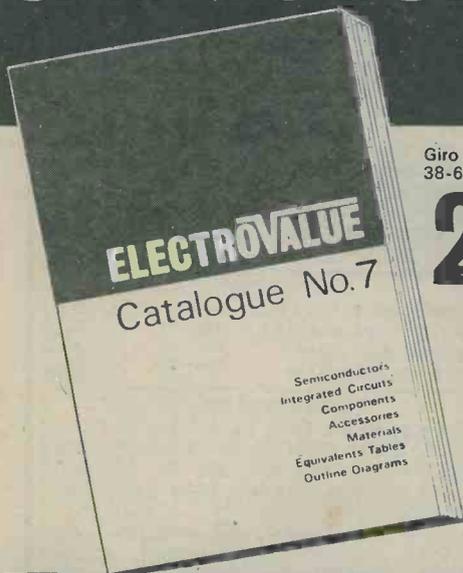

Giro Account No.
38-671-4002

25p

including
25p Refund
Voucher

2nd.
Printing
(Green and
yellow covers)

The best yet!

112 pages (plus covers) and our best yet! Practically all items in catalogue 7 are there as the result of information fed by our computer, enabling us to control stock-buying in relation to demand with greater accuracy and real benefit to customers. This means that your orders, which we microfilm for record keeping, are handled with utmost speed and efficiency. EV prices remain keenly competitive and in addition there are discounts as well, to give you further savings. Among the well known firms whose products we carry are those of SIEMENS, NEWMARKET, RADIOHM, SOLDERSTAT, GUEST INTERNATIONAL as well as Texas Instruments, Mullard and others.

Send 25p now for EV Catalogue 7. It includes a refund voucher for 25p allowable on orders for £5 or more list value.

● DISCOUNTS

Available on all items except those shown at NETT PRICE

10% on orders from £5 to £14.99 list.

15% on orders £15 and over.

● WE PAY POSTAGE

and packing in U.K. For mail orders for £2 list value and under, there is an additional handling charge of 10p.

● GUARANTEE OF QUALITY

All items guaranteed fully to makers' specifications. Everything brand new—no "seconds", makers' rejects or clearance offers.

ELECTROVALUE LTD

Dept REC.12 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB Telephone Egham 3603 Telex 264475

All mail orders and communications to above address

● NORTHERN BRANCH

680 Burnage Lane, Manchester M19 1NA
Hours (both addresses) 9.00-5.30. Saturdays 9.00-1.00 p.m.



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn – and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy – making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering – yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits – assemble components – build things – experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. AT NO EXTRA CHARGE! And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for FREE 76 page book – see how easy it is – read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

POST
TODAY FOR
FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. BRE 85
READING RG7 4PF

BRE 85

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS



HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

COMPONENTS

HOBBYIST AMATEUR - DOMESTIC - SURPLUS - INDUSTRIAL - JUST A FEW OF OUR BARGAINS ARE LISTED BELOW - SEND STAMPED ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS. THESE OFFERS APPLY ONLY TO MAIL ORDER AND NOT SHOP SALES.

GOODS SENT AT CUSTOMER'S RISK, UNLESS SUFFICIENT PAYMENT FOR INSURANCE INCLUDED (2p per £1 min 5p)

VALVE BASES	
Printed circuit B9A - B7G	4p
Chassis B7 - B9G - B7G	4p
Shrouded chassis B7G - B9A	6p
B8A - B9A chassis - B12A tube	6p

TAG STRIP	WRIST COMPASS
6 way 4p Single 1p	30p with Needle Lock

1½ glass fuses— 250 m/a or 3 amp (box of 12)	18p
3" tape spools	8p
10K+10K Log Switched Pot	55p
PVC or metal clip on M.E.S. bulb holder	5p
All metal equipment Phono plug	2p
Bulgin, 5mm Jack plug and switched socket (pair)	30p
12 volt solenoid and plunger	40p
250 RPM 50 c/s locked frequency miniature mains motor	50p
200 OHM coil, 2¼" long, hollow centre	10p
Belling Lee white plastic surface coax outlet Box	30p
R.S. 12 way standard plug and shell	50p

SWITCHES			Type	
Pole	Way			
4	2	Sub. Min. Slide	18p	
6	2	Slide	20p	
4	2	Lever Slide	15p	
6	4	} Wafer Rotary	30p each	
4	3			
3	7			
2	5			
1	3	+ off Sub. min. edge	10p	
1	3	13 amp small rotary	12p	
2	2	Locking with 2 to 3 keys	£1.50	
2	1	2 Amp, 250V A.C. rotary	20p	
1	2	Toggle	10p	

COMPUTER AND AUDIO BOARDS
CONTAINING A SELECTION OF REASONABLE LEAD TRANSISTORS, SOME POWER, SILICON, GERMANIUM, ZENER DIODES, POT CORES HI-STAB RESISTORS, SOME WIREWOUND, CONDENSERS, CHOKES, TRIMPOTS, ELECTROLYTICS, ETC.
3lb. for 75p + 30p post and packing
7lb. for £1.50 + 60p post and packing

SKELETON PRESETS
SLIDER, HORIZONTAL OR VERTICAL STANDARD OR SUBMIN. 6p

KNOB
SILVER METAL PUSH ON WITH POINTER, OR WHITE PLASTIC, GRUB SCREW, WITH POINTER AND SILVER CENTRE 10p EACH.

ZM1162A INDICATOR TUBE
0-9 Inline End View. Rectangular Envelope 170V 25M/A £3.60

RESETTABLE COUNTER
English Numbering Machines LTD.
MODEL 4436-159-989
6-14 volt, 6 digit, illuminated, fully enclosed. £2.50

TO3 Mica Washer 2p
18 volt 4 amp charger, bridge rectifies 60p
GC10/4B Cold Cathode £5.00
Brand New Boxed 6K7G 25p

ELECTROLYTICS MFD/VOLT. Many others in stock

5p. 1/75, 2/75, 2.5/64, 4/60, 5/50, 6/3, 6/25, 8/6, 8/40, 8/50, 8/150, 12/50, 15/35, 16/40, 16/50, 20/12, 25/3, 25/6, 25/12, 25/25, 25/30, 50/10, 50/12, 50/25, 50/50, 64/10, 100/6, 100/12, 100/15, 100/18, 100/25, 125/10, 150/12, 150/25, 200/3, 250/6, 200/12, 500/6.	30, 260/12, 330/10, 9p. 400/16, 550/12, 20p. 8/500, 16/450, 100/200, 100/250-275, 16-32/275, 32-32/275, 100-100/150, 100-100/275. 50-50/300: Solid Tantalum, 8/20, 10/20, 12/20. 50p. 8/800, 2000/50, 12,000/12, 32-32-50/300.
6p. 1/350, 2/350, 150/40, 250/18, 250/	£1,100-100-100-150-150/320.

INDICATORS

Arcoelectric green, takes M.E.S. bulb	20p
Bulgin D676 red, takes M.E.S. bulb	20p
12 volt red, small pushfit	20p
Mains neon, red. pushfit	20p

CAPACITORS

Mixed type PFDS, 2p. 1, 3.3, 4.7, 5.6, 10, 12, 15, 16, 18, 20, 22, 24, 25, 27, 30, 33, 37, 39, 47, 50, 56, 68, 88, 100, 110, 120, 150, 200, 220, 250, 300, 330, 470, 500, 600, 680, 800, 1000, 2200, 3000, 3300, 5000.	
Poly, met., film, paper, etc. MFD/Volt, 3p. .001/1250, .005/250, .03/350, .03/12, .03/200, .033/100, .0068/70, .056/350, .061/035, .069/350, .075/350, .08/350, .1/350, .1/500, .13/350, .25/150.	
4p. 1500, 1800, 2200, 3000, 3300, 6800, 8200 PFD. .01/350, .013/350, .05/125, .05/250, .068/200 .25/350.	
5p. .033/100, .1/250, .5/350.	
6p. .1/600, .1/1500, .22/250, .5/250	
10p. .01/1000, 1/350, 8/20, .1/900, .22/900, 4/16, .25/250 AC (600VDC)	
40p. 5/150, 9/275AC, 10/150, 15/150, 40/150.	

TRIMMERS, 20p each

100PF Ceramic, 30PF Beehive, 12PF PTFE	
2500PF 750 volt, 33PF MIN. AIR SPACED	
5PF, MIN. AIR SPACED, 50PF CERAMIC.	

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 3p each	
---	--

CAN CLIPS

1" or 1½" or 3"	2p
LABGEAR MAINS DROPPER	
36 ohm 25 watt + 79 ohm 9 watt	25p

TUNING CONDENSERS 50PF, 50p

2 Amp Suppression Choke	5p
---------------------------------	----

PAXOLINE

3 x 2½ x 1½"	2p
4½ x 1½ x 1½"	2 for 1p
220K 3 watt resistors	2p
100 ohm 3 watt resistor	4p
VALVE RETAINER CLIP, adjustable	2p
OUTPUT TRANSFORMERS	
Sub-miniature Transistor Type	25p
Valve type, centre tapped or straight	40p

3 pin din to open end, 1½yd twin screened lead 35p

Whiteley Stentorian 3 ohm constant impedance volume control way below trade at £1

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 7 p.m. Monday to Saturday also most Sundays.

Phone 01-223 5016

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AC107 .. 15p	BC148A/B, 9B/C .. 12p	BF115 .. 20p
AC127/8 .. 12p	BC157/8/9 .. 9p	BF167/173 .. 25p
AC188 .. 12p	BC158A/B .. 15p	BF178/9 .. 30p
AC128 .. 18½p	BC159C, 157A .. 15p	BF180/1 .. 25p
AD149 .. 40p	BC178A/B .. 16p	BF182/3 .. 40p
AD162 .. 33p	BC179B .. 22p	BF184 .. 17p
AF116/7 .. 13p	BC186/7 .. 25p	BF185 .. 22p
AF124/6/7 .. 20p	BC213L .. 11p	BF194/5 .. 10p
AF139 .. 30p	BC337/8 .. 19p	BF194A .. 14p
AF178 .. 30p	BC547 .. 12p	BF196/7 .. 13p
AF180/1 .. 45p	BC558A .. 12p	BF200 .. 25p
AF239 .. 38p	BCY40 .. 87p	BF262/3 .. 23p
ASY27 .. 30p	BCY70/1/2 .. 12p	BF336 .. 28p
ASY73 .. 26p	BD112/3 .. 52p	BFX29/30 .. 27p
BC107A or B .. 13p	BD115/6 .. 55p	BFX84/88 .. 22p
BC107/8/9 .. 9p	BD131/2 .. 35p	BFY50/1/2 .. 16p
BC108A/B .. 13p	BD135 .. 37p	BFY90 .. 60p
BC109B .. 18p	BD203 .. £1.41	BR101 .. 35p
BC147/8/9 .. 7p	BD232 .. 75p	BSV64 .. 50p
BC147A/B .. 13p	BD234/5 .. 75p	BSX21 .. 20p

BRIDGE RECTIFIERS

Amp	Volt RMS		Amp	Volt RMS	
½	1,600	BYX10 .. 30p	2	30	LT120 .. 30p
1	140	OSH01-200 .. 38p	0.6	6-110	EC433
1.4	42	BY164 .. 50p	Encapsulated with built-in heat sink .. 15p		

1 AMP RECTIFIERS

IN4003 .. 200 volt .. 5p
IN4004 .. 400 volt .. 6p
IN4005 .. 600 volt .. 7p
IN4006 .. 800 volt .. 8p
IN4007 .. 1,000 volt .. 8p

HIGH POWER RECTIFIERS

	Amp	Volt	
SR100 .. 1.5	100	7p	
SR400 .. 1.5	400	8p	
LT102 .. 2	30	10p	
BYX38-600 .. 2.5	600	48p	
BYX38-300R .. 2.5	300	42p	
BYX38-900 .. 2.5	900	54p	
BYX38-1200 .. 2.5	1,200	62p	
BYX49-600 .. 2.5	600	34p	
BYX49-300 .. 2.5	300	26p	
BYX49-900 .. 2.5	900	40p	
BYX49-1200 .. 2.5	1,200	52p	
BYX48-300 .. 6	300	40p	
BYX48-600 .. 6	600	50p	
BYX48-900 .. 6	900	60p	
BYX48-1200 .. 6	1,200	80p	
BYX72-150R .. 10	150	35p	
BYX72-300R .. 10	300	45p	
BYX72-500R .. 10	500	55p	
BYX42-300 .. 10	300	45p	
BYX42-600 .. 10	600	65p	
BYX42-900 .. 10	900	80p	
BYX42-1200 .. 10	1,200	95p	
BYX46-300* .. 15	300	£2.90	
BYX46-400* .. 15	400	£3.20	
BYX46-500* .. 15	500	£3.60	
BYX46-600* .. 15	600	£3.90	
BYX20-200 .. 25	200	60p	
BYX52-300 .. 40	300	£1.75	
BYX52-1200 .. 40	1,200	£3.00	

*Avalanche type

RG4-1250 Mercury vapour rectifier .. £8.00
1" Terryclips chrome finish .. 4p
Cinch 10-way terminal block .. 15p
Pair of LA2407 Ferro cores with adjuster .. 25p
Chrome Car Radio fascia .. 15p
Rubber Car Radio gasket .. 10p
DLI Pal Delayline .. £1.40
Relay socket .. 12p
Take miniature 2PCO relay
B7G or B9A valve can .. 2p
0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive, 4½" dia. .. 15p

OPTO ELECTRONICS

ORP12 .. 44p	Photo transistor
BPX40 .. 65p	BPX29 .. £1.40
BPX42 .. £2.48	OCY11 .. 35p
BPY10 .. £1.50	BIG L.E.D. 4½mm 2v 50mA max. RED .. 18p
(VOLTAGE)	ORANGE .. 31p
BPY68 .. £1.60	GREEN .. 31p
BPY69 .. £2.60	YELLOW .. 33p
BPY77 .. £2.60	

PNP PROGRAMMABLE UNIJUNCTION BRY39

F.E.T.'s

BFW10 .. 55p
BSV79 .. £1.30
BSV80 .. £1.10
N. Channel
BSV81 M.O.S.T. .. £1.56
BFS28 Dual M.O.S.T. 92p

Plastic, Transistor or Diode Holder .. 1p
 Transistor or Diode Pad 1p
 Holders or pads 50pper100

Philips Iron Thermostat .. 15p
Bulgin 2-pin flat plug and socket .. 10p
McMurdo PP108 8 way edge plug 15p
TO3 HEATSINK
Eurolec HP1 TO3B individual 'curly' power transistor type. Ready drilled 20p

Tested unmarked or marked ample lead ex new equipment

ACY17-20 .. 8p	OC71/2 .. 6p
ASZ20 .. 8p	OC200-5 .. 15p
ASZ21 .. 15p	TIC44 .. 24p
BC186 .. 11p	2G240 .. 2-50
BCY30-34 .. 10p	2G302 .. 6p
BCY70/1/2 .. 8p	2G401 .. 10p
BF115 .. 10p	2N711 .. 25p
BY127 .. 8p	2N2926 .. 7p
BZY88 series .. 5p	2N598/9 .. 6p
HG1005 .. 4p	2N1091 .. 8p
HG5009 .. 4p	2N1302 .. 8p
HG5079 .. 4p	2N1907 .. 2-50
L78/9 .. 4p	Germ. diode 2p
M3 .. 10p	GET120 (AC128 in 1" sq. heat sink) .. 20p
OA81 .. 4p	GET872 .. 12p
OA47 .. 4p	
OA200-2 .. 4p	
OC23 .. 20p	

BU105/01 .. £1.75	2N706 .. 8p
CA3001 .. £2.50	2N987 .. 42p
CV7042 (OC41 OC44, ASY63) .. 12p	2N1091 .. 55p
GET111 .. 72p	2N1302 .. 15p
MA393 .. 50p	2N2219 .. 20p
OC35 .. 40p	2N2401 (ASY26-27) .. 25p
TAA570 .. £1.39	2N2904/5 .. 18p
TAD100 .. £1.42	2N2906 .. 13p
2G302 .. 19p	2N2907 .. 20p
2N393 .. 50p	2N3053 .. 14p
	2N3055 (992) .. 39p

Amp	Volt	THYRISTORS	
1	240	BTX18-200 .. 75p	
1	400	BTX18-300 .. 85p	
1	240	BTX30-200 .. 40p	
6.5	500	BT102-500R .. £1.12	
10	700	BT106 .. 99p	
15	500	BT107 .. £1.20	
6.5	500	BT101-500R .. £1.15	
6.5	500	BT109-500R .. 90p	
20	600	BTW92-600RM .. £3.90	
15	800	BTX95-800R Pulse Modulated .. £18.00	

OTHER DIODES

IN916 .. 6p	BA182 .. 24p
IN4148 .. 4p	OA5/7/10 .. 20p
BA145 .. 14p	BZY88 Up to 15 volt .. 7p
Centercel .. 10p	BZX61 11 volt .. 17p
BZY61 .. 10p	BR100 Diac .. 23p

TRIACS

Amp	Volt	
6	400	Plastic .. 90p
25	900	BTX94-900 .. £7.50
25	1200	BTX94-1200 .. £10.20

CQY11B L.E.D. Infra red transmitter One fifth of trade .. £1	WESTINGHOUSE 28T10 30 AMP 1000VOLT THYRISTER WITHOUT NUT .. £5
--	--

PHOTO SILICON CONTROLLED SWITCH
 BPX66 PNP 10 amp .. £1.50

PAPER BLOCK CONDENSER

0.25MFD .. 800 volt .. 30p
1MFD .. 250 volt .. 15p
2MFD .. 250 volt .. 20p
2MFD .. 1.5 kv .. 50p
4MFD .. 250 volt .. 20p
15MFD .. 150 volt .. 50p

METAL CHASSIS SOCKETS

Car Aerial .. 7p
Coax .. 7p
5 or 6 pin 240° din .. 7p
Speaker din switched .. 7p
3.5mm Switched Socket .. 7p

ZN 414 AM RADIO IC £1.00

8 way Cinch standard 0.15 pitch edge socket 20p

U.E.C.L. 10 way pin connector 2B6000 OA1P10 .. 20p

U.E.C.L. 20 way pin connector 2A60000A1P20 .. 30p

U.E.C.L. 10 way pin socket 2B606001R10 .. 20p

U.E.C.L. 20 way pin socket 2B60800A1R20 .. 30p

BELLING LEE L1354 TV Aerial diplexer 10p

Philips electronic engineer kits add on series A20, E1004, E1005 £1.00 each (parts worth more)

TAA300 T0-74 1 Watt A.F. AMPLIFIER I.C. 4-5 to 9v £1.46

5lb New Mixed Components £2 plus 50p p & p

HANDLES
 Rigid light blue nylon 6½" with secret fitting screws .. 5p

Rotor with neon indicator, as used in Seafarer, Pacific, Fairway depth finders 20p each

Miniature Axial Lead Ferrite Choke formers 2p

DEE PLUG
 McMurdo DA15P 15 way chassis plug 20p

Fairway 18009 Coax. socket .. 5p

TIE CLIPS
 Nylon self locking 7" .. 2p

CINCH 150
 12 way edge socket .. 10p

1lb Mixed nuts, bolts, washers etc. 35p

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE
LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.
TOTAL GOODS PLUS CARRIAGE, ADD 8% V.A.T.

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11
 Open 10 a.m. till 7 p.m. Monday to Saturday
 'also most Sundays' Phone 01-223 5016

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.50. 3 for ONLY 55p + P. & P. 30p.
SPECIAL one as above PLUS Power Transistors ONLY 55p each + P. & P. 15p.
PAXOLINE BOARDS 7½ x 9" approx. 4 for 30p + P. & P. 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16½ x 4" approx. 2 for 55p

DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen 99p each.

VEROBOARDS

Packs containing approx. 50sq. in. various sizes, all 0-1 matrix 55p

REPANCO CHOKES & COILS

RF Chokes
CH1. 2.5mH 29p CH2. 5.0mH 30p
CH3. 7.5mH 31p CH4. 10mH 33p
CH5. 105mH 28p
COILS
DRX1 Crystal set 31p DR R2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 8p
1" Cores & Formers 10p

SWITCHES

DP/DT Toggle 36p SP/ST Toggle 30p

FUSES

1½ and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A.
QUICK-BLOW 5p each.

EARPHONES

Crystal 2.5mm plug 42p
Crystal 3.5mm plug 42p
8 ohms 2.5mm plug 22p
8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.85

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB £1.21

CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

BI-PAK

CATALOGUE AND LISTS
Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	6"	2"	£1.10
BV2	11"	6"	3"	£1.45

ALUMINIUM BOXES

BA1	5½"	4"	2½"	42p
BA2	4"	4"	1½"	45p
BA3	4"	4"	1½"	42p
BA4	5½"	4"	1½"	50p
BA5	4"	2½"	2"	42p
BA6	3"	2"	1"	34p
BA7	7"	5"	2½"	70p
BA8	8"	6"	3"	90p
BA9	6"	4"	2"	58p

P. & P. 10p on each box

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Sat. 9-5.30 p.m. Tel. 61593

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1.95

Chrome Finish

Model 60 £1.50



Ref. 36A. Record/Stylus Cleaning Kit 33p
Ref. 43. Record Care Kit £2.42
Ref. 31. Cassette Head Cleaner 58p
Ref. 32. Tape editing Kit £1.68
Model 9. Wire Stripper/Cutter 83p
Ref. 46. Spirit Level 62p

Ref. B. Stylus and Turntable Cleaning Kit 34p
Ref. P. Hi-Fi Cleaner 31p
Ref. 32A. Stylus Balance £1.37
Ref. J. Tape Head Cleaning Kit 62p
Ref. 56. Hi-Fi Stereo Hints and Tips 42p
Ref. 45. Auto Changer Groove Cleaner £1.08

ANTEX SOLDERING IRONS

X25. 25 watt £2.05
CCN 240. 15 watt £2.48
Model G. 18 watt £2.26
SK2. Soldering Kit £3.25
STANDS: ST3, suitable for all models £1
SOLDER: 18SWG Multicore 7oz £1.61
22SWG 7oz £1.61. 18SWG 22ft 51p
22SWG Tube 33p

ANTEX BITS and ELEMENTS

Bits No.
102 For model CN240 42p
104 For model CCN240 42p
1100 For model CCN240 42p
1101 For model CCN240 42p
1102 For model CCN240 42p
1020 For model G240 42p
1021 For model G240 42p
1022 For model G240 42p
50 For model X25 48p
51 For model X25 48p
52 For model X25 48p

ELEMENTS

ECN 240 £1.30 ECCN 240 £1.32
EG 240 £1.07 EX 25 £1.16

ANTEX HEAT SINKS 10p

VAT included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack	No. Qty.	Description	Price
C1	200	Resistors mixed values approx. count by weight	0.55
C2	150	Capacitors mixed values approx. count by weight	0.55
C3	50	Precision Resistors 0-1%, 0-01% mixed values	0.55
C4	75	¼W Resistors mixed preferred values	0.55
C5	5	Pieces assorted Ferrite Rods	0.55
C6	2	Tuning Gans, MW/LW VHF	0.55
C7	1	Pack Wire 50 metres assorted colours	0.55
C8	10	Reed Switches	0.55
C9	3	Micro Switches	0.55
C10	15	Assorted Pots & Pre-Sets	0.55
C11	5	Jack Sockets 3 x 3.5m 2 x Standard Switch Type	0.55
C12	30	Paper Condensers preferred types mixed values	0.55
C13	20	Electrolytic Trans. types	0.55
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets, etc.	0.55
C15	5	Mains Slide Switches	0.55
C16	20	Assorted Tag Strips & Panels	0.55
C17	10	Assorted Control Knobs	0.55
C18	4	Rotary Wave Change Switches	0.55
C19	2	Relays 6—24V Operating	0.55
C20	1	Pack Sheets of Copper Laminate approx. 20 sq. ins.	0.55

PLUGS AND SOCKETS PLUGS

PS 1	D.I.N. 2 Pin (Speaker)	0.11
PS 2	D.I.N. 3 Pin	0.12
PS 3	D.I.N. 4 Pin	0.15
PS 4	D.I.N. 5 Pin 180°	0.16
PS 5	D.I.N. 5 Pin 240°	0.16
PS 6	D.I.N. 6 Pin	0.17
PS 7	D.I.N. 7 Pin	0.18
PS 8	Jack 2.5mm Screened	0.18
PS 9	Jack 3.5mm Plastic	0.12
PS 10	Jack 3.5mm Screened	0.18
PS 11	Jack 1" Plastic	0.15
PS 12	Jack 1" Screened	0.22
PS 13	Jack Stereo Screened	0.36
PS 14	Phono	0.10
PS 15	Car Aerial	0.22
PS 16	Co-Axial	0.15

INLINE SOCKETS

PS 21	D.I.N. 2 Pin (Speaker)	0.14
PS 22	D.I.N. 3 Pin	0.20
PS 23	D.I.N. 5 Pin 180°	0.20
PS 24	D.I.N. 5 Pin 240°	0.20
PS 25	Jack 2.5mm Plastic	0.16
PS 26	Jack 3.5mm Plastic	0.16
PS 27	Jack 1" Plastic	0.30
PS 28	Jack 1" Screened	0.35
PS 29	Jack Stereo Plastic	0.30
PS 30	Jack Stereo Screened	0.38
PS 31	Phono Screened	0.18
PS 32	Car Aerial	0.22
PS 33	Co-Axial	0.22

SOCKETS

PS 35	D.I.N. 2 Pin (Speaker)	0.08
PS 36	D.I.N. 3 Pin	0.11
PS 37	D.I.N. 5 Pin 180°	0.11
PS 38	D.I.N. 5 Pin 240°	0.11
PS 39	Jack 2.5mm Switched	0.12
PS 40	Jack 3.5mm Switched	0.12
PS 41	Jack 1" Switched	0.20
PS 42	Jack Stereo Switched	0.30
PS 43	Phono Single	0.08
PS 44	Phono Double	0.10
PS 46	Co-Axial Surface	0.10
PS 47	Co-Axial Flush	0.20

LEADS

LS 1 Speaker Lead 2 pin D.I.N. plug to open ends approx 3 metres long (coded) 0.20

CABLES

CP 1	Single Lapped Screen	0.07
CP 2	Twin Common Screen	0.11
CP 3	Stereo Screened	0.12
CP 4	Four Core Common Screen	0.23
CP 5	Four Core Individually Screened	0.30
CP 6	Microphone Fully Braided Cable	0.10
CP 7	Three Core Mains Cable	0.09
CP 8	Twin Oval Mains Cable	0.07
CP 9	Speaker Cable	0.05
CP 10	Low Loss Co-Axial	0.18

CARBON POTENTIOMETERS

Long and Lin
47K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M.
VC 1 Single Less Switch 0.15
VC 2 Single D.P. Switch 0.28
VC 3 Tandem Less Switch 0.46
VC 4 1K Lin Less Switch 0.15
VC 5 10K anti-Log 0.46

HORIZONTAL CARBON PRE-SETS

0.1 watt 0.06 each
100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M.

IT'S NEW

IT'S POWERFUL
(15 15w R.M.S.) AND—
IT LOOKS GOOD!

THE
LEGIONAIRE
STEREO
AMPLIFIER



ORDER NOW—

ONLY £39.95 p. 8 p. 50p
OR Write for full details

WORLD SCOOP JUMBO SEMICONDUCTOR PACK

Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, ICs and Zeners. ALL NEW AND CODED.

APPROX 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak

Only £2 p. 8 p. 20p

RECORD STORAGE/ CARRY CASES

7in EP. 18½in x 7in x 8in (50 records) £2.10
12in LP. 13½in x 7½in x 12½in (50 records) £2.95

CASSETTE CASES

Holds 12 10in x 3½in x 5in. Lock and handle, £1.30

SPECIAL PURCHASE

2N3055. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one able! 11W, T03, Metal Case.
OUR SPECIAL PRICE 8 for £1

LOW COST CAPACITORS

0.01 µF 400V. 3p each
500µF 50V. Elect. 10p each

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tappings 4V, 7V, 8V, 10V, 14V, 15V, 17V, 19V, 21V, 25V, 31V, 33V, 40, 50V and 25V/0-25V.

Type	Amps	Price	P. & P.
MT50/1	4	£1.93	30p
MT50/1	1	£2.42	35p
MT50/2	2	£3.30	40p

CARTRIDGES

ACOS
GP91-1SC 200mV at 1.2cm/sec £1.35
GP98-1 280mV at 1cm/sec £1.85
GP96-1 100mV at 1cm/sec £2.80
J-2005 Crystal/Hi Output £1.05
J-2000C Crystal/Hi Output Compatible £1.20
J-2005S Stereo/Hi Output £1.75
J-2105 Ceramic/Med Output £1.95
J-2203 Magnetic 5mV/5cm/sec, including stylus £4.95
J-2203S Replacement stylus for above £3.00
AT55 Audio Technica magnetic cartridge 4mV/5cm/sec £3.30

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, ½ watt available in PAKS of 50 pieces, assorted into the following groups:
R1 50 Mixed 100 ohms-820 ohms 50p
R2 50 Mixed 1k 0-8.2k 0 50p
R3 50 Mixed 10k 0-82k 0 50p
R4 50 Mixed 100k 0-1M 0 50p
THESE ARE UNBEATABLE PRICES—JUST 1p EACH INCL. V.A.T.

BI-PAK SUPERIOR QUALITY

LOW - NOISE CASSETTES

C60, 36p; C90, 48p; C120, 60p

- the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10 AL20 AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po 3 WATTS f 1KHz	0.25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	f = 1KHz	100 k Ω
FREQUENCY RESPONSE -3dB	Po 2 WATTS	50 Hz-25KHz
SENSITIVITY for RATED O/P	Vs = 25V. R1 8Ω f = 1KHz	75mV. RMS
DIMENSIONS	—	3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power out for 2% T.H.D. (RL = 8Ω f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts	£2.50
AL 20. 5 watts	£2.85
AL 30. 10 watts	£3.20

POWER SUPPLIES

PS 12. (Use with AL10, AL20, AL30)	88p
SPM 80. (Use with AL30)	£3.25
FRONT PANELS PA 12 with Knobs	£1.00

PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20)	£4.35
PA 100. (Use with AL30 & AL60)	£13.15

TRANSFORMERS

T461. (Use with AL10)	£1.38 P. & P. 15p
T538. (Use with AL20, AL30)	£1.93 P. & P. 15p
BMT80. (Use with AL60)	£2.15 P. & P. 25p

PA12 PRE-AMPLIFIER SPECIFICATION

The PA12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with *Ceramic cartridges while the auxiliary input will suit most †Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 35mm.

Frequency response—
20Hz-20KHz (-3dB)
Bass control—
± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
†input 2. Impedance
30 K Ohms
Sensitivity 4mV

Look for our

SEMICONDUCTOR ADVERTISEMENTS in

Practical Wireless Wireless World Practical Electronics

ALL PRICES INCLUDE V.A.T.

The STEREO 20

The "Stereo 20" amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch, volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The "Stereo 20" has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14kHz.

£14.45



TC20 TEAK VENEERED CABINET

For Stereo 20 (front board undrilled) Size 10 1/2" x 8 1/2" x 3". £3.95 plus 30p postage.

SPM80 STEREO HEADPHONES

4-16 ohms impedance. Frequency response 20 to 20,000Hz. Stereo/mono switch and volume controls, £4.95

NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £3-95




- Max Heat Sink temp 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 1KHz
- Supply voltage 15-50 volts

- Thermal Feedback
- Latest Design Improvements
- Load — 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

STABILISED POWER MODULE SPM80

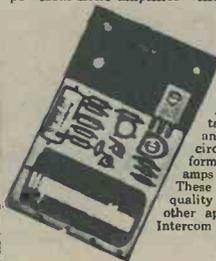

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disc Systems, Public Address, Intercom Units, etc. Handbook available 10p PRICE £3-25

TRANSFORMER BMT80 £2-15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATIONS

Frequency Response
Harmonic Distortion
Inputs: 1. Tape Head
2. Radio, Tuner
3. Magnetic P.U.
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.
Base Control
Treble Control
Filters: Rumble (High Pass)
Scratch (Low Pass)
Signal/Noise Ratio
Input overload
Supply
Dimensions

20Hz-20KHz ± 1dB
better than 0.1%
3-25 mV into 50KΩ
75 mV into 50KΩ
3 mV into 50KΩ

± 15dB at 20Hz
± 16dB at 20KHz
100Hz
8KHz

better than -65dB
+ 26dB
+ 35 volts at 20mA
292mm x 82mm x 35mm

ONLY £13-15

MK 60 AUDIO KIT

Comprising: 2 x AL60, 1 x SPM80, 1 x BMT80, 1 x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £28.75 plus 30p postage.

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets, etc. Kit price: £9.95 plus 30p postage.

All prices quoted in new pence Giro No 388 7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p Overseas add extra for airmail
Minimum order 50p. Cash with order please

Guaranteed Satisfaction or Money Back


DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	.. 24p
DTB4 Transistor & Valve circuitry for D.P. Coils	.. 24p
DTB9 Valve Type Coil Pack Application circuitry	.. 24p
MD 1 Decoder Circuitry for Stereo Reception	... 24p

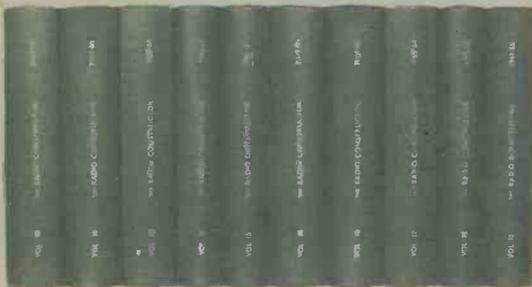All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers



LATEST BOUND VOLUME

No. 27

of
"Radio & Electronics
Constructor"

FOR YOUR LIBRARY

PRICE £2.20 P&P 33p

Comprising
772 pages
inc. index

AUGUST 1973
to JULY 1974

BOUND VOLUME No. 24 (August 1970 to July 1971)	PRICE £2.00 p. & p. 33p
BOUND VOLUME No. 25 (August 1971 to July 1972)	PRICE £2.00 p. & p. 33p
BOUND VOLUME No. 26 (August 1972 to July 1973)	PRICE £2.10 p. & p. 33p

Limited number of these volumes still available

We regret all earlier volumes are now completely sold out.
Available only from

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W9 1SN

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



12 Watt stereo amp
 Only **£10** 45p SPECIAL OFFER P. & P. LIMITED QUANTITY

This excellent little amplifier is of the latest integrated circuit design, and will work into 4, 8, or 16 ohm speakers. The reproduction is excellent for an amplifier of this size. Only 8" x 3 1/2" x 2". The case is made of chromed metal.

Tested and Guaranteed Paks



B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, 1" long, 3/8" dia. High speed P.O. type	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.	50p
H38	30	Short lead Transistors, NPN Silicon Planar types.	50p
H41	2	Sil Power transistors comp pair BD131/132	50p
H63	4	2N3055 Type NPN Sil. power transistors. Below spec. devices	50p
H64	4	3819 N Channel F.E.T.'s 2N3819 in plastic case	50p
H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66	50p
H66	4	40362 Type PNP Sil. transistors TO-5 can comp. to H65	50p
H69	8	Integrated Circuits DTL data supplied. Mbed Types, Flip Flops, Gates, Hex Invertors etc.	50p



Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	50p
B66	150	Germanium Diodes Min. glass type	50p
B83	200	Transistors, manufacturers rejects, AF, RF, Silicon and Germanium	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
H34	15	Power Transistors, PNP, Germ NPN Silicon TO-3 Can.	50p
H67	10	3819 N Channel F.E.T.'s plastic case type	50p
H68	10	Experimenters Pak of Integrated Circuits. Data supplied DTL & TTL, some marked	50p

Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any O-lm.A. meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.00 each

Telephone dials

Standard Post Office type. Guaranteed in working order. only 25p P. & P.

Electronic Transistor Ignition £6.00

Now in kit form, we offer this "up to the minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

New X-Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available

Essential for alignment of colour guns on all colour T.V. receivers.

Featuring plug-in IC's and a more sensitive sync. pick-up circuit, the case is virtually unbreakable - ideal for the engineer's tool box - and only measures 3" x 5 1/2" x 3"

Ready built unit only **£9.95** Complete Kit **£7.95** (and p&p but no batteries)



LM 380 AUDIO IC

We have just received a large consignment of LM380 IC's. These are specially selected to a higher grade and are marked with the number SL 60745.

This fantastic little 3 watt audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special price **£1.00** ea complete with data and projects book

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular 4p Transistors

TYPE "A" PNP Silicon alloy, TO-5 can.
 TYPE "B" PNP Silicon, plastic encapsulation.
 TYPE "E" PNP Germanium AF or RF.
 TYPE "F" NPN Silicon plastic encapsulation.
 TYPE "G" NPN Silicon similar ZTX 300 range

8 RELAYS for £1.00 p. & p. Various types 27p.

UHF TV Tuner Units

for 625 line channels 21 to 65

Brand new by a famous manufacturer

Data supplied **£2.50**

Plastic Power Transistors



40 WATT SILICON

Type No.	Gain	VCE	Polarity	Price
40N1	15	15	NPN	20p
40N2	40	40	NPN	30p
40P1	15	15	PNP	20p
40P2	40	40	PNP	30p

90 WATT SILICON

90N1	15	15	NPN	25p
90N2	40	40	NPN	35p
90P1	15	15	PNP	25p
90P2	40	40	PNP	35p

L.E.D.'s Complete with mounting grommet
 Red 25p Green 40p

INTEGRATED CIRCUITS

We stock a large range of I.C.'s at very competitive prices. These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights etc. Pocket Size 12p Wall Chart 18p

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low profile type
 16 pin type at 17p each

BOOKS

We have a large selection of Reference and Technical Books in stock.

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. only **50p**

Please send me the FREE Bi-Pre-Pak Catalogue

I enclose large SAE with 5p stamp

NAME

ADDRESS

Please add V.A.T. at current rate

MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 15p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co Reg No B20919

Dept.C. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
 TELEPHONE: SOUTHEND (0702) 46344.

Goodbye to the long wait



for electronic components.

Now there's Doram— a completely professional electronics service for the amateur.



7-day service.

If you've been buying electronic components long you'll know all about the long wait.

Somehow the things you really need never turn up on time.

Well, OK, now things have changed. Now there's Doram.

Doram is a brand-new deal for serious amateurs. It's a complete door-to-door components service operated by mail order.

Millions of components.

You just buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint of lager) and then you order from it.

We can offer you stocks of millions of components. With a choice of over 4,000 different lines.

And we're so confident of our service that if we can't supply the part you want within 7 days of receiving your order, we'll give you your money back. Immediately.

So you know just where you stand. You'll never waste time hanging around while we re-order.

No-quibble guarantee.

It's just about impossible to buy a defective part from us. Because our checking is so pains-taking.

But even if the unthinkable does happen—and you're unlucky—then

**I ENCLOSE 25p*. PLEASE SEND
ME THE NEW DORAM
CATALOGUE.**

*This will be refunded on orders of £5 (less VAT) or more received by us before 31st March, 1975.

Name _____

Address _____

REC/11/74

Doram Electronics Ltd.,
PO Box TR8,
Wellington Road Industrial Estate,
Wellington Bridge, Leeds LS12 2UF.

DORAM

we'll still make you happy quickly.


Because we offer a no-quibble replacement part service.

And our guarantee is guaranteed by the fact that we belong to the biggest electronics distribution Group in Britain.

All the goods supplied are branded goods. Produced by big-name manufacturers like RS, Mullard, SGS-ATES, Ferranti, Siemens etc.

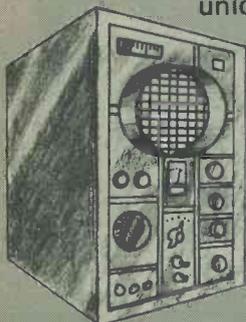1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

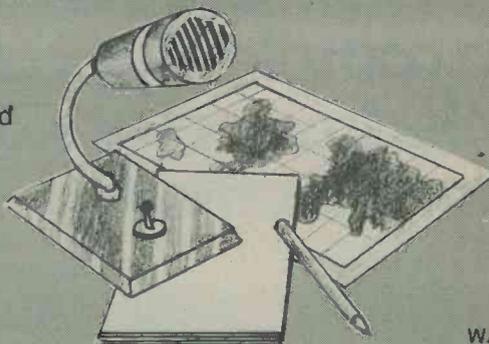2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



WAA

Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept AX 1274
 P.O. Box 156, Jersey; Channel Islands.

NAME _____

ADDRESS _____ Block caps please

THE MODERN BOOK CO

UNDERSTANDING IC OPERATIONAL AMPLIFIERS

By R. Melen & H. Garland Price £2.15

COLOUR T.V. WITH PARTICULAR REF. TO THE PAL SYSTEM PRICE £5.10
 by G. N. Patchett

TRANSISTOR RADIO SERVICING MADE EASY by W. Lemons PRICE £1.70

BEGINNER'S GUIDE TO COLOUR T.V. PRICE £2.70
 By G. J. King

BEGINNER'S GUIDE TO ELECTRONICS PRICE £2.10
 By T. L. Squires

SIMPLE TRANSISTOR PROJECTS FOR HOBBYISTS AND STUDENTS PRICE £1.40
 By L. Steckler

MULLARD DATA BOOK 1974/5 PRICE 50p

TRANSISTOR MANUAL By G.E. PRICE £1.30

BASIC THEORY AND APPLICATION OF TRANSISTORS PRICE £1.60
 By U.S. Dept. of the Army

ESSENTIAL FORMULAE FOR ELECTRONIC AND ELECTRICAL ENGINEERS PRICE £1.00
 By N. M. Morris

SIMPLE SINGLE CHANNEL RADIO

CONTROL by R. H. Warring PRICE £1.65

TROUBLESHOOTING WITH THE OSCILLOSCOPE PRICE £1.95
 By R. G. Middleton

INTEGRATED CIRCUITS (IC'S) AND TRANSISTOR GADGETS CONSTRUCTION HANDBOOK By B. B. Babani PRICE 70p

ELECTRONIC HOBBYIST'S IC PROJECTS HANDBOOK By B. Brown PRICE £1.55

T.V. SERVICING HANDBOOK PRICE £4.05
 By G. J. King

ELECTRONICS AN ELEMENTARY INTRO. FOR BEGINNERS By L. W. Owers PRICE £1.60

FOUNDATIONS OF WIRELESS AND ELECTRONICS By M. G. Scroggie PRICE £2.00

TEST EQUIPMENT FOR THE RADIO AMATEUR By H. L. Gibson PRICE £2.00

JAPANESE RADIO, RECORD AND TAPE PLAYER SCHEMATIC/SERVICING MANUAL PRICE £2.10
 By H. Davidson

ALL PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm	£7.75
Baker Group 35, 3, 8 or 15 ohm	£8.50
Baker Group 50/12, 8 or 15 ohm	£12.50
Baker Deluxe 12", 8 or 15 ohm	£10.75
Baker Major 3, 8 or 15 ohm	£8.50
Baker Superb 8 or 15 ohm	£14.50
Baker Regent 8 or 15 ohm	£7.75
Baker Auditorium 12"	£12.50
Celestion PSTB (for Uniflex)	£2.55
Celestion G12H 8 or 15 ohm	£15.00
Celestion G12M 8 or 15 ohm	£12.00
Celestion G15C 8 or 15 ohm	£24.00
Celestion G18C 8 or 15 ohm	£33.00
Celestion MH1000 8 or 15 ohm	£10.95
Coral 6 1/2" d/cone roll/surr. 8 ohm	£2.50
Coral 6 1/2" (larger magnet) 8 ohm	£3.15
Coral 8" d/cone, roll/surr. 8 ohm	£3.25
EMI 13 x 8, 3, 8 or 15 ohm	£2.25
EMI 13 x 8, d/cone 3, 8 or 15 ohm	£2.50
EMI 13 x 8 t/tw. 3, 8 or 15 ohm	£3.75
EMI 13 x 8 type 350, 8 or 15 ohm	£8.25
EMI 13 x 8 20 watt bass	£6.60
EMI 5" 98132CP 8 ohm	£2.50
EMI 6 1/2" 93850 4 or 8 ohm	£3.00
EMI 8 x 5, cer. mag. 8 ohm	£1.65
EMI 8 x 5, 10 watt, d/c roll/s 8 ohm	£2.50
EMI 10 x 6 93870 8 ohm	£2.25
EMI 2 1/4" tweeter 8 ohm	.65
Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2.80
Elac 6 1/2" d/cone, roll surr. 8 ohm	£3.50
Elac 6 1/2" d/cone 8 ohm	£2.65
Elac TW4 4" tweeter	£1.21
Elac 10" 10RM239 d/c 8 ohm	£2.65
Elac 8" 3 ohm	£2.50
Eagle Crossover 3, 8 or 16 ohm	£1.50
Eagle CT5 cone tweeter 8 ohm	£1.75
Eagle CT10 tweeter 8 or 16 ohm	£2.55
Eagle DT33 dome tweeter 8 ohm	£5.45
Eagle FF5 3 way crossover	£3.15
Eagle SN75 crossover with tw. control	£4.00
Eagle FF28 multicell, horn	£7.75
Eagle HT15 horn tw. 16 ohm	£3.80
Eagle HT21 horn tw. 8 ohm	£5.88
Eagle MHT10 horn tw. 8 ohm	£3.80
Eagle FR4 4" full range	£5.30
Eagle FR65 6 1/2" full range	£8.35
Eagle FR8 8" full range	£10.65
Fane Pop 15 watt 12"	£4.80
Fane Pop 25/2.25 watt 12"	£6.95
Fane Pop 50 watt 12"	£11.00
Fane Pop 55 12" 60 watt	£12.50
Fane Pop 60 watt 15"	£13.00

SPEAKERS

Fane Pop 100 watt 18"	£22.50
Fane Crescendo 12A 8 or 15 ohm	£29.00
Fane Crescendo 12B 8 or 15 ohm	£30.00
Fane Crescendo 15, 8 or 15 ohm	£36.00
Fane Crescendo 18, 8 or 15 ohm	£49.95
Fane 701 twin ribbon horn	£35.00
Fane 910 horn	£12.75
Fane 920 horn	£33.00
Fane 152/12a 15" 15 ohm	£16.00
Fane 801T 8" d/cone roll surr.	£7.00
Fane 803T 8" d/cone roll surr.	£5.25
Fane 805T 8" d/cone roll surr.	£3.50
Fane 808T 8" d/cone	£2.75
Fane 807T 8" d/cone roll surr.	£3.85
Goodmans 8P 8 or 15 ohm	£5.00
Goodmans 10P 8 or 15 ohm	£5.30
Goodmans 12P 8 or 15 ohm	£12.95
Goodmans 12P-D 8 or 15 ohm	£16.75
Goodmans 12P-G 8 or 15 ohm	£15.75
Goodmans 12AX 100 watt 8 or 15 ohm	£36.50
Goodmans 15AX 100 watt 8 or 15 ohm	£40.25
Goodmans 15P 8 or 15 ohm	£21.00
Goodmans 18P 8 or 15 ohm	£35.00
Goodmans Midax 750	£16.00
Goodmans Axent 100 tweeter & crossover	£7.25
Goodmans Audiom 100, 8 or 15 ohm	£12.00
Goodmans Axiom 401, 8 or 15 ohm	£17.25
Goodmans Twinaxiom 8" 8 or 15 ohm	£8.25
Goodmans Twinaxiom 10" 8 or 15 ohm	£9.00
Gauss 12" full range 8 ohm	£69.50
Gauss 12" Bass 8 ohm	£69.50
Gauss 15" full range 8 ohm	£75.00
Gauss 15" Bass 8 ohm	£75.00
Gauss 18" full range 8 ohm	£80.00
Gauss 18" Bass 8 ohm	£80.00
All the above Gauss (American) speakers are fitted with 4 1/2" voice coils and can handle 200 watts RMS.	
Kef T27	£5.25
Kef T15	£6.00
Kef B110	£7.25
Kef B200	£8.25
Kef B139	£14.25
Kef DN8	£2.00
Kef DN12	£4.95
Kef DN13	£3.30
Richard Allan 12" d/cone 3 or 15 ohm	£2.75
Richard Allan CG8T 8" d/c roll surr. 8 ohm	£6.35
STC 4001G super tweeter	£6.19
Wharfedale Super 10RS/DD 8 ohm	£9.80
2 1/2" 64 ohm, 70mm 8 ohm, 70mm 80 ohm	.65
2 1/2" 75 ohm	.50
7" x 4" 3, 8 or 15 ohm	£1.40
8" x 5" 3, 8 or 15 ohm	£1.50
10" x 6" 3, 8 or 15 ohm	£2.30

SPEAKER KITS (Carr. 75p each. £1.50 pair)

Baker Major Module 3, 8 or 15 ohm	each	£10.75
Fane Mode One	each	£9.90
Goodmans DIN 20-4 ohm	each	£9.75
Helme XLK25	pair	£22.00
Helme XLK30	pair	£14.95
Helme XLK50	pair	£39.95
Kefkit 2	each	£24.75
Kefkit 3	each	£36.75
Peerless 3-15 (3 sp. system)	each	£15.00
Richard Allan Twinkit	each	£8.95
Richard Allan Triple 8	each	£13.75
Richard Allan Triple	each	£19.95
Richard Allan Super Triple	each	£23.75
Wharfedale Linton 2 kit	pair	£19.25
Wharfedale Glendale 3 kit	pair	£34.50
Wharfedale Dovedale 3 kit	pair	£52.50

PA/DISCO AMPLIFIERS (Carr. and ins. £1)

Baker Major 100 watt	£49.75
Linear 30/40	£30.00
Linear 40/60	£35.00
Linear 80/100	£58.95
Linear 100 watt slave	£44.00
Eagle PRO A120, 120 watts RMS	£129.00
Eagle PRO A65, 65 watts RMS	£98.50
Eagle PRO A35, 35 watts RMS	£77.00
Eagle TPA40 mains/12v mobile	£50.00
Eagle HH5 36 watts mobile 12v.	£37.50
Eagle TPA20 paging amplifier	£45.00
Eagle RA859 Reverb (p. & p. 75p)	£18.25
Eagle RA856 Reverb (p. & p. 75p)	£12.50

MICROPHONES (p. & p. 50p)

Shure 515 SB	£14.95
Shure 515 SA	£15.75
Shure 545	£29.95

FREE with loudspeaker orders over £7 - "HiFi Loudspeaker Enclosures" book

All items guaranteed new and perfect

Prompt despatch

Carriage: 38p per speaker, 20p per tweeter, crossover or 2 1/2"/70mm speaker, kits 75p each (£1.50 pair)

ALL PRICES QUOTED INCLUDE VAT.

Send stamp for free booklet 'Choosing a speaker'

Big discounts on Grundig, ITT, Koyo, etc. Send stamp for list

WILMSLOW AUDIO

DEPT RC

LOUDSPEAKERS: SWAN WORKS
BANK SQUARE, WILMSLOW, CHESHIRE

AMPLIFIERS, RADIO ETC.

10 SWAN ST., WILMSLOW, CHESHIRE



Agfa Cassettes

Agfa Low Noise Cassettes
AT LESS THAN HALF PRICE!

AGFA HIGHDYNAMIC SUPER

AGFA STEREO-CHROM
CHROMIUM DIOXIDE

SAME DAY DESPATCH
WILMSLOW AUDIO

10 Swan Street, Wilmslow, Cheshire.
SK9 1HF
Cut-price prerecorded cassettes - send stamp for list

The best buy

	1	5	10
C60	37p	£1.80	£3.50
C90	50p	£2.48	£4.95
C120	63p	£3.10	£6.20
	1	5	10
C60+6	50p	£2.40	£4.70
C90+6	68p	£3.35	£6.60
C120	99p	£4.90	£9.90
	1	5	10
C60	85p	£4.20	£8.30
C90	£1.08	£5.35	£10.60



Well here's a fine how d'y do! Santa himself caught in the act of 'borrowing' a few of our catalogues . . . and Rudolph laughing his silly head off! We can't see the old chap getting away with it, but we did warn him to lay in a large stock of catalogues. Well, let's hope he gets bailed out in time to deliver one to you. The demand for this famous components catalogue grows by leaps and bounds each year. We at Home Radio Components work hard on it to make sure it more than comes up to everybody's expectations. If you haven't seen one you really should treat yourself for Christmas. It costs 65 pence plus 33p packing and postage, but with it we give you 14 vouchers, each worth 5p when used as directed. That means you can get 70 pence back. In which case this magnificent publication will have cost you only 28 pence! It can be bought over our counter at Mitcham for only 65p . . . or send the coupon below with a cheque or postal order today for 98 pence. If by any chance Santa Claus is still 'detained for questioning' we'll send your catalogue round by postman!



**A Happy
Christmas
to all our
readers.**

*The price of 98p applies only to customers
in the UK and to BFPO addresses*

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD., Dept. RC,
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd. No.
912966 London

HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422

RADIO & ELECTRONICS CONSTRUCTOR

DECEMBER 1974

Vol. 28 No. 5

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1974. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £3.30 (U.S.A. and Canada \$8.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

CONTENTS

HALF WATT I.C. AMPLIFIER by A. P. Roberts	270
CAN ANYONE HELP?	273
NEWS AND COMMENT	274
'CONSTANT CURRENT' CLASS A AMPLIFIER (Suggested Circuit 289) by G. A. French	276
OSCILLOSCOPE AMPLITUDE CALIBRATOR by A. Foord	280
SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin	284
DIODE 'SORTER-OUTER' by S. M. Peters	286
PULSE COUNTING F.M. TUNER – Part 1 by R. A. Penfold	288
AMSTERDAM RADIO EXHIBITION FIRATO-74	295
BATTERY VOLTAGE MONITOR by G. B. Brown	296
THREE WAVEBAND TRANSISTOR PORTABLE Part 1 by Sir Douglas Hall, K.C.M.G.	297
NOTES FOR NEWCOMERS – ZENER CLIPPING CIRCUITS by K. V. Logan	304
TRADE NEWS	306
IN YOUR WORKSHOP – Circuits and Techniques employed in stereo record players	307
CONSTRUCTOR'S DATA SHEET No. 93 (S.S.C. Wire Coil Lengths)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

The Radio & Electronics Constructor is printed by Carlisle Web Offset.

JANUARY ISSUE WILL BE
PUBLISHED ON 1st JANUARY

HALF WATT



A simple a.f. amplifier which can be assembled around an 8 pin d.i.l. integrated circuit

THIS LITTLE AMPLIFIER CAN BE BUILT ON A SMALL PIECE of 0.1 in. Veroboard having 22 by 9 holes, and it is capable of giving an output of 500mW r.m.s. into an 8Ω load when powered by a 9 volt supply. The amplifier is based on the Motorola MC1306P integrated circuit. This has a built-in pre-amplifier, enabling a variety of gain and input impedance options to be obtained.

The circuit is capable of superior results when compared with many discrete component amplifiers having a similar output power. The typical total harmonic distortion with an output power of 250mW at 1kHz is 0.5%. At 500mW it is typically 5%.

A Class B output stage is used, and the quiescent current drain of the amplifier is only about 4mA. The i.c. contains the equivalent of 14 transistors, 5 diodes and 8 resistors. It is housed in a standard 8 pin d.i.l. package.

I.C. CIRCUITRY

The internal circuit of the MC1306P i.c. is shown in Fig. 1. The input to the pre-amplifier is taken to pin 6. TR1 and TR2 are connected as a common emitter Darlington pair, and offer a high voltage gain.

It is not yet possible to fabricate large value capacitors as part of an i.c., and this has led to the development of unusual techniques in i.c. circuitry to enable supply decoupling and interstage coupling to be obtained without such capacitors.

D1, R3, TR5, D2, R4, D3 and R5 provide a number of stabilized voltages across the main supply, and one of these voltages is fed to the base of TR3. The emitter voltage of TR3 is approximately 0.65 volt positive of its base voltage, and the voltage across R1 is in consequence also stabilized. A constant current must therefore flow in R1, and TR3 operates as a constant current source forming the collector load for TR1 and TR2. Supply decoupling is thus provided.

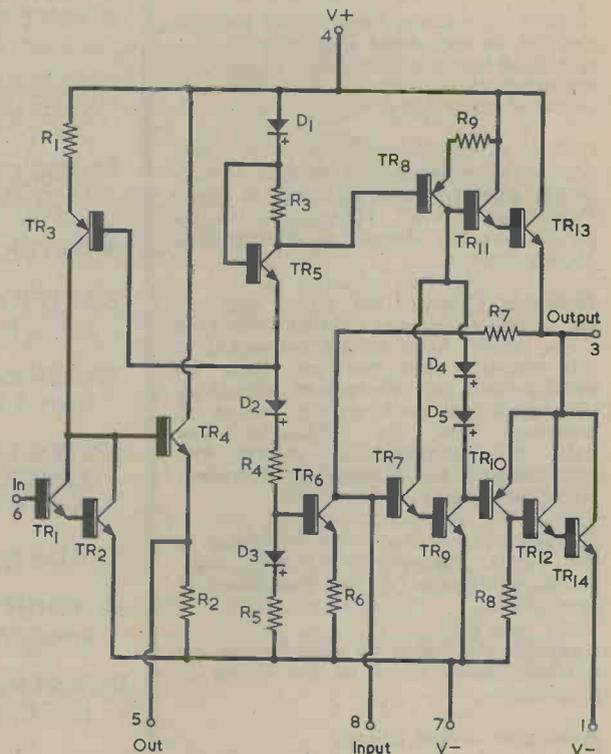


Fig. 1. The internal circuit of the Motorola i.c. type MC1306P. Pin layout is given in the assembly diagram of Fig 3

I.C. AMPLIFIER

By A. P. ROBERTS

TR4 is used as an emitter follower at the output of the pre-amplifier, and it provides an output impedance which is sufficiently low to fully drive the power amplifier section.

TR7 and TR9 are connected as a modified Darlington pair, and are the driver transistors. Their collector load consists of a constant current generator formed by TR8

and R9. D4 and D5 provide a small forward bias to the output transistors, so as to reduce crossover distortion to an unnoticeable level.

The output stage is a fairly conventional complementary configuration using TR11 and TR13 in an emitter follower Darlington pair for the amplification of positive-going output half-cycles, and TR10, TR12 and TR14 in a compound common emitter configuration for the amplification of negative-going half-cycles. R7, coupling back to the base of TR7, allows the output terminal to be at half supply voltage. The input impedance at pin 8 is such that the output of the pre-amplifier can be coupled direct to the input of the power amplifier.

The MC1306P is available from Jermyn Home Electronics, 112 Vestry Estate, Sevenoaks, Kent. It should be mentioned that there is a 50p charge for post and packing.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

R1	10k Ω
R2	220k Ω
R3	1k Ω
R4	2.2 Ω
VR1	5k Ω potentiometer, log, with switch S1

Capacitors

C1	0.1 μ F, type C280 (Mullard)
C2	50 μ F electrolytic, 10 V. Wkg.
C3	82pF, disc ceramic or silvered mica with side wires
C4	0.047 μ F, type C280 (Mullard)
C5	200 μ F electrolytic, 10 V. Wkg.

Semiconductor

IC1	Integrated circuit type MC1306P (Motorola)
-----	--

Switch


S1	s.p.s.t., part of VR1
----	-----------------------

Speaker

LS1	8 to 75 Ω speaker (see text)
-----	-------------------------------------

Miscellaneous

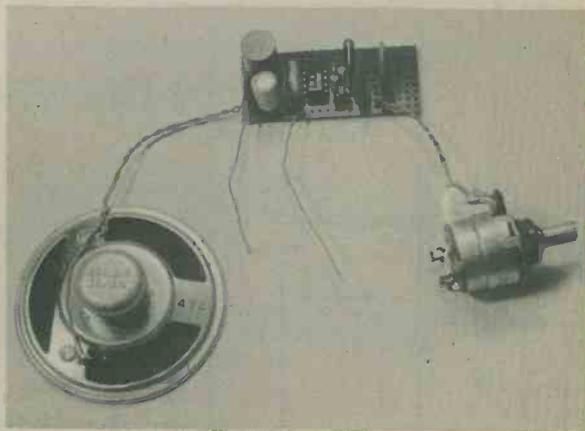9 volt battery (see text)
Battery connectors
Veroboard panel, 0.1 in. matrix



The prototype amplifier coupled to the volume control and speaker. The positive 9 volt lead from the board to switch S1 was not connected when this photograph was taken

PRACTICAL CIRCUIT

A circuit diagram of a practical audio amplifier using an MC1306P i.c. is shown in Fig. 2. This has been designed for use as the audio stages of a small portable radio, and can be fed from any normal a.m. superhet detector circuit.

The input signal is fed via volume control VR1, C1 and R1 to the input of the pre-amplifier section of the integrated circuit. The pre-amplifier is biased by R2. The values given to R1 and R2 determine the voltage gain and input impedance of the pre-amplifier. The input impedance is approximately equal to the value given to R1. The method of setting the gain at the required level is similar to that used with operational amplifiers, and the voltage gain is approximately equal to R2 divided by R1. This is 22 with the values used here, and assuming that VR1 is at a low volume setting. The gain reduces at higher volume settings in VR1 because of the additional resistance inserted in series with R1 by the control. The impedance of the circuit feeding the volume control can also have a small effect on voltage gain. (These comments do not mean that the volume control does not carry out its normal function of controlling signal amplitude. Adjusting it so that it inserts increasing resistance in series with R1 has the secondary effect of slightly reducing pre-amplifier gain.)

Obviously there is some limitation to the maximum gain and input impedance that can be obtained. The maximum voltage gain is 270, which is the open loop gain of the circuit (i.e. the gain with no negative feedback). The maximum input impedance at any gain setting is limited by the fact that R2 should not be raised above a value of $1M\Omega$ or poor d.c. stability may result. However, it is obvious that a large variety of gain and input impedance figures can be obtained by giving R1 and T2 the appropriate values.

Selecting the values of R1 and R2 for the required gain and input impedance is simple. R1 is given the value of the required input impedance, and R2 is then equal to R1 multiplied by the required pre-amplifier voltage gain.

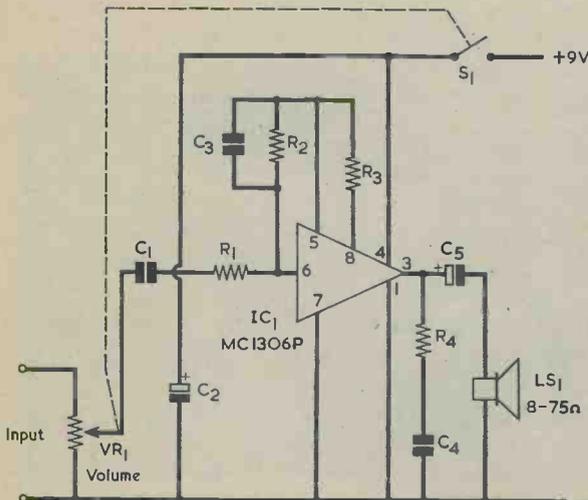


Fig. 2. Circuit of the a.f. amplifier incorporating the MC1306P integrated circuit

For more precise results when calculating the value of R2, the impedance of the source feeding R1 should also be taken into account.

In order to obtain good stability, the circuit is given a certain amount of high frequency attenuation by the inclusion of C3. This gives a $-3dB$ point where the reactance of C3 is equal to the resistance of R1 (and is at about 10kHz with the values employed here).

R3 couples the output of the pre-amplifier to the input of the power amplifier. The value of R3 sets the voltage gain of the power amplifier section in the same way that the value of R1 sets the gain of the pre-amplifier. The biasing resistor for the power amplifier is included in the i.c. (R7 in Fig. 1) and has a value of $10k\Omega$.

The manufacturer's data sheet recommends a value of between 500Ω and $3.3k\Omega$ for R3. With the value of $1k\Omega$ specified in the present circuit the power amplifier voltage gain is approximately 10 (i.e. $10k\Omega$ divided by $1k\Omega$).

C5 couples the output signal to the speaker. Since the impedance of the speaker is largely inductive it rises with frequency, and this can contribute to high frequency instability. R4 and C4 are therefore required to reduce the impedance across the output at the higher frequencies, and so maintain stable operation.

Only a single supply decoupling component is required, and this is C2. S1 is the on-off switch, and in the prototype amplifier is ganged with the volume control.

The unit gives an output of approximately 2 volts r.m.s. for 500mW into an 8Ω load, and with the values shown has a total voltage gain of 220. Neglecting the effect of the volume control resistance, an input of less than 10mV is theoretically required to produce the full rated output. The measured sensitivity of the prototype amplifier was somewhat less than this due to the presence of the volume control. In many cases the voltage gain of the unit will be higher than is required, and R2 can be reduced to a value between some $56k\Omega$ and $100k\Omega$ to produce a lower gain. With the values given in the Components List, the unit works well in conjunction with the popular ZN414 i.c., as well as with a.m. superhet circuits.

CONSTRUCTION

Despite its small size the amplifier is very easy to construct, as so few components are required. It is built on a Veroboard panel of 0.1 in. matrix, and details of this are shown in Fig. 3.

Start by cutting out a panel of the required size (22 by 9 holes with the copper strips running lengthwise) and then drill the two 6BA clear mounting holes. Next, cut the strips at the points indicated. The cuts at S2 and S8 isolate the strips at the mounting holes. Connect the two insulated link wires, then the capacitors and resistors, and lastly the integrated circuit. Be careful not to overheat the i.c. when soldering it into the circuit. The author used Mullard type C280 capacitors having side wires for C1 and C4.

The two electrolytic capacitors used had lead-outs at one end, but it will be equally in order to employ the more common type having lead-outs at opposite ends of the body. One lead-out can then pass through one of the requisite Veroboard holes and the other lead-out, passing down the side of the capacitor body, through the other Veroboard hole.

Finally, the external connections to VR1, S1, the

RADIO & ELECTRONICS CONSTRUCTOR

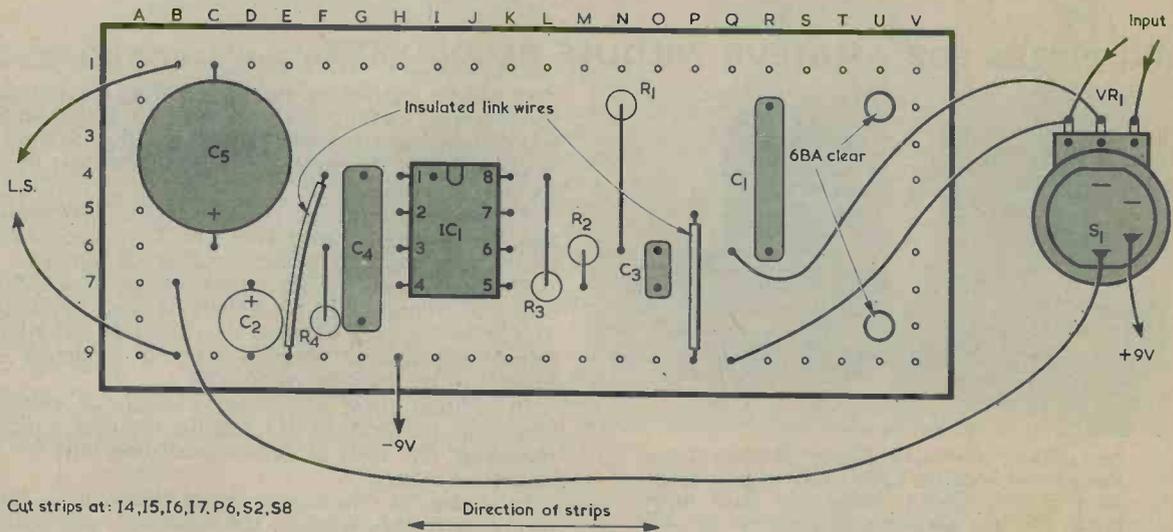


Fig. 3. Component layout on the Veroboard panel. As can be seen, few parts are required in addition to the integrated circuit.

speaker and the battery are made.

If the full rated output of 500mW is not required (and many small speakers are rated at only about 200mW or even less) a speaker with an impedance greater than 8Ω can be used. A maximum power of approximately 250mW is available with a 16Ω speaker, 160mW with a 25Ω speaker, and 53mW with a 75Ω speaker.

The circuit must not be used with a speaker having an impedance lower than 8Ω, nor with a supply of more than 12 volts.

When using the amplifier with a speaker of 16Ω or more a PP3 or PP4 battery is adequate to power the unit, but when using an 8Ω speaker a larger battery, such as a PP7 or PP9, should be used.

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received for to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

Taylor 94A TV Waveform and Alignment Generator – J. F. O'Hara, Ardagh, Rocheston Road, Douglas, Cork. To borrow or purchase manual or circuit.

Sanyo MR939 (Reel to Reel) and Akai CS30 (Stereo Cassette) – E. B. Davies, 103 Melbourne Road, Blacon, Chester. Circuits required.

Hammerstein Radiogram with Tape Recorder, Mercury 5?
– J. N. Shaw, 5 Yew Tree Road, Slough, Bucks. SL1 2AA.
Circuit required for this South African made model.

BIG PRIZES FOR AMATEUR WILDLIFE RECORDISTS



Top prize in this year's 'Scotch' Wildlife Sound Recording Contest is £250 worth of hi-fi equipment of the winner's choice from Rank Audio Visual. Pictured are two examples Akai CS-30D cassette deck, Akai 5200 amplifier and two Rank Domus 175 speakers

Other prizes include original watercolours featuring the subjects of the winning recordings, Grampian recording accessories and Scotch Hi-Fi tape

Top prize in this year's 'Scotch' Wildlife Sound Recording Contest, organised by 3M United Kingdom Limited, is £250 worth of Rank Audio hi-fi equipment.

This will be selected by the winner from the comprehensive range of units from Akai, Rotel, Rank Audio, Rank Domus and Empire. This prize will go to the 3M Wildlife Sound Recordist of the year, the best of the six class winners.

As last year, there are two categories – for novices and for experienced recordists who have won first or second awards during the six preceding 3M contests.

There are classes for birds, mammals and insects and outdoor 'atmosphere' recordings in each category. Top prize for each of these six classes is an original framed watercolour specially painted to depict the subjects of the winners' recordings.

In addition, there is a special prize of £20 worth of Grampian recording accessories for the most original recording, and reels of Scotch recording tape for all successful entrants.

In order to encourage better techniques when recording British Wildlife, the organisers are inviting not only the winners, but every entrant, to the London prize-giving in the spring of 1975, when the judging panel will give an appraisal of the entries. There is no entry fee, but all entries must be submitted on Scotch reel-to-reel tape or Scotch cassettes. Closing date is January 31st, 1975, and entry forms are available from W. R. Bowles, Public Relations Executive, 3M United Kingdom Limited, 3M House, Wigmore Street, London W1A 1ET.


MODULAR PROTOTYPE HARDWARE FROM LEKTROKIT

Lektrokit's modular prototype hardware – part of their total hardware capability for design and development engineers – consists of a complete and versatile range of rack and chassis kits of parts, including a full complement of components from which chassis, racks, trolleys etc. can be constructed quickly and economically.

Standard pieceparts ensure that kits can be assembled and reassembled into many different rack/chassis/cage sizes and card frames.

Its modular design approach permits the interchangeability of many parts, which means the chassis area can be extended as required, and enables individual assemblies to be stacked together to form more complex systems.

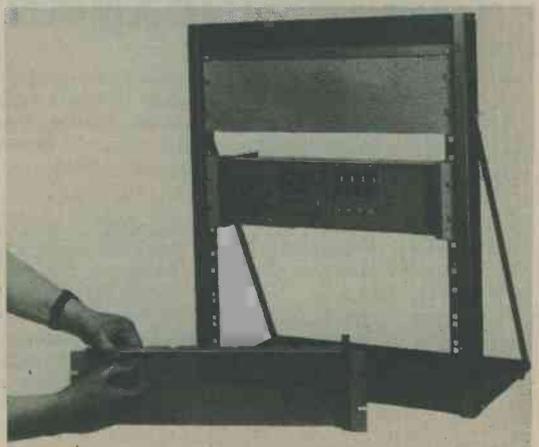Further details from Lektrokit Ltd., 3 Trafford Road, Reading, RG1 8JR, Berkshire.



COMMENT

NEW HEADPHONE FOR POPULAR HI-FI

Beyer Dynamic, the West Germany based manufacturer of microphones, headsets and audio equipment, have produced a new headphone, primarily intended for the popular hi-fi audio market. However, the quality of reproduction is still very high and the Beyer engineers claim that it will satisfy even the most discerning listeners.

This headset, coded DT 302, was featured prominently for the first time in the U.K. at the time of the Audio Fair.

The Beyer Dynamic DT 302 is a very lightweight headset. This is achieved by the design of the headband, which allows simple adjustment of the ear pieces up or down. These are protected by foam plastic pads eliminating any interference from 'local noise', at the same time being exceptionally comfortable to the wearer. Three metres of lightweight cable complete the DT 302 which will be retailed at £7.83 plus V.A.T.



*A unique high velocity open
aire stereophone, ultra light:
66 g (2.3 oz), with a wide
range frequency response of
exceptional fidelity due to
complete obviation of resonance
and inhibition of transient
response experienced
with conventional stereo-
phones*

HELPING HANDS

We have recently learned that the annual exhibition of *The British Amateur Electronics Club* has enabled the club to make a record donation of £457 to the Cancer Research Campaign; our congratulations to the club on such a splendid result.


Among the services members of the B.A.E.C. receive is an excellent Newsletter edited by their chairman, C. Bogod. Readers who may be interested in membership should write to the Honorary Secretary,

J. G. Margetts, 11 Peartree Avenue, Maidstone, Kent.


It is one of the delights of our hobby that so many are prepared to give their time and energy to assist others in its pursuit, whether as individuals or as officers of a club or society. It is an additional pleasure when groups help others who may be outside the sphere of the hobby's interest - a case of goodwill always being in season.

*We wish all our readers
a Happy Christmas
and a Prosperous New Year*

—Editor

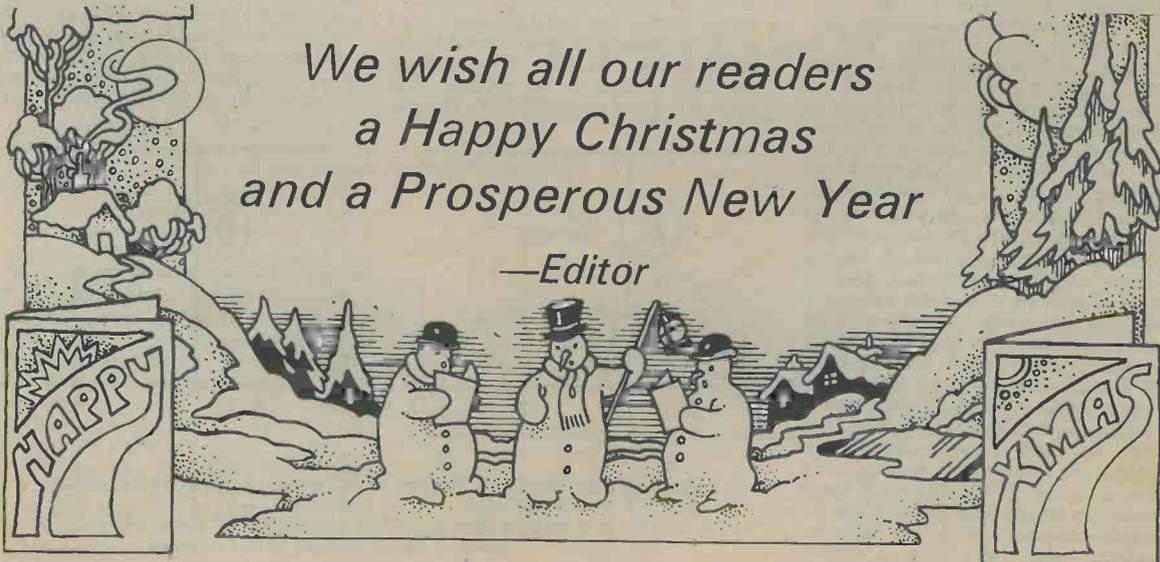

'CONSTANT CURRENT' CLASS A AMPLIFIER

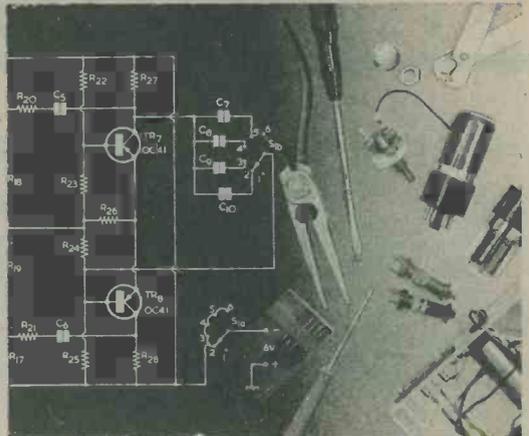

by G. A. FRENCH

SOME OF US WHO BIT OUR TEETH ON valves tend occasionally to conjure up nostalgic memories of the very simple Class A a.f. output stages which were the order of the day in those earlier times. A typical output circuit merely consisted of a valve anode coupled to the primary of a speaker transformer, the secondary of which then coupled to the speaker itself. The resultant reproduction was not in the high fidelity category, but it was quite adequate for low cost domestic entertainment equipment.

The advent of the transistor has resulted in the introduction of the Class B push-pull output stage. This has the considerable advantage of high efficiency, thereby allowing small transistors to produce relatively high audio output powers. Some level of crossover distortion is liable to occur when a very high efficiency is required, although this can usually be reduced to an acceptable level by the use of negative feedback. High efficiency in the a.f. output stages of battery driven equipment is obviously desirable because it results in a low drain on the battery supply. With mains-driven equipment the question of supply current is much less important, and the main advantage of a high efficiency output stage is that this allows large a.f. output powers to be obtained with reasonably small output transistors.

The author decided to investigate the possibilities of making up a mains driven a.f. amplifier having a true Class A output, and incidentally offering an output power inevitably lower than that which the output stage transistors would provide in Class B. He was pleased to find that such an amplifier could have quite a simple

circuit and that it gave good quality reproduction for normal domestic listening. The amplifier forms the basis of this month's 'Suggested Circuit' article, and it incorporates a constant current drive technique which the writer has not previously seen employed in this field.

CLASS A DRIVE

A simple method of providing a Class A drive to a speaker consists of using the output transistor as an emitter follower with its emitter current flowing directly through the speaker, as in Fig. 1(a). Signal voltage is applied to the base of the transistor, and this acts as a current amplifier with a voltage gain of unity. The circuit is capable of working reasonably well but it has the disadvantage that there is a continual standing current in the speaker. The speaker current increases when the out-

put transistor base goes positive and decreases when the output transistor base goes negative. At zero signal input the standing current causes the speaker voice coil to be displaced from its mechanical position of rest, and inward and outward displacements of the voice coil in the presence of signal may not then be symmetrical about the zero signal position.

A possible alternative method of driving the speaker is shown in Fig. 1(b). Here, the direct emitter current flows through a resistor, across which the speaker is connected by way of a high value electrolytic capacitor. In consequence, there is no standing direct current in the speaker, and voice coil displacements on either side of the mechanical rest position are symmetrical, with the speaker functioning under its designed conditions. Unfortunately, the resistor requires a low value, comparable with speaker impedance, if the

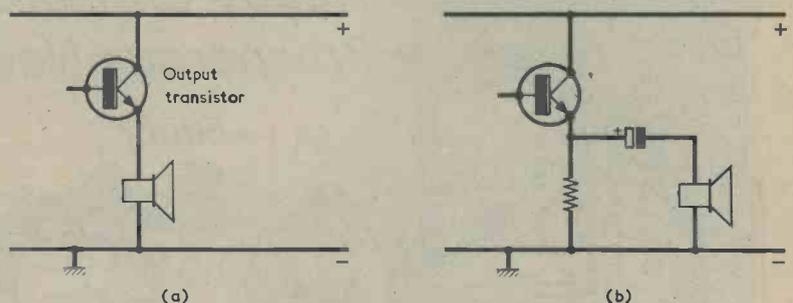


Fig. 1(a). One possible method of obtaining a Class A a.f. output stage
(b). If a resistor and capacitor are added, as here, there is no flow of direct current in the speaker

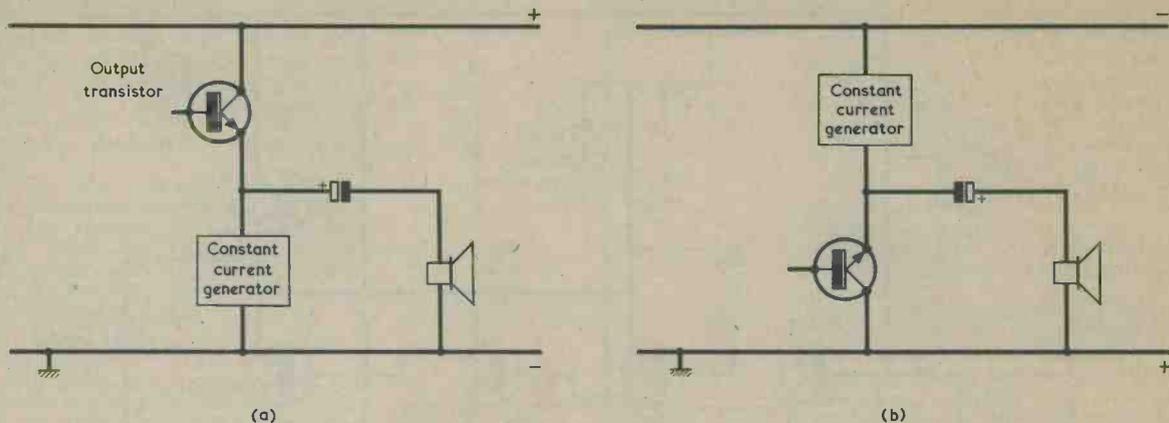


Fig. 2(a). An improvement is effected by allowing the standing direct current to flow through a constant current device
 (b). Slightly altering the circuit configuration produces several further advantages

transistor is to be brought onto proper operating conditions, whereupon a high proportion of the a.f. output power is wasted in the resistor.

Fig. 2(a) illustrates a new approach. Here, the resistor of Fig. 1(b) is replaced by a constant current generator, this being a device which allows the same pre-determined current to flow in it regardless of the voltage which appears (within limits) across its terminals. If the voltage at the base of the output transistor is varied the emitter voltage changes in sympathy, but the current flowing in the constant current generator remains unaltered. Thus, the constant current generator acts as an infinite resistance to alternating current. In Fig. 2(a) we have the situation where all the direct standing current from the output transistor emitter flows in the constant current generator, whilst all the alternating current is routed via the series capacitor to the speaker.

An even better configuration is shown in Fig. 2(b). The only change here is that the upper supply rail has been made negative instead of positive and we have now placed the speaker and its series capacitor across the output transistor instead of across the constant current generator. This arrangement forms a very effective Class A output coupling circuit provided that the constant current is greater than the highest peak signal current that will be passed to the speaker. In order that both negative and positive excursions of the signal can be handled equally, the output transistor will (at a first approximation) be biased so that its emitter is at half supply voltage in the absence of signal.

Having the constant current generator above the output transistor, as in Fig. 2(b), confers two advantages. The first of these is that it prevents any hum ripple voltages on the upper

supply rail reaching the speaker or the output transistor. The ripple voltages appear at the upper terminal of the constant current generator but, since this passes the constant current only, are not applied to the speaker or transistor. The second advantage is that all the supply current to the output transistor stage passes through the constant current generator, with the result that the current drawn from the supply remains continually at the same value both under zero signal and under full signal conditions. There are, in consequence, no problems with respect to power supply voltage regulation or bypassing, and the output stage will work just as well with a poorly regulated and bypassed supply as it will with a high performance supply.

The concept of constant current drain from the supply may be more readily understood with the aid of Fig. 3. In this diagram the battery is an accumulator and it has a voltage equal

to half the supply voltage. The transistor is biased so that, at zero signal, its emitter is also at half supply voltage. Under the circumstances, no current flows through the speaker. A positive-going signal half-cycle at the base of the transistor will cause its emitter to go positive also. There will then be two currents flowing in the emitter circuit: the constant current from the constant current generator plus a discharge current from the battery by way of the speaker. A negative-going signal half-cycle at the transistor base will cause the emitter to go negative of half supply voltage. This time the current from the constant current generator will become divided. Part of it will flow in the transistor emitter and the remainder will flow through the speaker into the battery, acting as a charging current for the latter. It will be seen that the transistor passes increased current with positive signal half-cycles and decreased current with negative signal half-cycles, the difference with the constant current passing, in both instances, through the speaker. Under normal conditions the average current in the transistor will be the constant current from the constant current generator. Also the overall discharge and charge currents in the battery will be equal and opposite giving an average battery current of zero. So far as the power supply is concerned, the only current which has been drawn from it is the continual constant current.

If we replace the battery of Fig. 3 with a large value capacitor the same effect will take place. Once the capacitor has become charged to half supply voltage after switching on the supply, it will behave in the same manner as the battery, undergoing discharge and charge currents on successive signal half-cycles. With the Fig. 3 arrange-

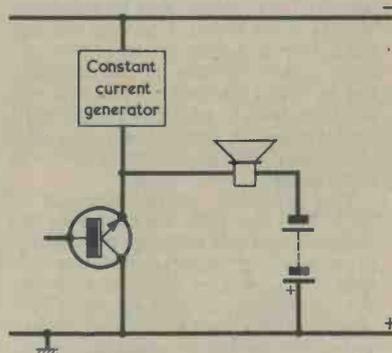


Fig. 3. The operation of the arrangement of Fig. 2(b) can be explained with the aid of this circuit

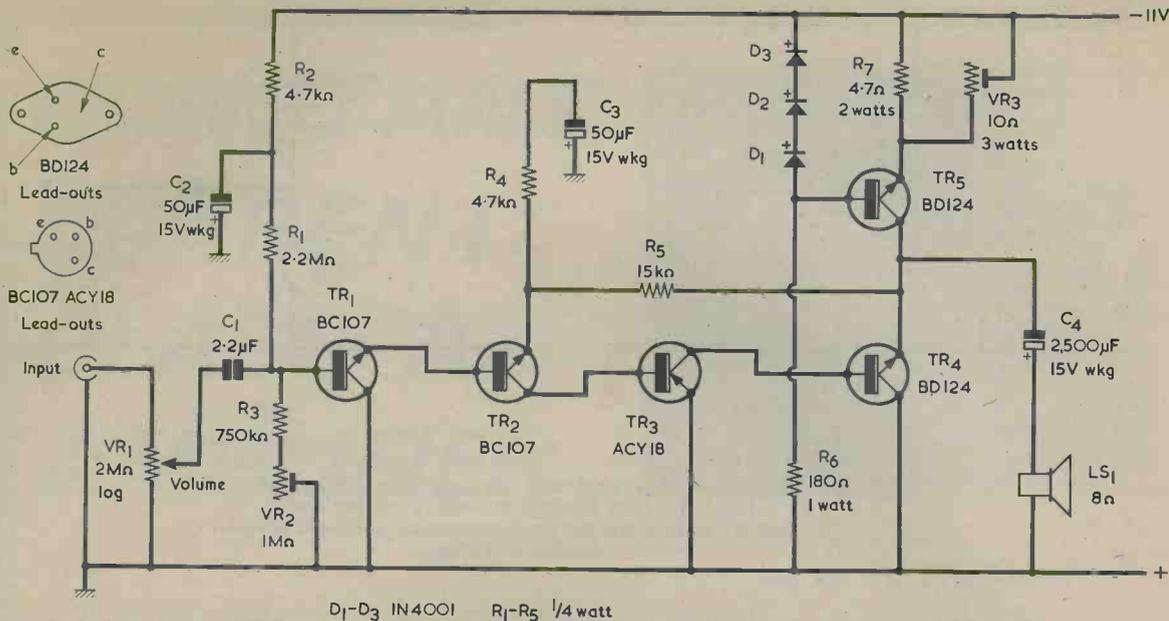


Fig. 4. A practical amplifier circuit incorporating a constant current output stage. This may be fully loaded by a crystal or ceramic pick-up

ment the large value capacitor would be between the speaker and chassis. It may just as usefully be between the transistor emitter and the speaker, as in Fig. 2(b).

Returning to Fig. 2(b), both the constant current generator and the output transistor pass an average current that is greater than peak signal current, and each has half the supply voltage across it. The overall power dissipation in the two devices is therefore well in excess of the maximum audio power which can be fed to the speaker. This low level of efficiency is accepted and it does not incur a serious cost hazard if the amplifier is mains driven.

PROVISIONAL DESIGN

It was decided to make up a small amplifier employing the principle shown in Fig. 2(b) to check results in practice. An arbitrary output power of 1 watt into an 8Ω loudspeaker was chosen as the design target.

A dissipation of 1 watt in 8Ω corresponds to an r.m.s. voltage of approximately 2.8 volts. (The square of 2.8 volts divided by 8Ω equals 1 watt.) The corresponding peak voltage is 3.9 volts. Thus, the overall voltage swing needed at the output transistor emitter is twice 3.9 volts or, roughly, 8 volts. A peak voltage of 3.9 volts across 8Ω corresponds, very nearly, to a current of 0.5 amp. It was decided in consequence to set up an output stage with a voltage swing of 8 volts and to provide a constant current of 0.55 amp, this being 50mA in excess of the possible maximum signal peak current. The simplified design treatment which was then instituted did not take into account possible base-emitter voltage

drops in the amplifier transistors, but in practice it was found that the final output voltage swing was still retained at around 8 volts.

The practical amplifier circuit is shown in Fig. 4, and here TR4 is the output transistor and TR5 is the constant current generator. The negative supply voltage is 11 volts. If it is assumed that 3 volts can be allowed to be lost across the constant current generator then 8 volts is available for output voltage swing.

The constant current generator configuration will be familiar to most readers. The base of TR5 is held firmly at a fixed reference voltage level with respect to its emitter supply point by the three forward biased silicon diodes D1, D2 and D3, whereupon emitter current can be pre-set by means of R7 and VR3. The collector current is very nearly equal to the emitter current and can be looked upon as a constant current. The current will be less likely to vary if the forward current through the diodes is well in excess of the constant current divided by the transistor hFE. In Fig. 4 the diode forward current is about 48mA, which is comfortably higher than the current required with the lowest gain transistor likely to be encountered.

The amplifier proper consists of TR2, TR3 and TR4. TR1 is an emitter follower, and it is added at the input to provide a high input impedance suitable for crystal or ceramic pick-ups. TR3 is a voltage amplifier driving TR4, and here we arrive at another advantage conferred by the constant current approach. In a conventional Class B circuit it is usual to have the voltage amplifier feed into a resistive collector load which is bootstrapped to the output. In consequence the voltage

amplifier collector feeds a steady current into its load whilst collector current changes due to signal are fed to the output transistors. With the present circuit there is a reasonably steady base current in TR4 resulting from the constant current in its emitter circuit. As a result, TR3 collector feeds this steady current to TR4 base and also passes to it the changing currents due to signal. It then becomes possible for TR3 collector to couple directly into TR4 base, effective 'bootstrapping' being given without the necessity for actual bootstrapping components. A circuit simplification is thus achieved.

TR2 couples directly into TR3 in a manner given in many direct coupled Class B amplifiers. D.C. negative feedback is applied via R5 from the emitter of TR4 to the emitter of TR2, and it causes the emitter of TR4 to be held at the half supply voltage. If, for any reason, TR4 emitter should attempt to go negative so also do the emitter and collector of TR2, and the base of TR3. Phase reversal in TR3 then causes TR4 base to go positive, counteracting the initial tendency of TR4 emitter to go negative. A similar self-correcting chain of events takes place if TR4 emitter attempts to go positive.

The a.c. feedback loop takes in R4 and C3, whereupon the amplifier voltage gain becomes R5 plus R4 divided by R4, or 4 times. This is adequate to load the amplifier with the output from a crystal or ceramic pick-up. The voltage gain can be increased, if desired, by reducing the value of R4.

As already mentioned, TR1 is merely an emitter follower which enables a high input impedance to be given. Its emitter can be conveniently

coupled directly to the base of TR1. The potential on TR1 base governs the potential on TR2 base, and this in turn governs the potential of the output emitter. The output emitter potential is set up to half-supply voltage by adjusting the pre-set potentiometer VR2.

TR2, TR3, TR4 and TR1 collector are all supplied from the voltage given by the constant current generator, TR5. The base of TR1 is supplied via the potentiometer consisting of R2, R1, R3 and VR2. Additional smoothing is given here by C2.

PRACTICAL OUTPUT SWING

In practice, it is impossible for the emitter of TR4 to be taken fully down to the positive supply rail because of base-emitter voltage drops in TR1, TR2 and TR4 itself. When, in the prototype, the base of TR1 was taken to chassis the emitter of TR4 fell to 1.6 volts above chassis potential. So the furthest positive excursion of TR4 emitter is limited to 1.6 volts above chassis potential. However, the 3 volts allowed for the constant current generator proved to be generous, and it was found that the collector of TR5 could, in practice, rise to about 9.5 volts above chassis. Thus, the 8 volt output swing required at the output emitter is very nearly achieved, and the target 1 watt output is just obtained. To ensure symmetrical working VR2 is adjusted so that the emitter of TR4 is mid-way between the two limiting voltages; i.e. at about 5.5 to 5.6 volts above chassis potential.

When the amplifier is running TR4 dissipates a steady 3 watts whilst TR5 dissipates a steady 3.6 watts. Both these transistors require heat sinks and the author employed flat metal sheets measuring 3½ by 5½ ins. in the prototype amplifier. Smaller heat sinks of the ribbed type would probably also be suitable. It is of course a simple matter to check transistor temperature by touching each transistor case with the back of the finger, and this is quite safe as there are no high voltages in the

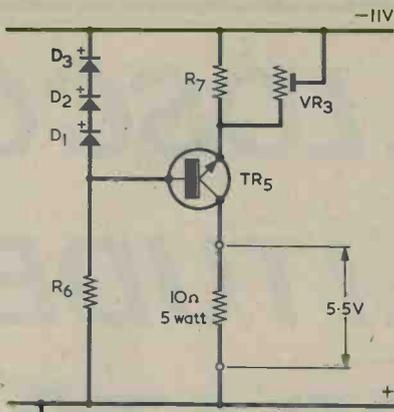


Fig. 6. Test circuit for setting up the constant current

amplifier. The transistors must have a tight thermal coupling to their heat sinks, and the heat sink for TR5 must be insulated from chassis. If a reasonably large chassis is used, TR4 could be bolted to it directly, the chassis then acting as its heat sink.

The power supply used by the author is shown in Fig. 5. The 12.6 volt transformer secondary was provided by two 6.3 volt windings of a heater transformer connected in series. Many valve h.t. mains transformers could be used here, the h.t. secondary being ignored. So far as new components are concerned there is an R.S. Components 'Hygrade' Filament Transformer offering two 6.3 volt 1.8 amp secondaries and this would be satisfactory for the power supply. The 3.9Ω current limiting resistor, R8, allows the requisite 11 volts to be produced across C5 when the supply is loaded by the amplifier. Supply voltages in excess of 11 volts should not be used.

In the constant current generator section of the amplifier, a voltage of about 2.1 volts appears across diodes D1 to D3, and R7 and VR3 are called

upon to drop some 1.4 volts at the constant current of 0.55 amps. This corresponds to a resistance of about 2.5Ω. VR3 was a Bulgin 3 watt wire-wound potentiometer whose maximum track current rating is, coincidentally, 550mA, and this is listed by Home Radio. R7 is connected in parallel with it to pass some of the emitter current and keep the current in VR3 below its maximum rating.

The amplifier and power supply should be assembled with, initially, no connection to TR5 collector. This collector is then temporarily connected to chassis via a 10Ω resistor, as in Fig. 6. A voltmeter is connected across the 10Ω resistor and VR3 is set to insert maximum resistance into circuit. The power supply is switched on and the resistance inserted by VR3 slowly reduced until the voltmeter indicates 5.5 volts. VR3 is then set up for the constant current of 0.55 amp, whereupon the amplifier is switched off, the voltmeter and 10Ω resistor removed, and the collector of TR5 connected into the amplifier circuit. This method of setting up VR3 does not incur excessive dissipation in TR5.

When VR3 has been set up, it is next necessary to set up VR2. The voltmeter is now connected between chassis and the emitter of TR4 and VR2 is adjusted for a voltage reading of 5.5 to 5.6 volts. Since this setting is to some extent dependent on the gain of TR2 and TR3 there is a slight chance that the desired voltage may, with some amplifiers built up to the circuit, be outside the range of VR2. If the lowest voltage obtained is greater than that desired, the value of R3 should be reduced slightly. If the highest voltage obtained is below that required, the value of R3 may be increased or that of R1 reduced. The amplifier must always be switched off when changing fixed resistor values in the input circuit.

All the components are readily obtainable with the possible exception of the two high wattage resistors R7 and R8. The precise value of R7 is not very important and it can in practice lie between 4.7Ω and 6.8Ω. In any event, a 4.7Ω resistor in 2½ watt rating is available from Home Radio. Similarly, Henry's Radio list a 4.7Ω 4 watt resistor which would also be satisfactory. If R8 cannot be obtained as a single resistor it could consist of four 1Ω 2½ watt resistors in series (Home Radio) or two 8Ω 9 watt resistors in parallel (Henry's Radio). Other series or parallel combinations are also feasible, and a slight discrepancy from the nominal value of 3.9Ω is permissible.

The completed amplifier gave a very satisfactory performance, and there was no evidence of instability despite the extended chain of direct transistor couplings. It may be used with speaker impedances greater than 8Ω at the expense of reduced output power. Speakers with impedances lower than 8Ω must not be used.

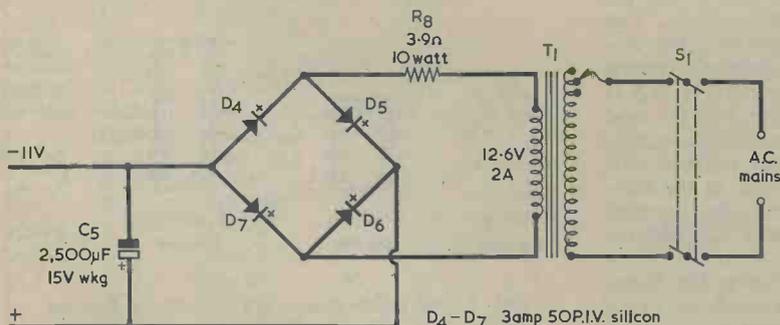


Fig. 5. The amplifier power supply

OSCILLOSCOPE AMPLITUDE CALIBRATOR

By A. Foord

This unit provides a.c. or d.c. voltages from 10mV to 10 volts for calibration or test purposes, and consists of a multivibrator followed by an accurate attenuator

THE CIRCUIT DIAGRAM FOR THE AMPLITUDE CALIBRATOR itself is shown in Fig. 1, with details of the attenuator and switch in Fig. 2. A relaxation multivibrator is formed by IC1 and associated components. With S1 in the 'DC' position the non-inverting input pin 3 is referred to earth via R1 and negative feedback (from the output pin 6 via R3 to the inverting input pin 2) holds the output close to earth potential. This stage is then isolated from TR1 because C6 is effectively open-circuit at d.c.

MULTIVIBRATOR OPERATION

When S1 is in the 'AC' position the circuit will oscillate at approximately 1kHz in a relaxation mode. The negative feedback loop from the output to input via R3 is still in operation but there is also a positive feedback loop via C1 to the non-inverting input. The circuit changes state regeneratively each time the two inputs are at the same potential. The voltage movement at the output point (across the diodes D1 and D2) is fully transmitted to the non-inverting input by C1, and the voltage at this input then begins to recover exponentially towards earth potential. When part of this movement has been completed the voltage at the non-inverting input reaches the same voltage as the inverting input (depending on the ratio of R3 and R2) and regeneration occurs again.

Then the output voltage, the non-inverting input voltage and the inverting input voltage levels all swing to the opposite side of earth potential and the recovery process takes place again. The waveforms are shown in Fig. 3, which is not drawn to scale. Two of the accom-

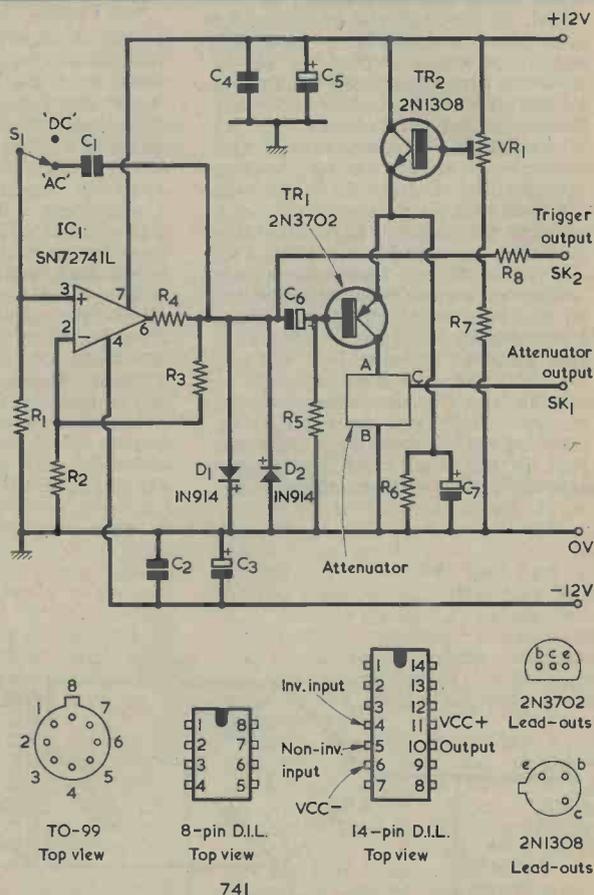


Fig. 1. The multivibrator and amplitude limiting section of the oscilloscope calibrator. The numbers at IC1 terminals in the circuit apply to the TO-99 and 8 pin d.i.l versions

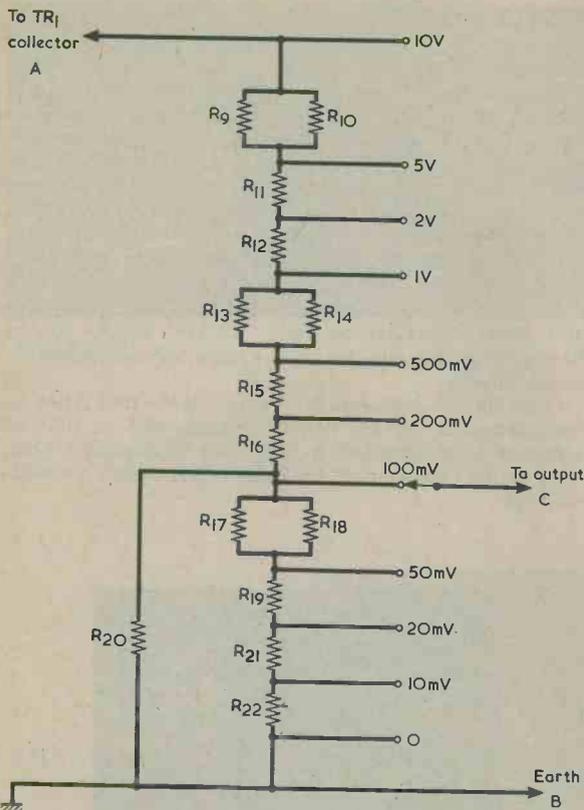


Fig. 2. The circuit of the attenuator. This gives output voltages ranging from 10mV to 10 volts

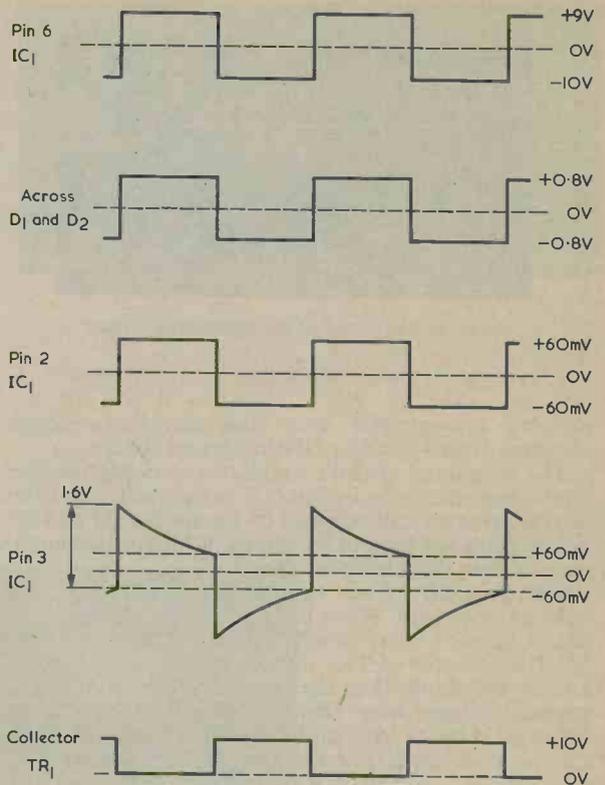


Fig. 3. Waveforms appearing at various points in the circuit. These are not drawn to scale

COMPONENTS

Resistors

(All fixed values $\frac{1}{2}$ watt)

R1	3.3k Ω 5%
R2	2.2k Ω 5%
R3	27k Ω 5%
R4	680 Ω 5%
R5	33k Ω 5%
R6	2.2k Ω 5%
R7	2.7k Ω 5%
R8	6.8k Ω 5%
R9	1k Ω 2%
R10	1k Ω 2%
R11	300 Ω 2%
R12	100 Ω 2%
R13	100 Ω 2%
R14	100 Ω 2%
R15	30 Ω 2%
R16	10 Ω 2%
R17	100 Ω 2%
R18	100 Ω 2%
R19	30 Ω 2%
R20	11 Ω 2%
R21	10 Ω 2%
R22	10 Ω 2%
VR1	1k Ω pre-set potentiometer, linear

Capacitors

C1	0.047 μ F 10%
C2	0.047 μ F ceramic
C3	10 μ F electrolytic, 16 V. Wkg.
C4	0.047 μ F ceramic
C5	10 μ F electrolytic, 16 V. Wkg.
C6	10 μ F electrolytic, 16 V. Wkg.
C7	10 μ F electrolytic, 16 V. Wkg.

Semiconductors


IC1	SN72741L or equivalent (see text)
TR1	2N3702
TR2	2N1308
D1	1N914
D2	1N914

Switches

S1	s.p.s.t. toggle
S2	single pole 11 way rotary

Miscellaneous

SK1, SK2 sockets.

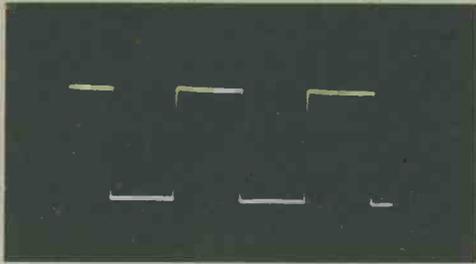

Waveform at pin 6 of the integrated circuit

panying photographs show the actual waveforms obtained at pins 3 and 6 of the integrated circuit.

The integrated circuit's amplitude switches between limits determined by its internal components, and this level is symmetrically clipped by the diodes D1 and D2 before being fed back to the inputs. R4 limits the output current from the integrated circuit.

TR2 provides a direct voltage slightly in excess of 10 volts at its emitter. When S1 is in the 'DC' position the circuit before C6 has no effect, and R5 turns TR1 hard on. The collector of TR1 therefore remains at 10 volts, and by switching S2 in the attenuator circuit of Fig. 2 stepped voltages from 10mV to 10 volts are available. When S1 is in the 'AC' position a 1.6 volt peak-to-peak square wave appears at the base of TR1 so that TR1 switches on and off. TR1's collector will therefore produce a square wave between zero and 10 volts, and again any peak-to-peak amplitude between 10mV and 10 volts may be switched to the output.

The integrated circuit used in the prototype and specified in the Components List is in the 8 lead TO-99 can. Other '741' i.c.'s such as the LM741CH, etc., can be employed, as also may the LM201H and LM301AH. Fig. 1 shows the appropriate pin assignments in 8 pin d.i.l. and 14 pin d.i.l. All pin references given in the text apply to the TO-99 or 8 pin d.i.l. encapsulation.

The performance of the unit is detailed in the Table.

CONSTRUCTION

Construction is not critical and may follow normal circuit practice. There is an output via R8 to SK2 which may be used as an oscilloscope trigger. C2 and C4 should be kept close to the integrated circuit to ensure that there is no danger of high frequency instability.

TABLE

OSCILLOSCOPE CALIBRATOR PERFORMANCE


Output	A.C. or d.c., 10mV to 10V in 10 steps.
Frequency	Approximately 1kHz.
Accuracy	±2%.
Power supplies	+12V at 21mA, -12V at 8mA.
Trigger output	1.6V peak-to-peak.

SETTING UP

With S1 in the 'DC' position check that pin 6 of the integrated circuit is approximately at earth potential and that the output can be varied by S2 over the required range. Output voltages will only be approximately correct at this stage. With S2 in the 'AC' position check that a square wave of about 1.6 volts peak-to-peak appears at the trigger output socket and that an output at SK1 is available.

If all is well, set S1 to 'DC' and S2 to '10V' and measure the d.c. output voltage at SK1. Adjust VR1 until this is at the correct value of 10 volts. Since the unit relies indirectly on the +12 volt supply for its 10 volt reference, the +12 volt supply should preferably be stabilized.

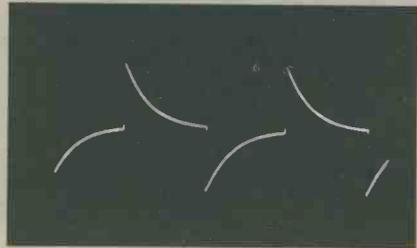Once the d.c. level has been adjusted the unit relies on the attenuator for the other voltages, and so that its accuracy is maintained it must not be loaded. When used as an oscilloscope calibrator this is not a disadvantage.




The waveform appearing at pin 3 of the i.c.


OSCILLOSCOPE GAIN CALIBRATION

The input stage of an oscilloscope has a similar arrangement to our amplitude calibrator, and signals greater than the most sensitive range of the oscilloscope are attenuated down to a common level before being applied to the amplifier. In setting the oscilloscope gain it is usual to switch to the most sensitive position (which may be 10mV or 50mV per centimetre of screen deflection), apply a known signal, and adjust the oscilloscope pre-set gain control until a correct reading is observed on the screen. The amplitude calibrator is ideal for this application because it can provide known signals, from 10mV peak-to-peak, which progress upwards in steps suitable for most oscilloscope calibration purposes.


For a direct coupled oscilloscope this gain setting could in theory be carried out at d.c. by measuring the shift in spot position as the calibrator is connected and disconnected; but in practice the gain setting should be obtained at 1kHz with the oscilloscope input set to 'a.c. coupled'. There are two reasons for this procedure. Firstly a nominally direct coupled oscilloscope may suffer a small gain reduction at d.c.; and secondly, because of non-linearity in the oscilloscope amplifier, a

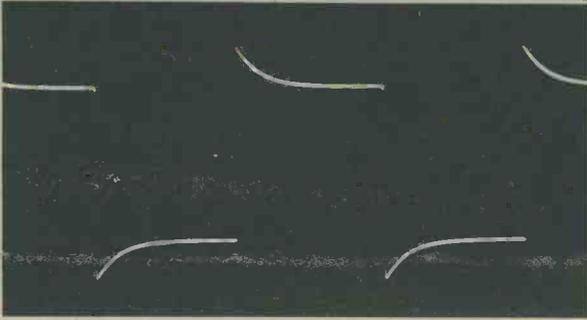

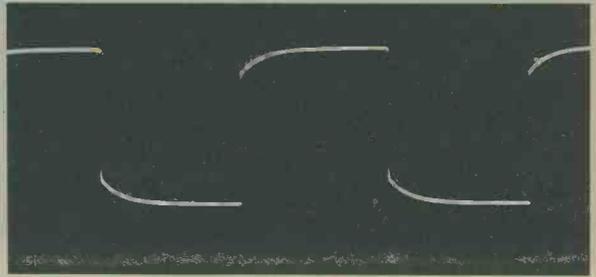The effect of over-compensating an oscilloscope attenuator



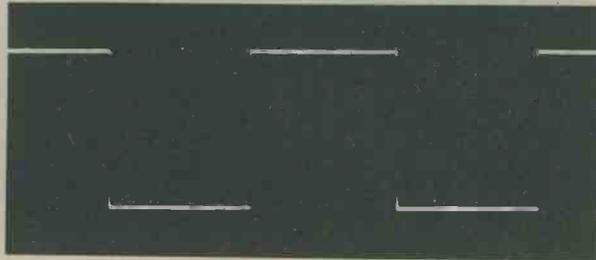Under-compensation gives the effect shown here



Trace given by a correctly compensated oscilloscope attenuator

d.c. voltage from zero volts at the bottom of the screen to (say) 10 volts at the top of the screen may not appear equal in amplitude to an a.c. coupled waveform of plus-and-minus 5 volts about the centre of the screen.

These points can easily be checked with the calibrator and it is normally only in home constructed oscilloscopes where non-linearity or low d.c. gain is experienced. Commercial instruments with their more complex circuits usually have a good performance.

Once the most sensitive range of the oscilloscope has been calibrated its built-in attenuator provides the other ranges with an accuracy which depends on the resistors used in its construction. If 1% resistors are used then the overall accuracy to be expected will depend quite a lot on the initial setting up and the care taken in reading off the oscilloscope screen. A typical accuracy would be 5% or better, and this is normally good enough for measurements taken with an oscilloscope.

OSCILLOSCOPE WAVEFORM CALIBRATION

For waveform adjustment each resistor in the oscilloscope attenuator has a parallel capacitor which is adjusted until the square wave visible on the screen has a flat top. The results of under- and over-compensation

are shown in the photographs. These capacitors should be adjusted starting with the most sensitive range and working towards the least sensitive range, since they are interdependent.

When the basic oscilloscope has been calibrated any attenuating probes ('X10' or 'X100', etc.) can be similarly compensated.

SIGNAL SOURCE

The calibrator may be used as a signal source subject to the limitations imposed on accuracy if it is loaded. For many purposes this is unimportant; for example, in circuit testing or fault-finding on feedback amplifiers the circuit either works with a well defined gain or it fails to work at all. If 100mV is fed into an amplifier with a gain of 10 then a quick check to determine that the output is approximately 1 volt is often all that is needed.

Alternatively, if accurate measurements are required then the output of the calibrator should be measured under the loaded working conditions.

The calibrator is useful for square wave testing of audio or feedback amplifiers since any imperfections like ringing, poor rise time, l.f. droop, etc., are quickly shown up. ■

SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

Shortwave listening as a hobby is, by its very nature, a somewhat lonely affair. Enthusiasts sit, often night after night and sometimes even into the small hours, operating their respective listening station whilst listening for those elusive Dx signals they have read about in journals such as this. Being a loner, it is apparent that without some form of regular communication, much that could be heard would be missed through lack of information.

News of current activities on the broadcast bands, which is a necessity for all actively engaged seriously in the hobby, is to be found in the publications of various short wave listener clubs. Two such clubs which provide a useful inflow of information are the International Short Wave League and the World DX Club; for further information see the Small Advertisement section in this issue.

An overseas source that can be thoroughly recommended is the Danish monthly 'Shortwave News' published by the Danish Shortwave Clubs International. Entirely in English, the issue for October, for instance, was of thirty-two pages plus cover and of this total, ten pages were of members reports (broadcast band tips) and the remainder on news and information. The journal is extremely well produced and contains many illustrations, the page size is 8½ x 11½ in. (approx.) and is duplicated. The annual fee is £3.40 and the address (U.K. representative) is N. R. Green, 14 Marsden Road, Blackpool, Lancs. FY4 3BZ, to whom payments should be made.

CURRENT SCHEDULES

● PAKISTAN

Radio Pakistan, Karachi, currently (at the time of writing) has an External Service in English as follows – from 0230 to 0245 news at slow-speed to the Far East on 17830 and on 21730; from 0430 to 0445 news at slow-speed to East Africa on 15325, 17830 and on 21590; from 1100 to 1115 news at slow-speed to West Europe on 15115 and on 17910; from 1530 to 1545 news at slow-speed to the Middle East on 11672 and on 15520; from 1745 to 1800 news at slow-speed to Eastern Europe and Western USSR on 9690 and on 11672 and from 2000 to 2045 to the U.K. on 7085 and on 9465. Note that frequencies are subject to some variation, that of the listed 15325 being actually measured by us on 15322.5 kHz.

● FINLAND

The Finnish Broadcasting Company, Helsinki, presents an External Service in English to Europe, North and South America from 1400 to 1430, from 1600 to 1630 and from 1800 to 1830 on 9550, 11755, 15185 and on 21605; to Europe and South America from 2030 to 2100 on 9550, 11755 and on 15185 and to North America from 0300 to 0330 on 9585.

● PORTUGAL

Radio Portugal, Lisbon, radiates an External Service in English to Eastern U.S.A. from 0200 to 0230 on 6025 and on 11935; to Canada from 0300 to 0345 on 11840; to Western U.S.A. from 0345 to 0430 on 6025 and on 11935; to the Far East from 0730 to 0900 on 17880 and on 21495; to India from 1345 to 1430 on 17895 and on 21495; to East and West Africa from 1745 to 1830 on 11875 and on 21495; to Europe from 2045 to 2130 on 6025.

● NIGERIA

The 'Voice of Nigeria', Lagos, daily offers an External Service in English to Africa, the Middle East and Europe, from 0555 to 0735 on 7275, 11770 and on 15185; to Africa, the Middle East and Europe, from 1530 to 1700 on 7275, 15120 and on 15185; to Africa, Middle East and Europe, from 1800 to 1930 on 7275, 11770 and on 15120.

● TURKEY

Radio Ankara listed a broadcast in English to Europe, the U.K., North Africa and North America from 2200 to 2230 on 11880, this has now been extended till 0115.

● CHINA

For Dxe's, the Ikechao regional relay station of the Inner Mongolia People's Broadcasting Service at Tunsheng operates on 4525 in Standard Chinese with relays of Peking's First Programme and the Inner Mongolia Regional Service from Huhehot from 2125 to 0101 and from 0945 to 1401, according to the BBC Monitoring Service.

● LEBANON

Broadcasts from Radio Beirut to Europe and Africa in English, Arabic and French, from 1830 to 2030 are now on 11795 and those to Central and North America in French, Arabic, English and Spanish, from 0130 to 0330 are now on 9675.

● EGYPT

The Radio Cairo 'Voice of Africa' Service now opens with a broadcast in English to East Africa from 1430 to 1515 on 17725.

● CLANDESTINE

The 'Voice of Iraqi Kurdistan' currently operates as follows – from 1600 to 1730 (to 1800 on Fridays) in Kurdish; from 1730 to 1800 (Sundays, Tuesdays and Thursdays) in Assyrian; from 1730 to 1800 (Mondays, Wednesdays, Saturdays) in Turkmen; from 1800 to 1900 in Arabic and from 1900 to 1925 in English. All transmissions from this pro-Barzani transmitter are on 6940 (but see Around the Dial) and on 10055.

● NORTH KOREA

Radio Pyongyang may be logged at 1800 when commencing their programme in English with station identification on 9977 and in parallel on 6338.

● **LIBERIA**

Monrovia (Voice of America) can be heard at 0730 on 7280, where we heard them presenting a talk on current world economics.

● **CZECHOSLAVAKIA**

Radio Prague at 0745 on 9505 with news of local affairs after the station identification, all in English.

● **MONACO**

Trans World Radio at 0720 on 7105 when presenting an evangelical programme in English.

● **CONGO**

R. TV Congolaise, Brazzaville, at 2014 on 15190 with primitively stirring African drums, chants and cries, the basis of all pop music!

● **CLANDESTINE**

The 'Voice of Iraqi Kurdistan' at 1810 on a measured 6941 with OM in Arabic, local music at 1815 then into Arabic harangue with both OM and YL speakers; lost under deliberate jamming at 1825. (See under Current Schedules).

● **AFGHANISTAN**

Radio Afghanistan at 1130 on 15195 with identification by OM and YL announcers in English, repeated twice, then news, commentary and 'Letter Box' programme, all directed to Europe.

● **PAKISTAN**

Radio Pakistan can be heard on many differing channels at various times throughout the day, here are some of those recently logged by us. On 4835 at 1603, OM with local news in English, sign-off at 1617 after talk by YL in English; on 7085 at 2035, identification by YL as 'World Service' then a newscast in English; on 15322.5 at 0917, programme of local music and songs; on 17770 at 1055, talk on India/Pakistan relations in English; on 17797 at 1059 interval signal (rather appealing and synonymous with the East), identification at 1100 in English then into Asian dialect and on 17910 at 1105, YL with news of Pakistan affairs at slow speed.

● **INDIA**

All India Radio can also be heard on many channels, both in the Overseas Service and the local Regional Services. On 3205, Lucknow at 1656 with local music and song programme; on 3295, Delhi at 1722 with local music and songs; on 3355, Kerseong at 1650 with OM and YL in duet; on 4800, Hyderabad with local music and Delhi on 11775 at 1005 with a newscast of Indian affairs in English.

● **KASHMIR**

Radio Srinigar at 1702 on 3277 when just fading in, local music and song programme.

● **MALAYSIA**

Penang on 4985 at 1510, announcements by OM in English, dance music Euro-style, songs in English, sign-off with National Anthem at 1630; Kuala Lumpur at 2220 on 4845, Indian-type songs and music in the Tamil Service; Kuching (Sarawak) at 2212 on 5005, OM with chants, YL announcer.

● **SRI LANKA**

Colombo on 4902 at 1622, local music and songs, Buddhist chants at 1703 after series of announcements; Colombo on 4870 at 1709, local music, OM with songs.

● **SINGAPORE**

Radio Singapore on 5010 at 1540 with programme of pop records (English), parallel on 5052.

● **INDONESIA**

RRI Jambi on 4927 at 1559 when signing-off with Hawaiian guitar rendering of 'Love Ambon' - a regular daily ceremony.

● **CAMBODIA**

We should really list this as Kmere Republic but most people refer to the country as Cambodia, except the pro-communist clandestine VUNFC (see last issue) who use the name Kampuchea. Anyway, listen on 4907 from around 1600 when you will hear the capital Phnom-Penh. We heard a programme of local pops, complete with guitars etc., must they copy our bad habits?

● **NIGERIA**

Lagos on 4990 at 2209, African songs and chants, also on 15120 at 2022 with a similar type of programme.

● **SWITZERLAND**

Berne at 0920 on 11775 and also in parallel on 9590, in English with 'Dateline', a programme about Swiss and European current affairs.

● **HOLLAND**

Hilversum at 0935 on 7210 with a current affairs programme in English.

● **CHINA**

Radio Peking at 1717 on 15095 with a talk in English on Chinese affairs.

● **GHANA**

Accra at 1730 on 3365, six pips and then news in vernacular by OM.

● **DOMINICAN REPUBLIC**

HJP Radio Commercial, Santo Domingo, on 4882 at 0620, OM with song in Spanish and typical local music.

HIBB La Voz del Papagayo, La Romana, on 5030 at 0622, Euro-type dance music records, identification at 0630 in Spanish.

● **VENEZUELA**

YVOI Radio Valera, on 4840 at 0400 with choral National Anthem at sign-off.

YVNM Radio Coro, on 4950 at 2247, songs in Spanish, Latin American style music.

YVNW Radio Bolivar, on 4770 at 0355, OM with song in Spanish, commercials with jingles, identification at 0356.

● **ECUADOR**

HCVP2 Sistema de Em. Atalaya, Guayaquil, on 4790 at 0417, LA music, two chimes then OM with identification.

● **HONDURAS**

HRVC Voz Evangelica, Tegucigalpa, on 4820 at 0422, a religious programme in English.

● **KASHMIR**

Azad Kashmir (Free Kashmir) on 3914 at 1812, local music, YL with songs, sign-off with (almost) endless choral anthem at 1835.

DIODE 'SORTER-OUTER'

By S. M. Peters

An inexpensive test circuit which is helpful when sorting out surplus diodes and rectifiers

A COLLEAGUE OF THE WRITER RECENTLY PURCHASED A batch of manufacturer's surplus silicon rectifiers by mail-order. On opening the pack he was a little surprised to find that the supplier had inserted a small note: 'Check polarity before use'. My colleague did this, to find that although all the rectifiers had the same shape, with the plastic housing curved at one end, the curved end was in some cases the rectifier anode and in other cases the rectifier cathode.

This is by no means an unusual state of affairs and it is, in any event, a wise course to check polarity with any unfamiliar or surplus diode, particularly if it is to be used as a rectifier in a power supply circuit. A rectifier connected wrong way round can cause havoc when the power supply is first switched on.

TEST UNIT

The test unit described in this short article requires few components and can be built in a relatively short time. The basic circuit approach is not new, but it may well be that the method of presentation of the results it gives is original.

The circuit of the 'Sorter-Outer' appears in Fig. 1, in which diagram T1 is a mains transformer having an 8 volt secondary. There are two test terminals, these being indicated in the diagram as 'A' and 'B'. The letters 'A' and 'B' are employed merely to identify the terminals for purposes of explanation in this article, and they do not appear as markings on the actual unit.

Let us now connect a diode to the terminals so that its cathode (the end marked with a plus sign in the diode symbol) connects to terminal 'B' and its anode to terminal 'A'. Thinking in terms of 'conventional current' (assumed to flow from positive to negative) the diode across the test terminals will then pass current during a.c. half-cycles in which the upper end of the 8 volt

transformer secondary is positive. This current will then flow, to the lower end of the secondary, via D2, R1 and light-emitting diode LED1, causing LED1 to light up. Current cannot flow in the LED2 circuit because it is blocked by D3. Similarly, current cannot flow through any part of the circuit on half-cycles which cause the upper end of the 8 volt secondary to be negative, because the current is then blocked by the test diode itself.

If the diode is connected to the test terminals with its cathode to terminal 'A', it will prevent the flow of

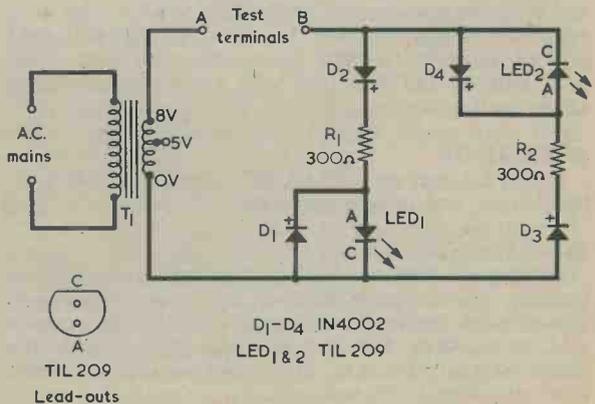


Fig. 1. The circuit of the diode test unit. Test diode polarity is indicated by illumination of one of the two light-emitting diodes

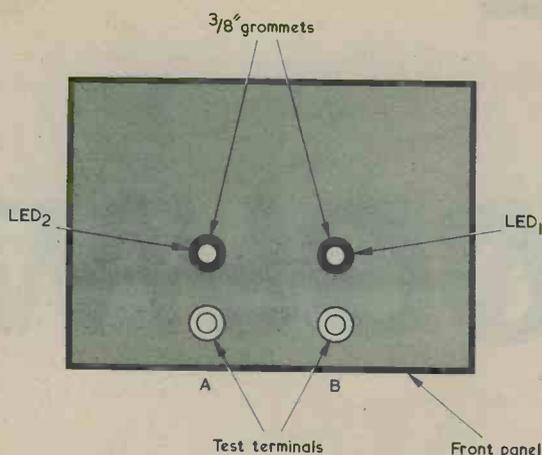


Fig. 2. A suitable front panel layout

current during half-cycles when the upper end of the 8 volt secondary is positive. It will, on the other hand, allow the passage of current when the upper end of the secondary is negative and the lower end is positive. This time the current flows from the lower end of the secondary through D3, R2, LED2 and the test diode to the upper end of the secondary. Light-emitting diode LED2 lights up.

Thus, LED1 lights up when the test diode cathode is at terminal 'B', and LED2 lights up when the test diode cathode is at terminal 'A'. When illuminated, the i.e.d.'s emit a bright red glow which one subconsciously associates with electrical positive or 'plus'. The front panel layout of the unit appears in Fig. 2, and it will be seen that LED1 is positioned alongside terminal 'B' and that LED2 is positioned alongside terminal 'A'. Connecting a diode to the test terminals results in a red (equals positive or 'plus') glow appearing at the terminal to which the diode cathode connects.

FURTHER POINTS

A few further points have to be dealt with before leaving the circuit of Fig. 1. It will be noted that diode D1 is connected across LED1 and diode D4 is connected across LED2. These two diodes are very probably not required but the author has included them to ensure that the reverse voltage across each i.e.d. cannot exceed 0.6 volt. Texas Instruments specify an absolute maximum reverse voltage of 3 volts for the TIL209 i.e.d. The reverse current which could flow through each i.e.d. via D2 or D3 is very low, but no reverse current figures for the TIL209 are available to the writer, and it was decided in consequence to follow an ultra-cautious policy and fit the two diodes D1 and D4. All the four diodes are silicon components type 1N4002.

Resistors R1 and R2 have a value of 300Ω and permit a current in each i.e.d. of about 30mA at half-cycle voltage peaks. Both resistors are 1/4 watt 5% types.

Transformer T1 is a small bell transformer of the type available in Woolworth's stores. Its secondary has

a 5 volt tap, which is unused. There is no mains on-off switch and the unit is simply plugged into the mains whenever it is required. If it is accidentally left plugged in after use no harm will result. Since T1 is a bell transformer it is intended to be continually connected to the mains supply, from which it draws negligible current when its secondary is unloaded.

As an added bonus the unit also indicates when a diode is short-circuited. Connecting a short-circuited diode across the test terminals causes both i.e.d.'s to light up. Neither diode will light up if the diode is open-circuited.

CONSTRUCTION

Component layout is unimportant apart from the fact that LED1 should be positioned alongside terminal 'B' and LED2 alongside terminal 'A'. The author used the front panel layout of Fig. 2, in which the i.e.d.'s have their bodies positioned in the centres of two 3/8 in. p.v.c. grommets. The dimensions of this front panel are approximately 3 1/2 by 2 1/4 in., and it is fitted to a box, 2 1/4 in. deep, which has the transformer mounted at the bottom. This is a case which the author happened to have on hand. Any other box, metal or plastic, of about the same size can be pressed into service. If the case is metal, the mains lead must pass into it through a grommet. The two terminals were insulated types having what are effectively sockets at the top into which the leads of diodes with wire ends can be quickly inserted. Wander socket plugs would be equally suitable. At the low voltages involved, the diode can be safely held in the fingers whilst being checked.

With the author's method of construction, the components were fitted to two 5-way tagstrips having the centre tag common with the mounting lug. These are secured to the rear of the front panel, whereupon wiring is carried out as illustrated in Fig. 3. The lead-outs of each i.e.d. are soldered to two of the tags, as shown.

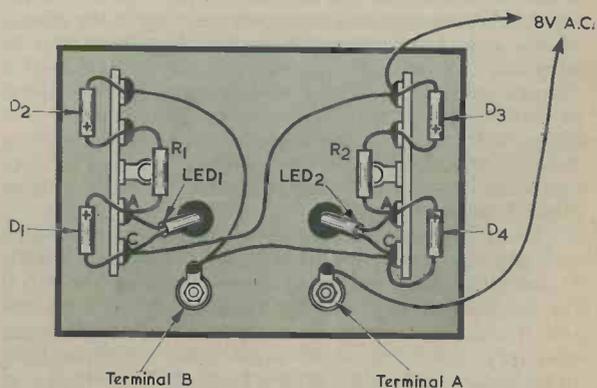


Fig. 3. All the components apart from the mains transformer can be mounted on the rear of the front panel

The author's unit has been in use for some months now, and has been successful in determining the polarity of a large number of silicon power rectifiers, as well as small silicon and germanium diodes. ■

PULSE COUNTING

By employing the pulse counting method of discrimination, this f.m. tuner performs as a superhet receiver having an i.f. amplifier which requires no tuned circuits at all. The tuner may be powered by a 9 volt battery or by a 9 volt power supply unit. Next month's concluding article will give details of construction and of setting up

Pa
By R. A

ALTHOUGH THE PULSE COUNTING TYPE OF F.M. TUNER has been popular in the past amongst home constructors it does not nowadays seem to be encountered as frequently, this being possibly due to the advent of low cost f.m. integrated circuits. It has also to be admitted that the pulse counting tuner is suitable for the provision of mono signals only, and that it cannot be employed for stereo reception. Nevertheless, if a high quality mono signal is required the pulse counting method still represents the simplest method of f.m. reception, and it still has economic advantages over other systems.

This article, together with a concluding article which will appear in next month's issue, describes a simple 6 transistor pulse counting tuner covering the v.h.f. f.m. band of 88 to 108 MHz. Provided it has a reasonably strong aerial signal the tuner is capable of giving an extremely good signal to noise ratio. With a fully modulated signal the a.f. output is about 250mV r.m.s. at an impedance of 5k Ω , and the unit is therefore suitable to feed a signal to virtually any power amplifier or tape recorder. The tuner can be either mains or battery powered, and it is housed in a home-made cabinet measuring 9½ by 7 by 4½ in.

BASIC CIRCUIT CONFIGURATION

A block diagram of the tuner is given in Fig. 1. As may be seen, the aerial couples to an r.f. amplifier stage. This stage provides very little gain, but it is nevertheless absolutely essential because it prevents radiation from the aerial of the oscillation produced in the following mixer-oscillator stage. The latter is a self-oscillating


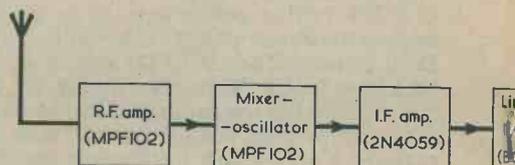


Fig. 1. Block diagram of simple f.m. tuner. This is a superhet and has RC coupling.

ING F.M. TUNER

Part 1

A. Penfold

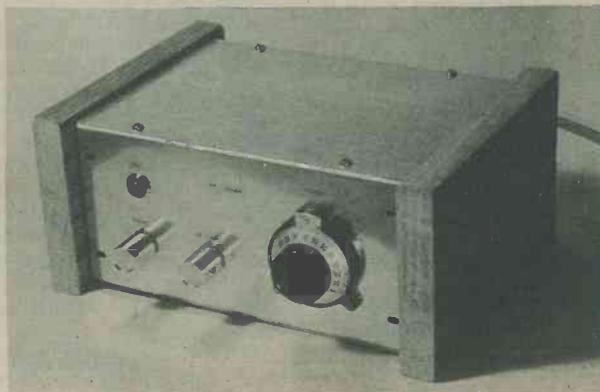


mixer and is tuned about 150kHz off the centre frequency of the received transmission. At the output of the mixer there are a number of v.h.f. signals together with the 150kHz difference frequency. The v.h.f. signals are filtered out, leaving the 150kHz signal, which is fed to the i.f. amplifier.

At the comparatively low frequencies involved here (about 225kHz maximum) ordinary RC coupled stages

can be employed in the i.f. amplifier. Silicon transistors with reasonably low values of collector load resistor are used, and the voltage gain will not be significantly lower than the high figure which would be given at ordinary audio frequencies.

The first i.f. transistor gives normal amplification. So does the second i.f. transistor, but this also provides amplitude limiting as well. Amplitude limiting is very important since it greatly reduces the noise and distortion which would otherwise be present on the final signal. The limiting process is extremely simple, and it relies upon there being a sufficiently large signal at the limiter stage for the signal to be automatically clipped. The voltage gain of the tuner is very high and can be in the neighbourhood of 100dB, or 100,000 times, whereupon only a fairly modest signal amplitude is required to initiate the limiting action. For instance, if an aerial signal of only 100 μ V r.m.s. is subjected to 100dB of linear amplification the output would be 10 volts r.m.s. However, the limiter stage, powered only by a 9 volt supply, could not produce such an output, and it would clip the signal to about 3 volts r.m.s. maximum. Thus, automatic limiting is achieved without circuit complications.

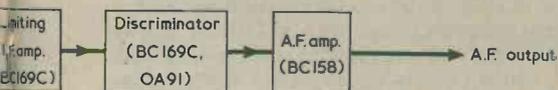

Showing the stages in the discriminator which incorporates 6 transistors operating in the i.f. stages

THE CIRCUIT

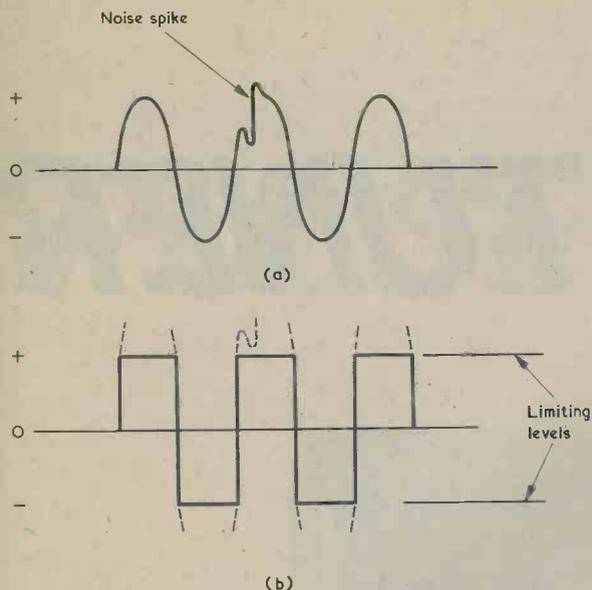


Fig. 2(a). A noise spike impressed on a signal waveform
 (b). The spike disappears if the signal is amplified such that the spike is outside limiting level

Fig. 2 illustrates how this clipping effects an improvement in the signal to noise ratio. Fig. 2(a) shows a hypothetical i.f. signal before clipping, together with a noise spike on the carrier. Fig. 2(b) shows the output of the limiter, and demonstrates that the noise spike has been removed since it is in the clipped portion of the signal. Obviously, if the signal is only poorly limited or the noise spike is very large the limiting action will only be partially effective. For this reason the highest signal amplitude must always be sought. The limiting action will of course reduce any form of noise which is modulated on to the carrier.

Another function of the limiter is to provide an output which has a constant voltage for the discriminator stage. The purpose of the discriminator is to produce an audio output signal which rises and falls in amplitude as the carrier rises and falls in frequency. If the amplitude of the signal at the input of the discriminator should vary with frequency, this will obviously cause distortion. The frequency response of the i.f. amplifier is not flat and would cause such distortion. However if, say, the response of the i.f. amplifier varies by 6dB over the range of frequencies involved, the resultant potential distortion will be eliminated if more than that 6dB of limiting is provided as the output voltage amplitude from the limiter will then be constant.

The a.f. output from the discriminator is insufficient to drive many amplifiers, and it is in consequence followed by a low gain audio stage.

The circuit diagram for the tuner is given in Fig. 3. TR1 is the r.f. amplifier, and this consists of a Jugfet (i.e. a junction gate field effect transistor) in the grounded gate mode. The output from TR1 is coupled to TR2 by the coupling winding L2. TR2 is basically a grounded gate Colpitts oscillator, using a second Jugfet. The oscillator coil is L3 and oscillator tuning is carried out by VC2. L4 is an r.f. choke. The output from the mixer is developed across R3. C5 bypasses the v.h.f. frequencies, leaving the required lower frequency i.f. signal. TR2 is very stable in operation, and no a.f.c. is required.

TR3 and TR4 are the i.f. amplifiers, TR4 operating also as the limiter. Both transistors function as straightforward common emitter amplifiers, and they provide the majority of the gain in the tuner.

TR5, in conjunction with D1, provides discrimination. The clipped signal from TR4 is applied via C9, and a series of fixed short duration pulses are produced across the collector load resistor, R9, there being one pulse for each input cycle. Thus, if input frequency increases, the average current through R9 increases also, causing the average voltage at TR5 collector to reduce. Similarly, if the input frequency decreases so does the average current in R9, with a consequent increase in the average voltage at TR5 collector. As a result, the average voltage at TR5 collector corresponds with the modulating voltage on the input signal. The series of pulses are at too high a frequency to be audible, but the average voltage at TR5 collector varies at audio frequency and constitutes the audio output of the discriminator.

TR6 is a common emitter audio amplifier having a fairly low gain due to the negative feedback provided by its unbypassed emitter resistor, R12. F.M. broadcast transmissions are given a certain amount of treble boost (pre-emphasis) as a simple method of noise reduction. The receiver must therefore be given a small amount of treble cut (de-emphasis) and this is the purpose of C12. In addition to providing treble cut, C12 also causes the pulses from TR5 to be integrated, thereby producing a conventional audio output. The collector load for TR6 is the potentiometer VR1, which acts as an output a.f. volume control. Resistor R11 is inserted in series with the positive supply to TR5 and TR6. This resistor causes hum level to be reduced when a mains supply is employed, and also decouples the positive supply lead if the tuner is power by a battery.

The method of reception employed in the tuner results in a somewhat unusual effect so far as tuning is concerned. Since the i.f. is only 150kHz a transmission can be tuned in both with the receiver oscillator 150kHz above the signal frequency and with it 150kHz below the signal frequency. With this low i.f. it is not feasible to provide r.f. tuned circuits which would allow reception at only one oscillator setting, and the overall effect is that there are two closely spaced dial settings at which each station can be received. Either of the dial settings may be employed. Since local stations on the f.m. band are well spaced out in terms of frequency, the double tuning effect has no adverse effect on performance.

Only two pre-set adjustments are required in the completed tuner. VR2 controls the amplitude of oscillation in TR2, and is adjusted to give the best sensitivity consistent with stable operation. VC3 is used to align the r.f. stage. No test gear is needed for either adjustment, and there is of course no complicated

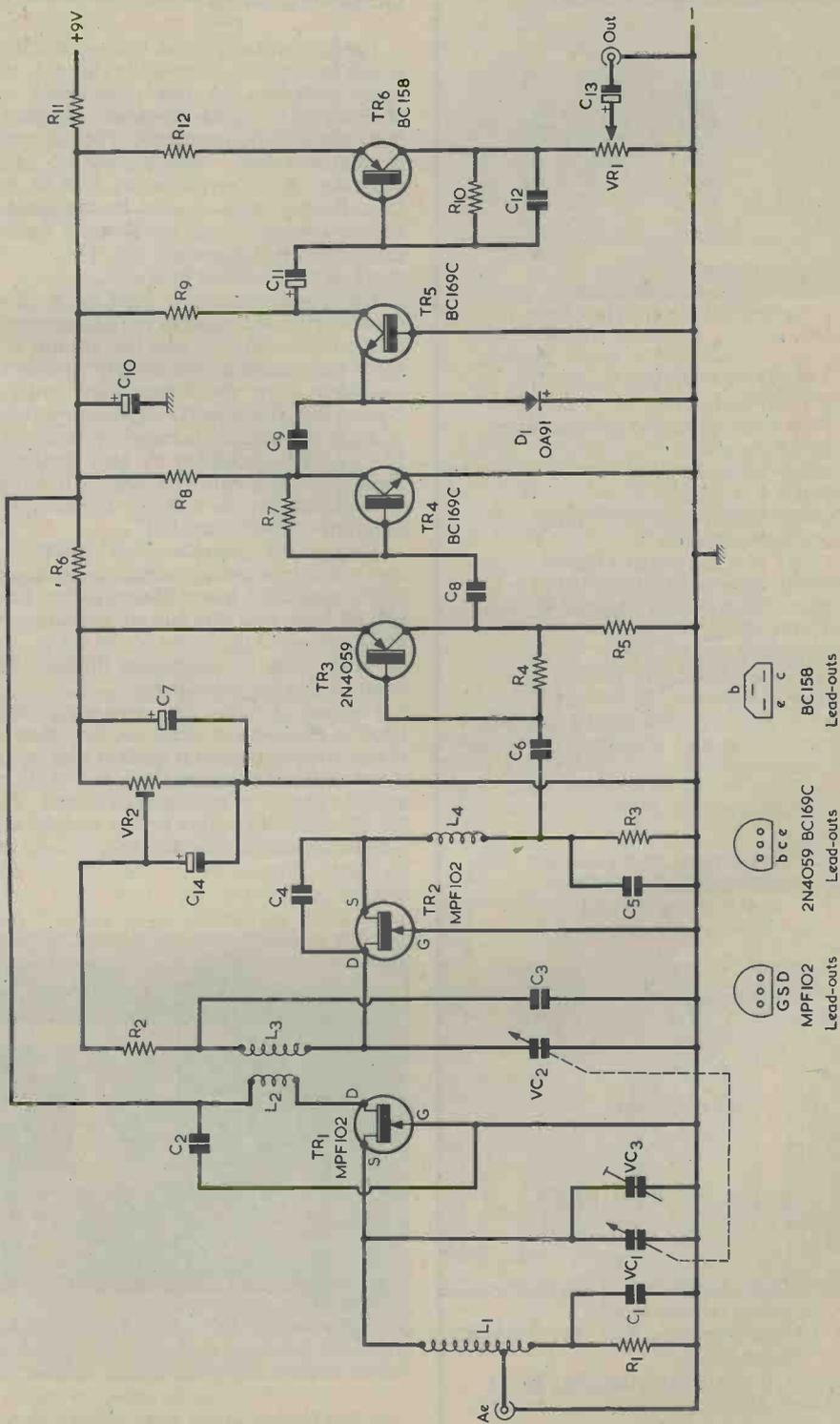


Fig. 3. The circuit of the f.m. tuner. This may be powered by a battery or by a mains supply unit

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

R1	330 Ω	R7	3.3M Ω
R2	1.5k Ω	R8	5.6k Ω
R3	10k Ω	R9	4.3k Ω
R4	820k Ω	R10	390k Ω
R5	6.8k Ω	R11	47 Ω
R6	820 Ω	R12	220 Ω

VR1	5k Ω potentiometer, log
VR2	10k Ω pre-set potentiometer, horizontal skeleton (see text)

Capacitors

C1	5,000pF disc ceramic
C2	0.022 μ F polyester
C3	560pF polystyrene or silvered mica
C4	4.7pF ceramic
C5	100pF ceramic
C6	0.022 μ F polyester
C7	100 μ F electrolytic, 10 V. Wkg.
C8	0.022 μ F polyester
C9	150pF polystyrene or silvered mica
C10	100 μ F electrolytic, 10 V. Wkg.
C11	10 μ F electrolytic, tantalum bead, 16 V. Wkg.
C12	4,700pF disc ceramic
C13	10 μ F electrolytic, 10 V. Wkg.
C14	10 μ F electrolytic, 10 V. Wkg.
VC1, VC2	15 + 15pF variable 2-gang (see text)
VC3	5pF air spaced trimmer, miniature (see text)

Inductors

(Details in Part 2)

L1, 2, 3	Aerial, coupling and oscillator coils, home-wound
L4	R.F. choke, home-wound

Semiconductors

TR1	MPF102	TR5	BC169C
TR2	MPF102	TR6	BC158
TR3	2N4059	D1	OA91
TR4	BC169C		

Switch

S1(a)(b)	D.P.S.T. rotary, toggle
----------	-------------------------

Miscellaneous

- 2 Knobs
- Vernier dial drive, 2 in., type T502 (Eagle)
- 2 tag strips (see Part 2)
- Coaxial socket
- Phono socket
- 2 'Universal' Chassis Sides, 8 by 4 in., Cat. No. CU56A (Home Radio)
- 6 4BA $\frac{1}{2}$ in. threaded spacers, Cat. No. 7/Z56A (Home Radio)
- Plain Veroboard, 0.1 in. matrix (see Part 2)
- Aluminium sheet, 18 s.w.g.
- Timber for cabinet ends (see text)
- 9-volt battery (optional - see text)
- Battery connectors (optional - see text)

i.f. and discriminator alignment, as occurs with a conventional f.m. tuner or receiver.


COMPONENTS

The components are in nearly all cases standard types which are readily obtainable through the normal mail-order suppliers. A few parts need some comment, however. C11 is, for instance, specified as a tantalum bead electrolytic capacitor. The capacitor needed here is available from Henry's Radio and a few other suppliers. VC3 is quoted as 5pF in the Components List. If this value cannot be obtained, the 10pF air-spaced trimmer listed by Henry's Radio as 'Type A1' can alternatively be employed. This component has been checked by the writer in practice.

The 2-gang capacitor used in the prototype has the construction indicated in the accompanying photograph of the tuner interior, and has a value of approximately 15pF each section. An exactly similar capacitor is not available from the larger mail order houses, but a 2-gang Jackson type 'O' capacitor having a capacitance of 16pF per section is listed by Home Radio. A 2-gang 25 + 25pF capacitor is also available from Home Radio, and this could be used as it stands, tuning being carried out over the first two-thirds of its travel from the minimum capacitance end.


The pre-set potentiometer specified for VR2 is a horizontal mounting skeleton component. The type 'PN', available from Electroval, Ltd., can be employed here, and this has tag spacing which allows it to fit directly into the holes of the 0.1 in. Veroboard panel on which the i.f. amplifier, limiter and discriminator components are mounted.

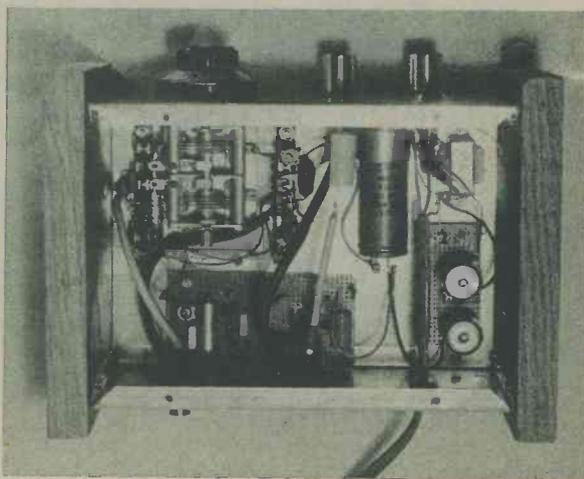Further details on remaining components will become apparent as these are discussed in the constructional information, and readers who have queries on any other parts are advised to wait until the concluding article appears in next month's issue. The parts needed for the optional mains power supply will also be dealt with in the concluding article.



The interior of the tuner when it is fitted with a mains power supply unit. Modular construction permits a clean and uncluttered layout

shows the positioning of the major components and the circuit modules. T1, C17 and the power supply unit component panel are not fitted if it is decided to have the tuner battery operated. The precise positioning of most of these parts is not critical, with the exception of the 2-gang tuning capacitor which must, of course, be positioned directly behind the tuning drive. Also, the r.f. and mixer modules should be positioned so that the two leads to the tuning capacitor fixed vane tags are reasonably short, and are not more than 1 in. long.

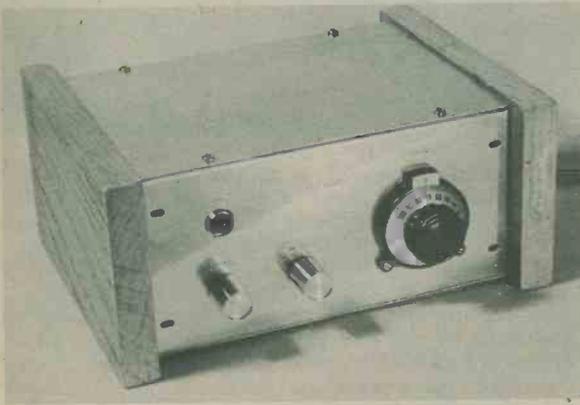


Another view of the front of the tuner. Legends cut from 'Panel Signs' Set No. 4 enhance the appearance

TUNING CAPACITOR MOUNTING

A mounting bracket is required for the 2-gang tuning capacitor VC1, VC2, and Fig. 6 shows two methods of providing this. The capacitor used in the prototype has its mounting holes on the underside of its frame and a bracket of the type shown in Fig. 6(a) is required. If the tuning capacitor has its mounting holes on its front plate (as has the Jackson type 'O' capacitor) the bracket should have the shape shown in Fig. 6(b). In both cases the purpose of the bracket is to raise the capacitor above the level of the tuner base plate and to align its spindle accurately with the tuning drive. No dimensions are given as these will depend on the particular capacitor employed. It is necessary for the capacitor and tuning drive to be aligned with reasonable precision as, otherwise, a smooth control of tuning will not be given.

The brackets in Figs. 6(a) and (b) are intended to be bolted to the base plate by means of 4BA bolts and nuts, and may be made from 18 s.w.g. aluminium. If possible, a thicker gauge of aluminium can be employed, should this be available, as it is desirable for the tuning capacitor to be mounted as rigidly as is reasonably possible.

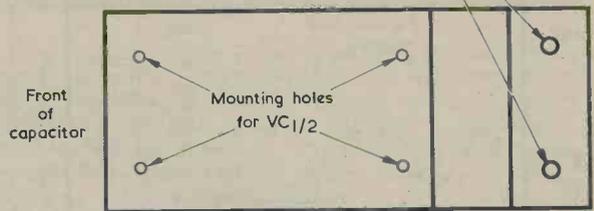
Mounting holes for securing bracket to base plate



Bent to this shape

(a)

Mounting holes for VC1/2

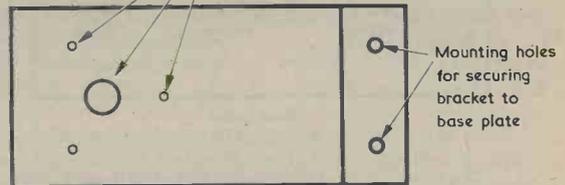

Bent to this shape

(b)

Fig. 6. The 2-gang tuning capacitor needs a mounting bracket to enable it to be mechanically aligned with the tuning drive. The bracket in (a) is suitable for capacitors having mounting feet, and that in (b) for capacitors with mounting holes in the front plate. Dimensions depend upon the capacitor employed

NEXT MONTH

The construction and setting up of the tuner will be described in next month's article. Details will also be given of the mains power supply unit.
(To be concluded)

DOUBLE REFLEX S.W. PERSONAL RECEIVER

In this receiver, described in the last October issue, D1 should be 1SJ50 and D2 1S44, and not as specified. The references to D2 at the end of the third line on page

153 and about two-thirds down the left column on page 154 now apply to D1.

AMSTERDAM RADIO EXHIBITION

FIRATO - 74



FIRATO - 74, HOLLAND'S RADIO AND T.V. Exhibition, was held recently. It is the 18th such exhibition and was thoroughly international in character, and was a good index of 'things-to-come' in the world of electronic entertainment; 24 countries exhibited.

Altogether there were 130 exhibitors; their exhibits covering radio and T.V., recording and playback equipment, video recorders, hifi audio equipment, aerial installations, electronic musical instruments, gramophone records, magnetic tapes, cassettes, etc., etc.

It was held in the Europa Hall, Amsterdam, and was jointly organised by RAI Gebouw B.V. and 'Stichting Firato Radiotoonstelling' (Foundation Firato Radio Exhibition).

We visited the exhibition on the first day, and from the crowds present, no one could doubt the popularity of this type of exhibition and the interest shown in what's new in this field.

The coming popularity of video tape recording of T.V. was apparent from equipment to be seen on a number of Stands. Video tape recorders of very reasonable size were to be seen and complete 'set-ups' of portable video recorder, T.V. camera of a size comparable to an 8 mm cine camera, and interface ancillary equipment, were available. The price is of course high, when compared to current home movie equipment prices, but for schools, etc., it is well within the sort of price they would be happy to pay, and without doubt, as production of this type of equipment increases, so prices will come down. We came across some interesting facts and figures on this question of cost.

A study of the price development of

radio, T.V. and sound reproduction equipment in recent years reveals that these products are far less sensitive to inflation than consumer goods in other trades. Price increases are indeed inevitable, as soon as the general percentage of inflation exceeds the percentage of the savings achieved by large production series and improved efficiency'.

There was a wonderful range of portable transistor radios on view - many quite sophisticated covering the full shortwave range of frequencies. Small portable mono cassette recorders of many varieties indicated the present popularity of this type of entertainment unit and some very elaborate stereo tape recorders provided the more serious recording enthusiast with ideas for future developments in his particular field of interest. Stereo radio reception was well covered by numerous makes of tuner, and the HiFi enthusiast continues to be well catered for by high quality record players.

An interesting feature of the Exhibition was the inclusion of musical instruments of the more conventional type, as well as the electronic variety. There were for instance, several stands showing band and orchestral wind instruments, as well as a good variety of electronic organs.

One or two interesting novelties caught our eye. One was a 'black box', called a 'Rhythm Maker'. It appeared to be an electronic oscillator making 'noise'. The unit appeared to feed into the aerial socket of a portable transistor radio, from the loudspeaker of which then issued much amplifier noise! The pitch and rhythm of this could be changed by controls on the

'black box'. The numbers of enthusiastic pop fans surrounding this exhibit prevented us from getting more details.

It is customary on the Continent, to take one's TV programmes from a variety of transmitters, located in different directions and as often as not in countries adjacent to one's own. At one time, most elaborate aerial arrays were to be seen, with antennae pointing to half a dozen or so TV stations located in different directions. The appearance was truly reminiscent of the proverbial 'christmas tree'! All this is giving way to rotators, so that one good directive aerial array can be swung round from one direction to another as required. The design of many of these arrays was interesting, and we were intrigued to see at least one making use of a small dish antenna - real Space Age Stuff!

We naturally were particularly interested in the exhibits by firms dealing in Constructional Kits. These we thought covered the field of Home Construction of radio and electronic projects very fully, and the kits appeared to be complete and well presented with a good deal of thought having gone into the instructions. The home construction of electronic equipment is obviously a quite well patronised hobby on the Continent.

As with most Exhibitions, one would have had to spend several days there to thoroughly cover all the exhibits shown. One short visit left us in no doubt however, that the European Electronics Industry has lots of 'goodies' up its sleeve for catching the eye of future customers.

Battery Voltage Monitor



By G. B. Brown

An ancillary circuit which prevents battery driven equipment operating at too low a supply voltage

QUITE A LOT OF TEST EQUIPMENT THESE DAYS IS BATTERY operated. A common practice here consists of incorporating a simple zener diode voltage regulator circuit to ensure that a stabilized supply voltage is available for the test equipment circuits. This is all very well in theory but, in practice, the voltage regulating circuit cannot normally cope with the situation where the battery voltage falls below the minimum at which the zener diode exerts control. What happens then is that the supply voltage in the equipment has a lower value than it should properly have, and the equipment is liable to give false readings or an otherwise incorrect performance. It is possible to guard against this state of affairs by periodically measuring the battery voltage or by fitting the equipment with a voltmeter. But the first of these approaches is tiresome and is liable to be forgotten, whilst the second incurs the expense of a permanently installed meter movement.

MONITOR CIRCUIT

The battery monitor circuit described in this short article allows the test equipment circuits to function as their own voltmeter. Above a predetermined level the supply voltage applied to the equipment is the same as the battery voltage (minus a small voltage dropped across a turned on transistor). This situation continues down to the predetermined battery level; but below this level the supply voltage to the equipment falls very rapidly with only a small further decrease in battery voltage.

With the author's circuit, the nominal supply voltage is 9 volts and the predetermined level approximately 8 volts. Below the predetermined level the supply voltage to the equipment falls to 5 volts for a decrease in battery voltage of only 0.1 volt, to 3 volts for a battery voltage decrease of 0.2 volt and to 1 volt for a battery voltage decrease of 0.3 volt. The test equipment will give an obvious indication of low supply potential at these rapidly falling voltages, and will thereby indicate that a new battery is required.


In the circuit the zener diode gives a reference voltage of 6.8 volts, this being maintained at battery voltages below 8 volts by means of R1. TR1 and TR2 form a compound amplifier having a total current gain, typically, of some 15,000 times. Thus, a very small current in TR1 base is capable of turning TR2 hard on. As battery voltage decreases the voltage at the upper end of R2 falls at the same rate, whereupon there is a rapid transition from the conducting to the non-conducting state in the transistors as the two silicon diodes, D1 and D2, cease to pass forward current.

The voltage at which the transistors turn off is dependent upon the actual zener voltage, within tolerance, of ZD1 and the forward voltage-current characteristics of D1 and D2. If turn-off occurs at too high a voltage, one of the diodes may be removed from circuit. Lower turn-off voltages may also be achieved by using a 6.2 or a 5.6 volt zener diode in the ZD1 position.

Resistor R3 is a current limiting resistor and its function is to prevent excessive charging currents passing through TR1 when a high value electrolytic capacitor is connected across the equipment supply rails immediately after the monitor circuit. If such a capacitor is not fitted, R3 may be omitted.

The author's unit gave a satisfactory performance for load currents from 5.5 to 60mA. With a 60mA load current there was an 0.5 volt drop across R3 and TS2, of which nearly 0.2 volt was due to R3. The monitor circuit incurs a drain on the battery of 1.5mA at 9 volts.

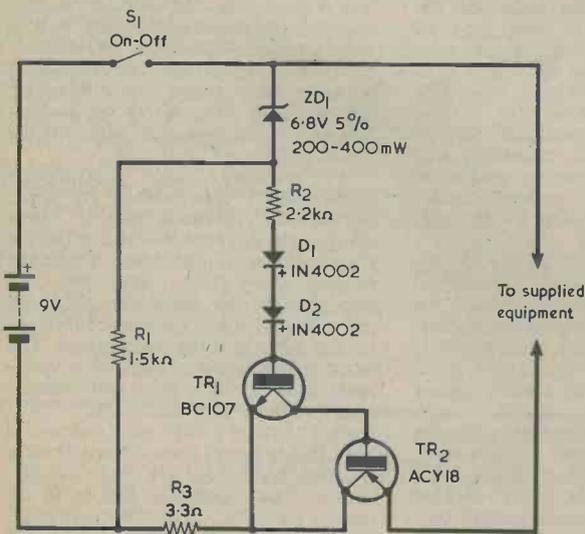Circuit of the battery voltage monitor. This ensures that the supply voltage passed to the subsequent equipment falls to a very low value for battery voltages below 8 volts



ACY18 BC107
Lead-outs

R1 - R3 1/4 watt 10%

THREE WAVEBAND TRANSISTOR PORTABLE


Part 1.

By
Sir Douglas Hall, K.C.M.G.,
M.A.(Oxon)

Covering long waves, medium waves and a short wave band from 19 to 60 metres, this receiver incorporates a 2-transistor reflex circuit which offers considerable amplification after its single aerial tuned circuit. Circuit operation and construction are described here, and next month's concluding article will give details of setting up and the assembly of a suitable case

THIS IS A THIRD ARTICLE DESCRIBING THE CONSTRUCTION of a receiver incorporating a new double reflex circuit which has been introduced by the author to readers of this magazine. The first article appeared in the May 1974 issue, and dealt with the 'Bifexette', a small 2-transistor portable covering medium and long waves and giving speaker reception of the more powerful stations. A double reflex short wave personal receiver was described in the second article (published in the October issue) and this consisted of an earphone receiver which required no external aerial or earth connection and which covered the short wave bands from approximately 19 to 50 metres.

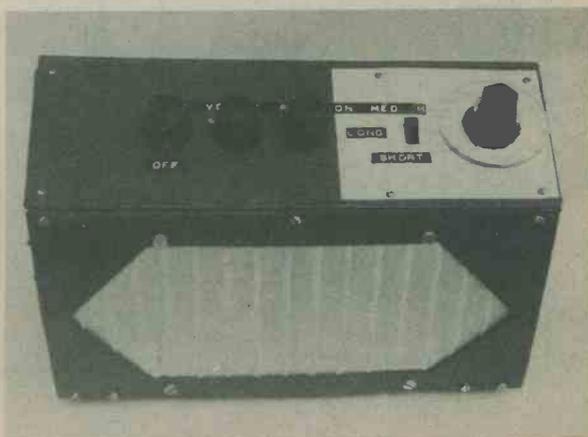The present article is devoted to the construction of a quite powerful three waveband portable working on long and medium waves and a short wave band extending from about 19 to 60 metres. Good loudspeaker reception is provided from a large number of stations on all three bands.



The completed receiver. This covers long, medium and short waves, and incorporates a sensitive reflex amplifying circuit

THE CIRCUIT

The circuit of the present receiver is shown in Fig. 1, in which TR1 and TR2 appear in the double reflex circuit. The operation of this configuration was discussed in detail in the article which dealt with the 'Biflexette', but a brief description will now be given as some readers may not have seen the earlier article or have it available. TR1 functions, at r.f., as a voltage amplifying f.e.t., feeding into TR2 which acts as an emitter follower. The r.f. signal is built up across L5, and diodes D1 and D2 provide detection. D1 offers a barrier to the passage of radio frequency current for purposes of reaction unless a small forward direct current is made to pass through it. This current is provided by the network comprising R2, VR1, R3 and R1, and its level is controlled by VR1. Since it varies the forward current in D1 and, hence, the impedance this diode presents to r.f. current, VR1 functions as a reaction control. A larger direct current is required on the short wave band, and this is obtained by short-circuiting R2 when short waves are selected.

Regeneration is in the Colpitts mode and C1 provides the tap into the tuned circuit on short waves. This

capacitance is augmented on medium waves by C2, whilst on long waves C4 comes into use in parallel with C1. This is by way of choke L4, which offers a relatively low impedance at long waves and a considerably higher impedance at medium and short waves. Using a choke in this manner saves the extra switching which would otherwise be required, and it becomes possible to employ a simple 2 pole 3 way switch for wavechange purposes. The author used a double pole slide switch having a central off position.

The a.f. signal which appears after detection is passed, via the ferrite rod aerial coils, to the gate of TR1, which once more functions as a voltage amplifier coupling to the base of TR2. This time TR2 operates as a common emitter amplifier, and the a.f. signal at its collector appears across volume control VR3. The signal at VR3 slider is then passed to the 'sliding bias' a.f. amplifier incorporating TR3 and TR4. Under no-signal conditions, base bias for TR3 is provided by way of VR4, D3 and R6. The collector current of TR3 is the base current for TR4, and VR4 is adjusted so that a small quiescent current flows in the two transistors. When an a.f. signal is applied to the amplifier it is rectified by D3 to produce an increased base bias current

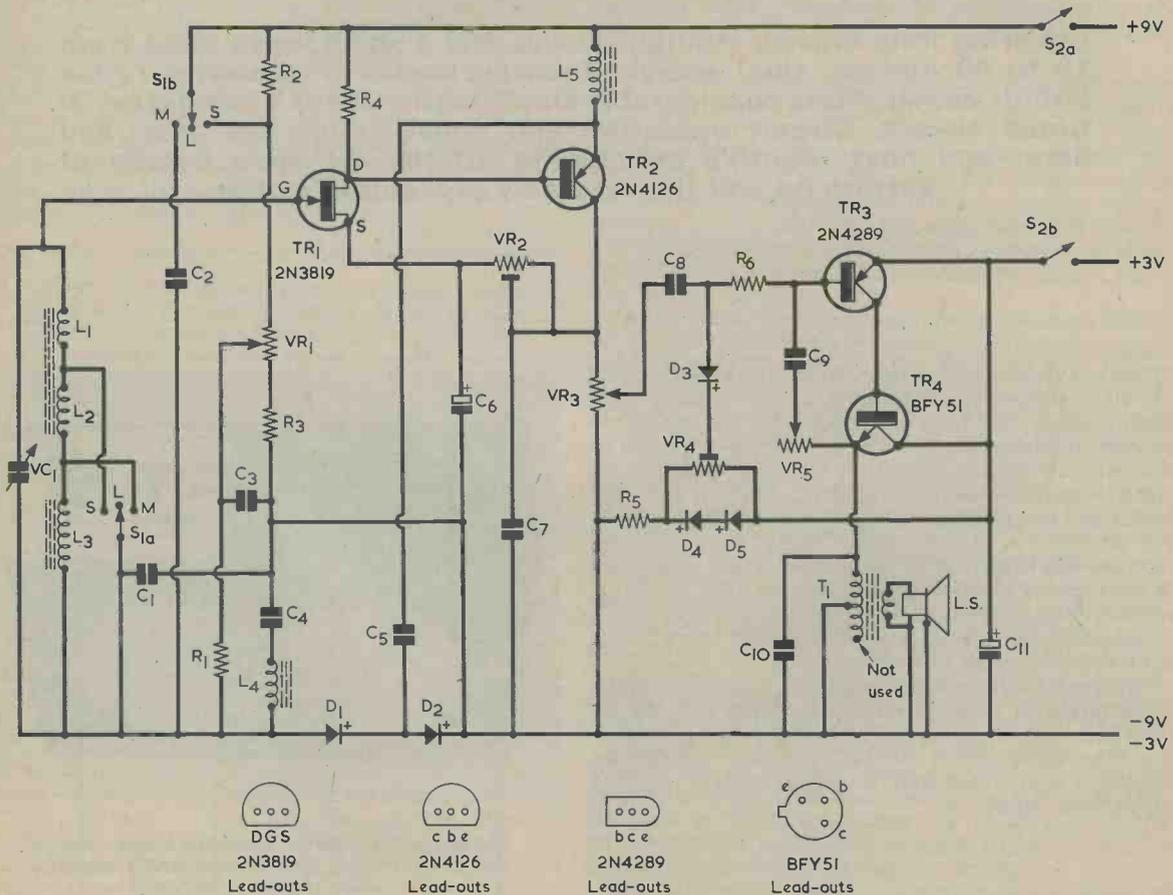


Fig. 1. The circuit of the three waveband transistor portable. TR1 and TR2 appear in a reflex circuit which offers amplification both at r.f. and at a.f.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10%)

R1	470k Ω
R2	1.5M Ω
R3	100k Ω
R4	3.9k Ω
R5	1k Ω
R6	10k Ω
VR1	500 or 470k Ω potentiometer, linear
VR2	27k Ω pre-set potentiometer, miniature slide
VR3	1k Ω potentiometer, log
VR4	1k Ω pre-set potentiometer, miniature skeleton
VR5	250 or 220k Ω potentiometer, log, with switch S2(a)(b)

Capacitors

C1	27pF silvered mica or ceramic
C2	68pF silvered mica or ceramic
C3	0.1 μ F polyester
C4	180pF silvered mica or ceramic
C5	1,000pF silvered mica or ceramic
C6	100 μ F electrolytic, 6.4 V. Wkg.
C7	0.1 μ F polyester
C8	0.1 μ F polyester
C9	0.01 μ F polyester
C10	0.1 μ F polyester
C11	800 μ F electrolytic, 4 V. Wkg.
VC1	150pF variable (see text)

Inductors

L1, L2, L3	see text
L4	1.5mH r.f. choke, type CH5 (Repanco)
L5	1.5mH r.f. choke, type CH5 (Repanco)
T1	Output transformer type TT56 (Repanco)

Semiconductors

TR1	2N3819
TR2	2N4126
TR3	2N4289
TR4	BFY51
D1	1SJ50 (R.S. Components)
D2	1S44
D3	1S44
D4	1S44
D5	1S44

Switch

S1(a)(b)	double pole switch, centre off, slide or toggle (see text)
S2(a)(b)	d.p.s.t. switch, part of VR5

Speaker

3 Ω speaker, 8 by 5 in.

Batteries

9 volt battery type PP3 (Ever Ready)
3 volt battery No. 800 (Ever Ready)

Miscellaneous

Ferrite rod, 7 by $\frac{3}{8}$ in.
Ferrite rod, 3 by $\frac{3}{8}$ in.
Ball drive type 4511/F (Jackson Bros.)
Spindle coupler type EH16 (Bulgin)
18-way group board (see text)
PP3 battery connector
4 knobs
4 small rubber feet
2 small brass hinges
 $\frac{1}{4}$ in. plywood
S.R.B.P. ('Paxolin') sheet
Fablon or Contact
Packet 1 in. spring clips No. LK2761 (Lektrokit)
Packet $\frac{3}{8}$ in. spring clips No. LK2721 (Lektrokit)
Speaker fabric
Bolts, nuts, washers, etc.

for TR3. The circuit functions such that, up to the overload point, the base bias available for TR3 is always greater than that needed to amplify the signal. This circumstance is achieved due to the negative feedback given by VR5 and C9, which reduces the gain of TR3 and TR4, together with the standing quiescent current which is initially present. Thus, TR3 and TR4 offer Class A amplification of the a.f. signal, drawing a current from the 3 volt supply which increases as signal strength increases. VR5 is made variable so that it may also function as a tone control.

D4 and D5 are included in circuit to stabilize the voltage across VR4, and thereby maintain the standing bias for TR3 as the battery voltage falls. These are silicon diodes and each gives a forward voltage drop of around 0.6 volt.

Transformer T1 couples TR4 to a 3 Ω loudspeaker. The transformer ratio employed is a little over 4:1, and presents a load of approximately 50 Ω to the emitter of TR4. A 35 Ω speaker could have been used instead, thereby dispensing with the need for a transformer. However, such a speaker offers a relatively high resistance, causing much of the available battery voltage to be lost and the audible volume at maximum output to be considerably reduced. Transformer T1 has a low

primary resistance and allows a higher output to be obtained. The need for a low resistance load for TR4 is of particular importance when a 3 volt supply is used. A 3 volt supply is attractive because it can be provided by an Ever Ready No. 800 (or equivalent) twin cell cycle lamp battery and this, at the time of writing, offers more power per penny than any other dry battery available.

COMPONENTS

Some points concerning the components required need to be dealt with next.

VR1, VR3 and VR5 should be small components. Those used by the author were type P20, available from Electrovalue Ltd., and having a body diameter of 0.79 in. Any other potentiometers of similar or smaller size may be employed. If difficulty is experienced in obtaining the 1k Ω log component required for VR3, a 5k Ω potentiometer may be employed instead with a 1.2k Ω resistor connected across its outside tags. The pre-set miniature slide potentiometer, VR2, is listed by Home Radio under Cat. No. VR101A. In the prototype, VC1 is an old but excellent Eddystone short wave air-spaced component. A suitable alternative is the Jackson



The parts which are visible inside the receiver when the hinged case is opened up

type C804 variable capacitor of the same value. Do not use a variable capacitor having metal end plates. Apart from D1 the semiconductors are generally available. It is essential to employ properly marked transistors. So-called equivalents may well be found not to work in this circuit. D1 is an R.S. Components diode type 1SJ50.

An 18 way group board is required. This is an R.S. Components 'Standard' group panel.

Two ferrite rods are employed, one being 7 in. by $\frac{3}{8}$ in. and the other 3 in. by $\frac{3}{8}$ in. Both of these will have to be obtained from a longer length of rod. The rod is marked with a file at the appropriate point and the excess then snapped off. The rods can be any grade other than blue grade, the latter being distinguished by a blue coding at one end. Blue grade ferrite is a low permeability type which is not suitable for the present receiver. It was handled by R.S. Components until a few years ago, and has since been discontinued. However, small stocks may still be held by some retailers.

As was mentioned earlier, the wavechange switch used by the author was a double pole slide switch having a centre off position. This type of switch is not advertised by the large mail order houses but readers who are fortunate enough to live near component retailers may be able to obtain one. Failing this, a double pole toggle switch with a centre off position can be employed. In the appropriate constructional diagrams which follow, the slide switch is assumed.

A flexible spindle coupler is required for VC1 and this should be an insulated type. The Bulgin type EH16 coupler can be employed here. In the hardware category are two small brass hinges, two 4BA bolts 2 in. long, two 4BA bolts $1\frac{1}{2}$ in. long and two 4BA bolts $1\frac{1}{2}$ in. long. The 9 volt PP3 battery is held by a 1 in. spring clip (Lektrokit LK2761) and the 7 in. ferrite rod by two $\frac{3}{8}$ in. spring clips (Lektrokit LK2721). These clips are available, in packets of ten, from Home Radio.

The speaker employed should have dimensions which do not exceed 8 in. by 5 in. by 3 in. If a speaker having any of its dimensions larger than these figures is used it will be necessary to amend the corresponding dimensions of the plywood and s.r.b.p. ('Paxolin') panels on which the parts are assembled.

CONSTRUCTION

Construction starts by taking the group board and cutting off three and a half pairs of tags (seven tags in all) so that it has the appearance shown in Fig. 2. Drill three $\frac{3}{8}$ in. holes to take the bushes of VR1, VR3 and VR5. Then fit these three components and wire up these and the other parts in the manner illustrated in Fig. 2. For ease of presentation, some components are shown outside the group board in the diagram, but in practice they should all be within the group board outline. All component wiring should be as short as is reasonably possible. Transformer T1 is fitted by soldering its mounting lugs to the two tags shown.

Next turn to Fig. 3, which shows three items, all of which are cut from s.r.b.p. sheet. The item in Fig. 3(a) is merely a bracket, and its large hole takes a grommet in which is fitted the 3 in. ferrite aerial rod. The piece in Fig. 3(b) is a platform on which are mounted the PP3 battery and the No. 800 battery. The No. 800 battery is fitted between two 4BA $1\frac{1}{2}$ in. bolts at holes E and C, with its positive terminal strip pressing against the bolt at hole C. A solder tag is fitted below at hole C, and the bolt provides the positive connection to the battery. A 4BA $\frac{1}{4}$ in. bolt at hole D, with a solder tag below, picks up the negative connection from the battery. When the battery is later fitted, its negative terminal strip is downwards, in contact with the $\frac{1}{4}$ in. bolt. The battery is then held down by means of the item shown in Fig. 3(c), this passing over the $1\frac{1}{2}$ in. bolts and being secured by 4BA nuts on the top. The positions of holes A and B in Fig. 3(b) depend upon the speaker mounting holes, as also does the small hole in Fig. 3(a), and these three holes are marked out and drilled later.

Cut out a piece of Fablon 2 in. by 3 in. and leave all the backing paper on except for a $\frac{1}{2}$ in. strip along one of the 2 in. sides. Wind the Fablon on to the 7 in. ferrite rod to form a loose-fitting sleeve 2 in. long. The $\frac{1}{2}$ in. strip of exposed adhesive is last to be wound on and it thereby secures the end of the Fablon to itself. Wind 11 turns of 26 s.w.g. enamelled wire on this sleeve with the turns spaced out so that the coil length is $1\frac{1}{2}$ in. Leave a few inches of wire at each end for later connections, securing the coil ends with a suitable adhesive tape. This is L1. Cut out a piece of Fablon $2\frac{1}{2}$ in. by 3 in. and make a similar sleeve, $2\frac{1}{2}$ in. long, for the 7 in. ferrite rod. Wind on 80 turns of 26 s.w.g. enamelled wire in a single layer with each turn touching the next. This coil is L2. Fit the two windings to the 7 in. rod so that they occupy the appropriate positions shown in Fig. 4(b). Both windings are in the same direction so that, when their inner ends are connected together, they are series-aiding. Make up a third Fablon sleeve $2\frac{1}{2}$ in. long in the same manner as the two previous sleeves. This is fitted to the 3 in. ferrite rod. Wind on four pies of 90 turns each (360 turns continuous in all) of 38 s.w.g. enamelled wire. The pies may be about $\frac{3}{8}$ in. wide and each separated from the next by about $\frac{1}{8}$ in. This last coil is L3 and the winding of the ferrite aerial coils is now completed.

A $\frac{1}{4}$ in. plywood panel measuring $8\frac{1}{2}$ by 3 in. is next cut out. This is the lower panel shown in Fig. 4(b) and the 7 in. ferrite rod is, later, fitted to this so that the rod and its mounting clips are just inside the adjacent long edge of the panel. A free margin of at least $\frac{1}{4}$ in. should be maintained inside the two 3 in. edges to take the edges of the receiver cabinet. Stick a piece of Fablon onto the panel over the area where the group board will

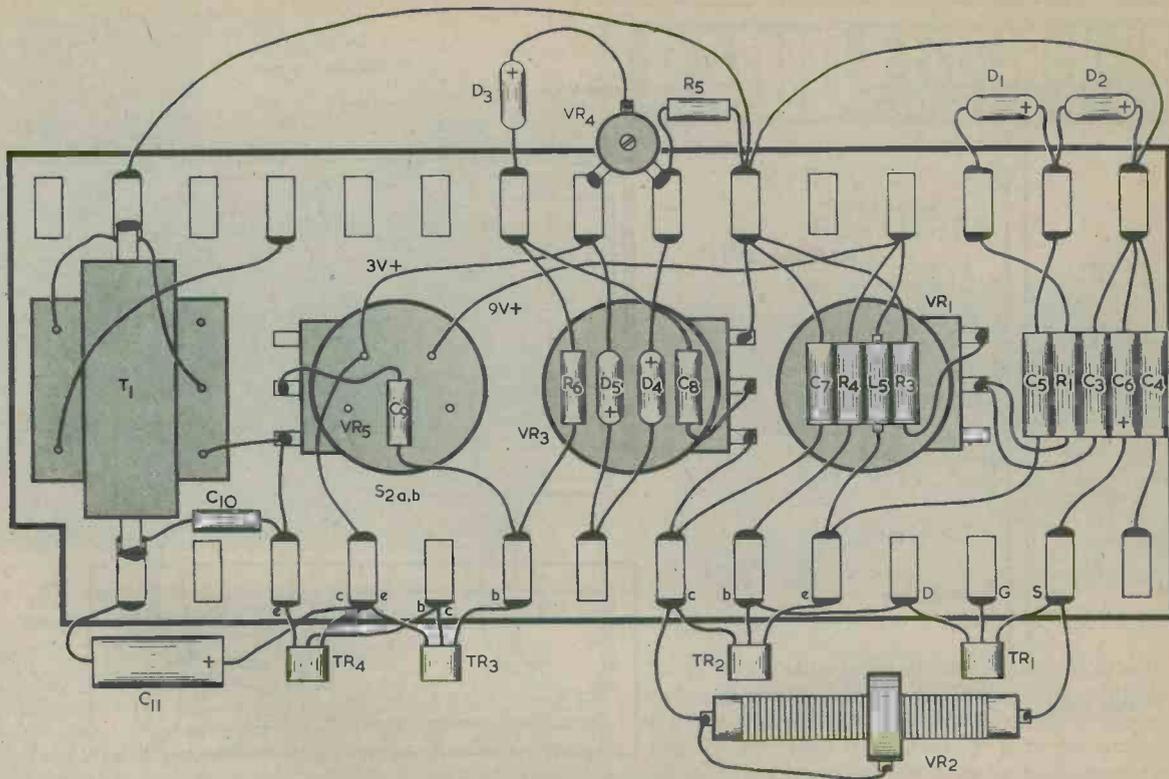


Fig. 2. Wiring on the group board. The 3 volt and 9 volt positive leads connect to separate poles of S2(a)(b)

be mounted, and make three holes to accept the bush mounting nuts of VR1, VR3 and VR5. The potentiometer spindles should be along the horizontal centre line of the panel, and this should allow just sufficient space on the panel for the 7 in. ferrite rod and its clips. Make a rectangular hole and two mounting holes for the slide switch S1(a)(b), or a single hole if a toggle switch

is used here. The switch is just to the right of the group board, as seen in Fig. 4(b).

Also to be mounted are the tuning drive and flexible coupler for VC1, of which details are given in Fig. 4(a). A $\frac{3}{8}$ in. hole is required for the flange of the tuning drive, and its centre is on the horizontal centre line of the panel and 1 in. in from the adjacent 3 in. edge. The capacitor

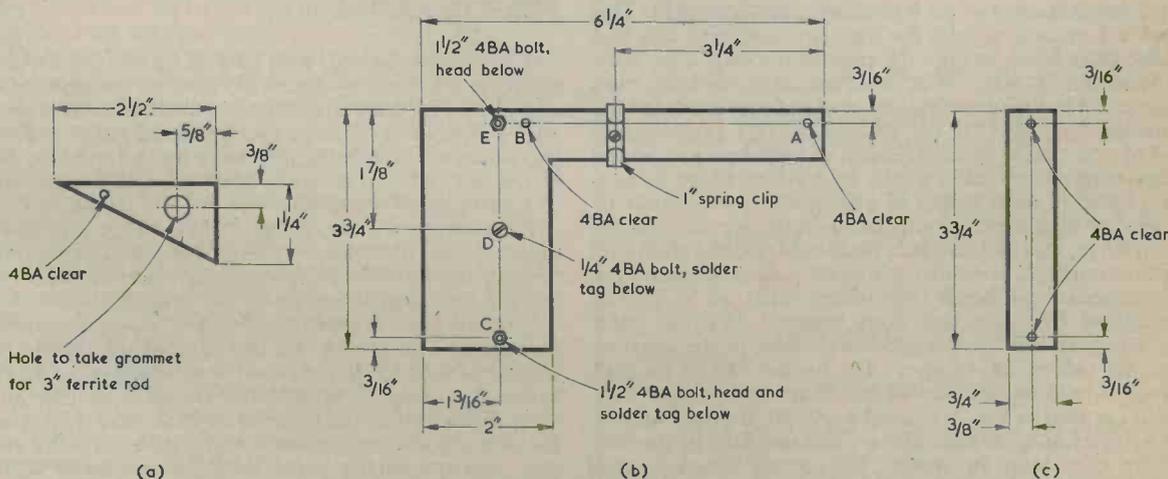


Fig. 3(a). The s.r.b.p. bracket on which the 3in. ferrite rod is mounted. The 4BA clear hole passes over one of the speaker mounting bolts
 (b). Dimensions of the battery platform. The 4BA clear holes, A and B, pass over two of the speaker mounting bolts, and their positions depend upon the positioning of the corresponding mounting holes in the speaker frame
 (c). The strip which secures the 3 volt battery

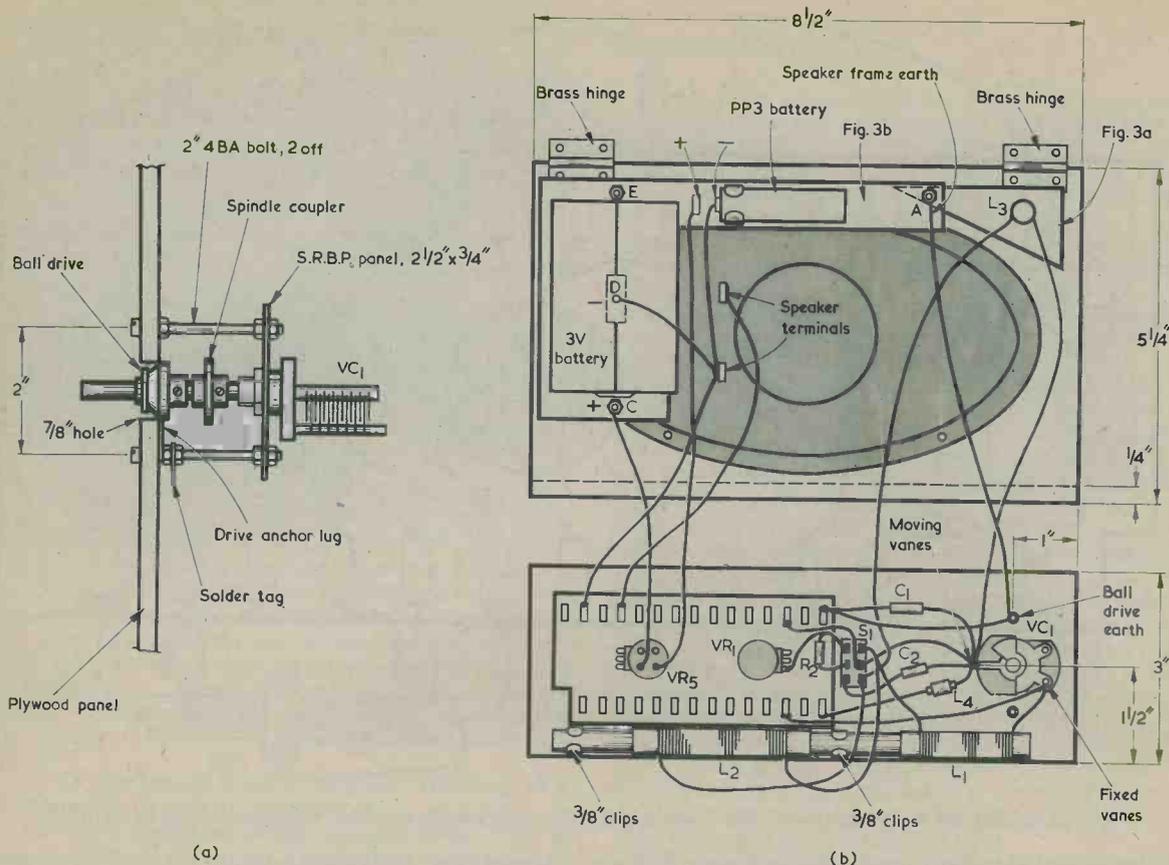


Fig. 4(a). Illustrating the manner in which VC1 is coupled to the ball tuning drive
 (b). Final wiring steps on the plywood and speaker panels. Ensure that the two connections to S2(a)(b) on the group board correspond with the 3 volt and 9 volt switch poles shown in Fig. 2

is fitted to a strip of s.r.b.p. measuring $2\frac{1}{2}$ by $\frac{3}{4}$ in. This has a $\frac{3}{8}$ in. central hole for the capacitor bush and two 4BA clear holes to take the ends of the 4BA 2 in. bolts shown in Fig. 4(a). These space the capacitor back from the panel in the manner illustrated, leaving space for the insulated coupler. If the spindle of VC1 projects forward too much it may be cut, as appropriate, or the capacitor spaced back a little by washers on its mounting bush. A short length of $\frac{1}{4}$ in. spindle, which may be metal or insulated, appears between the coupler and the ball drive, and this can be a piece cut from the shaft of a potentiometer, or similar component. It is necessary for the spindle, and hence the moving vanes, of VC1 to be insulated from the ball drive because, to avoid hand capacitance effects, the latter is earthed to the negative supply rail of the receiver. The anchor lug of the ball drive is held under the 4BA nut securing the upper 2 in. bolt (as seen in Fig. 4(b)) and a second 4BA nut secures a solder tag to which the earth connection to the ball drive may later be made. The group board is now affixed to the plywood panel with short wood screws or countersunk bolts and nuts, after which S1(a)(b) and the VC1 mounting assembly are also fitted. It may be necessary to cut a small piece from a corner of the $2\frac{1}{2}$ by $\frac{3}{4}$ in. s.r.b.p. strip to give clearance for the speaker frame.

FERRITE AERIAL

The 7 in. ferrite rod, with L1 and L2 on it, is fitted to the plywood panel by means of two $\frac{3}{8}$ in. spring clips, as shown in Fig. 4(b). The clips are positioned as shown, with L2 between the clips and L1 to the right of them, this latter winding being free to be moved over the end of the rod. When it is finally adjusted, one or two turns of L1 will be off the rod.

Next cut out a piece of s.r.b.p. $8\frac{1}{2}$ by $5\frac{1}{4}$ in. This is the upper panel illustrated in Fig. 4(b), and it has the speaker mounted on it. The speaker is fitted such that there is $\frac{1}{4}$ in. clear below its bottom edge, as seen in Fig. 4(b). If the speaker width is exactly 5 in., its upper edge will then be flush with the top edge of the panel. The surface of the s.r.b.p. panel below the speaker is screwed to the edge of the plywood panel when the two are, later, secured together. Mark out and drill four 4BA clear mounting holes for the speaker and then cut out a suitable aperture in the panel. Drill several holes at the bottom of the panel for the screws which will pass into the edge of the plywood panel. Four holes for the two hinges are also required, but it is better to leave these until later, when the case is being made up.

Bolt the speaker in place over a piece of speaker fabric. The two lower speaker mounting bolts in Fig.



The internal components, as seen from one side of the receiver

4(b) are $\frac{1}{2}$ in. long. The two upper bolts are $1\frac{1}{4}$ in. long and the first to be fitted is that at the left in the diagram. Before fitting the upper right-hand bolt scrape away the enamel at the speaker frame so that an earth connection may be made to this frame. Solder a piece of flexible wire to a 4BA solder tag, then fit the right hand bolt, securing the tag under the nut. Take up the s.r.b.p. piece of Fig. 3(a), and mark out and drill the 4BA clear hole in this such that, when it is passed over the upper right-hand speaker bolt, the piece will take up the position shown in Fig. 4(b). The right hand edge of the s.r.b.p. piece should be at least $\frac{1}{4}$ in. in from the adjacent $5\frac{1}{2}$ in. edge of the speaker panel. Fit the grommet and the 3 in. ferrite rod with L3 to the s.r.b.p. piece, pass the latter over the 4BA speaker bolt and secure it with a second 4BA nut. The 3 in. ferrite rod projects upward, perpendicular to the speaker panel.

Take the s.r.b.p. battery panel of Fig. 3(b) and mark out and drill the 4BA clear holes, A and B, on this such that, when the panel is passed over the two $1\frac{1}{2}$ in. speaker bolts, it takes up the position illustrated in Fig. 4(b). The left-hand edge of the platform should be at least $\frac{1}{4}$ in. in from the adjacent $5\frac{1}{2}$ in. edge of the speaker panel, and the upper edge (as seen in Fig. 4(b)) should be inside the top edge of the speaker panel. Solder a flexible lead to the solder tag at hole C of the platform and another lead to the tag at hole D. Fit a further nut over each of the $1\frac{1}{2}$ in. speaker bolts, pass the battery platform over these bolts, and fit two final nuts on top of the platform. Adjust these last four nuts so that the platform is held in a level position and just touches the frame of the speaker.


Complete the wiring shown in Fig. 4(b), this including C1, C2, R2 and L4. The wiring is carried out with the two panels disassembled.

The major part of construction is now complete. Next month's concluding article will deal with the procedure of setting up and the assembly of a case. The two panels of Fig. 4(b) are not secured together until the setting up has been completed.

(To be concluded)

RADIO & ELECTRONICS CONSTRUCTOR

OUR NEXT ISSUE FEATURES

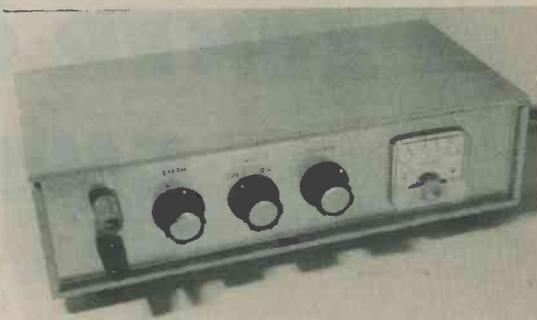

Offers a continuously variable output voltage ranging from 2.5 to 25 volts. This power supply unit features automatic output limiting for currents in excess of 600mA and a constant current voltage stabilizing reference circuit.

Many other articles
including

RADIO 2 CONVERTER

A novel converter unit allowing a medium wave transistor portable to receive the long wave Radio 2 signal. The converter output couples inductively to the medium wave receiver ferrite aerial and no interconnections are needed.

• • •
**LIGHT-EMITTING
DIODE CIRCUITS**

• • •
USUAL FEATURES

• • •
ORDER NOW

Price 25p

ON SALE 1st JANUARY

RADIO & ELECTRONICS CONSTRUCTOR

'NOTES FOR NEWCOMERS'

ZENER CLIPPING CIRCUITS

By K. V. Logan

When current flows through a zener diode in the forward direction it acts just like any other silicon diode

WE ARE ALL FAMILIAR WITH THE SIMPLE ZENER DIODE voltage stabilizing circuit which is shown in Fig. 1(a). The voltage across the zener diode is equal to its zener voltage, within tolerance, and the circuit provides voltage stabilization when the series resistor passes a current which is greater than that drawn by the circuit which the stabilized voltage supplies. The remaining current then flows through the zener diode.

What happens if, as in Fig. 1(b), we reverse the zener diode? We will now find that the current which flows through the zener diode is the forward current which flows through any conducting diode. The semiconductor material in a zener diode is silicon, and in Fig. 1(b) the diode acts just like any other silicon diode. The voltage dropped across it is then of the order of 0.6 volt.

TWO VOLTAGE LIMITS

Thus, a zener diode can limit voltage excursion in both directions. For one polarity the voltage is limited at the zener voltage of the diode, and for the other polarity it is limited at 0.6 volt. This fact can be of advantage if we want to clip an alternating voltage.

Fig. 2(a) shows an alternating voltage having a value of 20 volts peak. We apply this voltage via a series resistor to a 10 volt zener diode in Fig. 2(b). Fig. 2(c) shows, in solid line, the voltage which appears at the upper terminal of the zener diode with respect to the lower earth line. During positive half-cycles the device functions as a zener diode, and the half-cycles are clipped at 10 volts. On negative half-cycles the device

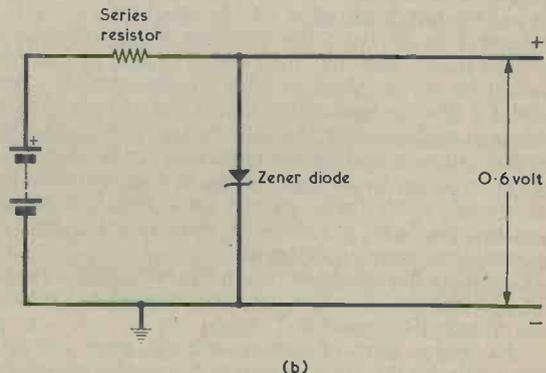
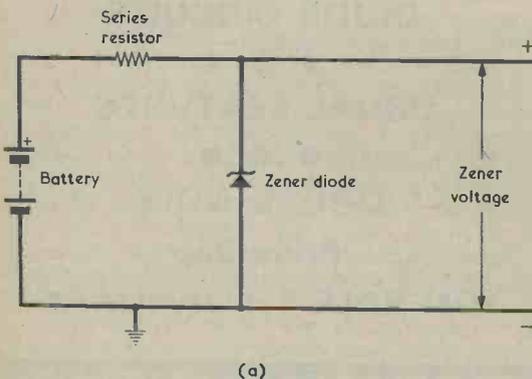


Fig. 1(a). A standard zener diode voltage stabilizing circuit
(b). In this circuit the zener diode is reversed, and it passes forward current

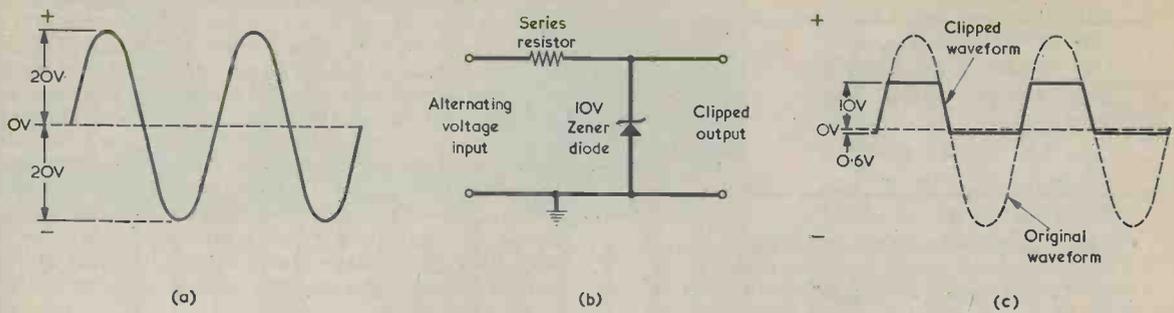


Fig. 2(a). A sine wave alternating voltage with an amplitude of 20 volts peak
 (b). Applying the alternating voltage to a 10 volt zener diode
 (c). The clipped waveform appearing at the upper terminal of the zener diode with respect to the earth line

functions as an ordinary silicon diode and it clips the half-cycles at 0.6 volt. In consequence, the diode has changed the original waveform to one having an amplitude of 10.6 volts peak-to-peak.

SPEECH CLIPPING

Speech clipping is often used in amateur transmitters to prevent over-modulation. A single zener diode can provide the clipping, but not in the circuit of Fig. 2(b) because the clipped waveform this gives is asymmetric and distortion would set in at the 0.6 volt clipping level. If, however, we feed the alternating voltage to the zener diode via a capacitor and take off an output via a second capacitor, as shown in Fig. 3(a), we would get symmetrical clipping at the output. Both capacitors need to have a low reactance at the frequency to be clipped. The first capacitor takes up a charge which allows successive half-cycles to be clipped at the same level along the half-cycle. These then appear, at the upper terminal of the diode and with respect to the earth line, in the form shown in Fig. 3(b). We now have

symmetrical clipping of the alternating voltage. However, the horizontal centre line of the clipped waveform (which represents its average voltage) is mid-way between the positive and negative clipping levels and is positive of earth potential. This is the same as having a symmetric alternating voltage plus a direct voltage, and we remove the direct voltage by means of the second capacitor. The output waveform is then that shown in Fig. 3(c).

The circuit of Fig. 3(a) can be used to clip the output of a communications receiver driving high resistance 2,000 Ω or 4,000 Ω headphones. The two capacitors may be 0.2 μ F for this application and the limiting resistor can be of the order of 1.2k Ω . A low zener voltage is preferable and a useful value would be 3.6 volts. The diode can be a 400mW component. The output from the receiver is then limited to a peak-to-peak level of 3.6 plus 0.6, or 4.2 volts. This could protect the receiver operator's ears from that nerve-shattering sound which is given when accidentally tuning through a powerful transmission with the volume turned too high.

Two zener diodes connected back to back as in Fig. 4

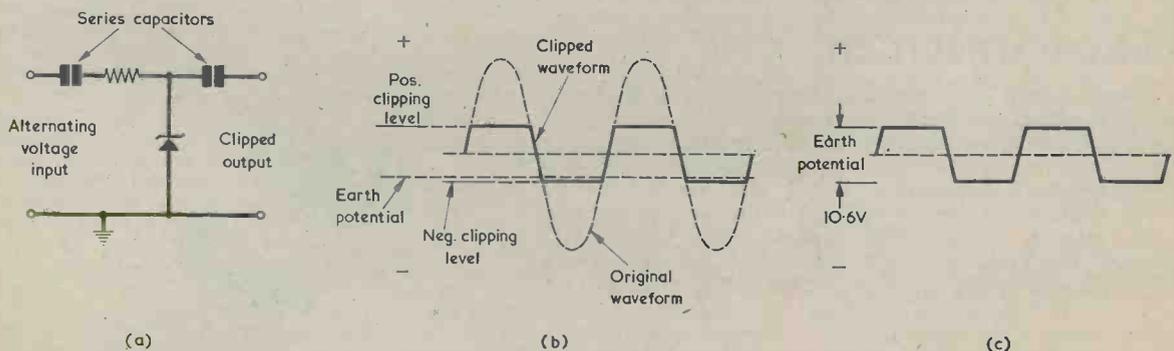


Fig. 3(a). Inserting capacitors in series with the input and output
 (b). The clipped waveform is now symmetric, but its average voltage is positive of the earth line
 (c). The second capacitor allows the average voltage of the waveform to become coincident with earth potential


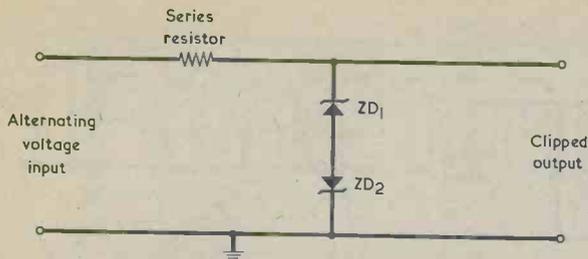


Fig. 4. Two zener diodes connected back to back provide symmetric limiting without the need for series capacitors, but limiting voltages cannot be made as low as with the single zener diode of Fig. 3(a).

give symmetrical clipping without the necessity for series capacitors, provided both diodes have the same zener voltage rating. When the upper input terminal in Fig. 4 is positive with respect to the earth line, ZD1 acts as a zener diode and ZD2 as an ordinary silicon diode. When the upper input terminal is negative, ZD1 acts as an ordinary diode and ZD2 as a zener diode. The peak level of the clipped signal is then the zener voltage of each diode plus 0.6 volt. This circuit does not offer clipping limit voltages that are as low as can be given by Fig. 3(a). With Fig. 4 the clipped peak-to-peak voltage (double the peak voltage with a symmetric waveform) is twice the zener voltage plus 1.2 volts, whereas in Fig. 3(a) the clipped peak-to-peak voltage is zener voltage plus 0.6 volt.

Trade News . . .

SEMI-CONDUCTOR CURVE TRACER

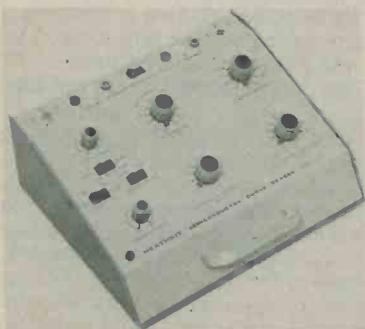

Anyone who works with solid-state circuits will appreciate the Heathkit IT-1121 Semi-Conductor Curve

Tracer. Just connect it to any oscilloscope with horizontal sensitivity of 0.5V/div. and vertical sensitivity of 1V/div. and get an accurate display of operating parameters for virtually any discrete semiconductor.

Connecting the IT-1121 to a scope is easy with the plug-in cables supplied. A calibration switch permits fast, accurate scope calibration. You can display fundamental parameters such as gain (beta), leakage, breakdown voltage, saturation, forward conduction voltage, output admittance, linearity, capacitance effects, temperature effects and others. The extensive manual included in each kit tells how to interpret each display, making the IT-1121 a valuable educational aid.

Kit K/IT-1121, £52.95. Assembled A/IT-1121, £127.45 (including 8% VAT and delivery within United Kingdom.) FREE catalogue available from: Heath (Gloucester) Ltd., Gloucester, GL2 6EE.

PRINTED CIRCUIT KIT

A printed circuit kit from Eagle International of Wembley, Middlesex contains all the items necessary to reproduce a printed circuit to exact individual requirements. Designated the PK3 it is supplied in a durable case complete with comprehensive instructions.

The contents of the kit include: polishing powder, etch resist, etching liquid, resist remover, flux, copper clad phenolic circuit boards, stencil knife, spatula and etching tray. Recommended retail price of the PK3 is £2.86 excluding VAT.



In your workshop



This month Smithy the Serviceman, aided as always by his able assistant Dick, is engulfed in the flood of repairs which never fails to appear just before Christmas. The pair are eventually left with a simple stereo record player, but this offers a few unexpected effects before it is finally repaired

IT WAS THE MORNING OF CHRISTMAS EVE.

As always occurred just before Christmas, the Workshop presented a scene of frenzied activity as Dick and Smithy wrestled with the recalcitrant radios, record players and TV receivers which had chosen this, of all times, to go on the blink.

Outside, the unheeding crowds scurried about their Yuletide business, engrossed with the last-minute preoccupations of purchasing presents for suddenly remembered aunts, of calculating oven times against turkey weights from at least three different formulae in three separate cookery books, of dreading the arrival of mothers-in-law, and of parcelling up toy drums as gifts for the children of hated enemies.

The Festive Season had also left its imprint inside the bustling Workshop, and this gave evidence of Dick's dedicated labours during the previous week. All the window panes bore little circles of cotton-wool in neat parallel rows, apparently representing an arrested instant during a precise, geometrically controlled snow-storm. Two gaily coloured paper chains stretched from corner to corner, crossing each other at the lamp in the centre, to the flex of which they had been securely fastened. Stuck incongruously to the wall above Smithy's bench was a huge plastic Santa Claus, and stuck to the wall above Dick's bench was an enormous and equally improbable rubber reindeer. Both of these, seemingly poised without support in mid-air, gave the impression that the slightest tremor would bring them tumbling to the floor. But Dick, who was no slouch when it came to adhesives, had taken the precaution of fixing the figures in place with liberal applications of Araldite. The rest of

the Araldite had come in useful too, and he had used it for sticking the mimic cotton-wool snow to the Workshop windows.

STEREO PLAYER

At the moment we join them, however, Dick and Smithy had no thoughts to spare concerning decorations or any other attribute of Christmas as they struggled with the sets they were servicing. Gradually the stock of receivers in the 'For Repair' rack diminished, whilst those which had been triumphantly carried over to the 'Repaired' rack increased in quantity. The morning passed on and, as Dick made his way yet again to the 'For Repair' rack, his first hurried impression was that there were still three units left on its shelves. The frown he had been exhibiting up to now suddenly changed to an expression of delighted surprise when he realised that the three units consisted of an inexpensive stereo record player and its two separate loudspeakers in their small cabinets.

"Hey, Smithy," he called out. "We're nearly at an end. I've just come to the last job!"

"Good show," grunted Smithy, from his bench. "I don't think I'll be long getting the TV I've got here finished, either."

Cheerfully, Dick carried the record player to his bench, after which he returned for the two speakers. He plugged these in at the rear of the record player unit then connected the latter to one of the row of mains sockets at the back of his bench. He switched on and listened expectantly. The record changer motor whirred just audibly into life but there was no evidence of any background noise or hum from the speakers. He selected a

record from a battered collection on the shelf above his bench and placed it on the changer. Unfastening the transit clip which held the pick-up in position on its rest, he then set the changer in operation. The record clattered down onto the turntable. The pick-up arm rose, moved to the edge of the record and then gently descended. There was a thin reedy sound from the stylus in the record groove, but no corresponding output from the two loudspeakers. Dick adjusted the volume, tone and balance controls, but the speakers maintained their silence.

Leaning over towards the back of the record player he rocked each speaker plug gently in its socket, and then experimentally moved the speaker wires near the points where they entered their plugs. All this was to no avail and, as he gave the speaker plugs a last visual appraisal, he was mildly surprised to note that a jack plug had been inserted into another socket mounted on the rear panel. The jack plug served no obvious purpose, and it had no lead connected to it. Dick scratched his head, then reached forward and pulled the plug out of the socket.

At once the two speakers came to life and they reproduced the sound from the record at good volume and with quite acceptable quality. With a satisfied expression, Dick turned the volume down.

"How about that, Smithy?" he called out exultantly. "I've cleared this last job without even having to get inside the cabinet!"

"Hang on a jiff," replied Smithy over his shoulder. "Let me just get the back on this set of mine, and then I'll come and join you."

Smithy put the last screw into the back of the television receiver on his bench and gave it a final check.

Satisfied with its performance he switched it off, walked over to his assistant's bench and flopped down on his assistant's stool.

"Phew," he said, pulling out a handkerchief and mopping his brow. "What a morning!"

"Well, it's nearly over now," stated Dick consolingly. "This record player I've got here is the last thing we've got to do before Christmas. So far as I can tell, I've already got it working."

"What was the snag?"

"When I turned it on," said Dick, "there was no sound from the speakers. Then I found this jack plug stuck, all by itself, into a socket at the back. As soon as I pulled it out the speakers came on and since then the record player's been going like a bomb."

JACK PLUG

Dick handed the Serviceman the offending jack plug. Smyth looked at it critically.

"There's something queer here," he remarked, raising his eyebrows. "The socket this plug was in would be meant to give a stereo output. But this isn't even a stereo jack plug. It's just an ordinary quarter inch jack plug giving two connections at its tip and its sleeve."

"Does that matter?"

"Well," replied Smyth. "It certainly introduces an element of mystery. The stereo type of jack plug has three connections: one for the right-hand channel and one for the left-hand channel." (Fig. 1.)

"What's the socket for, anyway? For an extra pair of speakers, or something?"

"It's for stereo headphones, you twit. You don't seem to realise it, but there's a very wide range of stereo headphones available these days."

"Is there? What sort of impedances do they have?"

"Most of them," replied Smyth, "have impedances in the 8 to 16 Ω range, but a few go up to 600 Ω or so. They're all hi-fi jobs and many of them use moving-coil assemblies to reproduce the sound."

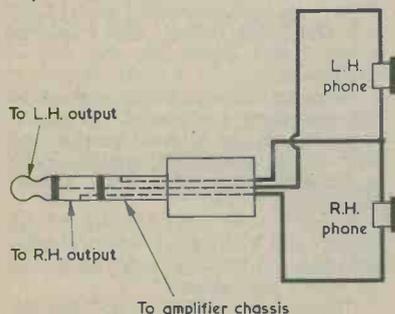


Fig. 1. Stereo headphones may be coupled to an amplifier by means of a 3-way jack plug. Typical connections are illustrated here

"Blimey," remarked Dick, impressed with this information. "I wonder what advantage there is in using hi-fi headphones? Why not just listen to the loudspeakers?"

"Apart from anything else," explained Smyth, "using stereo headphones means that you can listen to hi-fi without disturbing anyone else. Also, the phones help to keep out extraneous sounds."

Dick considered the situation.

"Stereo on headphones, eh?" he remarked eventually. "I suppose that if you turn your head to the right the whole orchestra moves round with you!"

"Let's not get involved in minor details," chuckled Smyth. "And let's concentrate on this record player instead. Now it's obvious that its jack socket is wired up so that the speakers are muted when a plug is inserted." (Fig. 2.)

"Fair enough," said Dick, "but why was the plug put there in the first place?"

Smyth frowned, then shrugged his shoulders.

"Goodness alone knows," he remarked helplessly. "Some customers do very strange things with their equipment, as you know. Perhaps somebody found the plug lying around and thought it belonged to the record player because it fitted the socket. Or it may have been a kid larking around. At any event, I don't think we'd better assume that we've made the record player completely serviceable just by pulling that plug out. There may have been another snag, and someone then put the plug in before the player was picked up for repair."

"Well, I hope that's not the case," remarked Dick. "I've had enough of fault finding for now. I want to get off on my Christmas holiday."

"So do I," confessed Smyth. "Anyway, we'll give this record player a quick check."

By now the record on the turntable had played to its end. Smyth set up the changer and started to play the record once more. Experimentally, he adjusted the record player controls.

"The volume control," he remarked, "is working okay. Ah yes, and so are the tone controls. And there doesn't seem to be any noticeable distortion on either channel. All that's left is the balance control."

Smyth adjusted the balance control over its range to find that, whatever its setting, the volume level on both channels remained entirely unaltered. He checked again. But it was quite evident that the control was having no effect whatsoever on the output levels of the two channels.

"There is a snag," he sighed. "Still, it should be a pretty easy one to clear up. Pop over to the filing cabinet, Dick, and get out the service manual for this record player. If it's going to be our last job before the Christmas holiday, we might as well tackle it in

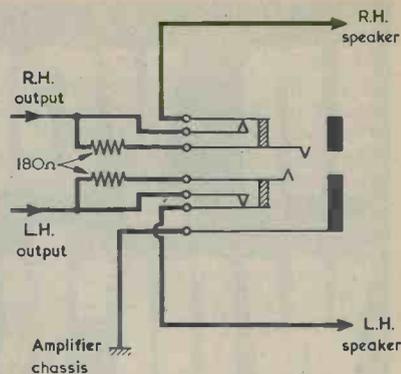


Fig. 2. A stereo headphone jack which automatically switches off the speakers when a jack plug is inserted. The outputs to the headphones are attenuated by series resistors, a representative value being shown

the correct routine manner."

Whilst Dick went in search of the manual, Smyth cycled the changer to its stop. After the pick-up arm had descended on its rest and the turntable had become disengaged he switched off the record player. He next slipped the transit clip over the pick-up arm, turned the player on to one side and started to remove the screws which held its cover underneath.

"This balance circuit looks dead simple," remarked Dick, returning with the service manual. "Here is it."

He placed the record player manual on the bench and pointed his finger at the circuitry around the balance control. (Fig. 3.)

Smyth glanced at the circuit briefly. "Yes," he agreed shortly, "it's the elementary arrangement you frequently get in these record players. All it consists of is a pot whose slider goes to chassis, and whose outside ends couple into the left and right channels after the pre-amplifier stages."

"You couldn't have anything much easier," remarked Dick, continuing on the theme. "When the slider of the pot goes downwards it causes less resistance to appear across the left-hand pre-amplifier output and more resistance to appear across the output of the right-hand pre-amplifier. The result is that the left-hand channel offers lower gain and the right-hand channel gives greater gain. And the reverse happens if the slider of the pot goes upwards."

"Exactly," confirmed Smyth, still busy with the screws securing the bottom cover. "And the end result is that you can set the balance control so that both channels give the same level of gain. Ideally, you should be able to set the balance control for equal sound from each speaker whilst playing a mono record."

RADIO & ELECTRONICS CONSTRUCTOR

**ANNUAL
SUBSCRIPTIONS
to this magazine
may be obtained
through your
newsagent
or direct from the
publishers
ONLY £3.30
per year, post free**

Please send remittance with name and address and commencing issue required to:

**DATA PUBLICATIONS LTD
57 Maids Vale London W9 1SN**

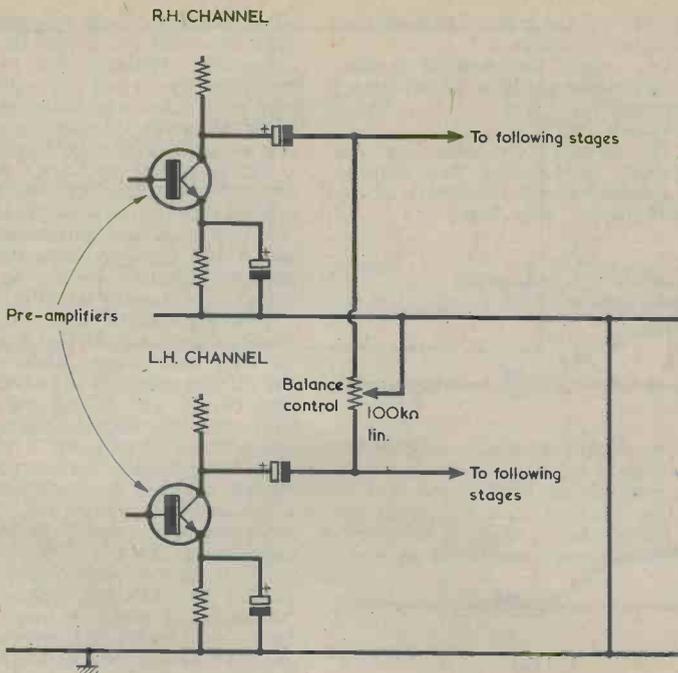


Fig. 3 A simple balance control network

"This particular balance circuit," commented Dick, frowning, "seems to be pretty fierce in operation. Why, you can adjust the pot for zero output on either channel. When the pot slider is at the bottom of its track the left-hand channel is killed completely. The same thing happens with the right-hand channel when the slider is at the top of its track."

"True," agreed Smithy, "the amount of control is very high. Some record players have equal value resistors in series with the balance control track ends so that the range of control is reduced. But others use a circuit of the type we have here. I suppose the idea is that a balance control of this nature satisfies the more compulsive type of knob twiddler. If he finds that one or other of the channels is completely silenced when the control is at the ends of the range, then he will be quite convinced that there must be a setting in the middle which gives correct balance." (Fig. 4).

OPEN-CIRCUIT

Smithy put down his screwdriver and removed the cover.

"Now what," he queried, "do you think will be the most likely cause of the snag we've got here?"

Dick thought for a moment.

"Since," he suggested, "the balance control has no effect on either channel, I would guess that the fault is common to both sides. Most probably there's an open-circuit between chassis and

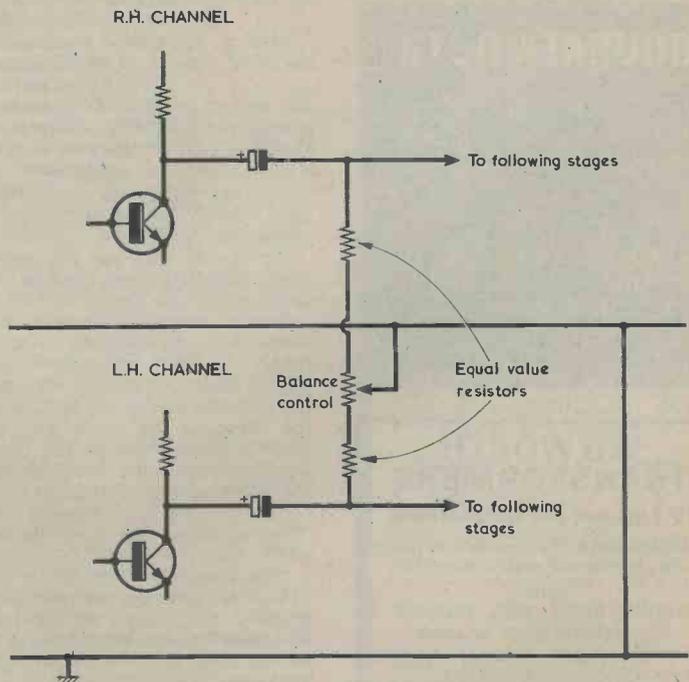


Fig. 4 In some stereo amplifiers the range of the balance control is reduced by inserting equal value resistors in series with the track ends

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English &
American radio and technical
books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP
Tel: 01-723 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS
LONDON, W.10
Tel: 01-969 3657

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.
70-72 Holdenhurst Road
Bournemouth
Telephone 25232

SURREY

WITWORTH TRANSFORMERS

TV Line out-put transformers
Manufacturers of the largest range in
the country. All makes supplied.

Modern
BAIRD, BUSH, GEC, PHILIPS
Replacement types ex-stock.
For "By-return" service, contact
London 01-948 3702

Tidman Mail Order Ltd., Dept. R.C.
236 Sandycroft Road,
Richmond, Surrey TW9 2EQ
Callers welcome.

the slider of the pot, or between the pot slider and its track."

"Very good," commended Smithy. "Let's next have a quick shufti inside. Oh dear!"

"What's up?"
"The chassis connection for the pot slider," said Smithy, "is to a solder tag eyeletted to the metalwork of the record player." (Fig. 5(a)).

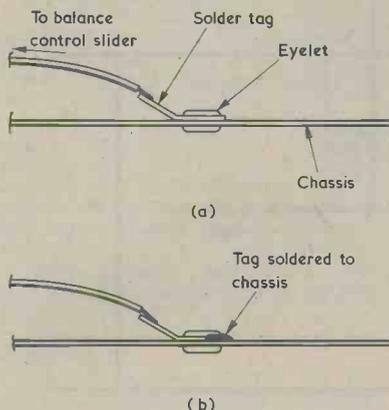


Fig. 5(a). The chassis connection for the balance control slider in the record player serviced by Smithy was made by way of a solder tag eyeletted to the chassis metalwork (b). To obviate the risk of a future intermittent connection, Smithy soldered the tag over to the chassis

"Is that bad?"

"It can be. Anyway I'll just check for continuity between chassis and the centre tag of the pot."

Smithy pulled Dick's testmeter towards him and set it to a low ohms range. He next connected one test clip to chassis at a point remote from the eyeletted solder tag and connected the other to the centre tag of the balance potentiometer. The testmeter needle was deflected only slightly from the left-hand end of its scale.

"Blow me," remarked Dick. "You've found the open-circuit first go!"

"Now watch."

Smithy picked up a screwdriver and prodded the chassis tag lightly with its blade. At once the testmeter needle moved over to the right, to indicate zero ohms.

"See what I mean?" went on Smithy. "That eyelet probably wasn't thumped down hard enough at the factory, with the result that the contact between the solder tag and the metal-

work had gone high resistance with time. Now that I've moved the tag the connection between the two will probably stay good for months or even years before it goes high resistance again. However, I'll make certain that this one doesn't go high resistance."

Smithy picked up Dick's soldering iron and a piece of solder, then applied them to the solder tag and the metalwork surface. After some moments the tag and metalwork were soldered together over most of the round section of the tag. (Fig. 5(b)).

The Serviceman next turned the record player over so that it stood on its base once more. After releasing the pick-up arm clip he switched it on and played the record once more. This time the balance control carried out its function correctly.

"Hooray," said Dick exuberantly, "that's the last job finished before Christmas."

He listened critically to the music from the speakers.

"That stereo player sounds jolly good," he remarked appreciatively. "I suppose it won't be long, though, before we'll be looking upon stereo as old hat and we'll be spending our time fixing up quadraphonic record players."

"It probably won't be long," agreed Smithy. "Four channel reproducing systems are a bit pricey at the time being but these are early days yet. Incidentally, it's possible to get a subjective 'all-round' sound effect with just the output of a stereo record player. Indeed, the scheme is used with some U.K. manufactured stereo amplifiers."

"Is it?" remarked Dick, surprised. "How does it work?"

"It works," replied Smithy, "by having two extra speakers which are positioned behind the listener. These are then fed with the channel difference signals at reduced level. Here's the idea."

Smithy scribbled out a circuit in the margin of the service manual (Fig. 6).

"What happens here," he went on, "is that the front right and front left speakers reproduce the right and left channels in normal manner. The two rear speakers are connected in series across the right and left outputs with a resistor between them to reduce their power level. When they're phased in the manner I've shown, the right-hand rear speaker reproduces an R-L signal and the left-hand rear speaker reproduces an L-R signal."

Dick looked at Smithy's circuit thoughtfully.

"Are those plus and minus signs alongside the speakers intended to indicate phase?"

"They are," confirmed Smithy. "They can, for instance, indicate the polarity across each speaker which is needed to make the cone move forwards, and this could be determined physically with the aid of a small dry battery applied to the speaker terminals."

RADIO & ELECTRONICS CONSTRUCTOR

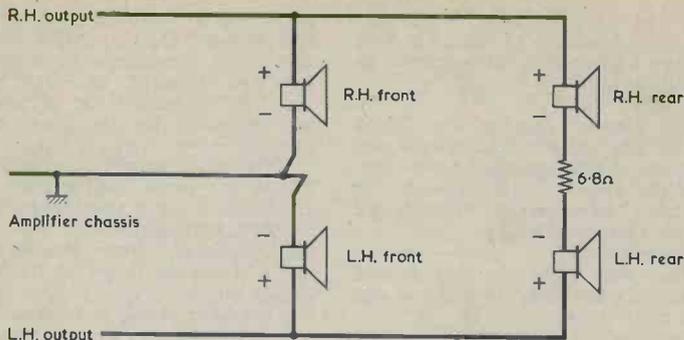


Fig. 6. A circuit which allows two loudspeakers behind the listener to reproduce the channel difference signals. The rear speakers should have the same impedance as the front speakers and the value shown for the resistor between them is representative. With high power amplifiers the resistor requires a rating of 3 watts. This circuit represents the '4D' mode of reproduction used in some Thorn stereo amplifiers

"How is it," asked Dick, "that the right-hand rear speaker reproduces an R-L signal whilst the left-hand rear speaker produces an L-R signal?"

"Simply because they're connected out of phase with each other," replied Smithy. "It's fairly obvious that the rear right-hand speaker is producing an R-L signal because the right-hand signal is applied to it in phase and the left-hand signal is applied to it out of phase. You can use the same sort of reasoning to see why the rear left-hand speaker produces an L-R signal. Don't forget that you indicate a reversal of phase by a minus sign. If you put R-L into brackets and put a minus sign in front, then the result when the brackets are removed is $-L+R$, or $L-R$!"

PILOT LAMP

"Well, that's a speaker system I didn't know about before," pronounced Dick. "Anyway, now that we have finished work let's start thinking about Christmassy things."

He leaned forward, opened a drawer in his bench and produced a small parcel wrapped in colourful paper. This sported a motif of robins and holly leaves intertwined against a background of snow.

"Here we are, Smithy," he announced, "here's my present for you."

"Ah, thank you, lad," intoned Smithy, taking the parcel from him. "Now let's see what we have here."

Carefully, the Serviceman removed the wrapping paper and placed it on one side. He looked doubtfully at Dick's present.

"Do you like it?" asked Dick eagerly.

"Why yes, of course," said Smithy uncertainly.

"I spent a lot of time choosing it."

"I'm certain you did."

"In fact it should just suit you."

"I have no doubt of it."

"The salesman said it was the most colourful tie he had in the shop."

"Oh, it's a tie," said Smithy. "Dear me, it's very wide, isn't it?"

"Not at all," responded Dick briskly. "Wide ties these days are all the rage, you know."

"I'm certain I'm most grateful," responded Smithy. "Now, let's see what I've got for you."

He walked over to his bench and returned with a package. Its wrapping paper had a pattern of robins and holly leaves intertwined against a snowy background.

"Why, that's a coincidence," remarked Dick. "Just the same paper that I used."

He removed the paper, then dubiously examined the contents of the package.

"Er - -," he remarked hesitantly, "they're very nice."

"I was sure you'd appreciate them," said Smithy cheerfully. "They should fit you just right."

"Fit me?" queried Dick suspiciously. "Whereabouts?"

"Why, on your shoes, you idiot. They're galoshes."

"Galoshes?"

"Galoshes," repeated Smithy. "You slip them over your shoes."

"Sounds kooky to me," remarked Dick disapprovingly. "Do people actually go around with things like these over their shoes?"

"Of course they do," returned Smithy irritably. "They're to keep out the rain and the snow."

"Oh, I see," said Dick, relieved. "Well, they should be jolly useful to me. Thanks very much, Smithy."

"I'm glad you like them," said

Your Local Supplier

SUSSEX

E. JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO.
MARCONI, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX


EIRE

PEATS for PARTS ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish
enthusiasts we supply
Radio & Electronics
Constructor
Data Books and
Panel Signs Transfers
Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

H.A.C. WORLD-WIDE RECEPTION

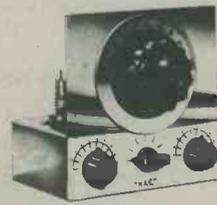

Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

SHORT WAVE KITS.

New 1975 range includes:

One valve models from £4.60.

Two valve battery operated portable

All-mains two valve receiver.

Transistor kits, short-wave and V.H.F.

Specialists in Short Wave components and accessories. Send stamped addressed envelope for free catalogue and test reports.

"H.A.C." SHORT-WAVE PRODUCTS
(Dept. RC.) P.O. Box 16
East Grinstead, Sussex RH19 3SN

AUDIO AMPLIFIERS



16 Transistor & Valve Designs for the Home Constructor

Amplifiers for Tuner Units, Record Players, Tape Recorders, Public Address, etc., etc.

Includes contributions by such well-known authors as

A. S. Carpenter, A. Kinloch, E. Govier, G. A. French, F. G. Rayer, P. F. Bretherick, K. Jones, D. Aldous, R. Murray-Shelley, C. Swires, G. A. Stevens and V. E. Holley.

Edited by J. R. Davies

124 pages

PRICE 53p

Postage 9p

To: DATA PUBLICATIONS Ltd.,
57 Maida Vale London W9

Please supply copy(ies)
of "Audio Amplifiers", Data
Book No. 18. I enclose cheque/
crossed postal order for.....

Name.....

Address.....

.....

.....

.....RC

BLOCK LETTERS PLEASE

Smithy in a mollified tone. "I must say it's very pleasant to have a nice mellow Christmassy atmosphere in the Workshop."

"Yes, isn't it?"
Dick glanced over at the record player. The record had finished and the pick-up had returned to its rest. Suddenly, Dick's eyes sharpened.

"Hello," he remarked, "There's still one little job outstanding."

"What's that?"
"The pilot light on that record player isn't working. Oh well, we can soon clear that!"

Impulsively, Dick turned the record player on its side and peered inside its cabinet. At once the pick-up arm left its rest and banged against the centre spindle of the changer.

"Trust you to knock things about," snorted Smithy irately. "Hadh't you better switch that player off before you start poking around inside?"

"There's no need," replied Dick airily, "it's only low voltage round the pilot lamp. Ah, here we are. The pilot lamp holder is one of those m.e.s. types that slide on and off. Wait a minute, it's a bit stiff."

Dick pulled at the refractory lamp holder. It suddenly came free, whereupon it shot out of Dick's grasp and, at the end of its two leads, rested on the case of one of the transistors on the printed circuit board. A frighteningly loud and raucous hum was reproduced by the left hand channel speaker, and Dick hastily flicked the bulb holder away from the transistor. The holder next came to rest on the chassis metalwork. The raucous hum from the loudspeaker ceased, to be succeeded by a quieter but far more unexpected and ominous hum emanating from the record player motor. After some moments there was a flash from one end of the circuit board and this last menacing hum stopped. Shaken, Dick switched off the record player.

"For the love of Pete," snarled Smithy furiously, "you'd wreck Fort Knox if they were dim enough to

leave you in there on your own for five minutes. Do you realise that you may have completely destroyed the left-hand channel of that record player? I wouldn't be surprised if you've burnt out the gram motor, too."

"The gram motor?" spluttered Dick. "How on earth can a pilot lamp circuit burn out a gram motor?"

"Just take a look at the power supply section," grated Smithy, pointing a trembling finger at the record player circuit. (Fig. 7). "For a start the amplifier supply is obtained from a low voltage overwind on the gram motor. The voltage from the overwind then goes into a silicon bridge rectifier. When that lamp holder was resting on the chassis, one or other of its tags, or its metal body, was creating a short which was causing the overwind to feed direct into a single silicon rectifier. With an overload like that, it was no wonder the gram motor started humming." (Figs 8(a) and (b)).

"What was the flash?"
"Hopefully," growled Smithy, "it was the fuse blowing."

"All right," continued Dick defensively. "Then why was there that loud hum from the speaker when the lamp holder was touching the transistor case?"

"Because," replied Smithy, "the transistor in question was a BC109 in the pre-amplifier stage. The BC109 is in a T0-18 metal can and, like many other T0-18 transistors, has its collector common with the can. You were injecting about 10 volts of raw a.c. into the output of the pre-amplifier stage."

"Stap me," said Dick contritely. "I hadn't realised it was possible for all these things to happen. Shall I put another pilot lamp in?"

"Blow the pilot lamp," said Smithy. "I'm more interested in seeing if the rest of the record player is still working. The safest thing you can do is get me a new fuse. The type I want is 800mA anti-surge."

Disconsolately, Dick walked over

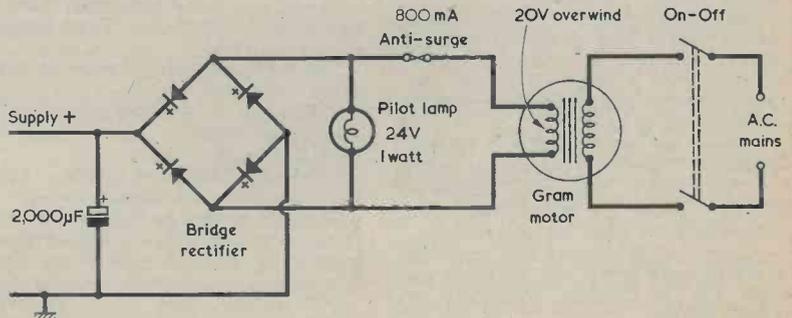


Fig. 7. Power supply circuit in which an overwind on the gram motor connects to a bridge rectifier

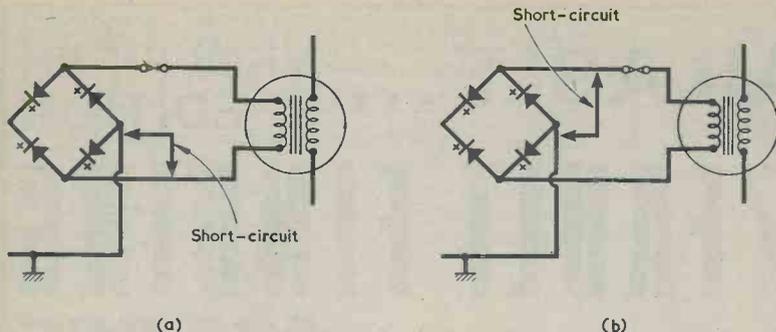


Fig. 8. If one of the terminals of the pilot lamp in Fig. 7 is short-circuited to chassis the resulting effect will be that shown in (a) or in (b). In either instance the gram motor overwind is effectively coupled to a single silicon rectifier

to the spares cupboard. Smythy temporarily wrapped a few turns of insulating tape round the lamp holder and its tags to ensure that it could not cause any more short-circuits. When Dick returned, Smythy quickly fitted the new fuse, set the record player upright and put the pick-up arm back on its rest. He switched on and started the changer cycle.

The pair listened with bated breath. The pick-up arm rose and descended on the revolving record. There was a slight hiss, and then the recording started. Dick and Smythy released their breath in a slow sigh of relief as the music was reproduced, just as before, from both channels.

CHRISTMAS SPIRIT

"Well, thank goodness for that," said Smythy with emphasis.

He went over to the spares cupboard, took out a spare pilot lamp and, after switching off the record player, fitted this to its holder. Steadfastly refusing all offers of help from his assistant he replaced the lamp holder in its correct place inside the record player, checked this out once more, then fitted the bottom cover.

"And that," he said with finality, "is that job done."

Dick handed him a record.

"Here," he said, "put this one on."

Carelessly, Smythy switched on the player again, put the record on the changer and set it in motion. Very soon, the Workshop was filled with the strains of "I'm Dreaming of a White Christmas" sung, as ever, by Bing Crosby.

"We couldn't," grinned Dick, his sturdy self-assurance once more returned, "let a Christmas go by without that record."

Now that the stresses of the day were over, Smythy allowed himself to gradually relax. With slowly increasing cheerfulness he gazed at the levitated Santa Claus above his bench and at the equally unsupported reindeer above Dick's. He glanced at the windows with their neat rows of pseudo-snow, giving the impression of an ordered cotton-wool-cushioned security at the heart of the maelstrom. He surrendered himself contentedly to a welcome period of tranquillity.

Dick coughed politely.

Smythy brought himself back to his surroundings. There was one more duty to be done.

Rising, he walked over to his bench, then returned accompanied by the pleasant clink of glass against bottle. Carefully, he charged Dick's glass, handed it to him, then filled his own.

"Well, Dick," he said, "a very Merry Christmas to you, lad."

"And," returned Dick warmly, "a very Merry Christmas and a Happy New Year to you, Smythy."

They rose, and held up their glasses. "Most important of all," stated Smythy, "let us next wish a Merry Christmas and a truly Happy New Year to all the readers who've put up with our antics over the last year."

They drank deeply.

"And," concluded Dick, "let us once more finish, as on so many previous Christmasses, by saying 'God bless us, every one!'"

NEW PRACTICAL PAPERBACKS FROM FOULSHAM-TAB

BASIC TV COURSE	£1.50
by George Kravitz	
NEW SKILL-BUILDING TRANSISTOR PROJECTS AND EXPERIMENTS	£1.45
by Louis E. Gardner Jr.	
RADIO CONTROL HANDBOOK	£1.90
by Howard G. McEntee	
TRANSISTORS: THEORY AND PRACTICE	£1.40
by Rufus P. Turner	
WORKING WITH SEMICONDUCTORS	£1.50
by Albert C. W. Saunders	
CASSETTE TAPE RECORDERS - HOW THEY WORK - CARE AND REPAIR	£1.60
by Walter Salm	
ELECTRONIC MEASUREMENTS SIMPLIFIED	£1.70
by Clayton Hallmark	
SOLID-STATE CIRCUITS GUIDEBOOK	£1.75
by Brice Ward	
10 MINUTE TEST TECHNIQUES FOR PC SERVICING	£1.60
by Art Magolis	
TV BENCH SERVICING TECHNIQUES	£1.65
by Art Margolis	
MINIATURE PROJECTS FOR ELECTRONIC HOBBYISTS	£1.45
by Ken W. Sessions Jr.	
FM STEREO/QUAD RECEIVER SERVICING MANUAL	£1.55
by Joseph J. Carr	
TROUBLESHOOTING SOLID-STATE WAVE GENERATING AND SHAPING CIRCUITS	£1.55
by Ben Gaddis	
THE 2-METRE FM REPEATER CIRCUITS HANDBOOK	£1.90
by Ken W. Sessions	
PINPOINT TRANSISTOR TROUBLES IN 12 MINUTES	£2.50
by Louis E. Gardner Jr.	




FOULSHAM-TAB LTD.
YEOVIL ROAD, SLOUGH, BUCKS.

NOW AVAILABLE... NEW FIFTH EDITION

TV FAULT FINDING

for 405/625 LINES

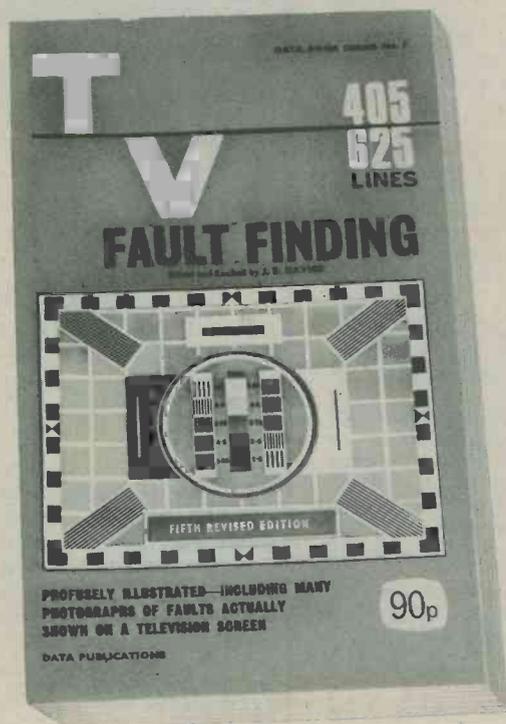

REVISED & ENLARGED

EDITED BY J. R. DAVIES

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

132 PAGES

90p
POSTAGE 9p

To Data Publications Ltd., 57 Maida Vale, London, W.9 1SN

Please supply the NEW EDITION OF "TV FAULT FINDING" DATA BOOK No. 5.....

I enclose cheque/crossed postal order for.....

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

SMALL ADVERTISEMENTS

Rate: 5p per word. Minimum charge 75p
Box No. 10p extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN

UNIQUE VHF KITS, 80 - 180 MHz, Receiver, tuner, converter. World wide sales. £4.50p. S.W. Kits also available. S.A.E. for literature. Johnsons (Radio C), Worcester, WR1 3QQ.

BATTERY ELIMINATOR KITS. Our well-known Mini Mains Pack Kits now complete with drilled insulated base 32 x 55mm. Fits into space of most large transistor batteries. Easy wiring instructions. Safe; silent mains transformer, silicon rects., smoothing capacitor, all top grade. For any ONE of these voltages (stage which): 3V, 300mA max.; 6V, 180mA; 9V, 120mA; 18V, 60mA. £1.50, VAT, INCLUDED. By mail only. U.K. post 5p. Amatronix Ltd., 396 Selsdon Road, South Croydon, Surrey, CR2 0DE.

FOR SALE: Polarised relays, suitable for RTTY terminal units. £1.00. Box No. G235.

BUILD THE MULLARD C.C. TV CAMERA. Complete kits now available from Crofton Electronics. Send large s.a.e. for details to:- 124 Colne Road, Twickenham, Middlesex, TW2 6QS. Telephone: 01-898-1569.

WANTED. Early radio books, prior to 1925. Box No. G236.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault Finding Guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex. Telephone Hastings 429066

ANTIQUÉ WIRELESS ENTHUSIASTS. For all your requirements in radio pre-1945 contact: Tudor Rees's Antique Wireless Service. Retail shop now open at 64 Broad Street, Staple Hill, Bristol. Telephone: 0272-565472.

SUPERB INSTRUMENT CASES by Bazelli. Manufactured from heavy duty P.V.C. faced steel. Hundreds of radio, electronic and hi-fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount. Prompt dispatch. Free literature: Bazelli, Dept. No. 26, St. Wilfrids, Foundry Lane, Halton, Lancaster, LA2 6LT.

CHROMASONIC ELECTRONICS. New list 10p. post free. Data Dept., 56 Fortis Green Road, London, N10 3HN.

FM RADIO Transmitter Modules complete with microphone and battery. Four simple connections only required. Return of post delivery. £4.50. E.E.S. Ltd., The Airport, Exeter, Devon.

HARDWARE SUPPLIES. Sheet aluminium, screws, nuts, washers, etc. Fascia panels in aluminium, individual requirements. Printed circuit boards, one-off or small runs, individual and for patterns published in this magazine. Send 10p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford-upon-Avon, Warwicks. CV37 9JP.

BENTLEY ACOUSTIC CORPORATION LTD.

All prices inclusive of V.A.T.

The Old Police Station, Gloucester Road, LITTLEHAMPTON Sussex. PHONE 6743

OB2	.40	9D7	.65	DY87	.65	EL32	.50	PCL82	.38	UL41	.75
2D21	.45	10F1	.75	DY802	.35	EL34	1.00	PCL83	.50	UL84	.42
3V4	.70	10F18	.55	EBCC	.75	EL41	1.00	PCL84	.45	UM80	.44
3R4GY	.80	10P13	.75	E180F	1.00	EL84	.31	PCL85	.55	UY41	.45
3U4G	.40	10P14	2.00	EA50	.27	EL91	.50	PCL86	.47	UY85	.35
5V4G	.50	12A6	.00	EABC80	.00	EL96	.50	PEN45	.80	X41	1.00
5Y3GT	.45	12AC6	.70	EA28	.38	EL90	.50	PE46	.50	X66	1.25
5Z4G	.45	12AD6	.65	EA472	.75	EM80	.45	PL36	.60	XC65	.28
6J30L2	.80	12AE6	.65	EA801	.75	EM81	.65	PL81	.30	AD140	.40
6AH6	.60	12AG6	.40	EBC21	.75	EM83	.55	PL82	.37	AD149	.55
6AQ5	.45	12AV6	.50	EBC41	.35	EM84	.40	PL83	.45	AD161	.50
6AT6	.45	12AV6	.50	EB81	.35	EM87	.70	PL84	.40	AD162	.50
6AU6	.30	12BA6	.45	EBF80	.39	EY1	.40	PL504	.75	AF114	.28
6AV6	.45	12BE6	.50	EBF83	.43	EY41	.55	PL508	.90	AF115	.17
6BA6	.28	12BH7	.50	EBF89	.32	EY87/6	.33	PL509	1.45	AF121	.33
6BE6	.35	12K5	1.00	EC92	.45	EY88	.40	PL802	.95	AF126	.20
6BH6	.60	14S7	.80	EC31	.50	EZ40	.50	PY33/2	.50	BC107	.14
6BK6	.55	19AQ5	.50	ECC35	.95	EZ41	.55	PY81	.35	BC108	.14
6BQ7A	.55	20P4	1.00	ECC40	1.00	EZ80	.28	PY82	.35	BC109	.14
6BR7	1.00	30C15	.80	ECC81	.34	EZ81	.29	PY83	.38	BC113	.28
6BR8	1.50	30C17	.80	ECC82	.33	EY01	.70	PY88	.40	BC118	.25
6BW6	.80	30F5	.80	ECC83	.33	EZ32	.50	PY90	.95	BC211	.42
6BW7	.70	30FL1	.67	ECC84	.35	GZ34	.60	PY800	.40	BF159	.28
6BZ6	.49	30FL2	.67	ECC85	.40	HVR2A	.00	PY801	.40	BF163	.22
6C4	.35	30T14	.78	ECC88	.44	QV03J	1.00	PY810	.40	BF180	.33
6C6	.40	30L15	.75	ECF80	.45	KTW61	1.0	RY10	.75	BY100	.20
6C9	1.00	30L17	.70	ECF82	.45	KTW62	1.50	R19	.60	BY126	.17
6CL4	.65	30P12	.80	ECF86	.75	KTW63	1.50	U25	.85	BY127	.20
6CU5	.75	30P19	.75	ECH31	.25	KTW63	1.00	U26	.66	OA91	.10
6E5	1.00	30PL1	.85	ECH42	.70	KTW63	1.00	U91	.75	OA95	.10
6F1	.75	30PL13	.95	ECH81	.33	KTW63	1.00	U801	.85	OC23	.42
6F6G	.50	30PL14	.85	ECH83	.44	KTW63	1.00	UABC80	.40	OC24	.42
6F18	.55	35L6GT	.75	ECH84	.44	PABC80	.38	UAF42	.60	OC44	.11
6F23	.80	35W4	.50	ECL82	.34	PC86	.60	UBC41	.60	OC45	.12
6F28	.67	35Z4GT	.70	ECL83	.70	PC88	.46	UBC81	.45	OC46	.17
6H6GT	.25	50B5	.85	ECL86	.40	PC97	.38	UBF80	.40	OC70	.14
6J5GT	.45	50C5	.60	EF22	1.50	PC90	.48	UBF89	.40	OC71	.12
6J6	.30	50C5	.60	EF40	.75	PC84	.40	UC92	.45	OC72	.12
6K7G	.30	DAF51	.38	EF41	.70	PC85	.44	UC84	.75	OC74	.25
6K8G	.45	85A2	.60	EF80	.26	PC88	.60	UC85	.45	OC75	.12
6L6GC	.58	ATP4	.50	EF83	1.00	PC89	.50	UCF80	.70	OC78	.17
6M7C	.50	AZ31	.60	EF85	.34	PC189	.57	UCB42	.75	OC78D	.17
6M7GT	.50	DAF91	.30	EF85	.34	PC86	.60	UF41	.70	OC82D	.12
6S67	.44	DAF96	.50	EF86	.45	PCF80	.40	UC81	.40	OC81D	.12
6S77	.55	DF91	.30	EF89	.27	PCF82	.40	UC82	.38	OC81D	.12
6V6GT	.17	DF96	.50	EF91	.37	PCF84	.59	UC83	.55	OC82	.12
6V6GT	.45	DK91	.45	EF92	.50	PCF86	.60	UF41	.70	OC82D	.12
6X4	.40	DK92	.70	EF98	.80	PCF80	.50	UF80	.35	OC83	.12
6X3GT	.45	DK96	.60	EF183	.30	PCF802	.50	UF85	.44	OC84	.26
7B6	.75	DL92	.40	EF184	.35	PCF805	.80	UF86	1.00	OC202	.47
7Y4	.75	DL96	.55	EH90	.35	PCF806	.50	UF89	.40	OC205	.47

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. Despatch charges:- Orders below £5, add 10p per order to cover up to three items, then each additional item 3p extra. Orders between £5 and £10 add 25p total. Orders over £10 post free. Same day despatch. Terms of business available on request. Any parcel insured against damage in transit for only 3p extra per parcel. Please enclose S.A.E. with any enquiries.

ENGINEERS

FREE

This 76 page
FREE book
shows how!

YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through our low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.

CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

Computer	<input type="checkbox"/>	Building	<input type="checkbox"/>	RADIO/TELECOMMS.	<input type="checkbox"/>	Garage Man.	<input type="checkbox"/>
Elec.	<input type="checkbox"/>	Civil Eng.	<input type="checkbox"/>	C & G	<input type="checkbox"/>	MAA/IMI Dip.	<input type="checkbox"/>
Electronic	<input type="checkbox"/>	Const. Eng.	<input type="checkbox"/>	Radio TV	<input type="checkbox"/>	GENERAL	<input type="checkbox"/>
Eng. Eng.	<input type="checkbox"/>	Heat & Vent.	<input type="checkbox"/>	C & G	<input type="checkbox"/>	Agric. Eng.	<input type="checkbox"/>
Install. & Wiring	<input type="checkbox"/>	Inst. of Builders	<input type="checkbox"/>	Prac. Radio & Elec.	<input type="checkbox"/>	Gen. Educ. Slide Rule	<input type="checkbox"/>
MANAGEMENT	<input type="checkbox"/>	Inst. Works and Highway	<input type="checkbox"/>	(with kit)	<input type="checkbox"/>	Refrigeratn.	<input type="checkbox"/>
Computer	<input type="checkbox"/>	Supers.	<input type="checkbox"/>	Radio	<input type="checkbox"/>	G.C.E.	<input type="checkbox"/>
Maintenance Eng.	<input type="checkbox"/>	Painting & Dec.	<input type="checkbox"/>	Amateurs Radio Serv.	<input type="checkbox"/>		
Mechanical Eng.	<input type="checkbox"/>	Surveying	<input type="checkbox"/>	TV Main & Serv.	<input type="checkbox"/>		
Welding	<input type="checkbox"/>	Storekeeping	<input type="checkbox"/>		<input type="checkbox"/>		
Work Study	<input type="checkbox"/>	DRAUGHTSMAN	<input type="checkbox"/>	AUTO & AERO	<input type="checkbox"/>		
ELECTRICAL & ELECTRONIC	<input type="checkbox"/>	Works Man.	<input type="checkbox"/>	Aero Eng.	<input type="checkbox"/>		
A.M.S.E. (Mech)	<input type="checkbox"/>	Prog.	<input type="checkbox"/>	A.M.I.M.	<input type="checkbox"/>		
Diag. Eng.	<input type="checkbox"/>	CONSTRUCTIONAL	<input type="checkbox"/>	A.E.C. Cert.	<input type="checkbox"/>		
Inst. Motor Ind.	<input type="checkbox"/>	A.M.S.E. (Civil)	<input type="checkbox"/>	Auto Eng. & G. Auto	<input type="checkbox"/>		
MANAGEMENT	<input type="checkbox"/>	Archit-cture	<input type="checkbox"/>	Eng.	<input type="checkbox"/>		
Computer	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Maintenance Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Mechanical Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Welding	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Work Study	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
ELECTRICAL & ELECTRONIC	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
A.M.S.E. (Mech)	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Diag. Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Inst. Motor Ind.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
MANAGEMENT	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Computer	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Maintenance Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Mechanical Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Welding	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Work Study	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
ELECTRICAL & ELECTRONIC	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
A.M.S.E. (Mech)	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Diag. Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Inst. Motor Ind.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
MANAGEMENT	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Computer	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Maintenance Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Mechanical Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Welding	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Work Study	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
ELECTRICAL & ELECTRONIC	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
A.M.S.E. (Mech)	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Diag. Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Inst. Motor Ind.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
MANAGEMENT	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Computer	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Maintenance Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Mechanical Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Welding	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Work Study	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
ELECTRICAL & ELECTRONIC	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
A.M.S.E. (Mech)	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Diag. Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Inst. Motor Ind.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
MANAGEMENT	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Computer	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Maintenance Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Mechanical Eng.	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Welding	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
Work Study	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		
ELECTRICAL & ELECTRONIC	<input type="checkbox"/>		<input type="checkbox"/>		<input type="checkbox"/>		

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in theissue of RADIO & ELECTRONICS CONSTRUCTOR

→			

15 words at 5p
= 75p.

ALL WORDING
IN
BLOCK LETTERS
PLEASE

I enclose remittance ofbeing payment at 5p a word. MINIMUM 75p.
Box Number, if required, 10p extra.

NAME

ADDRESS

Copy to be received four weeks prior to publication. Published on the 1st of every month.

PRECISION

POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

440V AC (+-10%)	63V Range	+1%	+2%	+5%
0.1µF (1 1/8" x 1/8") 50p	0.47µF	56p	46p	36p
0.22µF (1 1/8" x 8") 59p	1.0µF	66p	56p	46p
0.25µF (1 1/8" x 8") 62p	2.2µF	80p	65p	55p
0.47µF (1 1/8" x 1") 71p	4.7µF	£1.30	£1.05	85p
0.5µF (1 1/8" x 1") 75p	6.8µF	£1.64	£1.29	£1.09
0.68µF (2" x 1/2") 80p	10.0µF	£2.00	£1.60	£1.40
1.0µF (2" x 1/2") 91p	15.0µF	£2.75	£2.15	£1.90
2.0µF (2" x 1") £1.22	22.0µF	£3.50	£2.70	£2.55

TANTALUM BEAD CAPACITORS - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL AT 10p EACH; 10 for 95p; 50 for £4.00.

TRANSISTORS:

BC107/8/9 9p	BC183/183L 11p	BF194 12p	BFY51 20p
BC114 12p	BC184/184L 12p	BF196 13p	BFY52 20p
BC147/8/9 10p	BC212/212L 14p	BF197 13p	OC71 12p
BC153/7/8 12p	BC547 12p	AF178 30p	2N3055 50p
BC182/182L 11p	BC558A 12p	BFY50 20p	2N3702/4 11p

1N914 6p; 8 for 45p; 18 for 90p. 1N916 8p; 6 for 45p; 14 for 90p. IS44 5p; 11 for 59p; 24 for £1.00. IN4148 5p; 6 for 27p; 12 for 48p.

LOW PRICE ZENER DIODES: 400mW; Tol. +-5% at 5mA. Values available: 3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.5V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each; 6 for 39p; 14 for 84p. SPECIAL: 100 Zeners for £5.50.

RESISTORS: High stability low noise carbon film 5%, 1/4 W at 40°C; 1/4 W at 70°C. E12 series only - from 2.2Ω to 2.2MΩ ALL AT 1p EACH; 8p for 10 of any one value; 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

SILICON PLASTIC RECTIFIERS - 1.5 Amp - Brand new wire ended D027: 100 P.I.V. - 7p (4/26p); 400 P.I.V. - 8p (4/30p); 800 P.I.V. - 11p (4/42p). **BRIDGE RECTIFIERS:** 2 1/2 Amp. 200V - 40p; 350V - 45p; 600V - 55p.

SUBMINIATURE VERTICAL PRESETS - 0.1W only: ALL AT 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1K, 2.2K, 4.7K, 6.8K, 10K, 15K, 22K, 47K, 100K, 250K, 680K, 1M, 2.5M, & 5M.

TRANSFORMERS: Primary 220-240V, 12V @ 2A & 24V @ 1A. £2.00 plus 22p post.

PLEASE ADD 8% V.A.T. TO ORDERS. PLEASE ADD 10p POST AND PACKING ON ALL ORDERS BELOW £5.00. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona-fide companies. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

MARCO TRADING

Dept. C9, The Old School, Edstaston, NR. WEM, Salop.
Tel: WHIXALL (Salop) 464 (STD 094872) (Props: Minicost Trading Ltd.)

CJL PRICES INCLUDE P&P AND V.A.T.

- AERIAL**, telescopic, 15-120cm. £1.20
- AERIAL**, telescopic, h and v swivel, 15-80cm. £1.78
- EARPHONE**, stethoscope style, 8 ohm dynamic. £1.00
- HAND DRILL**, (Laytool), Compact precision drill .5/16" chuck. Gears totally enclosed. S/L bearings. £2.90
- INTEGRATED CIRCUITS**
- AUDIO POWER AMPLIFIER** (National) LM380 £1.00
- A.M. RADIO RECEIVER** (RCA) CA3123E £1.40
- F.M. STEREO DECODER** (Motorola) MC1310P £2.80
- I/C TIMER** (Signetics) NE555V £0.78
- D.I.L. SOCKETS** (pk of 3) 8 pin £0.50 14 pin £0.55
- KEYNECTOR**, rapid connect-single/multiple leads to mains. Built-in plano switches, neon & 13A fuse. £3.20
- MICROPHONE**, lightweight dynamic, remote start/stop 200 ohms, 100-10,000Hz, 6mV average output. £1.80
- MULTIMETER**, small and attractive, Vdc-10.50, 250, 1,000. Vac-10.50, 250, 1,000. Idc-100mA. R-150k. £4.95
- POWER SUPPLY COMPONENTS**
- SILICON BRIDGE RECTIFIER**, 100 P.I.V./2A £0.40
- ELECTROLYTIC CAPACITOR**, 2,200µF/50V £0.57
- ELECTROLYTIC CAPACITOR**, 5,000µF/25V £0.63
- SILICON POWER TRANSISTOR**, 2N3055 £0.60
- VOLTAGE REGULATOR** (Fairchild) uA7805 £1.70
- VOLTAGE REGULATOR** (Signetics) NE550A £0.80
- SIGNAL INJECTOR** produces audio through video signals, excellent-servicing amplifiers, radios, televisions, etc. £3.92
- SOLDERING IRON**, 25 WATT, (Antex), X25, 240V, Very low leakage, 1/8" long life bit (interchangeable). £1.85
- 3/32" bit £0.45 3/16" bit £0.45 Element £0.95
- STAND**, (Antex), ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits. £0.95
- SPEAKER**, miniature, 8 ohms, 70mm dia. £0.80

CJL

CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT

SMALL ADVERTISEMENTS

(Continued from page 315)

FOR SALE: Puffs and cans galore. Mica, ceramic, 2p each. Smoothing blocks 60p each. Quantity discount. Send 10p for list. Post and packing free on orders over £1.50. Quartic Electronics, 6 Stancliffe Avenue, Bulwell, Nottingham, NG6 9HP.

RADIO, TV AND OTHER VALVES. Large stocks 1930-1974. S.A.E. for quotations. Price list 15p. Also available transistors and stylii. Cox Radio, 19 The Parade, East Wittering, Sussex. Telephone: West Wittering 2023.

MAGNIFIERS, ideal for wiring printed circuit boards, etc. 4" dia. lens on flexible arm and heavy base £6.00, also Binomag headband magnifier — £5.70. Available by post from Revor Optical & Technical, 36 Baker Street, London W.1. Telephone: 01-836 4536.

EXPERIMENTERS! Hundreds of unusual items cheap. List No. 9, 6p. Grimsby Electronics, Lambert Road, Grimsby, Lincs. (Callers Saturdays only).

WORLD DX CLUB covers all aspects of SWling on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.60 a year. Enquiries to John Rush, 12 Northfield Road, Thatcham, Berks.

WANTED: Service manual for Hallicrafter's Skyrider communications receiver. Box No. G248.

PRINTED CIRCUIT BOARDS. PCB from your pattern £1 plus 5p per square inch. From published patterns in this magazine 50p per board. Add v.a.t. 5p P. & P. per pcb. Mail Order only. TEC, 241 Burnt-Oak Broadway, Burnt Oak, Middlesex.

QUARTZ CRYSTALS. 5675 kc/s to 8650kc/s in steps of 25kc/s. 1/2" pin spacing. £2 for 20 our selection. 7000 to 7175 £1.00 each. E.E.S. Ltd., The Airport, Exeter, Devon. Telephone 66523.

FOR SALE: Codar multiband G receiver in excellent condition. Price: £9.50. Telephone: 061-485 8301 evenings.


JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £2.00 per annum. (U.K. and British Commonwealth), overseas 6 Dollars or £2.50. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

RADIO & ELECTRONICS CONSTRUCTOR. Issues from August 1963 to July 1974, mint condition, best offer. Rylance, 46 Cedar Drive, Hatch End, Pinner, Middlesex.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.

(Continued on page 318)

BI-PRE-PAK Audio Bargains

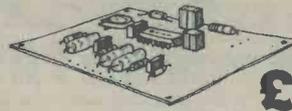

**STEREO
DECODER**

£4.50

incl. P. & P.

Ready-built unit, ready for connection to the IF stages of existing FM Radio or Tuner. The very latest 2nd Generation coil-less integrated circuit design, operating on this phase locked loop system, offering even better stereo separation. Only owing to our bulk buying capacity are we able to offer this at the old price.


LED stereo indicator lights available

Red at 25p Green at 40p


3 W_{R.M.S.} I.C. AMP

only **£1.50** incl. P. & P.
Order Code I.C.A. 1

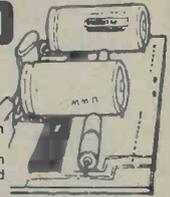On P.C. Board with all components or 2 on one board for £2.60. Order Code I.C.A. 1/S. These amps are supplied with a free booklet on connecting up, specifications and easy to build projects using the I.C.A. 1.



5W & 10W AMPS

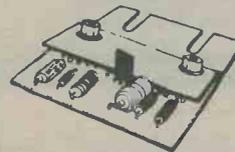

5W ONLY £1.80
10W ONLY £2.26

incl. P. & P.

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 1/4" x 1 1/2". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the U.K. Built and tested.

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit .15 edge connector.

Stereo Pre-Amp 1 (Pre 1) This unit is for use with low gain crystal or ceramic pick up cartridges. **£1.10**

Stereo Pre-Amp 2 (Pre 2) This unit is for use with magnetic pick-up cartridges. **£1.55**

Stereo Tone Control (STC) This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.10**

Instruction leaflet supplied with all units. Post and Packing included in prices.

PLEASE ADD VAT AT CURRENT RATE

I enclose £..... for..... 8 Tracks/..... 3W

Amps/..... 5W Amps/..... 10W Amps/.....

Stereo Pre-Amps 1..... Stereo Pre-Amps 2.....

Stereo Tone Controls (Please insert quantities and delete those not applicable).

Name.....

Address.....

BI-PRE-PAK
Co. Regn. No. 820919

Dept. C, 222/224, West Road,
Westcliff-on-Sea, Essex SS0 9DF
Tel: Southend (0702) 46344

ENGINEERS

FREE

YOURSELF FOR A

BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through our low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer.

Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

POST NOW

- | | | | | | |
|--|--------------------------|--|--------------------------|--|--------------------------|
| Build-As-You-Learn | <input type="checkbox"/> | Electronic Engineering | <input type="checkbox"/> | CITY & GUILDS Installations and Wiring | <input type="checkbox"/> |
| PRACTICAL RADIO AND ELECTRONICS (with kit) | <input type="checkbox"/> | Computer Electronics | <input type="checkbox"/> | CITY & GUILDS Electrical Technicians | <input type="checkbox"/> |
| Electrical Engineering | <input type="checkbox"/> | Computer Programming | <input type="checkbox"/> | CITY & GUILDS Telecommunications | <input type="checkbox"/> |
| Electrical Installations and Wiring | <input type="checkbox"/> | General Radio and TV Engineering | <input type="checkbox"/> | Radio Amateurs' Exam etc. etc. | <input type="checkbox"/> |
| Electrical Draughtsmanship | <input type="checkbox"/> | Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> | G.C.E. '58 'O' & 'A' LEVELS | <input type="checkbox"/> |
| Electrical Mathematics | <input type="checkbox"/> | Transistor Technology | <input type="checkbox"/> | Coaching for many major examinations | <input type="checkbox"/> |

To ALDERMASTON COLLEGE, Dept BRE 95, READING RG7 4PF BRE 95

NAME (Block Capitals Please)

ADDRESS

Other subjects

Accredited by C.A.C.C.

Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

RADIO MODELLER

ELECTRONIC BOOKS

MODEL RADIO CONTROL


Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.
134 pages.

Price £2.25

U.K. Packing & Postage 32p

ON SALE NOW
at all leading shops
or direct from:-

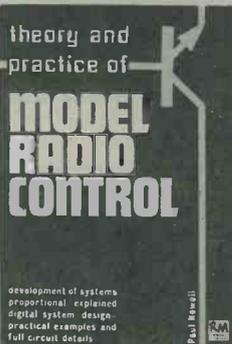RADIO MODELLER
BOOKS DIVISION,
64 Wellington Road,
Hampton Hill, Middx.



SMALL ADVERTISEMENTS

(Continued from page 317)

FOR SALE: Handbook of satellites and space vehicles £7.00. Self-sealing plastic bags 2 1/4" x 2 1/4", 100-30p, s.a.e. for sample. 5lbs mixed components £2.50. Avo 8 £20.00. Battery operated door chimes (need repair) 75p. Servisol switch cleaner 70p, 2 tins £1.00. 10 mixed LED'S £1.50. Valve tester £20.00. 2-speed drill with 'hammer' action, 3/8" chuck, £12.50. 75 yds x 2" Sellotape roll £1.00. Freezing spray aerosol £1.30. Bush CTU25 colour TV, serviced with new tuners, £125.00. 10" 8Ω speaker £2.75. 100mW walkie-talkies £27.00. 147kHz-220MHz signal generator £38.00. Reconditioned adjustable arm bench lamp £5.00. 24V input 500W 240V inverter £30.00. 50W hi-fi amplifier kit £12.50. Manufacturer's reject (repairable) walkie-talkies (retail £59.95) £30.00. Minifon pocket wire recorder, new condition, £8.00. S.A.E. for lists. Box No. G249.

BOUND VOLUMES of *Radio Constructor* for sale: Nos. 17-23 inclusive 1963 to 1970 (last three unbound). Best offer secures. Telephone: 01-722 7040.

FOR SALE: 5 new Pop-8-track cartridges £6.00. 50 ex-juke box records £3.50. Cassettes C60 40p, C90 50p, C120 60p. Cassette cube case MOCD36 £4.50. Head cleaners cassette 50p, 8-track 75p. Adaptor to play cassettes through car radio £12.00. Miniature radio, rechargeable batteries and recharger, £4.50. Box No. G250.

SUPER CONSTRUCTORS PACK containing 50 assorted spacers 4 and 6BA clearance and threaded types. Two 6" extension shafts, Two couplers, Two 2" extension shafts with couplers attached, 1 foot each of 2-4 and 6BA brass studding (3ft.), 20 tag strips, 2 trimmer converters, 100 mixed self-tapping screws, plus free gift. Bargain at £1.65p inclusive of postage. Electro-Mech Products, 7 Chantry Avenue, Bideford, Devon. Telephone: 6820.

FOR SALE: Electronic circuits manual £4.50. Also back numbers of *Radio Constructor* and *Wireless World*. Send for list. Box No. G251.

RADIO & TELEVISION AERIAL BOOSTERS. Improve weak reception. £3.10. 5 television valves, 45p. S.A.E. leaflets. Lancashire Mail Order (R), 6 William Street, Stubbins, Ramsbottom, Bury, Lancs.

MULLARD 10W RMS AMPLIFIER MODULES. Brand new for 24 volt 4 ohm operation. Tremendous offer, absolutely no extra components or hardware required. Supplied with circuit and full data for simple operation. £2.65 inclusive. LTE, 46 Minehead Road, South Harrow, Middlesex. Mail order only please.

RECITALS OF RECORDED MUSIC. The second Saturday evening of each winter month. Next recital: December 14th, 1974, 8 p.m. at Woodford Green United Free Church Woodford Green, Essex. Bus routes 20, 20A, 179 and 275 - alight at "The Castle" stop. Programme includes works by Bach, Handel and Ravel.

FOR SALE: Enamelled copper wire 2 1/2 oz. reels 30 s.w.g. only, 30p each. 250MΩ 1 in. pots, 5p each. Post and packing 10p. Daniel Collier, Sturtsbury Farm, Bumbles Green, Nazeing, Essex.

FOR SALE: Germanium point contact diodes, equivalent OA91. Branded. 5 for 25p inclusive. T.A.C., 59 Luckwell Road, Bristol, BS3 3ES.

(Continued on page 319)

RADIO & ELECTRONICS CONSTRUCTOR

SMALL ADVERTISEMENTS

(Continued from page 318)

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p. five sheets for 10p. postage 3p. Data Publications Ltd., 57 Maida Vale, London W9 1SN.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

MAKE NEW FRIENDS! The exciting reliable way. All areas, all ages. Write: S.I.M. Computer Dating (REC), 109 Queens Road, Reading, Berks.

ELECTRONICS MEN. You are, worth more than a measly £40 or £50 a week. Much more. And you do not need to be highly qualified. Last year I earned £3,600 for six months work. The other six months I had off. My booklet will tell you how I started and how you too could do similar if not better. No selling and no capital outlay except the price of the booklet. It's 65p from Alben, Site 3, Church Street, Diss, IP22 3DD.

ESSEX GARDENERS. Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

YOUNG MAN DISABLED needs work at home. Electronic/wire assembly. Would collect and deliver. Mr. B. Grimes, Llainwen, Glanrhyd, Cardigan, Wales, SA43 3PE.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

SITUATION VACANT

ENGINEER with sound electronics knowledge and experience required for our Wembley service dept. Good pay and prospects for suitable applicant aged 16 to 20. Close to trains, buses. Free lunches. Apply: Box No. G252.

C AND G EXAM

Make sure you succeed with an ICS home study course for C and E Electrical Installation Work & Technicians Radio/TV/ Electronics Technicians. Telecommus Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits.

Get the qualifications you need to succeed. Free details from:

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 233B Intertext House, London SW8 4UJ.
Or phone 01-622 9911

ESSENTIAL BOOKS!

HOW TO MAKE 2M & 4M CONVERTORS FOR AMATEUR USE. Available at last after many delays. Fully comprehensive. Contains circuits, lay-outs, component lists, diagrams and full instructional notes. Price 60p, p.p. 15p.

HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION. 40p, p.p. 15p.

THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Gives circuits, data and illustrations plus valuable information for British/USA receivers, transmitters, trans/receivers. Available later October. £4 including postage.

DIRECTORY OF GOVERNMENT SURPLUS WIRELESS EQUIPMENT DEALERS. Gives details of surplus wireless equipment stores and dealers including addresses plus equipment and spares that they are likely to have available. A valuable book only 50p, p.p. 10p.

GETTING THE BEST FROM YOUR COLOUR TV R. Maude. Essential advice for colour TV engineers and owners. Could save you pounds. 50p, p.p. 15p.

THE THEORY OF GUIDED ELECTROMAGNETIC WAVES. The most comprehensive book yet written about waveguides, transmission lines, cavity resonators. Over 500 pages. Ideal for anyone interested in Radar and UHF. Published at £11.50. Special offer £4.50, p.p. 50p.

MOBILE RADIOTELEPHONE EQUIPMENT HANDBOOK. Gives circuits, data and illustrations plus some valuable modifications for amateur use for commercial radiotelephone equipment including PVE and other popular makes. Available early November. £4.75, p.p. 35p.

HANDBOOK OF FIXINGS & FASTENINGS. B. Launchbury. Covers all aspects of fixings & fastenings. Includes characteristics and range of sizes, types and applications of nails, wood screws, light plugs, heavy masonry fixings, rivets, screws, washers, bolts etc. Essential for the do-it-yourself enthusiasts. Profusely illustrated. Published at £1. Special offer 50p per copy, p.p. 25p.



Send for this fully comprehensive catalogue of radio books. Free.

THE BARGAIN BOOK GAZETTE. Contains thousands of interesting new and out of print books at bargain prices. Subjects include all types of hobbies, collecting, 1001 interests. Published regularly and sent free on request.

Dept. R. C. GERALD MYERS (Publisher & Bookseller),
138 Cardigan Rd., Headingley, Leeds 6, Yorks. (Callers Welcome).

MASSIVE CLEARANCE BARGAINS

Bargain component parcels contain Resistors, Capacitors, Potentiometers, Knobs, Rotary, Slide, Switches, IF's, Tag Strips, Drive Drums, Springs, Coil Formers, Wire, Grommets, Relays, Pulley Wheels, Magnets, Transistor Panels etc., etc. Save yourself £s on these well selected parcels 6lbs net weight £1.00, p. p. 50p.

Brand new Wire-wound Resistors. 1-7 Watts. Good Selection. 100 for £1 p. p. 20p.

Mullard Ferrite Cores LA3 100 to 500KHz, 50p. LA4 10 to 30KHz. 75p. LA2100 3 to 200 KHz. 50p.

P.V.C. Flexible Connecting Wire Assorted Colours 100 yards for £1.00 p.p. 20p.

Assorted Capacitors, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection. 300 for £1. p. p. 20p.

Special Offer Electrolytic Capacitors Reversible 3600µF 70 volts H.D. Terminals 60p, p.p. 20p.

Please include 8% V.A.T. to total cost of goods.

MAIL ORDER ONLY XEROZA RADIO

1, EAST STREET,
BISHOPS TAWTON,
DEVON

MORSE MADE EASY!!!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.) Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. IN 4 WEEKS GUARANTEED. Complete course, 3 Records and Books, £4.95 incl. P.P.I. etc. (Overseas £1 extra). Or details only, 4p stamp. Or phone S. Bennett, G3HSC, 01-660 2896.

Box 38, 45 GREEN LANE, PURLEY, SURREY.

PLAIN-BACKED NEW STYLE SELF-BINDERS

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

for your other magazines

(max. format 7½" x 9½")



PRICE 85p P. & P. 18p

including V.A.T.

Available only from:—

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

Data Publications Ltd. 57 Maida Vale London W9 1SN

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
132 pages. Price 90p, postage 9p.
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**
88 pages. Price 70p, postage 7p.
- DB16 RADIO CONTROL FOR MODELS**
192 pages. Price 75p, postage 13p.
- DB17 UNDERSTANDING TELEVISION**
512 pages. Price £2.10, postage 25p.
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 53p, postage 9p.
- DB19 SIMPLE SHORT WAVE RECEIVERS**
140 pages. Price 80p, postage 9p.

I enclose Postal Order/Cheque for..... in payment for.....

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable from your local bookseller.

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

S.S.C. WIRE COIL LENGTHS

The Table lists lengths, in inches, of close-wound coils using s.s.c. (single silk covered) enamelled copper wire. Thus, a 50 turn coil of 24 s.w.g. wire has a length of 1.3in. Similar coil lengths will be given with s.r.c. (single rayon covered) enamelled wire.

Wire Gauge (s.w.g.)	10 Turns	20 Turns	30 Turns	40 Turns	50 Turns	60 Turns	70 Turns	80 Turns	90 Turns	100 Turns
16	0.70	1.4	2.1	2.8	3.5	4.2	4.9	5.6	6.3	7.0
18	0.52	1.0	1.6	2.1	2.6	3.1	3.7	4.2	4.7	5.2
20	0.40	0.80	1.2	1.6	2.0	2.4	2.8	3.2	3.6	4.0
22	0.32	0.64	0.96	1.3	1.6	1.9	2.2	2.6	2.9	3.2
24	0.25	0.51	0.76	1.0	1.3	1.5	1.8	2.0	2.3	2.5
26	0.21	0.41	0.63	0.84	1.0	1.3	1.5	1.7	1.9	2.1
28	0.17	0.34	0.52	0.70	0.87	1.0	1.2	1.4	1.6	1.7
30	0.15	0.29	0.44	0.59	0.73	0.88	1.0	1.2	1.3	1.5
32	0.13	0.26	0.39	0.52	0.65	0.78	0.91	1.0	1.2	1.3
34	0.11	0.22	0.33	0.45	0.56	0.67	0.78	0.89	1.0	1.1
36		0.19	0.29	0.39	0.48	0.58	0.68	0.77	0.87	0.96
38		0.15	0.23	0.31	0.39	0.46	0.54	0.62	0.70	0.77
40		0.13	0.20	0.27	0.33	0.40	0.47	0.53	0.60	0.67

Henry's

UK'S LARGEST STOCKIST OF ELECTRONIC COMPONENTS & EQUIPMENT
ALSO HI-FI · TV · TAPE RECORDER

ELECTRONIC COMPONENTS AND EQUIPMENT
More selection - Bigger Stocks for every purpose. Let us quote for your requirements. (Please enclose SAE with all enquiries).

You can build the Texan and Stereo FM Tuner TEXAN 20 + 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC-board, Gardners low field transformer, 6-IC's, 10-transistors plus diodes etc. Designed by Texas Instruments engineers for Henry's and. P.V.V. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input & control facilities. Stabilised supply. Overall size 15 1/2" x 22 1/2" x 6 1/2" mains operated. Free teak sleeve with every kit.

£31.00 (GB post paid)

BUILT + TESTED £37.50

STEREO FM TUNER

Features capacity diode tuning, led & tuning meter Indicators, stabilized power supply - mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8" x 22 1/2" x 6 1/2". Complete kit with teak sleeve.

£21.00 (GB post paid) BUILT + TESTED £24.95

Join the large band of Happy Constructors!



PORTABLE RADIO

Activity counter complete with power pack **£9.97 post £1**

CALCULATORS

Sinclair Cambridge kit **£13.50**
Sinclair Cambridge (built) **£17.50**
Sinclair Memory **£22.50**
Sinclair Scientific **£26.95**

DOSEMETRES

0-5R 62p } 45p each per dozen
0-50R 62p }
0-150R 62p }

GRAVINER INFRA RED DETECTOR

Designed for heat or light detector. Containing 931A photo multiplier & GK45 & network **£3.50**

UHF TV TUNERS

625 line receiver UHF transistorised tuners FM UK operation. Brand new. (Post/packing 25p each)
TYPE C variable tuning **£2.50**
TYPE B 4-button push-button (adjustable) **£3.50**

EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output, 8-16 ohm load, 30 volt max DC operation complete with data. Price **£1.50** each, or 2 for **£2.85**
Printed Circuit Panels **50p**



EMI SPEAKERS SPECIAL PURCHASE

13 x 8 chassis speakers (carr/pack 30p each or 50p pair)
*150 °C 10 watts 8 ohm twin cone **£2.20**
*450 10 watts 4, 8, 15 ohm with twin tweeters and crossover **£3.85** each
EV 15 watt 8 ohm with tweeter **£5.25**
350 20 watt 8, 15 ohm with tweeter **£7.80** each
*Polished wood cabinet **£4.80** carr. etc. 35p each or 50p pair



TRANSISTORISED MODULES TUNERS-POWER SUPPLIES-AMPLIFIER

AMPLIFIERS (all single channel unless stated)

4-300	9 volt	300 MW O/P 3-8 OHM, 1-10 MV I/P	£1.75
2004	9 volt	250 MW O/P 3-8 OHM, 10-100MV I/P	£2.70
104	9 volt	1 watt O/P 8-16 OHM, 10 MV I/P	£3.10
304	9 volt	3 watt O/P 4-8 OHM, 10 MV I/P	£3.95
535	12 volt	3 watt O/P 8-16 OHM, 150 MV I/P	£4.10
555ST	12 volt	1 1/2 + 1 1/4 O/P 8 OHM, 150 MV I/P	£5.95
E1208	12 volt	5 watt O/P 4-16 OHM, 25-60 MV I/P	£5.10
608	24 volt	10 watt O/P 4-8 OHM, 30-50 MV I/P	£4.95
410	28 volt	10 watt O/P 8 OHM, 160 MV I/P	£4.95
620	45 volt	30 watt O/P 4-8 OHM, 150 MV I/P	£9.95
Z40	30/25 volt	15 watt O/P 4-8 OHM, 100 MV I/P	£5.45
Z60	45/50 volt	25 watt O/P 4-8 OHM, 100-250 MV I/P	£6.95
SA6817	24 volt	6 + 6 O/P 8 OHM, 100 MV I/P	£10.20

FM MODULES

Mullard LP 1186 FM tuner (front end) with data 10.7 MHz O/P **£4.85**
Mullard LP 1185 10.7 MHz IF unit with data **£4.50**
Gorler Permeability FM tuner (front end) 10.7 MHz O/P **£4.20**

FM and AM TUNERS AND DECODERS

FMS231 (tu 2) 6 volt FM tuner **£7.95**
TU3 12 volt version (FM use with Decoder) **£7.95**
SD4912 Stereo Decoder for Tu3. 12 volt **£7.95**
SP62H 6 volt stereo FM tuner **£14.80**
A1007 9 volt MW-AM tuner **£11.95**
Sinclair 12/45 volt FM tuner stereo recorder for above **£7.45**
A1018 9 volt FM tuner in cabinet **£13.95**
A1005M (S) 9-12 volt Stereo decoder FM for above **£7.50**
1062 12 volt Stereo decoder General purpose **£6.50**

PREAMPLIFIERS

Sinclair Stereo 60 Preamplifier **£6.75**
E1300 CART/TAPE/MIC INPUTS 9 volt **£2.85**
E131 Stereo 3-30 mV mal cart 9 volt **£4.75**
FF3 Stereo 3 mV tape head 9 volt **£4.95**
3042 Stereo 5-20 mV Mag. cart. mains **£5.95**
EQ25 Mono 3-250 mV TAPE/CART/FLAT 9 volt **£1.95**

8% VAT TO BE ADDED TO ALL ORDERS (EXPORT VAT FREE)

SUPPLIERS OF ELECTRONICS FOR OVER 30 YEARS

Prices & descriptions correct at time of proof. Subject to change without notice **E&OE**

ELECTRONIC COMPONENTS

(Post/Packing 15p per 1-6 Items GB unless stated)
Ceramic Filters **40p pair**
Miniature 10.7 MHz filters
Radio IC Chip ZN414 Radio IC with circuit **£1.20**
Ultrasonic transducers with data/circuits **£5.90 pair**
TAA 960 **£1.75**
Strobe tubes ZFT8A (similar to 4A) **£4.00**
ZFT12A **£5.00**
7 segment indicators 3015F with data **£1.70 each**
Spring delay units HR42 9" twin spring, pp 20p **£3.30**
HR16 twin spring, pp 25p **£6.85**
Fibre optics 0.01" diam. mono filament, per 100 metres **£5.50**
0.13" diam. 64 fibres, per metre **£1.00**
15m diam. mares tails each **£10.50**

TAPE-HEADS

Marriot XRSP/17 1/2 Track High **£2.50**
Marriot XRSP/18 1/2 Track Med **£3.50**
Marriot XRSP/36 1/2 Track Med **£5.00**
Marriot XRSP/63 1/2 Track High **£1.75**
Marriot Erase heads for XRSP 17/18/36 (XES 11) **75p**
Marriot 13X1ZE 343 1/2 Track Erase **75p**
R/RPI Record/Play 1/2 Track **45p**
H/RP Single Track Rec/Play **35p**
Bogen Type UJL90 Erase **£1.50**
Miniature Stereo Cassette Rec/Play **£2.25**

INVERTOR KITS

15 Watt **£5.20 post 30p**
40 Watt **£6.80 post 40p**

P.P.9 BATTERY ELIMINATOR
Complete kit of parts including P/C boards **£1.95 complete kit**

TRANSISTORISED CONDUCTORS

UK's largest stockists of branded guaranteed devices at low prices
EXTRA DISCOUNTS Any one type
Extra 10% for 12+, 15% +25, 20% 100+
The above also applies to mixed SN74 series IC.
Get your free stock list now - new '74-75 edition now available (Ref. No. 36).

AMTRON KITS

AVAILABLE EX-STOCK. SEND FOR FREE LISTS

JOSTY KITS

AVAILABLE EX-STOCK. SEND FOR FREE LISTS

SINCLAIR MODULES AND KITS



SINCLAIR PROJECT 80

ST80 Stereo PreAmplifier **£11.95**
Audio Filter Unit **£6.95**
Z40 15Watt Amplifier **£5.45**
Z60 25Watt Amplifier **£6.95**
PZ5 Power Supplies for 1 or 2 Z40 **£4.98**
PZ6 Power Supplies (S Tab) for 1 or 2 Z40 **£7.98**
PZ8 Power Supplies (S Tab) for 1 or 2 Z60 **£7.98**
TRANSFORMER FOR PZ8 FM TUNER **£3.95**
STEREO DECODER **£11.95**
IC20 power amp kit **£7.95**
PZ20 power supply for 1 or 2 IC 20 **£5.45**
All above post paid (GB only)

PACKAGE DEALS carriage/packing 35p

2 x Z40, S780, PZ5 **£25.00**
2 x Z60, S780, PZ6 **£27.75**
2 x Z60, S780, PZ8 + Trans **£34.40**

SINCLAIR SPECIAL PURCHASES

*Project 60 stereo preamplifier **£6.75 post 20p**
*Project 605 Kit **£19.95 post 25p**
I.C. 12 6V AMP **£2.10 post 15p**
*Cambridge calculator kit **£13.50 post 15p**
Sinclair Cambridge Memory **£22.50**
Cambridge Calculator built **£17.50 (post 15p)**
Cambridge Scientific built **£26.95 (post 15p)**

Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA- Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
FREE stock list on request

Phone or call Best prices Barclay Access cards welcomed