

RADIO & ELECTRONICS CONSTRUCTOR

OCTOBER 1975

30p

IN
THIS
ISSUE
FREE


VEROBOARD PROJECT ONE



VERSATILE LIGHT ALARM

VEROBOARD PROJECT TWO

BROADCAST BAND RECEIVER

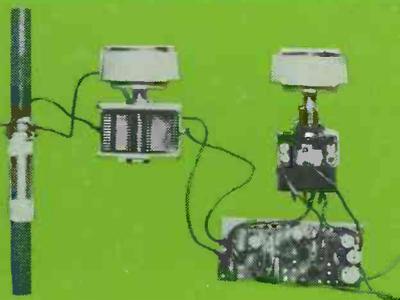

NEW TRANSISTORISED OSCILLOSCOPE

PART 2 (3 PARTS)

FREE PIECE OF VEROBOARD INSIDE



Each £3 unit of Home Unit Insurance gives you protection up to the limit shown

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or ½ units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company.

The Home Unit Policy can replace your existing insurances And remember - as you buy more possessions just add more Home Units at any time. *Quote Ref. 20/9468*

THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name

Address

20/9468

RADIO & ELECTRONICS CONSTRUCTOR

OCTOBER 1975
Volume 29 No. 3

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1975. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £4.00 (U.S.A. and Canada \$10.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

CONTENTS

VERSATILE LIGHT ALARM – Veroboard Project 1 by J. R. Davies	142
RECENT PUBLICATIONS	145
THE "TANTALISER" — An Electronic Game (Suggested Circuit 299) by G. A. French	146
NEWS AND COMMENT	148
TEN TIPS WITH INSULATING TAPE by K. Harker	150
CAN ANYONE HELP?	153
NEW TRANSISTORISED OSCILLOSCOPE – Part 2 by R. A. Penfold	154
BROADCAST BAND RECEIVER — Veroboard Project 2 by J. R. Davies	161
ANOTHER VERSATILE VERTICAL by V. S. Evans	167
AMATEUR RADIO TELEPRINTER SPEED STANDARDS by Arthur C. Gee	169
FOLDBACK LIMITING VOLTAGE REGULATORS by J. B. Dance	170
BATTERY CONDITION INDICATOR by P. R. Arthur	174
SHORT WAVE NEWS — For DX Listeners by Frank A. Baldwin	176
TRADE NEWS	178
IN YOUR WORKSHOP – Integrated Circuit Wheatstone Bridge	179
ELECTRONICS DATA – No. 3 (For the Beginner – Follow the Arrows)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

NOVEMBER ISSUE WILL BE
PUBLISHED ON 1st NOVEMBER

COMPONENTS

HOBBYIST - PROFESSIONAL - DOMESTIC - SURPLUS - INDUSTRIAL
 JUST A FEW OF OUR BARGAINS ARE LISTED BELOW - SEND STAMPED
 ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS.
 PAY US A VISIT. OVER 90% OF STOCK BELOW QUANTITY
 WHOLESALE PRICE. RETURN POSTAL SERVICE UNLESS CHEQUE.

Goods sent at customer's risk, unless sufficient payment for insurance included (2p per £1 Min 5p) U.K. only.

VALVE BASES	
Printed circuit B9A - B7G	2p
Chassis B7 - B9G - B7G	4p
Shrouded chassis B7G - B9A	6p
B8A - B9A chassis - B12A tube	6p

Speaker, 6" x 4", 5 ohm, ideal for car radio etc. £1

TAG STRIP - 6 way	3p	VHF Radio Tuner Head	80p
9 way	5p	Takes ECC 85	

1 1/4 glass fuses - 250 m/a or 3 amp (box of 12)	18p
3" tape spools	8p
Brand new Boxed 6K7G	25p
PVC or metal clip on M.E.S. bulb holder	5p
Geared Knob, Inner to Outer Ratio 8:1	60p
Bulgin, 5mm Jack plug and switched socket (pair)	30p
12 volt solenoid and plunger	30p
250 RPM 50 c/s locked frequency miniature mains motor	50p
200 OHM coil, 2 1/4" long, hollow centre	10p
Belling Lee white plastic surface coax outlet Box	30p
R.S. 12 way standard plug and shell	20p

SWITCHES		
Pole	Way	Type
4	2	Sub. Min. Slide
6	2	Slide
4	2	Lever Slide
2	2	Slide
1	3	+ off Sub. min. edge
1	3	13 amp small rotary
2	2	Locking with 2 to 3 keys
2	1	2 Amp 250V A.C. rotary
1	2	Toggle
Wafer Rotary, all types		
S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting		

1 1/2 METER AUDIO LEAD

5 pin din plug 180° both ends 68p

COMPUTER AND AUDIO BOARDS

VARYING PANELS WITH ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES ETC.

3lb for 85p + 60p post and packing
 7lb for £1.75 + 80p post and packing

Skeleton Presets Slider, horizontal or vertical standard or submin. 5p	Clear Plastic Boxes For component storage or projects, sliding lid. 1 1/2" x 1 1/2" 10p
--	---

KNOB

SILVER METAL PUSH ON WITH POINTER, OR WHITE PLASTIC, GRUB SCREW WITH POINTER AND SILVER CENTRE 8p EACH.
 1" DIAM. WITH 1 1/2" SKIRT SPUN ALUMINIUM GRUB SCREW FIXING, 1/2" 30p EACH.

ZM1162A INDICATOR TUBE

0-9 Inline End View. Rectangular Envelope 170V 2.5M/A £1.50

RESETTABLE COUNTER

English Numbering Machines LTD.
 MODEL 4436-159-989

6-14 volt, 6 digit, illuminated, fully enclosed. £2.50

Ferric Chloride, Anhydrous mil. spec. 1lb. bag 50p

TO3 or TO66	
Mica Washer	2p
18 volt 4 amp charger, bridge rectifier	50p
GC10/4B	£3.00

Telescopic aerial	
Closed 9 1/2", open 38 1/2"	
Fitted right angle TV plug, 50p	

RESISTORS	
1/4 - 1/2 watt	1p
1 watt	2p
Up to 5 watt wire	10p
10 watt wire wound	12p
15 watt	14p

Philips transformer, safety fused. In 200-220-240v. Out 240v 60ma + 6.3v 1a approx 2" x 2 1/2" x 2 1/2" £1.50

POTS

Log or Lin carbon	13p
Switched	25p
Dual Pots	38p
Dual & switch	50p
Lin wirewound	25p
Slider Pot	25p
Dual Slider	35p

THERMISTORS

VA1008, VA1034, VA1039, VA1040, VA1055, VA1066, VA1082, VA1100, VA1077, VA1005, VA1026	10p
	15p

RELAYS

12 volt S.P.C.O octal mercury wetted high speed	75p
P.O. 3000 type, 1,000 OHM coil, 4 pole c/o	60p
Mains or 12v d.p.c.o. heavy duty octal	60p

Boxed GEC KT88 valve £2

JAP 4 gang min. sealed tuning condensers New 25p
 Ex-eqpt. 2 or 4 gang 15p

ELECTROLYTICS MFD/VOLT. Many others in stock 70- 200- 300- 450-
 Up to 10V 25V 50V 75V 100V 250V 350V 500V MFD

10	4p	5p	6p	8p	8p	12p	16p	20p
25	4p	5p	6p	8p	8p	15p	18p	20p
50	4p	5p	6p	9p	13p	18p	25p	—
100	5p	6p	10p	12p	19p	20p	—	—
250	9p	10p	11p	17p	28p	—	85p	£1
500	10p	11p	17p	24p	45p	—	—	—
1000	13p	17p	40p	75p	—	£1.50	—	—
2000	23p	37p	45p	—	—	—	—	—

As total number of values are too numerous to list, use this price guide to work out cost of your actual value requirements, i.e. 2MFD, 30V would be 5p, or 330MFD, 50V would be 14p, etc. etc.
 8/20, 10/20, 12/20 Tubular tantalum 15p each
 16-32/275, 32-32/275, 100-100/150, 100-100/275 50-50/300 20p each
 50/50-385 30p
 12,000/12, 32-32-50/300, 700/200 100-100-100-150-150/320 50p each
 20-20-20/350 40p each

INDICATORS

Bulgin D676 red, takes M.E.S. bulb	20p
12 volt red, small pushfit	20p
Mains neon, red, pushfit	20p

CAPACITOR GUIDE - maximum 500V

Up to .01 ceramic 2p. Up to .01 poly 3p.
 Up to 1000PF silver mica 5p. 1,200PF up to .01 silver mica 10p. .013 up to .25 poly etc. 4p.
 .27 up to .68 poly etc. 6p
 Over 500 volt order from above guide and few others listed below.
 6p. .1/600; 10p. .01/1000, 1/350, 8/20, .1/900, .22/900, 4/16, .25/250 AC (600vDC) .1/1500
 40p. 5/150, 9/275AC, 10/150, 15/150, 40/150.

TRIMMERS, 20p each

100PF Ceramic, 30PF Beehive, 12PF PTFE 2500PF 750 volt, 33PF MIN. AIR SPACED 5PF. MIN. AIR SPACED, 50PF CERAMIC.

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 3p each
 Strong grey plastic box same design as die cast ali 4 3/8" x 2 3/8" x 1 1/2" 40p

1" or 1 1/8" or 3/4" CAN CLIPS 2p

MAINS DROPPERS

36 + 79 ohm	15p
66 + 66 + 158 ohm, 66 + 66 + 137 ohm	
17 + 14 + 6 ohm, 266 + 14 + 193 ohm	20p
50 + 40 + 1k5 ohm	
285 + 575 + 148 + 35 ohm	30p
25 + 35 + 97 + 59 + 30 ohm	

5 1/2" x 2 1/2" Speaker, ex-equipment 3 ohm	30p
2 Amp Suppression Choke	5p
3 x 2 1/2" x 1 1/8" PAXOLINE	2p
4 5/8" x 1/2" x 1/8"	2 for 1p
220K & 100 ohm 3 watt resistors	4p
VALVE RETAINER CLIP, adjustable	2p

OUTPUT TRANSFORMERS

Sub-miniature Transistor Type	25p
Valve type, centre tapped or straight	40p

3 pin din to open end, 1 1/2yd twin screened lead 35p

Whiteley Stentorian 3 ohm constant impedance volume control way below trade at 80p

Drive Cord 1p per yd.

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 7 p.m. Monday to Saturday - Also Sunday afternoons

Telephone: 01-223 5016

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AC107 .. 12p	BC179B .. 11p	BF180/1/2/3 .. 20p
AC128 .. 5p	BC184C .. 9p	BF184/5 .. 15p
AC176 .. 10p	BC186/7 .. 13p	BF194/5/6/7 .. 5p
AC278 .. 18p	BC213L/214B .. 9p	BF194A/195C .. 12p
AD149 .. 40p	BC261B .. 10p	BF200 .. 10p
AD161/2 matched pr. 69p	BC327 .. 12p	BF258 .. 24p
AF116/7 .. 12p	BC328 .. 10p	BF262/3 .. 23p
AF124/6/7 .. 20p	BC337/8 .. 14p	BF336 .. 25p
AF139/178 .. 30p	BC547/558A .. 7p	BFS28 Dual Mosfet 92p
AF239 .. 20p	BC548 .. 9p	BFW10/11 F.E.T. 26p
ASY27/73 .. 25p	BCX32/36 .. 12p	BFW30 .. £1.35
BC107A or B .. 9p	BCY40 .. 60p	BFW57/58 .. 20p
BC107/8/9 .. 7p	BCY70/1/2 .. 9p	BFX12 .. 20p
BC108A/B/109B/C 10p	BD112/3/5/6 .. 40p	BFX29/30/84/88 16p
BC147/8/9 .. 6p	BD131/2/3/5 .. 30p	BFY50/1/2 .. 12p
BC147A/B .. 8p	BD201/2/3/4 .. £1.00	BFY90 .. 50p
BC148A/B, 9B/C/S 8p	BD232/4/5 .. 46p	BR101 .. 30p
BC157/8/9 .. 6p	BDX77 .. £1.40	BRY39 } Programmable Unj Junction 31p
BC158A/B .. 11p	BF115 .. 12p	BRYS6 .. 34p
BC159B/C.157A 11p	BF167/173 .. 15p	BSV64 .. 40p
BC178A/B .. 12p	BF178/9 .. 20p	BSV79/80 F.E.T.s £1

BSV81 Mosfet .. 90p	OTHER DIODES
BSX20/21 .. 13p	IN916 .. 6p
BSY40 .. 28p	IN4148 .. 2.5p
BU105-01 .. 93p	BA145/148 .. 12p
CV7042 (OC41 OC44, ASY63) .. 7p	Centercel .. 10p
GET111 .. 40p	BZY61 .. 10p
OC35 .. 32½p	BB103/110 Varicap 18p
ON222 .. 30p	BA182 .. 18p
TIP30 .. 52p	OA5/7/10 .. 10p
TIP3055 .. 50p	BZY88 Up to 33 volt 6p
TIS88A FET .. 23p	BZX61 11 volt .. 16p
ZTX300 .. 8p	BR100 Diac. .. 19p
2N393/MA393 .. 30p	
2N706 .. 8p	
2N929 .. 14p	
2N987 .. 35p	
2N1507/2219 .. 17p	
2N2401/2412/2483 25p	
2N2904/5/6/7 .. 13p	
2N2907A .. 15p	
2N3053 .. 13p	
2N3054/3055 (or equiv) 35p	
2N3133 .. 18p	
2N3704 .. 10p	
2N4037 .. 35p	
2N5036 .. 60p	
2SA141/2/360 .. 31p	
2SB135/6/457 .. 20p	
40250 .. 60p	

BRIDGE RECTIFIERS			
Amp	Volt		
½	1.600	BYX10	30p
1	140	OSH01-200	30p
1.4	42	BY164	28p

INTEGRATED CIRCUITS	
741 8 pin d.i.l. op. Amp	20p
TAD100 AMRF	£1.00
CA3001 R. F. Amp	£1.00
TAA300 1wt Amp	£1.25
NE555v Timer	42p
TAA550 Y or G	31p
TAA263 Amp	65p
ZN414 RX	95p
7400/2/10/20/30	13p
7404	14p
7414	60p
7438/74/86	27p
7483	80p
LM300, 2-20 volt	50p
74154	£1.50

RECTIFIERS			
Amp	Volt		
IN4004	1	400	} 4p
IN4005	1	600	
IN4006	1	800	
IN4007	1	1,000	
BY103	1	1,500	15p
SR100	1.5	100	7p
SR400	1.5	400	8p
REC53A	1.5	1,250	14p
LT102	2	30	10p
BYX38-600	2.5	600	40p
BYX38-300R	2.5	300	36p
BYX38-900	2.5	900	45p
BYX38-1200	2.5	1,200	50p
BYX49-600	2.5	600	34p
BYX49-300	2.5	300	26p
BYX49-900	2.5	900	40p
BYX49-1200	2.5	1,200	52p
BYX48-300	6	300	40p
BYX48-600	6	600	50p
BYX48-900	6	900	60p
BYX48-1200	6	1,200	80p
BYX72-150R	10	150	35p
BYX72-300R	10	300	45p
BYX72-600R	10	600	55p
BYX42-300	10	300	30p
BYX42-600	10	600	65p
BYX42-900	10	900	80p
BYX42-1200	10	1,200	95p
BYX46-300*	15	300	£1.00
BYX46-400*	15	400	£1.50
BYX46-500*	15	500	£1.75
BYX46-600*	15	600	£2.00
BYX20-200	25	200	60p
BYX52-300	40	300	£1.75
BYX52-1200	40	1,200	£2.50

OPTO ELECTRONICS			
ORP12	44p	Photo transistor	
BPX40	65p	BPX29	£1.00
BPX42	£1.00	OCP71	30p
BPY10	£1.00	BIG L.E.D. 0.2"	
(VOLIAC)		2v 50mA max.	
BPY68	} £1.00	RED	14p
BPY69		ORANGE	} 16p
BPY77		GREEN	
Diodes		YELLOW	

THYRISTORS	
Amp	Volt
1	240
1	400
1	240
6.5	500
15	500
6.5	500
6.5	500
20	600
15	800
30	1000

TRIACS			
Amp	Volt		
6	400	Plastic	74p
25	900	BTX94-900	£4.00
25	1200	BTX94-1200	£6.00
12-0-12 50M/A Min. Txmfr. 90p			
Pair of LA2407 Ferroxc cores with adjuster 25p			
Chrome Car Radio facia 15p			
Rubber Car Radio gasket 5p			
DLI Pal Delayline 50p			
Relay socket 10p			
Take miniature 2PCO relay			
B7G or B9A valve can 2p			
0-30, or 0-15, black pvc. 360° dial, silver digits, self adhesive, 4½" dia. 10p			

PHOTO SILICON CONTROLLED SWITCH	
BPX66 PNP	10 amp £1.00
.3" red 7 segment L.E.D. 14	
D.I.L. 0-9 + D.P. display 1.9v, 10mA segmet	65p
COY11B L.E.D.	
Infra red transmitter	£1
One fifth of trade	

PAPER BLOCK CONDENSER		
0.25MFD	800 volt	30p
1MFD	250 volt	15p
2MFD	250 volt	20p
10MFD	500 volt	80p
4MFD	250 volt	20p
15MFD	150 volt	50p

SOLDER	
Multicore - 2½p foot	
ENAM. COPPER WIRE	
SWG.	PER YD.
18	3p
20-24	2p
26-42	1p

METAL CHASSIS SOCKETS	
Car Aerial	
Coax	
5 or 6 pin 240° din	} 9p
Speaker din switched	
3.5mm Switched Socket	

GARRARD	
GCS23T Crystal Stereo Cartridge	£1.00

WIRE ENDED GLASS NEONS	
5p	
PLASTIC, TRANSISTOR OR DIODE HOLDER	
1p	
TRANSISTOR OR DIODE PAD	
1p	
HOLDERS OR PADS	
50pper100	

WIRE ENDED GLASS NEONS	
5p	

HANDLES	
Rigid light blue nylon 6½" with secret fitting screws	5p
14 D.I.L. socket, gold plated contacts, NOT cheap type	13p
Miniature Axial Lead Ferrite Choke formers	2p

Tested unmarked, or marked ample lead ex new equipment

TO3 HEATSINK	
Europelec HP1 TO3B individual 'curly' power transistor type. Ready drilled	20p

DEE PLUG	
McMurdo DA15P 15 way chassis plug	10p
Fairway 18009 Coax socket	3p

ACY17-20	8p	OC71/2	5p
ASZ20	8p	OC200-5	10p
ASZ21	15p	TIC44	24p
BC186	11p	2G240	2-50
BCY30-34	10p	2G302	6p
BCY70/1/2	8p	2G401	10p
BF115	10p	2N711	25p
BY127	7p	2N2926	7p
BZY88 series	5p	2N598/9	6p
HG1005	2p	2N1091	8p
HG5009	2p	2N1302	8p
HG5079	2p	2N1907	2-50
L78/9	2p	Germ. diode 1p	
M3	10p	GET120 (AC128 in 1" sq. heatsink)	
OA81	2p		
OA47	2p		
OA200-2	3p	GET872	12p
OC23	20p	253230	30p

U.E.C.L. 10 way pin connector	
2B6000	10p
OA1P10	10p
U.E.C.L. 20 way pin connector	
2A60000A1P20	20p

TIE CLIPS	
Nylon self locking 7" or 3½"	2p

U.E.C.L. 20 way pin socket	
B260800A1R20	20p
3.5mm STEREO PLUG	
Metal screened	35p

CINCH 150	
12 way edge socket	10p

Philips electronic engineer kits add on series E1004	£1.00 each
RG4-1250 Mercury vapour rectifier	£5.00

1lb Mixed nuts, bolts, washers etc.	35p
-------------------------------------	-----

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE
LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.
TOTAL GOODS PLUS CARRIAGE, ADD V.A.T.

MAIL ORDER CUSTOMERS ONLY ADD 8% V.A.T.

NOW AVAILABLE . . .



Comprising
765 pages
inc. index

AUGUST 1974
to JULY 1975

LATEST BOUND VOLUME No. 28

of
"Radio & Electronics
Constructor"

FOR YOUR LIBRARY
PRICE £2.75 P&P 50p

BOUND VOLUME No. 25 (August 1971 to July 1972)

PRICE £2.00 p. & p. 50p

BOUND VOLUME No. 27 (August 1973 to July 1974)

PRICE £2.40 p. & p. 50p


Limited number of these volumes still available

We regret all earlier volumes are now completely sold out.
Available only from

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W9 1SN

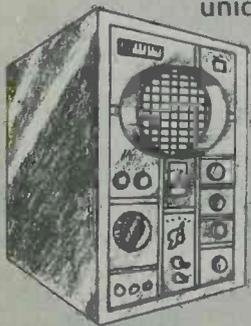1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

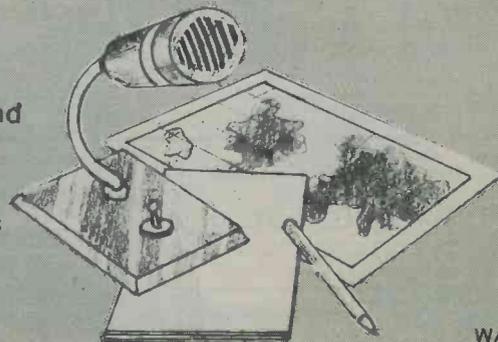2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



WAA

Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept REL 105
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ Block caps please



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohm £8.64
 Baker Group 35, 3, 8 or 15 ohm £10.25
 Baker Group 50/12, 8 or 15 ohm £14.00
 Baker Deluxe 12", 8 or 15 ohm £13.75
 Baker Major 3, 8 or 15 ohm £11.87
 Baker Superb 8 or 15 ohm £18.12
 Baker Regent 8 or 15 ohm £10.00
 Baker Auditorium 12" £16.25
 Celestion PST8 (for Unilex) £3.75
 Celestion G12H 8 or 15 ohm £18.45
 Celestion G12M 8 or 15 ohm £15.00
 Celestion G15C 8 or 15 ohm £30.25
 Celestion G18C 8 or 15 ohm £39.95
 Celestion MH1000 8 or 15 ohm £15.60
 EMI 13 x 8, 150 d/cone, 8 ohm £2.94
 EMI 13 x 8 type 350, 8 or 15 ohm £9.56
 EMI 13 x 8 20 watt bass £7.69
 EMI 5" 14A/730 mid-range 8 ohm £3.50
 EMI 6 1/2" 93850 4 or 8 ohm £2.90
 EMI 8 x 5, cer. mag. 8 ohm £1.87
 EMI 8 x 5, 10 watt, d/c roll/s 8 ohm £3.44
 EMI 10 x 6 93870 8 ohm £2.69
 EMI 2 1/2" tweeter 8 ohm .77
 Elac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm £3.64
 Elac 6 1/2" d/cone, roll surr. 8 ohm £4.06
 Elac 6 1/2" d/cone 8 ohm £3.12
 Elac TW4 4" tweeter £1.75
 Elat 10" 10RM239 d/c 8 ohm £3.12
 Elac 8" 3 ohm £2.87
 Eagle Crossover 3, 8 or 16 ohm £1.75
 Eagle CT5 cone tweeter 8 ohm £2.06
 Eagle CT10 tweeter 8 or 16 ohm £3.00
 Eagle DT33 dome tweeter 8 ohm £6.31
 Eagle FF5 3 way crossover £3.62
 Eagle SN75 crossover with tw. control £4.69
 Eagle FF28 multicell, horn £9.00
 Eagle HT15 horn tw. 16 ohm £4.40
 Eagle HT21 horn tw. 8 ohm £6.81
 Eagle MHT10 horn tw. 8 ohm £4.44
 Eagle FR4 4" full range £6.12
 Eagle FR65 6 1/2" full range £9.62
 Eagle FR8 8" full range £12.31
 Fane Pop 15 watt 12" £5.25
 Fane Pop 25T 30 watt 12" £7.50
 Fane Pop watt 12" £12.00
 Fane Pop 55 12" 60 watt £13.95
 Fane Pop 60 watt 15" £14.75
 Fane Pop 100 watt 18" £25.95

SPEAKERS

Fane Crescendo 12A 8 or 15 ohm £34.50
 Fane Crescendo 12B 8 or 15 ohm £36.50
 Fane Crescendo 15, 8 or 15 ohm £47.50
 Fane Crescendo 18, 8 or 15 ohm £62.95
 Fane 910 horn £14.95
 Fane 920 horn £33.95
 Fane 152/12a 15" 15 ohm £16.00
 Fane 801T 8" d/cone roll surr. £8.12
 Fane 808T 8" d/cone £3.44
 Fane 807T 8" d/cone roll surr. £5.75
 Goodmans 8P 8 or 15 ohm £5.50
 Goodmans 10P 8 or 15 ohm £5.80
 Goodmans 12P 8 or 15 ohm £13.95
 Goodmans 12P-D 8 or 15 ohm £16.95
 Goodmans 12P-G 8 or 15 ohm £15.95
 Goodman 12AX 100 watt 8 or 15 ohm £36.50
 Goodmans 15AX 100 watt 8 or 15 ohm £40.25
 Goodmans 15P 8 or 15 ohm £21.00
 Goodmans 18P 8 or 15 ohm £36.00
 Goodmans Hifax 750 £16.00
 Goodmans Axent 100 tweeter & crossover £7.44
 Goodmans Audiom 100, 8 or 15 ohm £13.90
 Goodmans Axiom 401, 8 or 15 ohm £20.00
 Goodmans Twinaxiom 8" 8 or 15 ohm £10.14
 Goodmans Twinaxiom 10" 8 or 15 ohm £10.75
 Gauss 12" full range 8 ohm £69.50
 Gauss 12" Bass 8 ohm £69.50
 Gauss 15" full range 8 ohm £75.00
 Gauss 15" Bass 8 ohm £75.00
 Gauss 18" full range 8 ohm £80.00
 Gauss 18" Bass 8 ohm £80.00
 £1.06 All the above Gauss (American) speakers are fitted with 4 1/2" voice coils and can handle 200 watts RMS.
 Kef T27 £6.06
 Kef T15 £6.94
 Kef B110 £8.37
 Kef B200 £9.50
 Kef B139 £16.50
 Kef DN8 £2.31
 Kef DN12 £5.75
 Kef DN13 £3.87
 Richard Allan CG8T 8" d/c roll surr. 8 ohms £7.37
 STC 4001G super tweeter £6.56
 2 1/2" 64 ohm, 70mm 8 ohm, 70mm 80 ohm .77
 2 1/2" 75 ohm .55
 7" x 4" 3, 8 or 15 ohm £1.63
 8" x 5" 3, 8 or 15 ohm £1.75
 10" x 6" 6, 8 or 15 ohm £2.69

SPEAKER KITS (Carr. 75p each. £1.50 pair)

Baker Major Module 3, 8 or 15 ohm each £13.44
 Goodmans Mezzo Twinkit pair £47.19
 Goodmans DIN 20 4 ohm each £13.44
 Helme XLK25 pair £25.44
 Helme XLK30 pair £17.19
 Helme XLK50 pair £46.25
 Kefkit 1 pair £48.44
 Kefkit 3 each £42.50
 Peerless 3-15 (3 sp. system) each £17.44
 Peerless 20/2 each £17.44
 Peerless 30/2 each £24.38
 Peerless 20/3 each £26.56
 Peerless 50/4 each £40.50
 Richard Allan Twinkit each £10.37
 Richard Allan Triple 8 each £15.94
 Richard Allan Triple each £23.12
 Richard Allan Super Triple each £27.50
 Wharfedale Linton 2 kit pair £23.12
 Wharfedale Glendale 3 kit pair £40.61
 Wharfedale Dovedale 3 kit pair £63.12

PA/DISCO AMPLIFIERS (Carr. and ins. £1)

Baker Major 100 watt £57.25
 Linear 30/40 £30.00
 Linear 40/60 £35.00
 Linear 80/100 £58.95
 Linear 100 watt slave £44.00
 Eagle PRO A120, 120 watts RMS £129.00
 Eagle PRO A65, 65 watts RMS £98.50
 Eagle PRO A35, 35 watts RMS £77.00
 Eagles TPA40 mains/12v mobile £50.00
 Eagle HHS 36 watts, mobile 12v. £37.50
 Eagle TPA20 paging amplifier £45.00
 Eagle RA859 Reverb (p. & p. 75p) £18.25
 Eagle RA856 Reverb (p. & p. 75p) £12.50

MICROPHONES (p. & p. 50p)

Shure 515 SB Low Impedance £17.31
 Shure 515 SA High Impedance £18.25
 Shure 545 Dual Impedance £34.69
 Shure 588 SB Low Impedance £23.12
 Shure 588 SA High Impedance £23.75

FREE with loudspeaker orders over £7 - "HiFi Loudspeaker Enclosures" book

All items guaranteed new and perfect

Prompt despatch

Carriage: 38p per speaker 12" and up 50p each, 25p per tweeter, crossover or 2 1/2" / 70mm speaker kits 75p each (£1.50 pair)

Including VAT - 25%

Send stamp for free booklet 'Choosing a speaker'

Big discounts on Grundig, ITT, Koyo, etc. Send stamp for list

WILMSLOW AUDIO

DEPT RC

LOUDSPEAKERS: SWAN WORKS BANK SQUARE, WILMSLOW, CHESHIRE

AMPLIFIERS, RADIO ETC. 10 SWAN ST., WILMSLOW, CHESHIRE


The Ultimate Radio!

GRUNDIG SATELLIT 2000

You've got your yacht, private aircraft, Rolls Comiche? — then all you need for a full set of status symbols is this latest model Grundig Satellit, Germany's top radio! Radio performance, appearance and sound quality are all superb. VHF/FM, MW, LW 10 SW bands plus bandspread, 27 transistors and 22 diodes. Battery/Mains (110/240v.). 2 speakers, 57" telescopic aerial.

Our Price £149.95 inc. VAT, carr. & ins.

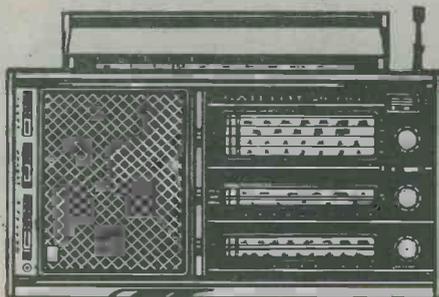Big discounts on Grundig, ITT, Koyo, etc. Send stamp for list.



WILMSLOW AUDIO, 10 SWAN STREET, WILMSLOW, CHESHIRE

TRANSISTORS

BRAND NEW FULLY GUARANTEED

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
AC107	0-20	BSY40	0-29	AF118	0-36	ORP61	0-41*	BC172	0-15
AC113	0-19	BSY41	0-29	AF124	0-31	P20	0-51*	BP167	0-22
AC115	0-20	BSY95	0-13	AF125	0-31	PC45A	0-20	BP173	0-22
AC117K	0-30	BSY95A	0-13	AF126	0-29	P397	0-43*	BF176	0-36
AC122	0-12	BU105	£2-04	AF127	0-29	ST140	0-13	BF177	0-36
AC125	0-18	CU11E	0-51	AF139	0-31	ST141	0-18	BF178	0-31
AC126	0-18	C400	0-31	AF178	0-51	TIP29	0-44	BF179	0-31
AC127	0-19	C407	0-28	AF179	0-51	TIP30	0-52	BF180	0-31
AC128	0-19	C424	0-28	AF180	0-51	TIP31A	0-56	BF181	0-31
AC132	0-15	C425	0-51	AF181	0-51	TIP32A	0-68	BF182	0-41
AC134	0-15	C426	0-36	AF186	0-51	TIP41A	0-68	BF183	0-51
AC137	0-15	C428	0-20	AF239	0-38	TIP42A	0-81	BF184	0-31
AC141	0-19	C441	0-31	AL102	0-68	TR843	0-31*	BF185	0-31
AC141K	0-30	C442	0-31	AL103	0-68	UT46	0-28*	BF187	0-28
AC142	0-19	C444	0-36	ASV26	0-28	ZN414	1-11	BF188	0-41
AC142K	0-28	C450	0-22	ASV27	0-31	ZN301	0-19	BF194	0-12
AC151	0-16	MAT100	0-19	ASV28	0-28	ZG302	0-19	BF195	0-12
AC154	0-20	MAT101	0-20	ASV29	0-26	ZG303	0-19	BF196	0-15
AC155	0-20	MAT120	0-18	ASV30	0-26	ZG304	0-25	BF197	0-15
AC156	0-20	MAT121	0-20	ASV31	0-26	ZG306	0-41	BF200	0-46
AC157	0-25	MJ E521	0-58	ASV32	0-28	ZG308	0-36	BF222	0-98
AC158	0-25	MJE2955	0-38	ASV34	0-36	ZN2926 R 0-13		BF257	0-46
AC166	0-20	MJE3055	0-57	ASV53	0-28	ZN2926 V 0-11		BF259	0-61
AC167	0-20	MJE3440	0-51	ASV56	0-28	ZN2926 R 0-10		BF259	0-61
AC168	0-25	MFF102	0-43	ASV57	0-26	ZN2926 R 0-10		BF259	0-61
AC169	0-15	MFF104	0-38	ASV58	0-28	ZN2926 D 0-10		BF263	0-56
AC176	0-20	MPP105	0-38	ASV73	0-28	ZN3010	0-71	BF270	0-36
AC177	0-25	OC44	0-38	ASZ21	0-41	ZN3011	0-15	BF271	0-31
AC178	0-29	OC20	0-36	BC107	0-67	ZN3053	0-18	BF272	0-31
AC179	0-29	OC22	0-47	BC108	0-68	ZN3054	0-47	BF273	0-31
AC180	0-20	OC23	0-49	BC109	0-68	ZN3055	0-42	BF274	0-36
AC180K	0-30	OC24	0-57	BD136	0-41	ZN3319	0-15	BFW20	0-61
AC181	0-20	OC25	0-39	BD137	0-46	ZN3391 A 0-17		BFX29	0-28
AC181K	0-30	OC26	0-30	BD138	0-51	ZN3392	0-15	BFX28	0-22
AC187	0-22	OC28	0-31	BD139	0-57	ZN3393	0-15	BFX35	0-31
AC187K	0-23	OC29	0-51	BD140	0-61	ZN3394	0-15	BFX46	0-22
AC188	0-22	OC25	0-43	BD155	0-81	ZN3395	0-18	BFX67	0-25
AC188K	0-23	OC36	0-51	BD175	0-61	ZN3402	0-21	BFX88	0-22
AC176	0-26	OC41	0-20	BD176	0-61	ZN3403	0-21	BFY50	0-20
AC177	0-25	OC42	0-25	BD177	0-67	ZN3404	0-29	BFY51	0-20
AC178	0-29	OC20	0-36	BD178	0-67	ZN3405	0-43	BFY52	0-20
AC179	0-29	OC22	0-47	BD179	0-71	ZN3414	0-18	CG309	0-37
AC180	0-20	OC23	0-49	BD180	0-71	ZN3415	0-18	CG339	0-20
AC180K	0-30	OC24	0-57	BD185	0-67	ZN3416	0-29	ZG339A	0-17
AC181	0-20	OC25	0-39	BD186	0-67	ZN3417	0-29	ZG344	0-19
AC181K	0-30	OC26	0-30	BD187	0-71	ZN3525	0-77*	ZG345	0-17
AC187	0-22	OC28	0-31	BD188	0-71	ZN3614	0-89	ZG371	0-17
AC187K	0-23	OC29	0-51	BD189	0-77	ZN3615	0-76	ZG373	0-18
AC188	0-22	OC25	0-43	BD190	0-77	ZN3616	0-76	ZG373	0-18
AC188K	0-23	OC36	0-51	BD195	0-87	ZN3646	0-09	ZG374	0-18
AC176	0-26	OC41	0-20	BD196	0-87	ZN3702	0-12	ZG377	0-31
AC177	0-25	OC42	0-25	BD197	0-92	ZN3703	0-12	ZG378	0-17
AC178	0-29	OC20	0-36	BD198	0-92	ZN3704	0-13	ZG381	0-17
AC179	0-29	OC22	0-47	BD199	0-92	ZN3705	0-12	ZG382	0-17
AC180	0-20	OC23	0-49	BD200	0-88	ZN3706	0-12	ZG401	0-31
AC180K	0-30	OC24	0-57	BD205	0-81	ZN3707	0-13	ZG414	0-31
AC181	0-20	OC25	0-39	BD206	0-81	ZN3708	0-08	ZG417	0-26
AC181K	0-30	OC26	0-30	BD207	0-98	ZN3709	0-09	ZN388	0-36
AC187	0-22	OC28	0-31	BD208	0-98	ZN3710	0-09	ZN388A	0-56
AC187K	0-23	OC29	0-51	BD209	0-98	ZN3714	0-09	ZN404	0-20
AC188	0-22	OC25	0-43	BD215	0-25	ZN3819	0-29	ZN404A	0-20
AC188K	0-23	OC36	0-51	BD217	0-46	ZN3820	0-51	ZN524	0-43
AC176	0-26	OC41	0-20	BD218	0-71	ZN3821	0-36	ZN527	0-50
AC177	0-25	OC42	0-25	BD219	0-77	ZN3823	0-29	ZN598	0-43
AC178	0-29	OC20	0-36	BD219	0-77	ZN3903	0-29	ZN599	0-46
AC179	0-29	OC22	0-47	BD219	0-77	ZN3904	0-31	ZN696	0-13
AC180	0-20	OC23	0-49	BD219	0-77	ZN3907	0-29	ZN697	0-14
AC180K	0-30	OC24	0-57	BD219	0-77	ZN3908	0-28	ZN698	0-25
AC181	0-20	OC25	0-39	BD219	0-77	ZN4068	0-12	ZN699	0-38
AC181K	0-30	OC26	0-30	BD219	0-77	ZN4059	0-10	ZN706	0-08
AC187	0-22	OC28	0-31	BD219	0-77	ZN4060	0-12	ZN708	0-12
AC187K	0-23	OC29	0-51	BD219	0-77	ZN4062	0-14	ZN708	0-12
AC188	0-22	OC25	0-43	BD219	0-77	BC113	0-10	ZN711	0-31
AC188K	0-23	OC36	0-51	BD219	0-77	BC114	0-16	ZN717	0-36
AC176	0-26	OC41	0-20	BD219	0-77	BC115	0-16	ZN718	0-25
AC177	0-25	OC42	0-25	BD219	0-77	BC116	0-16	ZN718	0-25
AC178	0-29	OC20	0-36	BD219	0-77	BC117	0-19	ZN718A	0-51
AC179	0-29	OC22	0-47	BD219	0-77	BC118	0-10	ZN726	0-29
AC180	0-20	OC23	0-49	BD219	0-77	BC119	0-31	ZN727	0-29
AC180K	0-30	OC24	0-57	BD219	0-77	BC120	0-81	ZN743	0-20
AC181	0-20	OC25	0-39	BD219	0-77	BC125	0-12	ZN744	0-29
AC181K	0-30	OC26	0-30	BD219	0-77	BC126	0-19	ZN914	0-16
AC187	0-22	OC28	0-31	BD219	0-77	BC132	0-12	ZN4061	0-12
AC187K	0-23	OC29	0-51	BD219	0-77	BC134	0-19	ZN4062	0-12
AC188	0-22	OC25	0-43	BD219	0-77	BC135	0-12	ZN4284	0-18
AC188K	0-23	OC36	0-51	BD219	0-77	BC136	0-18	ZN4285	0-18
AC176	0-26	OC41	0-20	BD219	0-77	BC137	0-18	ZN4286	0-18
AC177	0-25	OC42	0-25	BD219	0-77	BC139	0-41	ZN4287	0-18
AC178	0-29	OC20	0-36	BD219	0-77	BC140	0-31	ZN4288	0-18
AC179	0-29	OC22	0-47	BD219	0-77	BC141	0-31	ZN4289	0-18
AC180	0-20	OC23	0-49	BD219	0-77	BC142	0-31	ZN4290	0-18
AC180K	0-30	OC24	0-57	BD219	0-77	BC143	0-31	ZN4291	0-18
AC181	0-20	OC25	0-39	BD219	0-77	BC144	0-39	ZN4292	0-18
AC181K	0-30	OC26	0-30	BD219	0-77	BC147	0-10	ZN4293	0-18
AC187	0-22	OC28	0-31	BD219	0-77	BC148	0-10	ZN5172	0-12
AC187K	0-23	OC29	0-51	BD219	0-77	BC149	0-12	ZN5194	0-56
AC188	0-22	OC25	0-43	BD219	0-77	BC150	0-19	ZN5294	0-58
AC188K	0-23	OC36	0-51	BD219	0-77	BC151	0-20	ZN5296	0-56
AC176	0-26	OC41	0-20	BD219	0-77	BC152	0-18	ZN5457	0-39
AC177	0-25	OC42	0-25	BD219	0-77	BC153	0-29	ZN5458	0-39
AC178	0-29	OC20	0-36	BD219	0-77	BC154	0-31	ZN5459	0-41
AC179	0-29	OC22	0-47	BD219	0-77	BC157	0-19	ZN6122	0-19
AC180	0-20	OC23	0-49	BD219	0-77	BC158	0-12	ZN8301	0-51
AC180K	0-30	OC24	0-57	BD219	0-77	BC159	0-12	ZN8302A	0-43
AC181	0-20	OC25	0-39	BD219	0-77	BC160	0-46	ZN8302	0-43
AC181K	0-30	OC26	0-30	BD219	0-77	BC161	0-61	ZN8303	0-59
AC187	0-22	OC28	0-31	BD219	0-77	BC167	0-12	ZN8304	0-71
AC187K	0-23	OC29	0-51	BD219	0-77	BC168	0-12	ZN8305	0-80
AC188	0-22	OC25	0-43	BD219	0-77	BC169	0-12	ZN8306	0-80
AC188K	0-23	OC36	0-51	BD219	0-77	BC170	0-12	ZN8307	0-80
AC176	0-26	OC41	0-20	BD219	0-77	BC171	0-15	ZN8321	0-78
AC177	0-25	OC42	0-25	BD219	0-77	BC171	0-15	ZN8321	0-78

* 74 SERIES T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS.

Type	Quantities	Type	Quantities	Type	Quantities
	1 25 100+		1 25 100+		1 25 100+
7400	0-14 0-13 0-12	7448	£1-02 0-99 0-97	74122	1 05 0-63 0-68
7401	0-14 0-13 0-12	7450	0-14 0-13 0-12	74123	0-69 0-68 0-68
7402	0-14 0-13 0-12	7451	0-14 0-13 0-12	74141	0-79 0-78 0-77
7403	0-14 0-13 0-12	7453	0-14 0-13 0-12	74145	£1-20 £1-16 £1-11
7404	0-14 0-13 0-12	7454	0-14 0-13 0-12	74150	£1-39 £1-30 £1-22
7405	0-14 0-13 0-12	7460	0-18 0-13 0-12	74151	£1-20 £1-02 0-97 0-90
7407	0-38 0-31 0-29	7470	0-30 0-27 0-25	74153	0-83 0-88 0-88
7408	0-38 0-31 0-29	7472	0-30 0-27 0-25	74154	£1-57 £1-45 £1-44
7409	0-23 0-22 0-21	7473	0-38 0-36 0-32	74155	£1-11 £1-08 0-97
7410	0-14 0-13 0-12	7474	0-38 0-36 0-32	74156	£1-11 £1-06 £1-01
7411	0-23 0-22 0-21	7475	0-56 0-54 0-52	74157	0-93 0-88 0-81
7412	0-28 0-25 0-24	7476	0-41 0-40 0-39	74160	£1-30 £1-25 £1-22
7413	0-30 0-29 0-28	7480	0-5		

PO BOX 6 WARE HERTS

SUPER UNTESTED PAKS

Pak No.	Description	Price
1	120 Glass Sub-min. General purpose Germ. diodes	0-60
2	50 Mixed Germanium transistors AF/RF	0-60
3	75 Germanium gold bonded sub-min. like OA5, OA47	0-60
4	30 Germanium transistors like OC81, AC128	0-60
5	60 200mA sub-min. silicon diodes	0-60
6	30 Sil. Planar trans. NPN like BSY95A, 2N708	0-60
7	16 Sil. rect. TOP-HAT 750mA VLTG. RANGE up to 100	0-60
8	50 Sil. planar diodes DO-7 glass 250mA like OA200/202	0-60
9	20 Mixed voltage 1 Watt Zener Diodes	0-60
10	20 BAY50 charge storage diodes DO-7 glass	0-60
11	20 PNP Sil. planar trans. TO-5 like 2N1132, 2N2904	0-60
12	30 PNP-NPN Sil. transistors OC200 & 2S104	0-60
13	150 Mixed silicon and germanium diodes	0-60
14	20 NPN Sil. planar trans. TO-5 like 2N696, 2N697	0-60
15	10 3Amp sil. rectifiers stud type up to 1000 PIV	0-60
16	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0-60
17	8 1/2 Amp sil. rectifiers BZY213 type up to 600 PIV	0-60
18	20 Silicon NPN transistors like BC 108	0-60
19	12 1-5 Amp sil. rectifiers top hat up to 1000 PIV	0-60
20	30 AF. Germ. alloy transistors 2G300 series & OC71	0-60
21	25 MADT's like MHZ series PNP transistors	0-60
22	20 Germ. 1 Amp rectifiers QJM series up to 300 PIV	0-60
23	25 300 MHz NPN silicon transistors 2N708, BSY27	0-60
24	30 Fast switching silicon diodes like IN914 Micro-Min	0-60
25	10 1 Amp SCE's TO-5 can. up to 600 PIV CR81/25-600	£1-20*
26	25 Zener diodes 400 mW DO-7 case 3-33 volts mixed	0-60
27	15 Plastic case 1 Amp sil. rectifiers IN4000 series	0-60
28	30 Silicon PNP alloy trans. TO-5 BCY28 28302/4	0-60
29	25 Silicon planar transistors PNP TO-18 2N2906	0-60
30	20 Silicon planar NPN transistors TO-5 BFY50/51/52	0-60
31	30 Silicon alloy transistors 80-2 PNP OC200, S2322	0-60
32	20 Fast switching silicon trans. NPN 400 MHz 2N3011	0-60
33	30 P.F. Ger. PNP transistors 2N1303/5 TO-5	0-60
34	10 Dual transistors 6 lead TO-5 2N2060	0-60
35	25 Silicon trans. plastic TO-18 A.F. BC113/114	0-60
36	20 Silicon trans. plastic TO-5 BC115	0-60
37	7 3A SCR. TO66 up to 600 PIV	£1-20*
38	20 Unijunction transistors similar to T1843	0-60*
39	10 TO220A B plastic triacs 50V 6A	£1-20*
40	9 NPN Sil. power transistors like 2N3055	£1-20
41	12 NPN Sil. plastic power trans. 60W like 2N5294/5296	£1-20

Code No's mentioned above are given as a guide, to the type of device in the pak. The devices themselves are normally unmarked.

QUALITY TESTED PAKS

Pak No.	Quality Tested Paks	Price
Q 1	20 Red spot transistors PNP	0-60
Q 2	16 White spot R.F. transistors PNP	0-60
Q 3	4 OC 77 type transistors	0-60
Q 4	6 Matched transistors OC44/45/81/81D	0-60
Q 5	4 OC 75 transistors	0-60
Q 6	5 OC 72 transistors	0-60
Q 7	4 AC 128 transistors PNP high gain	0-60
Q 8	4 AC 128 transistors PNP	0-60
Q 9	7 OC 81 type transistors	0-60
Q 10	7 OC 71 type transistors	0-60
Q 11	2 AC 127/128 Complementary pairs PNP/NPN	0-60
Q 12	3 AP 116 type transistors	0-60
Q 13	3 AP 117 type transistors	0-60
Q 14	3 OC 171 H.F. type transistors	0-60
Q 15	7 2N2926 Sil. Epoxy transistors mixed colours	0-60
Q 17	5 NPN 2 x ST.141, & 3 x ST.140	0-60
Q 18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0-60
Q 19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-60
Q 20	4 OC 44 Germanium transistors A.F.	0-60
Q 21	4 AC 127 NPN Germanium transistors	0-60
Q 22	20 NKT transistors A.F. R.F. coded	0-60
Q 23	10 OA 202 Silicon diodes sub-min	0-60
Q 24	8 OA 81 diodes	0-60
Q 25	15 IN 914 Silicon diodes 75 PIV 75mA	0-60
Q 26	8 OA95 Germanium diodes sub-min-1N89	0-60
Q 27	2 10A 600 PIV Silicon rectifiers 1S425B	0-60
Q 28	2 Silicon power rectifiers BZY 13	0-60
Q 29	4 Sil. transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-60
Q 30	7 Silicon switch transistors 2N706 NPN	0-60
Q 31	6 Silicon switch transistors 2N708 NPN	0-60
Q 32	3 PNP Sil. trans. 2 x 2N1131, 1 x 2N1132	0-60
Q 33	3 Silicon NPN transistors 2N1711	0-60
Q 34	7 Sil. NPN trans. 2N2369, 500MHz (code P397)	0-60
Q 35	3 Silicon-PNP TO-5 2 x 2N2904 & 1 x 2N2095	0-60
Q 36	7 2N3646 TO-18 plastic 300 MHz NPN	0-60
Q 37	3 2N3053 NPN Silicon transistors	0-60
Q 38	5 PNP transistors 3 x 2N3703, 2 x 2N3702	0-60
Q 39	5 NPN transistors 3 x 2N3704, 2 x 2N3705	0-60
Q 40	5 NPN transistors 3 x 2N3707, 2 x 2N3708	0-60
Q 41	3 Plastic NPN TO18 2N3904	0-60
Q 43	5 BC 107 NPN transistors	0-60
Q 44	5 NPN transistors 3 x BC 108, 2 x BC 109	0-60
Q 45	3 BC 113 NPN TO-18 transistors	0-60
Q 46	3 BC 115 NPN TO-5 transistors	0-60
Q 47	4 NPN high gain transistors 2 x BC 157, 2 x BC 168	0-60
Q 48	3 BCY 70 PNP transistors TO-18	0-60
Q 49	3 NPN transistors 2 x BFY 51, 1 x BFY 52	0-60
Q 50	7 BSY 28 NPN switch transistors TO-18	0-60
Q 51	7 BSY 95A NPN transistors 300MHz	0-60
Q 52	8 BY 100 type silicon rectifiers	£1-20
Q 53	25 Sil. & Germ. trans. mixed all marked new	£1-50
Q 54	6 TIL 209 Red LED	£1-20*

MAMMOTH I.C. PAK

APPROX. 200 PIECES

Assorted full-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked—you to identify.

OUR SPECIAL PRICE £1.20p

WORLD SCOOP

JUMBO SEMICONDUCTOR PAK

Transistors—Germ. and Silicon. Rectifiers—Diodes Triacs—Thyristors—I.C.'s and Zeners. ALL NEW AND CODED

APPROX 100 PIECES

Offering the amateur a fantastic bargain PAK and an enormous saving—identification and data sheet in every pak.

ONLY £1.85p

UNTESTED LIN PAKS

Manufacturers "Fall Outs" which include Functional and part Functional Units. These are classed as "out-of-spec" from the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
ULIC709	= 10 x 709	0-60
ULIC710	= 7 x 710	0-60
ULIC741	= 7 x 741	0-60
ULIC747	= 5 x 747	0-60
ULIC748	= 7 x 748	0-60

C280 CAPACITOR PAK

Containing 75 of the C280 range of capacitors assorted in values ranging from -0.1uF to 2.2uF. Complete with identification chart.

FANTASTIC VALUE

ONLY £1-20p.

SIL. G.P. DIODES

300 mW 40 PIV (min) SUB-MIN FULLY TESTED! Ideal for Organ builders

30 for 50p, 100 for £1.50, 500 for £5, 1000 for £9.

G.P. SWITCHING TRANS

TO18 SIM. TO 2N706/8 BSY27/28/95A

All usable devices. No open and shorts. ALSO AVAILABLE IN PNP similar to 2N2906, BCY 70 20 for 50p, 50 for £1, 100 for £1.80, 500 for £5, 1000 for £14.

When ordering please state NPN or PNP

G.P. 100

30 WATT GERMANIUM TO3 METAL CASE Vceo 80V, Vceo 50V, IC 10A, Hfe 30-170 replaces the majority of Germanium power Transistors in the OC, AD NKT range.

1-24	25-99	100+
44p	41p	37p

G.P. 300

115 WATT SILICON TO3 METAL CASE

Vceo 100V, Vceo 60V, IC 15A, Hfe 20-100 suitable replacement for 2N3055, BDY11 or BDT20

1-24	25-99	100+
50p	48p	46p

INDICATORS

3015F Minitor 7 Segment Indicator £1.11p*
MAN 3M L.E.D. 7 SEGMENT DISPLAY
O.127" High Characters £1.76p*

ZENER DIODES

FULL RANGE IN STOCK

VOLTAGE RANGE 2-33V

400 mw	1-5 w	10 w*
8p	17p	30p

VOLTAGE REGULATORS

TO.3 Plastic Encapsulation

UA.7805/L129 5V

(Equiv. to MVR5V) £1-25p

UA.7812/L130 12V

(Equiv. to MVR12V) £1-25p

UA.7815/L131 15V

(Equiv. to MVR15V) £1-25p

UA.7818 18V

(Equiv. to MVR18V) £1-25p

EXCLUDE VAT

AT 25% TO ALL

*ADD 8%

NO VAT

add 20p overseas

Minimum order 75p

THYRISTORS

PIV	0-6A	0-8A	1A	3A	5A	5A	7A	10A	16A	30A
	TO18	TO92	TO5	TO66	TO66	TO64	TO48	TO48	TO48	TO48
10	0-18	0-18	—	—	—	—	—	—	—	—
20	0-15	0-18	—	—	—	—	—	—	—	—
30	0-18	0-22	—	—	—	—	—	—	—	—
50	0-22	0-28	0-20	0-25	0-36	0-36	0-48	0-51	0-54	£1-18
100	0-25	0-30	0-25	0-25	0-48	0-48	0-51	0-57	0-58	£1-43
150	0-31	0-38	—	—	—	—	—	—	—	—
200	0-38	0-44	0-25	0-30	0-50	0-50	0-57	0-62	0-62	£1-63
300	—	—	0-30	0-39	0-55	0-57	0-62	0-71	0-77	£1-79
600	—	—	0-39	0-48	0-69	0-69	0-78	0-99	0-90	—
800	—	—	0-58	0-65	0-81	0-81	0-92	£1-22	£1-39	£4-07

DIODES


Type	Price	Type	Price	Type	Price	Type	Price		
AA119	0-08	BY101	0-12	BY218	0-41	OA85	0-09		
AA120	0-08	BY105	0-18	BY217	0-38	OA90	0-07		
AA129	0-08	BY114	0-12	BY215	0-38	OA91	0-07		
AA Y30	0-09	BY124	0-12	BY219	0-28	OA95	0-07		
AA213	0-10	BY126	0-15	CG62	0A200	0-07	0A200	0-07	
BA100	0-10	BY127	0-16	(OA91Eq) 0-06	OA202	0-07	0A202	0-07	
BA116	0-21	BY128	0-16	CG61 (OA70)	SD10	0-06	SD10	0-06	
BA126	0-22	BY130	0-17	OA79) 0-07	SD19	0-06	SD19	0-06	
BA148	0-15	BY133	0-21	OA5 Short	1N34	0-07	1N34	0-07	
BA154	0-12	BY164	0-51	Leads	0-21	1N34A	0-07	1N34A	0-07
RA155	0-15	BYX38/300-43	OA10	0-14	1N914	0-06	1N914	0-06	
BA156	0-14	BYZ10	0-38	OA47	0-07	1N916	0-06	1N916	0-06
BA173	0-15	BYZ11	0-31	OA70	0-07	1N4148	0-06	1N4148	0-06
BB104	0-15	BYZ12	0-31	OA79	0-07	1S621	0-10	1S621	0-10
BY100	0-18	BYZ13	0-28	OA81	0-07	1S891	0-07	1S891	0-07

UNTESTED T.T.L. PAKS

Manufacturers "Fall Outs" which include Functional and part Functional Units. These are classed as "out-of-spec" from the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0-60	UIC72	= 8 x 7472	0-60
UIC01	= 12 x 7401	0-60	UIC73	= 8 x 7473	0-60
UIC02	= 12 x 7402	0-60	UIC74	= 8 x 7474	0-60
UIC03	= 12 x 7403	0-60	UIC75	= 8 x 7475	0-60
UIC04	= 12 x 7404	0-60	UIC76	= 8 x 7476	0-60
UIC05	= 12 x 7405	0-60	UIC80	= 5 x 7480	0-60
UIC06	= 8 x 7406	0-60	UIC81	= 5 x 7481	0-60
UIC07	= 8 x 7407	0-60	UIC82	= 5 x 7482	0-60
UIC10	= 12 x 7410	0-60	UIC83	= 5 x 7483	0-60
UIC13	= 8 x 7413	0-60	UIC86	= 5 x 7486	0-60
UIC20	= 12 x 7420	0-60	UIC90	= 5 x 7490	0-60
UIC30	= 12 x 7430	0-60	UIC91	= 5 x 7491	0-60
UIC40	= 12 x 7440	0-60	UIC92	= 5 x 7492	0-60
UIC41	= 5 x 7441	0-60	UIC93	= 5 x 7493	0-60
UIC42	= 5 x 7442	0-60	UIC94	= 5 x 7494	0-60
UIC43	= 5 x 7443	0-60	UIC95	= 5 x 7495	0-60
UIC44	= 5 x 7444	0-60	UIC96	= 5 x 7496	0-60
UIC45	= 5 x 7445	0-60	UIC98	= 5 x 7498	0-60
UIC46	= 5 x 7446	0-60	UIC99	= 8 x 7499	0-60
UIC47	= 5 x 7447	0-60	UIC100	= 8 x 7499	0-60
UIC48	= 5 x 7448	0-60	UIC121	= 5 x 74121	0-60
UIC50	= 12 x 7450	0-60	UIC141	= 5 x 74141	0-60
UIC51	= 12 x 7451	0-60	UIC151	= 5 x 74151	0-60
UIC53	= 12 x 7453	0-60	UIC154	= 5 x 74154	0-60
UIC54	= 12 x 7454	0-60	UIC193	= 5 x	

ELECTROVALUE CATALOGUE 7

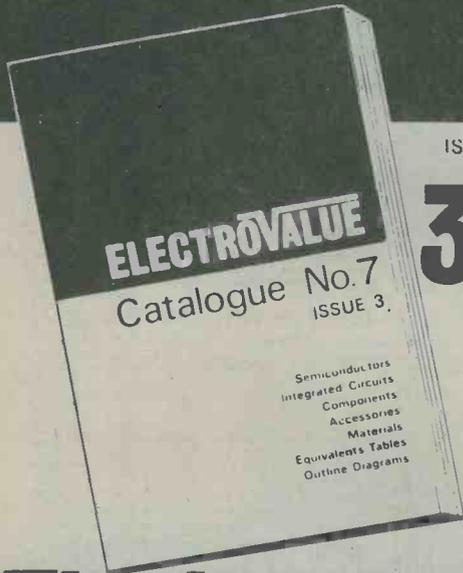

ISSUE 3

30p

including
25p Refund
Voucher

Up-dated
information
and prices.



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn – and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy – making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

No soldering – yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to read circuits – assemble components – build things – experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

Send now for **FREE** 76 page book – see how easy it is – read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

The best yet!

112 pages (plus covers) and our best yet! Practically all items in catalogue 7 are there as the result of information fed by our computer, enabling us to control stock-buying in relation to demand with greater accuracy and real benefit to customers. This means that your orders, which we microfilm for record keeping, are handled with utmost speed and efficiency. EV prices remain keenly competitive and with our new 3-month period price-stabilization policy, you can order in confidence. In addition there are discounts as well, to give you further savings.

Send 30p now for EV Catalogue 7 Issue 3. It includes a refund voucher for 25p allowable on orders for £5 or more list value.

● PRICE STABILIZATION

As from April 1st, Electrovalue prices are held for periods of 3 months without change (except in cases of violent market fluctuation) and reviewed thereafter at the end of each 3 month period instead of making day to day changes.

● DISCOUNTS

Available on all items except for a few shown at NETT PRICE

5% on orders from £5 to £14.99 list.

10% on orders £15 and over.

● WE PAY POSTAGE

and packing in U.K. (except Baxandall speaker cabinets) For mail orders for £2 list value and under, there is an additional handling charge of 10p.

● GUARANTEE OF QUALITY

All items guaranteed fully to makers' specifications. Everything brand new—no "seconds", makers' rejects or clearance offers.

ELECTROVALUE LTD

Section 6/4 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB Telephone Egham 3603 Telex 264475

All mail orders and communications to above address

● NORTHERN BRANCH

680 Burnage Lane, Manchester M19 1NA. Tel: 061-432-4945
Hours (both addresses) 9.00-5.30. Saturdays 9.00-1.00 p.m.

POST TODAY FOR FREE BOOK

To: ALDERMASTON COLLEGE
DEPT. CRE 10, READING RG7 4PF CRE 10

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721
Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS


POSTCODE




BIET

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

RADIO & ELECTRONICS CONSTRUCTOR

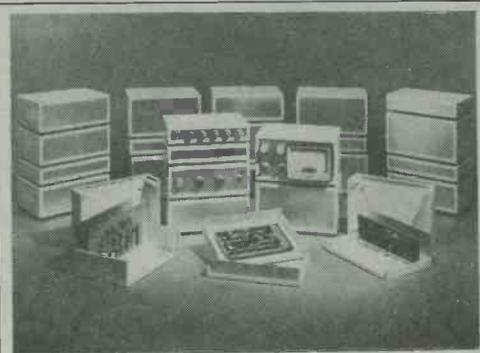


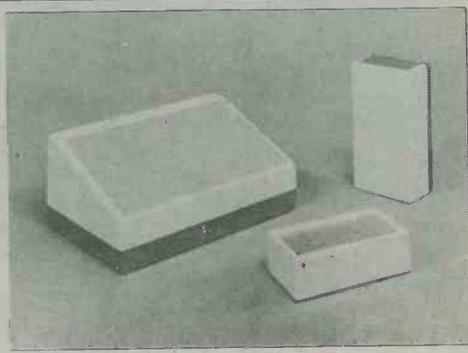A new range of plastic cases, attractively finished in light grey ABS with aluminium front and rear panels. Provision is made for both vertical and horizontal mounting of circuit boards.




These boxes have proved popular in industry, and are now available to the home constructor. High quality mouldings give projects the "professional" touch.

VERO FOR THE HOME CONSTRUCTOR

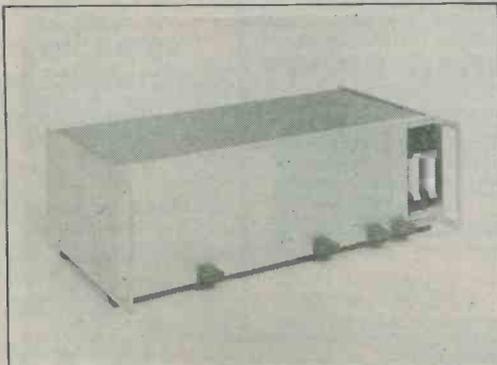

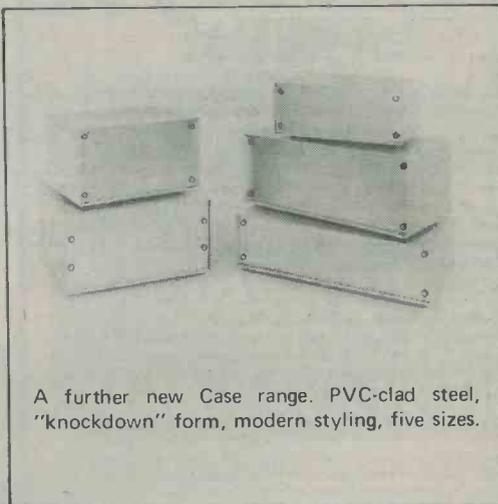For the more advanced project, this Card Frame/Case accepts plug-in modules and boards. Finished in natural anodised aluminium with light blue PVC coated covers.



A further new Case range. PVC-clad steel, "knockdown" form, modern styling, five sizes.


vero

VERO ELECTRONICS LIMITED, INDUSTRIAL ESTATE, CHANDLER'S FORD, HAMPSHIRE, SO5 3ZR
Telephone Chandler's Ford 2952 Cables Veroelec Southampton Telex 47551

RADIO & ELECTRONICS

Pricelist free with sae.
Product info folder 40p


CONSTRUCTED.

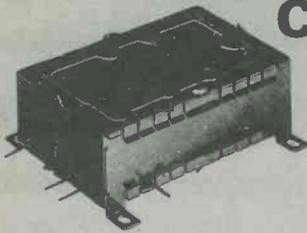

EF5600: Varicap FM tunerhead, AFC/AGC/MOSFET input. £10.00.



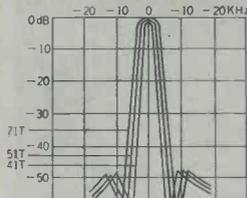
455kHz mechanical filters
£1.45 ea (4 or 7 kHz BW)



CFS
10.7MHz



ceramic FM
IF filter 40p.

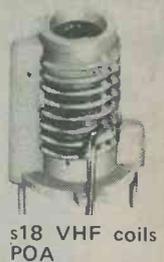

18 VHF coils
POA

Ambit is the wireless specialist. We supply tuners, tunerheads, components, modules and accessories specifically to provide a 'one stop' wireless constructor's source.

Here's a brief selection from our full range of ICs, components & modules:

AM radio system:

EC720 varicap tuned MW radio tuner with ceramic IF filter, and IC signal processing system. ... kit £8.00.

Three gang tuning diode MVAM1 : £2.75 each. 2 gang MVAM2: £1.05.

FM radio System:

Larsholt 7252 tuner. An electronically tuned 88-108 MHz receiver module. 1uV for 26dB S/N, mute, AFC, AGC, 'scan and hold', meter outputs for signal strength, tuning & frequency indication. Built and tested for £24.00.

Tuning Accessories:

WS150 150mm WW slider pot for direct scale readout. ... £3.00
9932 6 button preset pot. bank for pretuned station selection. ... £3.40
Meters (illuminated) for frequency, sig. strength, tuning. ... £2.50 each
Selection of 78 series voltage regulators for total stability, see lists.

AMBIT INTERNATIONAL 37 High Street, Brentwood, Essex.

All prices quoted exclude VAT. Postage 20p per order. Min CWO £2. Min. invoice £7.50.

Have you seen
this years most important
component catalogue yet?

**HENRY'S 1975
CATALOGUE
IS NOW AVAILABLE**



Don't buy another electronic component until you've consulted the Henry's 1975 issue! It's packed with more items than ever before - over 5000 in all, making the Henry's range of electronic components the largest in the UK for the home constructor. There are literally dozens of new lines and new ranges to get excited about! And many components are selling at reduced prices. Get your copy soon, and start reading these 200 pages of vital statistics about electronic components. If you don't, you'll miss out on a lot of kits, projects and test gear, apart from all the other products.

ONLY 50p
+20p p & p

Complete with
FREE 50p
Discount Voucher!

FREE to Educational
Establishments when ordered
on official headed notepaper.

Get your copy NOW - send remittance of 70p (cheque or P.O.)

MIDLANDS' NEW ELECTRONICS STORE
OPEN: 34/96 UPPER PARLIAMENT
STREET, NOTTINGHAM. TEL: (0602) 40403
LONDON: 231 TOTTENHAM COURT RD.
W1. LOWER SALES FLOOR)

Henry's
RADIO

ELECTRONIC FOOTBALL & TENNIS WITH THE FABULOUS VIDEO SPORT ON YOUR OWN TV

Play three exciting electronic ball games FOOTBALL, TENNIS, HOLE IN THE WALL on your own TV! Just plug Video Sport into the aerial socket of Your TV and away you go. Completely safe for you, your children and your TV. Mains operated.



OUR INCREDIBLE PRICE
£29.50 inc VAT

DEMONSTRATIONS NOW IN ALL CENTRES!

SPECIAL OFFER GARRARD CT4 STEREO CASSETTE TRANSPORT MECHANISM

Features:
★ Stereo Heads ★ Pause Control
★ Built in Motor Stabiliser ★ 12v DC Operation.
★ Auto Stop e.t.c.

Robust, precision engineered mechanism based on the "STARR" patented design. Ideal for use in Car stereo cassette players, Hi-Fi stereo cassette recorders, industrial and many other applications. Suitable for the "PW" Ascot Stereo Cassette Deck.



£13.50 incl. VAT p. & P. 35p

AM/FM MODULES LP1179 LP1171

Combined AM/FM tuner modules, together with a small number of R + C's Ferrite Aerial, make up a sensitive FM/MW/LW tuner. 6 Volts supply, supplied with data and circuit sheets.

LP1171 combined IF strip **£4.60**
LP1179 FM front end and AM gang **£4.60**
£8.62 the pair.
Suitable Ferrite aerial 87p.



ALL HENRY'S PRICES INCLUDE VAT

Electronic Centres
404-406 Electronic Component's & Equipment 01-402 8381
354 PA-Disco-Lighting High power Sound 01 402-5854
303 Special offers and bargains store
All mail to 303 Edgware Road London W2 1BW
Prices correct at time of preparation Subject to change without notice E & O E

Hi-Fr and
Electronics
Centres Open
9am - 6pm

UHF TV TUNERS

625 line receiver UHF transistorised tuners U.K. operation. Brand new. (Post packing 25p each)
TYPE A variable tuning slow motion drive **£3.50**
TYPE B 4-button push button (adjustable) **£4.60**
TYPE C variable tuning **£2.90**
TYPE D 6-button UHF/VHF tuner **£5.75**
AVO MOVEMENTS new condition **£8.50**
inc VAT

£26.25 (p. & p. 50p)
(also built and tested £31.20)

TEXAN STEREO AMPLIFIER

Features glass fibre PC board, Gardners low field transformer, 6-Cl.s. 10-transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972 Overall size 15 1/2 x 2 1/2 x 6 1/2 in. Mains operated. Free teak sleeve with every kit.



£29.95 (p. & p. 50p)
(also built and tested £39.95)

TEXAN STEREO FM TUNER

Features capacity diode tuning, LED and tuning meter indicators, mains operated. High performance and sensitivity. Overall size in teak sleeve 8 x 2 1/2 x 6 1/2 in. Complete kit with teak sleeve.

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

Bargains from our FREE Catalogue

20 large pages, filled with real bargains in transistors, I.C.s, components, equipment, etc. Send large S.A.E. with 7p stamp for your FREE copy of 6th Edition by return. Meanwhile, for prompt delivery order from this month's ad. NOW.

TRANSISTOR PACKS ALL 60p each TESTED AND GUARANTEED

- | | | | | | |
|-----|-----|---|-----|---|---|
| B79 | 4 | IN4007 Sil. Rec. diodes, 1,000PIV 1 amp. plastic | H39 | 6 | Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945 |
| B81 | 10 | Reed Switches, 1" long 1/2" dia. High-speed P.O. type | H41 | 2 | BD131/BD132 Complementary Plastic Transistors |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked | H65 | 4 | 40361 Type NPN Sil. Transistors TO-5 can comp. to H66 |
| H38 | 30 | Short lead Transistors, NPN Silicon Planar types | H66 | 4 | 40362 Type PNP Sil. Transistors TO-5 can comp. to H65 |

UNMARKED & UNTESTED

- | | | | | | |
|-----|-----|--|-----|----|---|
| B1 | 50 | Germanium Transistors PNP, AF and RF | H20 | 20 | BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts |
| B66 | 150 | Germanium Diodes Min. glass type | H34 | 15 | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202 | H67 | 10 | 3819N Channel FET's plastic case type |
| B86 | 100 | Diode Diodes sub min. IN914 and IN916 types | | | |

SILICON POWER TRANSISTORS—

Type	Gain	VCE	PLASTIC Price
40N1	15	15	20p
40N2	40	40	30p
40P1	15	15	20p
40P2	40	40	30p
90 WATT			
90N1	15	15	25p
90N2	40	40	35p
90P1	15	15	25p
90P2	40	40	35p

NEW X-HATCH GENERATOR Mk.2



Essential for Colour T.V. alignment of 4 patterns. Featuring plug in IC's and a more sensitive sync. pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—only measures 3" x 5 1/2" x 3". Operates from 3 U2 type batteries (extra).

P & P add 33p kit or complete **£7.93** Complete kit **£9.93** Ready built unit only **£9.93**

OVER 1,000,000 TRANSISTORS IN STOCK!

CAPACITOR DISCHARGE IGNITION UNITS

Transistorised. Simple to Fit. Improves performance, cuts fuel costs

P & P add 27p **£7.50**

MNFRS. AM/FM CHASSIS

To clear. No instructions or tuning drives, useful for experimenters. Not too difficult to get working. Make good portables

EACH £1

SUNDRY

Metrication Pocket Charts 12p. 8 assorted relays £1 00 (8). Rev. counter device (for cars) £1 00. U.H.F./TV Tuner Units, 625 lines, Rotary Tuning £2 50. L.M.380 Audio I.C. £1 00 and technical books of all kinds.

TERMS OF BUSINESS

V.A.T. Prices shown do NOT include V.A.T. Please add 25% to total value of your order, except for items marked with a * or (8%) for which the V.A.T. rate is 8%. No V.A.T. on overseas orders.

POSTAGE Except where stated, add 22p for postage & packing in U.K. Overseas—add £1, any difference being charged or refunded.

PAYMENT Cash with order. Cheque or money order. Minimum value—£1. You can also pay by ACCESS.

IMPORTANT—Every effort is made to ensure accuracy of prices and description at time of preparing this advertisement and going to press. Prices are subject to alteration without notice.

BI-PRE-PAK LTD

Co Reg No 8201919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.

TELEPHONE: SOUTHEND (0702) 46344.


WRITE ORDER SEPARATELY AND ATTACH COUPON IF REQUIRED

challenging values!



Stirling Sound

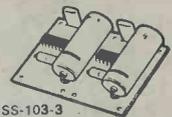STIRLING SOUND AUDIO MODULES come to you as basic units assembled on P.C.B.s enabling you to add required components in layouts of your own choice. Modules are tested and boxed before despatched and include well printed instructions.




SS-103-3

AMPLIFIER MODULES

Pre-amplifiers: tone control


- | | | |
|--------|--|--------------|
| SS.100 | Active tone control unit to provide bass, treble, balance and volume controls | £1.60 |
| SS.101 | Pre-amp for ceramic cartridge, tape and radio | £1.60 |
| SS.102 | Pre-amp for low output magnetic cartridge, tape and radio. With R.I.A.A. correction ...1dB at 1K | £2.25 |

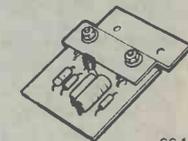

SS.105

POWER AMPLIFIERS


- | | | |
|----------|--|--------------|
| SS.103 | Compact I.C. amp. with 3 watts R.M.S. output. Operating voltage 6 to 22. Size 3 1/2" x 2" | £1.75 |
| SS.103-3 | Stereo version of above using one I.C. on each channel | £3.25 |
| SS.105 | A compact and useful all-purpose amplifier which will run excellently on a 12V supply. With 5 watt output, two make a good stereo amp. Size 2 1/2" x 1 1/2" | £2.25 |
| SS.110 | Similar in size to SS.105 but with a 10 watt output. Ideal for many domestic and small-size P.A. applications. Operates from 26 to 32V. | £2.75 |
| SS.140 | Excellently designed 40 watt R.M.S. (into 4 ohms) hi-fi amplifier. S/N ratio better than 75dB. THD better than 0.2%. Power requirements—45V. d.c. With 0-15" centre edge connections. Two can be bridged to give 80 watts R.M.S. into 4 ohms | £3.60 |

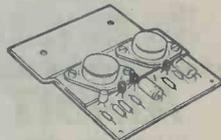

SS.140

THE MODULES TO BUILD A STEREO F.M. TUNER


- | | | |
|--------|--|--------------|
| SS.201 | Ganged tuning condenser with accurately engineered slow-motion drive in rugged housing. Excellent sensitivity. Tunes 88-108MHz. With A.F.C. facility. Operates from 6V—16V | £6.25 |
| SS.202 | I.F. stage (with I.C.) Pre-tuned. A.F.C. connection. Operates from 4-5 to 14V. | £5.25 |
| SS.203 | Stereo Decoder. Designed essentially for use with SS.201 and 2. This module can also be used in most mono FM tuners. A LED may be attached. Operating voltage 9-16V. d.c. | £5.62 |

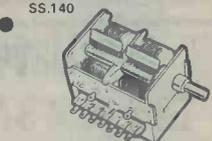

SS.201

POWER SUPPLY STABILIZER

- | | | |
|--------|--|--------------|
| SS.300 | Add this to an un stabilised supply (say typically 45V. output) to obtain a steady powerful working output adjustable from 12 to 60V. Essential for your audio and special systems. Money saving and very reliable. Ideal for workbench use. | £3.25 |
|--------|--|--------------|

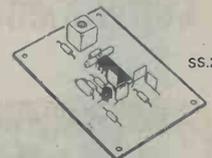

SS.202

MAINS TRANSFORMERS FOR ABOVE

- | | |
|--|------------------------------------|
| Add 38p P. & P. per transformer | |
| Type A | 18v/1A (Suit SS. 103) £1.50 |
| Type B | 25v/2A (Suit SS. 110) £2.00 |
| Type C | 30v/2A (Suit SS. 140) £3.25 |
| Bridge Rectifier Type A 27p Type B/C 38p | |




SS.203

STIRLING SOUND DISCO MINOR

Fully transportable. Console fitted twin turntables with cross fade, monitoring, L-R cueing, mic. with over ride. Ampower 40 loudspeaker has built-in mains powered 40 watt RMS power amp. Up to 10 Ampower may be added. With one Ampower and console **£100**

plus V.A.T. at 25% Carr. U.K. £3.50 (8%)

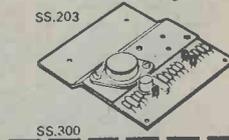

SS.300

To BI-PRE-PAK, 224-226 WEST RD., WESTCLIFF-ON-SEA, ESSEX

Please send

for which I enclose

inc. V.A.T.

Name

Address

REC 10



CHINAGLIA

PROFESSIONAL QUALITY
TEST EQUIPMENT



THE
MINOR

33 RANGES
20k Ω /V d.c.
4k Ω /V a.c.

WITH

- ROBUST CLASS 1.5 PRECISION MOVEMENT
- ACCURACY 2.5% D.C. AND 3.5% A.C.
- 12 MONTH GUARANTEE
- SELF-POWERED AND POCKET-SIZED
- OPTIONAL 30kV D.C. PROBE

PRICE £19.00 Inc. VAT (P. & P. 80p)
PROBE £9.50

For details of this and the many other exciting instruments in the Chinaglia range, including multimeters, component measuring, automotive and electronic instruments please write or telephone:

CHINAGLIA

(U.K.) LTD. 19 Mulberry Walk, London
SW3 6DZ Tel: 01-352 1897

TRADE ENQUIRIES WELCOMED

RADIO
&
ELECTRONICS
CONSTRUCTOR

NEW STYLE SELF-BINDER

for

"Radio & Electronics
Constructor"



The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.


PRICE
£1.00

including V.A.T.

P. & P. 20p

Available only from:—

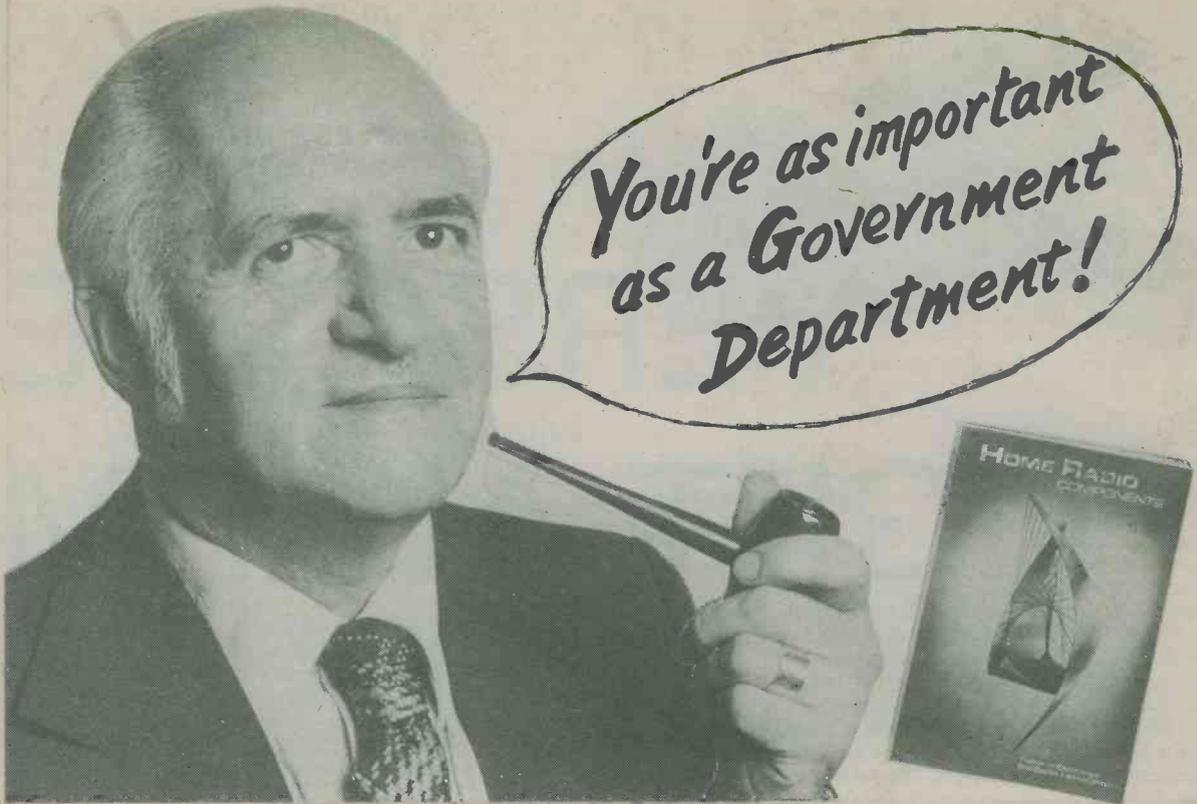Data Publications Ltd. 57 Maida Vale London W9 1SN



... at least, to Home Radio Components you are. I'm thinking of their Credit Account Service. They have of course always run accounts for supplying firms, colleges and Government Departments, but for years it was impractical to provide the same facilities for individuals. However, Home Radio Components have always looked upon their smallest customers just as important as their biggest, and after much thought and planning they devised a Deposit Credit Account matched to the needs of the small individual buyer.

The service is very convenient in many ways. For instance, thanks to their answer-phone service exclusively for the use of Credit Account customers, you can take advantage of the cheap phone rates after 6 pm week-nights and any time Saturday and Sunday. You not only save money, but you can often get your components much quicker. Briefly, the Credit Account Service works like this — you pay a deposit (you choose the amount) and you immediately get credit for double that amount. Home Radio then send you special

order forms and pre-paid envelopes, and advise you each month how much you have spent. You save quite a bit on postage costs, and having to draw only one cheque or P.O. a month makes quite a worthwhile additional saving. No wonder nearly 1000 customers are already using this service. Why not join them and save yourself money and frustration? First you will need the Home Radio Components catalogue. No constructor should be without one! For a book having 240 pages, listing about 6,000 components, illustrating nearly 2,000, the price of 85p is modest indeed. True, postage & packing adds another 33p, but every catalogue contains vouchers to the value of 70p when used against orders.

Full details of the Deposit Credit Account and an application form are included in the Catalogue. To take your first step to simpler, quicker component buying send the coupon with your cheque or P.O. for £1.18 today.

Today's finest Components
 Catalogue **85p** plus 33p POST & PACKING

POST THIS COUPON
 with cheque or P.O. for £1.18

The price of £1.18 applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME

ADDRESS

.....

.....

HOME RADIO (Components) LTD., Dept. RC
 234-240 London Road, Mitcham, Surrey CR4 3HD.

Regd. No. 912966, London

HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD. Phone: 01-648 8422



VERSATILE LIGHT ALARM

By J. R. Davies

This device turns itself on automatically at a certain light level, then produces an a.f. tone whose frequency varies with light intensity. It can be readily assembled on the piece of Veroboard which is given free with this month's issue.

In this issue we are presenting a free Veroboard for the use of readers. The Veroboard is of 0.15in. matrix and has 7 copper strips each with 16 holes. The board can be employed for quite intricate circuits and, doubtless, many readers will wish to assemble their own designs on it. For those who prefer to work to published designs, we are describing two projects in this issue which can be assembled on the Veroboard. The first of these projects appears in the present article.

The majority of constructors will nowadays have had experience in handling Veroboard, and they will be aware of the usefulness of this material. The copper strips can be cut at any hole, with the aid of a Vero spot face cutter or a twist drill of suitable size, in order to set up the particular circuit pattern required. Component lead-outs are passed through the holes in the board and can then be readily soldered to the strips. A small soldering iron of around 15 to 20 watts rating is preferred, and it is essential to use a radio-type resin-cored solder such as Ersin Multicore or Savbit. A paste or liquid flux must *never* be used, as it will leave a harmful residue.

LIGHT ALARM CIRCUIT

The circuit of the light alarm which forms the first Veroboard project appears in Fig. 1. This employs a photoconductive cell type ORP12, the resistance of which changes according to the light incident on it. In total darkness the ORP12 resistance is $10M\Omega$ or more, and when fully illuminated the resistance drops to a figure of some 75 to 300Ω . Thus, the resistance of the ORP12 decreases as the light falling on it increases.

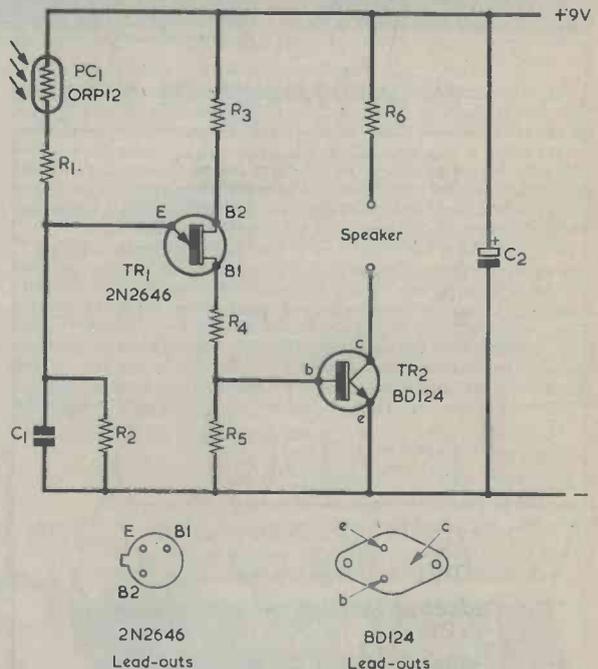



Fig. 1. The circuit of the light alarm. This produces an audible tone whose frequency varies with illumination of the ORP12. It also turns off automatically when the illumination falls below a certain level

The ORP12, in series with R1, couples to the emitter of the unijunction transistor, TR1. This acts as an audio oscillator in the following manner. Assuming for the moment that R2 is not in circuit, C1 charges via the ORP12 and R1 until the voltage on its upper plate reaches the emitter triggering level of TR1. At this level the transistor gives a negative resistance effect which causes the capacitor to discharge rapidly into R4, R5 and the base-emitter junction of TR2. After this discharge, C1 commences to charge again until the voltage across it reaches the emitter triggering level once more. Again it discharges, and then once more it starts to charge. This process repeats continuously, causing a series of pulses to be given at the base 1 of the transistor. The repetition frequency of these pulses depends on the resistance of the ORP12 and R1 and on the capacitance of C1. Both R1 and C1 are fixed, whilst the resistance of the ORP12 changes with light intensity. In consequence the pulse frequency increases as the intensity of the light incident on the ORP12 increases.

This is because the resistance of the ORP12 then decreases, and C1 charges more quickly.

Between pulses, a small standing current of about 1 to 2mA flows between the base 2 and base 1 of the transistor.

Transistor TR2 is a silicon power transistor which becomes conductive when its base is taken positive of its emitter by approximately 0.6 volt. Between the pulses from TR1, the base of TR2 is at a lower potential than 0.6 volt and so it passes no collector current. On the other hand, the pulses from TR1 take the base of TR2 up to the potential needed for the transistor to turn on, and it passes a heavy collector current when the pulses are present. If a 3Ω speaker is connected to the "Speaker" terminals, the amplified pulses from TR2 flow through it, the series resistor R6 limiting

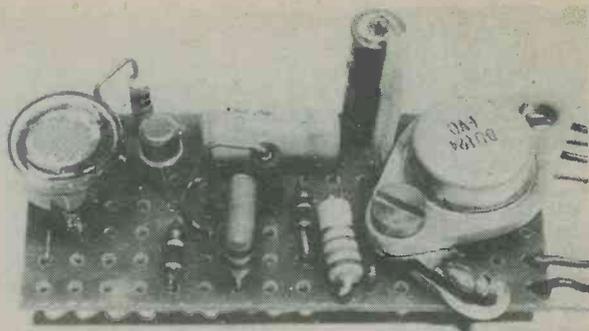

Mounting the light alarm components on the Veroboard results in a neat and functional final assembly

their amplitude to about 0.6 amp. The speaker then produces an audible tone having the same frequency as the pulses from TR1.

As has been noted, TR2 passes no current between pulses. As a result the average dissipation in this transistor is low. A power transistor is specified nevertheless, in order that the relatively high collector current pulses may be passed, but it does not need to be mounted on a heat sink. Similarly, resistor R6 is specified as a 2½ to 3 watt wire-wound component because of the high level of the current pulses it passes. As with TR2, the average dissipation in R6 is small.

Up to now, design functioning has been considered with the assumption that R2 is not in circuit. If we now take this resistor into consideration, there is an added effect on circuit operation. The ORP12, R1 and R2 form a potential divider, and if the ORP12 presents a high resistance the potential at the junction of R1 and R2 will be lower than the emitter triggering level of TR1, whereupon C1 cannot charge up to that level. In consequence TR1 does not produce any pulses and TR2 is continually turned off. If the resistance of the ORP12 is reduced (by allowing more light to fall upon it) the potential at the junction of R1 and R2 will rise above triggering level and TR1 will then commence to oscillate. Thus, below a certain level of illumination of the ORP12 the circuit is completely turned off, the only current drawn from the 9 volt supply being the 1 to 2mA standing base 2 to base 1 current in TR1 together with the much smaller current flowing through the ORP12, R1 and R2. Should the level of illumination of the ORP12 be increased, the circuit will commence to oscillate, the frequency rising with increasing light intensity.

With the component values shown, the circuit will be turned off in a fairly dark room but will at once commence to produce an audible tone if the room light is switched on or if a torch is shone on the ORP12. The circuit may, in consequence, be employed as an intruder alarm. It can also be used as a morning alarm. If positioned near a window it will cause a tone to be generated as the outside light increases at the start of the day. Other applications, mainly of a novelty nature, will readily suggest themselves to the reader.

The tone emitted by a 3Ω speaker coupled to the device is at a high volume level. If the ORP12 is illuminated by a 100 watt lamp some 8ft. away, the frequency of oscillation is of the order of 1kHz. At this

COMPONENTS

Resistors

(All ¼ watt miniature 10% unless otherwise stated)

R1 10kΩ

R2 100kΩ

R3 470Ω

R4 100Ω

R5 180Ω

R6 10Ω wire-wound, 2½ or 3 watt

Capacitors

C1 0.1μF, type C280 (Mullard)

C2 100μF electrolytic, 10V Wkg., subminiature (Mullard)

Semiconductors

TR1 2N2646

TR2 BD124

Photoconductive Cell

PC1 ORP12

Miscellaneous

Veroboard, 0.15in. matrix, 7 strips by 16 holes

3Ω speaker

9 volt battery

Battery connector clips

4BA solder tag

4BA nut and bolt

Wire, sleeving, etc.

frequency, current consumption from the 9 volt supply is approximately 18mA. The consumption reduces as frequency reduces; and it increases, to a maximum of some 23mA, when the ORP12 is highly illuminated.

The function of capacitor C2 is to ensure that a low impedance is always present across the supply rails. If this capacitor were omitted, the audible output of the circuit would reduce due to increasing internal resistance in the 9 volt supply battery as it ages. In Fig. 1, the two transistor lead-out insets show the transistors with their lead-outs pointing towards the reader. The metal case of the BD124 provides its collector connection.

CONSTRUCTION

A good idea of the general assembly can be gained from the accompanying photographs. As may be noted, both the ORP12 and TR2 are mounted by their lead-outs with their bodies above the surface of the Veroboard. The component and copper sides of the board are illustrated in Fig. 2, in which diagram the holes are given letter and number references to assist in explanation.

First, take up the Veroboard and cut the strips at holes B11, C3, D7, E3, E10 and F6. Fit and solder bare wire links between G1 and E1, and between C1 and B1. Similarly, fit and solder insulated wire links between E6 and C6, and between E11 and A11. The link between E6 and C6 should be curved slightly, to leave hole D6 clear.

Components are next fitted, each component lead-out being soldered to the appropriate copper strip after it has been inserted and the component set to its final position. Also, excessive leads projecting under the board are snipped off after soldering. Fit R2 between C5 and A5, C1 between C7 and A7, R1 between E9 and B9, R5 between D10 and A10, and R6 between G6 and F10. The four resistors are all fitted



The light alarm board, as seen from the other side

flat, i.e. their bodies are horizontal. Capacitor C1 is mounted by its side wires. Next fit R3 between G4 and F3, with its body vertical, as shown. Similarly fit R4 between D8 and D6 with its body vertical. Take a piece of thin flexible insulated wire about 1in. long and solder one end to a 4BA solder tag. Solder its other end at B12.

Take up the 2N2646 unijunction transistor, gently splay out its lead-outs and put the base 2 lead-out through F5, the emitter lead-out through E4 and the base 1 lead-out through D5. Solder these three lead-outs. Pass the two ORP12 lead-outs through E2 and C2, and position the ORP12 so that it is spaced away from the board by about 3/16 in. Solder its two lead-outs.

Prepare four thin insulated flexible wires, each about 1ft. long. These are for connection to the 9 volt battery and the speaker. Longer leads may be employed, should this be desired. Solder these wires to G16, F16, B16 and A16 respectively.

Take up the BD124, and identify its emitter and base lead-outs from the inset in Fig. 1. Using a short 4BA bolt and nut, affix the solder tag from hole B12 to the mounting hole of the transistor which is further away from the emitter and base lead-outs. Then pass the emitter lead-out through E14 and the base lead-out through D15. Position the BD124 so that it is spaced from the board by about 1/4 in. then solder its emitter and base lead-outs.

Take up C2 and pass a length of sleeving 3/16 in. long over its negative lead-out. (This lead-out is common with the capacitor can). The capacitor is mounted vertically between G11 and E12 as illustrated, with its positive lead-out at G11. First bend over the negative lead-out and then fit the capacitor. The purpose of the sleeving is to insulate its negative lead-out from the metal case of TR2.

OPERATION

The assembly of the light alarm is now complete. Make a careful check to ensure that all parts have been fitted correctly and that all solder joints are of good quality. Make certain that no two adjacent copper strips have been short-circuited together by stray "blobs" of solder.

If all is well, connect the leads from F16 and B16 to a 3Ω speaker. Connect the lead from A16 to the negative terminal of the 9 volt battery, and that from G16 to the battery positive terminal. A loud tone should at once be audible from the speaker. Pass a hand over the ORP12. The frequency of the tone should change as the light intensity on the ORP12 varies. Unless the room is very brightly lit, it should be possible to cause the oscillation to cease by cupping the hand over the ORP12 without touching it.

The light alarm is now complete and ready for use. After a little experience, the constructor will soon be able to assess the conditions of light and darkness which are required for reliable operation. ■

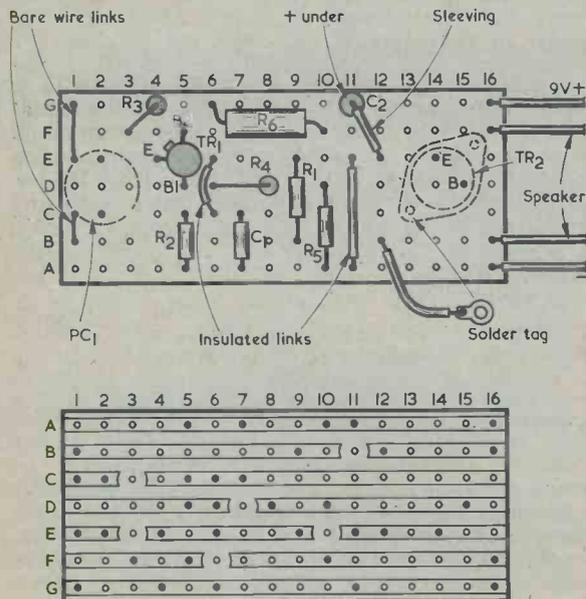


Fig. 2. The component and copper sides of the Veroboard assembly. The holes are given letter and number references to assist in describing construction

RECENT PUBLICATIONS



RADIO CONSTRUCTION FOR AMATEURS. By R. H. Warring. 128 pages, 220 x 135mm. (8½ x 5¼ in.) Published by Pitman Publishing Ltd. Price £2.00

This book is intended for the real beginner and it deals largely with simple a.m. receivers and a.f. amplifiers. After introductory chapters describing the basics of a.m. transmission and reception, and technical terms and component symbols, the book carries on to simple crystal sets. Tuned circuits are next dealt with, and further chapters are devoted to amplifiers, a.f. output stages, transistor biasing, t.r.f. receivers, regenerative and reflex receivers, and superhets. A relatively long and useful chapter discussing components follows, together with two final chapters covering circuit construction, field effect transistors and integrated circuits.

PRINCIPLES OF TRANSISTOR CIRCUITS, 6th Edition. By S. W. Amos, B.Sc., C.ENG., M.I.E.E. 328 pages, 220 x 135mm. (8½ x 5¼ in.) Published by Newnes-Butterworths. Price £3.20.

This is the 5th edition of *Principles of Transistor Circuits*, the 4th edition having appeared in 1969. The book has been kept up to date by the inclusion of more information on circuits using f.e.t.'s and the expansion of the treatment of switching circuits. Various small changes have also been made to eliminate dated information or to simplify and clarify the text.

The book starts with semiconductor physics and the basic principles of transistor operation. The main body of the book then deals in depth with transistor circuit design in amplifiers, oscillators, detectors, frequency changers, pulse and sawtooth generators, and digital applications.

Since the appearance of the first edition in 1959 the book has been adopted by many technical colleges as a standard course text. It has appeared in special editions in America and other countries, and in languages other than English. This present edition brings a work which has thus already been widely accepted fully up to the present time.

BEGINNER'S GUIDE TO COMPUTER LOGIC. By Gerald F. Stapleton. 196 pages, 220 x 135mm. (8½ x 5¼ in.) Published by Foulsham-Tab Ltd. Price £1.60.

This title comprises an American text with an introductory chapter for English readers. The book is divided into two parts, the first of which deals with the understanding of computer logic whilst the second describes logic projects which can be built by the amateur constructor.

Binary notation, logic operations, electronic logic circuits and logic applications are all dealt with in Part 1, which gives a clear and well illustrated explanation of its subject. An unusual technique is the provision in the text of 'key' paragraphs printed inside a heavy black border to draw attention, each paragraph giving a condensed summary of the concept being dealt with. This approach is useful in allowing pre-digestion of the matters being described as well as offering quick reviews when referring back to earlier points.

The projects described in Part 2 range from simple to quite complex circuits, and they are used to demonstrate specific logic operations. The first circuits to be described employ discrete components, the second employ r.t.l. integrated circuits and the third d.t.l. circuits. The projects allow a large number of experimental logic operations to be carried out including, for example, those for shift register and serial adder.

GETTING THE MOST OUT OF YOUR ELECTRONIC CALCULATOR. By William L. Hunter. 208 pages, 220 x 135mm. (8½ x 5¼ in.) Published by Foulsham-Tab Ltd. Price £1.85.

Now that pocket electronic calculators with their fantastic l.s.i. chips are becoming continually less expensive, any reliable information on their use is of value. The present volume, another book in the Foulsham-Tab list, deals with the use of calculators in an interesting and helpful manner. The book is concerned entirely with the operation of calculators and not with the functioning of the electronics inside.

Procedures for a very wide range of types of calculation are described including working with fractions, sales tax problems and conversion of metric to U.S. standards. The final chapter deals with American income tax calculations and has an academic interest only for the English reader.

The book is written in a comfortable style and offers an easy read, especially for those who are interested in numbers and problems with numbers.

The 'Tantaliser' — an electronic game

By G. A. French

Electronic games can offer quite a good deal of amusement, particularly where a contender has to exercise skill in winning. The game to be described in this month's "Suggested Circuit" falls into this category, and it presents simple operating rules without any element of chance.

On the front panel of the case housing the game circuitry are an on-off toggle switch, a push-button, a light-emitting diode and a meter. After the unit has been switched on the l.e.d. commences to become illuminated at regular intervals. If the push-button is pressed when the l.e.d. is extinguished a capacitor inside the unit starts to charge and the needle of the meter, which monitors the voltage across the capacitor, moves at a readily visible rate from zero towards the full-scale deflection end of its scale. Should the button be released, the meter needle remains at the position it held at the instant of release. If, however, the button is pressed when the l.e.d. is alight the capacitor discharges at a markedly higher rate than that at which it previously charged. The object of the game is to take the meter needle up to or beyond f.s.d. as quickly as possible, i.e. for the lowest number of flashes in the light-emitting diode.

This calls for two qualities on the part of the contender. If he is to charge the capacitor rapidly he must have a quick reaction time so that he presses the button as soon as possible after the l.e.d. has extinguished. The second quality is a good sense of timing, allowing the button to be released just before the l.e.d. becomes illuminated again. With a good sense of timing the contender can cause the capacitor to acquire a high level of charge during each period that the l.e.d. is extinguished. But if at any time he releases the button just fractionally too late the l.e.d. will light up whilst the button is pressed, the capacitor will discharge at a rapid rate, and the contender will have lost much of the ground he has so far achieved.

This is one of the tantalising elements which give rise to the title of the game. A second tantalising feature is that the movement of the needle towards f.s.d. is slower as the f.s.d. level is approached. Needle movement is still readily perceptible but its reduced speed makes the f.s.d. point tantalisingly more difficult to achieve. When f.s.d. has been reached, the meter needle will remain in this position provided the push-button is not inadvertently pressed again while the l.e.d. is alight. Switching the unit off and then on again discharges the capacitor and allows another game to commence. The meter sensitivity can be pre-set to vary the possible time in which f.s.d. can be reached. What is probably the most attractive adjustment is one which allows a reasonably skilled operator to obtain the f.s.d. reading after pressing the button about 10 times, but this figure is not mandatory and the circuit can be set up for successful completion at any number of button closures from about 6 to 14.

THE CIRCUIT

The circuit employed in the game appears in Fig. 1. The first point to observe is that transistor TR2 and zener diode ZD1 allow a stabilized voltage of about 9 volts to be available for the remainder of the components.

IC1 is a 555 timer, and it is connected up in a standard astable multivibrator circuit. The timer output is given at pin 3 and this output is high when C1 charges via R1 and R2, and is low when C1 discharges via R2 on its own. Thus, during the cycle, the time when the output is high is longer than that when it is low. The output connects via current limiting resistor R3 to the light-emitting diode LED1. This is extinguished when the timer output is high, and lights up when the timer output is low.

The output of IC1 also connects to the push-button S1, the contacts of which close when it is pressed. The

capacitor which becomes successively more and more charged as the game proceeds is C2. If S1 is pressed when the timer output is high, a charging current flows into C2 via R4, with diode D1 being reverse-biased. If, on the other hand, the button is pressed when the timer output is low, diode D1 becomes conductive and provides a rapid discharge path, in parallel with R4, via R5. For D1 to conduct, the capacitor has to have a voltage across its plates which exceeds the 0.6 volt forward voltage drop across D1 plus the small voltage at the timer output in the low condition, but in practice C2 very soon acquires this potential.

The situation as so far described can now be summed up. When the timer output is high the l.e.d. is extinguished. If S1 is pressed, a charging current flows into C2 via R4. When the timer output is low the l.e.d. is illuminated, and closure of S1 contacts causes C2 to be rapidly discharged via D1 and R5. This meets the basic game requirements described at the start of the article. It has also been shown that, during the cycle, the l.e.d. is alight for a shorter period than that during which it is extinguished. This factor is psychologically attractive, since the charge ("good") condition is longer than the discharge ("bad") condition.

The voltage across the capacitor is monitored by the voltmeter given by TR1, R6, R7 and meter M1. TR1 functions as an emitter follower and its base presents a very high resistance to C2. If this capacitor is a good quality modern component with a low leakage current it should be found that the voltage across it remains constant, or very nearly constant, for a long period after S1 has opened. Thus, the meter reading remains unaltered, or at worst substantially unaltered, after S1 has been released. The capacitor employed by the author in the prototype circuit was a Mullard type C437, and there was no significant shift in voltmeter reading after the button had been released. The voltage across the

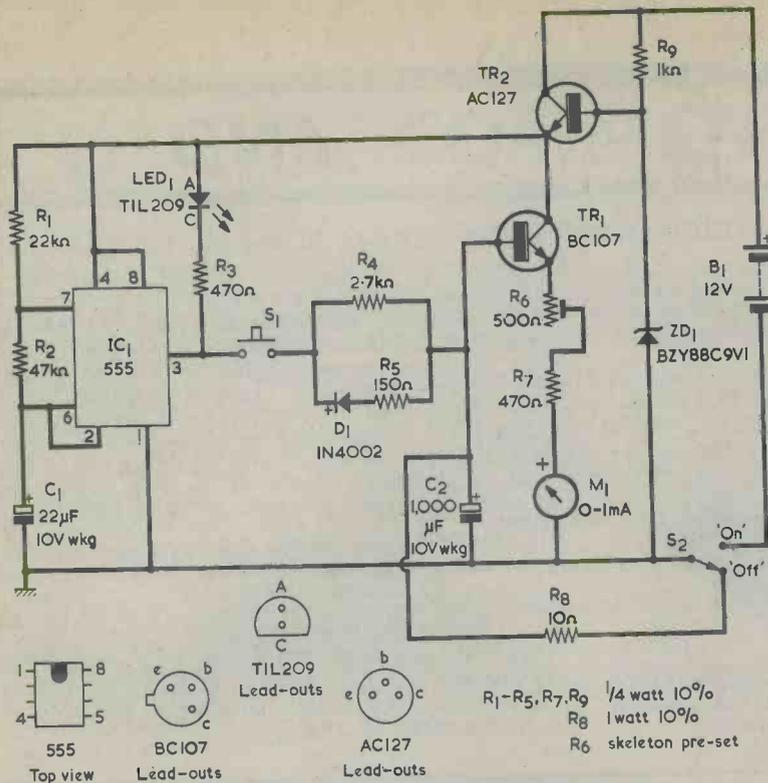


Fig. 1. The circuit of the "Tantalsør". The aim is to press S1 during the periods when LED1 is extinguished and thus charge capacitor C2 in the shortest period of time

capacitor at which meter M1 gives an f.s.d. reading should be of the order of 7 volts. A precise voltage cannot be specified here because of tolerances in the circuit, including tolerance on voltage in ZD1, and the degree of difficulty it is desired to impart to the game. For these reasons the pre-set variable resistor, R6, is included in series with the meter. It is an easy matter to set up R6, and the process is described later.

Due to the forward base-emitter voltage drop of about 0.6 volt in TR1, the meter does not give an indication until the voltage across C2 rises above this figure. This voltage delay matches the forward voltage drop of 0.6 volt in D1 which was just mentioned. Initial closure of S1 with the l.e.d. extinguished takes C2 quickly above the 0.6 volt level, after which the meter reads approximately zero when the capacitor is discharged to the lowest level of which the circuit is capable.

EXPONENTIAL CURVE

The rate of charge in C2 decreases as the voltage across its plates rises. This is to be expected as the capacitor charge follows the familiar exponential curve shown in Fig. 2, which represents charge time against voltage for a capacitor charging from a fixed direct voltage via a resistor. With the present circuit, the effect is that the

voltage across the capacitor increases more slowly when S1 is pressed than when the l.e.d. extinguished as the meter needle approaches full-scale deflection.

When switch S2 is in the "On" position it causes the negative terminal of the battery to be connected to the lower supply rail, and the unit is thus switched on. When S2 is set to "Off" it disconnects the battery and connects R8 across C2, thereby rapidly discharging C2. R8 is a current limiting resistor whose function is to prevent current surges at the switch contacts. S2 is a standard s.p.d.t. toggle switch.

The voltage stabilizing circuit given by ZD1, TR2 and R9 follows conventional practice. ZD1 is taken up to its zener voltage by way of the current flowing through R9, and TR2 acts as an emitter follower through which most of the current required by the remainder of the circuit flows. R9 can have a relatively high value as the zener diode specified goes into zener conduction at a very low current level, and the current drawn by TR2 base is extremely small. TR2 is a germanium rather than a silicon transistor since a germanium transistor has a lower base-emitter voltage drop and thereby allows a slightly higher voltage to be made available for the rest of the circuit. This advantage is admittedly of a very marginal nature, but since the transistor specified for TR2 is in the general range of low cost transistors its

use can be justified. The circuit offers an acceptable level of stabilization for battery voltages down to some 10.5 volts.

The battery can consist of two 6 volt batteries in series or any other combination which produces a total of 12 volts. The current drawn from the battery varies according to the state of IC1 and whether or not S1 is pressed. The average consumption is of the order of 12mA.

The length of the period when the timer output is low and the l.e.d. is illuminated is approximately equal (in seconds) to 0.7 times the product of R2 and C1 (in megohms and microfarads. This works out at about 0.7 second. The period during which the timer output is high is approximately equal to 0.7 times C1 multiplied by the sum of R1 and R2, and this is about 1 second. These periods appear, subjectively, to offer a good choice for operation of the game. The period lengths will vary slightly, in different versions of the circuit, because of tolerances on value in R1, R2 and C1.

When the unit has been assembled and checked out, R6 may be set to insert maximum resistance and a little practice obtained in operating S1. It will be found that the first period of non-illumination in the l.e.d., given immediately after switching on, is longer than the subsequent periods, and this enables C2 to be given an encouragingly high initial charge. S1 can, indeed, be held closed when S2 is set to the "On" position.


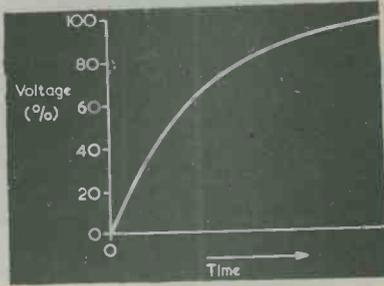


Fig. 2. Exponential capacitor charging curve showing that the rate of charge of a capacitor connected to a fixed voltage via a resistor decreases as the voltage across the capacitor increases. This last voltage is indicated as a percentage of the fixed voltage

A decision is next made concerning the number of closures in S1 which represent the target figure for the game. If the number chosen is 10, which in the writer's opinion is the best choice, one or more runs are attempted to produce as high a meter reading as is possible after this number of switch closures. On completion of a satisfactory run, S1 is left open and R6 adjusted for f.s.d. in the meter. The game is then set up and ready for use.

NEWS . . . AND

HEATHKIT CODE PRACTICE OSCILLATOR KIT

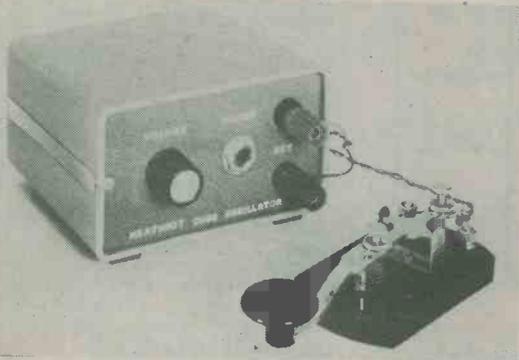

The Heathkit HD-1416 Code Practise Oscillator is as much fun to build as it is to use — and it also makes a great starter kit for a beginning CW operator.

Safe, portable, and reliable. The HD-1416 is designed in the Heath tradition of top quality and value. Most components mount on a single circuit board for easy assembly. The unit operates from a single inexpensive 9-volt transistor battery (not supplied) and is complete with telegraph key and phone jack. The oscillator, with built-in speaker, has a separate control for volume on the front panel — as well as a tone control accessible from the back of the cabinet.

The HD-1416 can also be used as a side tone oscillator with any transmitter using grid block keying — such as the Heathkit DX-60B.

Kit K/HD-1416, £7.00 including 8% VAT and delivery within the United Kingdom.

Free Catalogue with full details of the new HD-1416 and the complete range of Heathkit Electronic Kits, available from: Heath (Gloucester) Ltd., Bristol Road, Gloucester GL2 6EE.

NEW RADIO SHOW FOR BIRMINGHAM EXHIBITION CENTRE

— SOUND & VISION '76

Sound & Vision '76 will be the title of next year's TV and audio show to be held at the National Exhibition Centre, Birmingham (May 28th to 31st).

The show follows on from HEDA — the first International Home Electronics and Domestic Appliances Exhibition — a five day trade show sponsored by the Association of Manufacturers of Domestic Electrical Appliances (AMDEA) and the British Radio Equipment Manufacturers' Association (BREMA) which opens on May 23rd.

With the exception of the first day of the public

show, when the doors will open at noon, the TV and audio show will be open from 10 am to 10 pm daily including the Spring Bank Holiday Monday.

The HEDA trade show, which opens from 10 am to 7 pm, features for the first time the entire range of domestic electrical appliances, TV and audio under one roof.

Bookings have already topped the 13,000 square metres mark and the domestic appliances show has exceeded by 1,500 square metres the Electric Living Fair it replaces.

COMBINATION GRINDER AND POLISHER

This new top quality machine is attractively styled, very robustly constructed and designed to give long, trouble free service. It is particularly suitable for production and "Do it Yourself" Workshop use. Powered by a $\frac{1}{2}$ H.P. single or three phase motor with condenser starting. Fitted with 8" x $\frac{3}{4}$ " grinding wheel and a 6" polishing mop. Controlled by safety pull/push on/off switch. Approximate overall size: length 21", height 11", width 6". Weight approximately 67 lbs. Finish Grey Enamel. Supplied complete with fixing bolts and delivered in a strong wooden crate.

Price £55 plus £3.50 packing and carriage plus VAT. Supplied on 14 days satisfaction money refund guarantee.

Details from Hadley Sales Services, 112 Gilbert Road, Smethwick, Warley, West Midlands B66 4PZ.



COMMENT

CEEFAX AT SCIENCE MUSEUM

The BBC's CEEFAX system is on view at the Science Museum until November, CEEFAX is the BBC's dial-a-page information; at the touch of a button the viewer can switch from the conventional programme to any of a wide range of written pages of news, sport, travel, weather and numerous other subjects.

CEEFAX receivers provide all that a conventional television set does but in addition they have a decoder which picks out coded CEEFAX pulses "hidden" on a few spare lines of the television picture and converts them into the words and figures on the screen.

Concurrently with the development of CEEFAX, the IBA has developed a similar system called ORACLE.

CEEFAX is carried on the 625-line uhf service of BBC-1, and is available in most parts of the United Kingdom.

At present, CEEFAX carries 50 pages of news and information but gradually the service will expand.

So at the Science Museum you can see a service that could in a few years' time be commonplace in our homes.

The CEEFAX exhibit will be in the Radio Room on the 3rd Floor. It will be shown at all times except when the Museum's Radio Station is being demonstrated (i.e. 11.30 and 16.00 Monday to Friday and most Sunday afternoons).

NEW BOARD APPOINTMENT



Mr. Chable newly appointed Director of Doram Electronics Ltd.

Ron Marler, Chairman of Electrocomponents, Britain's biggest electronic component distribution Group has announced the appointment of Frank Chable to the Board of their mail-order component distribution subsidiary Doram Electronics Ltd, of Wellington Road Industrial Estate, Leeds.

Mr. Chable has had a long association with the Electrocomponents Group. He joined RS Components Ltd., in 1966, having spent twelve years as a Radio Communications Instructor with the Royal Air Force.

In June 1974, he was, together with Ron Marler and Don Turner, both of whom are Main Board Directors, instrumental in the launch of Doram and subsequently became General Manager of the Company.

IN BRIEF

■ West Midlands Readers will be interested to learn that Henry's Radio have opened an electronic components store at 94/96 Upper Parliament Street, Nottingham.

Stocks of their full catalogue range of components and equipment are maintained.

■ The British Amateur Electronics Club report that their tenth Exhibition, held at Penarth, Glamorgan, was again a great success and a record donation of nearly £550 was made to the Cancer Research Campaign.

Details of membership of B.A.E.C. may be obtained from J. G. Margetts, 11 Hazelbury Drive, Warmley, Bristol.

■ Amateur Radio Classes are being held at:- Glasgow College of Nautical Studies, 2 Thistle Street, Glasgow, C.5. Tuesdays and Thursdays from 7.00 pm to 9.30 pm. Gosforth Secondary School, Gosforth, Newcastle-upon-Tyne, Tuesdays from 7.00 pm to 9.00 pm. Candidates may sit the R.A.E. at the school.

■ 2 short courses of lectures are to be held at South London College, Knight's Hill, London, SE27 0TX.

1. Electronic Calculators. Tuesday evenings commencing 7th October.
2. Integrated Circuits. Thursday evenings commencing 9th October.

PRE-PUBLICATION OFFER

We are informed that publication of *Linear I.C. Circuit Applications* by G. Clayton has been postponed to mid-November.

We regret any inconvenience caused to readers by the delay. However it does mean that we can extend the offer until 31st October — see our advertisement pages.



"Drat that swarf!"

Ten tips with insulating tape

By K. Harker

The humble reel of plastic insulating tape can be put to a surprising number of useful applications.

There are a number of minor problems which are liable to confront the constructor and which can be solved by using ordinary plastic insulating tape. This is not to claim that insulating tape is an electronic cure-all, but it does lend itself to many versatile applications.

Let's begin with its electrical insulating uses. This may sound as self-evident as saying a resistor resists; but simple precautions can be all too easily overlooked in the absorption of trouble-shooting and setting-up procedures.

1: INSULATING WIRES

Wrapping insulating tape round bare wire seems as easy as losing an 8BA washer; but let's remind ourselves of the whens and wheres.

When fault-finding around a chassis the ends of some leads may have to be disconnected. It is safer to insulate an unsoldered end than to leave it dangling bare where it might short-circuit against metalwork and wreck a few components. Remember, too, that the wire may make accidental contact with you, and this is not a pleasant way of driving home the insulation moral if high voltages are involved.

The same applies to fitting in temporary leads as, for example, when connecting a milliammeter in circuit. Whether you solder the leads, twist the ends or use crocodile clips will depend mainly on how long the check will take and whether the connections are likely to be disturbed. But nothing is lost by adding a turn or two of tape. It is so easy to forget temporary connections, dangling somewhere in mid-air, when you are concentrating on meter readings.

Furthermore, a wire linked at both ends — as opposed to a free-hanging wire with one end detached — is probably more easily prone to accidental tugging. And even a temporary wrap-round of tape might be abraded if it chafes on, say, the sharp corner of a transformer tag, giving dire results. So make sure the insulation you add is thick enough to be suitable

wherever it happens to be. Preferably, rearrange the leads so that any joints hang well clear of trouble spots. Also, of course, extra turns of tape will themselves strengthen a joint, particularly if this is a twisted-wire type.

What counts is a cautious approach with two points in mind: protection of components and your own and other people's safety.

2: INSULATING SURFACES

In effect, insulating surfaces is the same as insulating wires, except that it is sometimes more convenient to stick tape to, say, a metal chassis than around component wires. Strips of tape can be affixed to the underside of a metal equipment case lid wherever there is a risk of components touching it when the lid is fastened home. A further instance occurs in the screening can of a tuning coil, as in Fig. 1,

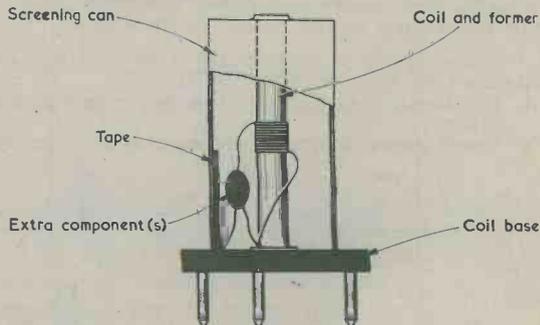


Fig. 1. When extra components are crowded inside a coil can, cover the adjacent internal surface with tape.

where resistors or capacitors which are also included in the can leave little space for individual insulation.

If you've just soldered in extra components dangerously close to the metalwork of a chassis, you'll have to poke a strip of insulating tape in with the components already in position. Tweezers or fine-nosed pliers can help to initially locate the strip. Once you've got a corner anchored, the flat of a broad-bladed screwdriver is useful for pressing the strip down on to the surface.

3: COLOUR CODING

Wrap a turn of tape round a wire (even though this is already insulated) for easy identification. For greatest benefit you'll need tapes of several colours. There are plenty of colours available.

This procedure can help if you ever find yourself using plain twisted 2-way flex with a meter. First check the leads for continuity, then mark both ends of one. Or for polarity identification you can mark both leads. An obvious combination is red positive and black negative or, should you wish to be in keeping with the revised mains lead coding, brown and blue respectively for "live" and "neutral".

If you are proposing to wire up a chassis which is complex enough to require several different colours of insulated wire for lead-tracing purposes, you can aid matters by colour coding the ends with a wrap-round of tape which is a different colour from the wire insulation. Thus, with five wire insulation colours and five colours of tape you have twenty possible combinations of different colours, as a glance at Fig. 2 will show. There are also five combinations of the same colour. In these cases, there is probably little point in adding the tape, since the wire insulation alone serves the same identification purpose. The same-colour combinations are represented by the diagonal of squares from top left to bottom right.

If you rough out such a table, you can put crosses in the squares as you proceed with the wiring up. These will guide you on which colour combinations you have already used.

		Insulating tape colour				
		red	orange	yellow	green	blue
Wire insulation colour	red		X	X	X	X
	orange	X		X	X	X
	yellow	X	X		X	X
	green	X	X	X		X
	blue	X	X	X	X	

Fig. 2. Table showing combinations of different colours (the crossed squares) obtainable with five basic colours of tape and wire insulation

4: LABELLING

Sometimes you might want to label wires for improved identification. For instance, when there are linking wires between two separate chassis, A and B, you can mark the wire ends to correspond with point numbers on the circuit diagram. Labels can be quickly made with a single wrap-round of tape, pressing the two ends together to form a writing surface about 1/4 in. square. Use a ballpoint pen of different colour from the tape to write on the connecting point numbers, such as, say, "A6 to B9". See Fig. 3. The other end of the lead would carry a label marked "B9 to A6". Write on both sides of the labels for easy viewing. You could be glad of these labels in later fault-finding if you have to detach wires and then solder them back in the right places.

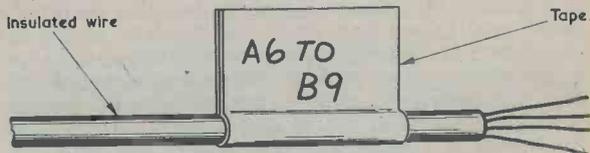


Fig. 3. Tape showing connecting points can be used to label a wire link

Components which need adjustment during setting-up procedures can be identified with small cut-out squares of similarly marked tape. With coils, such as "L2" if an i.f. strip, the label can be stuck to one side of the screening can. With pre-set variable resistors on printed circuit boards, labels are more conveniently stuck to an adjacent part of the board. As many such components are probably out of sight except during adjustment, neat hand-written labels serve adequately.

5: AIDING CONSTRUCTION

Occasionally, in assembly work, the positioning of nuts and bolts with the fingers becomes an impossibility; but you may be able to use insulating tape to anchor a nut over the appropriate hole in, say, a component baseplate before the plate is placed in its final awkward corner. As the bolt is screwed through it pushes the tape free of the nut. As is shown in Fig. 4(a), it helps if one end of the tape was originally

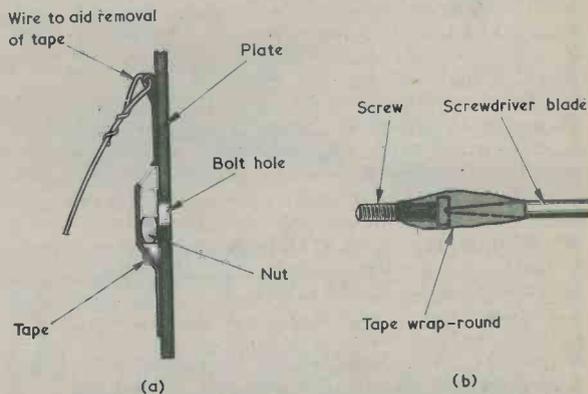


Fig. 4(a). Positioning a nut in an "awkward" place (b). How a screw may be temporarily secured to a screwdriver

wrapped round a length of spare wire. The tape can then be fished out of the difficult position by means of this "fishing-line."

Tightening the nut is another story but, if you can't get a spanner in, any long thin gadget pressed up against a side of the nut will usually hold it while the bolt is turned with a screwdriver.

The counterpart to this is fitting a screw through an inaccessible hole. A turn or two of tape can serve here to temporarily attach the screw to a suitably long screwdriver, with the blade already fitted into the screw head slot. Fig. 4(b) illustrates the idea. It is then a simple matter to push the screw through the hole and rotate it.

6: ANCHORING LEADS

You can often guard against the dangling leads snag mentioned in the first tip by temporarily taping insulated wires to an adjacent surface. The same applies when holding wires aside to give access for test prods, etc. You can also make more permanent fixtures where several wires run alongside each other by binding them in a group with tape at, say, 6in. intervals. Again, several wrap-rounds can help to fill up free space in any cleat or grommet through which the bundle runs, thereby holding it more securely.

In the more delicate task of coil winding, fine strips of tape can temporarily attach an enamel covered wire to the coil former before the bared end of the wire is permanently soldered into the base. After winding, the other end of the wire can be similarly anchored before snipping off the excess. A third strip laid along the coil can further help in fixing the coil turns. See Fig. 5. You can leave all such strips in position, even if you also intend to daub the turns with polystyrene cement to finally secure them.

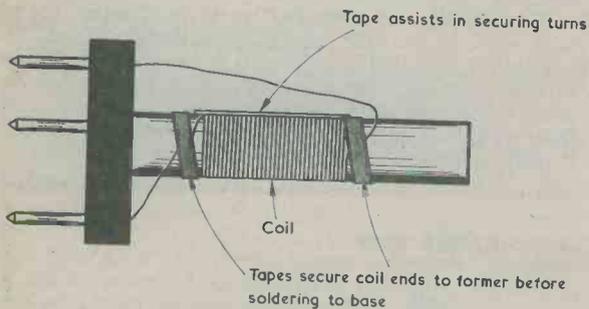


Fig. 5. Tape is a useful accessory in coil winding

7: GUIDING COIL TURNS

If you are winding a multi-layer coil and wish to contain the turns over a short length of the former you can build up two "bobbin ends" by first winding on two thin longish strips of insulating tape, as in Fig. 6. You will probably need quite a few turns in each to give sufficient depth to the coil zone in between. It may then be necessary to nick a slot or two in the tape nearer the coil former base to allow the coil ends to be led directly down to their tags.

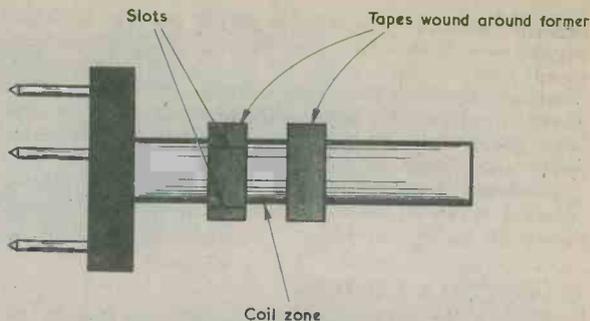


Fig. 6. "Bobbin ends" can be built up with tape to contain a multi-layer coil over a short length of former

8: INDICATING CONTROL SETTINGS

Should you be using a potentiometer without an indicator knob, and with no flat or screwdriver slot on the shaft, it is anybody's guess how far round you have set the wiper. A thin strip of tape can serve as a marker here.

With the three tags nearest you and the potentiometer set fully anticlockwise, attach the tape strip down the side of the shaft alongside the left hand tag. The strip should continue over the spindle end, as shown in Fig. 7(a). This continuation of the strip

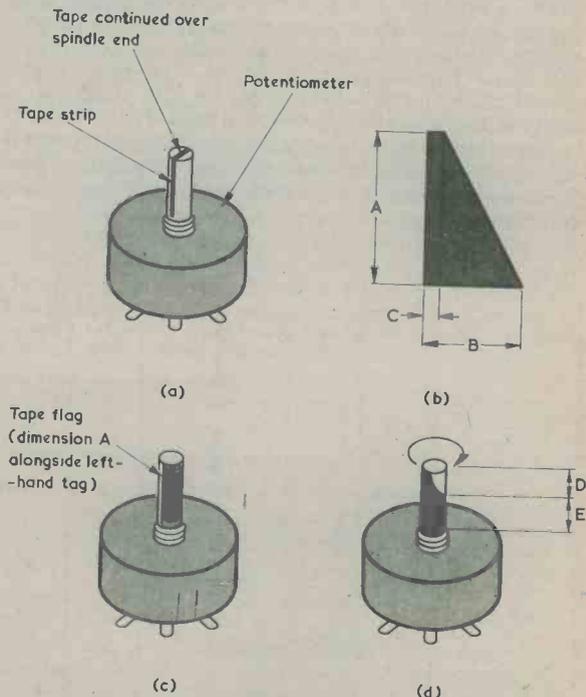


Fig. 7(a). Fixing a thin strip of tape to a potentiometer shaft to provide a marker (b). Alternatively, a "flag" of tape can be cut out, as here (c). The "flag" is wrapped around the potentiometer shaft (d). The ratio of D to E indicates amount of shaft rotation

provides a useful way of keeping it in view, to indicate wiper angle, when the rest of the strip becomes hidden round the back of the shaft.

An alternative way, possibly best used on shorter shafts, is to cut the tape to form a "flag", as in Fig. 7(b). Make dimension A the same as the length of the shaft, and B the same as the circumference. For $\frac{1}{4}$ in. shafts, B will be about 0.8 in. Dimension C should correspond roughly to the portion of circumference lying between the end stops, perhaps to about 40°. This makes C about 0.1 in. The dimension B minus C (0.7 in.) then corresponds to the approximate angle through which the potentiometer shaft can turn.

Again, with the tags nearest you and the wiper set fully anticlockwise, stick the flag to the shaft with its left hand edge alongside the left hand tag, as illustrated in Fig. 7(c). The tapering edge will thus be wrapped around the back. On adjusting the potentiometer the proportion of "exposed" shaft opposite the right hand tag, viewed directly from the front, will indicate the approximate proportion of full travel from the anticlockwise end. See Fig. 7(d). This is given as the ratio D to E of the dimensions shown.

9: MARKING A TUNING TOOL

Tape offers a similar aid when adjusting iron-dust or ferrite cores in higher frequency coils. In television i.f. alignment work, for example, a fraction of a turn can be critical; so it's of advantage to know how far you have turned a tuning slug in case you want to return it to its original position. You can't very well do this by noting the position of the slot in the end of the core if you want to keep the tuning tool in position!

All you need to indicate the angle which has been turned through is a thin strip of tape attached along one side on the tuning tool. Should this be a home made tool such as a cut-down plastic knitting needle with one end reshaped like a screwdriver blade, file a 1 in. length at the other end to a square cross-section. Then stick the tape along one of the flats, as in Fig. 8. The square shape helps you to "feel" the position in quarter-turns, a very useful feature if you are watching a meter or television test card.

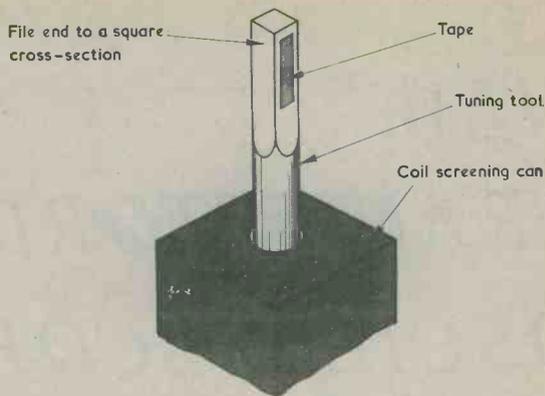


Fig. 8. Mark one side of a trimming tool with tape as a guide to fine adjustment of coil cores

The strip of tape gives visual confirmation of the number of quarter-turns made.

A commercially made trimming tool with a hexagonal end can have the square cross-section filed out on the wider part of its body.

10: SEALING OFF ADJUSTMENTS

Finally, if you are lining up a chassis which has a number of coils, each to be adjusted at a specified frequency, it's as well to know which ones you've already set up (or should not even touch at all). To make sure you don't accidentally tamper with them again the simple answer is to stick a square of insulating tape over the access-hole at the top of the screening can.

This may sound a negative sort of tip, but it's a good way of ensuring positive results in getting your tuning problems taped. ■

CAN ANYONE HELP?

Requests for information are inserted in this feature free of charge, subject to space being available. Users of this service undertake to acknowledge all letters, etc., received and to reimburse all reasonable expenses incurred by correspondents. Circuits, manuals, service sheets, etc., lent by readers must be returned in good condition within a reasonable period of time.

Codar CR45 - J. Edmundson, 60 Lime Tree Place, Stowmarket, P14 1BT - Instruction Book and Circuit Diagram - Borrow or purchase.


"Air Machines" by Wiston Reynolds - H. H. Seymour 74 Harold Estate, Pages Walk, London, SE1 4HW - Borrow or purchase.

Lafayette Model HE30 - J. Morgan, 43 September Road, Anfield, Liverpool 6 - Circuit and Servicing information required.

Radio Constructor and Radio Amateur - J. H. Luxton, Bergheim; Battery Hill, Fairlight Cove, Hastings, Sussex - Early 1950 issues of "Constructor" and issues before 1950 of "Amateur" wanted.

NEW TRANSISTORISED OSCILLOSCOPE

Part 2 By R. A. Penfold

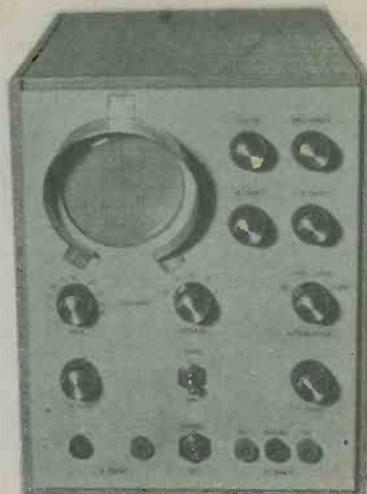

In last month's issue, details were given of metal-work and the power supply section of the oscilloscope. Most of the constructional work is described this month, including the assembly of the X and Y amplifiers, and the timebase and sync amplifier. The flyback blanking amplifier and other final points will be dealt with in next month's concluding article.

In the first part of this series, published last month, the overall functioning of the oscilloscope was described. Also given were constructional details of the power supply section, together with the full Components List.

We now proceed to the display section.

DISPLAY SECTION

Fig. 8 gives the circuit diagram of the display section. This is quite conventional, but has been modified slightly from the earlier design, mentioned last month, to use fewer components.

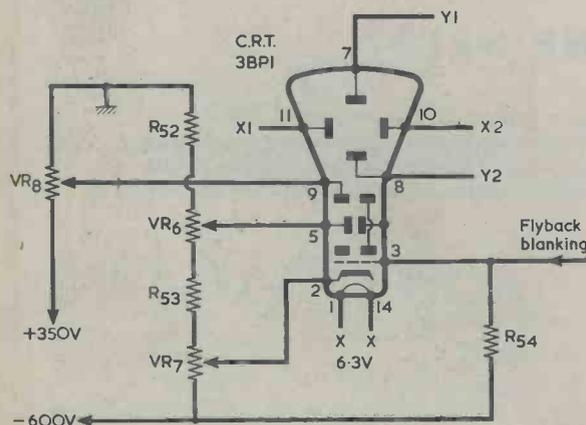


Fig. 8. The circuit of the display section of the oscilloscope

The astigmatism control, VR8, is required to ensure that the beam spot remains correctly focused at all parts of the screen. It is now powered from a 350 volt supply instead of the 124 volt supply, as in the previous oscilloscope, to give increased control.

A point to point wiring system is used in the assembly of the display section. There is no internal connection to pin 6 of the tube, and so R54 can conveniently be connected between pins 3 and 6 on the c.r.t. holder. VR8 is mounted on the rear c.r.t. bracket, and not on the front panel.

The 3BP1 tube is intended to operate with an e.h.t. supply of 1,500 volts, but it works perfectly satisfactorily with a 600 volt supply. The only effects of using this reduced voltage are a slight loss of trace brightness and an increase in deflection sensitivity.

To check that the display section is working properly, first earth the X and Y deflection plates temporarily to chassis and then switch the unit on. Check that VR7 controls the brightness of the spot and that VR6 enables the spot to be focused to a diameter of about 1mm. only. The spot should appear at about the centre of the screen.

The astigmatism control cannot be properly adjusted until the oscilloscope has been completed and its slider should be left at the centre of its track at this stage.

X AMPLIFIER

An extremely simple X amplifier is used, and the circuit diagram of this is shown in Fig. 9.

The input stage uses a 2N3819 field-effect transistor, TR3, in the source follower mode, this being the f.e.t. equivalent of the emitter and cathode follower circuits. TR3 is biased by R9, R10 and R11, while R12 is its source load resistor. VR1 operates as the X

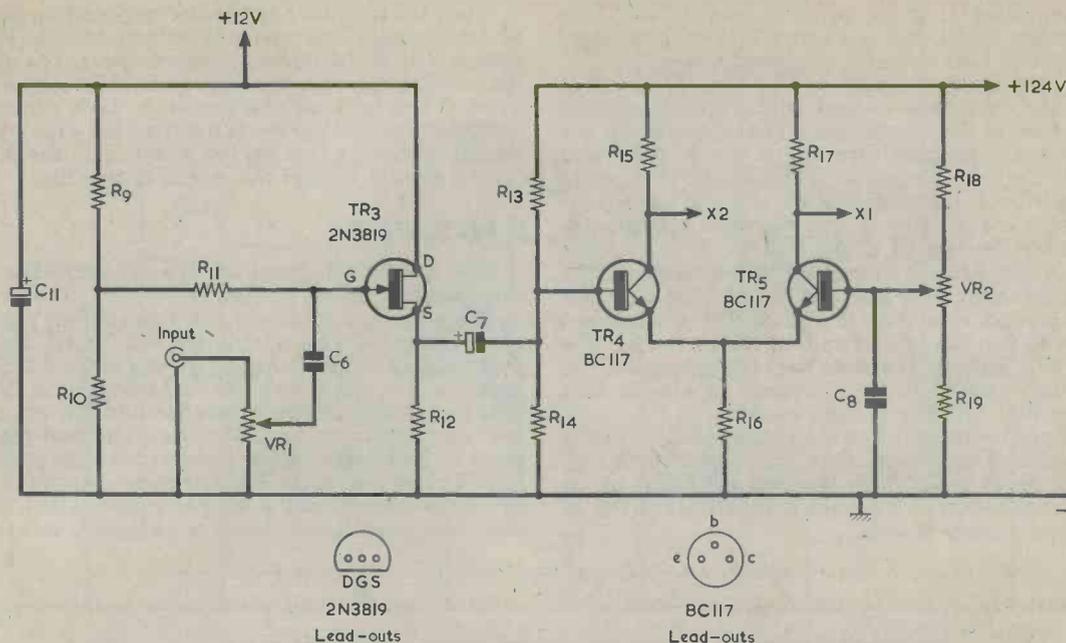


Fig. 9. The oscilloscope has a simple X amplifier in which voltage gain is governed by load resistor values

gain control and C6 provides d.c. blocking. The voltage gain of the input stage is slightly less than unity, and it is mainly used as a buffer stage to provide a high input impedance. The input impedance is $500\text{k}\Omega$ shunted by about 20pF .

C7 couples the output of TR3 to the input of the differential amplifier formed by TR4 and TR5. This type of amplifier has one input and two anti-phase outputs. TR4 and TR5 do not have to be matched as it is the resistor values which determine the static voltages and gains in the circuit and not the individual current gains of the transistors. For this reason, R13 to R17 are close tolerance components. One advantage of this circuit over that in the previous design is that no preset potentiometers are used, and so no setting up of the completed circuit is required.

The operation of the output stage is quite simple. R13 and R14 produce about 4.6 volts at the base of TR4, and in consequence about 4 volts are developed across R16, allowing for a voltage drop of approximately 0.6 volt in the base-emitter junction of TR4. If VR2, which is the X shift control, is adjusted to produce exactly the same voltage across R16, the circuit will be balanced. Of the 4mA flowing through R16, 2mA will flow through TR4 collector-emitter and R15, while the other 2mA will flow through TR5 collector-emitter and R17.

Obviously the voltages present at the outputs, i.e. TR4 and TR5 collectors, will be the same, and the spot will appear at the centre of the c.r.t. screen.

If a positive-going input signal is applied to TR4 base, this transistor will pass an increased collector-emitter current, and as a result the voltage at its collector will drop. The increased voltage across R16 will cause TR5 to pass a reduced collector-emitter current, and the voltage at its collector must therefore increase.



The X amplifier board is mounted at the front left of the chassis, partly below the cathode ray tube

An input signal of the opposite polarity will have the opposite effect, and will cause TR4 collector to go positive and TR5 collector to go negative.

The principal advantage of this type of circuit is that it enables a peak-to-peak output voltage of up to about 130 to be developed. The outputs of the amplifier are coupled directly to the X deflection plates of the tube. Capacitor C8 boosts the response of the amplifier at high frequencies, where it has a comparatively low reactance and provides a bypass to chassis for the base of TR5.

The X amplifier is assembled on a printed circuit board measuring 4 by 2 in., and the etching and component layouts are shown in Fig. 10. These are shown full size so that the copper pattern can be traced. The letters X-X indicate the same edge in both views. The input lead from VR1 is screened, as also is that between VR1 and the X input socket.

The board is mounted on the chassis in the position indicated in Fig. 3 (published last month) with C11 near the front panel. It is secured and takes up its chassis connection in the same manner as was the 12 volt power supply board.

When the amplifier has been completed and checked for mistakes, the unit may be switched on. By adjusting VR2 it should be possible to centre the spot on the screen, and VR2 should provide sufficient control to send the spot off the screen in both directions. Touching the non-earthly X input socket with a finger should produce a line on the screen, and the X gain control should control the length of this line.

Y AMPLIFIER

The circuit diagram of the Y amplifier and attenuator is shown in Fig. 11.

There are two inputs to the Y amplifier; one connects direct to VR3 and is the d.c. input, and the other, the a.c. input, connects by way of the d.c. blocking capacitor, C9. VR3 is the fine gain control. R20 to R24 form a simple step attenuator and also act as the gate bias resistance for TR6. The attenuator resistors must be high stability low-noise types, and must also have a close tolerance. The attenuator is not frequency compensated, but a simple modification, to be described next month, enables frequency compensa-

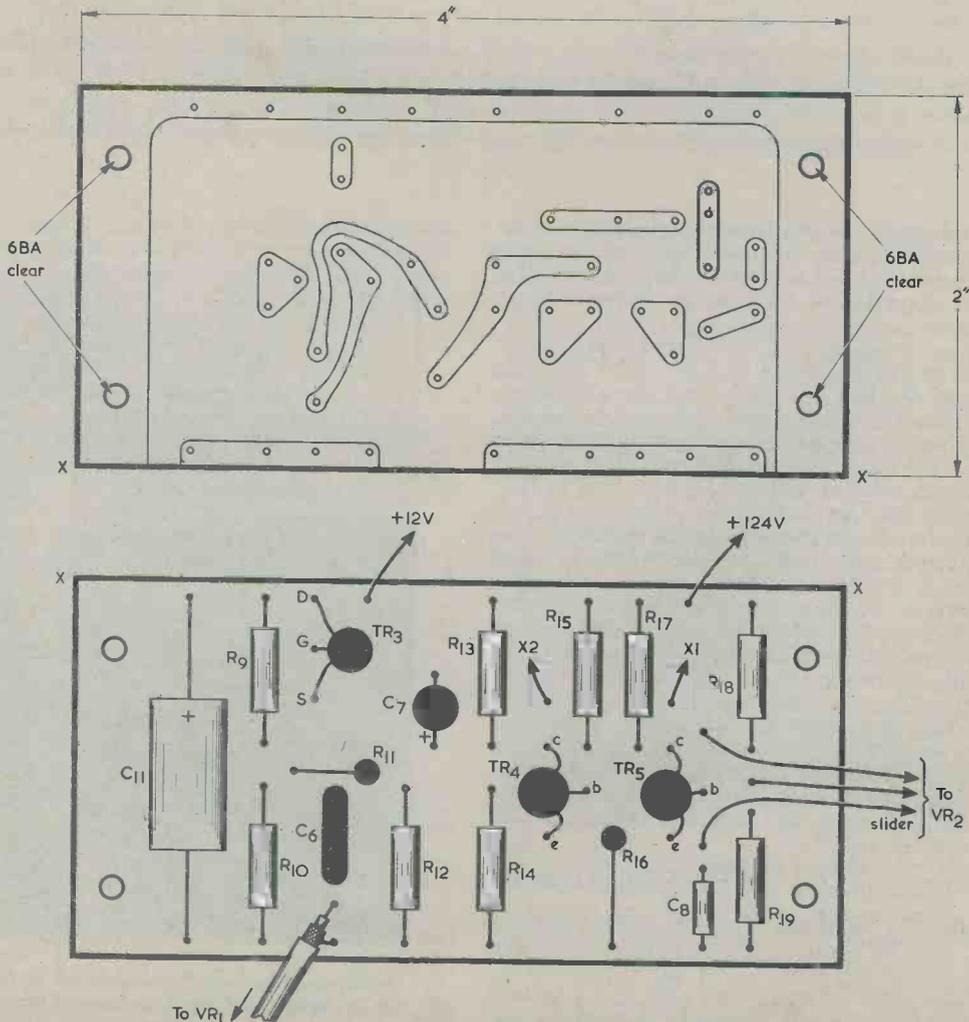


Fig. 10. Component and copper sides of the X amplifier board. This is reproduced full size for tracing, as are the diagrams for the other component boards

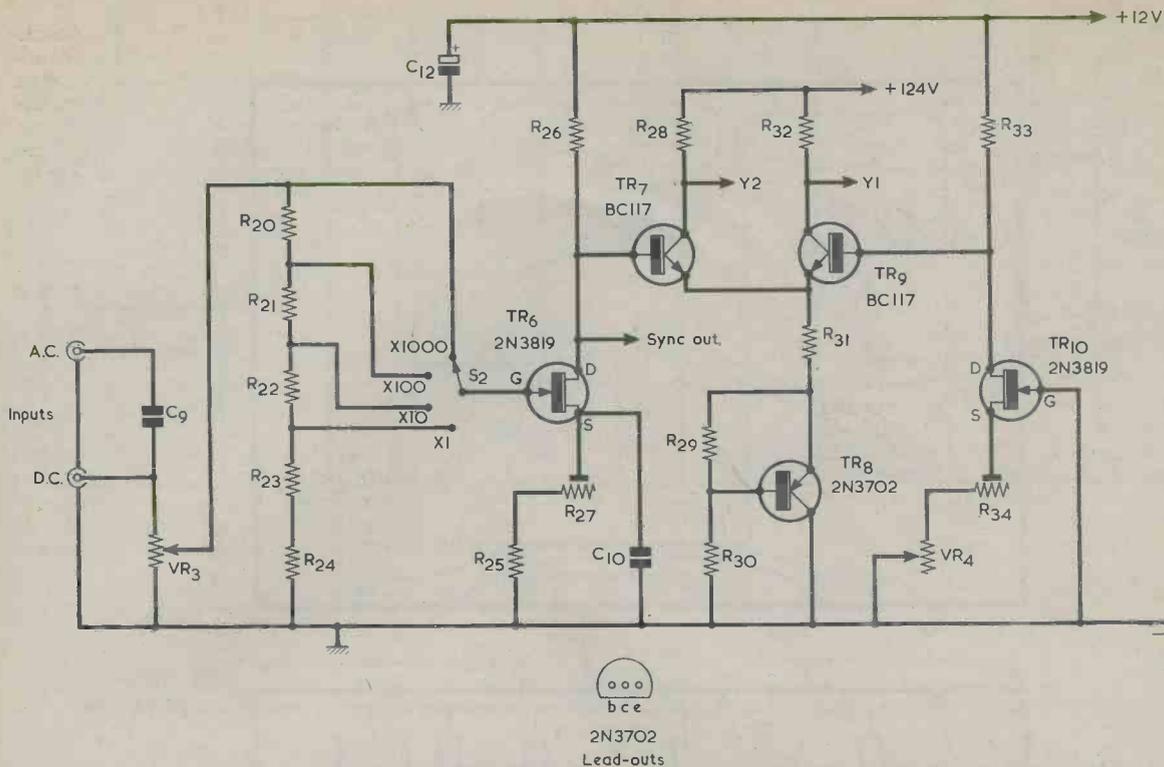


Fig. 11. The circuit of the Y amplifier and its input attenuator

tion to be incorporated if desired.

TR6 is used as a common source amplifier, and has R26 as its drain load resistor, and R27 together with R25 as its source bias resistor. C10 bypasses the source bias resistance at high frequencies and so provides high frequency boost.

TR7 and TR9 form a differential amplifier similar to that employed in the output of the X amplifier. The maximum output swing at TR6 drain in the negative direction provides a voltage which is rather high above chassis potential, and so TR8 is interposed between chassis and R31. TR8 functions as an 'amplified diode' and raises the lower end of R31 about 1 volt above chassis. It is not possible to increase the negative output swing of TR6, and so TR8 is used to increase the minimum input voltage requirement of the differential amplifier.


The base of TR9 is fed from a second common source f.e.t. circuit, rather than from a simple potential divider. This is necessary in order to provide temperature compensation. Any change in the voltage at TR6 drain caused by a change in ambient temperature is matched by a similar change at the drain of TR10. The circuit will thus remain balanced and the position of the trace on the screen will be unaltered.

VR4 is the Y shift control.

The Y amplifier is assembled on a printed circuit board which has dimensions of 4 by 2½ in. Etching details of this are shown full size in Fig. 12 together with the component layout. The board is mounted on the chassis in the position shown in Fig. 3 with the edge marked X-X in Fig. 12 nearer the front panel.

Screened leads are used for the input wiring and these should be kept as short as possible to keep the input capacitance low. The attenuator resistors are mounted on S2. This is a 3-pole 4-way rotary switch with two of the poles unused. (They are brought into use if the attenuator is modified for frequency compensation.) C9 is positioned between the a.c. and d.c. input sockets. Nothing connects to the sync output of the printed circuit board at this stage.

Wiring behind the panel above the Y amplifier board

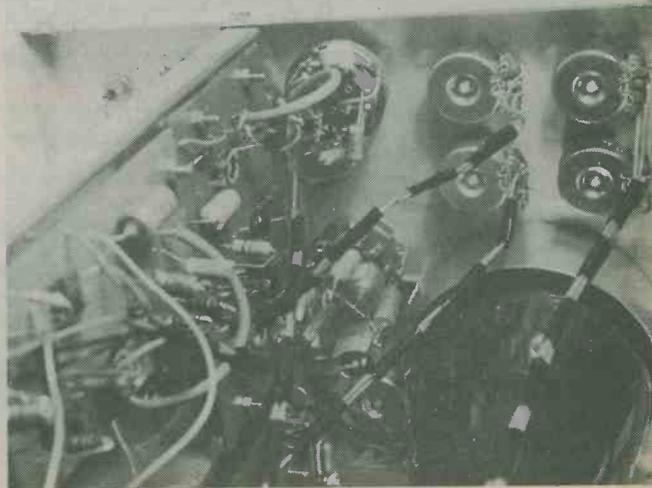

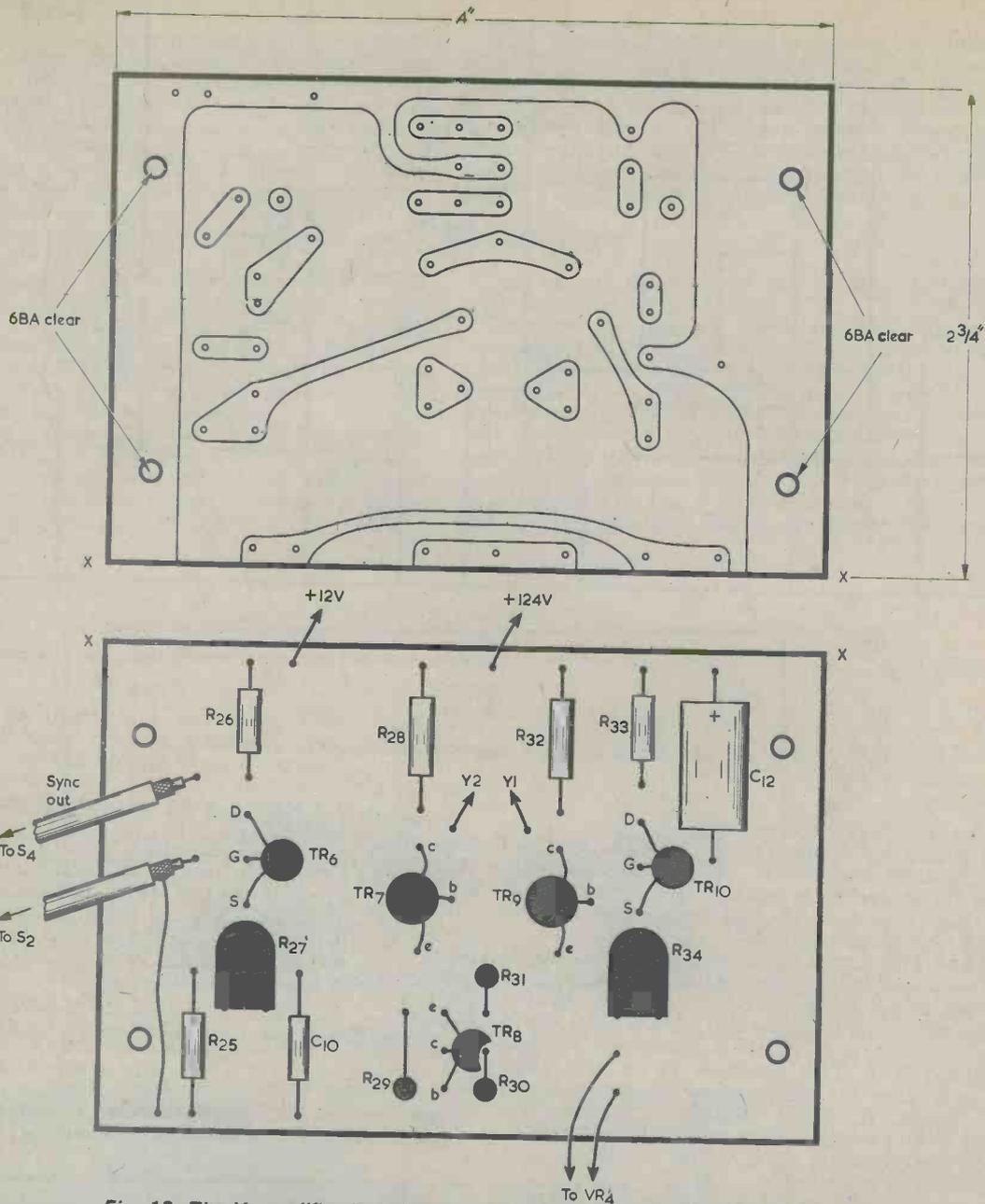


Fig. 12. The Y amplifier board after it has been etched and assembled

When the board has been checked for mistakes and installed on the chassis, set R27, R34 and VR4 to insert approximately half maximum resistance into circuit. Then switch the unit on.

Connect a 20,000 Ω per volt multimeter set to read 10 volts f.s.d. between TR6 drain and chassis, the negative test lead connecting to chassis. Adjust R27 to give a reading of 6.5 volts in the meter. Then adjust R34 to bring the spot to the centre of the screen. Check that the Y shift control can shift the spot off the screen at both the top and the bottom. Connecting a 9 volt battery to the d.c. Y input should shift the spot by a little less than 1cm. with the attenuator in the 'X1' position and the fine gain control at maximum.

TIMEBASE AND SYNC

The timebase circuit employs the popular NE555V integrated circuit or any of its equivalents. The circuit of the timebase generator and sync amplifier is given in Fig. 13. A detailed description of the NE555V will not be given as this has been the subject of many articles.

The timebase signal is generated across whichever of the capacitors is switched into circuit by S3(b). In position 0 of this switch the timebase is disconnected from the X amplifier input by S3(a), whilst S3(b) short-circuits TR12 collector to chassis to prevent stray capacitances allowing the timebase to oscillate.

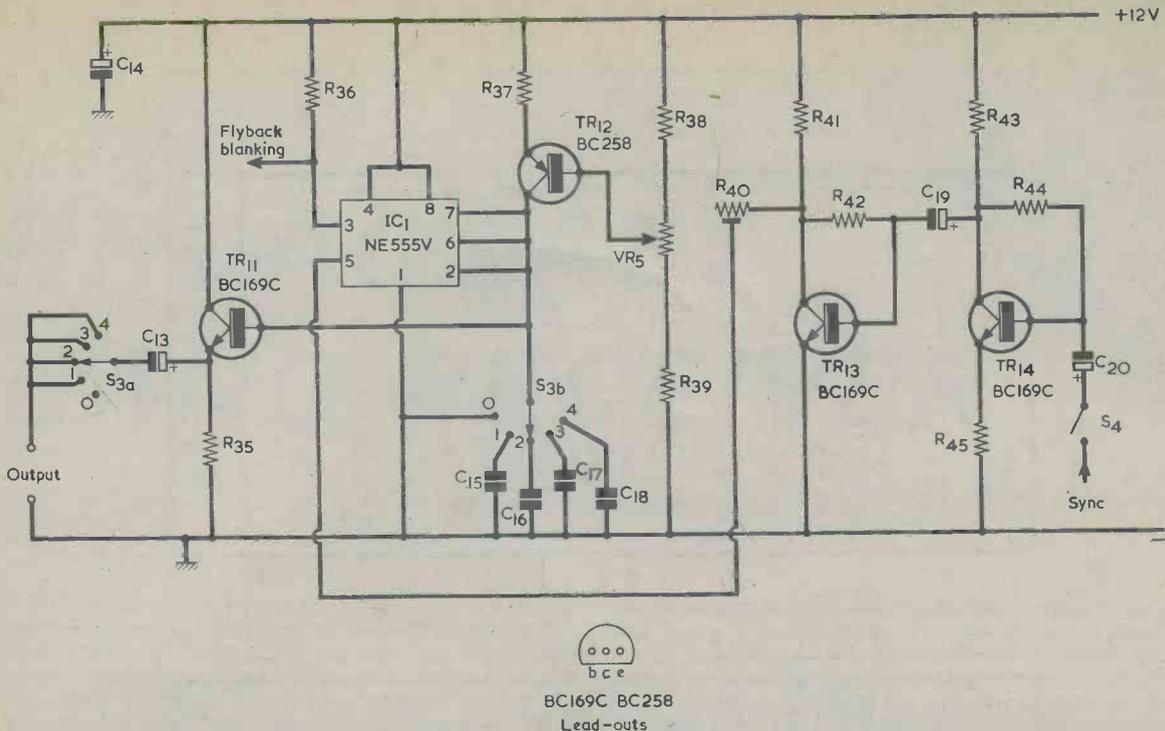


Fig. 13. The timebase section incorporates an NE555V timer with a constant current capacitor charging source

TR12 is connected as a constant current generator, the actual current which it produces being governed by the setting of VR5, which is the timebase fine frequency control. When the supply is applied the capacitor selected by S3(b) will begin to charge up via the constant current generator. Being fed from a constant current source, the capacitor will charge at a linear rate.

With pins 2, 6 and 7 of the NE555V connected together the capacitor will be allowed to charge to two-thirds of the supply potential. The capacitor will then be rapidly discharged by the i.c. until one-third of the supply potential appears across it. The i.c. then allows the capacitor to charge once more until two-thirds of the supply voltage is once again developed across it, whereupon it will again be quickly discharged to one-third of the supply potential.

This oscillation will continue, a 4 volt peak-to-peak linear sawtooth waveform being produced across the capacitor in the process. This signal is at a rather high impedance and is fed to the X amplifier via an emitter follower buffer stage, TR11. S3 functions as the timebase coarse frequency control.

During the short period when the capacitor is discharging the voltage at pin 3 of the i.c. goes low, and this pulse is amplified and used as the flyback blanking signal.

The sync signal from the Y amplifier is amplified by two common emitter amplifiers, TR13 and TR14. The amplified signal is fed to pin 5 of the i.c., where it modulates its triggering voltage and so locks the timebase frequency to a factor of the input frequency. This arrangement gives a stationary trace.

One problem with the sync circuit in the earlier oscilloscope was that adjusting the Y gain control altered the level of sync. This had the effect of shortening the trace and could even result in the number of


cycles displayed being reduced or increased as the Y gain was adjusted. The limiting action brought about by the use of an extra stage of gain in this circuit virtually eliminates that problem.

S4 is the sync on-off switch, and R40 is the sync pre-set level control.

The four timebase capacitors, C15 to C18, should preferably be close tolerance as this will enable the frequency ranges to ascend in multiples of approximately 10 times. They are listed as 5% plastic foil in the Components List, but it may be found easier to use a close tolerance silvered mica capacitor for C18. Capacitors with a tolerance of 10% can of course be employed, at a sacrifice of the relationship between ranges. The switch employed for S3 is a miniature 2-pole 6-way component with adjustable end stop set up for 5 ways. This is available from Henry's Radio, Ltd.

The timebase and sync circuits are assembled on a single printed circuit board which measures 4½ by 2in.

Side view giving details of the Y amplifier and timebase boards

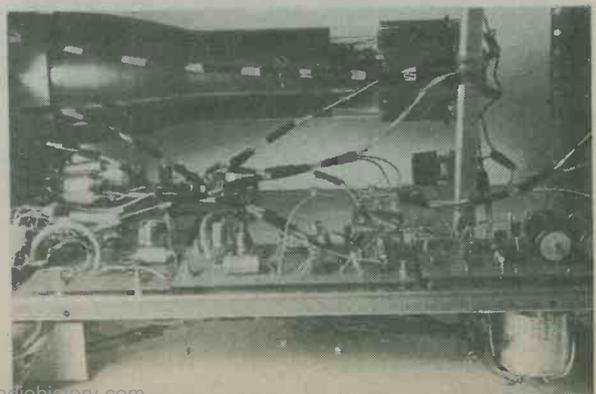

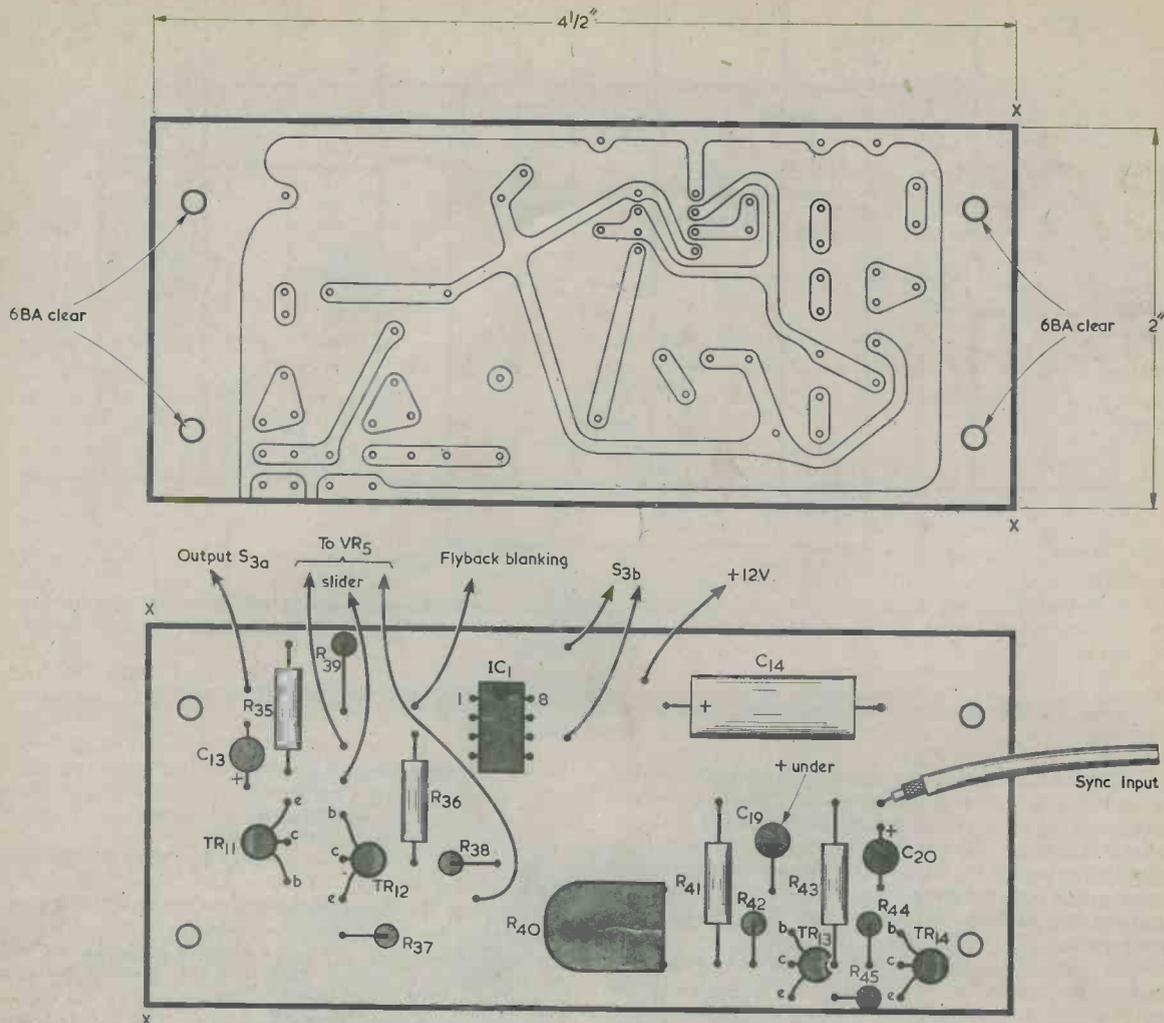


Fig. 14. The timebase component board in its completed form

Details of the etching of this are reproduced actual size in Fig. 14, which also shows the component layout.

The lead from the sync output on the Y amplifier to S4 is screened, as also is the lead from S4 to the timebase and sync board. The screened lead braiding may be earthed to chassis at any convenient point. The output from the timebase and sync board to S3(a) is not screened, but that from S3(a) to the X input is screened. C15 and C18 are soldered to the appropriate tags of S3(b). Note that R40 is slightly larger in physical size than R27 and R34 of Fig. 12. The smaller miniature size could be used for R40 as well, if desired, by slightly altering the copper pattern.

The timebase and sync board is mounted to the chassis in the position shown in Fig. 3, with TR14 near the front panel.

To test the timebase, first set S4 to the Off position, adjust R40 to insert about half maximum resistance into circuit and switch S3 to position 0. Turn the oscilloscope on and allow a minute or two for it to warm up. It should be working exactly as before until S2 is switched to position 1. A line should then appear

across the screen, and it should be possible to control the length of the line by adjusting the X gain control.

If the Y attenuator and fine gain controls are set at maximum and one of the Y input sockets is touched with a finger, a number of cycles should appear on the screen. VR5 should control the number of cycles produced. Then switch S4 to the On position and check that this synchronises the timebase properly. The sync gives a wide pull-in range, which can be adjusted to suit individual requirements by altering the setting of R40. If only a low level of sync is required R40 can be increased in value, say to 500kΩ.

NEXT MONTH

The only component board which has not yet been discussed is that for the flyback blanking amplifier. This will be described in next month's concluding article, which will also deal with adjustments and frequency compensation, including the provision of a frequency compensated input attenuator.

(To be concluded)




BROADCAST BAND RECEIVER

By J. R. Davies

This is the second of the two projects which can be assembled on the Veroboard presented free to readers in this month's issue. The receiver described here gives loudspeaker reception of local stations on the medium wave band. It may also be employed on long waves in areas where the Radio 2 signal on 1,500 metres is received at good strength.

The piece of Veroboard presented to readers this month is in a matrix of 0.15in. and has 7 strips by 16 holes. Methods of dealing with Veroboard are discussed at the start of the other Veroboard project article featured in this issue. The design described in the present article is for a receiver capable of driving a loudspeaker and which offers local station reception on the medium wave band. Since there is only one tuned circuit the selectivity is not as great as is possible with a superhet, but satisfactory reception of local signals which are reasonably well spaced in terms of frequency can be obtained. If desired, the receiver may also be employed for reception of the Radio 2 programme on 1,500 metres in areas where this transmission is received at good strength.

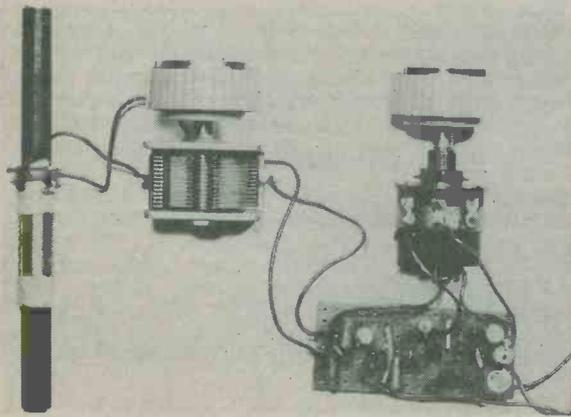

The Veroboard assembly wired up to VR1, S1, VC1 and a medium wave ferrite aerial

The circuit incorporates a ZN414 integrated circuit, this being followed by a 4-transistor a.f. amplifier which has been specifically designed to incorporate a very low quantity of components. A current-reading meter capable of measuring currents around 20mA is required for a test which is carried out after construction is complete. As a result of this test it may be necessary to alter the value of one resistor in the receiver, but the possibility of such a change being required is low.

CIRCUIT DESIGN

The circuit of the receiver appears in Fig. 1. The power for the receiver is provided by two 1.5 volt cells, these being switched into circuit by the on-off switch S1 (a) (b). This switch is ganged with the volume control VR1.

L1 is a ferrite rod aerial coil, and is tuned by the variable capacitor VC1. Further details of these two components are given later. They couple to the input of IC1, a ZN414 integrated circuit which functions both as an r.f. amplifier and as an a.m. detector. The ZN414 appears in a standard circuit with a 1.5 volt supply being applied to it from cell BY2. R2 is the output load resistor for the i.c., whilst C2, R3 and C3 are r.f. decoupling components. A detected a.m. signal free of r.f. content is thus applied to C4, and thence to the a.f. amplifier incorporating TR1 to TR4.

TR1 functions as an emitter follower feeding into the common emitter transistor TR2. The collector of TR2 couples directly to the bases of the output transistors, TR3 and TR4, and these provide a Class B output stage. Negative feedback, both at d.c. and a.c. is given via VR1 and R4.

Dealing first with the d.c. feedback, the purpose of this is to cause the output emitters, in the absence of signal, to take up a potential which is nearly equal to half the 3 volt supply potential. The base bias current for TR1 is taken from the output emitters via VR1 and R4, with the result that, should the output emitters go slightly positive in potential for any reason, an increased bias current flows into the base of TR1. The emitter current of this transistor increases proportionately, producing a higher base current and consequently a greater collector current in TR2. This increased collector current causes the output transistor bases to go negative, thereby

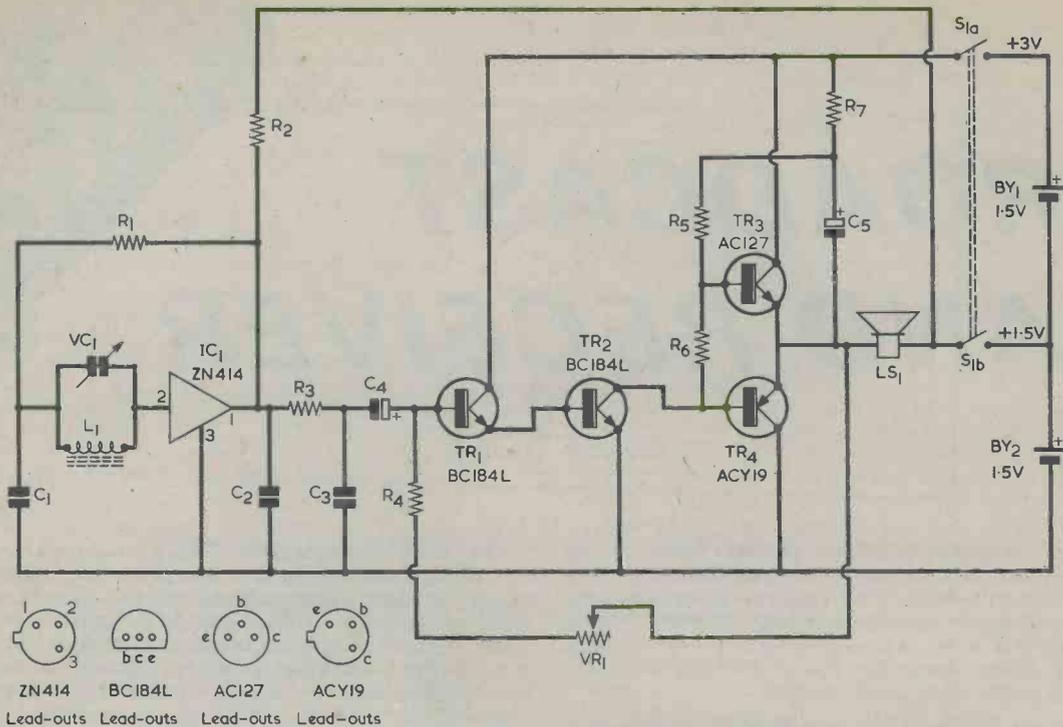


Fig. 1. The circuit of the broadcast band receiver. The low supply voltage enables the a.f. amplifier section to have a simple circuit with few components

COMPONENTS

Resistors

(All fixed values miniature $\frac{1}{4}$ watt 10% unless otherwise stated)

R1 100k Ω

R2 1k Ω

R3 680 Ω

R4 180 Ω

R5 68 Ω 5%

R6 18 Ω 5% (see text)

R7 15 Ω 5%

VR1 100k Ω potentiometer, log track, with S1 (a) (b)

Capacitors

C1 0.1 μ F type C280 (Mullard)

C2 0.1 μ F type C280 (Mullard)

C3 0.01 μ F type C280 (Mullard)

C4 4 μ F electrolytic, 4 to 10V Wkg., sub-miniature (Mullard)

C5 100 μ F electrolytic, 6.4 to 10V Wkg., sub-miniature (Mullard)

VC1 Variable air-spaced, value to suit ferrite aerial (see text)

Inductor

L1 Medium wave, or medium and long wave, ferrite aerial (see text)

Semiconductors

IC1 ZN414

TR1 BC184L

TR2 BC184L

TR3 AC127

TR4 ACY19

Switch

S1(a) (b) d.p.s.t. toggle (part of VR1)

Speaker

LS1 3 Ω speaker

Battery

BY1 1.5 volt cell

BY2 1.5 volt cell

Miscellaneous

Veroboard, 0.15in. matrix, 7 strips by 16 holes

2 knobs

Wire, sleeving, etc.

counteracting the initial positive voltage shift at the output emitters. The bias current required at TR1 base is very low, and the overall effect is that the circuit takes up a state of equilibrium in which the potential at the output emitters is very slightly positive of the voltage needed at TR1 base to maintain collector current in this transistor. Both TR1 and TR2 are silicon transistors with a typical voltage drop across their base-emitter junctions of some 0.7 volt, whereupon the output emitters take up a potential under no-signal conditions which is approximately 1.4 volts positive of the lower supply rail. Because of the low bias current requirement at TR1 base, the output emitters maintain this potential for all settings of VR1.

Under a.c. conditions, the voltage gain of the overall amplifier is approximately equal to the series resistance of VR1 and R4 divided by the impedance presented to the base of TR1 by the preceding circuitry. The impedance consists of R3 in series with the parallel combination of R2 and the output impedance of the ZN414. As a result, the a.f. amplifier section offers nearly the full voltage gain of which it is capable when VR1 inserts maximum resistance into circuit. The voltage gain falls continuously as VR1 is adjusted to insert reducing resistance, and it reaches a very low level when VR1 is set to insert minimum resistance. In consequence, VR1 controls the overall gain of the amplifier and functions as a volume control. It gives smooth control in practice and the circuit has the advantages of providing both d.c. and a.c. negative feedback as well as a volume control with two components, VR1 and R4, only. R4 is included to ensure that the resistance in the feedback path cannot be made lower than its own value. Without R4, the amplifier could break into supersonic oscillation when VR1 inserts minimum resistance.

SPEAKER COUPLING

Since the output emitters, under quiescent conditions, are very nearly at 1.5 volts above the lower rail, the speaker is connected directly between them and the junction of the two 1.5 volt cells. This method of connection renders unnecessary the high value electrolytic capacitor which would otherwise be required for speaker coupling. A relatively low value electrolytic capacitor, C5, couples the output emitters to the bootstrapping circuit given by R7 and R5. Since the upper end of R5 goes positive and negative in sympathy with the positive and negative signal excursions at the output transistor bases it presents a resistance to TR2 collector which is much higher than its actual physical value. The bootstrapping also provides an adequate source of collector current for TR2 when, in the presence of signal, the output bases go highly positive.

Because of the low supply potential, both TR3 and TR4 are germanium transistors with a consequent low voltage drop between their bases and emitters. Also the usual series emitter resistors, whose function is to limit thermal runaway current in the output transistors, have been omitted. Such resistors, if fitted, would seriously reduce the signal voltage available for the 3 Ω speaker. The common bias resistor, R6, has been given a value which allows a voltage of 0.32 volt to appear across it under quiescent conditions, and this voltage is just sufficient to bring most specimens of the AC127 and ACY19 used in the output circuit to the start of passing collector current. Because of the lack of protection against thermal runaway it is

desirable to keep quiescent current at a low level, even at the cost of a little crossover distortion. Such distortion will, in any case, only be apparent at high volume settings in VR1 whereupon the output signal will be at a high level with crossover distortion proportionately less noticeable. At lower volume settings in VR1, the increased negative feedback around the amplifier will itself reduce crossover distortion, if present. The author would add that he has operated the amplifier for considerable periods of time at both high and low output levels, and there has been no evidence of any tendency in the output transistors to even run warm.

Nevertheless, it is sensible to check the output transistor quiescent current after the receiver has been assembled, and this check consists of a simple measurement of overall receiver current. In the unlikely event that this indicates an excessively high quiescent current in TR3 and TR4 then the value of R6 can be reduced.

The use of a 3 volt supply instead of the more usual 6 or 9 volt battery is mainly concerned with the provision of a receiver circuit having a small number of components. The maximum output power which can be delivered to the speaker is of the order of several hundred milliwatts, and the current drawn from the 3 volt supply varies from a standing level of around 18mA to nearly 100mA on high output peaks. At medium volume settings the average current is around 30mA. The additional current drawn from BY2 by the ZN414 circuit is negligibly low, being only 0.3 to 0.5mA.

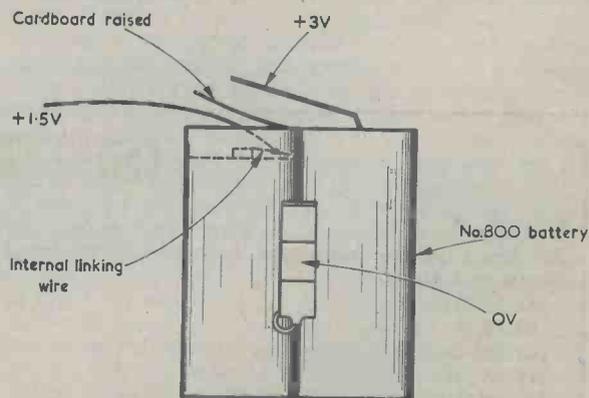


Fig. 2. An economical source of supply is given by a No. 800 cycle lamp battery. A connection to the internal wire linking its two cells provides the 1.5 volt supply point

The two 1.5 volt cells can consist of torch cells such as the HP2, but a more economical source of supply is given by a 2 cell cycle lamp battery, such as the Ever Ready No. 800. Access to the internal wire coupling the two cells together in this battery is obtained by raising the cardboard cover, and a lead can easily be soldered to this internal wire to provide the positive 1.5 volt supply point needed by the receiver. See Fig. 2.

FERRITE AERIAL

Before assembling the components on the Veroboard panel it is desirable to prepare a suitable ferrite rod aerial coil for L1. This has not been quoted as a specific part in the Components List because a number of options are available here.

Ready-wound manufactured medium wave, or medium and long wave, ferrite aerial assemblies are available from some component retailers, who usually state the value of tuning capacitor which should be employed with the assemblies. VC1 can then be given that value, or one which is slightly higher, should the latter be available.

If it is intended that the receiver be employed for medium wave reception only then all that is required is a medium wave ferrite aerial assembly. For adequate sensitivity the ferrite rod should not be shorter than 5in. If manufactured, the medium wave ferrite aerial coil will very probably have, in addition to the tuned winding, a second winding with a few turns for coupling to a low impedance transistor base input circuit. This coupling winding can be ignored and no connection is made to it. Should a manufactured ferrite aerial assembly also have a long wave winding on it, this is removed if it is intended to receive medium waves only. It is necessary to remove the long wave winding because such windings are frequently resonant, with their own self-capacitance, at frequencies in the medium wave band, and if left on the rod can cause unwanted absorption effects.

Should it be intended to have medium and long wave reception, the required wave band switching circuit is that shown in Fig. 3(a). As can be seen, the long wave winding is short-circuited on medium waves. The two windings should be connected so that they are series aiding, i.e. both windings are wound in the same direction and the inductance of the medium wave winding adds to that of the long wave winding when the long wave band is selected. As with the medium wave winding, any low impedance coupling winding on the long wave tuned winding should be ignored.

For constructors who wish to wind their own ferrite aerial, details are given for a medium wave version in Fig. 3(b). A medium and long wave home-wound coil assembly, together with the requisite wave band switching, is illustrated in Fig. 3(c). The letter and number references in Figs. 3(a), (b) and (c) apply to the holes in the Veroboard receiver panel at which they will connect. In both Figs. 3(b) and (c) the tuning capacitor may have a value between 250 and 310pF. Due to varying permeability between different ferrite rods it may be necessary to add or take off a few turns on the medium wave winding to enable it to cover the medium wave band precisely, and this can be done after the receiver has been assembled and checked out.

As already stated, the receiver is recommended for long wave reception only in areas where the Radio 2 transmission on 1,500 metres is at good strength. It is in any case easier to start initially with a medium wave aerial only, and then add a long wave winding and the appropriate switch after some experience with the completed receiver has been obtained.

Before carrying on to constructional details, a few words concerning components are required. The two electrolytic capacitors, C4 and C5, are specified as Mullard sub-miniature with a working voltage, for C4, between 4 and 10 volts, and a working voltage, for C5, between 6.4 and 10 volts. This choice of working

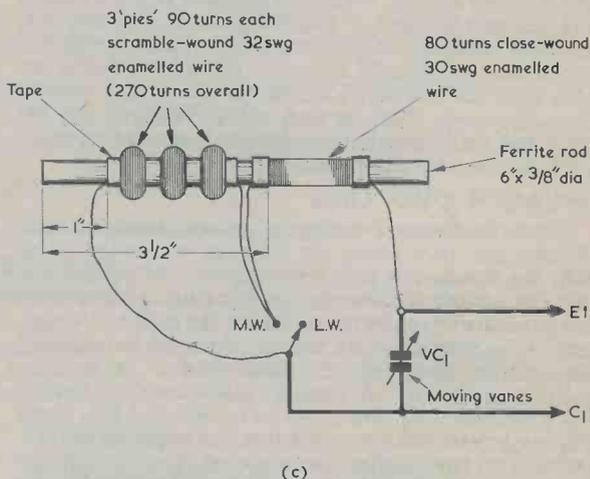
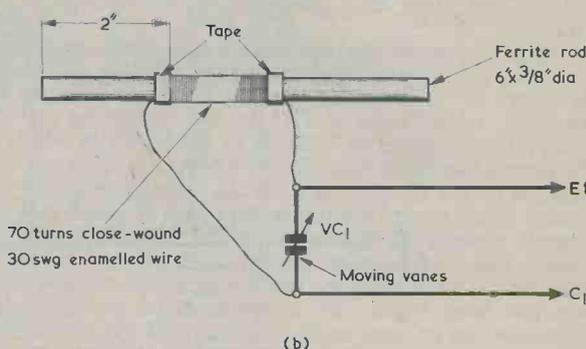
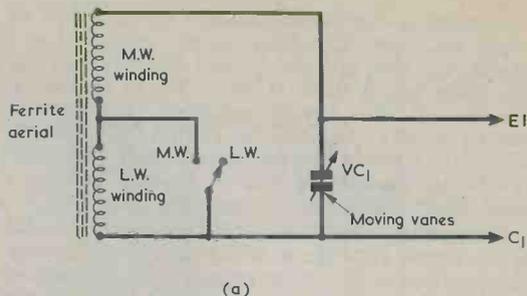


Fig. 3(a). A suitable wave band switching circuit if a ready wound medium and long wave ferrite aerial is used
 (b). Winding details for a home-wound medium wave ferrite aerial
 (c). A home-wound medium and long wave ferrite aerial assembly, and its wave band switching circuit

voltages takes in Mullard capacitors which are variously referred to as "type C426" or as being in the "015-016-017 range". C5 should have a diameter of 6.7mm. and a length of 18.5 to 20mm.

LS1 can be any 3Ω speaker. It will need to be mounted on a baffle or in an enclosure. For initial tests a suitable temporary baffle for a small speaker can consist of a piece of cardboard about a foot square with a hole in the centre having approximately the

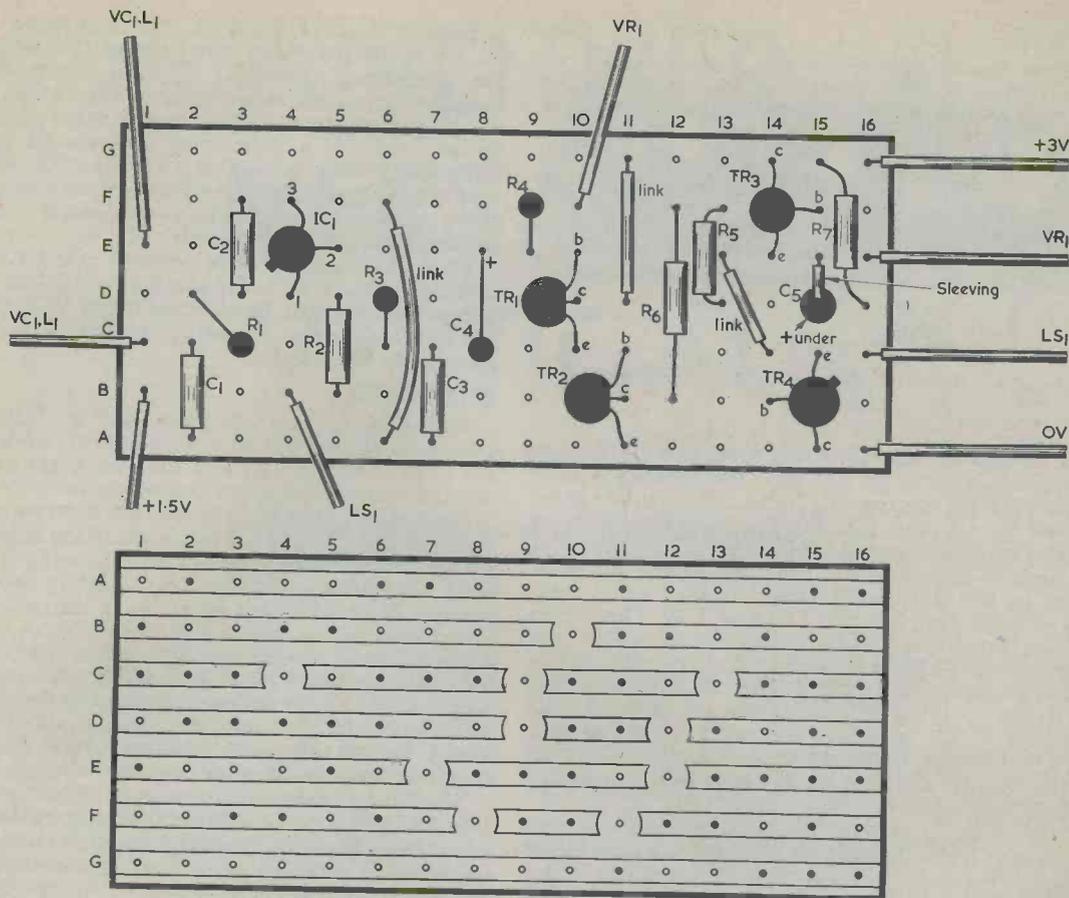


Fig. 4. Component and copper sides of the Veroboard panel

same dimensions as the speaker cone. The speaker is then simply stood on the bench with its cone upwards and the cardboard baffle placed over it. An elementary baffle of this nature makes a surprising improvement in audible volume and response.


ASSEMBLY

Having satisfied the points just discussed, assembly on the Veroboard panel may commence. Fig. 4 shows the component and copper sides of the panel with letter and number references to assist in the description of construction.


First take up the panel and, with a Vero spot face cutter or a twist drill of suitable size, cut the copper strips at holes B10, C4, C9, C13, D9, D12, E7, E12, F8 and F11. Next fit and solder thin insulated wire links between F6 and A6, between G11 and D11, and between E13 and C14. The link between F6 and A6 curves slightly to the right, as illustrated, to allow access to holes D6 and C6.

All components referred to next are soldered to the appropriate copper strips as they are fitted. There is no necessity to bend over any of the component leads excessively on the copper side of the board, and excess wire can be snipped off after soldering. Some resistors are fitted horizontally with their bodies parallel to the board surface, and some are fitted vertically in the manner indicated in the diagram. Fit R7 horizontally, positioning its body so that access is available to holes

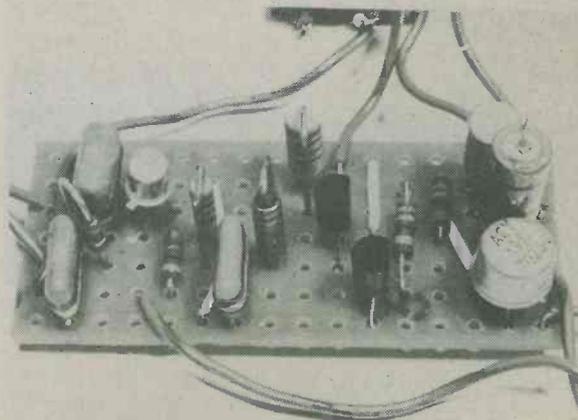F15 and E16. Fit R5 horizontally, spacing this a little way off the board so that its body is clear of the link wire at E13. Fit R6 horizontally, spacing this away from the board by about $\frac{1}{4}$ in. so that it can be easily removed later, if necessary. Fit R2 horizontally. Fit R1, R3 and R4 vertically in the positions illustrated.



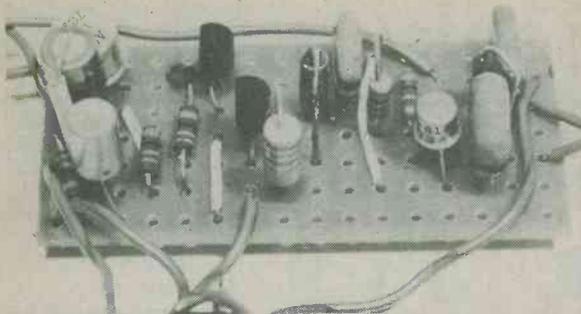A closer look at the components on the Veroboard



Another view of the completed Veroboard assembly

Fit C1 and C3 with their side wires passing through the holes indicated. Fit IC1, with its three leads passing through the appropriate holes. Fit C2 in the same manner as C1 and C3. Fit C4 vertically with its positive lead-out passing through E8. The polarity of the leads of this capacitor (and of C5) can be determined by the fact that the negative lead-out is common with the can. Next fit TR1 and TR2. The bodies of these transistors are above the holes through which their lead-outs pass, and not to one side as shown, for ease of presentation, in Fig. 4. Take up TR3 and identify its lead-outs with the aid of the inset in Fig. 1. The lead-outs of this transistor are rather close together and a little care is necessary in their location. Fit TR3 to the board with its body positioned centrally between hole rows G and E.

Take up C5, pass a $\frac{1}{4}$ in. length of thin sleeving over its negative lead-out and then bend this lead-out down alongside the capacitor body. Fit C5 vertically in the position shown, with its positive lead-out at D15. The purpose of the sleeving is to insulate the negative lead-out from the can of TR3 and thereby prevent possible crackles in the receiver output.

Fit a thin flexible insulated wire about 2ft. long to hole C16. This is one of the loudspeaker leads. Fit another similar wire, also about 2ft. long, to B4. This is the other loudspeaker lead. Both these leads may be shortened later, if desired. Fit a third wire, about 9in. long, to A16. This last wire connects to the negative terminal of BY2. Fit TR4 as indicated. It does not matter if the body of TR4 touches the insulating sleeve over the can of C5.

All the components are now fitted to the board. Next to be connected are leads passing to VR1/S1, and to L1 and VC1. VR1/S1 is positioned away from the board near the G row of holes. VC1 is positioned near the left hand end of the board, and the ferrite rod can be in any convenient position which does not too closely approach the board. Precise positioning of external components is not critical provided that the loudspeaker lead from hole C16 is kept away from L1, VC1 and the wiring to these. All the leads to the external components employ thin flexible insulated wire.

Fit a 2in. length of wire between E16 and the slider of VR1. Fit another 2in. wire between F10 and the zero volume end of VR1 track, so that the resistance inserted into circuit by VR1 increases as the spindle is turned clockwise. With an ohmmeter or continuity tester identify the tags corresponding to the two poles of S1(a), S1(b). It is important to ensure that the correct supply voltages, as indicated in Fig. 4, are applied to the board. If the 3 volt supply is inadvertently

applied to the ZN414 circuit, this i.c. may be damaged. Fit a $1\frac{1}{2}$ in. length of wire between G16 and one of the switch sections on VR1. Fit a 9in. length of wire to the other tag of this switch section. This is the positive 3 volt battery lead, but it is not connected to the battery yet. Fit a $2\frac{1}{2}$ in. wire between B1 and the remaining switch section on VR1. Fit a 9in. length of wire to the other tag of this second switch section. This is the positive 1.5 volt battery lead, and it is also not connected to the battery cells yet.

Fit a 4in. length of wire between hole C1 and the moving vanes of VC1. Fit another 4in. length of wire between E1 and the fixed vanes tag of VC1. Connect the ferrite aerial winding across VC1, using reasonably short leads.

CHECKING

Wiring up is now complete, and a visual check should be carried out to ensure that all solder joints are correct and sound, and that there are no short-circuits between adjacent copper strips.

Next ensure that S1 is turned off, then connect the zero volt and positive 1.5 volt leads to the appropriate points on the battery or two cells forming BY1 and BY2. Connect the positive 3 volt battery lead to the positive 3 volt battery point via a current-reading meter switched to read 0-50mA or 0-100mA. Connect the speaker to the loudspeaker leads. Switch on at VR1/S1, keeping VR1 close to the minimum volume position, and check the reading given by the meter. In all probability, this will lie between about 18 and 23mA. Should this be the case, no further checking is required, and the receiver is ready for use.

Should the current be in excess of 23mA, short circuit R6 with a piece of insulated wire having bared ends. The current indicated by the meter may remain unaltered or decrease. If the reading is unaltered, or if the decrease is 5mA or less, then no further checks are required and the receiver is ready to be used. Should the decrease in current be greater than 5mA then the value of R6 is too high and it needs to be reduced. Note the current reading in the meter with R6 short-circuited, then reduce the value of R6 until the current is less than 5mA greater than this short-circuit value. Reduction of the value of R6 is achieved by temporarily applying external resistors across it. If the desired lower current is given when 100 Ω is applied across R6, then its reduced value should be 15 Ω . Parallel resistors of 36 Ω and 22 Ω across R6 correspond to 12 Ω and 10 Ω respectively. When the required new value in R6 has been found, the existing resistor is carefully removed and the new value is fitted in its place.

As was stated earlier, it is very doubtful whether it will be necessary to replace R6 with a lower value component. The procedure just described is included for the sake of completeness of information.

Once the current check has been satisfactorily completed, the current-reading meter may be removed and a permanent connection made to the positive 3 volt point on the battery or cells. The receiver is then ready for use. The ZN414 is sensitive to supply voltage variations around 1.5 volts. If a brand-new battery offering terminal voltages higher than the nominal values is employed there may be oscillation and whistles between transmissions, these clearing when a strong signal is tuned in. This effect does not upset local station reception, and it disappears when the battery voltage has settled down to its nominal value. ■

ANOTHER VERSATILE VERTICAL

By V. S. Evans

How to tune an external Top Band loaded vertical aerial from the comfort of the shack.

This article is, to some extent, a follow-on from 'Versatile Vertical For Top Band' which appeared in the May, 1975 issue of *Radio & Electronics Constructor*. In the previous article the author described a loaded vertical aerial for the 160 metre amateur band which was primarily intended to be fitted to a car for mobile transmission and reception. The aerial employed aluminium alloy tubing with an adjustable section at the top for tuning together with a central loading coil.

Loaded vertical aerials of this nature can also be used at fixed locations, although there will then be difficulty in tuning if the aerial is mounted in an inaccessible place such as on a roof or at the top of a wooden pole. Series capacitive tuning is an accepted method of altering the resonant frequency of an aerial of this type, but the variable capacitance must be located at the base of the aerial.

REMOTE CONTROL

This article describes a remote control switching method which allows the operator to switch into use any one of four segments of Top Band for transmission and reception. A weatherproof unit at the base of the vertical loaded aerial contains two reed relay switches, the contacts of which are mounted inside hermetically sealed glass tubes, whereupon they are impervious to tarnish or corrosion. The glass tubes containing the switch reeds are each fitted within a solenoid, and the reeds are operated electromagnetically by passing a current through one or both of the solenoids from the shack. The unit also contains two pre-set trimmer capacitors which are taken in or out of circuit by the reed switches.

Fig. 1 shows the basic circuit and it will be seen that two trimmers, C1 and C2, are in series with the feed to the aerial. The reed switches are connected across the capacitors and their solenoids are coupled to switch S1(a)(b) in the shack. When this switch is in position 1 both solenoids are energised, both reed switches are closed and both trimmers are short-circuited. With the switch in position 2, C2 is short-circuited and C1 is in series with the aerial. Position 3 of the switch causes

C1 to be short-circuited and C2 to be in circuit, whilst setting the switch to position 4 brings both trimmers in series with the feed to the aerial.

A common earth connection to the solenoids is carried by the outer conductor of the coaxial cable between the transmitter or receiver and the aerial. This means that in addition to the normal coaxial feed there is also required a lightweight twin plastic cable which may be taped to the coaxial line.

SWITCH UNIT

A piece of Perspex or s.r.b.p. ('Paxolin') measuring $2\frac{1}{2}$ by $4\frac{1}{2}$ in., together with a strip of the same material $1\frac{1}{2}$ in. wide mounted at one end at right angles, will accommodate all the components required at the base of

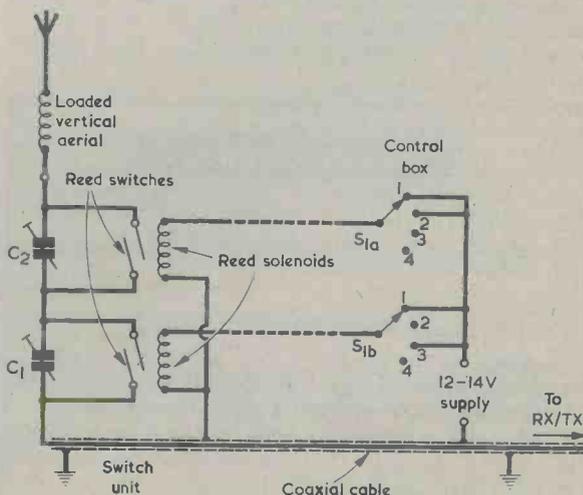


Fig. 1. The circuit used for remote tuning of the aerial. The control box is situated at the operating position.

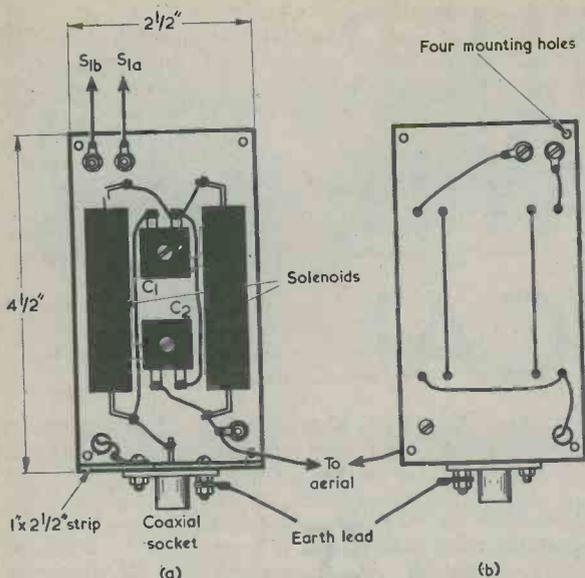


Fig. 2(a). Layout of components in the switch unit. The strip at the bottom is secured to the main panel by a small angle bracket. (b). The panel underside, showing the wiring to the solenoids.

the aerial. Fig. 2(a) shows layout and wiring. The glass reed switches should be treated with care as rough usage or overheating during soldering will break the glass. Fig. 2(b) shows the rear side of the panel and the wiring to the solenoids. The solenoids have two windings, which are connected in series for the present application. This explains why four connections are shown for each solenoid. Soldering to the solenoid pins should be carried out quickly, otherwise the former material will soften and the pins become loose.

Fig. 3 shows the switch unit contained in a suitable metal weatherproof box, which must be positioned close to the base of the aerial. The lead from the box to the aerial should be stranded copper with thick walled insulation, and must not be more than 12in. long.

COMPONENTS

Capacitors

C1 500pF mica trimmer (see text)
C2 250pF mica trimmer

Switch

S1(a)(b) 2-pole 4-way rotary

Reed Relays

2-off reed switches type 7-RSR-A (R.S. Components)
2-off solenoids, coils type 1 (R.S. Components)

Miscellaneous

Knob with pointer
Coaxial plug and socket
Perspex or s.r.b.p. panel
Weatherproof metal box
Nuts, bolts, solder tags, grommets, etc.

CONTROL BOX

The rotary switch can be mounted in a small box, being fitted with a knob and pointer. A white fascia showing the switch positions may then be glued behind the pointer. Four terminals are required at the rear of the box, these connecting to the two wires which couple to the reed switch solenoids, to earth and to a d.c. energising source of 12 to 14 volts. The energising voltage may be obtained from batteries, from a small mains power unit, or from the power supplies in either the transmitter or the receiver. In the last instance, the outer conductor of the coaxial cable will normally be common with the chassis of the transmitter or receiver. The energising source can be either positive or negative of earth. The two windings of each solenoid have a resistance of 800Ω, giving a total of 1,600Ω for each coil. The corresponding current is slightly under 10mA for each coil.

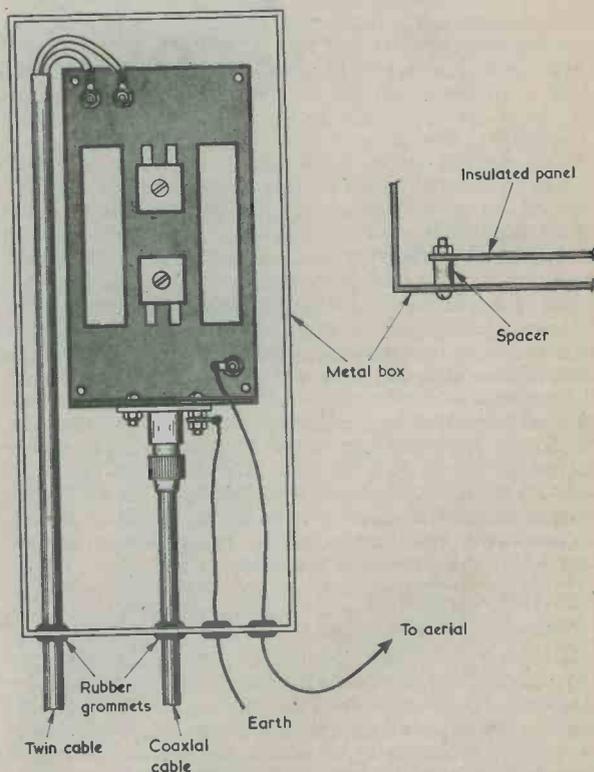


Fig. 3. The switch unit is fitted in a weatherproof box with wires entering through grommets at the bottom.

The two reed switches specified are rated at 2 amps. The two trimmer capacitors should be robust mica types and suitable components are type D4 or D5 from Henry's Radio, or type TP from Home Radio or Doram Electronics. The 500pF value specified for C1 is nominal and the nearest actual values available here are 120-750pF (Henry's Radio), 50-450pF or 150-750pF (Home Radio) and 100-580pF (Doram Electronics).

SETTING UP

The aerial and the switch unit may be mounted at a reasonably accessible position for adjustment and tuning. They should be well away from surrounding objects and a few feet off the ground. The coaxial and twin cables should be cut to the length that will be required for the final positioning of the aerial.

With the rotary switch in position 1 both trimmers are short-circuited, and the system should be tuned to a low part of the band, say 1.825MHz, by adjusting the telescopic top of the aerial. The switch is next set to position 2, whereupon C1 comes into circuit. This can be adjusted to tune to the next higher frequency point required. Setting the switch to position 3 brings in C2

on its own, and this should be tuned to a still higher frequency, as required. With the switch in position 4 both trimmers are in circuit, and the resonant frequency depends upon the previous adjustments and cannot be altered without affecting the previously set points.

It will be seen that there is a considerable variation permitted in the choice of band segments to suit the operator.

Some thought should be given to making the aerial loading coil waterproof in a permanent installation. Waterproofing compound, rather like plasticine, is obtainable from motor accessory shops. Alternatively, heavy greasing or tape could be employed to prevent the ingress of rain-water. ■

AMATEUR RADIO TELEPRINTER SPEED STANDARDS

By Arthur C. Gee

One of the most controversial topics in the world of amateur radio RTTY has been that of the speed at which the teleprinter should run. Ever since RTTY started in the UK this matter has constantly come up for consideration. Basically the difficulty arose from the fact that in this country the standard speed for commercial teleprinters is 50 bauds, whereas in America the commercial standard favoured at the start of RTTY was 45 bauds. The only source of teleprinters for the amateur has been surplus obsolete equipment sold cheaply by the commercial concerns, which meant that almost all the teleprinters coming on to the market in the UK were for 50 bauds. In America, and in those parts of the world where American equipment had been used extensively, the printers were for 45 bauds.

At first there was not too much difficulty. Most RTTY enthusiasts were happy to make QSO's with others in their own country, so here and to a certain extent in Europe 50 bauds became adopted as the standard. However, as the "art" developed it became quite commonplace to work Dx, and contacts across the Atlantic to American stations became the accepted thing. This of course brought into the open the question of what speed should be used — 45 or 50 bauds? The machines in this country usually had governed motors whose speed could be altered by a few simple ad-

justments, and these could be changed to the 45 baud speed without too much difficulty. In America the machines had synchronous motors whose speeds could not be altered. So those who wanted to work Dx with the US had to change their speeds to 45 bauds. On the other hand, those who only wanted to work "local" stations on v.h.f. or, say, 80 metres continued to leave their machines at 50 bauds. So the two speeds remained in use.

Intercontinental RTTY contacts are at present almost commonplace. Nowadays, you can call CQ-RTTY on 20 metres almost any time of the day, any day of the week, and get a reply. But most of the Continental stations are also interested in Dx, so they now use 45 bauds. In order to sort things out, BARTG via the RSGB presented a paper to the recent Region 1 IARU Conference at Warsaw, setting out the problem and making suggestions for resolving it.

BARTG proposed that the standard be 50 bauds. It must be said that they presented a very good case for retaining this speed, and produced a well prepared and technically sound paper. However, their proposal found no support whatsoever amongst other delegates, and the Conference voted massively for the adoption of 45 bauds as the standard speed for all future forms of amateur RTTY. So maybe, at last, this vexed question has been resolved. ■

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is the cover price stated on the issue, plus 8p postage.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available. Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

FOLDBACK LIMITING VOLTAGE REGULATORS

By J. B. Dance

Small integrated circuit voltage regulators can provide a stable output voltage having low ripple together with foldback current limiting to prevent accidental damage.

The SGS-Ates TBA 625 series of voltage regulator integrated circuits are encapsulated in small TO-5 transistor cases and provide maximum output currents of about 140mA. They are particularly suitable for use on individual circuit boards.

REASONS FOR USE

The reader who has never used an integrated circuit voltage regulator may well ask why he should consider using one now, since in most cases the amateur experimenter does not require particularly well regulated power supplies. There are three main advantages, and these will next be discussed.

First, the use of a suitable voltage regulator of the type under discussion enables the hum ripple at a power supply output to be reduced to about 1mV with very simple circuits. The regulator devices are smaller and cheaper than the large value electrolytic capacitors which might otherwise be required to provide the same level of smoothing.

Secondly, the writer uses the TBA 625B or the TBA 625C to provide power supplies with a very low hum level from which the supply for the varicap diodes of an f.m. tuner can be derived. Some form of regulator circuit is almost essential in this application and it is easier to employ an integrated circuit regulator than to build one with discrete components. In addition, the use of a regulated supply ensures that the tuning scale remains unaffected by mains voltage variations.

Finally, constructors who use many integrated circuits for experimental work may destroy appreciable numbers of these by accidentally short-circuiting some of their connections during experiments and thus allowing large currents to flow. The output current "folds back" in the devices being considered to about 30 to 45mA when the output is accidentally short-circuited. Such a current is unlikely to damage any normal device and the use of these voltage regulators in power supplies therefore offers almost

complete protection to the circuits being supplied with power.

The writer now almost always employs power supplies containing one of these regulators provided that they can supply enough current to the circuit concerned; they have been especially useful when he has been experimenting with pre-production samples of very new devices which are often irreplaceable. He has never had any device fail when this type of power supply has been employed.

The devices are particularly suitable for use on individual circuit boards where a number of these are operated from a single supply, since they eliminate the problems of unwanted coupling between boards. Although the output current is limited to about 140mA, methods of obtaining higher currents are available.

REGULATOR TYPES

The regulators are available in four different types, the main difference between them being their output voltages. The values of these output voltages and various other data are shown in the Table. The connections to all of the four types of device are shown in Fig. 1.

TABLE
The TBA 625 series of Regulators

	TBA 625A	TBA 435	TBA 625B	TBA 625C
Output voltage	5V	8.5V	12V	15V
Max. input voltage	20V	20V	27V	27V
Ripple rejection (I _{out} = 5mA 100Hz)	60db	57db	54db	51db
Short-circuit current	45mA	40mA	35mA	30mA
Output noise voltage, 10Hz to 100kHz	70μV	100μV	150μV	200μV

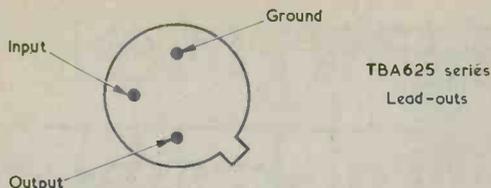


Fig. 1 Lead-outs for the TBA 625 series of voltage regulators

A typical circuit for providing a regulated positive output is shown in Fig. 2; the simplicity of this circuit is very striking. It is important that the $10\mu\text{F}$ capacitor C2 connected across the output should be soldered as close to the regulator as possible in order to ensure stability. The value of the reservoir capacitor C1 on the input side is determined by the value of the output current required and by the maximum permissible output ripple voltage.

As an example, one may consider the case of a TBA 625A used with C1 at $500\mu\text{F}$ and an output current of 100mA. If the ripple voltage across C1 at 100Hz is about 2V peak-to-peak, the output ripple is typically 4mV peak-to-peak.

CURRENT FOLDBACK

In order to protect the devices against excessive thermal dissipation under short-circuiting of the output, current limiting under these conditions must take place at a lower current than the normal maximum output current. The devices are therefore designed so that the current "folds back" when the resistance of the load falls below a certain value; this current foldback is shown in Fig. 3 for the four devices. The output voltage is guaranteed to be regulated to within 1% for output currents at least up to 100mA.

The maximum current and the short-circuit current both fall with increasing chip temperature; this further reduces the possibility of excessive thermal dissipation. The quiescent current is the input current when the output current is zero; it is about 9mA for the TBA 625A and TBA 435 at the maximum permissible input voltage of 20V for these devices and about 10mA for the TBA 625B and the TBA 625C at the maximum permissible input voltage of 27V.

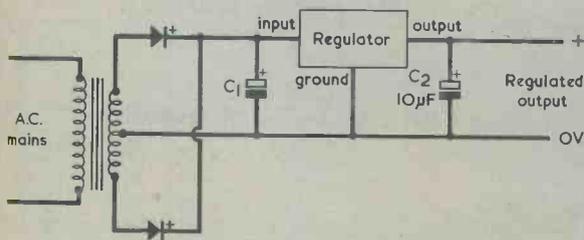


Fig. 2. The very simple voltage regulated power supply circuit which the regulators make possible

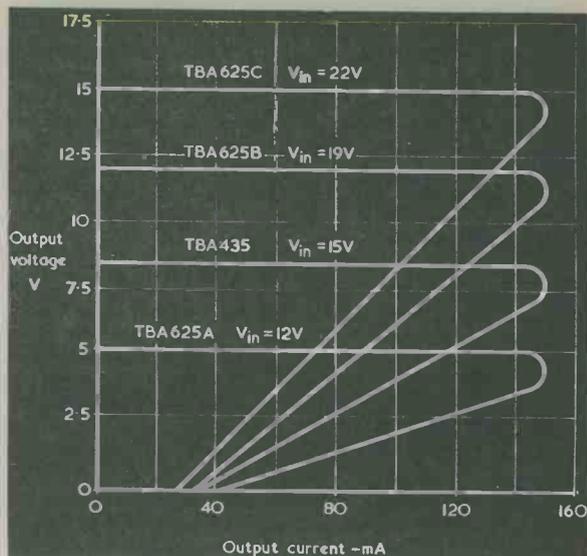


Fig. 3. Voltage, output current and foldback characteristics of the regulators

The ripple rejections fall to about 6db below the values shown in the Table as the output current rises to 140mA. The minimum amount by which the input voltage across C1 of Fig. 2 must exceed the output voltage across C2 for 1% regulation is shown in Fig. 4.

The quiescent power dissipation is equal to the input voltage multiplied by the quiescent current, but when an output current is drawn the dissipation is increased by an amount equal to the output current multiplied by the difference between the input and output voltages. Each device can dissipate up to about 0.7W at ambient temperatures up to 25°C , but if a


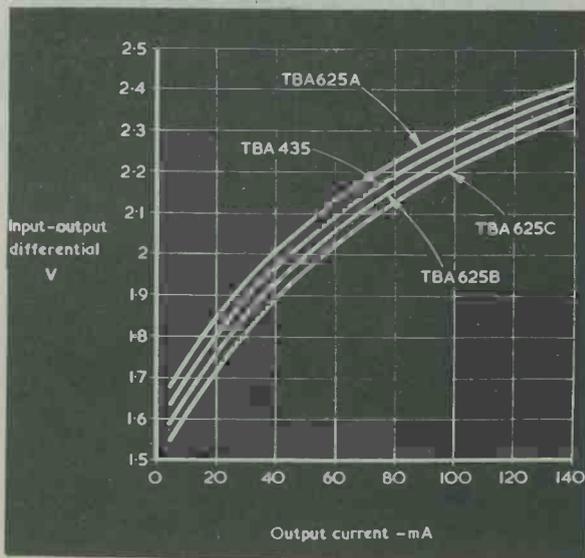


Fig. 4. Minimum input — output voltage requirements for 1% regulation

RADIO & ELECTRONICS CONSTRUCTOR

NOVEMBER ISSUE FEATURES

POWER SUPPLY FOR OP-AMPS

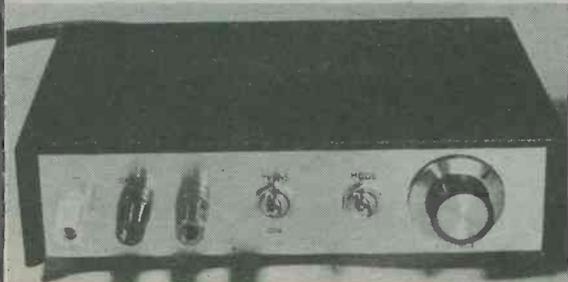

Using an ingenious voltage splitting technique, this power unit provides continuously variable positive and negative voltages for the supply of all standard operational amplifier circuits. Further features are voltage stabilization and overload current limiting.

★ ★ ★

THE 6/12 AMPLIFIER
Part 1 (2 parts)

★ ★ ★

WIDE RANGE METRONOME

**ALL THE USUAL FEATURES
PLUS
MANY OTHER ARTICLES
PRICE 30p**

Copies may also be obtained direct from the Publishers, 38p including postage. Published by Data Publications Ltd., 57 Maida Vale, London W9 1SN.

RADIO & ELECTRONICS CONSTRUCTOR

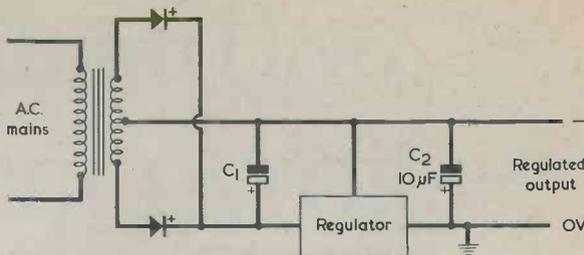


Fig. 5. Using a regulator to obtain a negative supply voltage

heat sink of thermal resistance $37^{\circ}\text{C}/\text{W}$ is fitted, the dissipation can be increased to 2W. The writer often uses Jermyn type 2215 TO-5 heat sinks with these devices, but in many cases no heat sink is required. For example, the TBA 625A can be used with a 12V input supply at output currents of up to 70mA without any heat sink even if the ambient temperature reaches 70°C . (It may be noted that the type H1 TO-5 heat sink listed by Henry's radio is rated at $10^{\circ}\text{C}/\text{W}$).

OTHER CIRCUITS

The devices may be used in the circuit of Fig. 5 when a negative regulated supply line is required. The performance is the same as that of Fig. 2.

A small increase in the output voltage can be obtained by inserting a resistor between the regulator device and ground, as shown in Fig. 6. The increase in the output voltage is equal to the value of this resistor multiplied by the quiescent current, the latter being indicated as IG. The maximum value of the resistor which can be employed (about 200Ω) produces an increase in the output voltage of about 2V; higher values of this resistor may result in blocking of the device with zero output voltage across it. If desired, the resistor of Fig. 6 can be made variable.

The circuit of Fig. 6 retains the foldback current characteristics on short-circuit; indeed, the short-circuit current is less than in the case of Fig. 2. The other features of the circuit of Fig. 2 are also retained.

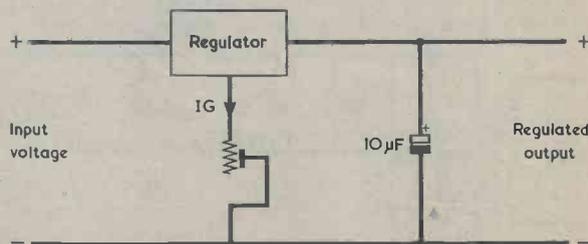


Fig. 6. The regulator output voltage can be increased by inserting a resistor in the manner shown here

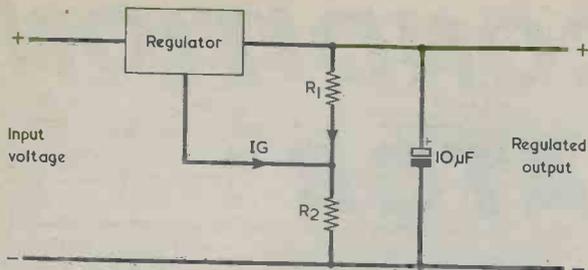


Fig. 7. Another method of obtaining an increased output voltage

Somewhat larger increases in the output voltage may be obtained by the use of the circuit shown in Fig. 7. The current flowing through R_1 increases the total current flowing through R_2 above the quiescent current, I_G . R_2 may be fixed or variable. As shown in Fig. 8, the foldback current characteristics are retained in the circuit of Fig. 7.

HIGHER CURRENTS

Various circuits have been published in which these regulators are used with one or more transistors to provide greater current outputs. Outputs of several amps are easily obtained with foldback to about 0.5A on short-circuiting of the output.

However, a simpler way of obtaining somewhat higher currents involves the use of another type of

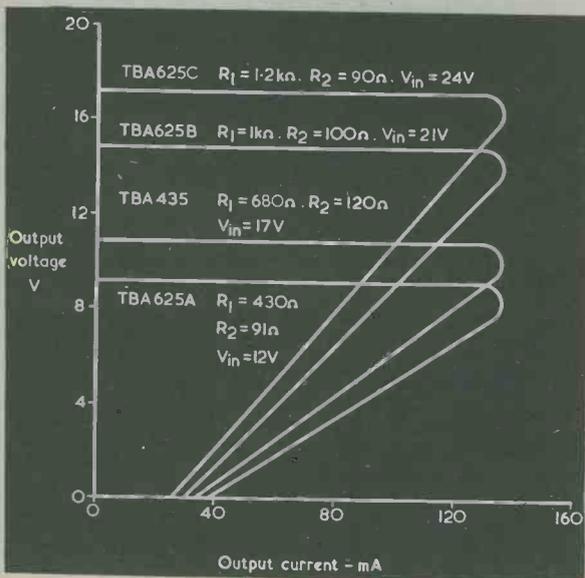


Fig. 8. Typical voltage and current characteristics for the circuit of Fig. 7

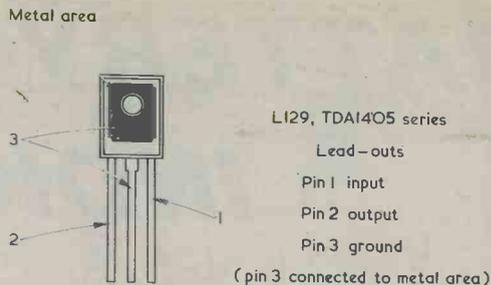


Fig. 9. The lead-outs of the higher current regulators discussed in the text

regulator in a TO-126 power transistor package of the type which can be fixed to a heat sink with a single bolt. The SGS-Ates L129 and TDA 1405 devices provide an output voltage of 5V at currents up to at least 600mA, the L130 and TDA 1412 devices provide currents of at least 500mA at 12V, and the L131 and TDA 1415 devices provide currents up to at least 450mA at 15V. Typical values of the maximum output currents are rather higher than the minimum values quoted, being namely 820mA, 720mA and 600mA for the respective types. The lead-out connections are shown in Fig. 9.

These power regulators can be used in exactly the same type of circuit as that of Fig. 2. The output capacitor may be 10 μ F, but in some cases a fairly high value of input capacitor may be required to supply the larger current to these devices. The L129, L130 and L131 devices can operate at room temperatures down to -20°C, whilst the TDA 1405, TDA 1412 and TDA 1415 devices have a minimum recommended operating temperature of 0°C.

For high levels of dissipation a heat sink measuring about 2in. square should be adequate. The maximum permissible dissipation without a heat sink is 1.25W.

Current foldback occurs when the output is short-circuited, the value of the short-circuit current being typically 200mA, 100mA and 85mA for the 5, 12 and 15V devices respectively. These regulators therefore provide a substantial amount of protection to any circuits they are feeding, but the protection against accidental short-circuits is obviously less than with the TBA 625 series of regulators.

Readers may wish to use these power regulators to supply current to integrated circuit power amplifiers which are not themselves short-circuit protected during the initial experimental period. The power regulators should provide ample protection for this purpose.

All the regulators referred to in this article, with the exception of the TBA 435, are listed by Chromasonic Electronics, 56 Fortis Green Road, London, N10 3HN.

CONCLUSION

In conclusion, the writer hopes that he has conveyed to readers his enthusiasm for the use of integrated circuit regulators in circuits where the regulation they provide may not be required but where the protection they give to other integrated circuits combined with their hum rejection is most valuable.

BATTERY CONDITION INDICATOR

By P. R. Arthur

A neat comparator circuit which can be fitted to battery operated equipment to maintain a check on battery voltage.

This simple little device makes a very useful addition to many pieces of test equipment as well as other types of electronic apparatus. The unit incorporates an indicator light which comes on when the supply voltage falls below a certain pre-set level. This triggering threshold can lie anywhere between 6 and 15 volts.

BATTERY CURRENT

One reason for including the device in an electronic equipment is that if the equipment draws a very low level of battery current the voltage drop caused by the increase in the internal resistance of the battery as it runs down will be relatively small. The equipment may therefore function properly even though the battery may be virtually exhausted. There is in consequence a very real risk that the battery electrolyte may begin to leak while the battery is still inside the equipment. Quite expensive damage can be caused in this way, as the author has found to his cost.

The risk can be avoided by using the battery condition indicator described here, as this can be set to indicate a dangerously low battery voltage which need not be much lower than the ordinary working voltage of the battery. The battery can then be changed in


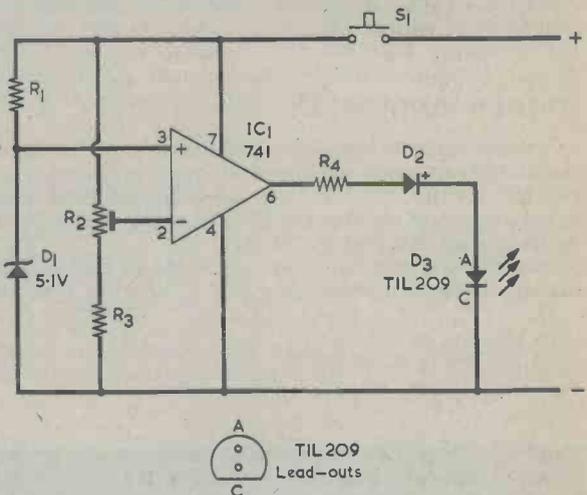


Fig. 1. The circuit of the battery condition indicator. The output of the 741 integrated circuit goes abruptly positive and lights the l.e.d. when the supply voltage falls below a pre-set threshold level

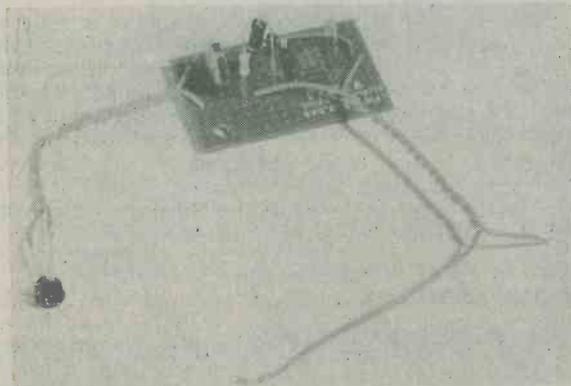

The battery condition indicator is wired up on a Veroboard panel. The l.e.d. couples to this via a 2-way flexible lead

time, even though the main equipment may have shown no signs of a failing battery.

The prototype has been included in a short wave converter which falls into the category just described, and it has proved to be very successful in use.

The device can also be used to advantage in equipment having a zener diode voltage stabilizing circuit with no means of monitoring the zener voltage. Many items of test equipment whose accuracy depends upon the provision of a constant stabilized supply voltage fall into this class. It is quite possible for the battery voltage to fall to a level which is too low to allow the zener diode to exert control, and the test equipment may then give misleading indications. Such a possibility can be eliminated by the fitting of the battery condition indicator.

CIRCUIT OPERATION

A 741 operational amplifier forms the basis of the unit, as can be seen in the circuit diagram given in Fig. 1. The 741 is employed as a voltage comparator.

The non-inverting input of the 741 is connected to the zener reference source given by zener diode D1. The diode is coupled to the positive rail via R1. The inverting input of the 741 is fed from a potential divider connected across the supply rails. A light-emitting diode, D3, is coupled to the output of the i.c. by way of current limiting resistor R4 and diode D2.


To give an example of circuit operation, let us assume that the device is to be set to indicate a fall in voltage to 10.2 volts and that the reference voltage given by D1 is exactly 5.1 volts. For this, R2 would be adjusted so that the voltage at the inverting input of the 741 is half the supply voltage. The output voltage of the i.c. is equal to the potential difference across its two inputs multiplied by its voltage gain. The 741 has a voltage gain of many thousands, and so a potential difference of less than a millivolt is required across the inputs to result in the output swinging either fully positive or fully negative.

When the supply voltage is higher than 10.2 volts the inverting input will be positive of the non-inverting input. The i.c. output will therefore be swung fully negative and the l.e.d. will not light. When the supply falls just fractionally below the 10.2 volt level the i.c. inverting input will be slightly negative of the non-inverting input, and the output of the i.c. will swing fully positive. In consequence the l.e.d. will light, so indicating that the supply voltage has fallen to the pre-set threshold level. The l.e.d. can, of course, be made to light at other pre-set voltages by making the requisite adjustment to R2.

D2 is included in the circuit as the voltage from the i.c. when the output is fully negative is approximately 2 volts. This is sufficient to cause the l.e.d. to become lit. The voltage drop of about 0.6 volt across D2 reduces this output level to a voltage which is just too low to light the l.e.d. D2 may be any silicon diode or small silicon rectifier capable of passing some 20mA forward current. The author used a BAY31 in the prototype.

Although the current drain of the battery condition indicator is not excessive, it is nevertheless shown as being connected to the supply via a push-button switch. Thus, no current at all is consumed unless the switch is depressed. The battery can conveniently be tested before and after each session during which the supplied equipment is employed.

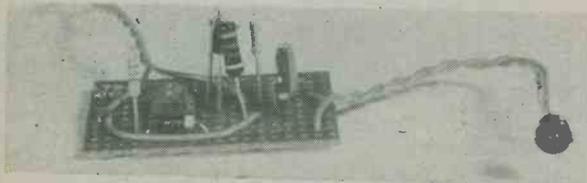The indicator can, alternatively, be connected permanently across the supply lines if preferred. The current consumption with the l.e.d. not lit is approximately 0.5mA at 6 volts, rising to about 1.5mA at 15 volts. When the l.e.d. is lit the current consumption becomes about 4.5mA at 6 volts rising to some 14mA at 15 volts.



Another view of the battery condition indicator. As may be seen, construction is simple and few components are required

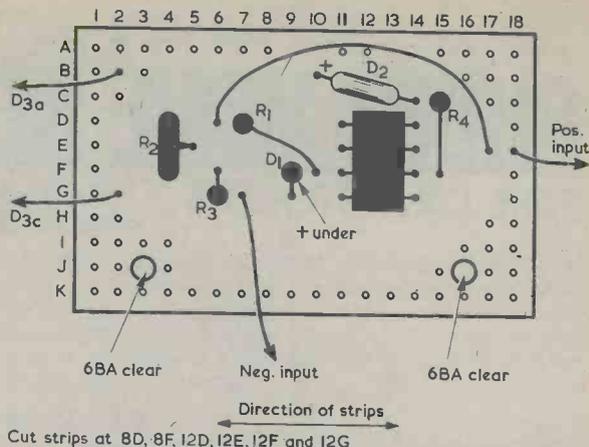


Fig. 2. The components are assembled on a small piece of Veroboard as shown here

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

R1 8.2k Ω

R2 1M Ω pre-set potentiometer, miniature skeleton, vertical

R3 470k Ω

R4 680 Ω

Semiconductors

ICI 741 in 8 pin d.i.l. package

D1 BZY88C5V1

D2 BAY31 or similar (see text)

D3 TIL209, with panel holder

Switch

S1 push-button, press to close (see text)

Miscellaneous

0.1in. pitch Veroboard, 18 holes by 11 strips

Connecting leads, etc.

CONSTRUCTION

With the exception of S1 and D3, the components are assembled on a 0.1in. pitch Veroboard having 18 holes by 11 copper strips. Complete details of this panel are shown in Fig. 2.

Commence construction by cutting out a panel of the specified size and then make the six breaks in the copper strips. Drill the two 6BA clear mounting holes with a No. 31 twist drill. The various components and the link wire can then be soldered in, leaving the i.c. until last. No socket for the i.c. was used on the prototype, although one can be employed if desired. No connections are made to pins 1, 5 and 8.


Finally, connect the l.e.d. and the leads which couple to the monitored supply lines.

SETTING UP

The only adjustment that is required is to give R2 a setting which causes the l.e.d. to light up at the required threshold voltage. The simplest way of achieving this is to connect the unit to a voltage which is equal to that at which it is desired the l.e.d. should turn on. Then R2 is adjusted as far in an anti-clockwise direction (when viewed from the side at which the l.e.d. connections are taken) as is possible without D3 becoming extinguished.

SHORT WAVE NEWS

FOR DX LISTENERS

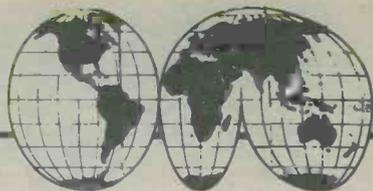

Times = GMT

Frequencies = kHz

By Frank A. Baldwin

In the August issue of this magazine readers of this feature will have read of the 90 metre band Dx that may be heard and have noted some of the stations currently being reported in the SWL press. It was pointed out that, although the 60 metre band is the favourite hunting ground of many broadcast band Dxers, others produce very good results on the aforementioned band despite the increased commercial interference. However, Dx transmissions may be heard on other bands and therefore the attention of followers of this monthly series is now directed on the next band up the dial — the 6MHz band.

6MHz DX

This band (49 metres) extends from 5950 to 6200kHz and within these limits, especially during late night and early morning sessions, many exciting transmissions may be logged. Recently, for instance, we heard Sierra Leone Broadcasting Service at Freetown on 5980 with a newscast in English and sign-off with the National Anthem at 2330.

Some of the stations reported are Radio Cultural, Guatemala on 5955 around 0430; R.TV Dominicana on 5970 at 0130; Radio Reloj, Costa Rica on 6006 at 0030; La Voz del Tolima, Colombia on 6040 at 0130; Radio Nacional, Buenos Aires on 6060 at 0100; La Voz del Llano, Colombia on 6115 at 0100; Radio Union, Lima on 6115 at 0130 and Radio Suyapa, Honduras on 6125 at 0130.

More convenient times would probably be 1630 RRI Jakarta, Indonesia on 6045 or 1900 Mozambique on 6050.

CURRENT SCHEDULES

The schedules published here are correct at the time of writing but sudden changes are sometimes made, the details of which cannot be included in some cases owing to the printing schedule of the magazine. Every effort is made to ensure that the information given is reliable, both from published schedules issued by various organisations and from our own observations. Where practicable, schedules are confirmed during listening sessions but obviously this is not possible with some of them.

● EGYPT

From Cairo, the Arab Republic of Egypt Broadcasting Corporation radiates an Overseas Service in English to Europe from 2145 to 2300 on 9805. Other broadcasts in English are as follows — from 0200 to 0330 to North America on 9475; to South East Asia from 1315 to 1430 on 17920; to East, Central and South Africa from 1515 to 1600 on 17725; to Central and South Africa from 1715 to 1830 on 17890 and to East, Central and South Africa from 2030 to 2200 on 17725. The broadcasts to Africa are announced as "The Voice of Africa".

● IRAQ

"Radio Baghdad" has an external Service in English to Europe from 1930 to 2020 on 9745.

● CUBA

"Radio Havana" offers an External Service in English to Europe from 2010 to 2140 on 11715.

● HUNGARY

"Radio Budapest" is in English to Europe from 1200 to 1240 Mondays to Fridays on 6025, 7155, 7220, 9585, 11910, 15160 and on 17780; from 2130 to 2200 on 5965, 7180, 9655, 9833, 11910, 15125 and on 17780. The Dx programme in English is from 1515 to 1530 on Tuesdays and Fridays on 6025, 7155, 9595, 9833, 11910, 15125 and on 17780.

● CZECHOSLAVAKIA

"Radio Prague" presents programmes in English to the UK from 1630 to 1700 on 5930 and 7345; to the UK and the Middle East from 1900 to 1930 on 5930, 7245 and on 7345; from 2000 to 2030 to the UK on 5930 and 7345 and from 2130 to 2200 on 6055.

The Radio Prague "Inter-Programme" in English to Europe may be heard from 0745 to 0800; 0845 to 0900; 0945 to 1000; 1045 to 1100 and from 1145 to 1200 all on 6055 and 9505. The "Inter-Programme" to Europe and North America may be heard from 0030 to 0100 on 6055 and 9740.

● SWITZERLAND

The "Overseas Service of S.B.C.", Berne, offers programmes in English as follows — from 0700 to 0730 to Australasia, Far East, South and Southeast Asia and Europe on 3985, 6165, 9535, 9590, 11775, 15305 and on 17840; from 1100 to 1130 to Africa and Europe on 3985, 6165, 9535, 15140, 15305, 17830 and 21520; from 1315 to 1345 to the Far East, Australasia, Southeast Asia, North and Central America and Europe on 3985, 6165, 9535, 11775, 15140, 15430, 17830 and 21520; from 1530 to 1600 on 3985, 6165, 9535, 15430, 17830 and 21520; from 2100 to 2130 to Africa and Europe on 3985, 6165, 9535, 9590, 11720, 11870 and 15305.

● ALBANIA

"Radio Tirana" radiates programmes in English to Europe from 0630 to 0700 on 7065 and 9500; from 1630 to 1700, 1830 to 1900, 2030 to 2100 and from 2200 to 2230 all on 7065 and 9480.

● BULGARIA

"Radio Sofia" has English transmissions directed to the UK and Eire from 1930 to 2000 and from 2130 to 2200 on 6070 and 9700. Other English programmes are as follows — to North America from 0001 to 0100 on 9700; to East and Central Africa from 1930 to 2000 on 15310 and 17825 and to Africa from 2105 to 2130 on 11730, 11765, 15310 and on 17825.

● EAST GERMANY

"Radio Berlin International — the Voice of the GDR", Berlin, presents an English service to Europe from 1730 to 1815 and from 2115 to 2200 on 7260; from 1830 to 1915 on 6080, 6115, 7185, 7300 and on 9730. Radio Berlin International is also in English from 1200 to 1245 to Southeast Asia on 11960, 15125 and 15320; from 1315 to 1400 to Central Africa on 17800, from 1400 to 1445 to Southeast Asia on 11960 and 15125; from 1530 to 1610 to Southeast Asia on 11960; from 1815 to 1900 to East and West Africa on 15170, 15255 and on 15390 and to West Africa from 2000 to 2045 on 15250 and 15390.

● JAPAN

"Radio Japan", Tokyo, radiates in English to Europe from 0800 to 0830 on 15390 and 15430 and from 1830 to 1900 on 9735 and on 11960.

● ROMANIA

"Radio Bucharest" maintains an External Service in English to Europe from 1300 to 1330 on 7195, 9690 and on 11940; from 1930 to 2030 on 7225 and on 9510 and from 2100 to 2130 on 7195 and on 9690.

● POLAND

"Radio Warsaw" operates an External Service in English for Europe from 0630 to 0700 on 7285, 9540 and 9675; from 1200 to 1230 on 7285 and 9540; from 1600 to 1630 on 6095, 7125, 7285 and on 9540; from 1830 to 1900 on 6095, 7125, 7285 and on 9540; from 2030 to 2100 on 7285 and 9540 and from 2230 to 2300 on 5995, 6135, 7285 and on 9540.

AROUND THE DIAL

● GHANA

Ejura at 2000 on 3350, interval signal of African drums, identification in English then time-check for "eight o'clock". This service is in both English and vernaculars, the weekday schedule being from 1600 to 2305, power is 20kW.

● GAMBIA

Banjul at 2055 on 4820, African drums, local music, announcements and newscast in vernacular at 2100. The evening schedule of this one (weekdays) is from 1625 to 2300 and the power is 3.1kW; not an easy one to log owing to a high powered USSR transmitter on the same channel.

● NIGERIA

Lagos at 1837 on 4990, newscast by OM in vernacular, several mentions of Kampala and Angola; musical interlude at 1840. This is the National Programme with an evening/afternoon schedule from 1500 to 2305, power is 10kW.

● ZAIRE

Lubumbashi at 1848 on 4750, OM with a talk in vernacular interspersed with local music and drums. This is the Home Service with the scheduled afternoon/evening transmission from 1500 to 2100 (weekdays). The power is 10kW and it is not an easy one owing to the surrounding commercial QRM.

● INDIA

All India Radio, Delhi, at 1910 on 3905, Arabic-type music, announcements by OM in Arabic, off the air suddenly at 1930, without National Anthem. This is the Home Service Arabic transmission, the power is variable from 20 to 100kW.

● SOUTH AFRICA

Johannesburg at 1900 on 3285, OM with a newscast in English after 6 pips time-check and station identification. This is the English Service which is on this channel from May until October the evening schedule (weekdays and Sunday) being from 1620 to 2115, Saturdays from 1620 to 2205, the power being 100kW.

● CHINA

Radio Peking at 2100 on 4800, YL in Chinese and short interludes of local music. This is the Home Service 1, the schedule being from 2000 to 0100, power variable from 120 to 240kW.

● LESOTHO

Maseru at 1854 on 4800, OM in vernacular, Euro-style pop records, YL announcer at 1900 then into programme of local pops. Tending to be irregular, Maseru reportedly has a schedule from 0400 through to 2030 (Sundays to 2135). The power is 10kW and the channel is subject to severe commercial QRM at times.

● LIBERIA

ELWA Monrovia at 2156 on 4770, OM with a religious programme in English.

Trade News . . .

MINI-BLOW TORCH BY FLAMINAIRE

The feature that distinguishes the Longs Mini-Blow Torch from any other similar product is its pencil point slim flame. This unique feature enables the user to concentrate the heat exactly where it is wanted and is invaluable to electronic engineers.

The 35gms butane gas cylinder has a life of 4-5 hours operating temperature up to 3,500°F. Refills are readily available.

The gas burner is fitted with a brass nozzle and has special cooling fins. It is the clever engineering of this burner that produces the unique pencil point flame.


A detachable solder pencil is included in the kit and its use can be readily appreciated.

The present cost of a Longs Mini-Blow Torch is £6.25 incl. VAT and p.p.

Details from Longs Ltd., Hanworth Lane Trading Estate, Chertsey, Surrey.



QUICK-DRI ETCH-RESIST MARKING PEN

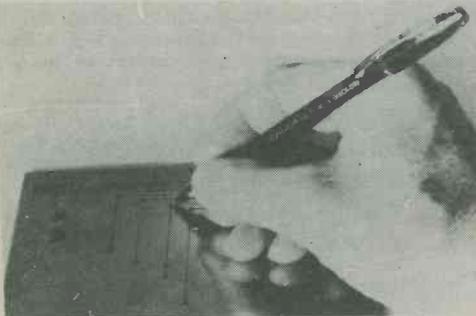

The unique Decon-Dalo 33 PC etch-resist marking pen for preparing printed circuit boards has been very well accepted by electronics engineers, both professional and amateur, since it was first offered by

Decon Laboratories some three years ago. A new improved version in the form of the 33 PC Quick-Dri is now available. As the name implies, the major improvement is a newly formulated etch-resist ink with rapid drying characteristics. It is necessary simply to draw the desired printed circuit on to a copper-clad board, allowing the track to dry for just two minutes before etching in ferric chloride or any other usual etching solution. A high degree of resistance to etchants is claimed and a professional high-quality board can be prepared very simply.

The Decon-Dalo 33 PC Quick-Dri is priced at £1.08 for 1, £4.43 for 6 or £8.80 for 12 (postage and VAT included), either direct from Decon or from radio supplies retailers.

Full details are available from Decon Laboratories Ltd., at Ellen Street, Portslade, Brighton, Sussex. BN4 1EQ.

MINIATURE MAGNIFIER FOR CLOSE SCRUTINY WORK

A unique miniature magnifier for precise, close scrutiny work, has been introduced by Northgate Instruments of 19 London Road, Gloucester. The magnifier easily attaches to tweezers, probes, scrapers or scalpels and features 8X magnification. It is fully adjustable with a $\frac{3}{4}$ " diameter (20mm) pivoting lens.

The new miniature instrument complements the comprehensive Northgate range of microscopes and magnifiers, varying from a pocket microscope with 30X magnification to a robust table-top magnifier with a 2-4X magnification.

Detailed literature and price lists are available on application to: Northgate Instruments Ltd., 19 London Road, Gloucester.



In your work-shop

This month we find Smithy the Serviceman on the point of completing a novel resistance measuring bridge with a range of 1Ω to $1M\Omega$. As always he is accompanied, for most of the time at any rate, by his able assistant, Dick.

"That's it!" called out Dick exuberantly. "Work's finished for today!"

Cheerfully, he turned off the switch that controlled all the mains outlets on his bench, divested himself of his overall coat and hung it on the hook behind the Workshop door.

"Blimey," remarked Smithy, glancing up at the clock, "you're in a hurry, aren't you? Not a nanosecond

after packing-up time and you're already set for the off."

"Ah," said Dick, putting on his jacket, "I don't want to be late getting away today."

"Why's that?"

"I've got a heavy date," replied Dick happily, "and she doesn't like being kept waiting."

PRIVATE JOB

"In that case," remarked Smithy, "I'd be the last person to hold you back."

"I wonder," remarked Dick tentatively, "if you could give me a lift as far as Joe's Caff. I said I'd meet her there, and Joe's Caff is on your way home."

"Well, I would normally," said Smithy, "but I'm afraid I'll be hanging on here for quite a bit yet."

"Fair enough," said Dick carelessly "I'll walk it instead. Cheers for now, Smithy."

"Cheerio."

Dick opened the Workshop door, then turned round as a thought struck him.

"Why're you staying late?" he asked, puzzled. "We're well ahead so far as work is concerned."

"I'm not doing any more servicing," said Smithy. "What I'm going to do is put the finishing touches to a little private job for myself."

"I see," said Dick. "Well, cheers for now, then."

"Cheerio."

But Dick seemed reluctant to depart. His ever active curiosity had been aroused.

"Er, what sort of a private job, Smithy?"

"A piece of test equipment," explained Smithy, as he cleared a working space on his bench. "It's a resistance measuring bridge."

"Just a resistance measuring bridge,

eh?" repeated Dick. "Well, that doesn't sound very exciting."

"It's got a few novel features in it," added Smithy. "For instance, it takes advantage of a circuit arrangement that was used recently by G. A. French in a 'Suggested Circuit'. And the null indicator incorporates an idea that originated in Australia."

"Does it, indeed?" said Dick musingly.

He glanced at the clock.

"Blow me," he exclaimed. "I really must rush now. Cheers then, Smithy."

"Cheerio."

The door closed behind his assistant, leaving Smithy alone in the now quiet Workshop. He opened the cupboard below his bench and produced a small metal case which he placed fondly on his bench. Visible on its front panel were two pointer knobs, one with a temporary paper scale behind it, a toggle switch, two light-emitting diodes and two insulated terminals. Smithy turned the case over, removed its back, then pulled a cardboard box with a few small resistors in it towards him. Contentedly, he took up one of the resistors, and started to wire it into the circuitry inside the metal case.

Just as he was returning his soldering iron to its rest, the Workshop door clattered open. Smithy turned round.

"Blimey, are you back?"

"I couldn't help wondering," said Dick in an irritated tone, "just exactly what those novel features in your resistance bridge were."

"Well," said Smithy, "there's a basic Wheatstone bridge set-up together with an unusual means of null indication. I'll show you what I mean. To start off with, I hardly need to tell you that a Wheatstone bridge consists basically of four resistors connected up like this."

Smithy pulled his note-pad towards him and quickly drew out a circuit. (Fig. 1(a).)

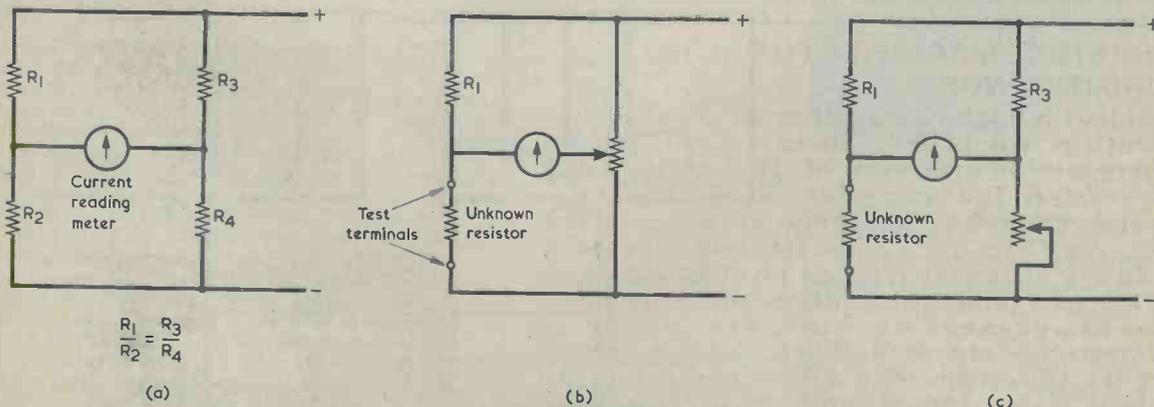


Fig. 1 (a). The Wheatstone bridge. Balance is given when the equation is satisfied

(b). Changing the two right hand resistors for a potentiometer allows the bridge to measure resistance

(c). Another version of the bridge when used for resistance measurement

"Two pairs of the resistors are connected across a d.c. supply with a null indicating device between them like I've shown here," he went on. "I've drawn a centre-zero current-reading meter as the null indicating device, and the bridge is said to be balanced when the resistance values are such that no current flows through the meter, whereupon it indicates zero. I've marked the resistors R1 to R4 and balance is given when the ratio of R1 to R2 is the same as the ratio of R3 to R4. Which is another way of saying that R1 divided by R2 equals R3 divided by R4. With this relationship between the resistors, both terminals of the meter are at the same potential and no current passes through it."

"I can see that," said Dick impatiently. "If you incorporate a potentiometer instead of having all the resistors fixed, then the circuit becomes capable of measuring resistance, doesn't it?"

"That's right," agreed Smithy. "A common approach here consists of replacing two of the resistors by a potentiometer. Like this."

Smithy sketched out a second circuit. (Fig. 1(b).)

"This arrangement," he continued, "has the advantages of simplicity and wide range. It is obvious that if the bridge balances when the slider of the pot is at the centre of its track, then the value of the unknown resistor is the same as R1 in my circuit. If the bridge balances when the slider of the pot is a third of the way up its track then there is twice as much track resistance above the slider than there is below it, and this will indicate that the unknown resistor has half the value of R1."

"In other words," put in Dick quickly, "there is twice as much resistance above the left hand meter terminal as there is below it."

"That's right," confirmed Smithy. "It is possible to provide a scale for the pot which is graduated in terms of the value of the unknown resistor. You connect the unknown resistor to the circuit, adjust the pot until you reach the null point where there is zero current in the meter and then read the value of the unknown resistor from the pot scale."

"That seems fair enough," said Dick. "Does that circuit have any snags?"

"The only drawback," said Smithy, "is that the pot scale is non-linear, and the readings get cramped at one end. I've used a different bridge circuit in my own little gadget. Here's the general idea."

Smithy drew another circuit. (Fig. 1(c).)

"What's the advantage here?"

"The circuit gives a linear pot scale," replied Smithy. "Let's say, for a start, that R1 and R3 in the circuit

are equal in value. The bridge will then balance when the resistance inserted by the pot is equal to the unknown resistance. If the pot has a linear track the amount of resistance it inserts into circuit is proportional to spindle rotation, and so you get a linear pot scale. If, next, you give R1 a value that is 10 times the value of R3 then you can use the same pot scale as you had previously, with all the readings on the scale multiplied by 10. Got it?"

BRIDGE CIRCUIT

"Yes, yes," said Dick restlessly. "Now how about getting on to the actual bridge circuit you used yourself?"

Smithy sketched a further circuit. (Fig. 2.)

"This is the basic set-up," he stated. "As you can see, there are six ranges, and I'll start off with the highest resistance one first. This is given when the switch is set to Range 6. The right hand side of the bridge then consists of a 20kΩ fixed resistor and a 20kΩ pot, whilst the left hand side consists of a 1MΩ fixed resistor and the unknown resistor. This resistor will be connected to the two test terminals."

"Well," said Dick, gazing at the circuit, "it's obvious that the maximum unknown resistance you can measure is 1MΩ, as balance will then occur when the slider of the pot is at the top end of its track. This will give 1MΩ and 1MΩ on the left hand side of the bridge, and 20kΩ and 20kΩ on the right hand side of the bridge. What's the lowest resistance you can measure, Smithy?"

"In theory, it's proportional to the lowest resistance that can be resolved by the pot. I've made an arbitrary choice of 100kΩ here, which is given when the 20kΩ pot inserts 2kΩ, so that the whole range with the switch in position 6 is 1MΩ down to 100kΩ."

"It could go lower though, couldn't it?"

"Oh yes," said Smithy. "But this 10 to 1 relationship combines nicely with the next range, which is 100kΩ down to 10kΩ. Also the fact that you can adjust the pot for readings on Range 6 below 100kΩ means that you can take the pot through the 100kΩ setting. It's always nice to be able to go a little beyond the final setting when you're adjusting a bridge."

"But," protested Dick, "you haven't allowed for that at the maximum resistance end of the range. If the pot has a value of 20kΩ the very highest reading you can get on Range 6 is exactly 1MΩ."

"True," agreed Smithy. "But don't forget that this circuit only shows the basic bridge. In the practical circuit, which you'll see in a moment, I've given the pot a value that is a little higher than 20kΩ, so that you can go through the maximum resistance setting as well. Now, there's another point I want to bring out, and that concerns the voltage on the upper test terminal. If a 1MΩ resistor is connected to the test terminals on Range 6, then the voltage on the upper test terminal is half the supply voltage. The supply voltage happens to be 9 volts, and so the upper test terminal is then at 4.5 volts relative to the bottom supply rail. If a 100kΩ resistor is connected to the test terminals then the voltage on the upper terminal is one-eleventh of the supply voltage which is, near enough, 0.82 volts. So, on Range 6, the null indicator is presented with voltages ranging from 4.5 volts above the lower supply rail down to 0.82 volt. Okay?"

"Sure," said Dick, entirely absorbed in Smithy's circuit. He had, already, completely, forgotten his assignment at Joe's Caff.

"As I've just mentioned," continued Smithy, "the next range down, Range 5, gives 100kΩ to 10kΩ. This is

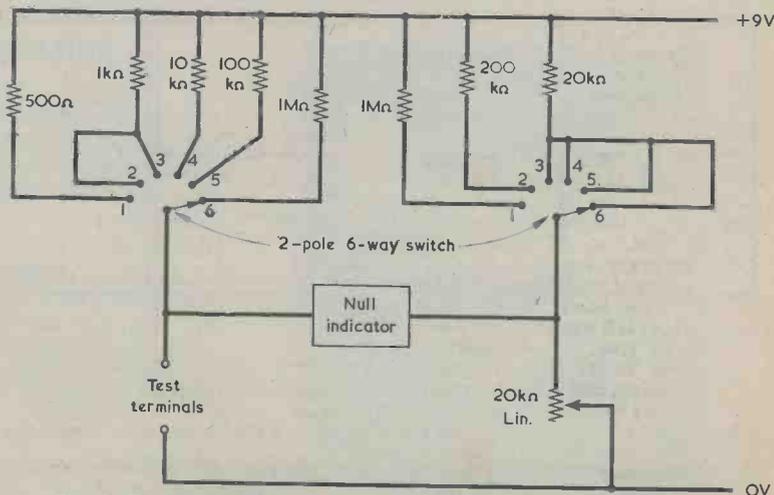


Fig. 2. The basic bridge section of the instrument constructed by Smithy

because the upper resistor on the left hand side of the bridge has been changed from 1M Ω to 100k Ω . Following from this, Range 4 gives 10k Ω to 1k Ω and Range 3 gives 1k Ω to 100 . In all these ranges, the voltage on the upper test terminal varies between 4.5 and 0.82 volts."

"Range 2," said Dick in a thoughtful tone, "is different. You've still kept the 1k Ω upper resistor on the left hand side, but you've changed the right hand upper resistor from 20k Ω to 200k Ω ."

"That's right," said Smithy. "The 1k Ω upper resistor is retained on the left hand side to keep current low in the test resistance. With R2 at this value, the maximum current which can flow with the test terminals short-circuited is 9mA. Changing the upper right hand resistor from 20k Ω to 200k Ω means that the bridge balances for test resistances that are one-tenth of the corresponding resistances on Range 3. So Range 2 measures test resistances from 100 Ω down to 10 Ω ."

Dick picked up the first of Smithy's sketches and looked critically at the equation written on it.

"Why, yes of course," he said after a moment's consideration. "Multiplying the top right hand resistance by 10 is the same as dividing the bottom left hand resistance by 10. Wait a minute, though, there's something that's just struck me."

"What's that?"

"On Ranges 3 to 6," said Dick, "the voltage on the upper test terminal varies from 4.5 to 0.82 volts. Won't the voltage variation be lower on Range 2?"

"It will be," confirmed Smithy. "If the test resistance is 100 Ω the upper test terminal voltage is 0.82 volt, and if it's 10 Ω the terminal voltage is approximately 0.09-volt. Now, let's move the switch on to Range 1. The upper right hand resistor is now changed to 1M Ω , and the upper left hand resistor to 500 Ω . Compared with Range 2 the upper right hand resistor is multiplied by 5 and the upper left resistor is divided by 2. So the range of test resistances at which the bridge will balance is the same as those for Range 2 divided by 10, and that comes out to 10 Ω down to 1 Ω ."

"I suppose," said Dick musingly, "you've made the upper left hand resistor 500 Ω to keep test resistor current low on this range as well."

"That's right," stated Smithy. "I've put an arbitrary top limit of 1M Ω for any section of the bridge. If I made the upper right hand resistor 1M Ω then the upper left hand resistor has to be 500 Ω to give a test resistance range of 10 Ω to 1 Ω . This is quite a reasonable value, and it limits current flow in the test resistor to 18mA maximum."

"What about the voltages on the upper test terminal?"

"For the test resistance of 10 Ω ," replied Smithy, "the upper test terminal voltage will be about 0.18 volt. If

the test resistance is 1 Ω the terminal voltage will be 0.018 volt only."

"Blimey," said Dick, "those voltages are pretty low, aren't they?"

VOLTAGE COMPARATOR

"They are rather," agreed Smithy. "and because of this the null indicator needs to have a high level of sensitivity. A centre-zero meter could be used, but in these days of integrated circuit op-amps, a voltage comparator is much more attractive. Because the bridge arm resistances can go up to 1M Ω , the input resistance of the comparator must be considerably higher than that value. Now, I happened to see the idea of using an op-amp comparator in a Wheatstone bridge in the Australian journal *Electronics Australia*, and all credit is due to that journal for this scheme and for a neat circuit which is used at the op-amp output. In the *Electronics Australia* circuit the two arms of a bridge go directly to the inverting and non-inverting inputs of a 741 op-amp and the output is monitored by two l.e.d.'s. In the circuit I've made up for myself the two arms of the bridge go to the op-amp inputs via silicon emitter follower transistors, which present an extremely high input resistance at their bases. And this idea came to me after reading a recent 'Suggested Circuit' by G. A. French in which he used an emitter follower in front of a 741 op-amp to produce a very high resistance electronic voltmeter. The 741 had its output connected back to its inverting input to make it a voltage follower, and the emitter of a BC107 coupled into its non-inverting input." (Fig. 3.)

"Ah yes," said Dick thoughtfully, "I remember that circuit. It appeared quite recently, didn't it?"

"Just a few months ago," said Smithy ruminatively. "Now, what was the date of the issue? Why yes, the date was last July."

Dick suddenly blanched and gave a strangled groan.

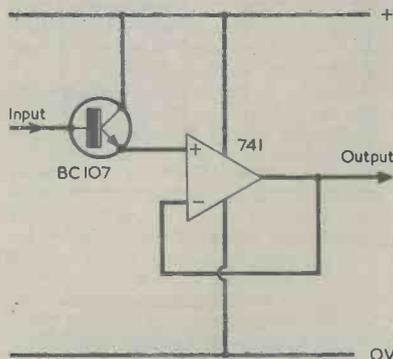


Fig. 3. Coupling a silicon transistor emitter follower to an op-amp input results in a very high input impedance. Here the transistor and the op-amp form a composite voltage follower

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP
Tel: 01-723 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS
LONDON, W.10
Tel: 01-969 3657

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.
70-72 Holdenhurst Road
Bournemouth
Telephone 25232
Closed all day Wednesday

SURREY

WITWORTH TRANSFORMERS

TV Line out-put transformers
Manufacturers of the largest range in the country. All makes supplied.

Modern
BAIRD, BUSH, GEC, PHILIPS
Replacement types ex-stock.
For "By-return" service, contact
London 01-948 3702

Tidman Mail Order Ltd., Dept. R.C.
236 Sandycombe Road,
Richmond, Surrey TW9 2EQ

Callers welcome.

Your Local Supplier

SUSSEX

JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO,
MARCONI, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish
enthusiasts we supply
Radio & Electronics
Constructor
Data Books and
Panel Signs Transfers
Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

RADIO & ELECTRONICS CONSTRUCTOR

ANNUAL
SUBSCRIPTIONS
to this magazine
may be obtained
through your
newsagent
or direct from the
publishers
ONLY £4.00
per year, post free

Please send remittance with name
and address and commencing issue
required to:

DATA PUBLICATIONS LTD
57 Malda Vale London W9 1SN

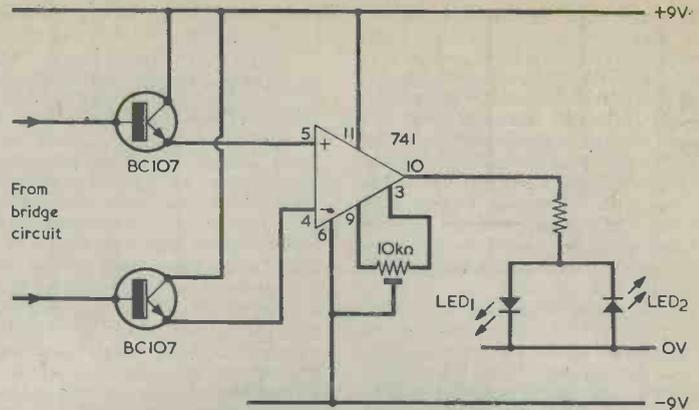


Fig. 4. The null indicator circuit. The i.c. pin numbers apply to the 14 pin encapsulation

"Date!" he repeated, standing up and rushing towards the door. "Date! Ye gods, she'll murder me. Cheers, Smythy!"

"Cheerio," called out Smythy to his assistant's fleeting back.

Left to himself Smythy philosophically picked up his soldering iron and proceeded to solder a further resistor in his resistance bridge. As he picked up the final resistor to be wired in, the knob of the Workshop door rattled. Smythy turned round.

"What, again?"

"It's no good," wailed his assistant, as he re-entered the Workshop. "I got half-way down the street and I found that I just had to find out how you connected those emitter followers to the op-amp."

"Well," chuckled Smythy, "I've heard of people being devoted to a subject but this is really ridiculous."

"It's my darned curiosity," complained Dick. "I get so flaming curious about electronic things that I just can't leave them till I've seen them right through to the end."

"Okay then," grinned Smythy. "I'll put you out of your misery and show you how I coupled the two emitter followers to the 741 inputs."

Smythy sketched out a further circuit. (Fig. 4.)

"As you can see," he continued, "the two inputs from the bridge go to the bases of two BC107's, and their emitters couple to the non-inverting and inverting inputs of the 741. It has been found by experience that the input resistances at the bases of the BC107's in a circuit like this are well in excess of 1MΩ, although this does involve the assumption that the transistors have lower leakage resistances than are quoted in their specifications. The voltage at each emitter is equal to that at each base less the voltage dropped in the base-emitter junction."

OUTPUT CIRCUIT

"What's that circuit at the i.c. out-

put? The one with two l.e.d.'s in it?"

"Those l.e.d.'s are used to indicate balance," explained Smythy. "As I said just now, this arrangement was employed in the *Electronics Australia* circuit. Let's assume for the moment that the input offset voltage for the op-amp is zero. When, under this condition, the non-inverting input of the op-amp is positive of the inverting input, the output of the op-amp swings positive and LED1 lights up. Similarly, when the non-inverting input goes negative of the inverting input the output swings negative and LED2 lights up. An interesting feature of the circuit is that the forward voltage appearing across the illuminated l.e.d. prevents the maximum reverse voltage rating of the non-illuminated l.e.d. being exceeded."

"Gosh, that's neat," said Dick. "I suppose you balance the bridge so that both l.e.d.'s are extinguished. This would occur when the op-amp output is zero."

"Adjusting for no illumination would be feasible if the pot in the bridge had very high resolution," replied Smythy. "However, there's so much gain in the op-amp that the closest you can get to this point with an ordinary pot is a setting at which an extremely slight movement of the slider causes one l.e.d. to extinguish and the other to come on. So you adjust for the point of changeover in the l.e.d.'s. If you introduce some noise in the system by, say, touching the test resistance on Range 6, you can arrive at a condition where both l.e.d.'s light up at a single setting of the pot, but all this really means is that you should keep your fingers away from the test resistor when you're measuring high values!"

"I see that you've connected a 10kΩ pot to pins 9 and 3 of the op-amp."

"Ah yes," said Smythy. "That's for offset null adjustment. In practice, we can't ignore the input offset voltage. As we saw just now, the voltages applied to the comparator circuit on Ranges 1 and 2 are very low, and an offset null

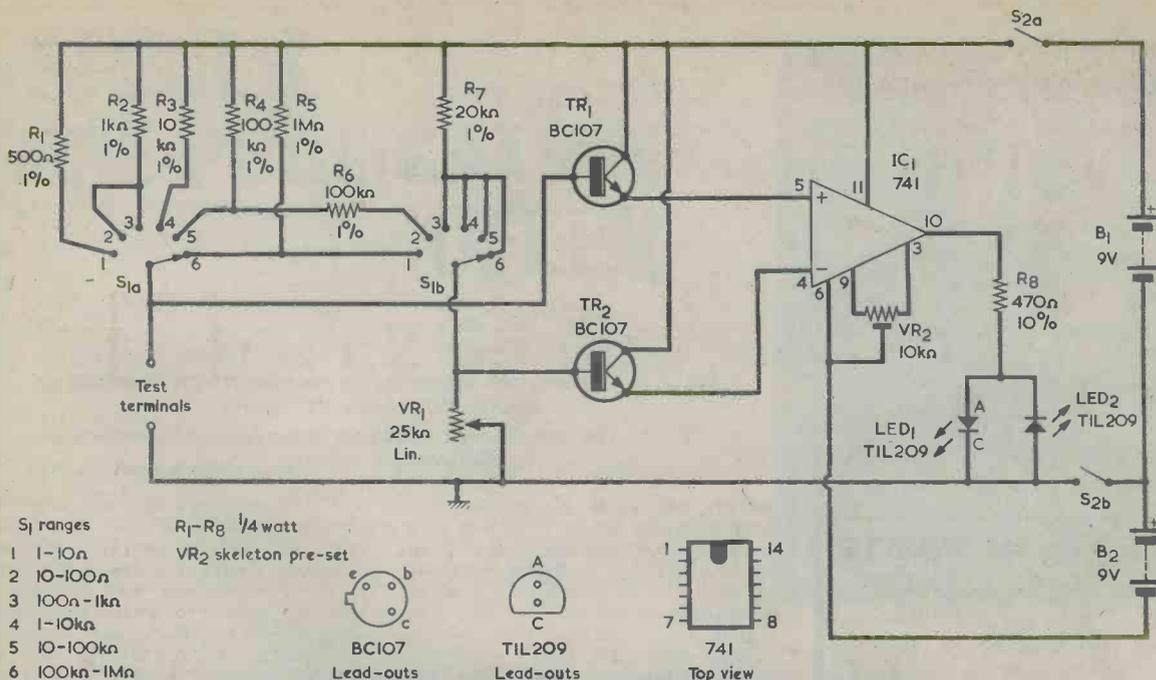


Fig. 5. Complete circuit of the bridge. The current drawn from each battery varies between about 1mA and 9mA according to which l.e.d. is illuminated. An additional current due to the bridge section is also drawn from battery B1

adjustment is essential to ensure that the op-amp output is at zero when both the transistor bases are at exactly the same potential. What we do in this case is make an offset null adjustment that takes in the two transistors as well as the op-amp."

"After all this introduction," stated Dick, "I reckon it's time I had a look at the complete circuit of the bridge."

"As you wish," said Smithy obligingly.

He reached to the back of his bench and produced a piece of paper on which a circuit had already been drawn out. (Fig. 5.)

"Here you are," he said proudly. "This is the complete circuit. It's the same as the bits I've been showing you except for some slight changes in the bridge section. I've saved one close-tolerance 1MΩ resistor by having R5 common to both Range 6 and Range 1. And the upper right hand 200kΩ resistor for Range 2 is given by R4 and R6 in series."

"Why did you do that, Smithy?"

"Partly," replied Smithy, "because it's a little easier to get hold of close-tolerance 100kΩ resistors than it is to obtain close-tolerance 200kΩ resistors. But the main reason is that R6 can be left out during initial setting up. It can be used to obtain the '1' and '10' calibration points on the pot scale, after which it's wired into the circuit."

"You've given the pot a value of 25kΩ instead of 20kΩ."

"True," confirmed Smithy. "You may remember that we said that the bridge pot needed a value slightly higher than 20kΩ. It's for this reason

that I chose 20kΩ for the basic value in the first place, because it is possible to obtain pots in practice which have nominal values of 22kΩ or 25kΩ. Now, the normal tolerance on resistance of the usual type of low cost pot is 20%, so you're bound to get a value of 20kΩ in it if its nominal value is 25kΩ. If you're using a better class type of pot with a closer tolerance on its track resistance, you could employ one with a nominal value of 22kΩ."

"Can VR1 be an ordinary carbon track pot?"

"It can be," replied Smithy. "You'd get better long-term results, though, with a moulded track pot. Best of all would be a wire-wound pot. It should be wired up so that the resistance it inserts into circuit increases as its spindle is turned clockwise."

Smithy selected a further resistor from the cardboard box on his bench.

"Apart from R6," he announced, "this is the last resistor to go in. Do you want to stay for the setting-up operation?"

Dick looked at the clock and nodded forlornly.

"I might as well," he said glumly. "I've cooked my goose completely now so far as my date is concerned."

Smithy soon had the resistor soldered in place. He then took up a standard 470kΩ resistor, connected it to the test terminals of the bridge, selected Range 6 and switched it on. He turned the spindle of VR1 experimentally. The illumination of the l.e.d.'s changed over abruptly at a central setting of the potentiometer.

"Ah, good," he remarked, pleased.

"The comparator seems to be doing its job properly. I'll do a spot of offset nulling next."

He switched off the bridge, short-circuited the test terminals with a piece of wire and connected a test lead terminated in two crocodile clips across VR1. (Fig. 6.)

"That's got the two transistor bases down to chassis potential," he remarked. "Now let's set up VR2."

He switched on again, whereupon one of the l.e.d.'s lit up. Taking up a small screwdriver he carefully adjusted VR2 until he found a point where the l.e.d. illumination changed

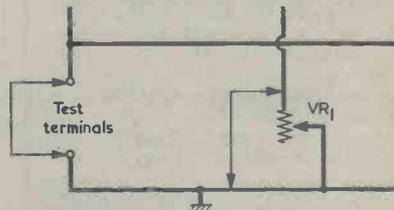


Fig. 6. The test terminals and VR1 are short-circuited for the offset null adjustment

over. He removed the two short-circuits.

"And that has got the offset null fixed up," he stated in a satisfied tone. "Calibration next!"

He took up the 100kΩ 1% resistor, shortly destined to become R6, and connected it to the test terminals. With the bridge still at Range 6, he next adjusted VR1 until the l.e.d.'s gave the



the audio amateur ?

The brain boggles at what old Johann could have done with his own console, preamp, 8-in-2 out mixer, octave equalizer, electrostatic speakers, or 24 inch woofer.

Come boggle with us.

the Audio Amateur

Yellow Oak Cottage
Tillington nr.
Hereford
HR48LQ

Send now for a free prospectus.

Name

Address

re

GAREX

Modulation transformers
Valve type 747, for 30W Tx £2.60
Transistor type, p/p NKT404 to QQV03-20a (or QQV03-10), with driver transformer to match - special offer - the two £1.45
Audio transformers - driver and output (2W) p/p NKT404 to 3Ω the two 70p NKT404 17p each, 4 for 60p
Mains transformer (multitap primary) 250-0-250V 200mA, 6-3V 5A, 5V 2A, fully shrouded, (suitable for 30W Tx - matching style to mod. transf.) £5.70
H.T. chokes 5H 80mA, 1-8H 125mA £1.10
Inverter Transformer Input 12V DC, output 170/380V 180mA £2.05
Relays GPO type 2400, 12V coil, 8A contacts, 4PCO or 2P make any 4 for £1.00
Neons min. wire end, 10 for 55p, 100 for £4.50
Slide Switches (new) min. DPDT 13p 2P3W 20p
PL259 UHF Plug 45p; Reducer 15p
BNC Free (cable mtg.) Socket "50Ω" 15p 12 ftr £1.30
Connection data supplied with transformers. Components are ex-equipment, in good condition, your satisfaction guaranteed.
Prices inclusive of UK Post, Packing and VAT at 25%
Mail order only Sole address:
GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH,
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 668684

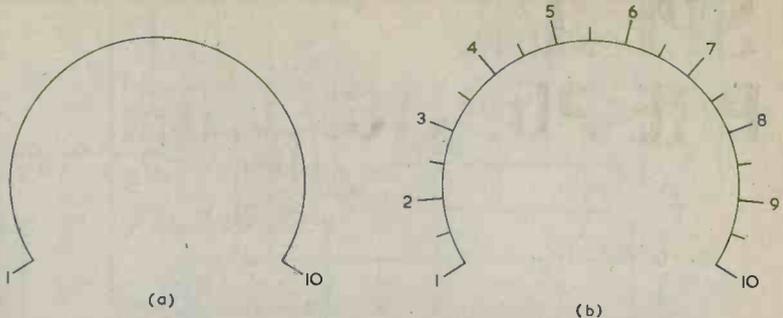


Fig. 7(a). The first step in marking up the scale for VR1 consists of finding the '1' and '10' points

(b). The scale is then filled in in linear fashion for the points between '1' and '10'

balance indication. He marked this point with the figure '1' on the temporary scale behind the knob of VR1. He then switched to Range 5 and re-adjusted VR1 for balance. This setting he marked on the scale as '10'. (Fig. 7(a).)

"And that's got the '1' and '10' points on the scale marked up," he said cheerfully. "Those two points will hold good on all the other ranges, and all I've finally got to do is mark out the intermediate values in linear fashion around the scale." (Fig. 7(b).)

A VISITOR

Smithy switched off the bridge and turned it over in order to instal the 100kΩ resistor in its final, R6, niche. There was a peremptory knock on the door. Frowning, Dick went to open it, and then gasped.

"Gosh, Jane," he stuttered. "I didn't expect to see you here."

"Well," came an indignant female voice, "you didn't think I'd spend all night chewing stale sandwiches down at Joe's, did you? They told me you were probably here, so I decided to come round and see for myself."

"Come on in," called out Smithy cheerily. "We've nearly finished."

The owner of the voice entered, to be enthusiastically appraised by the Serviceman. She had long auburn hair, and wore platform shoes, flared jeans and a gaily patterned blouse. She was obviously a member of Women's Lib, and deservedly so. Palpably, a dish.

She looked around her, then spotted the circuit of Smithy's bridge lying on his bench.

"Oh, that wouldn't interest you," said Dick condescendingly. "That's to do with electronics."

"I can see that, you twit," she replied, picking up the piece of paper. "So far as I can make out, it's the circuit of a resistance bridge."

"Hey?"

"Well, it must be," she returned decisively. "And this 741 operational amplifier and the two light emitting diodes will be for indicating balance."

His mouth sagging open, Dick gazed unbelievably at the girl. A glint came into Smithy's eyes.

"What," she asked, "are the two emitter followers doing in front of the 741?"

"They're to increase the input resistance," explained Smithy.

"Oh, of course," she remarked.

She pointed at the metal case on Smithy's bench.

"Is that the actual bridge?"

"It is, my dear," replied Smithy in a warm paternal tone. "I'm just on the point of soldering in the last resistor now. Would you like to see it working when I've done that?"

"I'd love to," she replied enthusiastically. "What's your name?"

"They call me Smithy."

"Well, Smithy, it's really nice to have someone intelligent to talk to for a change. All Old Snodgrass here can do is just grunt and mutter inanities."

And so started a very pleasant and cosy evening. Jane and Smithy put the resistance bridge through its paces and conversed learnedly about matters electronic whilst the fuming Dick, alias Old Snodgrass, was relegated to the background duties of making the tea and being sent down to Joe's Caff for cakes.

We've all had them. There are times when one simply cannot win.

EDITOR'S NOTE

The Australian article referred to by Smithy was "Experimental Bridge Type Ohmmeter" by David Edwards, and it appeared in *Electronics Australia* for June 1974. The article by G. A. French in the July 1975 issue of *Radio & Electronics Constructor* was "Low Cost Electronic Voltmeter." ■

IMPROVED COURTESY LIGHT FOR CARS

In this article, which appeared on page 14 of the August 1975 issue, it is regretted that Figs. 2 and 3 were accidentally transposed.

SPECIAL PRE-PUBLICATION OFFER

Paperback edition


(Published price £3.35) **£2.65** – Save 70p

Hardback edition

(Published price £6.90) **£5.25** – Save £1.65

All prices include P. & P.

THIS OFFER IS EXTENDED TO 31st OCTOBER

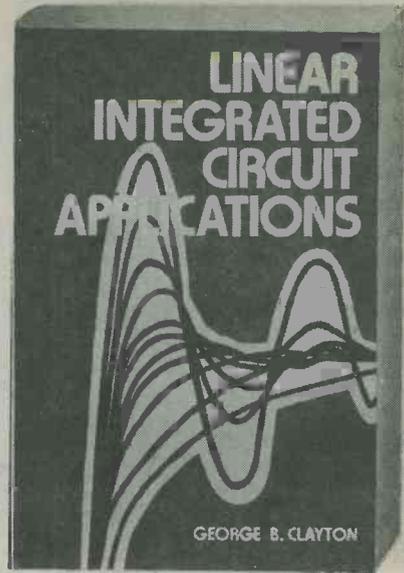

Published by Macmillan

The great practical value of integrated circuits is now fully established in the design of electronic circuits and systems. However, it has only been in recent times following the general acceptance of the first linear integrated circuits—operation amplifiers—that manufacturers have turned their efforts to a wider range of linear integrated circuits.

This book is concerned with these newer circuits now available which find their main use in signal measurement and processing systems.

A practical approach is emphasised throughout and the reader is encouraged to try out the devices for himself.

In this book the applications of operational amplifiers as measure-

ment amplifiers and the use of operational amplifiers in active filter circuits are dealt with. Subsequent chapters are concerned with the more recently introduced linear integrated circuits, monolithic integrated circuit modulators, four quadrant multipliers, timers, waveform generators and phase locked loops.

Numerical exercises are included at the end of each chapter. The book should prove useful to both the practising experimental scientist and the undergraduate student in scientific or engineering disciplines. The practical approach which it adopts should serve as a balance to the rather intensive theoretical treatment given in many undergraduate courses in electronic engineering.

To: **Data Publications Ltd., 57 Maida Vale, London W9 1SN**

Please send to me when published in November copy/ies of

LINEAR INTEGRATED CIRCUIT APPLICATIONS

..... Paperback edition
 Hardback edition (Please tick required edition.)

I enclose Postal Order/Cheque for

Name:

Address:

..... (Block letters please)

THE MODERN BOOK CO ABC OF HI-FI

By JOHN EARL

Price £4.00

NEWNES RADIO ENGINEER'S POCKET BOOK by H. W. Moorshead	PRICE £1.65	TRANSISTOR AUDIO & RADIO CIRCUITS by Mullard	PRICE £2.05
ELECTRONICS AN ELEMENTARY INTRO. FOR BEGINNERS by L. W. Owers	PRICE £1.65	PRINCIPLES OF TRANSISTOR CIRCUITS by S. W. Amos	PRICE £3.45
104 EASY PROJECTS FOR THE ELECTRONICS GADGETEER by R. M. Brown	PRICE £1.40	HI-FI FOR THE ENTHUSIAST by M. L. Gayford	PRICE £5.25
DIGITAL LOGIC BASIC THEORY & PRACTICE by J. H. Smith	PRICE £1.85	HOW TO BUILD SPEAKER ENCLOSURES by A. Badmaieff	PRICE £2.50
TRANSISTOR POCKET BOOK by R. G. Hibberd	PRICE £3.00	TEST EQUIPMENT FOR THE RADIO AMATEUR by H. L. Gibson	PRICE £2.10
BEGINNER'S GUIDE TO TRANSISTORS by J. A. Reddihough	PRICE £2.00	INTEGRATED CIRCUITS (IC's) TRANSISTOR GADGETS CONSTRUCTION HANDBOOK by B. B. Babani	PRICE 70p
RAPID SERVICING OF TRANSISTOR EQUIPMENT by G. J. King	PRICE £2.10	PRACTICAL ELECTRONICS SCIENCE PROJECTS by B. B. Babani	PRICE 85p
MAKING & REPAIRING TRANSISTOR RADIOS by W. Oliver	PRICE £1.40	COLOUR T.V. WITH PARTICULAR REFERENCE TO THE PAL SYSTEM by G. N. Patchett	PRICE £5.15
PRINCIPLES OF TELEVISION RECEPTION by W. Wharton	PRICE £1.85	ELECTRONIC ORGAN SERVICING GUIDE by R. G. Middleton	PRICE £2.80

ALL PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

PLAIN-BACKED NEW STYLE SELF-BINDERS

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

PRICE **95p** P. & P. 20p

including V.A.T.

Available only from:—

Data Publications Ltd. 57 Maida Vale London W9 1SN

for your other magazines

(max. format 7½" x 9½")



COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

SMALL ADVERTISEMENTS

Rate: 5p per word. Minimum charge 75p
Box No. 10p extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. —, **Radio and Electronics Constructor**, 57 Maida Vale, London, W9 1SN.

BUILD THE MULLARD C.C. TV CAMERA. Complete kits now available from Crofton Electronics. Send large s.a.e. for details to:- 124 Colne Road, Twickenham, Middlesex, TW2 6QS. Telephone: 01-898 1569.

VALVES, Radio, TV, Transmitting, Industrial. 1930 to 1975. 2200 types in stock. Many obsolete. List 20p. Quotations s.a.e. Postal export service. We wish to buy all types of valves. Wholesalers, dealers, etc., stocks purchased. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Telephone: West Wittering 2023.

SERVICE SHEETS for Radios/TV's etc. 50p and s.a.e. Catalogue 20p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

AERIAL BOOSTERS. Improve weak radio and television reception. Price £3.20. P. & P. 20p. S.A.E. for leaflets. **BARGAIN PACK POLYESTER (C280) CAPACITORS.** 250V/W and 400V/W. Very good mixed selection from 0.01µF to 2.2µF. Price 100 £1, P. & P. 15p. (Our choice). **VALVE BARGAINS**, 10p each, P. & P. 10p. ECC82, ECL80, EF80/183/184, PC86/88, PCF80/802, PCL82/84, PCL85/805, PL36/504, 30PL14, PY33/81/800. **COLOUR VALVES**, 12p each, P & P. 10p. PL508, PL509, PY500A. Lancashire Mail Order (R), 6 William Street, Stubbins, Ramsbottom, Bury, Lancs.

COLLECTORS: Dinky toys in fair condition, of approx. 1945 vintage. Offers? Box No. G267.

GRIMSBY ELECTRONICS FOR COMPONENTS. Relays, sirens, surplus equipment, etc. Sample pak 25p. List No. 10 8p. 95 Lambert Road, Grimsby, Humberside.

BURGLAR/FIRE ALARMS. Emergency lighting. Professional and D.I.Y. equipment. Catalogue 25p. Castle Alarms, Box W06, Windsor, Berks.

TO CLEAR BOOKSHELVES: *Handbook of Satellites and Space Vehicles* by R. Haviland, £3. *Medical Radiation Biology* by F. Ellinger, £3. *Space* by Patrick Moore, £2. *Rocketry and Space Exploration* by Haley, £2. *Health Physics* by Rees, £3. Box No. G274.

TREASURE HUNTERS! Construct highest performance electronic metal detector for under £2. Equals models costing up to £50. For simple illustrated plans send £1. Colin Lucas, 241 Upminster Road South, Rainham, Essex.

FOR SALE: Partially completed model patrol launch. 42 inch overall. Fitted Taplin Twin I/C engine, and steering control for twin rudders. Ideal for R/C. S.A.E. for details and offers? Box No. G275.

BENTLEY ACOUSTIC CORPORATION LTD.

All prices inclusive of V.A.T. at 25%

The Old Police Station, Gloucester Road, LITTLEHAMPTON Sussex. PHONE 6743

OB2 .45	10P14 2.34	EH10F 1.17	EM90 .44	PCL82 .45	UM80 .60
1A7GT .60	12A6 .75	EA30 .40	EL32 .60	PCL83 .50	UV41 .50
3V4 .82	12AC6 .90	EAB8C0 .40	EL34 1.00	PCL84 .50	UV55 .50
5U4G .90	12AD6 .90	EL41 .60	EL41 .60	PCL805 70	X41 1.00
5Y3GT .55	12AE6 .90	EAC91 .65	EL84 .36	PCL86 .55	X66 1.46
5Z4G .55	12AT6 .47	EAF42 .88	EL506 1.20	PFL200 .55	X6M1 .85
630L2 .80	12B06 .53	EAF801 .30	EM80 .53	PL3 .70	Z759 5.85
6AH6 .80	12AV6 .59	EB91 .23	EM81 .76	PL81 .53	AC165 .33
6AQ5 .53	12BA6 .53	EBCA1 .88	EM83 .64	PL82 .43	AD140 .47
6AT6 .53	12BE6 .59	EAC45 .45	EM84 .47	PL83 .50	AD140 .64
6AU6 .40	12BH7 .59	EBF80 .40	EM87 1.10	PL84 .50	AD161 .59
6AV6 .53	12BY7 .85	EBF83 .50	EY51 .50	PL504 .82	AD162 .59
6BA6 .41	12K3 1.17	EBF89 .40	EY87/6 .40	PL509 1.65	AF115 .20
6BE6 .44	19A05 .65	EC02 .25	EY87/6 .40	PY33/2 .50	AF121 .39
6BH6 .75	2014 1.17	ECC33 2.00	EZ40 .55	PY81 .40	AF126 .23
6B16 .64	30C15 .80	ECC35 2.00	EZ41 .55	PY82 .40	BC107 .16
6BQ7A .64	30C17 .85	ECC40 1.20	EZ60 .35	PY83 .45	BC108 .16
6BR7 1.20	30E3 .75	ECC81 .40	EZ81 .35	PY88 .47	BC109 .16
6BR8 1.25	30FL1 1.10	ECC82 .39	GZ12 .59	PY500 .47	BC113 .33
6BW6 1.00	30FL2 1.10	ECC83 .39	GZ14 .80	PY800 .45	BC118 .29
6BW7 .65	30FL14 .82	ECC84 .40	GZ14 .80	PY801 .45	BC211 .49
6BZ6 .57	30L15 .82	ECC85 .47	KTW61 1.76	PZ30 .50	BF158 .23
6C4 .47	30L17 .76	ECC88 .55	KTW62 1.76	QQV03/10	BF159 .33
6C6 .47	30P12 .88	ECC87 .41	ECF80 1.41	R19 .210	BF163 .26
6C9 2.00	30P19 .88	ECF80 1.41	ECF80 1.41	R19 .75	BF180 .39
6CL6 .76	30PL1 1.00	ECF82 .50	ECF82 .50	U25 .70	BY100 .23
6CU5 .88	30PL2 .50	ECF82 .50	ECF82 .50	U26 .65	BY126 .20
6D7 1.17	30PL13 .20	ECF84 .88	ECF84 .88	U191 .50	BY127 .23
6F1 .80	30PL141.29	ECF84 .88	ECF84 .88	U801 .80	QA88 .12
6F6G .60	35L6GT .88	ECH15 2.63	PC86 .70	U801 .80	QA75 .12
6F18 .64	35W4 .60	ECH15 2.63	PC86 .70	U801 .80	QA75 .12
6F23 .80	35ZAGT .82	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F28 .78	50B5 1.00	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6HGT 29	30C3 .70	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6ES 1.17	30PL13 .20	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F1 .80	30PL141.29	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F6G .60	35L6GT .88	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F18 .64	35W4 .60	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F23 .80	35ZAGT .82	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F28 .78	50B5 1.00	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6HGT 29	30C3 .70	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6ES 1.17	30PL13 .20	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F1 .80	30PL141.29	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F6G .60	35L6GT .88	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F18 .64	35W4 .60	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F23 .80	35ZAGT .82	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F28 .78	50B5 1.00	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6HGT 29	30C3 .70	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6ES 1.17	30PL13 .20	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F1 .80	30PL141.29	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F6G .60	35L6GT .88	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F18 .64	35W4 .60	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F23 .80	35ZAGT .82	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F28 .78	50B5 1.00	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6HGT 29	30C3 .70	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6ES 1.17	30PL13 .20	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F1 .80	30PL141.29	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F6G .60	35L6GT .88	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F18 .64	35W4 .60	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F23 .80	35ZAGT .82	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F28 .78	50B5 1.00	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6HGT 29	30C3 .70	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6ES 1.17	30PL13 .20	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F1 .80	30PL141.29	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F6G .60	35L6GT .88	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F18 .64	35W4 .60	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F23 .80	35ZAGT .82	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6F28 .78	50B5 1.00	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6HGT 29	30C3 .70	ECH15 2.63	PC88 .70	U801 .80	QA75 .12
6ES 1.17	30PL13 .20	ECH15 2.63	PC88 .70	U	

PRECISION

POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

440V AC (+10%)	63V DC Range	+1%	+2%	+5%
0.1µF (1 1/8" x 3/8") 51p	0.47µF 67p	50p	43p	
0.22µF (1 1/8" x 5/8") 64p	1.0µF 82p	62p	52p	
0.25µF (1 1/8" x 5/8") 67p	2.2µF 96p	75p	61p	
0.47µF (1 3/8" x 3/4") 80p	4.7µF £1.62	£1.13	94p	
0.5µF (1 3/8" x 3/4") 77p	6.8µF £1.96	£1.38	£1.13	
0.68µF (2" x 1 1/4") 93p	10.0µF £2.40	£1.95	£1.64	
1.0µF (2" x 1 1/4") £1.03	15.0µF £3.22	£2.79	£2.24	
2.0µF (2" x 1 1/2") £1.44	22.0µF £4.28	£3.68	£3.08	

TANTALUM BEAD CAPACITORS - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL AT 10p EACH; 10 for 95p; 50 for £4.00.

TRANSISTORS:

BC107/8/9 9p	BC183/183L 11p	BF194 12p	BFY51 20p
BC114 12p	BC184/184L 12p	BF196 13p	BFY52 20p
BC147/8/9 10p	BC212/212L 14p	BF197 13p	OC71 12p
BC153/7/8 12p	BC547 12p	AF178 30p	2N3055 50p
BC182/182L 11p	BC558A 12p	BFY50 20p	2N3702/4 11p

1N914 6p; 8 for 45p; 18 for 90p. 1N916 8p; 6 for 45p; 14 for 90p. 1S44 5p; 11 for 59p; 24 for £1.00. 1N4148 5p; 6 for 27p; 12 for 48p.

LOW PRICE ZENER DIODES: 400mW; Tol. +5% at 5mA. Values available: 3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.5V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each; 5 for 33p; 10 for 65p. SPECIAL: 100 Zeners for £6.00.

RESISTORS: High stability low noise carbon film 5%, 1/4 W at 40°C; 1/2 W at 70°C. E12 series only - from 2.2Ω to 2.2MΩ ALL AT 1p EACH; 8p for 10 of any one value; 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

SILICON PLASTIC RECTIFIERS - 1.5 Amp - Brand new wire ended D027: 100 P.I.V. - 7p (4/26p); 400 P.I.V. - 8p (4/30p).

BRIDGE RECTIFIERS: 2 1/2 Amp. 200V - 40p; 350V - 45p; 600V - 55p.

SUBMINIATURE VERTICAL PRESETS - 0.1W only: ALL AT 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1K, 2.2K, 4.7K, 6.8K, 10K, 15K, 22K, 47K, 100K, 250K, 680K, 1M, 2.5M, & 5M.

PLEASE ADD 25% V.A.T. TO ORDERS. PLEASE ADD 15p POST AND PACKING ON ALL ORDERS BELOW £5.00. Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona-fide companies. ALL EXPORT ORDERS ADD COST OF SEA/AIRMAIL.

MARCO TRADING

Dept. C6, The Old School, Edstaston, NR. WEM, Salop.
Tel: WHIXALL (Salop) 4645 (STD 094872) (Props: Minicost Trading Ltd.)

SMALL ADVERTISEMENTS

(Continued from page 187)

FOR SALE: Assorted transistors, untested, ample leads, 100 for £1.25. Ex-new electrolytics 100 for £1.25. Resistors 500 for £1.00. Computer panels, 3lbs. 85p, 50p. P. & P. Post on others 30p s.a.e. for list. Robert Broadbent, 24 Flaxton Street, Leeds, 11, West Yorks.

FOR SALE: Complete Widescreen film outfit. 9.5mm camera and projector with widescreen lens, screen, film, etc. Would exchange for other photo or radio gear or w.h.y.? S.A.E. for details to Box No. G276.

UNIQUE VHF KITS, 80-180MHz. Receiver, tuner converter. World wide sales. Send £5 or s.a.e. for literature. Johnsons Radio (C), Worcester, WR1 3QQ.

WANTED: Prism type spectrometer, suitable demonstration purposes, school, etc. Must be cheap. Repairable instrument would be suitable. Box No. G277.

KITS CONSTRUCTED. Send details for quote. Competitive prices. John Robinson, 5 Norfolk Place, Leeds 7, Yorks.

FOR SALE: 2m converter, mains operated. 24-26MHz. £8. Box No. G278.

INDESIT AUTOMATIC WASHING MACHINE service manuals. (Do it yourself repairs). With faults & diagrams. Complete with spare parts order forms. £2.50. Cheque or P.O. Marchant, Domestic Services, Shotton, Clwyd, N. Wales.

WANTED: To purchase sheet music, light classical, musicals, etc. Box No. G280.

FOR SALE: Polarised relays. Suitable for RTTY terminal units, etc. £1.00 each. Box No. G281.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

WANTED TO PURCHASE: All early books on radio, preferably before 1925. Box No. 282.

WANTED: "Everyday Electronics", January 1975. Whole issue or copy of articles. Price? John Hunt, 251 West Bruceton, Pittsburgh, PA 15236, U.S.A.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. Rita Shepherd, 59 Paintain Road, Loughborough, Leics., LE11 3LZ.

(Continued on page 189)

REVOR OPTICAL & TECHNICAL

12/13 HENRIETTA ST.,
LONDON W.C.2
Tel. 01-836 4536

£6.00
POST
FREE


4" dia. lens

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE.
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

S.A.E. FOR CATALOGUE

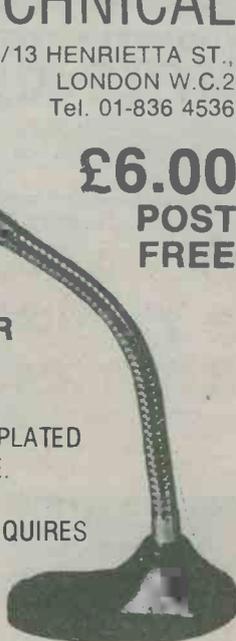(Subject to price ruling at the time of issue)



SMALL ADVERTISEMENTS

(Continued from page 188)

TO CLEAR: Xtals 2306, 2381, 2009KHz, $\frac{3}{4}$ " pin spacing, £1 each. Sigma type 72AOZ, 160TG-TCP, polarised relays, octal base, £2 24V d.c. miniature model motor 2" x $1\frac{1}{4}$ " diam, $\frac{3}{8}$ " shaft, £1. Cold cathode tube GC10B, £1. $1\frac{1}{2}$ " c.r.t. VLS492AG.F, £2. R.E.P. 3-reed tuned relay, £2. Miniature R.E.P. R/C relay, £1. $2\frac{1}{4}$ " mic. insert 25p. Radiospares miniature output for personal receiver, 50p. Transformer 3.2 ohm/600 ohm £1. Ditto 3000 ohm/600 ohm, £1. Telford Communications 2M bandpass aerial filter, £3. TC7 Bandsearcher, £3. 7X electric torch map magnifier, £1. Box No. G283.

FOR SALE: Lafayette model HA-63A general coverage receiver, with preselector & L.S. £35. Box No. G284.

COLLECTION OF STAMPS. IGY, railway centenary and similar. Cat. Value £150. Offers or w.h.y.? Box No. G285.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.

WANTED: Marine type chronometer and sextant. Box No. G286.

EXCHANGE: Crofton CCTV modules 1-2-3, lens control, panel, base, coils, manual, cost £30, for air pistol/rifle. Altree, Winsford House, Halwill, Beaworthy, Devon.

WANTED: A gauge O model loco, preferably steam. Box No. G287.

FOR SALE: Personal portable receiver chassis, contains speaker, transistors, I.F.'s, etc. £2. Box No. G288.

FOR SALE: Cossor 1049 Mk. 4 double beam scope, £20. Marconi - Signal generator TF801 10Mc/s-310Mc/s, £25. Audio generator TF195J 0/12Kc/s, £7. Advance-Signal generator E2 100kc/s-100Mc/s, £25. Audio generator J1 15c/s-50kc/s, £15. Avo 7, £10. Multiminor, £7. All in working order with handbooks. Carriage extra. S.A.E. for enquiries please. Box (Middx.) No. G289.

WANTED: Volume No. 24 *Radio & Electronics Constructor* (Bound) wanted by private collector. Also interested in buying other magazines, especially American ones. Preferably complete years. Not necessarily bound. Write first giving details and prices to Box No. G290.

WANTED URGENTLY suitable complete working amplifier assembly for "Collaro Studio" 2-track T-deck. All letters answered. Box No. G291.

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32 Mc/s at every 500Kc/s points. Each frequency is repeated. Two sheets for 5p., five sheets for 10p., postage 6p. Data Publications Ltd., 57 Maida Vale, London, W9 1SN.

(Continued on page 191)

VALVE BARGAINS

Any 5 60p, 10 90p, 50 £4.00, 100 £7.50. Your choice from the following list:

ECC82, ECL80, EB91, EF80, EF183, EF184, PC86, PC88, PC97, PC900, PCC84, PCC89, PCC189, PCF80, PCF802, PCF805, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14.

Colour Valves 30p each
PL508, PL509, PY500/A.

Press 4 Button UHF Tuners
£2.50

AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets.

B11 - For Stereo and Standard VHF Radio.

B12 - For the older VHF Television, please state BBC1 and ITV Channels.

B45 - For mono or colour this covers the complete UHF band.

All Boosters are complete with Battery and take only minutes to fit.

Price £3.90 each

BARGAIN PACKS


All Components in the Bargain Packs are unused and marked.
Pack 1 - Polyester (C280) Axial Leads Capacitors - 250V/W & 400V/W, very good mixed selection from 0.01uF to 2.2uF
Price 100 £1.25, 1000 £10 (our choice).

Pack 2 - Transistors - any 10 90p, any 100 £8 (your choice).
AC128 - AC176 - BC113 - BC115 - BC135 - BC153 - BC171 - BC172.

Pack 3 - 15 Mixed Plugs, mixed selection of co-ax, din 2-3-5 pins, jack standard - 3.5mm-2.5mm. Price £1.25.

Prices include VAT P&P under £1/10p, £1 to £3/15p, above £3/20p. Overseas at cost. Money back guarantee on all orders.

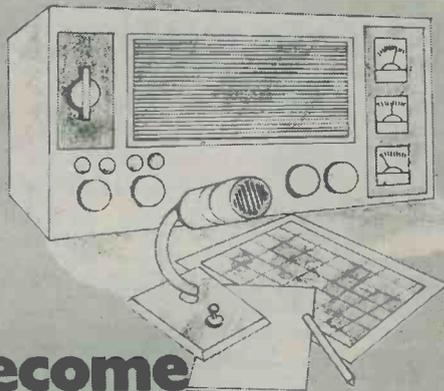ELECTRONIC MAIL ORDER LTD., 62A BRIDGE ST., RAMSBOTTOM, BURY, LANCs. Tel. Rams. 3036



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure, without obligation to: WAA
REB 105

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ (Block caps please)

RADIO MODELLER

ELECTRONIC BOOKS

MODEL RADIO CONTROL

Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.
134 pages.

Price £2.25

U.K. Packing & Postage 32p

ON SALE NOW
at all leading shops
or direct from:-

RADIO MODELLER
BOOKS DIVISION,
64 Wellington Road,
Hampton Hill, Middx.

theory and
practice of
**MODEL
RADIO
CONTROL**

development of systems
proportional explained
digital system design
practical examples and
full circuit details

Paul Newell

SPECIAL OFFER

FREE—741 Operational Amplifier I.C. with every copy of R. M. Marston's book "110 Operational Amplifier Projects for the Home Constructor", price £1.80. Includes circuits for musical instruments, fire alarm, burglar alarm, touch-activated switch and many other exciting projects.

ZN414 £1.10

Ferranti Application Booklet for ZN414 25p

**ZN1034E New Ferranti Precision Timer I.C.
£2.90**

Ferranti Data Sheets for ZN1034E 10p
741 Operational Amplifier I.C. 33p

RADNAGE RADIO & ELECTRONICS

2 Bottom Road, Radnage, High Wycombe, Bucks.
Prices inclusive. Add 15p Post and Packing UK, 60p Exports.
Mail order only

CLEARANCE BARGAINS

SPECIAL OFFER—Metallised Polyester Capacitors by Erie, Mullard, etc. Values include .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed, 100 for £2.00.

ASSORTED CAPACITORS, Silver Mica, Tubular and Disc Ceramics, Polystyrene. Tremendously good selection 300 for £1.70.

MULLARD FERRITE CORES LA3 54p, LA4 81p, LA2100 54p.
OUT OF SPEC. 2N 3055 5 for £1.08

CERAMIC FORMERS L23mm Diam. 13mm Bore 1 end Bmm other end 4mm 100 for £1.88.

ROTARY SWITCHES very good quality 1P x 18 way x 3 banks 65p
Please note all prices include Postage and V.A.T.

MAIL ORDER ONLY
XEROZA RADIO
1, EAST STREET,
BISHOPS TAWTON,
DEVON

ESSENTIAL BOOKS!

POWER SUPPLIES FOR ELECTRONIC EQUIPMENT. J. R. Nowicki. Published recently in 2 vols. A full treatment of all power supplies is given. Includes rectification, inverters, transverters, silicon diodes and other electronic devices. With full circuit diagrams and component values. Originally published at £4.50 per volume. Bargain price £4 for the 2 volumes incl. postage.

THE MOBILE RADIOTELEPHONE EQUIPMENT HANDBOOK. Gives circuits, data and illustrations plus some valuable modification details for COMMERCIAL RADIOTELEPHONE equipment. Price of this edition including postage £6.25.

HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION. 40p, p.p. 15p.

HOW TO MAKE 2M & 4M CONVERTORS FOR AMATEUR USE. Fully comprehensive. Contains circuits layouts, component lists, diagrams and full instructional notes. Price 60p, p.p. 15p.

THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK. Gives circuits, data and illustrations plus valuable information for British/USA receivers, transmitters, trans/receivers. £4 including postage.

DIRECTORY OF GOVERNMENT SURPLUS WIRELESS EQUIPMENT DEALERS! Gives details of surplus wireless equipment stores and dealers including addresses plus equipment and spares that they are likely to have available. A valuable book only 50p, p.p. 15p.

GETTING THE BEST FROM YOUR COLOUR TV. R. Maude. Essential advice for colour TV engineers and owners. Could save you pounds. 50p, p.p. 15p.

THE THEORY OF GUIDED ELECTROMAGNETIC WAVES. The most comprehensive book yet written about waveguides, transmission lines, cavity resonators. Over 500 pages. Ideal for anyone interested in Radar and UHF. Published at £11.50. Special offer £4.50 p.p. 50p.

INTERNATIONAL DICTIONARY OF SEMICONDUCTORS. A 2-volume electronics dictionary published at £16 available at less than half price. In 7 languages it proves an invaluable addition to any collection of electronics reference books. Contained are 1373 pages packed with information. In leather styled finish. Only £6.50, p.p. 50p.

THE RADIO CONTROL MANUAL. Contains numerous plans, photographs and instructions. A large format hardback book published at £1.25. Bargain price 60p, p.p. 20p.

THE THEORY AND DESIGN OF MAGNETIC AMPLIFIERS. 487 pages. Published at £1.75. Bargain price 75p, p.p. 25p.

WORKED EXAMPLES IN ALTERNATING CURRENT. A must for the student, technician and electrical engineer. Contains numerous examples and how they were arrived at. Published at £1.25. Bargain price 60p, p.p. 20p.

THE BARGAIN BOOK GAZETTE. Contains thousands of interesting new and out of print books at bargain prices. Subjects include all types of hobbies, collecting, 1001 interests. Published regularly and sent free on request.

Dept. R. C. GELALD MYERS (Publisher & Bookseller), 13B Cardigan Rd., Headingly, Leeds 6, Yorks. (Callers Welcome).

I.C. EXPERIMENTAL/EDUCATIONAL KITS

Learn about modern electronics with our new step-by-step Kits. Use and understand digital logic techniques. Kits contain specially selected I.C.'s, Holders, Veroboard, L.E.D.'s, instructions and data. First three Kits in the series are now available:

KIT ONE GATES
KIT TWO FLIP-FLOPS
KIT THREE SHIFT REGISTERS
Each Kit £3.50 (including P. & P.)
Also available: Experimenter's Pak, £3.00

Contains I.C.'s of Gates, Flip-Flops, Inverters, Counters, Holders and Data.

S.A.E. for further details to:

AUTOMATED HOMES

69 High Street, RYTON, Coventry CV8 3FJ
(Mail Order Only)

MORSE MADE EASY BY THE RHYTHM METHOD!

FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month: (Normal progress to be expected.)

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed. For Complete Course 3 Records & Books send £4.95 including P.P.I. etc. (overseas surface mail £1 extra.)

For further details of course Ring 01-660 2896 or send large S.A.E. for explanatory booklet to:—S. BENNETT, G3HSC
(Box 38) 45 GREEN LANE, PURLEY, SURREY

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the issue of RADIO & ELECTRONICS CONSTRUCTOR

15 words at 5p
= 75p.

**ALL WORDING
IN
BLOCK LETTERS
PLEASE**

I enclose remittance of.....being payment at 5p a word. **MINIMUM 75p.**
Box Number, if required, 10p extra.

NAME.....

ADDRESS

Copy to be received four weeks prior to publication. Published on the 1st of every month.

DATA BOOK SERIES

- DB5 TV FAULT FINDING**
132 pages. Price 90p, P. & P. 12p
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**
88 pages. Price 70p, P. & P. 10p
- DB16 RADIO CONTROL FOR MODELS**
Now out of print
- DB17 UNDERSTANDING TELEVISION**
512 pages. Revised edition available September
- DB18 AUDIO AMPLIFIERS**
128 pages. Price 53p, P. & P. 12p
- DB19 SIMPLE SHORT WAVE RECEIVERS**
140 pages. Price 80p, P. & P. 12p

I enclose Postal Order/Cheque for.....in payment for.....

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

*Postal Orders should be crossed and made payable to Data Publications Ltd.
Overseas customers please pay by International Money Order.
All publications are obtainable through your local bookseller.
Data Publications Ltd., 57 Maida Vale, London W9 1SN*

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS


ELECTRONICS DATA

FOR THE BEGINNER FOLLOW THE ARROWS

Arrows appear frequently in electronic circuit diagrams. An arrow drawn through a component symbol indicates that the value is variable, as with the variable resistor in (a) and the variable capacitor in (b). An arrow may indicate the slider, or wiper, of a potentiometer, as in (c), or the arm of a rotary switch, as in (d). Sometimes, an arrow is drawn alongside a potentiometer, as in (e), to indicate the direction of slider movement when the potentiometer spindle is turned clockwise.

Arrow-heads are drawn on connecting lines in a block diagram to indicate the direction of a process. They may indicate, for instance, the direction of a signal as it passes through a receiver.

When an arrow-head appears in a circuit diagram it usually indicates the direction of flow of a current, and the magnitude of the current may be printed alongside, as in (f). Normally, the arrow-head follows the convention that the current flows from positive to negative (even though the electrons which constitute the current flow from negative to positive). The symbol for a rectifier (g) is really an arrow-head with a bar at right angles, and the arrow-head indicates the current direction flow which the rectifier permits. Thus, the rectifier conducts when the anode is positive of the cathode. The arrow-head appears in other device symbols, such as that for a thyristor (h), for an n.p.n. transistor (i), and for a p.n.p. transistor (j). These arrow-heads indicate the direction of flow of current in the thyristor when it is turned on, and in the base-emitter junctions of the two transistors.

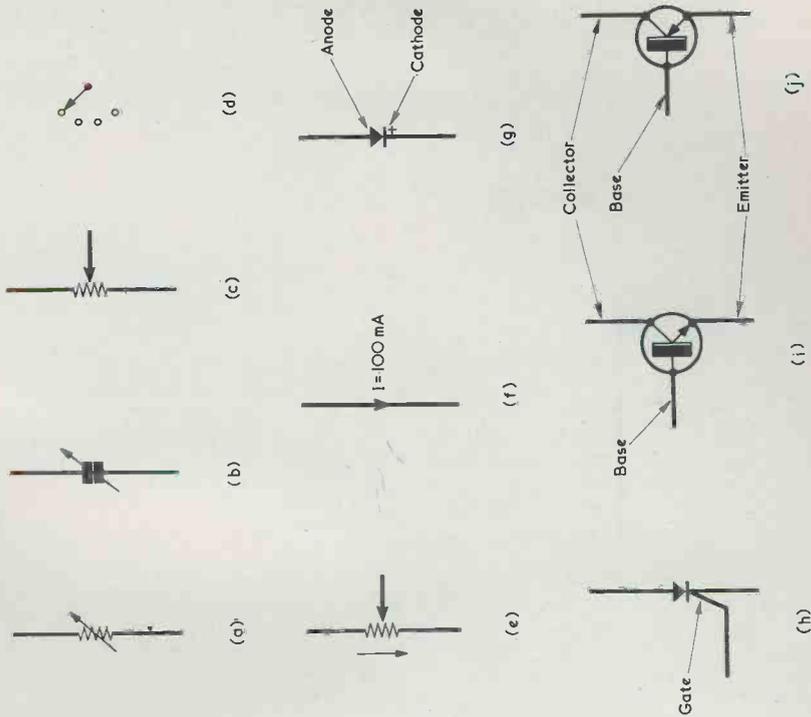


DIRECT SUPPLY SERVICE TO READERS . . .

TOWERS INTERNATIONAL TRANSISTOR SELECTOR

This is dead!

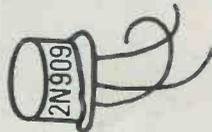If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. Its one of the most useful working books you will be offered this year. And probably the cheapest!



Japanese. And we think that they will solve 90% of your transistor enquiries.

Would this replace it?



In it you will find a really international selection of 10,000 transistor types - British, Continental European, American and

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Look at the entry for 2N909

TRANSISTOR NUMBER	PM DA LT	PACK-AGE	LEAD INFO	VCB MAX	VCE MAX	VEB MAX	I C MAX	T J MAX	P TOT	F T MIN	C DB MAX	H FE	H FE BIAS	USE	MFR	EURO EQVT	USA EQVT	ISS
2N909	NS	TO18	LO1	60V	30V	5V	200MA	175C	500MWF	50M	25P	110MN	50MA	AMG	SGI	BSX33	2N731	0

This is what you will learn from it

TYPE NO	POL & MAT	LEAD OUTLINE	LEAD OPEN TYPN	V _{CEO} MAX	V _{CE0} MAX	V _{EB0} MAX	I _C MAX	T _J MAX	P _{TOT}	C _{DB} MAX	H _{FE}	H _{FE} BIAS	USE	MFR	EURO EQVT	USA EQVT	ISS	
(EXAMPLE) 2N909	NS	TO18	LO1	60V	30V	5V	200 MA	175C	500MWF	50M	25P	110 MN	50 MA	AMG	SGI	BSX 33	2N 731	0

NUMERO-ALPHABETIC LISTING

N - NPN
P - PNP
G - GERMANIUM
S - SILICON

REFER TO CASE-OUTLINES APPENDIX C

REFER TO LEAD DETAILS-APPENDIX B

MAXIMUM PERMISSIBLE COLLECTOR-BASE VOLTAGE WITH EMITTER OPEN-CIRCUIT

MAXIMUM PERMISSIBLE COLLECTOR-EMITTER VOLTAGE WITH BASE OPEN-CIRCUIT

MAXIMUM PERMISSIBLE EMITTER-BASE VOLTAGE WITH COLLECTOR OPEN-CIRCUIT

MAXIMUM PERMISSIBLE COLLECTOR CURRENT

MAXIMUM PERMISSIBLE JUNCTION TEMPERATURE

MAXIMUM PERMISSIBLE DEVICE DISSIPATION - T_J IN FREE AIR AT 25°C C - WITH CASE SURFACE HELD AT 25°C °H - IN FREE AIR AT 25°C WITH METAL HEAT SINK ATTACHED TO DEVICE

MINIMUM FREQUENCY CUT OFF. F_c INDICATED IN K - KILOHERTZ M - MEGAHERTZ G - GIGAHERTZ

F_c - FREQUENCY AT WHICH COMMON-EMITTER CURRENT GAIN DROPS TO UNITY. TYPICAL F_c CAN BE TAKEN AS ROUGHLY TWICE F_c (MIN)

BIAS CURRENT AT WHICH CURRENT GAIN H_{FE} IS CHARACTERISED

CURRENT GAIN, NORMALLY D.C. (BUT SOMETIMES RELATED A.C. GAIN) AT I_C BIAS SPECIFIED - WHERE MIN ('MIN') ONLY IS SPECIFIED TYPICAL ('TP') CAN BE TAKEN AS TWICE MIN AND VICEVERSA

MAXIMUM COLLECTOR CAPACITANCE (TYPICAL USUALLY 1 TO 1 MAX) - NORMALLY EMITTER OPEN-CIRCUIT AND INDICATED BY 'P' - PICOFARAD OR 'N' - NANOFARAD - FOR HF DEVICES C_{DB} IS GIVEN AND PICOFARADS THEN INDICATED BY 'N' INSTEAD OF 'P'

FOOTNOTE

SUGGESTED 2N - JEDEC 2N - STANDARD POSSIBLE SUBSTITUTE

SUGGESTED PROELECTRON STANDARD POSSIBLE SUBSTITUTE

CODE INDICATION POSSIBLE SUPPLIER OF DEVICE - SEE 'SUPPLIER' APPENDIX F

CODE INDICATION OF APPLICATION USAGE - SEE APPENDIX A

*ISS COLUMN INDICATES ISSUE NO OF DATA LINE ENTRY

Tower's International Transistor Selector

by T. D. TOWERS
MBE, MA, BSc, C Eng, MIERE

£3.30
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

(Block capitals)