
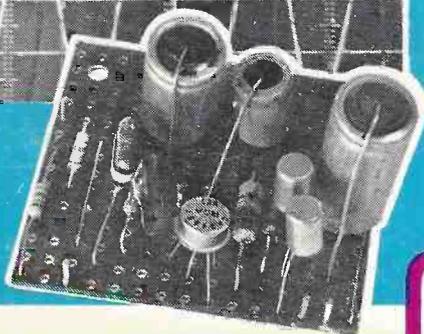


RADIO & ELECTRONICS CONSTRUCTOR


APRIL 1977

40p

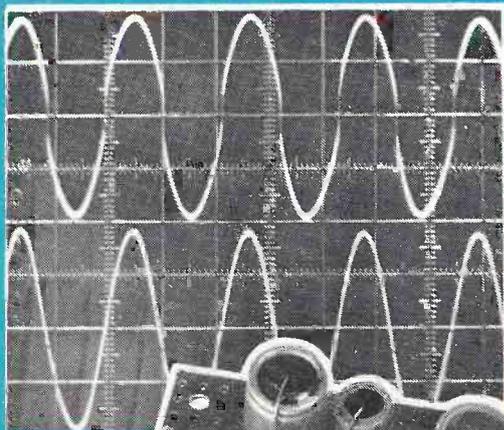

CMOS AUDIO AMPLIFIER

**METERLESS
TRANSISTOR
TESTER**

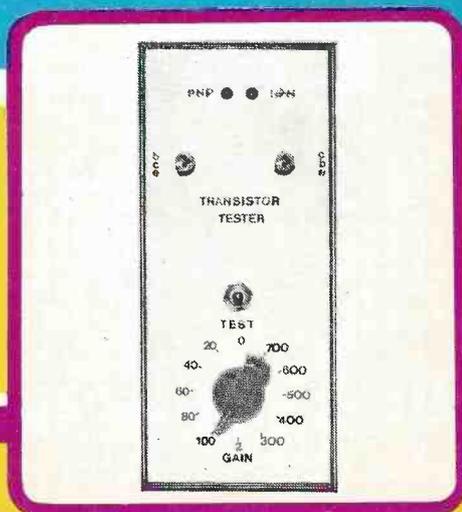

**ALSO
FEATURED**

**THE "M5" POCKET RECEIVER
Part 1**

NOEL M. MORRIS

**SEMICONDUCTOR
DEVICES**



MACMILLAN BASIS BOOKS IN ELECTRONICS

ANOTHER SPECIAL OFFER

For a limited period

By arrangement with Messrs. MacMillan we are able to offer the above book at a special low price to readers of RADIO & ELECTRONICS CONSTRUCTOR.

Normal Price£4.35

SPECIAL OFFER PRICE..... £3.50

Saving 85p

Both prices include postage and packing

In this introduction to semiconductor devices, the author provides a comprehensive survey of modern active and non-active semiconductor technology. Without leaning too heavily on device physics, he explains device functions and then illustrates their use with typical circuits and applications.

Following a summary of the physical basis of semiconductor elements — in non-mathematical terms — a study of bipolar and field-effect transistors leads to considerations of monolithic integrated circuits. More advanced charge-coupled devices, semiconductor memories and optoelectronic devices are studied in some detail.

CONTENTS

1. Semiconductors
2. Basic Semiconductor Devices
3. Semiconductor Diodes and the Unijunction Transistor
4. Bipolar Junction Transistors, Amplifiers & Logic Gates
5. Field-Effect Transistors, Amplifiers and Logic Gates
6. Monolithic Integrated Circuits
7. Charge-coupled Devices
8. Semiconductor Memories
9. Thyristors and other Multilayer Devices
10. Optoelectronics

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies of

SEMICONDUCTOR DEVICES

I enclose Postal Order/Cheque for £.....

Name

Address

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

RADIO & ELECTRONICS CONSTRUCTOR

APRIL 1977
Volume 30 No. 9

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 Telegrams
Databux, London

© Data Publications Ltd., 1977. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £5.50 (U.S.A. and Canada \$11.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.


Production.—Web Offset.

METERLESS TRANSISTOR TESTER by Bruce Woodland	534
500th EDITION OF WORLD RADIO CLUB Report by Ron Ham	539
NEWS AND COMMENT	540
POLARITY/BASE RESOLVER (Suggested Circuit 317) by G. A. French	542
THE "M5" POCKET RECEIVER — Part 1 by Sir Douglas Hall, K.C.M.G.	546
CMOS AUDIO AMPLIFIER by R. A. Penfold	551
"HEADS OR TAILS?" — by J. R. Davies	556
MOBILE AMATEUR RADIO LOG REQUIREMENTS	558
ANTIQUE AND WARTIME RADIO by Ron Ham	559
SURGE CURRENTS (Notes for Newcomers) by R. J. Caborn	561
CATALOGUE	563
TRADE NOTES	563
SHORT WAVE NEWS — For DX Listeners by Frank A. Baldwin	564
MEDIUM AND LONG WAVE SUPERHET — Part 2 by A. P. Roberts	566
IN YOUR WORKSHOP — TV Repair	570
RADIO TOPICS by Recorder	576
WORKSHOP AIDS	578
ELECTRONICS DATA No. 21 (For the Beginner — Screening)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

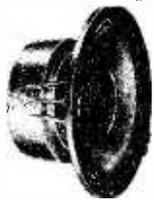THE MAY ISSUE WILL BE
PUBLISHED ON 2nd MAY



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25, 3, 8 or 15 ohms
 Baker Group 35, 3, 8 or 15 ohms
 Baker Group 50/12 8 or 15 ohms
 Baker Group 50/15 8 or 15 ohms
 Baker Deluxe 12" 8 or 15 ohms
 Baker Major 3, 8 or 15 ohms
 Baker Superb 8 or 15 ohms
 Baker Regent 12" 8 or 15 ohms
 Baker Auditorium 12" 8 or 15 ohms
 Baker Auditorium 15" 8 or 15 ohms

Castle BRS/DD 4/8 ohms
 Celestion G12M 8 or 15 ohms
 Celestion G12H 8 or 15 ohms
 Celestion G12/50 8 or 15 ohms
 Celestion G12/50TC 8 or 15 ohms
 Celestion G15C 8 or 15 ohms
 Celestion G18C 8 or 15 ohms
 Celestion HF1300 8 or 15 ohms
 Celestion HF2000 8 ohms
 Celestion MH1000 8 or 15 ohms
 Coles 4001 G&K

Decca London ribbon horn
 Decca London CO/1000/8 Xover
 Decca DK30 ribbon horn
 Decca CO/1/8 Xover (DK30)

EMI 14 x 9 Bass 8 ohms 14A770
 EMI 8 x 5, 10 watt, d/cone, roll surr.
 EMI 6 1/2" d/cone, roll surr. 8 ohms
 Elac 59RM109 (15) 59RM114 (8)
 Elac 6 1/2" d/cone, roll surr. 8 ohms
 Elac 10" 10RM239 8 ohms
 Eagle FR4
 Eagle FR65
 Eagle FR8
 Eagle FR10
 Eagle HT15
 Eagle HT21
 Eagle MHT10
 Eagle FF28 multicell. horn

Fane Pop 15, 8 or 16 ohms
 Fane Pop 33T, 8 or 16 ohms
 Fane Pop 50, 8 or 16 ohms
 Fane Pop 55, 8 or 16 ohms
 Fane Pop 60, 8 or 16 ohms
 Fane Pop 70, 8 or 16 ohms
 Fane Pop 100, 8 or 16 ohms
 Fane Crescendo 12A, 8 or 16 ohms
 Fane Crescendo 12BL, 8 or 16 ohms
 Fane Crescendo 15/100A, 8 or 16 ohms
 Fane Crescendo 15/125, 8 or 16 ohms

SPEAKERS

Fane Crescendo 18, 8 or 16 ohms
 Fane 910 Mk.II horn
 Fane 920 Mk.II horn
 Fane HPX1 crossover 200 watt
 Fane 13 x 8, 15 watt dual cone
 Fane 801T 8" d/c, roll surr.
 Goodmans Axent 100
 Goodmans Audiom 200 8 ohms
 Goodmans Axiom 402 8 or 15 ohms
 Goodmans Twinaxiom 8, 8 or 15 ohms

Goodmans 8P 8 or 15 ohms
 Goodmans 10P 8 or 15 ohms
 Goodmans 12P 8 or 15 ohms
 Goodmans 12PG 8 or 15 ohms
 Goodmans 12PD 8 or 15 ohms
 Goodmans J2AX 8 or 15 ohms
 Goodmans 15AX 8 or 15 ohms
 Goodmans 15P 8 or 15 ohms
 Goodmans 18P 8 or 15 ohms
 Goodmans Hifax 750P
 Goodmans 5" midrange 8 ohms
 Gauss 12"
 Gauss 15"
 Gauss 18"

Jordan Watts Module, 4, 8 or 15 ohms

Kef T27
 Kef T15
 Kef B110
 Kef 8200
 Kef B139
 Kef DN8
 Kef DN12
 Kef DN13 SP1015 or SP1017
 Lowther PM6
 Lowther PM6 Mk.I
 Lowther PM7
 Peerless KO10DT 4 or 8 ohms
 Peerless DT10HFC 8 ohms
 Peerless KO40MRF 8 ohms
 Peerless MT225HFC 8 ohms

Richard Allan CA12 12" bass
 Richard Allan HP8B
 Richard Allan LP8B
 Richard Allan DT20
 Richard Allan CN8280
 Richard Allan CN820
 Richard Allan Super Disco 60W 12"
 Coles 4001 G&K
 Tannoy 10" Monitor HPD
 Tannoy 12" Monitor HPD
 Tannoy 15" Monitor HPD

SPEAKER KITS

Baker Major Module 3, 8 or 15 ohms each
 Goodmans DIN 20 4 or 8 ohms each
 Goodmans Mezzo Twin kit pair
 Helme XLK 20 pair
 Helme XLK 30 pair
 Helme XLK 35 pair
 Helme XLK 40 pair
 KEFkit 1 pair
 KEFkit III each
 Peerless 1060 pair
 Peerless 1070 each
 Peerless 1120 each
 Peerless 2050 pair
 Peerless 2060 pair
 Richard Allan Twin assembly each
 Richard Allan Triple 8 each
 Richard Allan Triple 12 each
 Richard Allan Super Triple each
 Richard Allan RAB Kit pair
 Richard Allan RA82 Kit pair
 Richard Allan RA82L Kit pair
 Denton 2XP Kit pair
 Wharfedale Linton 3XP Kit pair
 Wharfedale Glendale 3XP Kit pair

HI-FI

ON DEMONSTRATION

Akai, Armstrong, Bowers & Wilkins, Castle, Celestion, Dual, Chartwell, I.M.F. RAM, Neel, Dalesford, Sansui, J.R. Formula 4, Ortofon, Linn Sondak, Stanton, Pickering, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone, Wharfedale, etc.
 —Ask for our HiFi price list—

THIS MONTH'S SPECIALS (Carr. £2.50)

ROTEL RA312£66.00
 SANSUI 331£109.00
 TRIO KR2600£109.00
 VIDEOTONE MINIMAX II£46.95
 SANSUI SC2000/2002£145.00
 PIONEER CTF2121£136.00
 ROTEL RX15211£91.00

We stock the complete Radford range of amplifiers, preamplifiers, power amplifiers, tuners etc., and also Radford Audio Laboratory equipment, low distortion oscillator, distortion measuring set, audio noise meter etc.

ALL PRICES INCLUDE VAT

(Prices correct at 10/3/77)

Send stamp for free 38-page booklet "Choosing a Speaker"

All units guaranteed new and perfect Carriage and insurance

Speakers up to 12" 60p; 12" £1.00; 15" £1.75; 18" £2.50; Kits £1.00 each (£2.00 per pair); Tweeters & Crossovers 33p each.

WILMSLOW AUDIO

DEPT REC

LOUDSPEAKERS, MAIL ORDER AND EXPORT:
 SWAN WORKS, BANK SQUARE, WILMSLOW
 HIFI, RADIO & TV: SWIFT OF WILMSLOW, 5
 SWAN STREET, WILMSLOW CHESHIRE
 PA, HIFI & ACCESSORIES: WILMSLOW
 AUDIO, 10 SWAN STREET, WILMSLOW
 CHESHIRE

TELEPHONE: LOUDSPEAKERS, MAIL ORDER
 AND EXPORT WILMSLOW 29599
 HIFI, RADIO ETC., WILMSLOW 26213

Access & Barclaycard Orders
 accepted by phone

COMPLETE KITS IN STOCK FOR

**RADFORD STUDIO 90, RADFORD MONITOR 180,
 RADFORD STUDIO 270, RADFORD STUDIO 360,
 HIFI ANSWERS MONITOR (Rogers), HIFI NEWS NO
 COMPROMISE (Frisby), HI FI NEWS STATE OF THE
 ART, WIRELESS WORLD TRANSMISSION LINE
 (Bailey), PRACTICAL HIFI & AUDIO MONITOR (Giles),
 PRACTICAL HIFI & AUDIO TRIANGLE (Giles),
 POPULAR HIFI (Colloms) ETC.**

**On Dem. Answers Monitor, State of Art, etc.
 Construction leaflets for Radford, Kef, Jordan Watts,
 Tannoy, HIFI Answers Monitor, Free on request**

**PA Amplifiers, microphones etc. by
 Linear, Shure, Eagle, Beyer, AKG etc.
 FREE with orders over £10**

"Hi-Fi Loudspeaker Enclosures" Book

Stirling Sound

Q.V. MODULES FOR COST CONSCIOUS CONSTRUCTORS


MADE IN OUR OWN U.K. FACTORY

NEW THIS MONTH!

UNIT TWO FOR LOW AND HIGH OUTPUT CARTRIDGES

Here's another real money saver from Stirling Sound! Wire it into your system and style it how you wish. Full instructions make this completely straight-forward. Use Stirling Sound power amps. for choice, but: Unit Two will work superbly in any system. Active tone control circuits give bass and treble rise and cut of +5dB each, accepts inputs from 1 to 5 mV; RIAA corrected also adaptable for ceramics, etc. S/N ratio — 60dB; channel separation typically 56dB; frequency range — 30-20,000 Hz ±1dB. Tested before despatch (ready built) and guaranteed. For 10-20 V. operation.

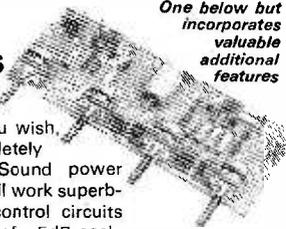Unit Two is styled similarly to Unit One below but incorporates valuable additional features



£10.85


100 watt R.M.S. POWER AMP and MATCHING 70 V. POWER SUPPLY Your chance to save £1.95

Today's best 100 watt value now made even greater by including the Stirling Sound SS.370 power supply together at the sensational price of £21.00*. A ruggedly built and guaranteed assembly, ideal for disco, P.A., guitar use etc. Normal selling price for items bought separately is £22.95* — already superb value — so don't delay — order NOW!



- SS.1100**
100 watt R.M.S. power amp with heatsink type mounting flange **£9.45***
 - Full size heat sink **£1.00**
 - SS.370**
70V/2A power supply with low volt take-off **£12.50***
 - SS.1100H**
(with large heat sink) and **SS.370** **£21.00***
- (P/P £1.00 where SS.370 is ordered)

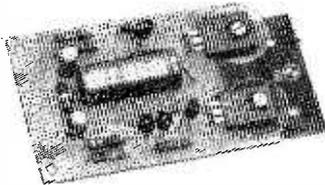MORE STIRLING SOUND Q.V. MODULES TO SAVE YOU MONEY



POWER AMPLIFIERS 3-40 Watts R.M.S.

- SS.103** 3 watt r.m.s. mono. Short-circuit protected. Uses one I.C. **£1.75**
 - SS.103-3** Stereo version of above using two I.C.s **£3.25**
 - SS.105** 4 watts r.m.s. into 3 ohms, using 12V **£2.25**
 - SS.110** 10 watts r.m.s. using 24V and 4 ohms load **£2.75**
 - SS.120** 20 watts r.m.s. into 4 ohms, using 34V **£3.25**
 - SS.140** Delivers 40 watts r.m.s. into 4 ohms using 45 volts supply unit such as **SS.345**. Ideal for small disco. P.A. etc. **£3.95***
- If ordering Stirling Sound power supply units with Modules **SS.103** to **SS.120**. V.A.T. becomes 12½%.

TONE CONTROLS/PRE-AMPS

- SS.100** Active toned control, stereo. 15dB on bass and on treble **£1.60**
- SS.101** Pre-amp for ceramic cartridges, etc. Stereo. Passive tone control details supplied. **£1.60**
- SS.102** Stereo pre-amp for low output magnetic P.U.s. R.I.A.A. corrected **£2.65**

LARGE 12p S.A.E. BRINGS LATEST STIRLING SOUND 16 LARGE PAGE EQUIPMENT AND COMPONENTS PRICE LIST

UNIT ONE TONE CONTROL/PRE-AMP

A real money saver this. Compatible with all relevant Stirling Sound modules as well as other makes.

Combined pre-amp with active tone-control circuits. ±15dB at 10KHz treble and 30Hz bass. Stereo, Vol./balance/treble/bass. 200mV out for 50mV in. Operates from 10 to 16V supply. **£7.80**

UNIT TWO — See above F.M. TUNING MODULES

- SS.201** Front end tuner, slow geared drive, two gang, A.F.C. facility. Tunes 88-108 MHz. **£5.00**
- SS.202** I.F. amplifier. Metering and A.F.C. facilities **£2.65**
- SS.203** Phase Lock Loop Stereo Decoder for use with the above or other FM mono tuners. A LED may be fitted. **£3.85**

- SS.203-1 COIL-TYPE STEREO DECODER** for use with **SS.201** and **SS.202**, recommended where economy is called for. Available in two forms:-
with I.C. for neg. earth **£2.50**
Transistor type for pos. earth **£2.00**

WHAT QV MEANS TO YOU

It means Stirling Sound **QUALITY** and **VALUE** from modules made in our own **Essex factory**. They are all tested and guaranteed and offer unbeatable value. Designed by highly specialist electronic engineers with wide experience of constructors' and experimenters' needs. **WATCH HOW THE STIRLING SOUND RANGE GROWS!**

POWER SUPPLY UNITS WITH 13-15V TAKE-OFF POINTS Except **SS.312**



NOW 8

TO CHOOSE FROM

Complete with mains transformers and low volt take-off points (not **SS.300**). All at 8% V.A.T. rate.

			P/P
SS.312	12V/1A	£3.75*	50p
SS.318	18V/1A	£4.15*	50p
SS.324	24V/1A	£4.60*	50p
SS.334	34V/2A	£5.20*	50p
SS.345	45V/2A	£6.25*	50p
SS.350	50V/2A	£6.75*	50p
SS.370	70V/2A	£12.50*	£1

SS.300 Power stabilising unit 10-50V adjustable for adding to unstabilised supplies. Built-in protection against shorting (p/p 35p) **£3.26***

SS.310/50 Stabilised power supply with variable output from 10V to 50V/2A. Built-in protection against shorting (p/p 50p) **£11.95***

WHEN ORDERING add 35p for p/p unless stated otherwise. V.A.T. add 12½% to total value of order unless price shows * when V.A.T. is 8%. Make cheques, etc. payable to Bi-Pre-Pak Ltd. Every effort is made to ensure correctness of information at time of going to press. Prices subject to alteration without notice.



A member company of the Bi-Pre-Pak group established 1959
Dept. RC.4, 220-224 WEST ROAD
WESTCLIFF-ON-SEA, ESSEX SSO 9DF
Telephone Southend (0702) 46344

Personal callers welcome

SPECIAL DE-LUXE 25 WATT HI-FI AMP BARGAIN

Made to sell at £7.25

LIMITED NUMBER AVAILABLE AT £5.20

This is the Bi-Pre-Pak **SS.125**, designed and made for the connoisseur market of hi-fi and technical specialists. Gives 25 w.r.m.s. into 8 ohms using 50V, 22 w.r.m.s. into 4 ohms from 33V. input sensitivity — 150 mV for full output; distortion less than 0.05% at all powers. With full instructions. **TESTED & GUARANTEED**. LIMITED NUMBER ONLY AVAILABLE. Ideal for test and lab. work, super hi-fi etc.



SS.125
Power Amp

THE MODERN BOOK CO

WORLD RADIO T.V. HANDBOOK 1977

by J. M. Frost Price: £5.50

UNDERSTANDING MICROPROCESSORS
by Motorola PRICE: £3.75

OP-AMP CIRCUIT DESIGN & APPLICATIONS
by J. Carr PRICE: £4.00

SIMPLE ELECTRONICS FOR MODELLERS
by I. R. Sinclair PRICE: £3.30

**HAM RADIO A PRACTICAL GUIDE
& HANDBOOK**
by K. Uilyett PRICE: £5.00

**BUILD-IT BOOK OF MINIATURE TEST &
MEASUREMENT INSTRUMENTS**
by R. P. Haviland PRICE: £3.30

MICROELECTRONICS
by C. L. Hallmark PRICE: £3.75

**TOWERS' INTERNATIONAL TRANSISTOR
SELECTOR**
by T. D. Towers PRICE: £5.10

RADIO COMMUNICATION HANDBOOK VOL. I
by RSGB PRICE: £8.00

THE RADIO AMATEUR'S HANDBOOK 1977
by A.R.R.L. PRICE: £6.50

ELECTRONICS FAULT DIAGNOSIS
by I. R. Sinclair PRICE: £3.25

**110 ELECTRONIC ALARM PROJECTORS FOR
THE HOME CONSTRUCTION**
by R. M. Marston PRICE: £2.25

CASSETTE TAPE RECORDERS
by J. Earl PRICE: £5.15

MASTER ELECTRONICS IN MUSIC
by T. D. Towers PRICE: £2.85

HI FI IN THE HOME
by J. Crabbe PRICE: £3.00

HI FI YEAR BOOK 1977
PRICE: £3.60

BUILD YOUR OWN WORKING ROBOT
by D. L. Heisermañ PRICE: £3.60

THE CATHODE RAY OSCILLOSCOPE & ITS USE
by G. N. Patchett PRICE: £4.00

PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

NEW STYLE SELF-BINDER

for
"Radio & Electronics
Constructor"



The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

PRICE

£1.20

including V.A.T.

P. & P. 30p

Owing to heavy demand please allow 27 days for delivery.

Available only from:—

Data Publications Ltd.

57 Maida Vale London W9 1SN

PRECISION IN YOUR HAND!

with the PRECISION
PETITE miniature electric drills



The Mk. II P1 drill illustrated is excellent for speedy work on p.c. boards, light metalwork and plastics. It operates from a 9-14v. d.c. source @ 2 amps and turns at 10,000 r.p.m. with 120 cmg. torque. A wide range of accessories is available.

ALSO the New P2 drill . . . more powerful, faster and of larger capacity has 4 collets for 0 to 3.5 mm. tool shanks, long ball bearing shaft and powerful motor running at 12,000 r.p.m. with 320 cmg. torque 12v d.c. @ 3 amps.

PRICES inc V.A.T.

● Mk. II Drill Stand	4.40	35 p.p.
● Mk. II Drill Only	8.79	35 p.p.
● Flexible Shaft	5.46	25 p.p.
● Transformer	6.00	70 p.p.
● Variable speed Transformer	8.25	70 p.p.
● S.30 Kit (Drill with 30 tools)	17.62	85 p.p.
● Kit Complete	33.48	1.15 p.p.
● P2 Drill only	16.50	65 p.p.
Replacement accessories		40p each
Postage for spares (any quantity)		15p


Sole Distributors: **PRECISION PETITE LTD.**

Send 9in. x 4in. SAE for illustrated leaflets and order form

119a High Street, Teddington, Middlesex TW11 8HG
Tel.: 01-977 0878 24hr Telephone Enquiry Service

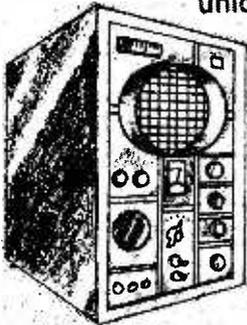1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lerna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

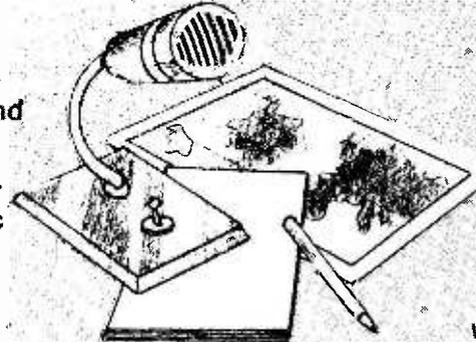2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,
P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ Block caps please

REC 47

THE 'NUTS & BOLTS' OF THOSE PROJECTS!

TRANSFORMERS

MINIATURE MAINS Pri 240V
with two independent secondary windings.

No.	Type	Price
2024	MT280 0.6v, 0-6v RMS 280mA	£1.30*
2025	MT150 0-12v, 0-12v RMS 150mA	£1.30*

MINIATURE MAINS Pri 240v

No.	Secondary	Price
2021	6v-0-6v 100mA	£1.30*
2022	9v-0-9v 100mA	85p
2023	12v-0-12v 100mA	£1.30*

1 amp MAINS Pri 240v

No.	Secondary	Price
2026	6v-0-6v 1 amp	£2.70* p&p 30p
2027	9v-0-9v 1 amp	£2.20* p&p 30p
2028	12v-0-12v 1 amp	£2.60* p&p 30p
2029	15v-0-15v 1 amp	£2.90* p&p 30p
2030	30v-0-30v 1 amp	£3.80* p&p 30p

STANDARD MAINS Pri 240v
Multi-tapped secondary mains transformers available in 1/2 amp 1 amp and 2 amp current rating. Secondary taps are 0-19-25-33-40-50v.
Voltages available by use of taps:
4, 7, 8, 10, 14, 15, 17, 19, 25, 31, 33, 40, 50, 25-0-25 volts.

No.	Rating	Price
2031	1/2 amp	£3.42* p&p 30p
2032	1 amp	£4.40* p&p 50p
2033	2 amp	£5.45* p&p 85p

AUDIO OUTPUT Pri 1.2k Secondary 5 ohms
200mW Dimensions 20 x 16 x 15
Order no. 2037 £0.25*

MINIATURE INTER/DRIVER

Pri 20k Secondary 1k Ratio 5:1
Order no. 2038 £0.23*

LT710 MIN INPUT

Pri 100k Secondary 1k 15 x 13 x 13mm
Order no. 3051 £0.42*

LT711 MIN DRIVER

Pri 10k Secondary 2k-C.T. 15 x 13 x 13mm
Order no. 2040 £0.35*

LT712 MIN OUTPUT

Pri 500 ohm Secondary 8 ohm 100mW 15 x 13 x 13mm
Order no. 2041 £0.28*

LT717 MIN INPUT

Pri 150k Secondary 1k 20 x 15 x 15
Order no. 2042 £0.52*

LT719 MIN INPUT

Pri 20k Secondary 1k 20 x 15 x 15mm
Order no. 2043 £0.32*

LT722 MIN DRIVER

Pri 10k Secondary 2k-C.T. 20 x 15 x 15mm
Order no. 2044 £0.32*

LT724 MIN OUTPUT

Pri 1.2-C.T. Secondary 3.2 & 8 ohm 200mW
Dimensions 20 x 15 x 15mm
Order no. 2045 £0.38*

LT726 MIN OUTPUT

Pri 500 ohm Secondary 3.2 & 8 ohm 200mW
Dimensions 20 x 15 x 15mm
Order no. 2046 £0.38*

LT728 MIN DRIVER

Pri 1k C.T. Secondary 500 ohm C.T.
Dimensions 25 x 20 x 20mm
Order no. 2047 £0.43*

LT729 MIN OUTPUT

Pri 200 ohm C.T. Secondary 3.2 & 8 ohm 400mW
Dimensions 25 x 20 x 20mm
Order no. 2048 £0.39*

LT730 MIN OUTPUT

Pri 500 ohm C.T. Secondary 3.2 & 8 ohms 500mW
Order no. 2049 £0.42*

L.E.D.'s

Type	Size	Order no.	Colour	Price
TIL209	.125"	1501	RED	.12p
TIL211	.125"	1502	GREEN	.25p
TIL213	.125"	1503	YELLOW	.25p
FLV115	2"	1504	RED	.12p
FLV310	2"	1505	GREEN	.25p
FLV410	2"	1506	YELLOW	.25p

2nd Grade L.E.D.'s

A pack of standard sizes and colours which fail to perform to their very rigid specification, but which are ideal for experiments.

Order no. 1507 £0.90

L.E.D. CLIPS

Pack of 5	Size	Order no.	Price
Pack of 5	.125"	1508/125	.15p
Pack of 5	2"	1508/2	.30p

NUTS & BOLTS

BA BOLTS — packs of B.A. Threaded cadmium plated screws, slotted cheese head. Supplied in multiples of 100.

Type	No.	Price	Type	No.	Price
1-0BA	839	£1.12	1-4BA	845	£0.51
1-0BA	840	£0.83	1-4BA	846	£0.38
1-2BA	842	£0.89	1-4BA	847	£0.33
1-2BA	843	£0.54	1-6BA	848	£0.50
1-2BA	844	£0.63	1-6BA	849	£0.30
			1-6BA	850	£0.33

BA NUTS — Packs of cadmium plated full nuts in multiples of 100.

Type	No.	Price	Type	No.	Price
05A	855	£0.90	4BA	857	£0.42
2BA	856	£0.60	6BA	858	£0.36

BA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 100.

Type	No.	Price	Type	No.	Price
08A	859	£0.19	4BA	861	£0.12
2BA	860	£0.15	6BA	862	£0.12

SOLDER TAGS — hot tinned supplied in multiples of 100.

Type	No.	Price	Type	No.	Price
08A	851	£0.42	4BA	853	£0.30
2BA	852	£0.36	6BA	854	£0.30

INSTRUMENT CASES. In two sections. Vinyl covered top and sides. aluminium bottom. front and back.

No.	Length	Width	Height	Price
156	8"	5 1/2"	2 1/2"	£0.15
156	11"	6"	3"	£1.80*
157	6"	4 1/2"	1 1/2"	£1.25*
158	9"	5 1/2"	2 1/2"	£1.60*

ALUMINIUM BOXES. Made from bright ali. folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2"	2 1/2"	1 1/2"	£0.62*
160	4"	2 1/2"	1 1/2"	£0.62*
161	4"	2 1/2"	1 1/2"	£0.62*
162	4 1/2"	2 1/2"	1 1/2"	£0.78*
163	4"	2 1/2"	2"	£0.64*
164	3"	2"	1 1/2"	£0.44*
165	7"	5"	2 1/2"	£1.04*
166	8"	6"	4"	£1.32*
167	6"	4"	4"	£0.86*

BRIDGE RECTIFIERS

SILICON 1 AMP	Type	Order No.	Price
50vRMS	BR1/50		£0.25
100vRMS	BR1/100		£0.28
200vRMS	BR1/200		£0.30
400vRMS	BR1/400		£0.35

SILICON 2 AMP	Type	Order No.	Price
50v	BR2/50		£0.40
100v	BR2/100		£0.45
200v	BR2/200		£0.50
400v	BR2/400		£0.55
1000v	BR2/1000		£0.65

FUSE HOLDERS & FUSES

Description	Order No.	Price
20mm x 5mm chassis mounting	506	£0.07*
1 1/2" x 1" chassis mounting	507	£0.10*
1 1/2" car inline type	508	£0.20*
Panel mounting 20mm	509	£0.22
Panel mounting 1 1/2"	510	£0.24

QUICK BLOW 20mm	Type	No.	Type	No.
150mA	611	1A	615	3A
250mA	612	1.5A	616	4A
500mA	613	2A	617	5A
800mA	614	2.5A	618	ALL 5p EACH

ANTI-SURGE 20mm	Type	No.	Type	No.
100mA	622	1A	625	2.5A
250mA	623	2A	626	3.15A
500mA	624	1.6A	627	5A

QUICK BLOW 1 1/2"	Type	No.	Type	No.
250mA	631	500mA	632	800mA
		ALL 7p EACH		

Type	No.	Type	No.
1A	635	2.5A	638
1.6A	636	3A	639
		ALL 6p EACH	

Just a selection from our huge stocks!

SEE OUR 1977 CATALOGUE

126 pages packed with valuable information

ORDER NOW ONLY 50p plus 15p p&p

SWITCHES

Description	No.	Price
D.P.D.T. miniature slide	1973	£0.10*
D.P.D.T. standard slide	1974	£0.12*
Toggle switch S.P.S.T.	1975	£0.33*
1 1/2 amp 250v AC		
Toggle switch D.P.D.T.	1976	£0.38*
1 amp 250v AC		
Rotary ON-OFF mains switch	1977	£0.42*
Push switch — Push to make	1978	£0.13*
Push switch — Push to break	1979	£0.18*

ROCKER SWITCH Colour No. Price
A range of rocker RED 1980 £0.22*
switches SPST — BLACK 1981 £0.22*
moulded in high WHITE 1982 £0.22*
insulation. Material BLUE 1983 £0.22*
available in a choice of YELLOW 1984 £0.22*
colours ideal for small LUMINOUS 1985 £0.22*
apparatus

Description	No.	Price
Miniature S.P.S.T. toggle		
2 amp 250v AC	1958	£0.50*
Miniature S.P.S.T. toggle		
2 amp 250v AC	1959	£0.55*
Miniature D.P.D.T. toggle		
2 amp 250v AC	1960	£0.65*
Miniature D.P.D.T. toggle centre off — 2 amp 250v AC	1961	£0.85*
Push button S.P.S.T. 2 amp	1962	£0.65*
250v AC		
Push button S.P.S.T. 2 amp	1963	£0.68*
250v AC		
Push button — D.P.D.T. 2 amp	1964	£0.80*

MIDGET WAFER SWITCHES
Single-bank wafer type — suitable for switching at 250v AC 100mA or 150v DC in non-reactive loads make-before-break contacts. These switches have a spindle 0.25" dia and 30° indexing.

Description	Order No.	Price
1 pole 12 way	1965	£0.48*
2 pole 6 way	1966	£0.48*
3 pole 4 way	1967	£0.48*
4 pole 3 way	1968	£0.48*

MICRO SWITCHES Order No. Price
Plastic button gives simple on-off action
Rating 10 amps 250v AC 1969 £0.20
Button gives 1 pole change over action
Rating 10 amp 250v AC 1970 £0.25

DISPLAYS

LED Type	Order No.	Price
BDL707 .3" single	1510	£0.80
BDL747 .6" single	1511	£1.50
BDL727 .5" double	1512	£1.80

COLD CATHODE 1TT 5087 ST
Side viewing indicator tubes. Displays 0-9 and decimal points. Wide viewing angle — operates from 180v with 16k series anode resistors — character height 16.5mm pin connections supplied.
Order No. 1513 Price £0.60

VOLTAGE REGULATORS

Positive Regulators TO220 case			
MVR 7805 5v	£1.25	MVR 7815 15v	£1.25
MVR 7812 12v	£1.25	MVR 7824 24v	£1.25

Negative Regulators TO220 case			
MVR 7905 5v	£2.00	MVR 7915 15v	£2.00
MVR 7912 12v	£2.00	MVR 7924 24v	£2.00

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER

V.A.T.
ADD 12 1/2% TO PRICES MARKED*
ADD 8% TO OTHERS EXCEPTING THOSE MARKED‡. THESE ARE ZERO

BI-PAK

Dept. C5, P.O. Box 6, Ware, Herts.

Shop at: 18, Baldock Street, Ware, Herts.
Open 9 to 5.30 Monday to Saturday

SEMI-CONDUCTORS COMPONENTS

PANEL METERS

4" RANGE

Size 4 1/4" x 3 3/4" x 1 3/8"

Value	No.	Price
0-50UA	1302	£4.50
0-100UA	1303	£4.50
0-500UA	1304	£4.50
0-1MA	1305	£6.00
0-50V	1306	£6.00

2" RANGE

Size 2 3/8" x 1 3/4" x 1 1/2"

Value	No.	Price
0-50UA	1307	£3.50
0-100UA	1308	£3.50
0-500UA	1309	£3.50
0-1MA	1310	£3.50
0-50V	1311	£3.50

MR2P TYPE

Size 42 x 42 x 30mm

Value	No.	Price
0-50UA	1313	£4.80
0-1MA	1315	£3.20

EDGEWISE

Size 3 1/2" x 1 1/8" x 2 1/4"

Value	No.	Price
0-1MA	1316	£4.05
0-500UA	1317	£4.05

MINIATURE

BALANCE/TUNING METER

Size 23 x 22 x 26mm

Sensitivity 100/0/100MA

No.	Price
1318	£1.95

BALANCE/TUNING

Size 45 x 22 x 34mm

Sensitivity 100/0/100UA

No.	Price
1319	£2.00

MIN. LEVEL METER

Size 23 x 22 x 26mm

Sensitivity 200UA

No.	Price
1320	£1.95

Vu METER

Size 40 x 40 x 29mm

Sensitivity 130UA

No.	Price
1321	£2.00

NEWNES TECHNICAL BOOKS

No. 229 BEGINNERS GUIDE TO ELECTRONICS PRICE £2.25†

No. 230 BEGINNERS GUIDE TO TELEVISION PRICE £2.25†

No. 231 BEGINNERS GUIDE TO TRANSISTORS PRICE £2.25†

No. 233 BEGINNERS GUIDE TO RADIO PRICE £2.25†

No. 234 BEGINNERS GUIDE TO COLOUR TELEVISION PRICE £2.25†

No. 235 ELECTRONIC DIAGRAMS PRICE £1.80†

No. 236 ELECTRONIC COMPONENTS PRICE £1.80†

No. 237 PRINTED CIRCUIT ASSEMBLY PRICE £1.80†

No. 238 TRANSISTOR POCKET BOOK PRICE £3.90†

No. 225 110 THYRISTOR PROJECTS USING SCRS & TRIACS PRICE £2.50†

No. 227 110 COS/MOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR PRICE £2.25†

No. 226 110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR PRICE £2.50†

No. 239 ELECTRONICS POCKET BOOK PRICE £3.75†

No. 238 TRANSISTOR POCKET BOOK PRICE £3.90†

No. 225 110 THYRISTOR PROJECTS USING SCRS & TRIACS PRICE £2.50†

No. 227 110 COS/MOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR PRICE £2.25†

No. 226 110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR PRICE £2.50†

No. 239 ELECTRONICS POCKET BOOK PRICE £3.75†

No. 239 30 PHOTOELECTRIC CIRCUITS & SYSTEMS PRICE £1.80†

Also a full '77 range of Technical and Data Books — See our Catalogue

ORDERING

PLEASE WORD YOUR ORDERS EXACTLY AS PRINTED, NOT FORGETTING TO INCLUDE OUR PART NUMBER.

V.A.T.

ADD 12 1/2% TO PRICES MARKED*
ADD 8% TO OTHERS EXCEPTING THOSE MARKED†. THESE ARE ZERO

SUPER UNTESTED PAKS

Pak No.	Order No.	Price
U50 100 Germ. Gold bonded DA47 diode	16130	£0.60
U51 150 Germ. TO181 diode	16131	£0.60
U52 100 Silicon Diodes 200mA OA200	16132	£0.60
U53 150 diodes 75mA 1N4148	16133	£0.60
U54 50 Sil Rect Top Hat 750mA	16134	£0.60
U55 20 Sil Rect Stud Type 3 Amp	16135	£0.60
U56 50 400mW Zeners D07 Case	16136	£0.60
U57 30 NPN Trans BC107/78 Plastic	16137	*£0.60
U58 25 PNP TO39 2N697/2N1711 sil	16138	*£0.60
U59 25 PNP TO59 2N2905 silicon	16139	£0.60
U60 25 PNP TO18 2N706 silicon	16140	£0.60
U61 25 PNP BFY50/51	16141	£0.60
U62 20 PNP Plastic 2N3906 silicon	16142	*£0.60
U63 20 PNP Plastic 2N3905 silicon	16143	*£0.60
U64 30 PNP Plastic BC117/78 Plastic	16144	*£0.60
U65 30 Germ. 0071 PNP	16145	*£0.60
U66 15 Plastic Power 2N3055 NPN	16146	£1.20
U67 10 T03 Metal 2N3055 NPN	16147	£1.20
U68 20 Unijunction trans 1S43	16148	£0.60
U69 10 1 amp SCR TO35	16149	£1.20
U70 8 3 amp SCR TO66 case	16150	£1.20

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

COMPONENT PAKS

PACK NO	QTY	ORDER NO	PRICE
C1	200	16164	*0.60
C2	150	16165	*0.60
C3	50	16166	0.60
C4	80	16167	*0.80
C5	5	16168	*0.60
C6	2	16169	*0.60
C7	1	16170	0.60
C8	10	16171	*0.60
C9	3	16172	*0.60
C10	15	16173	*0.60
C11	5	16174	*0.60
C12	30	16175	*0.60
C13	20	16176	*0.80
C14	1	16177	*0.60
C15	5	16178	0.60
C16	20	16179	0.60
C17	15	16180	*0.60
C18	4	16181	*0.60
C19	2	16182	*0.60
C20	1	16183	0.60
C21	15	16184	0.60
C22	50	16185	0.60
C23	60	16186	*0.60
C24	25	16186	*0.60
C25	30	16187	0.60

SLIDER PAKS

PACK NO	QTY	ORDER NO	PRICE
S1	6	16190	*0.60
S2	6	16191	*0.60
S3	6	16192	*0.60
S4	6	16193	*0.60
S5	6	16194	*0.60
S6	6	16195	*0.60

CASSETTES

BI-PAK LOW COST

Order No.	Price
C60 301	£0.36
C90 302	£0.45
C120 303	£0.84

AGFA COLOUR COMPACT

Order No.	Price
C60 304	£0.88
C90 305	£0.95
C120 306	£1.29

AGFA STEREOCHROME

Order No.	Price
C60 307	£1.29
C90 308	£1.56
C120 309	£2.22

AGFA S. F. D.

Order No.	Price
C60 310	£0.96
C90 311	£1.23
C120 312	£1.80

T.D.K. S.D.

Order No.	Price
C60 321	£0.96
C90 322	£1.44
C120 323	£2.04

T.D.K. E.D.

Order No.	Price
C60 324	£1.48
C90 325	£2.05

T.O.K. SUPER AVILYN

Order No.	Price
C60 326	£1.53
C90 327	£2.20

C30 LETTER TAPE Complete in mailing box — 15 mins each side.
Order No. 3193 Price £0.35

MAMMOTH I.C. PAK

APPROXIMATELY 200 PIECES

Assorted fall-out integrated circuits, including: Logic, 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked — you to identify.

Order No. 16223
OUR SPECIAL PRICE £1.20*

LINEAR PAKS

Manufacturers "Fall Outs" which include Functional and part Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

U721 30 Assorted Linear Types. 709-741-747-748-710-588 Etc.
ORDER NO. 16222 PRICE *£1.50

U785D FM STEREO DECODER
5 I.C.'s 76110 Eqv. to MC1310P-MA767. Data supplied with pak.
ORDER NO. 16229 PRICE *£1.50

U76A AUDIO POWER OUTPUT AMPLIFIERS
8 Assorted types SL403 76013 76003 etc
Data supplied with pak.
ORDER NO. 16228 PRICE *£1.00

74 SERIES PAKS

Manufacturers "Fall Outs" which include Functional and part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

74G 100 Gates assorted 7400-01-04-10-50-60 etc.
Order No. 16224 £1.20

74F 50 Flip-Flops assorted 7470-72-73-74-76-104-109 etc.
Order No. 16225 £1.20

74M 30 MSI Assorted Types. 7441-47-90-154 etc.
Order No. 16226 £1.20

VEROBOARD PAKS

VB1 Approx 30 sq. ins. various sizes. all 1" matrix.
Order No. 16199 £0.80

VB2 Approx 30 sq. ins. various sizes. 15" matrix.
Order No. 16200 £0.80

BIG VALUE JUMBO COMPONENT PAKS

Mixed Electronic Components

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight.
Order No. 16221. £1.50 + 85p p&p

C280 CAPACITOR PAKS

75 Mullard C280 capacitors, mixed values ranging from .01uF to 2.2uF complete with identification sheet.
Order No. 16204 *£1.20

CABLES

Description	Order No.	Price per Meter
CP1 Single Microphone	3126	0.07
CP2 Twin Microphone	3127	0.13
CP3 Stereo Screened	3128	0.14
CP4 4 core Screened	3129	0.25
CP5 4 core Indiv. Screened	3130	0.26
CP6 Single Mic/phone H/duty	3131	0.12
CP7 3 core Mains (5amp)	3132	0.09
CP8 2 core Oval (2.5amp)	3133	0.08
CP9 2 core Speaker	3134	0.07
CP10 Low-Loss U.H.F.	3135	0.14
CP11 Multicore: Bway	3146	0.25
	1536	0.40
CP12 Standard VHF Coax	3232	0.10

Just a selection from our huge stocks

SEE OUR 1977 CATALOGUE

126 pages packed with valuable information

ORDER NOW ONLY 50p plus 15p p&p

WORLD SCOOP! JUMBO SEMICONDUCTOR PAK

Transistors-Germ. and Silicon Rectifiers Diodes - Triacs - Thyristors - I.C.'s and Zeners. ALL NEW & CODED. Approx. 100 Pieces. Offering the amateur a fantastic bargain PAK and an enormous saving identification and data sheet in every pak.
Order No. 16222 £2.25

BI-PAK

DEPT C5, P.O. BOX 6, WARE, HERTS.
SHOP 18 BALDOCK ST, WARE, HERTS.
AT OPEN 9 to 5.30 Mon/Sat.

PRECISION POLYCARBONATE CAPACITORS

ALL HIGH STABILITY - EXTREMELY LOW LEAKAGE

440V AC (+10%)	63V DC Range	-1%	+2%	+5%
0.1µF (1 1/2" x 1 1/2")	68p	0.47µF	£1.32	77p
0.22µF (1 1/2" x 1 1/2")	86p	1.0µF	£1.56	91p
0.25µF (1 1/2" x 1 1/2")	92p	2.2µF	£1.98	£1.32
0.47µF (1 1/2" x 1 1/2")	£1.10	4.7µF	£2.82	£1.88
0.5µF (1 1/2" x 1 1/2")	£1.16	6.8µF	£3.48	£2.32
0.68µF (2" x 1 1/2")	£1.25	10.0µF	£4.98	£3.32
1.0µF (2" x 1 1/2")	£1.37	15.0µF	£7.14	£4.76
2.0µF (2" x 1 1/2")	£1.95	22.0µF	£9.66	£6.44

TANTALUM BEAD CAPACITORS - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V; 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL AT 12p EACH: 10 for £1.10; 50 for £5.00.

TRANSISTORS:

BC107/8/9	9p	*BC183/183L	11p	*BF194	12p	BFY51	20p
*BC114	12p	*BC184/184L	12p	*BF196	13p	BFY52	20p
*BC147/8/9	10p	*BC212/212L	12p	*BF197	13p	OC71	20p
*BC157/8/9	12p	*BC547	12p	AF178	10p	2N3055	50p
*BC182/182L	11p	*BC558A	12p	BFY50	20p	*2N3702/411p	

1N914 6p; 8 for 45p; 18 for 90p. 1N916 8p; 6 for 45p; 14 for 90p. 1S44 5p; 11 for 59p; 26 for £1.00. 1N4148 5p; 6 for 27p; 12 for 48p.

LOW PRICE ZENER DIODES: 400mW; Tol. +5% at 5mA. Values available: 3V; 3.6V; 4.7V; 5.1V; 5.6V; 6.2V; 6.8V; 7.5V; 8.2V; 9.1V; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V. All at 7p each; 5 for 33p; 10 for 65p. SPECIAL: 100 Zeners for £6.00.

RESISTORS: High stability low noise carbon film 5%, 1/4 W at 40°C; 1/4 W at 70°C. E12 series only - from 2.2Ω to 2.2MΩ ALL AT 1p EACH; 8p or 10 of any one value; 70p for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) £5.00.

SILICON PLASTIC RECTIFIERS - 1.5 Amp - Brand new wire ended D027: 100 P.I.V. - 7p (4/26p); 400 P.I.V. - 8p (4/30p).

BRIDGE RECTIFIERS: 2 1/2 Amp. 200V - 40p; 350V - 45p; 600V - 55p.

SUBMINIATURE VERTICAL PRESETS - 0.1W only: ALL AT 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1K, 2.2K, 4.7K, 6.8K, 10K, 15K, 22K, 47K, 100K, 220K, 680K, 1M, 2.5M, & 5M.

PLEASE ADD 8% VAT TO ALL ITEMS EXCEPT THOSE MARKED WITH * WHICH ARE 12 1/2%. PLEASE ADD 20p POST AND PACKING ON ALL ORDERS.

Send S.A.E. for lists of additional ex-stock items. Wholesale price lists available to bona-fide companies. ALL EXPORT ORDERS PLEASE ADD COST OF SEA/AIR MAIL.

MARCO TRADING


Dept. P1, The Old School, Edstaston, WEM, Salop. Tel: WHIXALL (Salop) 464/5 (STD 094872) (Props: Minicost Trading Ltd.).

NOW AVAILABLE . . .

LATEST BOUND VOLUME No. 29

of

"Radio & Electronics Constructor"

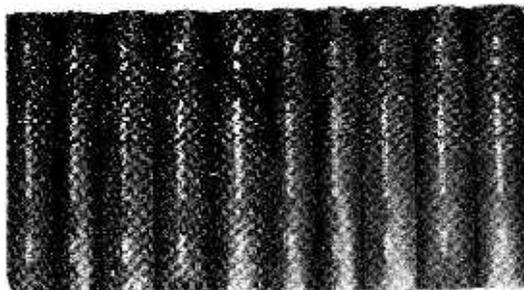

AUGUST 1975 to JULY 1976

Comprising
776 pages **PRICE £3.10 P&P 75p**
inc. index

BOUND VOLUME No. 27
(August 1973 to July 1974)

BOUND VOLUME No. 28
(August 1974 to July 1975)

PRICES
VOL. 27

£2.40 per volume P&P 75p

VOL. 28

£2.75 per volume P&P 75p

Limited number of these
volumes still available.


We regret all earlier volumes are now
completely sold out.

Available only from

DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

Still the *simplest, fastest* way
of constructing your
electronic circuits. Vero
Electronics Ltd manufacture
boards to suit most of your
requirements, including,
Verostrip, Dual in line I.C.
boards, Plain Boards, etc. A
new catalogue is available
(price 10p + S.A.E. at least 7" x 9")

VEROBOARD

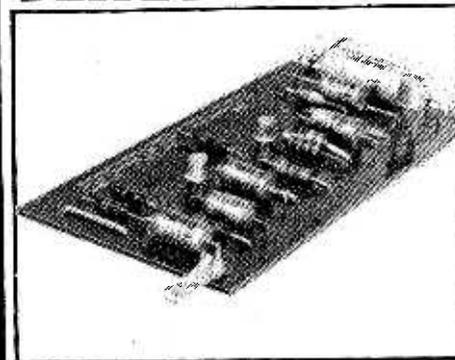

Vero Electronics Limited, Retail Dept.,
Industrial Estate, Chandler's Ford, Hants., SO5 3ZR
Telephone: Chandler's Ford 2956 (STD 04125)

RETURN OF POST MAIL ORDER SERVICE



NEW BSR HI-FI AUTOCHANGER

STEREO ANO MONO
Plays 12", 10" or 7" records
Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. AC 200/250V
Size 13 1/2" x 11 1/2"
Above motor board 3 1/2"
Below motor board 2 1/2"
With STEREO/MONO CARTRIDGE **£11.95** Post 75p
Single player version with cueing device **£13.50**




ELAC 10in HI-FI UNIT
10 watt, 15 ohm full range unit, 35 to 16,000 c.p.s. Base resonance 40 c.p.s.
BARGAIN PRICE £4.50 post 45p

HEAVY METAL PLINTHS
With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Silver grey finish. Size 12 1/2" x 14 1/2" x 7 1/2"
Size 16 x 13 1/2" x 7in **£7.50** Post £1.25

EXTRA LARGE PLINTH & COVER
Size: 20in. x 19 1/2in. x 9in. TEAK FINISH
CALLERS ONLY £18.50

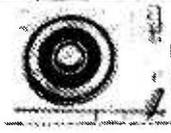
TINTED PLASTIC COVERS Post £1
Size: A 14 1/2in. x 12 1/2in. x 4 1/2in. £2.50 B 20 1/2in. x 12 1/2in. x 4 1/2in. £3.00 C 17 1/2in. x 13 1/2in. x 3 1/2in. £3.25 D 19in. x 14 1/2in. x 4 1/2in. £3.50 E 16 1/2in. x 14in. x 4in. £3.50
Ideal for record decks, tape decks, etc.



R.C.S. DISCO DECK SINGLE RECORD PLAYER
Fitted with auto stop, compatible cartridge. Base-plate. Size 11in. x 8 1/2in. Turntable. Size 7in. diameter. A/C mains. 220/250V motor has a separate winding 14 volt to power a small amplifier.
3 speeds plays all size records
Two for £13.

COMPLETE STEREO SYSTEM
Two full size loudspeakers 13 1/2" x 10" x 3 1/2". Player unit clips to loudspeakers making it extremely compact. Overall size only 13 1/2" x 10" x 8 1/2". 3 watts per channel, 2 amps all records
33 rpm 45 rpm. Separate volume & tone controls 240V AC mains
Attractive Teak finish Weight 13lbs
Bargain Price **£22.50** 85p carriage

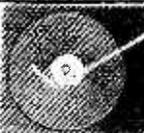GARRARD MINICHANGER
Plays all size records. 3 speed. Size 12 x 8 1/2in. Complete with stereo/mono cartridge
£9.95 Post 75p



CASSETTE RECORDER MOTOR ONLY. 6 Volt. Will replace many types. Ideal for models £1.25

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in. sides 6 x 4in. 70p; 8 x 6in. 90p; 10 x 7in. £1.15; 14 x 9in. £1.50; 16 x 6in. £1.45; 12 x 3in. 87p; 16 x 10in. £1.70. All boxes, many sizes in stock.

ALUMINIUM PANELS 18s.w.g. 6 x 4in. 15p; 8 x 6in. 25p; 10 x 7in. 30p; 12 x 5in. 30p; 12 x 8in. 40p; 16 x 6in. 45p; 14 x 9in. 50p; 12 x 12in. 55p; 16 x 10in. 75p.

ALUMINIUM ANGLE BRACKET 6in long x 1/2 x 1/2 15p.
1 1/2inch DIAMETER (VA) CHANGE SWITCHES 45p. EA. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way. 1 p. 1 1/2 way, or 4 p. 2-way, or 4 p. 3-way

TOGGLE SWITCHES. sp. 20p. dp. 25p dp. dt. 30p.
D.P.D.T. CENTRE OFF 65p. **S.P.D.T. CENTRE OFF** 45p.
Many types TOGGLE SWITCHES in stock

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2" x 1 1/2" x 3". Response 20 cps to 250 Kcs. 26 db gain.
For use with valve or transistor equipment. Post
Full instructions supplied. Details S.A.E. **£1.46** 30p

NEW ELECTROLYTIC CONDENSERS

2/350V 20p	250/25V 18p	16+16+16/275V 45p
4/350V 20p	500/25V 20p	16+50/300V 50p
8/350V 22p	100+100/275V 65p	32+32/450V 75p
16/350V 30p	150+200/275V 70p	100+50+50/350V 85p
32/500V 50p	8+8/450V 50p	32+32+32/350V 75p
25/25V 10p	8+16/450V 50p	30,000/25V 95p
50/50V 10p	16+16/450V 50p	4700/63V 95p
100/25V 10p	32+32/350V 50p	420/600V £1.50

LOW VOLTAGE ELECTROLYTIC CONDENSERS
22, 25, 50, 68, 150, 470, 500, 680, 1500, 2200, 3300, mfd all 6 volt 10p ea.
22, 25, 50, 100, 150, 200, 220, 330, 470, 680, 1000, 1500, 2200, mfd all 10 volt 10p ea.
220, 330, 1000, 4700, mfd all 4v. 10p ea.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p; 4700/63V 95p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 35V 85p; 50V 95p.
500V-0.001 to 0-1 10p; 0.25 12p; 0.47 25p.
CERAMIC 1pF to 0.01mF. 5p. Silver Mica 2 to 5000pF. 5p.
PAPER 350V/0.1 7p, 0.5 18p, 1mF or 2mF 150V 15p.
MICRO SWITCH single pole changeover 20p.
MICRO SWITCH sub min 25p.
TWIN GANG. "0-0" 208pF + 176pF £2. TWIN 365pF 50p.
Slow motion drive 365pF + 365pF with 25pF + 25pF 65p.
500mF standard twin gang 70p. 120 pF twin gang 50p.

ELAC 9 x 5in. HI-FI SPEAKER TYPE 59RM. THIS FAMOUS AND WIDELY USED UNIT NOW AVAILABLE AT BARGAIN PRICE **£3.45** 10 WATT, 8 OHM. CERAMIC MAGNET.

NEON PANEL INDICATORS. 250V Red or Amber. 30p
RESISTORS. 1w. 1/2w. 1/4w. 20%, 2%, 5%, 10% to 10M.
HIGH STABILITY. 10% to 10 meg. 12p.
Ditto 5%. Preferred values. 10 ohms to 10 meg. 5p.
WIRE-WOUND RESISTORS. 5 watt, 10 watt, 15 watt. 10 ohms to 100k. 12p each; 2w 0.5 ohm to 8.2 ohms 15p.
TAPE OSCILLATOR COIL. Valve type 35p
FERRITE ROD 6" x 1/2" 30p; 6" x 3/4" 20p; 3" x 3/4" 10p.
TAG STRIP 28 way 14p.

MAINS TRANSFORMERS ALL POST 50p each
250-0-250V 80mA. 6-3V 2A £2.95
250-0-250 80mA. 6-3V 3-5A. 6-3V 1A or 5V 2A £4.60
350-0-350 80mA. 6-3V 3-5A. 6-3V 1A or 5V 2A. £5.80
300-0-300 120mA. 6-3V 4A C.T. 6-3V 2A £7.00
220v 45ma. 6-3v 2a. £1.75
HEATER TRANS 6-3v 3 amps £1.45 1amp. 95p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs 2 amps 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30V £4.60
1amp 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60, £4.60
2a. 6, 8, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £7.00
3a. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £8.70
5a. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60 £11.25
5. 8, 10, 16v 1/2a £2. 6-0-6v 500mA £1. 9v 1a £1
12v 300mA £1. 12v 500mA £1. 12v 750mA £1.
10v 4A tapped 10v or 30v £2.95. 20v 3a £2.
40v 2a £2. 75 30v 5A and 34v 2A ct. £3.50.
20-0-20v 1a £2. 30v 1 1/2a £1.75. 20v 1/2a £1.75. 1a £2
1 amp Transformer, mounted on panel with input and output fuses supplies 0.20v, 40v, 60v or 20-0-20v £3.50
A.U. TRANSFORMERS 115v to 230v or 230v to 115v
150w £5; 250w £6; 400w £7; 500w £8.
CHARGER TRANSFORMERS. Input 200/250v for 6 or 12v 1 1/2a £2.75 4a £4.60.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v outputs 1 1/2a 40p; 2a 55p, 4a 85p.

R.C.S. STABILISED POWER PACK KIT
All parts including printed circuit and instructions to build this unit. Voltages available: 6v, 7.5v, 9v, 12v. Up to 100mA output. **£2.95** Post 45p
Please state voltage required.

STEREO FM/AM TUNER AMPLIFIER CHASSIS BY KUBA
This all transistor chassis has push button selection for long, medium short and V.H.F. wave bands. Features A.F.C. on V.H.F. band with automatic Stereo beacon light. Volume tone and balance controls with push button mains on/off switch. An built-in variable capacitor and 100% efficient 100% efficient 100% efficient. Four watts per channel output. (Chassis size 17 1/2 x 4 x 5in) **£33.50** POST £1.50

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With tweeter **£5.95**
And crossover, 10 watt **Post 45p**
Size: 3 or 8 ohm **£8.50**
15 watt version **£15.50**
8 or 15 ohm **£9.50**
20 watt version **£7.50**
8 or 15 ohm **£6.50**
as illustrated **£6.50**
Bass units only 20W **£6.50**
Bass units only 15W **£4.95**
Bass units only 10W **Post 65p**

Bookshelf Cabinet £7.50
Teak Veneer. For above units. Post £1.50

R.C.S. 10 WATT AMPLIFIER KIT

This kit is suitable for record players, tape play back, guitars, electronic instruments or small P.A. systems. Two versions are available. A mono kit or a stereo kit. The mono kit uses 13 semiconductors. The stereo kit uses 22 semiconductors with printed front panel and volume, bass and treble controls. Spec. 10 watts output into 8 ohm and 15 ohms. Response 20 cps to 30Kc/s. Input from 20mV high imp. Size 9 1/2in x 3in x 2in.
Mono kit **£11.25** Stereo kit **£17.50** Post 45p

LOUDSPEAKERS P.M. 3 ohms. 7 x 4in. £1.25; 6 1/2in. £1.50; 8 x 5in. £1.60; 8in. £1.75; 10 x 6in. £1.90; 10in. £2.50
SPECIAL OFFER LOUDSPEAKERS! All Brand New. 3 ohm. 2 1/2in. 2 1/2in. 3in. 5in. 8 ohm. 2 1/2in. 2 1/2in. 5 x 3in. 5in. 15 ohm. 3 1/2in. 5in. 6 x 4in. 5 x 3in. 7 x 4in. 25 ohm. 7in. 3in. 5 x 3in. 7 x 4in. 35 ohm. 3in. 5in. 80 ohm. 2 1/2in. 2 1/2in. 120 ohm. 3in. **£1.25 EACH**

TWEETER VOLUME CONTROL 15 ohm 10 watt with 1in. long threaded bush for wood panel mounting. Will suit all tweeters **75p**

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in. diameter 4W £2.50, 10in. diameter 5W £2.95, Post 25p. 12in. diameter. 6W £3.50, 3 or 8 or 15 ohm models. **SPEAKER COVERING MATERIALS.** Samples Large S.A.E. Horn Tweeters 2-16Kc/s 10W 8 ohm or 16 ohm £3.60. Dr. Luke Horn Tweeters 2-18 Kc/s. 15W. 8 ohm £3.60. **TWO-WAY 3,000 cps CROSS OVERS** 3, 8 or 15 ohm £1.90 **3-WAY CROSSOVER** 850 cps and 3000 cps (25 watt) £2.20 **100 WATT HORN TWEETER** £10.95

GOODMANS CONE TWEETER £3.25
18,000 cps. 25 watts. 8 ohm.
5 1/2in. Woofer 10 watt. Price £4.95.

ELECTRO MAGNETIC PENDULUM MECHANISM
1 1/2v d.c. operation over 250 hrs continuous on SP2 battery. Fully adjustable. Swing and speed. Ideal displays teaching electro magnetism or for metronome, strobe etc. 55p. Post 20p

WEYRAD TYPE COILS
P50/1AC 60p | RA2W £1.20 | Twin Gang £2
P50/2CC 40p | OPT1 85p | Printed Circuit 85p
P50/3CC 40p | LFDT4 85p

COAXIAL PLUG 10p. **PANEL SOCKETS** 10p. **Line 18p.** **OUTLET BOXES, SURFACE MOUNTING** 40p
BALANCED TWIN RIBBON FEEDER 300 ohms. 5p. **yd JACK SOCKET** Std. open-circuit 20p. closed circuit 25p. **Chrome Lead Socket** 45p. **Phono Plugs** 10p. **Phono Socket** 8p. **JACK PLUGS** Std. Chrome 30p. 3.5mm Chrome 15p. **DIN SOCKETS** Chassis 3-pin 10p. 5-pin 10p. **DIN SOCKETS** Lead 3-pin 18p. 5-pin 25p. **DIN PLUGS** 3-pin 18p. 5-pin 25p. **VALVE HOLDERS** 5p. **CERAMIC** 10p. **CANS** 5p.

R.C.S. 100 WATT VALVE AMPLIFIER CHASSIS

Professional model. Four inputs. Treble, Bass, Master Volume Controls. Ideal disco, P.A. or group. 5 speaker outputs very robust job **£85** plus £2.50 carr. S.A.E. for details

NEW MIXER/AMP 150 WATT
PROFESSIONAL TRANSISTOR AMPLIFIER **£68**
4 inputs. 3 outputs separate volume treble. Carr. £1.50 and bass controls. Ideal disco or group. P.A. amplifier. Send for leaflets on Disco Gear, Cabinets, etc.

RADIO COMPONENT SPECIALISTS

Minimum post 30p. Access and Barclaycard welcome Phone your Order Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)
Components Lists 10p. Cash price includes VAT Rail Selhurst. Tel. 01-684 1665

TRADE COMPONENTS

JUST A FEW BARGAINS ARE LISTED - SEND STAMPED ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS. PAY A VISIT. OVER 90% OF STOCK BELOW QUANTITY WHOLESALE PRICE. ALL PRICES INCLUDE THE ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE

Goods sent at customer's risk, unless sufficient payment for registration (1st class letter post) or compensation fee (parcel post) included.

VALVE BASES	
Printed circuit B9A-B7G	3p
Chassis B7-B7G	9p
Shrouded chassis B7G-B9A-B8A	10p
B12A tube	9p

Speaker 6" x 4" 5 ohm ideal for car radio 70p

TAG STRIP	6 way	3p	5 x 50pF or 2 x 220pF
9 way	5p	Single	1p trimmers 20p

BOXES — Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 32½p

Clear perspex sliding lid, 46 x 39 x 24mm 10p

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 48p; 80 x 150 x 50mm black 70p; 109 x 185 x 60mm black £1.10

ALUMINIUM

3" x 2" x 1"	39p	4" x 2½" x 2"	44p	12" x 5" x 3	£1.20
2¾" x 5¼" x 1½"	45p	4" x 5¼" x 1½"	54p	10" x 7" x 3"	£1.22
4" x 4" x 1½"	45p			12" x 8" x 3"	£1.50
4" x 2¾" x 1½"	45p				

SWITCHES			
Pole	Way	Type	
4	2	Sub. Min. Slide	18p
6	2	Slide	20p
1	3	13 amp rotary	6p
2	1	2 Amp 250V A.C. rotary	20p

12 bank, multi-pole/way push-button (4 interlocking) 30p

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 20p
S.P.S.T. dot 13 amp, oblong, push-fit, rocker 15p

AUDIO LEADS

5 pin din plug 180° both ends 1½ Mtr., 80p
3 pin din to open end, 1½ yd twin screened 35p
Phono to Phono plug, 6ft. 35p

COMPUTER AND AUDIO BOARDS

VARYING PANELS WITH ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES ETC.

3lb for 85p + 85p post and packing
7lb for £1.95 + £1.20 post and packing

1k horizontal preset with knob	3p	3" Tape Spools	3p
		1" Terry Clips	4p
		12 Volt Solenoid	30p

TV KNOB

Dark grey plastic for recessed shaft (quarter inch) with free shaft extension 5p

ENM Ltd. cased 7-digit counter 2¼ x 1¾ x 1¼" approx. 12V d.c. (48 a.c.) or mains 75p

ZM1162A INDICATOR TUBE

0-9 Inline End View. Rectangular Envelope 170V 2.5M/A £1

REGULATED TAPE MOTOR

9v d.c. nominal approx 1½" diameter 60p

12v 8 amp Transformer £2.50 (p&p 85p)

Ferric Chloride, Anhydrous mil. spec. 1lb bag 40p

Car type panel lock and key 40p
18 volt 4 amp charger, bridge rectifier 79p
GC10/4B £3.00

Telescopic aerial Closed 9½", open 38½"
Fitted right angle TV plug, 50p

Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 32½p

Clear perspex sliding lid, 46 x 39 x 24mm 10p

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 48p; 80 x 150 x 50mm black 70p; 109 x 185 x 60mm black £1.10

ALUMINIUM

3" x 2" x 1"	39p	4" x 2½" x 2"	44p	12" x 5" x 3	£1.20
2¾" x 5¼" x 1½"	45p	4" x 5¼" x 1½"	54p	10" x 7" x 3"	£1.22
4" x 4" x 1½"	45p			12" x 8" x 3"	£1.50
4" x 2¾" x 1½"	45p				

RESISTORS
¼ ¼ ¼ watt 1p
1 watt 2p
Up to 15 watt wire wound 6p
1 or 2% five times price.
Cinch 8 way std 0.15 pitch edge connector 20p

Semiconductor Data Book 171 pages. Covers Japanese types 25A12 through to 2SD335. Type/connection/parameter details £1.50
No VAT

POTS
Log or Lin, single or dual, switched carbon or wire-wound, rotary or slider. All types 16p
1.5m Edgetype 3p

Skeleton Presets
Slider, horizontal or vertical standard or submin. 5p

THERMISTORS
VA1008, VA1034, VA1039, VA1040, VA1055, VA1066, VA1082, VA1100 } 10p
VA1077, VA1005, } 15p

RELAYS
12 volt S.P.C.O octal mercury wetted high speed 40p
P.O. 3030 type, 1,000 OHM coil, 4 pole c/o 40p
Mains or 12v d.p.c.o heavy duty octal 50p

3.5mm metal stereo plug 20p

JAP 4 gang min. sealed tuning condensers 20p

ELECTROLYTICS MFD/VOLT. Many others in stock
70- 200- 300- 450-
Up to 10V 25V 50V 75V 100V 250V 350V 500V MFD

10	4p	5p	6p	8p	10p	12p	16p	20p
25	4p	5p	6p	8p	10p	15p	18p	20p
50	4p	5p	6p	9p	13p	18p	25p	—
100	5p	6p	10p	12p	19p	20p	—	—
250	9p	10p	11p	17p	28p	—	85p	£1
500	10p	11p	17p	24p	45p	—	—	—
1000	13p	22p	40p	75p	—	£1.50	—	—
2000	23p	37p	45p	—	—	—	—	—

As total values are too numerous to list, use this price guide to work out your actual requirements

8/20, 10/20, 12/20 Tubular tantalum 20p each
16-32/275V. 100-100/150V. 100-100/275V 30p;
50-50/385V. 12,000/12V. 32-32-50/300V. 20-20-20/350V 60p; 700 mfd/200V £1.00; 100-100-100-150-150/320V £2.00.

RS 100-0-100 micro amp null indicator
Approx. 2" x ¾" x ¾" £1.50

INDICATORS
Bulgin D676 red, takes M.E.S. bulb 30p
12 volt or Mains neon, red pushfit 18p
R.S. Scale Print, pressure transfer sheet 10p

CAPACITOR GUIDE - maximum 500V

Up to .01 ceramic 3p. Up to .01 poly 4p.
.013 up to .1 poly etc. 5p. .12 up to .68 poly etc. 6p. Silver mica up to 360pF 8p, then to 2,200pF 11p, then to .01 mfd 18p.
8p. .1/600: 12p. .01/1000, 8/20. .1/900, .22/900, 4/16. .25/250 AC (600VDC) 40p.
5/150, 9/275AC, 10/150, 40/150.

Many others and high voltage in stock.

FORDYCE DELAY UNIT
240 volt A.C./D.C. Will hold relay, etc., for approx. 15 secs after power off. Ideal for alarm circuits, etc. £1

CONNECTOR STRIP
Belling Lee L1469, 4 way polythene. 6p each

1½ glass fuses 250 m/a or 3 amp (box of 12) 6p
Bulgin. 5mm Jack plug and switched socket (pair) 30p
Reed Switch 28mm. body length 5p

MAINS DROPPERS

66+66-158 ohm, 66+66+137 ohm
17+14-6 ohm, 266+14+193 ohm } 5p
50+40+1k5 ohm }
285+575+148+35 ohm } 5p
25+35+97+59+30 ohm }

5½" x 2½" Speaker, ex-equipment 3 ohm 30p
2 Amp Suppression Choke 8p

3 x 2½ x 1½" } PAXOLINE 4p
4½ x ½ x ½" } 1p
PCV or metal clip on MES bulb Holder 4p
VALVE RETAINER CLIP, adjustable 2p

OUTPUT TRANSFORMERS

Sub-miniature Transistor Type 25p
Valve type. 40p

Transformers 6 volt ½A 25p
Whiteley Stentorian 3 ohm constant impedance volume control way below trade at 80p
RS Yellow Wander Plug Box of 12 25p
18 SWG multicore solder 2½p foot

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request

Terms: Payment with order Telephone: 01-223 5016

SEMICONDUCTORS

Full spec marked by Mullard, etc. Many other types in stock

AC107	16p	BC555/6/7/8/9	9p
AC128/176	8p	BCX32 36	12p
ACY28	19p	BCY40	50p
AD149	40p	BCY70/1/2	12p
AF116	161p	BD112/3	50p
AF124/6/7	25p	BD115/6	31p
AF139	20p	BD131/2/3	35p
AF178/80/81	30p	BD135/6/7/9	30p
AF239	30p	BD140/142	30p
ASY27/73	30p	BD201/2/3/4	80p
		BD232/4/5/8	49p
		BDX77	£1
		BD437	50p
		BF115/167/173	15p
		BF178/9	20p
		BF180/112/3/4/5	15p
		BF194/5/6/7	6p
		BF194A, 195C	8p
		BF200A, 258, 324	20p
		BF202/3	30p
		BF336	£1
		BFS28 Dual Mosfet	27p

BFW10/11 F.E.T.	40p
BFW30	£1
BFW57/58	17p
BFX12/29/30	20p
BFX84/88/89	17p
BFY50/51/52	13p
BFY90	50p
BR101	30p
BRY99/56	26p
BSV64	30p
BSV79/80 F.E.T.s	80p
BSV91 Mosfet	90p
BSX20/21	14p
BSY40	27p
BSY95A	12p
CV7042 (OC41/44 ASY63)	5p
GET111	40p
OC35	45p
ON222	20p
TIP30/3055	45p
TIS88A F.E.T.	23p
ZTX300/341	7p
2N393 (MA393)	30p
2N456A	50p
2N929	14p
2N967	40p
2N1507/2219	15p

2N2401	30p
2N2412	70p
2N2483	23p
2N2904/5/6/7/7A	15p
2N3053	14p
2N3055 R.C.A.	50p
2N3704	8p
2N3133	20p
2N4037	34p
2N5036 (Plastic 2N3055)	30p
25A141/2/360	31p
25B135/6/457	20p
40250 (2N3054)	30p

OTHER DIODES

1N916	6p
1N4148	2p
BA145	14p
Centercel	24p
BZY61/BA148	10p
BB103/110 Varicap	15p
BB113 Triple Varicap	37p
BA182	13p
OA5/7/10	15p
BZY88 Up to 33 volt	7p
BZX61 11 volt	15p
BR100 Diac	15p

BRIDGE RECTIFIERS

Amp	Volt		
1	1,600	BYX10	30p
1	140	OSH01-200	26p
1.4	42	BY164	40p
0.6	110	EC433	8p
5	400	Texas	90p

NEW B.V.A. VALVES

6BW7	60p
EB91	34p
ECH81	34p
ECL80	36p
EF80	34p
EF183	34p
EY86/7	34p
PC86	53p
PC88	53p
PC97	36p
PCC84	34p
PCC89	45p
PCC189	45p
PCF80	34p
PCF82	34p
PCF801	46p
PCL82	34p
PL81	35p
PY500A	80p
PY81/800	38p
R20/U26	50p

INTEGRATED CIRCUITS

TAA700	£2.00
TBA800	£1.00
741 8 pin d.i.l. op. Amp	24p
TAD100 AMRF	£1
CA3001 R.F. Amp	50p
CD4013 CMOS	36p
TAA300 1wt Amp	£1
TAA550 Y or G	22p
TAA263 Amp	65p
7400	10p
7402/4/10/20/30	14p
7414	56p
7438/74/86	24p
7483	69p
LM300, 2-20 volt	£1
74154	90p
TBA550Q	£1.50

RECTIFIERS

Amp	Volt		
IN4004/5/6	1	4/6/800	5p
IN4007/BYX94	1	1250	5p
BY103	1	1,500	181p
SR100	1.5	100	7p
SR400	1.5	400	8p
REC53A	1.5	1,250	14p
LT102	2	30	10p
BYX38-300R	2.5	300	40p
BYX38-600	2.5	600	45p
BYX38-900	2.5	900	50p
BYX38-1200	2.5	1,200	55p
BYX48-300R	2.5	300	26p
BYX49-600	3	600	35p
BYX49-900	3	900	40p
BYX49-1200	3	1,200	52p
BYX48-300R	6	300	40p
BYX48-600	6	600	50p
BYX48-900	6	900	60p
BYX48-1200R	6	1,200	80p
BYX72-150R	10	150	35p
BYX72-300R	10	300	45p
BYX72-500R	10	500	55p
BYX42-300	10	300	30p
BYX42-600	10	600	65p
BYX42-900	10	900	80p
BYX42-1200	10	1,200	95p
BYX46-300R*	15	300	£1.00
BYX46-400R*	15	400	£1.50
BYX46-500R*	15	500	£1.75
BYX46-600*	15	600	£2.00
BYX20-200	25	200	60p
BYX52-300	40	300	£1.75
BYX52-1200	40	1,200	£2.50

OPTO ELECTRONICS

Diodes		Photo transistor	
TIL209 Red	10p	BPX29	80p
BPX40	50p	OC71	34p
BPX42	80p		
BPY10	80p		
(VOLT/AC)			
BPY68	} 80p	BIG L.E.D. 0.2"	
BPY69		2v 50mA max.	
BPY77		ORANGE	14p
		YELLOW	14p
		RED	14p

THYRISTORS

Amp	Volt		
1	240	BTX18-200	30p
1	400	BTX18-350	35p
1	240	BTX30-200	30p
15	500	BT107	£1
6.5	500	BT101-500R	90p
6.5	500	BT109-500R	£1.00
20	600	BTW92-600RM	£3.00
15	800	BTX95-800R Pulse Modulated	£8.00
30	1000	28T10 (Less Nut)	£3.00

PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp £1.00

3" red 7 segment L.E.D. 14 D.I.L. 0-9+D.P. display 1.9v 10mA segment, common anode 61p DL747.6" £1.25 Minitron 3" 3015F filament £1.10

PAPER BLOCK CONDENSER

0.25MFD	800 volt	30p
1MFD	250 volt	15p
2MFD	250 volt	20p
4MFD	250 volt	20p

GARRARD

GCS23T Crystal Stereo Cartridge	66p
Mono (Stereo compatible). Ceramic or crystal	60p

HANDLES

Rigid light blue nylon 6 1/2" with secret fitting screws	5p
Belling Lee white plastic surface coax outlet box	20p

COY11B L.E.D. Infra red transmitter £1 One fifth of trade

Plastic, Transistor or Diode Holder 1p

Transistor or Diode Pad 1p

Holders/overpads 50pper10p

I.C. extraction and insertion tool 32p

CHASSIS SOCKETS

Car Aerial	9p
Coax	3p
5 pin 180°	9p
5 or 6 pin 240° din	6p
speaker din switched	5p
3.5 mm switched	5p
stereo 1/2" jack enclosed	10p

Philips Iron Thermostat 15p

McMurdo PP108 8 way edge plug 10p

TO3 HEATSINK

Euroelec HP1 TO3B individual 'curly' power transistor type. Ready drilled 12p

CRAZY OFFERS

2200 mfd.	64v	40p
2500 mfd.	40v	30p
8 mfd.	500v	6p
400 mfd.	16v	4p
.1 mfd.	500v	1 1/2p
.1 mfd.	1500v	2p
2200 mfd.	25v	30p
1000 mfd.	200v	25p
10000 mfd.	15v	12p
1250 mfd.	35v	10p
6800 mfd.	10v	6p
32+32 mfd.	275v	8p
16+32 mfd.	350v	12p
8+8 mfd.	350v	8p
150 mfd.	35v	4 1/2p
100 mfd.	70v	4 1/2p
1 mfd. non-polar	350v	3p
680 mfd.	100v	10p
15 mfd.	160v	3p
4700 pf. sub min	500v	1 1/2p
4700 mfd.	63v	70p
300 mfd.	450v	25p

Miniature Axial Lead Ferrite Choke formers 2p

*Avalanche type

Amp	Volt	TRIACS	
6	800	Plastic RCA	£1.20
25	900	BTX94-900	£4.00
25	1200	BTX94-1200	£6.00

Mullard Data Book 40p

RS 2mm Terminals Blue & Black 5 for 40p

Chrome Car Radio fascia 15p

Rubber Car Radio gasket 5p

DLI Pal Delayline 50p

Relay socket Take miniature 2PCO relay 10p

B7G or B9A valve can 5p

0-30, or 0-15, black pvc. 360° dial, silver digits, self adhesive, 4 1/2" dia. 10p

Tested unmarked, or marked ample lead ex new equipment

ACY17-20	8p	OC71/2	5p
AS220	8p	OC200-5	8p
AS221	30p	TIC44	24p
BC186	11p	2G240	£1
BCY30-34	8p	2G302	5p
BCY70/1/2	8p	2G401	5p
BF115	10p	2N711	25p
BY126/7	4p	2N2926	4p
HG1005	10p	2N598/9	6p
HG5009	3p	2N1091	8p
HG5079	3p	2N1302	8p
L78/9	3p	2N1907	£1
M3	10p	Germ. diode	1p
OA81	3p	GET120 (AC128 in 1" sq. heat sink	15p
OA47	3p	GET872	12p
OA200-2	3p	2S3230	30p
OC23	20p		

I.C. extraction and insertion tool 32p

GARRARD

RS 10 Turn Pot 1%	
250, 500 Ω, 1K, 50K	£1

Copper coated board 10" x 9" approx 25p

TIE CLIPS

Nylon self locking 7" or 3 1/2" 2p

Geared Knob 8-1 ratio 1 1/8" diam, black 70p

R.S. 2 1/2" 35 ohm loud speaker 60p

RS 10 Turn Pot 1% 250, 500 Ω, 1K, 50K £1

Copper coated board 10" x 9" approx 25p

TIE CLIPS Nylon self locking 7" or 3 1/2" 2p

Geared Knob 8-1 ratio 1 1/8" diam, black 70p

R.S. 2 1/2" 35 ohm loud speaker 60p

SMALL ORDERS, ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE

MAIL ORDER CUSTOMERS ONLY ADD 8% VAT-I PAY BALANCE ON 12 1/2% ITEMS

LARGE ORDERS, ADD SUFFICIENT FOR POSTAGE, INSURANCE, ETC.

ALL ENQUIRIES, ETC., MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

TOTAL GOODS PLUS CARRIAGE, ADD V.A.T.

COME TO THE NORTH'S PREMIER AMATEUR RADIO EVENT!

NORTHERN RADIO SOCIETIES ASSOCIATION ANNUAL

CONVENTION & EXHIBITION

BELLE VUE—MANCHESTER

SUNDAY 24th APRIL 1977 — DOORS OPEN AT 11 a.m.

- ★ Trade Stands
- ★ Inter-Club Quiz
- ★ Construction Contest
- ★ RSGB Bookstall
- ★ Club Display Stands
- ★ Grand Raffle
- ★ Club Stand Trophy
- ★ RTTY & Repeater Exhibits


Ample car parks and facilities for the family including
ZOO and FUN FAIR!

Talk-in for FM mobiles on 2 metres S22 and R6 (GB3MP) and on 70cms 433.2 MHz
and RB4 (GB3MR)

EXHIBITION HALL ENTRANCE IS AT REAR OF BELLE VUE,
OPPOSITE MAIN CAR PARK — OFF HYDE ROAD, A57

REVOR OPTICAL & TECHNICAL

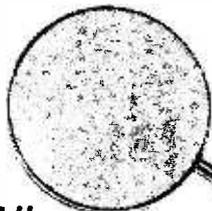42 TAVISTOCK STREET
LONDON W.C.2
Tel. 01-836 4536



4" dia. lens

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE,
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)

£10.00

POST
FREE

THE METAC DIGITAL CLOCK

★ COMPLETE KIT ★



- Pleasant green display. 12/24 Hour readout
- Silent Synchronous Accuracy. Fully electronic
- Pulsating colon. Push-button setting
- Building time 1 hr. Attractive acrylic case
- Easy to follow instructions. Size 10.5 x 5, 7 x 8 cm
- Ready drilled PCB to accept components

KIT PRICE £9.60 + 76p VAT

**SAME DAY DESPATCH: ORDERS RECEIVED
BEFORE 2.00 P.M. ARE POSTED ON THE SAME DAY**

SEND YOUR ORDER TO

DAVENTRY

UXBRIDGE

**METAC ELECTRONIC AND TIME
CENTRE**



67 HIGH STREET
DAVENTRY
NORTHANTS.
TEL. 76546

3 THE NEW ARCADE
HIGH STREET
UXBRIDGE MIDDLESEX.
TEL. Uxbridge (0895) 56961



Cash, Cheque or Postal Order or if you wish to use
Barclaycard or Access, simply quote name, address
and card number when ordering

CUSTOM CABINETS

We build all types of loudspeaker enclosures, disco consoles, amplifier cases etc., to our designs or for your special requirements.

HOME CONSTRUCTORS

Professionally finish your equipment using our specialist fittings:

Recessed pocket handles approx W5 $\frac{1}{4}$ " x H2 $\frac{3}{8}$ " x D3" 38p each

Lifting bar recessed handle approx W6 $\frac{1}{4}$ " x H10 $\frac{3}{8}$ " x D2 $\frac{3}{8}$ " £1.96 each

Corner protectors (black nylon) for rounded edges, supplied with screws and brads 11p each

Corner protectors (metal) 1 $\frac{1}{4}$ " for square edges, supplied with screws 10p each

Standard jack socket recessed mounting plate 9p each

Cabinet feet 1 $\frac{1}{2}$ " dia x $\frac{3}{8}$ " high (black polyethylene) 9p each

Black "Vynide" cabinet covering approx 52" wide £1.90 per yard

Black "Vynair" baffle covering approx 52" wide £2.60 per yard

1 $\frac{1}{2}$ " speaker fixing bolts, C/S with left-hand wood screw into baffle, including washers and nut. 2BA 5p each; 4BA 4p each

Pre-cut cabinet parts/baffles etc. price on application
Prices include VAT On orders under £5 please add 60p towards postage and packing


SURREY AUDIOTRONICS

51B LIND ROAD, SUTTON, SURREY

For expert advice

Tel: 01-643 0005

INTRODUCING

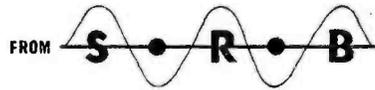

A New Miniature Soldering Iron

220-240 Volts
16-18 Watts

Insulation tested at 1500 Vac

BIT TYPE

19 1.5mm

20 30mm

21 4.5mm

22 6.0mm

with
7★
FEATURES

★ Lightweight

★ Slim, easy to hold

★ Four tip sizes

★ Complies with
Consumer Protection
Regulations B.S. No 3456 2/14

★ All parts easily replaced

★ New bit securing method

★ Built in suspension hook



As
Advertised
on TV

PRICES: IRONS £3-70 each
BITS 41p each

(Inc. VAT and P&P)

Trade enquiries welcome.

Cheques & Postal Orders to Manufacturers & Distributors

S. & R. BREWSTER LIMITED

86-88 UNION STREET, PLYMOUTH, PL1 3HG

Telephone: 0752-65011



Ever
get the
HUMP
Rigolletto?

No - I do Verdi well by
getting all my components
from HOME RADIO!

Forgive the terrible puns. If you don't quite twig 'em have a word with your opera-going friends and they will reveal all! Frankly, we've used the characters above simply to catch your attention and to lead you on to the more interesting point that Home Radio Components Ltd. are the people to deal with when you need components for the projects featured in this magazine, or for any other electronic gadget you may be creating. Thousands of constructors have proved that they get good advice, good components, good value, good service from Home Radio. Many buy over the counter at Mitcham, many purchase by Mail Order sending a cheque or P.O. each time they need something, and a growing number of customers are proving the advantages of joining the Home Radio Credit Account Scheme. Whichever method you opt for you'll need a Home Radio catalogue. Read all about it in the paragraph below.

Please write your Name and Address in block capitals

NAME

ADDRESS



POST THIS COUPON
with cheque
or p.o. for
£1.40

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD


Regd No 912966 London

The famous Home Radio Components Catalogue comprises 200 pages, listing about 5,000 items, nearly 2,000 of them illustrated. Everything is set out so clearly and concisely that the catalogue is a pleasure to use. When you buy one we also send you a free mini catalogue filled with extra special bargains. The saving on some purchases from this bargain list alone can more than pay for the catalogue, which costs £1 plus 40p for post and packing. Send off the coupon with your cheque or P.O. for £1.40 now. The catalogue and bargain list will come to you by return post.

HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD. Phone: 01-648 8422

METERLESS TRANSISTOR TESTER

By Bruce Woodland

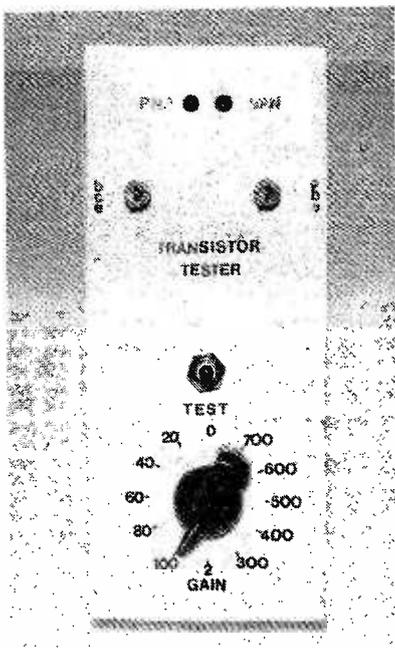

This test instrument allows the rapid determination of polarity and large signal gain of bipolar transistors. An l.e.d. readout replaces the usual moving-coil meter, conferring economic advantages and resistance to mechanical shock. The battery current demand is low and virtually the absolute minimum of manipulations is necessary to evaluate a transistor.

Many constructors augment their transistor supplies by the purchase of mixed untested transistors and reclaimed devices from computer boards. Again, during the design of circuitry it is often desirable to have at least a rough idea of the gain of a transistor even when this is a new marked device. For all these requirements some form of transistor tester is necessary.

SPECIFICATION

A quick look at the data sheet of any transistor will demonstrate the large number of tests which must be carried out to fully evaluate it. Fortunately, most home constructor applications require answers to three questions only:

1. Is the device functional?
2. What is its polarity?
3. What is its gain?

When a large number of devices are to be checked a testing instrument which is quick to use and involves the minimum of manipulations is obviously the most desirable. The tester to be described falls into this category and readily provides answers to the three basic questions just noted. No meter is incorporated, and so the cost and size can be kept to quite a small level.

PRINCIPLE

The block diagram of Fig. 1 illustrates the principle of operation of the transistor tester. A square wave oscillator provides an alternating voltage such that one output is at 2.7 volts positive when the other is at 2.7 volts negative, and vice versa, both voltages being

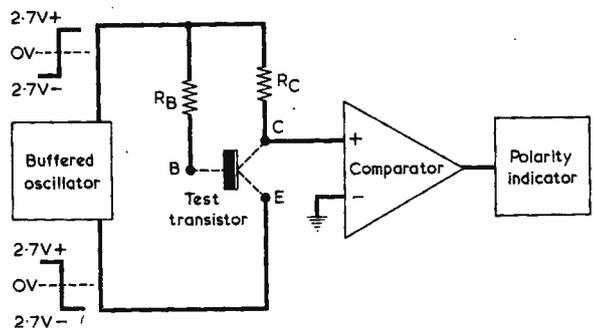


Fig. 1. Block diagram illustrating the operation of the meterless transistor tester

with respect to earth. One output is applied to the emitter of the transistor under test, whilst the other is applied to the transistor base via RB and to the transistor collector via RC.

If the transistor is a p.n.p. type (and assuming the requisite values in RB and RC) it will be turned on when the collector is negative and the emitter positive. The collector will then be positive of earth. When the polarities at the collector and emitter are reversed the transistor simply becomes non-conducting. Thus the presence of a p.n.p. transistor is indicated by a positive voltage at the collector during the half-cycles from the square wave oscillator when the voltage applied to RB and RC is negative. During the other half-cycles the collector will also be positive because a positive voltage is then applied to RC.

The reverse holds true with an n.p.n. transistor, the collector of which goes negative.

The collector is connected to the non-inverting input of an operational amplifier which has two light-emitting diodes wired in opposing polarity in its feedback loop. If the non-inverting input goes positive the op-amp output follows, lighting the l.e.d. which indicates "p.n.p.". Similarly, when the non-inverting input goes negative the other l.e.d. lights up, to indicate "n.p.n.".

If the transistor under test has an open-circuit collector, both l.e.d.'s will be illuminated, because the op-amp output then follows the square wave oscillator. The same will happen if the value RB is too high to allow the transistor to turn on.

BIAS RESISTOR VALUE

We may next investigate the value of RB which is required to cause the collector of the test transistor to be just at mid-rail voltage, i.e. at earth potential, during half-cycles when the transistor is conductive. The full rail voltage is twice 2.7 volts, or 5.4 volts, and we shall assume that the test transistor is a silicon type with a base-emitter forward voltage drop of 0.7 volt. Under these circumstances the current in RC is 2.7 volts divided by RC, whilst the current in RB is 5.4 volts minus 0.7 volts, or 4.7 volts, divided by RB. The gain is IRC divided by IRB, and this is equal to the first expression in Fig. 2. The second equation then gives an expression for RB. In the practical circuit RC is 4.3k Ω , leading to the third and fourth equations in Fig. 2.

It will be seen from the last equation that RB in kilohms is equal to gain multiplied by 7.5. Thus, the collector of a transistor with a gain of 20 will be at earth potential when RB has a value of 150k Ω . The corresponding value of RB for a gain of 40 is 300k Ω , for a gain of 60 is 450k Ω , and so on.

The last equation in Fig. 2 is a little inaccurate for germanium transistors, with their base-emitter forward voltage drop of about 0.15 volt, but the error is not in practice of any serious significance. Most transistors encountered these days are, of course, silicon types.

We can now see how the arrangement of Fig. 1 can be employed for first determining the polarity of a transistor and then its gain. Should RB initially be given a relatively low value the test transistor, if serviceable, is bound to be turned on, whereupon one of the two l.e.d.'s will light up to indicate polarity. The value of RB is then increased until the collector of the test transistor passes earth potential, causing both l.e.d.'s

$$\text{GAIN} = \frac{2.7}{RC} \times \frac{RB}{4.7}$$

$$RB = \text{GAIN} \times \frac{RC}{2.7} \times 4.7$$

$$RB (\text{k}\Omega) = \text{GAIN} \times \frac{4.3}{2.7} \times 4.7$$

$$RB (\text{k}\Omega) = \text{GAIN} \times 7.5$$

Fig. 2. Equations developing the relationship between RB and test transistor gain when the transistor collector is at earth potential

to be illuminated. The value of RB at which this occurs then gives an indication of the gain of the transistor.

WORKING CIRCUIT

The full working circuit appears in Fig. 3. This has two integrated circuits, of which IC1 is a CMOS MC-14049 hex inverter/buffer and IC2 is a 741 op-amp. Two of the inverters of IC1, in association with C1, R1 and R2, form a simple square wave oscillator with a roughly equal mark-space ratio running at approximately 2.5kHz. The remaining four inverters are parallel coupled in pairs to increase their current sink and source capabilities, and are arranged to provide complementary polarity outputs from the oscillator. One output connects to the emitter of the test transistor and the other to R6, which replaces RC of Fig. 1. RB of Fig. 1 is replaced by R7 and whatever resistance, in R8 to R17, is switched in by S2.

A CMOS device is employed for IC1 as it is necessary to have a symmetrical voltage swing about earth. A t.t.l. device would be unsuitable.

The feedback loop around IC2 includes LED1, LED2 and R4. R3 sets the sensitivity such that 0.1 volt difference between the test transistor collector and earth corresponds to a flow of 10mA in the appropriate l.e.d. The l.e.d. current is limited by R4. When the non-inverting input goes positive the i.c. output follows and LED1 lights up. LED2 is illuminated when the non-inverting input goes negative.

A dual rail supply which is nominally 2.7 volts positive and negative of earth is given by the circuit comprising R5, ZD1, ZD2, C2 and C3. The push-button S1 ensures that power is only demanded from the 9 volt battery during an actual test, thus prolonging battery life. The current requirement is about 16mA, whereupon a PP3 battery is quite suitable.

It may be felt that, bearing in mind the internal output stage of a 741, a dual 2.7 volt supply may be insufficient to allow the l.e.d.'s to be illuminated. No

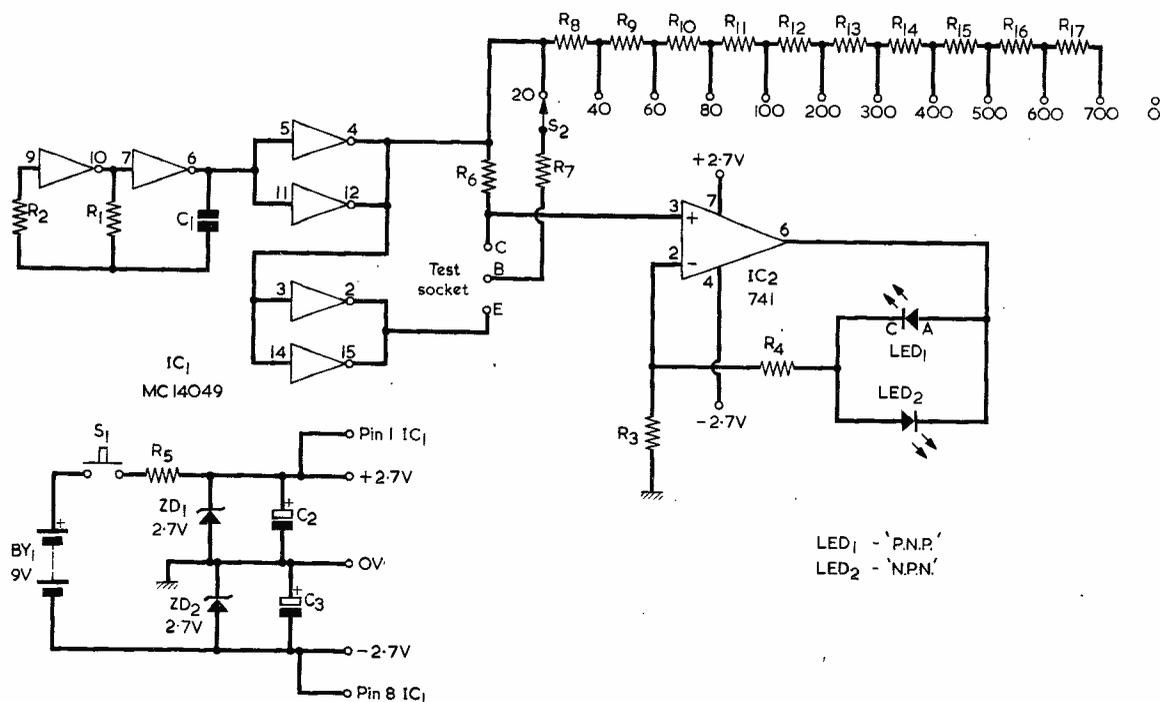


Fig. 3. Full circuit diagram for the transistor tester. The numbers at the contacts of S2 indicate the corresponding gain figures

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5%)

- R1 39k Ω
- R2 68k Ω
- R3 10 Ω
- R4 68 Ω
- R5 220 Ω
- R6 4.3k Ω
- R7 150k Ω
- R8 150k Ω
- R9 150k Ω
- R10 150k Ω
- R11 150k Ω
- R12 750k Ω
- R13 750k Ω
- R14 750k Ω
- R15 750k Ω
- R16 750k Ω
- R17 750k Ω

Capacitors

- C1 0.01 μ F type C280 (Mullard)
- C2 20 μ F electrolytic, 10 V. Wkg.
- C3 20 μ F electrolytic, 10 V. Wkg.

Semiconductors

- IC1 MC14049 or CD4049
- IC2 741, 8 pin d.i.l.
- ZD1 BZY88C2V7
- ZD2 BZY88C2V7
- LED1 red l.e.d. (see text)
- LED2 red l.e.d. (see text)

Switches

- S1 press-button, push to close, miniature
- S2 1-pole 12-way rotary, miniature

Battery

- BY1 9 volt battery type PP3 (Ever Ready)

Miscellaneous

- Pointer control knob
- 8 pin i.c. holder
- 16 pin i.c. holder
- Battery connector
- Printed circuit board
- Materials for case (see text)

trouble was experienced in this respect with the prototype, which worked satisfactorily with battery voltages down to 6 volts. Taking into account the relatively high slope resistances of 2.7 volt zener diodes at low currents, this would indicate a comfortable voltage margin. The author employed l.e.d.'s of about 0.2in. diameter obtained from Radio Shack of Battersea.

CONSTRUCTION

The construction of the tester can be carried out in any reasonable manner preferred by the reader, and the following details of the author's instrument may be helpful as a guide.

The prototype is housed in a home-made case having internal dimensions of 5½in. long by 2in. wide by 1½in. deep. The sides and ends consist of ½in. wood and the front panel of s.r.b.p. sheet. The sides, ends and front are covered overall with Formica. The back consists of a piece of aluminium with flanges at the end which provide a push fit.

The printed circuit board is mounted on three ½in. spacers tapped 6BA, these being secured to the s.r.b.p. panel by countersunk 6BA screws whose heads are covered by the outside Formica. The body of S1 is

between the front panel and the component side of the printed board, appearing between R5 and ZD2. A miniature press-button was employed here. Larger push-buttons would necessitate increased spacing between the front panel and the board, and a corresponding increase in case depth. The author fitted two transistor sockets on the front of the case, one wired for transistors with a BCE lead-out configuration and the other for transistors with a CBE configuration. The l.e.d.'s are mounted directly on the printed board, being positioned such that their forward ends just fit into two holes drilled for them in the front of the case.

The ten transistors, R8 to R17, are mounted directly to the tags of S2. There is just sufficient space behind the printed board to take a PP3 battery, this being insulated from the copper pattern of the board by a piece of foam plastic sheet. The front panel is marked up with gain figures for S2, these corresponding to the gain figures shown in the circuit diagram of Fig. 3. The legend "PNP" appears alongside LED1 and "NPN" alongside LED2. The identifying letters "B", "C" and "E" appear, as applicable, beside the transistor holders.

The printed board is reproduced full-size in Fig. 4.


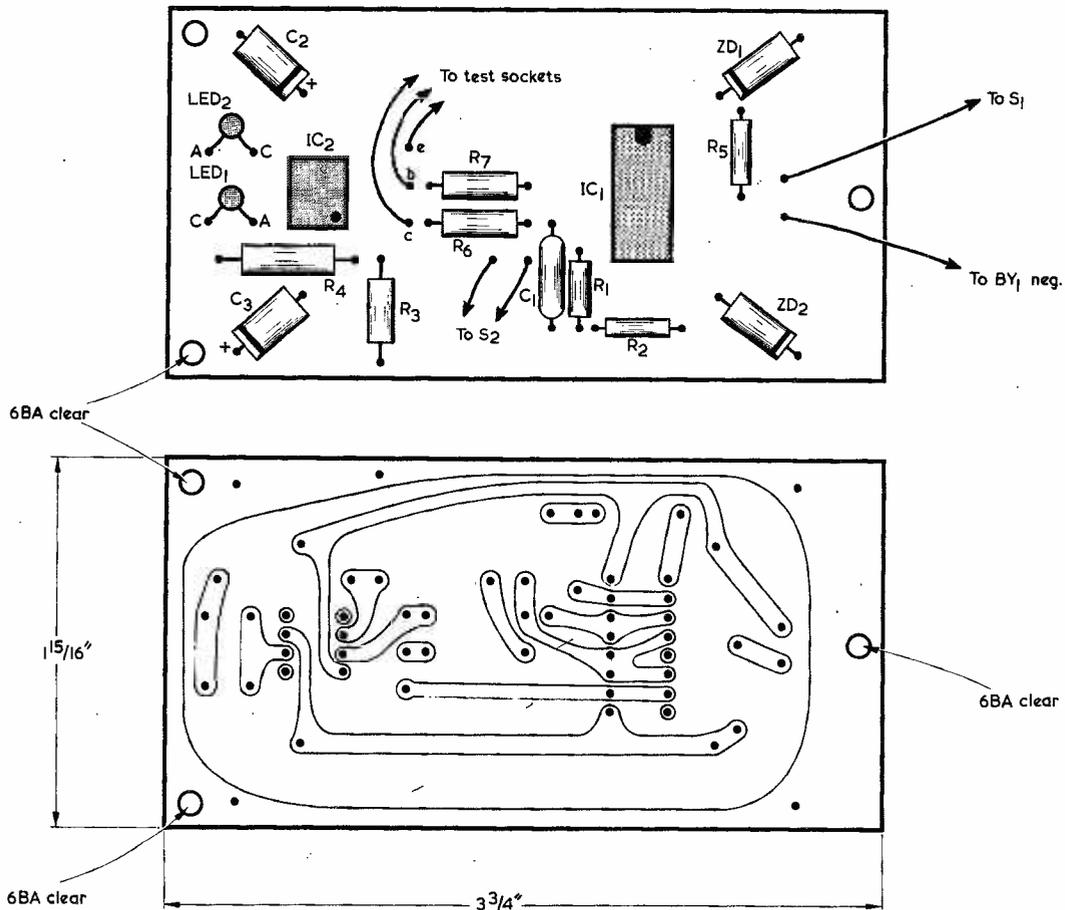


Fig. 4. Component and copper sides of the printed board. This is reproduced full size for tracing

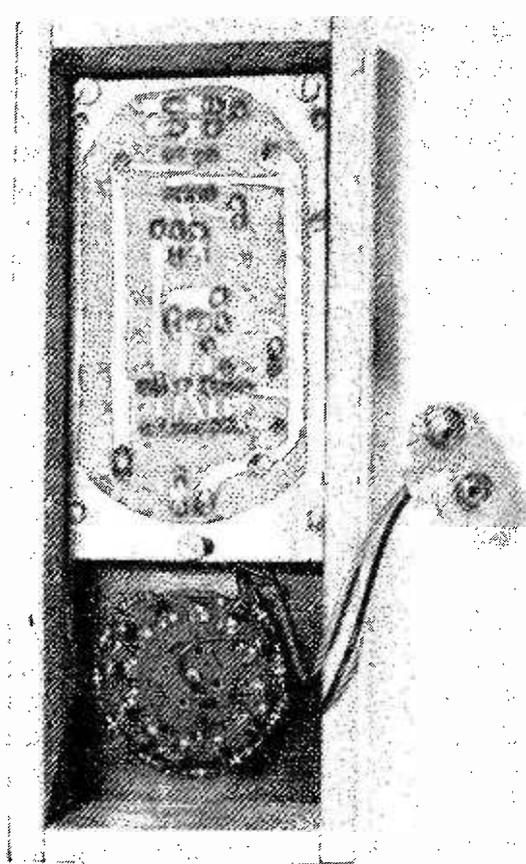


Layout inside the tester. There is space for a PP3 battery over the printed board

It is strongly recommended that integrated circuit holders be used for IC1 and IC2, whereupon these two i.c.'s may be plugged in after all soldering is completed and the wiring has been checked. Fig. 5 shows the resistors which are soldered to the tags of S2.

USING THE TESTER

To use the tester first connect the transistor to be checked to the instrument. Set S2 to "20" and press S1. If the transistor is a satisfactory component and has been connected correctly, either the "PNP" or the "NPN" l.e.d. will light.

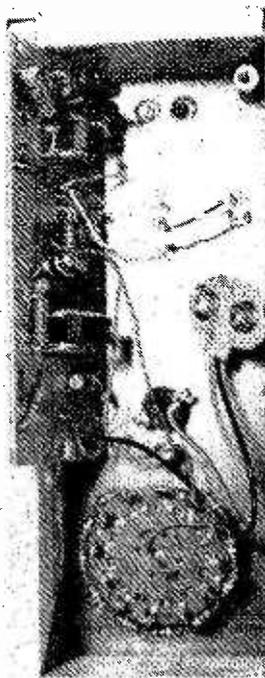Keeping S1 pressed, rotate S2 to higher gain figures until both l.e.d.'s light up. The highest gain setting with only one l.e.d. alight is the value taken, the exact value lying between the two figures. If the transistor is not faulty, both l.e.d.'s should be alight when S2 is in the "O" position.



In this view the printed board has been moved to one side. On the front panel can be seen the two holes for the l.e.d.'s, the connections to the transistor holders and switch S1


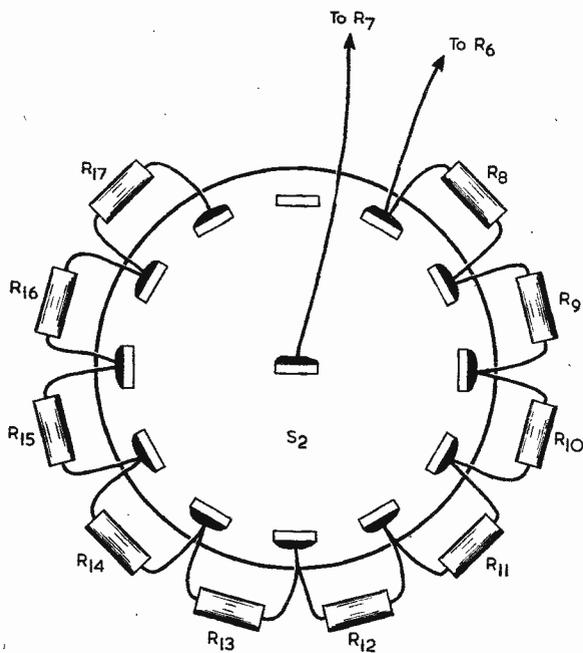


Fig. 5. Resistors R8 to R17 are wired directly to the tags of S2. The two wires connect to R6 and R7 on the printed board

Normally, the transition from one l.e.d. being alight to two being alight should be of an abrupt nature as S2 is moved from one position to the next. However, it may be found with quite a few transistors that the second l.e.d. commences to glow faintly at the setting of S2 which is just below that at which both l.e.d.'s are fully illuminated. This will occur if the gain of the transistor is such that the collector voltage is just short of reaching earth potential. The gain figure is then that at which the second l.e.d. glows faintly, and will be more accurate than is given when the change from one l.e.d. to two l.e.d.'s is of an abrupt nature. ■

500th EDITION OF WORLD RADIO CLUB

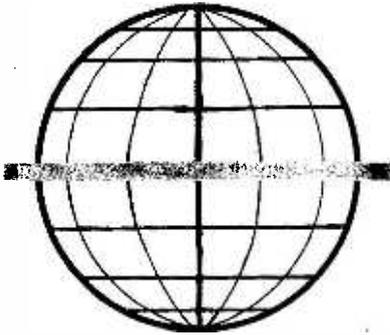

Report by Ron Ham

Since it began on July 1st, 1967, more than 32,000 members have joined World Radio Club, a popular weekly programme broadcast by the BBC World Service for the benefit of shortwave listeners, and those who want to know more about the technical side of radio communication.

During the past decade, the lifetime of the programme, there has been a fantastic advance in electronics which has reflected in the design of radio receivers and transmitters, broadcasting and recording techniques, and in the world of amateur radio. Throughout this period, World Radio Club producers have done their best to keep its listeners informed of the progress with hundreds of outside interviews at places where the developments were being made. The Club's reporters have been to both national and international exhibitions and talked to representatives on their stands about their particular radio products. Listeners have heard reports from factories, schools, research labs, and the armed forces, in fact they have talked about anything from the worlds smallest television set to the giant radio telescope at Jodrell Bank. Frequently outside specialists have been called in to take part in a particular programme along with their regular team. Often an article of special interest has appeared in one of the technical journals and soon afterwards, the author, or a representative of that journal, has been invited to WRC to discuss the subject further.

With this sort of background it was no surprise when the BBC invited, for the first time, an audience of radio enthusiasts to Bush House (HQ BBC World Service) to witness, and celebrate the recording of the 500th edition of World Radio Club, and furthermore, to take part in the programme by putting questions to a panel of experts. As usual, Frank Hennig,

G3GSW, was in the chair and the panellists were Bill Wood, Head of the BBC's Engineering Information Department, Desmond Colling of the International Shortwave League, and Henry Hatch, G2CBB well known to listeners because, for many years he has answered members' technical problems in a straightforward and uncomplicated manner.

Questions from the audience about AM or FM, Fading, Amateur call signs, frequency allocations, and the sunspot cycle were adequately answered by the team in the true club spirit which has been the programme's hallmark since it began.

Among the enthusiastic studio audience were many people who had taken part in previous programmes as well as representatives from the technical press, radio clubs, and shortwave organisations. The RSGB President, Lord Wallace of Coslany and General Manager, George Jessop, G6JP, were in the audience and Lord Wallace delighted everyone when he told Frank Hennig that now he is President, everybody calls him George which emphasises the friendly atmosphere which exists throughout the world of amateur radio.

Richard Lambley, G8LAM, who has been producing the programme on a temporary basis read a letter of good wishes from the European DX Council and Reg Kennedy, regular producer, told of the time when his tape recorder belched out smoke while he and former chairman, Peter Baresby, were flying with the RAF in a piston aircraft over the north-Atlantic interviewing the crew for WRC. It was the human items like these that helped to make the evening of February 11th a most enjoyable one for all of us who were there.

The writer would like to add his good wishes for the future of World Radio Club, and to thank the BBC for a wonderful evening.

MASSIVE EXPORT CONTRACT

It is pleasant to report a massive export contract won by companies in the GEC-Marconi Electronics group. The contract, worth £150 million, has been awarded to GEC-Transportation Projects Limited for the provision of electrification, telecommunications, signalling and locomotive equipment operating at 25kV a.c. for Brazil's Federal Railway Network.

As well as system design responsibility, the contract includes the supply of equipment and services for a new "steel railway" which will run from the iron ore centre of Belo Horizonte to the major steel complex at Volta Redonda a distance of some 400 kilometres.

When completed in early 1982 the new rail link will carry quadruple-headed trains of up to 12,000 tons at speeds reaching 60 kilometres per hour.

It is expected to transport 50 million tons of iron ore each year from Belo Horizonte and Jaceaba to Volta Redonda, and it will also provide a limited passenger service between the areas.

In addition, the contract provides for the electrification of the existing line which runs for some 450 kilometres from the port of Sepetiba near Rio de Janeiro via Volta Redonda to Manoel Faio near Sau Paulo.

This latest contract, the largest ever placed by the Brazilian Railway Authority, involves several GEC companies in the supply of equipment. Electrical equipment for the locomotives will be manufactured by GEC Traction Limited; signalling systems by GEC-General Signal Limited, substation equipment by

GEC Switchgear Limited and GEC Power Transformers Limited, and cables, microwave radio and multiplex communications equipment by GEC Telecommunications Limited and Telephone Cables Limited. Further, the overhead contact system will be provided by Balfour Beatty Power Construction Limited, and a training programme for the Brazilian operating staff will be arranged by Transmark, the British Rail consultancy organisation.

GEC-Transportation Projects was set up in 1972 to seek comprehensive contracts in the expanding field of railway electrification and metro systems, incorporating equipment manufactured by the GEC product companies. It has certainly achieved an outstanding success in its Brazilian venture.

AID TO INSTALLING FM RADIO AERIALS

A single co-axial downlead can be used to connect both a television aerial and an FM radio aerial, using a new twin TV/FM outlet unit introduced by MK Electric.

This means that a householder can make use of his existing television downlead when he decides to install an FM aerial in the loft or developers can add to the "sellability" of new homes by providing for connection of FM radio as well as television aerials.

Two of the new MK 3522 isolated TV/FM socket-outlets units will be required, installed on a "back-to-back" arrangement with one in the normal television aerial outlet position and the other suitably located in the loft. The co-axial downlead is con-

nected to the rear of this second unit, and the TV and FM aerials are connected into the front-plate using normal co-axial plugs.

The twin TV/FM outlet unit will fit into the same box as the normal co-axial TV outlet and the two sockets are clearly engraved "TV" and "FM".

Although suitable for use in this way, the new twin outlet unit has been introduced by MK primarily to meet stringent regulations that have been proposed for multi-outlet aerial installation in blocks of flats etc. It is anticipated that, if introduced, these regulations will call for a 2,000V isolation value for the outlet units.


Recommended retail price of the 3522 isolated TV/FM co-axial socket-outlet is £3.08 plus VAT.

RADIO AMATEURS ASSIST SCIENTIFIC EXPEDITIONS

Following our comments in the January issue regarding the giving of news of activities and developments outside the scope of the individual shack or workshop, we are indebted to the latest edition of Region 1 News, the Journal of the International Amateur Radio Union Region 1 Division, for news of cooperation between Italian Radio Amateurs and recent scientific expeditions.

At the beginning of 1976, a team of fifteen Italians explored the King George Islands in Antarctica. This expedition was directed by Italian radio Amateur Renato Cepparo, I1SR. The programme of the expedition included biological studies, geological observations and exploration of some of the Island's mountains. One of the mountain peaks was named "CIMA RADIOAMATORI", to commemorate the very helpful work carried out by radio amateurs in sustaining communications between the expedition and Italy. Radio contact with the expedition was maintained by radio Amateurs from the town of Monza, near Milan, most of the contacts being on the 14MHz Amateur band.

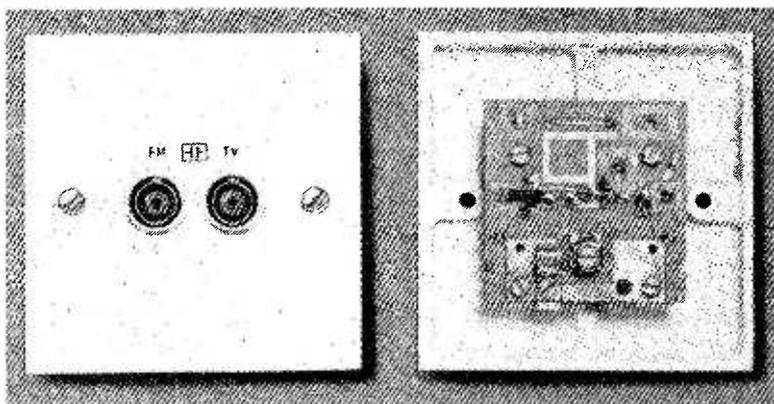During July and August of last year, another Italian expedition visited Greenland and they had a volunteer radio operator in 14CDH. The expedition call sign was 14CDH/OX. The base camp was near Umiyamako Muna, close to latitude 72°N, and the radio station was operated from a tent.



COMMENT


EMI LAUNCH NEW PROFESSIONAL AUDIO RECORDING TAPES

EMI Tape Limited, of Hayes, Middlesex, has introduced a new range of professional audio recording tape — the EMITAPE 830 series.

The EMITAPE 830 range is based on a high-output low-noise professional tape developed specifically for high quality reproduction in studio mastering and broadcast applications. Its most significant features are increased high/low frequency magnetic remanence values and an excellent signal-to-print ratio. In addition, the extremely low modulation noise and low head wear properties previously associated with the highly successful EMITAPE 815 broadcast quality tape have been incorporated in the new product.

The new tape initially will be available in three formats: 831 non-backed standard play; 832 matt-back standard play, particularly good for non-pressure pad high-speed spooling; and 833 long play for use with low tension battery recorders, with a range of widths to suit studio requirements.

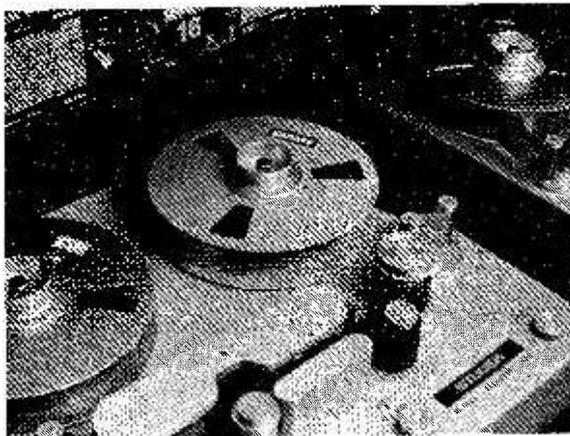The 830 series has a much higher magnetic remanence which gives an improved signal to noise ratio of 77dB. This has been achieved by EMI Tape's new oxide formulation and a new type of production process. Reduced intermodulation and third harmonic distortion gives the tape, for instance, less than



1/3% third harmonic distortion at the 1KHz I.E.C. (International Electro Technical Commission) reference level. To provide a greater built-in overload fail-safe, EMI Tape has improved the headroom to give a maximum output of +8.5dB for 3% harmonic distortion at 1KHz. This high 1KHz output is complemented by a similar output at 10KHz.

NORTHERN RADIO SOCIETIES' ASSOCIATION

The Annual Convention and Exhibition of the NRSA, which is sponsored by radio societies in the North of England, will take place at Belle Vue, Manchester on Sunday, 24th April, 1977.

The doors will open at 11.00 am and there

will be a record number of trade exhibitors in attendance, as well as club display stands.

Other highlights will include a Grand Raffle, an Inter-Club Quiz and a Construction Contest (s.a.e. for rules to Mr. John D. Clifford — G4BVE of 10 Arley Avenue, Bury, BL9 5HD).

XEROZA RADIO MOVES TO LONDON

Xeroza Radio, formerly of Bishop's Tawton, Devon, have now removed to new premises at 306 St. Paul's Road, Highbury Corner, London N.1.


They have extensive stocks of electronic components and carry a complete range for radio and electronics constructors.

The business is under the control of Mr. Tom Powell who has had many years experience in the component field.


● Mrs. Rita Shepherd, G3NOB, has retired from the position of Honorary Secretary of the Radio Amateur Invalid and Bedfast Club. The new Honorary Secretary is Mr. H. R. Boutle, G2CLP, who is, incidentally, Business Manager of the famous Shuttleworth Collection of aircraft. Mr. Boutle's address is 14, Queen's Drive, Bedford MK41 9BQ.

● Messrs Radio Shack, of 161 St. John's Hill, Battersea, London SW11, have informed us that they have on a number of occasions recently been confused with the famous American firm of the same name who are, of course, associated with the Tandy Corporation of Bilston Road, Wednesbury, W. Midlands. This can cause particular difficulty when components or equipment is involved.

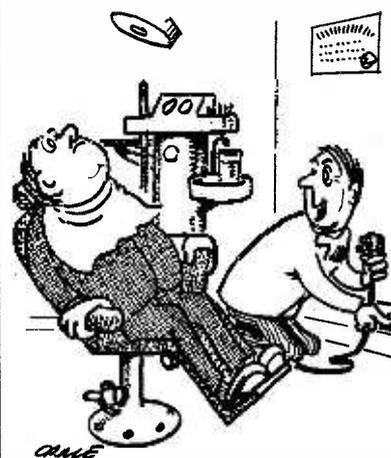We trust that readers will note the distinction to avoid inconvenience to both firms.



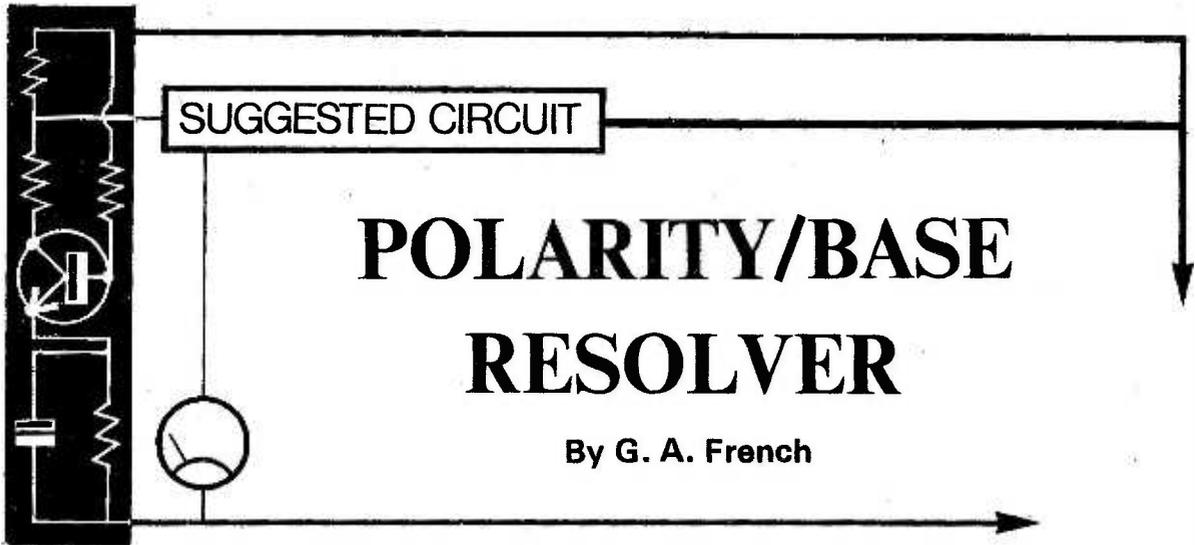"Looks as though all you'll need this time is two small stoppings and a 13 amp fuse!"



POLARITY/BASE RESOLVER

By G. A. French

It is often possible to obtain job-lots of unmarked bipolar transistors at very low cost, whereupon it then becomes necessary to sort these out into n.p.n. and p.n.p. types, and to determine their lead-out functions. Such a process can be very tedious if, say, a multimeter switched to an ohms range is employed to find the transistor polarity, and it can still be excessively time-consuming if a standard transistor gain meter is used. This article describes an extremely simple and in-

expensive item of test equipment which not only determines the polarity of a bipolar transistor but also identifies its base lead-out. In consequence, much of the initial sorting of unmarked transistors can be carried out with negligible difficulty and expenditure of time. The test instrument also provides a rough and ready check for transistor serviceability, since it will indicate whether a transistor has an open-circuit or short-circuit junction.

RESOLVER CIRCUIT

The circuit of the polarity/base resolver appears in Fig. 1, and it will be seen that it requires very few components. There are three test terminals, three light-emitting diodes, three resistors, a 3-way rotary switch, a single pole on-off switch and a 4.5 volt battery.

The transistor to be checked is connected to the three test terminals with S2 closed. S1 is then taken through its three positions. If all three l.e.d.'s light up for one position and only one l.e.d. lights up at the remaining two positions, then the transistor is an n.p.n. type and the switch position at which all three l.e.d.'s are illuminated corresponds to the base lead-out. Thus, should all the three l.e.d.'s be lit when the switch is at position 3, then the base lead-out connects to test terminal 3.

If it is found that all three l.e.d.'s light up at two positions of S1 and a single l.e.d. is lit at the third position, the test transistor is p.n.p. Further, the switch position at which the single l.e.d. is illuminated corresponds to the base lead-out of the transistor.

The currents flowing in the circuit are low and there is no necessity to turn off S2 when connecting a transistor to the terminals. S2 can be turned

on at the start of a checking session and turned off at the end. Its function is merely to prevent battery current drain when the instrument is not in use.

The operation of the circuit is quite easy to follow and it is helpful to remember that a bipolar transistor can be looked upon as two junction diodes connected back-to-back, as in Fig. 2. It should also be borne in mind that "conventional current" is assumed to flow from positive to negative, and that it flows in a diode in the direction indicated by the arrow-head which constitutes part of the diode symbol. It also flows in the direction indicated by the emitter arrow-head in the transistor symbol.

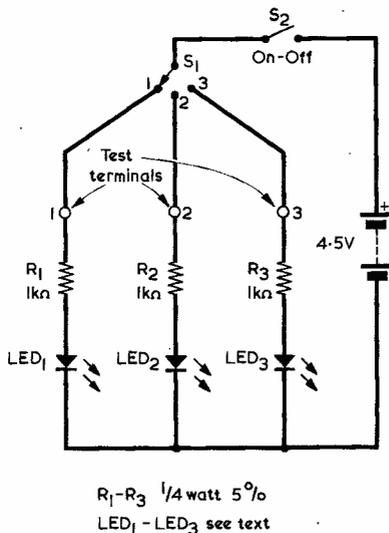


Fig. 1. The circuit of the polarity/base resolver. Despite its sophisticated performance this requires very few components

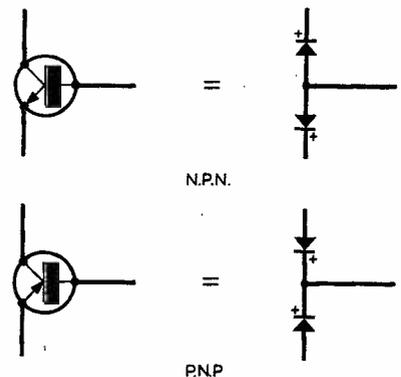


Fig. 2. Bipolar transistors may be looked upon as two diodes connected back-to-back. The corresponding diodes for n.p.n. and p.n.p. transistors are shown here

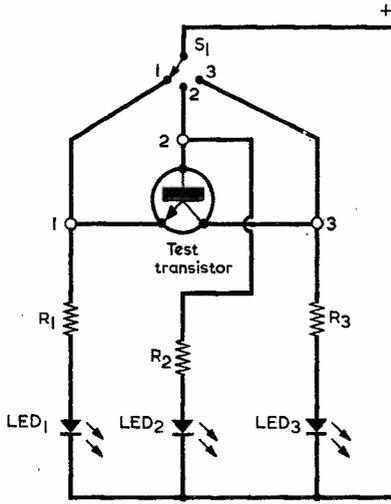


Fig. 3. Connecting an n.p.n. transistor to the resolver. All three l.e.d.'s are lit when the switch is in position 2

N.P.N. TRANSISTOR

Fig. 3 illustrates the situation where an n.p.n. transistor is connected to the test terminals. We shall assume that the base lead-out is connected to terminal 2.

When switch S1 is in position 1, current flows through R1 and LED1, causing this l.e.d. to light up. Current cannot flow into the remainder of the circuit because it is stopped by the emitter-base junction of the transistor, which acts as a reverse connected diode. As a result, only LED1 is illuminated. If S1 is taken to position 3, current flows in R3 and LED3, causing this l.e.d. to be illuminated. Again, current cannot flow into the rest of the circuit because the collector-base junction of the transistor functions as a reverse connected diode. In consequence, only LED3 is lit.

If S1 is taken to position 2, current flows in R2 and LED2, whereupon LED2 lights up. Both the base-emitter and base-collector junctions now act as forward connected conducting diodes, and current flows through these into R1 and LED1 and into R3 and LED3. As a result, all three l.e.d.'s are illuminated.

To sum up, taking S1 through its three positions causes a single l.e.d. to be illuminated at positions 1 and 3, and all three l.e.d.'s to be illuminated at position 2. These results indicate that the test transistor is an n.p.n. type and that its base is connected to terminal 2. Had the base been connected to terminal 1 the three l.e.d.'s would have lit up with S1 in position 1. Similarly, if the base had been connected to terminal 3, the three l.e.d.'s would be illuminated with S1 in position 3.

P.N.P. TRANSISTOR

We turn next to the situation which arises when a p.n.p. transistor is connected to the test terminals, as occurs in Fig. 4. Once more we connect the base lead-out to terminal 2 and we shall start by examining the situation when S1 is in position 2.

With the circuit in this state, current passes through R2 and LED2, causing this l.e.d. to light up. Current cannot flow to terminal 1 because the base-emitter junction of the transistor acts as a reverse connected diode. Similarly, current cannot flow to terminal 3 since the base-collector junction also acts as a reverse connected diode. Thus, only LED2 lights up.

When we come to consider the remaining positions of S1, circuit functioning becomes more complex and takes advantage of active transistor operation in addition to passive diode conduction.

Fig. 5(a) shows the situation with S1 in position 1. Current flows through R1 and LED1, and LED1 lights up. The emitter-base junction of the transistor acts as a forward conducting diode and current flows also into terminal 2 and thence into R2 and LED2. LED2 becomes illuminated. Since there is now a relatively high current in its emitter-base junction the transistor turns on and passes collector

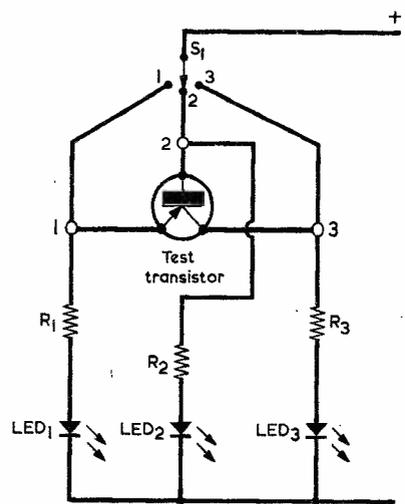


Fig. 4. Here, a p.n.p. transistor is connected to the circuit. With S1 in position 2, only one l.e.d. is illuminated

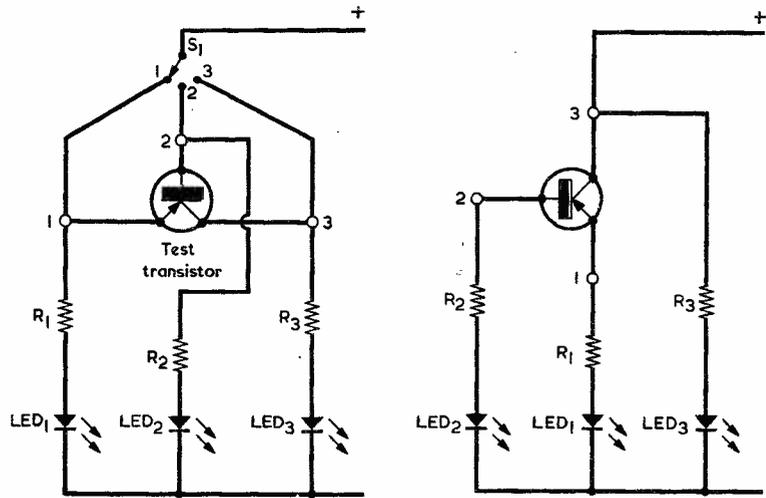


Fig. 5(a). When the switch is in position 1, all three l.e.d.'s light up

(b). With the circuit redrawn, the transistor may be recognised as being in the common emitter mode.

current, this flowing into R3 and LED3, which also lights up. The consequence is that all three l.e.d.'s are illuminated.

The circuit can be more readily followed if we omit the switch and redraw the circuit of Fig. 5(a) in the manner shown in Fig. 5(b). What we now have can be readily recognised as a common emitter amplifier with base bias from the negative rail being provided via LED2 and R2. The transistor is therefore turned on and causes collector current to be passed via LED3 and R3. Since the base and collector currents are approximately equal the circuit configuration requires only that the transistor has a current gain of unity, and such a requirement will obviously be met by any serviceable transistor.

In Fig. 6(a) we have the switch in position 3, whereupon current flows in R3 and LED3. The collector-base junction of the transistor acts as a forward connected diode and allows current to flow into R2 and LED2. Due to a minor anomaly associated with the bipolar transistor, current also flows from the emitter of the transistor into R1 and LED1. All three light-emitting diodes become illuminated.

To follow this situation more clearly, Fig. 6(b) shows the circuit of Fig. 6(a) rearranged and without the switch. Now, due to the symmetrical construction of a junction transistor it is possible for the device to function as a working transistor with the collector acting as an emitter and the emitter acting as a collector. The current gain offered by a transistor working in this mode is, normally, much lower than that given when the transistor is connected correctly but, in practice, the gain is found to be greater than the unity figure required by the present circuit. In Fig. 6(b) a base current flows in the base-collector junction (with the collector acting as an emitter) whereupon current flows in the circuit connected to the emitter (acting as a collector).

Reviewing the circuit operation illustrated in Fig. 4 to Fig. 6(b), a single l.e.d. lights up when S1 is in position 2 and all three l.e.d.'s light up when S1 is in positions 1 and 3. This identifies the transistor as a p.n.p. type with its base connected to terminal 2.

PRACTICAL POINTS

The author checked the prototype circuit with a wide range of transistors of both polarities, these consisting of modern silicon small signal and power types, and germanium small signal and power types. A few of the germanium transistors were very early types, such as the OC44, OC45 and OC71. All transistors checked out successfully in the manner just described.

Although not encountered by the author, there is a slight risk that some germanium power transistors may pass reverse leakage currents which

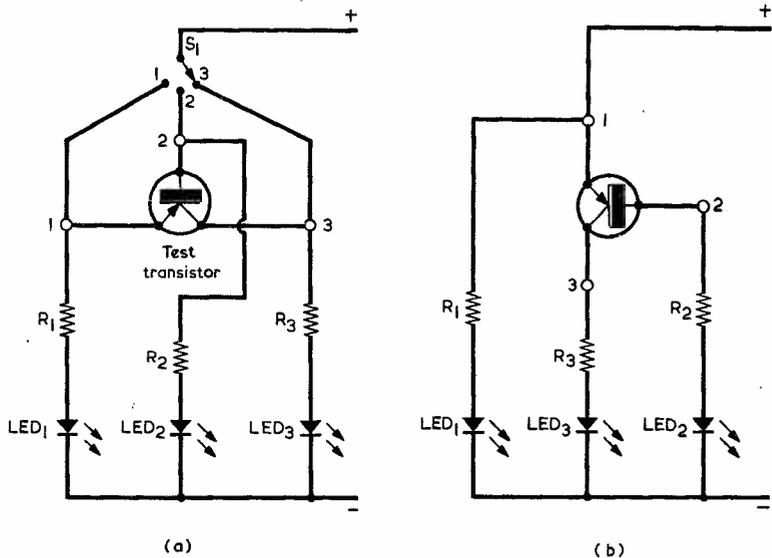


Fig. 6(a). All three l.e.d.'s are lit also when the switch is in position 3

(b). Rearranging the diagram shows transistor operation more clearly

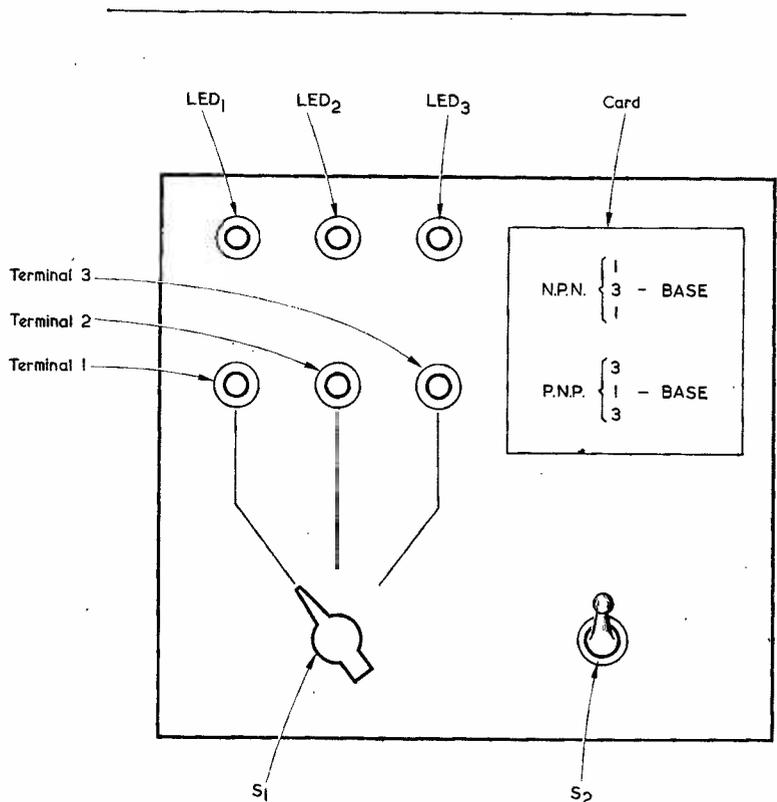


Fig. 7. A suitable front panel layout for the polarity/base resolver

could cause an l.e.d. to be partially illuminated when, properly, it should be extinguished. If this should occur, the partly lit l.e.d. should be considered as being extinguished and the transistor concerned looked upon as a specimen which passes a suspiciously high reverse leakage current. It is possible also that some p.n.p. transistors may not function adequately in the "wrong way round" mode of Figs. 6(a) and (b). Such an eventuality has to be mentioned for completeness but, in the writer's experience, it simply did not happen with any transistor checked by him.

Should it be found that a transistor does not cause illumination of the l.e.d.'s in one of the two manners just described, it is possible that it has a short-circuit or open-circuit junction or that it is, say, a field-effect transistor. A transistor with four lead-outs may be a bipolar type having one lead-out connecting to a shield and to the metal can. This lead-out can be identified with an ohmmeter before connecting the remaining three lead-outs to the test terminals.

The current flowing in each l.e.d. is of the order of 2mA and, assuming a forward voltage drop of 2 volts in each l.e.d., the highest voltage appearing at the test terminals will be 2.5 volts only. These low currents and voltages should not damage any transistors, including field-effect types, connected to the test terminals. In Fig. 5(a) the emitter current of the transistor is the sum of the base and collector currents, i.e. about 4mA. Similarly, the collector current in Fig. 6(a) is about 4mA. Such a current is still more than adequately low to ensure that no damage is caused to the transistor.

The three l.e.d.'s can be any small red types having reasonable sensitivity. Red l.e.d.'s Type 4, as supplied by Doram Electronics, were employed in the prototype circuit, and these give a surprisingly high light output at a forward current of 2mA. However, most other l.e.d.'s should offer a similar performance. With the Doram l.e.d.'s the anode lead-out is shorter than the cathode lead-out. The cathode lead-outs are those which connect to the negative rail.

The unit can be assembled in a small plastic case with S1, S2, the three l.e.d.'s and the test terminals on the front panel. A suggested panel layout is shown in Fig. 7. S1 is provided with a pointer knob, and lines are drawn on the panel linking it with the corresponding test terminals. This gives quick operation and there is no need to show the numbers 1, 2 and 3 on the panel itself. Also affixed to the panel is a card stating that n.p.n. transistors are identified by the fact that all three l.e.d.'s are lit at one switch position, whilst all three l.e.d.'s are lit at two positions for p.n.p. transistors. The card gives a reminder that the base lead-out is identified by three l.e.d.'s for n.p.n. transistors, and by one l.e.d. for p.n.p. transistors. ■

NEXT MONTH'S SPECIAL PROJECTS

• • •

CMOS CRYSTAL CALIBRATOR



A simple but comprehensive crystal calibration oscillator.


1 MHz — 500 kHz — 250 kHz — 100 kHz

• • •

MEDIUM AND DUAL SHORT WAVE RADIO

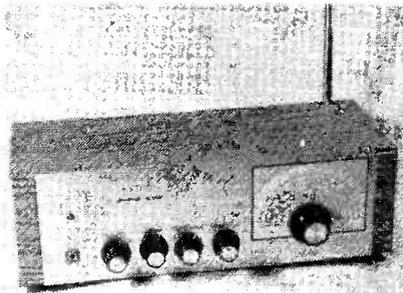Part 1

A self-contained 3-transistor design covering the medium wave band and 2 short wave bands.



ALL THE USUAL FEATURES
PLUS
MANY OTHER ARTICLES

ORDER NOW!

ON SALE
2nd MAY

THE "M5"

POCKET RECEIVER

Although this medium wave receiver is small enough to fit into a pocket it incorporates a full size 5 by 3 inch elliptical speaker and is specifically designed for economy of operation. The first two transistors are employed in a reflex circuit which provides a high level of amplification both at radio and at audio frequencies.

Almost all small portable receivers, whether commercially built or designed for home construction, have a weakness, in the author's opinion, in that too small a proportion of the space available is allowed for the speaker and the battery. Miniature speakers do not make a pleasant sound. The quality given by the 5 by 3 in. elliptical speaker used in the present design is far better than that obtainable, say, from the speaker measuring 2½ in. in diameter. And very small batteries like the PP3 normally employed in such receivers cause expensive running costs unless the current passed is only about 2 or 3mA — hardly practicable if speaker operation is required at anything above a whisper.

The present receiver uses a battery consisting of two HP2 or SP2 cells, giving a nominal 3 volts from which 25mA is drawn. A perfectly satisfactory output volume is obtained for a pocket receiver. For similar results to be obtained from a 9 volt battery a current of about 10mA would need to flow (we are considering total receiver current, not that drawn by the output stage only.). At the time of writing, two HP2 cells cost rather more than one PP3. Two SP2's cost less, but these will not give quite the same life as HP2's. According to figures supplied by Ever Ready, HP2 cells will give 205 hours at 25mA for an end point of 25% of the initial voltage, this assuming use at 4 hours per day. Under the same conditions only 18 hours use will be obtained from a PP3 at 10mA. Allowing for the extra cost of two HP2's, the economy of the arrangement used in this receiver is still about 8 times as good as that which would be given by a similar output from a PP3 battery. Which, when all is said and done, is worth having. Who would not jump at a mini which averaged 320 m.p.g.!

SPEAKER

The case of the receiver measures approximately 5½ by 4½ by 1½ in., and the set can be carried in a jacket pocket or lady's handbag. It is built around the Doram Electronics 3-4 Ω speaker code number 248-785, which has nominal dimensions of 5 by 3 in. In

practice the speaker is a little less than 5½ in. long and is 2½ in. wide. The mounting centres are 125.5 by 39.6mm., or approximately 5 in. by 1½ in., whilst the magnet diameter is ¾ in. We have been assured by Doram Electronics that, so far as can be reasonably maintained, speakers supplied against the code number just given will continue to have the same dimensions as that used in the prototype.

If a speaker having different dimensions is employed there may well have to be changes in the dimensions of the sections of the red receiver. This comment applies also to speakers having a magnet of different diameter. However, the circuit will work well with any 3 Ω speaker, and constructors who are not interested in miniature design can obtain excellent results using, say, an 8 by 5 in. speaker.

With reference to the name given to this receiver, the design is based on the author's "Miniflex" principle, which has formed the basis of four receivers appearing in earlier issues of this journal. A number of improvements have been made in the design and, of course, the layout and component details are quite new. The choice of title, "M5", is thus understandable.

Constructors are advised to study the diagrams carefully, and to read all the constructional details, before commencing work on the receiver. This will ensure that the parts are assembled together in correct manner.


CIRCUIT DETAILS

The circuit is shown in Fig. 1. The signal is picked up on the ferrite aerial winding, L1, which is tuned by VC1, and is applied to the base of TR1. Capacitor C1 provides a capacitive tap across the tuned circuit and allows reaction in the Colpitts mode to be provided without the necessity for a separate feedback winding. Selectivity is controlled to some extent by the value of C1. A value of 1,000pF gives slightly greater signal strength but with a small reduction in selectivity, whilst 470pF gives very good selectivity but with possibly unsatisfactory reaction at the higher frequen-

Part 1

By

Sir Douglas Hall, K.C.M.G.

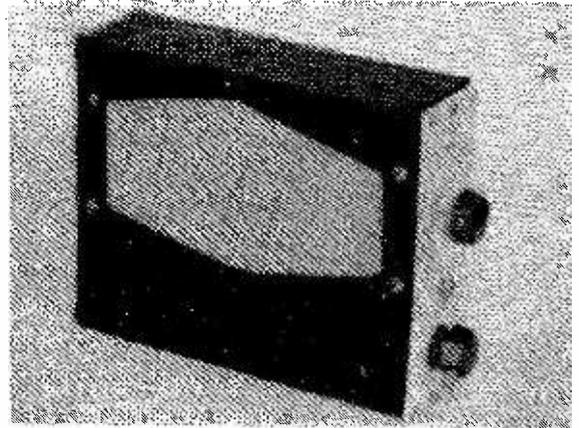

cies. The value of 680pF quoted in the Components List gives a good compromise.

TR1 is an emitter follower, and the r.f. signal at its emitter is applied to the base of TR2. At radio frequencies TR2 functions as a high gain common emitter amplifier, producing an output signal across the r.f. choke L2. This is applied to diode D1, which rectifies the signal and applies the detected a.f. back to the base of TR1 via L1. Note that D1 is a silicon

diode and that a germanium diode must not be used here. C2 shunts the diode and allows some feedback of the r.f. signal for regenerative purposes.

Once again TR1 functions as an emitter follower and the signal across R1 is applied to the base of TR2 which, at audio frequencies, similarly functions as an emitter follower. Indeed, the two transistors form a Darlington pair at a.f., whereupon the output at TR2 emitter is at very low impedance — of the order of 50 Ω. An interstage transformer, T1, is then employed

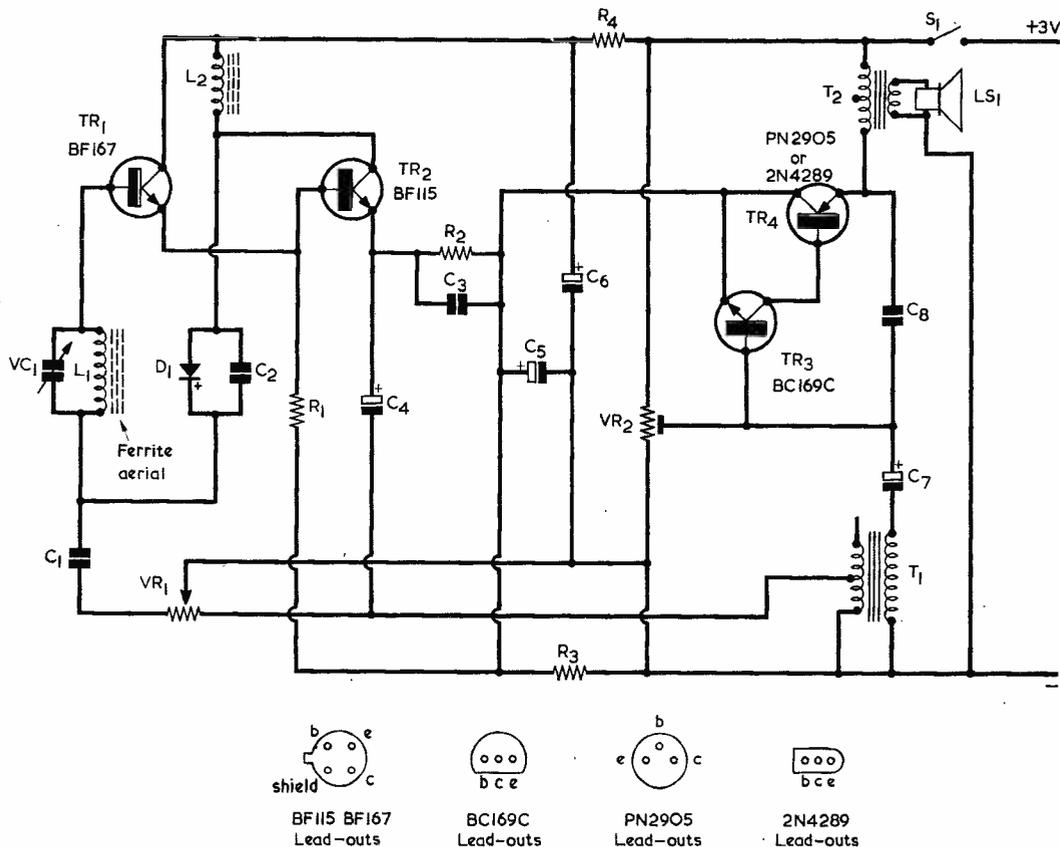


Fig. 1. The circuit of the "M5" medium wave portable receiver

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

R1 6.8k Ω

R2 390 Ω

R3 2.2 Ω

R4 82 Ω

VR1 220 Ω potentiometer, linear (see text)

VR2 100k Ω pre-set potentiometer, 0.1 watt skeleton, horizontal

Capacitors

C1 680pF silvered mica

C2 47pF silvered mica

C3 0.1 μ F plastic foil

C4 100 μ F electrolytic, 3 V. Wkg., axial (Siemens)

C5 1,000 μ F electrolytic, 3 V. Wkg., axial (Siemens)

C6 100 μ F electrolytic, 3 V. Wkg., axial (Siemens)

C7 2.2 μ F electrolytic, 25 V. Wkg., axial (Siemens)

C8 47pF silvered mica

VC1 300pF variable, "Dilemin" (Jackson)

Inductors

L1 ferrite aerial (see text)

L2 2.5mH r.f. choke, type CH1 (Repanco)

T1 Interstage transformer type LT44 (Eagle)

T2 Output transformer type TT56 (Repanco)

Semiconductors

TR1 BF167

TR2 BF115

TR3 BC169C

TR4 PN2905 or 2N4289

D1 1S44

Switch

S1 d.p.d.t. slide switch (see text)

Speaker

LS1 3-4 Ω 5 by 3in., code no 248-785 (Doram)

Miscellaneous

2-off HP2 cells (Ever Ready)

28-way tagstrip (see text)

Ferrite rod, 4 by $\frac{1}{8}$ in.

Spring clip, type no. LK-2721 (Lektrokit)

2-off control knobs

6BA studding

Spring (see text)

Materials for case (see text)



Nuts, bolts, wire, etc.

to give a step-up in voltage (as against the more usual step-down arrangement encountered in transistor circuits). There is in consequence a "free" voltage amplification of 10 times before further a.f. amplification is given by TR3.

TR3 gives a very large degree of amplification and its collector connects directly to the base of TR4, which operates as a Class A emitter follower output transistor. TR4 emitter couples to the primary of output transformer T2, whose secondary couples in turn to the speaker. Pre-set potentiometer VR2 sets the bias current for the base of TR3 and is adjusted such that TR4 passes an emitter current of 23mA. A

typical transistor in the TR4 position can be expected to have a current amplification of 150, whereupon a base current of about 150 μ A will produce the desired emitter current. This base current is also, of course, the collector current of TR3. Since TR3 collector current is only about 150 μ A, and since it has a current gain of about 500, its input impedance is high and there is no significant damping of the winding of T1 which feeds it. The overall amplification is therefore good as also, within the limitations of the output power available, is the quality of reproduction.

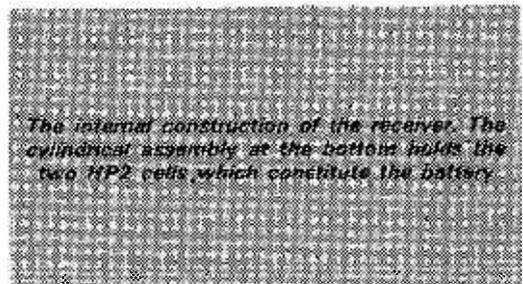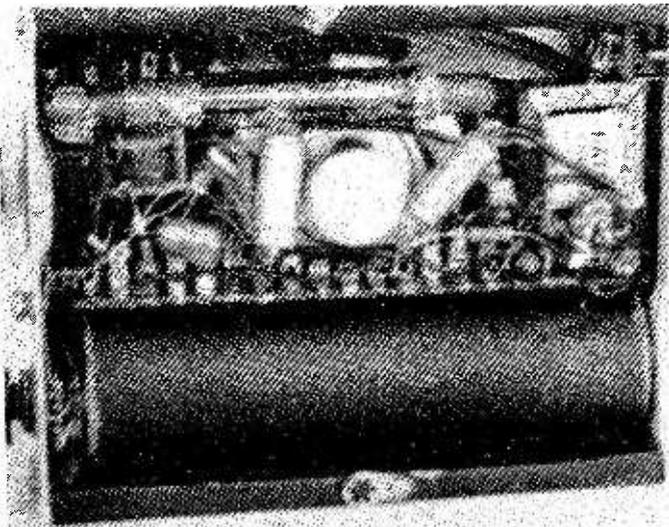R3 provides negative feedback at d.c. for TR3 and TR4, a.f. feedback being cancelled here by the large



The internal construction of the receiver. The cylindrical assembly at the bottom holds the two HP2 cells which constitute the battery.

value capacitor, C5. The main purpose of C8 is to prevent amplification by TR3 and TR4 of any r.f. signal which may filter through to these two transistors. C8 also provides a little top cut.

Volume and reaction are controlled by VR1. As the slider of this potentiometer approaches the end of the track connecting to C1 regeneration increases. On the other hand, as the slider approaches the end of the track connecting to the input winding of T1 the resistance across that winding reduces until, at zero setting, no audio signal at all is applied to TR3. The overall effect is that of an efficient reaction control combined with an equally efficient audio frequency volume control.

The type of component chosen for T2 is important. The d.c. resistance of its primary must be very low, as is essential when a 3 volt supply is available and only a small voltage drop can be afforded. Initially, the author employed an R.S. Components output transformer type T/T7. This has now been discontinued, but the author mentions the fact in case readers may have one of these transformers in their spares box. A suitable alternative is the Repanco type T/T56 output transformer. The Repanco transformer is modified by the removal of its clamp.

Due to the small size of the receiver and other fac-

tors, a number of the components have to be specified by make and type. All the electrolytic capacitors are Siemens axial types, these being listed by Electrovalue Ltd., 28 St. Jude's Road, Englefield Green, Egham, Surrey, TW20 0HB. Potentiometer VR1 is a type P20 component, also available from Electrovalue. One of the two alternatives for TR4, the PN2905, is again stocked by Electrovalue.

Slide switch S1 should be a miniature d.p.d.t. slide switch having fixing centres at approximately 1½ in. (29mm.). A miniature 28-way R.S. Components tagstrip is required, and this can be obtained from Doram Electronics as a 28-way tagstrip type B. The ferrite rod is 4 in. by ⅜ in. and may be obtained in this size, or can be a longer rod cut down. In the latter instance a V-cut is made with a triangular file all round the rod at the point where it is to be broken and it is then tapped sharply against the bench. The ferrite rod is held by a ⅜ in. spring clip, this being a Lektrokit part no. LK2721 which is available (in packets of 10) from Home Radio. Home Radio can also provide 12 in. lengths of 6BA brass studding (threaded rod), which is required for the receiver assembly.

A small spiral spring is required for fitting between the two cells. This can be obtained from a cycle or hardware store, and further details of it are given later.

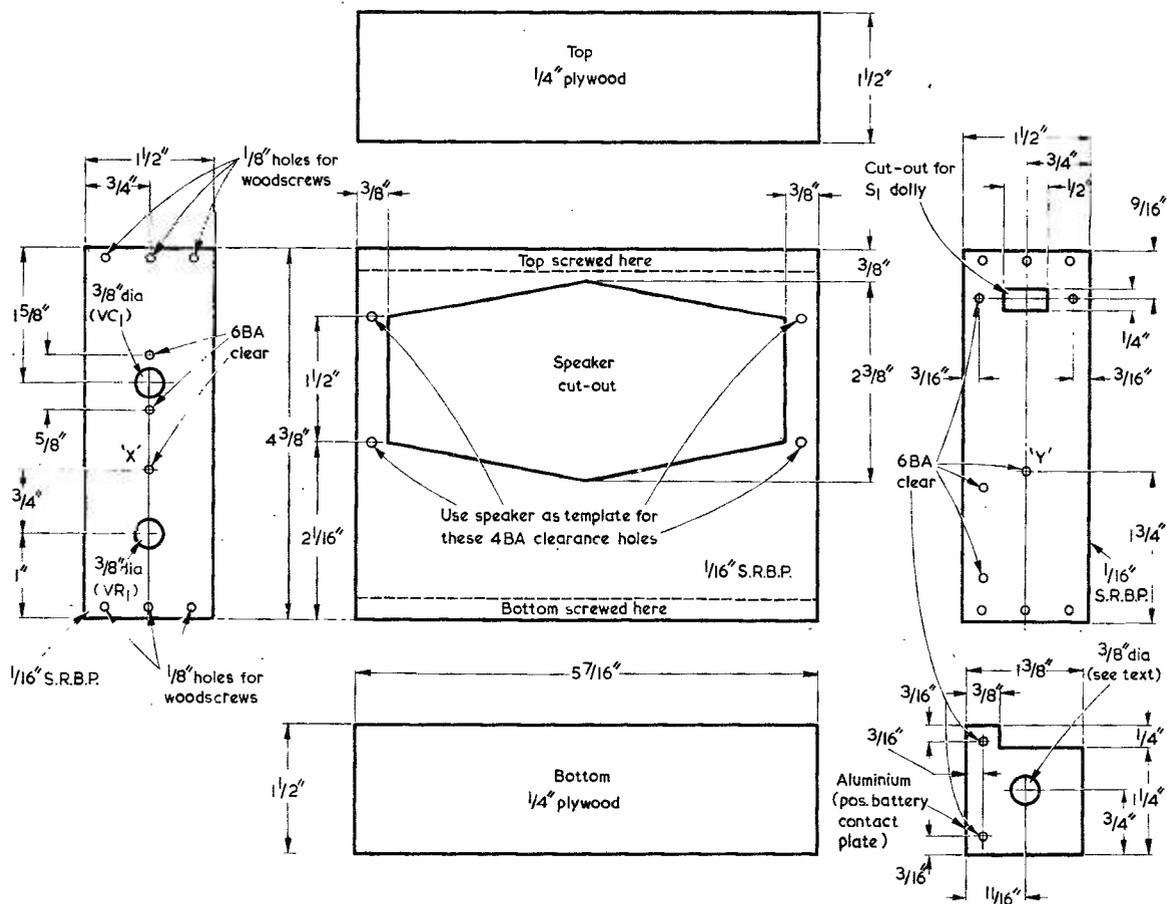


Fig. 2. Details of the sections which make up the receiver case

CONSTRUCTION

Construction starts with the cutting out of the items shown in Fig. 2. It will be seen that the materials used here are small pieces of $\frac{1}{8}$ in. plywood, $\frac{1}{8}$ in. s.r.b.p., and aluminium sheet of any gauge between 16 and 20 s.w.g. First cut out and drill the s.r.b.p. speaker panel and cut out the top and bottom plywood panels. Screw the top and bottom to the speaker panel using five countersunk screws for each plywood piece and then cover this assembly with Fablon of a suitable choice.

Take up VR1. The metal back of the case of this potentiometer makes contact with the negative side of the battery formed by the two HP2 cells, and it will be found that an extension of the plastic spindle protrudes slightly at the back (to couple with the switch in a combined potentiometer and switch). File down this extension, so that the HP2 cell will be able to make reliable contact with the potentiometer back.

Next cut out the two s.r.b.p. sides. The two 6BA clear holes on either side of the spindle hole for VC1 take 6BA bolts which secure the capacitor in place. It will be found that VC1 frame is very close to, or touches, the speaker frame when the sides are assembled, and it may be necessary to shift the 6BA clear holes very slightly to the left, as shown in Fig. 2. This was not needed with the prototype, but the point can be checked at the present state of construction. The orientation of VC1 can be seen in the wiring diagram of Fig. 3.

The fixing holes and dolly slot dimensions for slide

when the tip of the drill just appears. The resulting depression ensure good seating for the battery positive stud. The contact plate is used as a template to mark out the corresponding two 6BA clear holes in the s.r.b.p. panel. Position of the aluminium plate on the s.r.b.p. panel so that there is a $\frac{1}{8}$ in. free at the bottom (to give clearance for the plywood bottom panel) and $\frac{1}{8}$ in. clearance on either side, then mark out and drill the holes in the s.r.b.p. panel. Fit the contact plate, and cover both the s.r.b.p. panels with Fablon. A contrasting colour of Fablon for the sides, as against the front, top and bottom, gives an effective finish. The prototype had plain black for the front, top and bottom, and plain yellow for the sides and back (to be described later). Mount VC1, VR1 and S1, and also wire in C1, all as shown in Fig. 3. Then put the two s.r.b.p. panels on one side for the time being.

Make up a sleeve of paper or Fablon about 3 in. long, and put it on the ferrite rod. Close-wind 70 turns of 26 s.w.g. enamelled wire in a single layer on this sleeve, the winding starting about $1\frac{1}{4}$ in. from one end of the rod. Anchor the coil ends with tape and put the rod on one side for use later.

Mount the speaker over a piece of thin gauze, using three 1 in. roundhead 4BA bolts and one $\frac{1}{8}$ in. roundhead 4BA bolt. Following the view shown in Fig. 3, fit the three 1 in. bolts at the bottom and upper left hand speaker holes, and the $\frac{1}{8}$ in. bolt at the upper right hand speaker hole. As will be deduced from the diagram, two tagstrips and the ferrite aerial clip will be mounted on the 1 in. bolts.

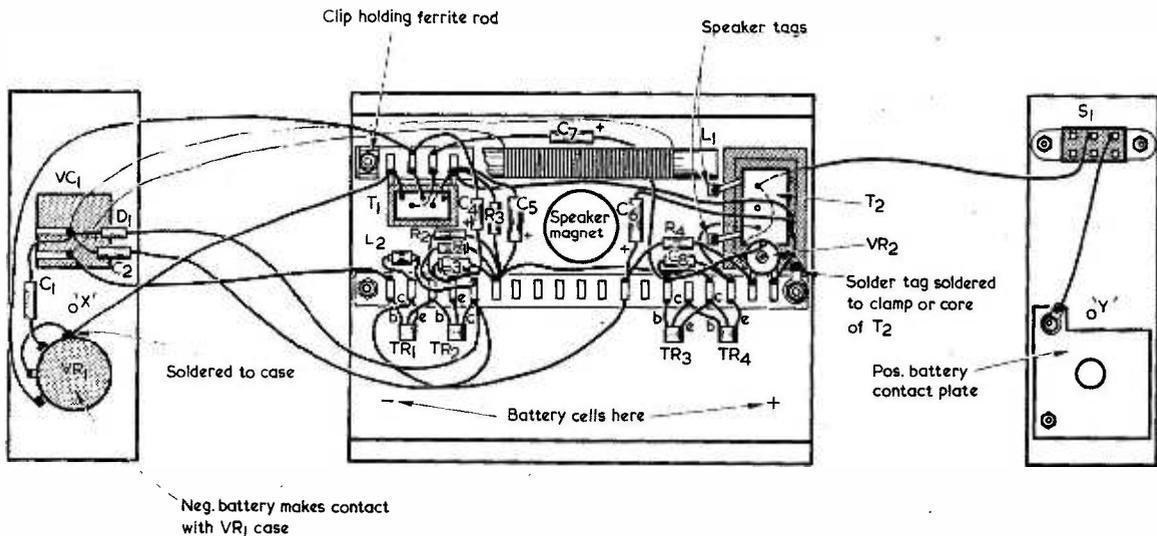


Fig. 3. Wiring and layout of the components in the receiver. Note that part of the circuit is completed via the clamp feet of T1

switch S1 on the right hand s.r.b.p. panel (again as seen in Fig. 2) correspond to those required by the switch used by the author. They may require slight modification with other switches. When mounted, the body of the switch is on the inside of the s.r.b.p. panel.

The aluminium plate in Fig. 2 provides the battery positive connecting point. The $\frac{3}{8}$ in. hole in its centre is not drilled all the way through, and drilling ceases

NEXT MONTH

In next month's issue, the concluding article will complete the constructional details for this receiver and will describe the simple setting up procedure required to bring it into full working order.

(To be concluded)


SPECIAL PROJECT . . .

CMOS

AUDIO AMPLIFIER

By R. A. Penfold

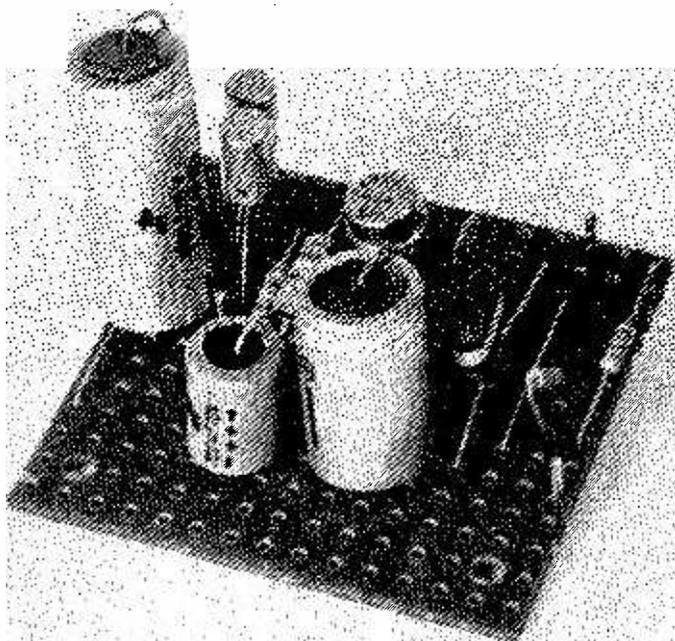Incorporating a linear CMOS integrated circuit, this unusual a.f. amplifier offers a low quiescent power supply drain and requires no protection against thermal runaway in the output transistors.



As anyone who has designed a Class B transistor a.f. amplifier will know, one of the main problems is the elimination of significant levels of crossover distortion. This type of distortion is particularly troublesome since it increases with decreasing output power, and it is at low levels that the distortion is most noticeable.

OUTPUT STAGE

A basic Class B emitter follower output stage is shown in Fig. 1. TRA is the driver transistor and the circuit is set up such that under quiescent no-signal conditions its collector potential is approximately mid-way between the positive and negative supply rails. If a signal is applied the collector then goes

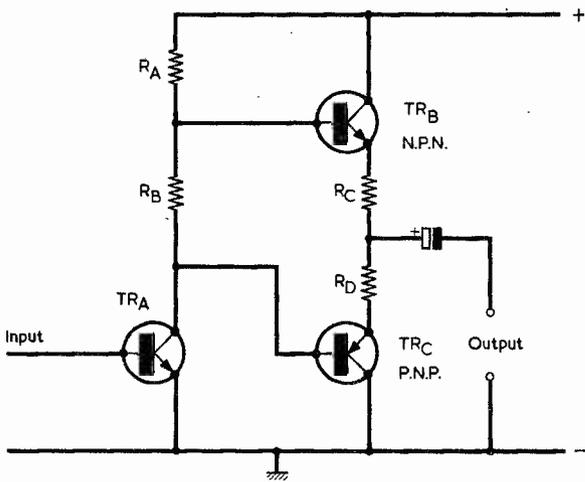


Fig. 1. Basic circuit for a complementary emitter follower Class B output stage

positive and negative in response to the signal waveform. When it goes positive, transistor TRB becomes conductive and acts as an emitter follower, causing a corresponding voltage to be passed to the output load. TRC becomes conductive as an emitter follower when the collector of TRA goes negative. TRB and TRC do not offer any voltage gain but provide a high level of current amplification, whereupon the output load can have a relatively low impedance. The load is normally, of course, a loudspeaker.

Let us assume for a moment that RB is not in circuit and that the bases of TRB and TRC are connected together. If the output transistors are silicon types, TRB will not then become conductive until its base is taken some 0.65 volt positive of its emitter. In the same way, TRC will not become conductive until its base is taken about 0.65 volt negative of its emitter. The result will be a very high degree of crossover distortion in the output signal, as is illustrated in Fig. 2 where the central part of the signal waveform is not amplified at all. The waveform in Fig. 2 has a peak amplitude of some 3 or 4 volts, and it is obvious that the crossover distortion will become proportionately more severe for signals of lower amplitude.

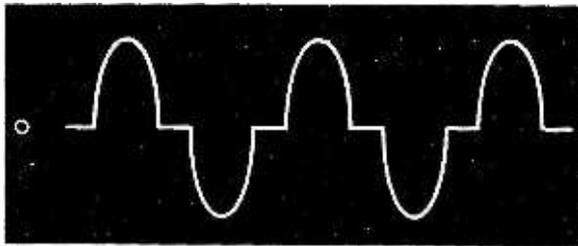


Fig 2. If RB of Fig. 1 were omitted and the output transistor bases connected together, a sine wave input would be reproduced at the output in the manner shown here

Germanium transistors do not become conductive until the base is taken about 0.2 volt forward of the emitter. If TRB and TRC of Fig. 1 were germanium transistors, they would not amplify until the signal at TRA collector passed 0.2 volt positive and negative of the quiescent level. Again, a high degree of crossover distortion would result.

It is to prevent crossover distortion that resistor RB is interposed between the bases of TRB and TRC. The collector current of TRA flows through RB, and the latter can be given a value such that it drops about 1.3 volts (twice 0.65 volt) for silicon output transistors or about 0.4 volt (twice 0.2 volt) for germanium output transistors. Thus, both output transistors are just conductive under quiescent conditions, and respond to small as well as large signal excursions at the collector of TRA. In consequence the crossover distortion is reduced.

It is not, unfortunately completely eliminated. This is because the current gain of the output transistors is lower when they are just conductive than it is when they pass an appreciable collector and emitter

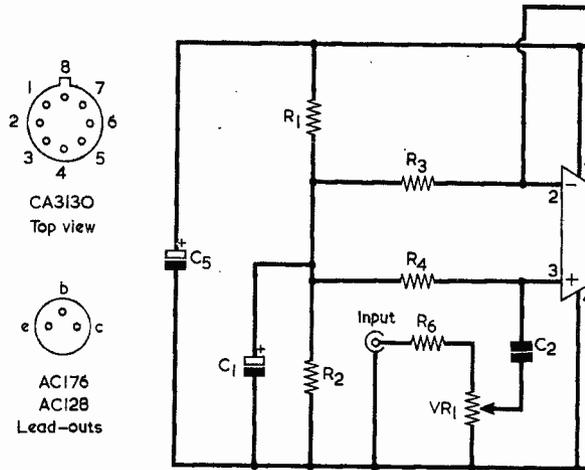


Fig. 3. The circuit of the CMOS audio amplifier. The ditic

current. One way of further reducing the crossover distortion which still remains is to give RB a higher value again, causing the output transistors to pass an appreciable current under quiescent conditions. Such an approach, however, raises further problems.

THERMAL RUNAWAY

If the two output transistors pass a significant current under quiescent conditions there is a waste of supply power, and this is an undesirable feature if the amplifier is battery driven. What is, perhaps, a more important point is that there is an increased risk of thermal runaway.

Should the temperature of the output transistors increase due to normal power dissipation or to a high

Germanium transistors do not become conductive until the base is taken about 0.2 volt forward of the emitter. If TRB and TRC of Fig. 1 were germanium transistors, they would not amplify until the signal at TRA collector passed 0.2 volt positive and negative of the quiescent level. Again, a high degree of crossover distortion would result.

It is to prevent crossover distortion that resistor RB is interposed between the bases of TRB and TRC. The collector current of TRA flows through RB, and the latter can be given a value such that it drops about 1.3 volts (twice 0.65 volt) for silicon output transistors or about 0.4 volt (twice 0.2 volt) for germanium output transistors. Thus, both output transistors are just conductive under quiescent conditions, and respond to small as well as large signal excursions at the collector of TRA. In consequence the crossover distortion is reduced.

It is not, unfortunately completely eliminated. This is because the current gain of the output transistors is lower when they are just conductive than it is when they pass an appreciable collector and emitter

ambient temperature, their base-emitter turn-on voltages become decreased, whereupon they are capable of passing under quiescent conditions an increased current. This in turn raises their temperature again, with a consequent further reduction in base-emitter turn-on voltage. The process is self-sustaining and can lead eventually to the transistor temperatures becoming so high that they burn out. The effect is known as thermal runaway.

Partial prevention of thermal runaway can be achieved by replacing RB with a temperature sensitive voltage dropping device such as a thermistor, a diode or a diode-connected transistor. The voltage across the device falls as its temperature increases, whereupon the base-emitter voltages applied to the output transistors decrease. An approach of this nature assists in preventing thermal runaway due to high ambient temperature, although it cannot guard against temperature rise due to power dissipation in the output transistors themselves unless the voltage dropping device is thermally coupled to them.

Another method of reducing the risk of thermal

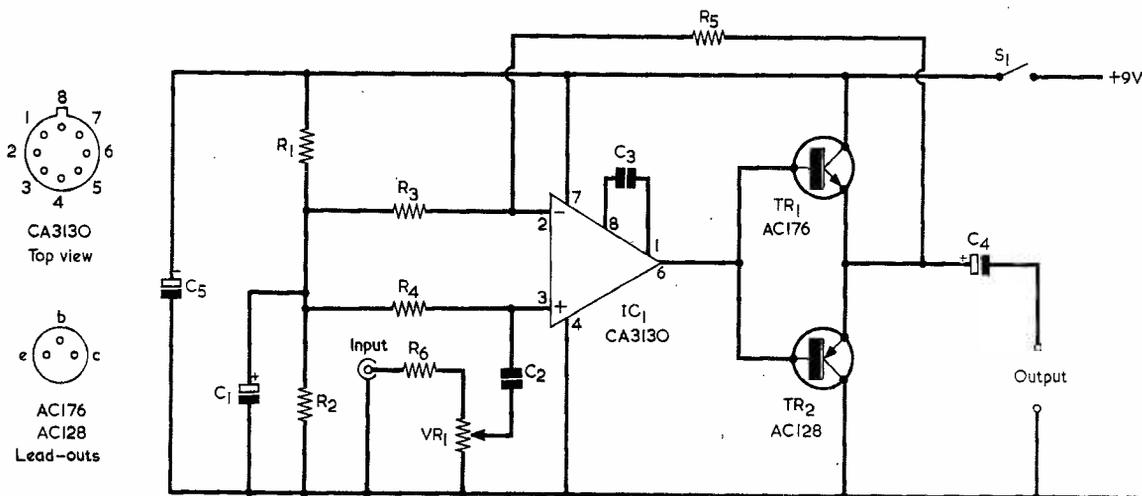


Fig. 3. The circuit of the CMOS audio amplifier. The output transistors are cut off under quiescent conditions

current. One way of further reducing the crossover distortion which still remains is to give RB a higher value again, causing the output transistors to pass an appreciable current under quiescent conditions. Such an approach, however, raises further problems.

THERMAL RUNAWAY

If the two output transistors pass a significant current under quiescent conditions there is a waste of supply power, and this is an undesirable feature if the amplifier is battery driven. What is, perhaps, a more important point is that there is an increased risk of thermal runaway.

Should the temperature of the output transistors increase due to normal power dissipation or to a high


runaway consists of inserting low value resistors, RC and RD, in series with the emitters, as illustrated in Fig. 1. If the output transistor current increases, so does the voltage dropped across the resistors, with a corresponding reduction in the transistor base-emitter voltages. Naturally, some of the output power is wasted in the resistors.

In the amplifier circuit which is described in this article, advantage is taken of a CMOS linear op-amp to provide an output stage having none of the drawbacks which have just been detailed. Both the output transistor bases are connected together, whereupon the risk of thermal runaway is removed and resistors RC and RD are not required. Also, the very high gain of the CMOS op-amp enables a negative feedback loop to be set up which brings crossover distortion down to a negligibly low level.

ambient temperature, their base-emitter turn-on voltages become decreased, whereupon they are capable of passing under quiescent conditions an increased current. This in turn raises their temperature again, with a consequent further reduction in base-emitter turn-on voltage. The process is self-sustaining and can lead eventually to the transistor temperatures becoming so high that they burn out. The effect is known as thermal runaway.

Partial prevention of thermal runaway can be achieved by replacing RB with a temperature sensitive voltage dropping device such as a thermistor, a diode or a diode-connected transistor. The voltage across the device falls as its temperature increases, whereupon the base-emitter voltages applied to the output transistors decrease. An approach of this nature assists in preventing thermal runaway due to high ambient temperature, although it cannot guard against temperature rise due to power dissipation in the output transistors themselves unless the voltage dropping device is thermally coupled to them.

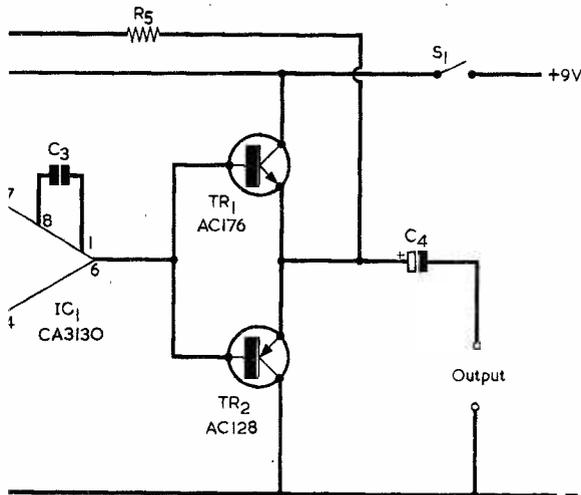Another method of reducing the risk of thermal



output transistors are cut off under quiescent conditions

runaway consists of inserting low value resistors, RC and RD, in series with the emitters, as illustrated in Fig. 1. If the output transistor current increases, so does the voltage dropped across the resistors, with a corresponding reduction in the transistor base-emitter voltages. Naturally, some of the output power is wasted in the resistors.

In the amplifier circuit which is described in this article, advantage is taken of a CMOS linear op-amp to provide an output stage having none of the drawbacks which have just been detailed. Both the output transistor bases are connected together, whereupon the risk of thermal runaway is removed and resistors RC and RD are not required. Also, the very high gain of the CMOS op-amp enables a negative feedback loop to be set up which brings crossover distortion down to a negligibly low level.

THE CIRCUIT

The complete circuit of the amplifier is given in Fig. 3, and it will be seen that this is quite simple and requires few components. The input and driver stages are provided by the CMOS op-amp, which is a CA3130. The output transistors are germanium types rather than silicon, since their lower base-emitter forward voltages permit a slightly higher output voltage swing. They are connected in a complementary emitter follower output circuit. The amplifier will provide an output power of about 300mW into a 15Ω speaker. Higher impedance speakers can also be used but will cause a reduction in the maximum output power. With a 40Ω speaker, for example, the maximum output power is limited to about 125mW. Speakers with impedances lower than 15Ω should not be used.

An input of slightly more than 100mV r.m.s. is required for maximum output, and the input impedance is about 120kΩ. Both these figures apply when the volume control, VR1, is set to maximum. They can be altered to some extent to suit individual requirements by changing component values, and this aspect is discussed later.

The amplifier has a quiescent current demand of approximately 3.5mA from the 9 volt battery, this consisting of the current drawn by IC1 plus a small current in R1 and R2. In the absence of an input signal only leakage current flows in the output transistors. At full output the current consumption is at an average level of around 50mA.

COMPONENTS

Resistors

(All fixed values ¼ watt 5%)

R1 5.6kΩ

R2 5.6kΩ

R3 12kΩ

R4 220kΩ

R5 220kΩ

R6 10kΩ (See text)

VR1 220k · potentiometer, log

Capacitors

C1 330μF electrolytic, 10 V. Wkg.

C2 0.1μF type C280 (Mullard)

C3 150μF ceramic

C4 680μF electrolytic, 10 V. Wkg.

C5 100μF electrolytic, 10 V. Wkg.

Semiconductors

IC1 CA3130

TR1 AC176

TR2 AC128

Switch

S1 s.p.s.t. switch

Miscellaneous

Speaker (see text)

9 volt battery

Battery connector

Veroboard, 0.15in. Matrix

Veropins, 0.15in. type

Input socket (see text)

Screened wire.

All in all, the circuit of Fig. 3 is very versatile and will have many possible uses.

Considering the circuit in detail it will be seen that IC1 is used as a non-inverting amplifier. Both its inputs are coupled via resistors to the junction of R1 and R2, which provides a voltage which is central between the supply rails. C1 is a bypass capacitor.

Since the input impedance of the non-inverting input at lead-out 3 of the i.c. is extremely high, R4 can have any value. The input impedance of the amplifier can, if desired, be altered by changing the values of R4 and the volume control. C2 provides d.c. blocking at the non-inverting input. The 10k Ω resistor, R6, has no significant effect on a.f. performance and is merely a surge current limiting resistor to protect the i.c. if the input is derived from a battery powered pre-amplifier.

C3 is the compensating capacitor for the i.c. and prevents it from breaking into oscillation. No connection is made to lead-out 5 of the i.c. The output is taken from lead-out 6 and is applied directly to the bases of TR1 and TR2. C4 is the output d.c. blocking capacitor, whilst C5 is the supply bypass capacitor for the whole amplifier. S1 is the on-off switch.

NEGATIVE FEEDBACK

Negative feedback from the emitters of TR1 and TR2 to the inverting input of the i.c. is provided by R5 and R3. The voltage gain of the amplifier is equal to $(R3 + R5)$ divided by R3, and this works out as a little under 20 times, or 26dB, with the resistor values specified. The open loop voltage gain of the CA3130 (i.e. the gain without feedback) is extremely high, being typically 320,000 times. Thus, a very large amount of negative feedback is provided in the circuit.

The manner in which the feedback takes up the output base voltage range at which neither transistor conducts is quite simple. Assume that both the non-inverting input and the output of the i.c. are at zero potential. Theoretically, the output transistors are non-conductive and there is no negative feedback.

The non-inverting input now starts to go positive. The slightest positive excursion at the op-amp input will cause its output to swing to the positive level required to cause TR1 to become conductive, whereupon the negative feedback loop will then come into operation. Similarly, the slightest negative excursion of the input will take the op-amp output sufficiently negative to turn on TR2 and cause the feedback loop to be completed once more.

As an input signal passes through zero level there will be an instant when the op-amp has its full open loop gain and its output swings from one transistor base to the other, thereby re-introducing negative feedback and normalising the gain. The input signal range over which the op-amp output changes from one transistor to the other is extremely small, whereupon crossover distortion is virtually eliminated.



The assumption was made just now that the op-amp non-inverting input and output were at zero level. In practice, the op-amp output would not remain steady at zero level but, due to the very high open loop gain, would swing from one transistor base to the other, actuated by the inevitable low noise level at the input.

In the accompanying oscillogram the lower trace shows a 500Hz sine wave applied at a power level of a few milliwatts to a 15 Ω speaker. The corresponding waveform at the output of the op-amp is illustrated by the upper trace. The greatly increased gain in the op-amp near the waveform centre can be clearly observed.

CONSTRUCTION

The amplifier is assembled on a piece of Veroboard of 0.15in. matrix having 15 holes by 14 copper strips. The component and copper sides of this board are shown in Fig. 4. Before mounting any components, the two 6BA clear holes are drilled and the three breaks made in the copper strips.

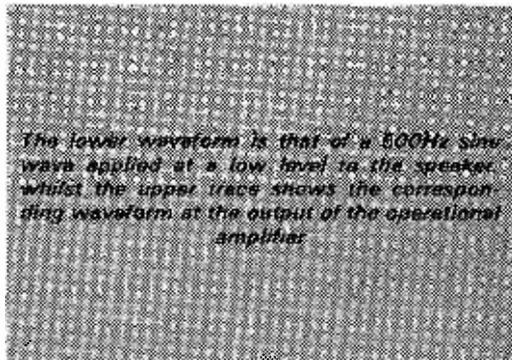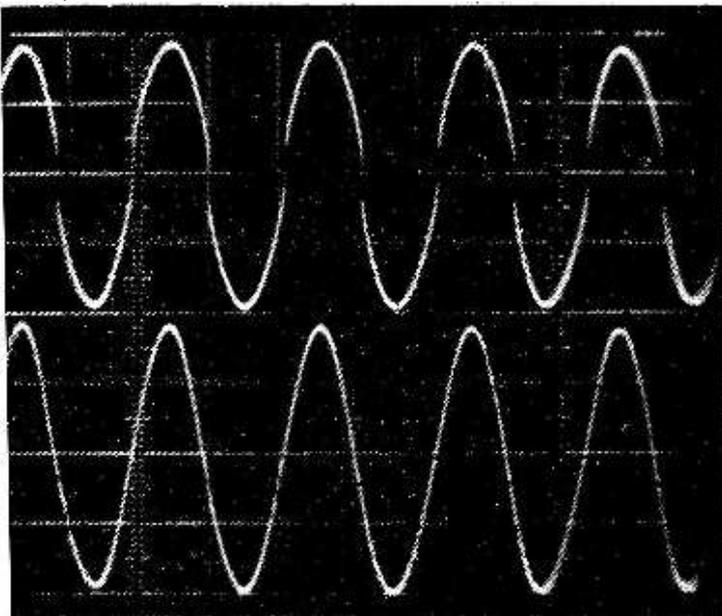The components and wire links may then be soldered to the board. To avoid damage to the integrated circuit, the soldering iron employed must




have a reliably earthed bit. Being germanium transistors, TR1 and TR2 are more liable to damage by heat than silicon types, and their lead-outs should be soldered reasonably quickly. Veropins are fitted for the external connections to the speaker, the battery, S1 and VR1. R6 is not fitted on the board and is wired between VR1 and the input socket. The latter can be a jack socket, phono socket or any other type of socket preferred. S1 may be ganged with VR1 if desired.

The circuit has a fairly high gain and input impedance, and the input and output are in phase. Screened leads must therefore be used in the input circuit. Otherwise, there could be feedback between the output and input wiring with consequent instability.

A suitable battery is the Ever Ready PP9.

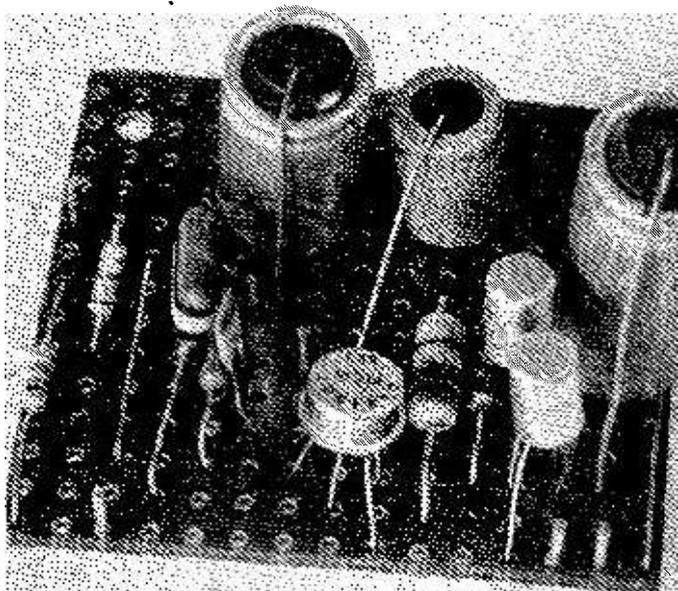The output quality is well above average for a simple battery operated amplifier, and this is due to the large amount of negative feedback which is employed. The noise level is also very low, as is to be expected when an op-amp provides the voltage amplification. The unweighted noise level of the prototype (input short-circuited) is approximately -80dB.



Another view of the amplifier

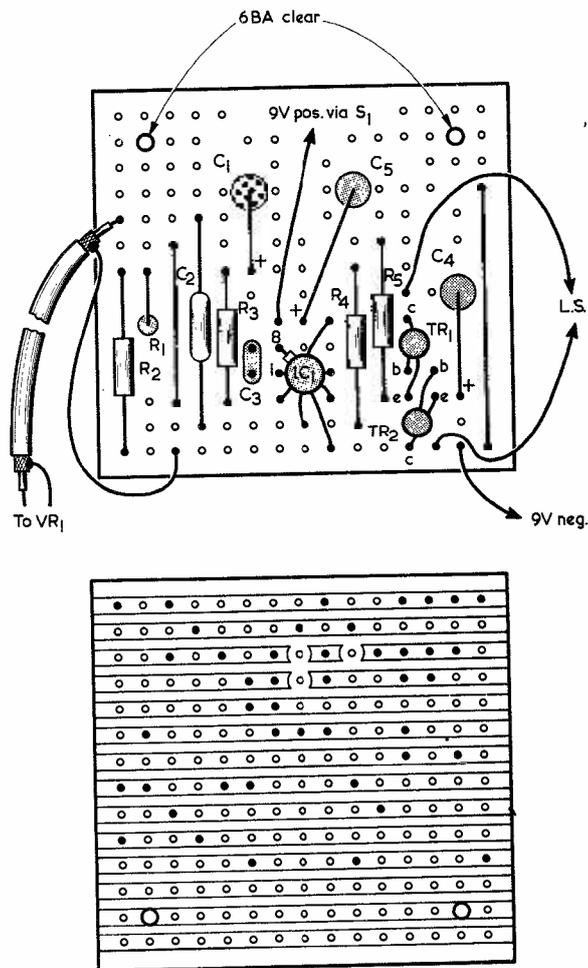


Fig. 4. Component and copper sides of the Veroboard panel on which the amplifier is assembled

MODIFICATIONS

If required, the gain and input impedance of the circuit are easily modified. The voltage gain is varied by altering the value of R5, working to the expression for gain which was given earlier. However, R5 should not be given a value greater than 680k Ω as the output quality may then deteriorate. With R5 at 680k Ω the input required for maximum output is only about 35mV r.m.s. Slightly in excess of 2 volts r.m.s. is required at the amplifier output for maximum power.

The input impedance is determined by VR1 and R4. It is desirable for these to have approximately the same value whereupon the input impedance (with VR1 set to maximum) is approximately R6 plus one-half of R4. If the input impedance is reduced significantly the value of C2 should be increased proportionately, as there will otherwise be a loss of bass response. If an electrolytic capacitor is employed here, the negative lead-out connects to VR1 slider. Instability may be a problem if the input impedance is increased, and this can be cured by adding a 100pF capacitor between lead-out 3 of the i.c. and the negative rail. This reduces the input impedance of the circuit at high frequencies and so reduces unwanted feedback to an insignificant level. There is plenty of space for the extra capacitor on the Veroboard panel.

R6 is included to meet the manufacturer's specification that input currents at the inputs of the CA3130 should not exceed 1mA. If the amplifier were preceded by a pre-amplifier with an output coupling capacitor, the situation is feasible in which a current surge could flow at switch-on or switch-off of the pre-amplifier. R6 has a value suitable for a pre-amplifier powered by a 9 volt battery. It should be increased for pre-amplifiers with a higher supply voltage. A value of 15k Ω would be suitable if the pre-amplifier had a 12 volt supply, and so on. As already stated, R6 plays no part otherwise in the functioning of the amplifier. ■

"HEADS OR TAILS?"

by J. R. Davies

Apart from describing a very simple electronic "heads or tails" device, this article also illustrates a method of obtaining a 50-50 square wave from a 555 timer.



Electronic 2-state gambling devices which offer a random output when a push-button is pressed have become popular over recent years. Currently, design has reached the stage where the output of a multivibrator is passed, via a press-to-break push-button, to the clock input of a J-K flip-flop. Two light-emitting diodes are driven by the Q and not-Q outputs of the flip-flop, these outputs changing state with each pulse from the multivibrator. There is then a true 50:50 possibility of either i.e.d. being illuminated when the push-button is pressed.

The circuit to be described here incurs a slight regression in design approach because it does not take advantage of the true 50:50 option provided by a J-K flip-flop. On the other hand it is extremely simple to assemble, requires very few components and can be set up for 50:50 operation as closely as can be determined by a multimeter set to an appropriate voltage range. What will be of greater interest to the serious experimenter is the fact that the circuit demonstrates a means of obtaining a 50:50 square wave from a 555 timer when it is connected as a standard astable multivibrator.

CIRCUIT OPERATION

The circuit of the 555 "Heads or Tails" appears in Fig. 1. For the time being components VR1 and R1 should be ignored.

After switch-on at S2, C1 commences to charge via R2 and R3 until the voltage at its upper plate reaches two-thirds of supply potential. The comparator at pin 6 of the i.c. is then triggered, causing the internal flip-flop to change state and pin 7 to go low in voltage. The capacitor then discharges via R3 on its own until the voltage on its upper plate falls to one-third of supply potential. The comparator coupled to pin 2 is then actuated, pin 7 becomes open and the capacitor charges once more via R2 and R3. The oscillations thus continue with the upper plate of C1 alternately rising to two-thirds of supply potential and falling to one-third of supply potential.

The output at pin 3 goes high when the capacitor charges and goes low when the capacitor discharges. When the output is high a current flows through R5 and LED2, whereupon this i.e.d. lights up. With the output low, current flows through R4 and LED1, causing the latter i.e.d. to become illuminated. In consequence the two i.e.d.'s light successively. The output at pin 3 is virtually completely isolated from the internal comparator trigger circuits.

If push-button S1 is pressed, the circuit to pins 2 and 6 of the i.c. is broken. Should this occur at an instant when the capacitor is charging it continues to charge until it reaches supply potential, and the output at pin 3 remains in the high state with LED2 continually lit. Had the circuit been broken when the capacitor was discharging, it would continue to discharge and the output at pin 3 would be maintained in the low state, with LED1 continually illuminated. Thus, pressing S1 causes either LED1 or LED2 to remain lit, and this provides the "heads or tails" function of the circuit. Releasing S1 causes the multivibrator to resume oscillation with LED1 and LED2 alternately flashing.

The circuit runs at a frequency of the order of 7Hz. This is sufficiently slow to enable the alternate illumination of LED1 and LED2 to be perceived but,

COMPONENTS

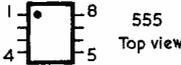
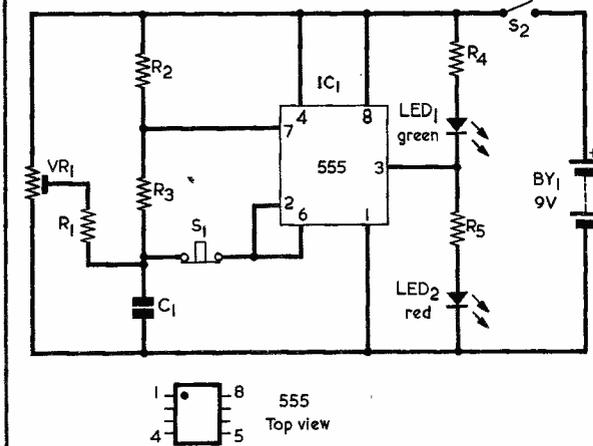


Fig. 1. The circuit of the 555 "Heads or Tails?" A feature of the design is that VR1 can be adjusted for a 50:50 square wave output from the 555

Resistors (All fixed values $\frac{1}{4}$ watt 5%)

- R1 470k Ω
- R2 4.7k Ω
- R3 100k Ω
- R4 1k Ω
- R5 1k Ω
- VR1 100k Ω , pre-set potentiometer, skeleton

Capacitor C1 1 μ F plastic foil

Semiconductors

- IC1 555
- LED1 green l.e.d.
- LED2 red l.e.d.

Switches

- S1 push-button, press-to-break
- S2 s.p.s.t., toggle

Battery

- BY1 9 volt battery

with human reaction time at about a third of a second, is just too fast to allow the push-button to be pressed at the appropriate instant by observation of the l.e.d.'s. Assuming that the output at pin 3 is a 50:50 square wave, the selection of either l.e.d. then becomes a random process.

SQUARE WAVE OPERATION

If VR1 and R1, which we have ignored up to now, were not in circuit, the output of the 555 could not, however, be a 50:50 square wave. This is because the capacitor charges via the two resistors R2 and R3 and discharges via the single resistor R3. In consequence the charge section of the multivibrator cycle is longer than the discharge section. It would be possible to have the output approach a 50:50 sine wave by making R2 very much smaller than R3. In the present circuit R2 has a value which is about one-twentieth of R3 and so the charge period is some 5% longer than the discharge period.

It is also assumed when discussing the 555 i.c., that internal flip-flop triggering occurs at precisely two-thirds and precisely one-third of supply voltage whereas, in practice, there must be some tolerance in the resistances in the internal potential divider to which the comparators connect. In the writer's experience, however, there is a remarkably high degree of consistency between the performance of 555 i.c.'s of different manufacture so far as flip-flop actuation is concerned.

Thus, without VR1 and R1, the circuit can be looked upon as providing what closely approaches a 50:50 square wave. When VR1 and R1 are introduced it becomes possible to obtain a virtually true 50:50 output, because all that is required is to adjust VR1 such that the charge period of C1 is slightly reduced and the discharge period is slightly increased. If the out-

put of the 555 were connected to an accurate oscilloscope, VR1 would merely be adjusted to provide the requisite square wave, this normally being given with the slider of VR1 slightly positive of the mid-supply voltage. For the circuit to operate R1 requires a value which is about 5 times that of R3 or greater.

VR1 may also be set up with the aid of a multimeter having (preferably) a resistance on its voltage ranges of 10,000 ohms per volt or more, and to see how this can be done it is necessary to examine the output circuit of the 555 i.c.

The output circuit is shown, in slightly simplified form, in Fig. 2, where the output transistors are TRB,

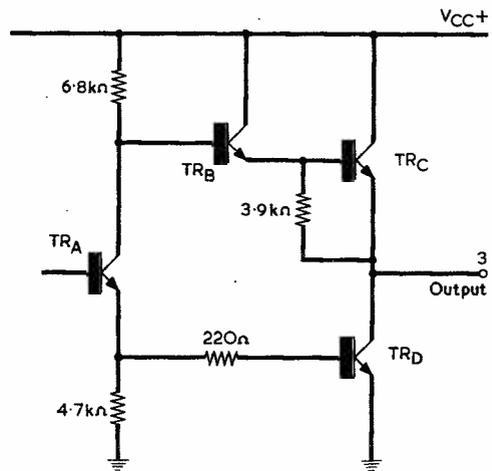


Fig. 2. The internal output stage circuit of the 555 timer i.c.

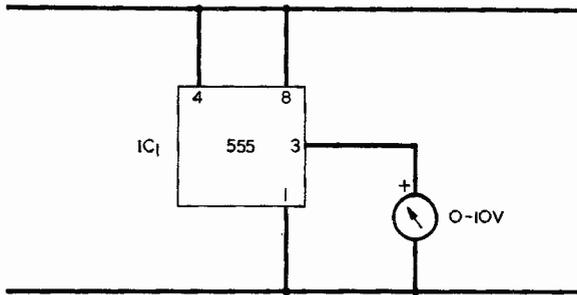


Fig. 3. Connecting a voltmeter to allow VR1 to be set up

TRC and TRD, these being driven by TRA. The earth symbols represent the negative supply rail. TRA is turned off when the output is required to be in the high state, whereupon the Darlington pair given by TRB and TRC receive an input base current via the $6.8k\Omega$ resistor. For low output currents to the negative rail pin 3 then becomes negative of the positive supply rail by the voltage drops in two base-emitter junctions, these adding to a typical value of around 1.2 volts. For the low output condition TRA is turned on, driving a base current through TRD and drawing the base of TRB down to a low level. TRD turns hard on and, for low currents to the positive rail (and working from Signetics data) drops to considerably less than 0.1 volt.

A check for 50:50 square wave operation can therefore be carried out by connecting a voltmeter between pin 3 and the negative rail, measuring the voltage given when the output is high, then adjusting VR1 of Fig. 1 for an output voltage of exactly half that value with the multivibrator running. Assuming

a virtually instantaneous change from the low to the high state and vice-versa, the length in time of alternate half-cycles of the output waveform will then be equal.

SETTING-UP

The setting-up process is illustrated in Fig. 3. The circuit of Fig. 1 is assembled with the exception that no connection is made between pin 3 and the junction of LED1 and R5. A multimeter switched to read 0-10 volts, or a suitable similar range, is connected between pin 3 and the negative rail. VR1 is adjusted to a central setting and S2 is closed. S1 is then pressed one or more times until a high reading is given in the voltmeter. This reading is noted. S1 is then released and VR1 is adjusted for an indication in the voltmeter which is exactly half the previous reading. Because of the relatively slow speed of the multivibrator the meter needle may vibrate slightly on either side of the central reading but this does not prevent an accurate reading being obtained. The circuit is then set up and can be brought into use by removing the multimeter and connecting the l.e.d.'s to the output.

The circuit functions satisfactorily with quite a high internal resistance in the battery and there is no need for a high value electrolytic bypass capacitor across the supply rails. C1 is a plastic foil capacitor, which nowadays infers a polyester dielectric. The two l.e.d.'s are mounted on the front panel of the completed unit in company with S1 and S2, and require panel mounting bushes. The author employed green and red l.e.d.'s Type 4, which are available from Doram Electronics and which have the anode lead (coupling to the positive supply) shorter than the cathode lead. However, any other similar l.e.d.'s may be employed instead.

The current drawn is of the order of 10mA with S1 closed or open, and a 9 volt PP6 battery would be suitable

MOBILE AMATEUR RADIO LOG REQUIREMENTS

One of the most pleasing of the changes which have been introduced into the new amateur radio transmitting licence regulations, now being issued to radio amateurs in this country by the Home Office, is that relating to the keeping of log books recording the activities of mobile amateur radio stations. The detail required in the past has been supplanted by much more reasonable — and practical requirements.

It is also now not necessary to take out a separate licence for mobile work. The new licence covers mobile operation from 'any vehicle or vessel, but not on the sea or within any estuary, dock or harbour'. It also covers mobile operation "as a pedestrian"! It should be noted that it does not permit operation from an aircraft nor may the station be used from a public transport vehicle. When used as a mobile station in the permitted manner, as indicated above, the suffix "/M" shall be added to the call sign.

The keeping of a Log Book, recording the times and other details of transmissions, has always been an accepted requirement of operating an Amateur Radio Station and is welcomed by all reasonably minded radio amateur operators. The requirements

for mobile operation in this connection have, however, been somewhat onerous in the past. Now, however, the new requirements make things much easier and more practical. A separate log book may be maintained for mobile or pedestrian use, distinct from the main station log. "Entries made in respect of calls made when operating from a vehicle or vessel, or as a pedestrian, should be made as soon as practicable after the end of the journey and must consist of date, geographical area of operation, frequency band(s) used and time of commencement and end of journey".

It is interesting to note the inclusion of "Pedestrian mobile operation" along with vehicular mobile operation in the new licence regulations. This has no doubt been done because of the greatly increased popularity of "hand held" miniaturised radio telephony equipment which is now so readily available. It is now commonplace at radio gatherings and meetings, to see portable, miniaturised, amateur radio telephony equipment, slung over the shoulders of those present in the manner and quite as conveniently as the more usually carried camera!

A.C.G.

ANTIQUÉ AND WARTIME RADIO

By Ron Ham

The author is presenting his collection of antique and wartime radio equipment this year from April 1st to October 31st at the Cornwall Aircraft Park at Helston, Cornwall.

Here are some of the items which will be exhibited.

HORN LOUDSPEAKER

The first photograph shows a early receiving installation which comprises an Amplion horn loudspeaker together with a Gecophone "kit" receiver on its right. Just visible on the left is one of the first a.c. mains radios, this being of Philips manufacture. The loudspeaker, with its fancy wooden horn, sold for £5 5s. in 1924.


The second photograph takes us up to the start of World War 2, the set on the left being the aircraft transmitter-receiver type TR9, which was in use with the RAF from around 1938 to the early 1940's. This set, working on short wave frequencies, provided voice communication between aircraft, and between aircraft and ground. The receiver was a t.r.f. design with pre-set regeneration between its r.f. stages and employed the old 4 pin 2 volt filament valves. These were powered by a 2 volt accumulator mounted externally. Inside the housing are two further batteries: a 120 volt high tension battery and a grid bias battery.

To the right is a version of the transmitter-receiver type TR1133 which superseded the TR9. This operated on v.h.f between 100 and 125MHz and the set illustrated has crystal controlled receiver oscillator tuning. The valves are 6.3 volt indirectly heated types and the equipment had 4 pre-tuned channels, selected by a push-button unit in the aircraft cockpit.

TWO "CIVVIES"

The third photograph shows two wartime receivers for which the author has great affection and which have attracted much attention on previous occasions.

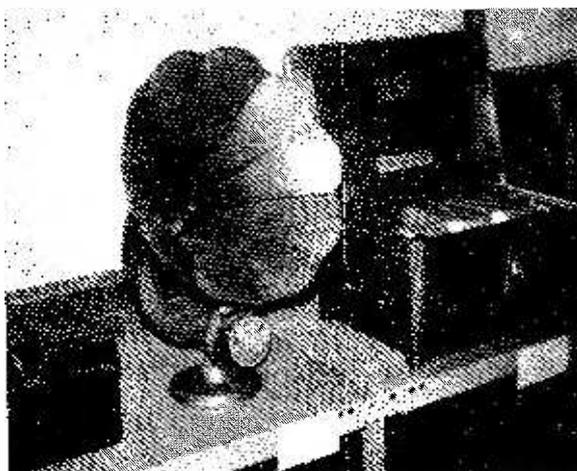The receiver on the left, made in 1943, is the medium-wave-only "WCR" or Wartime Civilian Receiver, and it is still in good voice after all these years. In the author's exhibition held at Worthing Museum last year it pounded out programmes from either BBC Radio 1 or BBC Radio Brighton for 12 hours every weekday throughout the 6 weeks of the exhibition.




In the centre is an Amplion horn loudspeaker of 1924 vintage, this being flanked on its right by a Gecophone "kit" receiver and on its left by an early Philips mains set

What did you get in 1943 for your £12 3s 4d. (including Purchase Tax)? A bare but well made wooden cabinet with the absolute minimum of radio components on the chassis inside. The yellow metal dial (no glass) is inscribed with the words "Home" and "Forces", while underneath are just two knobs for volume and tuning, the on-off toggle switch being mounted on the chassis at the rear of the cabinet. The mixer and i.f. valves are red metallised types, there is a large glass rectifier and an equally large output pentode. Because the set was made in wartime the only identification on the valves is a BVA number. To save both space and power requirements the signal rectifier is a Westector.

The set in the picture spent the latter part of its life in a garden shed, and when the author received it some three years ago he cleaned the chassis and valveholders, oiled the moving parts and used a vacuum cleaner to clean the muck from the

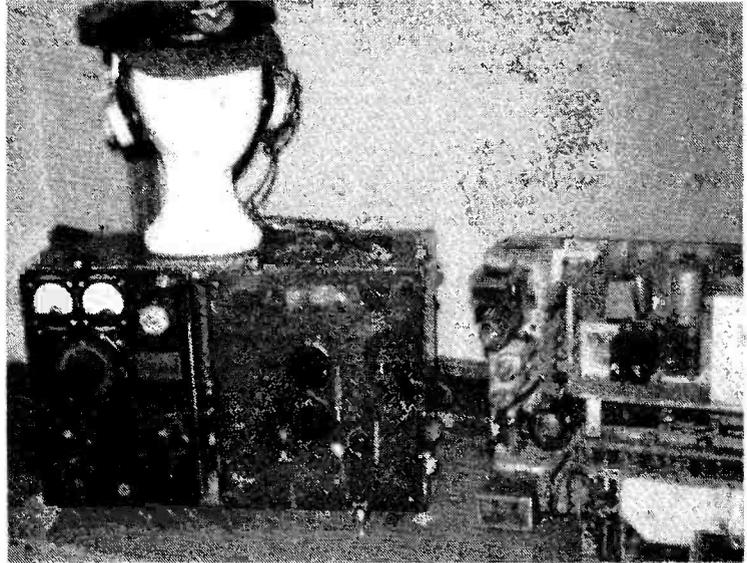The equipment with the two meters at its top left is the TR3 aircraft transmitter-receiver, with which the RAF entered the last war in 1939. To its right is a TR1133 with the cover removed, this being the v.h.f. aircraft transmitter-receiver which replaced the TR3 set.



loudspeaker. A cautious switch-on and the set burst into life, and has been going ever since with all the original parts.

NATIONAL HRO

How many readers looking at the second receiver in the illustration will at once say that it is the "good old HRO"? And how right they will be; many of these sets were used during the war on active service and quite a number are still being employed by amateurs today.


The actual set in the photograph was the property of the late Nell Corry (G2YL) and is not one of the later versions with 6.3 volt valves. Instead, this is one of the originals with the old 2.5 volt Americian UX-based valves.

A full description of the circuit and other details of this early communications receiver appeared in *The Wireless World* for August 18th 1938 (then published weekly at 4d). Its cost, with 4 coil units but less

loudspeaker and power supply unit, was £49.15s.

Any HRO enthusiast will confirm that from the mechanical point of view the HRO is beautifully turned out. The tuning drive and dial are the highlights of the mechanical design; in fact, the effective tuning scale length is about 12 ft.

When Nell gave the author this set, shortly before she died, she warned that it had not been used for 25 years. The author located an old mains transformer made by Rich & Bunday in the mid-thirties which delivered 2.8. volts at 10 amps. Who could not resist coupling together these two old timers? An h.t. supply was soon knocked up and a speaker complete with transformer (the HRO output is at high impedance) connected to the receiver. Imagine the author's pleasure when the 9 valves all lit up, the "S" meter jerked into life and the set was once again receiving short wave signals. Knowing these old sets, the author had expected it to work, and he is delighted to have this particular model in his collection.

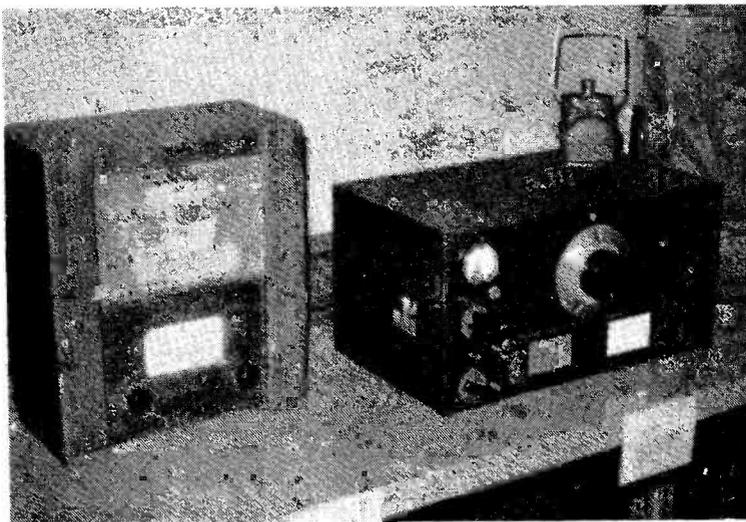

Two "civvy" receivers which played an important part in World War II. In the wooden cabinet is a Wartime Civilian Receiver which functioned on medium waves only. Many readers will recognise the other receiver, a very early version of the famous National HRO.

NOTES FOR NEWCOMERS

SURGE CURRENTS

by R. J. Caborn

It pays to keep an eye open for the possibility of large surge currents when designing new circuits

In the early 1940's the author was engaged in the repair of American communications receivers. One popular model had what appeared at the time to be a somewhat unusual b.f.o. switching circuit. When the receiver b.f.o. was switched on for the reception of Morse signals the automatic gain control bias line was connected by a section of the b.f.o. switching circuit to chassis. If this was not done the b.f.o. signal applied to the detector would cause a small a.g.c. voltage to be produced, thereby reducing receiver sensitivity.

LIMITER RESISTOR

The apparently unusual feature of this b.f.o. switching circuit appears in Fig. 1, where the switch section shown is that which takes the a.g.c. line to chassis. When the b.f.o. was off the a.g.c. voltage appeared across the $0.05\mu\text{F}$ capacitor, and this could rise to some 8 volts or so. Turning on the b.f.o. caused the capacitor to be short-circuited via the 100Ω resistor, whereupon the a.g.c. voltage, relative to chassis, was reduced to zero. It should be added that the receiver was, of course, a valve model in which the resistors in the a.g.c. circuit were of the order of $470\text{k}\Omega$ or more. Compared with these the 100Ω resistor of Fig. 1 was virtually a dead short.

Why, then, had the designer put it in?

The answer is that it was a current surge limiting resistor. If the switch had short-circuited the capacitor directly there would have been a tiny spark at the switch contacts each time they closed, even from a $0.05\mu\text{F}$ capacitor charged to only 8 volts. The resultant damage to the contacts would probably have been quite negligible after hundreds of switch operations, but what would have happened when these went into the thousands, as could easily happen over the years? Wisely, the designer took no chances and made certain that the surge current at the instant of switch closure was always safely limited by the 100Ω resistor. The instantaneous surge current with the resistor in circuit could be of the order of 80mA.

Without it, the instantaneous current as the capacitor discharged could well have been several amps.

Most of us have charged an electrolytic capacitor and then either accidentally or purposely discharged it. If the capacitor has a value of $100\mu\text{F}$ or so and is charged to several hundred volts, the spark at discharge can sound like a pistol shot. Connecting a switch direct across a charged capacitor of this nature and then closing it would lead to the very early demise of the switch.

So, whenever a circuit requires that a capacitor be rapidly discharged by a switch, it is always wise to insert a current limiting resistor in series, as was done in Fig. 1. In general, this requirement applies to capacitors above some $0.02\mu\text{F}$, and it definitely applies to all electrolytic capacitors. For low voltage circuits a current limiting resistor of about 10Ω to 30Ω is usually quite adequate and in most instances a $\frac{1}{4}$ watt component will be satisfactory.

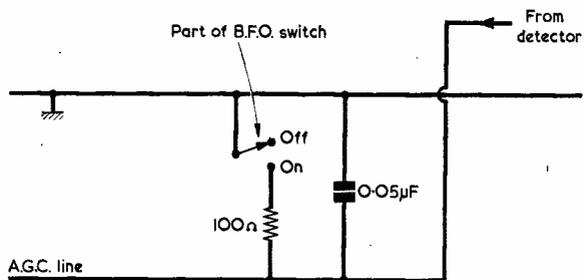


Fig. 1. Part of a b.f.o. switching circuit in a communications receiver. Its main interest lies in the use of a current limiting resistor in the capacitor discharge circuit

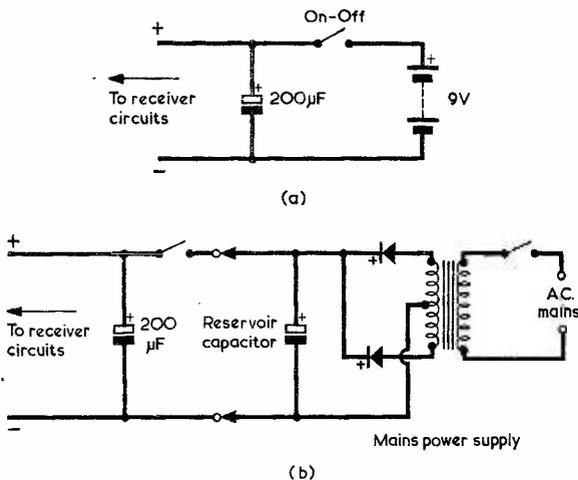


Fig. 2(a). In this common transistor radio circuit the switch-on current surge is mainly limited by the internal resistance of the battery (b). The switch-on surge can be significantly greater if the battery is replaced by a mains power supply.

SWITCH-ON SURGES

There is also a surge current when a voltage is suddenly applied to a discharged capacitor. A very common example is shown in Fig. 2(a) in which a 9 volt battery connects to a transistor radio having a capacitor of, say, $200\mu\text{F}$ across its supply rails. At the instant of switch closure a surge current flows into the discharged capacitor which can be looked upon, at that instant, as being a short-circuit. Fortunately, the magnitude of the current is largely limited by the internal resistance of the battery. With a PP9 battery this is of the order of 10Ω , whereupon the instantaneous surge current at switch-on is a little less than an amp.

The situation changes markedly if the set-owner decides to economise by replacing the battery with a mains power supply, as in Fig. 2(b). If, with this arrangement, the a.c. mains supply is switched on first, a rectified voltage at low impedance is developed across the reservoir capacitor. Turning on the receiver switch can then cause a surge current considerably higher than an amp to flow. Thus, to ensure long life

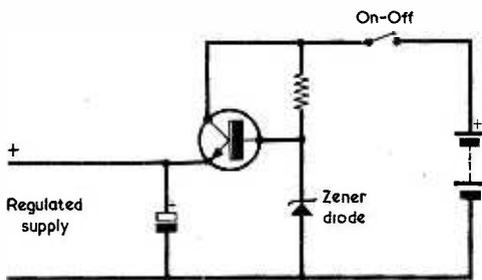


Fig. 3. A popular voltage regulator circuit. At switch-on a surge current flows into the discharged electrolytic capacitor connected to the transistor emitter

of the receiver on-off switch it is always preferable to close the receiver switch before turning on the mains supply.

Another circuit in which an initial high current surge can flow at switch-on is given by the emitter follower voltage regulator of Fig. 3. At the instant of closing the on-off switch the transistor is turned fully on, and the surge current flowing into the discharged electrolytic capacitor is largely limited by the battery internal resistance only. For applications like this it is a good policy to choose a transistor which is capable of passing a peak collector current of an amp, even if the running current drawn from the emitter in normal use is only in the region of, say, 20mA. A good candidate here is the BFY50 which, although it is in a small TO-5 can, has a peak collector current rating of 1,000mA. If a transistor having a maximum collector current rating of the order of 100mA were employed, it is quite possible that it may mysteriously expire one day when the on-off switch is closed.

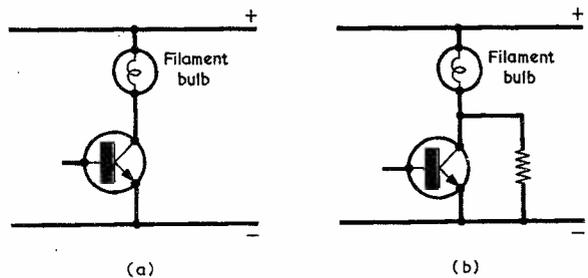


Fig. 4(a). A simple circuit in which a transistor is used to turn on a filament bulb (b). Adding a resistor, as described in the text, can reduce the initial switch-on current surge in the bulb

FILAMENT LAMPS

Apart from capacitors, another cause of heavy current surges is given by filament lamps. It does not always seem to be remembered that the cold resistance of a filament lamp can be lower than one-tenth of its hot resistance, whereupon switch-on surge currents can be surprisingly high. It is, indeed, a salutary exercise to check the cold resistance of several lamps with the aid of an ohmmeter. A 240 volt 100 watt domestic light bulb consumes some 0.4 amp when it is switched on and has a hot resistance of about 570Ω . The cold resistance of such a bulb is, typically, only 40Ω !

Turning to smaller lamps, a 2.5 volt 0.3 amp flash-lamp bulb will have a hot resistance, at 2.5 volts, of about 8Ω . Its cold resistance will normally be lower than 1Ω .

The fact that filament lamps have such relatively low cold resistance values should always be borne in mind when these are switched on by transistors, as occurs in Fig. 4(a). A useful dodge here is to add a resistor across the transistor, as in Fig. 4(b). When the transistor is turned off, the resistor allows a current to flow which causes the bulb filament to be just below the visible glow level. The bulb resistance is then well above its cold value, and less initial surge current flows in the transistor when it turns on and causes the bulb to light up at full brightness. ■

CATALOGUE

MAPLIN ELECTRONIC SUPPLIES

The new 1977-78 Maplin Electronic Supplies Catalogue has now been published and is readily available to readers who mail the coupon on the back page of this issue.

Considerably bigger than the previous Maplin Catalogue the present edition has no less than 216 large pages measuring 11 $\frac{1}{4}$ by 8in. with over 1,000 photographs and drawings. Over 30 pages give full details of constructional projects, and a considerable amount of useful information is provided with individual components including in particular linear integrated circuits.

The exceptionally wide range of items listed includes test gear, electronic organ components, TV game i.c.'s, disco effects, technical

books, coils, transformers, cases, tools and a full and comprehensive selection of resistors, capacitors and discrete and integrated semiconductor devices. All products are identified by order codes or descriptions and type numbers, and a full index allows items to be located in the Catalogue with the minimum of delay.

Full information on ordering, postage and VAT is given in an early page in the Catalogue, with corresponding notes in French, German and Italian for overseas clients. The new Maplin Catalogue has been carefully prepared and is very well presented, and should be of considerable value to anyone interested in electronics.

TRADE NOTES

LEADLESS CHECKER


The first of the two accompanying photographs illustrates an intriguing item of test equipment which has just been introduced in the United States. Referred to as a Leadless Continuity Checker it is marketed by Transonics Electronic Distributors, 9305 N.E. 11th Street, Vancouver, Washington 98664.

The interesting feature of the Leadless Continuity Checker is that it requires no return lead. The return circuit is made via the body of the person using the device. In the photograph, for instance, the person tracing through the multi-core cable simply puts the finger of one hand on the lead to be traced. The checker is then held in the other hand and its tip


is applied to the leads at the opposite end of the cable in turn. When the correct lead has been located an l.e.d. built into the checker lights up.

The checker is also capable of testing capacitors and diodes. One lead-out of the component is held in one hand and the checker in the other; with diodes, both serviceability and polarity may be determined. Other functions associated with a continuity tester can also be carried out.

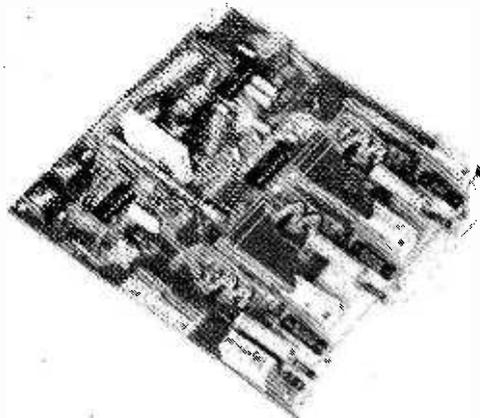Since no return wire is required the checker may be conveniently clipped into a pocket like a pen. The voltage at the tip of the checker in the stand-by mode is 0.5 volt and maximum testing current is 11 μ A.



PAL DECODER

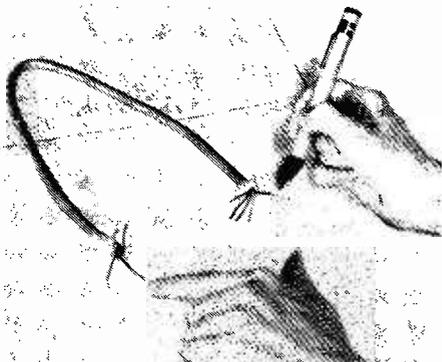

In the second photograph can be seen an assembled PAL decoder card, for colour television receivers, incorporating three new integrated circuits introduced by SGS-ATES. It is stated that these incorporate the highest degree of integration possible within 16 lead d.i.l. packages for the decoder application, and that the external component requirement is reduced by 10 to 20% compared with existing assemblies, thereby giving increased reliability and savings in space and cost.


The i.c.'s concerned are type numbers TDA2140, TDA2150 and

TDA2160, and further advantages conferred are low spread of brightness, contrast and saturation controls with a consequent avoidance of pre-setting, a wide range of output black level adjustment, compensation for chroma delay line attenuation by an a.c.c. loop, high noise immunity, and the provision of a composite blanking and burst key pulse generator together with an independent video signal output for a sync generator.

Further information on the three i.c.'s and the associated circuitry is available from SGS-ATES (United Kingdom) Ltd., Walton Street, Aylesbury, Bucks.

SHORT WAVE NEWS

FOR DX LISTENERS

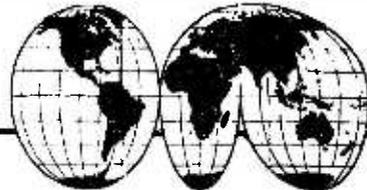

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

We commence this month with some news of two clandestine transmissions and some schedules of programmes designed for local consumption in the Domestic Services of the countries concerned which may be heard here in the U.K.

● CLANDESTINE

The "Voice of Arab Syria" reportedly operates on **9510** from 0800 to 0900 in Arabic. The programmes are, of course, anti-government and critical of the present Syrian Regime.

The "Voice of the Communist Party of Turkey" now radiates anti-Turkish government programmes on **6200** daily from 0810 to 0840 (Sundays to 0900).

● DOMESTIC SERVICES

"Radio Pakistan", Karachi, has a Domestic Service which is best heard here in the U.K. from around 1500 through to 1810 on **3890** and **4735**. Programmes from Rawalpindi may be logged from around 1500 to 1800 on **4060** and from Islamabad from 1630 to 1810 on **3330** and on **4785**. All this information accords with their published schedule but past experience has taught that the actual frequencies used quite often differ from those announced or published.

There is also a Regional Network in which programmes in various local languages and English are taken from the above network and radiated from Quetta on **3240**, **3270**, **3990** and **5980** and from Peshwar on **3155** and on **6080**.

● IRAN

"Radio Iran" with its First Programme may be logged throughout the entire 24-hour period on various channels but that period from 1630 to 2030 is probably convenient for most listeners. The frequencies are **8215**, **11930** and **15085**, the language of course being Persian (Farsi).

CURRENT SCHEDULES

The frequencies and times quoted here are correct at the time of writing but either can be subject to change at short notice.

● HUNGARY

"Radio Budapest" broadcasts to Europe in English from 1200 to 1240 (Monday to Friday inclusive only) on **6150**, **7155**, **9585**, **11910**, **15160** and on **17785**; from 1515 to 1530 (Tuesdays and Fridays only) a Dx programme on **6110**, **7200**, **7215**, **9585**, **11910** and on **15160**; from 2130 to 2200 on **5965**, **7150**, **7200**, **9655**, **11910** and on **15415**.

● BANGLADESH

"Radio Bangladesh", Dacca, presents an External Service in English to Europe from 1230 to 1300 on **11900** and **15270**; from 1815 to 1915 on **11890** and **15410**.

● GREECE

"Voice of Greece", Athens, produces a daily newscast in English from 1920 to 1930 on **6140**, **7215** and on **9675**.

● NETHERLANDS

"Radio Nederland Wereldomroep", Hilversum, operates in English to Europe as follows — from 0930 to 1050 on **5955**, **6045**, **7240** and **9660**; from 1400 to 1520 on **5955**, **6045**, **11740** (Madagascar transmitter), **15120**, **15185** and **17810**; from 1830 to 1950 on **6020**, **11730** and on **15375**; from 2000 to 2120 to West Europe from the Madagascar relay on **11730**.

● ROMANIA

"Radio Bucharest" schedule lists the following programmes for Europe. From 1300 to 1330 on **9690**, **11940** and **15250**; from 1930 to 2030 on **6150** and **7195**; from 2100 to 2130 on **5990** and **7225**.

● BULGARIA

"Radio Sofia" has an External Service in English to the U.K. and Eire from 1930 to 2000 on **6070** and **9700** also from 2130 to 2200 on **9700**.

● ALBANIA

"Radio Tirana" is in English to Europe from 0630 to 0700 on **7065** and **9500**; from 1630 to 1700 on **7065**, **9480** and on **11985**; from 1830 to 1900 on **7065** and **9480**; from 2030 to 2100 and from 2200 to 2230 also on the latter two channels.

● CZECHOSLOVAKIA

"Radio Prague" features programmes in English to the U.K. and Eire from 1900 to 1930 on **5930**, **7245** and on **7345**; from 2000 to 2030 on **5930** and **7345** and from 2130 to 2200 on **6055**.

The Radio Prague Inter-Programme for Europe in English may be heard on **6055** and **9505** from 0745 to 0800; 0845 to 0900; 0945 to 1000; 1045 to 1100 and from 1145 to 1200 the programme consisting of a feature, news bulletin or news summary.

● TAIWAN

The "Voice of Free China", Taipei, directs a programme in English to Africa, the Middle East and Europe from 2130 to 2230 on **9510**, **9600**, **11860**, **15225** and on **17720**.

● PAKISTAN

"Radio Pakistan", Karachi, has an External Service in which programmes in English are radiated to Europe as follows — from 1100 to 1115 (a newscast read at slow speed) on **15110** and **17665**; from 1815 to 1820 (newscast) on **6110** and **7085** and from 2115 to 2145 (newscast and feature) on **6210** and **7085**.

The World Service directed to the U.K. is as follows — from 0830 to 1100 in Urdu on **15110** and **17665**; from 1915 to 2045 in Urdu, from 2045 to 2115 in Sylheti on **6210** and on **7085**.

● POLAND

"Radio Warsaw" produces programmes in English for Europe from 0630 to 0700 on **6135, 7270** and **9675**; from 1200 to 1230 on **6095** and **7285**; from 1600 to 1630 on **6135** and **9540**; from 1830 to 1900 on **6095** and **7285**; from 2030 to 2100 on **6095** and **7285** and from 2230 to 2300 on **3955, 5995, 6135, 7125** and on **7270**.

AROUND THE DIAL

● CHINA

Radio Peking on **6645** at 1404, OM and YL in Kazakh in the Domestic Service with a programme for minority groups, scheduled from 1400 to 1455.

Radio Peking on **6790** at 1357, YL in Standard Chinese to Taiwan scheduled from 0830 to 1903 and from 2000 to 0129 on this channel.

Urumchi on **4970** at 1441, YL in Kazakh in the Domestic Service.

PLA Fukien on **4380** at 1551, YL in Chinese to Taiwan and other offshore islands, scheduled on this frequency from 0230 to 1900.

Radio Peking on **6540** at 1933, OM in Italian in a programme directed to Somalia, scheduled from 1930 to 2000 at this point on the dial.

Radio Peking on **7620** at 1935, OM with a newscast in English directed to North and West Africa, scheduled from 1930 to 2030 (the programme — not a one hour news reading!).

Radio Peking on **7385** at 1400 when signing-off with "East is Red", followed by the Tamil programme directed to South Asia, scheduled from 1400 to 1430.

Wulumqi on **4110** at 1610, OM's in chorus, mandolin-type instrumental music in the Uigher Service.

Wuhan on **3940** at 1525, classical Chinese music, YL announcer.

Radio Peking on **6860** at 2025, signing-off with "Internationale" after the programme in Esperanto, scheduled Fridays and Saturdays from 2000 to 2030.

Wulumqi on **4220** at 1615, OM in Mongolian in the Home Service.

Wulumqi on **4500** at 1620, YL with aria in Chinese opera.

Radio Peking on **2460** at 1542, Chinese orchestral music, YL announcer.

● TURKEY

Ankara on **11880** at 1350, local music and songs in a programme for Turks abroad, scheduled from 0400 to 1330 and from 1630 to 2100 on this channel.

INDONESIA

RRI Palembang on **4855** at 1450, YL with songs in local-style, OM announcer, orchestral music.

● PAKISTAN

Radio Pakistan, Karachi on, **7280** at 1328, interval signal, identification and programme in vernacular.

Islamabad on **3330** at 0140, YL with song in the Home Service then local-style music programme.

Karachi on **7085** at 2145, signing-off with choral National Anthem after announcements in English.

Karachi on **3390** at 1555, OM with songs in Urdu, local-style music. Quetta on **3240** at 1511, YL with song in Urdu, orchestral music, OM announcer.

● BURMA

Rangoon on **4725** at 1410, YL in Burmese, local pop records. Suddenly off without National Anthem at 1415.

● KHMER REPUBLIC

Phnom-Penh on a measured **4908** at 1429, YL in Khmer (Cambodian), songs and music in the distinctive local style.

● CAMEROON

Garoua on **5010** at 1832, OM with the world news in English. Also at 2200 when signing-off with National Anthem and interval singing after epilogue in Arabic.

● NIGERIA

Lagos on **4900** at 2000, interval signal (talking drum), 6 pips, identification and the news in English. They have been logged on this channel since early December.

● BRAZIL-1

Radio Ribra Preto on **3205** at 0535, OM in Portuguese, local songs and music despite the schedule (should close at 0400). Still there as late as 0610 fade-out.

Radio Clube do Para on **4855** at 2218, OM with a sports commentary in Portuguese.

Radio Timbira on **4976** at 2126, OM in Portuguese, ads, jingles and identification.

Radio Poti on **4964** at 2135, OM's with a discussion in Portuguese.

Emisora Rual on **4948** at 2213, YL with song in Portuguese, OM with a talk at 2215.

Radio Dif, Sao Paulo on **6095** at 0120, OM with an excited commentary in Portuguese.

● VENEZUELA

Radio Occidente, Tovar, on **3225** at 2353, Latin American music in typical local style, OM announcer. The schedule of this one is from 1030 to 0300 and the power is 1kW.

Radio Valera, Valera on **4840** at 0216, OM in Spanish with a long talk about Venezuelan commercial and political affairs.

Radio Sucre, Cumana, on a measured **4959** at 0225, OM with a political talk in Spanish followed by identification and local-style dance music. The schedule is from 1000 to 0400 and the power is 1kW.

Radio Libertador, Caracas, on **3245** at 0131, OM with identification in Spanish followed by a political talk about the Presidency. The schedule of this one is from 1000 to 0400 and the power is 1kW. Reportedly there is a newscast in English from 2200 to 2230 which the writer has never yet succeeded in logging — but hope springs eternal!

Radio Monogas, Maturin, on **3325** at 0136, oddly enough in parallel with Radio Libertador on **3245** together with other Venezuelan stations on the 60 metre band.

● BRAZIL — 2

Radio Nacional, Brasilia, on **11780** at 2059, which I must confess is a more reasonable hour to listen to South America, with the bell-chime interval signal, identification by OM and the English programme commencing with a newscast mainly composed of items about the Brazilian domestic scene.

● ECUADOR

Radio Quito, Quito, on **4920** at 0325, OM with a local newscast in Spanish with many mentions of Quito.

NOW HEAR THIS


● PAPUA NEW GUINEA

NBC Boroko on **4890** at 2000, National Anthem, OM in Pidgin with a newscast till 2010 then signal lost under interference.

MEDIUM AND LONG WAVE SUPERHET

by A. P. Roberts

Part 2

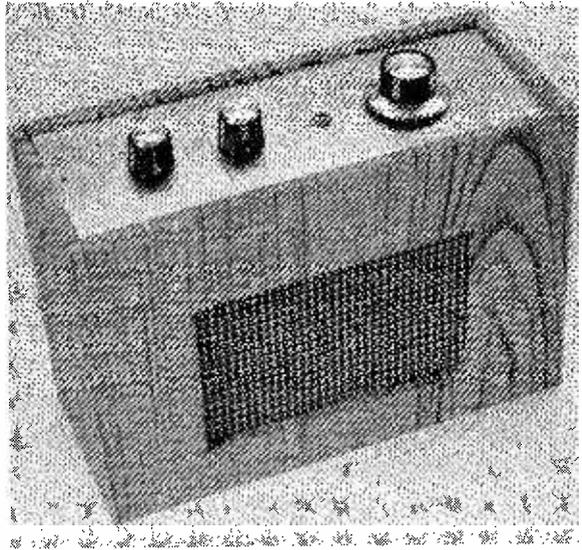

In this concluding article the assembly of the component panel is described, after which details are given of final wiring and alignment.

COMPONENT PANEL

All the components and the ferrite aerial are mounted and wired up on a plain s.r.b.p. ("Paxolin") panel having the dimensions shown in Fig. 4. This diagram is reproduced full size and may be traced, if desired.

First, the panel is cut out to the desired size by means of a hacksaw, after which the two 6BA clear holes and the holes for component wires are drilled out. A small diameter drill is used for the component wire holes. Since it is possible that the constructor will not obtain a trimmer having precisely the same dimensions as that used by the author, the two holes for TC3 should be marked out with the aid of the actual component to be used. This should be a trimmer having a tag at each end of its body rather than two tags at one end. For greatest accuracy, the constructor is also advised to mark out the holes for the tags and mounting lugs of the oscillator coil and the two i.f. transformers with the aid of the components themselves. The same comment applies to TR2 and TR3. These two transistors have lock-fit pins instead

of wire lead-outs, and the pins pass through the holes in the panel which are drilled for them.

The components are mounted on the panel and their lead-outs bent flat against its underside. The oscillator coil and i.f. transformers are held in position by bending their mounting lugs outward against the underside of the board. A similar procedure is adopted with the pins of IC1 and the tags of TC3. The ferrite aerial is secured to the panel by two lengths of single strand p.v.c. insulated wire. These are looped over the ferrite rod, taken through the appropriate holes in the panel, and then each set of wire ends is twisted tightly together so as to firmly secure the rod to the panel. Note that only the insulated wires should be twisted together. If the bare wire itself is twisted together it will constitute a shorted turn which will prevent the ferrite aerial from functioning properly.

When all the components have been mounted, the lead-out wires are cut to length where necessary and soldered together, as shown in Fig. 4. Tinned copper wire of around 22 s.w.g. is employed where lead extensions are required or to bridge wiring gaps. Note that part of the negative supply rail circuit is completed via the mounting lugs of the oscillator coil.

FURTHER WIRING

The component panel is secured to the front panel by means of a bracket having the dimensions shown


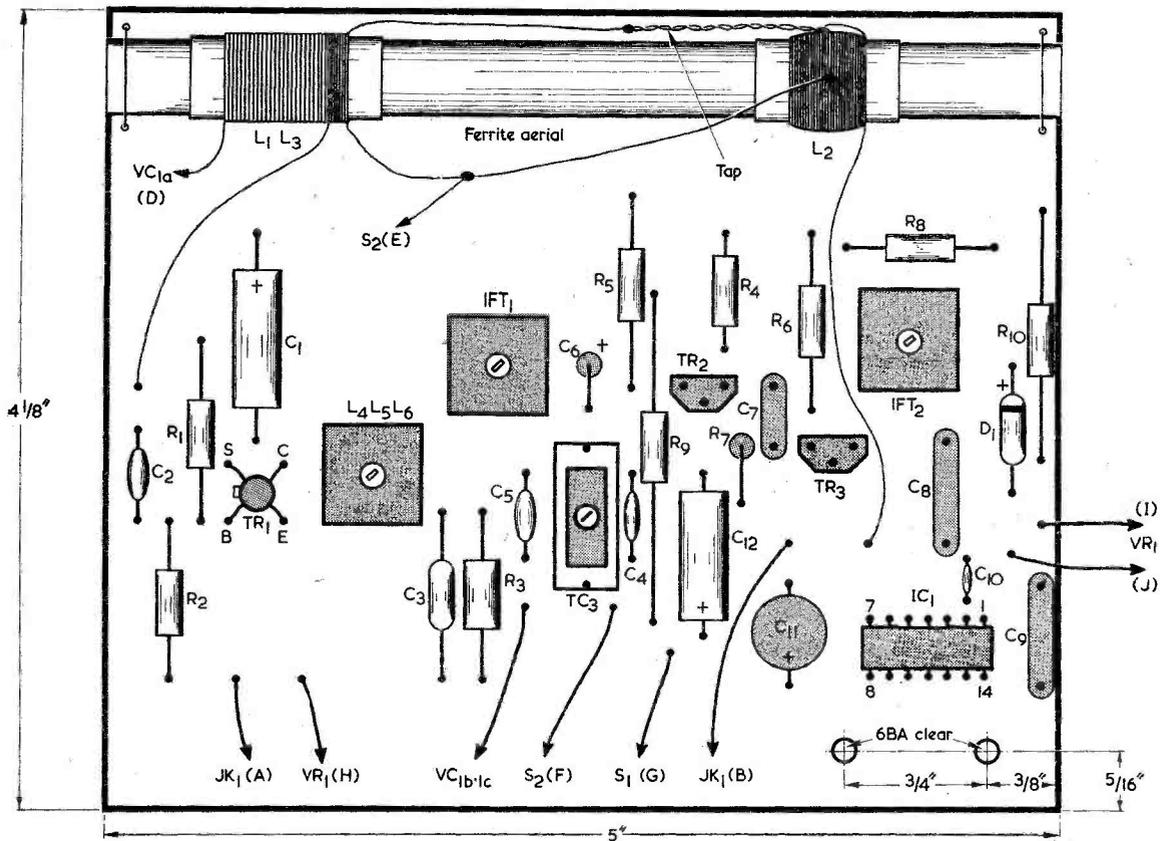


Fig. 4. The component and wiring sides of the component panel. This is assembled on a piece of plain s.r.b.p. board, and is reproduced full size

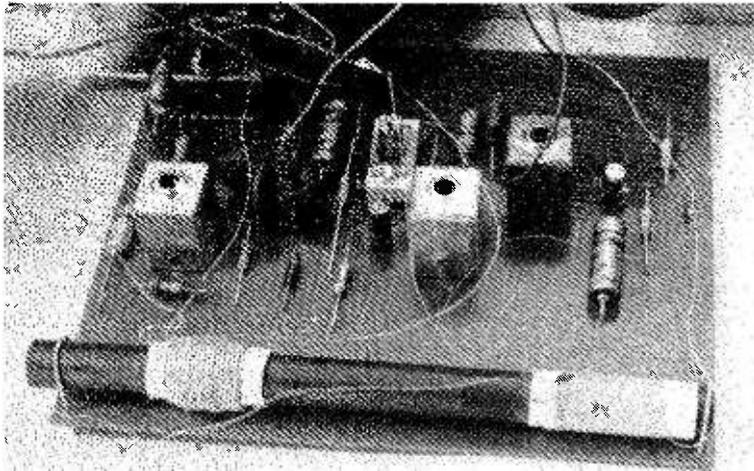

A close look at the component panel

in Fig. 5. This is secured to the front panel under the mounting bushes of VR1 and S2. The bracket is made of 18 s.w.g. aluminium. Should it be necessary for the 3in. dimension of the front panel to be increased, the 1½in. dimensions of the bracket should also be increased by the requisite amount.

All the remaining wiring of the receiver is shown in Fig. 6. P.V.C. insulated wire is employed to couple the front panel and component panel sections together, and this should be kept reasonably neat and short. However, the leads to the speaker should be flexible and about 10 to 12in. long. Switch S2 is any single pole 2 way rotary switch. That employed in the

prototype and visible in the photographs was a 4 pole switch with no connections made to three of the poles.

It should be possible to trace out the ferrite aerial connections from Figs. 4 and 6. If any doubt exists this can be dispelled by referring back to the circuit diagram of Fig. 1. The tap in L2 is electrically nearer the earthy end of the coil, which connects to the negative supply rail. If an ohmmeter is available, the resistance between the tap and the earthy end of the coil will be found much lower than the resistance between the tap and the non-earthly end.

The quiescent current consumption of the set is about 7mA, but it rises to many times this value when the receiver is used at high volume levels. In the interest of good battery economy it is necessary to use a fairly high capacity 9 volt battery such as a PP6, PP7 or six HP7 cells in a suitable holder. There is plenty of space for the battery under S2, and a simple bracket can be made up to hold it in place.

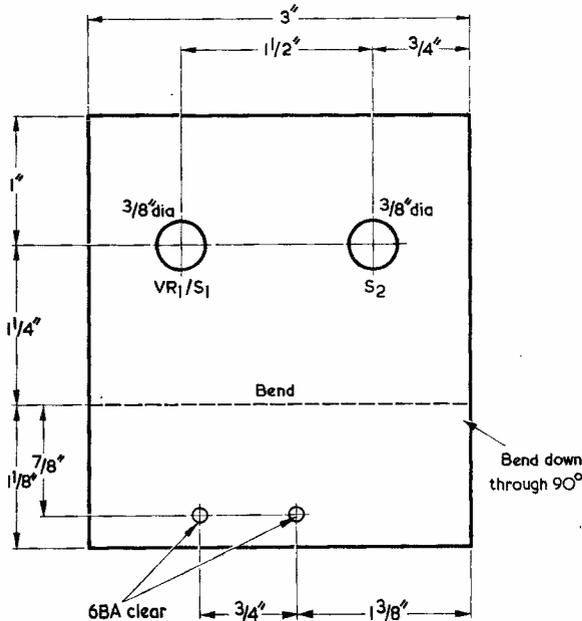


Fig. 5. The bracket which secures the component panel at the rear of the case

ALIGNMENT

The i.f. and mixer-oscillator circuits have to be aligned before the front panel and component panel assembly can be fitted in the case. Alignment commences with the i.f. stages.

Upon initially switching on it should be possible to tune in one or two stations with S2 in the medium wave position. The medium wave aerial coil can be moved along the ferrite rod to peak one of the transmissions. If a multimeter having a sensitivity of 10,000 Ω. per volt or more on its voltage ranges is available, this can be connected across VR1 with the positive test lead connecting to the negative supply rail. It should be switched to read voltages of the order of several volts. The receiver is then carefully tuned to a station and the i.f. transformer cores adjusted for a maximum voltage reading.

In the absence of a meter the receiver may be tuned to a fairly weak station and the i.f. transformer cores adjusted for maximum volume. A strong signal cannot be used in this case because of receiver a.g.c. action.

The i.f. transformers are pre-aligned at the factory and very little adjustment of the cores should be required. Obviously, the cores must not be tampered with prior to the process of alignment. The cores


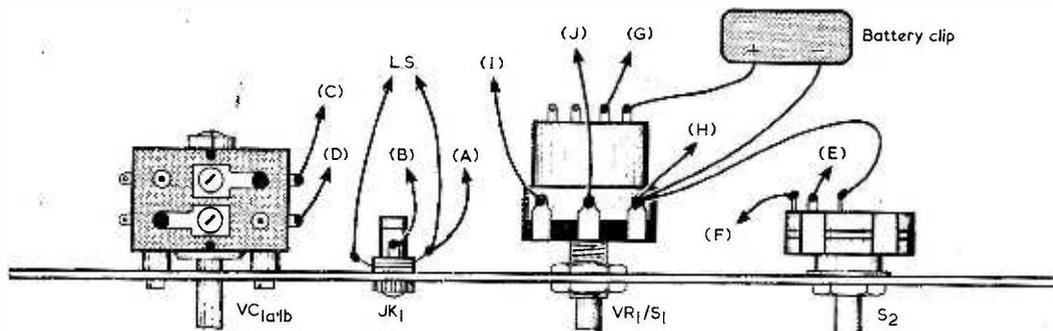


Fig. 6. The wiring to the components on the front panel. Not shown here is the bracket of Fig. 5. This is mounted behind the front panel on the bushes of VR1/S1 and S2

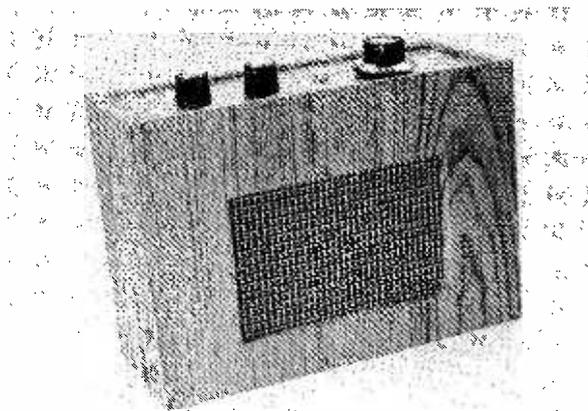A further view of the completed receiver. The larger control knob is that for the tuning capacitor



should be adjusted with a proper trimming tool, such as the Denco type TT5. An ordinary screwdriver could damage them.

Trimmer TC2 is adjusted to give the set the correct frequency coverage. If no suitable r.f. signal generator is to hand it is probably best to wait until after dark when Radio Luxembourg on 208 metres can be received. TC2 is adjusted so that this station is received with the tuning capacitor close to its minimum capacitance setting.

If the multimeter is available and is connected across VR1, tune to a consistently strong signal at the high frequency end of the band (the same end as Radio Luxembourg) and adjust TC1 for maximum voltage. Tune to a similarly strong signal at the low frequency end of the band (tuning capacitor vanes nearly fully enmeshed) and move the medium wave coil along the ferrite rod for maximum signal strength. Retune to the high frequency end and re-adjust TC1, then return to the low frequency end and re-adjust the position of the medium wave coil on the ferrite rod. Repeat the procedure until no further improvement can be obtained.


If no meter is available, these adjustments may be made for maximum volume, choosing weak transmissions instead of strong ones.

Carefully tape the medium wave coil to the ferrite rod so that it cannot be accidentally moved from its correct setting.

Put S2 to the long wave position, and set the tuning capacitor to about the centre of its range. Adjust TC3 to accurately tune in Radio 2 on 1,500 metres. Finally, slide the long wave coil along the rod for best reception and then tape it in place. Alignment is now complete and the front panel and component panel assembly can be fitted in the receiver case.

The procedure just described involves no adjustment of the oscillator coil core, which should be correctly set at the factory. If desired, the low frequency end of the medium wave range may be altered by adjusting the oscillator coil core, but this will then necessitate repeating the entire mixer-oscillator alignment process. In general, it is best to leave the oscillator coil core undisturbed, this being particularly the case when an r.f. signal generator is not available.

In your workshop

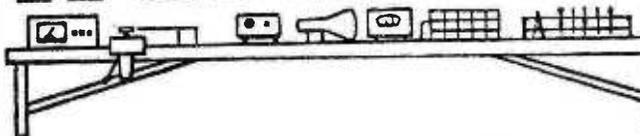

This month Smithy's assistant, Dick, sets out on the repair of a television receiver with a fault in the frame sync section. In the process he is given valuable, albeit somewhat disturbing, assistance by the Serviceman himself.

Whistling contentedly, Dick picked up the only set left on the "For Repair" rack, a 14 inch 625 line black and white television receiver, and carried it over to his side of the Workshop. He plugged it into one of the row of assorted mains sockets at the back of his bench, connected the u.h.f. aerial and switched on. At once the sound channel of one of the local transmitters became audible from the speaker of the set.

As he waited for the picture tube to warm up he glanced cheerfully out of the window. Outside, the warm glow of an April sun permeated the late afternoon sky. It was patent that God was in His heaven and, for the time being at any rate, all was well with Dick's particular world.

FRAME FAULT

The screen of the receiver lit up to reveal a bright and well contrasted picture which was out of vertical synchronisation. Humming to himself, Dick gazed for a moment at the frames as they rolled downwards, then he turned the set partly round, located the vertical hold control and adjusted it experimentally. He found a critical setting at which the picture remained steady momentarily then he took his hand away from the control.

The frames started to roll upwards. "Well," came Smithy's voice at Dick's ear, "you've picked yourself a nice easy one this time."

Dick jumped.

"Dash it all, Smithy," he snorted. "I do wish you wouldn't keep creeping up on me like that. It's nothing short of shattering to suddenly have a disem-

bodied voice blast into your lug-hole unannounced."

"I was talking," retorted Smithy, ruffled, "in my normal voice. It's a fine thing I must say if two people in the same working place can't speak to each other every now and again."

"Yes, but you don't just speak to people," stated Dick heatedly. "You sidle up to them first."

"I do not sidle," replied Smithy indignantly. "I've never sidled in my life."

"You're always sidling," accused Dick. "Stap me, you sidled just now. Anyway, I've forgotten what it was you said."

Smithy made a brave attempt to dissipate his irritation.

"What I said," he grated, "was that you've picked a nice easy fault."

"You mean this set?"

"I do."

"How is it easy then?"

"Well, just look at it. You've got an excellent picture with a steady line lock. All that's wrong with it is that there's a loss of frame sync at or after the sync separator. You couldn't have it much simpler."

"Simple you call it? Blimey, the fault could be anywhere. What about the frame timebase?"

"The frame timebase is almost certainly all right," pronounced Smithy. "Not only were you able to take the frame hold control to correct frame frequency, but you could also adjust it on either side of that frequency. When you had the frames rolling downwards the timebase was running above frame frequency and when they rolled up it was running below frame frequency.

So the frame timebase is working just as it should do, and its hold control has a good wide range of adjustment. All that the timebase needs is a spot of sync."

"Perhaps you're right," admitted Dick grudgingly. "If there are no sync pulses getting to the frame timebase then it has no reference frequency to follow."

"That would be a true presentation of the facts if we were talking about a horizontal flywheel sync circuit," Smithy corrected him, "but the situation is different with a frame timebase. Don't forget that in a conventional frame timebase the frame hold control actually varies the length of the scan section of the timebase waveform, the short flyback section being the same length whatever the length of the scan section. You then adjust the frame hold control so that, without sync pulses, the timebase would run slightly below frame frequency. This corresponds to the scan section of the waveform being a little too long. The sync pulses trigger the timebase into flyback, so that the timebase then runs at sync pulse frequency."

"Fair enough," said Dick. "Well, I might as well get the service manual out for this set."

"There's no need," stated Smithy. "I've got it here."

SERVICE MANUAL

Smithy placed the manual in front of his astonished assistant, then opened it at the circuit diagram of the receiver.

"Hell's teeth," gasped Dick. "Have you got second sight or something?"

First of all you almost completely diagnose what's wrong with this set, and then you produce its service manual out of thin air. I don't get it."

"All that's happened," explained Smithy patiently, "is that I finished my last job for the day just as you were picking up that TV. So I thought I'd do the TV with you, whereupon I first got its service manual out of the filing cabinet. Okay?"

"Yes, I suppose so," grunted Dick reluctantly. "But it seems to me that there's no end of sidling and pussyfooting going on this afternoon."

"Now just stop that," snarled Smithy. "I'm getting more than a bit fed up with your comments about my movements. Let's have a look at this circuit."

"All right then," said Dick, switching off the television receiver and turning his attention to the diagram. "Where's a good place to start?"

"At the vision detector," replied Smithy promptly, as he pointed to the appropriate section of the circuit. "Seeing that we've got a case of missing sync pulses it will be a good plan to trace through from the vision detector,

keeping in mind the sync pulse polarity at the subsequent circuit points." (Fig. 1.)

"Well," said Dick, "for a start the 625 lines signal has negative modulation with sync pulse tips corresponding to maximum signal amplitude. The vision detector diode is connected so that it passes negative half-cycles, and so the sync pulses in the detected signal will be negative going."

"Very good," remarked Smithy, pleased. "Now, the signal at this stage splits into two directions. In one direction it goes off to the 6MHz intercarrier sound amplifier and in the other it goes to a video amplifier transistor. The intercarrier amplifier won't have any effect on frame sync pulses and so we carry on to the video amplifier transistor."

"The signal splits up in two directions there, too," remarked Dick, his finger tracing out the circuit lines in the diagram. "One direction is from the transistor emitter and the other is from the transistor collector."

"Right," confirmed Smithy. "The signal from the emitter goes to the video output transistor, which then couples to the cathode of the picture

tube. Unless we have a really way-out fault we can next eliminate that part of the receiver as well. As a matter of passing interest, you'll see that there's a 6MHz acceptor tuned circuit coupled to the emitter. This is a 6MHz trap, and it prevents the 6MHz intercarrier signal getting to the video output stage."

"The signal we want is from the video amplifier collector," said Dick excitedly. "Look, it couples direct to the sync separator transistor."

"And so it does" agreed Smithy. "Now, the signal going to the video amplifier base had negative going sync pulses. The signal at the collector will be inverted and so it will have positive going sync pulses."

"How does that sync separator work, Smithy?"

"It just amplifies the most positive part of the signal," said Smithy. "If you forget that series 1kΩ resistor in its base circuit for the time being, the 0.22μF coupling capacitor charges up such that the base-emitter junction of the sync separator is fully conductive when the sync pulse tips are present. The signal amplitude is quite high at this point of the circuit, and so the

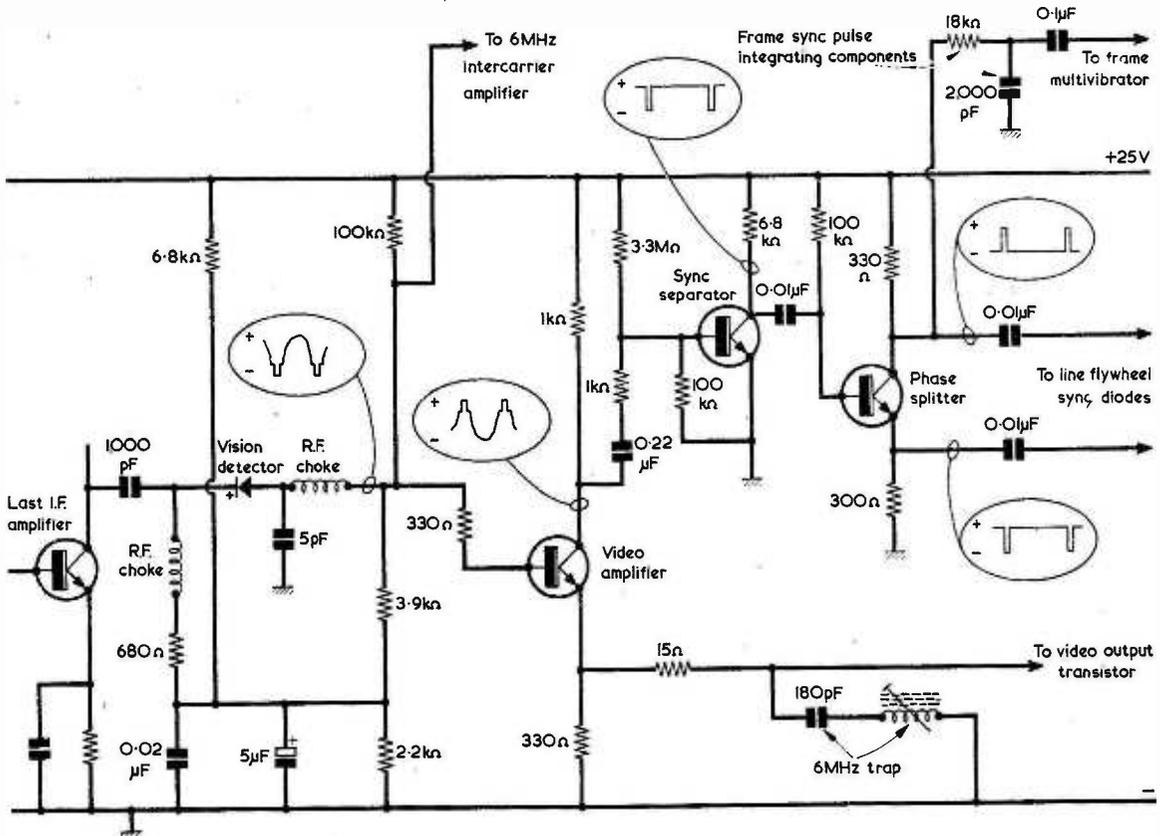


Fig. 1. The stages between the vision detector and the phase splitter transistor in the monochrome 625 line television receiver serviced by Dick and Smithy

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP
Tel: 01-723 4185/2926

ESSEX

GLASS FIBRE P.C.B.'s

From your own tape, films or in master. Send S.A.E. for quotation.

RADIO ELECTRONICS AND CONSTRUCTOR P.C.B.'s

Send S.A.E. for details.

Dept. RE

PROTO DESIGN

4 Highcliffe Way,

Wickford,

Essex, SS11 8LA.

SUSSEX

JEFFRIES

For
Hi-Fi Equipment
Tape Recorders
Television
Transistor Radios

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs
Transfers

Also a postal service

PEATS
the world of electronics
25 Parnell Street, Dublin 1. Telephone 749972

sync separator transistor is simply cut off by the signal between pulses." (Fig. 2.)

"Then," said Dick slowly, "the sync separator only passes collector current when the sync pulses are present."

"That's right," agreed Smithy. "All you get at its collector are pulses which appear at the same time as the pulses applied to its base. These must, of course, be negative going."

FLYWHEEL SYNC

"You said to ignore that 1k Ω series resistor just now," said Dick. "What does it do?"

"Not a great deal," admitted Smithy. "In company with the 0.22 μ F capacitor it offers a time constant which enables the sync separator to handle the signal at its base more readily. Also, it limits peak charging current in the capacitor. Now, let's see where those negative going sync pulses at the sync separator collector go. In this particular receiver they are passed to a phase splitter stage whose major function is to operate the line flywheel sync section. However, our present interest is with frame pulses so we'll just give the line flywheel sync section a miss."

"Hey, wait a minute," interjected Dick. "We could at least take a quick look at it."

Smithy glanced at his watch and frowned.

"Well, it will have to be pretty quick, then," he remarked. "As we saw just now we have negative going sync pulses going into the base of the phase splitter. These will be large enough to turn off the phase splitter when they're present, with the result that we'll get

large positive going sync pulses at the collector of the phase splitter and large negative going pulses at its emitter. These then go to the flywheel sync diodes coupled to the line timebase."

Smithy pointed to the diodes in the service manual diagram. (Fig. 3.)

"Those pulses," he resumed, "cause the two diodes to become conductive when the sync pulses are present and to be non-conducting when the pulses are absent. Applied to the centre of the diodes is a waveform derived from the line output stage which has a steeply falling ramp corresponding to the line flyback period and a much less steep rising slope corresponding to the line scan period. When the line timebase is running correctly the steep ramp is applied to the diodes at the same time as they are made conductive by the sync pulses. In consequence, and ignoring the line hold potentiometer for the moment, the voltage at the centre of the two 12k Ω resistors across the diodes becomes the same as that held by the steep ramp when the diodes conduct. This is the control voltage for the line timebase frequency. If the line timebase tries to run too slowly an earlier part of the steep ramp coincides with the sync pulses and the control voltage goes positive. Conversely, if the timebase tries to run too fast the control voltage goes negative. The control voltage is applied via what is effectively a smoothing circuit, which provides the flywheel effect, to the timebase oscillator, and it controls the oscillator frequency in such a manner as to counteract any changes in it." (Fig. 4.)

"What about that line hold potentiometer?"

"Ah," said Smithy, "I was coming to that. The line hold potentiometer

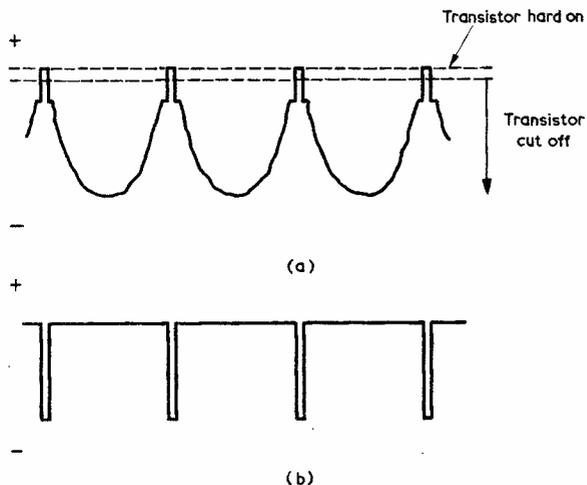


Fig. 2(a). The sync separator transistor is only conductive in the presence of sync pulse tips at its base

(b). The collector waveform of the sync separator consists, in consequence, of inverted sync pulse tips only

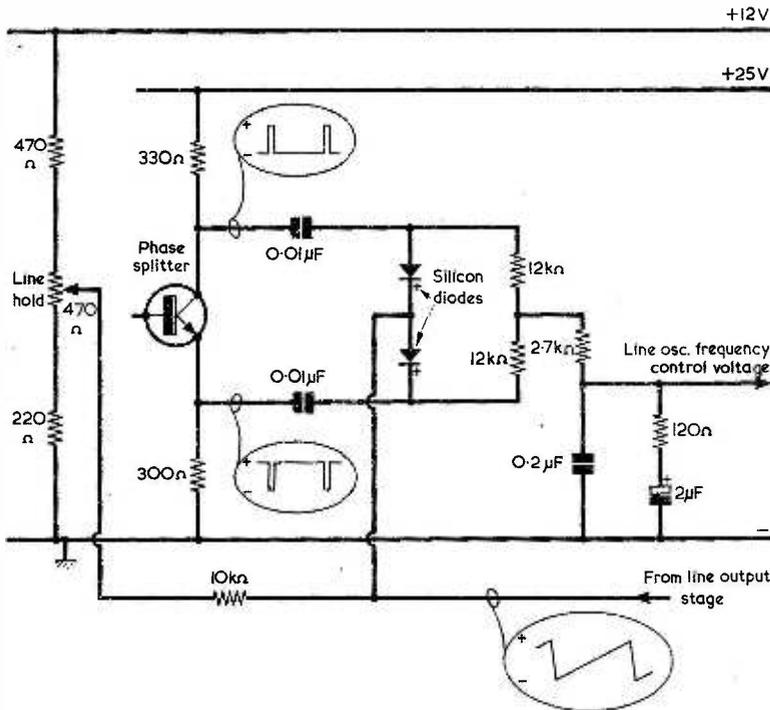


Fig. 3. The anti-phase pulses from the phase splitter are applied to the line flywheel sync diodes, causing these to be conductive when the pulses are present


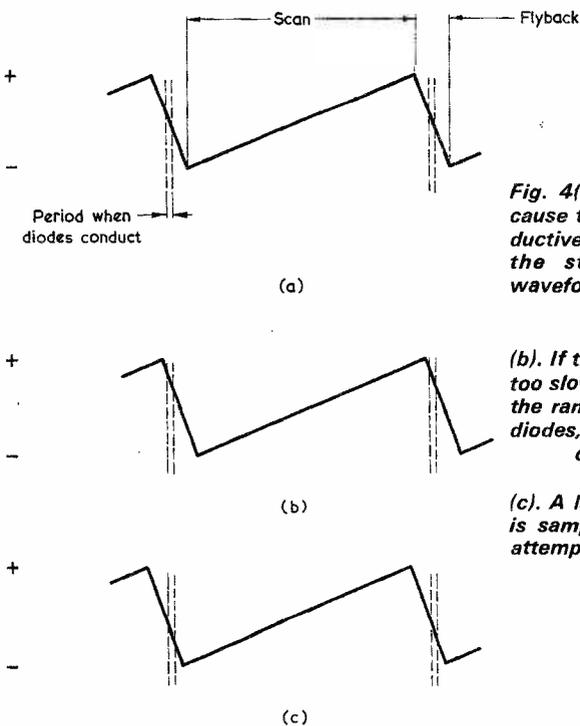


Fig. 4(a). Here, the pulses cause the diodes to be conductive at a central part of the steep ramp in the waveform from the line output stage

(b). If the line oscillator runs too slowly, an earlier part of the ramp is sampled by the diodes, giving a positive control voltage

(c). A later part of the ramp is sampled if the oscillator attempts to run too quickly

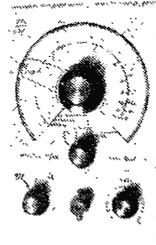AN AUDIO SIGNAL GENERATOR for only £14.95!



STAR FEATURES:


- ★ 15Hz-150KHz
- ★ Sine/Square Wave Output
Variable 0-3V PkPk
- ★ Very Low Current Consumption,
9V Btty
- ★ One IC Plus 4 Transistor Circuit
- ★ Smart ABS Case, drilled and
screen printed
- ★ KIT includes All Components,
Drilled PCB, Controls, etc.
- ★ Unbeatable Value:
KIT.....ONLY £14.95 (pp 70p)

Owing to heavy demand, there is
now a waiting list for six months.

CWO To:

WELLTEX MFG. CO.,
9 Sirdar Strand, Gravesend
DA12 4LP
(C.O.D. orders accepted)

MORSE MADE EASY

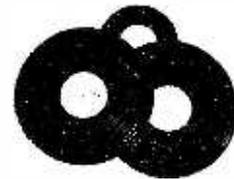

BY THE RHYTHM METHOD!

These courses, which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words.

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed. The Complete Course consists of three records as well as instruction books. For Complete Course send £5.00 including P.P.I. etc. (overseas surface mail £1 extra).

THE MORSE CENTRE

Box 8, 45 Green Lane, Purley, Surrey.
I enclose £5.00 or large s.a.e. for explanatory booklet.

Name.....

Address.....

setting modifies the voltage present at the diodes when they conduct. It provides a reference voltage which allows the overall circuit to run at correct line frequency, with the frequency still being held steady by the sampling of the waveform from the line output stage."

Smithy stopped talking and looked expectantly at his assistant.

"Blimey," said Dick, "you really were quick with that explanation."

"I had to be," stated Smithy. "It's missing frame sync pulses we're looking for, not missing line sync pulses. Still, that little sojourn with the line flywheel sync circuit did have one beneficial result. Since the line sync is working, it's obvious that there are positive going sync pulses at the collector of the phase splitter. When the broad frame pulses are transmitted these should be integrated by the following 18kΩ resistor and 2,000pF capacitor, whereupon large positive going frame sync pulses are available for the frame timebase multivibrator."

"Let's take a look at that next," said Dick quickly.

FRAME MULTIVIBRATOR

"Oh, all right," conceded Smithy. "At least it will be more to the point to discuss this than it was to talk about the line flywheel sync circuit. Here's the multivibrator bit."

Smithy indicated another part of the diagram. (Fig. 5.)

"Now," he continued, "this multivibrator controls an output stage which drives the frame deflection coils and which provides its own waveform shaping. All that the multivibrator has to do is to run at the correct frequency and to give scan and flyback periods of the correct length. During the scan period the right hand transistor is cut off and during the flyback period it is turned on. Shall we have a go at it first without sync pulses?"

"Yes, please."

"Right," said Smithy. "We can start at a moment in the multivibrator cycle when the right hand transistor is off and is just about to turn on. It's turned off because its base has been taken positive by the 0.22μF capacitor, which is discharging into the resistors connected to the base. Don't forget that the transistors in this multivibrator are p.n.p. instead of n.p.n., as all the previous ones have been. When the right hand transistor starts to pass current its collector goes positive, reducing the current flowing via the 10kΩ resistor to the base of the left hand transistor. The collector current of the left hand transistor reduces, the collector voltage goes negative and turns the right hand transistor on harder via the 0.22μF capacitor. The usual cumulative amplification in a multivibrator then takes place and it ends with the right hand transistor fully on and the left hand transistor cut off. The circuit stays in this state for the short period

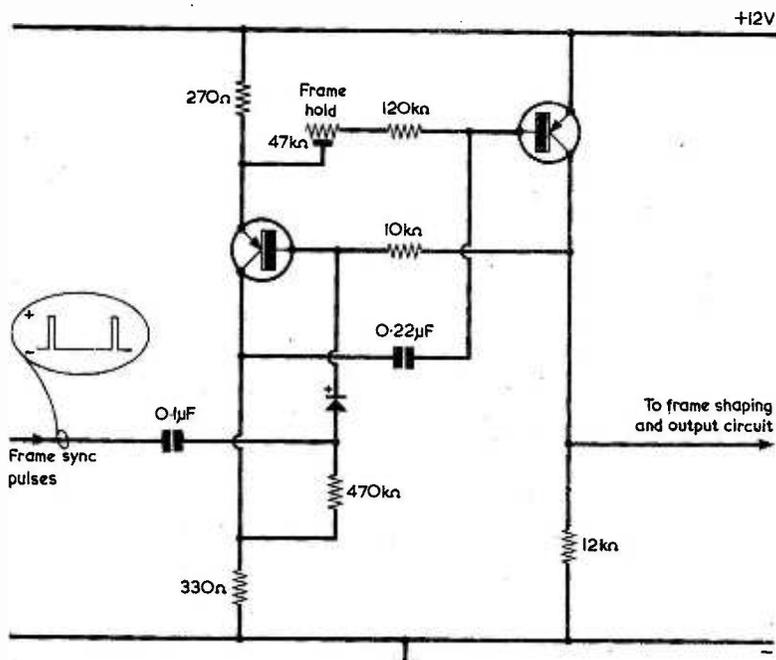


Fig. 5. The frame, or vertical, multivibrator in the television receiver. The 0.1μF capacitor is the same component that appears in Fig. 1, and the shape of the frame sync pulse is idealised. (This and the preceding circuits are slightly simplified versions of the circuit employed in the Thorn 1590-1591 series of television receivers.)

required for the 0.22μF capacitor to charge via the emitter-base junction of the right hand transistor and the 330Ω resistor. This is the flyback period."

Smithy paused.

"That's all nice and easy to follow up to now," commented Dick. "What happens next?"

"As soon as the 0.22μF capacitor becomes fully charged the base current in the right hand transistor reduces and the base goes slightly positive. There is a reduction in collector current, causing the collector to go negative and allow a small base current to flow into the left hand transistor. This is all that is needed to start the reverse changeover in the multivibrator. As soon as the left hand transistor starts to draw current its collector goes positive, and the 0.22μF capacitor takes the base of the right hand transistor positive, completely cutting this transistor off. We have now started the long scan period, with the left hand transistor turned fully on, so that its emitter is negative of the base of the right hand transistor. The duration of this period is the time needed for the 0.22μF capacitor to discharge into the 120kΩ resistor and the 47kΩ pot."

"And that," chimed in Dick, "will be a much longer period than the one when it charged via the 330Ω resistor because the resistance values are a lot higher."

"You've got it," said Smithy. "Also, the length of the scan period is controlled by the 47kΩ pot, which in consequence becomes the frame hold control."

"Right," said Dick. "Let's now put in the frame sync pulses."

"They're easy," said Smithy. "As we already know they're positive going, and they're applied via a diode to the base of the left hand transistor. They then turn this transistor off and initiate the flyback period a little earlier than it would otherwise start. This assumes, of course, that the 47kΩ pot is adjusted so that the frame scan period without sync pulses is a little longer than the period when sync pulses are applied."

Smithy stopped and Dick gazed at the circuit diagram of the television receiver with enhanced understanding.

"I certainly," he remarked, "know my way around this circuit a lot better than I did before."

Smithy gave a mock bow.

"Our earnest aim," he intoned, "is to provide satisfaction for our clientele."

"Indeed. Now, as you said earlier on, the frame multivibrator must be working all right. And there must be positive going sync pulses at the collector of that phase splitter transistor."

"Correct."

"So that only leaves the components

in between."

"Which," pointed out Smithy, "consist of one 18kΩ resistor, one 2,000pF capacitor, one 0.1μF capacitor and a diode. With, perhaps, a possible suspect in the 470kΩ resistor connected to the diode. I told you it was an easy one."

FAULT LOCATION

"With a bit of luck I'll be able to find it with an ohmmeter," pronounced Dick. "Anyway, here goes."

He disconnected the receiver from the mains and removed its back. After that he pulled his battered multimeter towards him, switched it to an ohms range and adjusted its set-zero control.

"I'll leave you to get on with it for a minute or two," said Smithy. "I've just got to finally screw up the back on the set I finished before I came over here."

Smithy walked back to his bench to complete his work, whilst Dick located the 18kΩ resistor connecting to the collector of the phase splitter transistor. He reasoned that as one side of this connected to two capacitors he would get an accurate reading of its value by simply applying his test prods to the resistor lead-outs. This he next proceeded to do. (Fig. 6(a).)

The testmeter indicated 1.2kΩ. "Smithy," he called out happily, "I've drawn blood first go! The 18kΩ resistor is reading low in value."

Jubilantly he picked up his soldering iron and applied it to the printed board, after which he carefully removed one of the resistor lead-outs from the board. Unknown to him, Smithy had now returned and was standing alongside him. As a routine check, Dick connected the testmeter prods to the 18kΩ resistor, which now had one of its lead-outs free of the circuit. The meter showed 18kΩ.

A grin passed over Smithy's face and he moved quietly to the spares cupboard then returned, just as quietly, to his assistant's side.

Frowning, Dick soldered the resistor back in place on the board and measured its resistance once more. Again the testmeter indicated 1.2kΩ. Puzzled, Dick decided to check elsewhere. He next applied his testmeter between the receiver chassis and the junction of the 18kΩ resistor and the 2,000pF capacitor. The meter indicated zero ohms. (Fig. 6(b).)

"Ah," muttered Dick to himself, "that's more like it."

This time he unsoldered one lead of the capacitor from the board. He applied the testmeter prods to the capacitor and was rewarded again with a reading of zero ohms.

He unsoldered the remaining capacitor lead and removed it from the board. Silently, Smithy reached forward and presented him with a new 2,000pF capacitor.

"Oh thanks, Smithy," said Dick absently.

He bent the capacitor leads so that

they would fit into the holes in the printed board, then suddenly stopped. A look of alarm spread over his face.

"Hey, what happened then?"

"I gave you a new 2,000pF capacitor."

Dick turned and pointed a trembling finger at the Serviceman.

"You've done it again," he accused. "Not only have you once more crept up on me without my knowing, but you've jumped one step ahead of me in fixing this set. There's something supernatural about you today, Smithy. It's either that, or you've got a time machine so that you can make little leaps back and forward in time."

"I just exercise," stated Smithy modestly, "a little informed foresight."

"Informed foresight?" repeated Dick incredulously. "The way you're acting you should be able to see into the middle of next week. I tell you, you're getting decidedly spooky. First of all, you've started gliding soundlessly around all over the place and when you get where you're going you just *hover!* And how on earth were you able to hand me a new capacitor just after I'd found out that the one in the set was short-circuited?"

"I guessed," explained Smithy, "that the 2,000pF capacitor in the set was shorted when the 18kΩ resistor read low when it was connected to the board and then showed its correct value when one of its leads was disconnected. Pretty well the only component which could cause these two readings was that 2,000pF capacitor."

"But," protested Dick, "how could that capacitor cause the low reading even if it was shorted?"

"Because it's connected to chassis, and the other end of the 18kΩ resistor couples via a 330Ω resistor to the positive rail. In many transistor TV circuits there is quite a low resistance between a positive supply rail and chassis because of base bias networks and similar resistive circuits between the two. So these were effectively connected across the 18kΩ resistor by way of the short-circuited capacitor."

Dick continued to gaze suspiciously at the Serviceman.

"Well, fair enough," he remarked eventually. "But I hope you're not going to get up to any more tricks like that. This has been an extremely unsettling afternoon."

TEAMWORK

With which words Dick once more picked up his soldering iron and fitted the new capacitor to the board. After snipping off the excess lead-out wires on the copper side of the board, he turned the set round, plugged it into the mains again and switched it on.

After a period the cathode ray tube reproduced a picture which was firmly locked in both the horizontal and vertical directions. Dick checked the frame hold control, to find that this had a good and very satisfactory lock-in range. It was obvious that the frame

GAREX

Experimenter's H.T. transformer; multitap primary, 5 sec. windings: 35V 200mA, 75/115V 150mA, 50V 500mA, 150V 300mA, 170/220V 300mA. Wt. 6kg. **£5.50**
Relays: GPO type 2400 (medium size); 200+200Ω coil (12-24V), 8A contacts 4PCO+1M 10kΩ coil (50V+), 2 Make, 8A 14kΩ coil (50V+), 2PCO+1 break. Type 3000 (large): 2k coil (24V) 1B+3M, 2k coil (24V) 2PCO, 8A 100+100 coil (3-12V) 4PCO.

All new, 60p each, any 5+: 40p
H.T. chokes 5H 80mA, 1-8H 125mA **£1.25**
Neons min. wire end, 55p/10; **£4/100**
Slide Switches min. DPDT 18p ea; 5+: 14p
2 pole, 3 position 22p ea; 5+: 18p
PL259 UHF Plug & Reducer 68p; 5+: 60p
SO239 UHF Socket panel mtd. 55p; 5+: 45p
BNC cable mtg Socket 50Ω 20p; 5+: 15p
57 values, 5% carbon film, ½W or ¼W.
Starter pack, 5 each value (285) **£2.40**
Mixed pack, 5 each ½W + ½W (570) **£4.65**
Standard pack, 10 each (570) **£4.65**
Giant pack, 25 each (1,425) **£11.65**
Nunicators XN3 75p each; 5+: 63p
I.C.'s (new, full spec.) CD4001AE 25p
SN76660 **£1.12**, 723 (TO5) 90p
NE555 Timer 65p
709 (TO5); 741 (DIL-8) Op. amps 30p each
5+ I.C.'s (any mix) at 20% discount
Nicaid rechargeable cells HP7 size **£1.05**
each; 4+: 95p; 10+: 88p. Brand new.
We stock amateur V.H.F. equipment and mobile aerials, s.a.e. details.
Distributors for J. H. Associates Ltd. (switches and lamps)

Prices include UK Post, Packing & VAT
Mail order only Sole Address:
GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH,
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 668684

RADIO & ELECTRONICS CONSTRUCTOR

ANNUAL
SUBSCRIPTIONS
to this magazine
may be obtained
through your
newsagent
or direct from the
publishers

ONLY **£5.50**
per year, post free

Please send remittance with name
and address and commencing issue
required to:

DATA PUBLICATIONS LTD
57 Malda Vale London W9 1SN

Radio Topics

By
Recorder



I should imagine that I am in company with most electronically minded home constructors when I admit to the fact that I am something of a hoarder. I just can't bring myself to throw out things unless they have a nuisance value which definitely outweighs any advantage they may possess. Into this last category fall such obvious items as broken down capacitors and resistors which have shifted in value. The rest remain.

Although this means that quite a lot of space is cluttered up with components and hardware for which there is no apparent use, the availability of the odd part can at times be of considerable help in solving some of the more unusual problems that arise. Let me give a few examples.

POWER SUPPLY SWITCH

Amongst my equipment is a variable voltage power supply, the mains input of which is turned on and off by means of a double pole rotary toggle switch. When, some time ago, I turned the power supply on at the start of a working session the internal insulation between the two switch poles broke down, causing an impressive crack and the untimely demise of the cartridge fuse in the mains plug. What was obviously required was a new switch, but I just didn't have on hand a replacement of the same type. This fitted in a $\frac{3}{8}$ in. front panel hole, whilst all I had available were standard sized dolly operated toggle switches requiring a larger panel hole. I didn't particularly relish the idea of filing the existing panel hole wider to take one of these. One reason was that the rotary switch knob matched in with the remaining control knobs on the

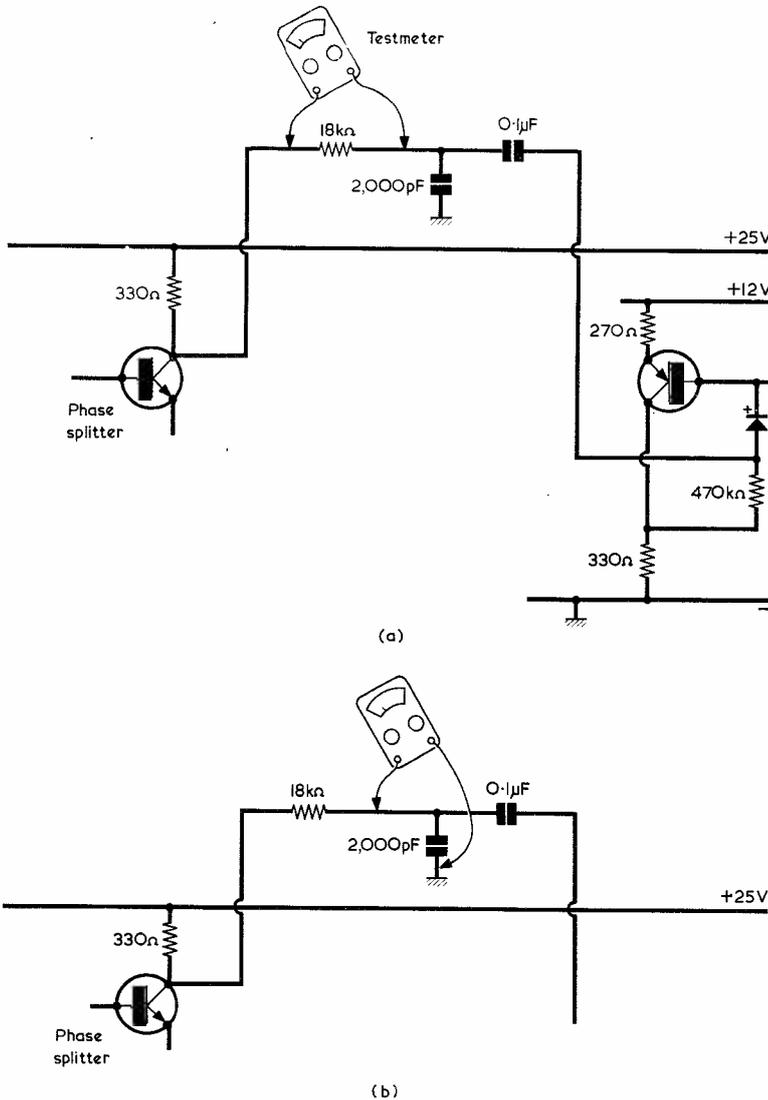


Fig. 6(a). Dick initially checked the resistance of the 18kΩ resistor in the frame sync pulse integrating circuit following the phase splitter. Part of the frame multivibrator is also shown here

(b). Dick's second check consisted of applying his testmeter to the 2,000pF capacitor

sync pulses were now finding their way, fully integrated and completely unobstructed, to the multivibrator in the frame timebase.

"There you are, Smithy," said Dick triumphantly, turning to his side. "Another set finished and . . ."

But Smithy had vanished.

Unnerved, Dick gazed around the empty Workshop. There was suddenly a rattle at the door handle, after which Smithy entered, rubbing his hands together briskly.

"Where the heck," asked Dick, "did you disappear to?"

"To my usual port of call," replied Smithy innocently. "I tend to pop out there now and again throughout the day. Ah, I see that that TV is working all right now. We did a good job there."

"We?"

"We," confirmed Smithy cheerfully. "There's nothing to beat teamwork between two people, where each one knows precisely what the other one is up to."

And it has to be recorded that Dick, on hearing this estimable observation on the part of the Serviceman, for once had no reply to offer at all.

front panel, and a second reason was that I would in any case be able to get a new rotary switch of the correct type in a few days.

Then the inspiration bulb glowed. Hidden away amongst my junk was an old 1M Ω volume control with switch which had once been fitted to a valve radio. I mounted this volume control in place of the faulty rotary switch, connecting the wires from the previous component to the switch section at the back of the potentiometer. Obviously, no connections were made to the potentiometer tags themselves.

I was then in business again. After switching on with the improvised switch there was now a considerable amount of spindle travel available in the clockwise direction which served no useful function, but this didn't matter. I hadn't had to carry out any metal-bashing work on the front panel and I now had a perfectly satisfactory on-off switch. As things happen, it was about several months before I finally got round to obtaining a proper rotary switch and fitted it in place of the temporary one!

HEAT SINKS

At another time I was playing around with an a.f. amplifier circuit which had an AC127 and an AC128 in the output stage. These transistors are both housed in TO-1 cans, and they were running just a little warmer than I liked. Once again my stock of old parts came to the rescue and I unearthed a couple of valve top cap connector clips, which fit very nicely over TO-1 transistor cases. I soldered a 1in. square piece of tinfoil to each clip and then passed the clips over the transistor bodies. A rough and ready form of heat sink, I'll agree, but it sufficed to keep those two transistors at a safely low operating temperature.

Turning to components which are rather more modern than the AC127 and AC128, I recently did some circuit experiments with i.c. op-amps having eight lead-outs disposed in a circle. I am not too keen on these, as I find the dual-in-line i.c.'s much more convenient to handle and wire up. So I wired the i.c.'s to the tags of B9A

valveholders, the latter being mounted with the tags uppermost. Obviously, no connection was made to one of the valveholder tags. The resulting appearance was admittedly rather non-technical, but the valveholders adequately served their purpose in providing what were effectively 9-way circular tagstrips.

I also keep scraps of 0.1in. Veroboard if these are not too small. They are ideal as templates for marking out and even drilling the holes in a printed board for d.i.l. integrated circuits or their holders.

And so it goes on. It is quite amazing what uses one can find for odd parts, particularly those which have hung over from the old valve days. As for things like bolts, nuts and similar items, my collection goes back to the early 1950's. But then, who heard of a radio construction enthusiast who ever threw away a single nut or bolt?

A SOCIAL NOTE

Looking back over some of my jottings of 12 years or so ago, I detect a welcome change which has been brought about by the increasingly large numbers of colour television receivers installed throughout the country. In those earlier days of black and white TV's, one of the perils of being known as someone connected with electronics was being approached by acquaintances who wanted their television sets repaired on the cheap. It was surprising how many people, at that time, were prepared to drop the most outrageous hints in order to cajole you into fixing some clapped-out old monochrome receiver.

Not so nowadays, I'm happy to say. Anyone who has a colour TV regards it with the utmost veneration, and the last thing he wants is someone who doesn't wear a professional service engineer's hat tinkering around with its innards. And so you can relax in company and chat about electronics as much as you like, without being subject to the blandishments of those television owners whose sets "have only got a wire loose".

A pleasant change indeed.

TRANSISTOR TYPE NUMBERS

You would think that, if two transistors have the same type number, they should be identical regardless of the manufacturer. This is not always the case, however, and occasional differences tend to creep in.

An example I bumped into recently is concerned with the BFY50, BFY51 and BFY52 "family" of transistors. These are n.p.n. silicon planar transistors intended for general purpose industrial applications. They are listed by Mullard, in whose data they are described as being housed in a TO-5 can. They are also listed by Texas Instruments, who describe them as being in a TO-39 case!

The Mullard and Texas Instruments data on the transistors are virtually identical and each version of the transistor has the same lead-out layout, with the collector connected to the can. In practice, there isn't a great of difference between the TO-5 and TO-39 encapsulations, both of which have the usual locating lug. Whereas the width of the TO-5 can is 8.20 to 8.50mm., the width of the TO-39 can is 7.75 to 8.51mm., and other dimensional discrepancies are of the same minor order.

Still, it's a little disconcerting when one first encounters two different encapsulations for the same transistor.

Another transistor which appears in more than one guise is the n.p.n. 2N3404. This is listed by American General Electric and appears also in the old Brimar lists, and the lead-outs appear in the order: base, collector, emitter. It is listed also by Sescosem, however, who show the lead-out order as: collector, base, emitter.

It is very rarely that incongruities of this type crop up. I remember one popular f.e.t. whose manufacturer, some years ago, issued data sheets in which the drain and source lead-out identifications were transposed. In this instance the difference between the two sets of data didn't really matter as, in practice, the f.e.t. seemed to work quite happily connected either way round! ■

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.




We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 40p plus 11p postage.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available. Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

WORKSHOP AIDS

TEST INSTRUMENT RANGE

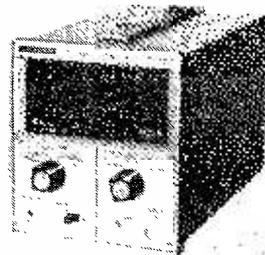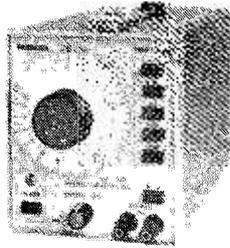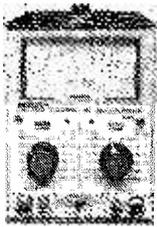

C. E. Hammond & Co. Ltd., 105 Oyster Lane, Byfleet, Surrey, announce the availability of the following Leader Test Instruments: *Model LDC-821 Digital Frequency Counter* with the following features: Automatic control of trigger level; Easy-to-read display tubes, unlike 7-segment indicators; Four gate times for good resolution; High sensitivity — only 50mVrms input required; Compact construction. *Model LAG-120 Audio Generator* with the following features: Wide frequency range — 10Hz to 1MHz with flat output response; Synchronizing with an external frequency source is possible when required; Compact construction requires only a small space on the bench. *Model LMV-186A Stereo AC Millivoltmeter* which has been developed especially for voltage measurement from two separate inputs at similar levels. *Model LEM75 Electronic Multimeter* with the following features: Battery operated for portability; Mirror-backed scales for accurate readout; Measures both DC and AC currents to 300mA; Tilt stand for easy viewing.


VERO WIRE KIT

Vero Electronics Ltd., have improved their Verowire® prototyping system by the addition of a number of items.

The system itself is designed for the fast and easy construction of prototype breadboards or short production runs. Interconnections are made by means of a polyurethane-insulated wire, dispensed through a wiring pen. This enables fine wiring to be achieved quickly and in a single operation. Soldering of the whole board can likewise be consolidated into a single task, since the heat of the solder melts the wire insulation, which acts as a flux, avoiding the repetitive and time-consuming cut-strip-route-solder routine.

The Verowire® kit now contains spools of wire in four different colours to facilitate the identification of wires. Each spool contains 40 metres of 0.15 mm. diameter wire, rated at 0.030 amps. A soldering iron, Order Code 22-0176E, is now available for use with Verowire. This iron is fitted with 1.8 metres of twin core mains cable, and is notable for its very low current leakage.

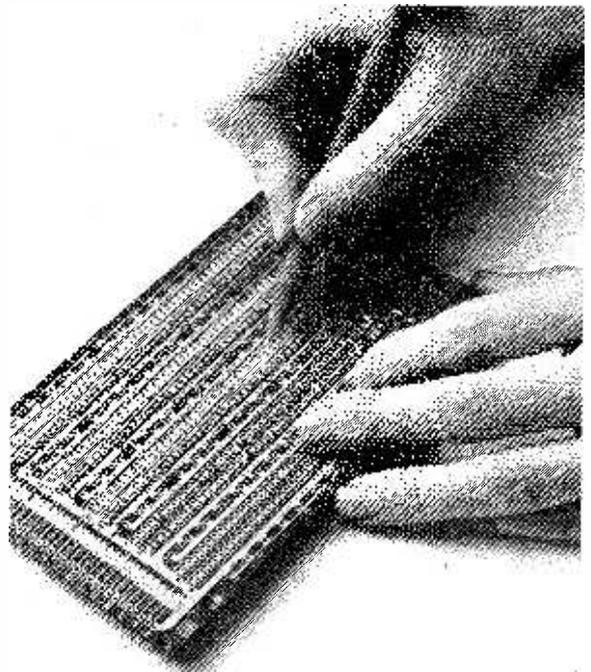Full details of the improved Verowire® system are available in a new leaflet from Vero Electronics, Industrial Estate, Chandlers Ford, Eastleigh, Hampshire.



SMALL ADVERTISEMENTS

Rate: 8p per word. Minimum charge £1.00
Box No. 20p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *Radio and Electronics Constructor*, 57 Maida Vale, London, W9 1SN.

TREASURE HUNTERS! Construct 11-transistor metal detector giving £300 performance. 10 page illustrated plans, send £1. C. H. Lucas, 241 Upminster Road South, Rainham, Essex.

WANTED TO PURCHASE: All early books on radio, preferably before 1925. Box No. 282.

MAINS TRANSFORMERS. 240V Pri. Two separate secondaries. 7½V at 500mA each. £1 each plus 35p p&p. NF Electronics, Church Lane, Flax Bourton, Bristol.

SERVICE SHEETS for Radios/TV's etc. 50p and s.a.e. Catalogue 20p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

HOW TO BUILD a cheap set of good quality speakers. Leaflet 20p plus s.a.e. Ex-TV speakers, 3 ohm, 50p plus 25p post/pkg. Circuit diagrams back to 1933, 25p each plus s.a.e. Reply to: R.U.L., 19 Reginald Road, Eastney, Portsmouth, Hants. PO4 9HL.

WANTED: Large and small quantities of transistors, I.C.'s, displays, etc., etc., Call any Saturday to: 306 St. Paul's Road, London N.1. Telephone: 01-359 4224.

SIX 7-SEGMENT LED DISPLAYS £1. Ex-equipment but guaranteed in arrays of 6, with data. Mr. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

ANTIQUE RADIO BOOKS. Newnes "Television & Short Wave Handbook" by F. J. Camm, 1935, £3.00. News Chronicle "Wireless Constructor's Encyclopaedia" by F. J. Camm, 3rd edition, circa 1930, £3.50. Prices include postage and packing. Box No. G318.

60kHz MSF RUGBY RECEIVERS BCD time-of-day output. High performance PLL 5V operation, pulsating LED. Kit or assembled instrument available. Prices £14.08-£23.47. Details: Toolex, Sherborne, Dorset.

FOR SALE: Fuzz kit £1, AC128 10p, C60's 50p. All inclusive. Delos Electronics, 76 Ber Street, Norwich, Norfolk.

TV REPAIRS SIMPLIFIED. Full repair instructions individual British sets £4.50; request free circuit diagram. Stamp brings details of unique TV publications. Auserec, 76 Churches, Larkhall, Lanarkshire.

GRIMSBY ELECTRONICS, LAMBERT ROAD, GRIMSBY: For components, cases, Veroboard, surplus, etc. by return. Lowest prices. Bargains list 9p. (Callers Saturdays only).

(Continued on page 581)

THE Amateur Radio Event of Jubilee Year RSGB INTERNATIONAL RADIO COMMUNICATION EXHIBITION AND CONVENTION

Alexandra Palace, London N22
6-8 May 1977

LARGE TRADE EXHIBITION

Equipment and components from leading manufacturers by well-known suppliers

LECTURES

On Microwave, VHF/UHF, HF and SWL topics
(See April *Radio Communication* for details)

MEMBERS' MART - Sunday May 8

DINNER/DANCE - Saturday May 7

FOR THE FAMILY - All the free facilities and attractions of Alexandra Park

OPENING HOURS:


11am-7pm Friday; 11am-6pm Saturday;
11am-5pm Sunday

ADMISSION:

Exhibition and lectures (at the door): Adults 40p; children under 14, 20p

Dinner/Dance (tickets in advance): £5.50

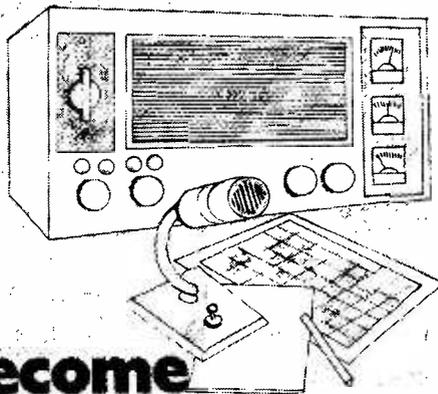Bookings for trade exhibition and members' mart space, and applications for dinner/dance tickets, should be made to J. Hitchins, RSGB, 35 Doughty Street, London WC1N 2AE



Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

WAA

Brochure, without obligation to: REK 47

**BRITISH NATIONAL RADIO
& ELECTRONICS SCHOOL,**

P.O. Box 156, Jersey, Channel Islands.

NAME _____

ADDRESS _____ (Block caps please)

Free!

Use the **NEW Strip-fix Plastic** **PANEL SIGNS**

★ **SET 3 - Wording - WHITE**

★ **SET 4 - Wording - BLACK**

Over 1,000 words and symbols, covering more than 300 terms, in each set

Illustration of actual size = RADIO

★ **SET 5 - DIALS**

6 sheets containing one Large and two Medium scales, Large Horizontal Tuning scale, Frequencies, 12 Control Panels

- Easy to fix
- Stapled in booklet form
- Designed to hang above workbench
- Pocket for loose cuttings
- Professional finish



PRICE

SET 3: 75p

SET 4: £1.00

SET 5: 38p

(P. & P. 7p per set)

ALL PRICES INCLUDE V.A.T.

The Perfect Transfer for the Home Constructor

To Data Publications Ltd., 57 Maida Vale, London, W.9 1SN

Please supply Panel Signs as follows: Set 3 Set 4 Set 5

I enclose cheque / crossed postal order for (Tick which set is required)

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

SMALL ADVERTISEMENTS

(Continued from page 579)

COLLECTORS' ITEMS: Bound volumes of *The Wireless World* (which was then published weekly) for 1931, 1932, 1933, 1934, 1935, 1936, 1937, 1938 and 1939 (nine months only for this year due to outbreak of war). Two volumes per year, total of 18 volumes. All in very good condition. Offers invited. Box No. G319.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. Rita Shepherd, 59 Paintain Road, Loughborough, Leics., LE11 3LZ.

WANTED: Plug for the 6 volt d.c. socket on the Bush TP60 Cassette Tape Recorder. Box No. G326.

FOR SALE: Merit Chemistry Set No. 2. Cat. No. 802. Offers? Box No. G327.

FOR SALE: Heathkit DX60 Phone-CW Transmitter, with HG10 80-2M VFO Unit. Heathkit 5-band receiver HR10 for AM, CW and SSB. £50.00. s.a.e. for details. — Box No. G328.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

FOR SALE: 108-136MHZ Receiver. Size 5in. x 3in. x 2in. Pocket size. Easily adjusted to tune over 144MHz band with good sensitivity. £16.50 post and packing paid. Romak Engineering Ltd., Dept. RE, 10 Hibel Road, Macclesfield, Cheshire SK10 2AB.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars, Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

BOOKS TO CLEAR: *Admiralty Handbook of Wireless Telegraphy*, Vol. I, 1938 — H.M. Stationery Office, £1.50. *Radio Servicing — Theory & Practice*, 1950, by Abraham Marcus, £1.50. *Introductory Radio — Theory and Servicing*, 1948 (With Teacher's manual) by H. J. Hicks, £1.50. *Klystron Tubes*, by A. E. Harrison, 1947, £1.50. *An Approach to Audio Frequency Amplifier Design*, 1957, G.E.C. Publication, £1.25. *Television Engineers' Pocket Book*, 1954, by Molloy & Hawker, 50p. *Radio Servicing Pocket Book*, 1955, by Molloy & Hawker, 50p. All prices include postage. — Box No. G329.

MULLARD COMPONENTS, Send s.a.e. for free list to P.M.S. Dept REC6, PO Box 6, Crawley, Sussex, RH10 6LH.

(Continued on page 583)



ETCHING KIT

All you need to make your own PRINTED CIRCUITS

Full instructions, Copper Clad Board, Ferric Chloride, Dish and Pen

Price incl. VAT & Postage **£4.75**

Send cheque or P.O. today to:
HOME RADIO COMPONENTS LTD.

240 London Road, Mitcham,
Surrey, CR4 3HD

VALVE BARGAINS

Any 5-64p, 10-£1.20. 50-£5.00.
Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL86, PCL805, PL504, PY81/800, PY88, 30PL-14, 6F28.

Colour Valves—PL508, PL509, PL519, PY500/A. All tested. 35p each.

Aerial Splitters—2 way, 75 OHMS, Inside Type, £1.50.

Press Button UHF Tuners—4 Button Transistor — British made — £2.50 each..

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11—For TH stereo and standard VHF/FM radio.

B12 — For the older VHF television — Please state channel numbers.

B45—For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. **£3.80**


60p BARGAIN PACKS

All Packs Un-used Parts—PK1-40-C280 (Mullard) Axial Lead Capacitor mixed values from .01uF to .47uF (250V/W). PK2-30-C281 (Mullard) Radial Lead Capacitors mixed values from .051uF to 1.5uF (250V/W). PK3-6 Co-ax. plugs. PK4-6 Co-ax connectors. PK5-8-5 m/m formers with slugs. PK6-25-AC128 Transistors. PK7-3 BF200 (VHF) Transistors. PK8-2 BF182 (UHF) Transistors. PK9 Any 6 Transistors BC108, BC113, BC135, BC153, BC171, BC172, BF194, BF195, BF196, BF197, PK10 8-1 amp 400 volts rectifiers. PK11 4-5 pin din plugs (180°). PK12-5 PP3 Battery Connectors.

All prices include VAT. P&P 20p per order. Please send uncrossed P.O. or Cheques for returning if we are out of stock of Bargain Packs or older types of new valves.

ELECTRONIC MAILORDER LTD.
62 BRIDGE ST., RAMSBOTTOM, BURY, LANCS.
TEL. RAMS. (070 682) 3036.

THE OPEN DOOR TO QUALITY

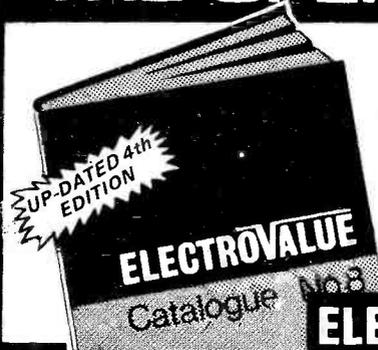

4th ISSUE INCLUDES NEW METERS AND SWITCHES as well as items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts continue on many purchases, Access and Barclaycard orders are accepted.

SEMI-CONDUCTORS ● COMPONENTS ● ACCESSORIES ● TOOLS
*** FREE POSTAGE** on all C.W.O. mail orders over £2 list value (excluding VAT) in U.K., add 15p handling charge.

144 pages
40p
 Post paid
 inc. refund
 voucher
 worth
40p

All communications to Head Office, Dept. RC4, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Phone Egham 3603 Telex 284475. Hours 9-5.30 daily; 1 pm Sats. NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone 061 432 4945. Hours 9-5.30pm, 1 pm Sats.

ELECTROVALUE LTD

MULLARD FERRITE CORES — LA3 100 to 500 kHz, 75p; LA5 30 to 100 kHz, 100p; LA7 10 kHz, 100p
 LA13 for W.W. Oscilloscope, £2.00.

SPECIAL OFFER — Metallised Polyester Capacitors by Erie, Mullard, etc. Values include: .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed. 100 for £3.00.

1N4148 SWITCHING DIODES, 10 for 30p; 50 for £1.25; 100 for £1.50; 1,000 for £12.50.

TRANSISTORS — All branded BC147, BC148, BC149, BC157, BC158, BC159, BF194, BF195, BF196, BF197, 10p each or 100 for £8.50.

Please note all prices include UK Postage and appropriate VAT @ 8% or 12½%

XEROZA RADIO

306 ST. PAUL'S ROAD, Highbury Corner, London N1
 Tel: 01-226 1489

'Management Information Systems'

An instruction Manual for Business Students

Deals with the underlying principles of systems and is a companion volume to "Data Processing" by Oliver & Chapman.

45 pages. **Price 75p** including postage

From:

D. P. PUBLICATIONS, 4 AMPORT CLOSE
 WINCHESTER, HANTS.

A CAREER IN RADIO

Start training **today** and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for **you**.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
 Radio TV Electronics Technicians'
 Electrical Installations Technicians'
 Electrical Installation Work
 Radio Amateurs

MPT Radio Communications Cert.

**EXAMINATION STUDENTS —
 GUARANTEED COACHING
 UNTIL SUCCESSFUL**

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
 Electronic Engineering & Maintenance
 Computer Engineering/Programming
 Radio, TV & Audio Engineering & Servicing
 Electrical Engineering, Installations & Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name..... Age

Address.....

Occupation.....

ICS

Accredited
 by CACC
 Member of
 ABCC

To:
 International Correspondence Schools,
 Dept 789D, Intertext House, LONDON
 SW8 4UJ or phone 01-622 9911 (all hours)


For the Radio Amateur

HAM RADIO

A Practical Guide and Handbook

KENNETH ULLYETT
 26 illustrations £4.50

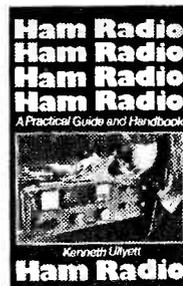Without the use of mathematics, circuit diagrams or scientific formulae, the author initiates the amateur in setting up a communications receiver which can, in perfect conditions, span the globe for shortwave listening. Exchange QSL (message-received) cards, technical examinations, setting up transmitters and handling morse and continuous wave codes are also included.



MAKE YOUR OWN ELECTRICITY

TERENCE McLAUGHLIN
 33 illustrations £3.95

Learn to make and control your own power supply with simple, economical generating equipment. Full construction details and circuit diagrams are provided for efficient harnessing of the wind, sun and water as well as oil and other available sources.

DAVID & CHARLES
 Brunel House Newton Abbot Devon

SMALL ADVERTISEMENTS

(Continued from page 581)

MULLARD HI-SPEED Valve tester with cards and manual, £25. Old Avo Valve tester with manual, £10. Newnes *Radio & TV Servicing*, Vols. I to V plus '57-58 and '59-60, £8. *Wireless World* 1939 to 1965. Offers? Priest, 21 Levens Grove, Blackpool, Lancs., FY1 5LA.

I SHALL BE PLEASED TO SUPPLY your components for projects in this magazine. State your requirements for a quotation. Barras Electronics, 11 North Street, Coventry, Warwickshire.

WANTED: *Radio Constructor* for August, September & October 1968. Also back copies of ARRL Handbook, CQ, QST, etc. Box No. G330.

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32 Mc/s at every 500Kc/s points. Each frequency is repeated. Two sheets for 5p., five sheets for 10p., postage 7p. Data Publications Ltd., 57 Maida Vale, London, W9 1SN.

SURPLUS SEMICONDUCTORS. All new and marked. OC28, OC29, BD181, BDY20, BD116, RCA40411, 50p each. AU110, R2008B, £1 each. AF118, AC176/K, 25p each. TAA630Q (G8 decoder) £2. Box No. G331.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

SPONSORS required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational, Educational. You can be involved. Write to: NAS Secretary, The Manse, Back Lane, Wymondham, Norfolk.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norfolk, NOR 85S.

H.M. ELECTRONICS

275a Fulwood Road, Broomhill
SHEFFIELD S10 3BD Tel: 0742-669676

BEC CABINETS (Book End Chassis)

Standard Cabinet	GB2	14" x 7" x 3"	
GB1	14" x 6" x 2"	GB3	14" x 9" x 4"
GB1A	9" x 6" x 2"	GB4	14" x 9" x 6"

Send 15p for wallet of leaflets.

A beautifully designed modern cabinet with simulated black leatherette top (PVC bonded to metal) solid wooden end cheeks, with room at the back for Output Sockets etc. felt pads are fitted on bottom of cheeks for non-scratch.

PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines

(max. format 7½" x 9½")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE £1.15 P. & P. 30p

Owing to heavy demand please allow
27 days for delivery

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price **35p** each, postage 11p

Issue(s) required

Annual Subscription

Price **£5.50**, post free, commence with.....issue

Bound Volumes:

Vol. 27. August 1973 to July 1974	Price £2.40 , post & pkg 75p
Vol. 28. August 1974 to July 1975	Price £2.75 , post & pkg 75p
Vol. 29. August 1975 to July 1976	Price £3.10 , post & pkg 75p

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only Price **£1.20**, post & pkg 30p

With no title on spine, maroon Price **£1.15**, post & pkg 30p

With no title on spine, green Price **£1.15**, post & pkg 30p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages	Price 90p , P. & P. 18p
DB6 Radio Amateur Operator's Handbook, 88 pages	Price 70p , P. & P. 12p
DB17 Understanding Television, 504 pages	Price £3.25 , P. & P. 60p
DB19 Simple Short Wave Receivers 140 pages	Price 80p , P. & P. 18p

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White Price **75p**, P. & P. 7p

Set 4: Wording — Black Price **£1.00**, P. & P. 7p

Set 5: Dials Price **38p**, P. & P. 7p

Prices include V.A.T. on Panel Signs

I enclose Postal Order/Cheque for.....in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

ELECTRONICS DATA

FOR THE BEGINNER


SCREENING

Screening, or shielding, is employed to prevent unwanted signal radiation or pick-up, or unwanted coupling. In (a) a stray capacitive coupling exists between two equipment signal points, X and Y; this is almost completely removed in (b) by the metal screen (shown, as is customary, in broken line). Both points now have a stray capacitance to the equipment chassis, and virtually none with each other. Complete capacitive screening is achieved by enclosing one point in a metal casing, as in (c). These are examples of electrostatic screening.

The two radio frequency coils in (d) can have an inductive, or magnetic, coupling between them which is much greater than the stray capacitive coupling. One coil is placed in a metal screening can in (e); eddy currents induced in the inside surface of the can produce a magnetic field opposing that due to the coil and very nearly cancel it out. Complete isolation between the two coils is given in (f), where both are in cans.

Eddy current magnetic screening is less effective at low frequencies and an inductive component may then be screened by enclosing it in a can of high permeability metal (i.e. metal in which a changing magnetic field flows readily). The magnetic field around the component, or an external field impinging on it, flows readily in the screen and is largely prevented from passing through. In (g) a microphone transformer is so screened.

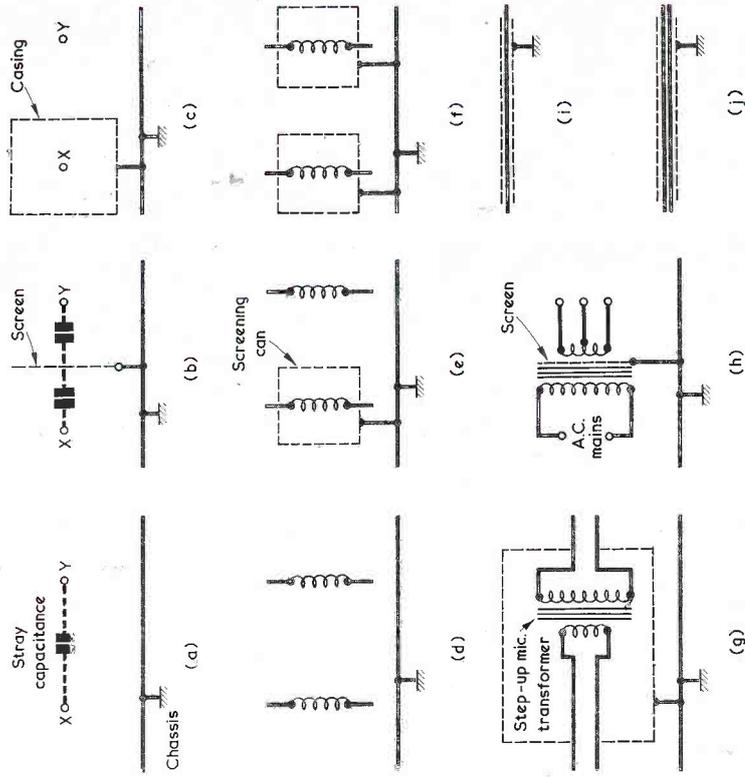In (h) a non-magnetic metal shim, which does not form a complete turn, has been interposed between the primary and secondary of a mains transformer. This provides electrostatic screening between the windings. Screened cables are shown in (i) and (j).



The new Maplin Catalogue is no ordinary catalogue...

Hundreds of fascinating new lines.

Several major new projects to build.

MAPLIN ELECTRONIC SUPPLIES



SUPERSONIC SAME DAY SERVICE!

QUALITY COMPONENTS FAST!

Super Discount Scheme - saves you pounds!

Handfuls of photo-graphics and illustrations



We stock some super digital clocks. A mains driven clock with alarm, snooze and all the features you'd expect. A digital car clock with automatic display blanking when you switch the engine off. A very accurate timer that switches on at a preset time and off at a tape-time — if you've got a tape-recorder there's no need to miss your favourite programmes ever again.



The book section contains over 150 titles of books about electronics, radio, TV, Hi-fi etc. Browse through the pages and choose from some of the best titles around including a superb set of books that will teach you electronics by experimentation! (Foot of catalogue page 142)



Pages 59 to 61 of our catalogue show you our range of Veroboards and S-Decs or if you prefer to make your own PCB's a range of etching systems including the novel Dato etch-in-a-bag system, plus printed circuit transfers for that professional finish to your boards.

Catalogue includes a very wide range of components: hundreds of different capacitors; resistors; transistors; I.C.'s; diodes; wires and cables; discotheque equipment; organ components; musical effects units; microphones; turntables; cartridges; styli; test equipment; boxes and instrument cases; knobs, plugs and sockets; audio leads; switches; loudspeakers; books; tools — AND MANY MANY MORE.



* Our bi-monthly newsletter keeps you up to date with latest guaranteed prices — our latest special offers (they save you pounds) — details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

SEND THIS COUPON FOR YOUR COPY OF OUR CATALOGUE ON APPROVAL! Price 50p — SEND NO MONEY NOW

Please rush me a copy of your brand new 1977/78 catalogue by return of post. Only if I am completely satisfied that it is worth every penny, will I send 50p within 14 days of receipt. If I am not satisfied, I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME _____

ADDRESS _____

REC4

Maplin Electronic Supplies P.O. Box 3, Rayleigh, Essex, SS6 8LR

**DON'T DELAY
POST COUPON NOW
IT COULD BE THE
BEST 50p YOU'VE EVER SPENT**

MAPLIN

ELECTRONIC SUPPLIES
P.O. BOX 3, RAYLEIGH, ESSEX SS6 8LR

Telephone: Southend (0702) 715155

Call at our shop: 284 London Road, Westcliff-on-Sea, Essex
(Closed all day Monday) Telephone: Southend (0702) 47379