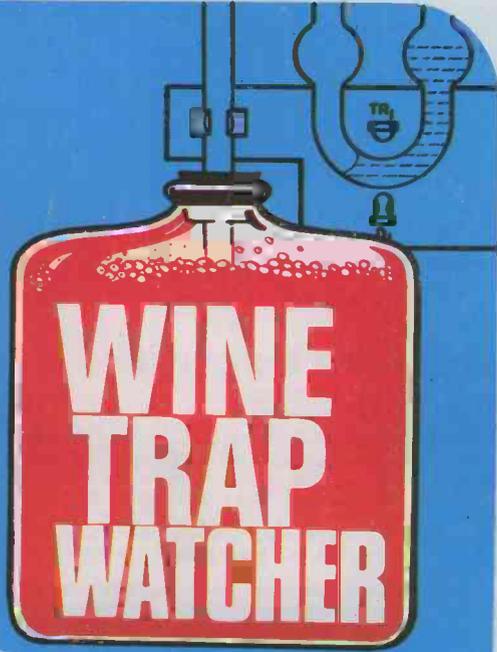


# RADIO & ELECTRONICS CONSTRUCTOR

JUNE 1980  
55p



**DUSK TO  
DAWN  
SWITCH**



**WINE  
TRAP  
WATCHER**

**PASSIVE  
LOGIC  
PROBE**




**ALSO  
FEATURED**

**ROBUST BURGLAR ALARM**

# DIRECT SUPPLY SERVICE TO READERS
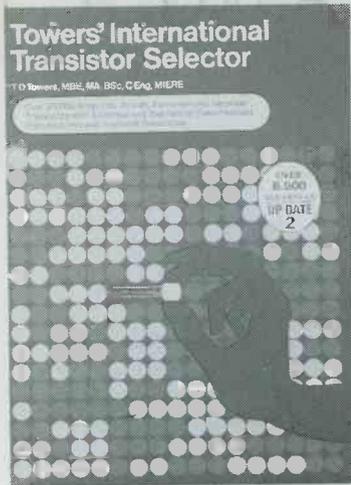
## TOWERS INTERNATIONAL TRANSISTOR SELECTOR (NEW REVISED EDITION)



This is dead! 

Would this replace it?




If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest!

In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price **£10.35 inc P&P**
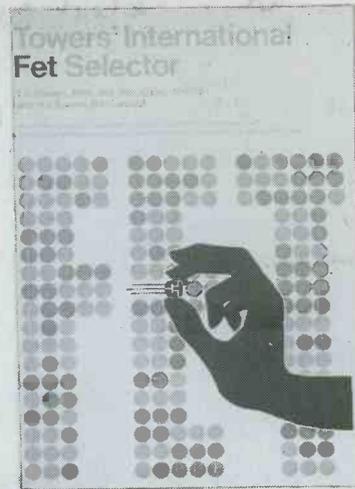
## TOWERS INTERNATIONAL FET SELECTOR (JUST PUBLISHED)



If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price **£4.00 inc P&P**

(Please allow 21 days for delivery)

**Tower's International Transistor Selector** by **T. D. Towers**  
MBE, MA, BSc, C Eng, MIERE  
**£10.35**  
inc. post and packing

To:—DATA PUBLICATIONS LTD.  
57 MAIDA VALE  
LONDON W9 1SN

Please send me . . . . . copy/copies  
to the address shown below

NAME . . . . .

ADDRESS . . . . .

(Block capitals)

**Tower's International FET Selector** by **T. D. TOWERS**  
MBE, MA, BSc, C Eng, MIERE  
**£4.00**  
inc. post and packing

To:—DATA PUBLICATIONS LTD.  
57 MAIDA VALE  
LONDON W9 1SN

Please send me . . . . . copy/copies  
to the address shown below

NAME . . . . .

ADDRESS . . . . .

(Block capitals)

# RADIO & ELECTRONICS CONSTRUCTOR

JUNE 1980  
Volume 33 No. 10

Published Monthly

First published in 1947

Incorporating The Radio  
Amateur

Editorial and Advertising Offices  
57 MAIDA VALE LONDON W9 1SN

Telephone  
01-286 6141

Telegrams  
Databux, London

© Data Publications Ltd., 1980. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

**Annual Subscription:** £8.50, Eire and Overseas £9.50 (U.S.A. and Canada \$20.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

**Technical Queries.** We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

**Correspondence** should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

**Opinions** expressed by contributors are not necessarily those of the Editor or proprietors.

**Production** – Web Offset.

ROBUST BURGLAR ALARM – Suggested Circuit by G. A. French	588
STOP-GO CONTINUITY TESTER by D. Snaith	591
NEWS AND COMMENT	592
WINE TRAP WATCHER – Electronic watcher monitors wine trap bubbles and indicates the end of fermentation – by Owen Bishop	594
CALCULATORS AND PARALLEL – R by R. J. Caborn	597
MODULATED ALARM GENERATOR by I. M. Attrill	598
PASSIVE LOGIC PROBE by M. V. Hastings	601
DUSK-TO-DAWN SWITCH – Turns light on at dusk, off at dawn – by R. A. Penfold	604
THREE VOLTAGE MULTIPLIERS by William Steward	609
CONSTRUCTOR'S CROSSWORD – Compiled by J. R. Davies	611
WIEN BRIDGE A.F. SIGNAL GENERATOR – 15Hz to 25kHz in 3 switched ranges – by A. P. Roberts	612
SHORT WAVE NEWS – For DX Listeners – by Frank A. Baldwin	618
THE SHUDDERY PICTURE – In Your Workshop	620
TRADE NEWS	626
IN NEXT MONTH'S ISSUE	632
DIFFERENTIATION AND INTEGRATION Electronics Data No. 58	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.


THE JULY ISSUE  
WILL BE PUBLISHED  
MID JULY

# Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

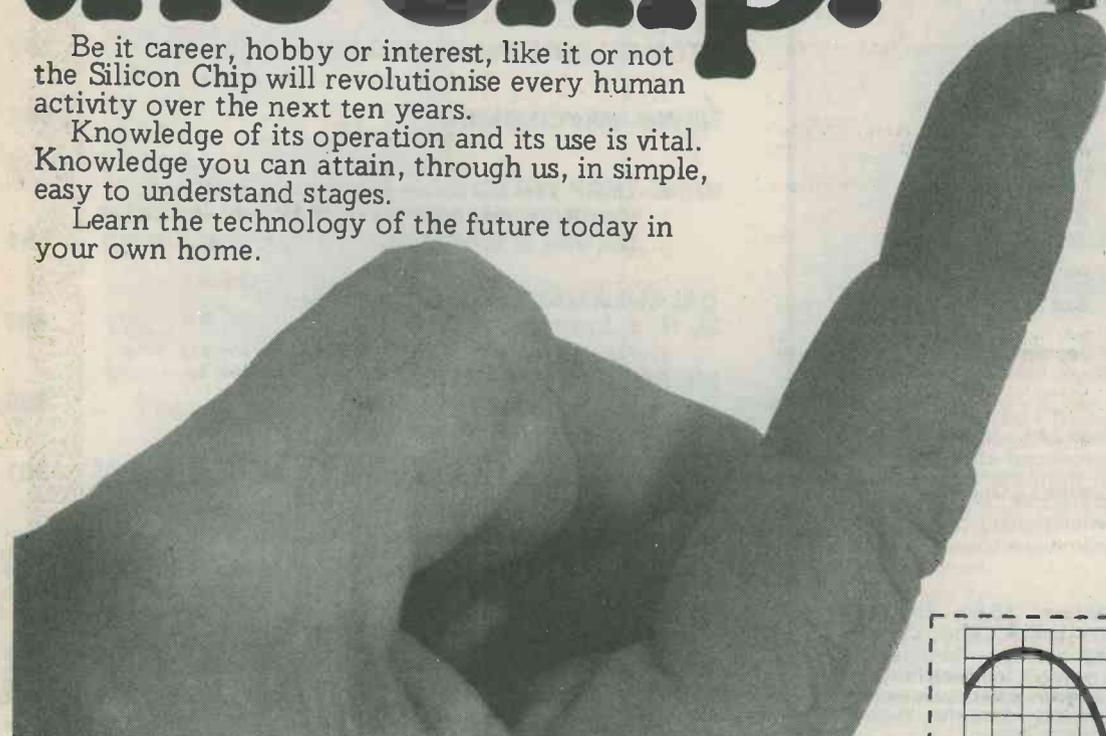Learn the technology of the future today in your own home.



## ELECTRONICS



Build your own oscilloscope

Learn to draw and understand circuits.

Carry out over 40 experiments.


## DIGITAL TECHNIQUES

From watches to sophisticated instrumentation, Digital Electronics adds scope to hobby or career.


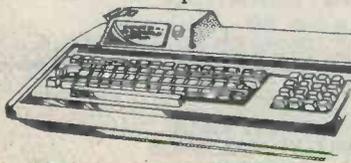
## COMPUTER TECHNOLOGY


Learn to operate and programme your own home computer.


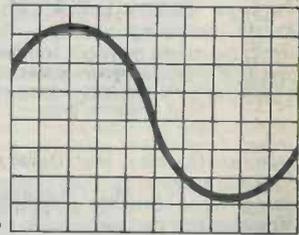
# FREE BROCHURES



No previous knowledge is necessary.  
— Just clip the coupon for a brochure



## TUTORCOURSE ELECTRONICS

Please rush me details of your ELECTRONICS COURSE

Name

Address

RER/6

Block Caps. Please

Post now, without obligation to:

**British National Radio & Electronics School.**

P.O. Box 156, Jersey, Channel Isles

ALL PRICES INCLUDE V.A.T. AND P. & P.

SAME DAY SERVICE

QUALITY COMPONENTS

<b>L.E.D.s</b>		Push to make Switches	16p
Red .2	12p	Push to break Switches	22p
Green .2	21p	DPDT Slide Switches, Fixing centres 29mm	15p
Yellow .2	21p	Sub min DPDT Slide Switches	17p
Red .125	12p	Standard DPDT Toggle Switch with chrome dolly	49p
Green .125	21p	Sub min toggle switches, Fixing hole dia: 5mm	
Yellow .125	21p	SPST Toggle	68p
uA 741 8 pin	26p	SPDT Toggle	72p
NE555	31p	DPDT Toggle	80p
<b>Sub-min Transformers</b>		Rotary Switches	
6-0-6v 100mA	£1.15	1p 12w, 2p 6w, 3p 4w, 4p 3w	All 48p each
9-0-9v 75mA	£1.15	2.5 Jack Plugs Plastic body	10p
12-0-12v 100mA	£1.15	3.5 Jack Plugs Plastic body	11p
Chassis mounting fuse holders.		2.5 Open framed Jack Sockets	10p
20mm	8p	3.5 Open framed Jack Sockets	10p
5 pin 180 Din Plugs	13p	<b>Sub-min Presets</b>	
5 pin 180 Din Sockets. Standard metal type	13p	Horiz: 100 ohms, 220 ohms, 470 ohms, 1k, 1k5, 2k2, 4k7, 10k, 22k, 47k, 100k	
Printed.Circuit Board bonded paper, copper cald single sided.		Vert: 470 ohms, 2k2, 4k7.	
Approx. 2 x 8½	15p	All price 7p each	
Approx. 4½ x 9	31p	<b>Heatsinks</b>	
Etch Resist Pen	£1.07	4 inch long, for use on printed circuit boards and suitable for external mounting on equipment. Undrilled. Black anodised finish.	
PP3 Battery Clips	7p	Price:	85p
PP9 Battery Clips	16p	Cast aluminium, approx: 4½ x 2 x 2, drilled to take one TO3 transistor in the centre. Sprayed Black.	
Crocodile clips with vinyl insulation sleeves, in pairs Red and Black	17p	Price:	80p
4mm Banana Plugs Red or Black	12p	Cast aluminium, approx: 3½ x 5½ x 1½, takes two flat plastic type transistors on rear side of fins. Ideal for mounting at the edge of P.C. boards and on the rear of chassis. Sprayed Black.	
4mm Banana Sockets Red or Black	14p	Price:	85p
4mm Terminal Posts Red or Black	26p	Black plastic self adhesive insulation tape. ¾" wide 18m long.	
<b>13 amp Plugs</b>		Price:	42p
White plastic plug fitted with 13 amp fuse and cable grip.		14mm square self adhesive feet, brown or white. Set of four	16p
Price:	48p	<b>Low profile d.i.l. I.C. Sockets</b>	
White unbreakable plug with a rubber outer cover and hard plastic insert. Fitted with 13 amp fuse and cable grip.		8 pin	10p
Price:	62p	14 pin	12p
High Quality Desolder tools	£4.75	16 pin	13p
Mains tester screwdriver with neon indicator in handle. Tests 100 to 500 volts.		18 pin	15p
Price:	52p	40 pin	34p
Seven section Telescopic Aerials, Chrome finish, with swivel. Collar fixing.	82p	20 pin	16p
2 pole 2 way Latchswitches	10p	22 pin	18p
40mm dia. 8 ohms .2 watts Speakers.		24 pin	19p
Price:	75p	28 pin	24p
Extra Flex. Flexible wire ideal for test leads. Max. current 6A. Black or Red.		Mixed pack ¼ watt Resistors, E12 series 10 off each value.	
Price:	13p per metre.	Price:	
Magnetic earpiece, 8 ohm impedance, with 1m lead and 3.5mm jack plug	15p	Mixed Pack ¼ and ½ watt Resistors approx. 500 items.	
		Price:	
		£3.50	
		Mixed pack ceramic tube, ceramic disc, polystyrene, silver mica, ceramic plate, mixed dielectric, etc. ½ kg.	
		Price:	
		£1.50	
		Pack of 50 mixed rubber grommets	
		42p	
		6mm dia. Wire Neons 90 volts	
		6p	
		Two pin Loud speaker plugs	
		12p	
		Two pin Loud speaker sockets, plastic	
		10p	
		57mm dia. 8 ohms .1 watts Speakers.	
		Price:	
		75p	
		Three core, blue, brown, green/yellow P.V.C. insulated 13/0.2mm copper conductors sheathed overall in White P.V.C. Nominal O.D. .9mm. Nominal current rating: 2.5 amps.	
		Price:	
		20p per metre	
		Crystal earpiece, with 1m lead and 3.5mm jack plug	
		40p	

Please add 50p handling charge to all orders  
 OUR NEW CATALOGUE IS NOW AVAILABLE.  
 SEND 22p FOR YOUR COPY

HARRISON BROS. P.O. Box 55, Westcliff-on-Sea  
 Essex SS07LQ

Telephone: Southend-on-Sea (0702) 32338

TRADE ENQUIRIES WELCOME

### MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3rpm Motors 32p. 6 volt standard cassette motors new £1.20. 8 track 12V Replacement Motors 55p. Cassette Motors 5-8VDC ex. equip. 70p. Geared Mains Motors (240V) 2.5 rpm 75p. 115VAC 4rpm Geared Motors 95p.

### SEMICONDUCTORS

LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. TBA800 50p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. AD161/2 70p. ZN414 75p. BD238 28p. BD438 28p. IN4005 10 for 35p. TIL305 alpha numeric displays £2.50. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p.

### PROJECT BOXES


Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

### MOTOROLA PIEZO CERAMIC TWEETERS

No crossover required



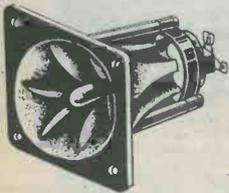2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65



3.5" Super Horn (flush mounting), maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8-2.8kHz, £4.50

### MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

### MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

### JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

### TRANSFORMERS

All 240VAC Primary (post-age per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).

### TRIAC/XENON PULSE TRANSFORMERS

1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

### MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95 CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT Crystal replacement 35 x 10mm 40p. GRUNDIG electric inserts with FET pre-amp, 3-6VDC operation £1.00.


### LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

### RIBBON CABLE

8 way single strand miniature 22p per metre.

### SPECIAL OFFER TAPE HEAD DEMAGNETIZER

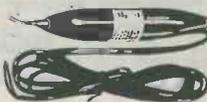

240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply, £14.95 and £1.20 p&p (CCT supplied).

### MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50



20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £9.75.

### MURATA MA401

40kHz Transducers. Rec/Sender £3.50 pair.

### TELEPHONE PICK UP COIL

Sucker type with lead and 3.5mm plug 62p.

### RELAYS

Plastic Encap. Reed Relay, 0.1 matrix. 1k  $\Omega$  coil, 9-12VDC normally open, 35p. Miniature encapsulated reed relay 0.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. Min. sealed relay, P.C. mounting, 6-9vdc operation changeover 3 amp contacts, new 85p. Metal Cased Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each. Magnets 1/2" long 1/8" thick with fixing hole, 10 for 40p.

Dalo 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.

### TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.A.E. for illustrated lists

### TMK500 MULTIMETER



TMK500 30,000 ohms per volt. 1KV AC/DC., D.C. Current to 12 amps. Resistance to 60 meg in 4 ranges, mirror scale, with built in buzzer for continuity testing £20.95

### YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

### CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

### POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 400mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

### AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double In line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

### BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 63p. Carters 12 volt Minimate Alarm sirens £7.65p. 12VDC siren, all metal rotary type, high pitched wail, £6.25.

### TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95

Antex Model X25 25 watt soldering irons, 240VAC £3.95

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each. Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

### SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p. DPDT (8 x 7 x 7mm) 55p. DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

G.P.O. Telephone handsets £1.95. Electrolytic Caps, can type, 2,200mfd and 2,200mfd 50VDC 35p each.

### RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

### TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

# PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST

# GREENWELD

443G Milbrook Road Southampton SO1 0HX

All prices include VAT at 15% — Just add 40p post

## BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

SAVE ON TIME — No delays in waiting for parts to come or shops to open!

SAVE ON MONEY — Bulk buying means lowest prices — just compare with others!

HAVE THE RIGHT PART — No guesswork or substitution necessary!

All packs contain Full Spec. Brand New, Marked Devices — Sent by return of post. V.A.T. Inclusive Prices.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210 **£3.69**

K002 Extended range, 22pF to 0.1uF, 330 values **£5.53**

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47uF, 110 altogether for **£5.07**

K004 Mylar capacitors, min. 100V type 10 each all values from 1000pF to 10,000pF. Total 130 for **£4.05**

K005 Polystyrene capacitors, 10 each value from 10pF to 10,000pF, E12 series 5% 160V. Total 370 for **£12.67**

K007 Electrolytic capacitors 25V working, small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 10uF. Total 70 for **£3.59**

K008 Extended range, as above, also including 220, 470 and 1000uF. Total 100 for **£6.05**

K021 Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£6.15**

K022 Extended range, total 850 resistors from 1R to 10M **£8.50**

K041 Zener diodes, 400mW 5% BZY88 etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for **£16.37**

K042 As above but 5 of each value **£9.31**

## £1 BARGAIN PACKS

K101—16 BC239B N.P.N. Low Noise **£1.00**

K102—15 BC349B N.P.N. Low Noise **£1.00**

K103—10 BC546B N.P.N. 80 Volt **£1.00**

K104—18 BC182B N.P.N. 60 Volt **£1.00**

K105—50 IN4148 Silicon Diode **£1.00**

K106—18 BC184L N.P.N. Low Noise **£1.00**

K107—18 BC213L P.N.P. General Purpose **£1.00**

K108—8 2N5060 30N .8A SCR **£1.00**

K109—15 BC114 N.P.N. Low Noise **£1.00**

K114—15 XK6116 (BF241) N.P.N. 200MHz **£1.00**

K115—18 SP1218 (2N3702) P.N.P. Gen. Purpose **£1.00**

K117—10 BF450 P.N.P. T.V. IF Amp. **£1.00**

K118—16 MF4101 N.P.N. 60V Low Noise **£1.00**

K124—50 .02uF Disc Ceramics **£1.00**

K125—200 1k 5% 1W. CF Resistors **£1.00**

## VU METERS

Voo2 Twin type, 2 meters 40 x 40mm and driver board, supplied with circuit and connexion data. **£3.50**

Voo3 New type, just in. Twin type moulded in one piece, 80 x 40mm (No driver board but suitable circuit supplied) **£2.50**

## INVERTER

Prepare for the Power Cuts! Ready built inverter, 24V DC 290 x 55 x 37mm in, will power 6 x 8W fluorescent tubes. Circuit supplied. Only **£2.90**

## THE NEW 1980 GREENWELD CATALOGUE

### FEATURES INCLUDE:

- 60p Discount Vouchers
- Quantity prices for bulk buyers
- Bargain List Supplement
- Reply Paid Envelope
- Priority Order Form
- VAT inclusive prices

PRICE 40p plus 20p POST

## VERO OFF CUTS

Packs of 100 sq ins of good size pieces about 4 x 3" in the following types:

K541 0.1" copper clad **£1.80**  
K544 0.1" plain **£1.60**  
Also pieces 2 1/2 x 1" — 10/£1.20 100/£9  
17 x 3 1/2" x 0.1" sheets — 10/£16.50

Large range of Standard Veroboard and boxes/cases in stock. Details in catalogue. 45p

SCOOP! Verobox type 2522, unused but has 3 1/2" holes in one end and 1 1/4" hole the other, so instead of £3.96, we are selling these at **£1.85**

## COMPONENT TRAY

Attractive yellow tray 285 x 165 x 42mm with clear hinged lid and moveable compartments. Up to 15 can be made from dividers supplied. As an added bonus, a selection of new surplus components are included, all for the special low price of **£3.95**.

## SCR PANEL & REED PANEL

Z525 contains 11 800mA 60V 2N5061 SCR's, 11 6V8 zeners, 11 IN4004 diodes plus R's, C's, etc. Only **£1.00**  
Z527 2 x 6V reed relays, 6 x 2S030 or 2S230 6 x 400V recls, plus R's only 50p

## BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer all metal construction. 50mm dia x 20mm 70p  
Z402 Miniature type 6, 9 or 12V buzzer, only 22 x 15 x 16mm. Very neat 53p  
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only **£1**  
W890 DIL reed relay — SPCO 2.4 V — 10V 200R coil. Only **£2.20**  
W892 Heavy duty 12V relay, ideal for car use — single 15A make contact. Coil 25R 85p

## CLOCK CASE BARGAIN

Z472 Oval format, overall size 130 x 68 x 87mm deep, with built in stand. Rear panel drilled to accept 4 switches and alarm 60p

## 74 SERIES PACK

Selection of boards containing many different 74 series IC's for **£1**; 50 for **£2.20**; 100 for **£4**.

## PC ETCHING KIT MK III

Now contains 100 sq. ins. copper clad board, 1lb Ferric Chloride, an etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions **£4.95**

## POWER DARLINGTON PAIR

Plastic version (TOP66 case) transistors type BD695A/BD696A. Just look at the spec!! 70W 8A 45V — Hfe 750 at 4A!! Special low price — **£1.20** per pair.

## TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly Low, Low Price!!

Almost all are marked with type number — almost all are full spec devices, some have bent leads. Over 30 different types have been found by us, including BC184/212/238/307/328; BF196/7; ZTX107/8/9/342/450/550, etc. Only available as a mixed pack at **£3/100; £7/250; £25/1000**.

# ELECTROVALUE

SUPPLIERS OF COMPONENTS THAT COUNT



**SIEMENS**  
SEMI-CONDUCTOR  
CAPACITORS  
FERRITES

**NASCOM**  
MICRO COMPUTERS  
AND  
ANCILLARIES

**VERO**  
BOARDS  
CASES &  
KITS

**ISKRA**  
RESISTORS

**RADIOHM**  
POTENTIOMETERS  
OPTO-ELECTRONICS

**BREADBOARDS**

**SOLDER TOOLS**

**SWITCHES**

**CATALOGUE 10**

## OUR MINI-SELECTION POINTS THE WAY!

### EXAMPLE ONE — SOLDERING IRONS

Aryx 50	£12.08 net	Antex x 25	£4.83 net
Isotip	£25.90 net	Desolder tool SR3A	£7.48 net
Antex C	£4.83 net	500 gm reel solder	£6.81 net

### EXAMPLE TWO — PRINTED CIRCUIT MATERIALS

PCB's 300 x 150 mm		Etch Resist Pan	£1.14
SRBP S/S £1.38	D/S £1.73	Breadboards	
F/Glass S/S £1.96	D/S £2.13	Bimboard	£9.23
Positive resist 75cc	£1.67	Eurobreadboard	£6.56 net
Ferric Chloride 500 g	£3.45	T-DeC	£5.18

### EXAMPLE THREE — SWITCHES

Chrome toggle		13A time switch adaptors	
Std. SPDT 65p	DPDT 89p	Smiths TS100	£14.43 net
Min. SPDT 66p	DPDT 92p	Wavechange, Lorlin, 1P12W, 2P6W, 3P4W, 4P3W	46p each

### EXAMPLE FOUR — CAPACITORS BY SIEMENS

Polyester 7.5mm PCM  
1, 1.5, 2.2, 3.3, 4.7uF, 10, 15, 22, 33, 42uF 8p each, .1uF 12p, .15uF 15p, 22uF 18p, .33uF 21p, .47uF 27p, .68uF 34p, 10mm PCM 1uF 37p.  
Electrolytic, axial, (uF/V)  
1/40 24p, 1/100 15p, 2.2/25 24p, 2.2/63 15p, 4.7/16 24p, 4.7/40 15p, 10/25 15p, 10/40 18p, 22/25 18p, 22/40 18p, 22/63 19p, 47/10 18p, 47/25 18p, 47/40 16p, 47/63 20p, up to 1000/16V 36p, then 1000/25V 49p to 47/16 65p.  
Also full supporting ranges of other ceramic, plastic and electrolytic caps.

### EXAMPLE FIVE — POTENTIOMETERS BY RADIOHM

Single gang lin or log	34p	(Twin types stereo matched)	
Twin gang lin or log	93p	Slider knobs	10p each.
Mono slider lin or log	83p	Presets lin, horiz, or vert at	10p
Twin slider lin or log	136p		

### EXAMPLE SIX — RESISTORS

1/2, 1/4, 1/8, 1/16 2.3p 1W 6p  
Wirewound from 21p

## AND AS FOR SEMI CONDUCTORS . . .




1N914	6p	40673	99p	MU481	£1.70	T1P41A	69p
1N4007	9p	AC128	36p	MJ491	£1.88	T1P41C	74p
1N4148	5p	AC176	67p	MJ2955	97p	T1P42A	69p
1N5402	19p	AD136	£4.25	MJE2955	£1.13	T1P42C	74p
2N1599	£1.01	AD149	£1.01	MJE3055	£1.00	T1P2955	69p
2N2369A	24p	AD161	40p	MPSA12	42p	T1P3055	69p
2N3055	81p	AD162	52p	MPSA63	44p	T1S43	40p
2N3702-11	11p	AF127	43p	OA47	14p	W02	35p
2N4443	£1.78	AL102	£1.84	OA90	8p	2T x 107, 9	14p
2N4444	£2.28	BA379	29p	OA91	8p	2T x 300	14p
2N4991	98p	BF103	43p	OA202	16p	62T x 500	16p
2N5457-9	45p	BB104	70p	OC29	£1.23		This is
40HF40	£2.25	BB105	37p	OC36	£1.18		but a fraction
40361	49p	C106D1	52p	T2800D	£1.20		of what we
40362	49p	E1110	92p	T1P31A	52p		carry.
40636	£1.69	E1210	97p	T1P32A	52p		

**INFORMATION** — To show everything we supply would take about seven pages of closely packed type in this journal — the range is enormous including not only opto devices and very advanced sophisticated items, but all the everyday things you need as well down to nuts and washers! IT'S ALL IN CATALOGUE 10 — OUR 120 PAGE CATALOGUE FREE FOR THE ASKING. PRICES AND V.A.T. — All prices quoted here include V.A.T. for U.K. orders. Overseas buyers deduct 13% when ordering.

**POSTAGE** — For orders up to £5.57 value (U.K.) please add 40p for p/p. If orders sent post free in U.K. Overseas orders sent at cost (Min. 40p).

**DISCOUNTS** — 5% allowed on non-net items if order value exceeds £11.50, 10% if order value exceeds £29. Quantity discount prices on most components.

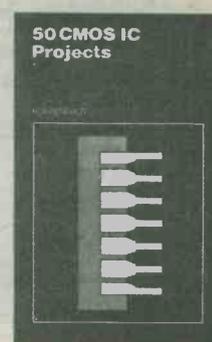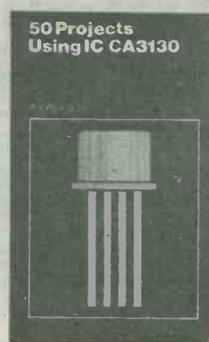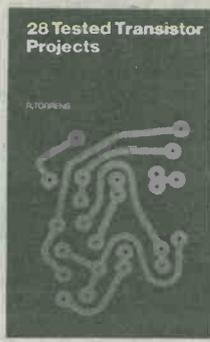**ELECTROVALUE LTD.** Dept. 28(A), St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 Telex 264475. Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.



# DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

18. 50 Projects Using IC CA3130	£1.25	40. Projects in Opto-Electronics	£1.25
19. 50 CMOS IC Projects	£1.25	41. Radio Circuits Using IC's	£1.35
20. A Practical Introduction to Digital IC's	95p	42. Mobile Discotheque Handbook	£1.35
22. Beginners Guide to Building Electronic Projects	£1.25	43. Electronic Projects for Beginners	£1.35
23. Essential Theory for the Electronics Hobbyist	£1.25	44. Popular Electronic Projects	£1.45
26. 52 Projects Using IC741	95p	45. IC LM3900 Projects	£1.35
28. Two Transistor Electronic Projects	85p	46. Electronic Music and Creative Tape Recording	£1.25
29. How to Build Your Own Metal and Treasure Locators	£1.00	47. Practical Electronic Calculations and Formulae	£2.25
30. Electronic Calculator Users Handbook	95p	48. Radio Stations Guide	£1.45
31. Practical Repair and Renovation of Colour TVs	£1.25	49. Electronic Security Devices	£1.45
32. Handbook of IC Audio Preamplifier and Power Amplifier Construction	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	51. 50 Circuits Using 7400 Series IC's	£1.45
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	52. Second Book of CMOS IC Projects	£1.50
35. Fun and Games with your Electronic Calculator	75p	53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
36. 50 (FET) Field Effect Transistor Projects	£1.25	54. Beginners Guide to Digital Techniques	95p
37. 50 Simple L.E.D. Circuits	75p	55. 28 Tested Transistor Projects	£1.25
38. How to Make Walkie-Talkies	£1.25	56. Digital IC Equivalents and Pin Connections	£2.50
39. IC 555 Projects	£1.75	57. Linear IC Equivalents and Pin Connections	£2.75

POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days . . . . . copy/copies

Book Nos: . . . . .

. . . . .

. . . . .

I enclose Postal Order/Cheque for £ . . . . .

Name . . . . .


Address . . . . .

. . . . .

(Block Letters Please)

*(We regret this offer is only available to readers in the U.K.)*

## Complete Audio/Tuner Kits

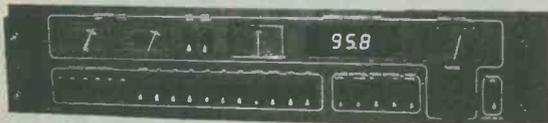

### Mk III FM Tuner series

Carriage for Mk III tuner £3 inc

The Mark III series FM tuner has been updated, and now includes a centre zero tuning meter as standard. The instruction manual has been meticulously revised, enabling easy assembly by constructors of various levels of experience - a preview copy may be purchased for £1.00.

Mark III A series 'Reference series' tuner modules .....£171.35 inc.  
Mark III B series 'Hyperfi' modules, with switched IF BW, pilot cancel decoder .....£198.95 inc.

A matching synthesiser unit will be made available later this year, and can be retrofitted to either version. All versions include digital frequency readout/clock, VU deviation meters, 6 preset stations, 10 turn pot manual tuning, toroidal PSU, output level adjustment, 110/240v AC input. Full alignment service available.

### Power Amplifier

Style and performance - with a real 'belt and braces' PSU design.

After a couple of preview comments, it seems that many of you are waiting to hear about the matching HMOSEF power amplifier for the Mk III tuner. Well, it's out at last - complete with twin toroidal PSUs for comfortable 80W RMS per channel, over 100W peak, but limited by thermal shutdown of the HMOS. 10W-100W log LED output peak indicator, DC offset protection and switch-on pause relay. AC or DC input coupling, direct or relay protected output terminals. The works. Only one version of this item: Complete kit .....£178.25 inc. Carr. £5.

### Preamplifier

More features and facilities, thanks to DC switching and control design


Previewing the most comprehensive audio preamplifier yet..... DC switching of 7 inputs, plus two tape in/out, 2 low pass, 2 high pass active filters, genuine volume related loudness, 1dB channel matching, with DC volume, balance, bass and treble controls. Suitable for bus/remote control, tape dubbing, switched monitor etc. 80dB S/N, THD >75dB or better. Pluggable PU equalization boards, tone control override. Price for complete unit about £149 ex VAT.

## Semiconductors

### Radio/Communications ICs

FOR COMPLETE LISTINGS - SEE OUR NEW PRICELIST


CA3089E	2.11	HA1197	1.61	SD6000	4.31
CA3189E	2.53	CA3123E	1.61	TD4420	2.59
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38
HA11225	2.47	TBA651	2.53	MC1350P	1.38
HA12412	2.81	TDA1090	3.51	KB4412	2.24
KB4420	1.95	TDA1220	1.61	KB4413	2.24
TBA120S	1.15	TDA1083	2.24	KB4417	2.53
KB4406	0.80	TDA1062	2.24	MC3357P	3.16

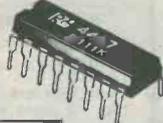

### VARICAP DIODES.....

A section from our PL:

BA102	0.35	16:1 ratio AM tuning	
BB204	0.41	KV1215 9v triple	2.93
BB105	0.41	KV1211 9v dual	2.01
BB109	0.31	KV1225 25v triple	3.16
MVAM2	1.93	BB212 9v dual	2.25

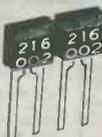

### POWER MOSFETS

100W PA's made simple

Since pioneering the 100W complementary MOSFET technique - Hitachi have developed a range of output devices and drivers that ought to revolutionise opinions and attitudes towards the design of all LF amplification systems. We have a new 48 page application note (£1.50 inc) and complete sets of parts, modules and now the new complete PA system (see above).  
25K133 120v N-ch 100W MOSFET £6.33 2S/48 Pch complement £6.33  
25K135 160v N-ch 100W MOSFET £7.29 2S/50 Pch complement £7.39  
PA101B Kit for 100W MOSFET PA less Heatsink £16.10. (£23 inc heatsink/bkt)

### ULTRA LOW NOISE PU PREAMPLIFIER

The HA12017 is the last word in PU preamps, and general low noise audio design. It is an SIL IC, with 86dB S/N in RIAA configuration, 10v RMS output capability, 0.002% typ THD at 10v RMS output (imagine the overload margin !!). It comfortably supercedes discrete circuit designs in terms of price/performance, and takes the art beyond the TDA1042's capabilities. (Replaces HA1457) £1.80 each - or an RIAA applications PCB with two ICs for £5.75. Complete with Rs&Cs £9.95.

### Radio Control ICs

We have various RC ICs, including NE544 NE5044, and two new ones from OKI

KB4445 - 4 channel dig.prop. FM TX IC. 30mW out (amplifiable) -£2.30 inc  
KB4446 - 4/5 ch. dig. prop FM RX IC. Suits KB4445 or RCME syst. £2.65.  
KB4445/6 pair: £4.75. New 8 page data sheet 35p + SAE. More RC ICs in list

### CMOS, LPSNTTL, TTL, MPU:

Listings in the new pricelist.

Most CMOS is available in low volume - also LPSN. Standard lines and TTL OK.

Things like ICM7216B, ICL8038, 8080A, 6800P, 2708, NE555, NE556, etc

### Coming Soon.....

Contain yourselves, RF fans! Not yet ready for a full launch until autumn, but previewed here:-

### SSB transceiver system : 10kHz to 1000MHz !!

A modular VLF to UHF SSB TX/RX system at last. With the correct first mixer, the basic PCB covers 10kHz to 1000MHz - using LO fed from ext. source (Our 2 IC Mullard synth for instance) and RF PA for TX. Op. 0.2uV basic sensitivity in HF. Typ cost for HF synth SSB RX will be less than £200. Add an RF PA for full TRX for another £50. See one in our foyer, and marvel.

CALL OURS 0476 551111 - all times by 11pm  
PHONE: SHOW US IN 10000 VAT  
POST-PACKAGE CHARGE NOW 35p

Please send an SAE with all enquiries.  
Phone orders by ACCESS - but minimum £5  
Callers welcome

**ambit**  
INTERNATIONAL

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

## Radio/Audio/Communications Modules

### LW-MW-SW-SW DC tuned and switched

91072- All switching of bands by a single pin to gnd. Varicap tuned, with LO output for synth. MW/LW version or MW/LW plus 1 or 2 SW bands MW/LW: £15.58 +1SW £16.73



### VHF Tunerheads

Europe's largest stock range for broadcast and communications. Probably also the world's - details in the catalogues and PL. Specials are also supplied in the region 30-220MHz.

### Pilot Cancel PLL Stereo decoders

Again, Europe's widest range of stereo decoders including pilot cancel PLL types. The pic shows the 944378 - pilot cancel including post decoder 26/38kHz filtering and muting preamp output

944378-2 £26.45



### Switched bandwidth FM IF strips

Broadcast FM IF strips for all occasions, including the new 911225 - with diode switched narrow filter option, ultra linear phase ceramic filters, 84dB S/N, and 0.04% THD (40kHz deviation). Plus usual things like AGC, AFC, dev. mute, level meter drive. £23.95 (supplied in screen can with 0.1 edge connection system) Also the 7230 hyperfi series - as the 911225, but with slope controlled AFC that operates in conjunction with signal level - and an extra IF amp stage for DXing.

### Various digital frequency displays

The World's largest range of receiver DFM's is now joined by the DFM7 (shown) - and L shaped version of the DFM3 with remote display mount connector possibility. 1kHz SW resolution with 455kHz or 10.7MHz offsets, 100Hz res up to 3.9999MHz, and VHF to 299.9 MHz in 10kHz steps : £41.75



## Components

### Crystal Filters

Most popular types are available ex-stock, and in quantity.

10.7MHz	25kHz Channel spacing 8pole	£16.67
	12kHz	£17.82
	2.4kHz SSB	£19.78
	Monolithic dual roofing filter	£2.30
34.5MHz	1.3dB loss, 80dB stopband HF first filter in synth. RX	£36.80
RC XTALS	FM pairs (no splits)	£3.74
	AM pairs	£3.57
USB/LSB	Xtals for 10.7SSB filter	£2.88 ea



### Piezo Sounders

The most efficient warning sounders yet

The latest thing in electro-acoustic efficiency. 1mA of drive from CMOS will give an SPL of 83dB - 10v RMS drive from CMOS uses 3mA for 100dB SPL at 4.8kHz (88dB at 1.65kHz) The data sheets shows various drive circuits, and give full specifications with regard to broadband responses and power consumption etc. 1 off 44p inc. 100 off 2875p (25p ex vat)



### Keyboard switches and caps

From the world's most widely used switch manufacturers - ALPS - come the biggest and best range of keyswitches, and data entry keyboard switches. The SCM81101 is shown here, with the KT5 2-part cap (with clear top, to enable easy fitting of your chosen legend. Other types are available with built in LED, 90° mounting etc.  
SCM81101 : 17p, KT5 : 16p - or 29p/pair



### LCD CLOCKS

Clocks use 7.5v at 15uA only - DVM 9v/1mA

### LCD DVM

CM161: 7mm LCD 12/24hr, alarms etc £11.44 each  
CM172: 13mm, 12hr, alarms, timer etc £14.32 each  
CM174: 13mm, 12hr, min/sec stopwatch £14.32 ea  
DVM 176: ICM7106 based LCD 3 1/2 digit £22.36 each



## WHAT'S NEW at AMBIT

NEW PRICELIST/SHORTFORM:- 28 pages, FOC with A5 SAE pse

Bigger print than our recent one page list - and vastly extended

If you still need convincing to invest £1.60 in the cats, be mean and get this first.

POWER MOSFET APPLICATIONS HANDBOOK by HITACHI

£1.50 each - or free with pairs of HMOS and the PA101B

Everything you should know about HMOSEF devices theory and applications.

**TRANSISTORS**

AC126	16p	BD238	28p
AC127	16p	BD239C	29p
AC128	5p	BD245	44p
AC153	11p	BD255	35p
AC176	11p	BD437	35p
ACV20	30p	BD438	28p
ACV21	20p	BD678 Pwr. Dwl.	50p
ACV28	22p	BDX77	87p
AD161/162		BDY20	86p
match pair	70p	BF115	11p
AF116	21p	BF167	18p
AF119	35p	BF173	18p
AF124	27p	BF178	23p
AF126	27p	BF179	23p
AF127	27p	BF180	12p
AF139	35p	BF181	8p
AF178	35p	BF182	18p
AF180	35p	BF183	18p
AF181	33p	BF184	18p
AF239	35p	BF185	18p
ASV60	35p	BF194/A	5p
ASV63	4p	BF195/C/D	5p
ASV73	35p	BF196	5p
ASZ21		BF198	5p
AU110	£1.43	BF200	13p
AU113	£1.18	BF224	4p
AU110	70p	BF244C	7p
BC107/A/B	6p	BF245	6p
BC108/A/B/C	6p	BF256	6p
BC109/B/C	6p	BF256LB/LC	6p
BC125B	3p	BF257	20p
BC140	15p	BF262	29p
BC141	11p	BF263	29p
BC147/A/B/C	5p	BF274	8p
BC148/A/C	5p	BF324	31p
BC149/A/B/C/S	5p	BF336	16p
BC154	7p	BF355	15p
BC157/A	5p	BF394B	3p
BC158/A/B	5p	BF451	6p
BC159/B/C	5p	BF494	10p
BC171B	8p	BF615	27p
BC172	6p	BF617	27p
BC172c	7p	BFQ35	15p
BC173	7p	BFQ37	15p
BC177A	14p	BFQ85	15p
BC178A/B/C	14p	BFQ85	15p
BC179B	14p	BFQ85	15p
BC182/AL	5p	BFQ85	15p
BC182L	3p	BFQ85	15p
BC183/AL/LC/B	3p	BFS21 FET pair	£3
BC184L	5p	BFS28 Dual MOS FET	£3
BC186	21p	BFT30	15p
BC187	8p	BFT31	15p
BC204	11p	BFT39	15p
BC212L/B	5p	BFT41	15p
BC213L	5p	BFT60	6p
BC213LA	3p	BFT61	15p
BC213LB	4p	BFT70	15p
BC214B	5p	BFT71	15p
BC214L	3p	BFW10 FET	46p
BC237A	7p	BFW11 FET	46p
BC238	5p	BFW30	15p
BC238B/C	7p	BFW57	18p
BC239C	7p	BFW58	18p
BC251	3p	BFX12	23p
BC257B	7p	BFX29	15p
BC258B/C	7p	BFX30	16p
BC259C	7p	BFX37	16p
BC302	15p	BFX84	20p
BC304	15p	BFX85	14p
BC307	7p	BFX88	20p
BC308B/C	7p	BFX89	20p
BC309B	7p	BFX99	20p
BC327	5p	BFY52	15p
BC328	6p	BFY55	13p
BC338	5p	BFY75	15p
BC382L	7p	BFY90	20p
BC384B	7p	BLY10	23p
BC547/A/B	5p	BR101	20p
BC548/A/B/C	5p	BRY39	Prog. Uni. Junction 29p
BC549C	5p	BRY56	Junction 29p
BC556	5p	BSV64	36p
BC557/B	5p	BSV79	50p
BC558A	5p	BSV80	50p
BC559	5p	BSV81	50p
BC612L	4p	BSX19	15p
BCW71R	1p	BSX19	15p
BCX32	10p	BSX20	10p
BCX34	10p	BSX21	10p
BCX36	10p	BSX78	8p
BCY11	28p	BSY40	20p
BCY31	59p	BSY95A	10p
BCY56	10p	BU105	78p
BCY70	8p	BU105/04	78p
BCY71	8p	BU204	63p
BCY72	8p	BU208	90p
BCY79B	15p	DI693	£2.85
BCZ11	32p	GET102	46p
BD113	57p	GET111	46p
BD115	35p	GET120	30p
BD(BRC)116	46p	M103G MOSFET	30p
BD133	28p	MA393	25p
BD135	25p	MD7000	£2.25
BD136	25p	ME2	13p
BD137	28p	ME0412	14p
BD138	28p	MEB003	20p
BD137/B		MJ481 (BDY23)	23p
match pair	60p	MJE371	40p
BD139	17p	MJE2371	80p
BD140	26p	M N 15 Russian	25p
BD142	35p	M P 41/A Russian	25p
BD156	50p	MPF131 Dual	15p
BD201	64p	MOSFET	15p
BD202	86p	MPU131 Prog. Uni. J.	15p
BD203	86p	MRF502 Improved	15p
BD204	86p	BFY90	50p
BD232	52p	116A Russian	25p
BD233	20p		
BD234	13p		
BD235	35p		

2N2907/A	9p
2N2926	4p
2N3020	25p
2N3053	18p
2N3054	35p
2N3055RCA	68p
2N3133	24p
2N3283	25p
2N3418	15p
2N3553	56p
2N3583	18p
2N3614	75p
2N3645	3p
2N3703	3p
2N3704	4p
2N3707	3p
2N3711	3p
2N3714	54p
2N3794	14p
2N3799	18p
2N3823	25p
2N3904	3p
2N3906	18p
2N4000	15p
2N4026	5p
2N4031	15p
2N4062	4p
2N4285	17p
2N4891	30p
2N4896 40v 25w	36p
2N4900 80v 25w	36p
2N4918	15p
2N5147	15p
2N5248 FET	40p
2N5484	3p
2N6027/B.P.U.J.T.	3p
2N6124	24p
2N6385 PWR. DARL.	54p
2S701	18p
2SA12	42p
2SA50	36p
2SA80	36p
2SA83	36p
2SA141	36p
2SA142	36p
2SA234	50p
2SA235	50p
2SA354	38p
2SA360	34p
2SA367	56p
2SA518	38p
2SA634	80p
2S856	25p
2S876	25p
2S877	25p
2S8135	25p
2S8136	25p
2S8156	60p
2S8176	20p
2S8176	20p
2S8187	20p
2S8457	25p
2SD28	80p
2SD315D	80p
40235	50p
40250	36p

**ELECTROLYTICS** - Hundreds more in catalogue Value/Voltage

Tant Bead .033/35v 3p. .22, 47/35v 6p. .1, 1/35v, 47/6.3v 8p. .22/20v. 3.3/16v, 4.7/35v, 10/25v, 22/16v 9p. 10/3v 10p. 2.2/50v 11p. 3.3/35v 12p.

**Wire End**  
 63v 2.2, 31p. 4.7, 4p. 10, 33, 5p. 2.5 3p. 1.5, 22, 47 6p. 68, 100, 220 8p. 150 7p. 330 8p. 470 12p. 1000 29p. 25v 6, 6.4, 10, 12, 16, 22, 25, 30, 33, 40, 47, 50, 64 4p. 100, 150, 160, 330 6p. 220 7p. 250, 300, 470 8p. 680 11p. 1000 11p. 22/16, 3.3/50, 10/50 4p. 100/10, 47/16.5p. 100/16, 100/35, 220/16 6p. 470/6.3, 10/350, 470/16 8p. 1000/16 10p. 1500/6.3, 71p. 2200/10 20p. 4700/10 9p. 15/160 7p. CANS 250/300, 45p. 25,000/25 50p. 100/275 14p. 2000/100 82p. 1000/100 70p. 8 plus 8/450 9p. 10,000/16 36p. 2000/50 35p. 2000 plus 2000/50 40p. Full range in catalogue.

**CAPACITORS:** up to 500v: Ceramic up to 4700pF 2p. to .047 2p. to .15p. to 1mfd 8p. Silvermica up to 5000pF 5p. to .01 21p. Poly, etc up to 820pF 3p. to 0.1 2p. to .27 5p. to 4.7 5p. 59p. 68 11p. 047/630V 11p. .1, .22/900v 15p. .3/600v 4p. 97/160v 71p. 1mfd up to 250v 10p. 1.5/100 9p. 2.2mF up to 100v 14p. 4/16v 25p. 4.7/63 10p. 6.8/63, 25/50 19p. 10/100 30p. 8/20v 40p. CAN 1/350 12p. 8/660 vac £2. 3/660 vac £1.75. 5p. 6/450 vac 98p. Pulse Tube: 8-12kv, 10, 47, 56, 82, 100, 120, 300pF 2p each. Hundreds of others in Catalogue.

**TV MAINS DROPPERS**  
 5 assorted multiple units for . . . . . 45p

**16 Watt Power Amp. Module**  
 35v 1A power required, giving 16 watt RMS into 8 **£3.65**  
 RS neg. volt regulator 103, 306-099 (equiv. MPC900) 10A, 100 watt 4-30 volt. Adjustable short circuit protection. Sacrifice at 75p

**RESISTORS**  
 1/4 1/2 watt . . . . . 1p  
 1 watt . . . . . 1p  
 1 or 2% . . . . . 1p  
 Up to 15W w/wound 10p, 10 same value 75p

**Skeleton Presets**  
 Slider, horizontal or vertical standard 7p or submin 5p.

**THERMISTORS and V.D.R.'s**  
 CZ1/2/6/11/14, KR22, KT150, VA1005/6/8/10/1010/1033/4/7/8/9/1040/1053/5 /1066/7/1074/6/7/1082/6/1091/6/7/8/1100/3/8/8602. 6/7/8/1100/3/8/8602. Rod with spot blue/fawn/green. E239DDP120/218/224/338 / 340 / 350 / 352 / YF020 E220ZZ /02 KR100C . KR150 . E23 glass bead. YG150-S534 bead . KB13 . E299 DHP230 . 300K 2 Glass bead All 7p each

**RELAYS**  
 RS/Alma reed relay, 1K12v or 3k Ω 18-30v d.c. coil, normally open 12v d.p.c.o. heavy duty octal . . . . . £1 600 A 4 p/co min sealed 75p. Base 10p. D.I.L. 3.7-12V S.P. £1.00

**MOTOROLA EX-EQUIPMENT (unused) 2N3055 28p**

**MARKED FULL SPEC DIGITAL I.C.'s**  
 25 for £1 Branded - New

**HUGHES MICRO ELECTRONICS 400MW ZENER DIODES 200 IN CLEAR PLASTIC HINGED LID COMPONENT BOX £3.65**  
 3V, 3.6V, 3.9V, 4.3V, 4.7V, 11V or 13V

**RESISTOR PACKS**  
 10 for 4p 5K6 1w 100 for 40p 100K 1w 1K8 1w 1M8 1w 2M7 1w 10 for 9p 1K 1/2w 3K9 1w 100K 1/2w 2M2 1/2w 3M3 2w 1M5 1w 200 for 80p 1w 5% Carbon film 100K, 9K1, 1K2, 47K 1/2w 5% Carbon Film 100 for 20p 2.2, 5.6, 180, 360, 560, 3K6

**END OF LINE STOCK ITEMS AND COMPUTER & AUDIO BOARDS/ASSEMBLIES WITH VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS TRIMPOTS, POT CORES, CHOKES, INTEGRATED CIRCUITS, ETC.**  
 31b for £2.30 71b for £4.30

1k horizontal preset with knob 10 for 40p | 3" Tape Spools 5p | 12 Volt Solenoid Box of 3 £1.20

ENM Ltd. cased 7-digit counter 2 1/2 x 1 1/2 approx. 12V d.c. (48 a.c.) or mains **£1.10**

Auto charger for 12v Nicads, ex-new equipment . . . . . **£3.95**

**SAPPHIRE STYLII.** 10 different; dual and single point, current and hard to get types. My mix £1

**INDICATORS**  
 Bulgin D676 red, takes M.E.S. bulb . . . . . 38p  
 12 volt, or Mains neon, red pushfit . . . . . 23p  
 R.S. Scale Print, pressure transfer sheet Pack 4 48p

PAY A VISIT - THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMER'S RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

**TRADE COMPONENTS**

ESTABLISHED 23 YEARS  
**BRIAN J. REED**  
 161 ST. JOHNS HILL, BATTERSEA, LONDON SW11 1TQ  
 Open 11 a.m. till 7 p.m. Tues. to Sat. Telephone 01-223 5016  
 Terms: Payment with order only. VAT receipts included with goods

# VAT & POST PAID

(2nd Class or Parcel)  
**MINIMUM ORDER £3** (excluding catalogue) OTHERWISE ADD  
 50% FOR SMALL ORDER HANDLING COSTS (UNDER £1.00)  
**TOTAL ALSO INCLUDE 12p S.A.E.**

UK - Postal Orders for same day service. Cheques require 8 days from a Monday banking to ensure clearance. Export - banker's draft (sterling) same day service. Foreign currency money orders etc. can lose value and take 4-6 weeks to clear. VAT content becomes documentation charge.

Due to lack of space, items (i.e. pots, caps, etc.) can only be collectively priced. Catalogue often shows much lower individual value price.  
**ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE**

**BOXES** - Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 67p; Clear perspex with sliding lid, 46 x 39 x 24mm 11p. ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 69p; 80 x 150 x 50mm black £1.09; 110 x 190 x 60mm black £1.62.  
**DIECAST ALI** superior heavy gauge with sealing gasket, approx. 6 1/2" x 2 1/2" x 1 1/2" £1.60; 3 1/2" x 2 1/2" x 1 1/2" £1.10.  
**VARIABLE CAMM PROGRAMMER** 10, 12 or 15 pole 2 way, 50VAC motor—series with 1mf, or 3k 10W or 15W pygmy bulb for mains operation. Ex equipment £3.10

**CATALOGUE**  
 5300 ITEMS AT PRICES YOU WOULD NOT BELIEVE BEFORE INFLATION. YOUR MONEY MUST GO TWICE AS FAR 75p PLUS 30p POST.

## OPTO ELECTRONICS

Photo Diodes: BPX40, BPX42, BPY10, CQY77, CQY17, BPY68, BPY69, BPY77 36p.  
 Wire end neons 4p.  
 Photo transistors: BPX29, BPX43, BP103, 2N5777 Darlington, 36p. OCP71 40p. LED's (Mullard Selmens) Red .2" 8p. .125" 9p; Green .2" 11p; .125" 12p; Micro Yellow LD481 7p.  
**PHOTO SILICON CONTROLLED SWITCH** BPX66 PNP 10 amp 36p

## 7 SEGMENT L.E.D. DISPLAYS

.3" Red com. anode 81p  
 .5" Red FND 5.0 C.C. 72p  
 .6" Green R.S.C.A. £1.77  
 5082-7650 Red com. anode  
 5082-7653 Red com. cath  
 5082-7600 Yellow com. anode  
 H.P. Highbrilliance .43" 72p

## HEWLETT PACKARD MULTIPLEXED .12" 7 SEGMENT LED DISPLAYS

3 Digit HP 5082 7413 45p  
 4 Digit HP 5082 7414 45p  
 5 Digit HP 5082 7415 45p  
 Mlnitron 0.3in 3015F filament £1.25  
 Infra red transmit diodes CQY11B or LD27 High power 1.6-2v or 3-3.5v Pulse 53p  
 LD242 36p  
 H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p  
 Data Sheet 10p  
 CNY17/1 opto coupler 70p  
 Cold cathode tubes I.T.T. G517A or 5870L 60p

## MORE DIGITAL I.C.s

SN15846 37p  
 SN15851 50p  
 SN15858N 55p  
 SN15862 6p  
 SN15844P 4p  
 SGS308 Op Amp 4p  
 8080A C.P.U. £3.60  
 2716 Errom. £14.00  
 MK4012 Memory 38p  
 930DC/933DC 4p  
 936DC/937DC 4p  
 946DC/949DC 4p  
 961DC/962DC 4p  
 963DC 4p  
 9093DC 4p  
 9112DC 4p  
 930399-256 4p  
 930399-500 4p  
 930399-480 4p  
 930399-512 4p  
 953-42300 4p

DIODES			
AA113	9p	OA7	25p
AA119	7p	OA10	25p
AAZ15	15p	OA47	7p
B1	11p	OA70	10p
BA116	30p	OA75	11p
BA128	21p	OA79	11p
BA145	21p	OA81	31p
BA148	12p	OA95	8p
BA182 Varicap	6p	OA200	21p
BAX14	21p	OA202	21p
BAX54	8p	IGP7	11p
BAY36P	21p	IGP10	11p
BB103 Varicap	6p	IN622	21p
BB104 Varicap	16p	IN914	11p
BB109 Varicap	24p	IN916	21p
BB110B Varicap	24p	IN935B	71p
BB113 Triple Varicap	43p	IN935B	71p
		IN937B	71p
BB139	£1	IN941B	71p
BY206	71p	IN942B	71p
BY207	23p	IN943B	71p
BY402	21p	IN3064	21p
BY403	21p	IN3716 Tunnel Diode	30p
Centercell	3p	IN4009	21p
CG651	9p	IN4148	1p
CR HG/3	10p	IN4150	21p
CSD117YLZ	21p	IN4151	21p
CV7095	21p	IN4152	21p
CV7098	21p	IN4446	21p
DC2845 Microwave	20p	IN4449	21p
DOG53	11p	IN5456	15p
FSY28A	40p	5082 2900 RF Schotky Barrier	20p
HG1012	10p		
HS2091	11p		
MPN3401	30p		
OAS	25p		

RECTIFIERS			
Type	Volt	Amp	Price
BY103	1500	1	3p
BY127	1250	1	4p
BY212	EHT		6p
BY235	600	1 1/2	71p
BY236	900	1 1/2	71p
BY238	1200	1 1/2	9p
BY264	300	3	9p
BY265	600	3	11p
BY266	900	3	11p
BY274	300	5	14p
BY275	600	5	17p
BY277	1200	5	27p
BY299	800	2	4p
BY1202	2kV	10mA	6p
BYX20-200	200	25	72p
BYX22-200	200	1 1/2	25p
BYX38-300R	300	2 1/2	48p
BYX38-600	600	2 1/2	52p
BYX38-900	900	2 1/2	60p
BYX38-1200	1200	2 1/2	65p
BYX42-300	300	10	36p
BYX42-900	900	10	92p
BYX42-1200	1200	10	107p
BYX46-300R	300	15	£1.19
BYX46-400R	400	15	£1.19
BYX46-500R	500	15	£2.00
BYX46-600	600	15	£2.30
BYX48-300R	300	6	47p
BYX48-600	600	6	60p
BYX48-900	900	6	70p
BYX48-1200R	1200	6	92p
BYX49-300R	300	3	35p
BYX49-600	600	3	42p
BYX49-900	900	3	47p
BYX49-1200	1200	3	60p
BYX52-300	300	40	£2.05
BYX52-1200	1200	40	£2.90
BYX72-150R	150	10	42p
BYX72-300R	300	10	52p
BYX72-500R	500	10	65p
BYX94	1250	1	5p
E250C50	250	1	14p
LT102	30	2	15p
M1	68	1	5p
MR856	600	3	24p
OA210	400	5	33p
RAS3 IOAF	1250	1 1/2	48p
Avalanche			
REC53A	1250	1 1/2	16p
S10BR30	1000	30	£2.00
SKE4G	200	6	30p
SR100	100	1 1/2	9p
SR400	400	1 1/2	10p
IN4002	100	1	3 1/2p
IN4004	400	1	4 1/2p
IN4005	600	1	6p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	1 1/2	10p
IN5402	200	3	11p
IS138	800	2 1/2	21p
IS921	100	1 1/2	8p
25G100	100	60	£4.35

BRIDGE RECTIFIERS			
Amp	Volt		Price
1/2	1,600	BYX10	34p
1	140	OSH01-200	25p
0.6	110	EC433	20p
5	400	Texas	85p
2 1/2	100	I.R.	40p
3 1/2	100	B40C 3200	58p
1/2	60V	BC30 C350	23p

DIGITAL/COMPUTER	
7400	10p
74000	26p
74LS00	13p
74S00	18p
7401	71p
74H01	26p
7402	11p
7404	11p
54/7406	15p
74LS08	15p
7410	10p
74L10	25p
74H10	26p
7414	18p
7417	39p
7420	11p
74S20	50p
74S22	18p
7425	18p
7426	16p
5430	12p
7430	11p
74L30	11p
7432	13p
54/7437	14p
7438	14p
7442	26p
74LS42	40p
7445	42p
7450	11p
74H50	26p
7451	71p
7454	11p
74L54	11p
54/7472	20p
74L72	25p
5473	12p
7473	17p
74H73	18p
7474	13p
74L74	25p
7475	24p
54/7476	19p
7480	22p
7482	71p
7483	45p
74LS83	47p
54/7486	18p
7489	40p
54/7490	25p
7493	25p
54/7495	25p
74LS98	£1.25
74107	20p
74LS107	26p
74S112	38p
74118	75p
74121	12p
74122	18p
54/74123	35p
74132	44p
74141	42p
74LS145	93p
74150	25p
74151	32p
74154	35p
74155	12p
74157	12p
74165	58p
74167	23p
74173	44p
74180	12p
74176/8280	30p
74192	33p
74LS192	60p
74193	38p
74196	36p
74LS196	90p
74197	50p
74LS221	80p
74293	80p
74298	£1.00
74490	£1.30
82S90	90p
82S129	£5
93S10	£1.00
9311	£1.20
CD4011	25p
CD4012	14p
CD4013	13p
CD4013	23p
CD4019/MC14519	25p
CD4028/MC14028	42p
CD4050	25p
CD4066	27p
CD4069	13p
AY3-8500	£2.00
AY5-8300	36p
D3624	36p
MM2102	73p
IM5623	36p
MM8008	36p
MM5233	36p
DM8214	36p
TMS4034 memory	£1.08
40 x 9 BIT F1F0 2MHz	
3351-2DC	£1.07

BRIDGE RECTIFIERS	
Miniature	Meter
2 1/2	350V
2 1/2	500V

LINEAR I.C.s	
555	20p
702CL	25p
709/72709	18p
710	28p
724	20p
741	16p
748	36p
7805 (T0.3) Volt Reg.	64p
BRC M300 Volt Reg.	£1.40
BRC/MC1310P	35p
BRC/MC1330	85p
BT7822	£1.75
(T)CA270AE	£1.00
(T)CA270CW/AW	35p
CA3001	86p
CA3028A	75p
CA3044	£1.20
CA3046	40p
CA3054	69p
CA3065	36p
CA3083	65p
CA3132EM	£2.22
CA3146E	90p
CA3183	80p
FC/MCP3725	45p
LM300 Volt Reg.	86p
LM309 (Ex. equip.)	60p
LM328 Volt Reg.	20p
LM34076	36p
LM343 Amp	4p
LM1303N	65p
LM/MC1458N	19p
LM3900	36p
MC1306P	40p
MC1307P	35p
MC1312P	40p
MC1314P	35p
MC1315P	35p
MC1350P	35p
MC1357P	35p
MC3302L	75p
MC4044P	£1.00
MC4344P	£3.50
MIC7C	25p
ML237B	£1.00
MT300	8p
MT305 Volt Reg.	8p
SAA1010	34p
SAA661	36p
SAA1025	£4.00
SN403A	36p
SN75107	£1.15
SN75108	36p
SN75110	46p
SN75235N	11p
SN75451	36p
SN76001	36p
SN76003	36p
SN7603N	£1.10
SN76013	36p
SN76013ND	£1.18
SN76023	38p
SN76110P	35p
SN76115N	35p
SN76131	58p
SN76226	58p
SN76227	59p
SN76228N	£1.60
SN76396 (TBA396)	35p
SN76650N	50p
SN76660N	12p
SN76666N	35p
TAA2263	75p
TAA300	£1.00
TAA320	35p
TAA550 Volt Reg.	£2.30
TAD700	23p
TAD100	£1.22
TBA120S/CQ/SB/B	25p
TBA240	£3.90
TBA395Q	£1.50
TBA550	£1.61
TBA800	52p
TBA810	36p
TBA920	70p
TCA270Q/SA/AE/OS	£1.00
TC270S0Q	55p
TCA440	£1.25
TCA4401	£1.25
TCEP100	£1.00
TDA2610	71p
TDA2680	71p
TDA2690	71p
TL720	28p
TYA0171	4p
XR215	£2.00
ZN414	79p
C500 calculator	37p
AJ371-002	4p
FCJ101	50p
FCJ201	18p
FZH151	16p
FZH191	18p
FZH201	18p
MC833P	4p
MC837P	4p
MC846P	4p
MC862P	4p
MC863P	4p
MM5387N	£3.00
MC830P	4p
SN158093	50p
SN158097	4p
SN158099	50p
SN15836	25p
SN15845	50p

BRIDGE RECTIFIERS	
Miniature	Meter
2 1/2	350V
2 1/2	500V
1	400V
1	400V
1	200V
1	50V
1 1/2	800V
1 1/2	75V
1 1/2	150V

# BRIAN J. REED

SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS  
Cut out and keep these 3 pages. Over the months they will ring to you 6,000 items stocked.

VALVES MAINLY B.V.A.		78p		43		£1		E182CC		£4		HP4106c		£1		PEN400		£1.10		U16		£1.20	
1AG4	£1.30	6SK7	78p	44E	£1.50	EA50	55p	EA50	55p	HP4106c	£1	PEN400	£1.10	U16	£1.20								
1AH4	£1.30	6SL7GT	90p	44E	£1.50	EA52	55p	EA52	55p	HVR2	£1.30	PEN453DD	£1.10	U14	£1.30								
1AJ5	£1.30	6SN7	90p	38	90p	EA56	£1.70	EA56	£1.70	JC140	£1.50	PEN4A	£1.30	U35	£1.20								
1CI	65p	6S07	95p	50BC4	£1.50	EAC91	81p	EAC91	81p	K3	£1.90	PENB4	£1.50	U21	£1.50								
1C5GT	70p	6UAGT	£1.10	50C5	£1.50	EAF42	£1.50	EAF42	£1.50	KT32	65p	PFL200	£1.10	U24	£1.50								
1D5	£1	6USG	£2.35	53CG	56	EAF801	£1	EAF801	£1	KT33C	95p	PL36	60p	U27	£1.30								
1D6	£1	6U7G	73p	56	75	EB41	£1.25	EB41	£1.25	KT35	£2.35	PL38M	90p	U37	£1.50								
1D8GT	£1	6U8	70p	75B1	£1.40	EB34	60p	EB34	60p	KT45	£1.30	PL81	62p	U70	60p								
1E7	£1	6UG	£1.50	75C1	£1	EB91	£1.40	EB91	£1.40	KT44	£1.05	PL82	45p	U81	£1.05								
1FD9	55p	6V6GT	70p	78	90p	EBC33	£1	EBC33	£1	KT66	£3.70	PL83	35p	U84	£1.50								
1G5	£1.20	6X4	75p	83A1	£2	EBC81	65p	EBC81	65p	L28	£1.50	PL84	55p	U92	75p								
1L4	45p	6X5G	60p	85A2	£1.00	EBC90	83p	EBC90	83p	L240	£1.50	PL504	£1.48	U153	70p								
1LC6	£1.10	7AN7	46p	90A	£3	EBC91	65p	EBC91	65p	LP2	£1.50	PL519	£3.35	U191	35p								
1LD5	95p	7B6	£1	90AV	£9	EBF32	£1.50	EBF32	£1.50	M8081	80p	PM1A	£1.50	U193	70p								
1N5GT	95p	7B218	£1.50	90AV	£9	EBF80	£1.50	EBF80	£1.50	M8083	£1.50	PM1DG	£1.50	U251	£1.40								
1U5	£1	7C5	£1.75	90C1	£1.50	EBF89	55p	EBF89	55p	M8098	£3.75	PM1HF	£1.50	U301	60p								
1W4 350	£1.50	7D3	£1	142BT	£1	EBL21	£1.30	EBL21	£1.30	M8100	£1.20	PM1HL	£1.50	U403	95p								
2D13C	£1	7D8	£1	150B3	£2.60	EC86	£1	EC86	£1	M8204	£1.30	PM1LF	£1.50	UAF42	75p								
2X2A	£1	7F7	£1.40	150C4	£1.40	EC88	80p	EC88	80p	M8207	£1.90	PM2A	80p	UB41	£1.05								
3A8GT	£1.10	7H7	£1	185BTA	£1.50	EC70	£1.30	EC70	£1.30	M8212	80p	PM2DX	£1.50	UBC81	60p								
3A167M	£1.10	7Y4	£1	202MPG	£1	EC91	£1.30	EC91	£1.30	ME1400	£3	PM3A	£1.50	UBF80	60p								
3B28	£5.20	907	£1	210RC	£1.10	EC8010	£1.50	EC8010	£1.50	MH4	£1.20	PM6	£1.50	UBF89	65p								
3M5	£1	10C1	£1.20	2155G	£1	ECC31	£1.55	ECC31	£1.55	MH4	95p	PM12A	£1.40	UBL21	90p								
3Q4	95p	10C2	60p	220VSS	£1.05	ECC33	£2.15	ECC33	£2.15	MH4	95p	PM2	£1	UCC44	£1.50								
5B254M	£7.50	10F1	60p	329 Barreta	£4.50	ECC35	£2.15	ECC35	£2.15	MH4015	£1.50	PM24MA	£1.20	UCC84	75p								
5B255M	£7.50	10F9	85p	841A	£6.90	ECC40	£1.15	ECC40	£1.15	MHL4	£1.15	PP3-250	£4.50	UCC85	60p								
5V4G	85p	10L1	£1	1821	£1	ECC84	56p	ECC84	56p	MP-PEN	£1	PP2018	£1.50	UCF80	85p								
5Y3GT	75p	10LD11	£1	1909A Barreta	£1.50	ECC85	55p	ECC85	55p	PT2	£1	PT2	£1	UCH21	£1.30								
5Z4GT	85p	10P13	75p	1909H	£1.50	ECC86	£1.45	ECC86	£1.45	PT4	£1	PT4	£1	UF25	£1.05								
5U4GB	£1	10P14	£1.10	1941A	£1.50	ECC88	76p	ECC88	76p	MKT4	£1.50	PT4	£1	UF80	55p								
6/30L2	£1	11E2	£12.50	2050	£2.30	ECC91	70p	ECC91	70p	MS48	£1.20	PT4	£1	UF85	55p								
6A7	£1.20	12A6	75p	2103	£1.50	ECC189	£1	ECC189	£1	MU12	£1.25	PT4	£1	UF86	£1.50								
6A8GT	75p	12AH8	£4	4152	£2	ECC804	£1.30	ECC804	£1.30	MU14	£1.25	PT4	£1	UL41	95p								
6AK6	95p	12AT6	55p	5726	£1	ECC807	£1.95	ECC807	£1.95	MVSPEN-B	£1.60	PT4	£1	UL44	£1.50								
6AK9	£1.50	12AU6	70p	5965	£1.05	ECF80	65p	ECF80	65p	N31	£1	PT4	£1	UL46	£1								
6AM6	80p	12AV6	85p	6060	£1.05	ECH21	£1.30	ECH21	£1.30	N37	£1.50	PT4	£1	UM80	75p								
6AN5	£3	12AY7	£1	6063	£4.15	ECH81	74p	ECH81	74p	N42	£1.50	PT4	£1	UU2	£1.30								
6AS6	£1	12BA6	65p	6080	£3.55	ECH84	80p	ECH84	80p	N77	£1.50	PT4	£1	UU3	£1.30								
6AS7G	£1.45	12BB6GT	70p	6158	£2.75	ECL80	60p	ECL80	60p	NT2 Ex. equip	20p	PT4	£1	UU4	£1.30								
6AT6	83p	12BE6	75p	7475	£1.05	ECL85	80p	ECL85	80p	N78	£10.10	PT4	£1	UU5	£1.30								
6AV6	65p	12BH7A	£1.05	8068	90p	EF32	£1.50	EF32	£1.50	N148	70p	PT4	£1	UU8	£3								
6AW8A	£1	12BY7	70p	A50N	£6	EF41	90p	EF41	90p	N329	82p	PT4	£1	UU12	55p								
6B6	£1.50	12C8GT	£4.80	A2293	£6.40	EF42	£2.40	EF42	£2.40	N369	70p	PT4	£1	UY1N	75p								
6B8GT	50p	12E1	80p	A80A	93p	EF50	60p	EF50	60p	OA2	75p	PT4	£1	UY21	£1.30								
6B8G6	£1.25	12H6	55p	A2900	£8.15	EF55	£1.85	EF55	£1.85	OB2	60p	PT4	£1	UY42	75p								
6BH6	£1.10	12J5GT	90p	ACPEN	£1.30	EF82	£1.90	EF82	£1.90	OC3	90p	PT4	£1	V4	£1.50								
6BJ6	£1.15	12J7GT	90p	AC2PEN	£1.30	EF85	50p	EF85	50p	OZ4A	£1.90	PT4	£1	V10	£1.50								
6BK4	£1.70	12K5	£1.50	AC2PENDD	£1.30	EF86	85p	EF86	85p	PABC80	55p	PT4	£1	V914	£1								
6BN6	£1	12K7GT	80p	ACS2	90p	EF91	85p	EF91	85p	PC86	55p	PT4	£1	VA26T	£1.50								
6BQ7A	80p	12K8	80p	ACS2PEN	90p	EF92	76p	EF92	76p	PC88 Pack of 5	55p	PT4	£1	VHT4	£1								
6BR7	£2.20	12SA7GT	£1.10	AC2ZHL	95p	EF99	£1	EF99	£1	PC88	35p	PT4	£1	VLS631	£8.25								
6BS7	£2.95	12SK7	£1	ACSG	£1	EF80 Pack of 5 for	76p	EF80 Pack of 5 for	76p	PC86	85p	PT4	£1	VM4V	£1.50								
6BW7 Pack of 5	£1	12SN7	£1.80	ACSGVM	£1.10	EF183	87p	EF183	87p	PCC84	60p	PT4	£1	VMP4GK	£1.30								
6BZ6	85p	12SN7	70p	ACTH1	£1	EF184	74p	EF184	74p	PCC85	90p	PT4	£1	VMS4B	£1.70								
6C5GT	80p	12SQT	65p	ACTP	£1	EK2	£1.30	EK2	£1.30	PCC88	88p	PT4	£1	VP4B	£1								
6C6	70p	14S7	£1.20	ACVPI	£1.75	EK90	68p	EK90	68p	PCC805	88p	PT4	£1	VR54	55p								
6CB6	75p	18	£1	ADHL	£1	EL6	£1.50	EL6	£1.50	PCC806	88p	PT4	£1	VR59	70p								
6D1	55p	19A05	75p	AL60	£1.75	EL31	£1.50	EL31	£1.50	PCC189 Pack of 5 for	£1	PT4	£1	VR78	50p								
6D2	55p	19H4	£23.00	AZ41	56p	EL38	£1.50	EL38	£1.50	PCF82	50p	PT4	£1	VR92	55p								
6D6	60p	20-60.15	£1.50	B9-20	£1.50	EL32	95p	EL32	95p	PCF84	80p	PT4	£1	VS10G	£26								
6F8	£1.10	Barreta	£1.50	B36	£1.80	EL81	80p	EL81	80p	PCF86	63p	PT4	£1	VS10H	£28.75								
6F5	£1.25	20C1	£1.50	C1134	£11.80	EL83	95p	EL83	95p	PCF87	92p	PT4	£1	VS24	£1.50								
6F8G	85p	20D1	35p	CL4	£1.30	EL86	80p	EL86	80p	PCF201	£1.10	PT4	£1	VT109	£1.50								
6F7	£1.50	20F2	35p	CR958A	£1.20	EL91	£1.85	EL91	£1.85	PCF80	25p	PT4	£1	VT126	£1.50								
6F13	95p	20L1	35p	CT15	£1	EL95	85p	EL95	85p	PCF806	80p	PT4	£1	VU133	£1.25								
6F14	80p	20P3	55p	CV2179	£7.50	EL822	£5.10	EL822	£5.10	PCF808	£1.60	PT4	£1	W30	£1.50								
6F15	75p	20P4	75p	CVX850	£1.20	EM1	50p	EM1	50p	PCL81	75p	PT4	£1	W42	£1								
6F17	80p	20P5	60p	DAC32	90p	EM4	£1.50	EM4	£1.50	PCL82	85p	PT4	£1	W61	£1.75								
6F19	50p	25A6	90p	D77	55p	EN10	£1.50	EN10	£1.50	PCL83	£1.05	PT4	£1	W150	95p								
6F23	65p	25L6	96p	D41	£1	EY86/87	£1.50	EY86/87	£1.50	PCL85/805	49.90	PT4	£1	WD2	£1.50								
6F24	£1.10	25Z6	£1	D43	95p	EY88	75p	EY88	75p	PCL86	£1.50	PT4	£1	W61	95p								
6F25	£1.25	27S1	£1	DDL4	£1	EY500A	£1.60	EY500A	£1.60	PCL801	95p	PT4	£1	X81	£2.45								
6F26	50p	27U1	£1	DDT4	95p	EZ40	70p	EZ40	70p	P41	95p	PT4	£1	XH1.5	70p								
6F28	£1.10	27YU	£1	DF33	95p	EZ80	63p	EZ80	63p	P61	80p	PT4	£1	XP1.5	70p								
6F32	95p	30C1	£1.04	DF92	95p	EZ81	66p	EZ81	66p	P240	£1	PT4	£1	YSM4	£1.50								
6F33	£4.80	30C15	60p	DF97	£1.45	EZ90	75p	EZ90	75p	PEN4DD	£1	PT4	£1	Z66	95p								
6H1	£12.70	30C17	80p	DG2	£1.50	FC4	£1	FC4	£1	PEN4VA	£1	PT4	£1	Z152	60p								
6H6	60p	30C18	£1.65	DH63	85p	FW4/500	£2.85	FW4/500	£2.85	PEN20	£1.50	PT4	£1	Z193	£1.50								
6J5GT	90p	30F5	£1.10	DH81	95p	G1/371K	£7.40	G1/371K	£7.40	PEN45	£1.10	PT4	£1	Z900T	£1.80								
6J6	60p	30FL1	£1.34	DH107	£1.50	G8	£1.50	G8	£1.50	PEN220A	£1	PT4	£1	ZA7022	£1.50								

# LATEST BOUND VOLUME No. 32

of  
"Radio & Electronics  
Constructor"



SEPTEMBER 1978 to AUGUST 1979

Comprising  
776 pages  
inc. index **PRICED £5.50 P&P £1.30**

**BOUND VOLUME No. 27**  
(August 1973 to July 1974)  
**Price £3.00 P&P £1.30**

**BOUND VOLUME No. 28**  
(August 1974 to July 1975)  
**Price £3.20 P&P £1.30**

**BOUND VOLUME No. 29**  
(August 1975 to July 1976)  
**Price £3.50 P&P £1.30**

**BOUND VOLUME No. 30**  
(August 1976 to July 1977)  
**Price £3.70 P&P £1.30**

**BOUND VOLUME No. 31**  
(August 1977 to August 1978)  
**Price £5.20 P&P £1.30**

Limited number of these  
volumes still available.

We regret all earlier volumes are now  
completely sold out.

Available only from  
**DATA PUBLICATIONS LTD.,**  
35 MAIDA VALE, LONDON, W9 1SN

**VIDEO RECORDERS** Philips type LDL1000 we have a small stock of these items standard mains I/P complete with cover approx ext. size 18 x 12 x 10" supplied complete untested with one reel of tape and copy of Service Handbook good cond. **£185.** U.H.F. Rx Ass. single chan unit with crystals for 243Mc/s 11 min. valves in double conversion circ O/P for 100 ohm phones reqs. 200v HT and 6.3ac new cond. **£16.50**

**TRANS** Auto 200/250v to nom 115v at 560 watts fully enc. with term conn. size 6½ x 3½ x 3½" new cond. **£13.50**

**RECORDING TAPE** standard Ampex ¼" Audio tape 3600 Ft on 10½" spools new Mil spec **£7.50**

**AUDIO TEST SET CT373** three function bench unit comprises Audio osc 17c to 170Kc, AC VTVM multi range and Distortion measuring unit standard mains I/P high grade unit with handbook fuller spec. on request **£80.**

**MAINS TRANS** 240v to 340-250-0-250-340v at 210 Ma LTs 6.3v at 5 amp twice and 5v ct at 5 amps will do 700v DC at 250Ma with no LT load new cond. **£9.50**

**THERMISTORS** ITT type G24B bead type approx. 3.8mm dia. temp. range 20 to 200°C new **80p ea.**

**PAINTON INST SWTS** two types 7p 15w 7b **£4** and 4p 15w 4b **£3** both with knobs.

**HELIPOT DIALS** Colvern 10 Tr **£1.50** or Beckman 15 Tr **£2.50** also 30 and 100K Helipot **£1 ea.**

**POWER UNITS CT397** Variable O/P bench p.u. 0 to 500 v DC at 100Ma to 350v and 6.3 ac 3 amps with Volt/Ma meter in case tested **£22** also small stab p.u. 135v 20Ma and 6.3 1 amp neat unit made for BC221 or sim. freq. meters **£12.**

**INDICATOR UNIT ALA-6** with 3" CRT 3WP1 okay for scope use 13 min. valves as int. 400c p.u. in case size 10 x 8 x 21" supplied with circ. was part of A/C DF equip. **£25.**

**SIL DIODES** stud type 100 PIV 10 amps 4 for **£1.50** 1000 PIV 10 amps 4 for **£2.50** 200 PIV 35 amps 4 for **£3.50** all new.

**POWER UNIT INVERTOR** 115v I/P gives AC O/Ps at 20Kc contains 6x pot cores, H.V. transis., 10x transis., 2x Thyr., diodes, 20mm fuse holders, etc. in case 9 x 3½ x 4" with circ. **£4.50**

**FANS** extractor type 230v mount flange 7 x 8" new Adm. **£8.50** also HD single ended blower 240v outlet 2½ x 3½" 2850 RPM new **£11.50**

**NON IND RES** Morganite 150 ohm 20% size 6 x 1" dia with mt clips est 40w 3 for **£4.50.**

**RADIO KIT** contains 6" pliers narrow nose, small screwdriver, neon mains tester, 4x egg insulators, 100ft. Ae wire, 30ft. reel Ae, crystal adap., etc. **£5.50**

**POWER SIGNAL GENERATOR** covers 1.5 to 12Mc/s in 3 bands VFO control direct calibration nom O/P 20 watts into 70 ohm this can be varied over wide limits by variac control of P.A. stage HT voltage, valves 6F17 Osc and 5B254 P.A fitted PA current and RF O/P voltage meters standard 240v I/P good cond. in 19" transit case **£45.**

**MAINS FILTERS** size 2½ x 1½ x 1" rated 250v 1.5a new **£2.20.**

**AERIALS** Aircraft dipole aerial length 50½" center moulder fairing with BNC conn. for use on 20/50Mc/s or if int. loading coil removed about 125Mc/s £2 or 2 for **£3.50** also Blade aerials on machined base with BNC conn 10" new cond. **£1.75 T.V.**

**TUNER UHF** manual tuned type with circ. new **£2.60** or 10 for **£20.**

**TUNING CONDS** dual gang 500pf per section with 3/8th ceramic shaft air spaced new **£3.50.**

**CRYSTALS** mostly 10XJ types in freq. range 5 to 7.5Mc/s 20 ass for **£2.30.**

**AUDIBLE WARNING DEVICES** small unit size 1½" dia works on 12v DC gives loud tone about 800cc new **£1 ea.** 2 for **£1.70.**

**TRANSISTOR INVERTOR** 12v DC I/P O/Ps 425v DC 125Ma or 180v DC 40 Ma also 6v DC at 2.5 amps in case size 5½ x 4 x 3" tested with circ. **£10.50.**

**HAND GENERATORS** for use with MK123 T/R 110v 40 watts cont. 100c/s new cond. in fitted case with accs. **£25.**


**VALVE AUDIO TRANS** O/P trans. 5K to 600 and 8 ohm 1 watt 50c to 15Kc potted **£3.50** I/P trans 250 ohm to 50K potted **£2.**

**WIDE BAND AMPLIFIER** general purpose unit 240v I/P as 3 gain settings of 10, 50 and 100 at bandwidths of 50, 40 and 15Mc/s supplied with probe unit can be used as VTM with rect. unit supplied to drive ext. 500Ua meter complete with valves mains conn. in case, circ. and inst. supplied **£22.**

Above prices include carriage and VAT, good ex. equip. unless stated new. SAE with enquiry or 2 x 10p stamps for List. 25.
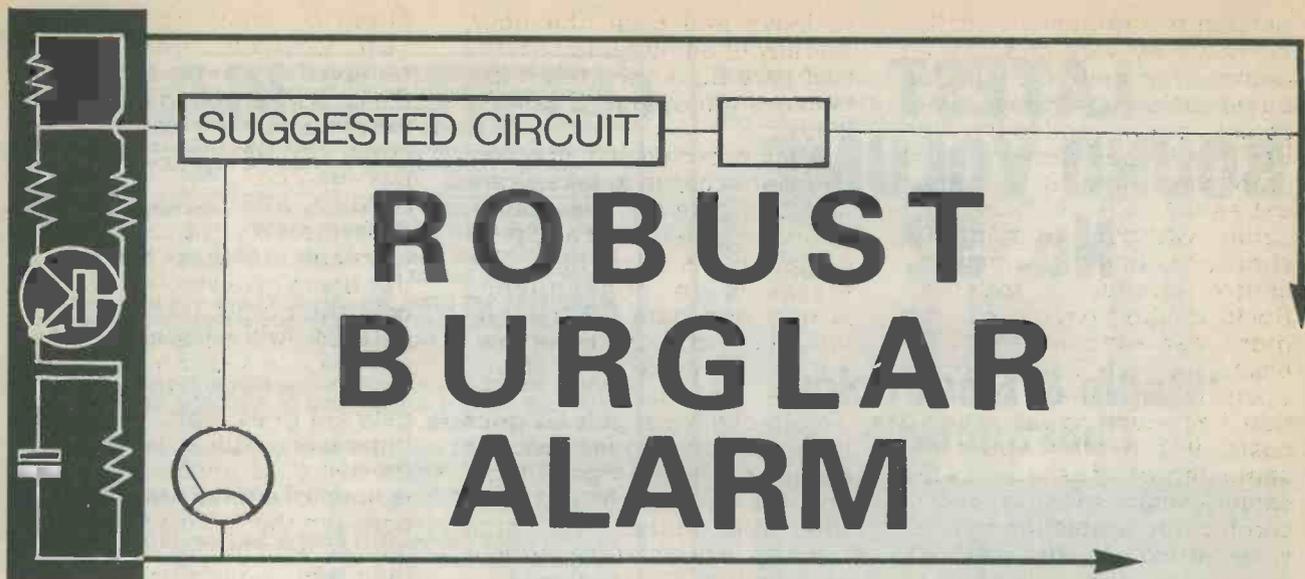
## A. H. SUPPLIES

Dept. RC1, 122, Handsworth Road,  
Sheffield. S9. 4AE. Ph. 444278 (0742)



By G. A. French

A large number of burglar alarm designs are available to the public these days, and they range from very simple installations incorporating little more than a relay, bell and battery to very complicated circuits requiring more than a hundred electronic components. It can be argued that an excessive quantity of parts in a burglar alarm system is not a desirable feature, on the grounds that a large number of components increases the risk of failure.

For normal domestic protection a very high degree of security can be given by quite simple intruder alarms and a suitable circuit for such an alarm is described in this article. The system is intended for installation indoors in dry conditions, and particular emphasis has been placed on running economy. The circuit has an inhibit feature which disarms the alarm for a short period after switching on, thereby allowing the occupier of the premises to turn it on and leave the premises without triggering the alarm. The inhibit circuit is automatically reset when the alarm is switched off again.

### OPERATING REQUIREMENTS

A number of conflicting requirements have to be satisfied in the design of a low cost burglar alarm. The question of a power supply has first to be

settled, and battery operation is normally to be preferred since there is then no risk of failure to operate due to mains power cuts and the like.

A simple d.c. operated circuit will be employed, in which the alarm is triggered by guard switches or other switching devices installed at or near doors and windows, whereupon the next point which has to be decided is whether triggering is to be given when the guard circuit is opened or when it is closed. With the first method a current flows continually through the guard circuit is opened or when it is closed. With the first method a current flows continually through the guard switches, and these break the circuit to trigger the alarm when the appropriate door or window is opened.

No current flows with the second approach until one of the protective switches is closed. The first method of operation is normally considered the better because it has a fail-safe feature. If any of the wires in the circuit is cut the alarm is triggered. On the other hand, there is the necessity of providing the continual guard current which, if the installation is to be robust and reliable, must have a magnitude of at least a milliamp. With a 9 volt energising supply this corresponds to a working impedance of 9k $\Omega$  or less, and there is then little risk of non-operation due to leakage across switch ter-

minals and similar occurrences. The writer recently heard of a continual current installation in which the current was much lower than a milliamp, and in which one of the switches ceased to operate simply because it had been painted over. Even when dry, the paint caused sufficient leakage across the switch terminals to prevent the alarm being triggered when the switch contacts opened.

In these days of CMOS gates which operate at microamp level, a continual current of 1mA or more seems rather large. If an alarm employing a 1mA continual current were switched on for long periods, smaller batteries in the PP3 and PP6 category would become exhausted relatively quickly. Even with a larger PP9 battery, regular checks would be required to ensure that its voltage was being maintained at an adequately high level. Batteries are expensive, and a system which requires frequent battery replacement would prove costly in the long run.

This factor makes it desirable to take a second look at the open-circuit method of operation, with which the guard switches are normally open and no continual current flows. With such a system it is possible to obtain protection against wire cutting which is very nearly as effective as is given in a continual current installation. The alarm to be described requires that con-

nection to the guard switches be made by way of screened cable. If flexible insulated audio cable with a braided wire screen, as opposed to the type having a lapped wire screen, is employed here it becomes extremely difficult to cut the cable without momentarily short-circuiting the screen and centre conductor together. Such a short-circuit can be more than adequate to trip an electronic latch. To sum up, the open-circuit method of operation has much lower running costs, it can offer about the same degree of security as the closed-circuit method and it can include protection against wire-cutting. In the author's experience, the only way of cutting braided screen audio cable without causing a momentary short-circuit is to first remove the outer insulation, cut the braiding all round a diameter of the wire without accidentally contacting the centre conductor, push back the braiding and then cut the centre conductor.

### CIRCUIT DESIGN

The full circuit of the burglar alarm is given in Fig.1. It is assumed that there is only one guard switch, this being the normally open switch S1. The switch could be mounted at a door so that it closes when the door is opened, and it connects to the main part of the circuit via screened cable of the type just referred to. The active devices in the circuit are four gates in a quad NAND i.c. type CD4011, and a BC107 transistor.

When switch S2 is moved from the "Off" to the "On" position, power is applied to the circuit and the short-circuit (via current-limiting resistor R3) across C1 is removed. C1 commences to charge slowly via R2. When C1 is in the discharged or only partly charged state, the voltage at pins 1 and 2 of gate G1 is high, and the gate output at pin 3 is low. Gate G2 output is consequently high, and it stays high regardless of whether S1 is open or closed. The outputs of gates G3 and G4 are low. The circuit is now going through its initial inhibit period after switch-on, and it gives time for the occupant of the protected premises

to leave and close the door, thereby opening switch S1. Pin 6 of gate G2 is then taken low because the output of gate G4 is low.

After a period, C1 acquires sufficient charge to take pins 1 and 2 of gate G1 low, whereupon the gate output and pin 5 of gate G2 is taken high. The alarm is in consequence armed, and gate G2 has one input high and one input low.

If, now, switch S1 is closed (or the screened wire short-circuited) pin 6 of gate G2 goes high. Its output goes low, the output of gate G4 goes high, and the two gates latch into this new state. The latch remains in this state regardless of whether S1 is closed or opened, and it requires only a very momentary closure in S1 to achieve the requisite triggering. Previously, the output of gate G3 was low, causing TR1 to be cut off. G3 output is now high and TR1, functioning as an emitter follower, energises relay RLA. The relay contacts cause the bell (or any other warning device) to be actuated, and the bell can only be sil-

enced by returning S2 to the "Off" position. Power is then removed from the circuit and C1 is discharged via R3, with the result that the alarm is reset ready for the next time it is switched on.

When, after arming, switch S1 is open, the impedance at its terminals is of the order of 3kΩ, this being given by R4 in series with the output impedance of gate G4. At the instant of closure there is a current pulse of some 3mA before the output of gate G4 goes high. The same impedance still exists across the switch terminals, but there is now, of course, no potential between them. This low impedance working will prevent incorrect operation due to leakage across switch terminals and similar effects.

As C1 charges during the initial inhibit period, the output of gate G1 stays low until its input voltage reaches the level at which linear amplification takes place. The output then swings fairly quickly to the high state. It is quite in order to switch on at S2 and leave S1 continually closed. All that

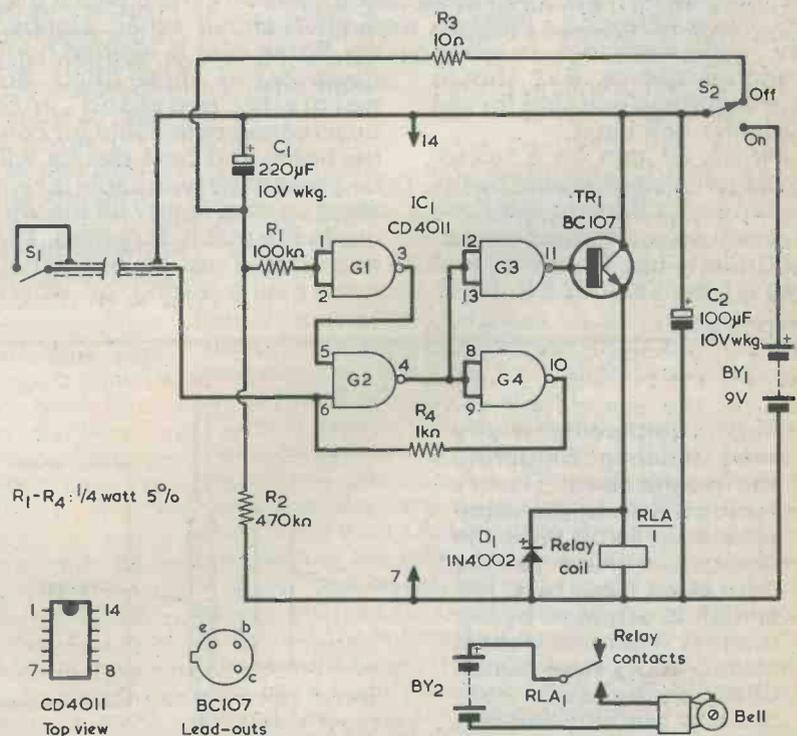


Fig. 1. The circuit of the burglar alarm. This features very low running current, automatic latching, turn-on inhibit timing, low impedance guard wiring and protection against wire-cutting.

then happens is that the alarm sounds at the end of the inhibit period. The inhibit period with the prototype circuit was 1 minute and 15 seconds, but this may vary somewhat with units built up to the circuit due to tolerances in value in C1, and differences in transfer characteristic in gate G1. The inhibit period is roughly proportional to the value of C1 and can be extended, if desired, by increasing that value.

Resistor R1 has no effect on circuit performance as so far described, and its only function is to prevent heavy currents flowing in the input protective diodes of gate G1 during switch-off. If the alarm is switched off with the relay energised, there is an instant, with the switch arm between contacts, when C2 discharges rapidly whilst C1 discharges slowly.

#### COMPONENTS

All the components are standard readily available types. Relay RLA is a miniature "Open Relay" with 410Ω coil, available from Maplin Electronic Supplies. Switch S2 may be a normal toggle type or a type which is operated by a key. Battery BY1 is a 9 volt battery of any type, and a PP9 battery will represent a good economic choice. BY2 should have a voltage suitable for the particular bell used.

Switch S1 can be a micro-switch which is operated by the opening of a door or window, or it can be a dry reed switch controlled by a permanent magnet, as illustrated in Fig.2.

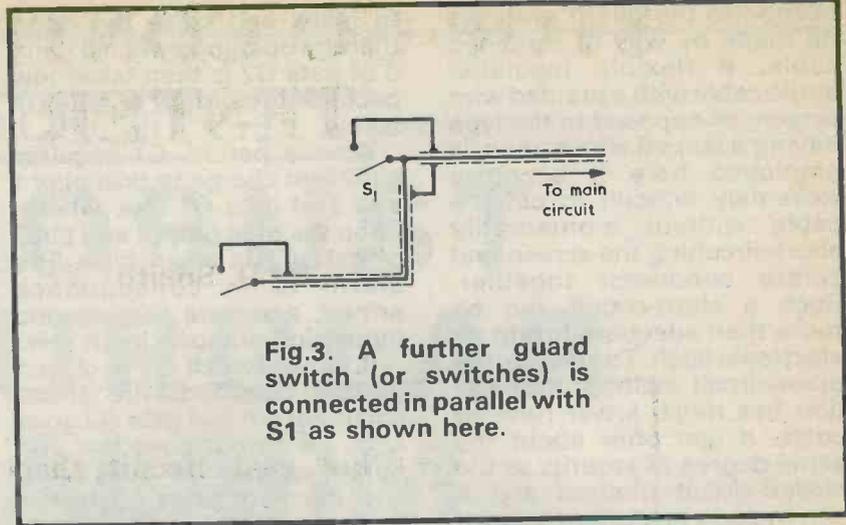


Fig.3. A further guard switch (or switches) is connected in parallel with S1 as shown here.

When more than one switch is required the switches are connected in parallel, as shown in Fig.3. It is important that the braiding of the screened wire is always connected to the positive rail of the circuit, as indicated in Fig.1. Apart from its function of providing a momentary short-circuit when it is cut, the wire screens the centre conductor and prevents pick-up of static and noise which would otherwise be passed to pin 6 of gate G2.

The circuit can also be used with pressure mats which give a short-circuit when stepped on. Some care is needed here, however, as these mats are normally provided with unscreened twin cable for connections, and best results will be given if the twin cable is kept short so that nearly all the wiring to the mat is screened. The mat should not be positioned near mains wiring or where

pick-up of electrical noise is likely.

The main part of the circuit can be housed, complete with batteries, in a small case situated in an unobtrusive or hidden location. If the case is metal it should be made common with the positive rail so that it has the same potential as the screened wire braiding.

#### CURRENT CONSUMPTION

The current consumption of the circuit is very low after an initial few minutes following switch-on. The current consumed by the prototype was first measured with S1 continually open. Immediately after setting S2 to "On" the main current which flows is charging current in C1, which starts at around 20μA. The current rises when gate G1 commences to go through the linear amplification range, rising to a momentary peak of about 1mA. The current then quickly falls to around 100μA, after which it decreases more slowly. Some three to four minutes after switch-on the current drawn from the 9 volt battery is less than 2μA, and it then stays at this very low level. The current is due to leakage in the two electrolytic capacitors, in IC1 and in TR1. If S1 is closed during the inhibit period the current rises to approximately 4mA, falling to the level just described when the switch is opened again. When S1 is closed after the inhibit period, causing the relay to energise, the current rises to 20mA. ■

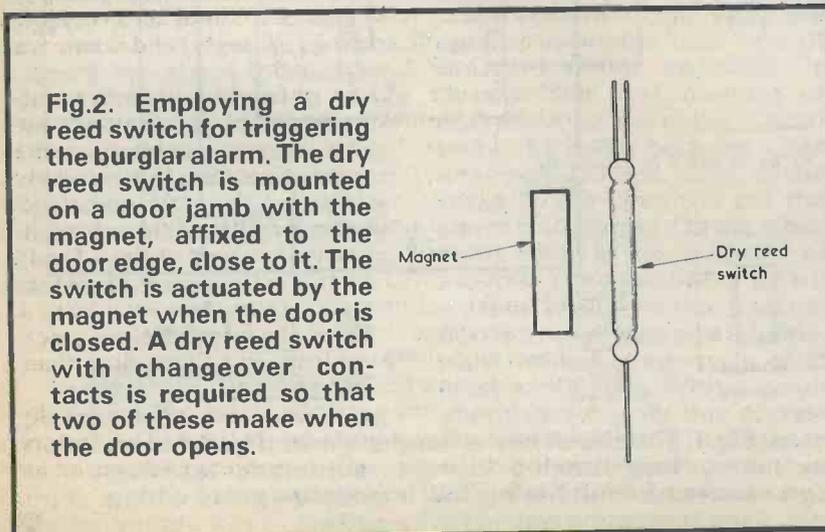


Fig.2. Employing a dry reed switch for triggering the burglar alarm. The dry reed switch is mounted on a door jamb with the magnet, affixed to the door edge, close to it. The switch is actuated by the magnet when the door is closed. A dry reed switch with changeover contacts is required so that two of these make when the door opens.

# STOP-GO CONTINUITY TESTER

By D. Snaith

Very low cost circuit checks  
continuity and detects resistance.

Fig.1 shows a continuity tester incorporating a red 1.e.d., a green 1.e.d., a silicon diode, two resistors and a 4.5 volt battery. Two test leads with prods connect to the test terminals and the device functions as a low ohms continuity tester.

## CIRCUIT FUNCTION

When S1 is closed with the test terminals open-circuit, current flows through D1, LED1 and R2, causing LED1 to light up. About 2 volts is dropped across this 1.e.d. If the test terminals are now short-circuited current flows through LED2 and this 1.e.d. becomes illuminated. The forward voltage dropped across LED2 is also of the order of 2 volts, where-upon the voltage available for LED1 is equal to this voltage minus about 0.6 volt dropped across D1. LED1 extinguishes. Resistor R1 ensures that sufficient voltage is dropped across D1 to give complete extinction of LED1.

Thus, when the circuit is used as a continuity tester, continuity is indicated by the red 1.e.d. going out and the green 1.e.d. turning on.

However, the tester also indicates resistance in the circuit being checked. With the prototype, connecting

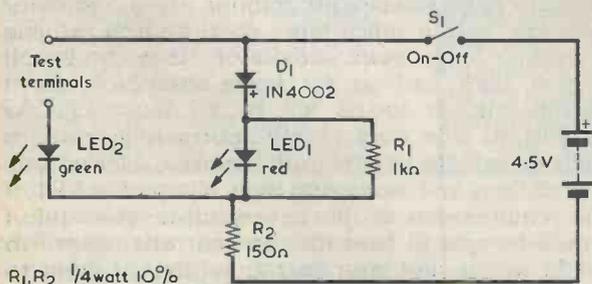


Fig. 1. The circuit of the tester. A short-circuit or very low resistance across the test terminals causes the red 1.e.d. to extinguish and the green 1.e.d. to turn on.

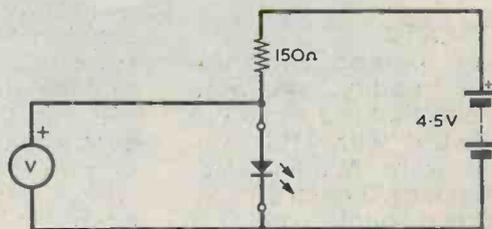


Fig. 2. Before assembling the tester, the forward voltage drops in the 1.e.d.'s to be used can be checked with this circuit.

a resistance of  $10\Omega$  across the test terminals results in a just perceptible glow in the red LED1. Increasing resistance across the test terminals results in increasing brightness in LED1. This state of affairs continues until, at a resistance of around  $2k\Omega$ , the red 1.e.d. is fully illuminated and the green 1.e.d. is nearly extinguished. In consequence, the circuit indicates very low resistance (only the green 1.e.d. alight) and resistance above  $10\Omega$  (both 1.e.d.'s alight).

Similar results will be obtained with other continuity testers built up to the circuit. It is desirable for the red and green 1.e.d.'s to have roughly the same forward voltage drop when alight, and this is usually given when both 1.e.d.'s are of the same make and type. Before assembly, the forward voltage drop of the 1.e.d.'s can be checked with the aid of the 4.5 volt battery and the  $150\Omega$  resistor in the test circuit of Fig. 2, in which the voltmeter is a testmeter switched to a low d.c. volts range. It should be found that the green 1.e.d. has a slightly lower forward voltage drop than the red 1.e.d., and this satisfactory.

About 15mA flows in either 1.e.d. when it is fully illuminated, giving a good bright glow. The battery can be three 1.5 volt cells connected in series or an Ever Ready "flat" 1289 battery.

---

# NEWS . . . AND

---

## LEAD FORMING TOOL


The hand-held tool which you can see in the photograph is intended for the bending of

electronic component lead-outs prior to insertion into printed circuit boards. Known

as the lead forming tool Model PR2, it has been introduced by Eraser International Ltd., Unit M, Portway Industrial Estate, Andover, Hants, SP10 3LU. It is intended for axial lead components such as resistors, diodes and capacitors. The wire bends are at right angles with pitch centres between 12mm. and 15mm.

An ingenious and very simple means of setting up the tool is incorporated. By turning a knob on the side of the tool, two pointers are lined up with the holes on the board into which the component is to be inserted. The bending dies are then automatically set up to the correct spacing, after which it is merely a matter of inserting components into the tool and operating its handles to obtain the desired lead-out bends.

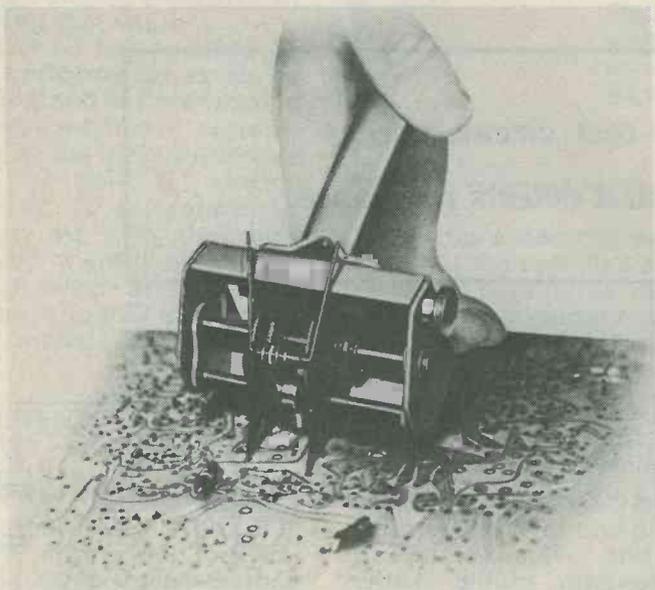The bending jaws on the tool incorporate a spring system which automatically compensates for different diameter leads and thus eliminates nicking and damage. Further details on the Model PR2 may be obtained from Eraser International.



The Eraser International lead forming tool Model PR2. The knob at the right is adjusted so that the two pointers at the bottom line up with the holes in the board into which the components are to be inserted. The tool is then set up and will bend both leads of components to be inserted by operation of the handles.

---

## OSCAR 9 DISASTER

Many readers will no doubt, have heard by now that the launch of the European Space Agency LO2 rocket, ended in disaster! The launch date of May 23rd., was adhered to, but the count down was held up for several periods during the 'window' available for launching. Right at the end of this launching time period 'window', the announcement came through that launching was to take place and a successful firing took place. Almost immediately after this successful lift-off, the announcement came that one of the four first stage rocket motors was not functioning properly. This announcement was followed almost immediately by the news that there had been an explosion and the rocket, with its satellites of course, had fallen into the sea, some six hundred kilometres, down course. So that was the end of OSCAR 9!, and of "Firewheel" of course!

Having seen OSCAR 9 during its construction in Washington, and met some of the folk concerned with its design and construction, the writer feels terribly sorry for them having all their work and

hopes destroyed in this way. Especially as the satellite itself may well have proved totally satisfactory and functioned perfectly. What the future for AMSAT and the OSCAR 9 project will be, is too early to assess at this stage. It was to have taken the amateur radio satellite programme into a completely new era, with a much more sophisticated satellite, providing a far more satisfactory communications system than had so far been attempted. Great disappointment too is felt by all those OSCAR enthusiasts who were keenly anticipating extending their knowledge to cope with the more difficult orbit calculations and modifying their equipment to meet the requirements of this new satellite technique. It would be nice to hear that another attempt will be made in the not too distant future, to launch a replacement, but the expense required and the amount of work involved in providing a replacement, must be almost too daunting a prospect to contemplate with equanimity. We will, of course, keep readers informed of future plans as we hear of them.

# ... COMMENT

## MICROCOMPUTER FAMILY

The second photograph shows a selection of modules from the RCA Solid State CDP1802 COSMAC microprocessor. Designed for this consists of a complete family of single-board microcomputer systems based on the CDP1802 COSMAC microprocessor. Designed for the smaller volume user who needs to implement a microcomputer system rapidly and economically, the CDP18S600 Microboard family uses a universal plug-in backplane system for ease of setting up and modification, and is based on CMOS technology with its advantages of low power consumption and high immunity to electrical noise.

The RCA Microboard family comprises two single-board microcomputers with differing memory capacities, a range of add-on memory boards and expansion modules, 5-card and 25-card chassis/backplane units, a milliwatt power supply, and two prototyping systems. All Microboard modules are compatible with existing RCA COSMAC Development Systems to facilitate rapid hardware and software development.

Each RCA Microboard module measures 4.5 by 7.5 inches, and any Microboard module works in any location on the universal backplane. Software development can commence as soon as the modules are plugged in, and modules can easily be exchanged or added to match changing design requirements.

The use of CMOS technology means that power consumption is measured in milliwatts,



and a complete system can be powered from nickel-cadmium rechargeable batteries. Alternatively, the ability of the CMOS circuitry to operate over a wide voltage range allows low cost power supplies with extended regulation limits to be used. The low power consumption also eliminates the need for special cooling arrangements.

The RCA microcomputer family has excellent immunity to electrical noise, and will operate reliably in high-noise process-control, automotive or production monitoring environments, with no necessity for ground planes or extra decoupling capacitors.

Each of the RCA Microboard computers contains a CDP1802 microprocessor, crystal-controlled clock, read/write memory, parallel input/output ports, serial communications interface, "power-on" reset, expansion interface and sockets for user-selected read-only memories. The two computers are the CDP18S601 (4kbyte


RAM; sockets for 4/8kbyte ROM/PROM) and the CDP18S603 (1kbyte RAM; sockets for 4/8kbyte ROM/PROM).

Memory modules include 4kbyte, 8kbyte and 16kbyte RAM boards with battery back-up, and an 8/16kbyte ROM/PROM board. Other expansion modules available on Microboards are a UART interface, a combination memory-input/output module, digital/analog and analogue/digital converters, and a control and display module.

The two Microboard prototyping systems available from RCA each contain a Microboard computer together with a control/display module, a 5-card chassis in a protective case, a power converter, a breadboard for prototyping, cables and connectors, utility software, and technical literature.

The manufacturers are RCA Limited, Solid State - Europe, Sunbury-On-Thames, Middlesex, TW16 7HW.

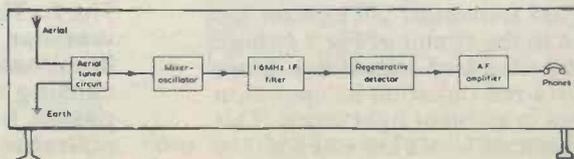"I know you got it out of the book, but it still doesn't sound right!"



# WINE TRAP WATCHER

By Owen Bishop

## Electronic watcher monitors wine trap bubbles and indicates the end of fermentation.

One of the joys of home wine-making is to sit back and watch the bubbles of gas passing rhythmically through the trap. Each bubble represents an increase in the final strength of the wine, so that the more bubbles the merrier! But when the wine has nearly finished fermenting, bubble-watching can become tedious. Has it really finished or is it "stuck"? Is it time to get on to the next stage of the process? When the bubbles come only once an hour, or even less frequently, a lot of time can be wasted in bubble-watching. Yet if you take your eye off the trap for even one second you can easily miss the bubble that you have been waiting for.

The device described here watches the trap for you. Set it and leave it; when you come back half an hour or more later an l.e.d. will be lit if there has been any bubble while you have been away. If there has been, press the Reset button to extinguish the l.e.d. and re-arm the watcher and return again later.

The trap watcher simply clips on to the main stem of the glass trap, which requires no modification. You only need one trap watcher and you just clip it to the trap of whichever demijohn is currently thought to be reaching the end of fermentation.

For those not yet initiated in the delights of home wine-making, the equipment can be obtained at Boots and from some health food stores. The basics consist of a 1-gallon demijohn, a cork stopper and the trap, which should be glass. The trap is partly filled with water.

### HOW IT WORKS

When the watcher probe is clipped onto the trap, the infra-red l.e.d., D1, is on one side of the trap tube and the photo-darlington transistor, TR1, is on the other. These are shown in the circuit of Fig.1 (where TR1 is represented as a standard transistor). Since the device works by infra-red radiation its operation is unaffected by changes in ambient light levels. This is specially important because wines are often left to ferment in cupboards or fairly dark rooms and it would be no use for the watcher to be triggered by the

opening of a cupboard door or the switching on of a light. The probe semiconductor components are positioned at the bottom of the trap loop so that the radiation from the l.e.d. passes through that part of the tube which contains water. Under these conditions the radiation is to a certain extent focused by the tube acting as a lens, and sufficient radiation reaches the phototransistor to cause a collector current to flow through R2. A low voltage, of about 1 volt, is passed to pin 1 of the CD4001 quad NOR gate, IC1.

The two gates associated with pins 1 to 6 form a bistable, and it will be remembered that the output of a 2-input NOR gate is high only when both its inputs are low. When the reset button S2 is pressed, pin 4 goes low, as also does pin 2. Since pin 1 is also low, pin 3 is high and the bistable remains in this state when S2 is released. The third gate functions as an inverter, and its output at pin 12 is now low.

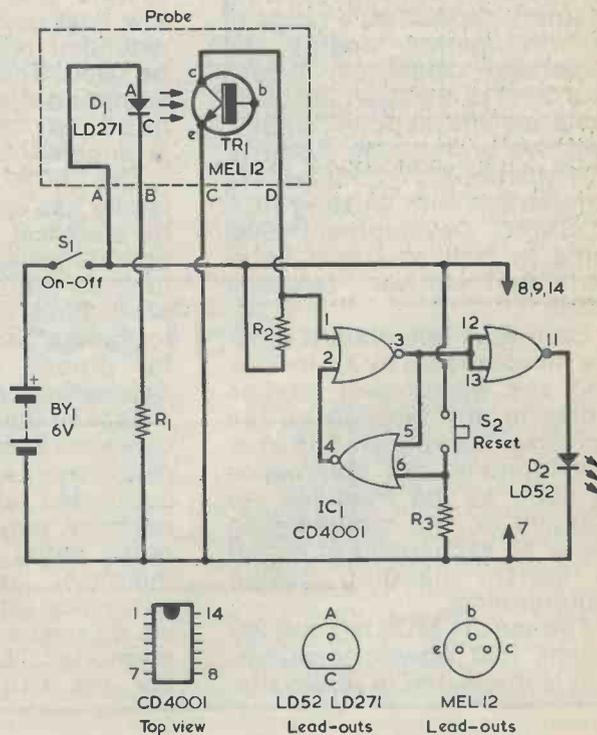


Fig.1. The circuit of the wine trap watcher. The infra-red light from D1 illuminates the phototransistor TR1, causing it to conduct. When a bubble passes between the two devices TR1 collector voltage goes momentarily high, triggers the CD4001 bistable and causes l.e.d. D2 to light up.


When a bubble passes through the trap tube between D1 and TR1 the refraction of light at the surface of the bubble causes a momentary reduction in the amount of radiation reaching the phototransistor. Its collector current reduces and the collector voltage goes high for a very brief period, causing pin 3 of the bistable to go low. Since both inputs of the lower gate are now low its output, at pin 5, goes high and the bistable latches in this new state. The low output at pin 3 turns on l.e.d. D2 by way of the inverter.

The bistable is returned to its previous state, with D2 extinguished, by pressing S2. S2 is also pressed to reset the bistable if it should happen to take up the triggered condition after switch-on at S1.

The phototransistor type MEL12 is available from Maplin Electronic Supplies. The LD271 infra-red l.e.d. specified for D1 may be obtained from A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London, NW6 4TA, as also may the LD52 specified for D2. However, D2 is not a critical component and any small red l.e.d. can be used here. Current consumption from the 6 volt battery is about 24mA with D2 extinguished and about 26mA when it is lit. The battery may consist of four HP7 cells, though it is more economical in the long run to use four HP2 cells. These can be fitted in a suitable battery holder. The circuit will work without modification from a 4.5 volt battery or a 9 volt battery, with current consumption proportionally reduced or increased accordingly.
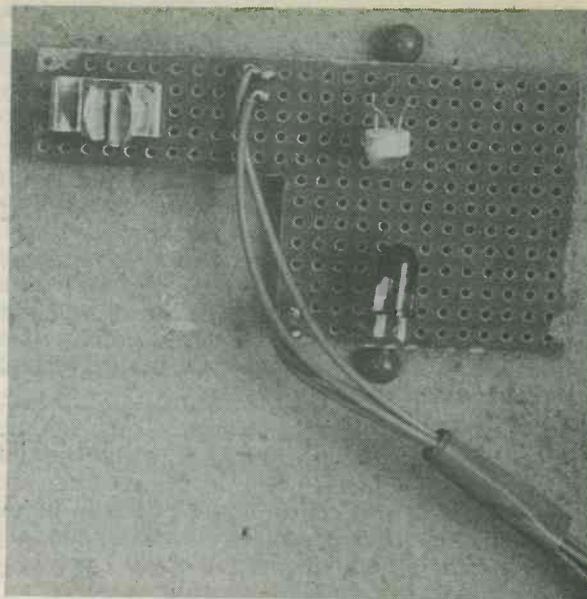
## CONSTRUCTION

The infra-red l.e.d. and the phototransistor are mounted on a small piece of 0.1in. Veroboard cut out as shown in Fig.2. A small metal clip of a size suitable for the main stem of the trap is secured to the board with a short 8BA bolt and nut. After cutting out the Veroboard the appropriate hole for the clip is drilled 8BA clear and the three cuts in the strips are made. Note that no connection is made to the base of TR1, and its lead-out may be cut short. After the two semiconductor devices have been soldered in approximately the correct positions, align them carefully by bending their lead-outs so that their axes coincide and



Close-up of the probe assembly. On this are mounted the metal clip, the infra-red l.e.d., the phototransistor and four Veropins for the connections to the main board.

so that, when the probe is clipped onto the trap, the radiation from l.e.d. to phototransistor passes across the whole diameter of the trap tube. This adjustment is not difficult to make, there being a tolerance of a millimetre or so in the positioning of l.e.d., phototransistor and tube.

The remaining circuitry is assembled on a Veroboard panel having the layout shown in Fig. 3. If mounting holes are required they may be drilled 8BA clear at holes 017 and C17. If such holes are drilled, it is desirable to cut the strips at P15, 015, N15, D15, C15 and B15 to isolate the mounting nut or spacing washer from the remainder of the board. IC1 is a

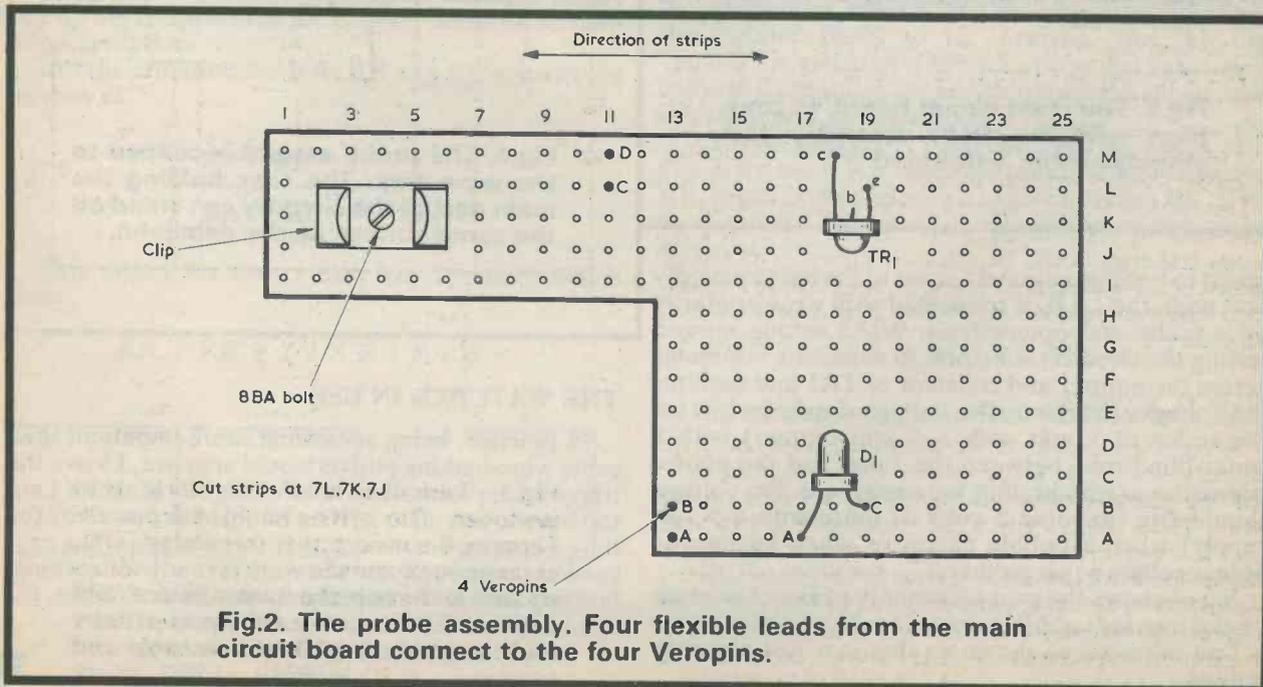


Fig.2. The probe assembly. Four flexible leads from the main circuit board connect to the four Veropins.

CMOS device which can be damaged by high static voltages, and it should be the last component to be soldered to the board, using an iron with a reliably earthed bit. Alternatively, a 14-way i.c. holder may be soldered to the board, and the i.c. plugged into this.

The Veroboard of Fig. 3, together with the on-off switch, Reset switch, 1.e.d. D2 and the battery may be fitted into any small plastic case, or plastic case with metal front panel, which will accommodate them. Four flexible leads about 15in. long pass from a hole in the side of the case to the probe board. The prototype, shown in the photograph, employed a sequential action push-button for S1, but a standard toggle switch would be preferable.

There should be no problems in setting up the circuit and getting it to work first time, though there is the difficulty of not being able to see whether the infrared 1.e.d. is on, off or not functional. When connected with correct polarity and functioning properly, there is a voltage drop of about 1 volt between the two terminals. If you measure this drop and

## COMPONENTS

### Semiconductors

D1 LD271  
D2 LD52 (see text)  
TR1 MEL12  
IC1 CD4001

### Resistors

(All  $\frac{1}{4}$  watt 10%)  
R1 180 $\Omega$   
R2 1k $\Omega$   
R3 15k $\Omega$

### Switches

S1 s.p.s.t. toggle  
S2 push-button, press to make

### Battery

BY1 6-volt battery (see text)

### Miscellaneous

Veroboard, 0.1in. matrix  
11-off Veropins, 0.1in. size  
Spring clip (0.3in. diameter)  
Case (see text)  
Nuts, bolts wire and wine.

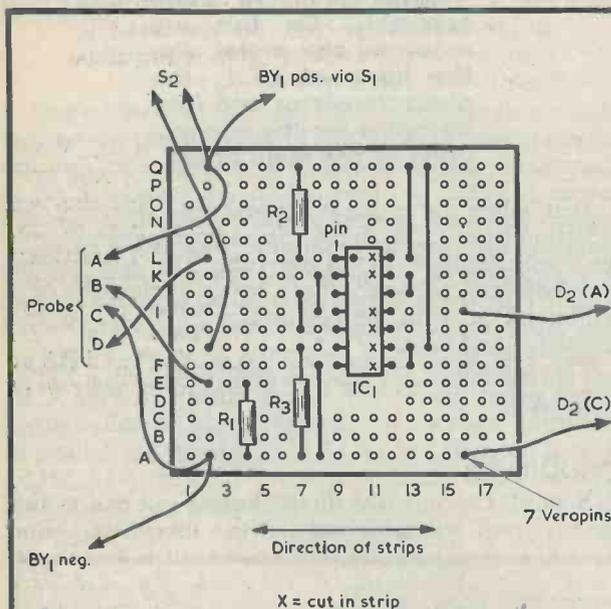


Fig.3. The main circuit board. In company with the probe assembly, this employs 0.1in. Veroboard.

find it to be approximately equal to the battery supply potential, the 1.e.d. is connected with wrong polarity or is faulty and open-circuit. When setting up and testing the circuit it is helpful to connect a voltmeter across the emitter and collector of TR1 and monitor the voltages obtained. The voltage should be low (of the order of 1 volt with a 6 volt battery) with a water-filled tube between the 1.e.d. and the photo-transistor, or with nothing between them. The voltage should rise (to some 3 volts or more with a 6 volt supply) when a bubble passes or when an opaque object comes between them.

Fig. 4 shows the probe assembly of Fig. 2 in place on the trap for bubble monitoring. The level of water is best adjusted as shown so that it is just about to bubble.

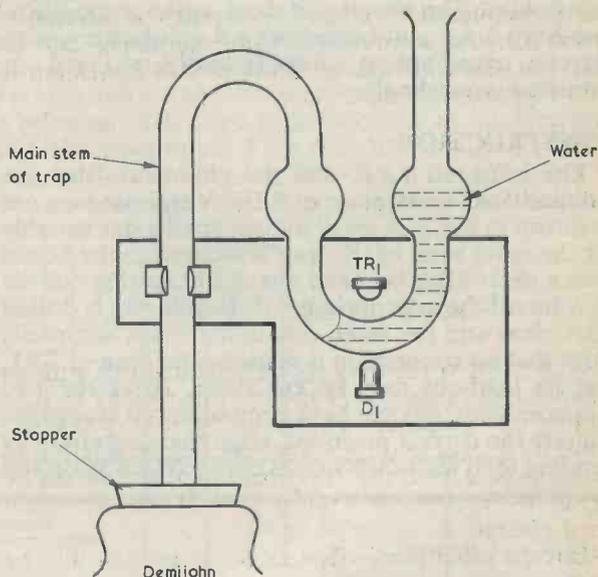


Fig.4. The probe assembly clipped to the wine trap. The case holding the main part of the circuitry can stand on the same surface as the demijohn.

## THE WATCHER IN USE

In practice, being somewhat more impatient than some wine-making purists would approve, I leave the trap watcher for half an hour or slightly longer if I am too busy to attend to it. If no bubble has passed by the time I return, I consider that fermentation has proceeded far enough and the wine is ready for racking, bottling and, in the happily not too distant future, for drinking.

Cheers!

# CALCULATORS AND PARALLEL - R

By R. J. Caborn

Parallel-R problems with low cost calculators are easy

Is your pocket calculator one of those inexpensive types with very basic logic and no memory? This is the sort of calculator which simply does the last thing you tell it to do. Ask it to solve  $2 + 6 \times 4$  and it will give you an answer of 32 instead of doing the multiplication before the addition and giving a proper answer of 26.

At first sight, such a calculator cannot do parallel-R calculations without fiddling about with paper and pencil. However, provided the calculator has a reciprocal ( $1/x$ ) key it can tackle parallel-R problems with a very easy keying sequence. As we shall see, the sequence is also suitable for calculators with higher level logic.

## PARALLEL-R

In Fig. 1 the total resistance,  $R_C$ , of two resistors,  $R_A$  and  $R_B$ , in parallel is given by the question.

$$\frac{1}{R_A} + \frac{1}{R_B} = \frac{1}{R_C}$$

At first sight the only way of tackling this with an inexpensive calculator is to begin by keying in  $R_A$ , finding its reciprocal and writhing that reciprocal down on a piece of paper. Then clear, key in  $R_B$ , find its reciprocal, add the reciprocal of  $R_A$  and finally key up the reciprocal of the answer. Hardly a streamlined operation.

But the equation for  $R_A$ ,  $R_B$  and  $R_C$  can also be written as

$$\frac{R_A + R_B}{R_A \times R_B} = \frac{1}{R_C}$$

This makes for a very easy key sequence which runs:

$$R_A + R_B = 1/x \times R_A \times R_B =$$

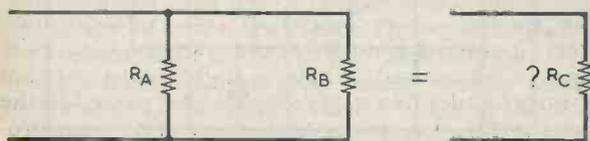


Fig. 1. A common problem in electronics. We know the values of  $R_A$  and  $R_B$ , but how do we find their combined value,  $R_C$ ?

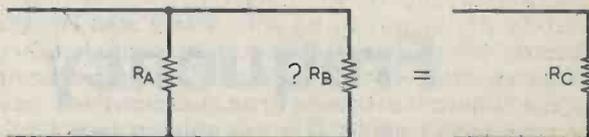


Fig. 2. Another version of the problem. What resistance,  $R_B$ , do we need to connect across  $R_A$  to give a required combined value of  $R_C$ ?

The answer after the second "equals" is  $R_C$ . What we are doing here is adding  $R_A$  and  $R_B$ , and then inverting the result by pressing  $1/x$ . After that we march all the way below the fraction bars of the equation with the multiplications by  $R_A$  and then  $R_B$ . The final answer is  $R_C$  without further inversion because  $R_C$  is also below the fraction bar. Try it with  $R_A$  at  $30\Omega$  and  $R_B$  at  $10\Omega$ . The answer is  $7.5\Omega$ . Again, run the sequence with  $R_A$  at  $27k\Omega$  and  $R_B$  at  $39k\Omega$ . The answer (corrected to 2 significant figures) is  $16k\Omega$ .

## FINDING $R_B$

Funnily enough, the first "equals" is not really required with the more inexpensive machines. After the addition of  $R_A$  and  $R_B$  the answer is already in the register ready to be inverted. But the first "equals" is essential with more powerful calculators because it separates the addition from the subsequent inversion and multiplication.

Another parallel-R problem crops up when, as in Fig. 2, we know  $R_A$  and want to find what resistance,  $R_B$ , to put in parallel with it to give a known  $R_C$ . If we carry out the same sort of calculation as before, we arrive at

$$\frac{R_A - R_C}{R_A \times R_C} = \frac{1}{R_B}$$

The corresponding calculator key sequence is:

$$R_A - R_C = 1/x \times R_A \times R_C =$$

Use the sequence to find what value ( $R_B$ ) we need to connect across  $20\Omega$  ( $R_A$ ) to give a final resistance ( $R_C$ ) of  $12\Omega$ . You'll find that the answer is  $30\Omega$  precisely.

Happy calculating!

# Modulated Alarm Generator

By I. M. Attrill

## Frequency modulated audio alarm with 10 watt output.

There are many types of electronic project where a relay is used to switch on an audible alarm generator when the circuit is activated. These are primarily alarm projects, such as burglar alarms, fire alarms, freezer alarms, etc. The audible signal can be produced by a bell, or other form of electromagnetic device, but it is increasingly common for an electronic circuit driving a loudspeaker to be used. This type of arrangement gives excellent reliability, and is usually very effective because quite complex sounds can be generated with little difficulty. It should perhaps be explained that for best results from this type of equipment a complex sound is far better than a simple one, such as a sine wave or other straightforward type of signal. Simple signals tend to be not very noticeable due to their monotonous nature and because they are readily masked by other noises. On the other hand, signals which are continually changing in some way are much more noticeable and are not easily masked by other sounds.

The circuit described in this article is for a powerful audible alarm generator which can be used in burglar alarm systems or for other warning purposes. When used with an 8Ω speaker and a 28 volt supply it offers an output power of over 10 watts, and this should be more than adequate for any normal applications. In some cases such a power would be in excess of what is required, but lower output powers can be provided by simply using lower supply voltages.

Alarm generators of this type normally give an amplitude or frequency modulated tone. A frequency modulated tone is, in general, more capable of catching attention, and frequency modulation is employed in the circuit presented here. The audio output tone is modulated up and down in pitch at a rate of a few Hertz, giving a sound that immediately makes its presence felt.

### TWO OSCILLATORS

The circuit is given in Fig.1, and this really breaks down into two sections, a high power audio oscillator based on IC2 and a low frequency modulating oscillator based on IC1. Both oscillators use the same type of circuit. The modulating oscillator employs an operational amplifier type 741 whilst the audio oscillator, which directly drives the speaker, uses a power amplifier type TDA2030. IC2 has an inverting (-) input and a non-inverting (+) input and can be looked upon as an operational amplifier incorporating a high power Class B output stage.

The TDA2030 is a modern device and it has the advantage that its heatsink tab is common with its


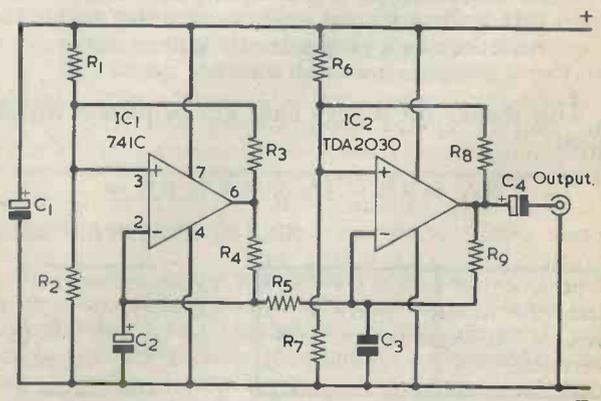


Fig.1. The circuit of the modulated alarm generator. Power output is dependent on the supply voltage.

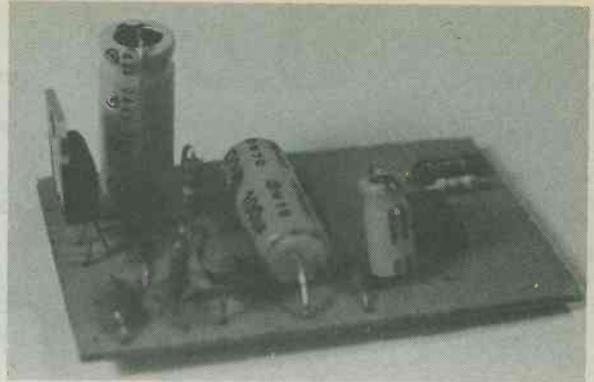The completed alarm generator unit. The use of a power i.c. with inverting and non-inverting inputs allows a low component count.



negative supply pin. In consequence there is normally no necessity for its heat tab to be insulated from its heatsink and the latter can be bolted directly to the tab. If the warning generator is housed in a metal case the i.c. heat tab can be bolted to one side of the case, whereupon the case itself provides heatsinking. It is necessary for the case to be common with the negative supply but such a connection is, of course, one that is normally employed.

The oscillator in which IC2 appears functions in the following manner. If R8 were not in circuit, the non-inverting input would be biased at half the supply potential by the equal value resistors, R6 and R7.

At switch-on C3 is discharged, whereupon the inverting input is negative of the non-inverting input and the i.c. output swings fully positive. R8 then causes the non-inverting input to be taken positive of the half-supply potential. C3 charges via R9. After a period, C3 charges sufficiently for the voltage at the inverting input to approach and become equal to the voltage at the non-inverting input. The amplifier output starts to swing negative and, due to the presence of R8, this causes the non-inverting input to go negative also. The result is that the inverting input is now further positive of the non-inverting input, so that the i.c. output swings more negative again. The regenerative action provided by R8 causes the i.c. output to very quickly swing fully negative, at which potential it is held by the charged C3.

C3 next commences to discharge via R9 into the now low amplifier output. As C3 discharges the inverting input goes negative until it approaches the voltage at the non-inverting input. A reverse process then takes place, with R8 again providing regeneration, and it ceases with the output fully positive again and with C3 once more charging.

Further cycles proceed in the same manner, giving an output square wave which, with the values specified and assuming that no frequency modulation is applied, is of the order of 1kHz.

As already mentioned, IC1 appears in the same basic oscillator circuit, but the component values around it are such that it oscillates at a much lower frequency, of only a few Hertz. The waveform across the continually charging and discharging C2 is roughly triangular, and the voltage on the positive terminal of C2 is applied via R5 to C3 in the audio oscillator. This arrangement provides frequency modulation of the audio oscillator, whose frequency increases as the voltage from C2 goes positive.

The output of IC2 couples to the loudspeaker via d.c. blocking capacitor C4. C1 is a supply decoupling capacitor.

## CONSTRUCTION

A suitable printed circuit design for the project is given in Fig.2, in which the board is reproduced full-size. This is etched and produced in the usual way and should not provide any difficulties. Other constructional methods incorporating stripboard or plain matrix board can be used if preferred, and the layout is not particularly critical provided that wiring is reasonably short.

IC2 is mounted vertically, with its heat tab just slightly outside the edge of the board. This allows it to


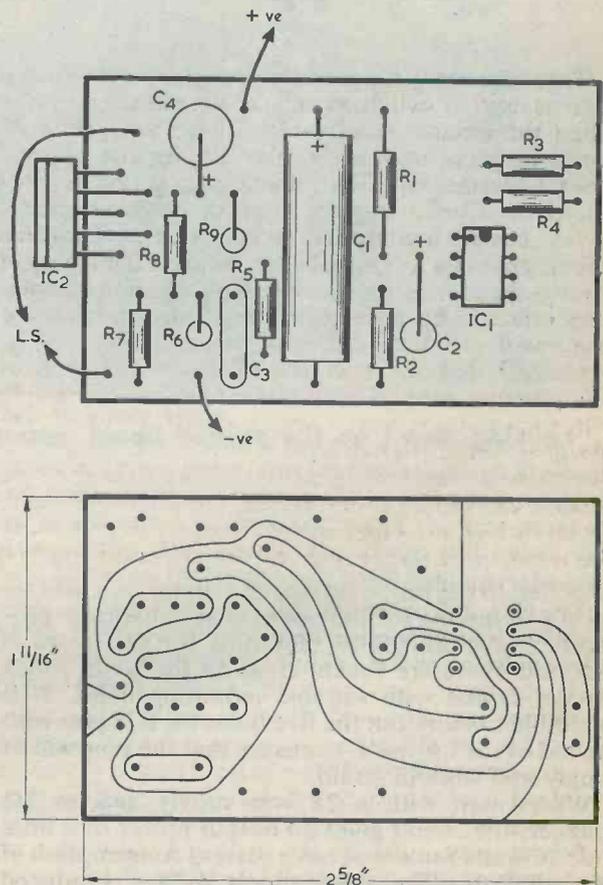


Fig.2. The alarm generator is assembled on a small printed circuit board. The heatsink surface of IC2 is just slightly outside the left hand edge of the board.

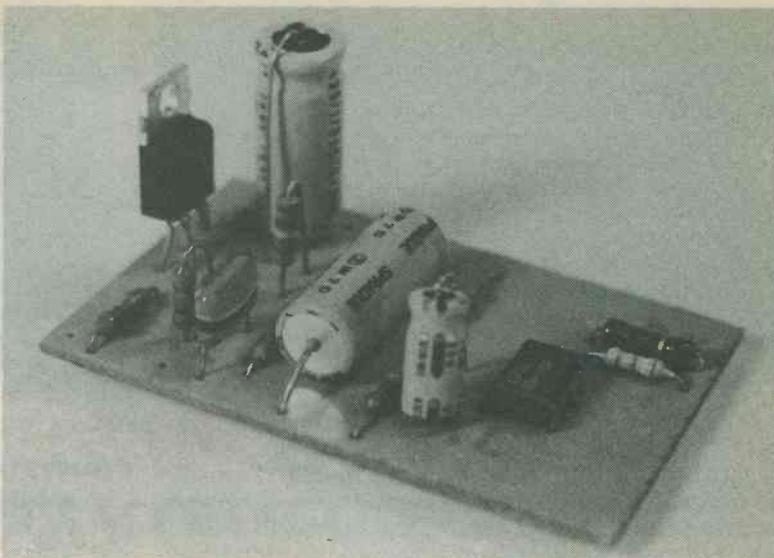Another view of the modulated alarm generator. The heat tab of IC2 is intended to be bolted to the side of a metal case.



## COMPONENTS

### Resistors

(All  $\frac{1}{4}$  watt 5%)

R1 4.7k $\Omega$

R2 4.7k $\Omega$

R3 22k $\Omega$

R4 39k $\Omega$

R5 27k $\Omega$

R6 56k $\Omega$

R7 56k $\Omega$

R8 270k $\Omega$

R9 120k $\Omega$

### Capacitors

C1 100 $\mu$ F electrolytic, 40 V. Wkg.

C2 10 $\mu$ F electrolytic, 25 V. Wkg.

C3 0.022 $\mu$ F type C280

C4 220 $\mu$ F electrolytic, 25 V. Wkg.

### Semiconductors


IC1 741 in 8 pin d.i.l.

IC2 TDA2030

### Miscellaneous

8 $\Omega$  loudspeaker of suitable power rating

Printed circuit board.

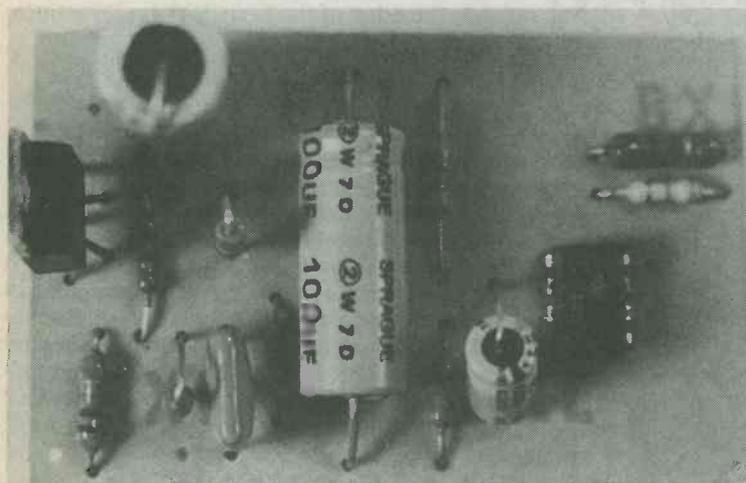

Looking down on the printed board assembly.

be bolted to the inside surface of a metal case, whereupon a mounting for the board is automatically provided. If a more robust mounting for the board is required, there are vacant areas on the p.c.b. which can be drilled with suitable mounting holes. It is advisable to mark out the five holes for IC2 pins with the aid of the i.c. itself, to ensure that the pins will fit snugly and without strain.

When used with a 28 volt supply and an 8 $\Omega$  speaker, the circuit gives an output power of a little over 10 watts r.m.s. and has a current consumption of about 550mA. The power supply voltage is reduced for lower output powers. With an 8 $\Omega$  speaker the output is approximately 5 watts r.m.s. with a 20 volt supply, 2 watts r.m.s. with a 12 volt supply and 1 watt r.m.s. when a 9 volt supply is used. Current consumptions at these three supply voltages are approximately 400mA, 275mA and 140mA respectively. The sup-

ply voltage must not be allowed to exceed 36 volts, which is the maximum permissible for both the i.c.'s. It is important to ensure that the 8 $\Omega$  speaker is capable of handling the output power fed to it.

Returning to the subject of heatsinking, this is mainly required with supply voltages of more than about 15 volts, and a small commercial finned aluminium heatsink of about 25 by 50mm. will suffice if anything more substantial is difficult to arrange. However, it is always preferable, wherever possible, to employ a heatsink that is significantly larger than the minimum required. The TDA2030 has thermal shut-down circuitry, and will simply stop working and draw very little supply current if it should be allowed to overheat. It will then work normally again when it has cooled down to a more acceptable temperature. The device also has output short-circuit protection circuitry. ■

# PASSIVE LOGIC PROBE

By M. V. Hastings

## DETECTS HIGH, LOW, FLOATING AND PULSING OUTPUTS.

## SUITABLE FOR T.T.L. AND CMOS.

A logic probe is a very useful item of test equipment for anyone who deals with digital circuits, even if they do so only occasionally. The purpose of a logic probe is merely to indicate the logic state at the point under investigation, and this can be accomplished with a simple passive circuit. Although they have their limitations such circuits are perfectly adequate in practice for nearly all logic tests. A very simple and inexpensive logic probe with an extended performance is described in this article, and it is suitable for use with CMOS and t.t.l. circuitry.

### CIRCUIT DESIGN

In its most basic form, a logic probe can consist of an l.e.d. indicator and series resistor, as shown in Fig.1 (a). The terminal marked "NEG" is connected to the negative supply rail of the logic circuit being checked, and the "IN" terminal is applied to the logic test points. If a test point is at 1 (or high) the l.e.d. will light up and if it is at 0 (or low) the l.e.d. will remain extinguished.


There are drawbacks with this ultra-simple arrangement. If the test point is between the two logic states, or is switching rapidly between the two states,


the l.e.d. will glow reasonably brightly, giving the impression of a steady logic 1 state. Also, if the test point is open-circuit the l.e.d. will not light up, giving the same indication as for a logic 0.

These problems can be partially overcome with the circuit of Fig.1(b), which has two l.e.d. indicators to show the logic state at the test point. As in the previous circuit the "NEG" terminal connects to the logic circuitry negative rail. The "POS" terminal connects to the positive supply rail, and the "IN" terminal to the test point. If the test point is at 1 RA and DA are effectively short-circuited, whilst DB lights up. The reverse happens with the test point at logic 0, and DA then becomes alight.

With the input disconnected, or connected to an open-circuit test point, current flows through DA and DB, and both l.e.d.'s light up. They will also both light up, to indicate a fault condition, if the test point is between the two logic levels. There still exists the flaw, however, that both l.e.d.'s will light up if the test point is switching rapidly between the two logic levels. What is required, ideally, is additional circuitry to allow differentiation between a faulty output state and a rapidly pulsing one.

Fig.1 (a). In its simplest form, a logic probe can consist of an l.e.d. and a series current limiting resistor (b). More meaningful indications are given with a probe having two l.e.d.'s.

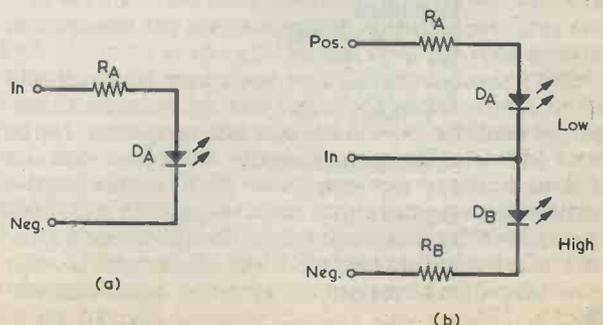

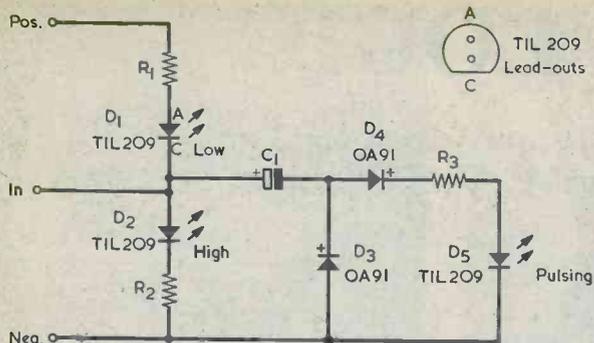


**Fig.2. The circuit of the passive logic probe.**

The circuit which was finally adopted is shown in Fig.2. and this overcomes the shortcomings of the previous circuits. R1, D1, D2 and R2 are the same as RA, DA, DB and RB in Fig. 1 (b), and behave in precisely the same manner. When there is a steady state at the input, no matter what this state happens to be, C1 provides d.c. blocking and the third l.e.d., D5, cannot be turned on. If, on the other hand, the test

point being checked is switching rapidly between the two logic levels, the input signal is coupled via C1 to diodes D3 and D4, which rectify it. The resultant positive pulses are then fed to D5 via current limiting resistor R3, and this time D5 does light up.

The accompanying Table summarises the logic probe indications for all the possible input states.

TABLE	
INPUT STATE	PROBE INDICATION
Low	D1 lights up
High	D2 lights up
Floating	D1 and D2 light up
Between logic levels	D1 and D2 light up
Fast pulsing	D1, D2 and D5 light up
Slow pulsing	D1, D2 and D5 pulse on at the appropriate rate

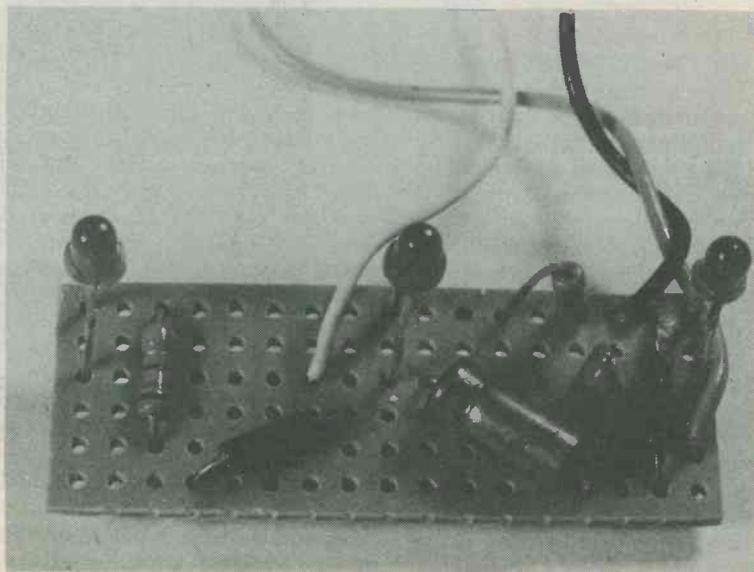

**The logic probe components are soldered to a 0.1in. Veroboard panel.**

### COMPONENTS

#### Resistors

(All 1/4 watt 5%)

R1 1.8kΩ

R2 1.8kΩ

R3 560Ω

#### Semiconductors

D1 TIL209

D2 TIL209

D3 OA91

D4 OA91

D5 TIL209

#### Capacitor

C1 10μ Felectrolytic, 25v. Wkg.

#### Miscellaneous

Verobox type 75-1469L

Veroboard, 0.1in. matrix

3 panel-mounting l.e.d. bushes

2 crocodile clips (see text)

6BA or M3 bolt, 1in. or more

Wire, solder tag, etc.

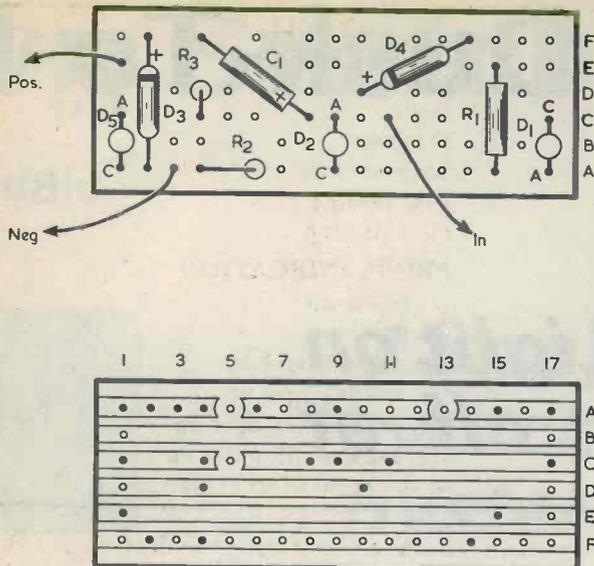



Fig.3. All the components are assembled on a small Veroboard panel, as shown here.

### ASSEMBLY


The components are accommodated on a small piece of 0.1in. Veroboard having 6 copper strips by 17 holes. This board is illustrated in Fig. 3. Be careful not to omit the three breaks in the copper strips, and remember that D3 and D4 are germanium diodes which can be overheated if the soldering iron is applied to their lead-outs for too long a period.

There are no mounting holes in the board, because it will be held in place firmly when D1, D2 and D5 are fitted into their panel-mounting bushes. The author's probe is housed in a plastic Verobox type 75-1469L, which has nominal outside dimensions of 71.5 by 49 by 24.5mm. A small case of this nature is required because it is intended that it be held in the hand whilst probing logic circuits.

The three holes for the l.e.d. bushes are drilled on the side of the case which is opposite the removable lid, and their centres are spaced by 0.8in. The layout is shown in the photographs. Legends taken from Panel-Signs Set No.4 (available from the publishers of this journal) are affixed to the panel alongside the l.e.d.'s, with D1 identified as "LOW", D2 as "HIGH" and D5 as "OSC". A test prod is secured to the case at the D1 end, and it consists of a 6BA or M3 bolt at least 1in. long. A solder tag is secured under the bolt head inside the case, and the "IN" connection from the component board is soldered to this. Two small holes are drilled in one of the 71.5 by 24.5mm. sides of the case, and the positive and negative supply leads pass through these. Flexible insulated leads about 2ft. long are required here. The positive lead should be red and the negative lead black. The leads are terminated in small crocodile clips with vinyl insulating sheaths having, preferably, the same colours as the wires.

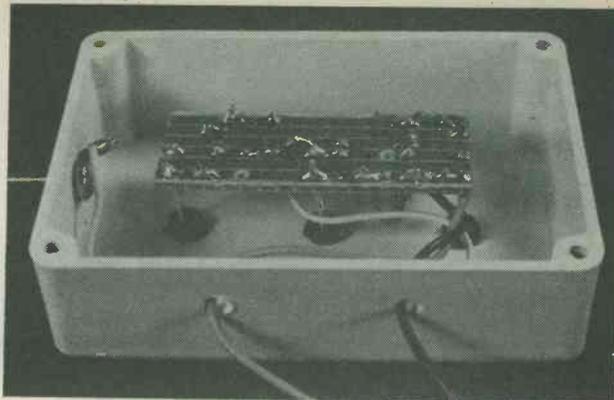

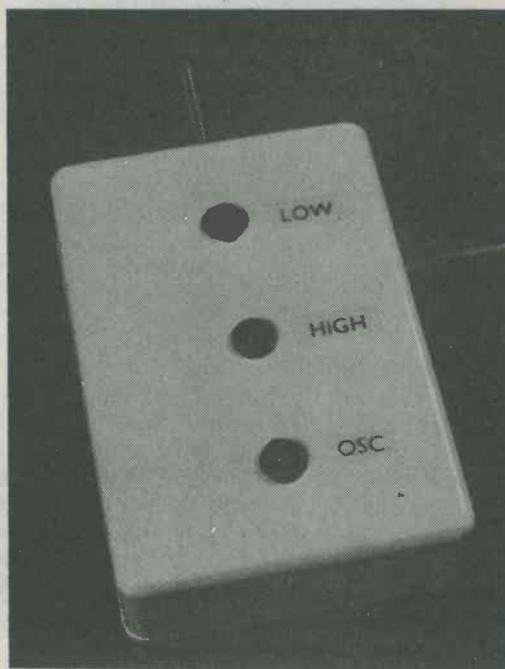The board is secured inside the plastic case by passing the three l.e.d.'s into their panel-mounting bushes.



The three l.e.d.'s take up the positions illustrated here

### USING THE PROBE

In use, the two crocodile clips are connected to the appropriate supply rails of the equipment under test, and the prod at the end of the case is applied to the circuit points which are being investigated. The current consumed by the logic probe depends on the supply voltage in the equipment being checked, but will only be in the order of 1.5 to 8 mA. The l.e.d. current can be quite low when the probe is used to check low voltage circuits, but results are satisfactory using standard l.e.d.'s, such as the TIL209 indicated in the Components list. "High brightness" l.e.d.'s are now available however and, if used will give even better results.

# Dusk-To-Dawn

By R. A.

## • Turns Light on at dusk, off at dawn.

This device is a light operated switch which turns on a lamp when darkness falls and switches it off again at dawn. It has two main uses, one of which is to automatically operate a porch light or a light in the hall. The other is to act as a burglar deterrent, for use when premises are to be left unoccupied for a few days. In this case the unit can switch on a hall light, a table lamp in a front room or any other light which will be visible from outside. An observer would then be given the impression that the premises are occupied.

### MAINS OPERATION

Since the unit will be controlling a mains load and will need to be switched on for prolonged periods, both circuit convenience and economy of use call for mains operation. As can be seen from the circuit diagram shown in Fig. 1, a simple unregulated mains power supply is employed. The mains supply is applied via on-off switch S1 to the primary of transformer T1, which provides isolation from the mains

and offers a suitably low secondary voltage. This is full-wave rectified by D1 and D2, with C1 acting as a reservoir and smoothing capacitor. The off-load voltage (when the relay is de-energised) across C1 is about 17 volts, this falling to about 13 volts under maximum load conditions (when the relay is energised). These quite large variations in supply voltage are unimportant in the present application.

A rather unusual feature in the light switching circuitry is the use of an LM380 audio power amplifier. In practice, this represents a good choice because the LM380 has high output current capability together with differential inputs. In consequence it behaves as an operational amplifier having a high power output stage.

The voltages applied to the non-inverting input at pin 2 of the LM380 is taken from the junction of R1 and the photoconductive cell PCC1. The resistance of PCC1 varies with the light falling upon it; the resistance is greater than 200m $\Omega$  in total darkness and falls to a few kilohms when the cell is brightly illumi-

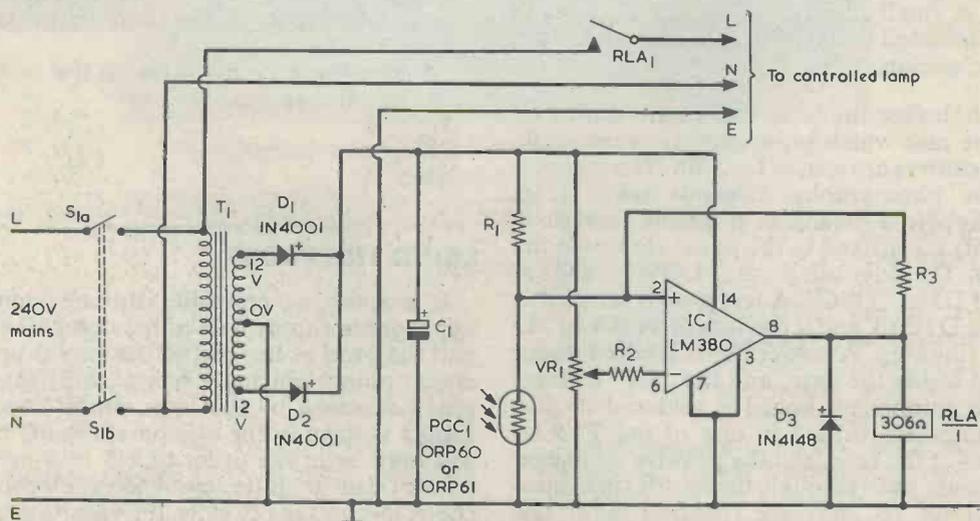


Fig. 1. The circuit of the dusk-to-dawn switch. IC1 functions as a voltage comparator with feedback to its non-inverting input via R3

# Lamp Switch

A. Penfold

## *•Snap-action switching with hysteresis.*

nated. The voltage applied to pin 2 therefore goes more positive as the illumination on the cell decreases.

A reference voltage selected by VR1 is applied to the inverting input at pin 6 via R2. VR1 is adjusted to give a reference voltage suitable for the conditions in which the unit is to be used. If the light on the photoconductive cell is high the non-inverting input of the LM380 is negative of the voltage on the inverting input and the output of the i.c. is fully negative. As the light falling on the cell decreases in intensity the voltage at the non-inverting input rises until it becomes equal to and commences to pass that at the inverting input. The i.c. output then swings fully positive. The reverse action takes place if the illumination on the photoconductive cell is initially low and then increases.


The coil of a relay is connected between the output of the LM380 and the negative rail and this is de-energised when the i.c. output is fully negative. It becomes energised when the i.c. output goes fully positive. The lamp which is controlled by the unit is coupled to the mains via a make contact set on the relay, with the result that this lamp lights up when the

light incident upon the photoconductive cell falls below the preset level. D1 is a protective diode which prevents the formation of a high reverse e.m.f. across the relay coil when the relay de-energises.

Reference has not yet been made to resistor R3, which provides a "snap-action" triggering effect, as well as hysteresis. The triggering effect is required because it would otherwise be possible for a certain critical light level to cause the output of the LM380 to lie at voltages which are mid-way between the fully negative and positive conditions. This is undesirable, because it could result in the relay alternating between the de-energised and energised states, with the controlled lamp being switched on and off accordingly. Hysteresis introduces a resistance to change. If the lamp is switched on at one low light level, the light intensity has to increase above that level by a significant amount before the lamp switches off again. The hysteresis ensures that the lamp is not switched on and off needlessly when the light on the photoconductive cell falls to the triggering level.

The effect of R3 is to provide positive regeneration from the output of the LM380 back to its non-inverting input. If the light intensity is high the

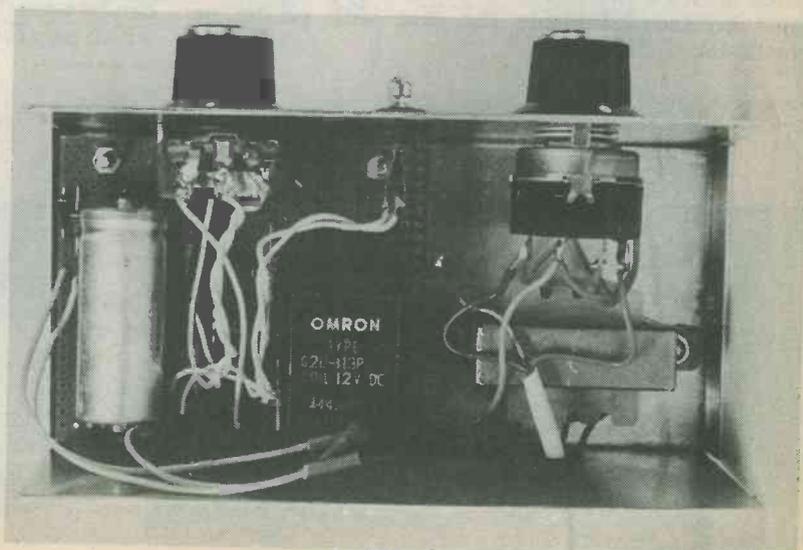Inside the case, the mains transformer is behind the on-off switch. The component panel is below and behind the sensitivity potentiometer. Connections to the photoconductive cell are made to its lead-outs, which project inwards from the front panel



LM380 output will be fully negative and R3 will be effectively in parallel with the photoconductive cell. As the light intensity decreases the voltage at the non-inverting input of the i.c. becomes equal to that at the inverting input. The i.c. output starts to go positive, whereupon R3 causes the non-inverting input to go further positive. The regenerative action results in the i.c. output changing rapidly to its full positive state. R3 is now effectively in parallel with R1 so that, to trigger the circuit to its previous state, the photoconductive cell resistance must fall to a lower value than that needed to trigger the i.c. output positive.

### CONSTRUCTION

The prototype switch is housed in a vinyl covered aluminium box having dimensions of 127 by 63 by 57mm. This is a case type WB1, available from Maplin Electronic Supplies. Any similar metal case will be suitable provided that it is large enough to accommodate the components.

S1 is mounted on the left-hand side of the front panel with VR1 on the right hand side. PCC1 is mounted in the centre of the panel, being held in a reasonably tight fitting rubber or p.v.c. grommet. If desired, the cell could be remote from the main unit, being coupled to it by way of a short length of 2-core cable. This could be terminated in a plug fitting into a suitable 2-way socket in the panel centre. However, the cable connecting to the cell should be kept well clear of mains wiring in case pick-up of hum or noise causes unpredictable operation. There is no risk of this when the cell is mounted as in the prototype, since the metal case automatically provides screening.

The cell can be either an ORP60 or an ORP61. These are identical except for the positioning of their light-sensitive areas. The ORP60 has its sensitive surface facing the end of the glass encapsulation, whereas the ORP61 has this surface facing one side (indicated by a coloured dot on the body of the component). When fitted as in the prototype, the ORP60 should be used.

Mains transformer T1 is mounted behind the on-off switch, well to the rear of the case. A solder tag is secured under one of its mounting nuts to provide a chassis connection. Two holes are required in the rear panel, one for the mains input lead and the other for the output lead passing to the controlled lamp. Both holes must be fitted with grommets and both leads must be secured inside the case with plastic or plastic-faced clamps.

### COMPONENTS

#### Resistors

(All fixed values  $\frac{1}{4}$  watt 5% unless otherwise stated)

R1 470k $\Omega$

R2 470k $\Omega$

R3 2.2M $\Omega$  10%

VR1 47k $\Omega$  potentiometer, linear

#### Capacitor

C1 1,000 $\mu$ F electrolytic, 25 V. Wkg.

#### Transformer

T1 mains transformer, secondary  
12-0-12V 100mA

#### Semiconductors

IC1 LM380

D1 1N4001

D2 1N4001

D3 1N4148

#### Photocell

PCC1 ORP60 or ORP61 (see text)

#### Relay

RLA1 306 $\Omega$  relay with changeover contact set  
(see text)

#### Switch

S1(a) (b) d.p.s.t., rotary toggle

#### Miscellaneous

Metal case (see text)

Plain matrix board, 0.1 in.

2 control knobs

Mains lead

Wire, nuts, bolts, etc.

The remaining components are assembled on a plain 0.1 in. matrix board having 27 by 22 holes. This is cut down from a larger board, after which the two mounting holes are drilled. Wiring is then carried out as in Fig.2, with component lead-outs pressed flat against the board underside and soldered to each other as required. Where lead-outs are too short, bridging leads of around 22 s.w.g. tinned copper wire can be used. The relay employed has connecting pins which pass through the board holes as indicated in the

Two holes, with grommets, are needed for the mains input and output leads. The output lead was not fitted when these photographs were taken




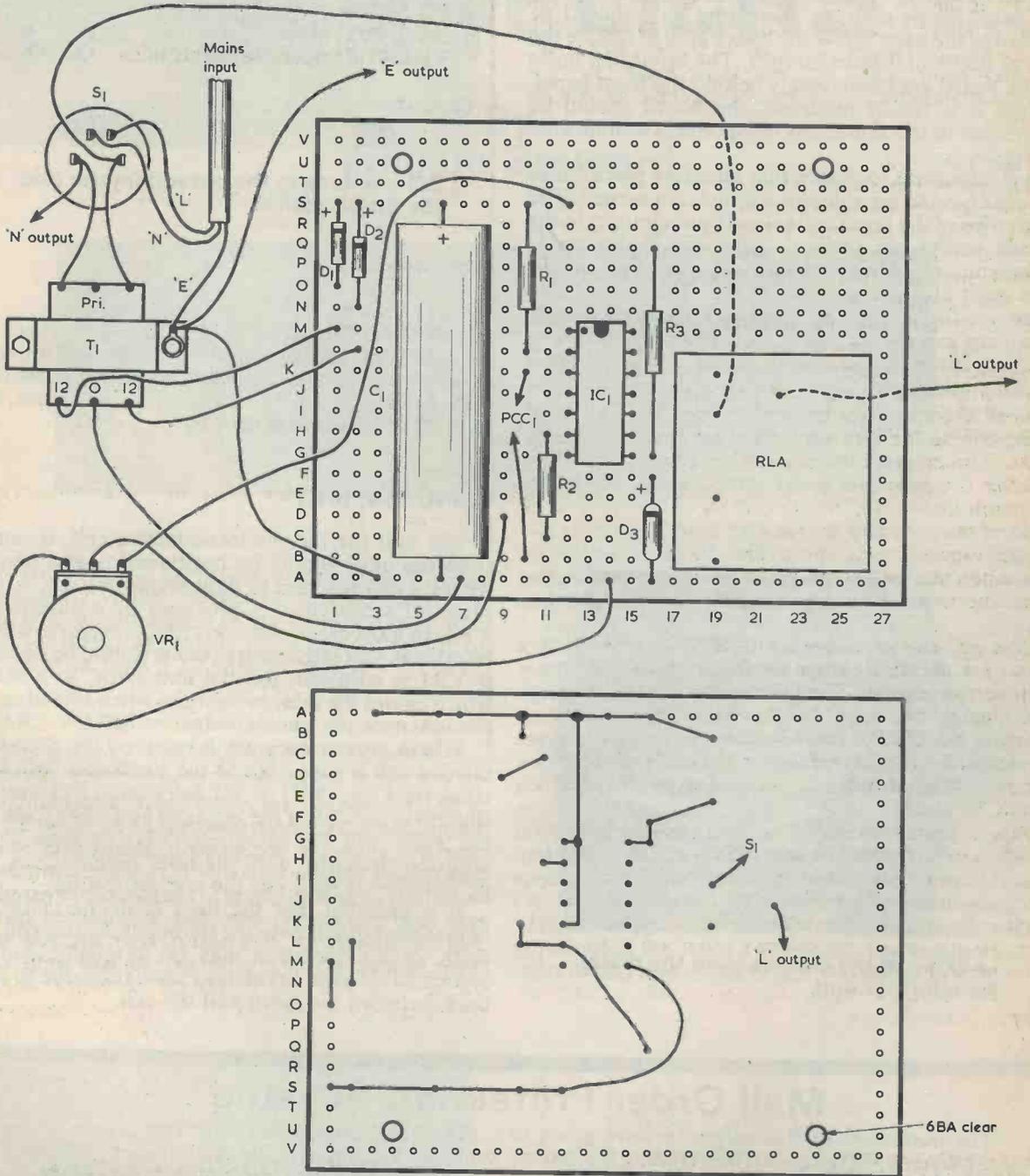


Fig.2. Most of the components for the switch are assembled on a plain matrix board. Interconnections are made below the board by way of component lead-outs and bridging wire.

diagram. This is a "Relay Flat 12V", which is also available from Maplin Electronic Supplies. At 250 volts a.c., its contacts are rated at 8 amps maximum for resistive loads.

The completed board is secured to the base of the case by 6BA screws and nuts, 12.5 mm. spacing washers keeping its underside clear of the bottom of the case. Strips of p.v.c. insulating tape should be affixed to the base below the board area to reduce the risk of accidental short-circuits. The mounting holes of the board are immediately behind the front panel. Before it is finally mounted, the board should be connected to the remaining components as indicated in Fig.2.

It is important to ensure that all safety precautions are observed so far as mains wiring is concerned. The earth wire of the input mains lead must connect to the chassis solder tag secured under the mains transformer mounting nut, and the earth wire of the output lead must also connect to this tag. The output lead passes to the controlled lamp and, if this is a table lamp, any metalwork on the lamp should be properly earthed. If the output simply passes to a lampholder without metalwork then the output lead will not require an earth wire. The unit should not be coupled into existing installed lighting circuits.

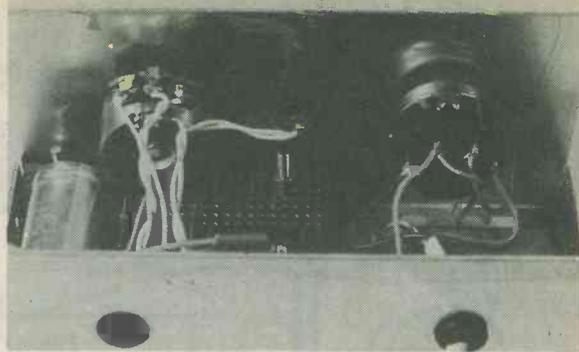

Connections to the potentiometer and the on-off switch


Before connecting to the on-off switch, check the tag positions with a continuity tester. With some switches the relative tag positioning may differ from that shown in Fig.2. The switch must, of course, be a type suitable for mains voltages.

#### USING THE UNIT

The unit (or the photoconductive cell, if remote from the unit) should be positioned near a window where it can respond to light levels outside. A wide range of sensitivities is provided by adjustment of VR1. In most cases, the exact triggering level will not be critical, and satisfactory results should be obtained if VR1 is adjusted, by trial and error, to a setting which causes the relay to energise when a hand casts a shadow over the photoconductive cell.

Where greater accuracy is required the photoconductive cell is subjected to the particular light level concerned and VR1 is set fully anti-clockwise. Its slider will then be at the negative end of its track and the relay will be energised. VR1 is then slowly adjusted clockwise until the relay de-energises. The potentiometer then has the correct setting.

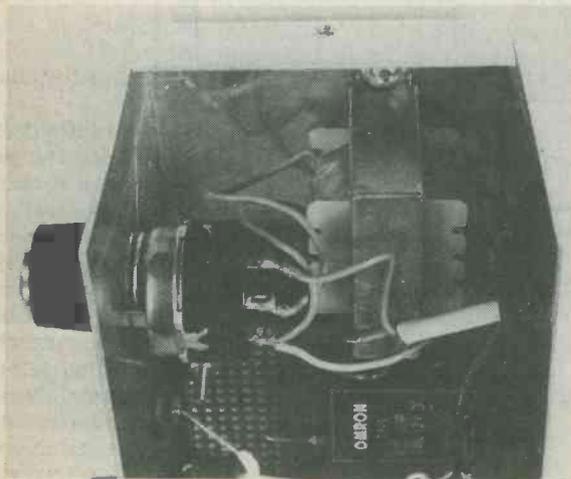It is essential that the light from the controlled lamp does not fall onto the photoconductive cell. If it does, circuit operation may be unreliable and the system could even break into oscillation due to feedback between the lamp and the cell. ■



Looking at the chassis from the mains transformer end

## Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who fail to supply goods or refund money and who have become the subject of liquidation or bankruptcy proceedings. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

# THREE VOLTAGE MULTIPLIERS

By  
William Steward

Obtaining increased voltages from fixed voltage supplies.

The circuit shown in Fig. 1 is capable of stepping up a fixed direct voltage between 8 and 15 volts to a higher level for the supply of low current equipment. It can, for instance, provide a low current supply of some 20 volts from a 12 volt car battery.


## SQUARE WAVE


IC1 is a bipolar 555 timer and it produces, at its output pin 3, a square wave having a frequency of approximately 350Hz. When the output voltage is high, C2 becomes charged via diode D1, whilst diode D2 is reverse biased. During the following low voltage output at pin 3, D1 becomes reverse biased and the negative terminal of C2 goes negative of the negative supply rail. D2 becomes conductive and the charge in C2 is passed into C3. An output voltage higher than that of the 8 to 15 volt supply then

becomes available between the original positive rail and the negative terminal of C3.

For maximum efficiency, the 555 output should be a 50:50 square wave in order that C2 should charge via D1 for the same length of time in which it then discharges into C3. A 50:50 output is achieved due to the choice of values for R1, R2 and R3. R2 and R3 are the two timing resistors normally associated with a 555 multivibrator and are given equal values. R1 is given a value which is 4 times (approximately) that of either R2 and R3. R1 increases the charging current for C1 and decreases the discharge current during the multivibrator cycle, and with the resistance ratios specified causes the 555 to produce a 50:50 output. (A fuller explanation of this effect was given in "50:50 Output From The 555" by J.R. Davies, which appeared in the April 1978 issue. The resistor value ratio is also applicable to the CMOS ICM7555).

Fig. 1. One of the voltage multipliers. Basically a voltage doubler, it produces an output voltage that is higher than the original supply voltage

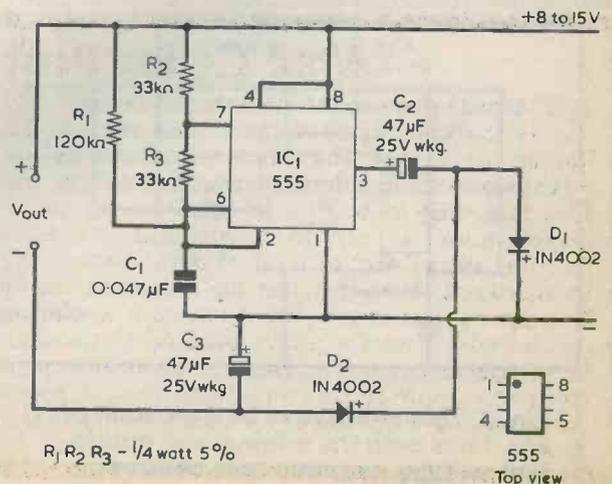

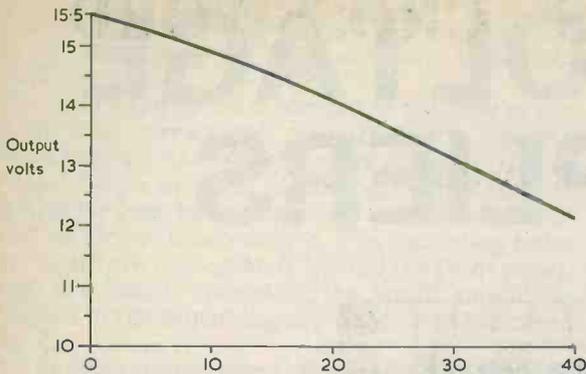


**Fig. 2. Regulation curve showing multiplied output voltage at different output currents with a 9 volt supply**

### VOLTAGE DOUBLER

The circuit of Fig. 1 is a classic voltage doubler but, in practice, the output voltage is significantly less than twice the supply voltage. This is due to four causes. First, there is an 0.6 volt drop in D1 when C2 charges and, second, there is another 0.6 volt drop in D2 when C2 discharges into C3. Thirdly, pin 3 of IC1 does not go fully to the negative rail when the output is low. The pin 3 voltage is about 0.1 volt positive of the negative rail at a sink current of 10mA, rising to some 0.5 to 0.8 volt at 40mA. The fourth cause is the most serious of all and is given when pin 3 of the i.c. is high. At very low source current the voltage at pin 3 is typically 1.2 volt negative of the positive rail, and this drop rises to about 1.5 volt at a source current of 40mA. These four factors cause the multiplied output voltage at zero output current to be equal to about 2.5 volts less than twice the original supply voltage. For a 9 volt supply the zero current output voltage is therefore 18 minus 2.5, or 15.5 volts, and for a 12 supply it is 21.5 volts.

The regulation of the output voltage is fairly good and a typical regulation curve for a 9 volt input is shown in Fig. 2. The output voltage drops from 15.5

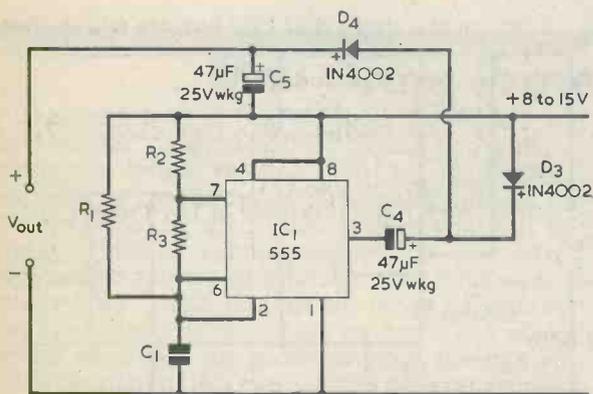


**Fig. 3. This alternative to the circuit of Fig. 1 has both the original and multiplied voltage negative rails common**

to slightly more than 14 volts at 20mA and to slightly more than 13 volts at 30mA.

Rectifiers in the 1N4001 to 1N4007 series can function with square waves up to around 5kHz before losing rectification efficiency, and so the choice of 350Hz for multivibrator frequency is reasonable. This frequency allows C2 and C3 to have fairly low values and no significant improvement in the regulation is given by increasing these.

An alternative circuit offering the same performance as that of Fig. 1 is shown in Fig. 3. R1, R2, R3 and C1 have the same values as in Fig. 1. This time, C4 charges via D3 when the 555 output is low, and then discharges via D4 into C5 when the i.c. output is high. With Fig. 3 the negative supply and multiplied voltage rails are common, whilst with Fig. 1 it is the positive rails which are common. These factors may determine which of the two circuits is chosen for any application.

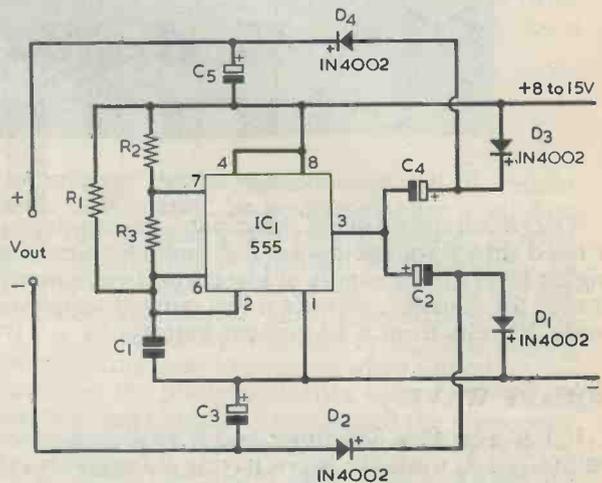


**Fig. 4. The two circuits combined. Component values are the same as were shown in Fig. 1 and Fig. 3**

The two circuits are combined in Fig. 4 to give output voltages which are both positive and negative of the original supply rails. The zero current output voltage is now 3 times the original supply less about 5 volts. However, the regulation is about 4 times worse than the regulation curve of Fig. 2 because the 555 output has to drive two circuits at the same time instead of one, and output voltage drops by some 5 volts at an output current of 10mA. An attractive application for Fig. 4 could be to have it power an operational amplifier whose output voltage is required to swing up to and outside both the original supply rails.

In all the circuits, the current drawn by the 555 for zero output current is around 5mA for an 8 volt supply rising to some 10mA for a 15 volt supply. The current drain increases proportionately with increasing output current from the multiplied output voltage.

# CONSTRUCTOR'S CROSSWORD

Compiled by J.R. Davies

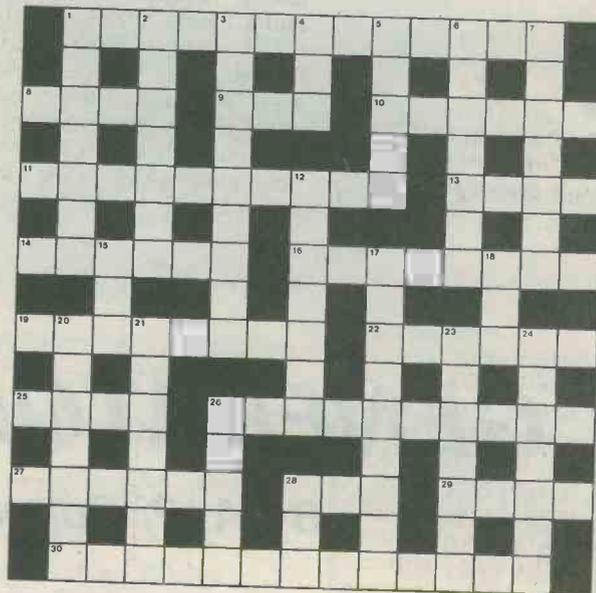

## Clues Across


1. Powerful X-measuring device. (13)
8. One small item lost in radio tape transfer. (4)
9. This PP3 battery gives more than 9 volts. (3)
10. Cliff-hanging transmission has its bits in sequence. (6)
11. Active device can sort strain out. (10)
13. Copper wiring aid. (4)
14. To react and/or resist. (6)
16. All one's inputs give zero output here. (4,4)
19. What good little red, green and blue beams do. (8)
22. To put in, with ion loss shows transducer shortcoming. (6)
25. This cell controls light intensity. (4)
26. Sees, dreads, mixed-up, words in RAM? (10)
27. Expansion of 16's function. (3,3)
28. Talk down to airmen. (1,1,1)
29. Large fire fairly does this to household current. (4)
30. F.M. circuit responding to proportional representation. (5,8)

## Clues Down

1. Computer controller favours metric units. (7)
2. Aintree beginner. (7)
3. Descriptive of distorting amplifier. (3-6)
4. Brute force morse modulation. (1,1,1)
5. Low noise microwave amplifier. (5)
6. Rotating the lathe controls. (7)
7. A display of digits. (4-3)
12. Another wiring aid comprises 6 of one and 4 of the other. (3-4)
15. TV camera horizontal sweep. (3)
17. Sound studio circuit which blanks out background. (5,4)
18. Even on the shelf, that PP3 battery will do this. (3)
20. Sixty seconds squared. (3,4)
21. Out of the norm. (7)
23. First component the serviceman checks. (7)
24. Put the data in again. (2-5)
26. Electronically sound. (5)
28. British radar could double at the races. (3)

(Solution on page 625)

# WIEN BRIDGE A.F.

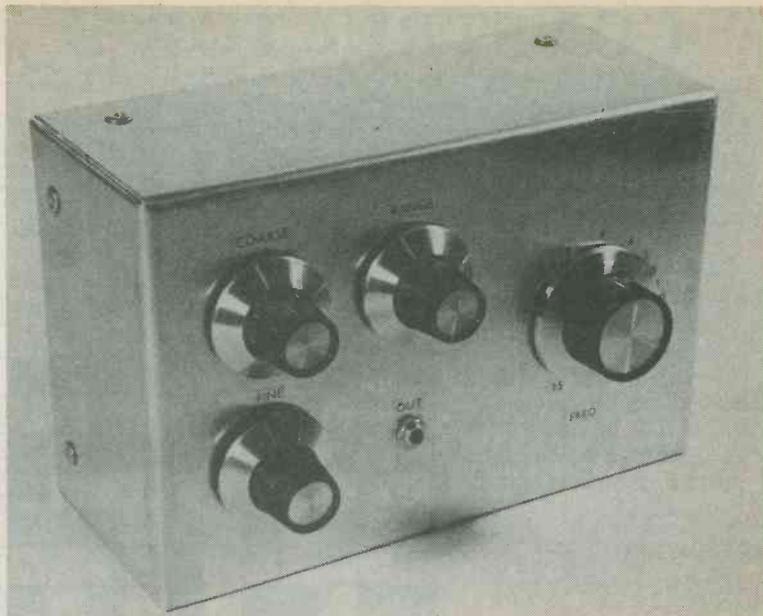

## SIGNAL GENERATOR

By A. P. Roberts

15Hz to 25kHz in 3 switched ranges

Automatic gain control maintains  
pure sine wave output.

An a.f. signal generator is a very useful piece of equipment to have in an electronics workshop, and even a simple instrument can prove to be invaluable on numerous occasions. The unit described here provides a sine wave output of good purity over a frequency range of about 15Hz to 25kHz. This is covered in three bands which have the following approximate limits: Range 1, 15Hz to 250Hz; Range 2, 150Hz to 2.5kHz; Range 3, 1.5kHz to 25kHz. The maximum output amplitude is about 1 volt r.m.s., but this can be attenuated to 100mV or 10mV r.m.s. by means of a switched attenuator. A continuously variable output attenuator is also incorporated. The circuit is battery powered.

### WIEN OSCILLATOR

In common with many other a.f. signal generators, this design employs a Wien Bridge oscillator. A Wien network has the basic circuit of Fig.1 (a), with the input-to-output frequency response of Fig.1 (b). In

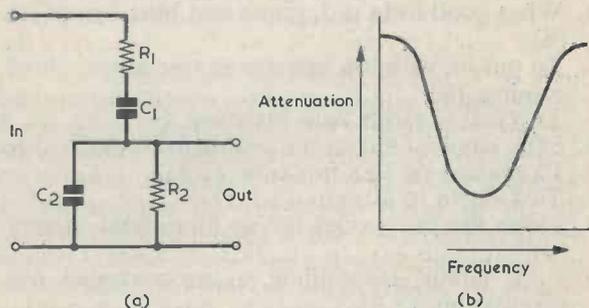


Fig.1(a). A Wien network has two resistors and two capacitors connected as shown here


(b). The network offers minimum attenuation at a frequency which is governed by the values of resistance and capacitance

effect, R1 and C1 form a high pass filter which attenuates lower frequencies, whilst R2 and C2 function as a low pass filter attenuating higher frequencies. If R1 is made equal to R2, and C1 equal to C2, the frequency of minimum attenuation is given by:

$$f = \frac{1}{2\pi RC}$$

Where R and C are the values of R1 and C1.

Fig.2 shows a typical Wien Bridge oscillator, in which the output of an operational amplifier is fed back, to the non-inverting input, by way of the Wien Bridge network. The circuit is capable of oscillating at the frequency of minimum attenuation in the network

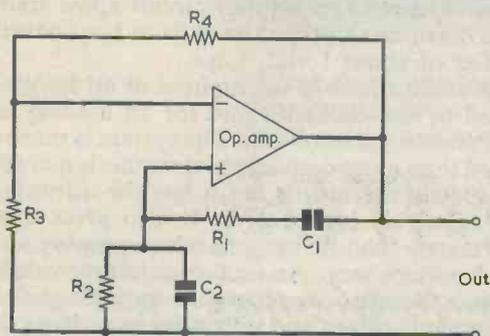

**Fig.2. Basic circuit for a Wien Bridge oscillator. Negative feedback is provided by R4 and R3, and these should provide just sufficient gain to allow oscillation to occur**

provided that the amplifier has sufficient gain to overcome the loss in the network which is given at that frequency. The voltage gain required by the amplifier is quite small, being only about 3 times.

It is, of course, an easy matter to provide such a low voltage gain. On the other hand it is important that the amplifier voltage gain should not be higher than that required to just produce oscillation at the Wien Bridge frequency, since the oscillation can then become violent, with clipping of the amplifier output signal and the creation of harmonics. Amplifier gain can be reduced by the negative feedback to the inverting input which is given by R4 and R3, whereupon the voltage gain is equal to R4 divided by R3.

At first sight it might appear that all that is required for satisfactory oscillation is to simply make R4 3 times the value of R3, and this could be achieved by using a pre-set variable resistor for one of these two components, the variable resistor being set up so that the amplifier has just sufficient gain to allow oscillation without clipping. In practice, however, a single setting of the resistor could not cater for slight variations in gain due to changes in temperature, supply voltage and loading, and the situation is made worse when, as in the present design, the resistances and capacitances in the Wien Bridge network are adjusted to provide different output frequencies. The only way of solving the problem is to use a gain control circuit in which the level of negative feedback is automatically adjusted to suit the particular operating conditions and the frequency at which the oscillator is running.

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{4}$  watt 5% unless otherwise stated)

- R1 4.7k $\Omega$
- R2 4.7k $\Omega$
- R3 680 $\Omega$
- R4 39k $\Omega$
- R5 680 $\Omega$
- R6 4.3k $\Omega$  2%
- R7 430 $\Omega$  2%
- R8 47 $\Omega$  2%
- R9 180k $\Omega$
- R10 390 $\Omega$
- VR1 10k $\Omega$  dual-gang potentiometer, linear
- VR2 5k $\Omega$  or 4.7k $\Omega$  potentiometer, linear, with switch S3

### Capacitors

- C1 100 $\mu$ F electrolytic, 10V. Wkg.
- C2 100 $\mu$ F electrolytic, 10V. Wkg.
- C3 1 $\mu$ F plastic foil, 5%
- C4 0.1 $\mu$ F plastic foil, 5%
- C5 0.01 $\mu$ F plastic foil, 5%
- C6 1 $\mu$ F plastic foil, 5%
- C7 0.1 $\mu$ F plastic foil, 5%
- C8 0.01 $\mu$ F plastic foil, 5%
- C9 10 $\mu$ F electrolytic, 10V. Wkg.
- C10 10 $\mu$ F electrolytic, 10V. Wkg.
- C11 100 $\mu$ F electrolytic, 10V. Wkg.

### Semiconductors

- IC1 LF351
- TR1 BC109
- D1 1N4148
- D2 1N4148
- D3 TIL209

### Photocell

- PCC1 RPY58A

### Switches

- S1 3-way 4-pole rotary (only 2 poles used)
- S2 3-way 4-pole rotary (only 1 pole used)
- S3 s.p.s.t. toggle, ganged with VR2

### Socket

- SK1 3.5mm. jack socket

### Miscellaneous

- Metal case (see text)
- Veroboard, 0.1in. matrix
- 9-volt battery type PP3
- Battery connector
- 4 control knobs
- Nuts, bolts, wire, etc.

## THE CIRCUIT

The full circuit of the a.f. signal generator is given in Fig.3. In this diagram the operational amplifier is an LF351, which has an f.e.t. input and gives low levels of noise and distortion. The non-inverting input is biased to half the supply potential by R1 and R2, the junction of these two resistors coupling to the input via R3 and VR1 (a). The junction is effectively at earth potential for audio frequencies due to the high value bypass capacitor, C2. This configuration allows the circuit to function with a single supply instead of the dual supplies that are normally employed with operational amplifiers.

The resistive parts of the Wien network are given by R3 plus VR1(a) and R5 plus VR1(b). VR1(a) and VR1(b) are the two halves of a dual-gang potentiometer, and this potentiometer provides continuous adjustment of oscillator frequency within the range selected by S1(a) (b). The switch selects the capacitive sections of the network, consisting of C3 and C6, C4 and C7, and C5 and C8, to give the three oscillator ranges.

Voltage gain is controlled by the negative feedback components PCC1 and R4. PCC1 is a cadmium sulphide photoconductive cell whose resistance decreases as the light intensity falling on it rises. When it is in total darkness (as it can be in the present design) it has a resistance of at least 200k  $\Omega$  which would allow a voltage gain in the operational amplifier of at least 5 times. Such a gain is sufficient to cause violent oscillation.

The output from the oscillator is coupled via C10 and R9 to the voltage doubling rectifier and smoo-

thing circuit comprising D1, D2 and C11. The rectified positive voltage is then applied to the base of TR1 and, if it is sufficiently high, causes this transistor to become conductive and to turn on the l.e.d., D3. R10 is a current limiting resistor.

The components are physically arranged so that the light output from D3 is aimed at the sensitive surface of PCC1. Thus, as soon as the l.e.d. lights up the resistance of PCC1 reduces, as also in consequence does the voltage gain of the operational amplifier. The circuit is then caused to stabilize at an output level from the operational amplifier which just allows D3 to turn on. The circuit cannot operate at a higher output level because D3 would then be brighter and reduce the resistance of PCC1, and it cannot operate at a level below that at which D3 is turned on because the PCC1 would then allow an excessively high gain. The circuit therefore gives gentle oscillation and a very pure low-distortion output. The component values in the rectifier circuit allow stabilization to occur at an output level from the operational amplifier of about 1 volt. r.m.s.

This stabilization is maintained at all frequencies covered by the oscillator and for all loading levels, within reason, on its output. The system is more complicated than more conventional methods incorporating a special thermistor but it has the advantage of being relatively inexpensive. It also gives a better performance than do systems which employ an f.e.t. in the feedback loop. An f.e.t. does not provide a true resistance because its resistance varies significantly with applied voltage and it thereby introduces distortion.

The output of the operational amplifier is applied


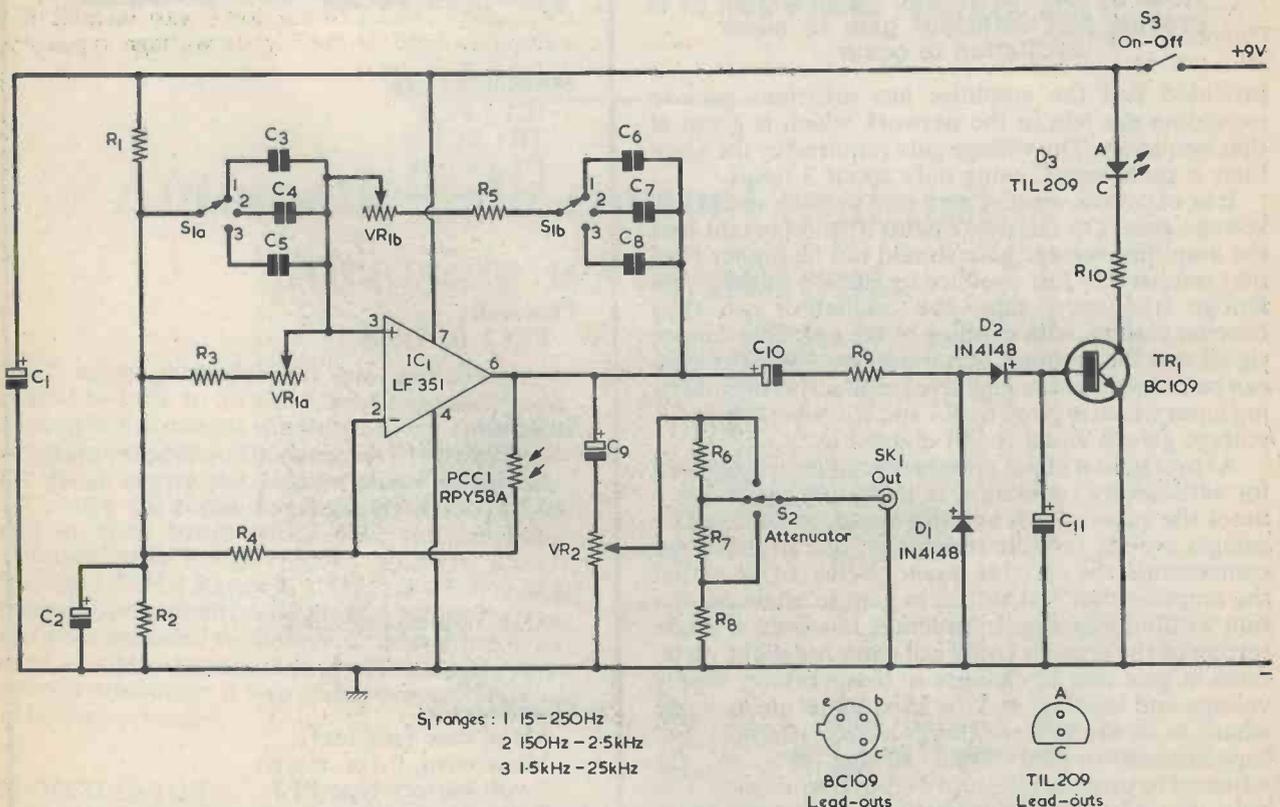


Fig.3. The complete circuit of the a.f. signal generator. The light output from D3 falls on the photoconductive cell PCC1, and this provides an automatic control which maintains amplifier gain at the level required for correct oscillation

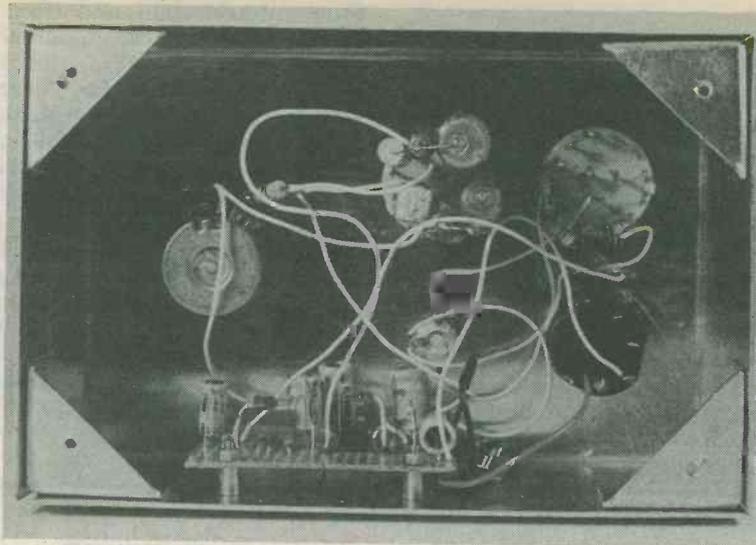


Apart from the components associated with the front panel, the main part of the circuitry is assembled on a Veroboard panel

via C9 to the continuously variable attenuator, vR2. The slider of this potentiometer connects, in turn, to the 3-step attenuator, given by R6, R7, R8 and S2. The output socket, SK1, is a 3.5mm. jack socket.

S3 is the on-off switch and C1 is the only supply decoupling component which is required. Current consumption from the 9 volt battery is only 3.5mA.

Most of the components are generally available. The photoconductive cell required for PCC1 is available from Maplin Electronic Supplies as also is IC1. A

reasonably good frequency registration between ranges is given if the capacitors in the Wien network have tolerances on value of 5% or better. Polycarbonate capacitors with 5% tolerance can be obtained from Maplin Electronic Supplies. The three attenuator resistors, R6, R7 and R8 should have a tolerance on value of 2% or, better, 1%. It is, of course, quite in order to employ  $\frac{1}{2}$  watt instead of  $\frac{1}{4}$  watt resistors here, if the higher wattage types are more readily available.

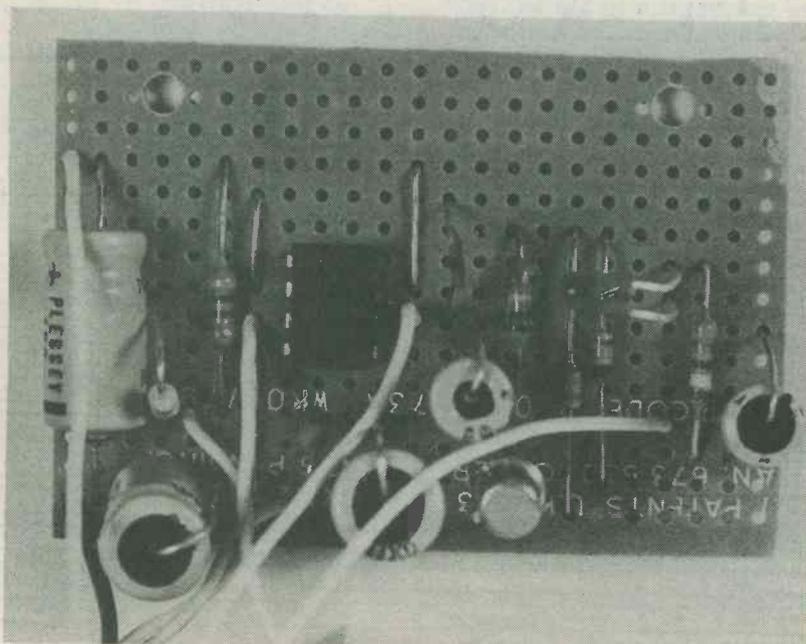

The Veroboard module. The l.e.d., D3, can be discerned with its light output directed towards the photoconductive cell

## CONSTRUCTION

The signal generator should be housed in an all-metal case, and the author employed an aluminium chassis with baseplate measuring 6 by 4 by 2½ in. The baseplate becomes the rear panel of the box thus formed. Any other metal case of about the same dimensions will be satisfactory and, for instance, an aluminium box measuring 6 by 4 by 3 in. is listed by Harrison Bros., P.O. Box 55, Westcliff-on-Sea, Essex, SS0 7LQ. The general layout can be seen in the accompanying photographs, and is not particularly critical.

Looking at the front panel, S2 and VR2 are to the left, with S2 above VR2. S1(a) (b) is to the right of S2 and the output jack socket is to the right of VR2.

Further to the right, and fitted with a larger knob, is the dual-gang potentiometer, VR1(a) (b). Secured to the bottom of the case with 6BA screws, nuts and spacing washers in the Veroboard assembly. The Veroboard is oriented such that its mounting holes are to the rear of the case. There is plenty of space for the battery, which can be held in place with a simple home-made clamp. The metal case is common with the negative supply rail, the connection being made via the mounting bush and nut of SK1.

The Veroboard is illustrated in Fig.4 and this is prepared and wired up in normal fashion. Note that IC1 has a Jfet and not a MOSFET input, so that it does not require any special handling precautions. The lead-out wires of D3 are bent at right angles, so that it is directed at PCC1. The two components do

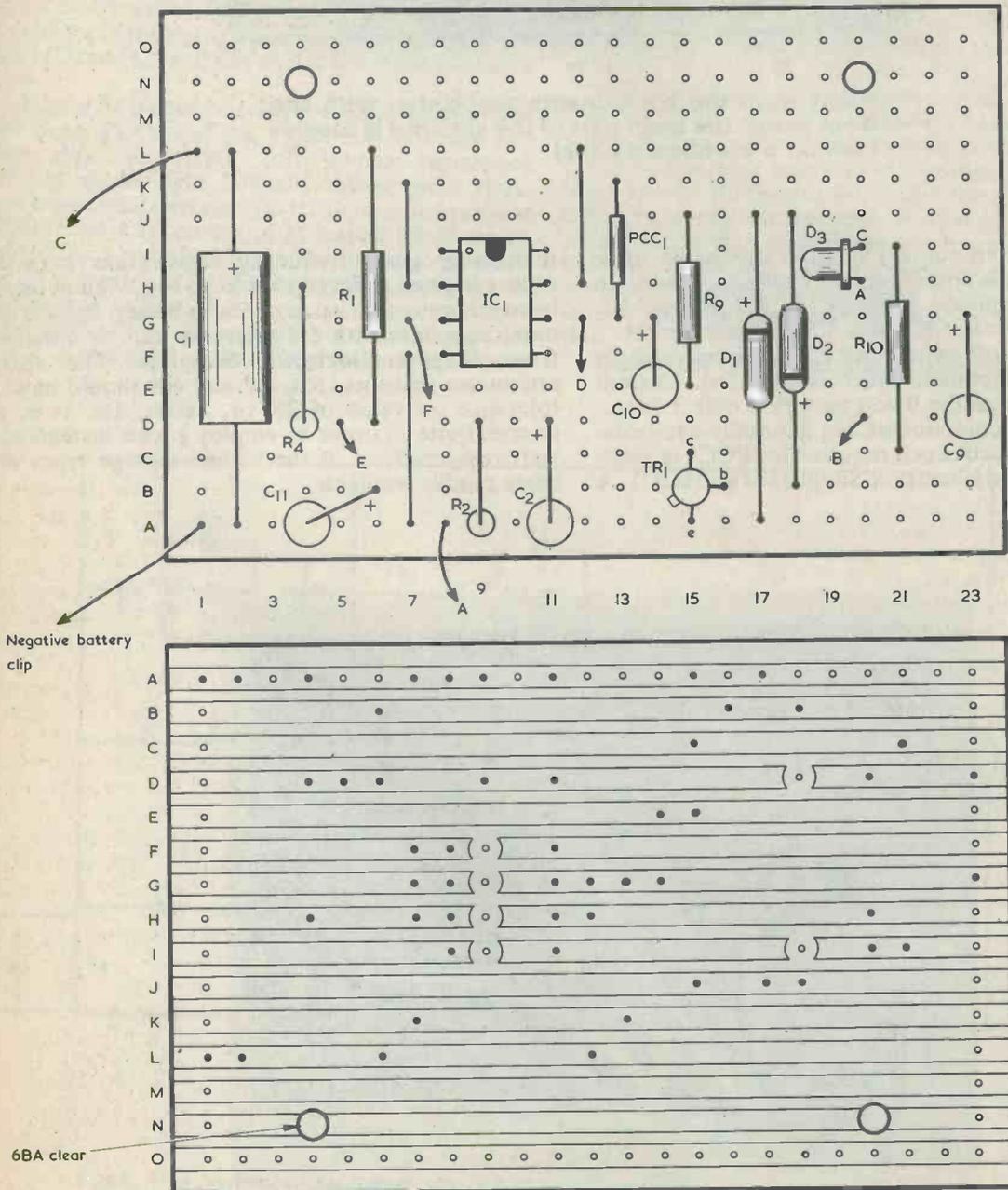


Fig.4. Details of the Veroboard assembly. The leads of D3 are bent through a right angle so that its light output is directed towards PCC1

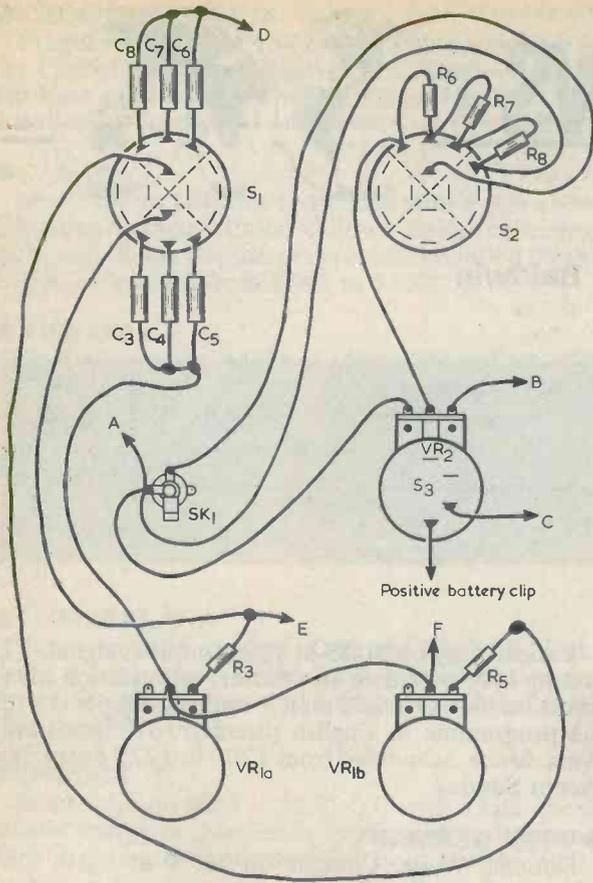


Fig. 5. The point-to-point wiring to the front panel components. The two sections of dual-gang potentiometer VR1 are shown separated to assist clarity. A tag on the adjacent pole of S2 is used as an anchor tag for R8. The letter references "A" to "F" correspond to the similar letters in Fig. 4


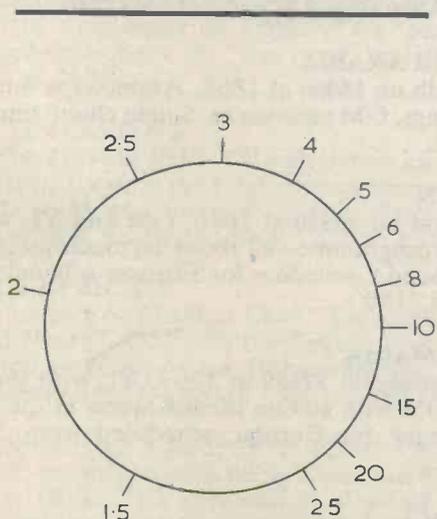


Fig. 6. This scale may be copied if suitable test instruments for calibration are not available

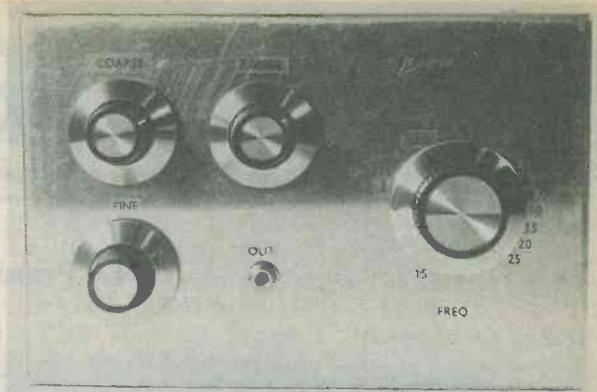

Front panel layout of the prototype.

not have to be adjusted so that they are right next to each other and they do not have to be carefully aligned. This is because in operation only a very small amount of light has to be received by PCC1 from D3 to produce the required stabilizing action. Even a poor coupling between the two devices will prove sufficient. The light sensitive surface of PCC1 faces the i.e.d., and this is the surface to which its lead-out wires do not connect.

The wiring external to the Veroboard is shown in Fig. 5. Interconnections to the board are identified by the letters "A" to "F". For example, point "A" in Fig. 4 connects to point "A" in Fig. 5. The two sections of VR1(a) (b) are shown separately for reasons of clarity.

When wiring has been completed and checked out, the signal generator is ready for testing and calibration.

### CALIBRATION

To obtain maximum usefulness from the signal generator it is necessary to provide a scale or otherwise indicate output frequencies around the control knob of VR1. Ideally, the dial would be calibrated with the aid of a frequency meter. If an accurately calibrated a.f. signal generator is already available this can be used to calibrate the unit. By listening to the outputs of both generators it is possible to adjust them to produce the same note and thus bring them to the same operating frequency. Another possible alternative is to use an oscilloscope and compare the signal generator output with the 50Hz mains supply. Calibration on any one range should be adequate for the other two ranges.


If no suitable test gear for calibration is available, the scale shown in Fig. 6 can be copied and used. This will give reasonable accuracy, although not as great an accuracy as is possible with the other methods.

Several points need to be made before ending. After switch-on, or when S1(a) (b) or VR1(a) (b) is adjusted, the circuit may take a second or two to adjust the gain to the required level. During this brief period the generator may oscillate violently or cease to oscillate. This slow response time is quite normal in signal generators of this type and, indeed, is desirable in the interests of low distortion since it means that the resistance of PCC1 cannot alter at oscillation frequency.

Finally, the signal generator can only function if ambient light is excluded from PCC1. The circuit will therefore fail to oscillate when the rear panel of the case is removed, or even if the case is not reasonably light-proof.

# SHORT WAVE NEWS

## FOR DX LISTENERS

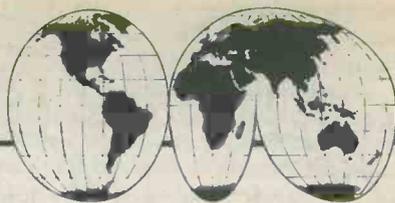

By Frank A. Baldwin

*Times = GMT*

*Frequencies = kHz*

We are now in the season for LA (Latin American) dx'ing and many listeners will be burning the midnight and early morning oil in attempts to log some of the many transmitters currently operating from that continent. Listed below are a few recently received stations logged on the 60 metre band – the paradise for LA-philes.

### ● COLOMBIA

La Voz del Cinaruco, Arauca, on **4865** at 0211, OM with a talk in Spanish about Colombian internal affairs. "The Voice of Cinaruco" has a 24-hour schedule and the power is 1kW.

La Voz del Norte, Cucuta, on **4875** at 0213, local-style dance music, OM with full station identification at 0215. The schedule is from 1000 to 0500 and the power is 5kW.

Emisora Meridiano 70, Arauca, on **4925** at 0234, OM with announcements in Spanish followed by a sports commentary. The schedule is from 1000 to 0330 (to 0500 on Saturdays) but all times are variable. The power is 1kW and this station identifies as "Radio Centro".

### ● ECUADOR

Radio Centinela del Sur, Loja, on **4890** at 0223, OM with announcements in Spanish, local-style music, identification and sports commentary at 0230. The schedule is from 1145 to 0430 (variable closing time), the power is 2.5kW and it identifies as "Radio Musical".

### ● HONDURAS

Radio Progreso, El Progreso, on **4920** at 0230, OM announcements in Spanish, identification. Schedule is from 0900 to 0500 (Sundays to 0700) and the power is 5kW.

## AROUND THE DIAL

### ● VATICAN

Vatican City on **11700** at 2100, interval signal followed by station identification and the French programme for West Africa, scheduled from 2100 to 2115.

Vatican City on **21485** at 1200, interval signal, YL (young lady = female announcer) with station identification then OM (old man = male announcer) with the programme in English directed to Central and West Africa, scheduled from 1200 to 1220 every day except Sunday.

### ● WEST GERMANY

Deutsche Welle, Cologne on **21590** at 1210, OM with a talk in the German programme beamed to South America, scheduled on this channel from 1200 to 1220.

### ● GREECE

Athens on **21455** at 1217, YL with songs, local-type music in the Greek programme intended for North America, scheduled from 1200 to 1250.

### ● ALGERIA

Algiers on **11810** at 2104, OM with a newscast in the English programme radiated in the External Service – target area unknown – scheduled from 2100 to 2130. Also logged in parallel on **11740**.

### ● SAUDI ARABIA

Riyadh on **15060** at 1858, Arabic-type music, YL with songs, OM announcer. Single chime time-check at 1900.

### ● SPAIN

Madrid on **15340** at 2046, OM and YL with the English programme – all about the medieval battles in and around Grenada – for Europe, scheduled from 2010 to 2110.

### ● ROUMANIA

Bucharest on **17850** at 1307, YL with the world news, OM with station identification in the English programme for Europe, scheduled from 1300 to 1330.

### ● ISRAEL

Jerusalem on **11630** at 1512, OM with a talk in Hebrew in a relay of the domestic service Network B for listeners abroad, scheduled from 1400 to 2315 on this channel.

## ● CZECHOSLOVAKIA

Prague on 17840 at 1532, OM with a newscast in the English programme for Africa, South Asia, the Far East and Europe, scheduled from 1530 to 1625. Also logged in parallel on 11990.

## ● CANADA

Montreal on 11935 at 1550, OM with a talk about Canadian financial affairs – fellow inflation sufferers I gathered – in the English programme intended for the USSR, scheduled from 1545 to 1600.

## ● KUWAIT

Radio Kuwait on 11665 at 1803, OM and YL with the English programme to Europe, and the Arabian Gulf, scheduled from 1800 to 2100 on this channel.

## ● AUSTRIA

Vienna on 6155 at 1834, OM with the local news in the English programme for Europe, East and South Africa and the Middle East, scheduled from 1830 to 1900.

## ● SWITZERLAND

Berne on 6165 at 1841, OM and YL with 'Talk-back', a programme in the English transmission for Africa, South America and Europe, scheduled from 1815 to 1845.

## ● SWEDEN

Stockholm on 6065 at 1850, YL with a talk about atomic energy in Sweden in the English programme for Europe and Africa, scheduled from 1830 to 1900.

## ● BULGARIA

Sofia on 17825 at 1857, OM with station identification in the English programme to Africa, scheduled from 1830 to 1900.

## ● NETHERLANDS ANTILLES

Bonaire on 17695 at 2115, OM with a programme about stamp collecting in the English transmission to Central and West Africa, scheduled from 2030 to 2120. This is a relay of Radio Nederlands, Lopik.

## ● NEW ZEALAND

Wellington on 15345 at 0442, light orchestral music, OM announcer in English, six 'pips' and announced time-check for "five p.m.", station identification at 0500.

## ● SWITZERLAND – 2

Berne on 21570 at 1315, YL with station identification and world news in the English programme for the Far East, South and South East Asia, Europe and North America, scheduled from 1315 to 1345.

## ● SOUTH AFRICA

Johannesburg on 21535 at 1309, "Big Band Sound with Ted Heath", OM with the English programme for Central and East Africa, Europe and the Middle East, scheduled from 1300 to 1550 (to 1600 on Sundays).

Johannesburg on 3250 at 1812, YL with pop song in English, the programme being wiped out by interference at 1814. This is 'Radio Five' which broadcasts in English and Afrikaans from 0300 to 0545 and from 1535 to 2200.

## ● CHINA

Radio Peking on 6590 at 1810, YL with the English

programme for South Asia, scheduled here from 1800 to 1900.

Radio Peking on 7480 at 1814, OM with the programme in Persian directed to Iran and Afghanistan, scheduled from 1800 to 1830.

Radio Peking on 7525 at 1805, OM with the programme in Standard Chinese to Europe, North Africa and West Asia, scheduled on this channel from 1730 to 1830.

Radio Peking on 9900 at 1918, YL with Chinese songs in the Hausa programme intended for West Africa, scheduled from 1900 to 1930.

CPBS (Central People's Broadcasting Station) Peking on 11290 at 2005, OM in Chinese in the Domestic Service 1 programme for local consumption, scheduled on this frequency from 2000 to 2200.

Radio Peking on 11575 at 1912, Chinese orchestral music during the French programme to Europe and Africa, scheduled from 1830 to 1930.

Whilst trying to receive the foregoing channels, why not try 6520 between 1830 and 1925 GMT when Radio Peking broadcasts in Russian with a reversed tape transmission? The purpose of such transmissions is unknown although several theories have been advanced. Even if you don't understand what you hear – and who does? – at least you can enter into your log one of the strangest of all short wave broadcasts.

## ● NORTH KOREA

Seoul on 7550 at 2007, OM with the local news in the English programme for Africa and Europe, scheduled from 2000 to 2030.

## ● CONGO

R.TV Congolaise, Brazzaville, on 3265 at 1820, local-style music, drums, YL with a song in vernacular. The schedule is from 0400 to 0700 and from 1700 to 2100 (closing time is variable) and the power is 50kW.

## ● LIBERIA

ELWA Monrovia on a measured 3227 at 1825, OM with a sports commentary in English. The schedule is from 0600 to 0800 and from 1805 to 2220 and the power is 10kW. Supposedly only a vernacular service on this channel!

## ● CAMEROON

A new one here. Bafoussam on 4000 at 1835, OM with a news commentary in English. Schedule and power unknown at the time of writing, but thought to be about 20kW.

## ● PORTUGAL

Lisbon on 6185 at 0517, OM with the local news in the English programme for Western Canada and all USA, scheduled from 0500 to 0530.

## ● JAPAN

Tokyo on 21610 at 0747, YL with songs in Japanese, OM announcer in the French programme to Europe, scheduled from 0730 to 0800. OM with station identification and announcements at the commencement of the English programme for Europe at 0800, scheduled from 0800 to 0830.

## ● AUSTRIA

Vienna on 6000 at 0458, interval signal of chimes, YL with many identifications in Austrian, schedule of the 0500 programme on this channel is unknown.

# In your Work -Shop

# THE SHUDDERY PICTURE

Here's your chance to beat  
Smithy at his own game.

## "Shuddery Picture"

Dick looked at the tag tied to the black and white television set on his bench and frowned. For many years he and Smithy had been servicing sets which were frequently sent to them without an indication of their faults, so that not only did they have to repair each set but they had first to find out what it was in the set that *needed* repairing. In most cases the faults were obvious enough but there had been one or two annoying misunderstandings. There had been the perfectly serviceable colour television receiver which Smithy had decided to put on soak test for several days to check whether it had an intermittent, only to find later that the customer's aerial had blown down and was picking up only sufficient signal to resolve a noisy monochrome picture with little colour. And there had been the little novelty radio housed in a very realistic copy of a Coca-Cola bottle which had stood on the "For Repair" rack for over a week because Smithy thought that Dick had brought it in for lunch-time refreshment whilst Dick had thought that Smithy had done precisely the same thing.

So Smithy had started a campaign and now nearly all the sets came in with a note defining the customer complaint. Some of these had

mildly surrealistic undertones, such as the description "Power Getting Through" appended to a music centre with an almost ear-shattering mains hum, but in general the system was working well.

"Shuddery Picture" looked promisingly explicit. Dismissing the fleeting thought that perhaps the set only worked when Hammer horror films were being transmitted, Dick connected an aerial to it, plugged it into the mains and switched on.

## PICTURE TROUBLE

The sound channel of one of the local transmitters became audible and, after a short while, the picture appeared. Dick looked at it carefully. It was rock-steady with not a trace of movement which could conceivably fall into the category of "shuddery". The receiver had a rotary tuning control and Dick adjusted this to pick up, in turn, the other two local channels. On both of these the picture locked in solidly, with no tremors or shakiness whatsoever in either the horizontal or vertical directions. Experimentally, Dick adjusted the control so that the tuning passed slowly through, from either side, the last local channel he had selected.

As soon as the tuning was sufficiently close to the correct setting for video information to

appear the picture snapped firmly into position. Dick tuned the set properly again and gazed at the picture. The receiver was presenting a nature documentary in which one particularly revolting little arthropod was engaged in doing quite unspeakable things to another equally repulsive insect. A commentary droned on in the background.

Dick adjusted the contrast and then the brightness control. All that the contrast control did was to vary the contrast of the picture and all that the brightness control did was to vary the brightness. The only control left on the front panel of the set was for volume. Dick turned this up, and his eyes sharpened as a momentary tiny spasm shook the lower half of the picture. He advanced the control to its full extent, causing the Workshop to be filled with the sound of the commentary.

Whenever the reproduced sound reached a peak there was a definite vertical tremor in the picture. The movement was small but noticeable and would certainly be a source of irritation to any perfectionist viewer. It was, without a doubt, a shuddery picture within the meaning of the Act.

Dick turned down the sound, causing the picture to resume its former steadiness, and

walked over to the filing cabinet. The service manual for the set was in stock and he returned to his bench, studying its circuit diagram. Laying the manual down on the bench, he concentrated on the audio amplifying section. (Fig.1.)

After some moments, he once more turned the receiver volume control to its maximum position, to observe again the return of the picture jitter. There was a grunt of irritation from the other side of the Workshop, where Smithy was deeply engrossed in examining the entrails of a multi-transistor music centre. A sudden inspiration caused Dick to rummage through his spares box, and he produced a 3.5mm. jack plug to which no wires were connected. He inserted the plug into the earphone socket of the receiver, whereupon the circuit to its internal speaker was broken and it became silent.

The picture jitter at once disappeared.

Dick pulled out the jack plug, to cause the return of both the sound and the picture jitter, and then reinserted the plug to remove both.

"For the love of Mike," roared out Smithy from his bench, "Can't you do any servicing without deafening everybody within a mile's radius?"

"I'm trying," said Dick reproachfully, "to find out what's wrong with this TV."

"Do you have to do it with the sound going full blast?"

Dick assumed the tone of one who conveys an elementary fact of life to an idiot.

"The fault," he remarked patronisingly, "only comes on when the sound is turned up high. The picture then trembles up and down."

"Oh."

There was silence for some moments.

"Is it," called out Smithy, "a modern solid-state set?"

"It is," confirmed Dick.

"Oh."

Again there was silence.

"We used to get that sort of trouble," stated Smithy after a pause, "with the old TV sets which used valves. Valves sometimes went microphonic and they used to cause quite weird faults when the sound

from the speaker caused their electrodes to vibrate."

Dick scanned the circuit diagram in the manual.

"There are," he said positively, "no valves in this set."

"Oh."

### ENTER SMITHY

The silence fell again, but was broken this time by the scraping of Smithy's stool on the floor. Resignedly, the Serviceman dropped his test prods on his bench and walked over to his assistant's side.

"I suppose," he sighed, "I'm once more going to get hooked on one of your jobs instead of getting on with my own work, but at least I'd like to see what this fault looks like."

"Okay," said Dick, turning down the volume control on the receiver. "Now, if I take this jack plug out you'll see how the set behaves when the output volume is low."

He removed the plug. Smithy examined the picture closely.

"As you can see," resumed Dick, "everything's just as it should be and the picture is perfectly steady. Now I'll turn the volume up."

Dick adjusted the control to its maximum setting.

"Yes, I can see the trouble," stated Smithy, raising his voice to compete with the sound level from the speaker. "It's vertical frame judder which coincides with high level peaks of sound from the speaker. There's not a great deal of judder, but still enough to spoil the entertainment value of the picture."

"Right," said Dick. "Now, I'll put in this jack plug and silence the speaker."

He proceeded to do so, and Smithy gazed at the now perfectly stable picture on the tube screen.

"Humph," he grunted. "Well, in the old days, the first thing I'd have done would have been to change the oscillator valve or valves in the vertical timebase. A microphonic valve here would be the obvious thing to suspect since it could be affected acoustically by the sound from the speaker. But you say this set is all solid-state, don't you?"

"Here's the circuit," said Dick, pointing to the service manual. "If you look at the a.f. amplifier section you'll see that it's got an earphone socket which mutes the speaker when a jack plug is inserted. That's what gave me the idea of

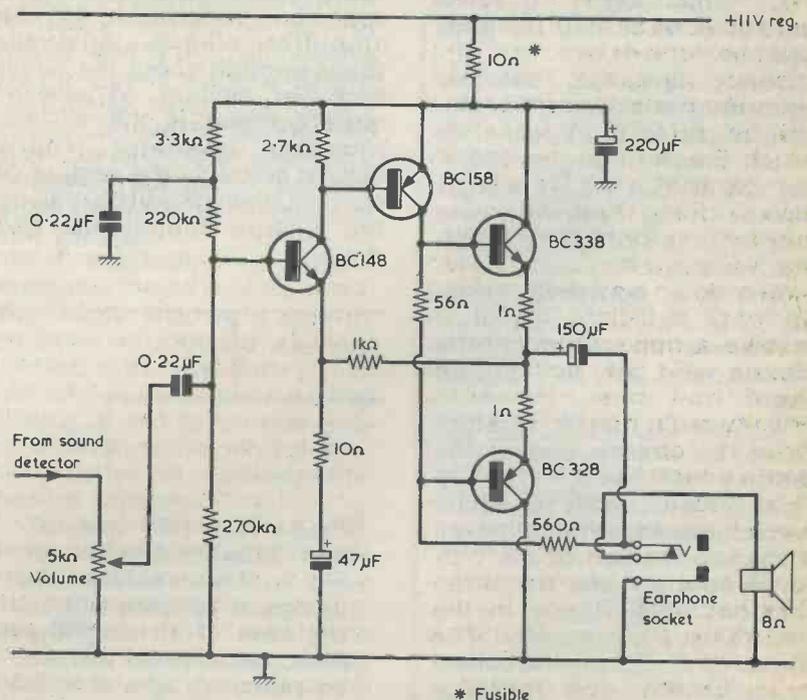


Fig.1. Typical a.f. amplifier section for a television receiver. Inserting a jack plug in the earphone socket mutes the speaker.

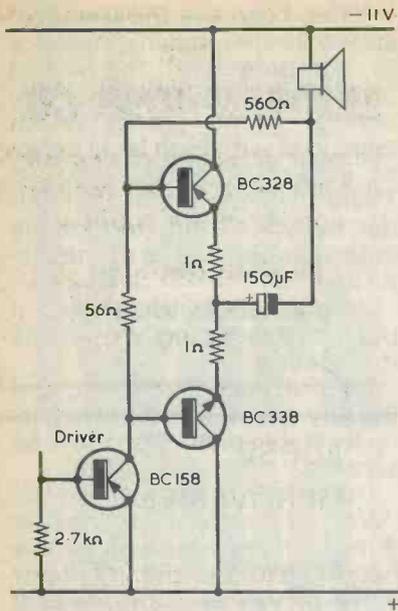


Fig.2. If the driver and output transistor circuitry is redrawn with the negative rail at the top (and the earphone socket omitted for simplicity) the 560Ω resistor is plainly seen to be a bootstrap resistor.

seeing what would happen when there was no sound from the speaker. Incidentally, that a.f. amplifier looks a bit funny to me."

"In what way?" queried Smithy as he turned his gaze towards the circuit.

"Well," said Dick, "the two emitters of the output transistors couple to the speaker in the usual way through a 150μF electrolytic. But there's a 560Ω resistor going back from the speaker to the base of the bottom transistor."

"That's a bootstrap resistor."

"A bootstrap resistor? At the chassis end of the output stage?"

"It doesn't matter whether it's at the chassis end or the positive rail end," replied Smithy. "If you were to redraw the circuit with the negative rail at the top instead of the bottom, you'd see the bootstrap function more clearly in the way it's usually presented. The bootstrap resistor is the collector load of the driver transistor and, since the end of the resistor which couples to the speaker goes negative in sympathy with the voltage at the

output emitters, it ensures that there's always plenty of base current available for the p.n.p. output transistor." (Fig.2.)

"Ah yes," said Dick slowly. "I can see what you mean now. It's the way the circuit is drawn that threw me. There's another thing."

"What's that?"

"There's a 10Ω resistor with an asterisk alongside it." (Fig. 3).

"That's a special fusible resistor," explained Smithy. "It's designed to burn out if a fault condition in the amplifier causes excessive current to be drawn from the regulated 11 volt supply."

"Regulated 11 volt supply, eh? Well, if the 11 volt supply is regulated why do you need that 220μF bypass capacitor after the 10Ω resistor?"

"These TV regulated supplies," said Smithy, "are usually of the discrete transistor type and they aren't always very fast acting. They provide a steady voltage to all the stages they power but the a.f. amplifier section still requires a fat electrolytic like that 220μF capacitor across its supply rails to ensure there's a low supply impedance across it. And, of course, the 220μF capacitor ensures that the 10Ω fusible resistor doesn't provide a common impedance to the amplifier stages. Anyway, that's enough about the audio amplifier section. What's of more interest is the vertical timebase oscillator. That's almost certainly the section of the circuit which will be making the picture judder up and down."

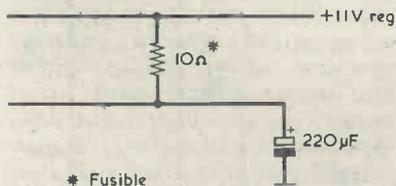


Fig.3. The 10Ω resistor and 220μF capacitor of Fig.1. The resistor is designed to burn out in the case of an amplifier fault, and should always be replaced by a similar component. The 220μF capacitor provides a low supply impedance across the a.f. amplifier.

## VERTICAL OSCILLATOR

Smithy pulled the service manual towards him and pointed his finger at the vertical oscillator section. (Fig.4.)

"Here we are," he announced, "and it's it's just a simple multivibrator."

"It's only got one cross-coupling capacitor between the two multivibrator transistors," objected Dick. "The other cross-coupling component is a 10kΩ resistor."


"Not to worry," said Smithy soothingly. "The arrangement is still a simple one. It's pretty obvious, of course, that the right-hand multivibrator transistor is the one which cuts off during the scan period and which turns on during flyback."

"Hell's teeth," said Dick irritably. "How the heck can you say it's pretty obvious which transistor is cut off during the scan period? Dash it all, you've only just *seen* the flaming circuit!"

"I'll explain in a minute," replied Smithy loftily. "Just take my word for it for the time being. Now, if the right-hand transistor is turned off during the scan period the left-hand transistor is turned on, with current flowing to its base from the positive rail through the 2.2kΩ resistor and that 10kΩ resistor you mentioned just now. The transistor to the left of the multivib is the sync separator, and the waveforms in the manual tell us that this has negative-going sync pulses from the received signal at its collector. Okay?"

"So far," admitted Dick guardedly.

"Good! Negative-going line sync pulses are smoothed out by the 15kΩ resistor and the 2,200pF capacitor which follow the sync separator collector, but when the broad vertical sync pulses arrive they are integrated by the 2,200pF capacitor to produce a large negative pulse which is applied via the first diode in the circuit to the base of the left-hand multivibrator transistor. This pulse cuts off the transistor and current flows from the regulated 11 volt supply through the 680Ω resistor and the 0.33μF cross-coupling capacitor into the base of the right-hand transistor, which

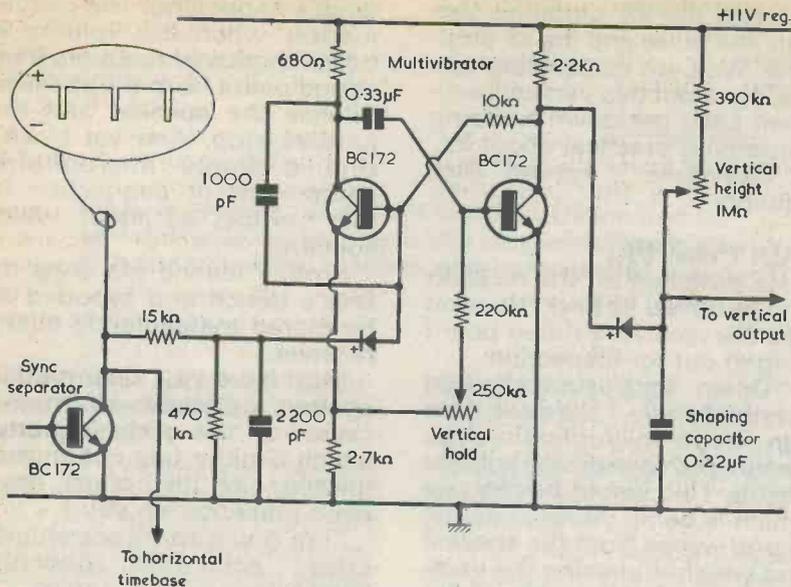

**Fig.4. Vertical timebase oscillator employing a multivibrator to discharge a shaping capacitor during flyback. The slowly increasing voltage across the capacitor is applied to the vertical output stage, which drives the vertical deflection coils. This diagram and Fig.1 are slightly simplified versions of monochrome TV circuits encountered in practice.**

then turns hard on. The 0.33µF capacitor charges rapidly and, at the end of the vertical sync pulse, the base of the left-hand transistor goes sufficiently positive for it to start conducting again. That process will be assisted by the 1,000pF capacitor between its collector and base, as the collector will still be going positive. The reverse multivibrator changeover then takes place, with the left-hand transistor turning on again and the right-hand transistor cutting off. The charged 0.33µF cross-coupling capacitor will hold the right-hand transistor base negative of its emitter, and the capacitor will discharge slowly via the vertical hold pot and the series 220kΩ resistor. We are now in the scan period of the multivibrator cycle, and the capacitor will have just discharged sufficiently for the next vertical sync pulse to trigger the oscillator into flyback again."

"There's a second diode," said Dick pointing at the circuit. "It couples the collector of the right-hand transistor to a 0.22µF capacitor going to

chassis and also to the vertical height control."

"That 0.22µF capacitor is the vertical shaping capacitor," explained Smithy. "It's discharged by the right-hand multivibrator transistor during flyback, and is then allowed to charge slowly via the height control pot and the 390kΩ resistor above it during the scan period. The gradually increasing voltage across the capacitor provides the vertical scan voltage."

"I'm beginning to understand now," said Dick thoughtfully, "why you were able to say so quickly that it was the right-hand multivibrator transistor which turned on during flyback. It had to be that one because it was the only transistor which could discharge the shaping capacitor."

"You've got it," agreed Smithy. "There are other pointers to which transistor does what but that's the most obvious one."

"I see," commented Dick, "that this circuit is powered by the 11 volt regulated supply rail."

"It is," agreed Smithy. "It's the same 11 volt rail which

THE  
**MODERN BOOK CO.**  
Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET  
LONDON W2 1NP  
Tel: 01-402 9176

## MORSE IMPROVEMENT

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. Suitable for R.A.E. preparation. (B) 12-24 w.p.m. computer produced professional level operator material including international symbols.

Price each: complete with instruction and exercise booklets £4.75 including postage. Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £4.75 including postage

Overseas Airmail £1.50 extra.

**MHEL ELECTRONICS (Dept. R)**  
12 Longshore Way, Milton,  
Portsmouth (UK), PO4 8LS

## GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £47.15 inc. VAT. Crystals, if required: £2.60 each. All popular 2m. channels in stock. Marine band version (156 162MHz) £47.15 (xtals £2.90). Mains psu for above £11.95. Pocket VHF Receiver 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz £57.95. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8Ω) input and output for extr. speaker amplification, with circuit £2.75.

Neons min wire end 70p/10: £4.50/100

Slide switches min DPDT 20p ea; 5 plus: 16p

Resistor Kits E12 series, 22Ω to 1MΩ 57 values, 5% carbon film, 1/4W or 1/2W Starter pack, 5 each, value (285) £3.10

Mixed pack, 5 each 1/4W plus 1/4W (570) £5.55

Standard pack, 10 each (570) £5.55

Giant pack, 25 each (1,425) £13.60

BNC Cable mtg socket 50Ω 25p; 5 plus: 20p;

PL259 UHF Plug and Reducer 75p; 5 plus: 67p;

SO239 UHF Socket panel mtd. 60p; 5 plus: 50p;

Nicad rechargeables physically equiv. to zinc-carbon types: AAA (016) £1.80; AA(U7) £1.30;

C(U11) £3.35; PP3 £5.55. Any 5 plus: less 10%. Any 10 plus less 20%.

We stock V.H.F. & U.H.F. mobile aerials s.a.e. details.

Access - Barclaycard

PRICES INCLUDE UK POST, PACKING & VAT

Mail order only

Sole Address

**GAREX ELECTRONICS**  
7 NORVIC ROAD, MARSWORTH,  
TRING, HERTS HP23 4LS  
Cheddington (STD 0296) 668684

## PEATS for PARTS

### ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish  
enthusiasts we supply:

Radio & Electronics  
Constructor Data Books  
Panel Signs Transfers

Also a postal service

# peats

the world of electronics

25 Parnell Street, Dublin 1. Tel 749972

## ELECTRONIC TUTOR KITS


Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

RXG ELECTRONICS LTD.

15 Walnut Tree Crescent,

Sawbridgeworth, Herts, CM21 9EB.

## MORSE MADE EASY

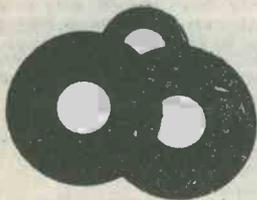

### BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750gms). Details only s.a.e.

### THE G3HSC MORSE CENTRE

S. Bennett, (Box 8), 45 Green Lane,  
Purley, Surrey.

Name .....

Address .....

supplies the a.f. amplifier section, the tuner and the i.f. amplifier. Well, we've done enough talking about this vertical oscillator. Let's get down to doing something practical about it."

"Okeydoke," agreed Dick equably.

### FAULT FINDING

He switched off the receiver and removed its back. He soon had the receiver printed board hinged out for inspection.

"Down to business," said Smithy briskly. "Let's see if we can find a microphonic component in this vertical oscillator circuit. This would be the one which is being vibrated by the sound waves from the speaker and which is causing the vertical picture judder when these waves are at a high level. It won't be microphonic in the same way that those old valves were microphonic but it will probably be a component having an intermittent connection at one of its lead-outs or something of that order. All I've got to do," he concluded confidently, "is gently tap each component in turn until I find the one which causes the judder."

Smithy consulted the service manual and located the vertical oscillator components. Dick switched on the receiver, with its speaker silenced by the jack plug fitted in the earphone socket, and gazed at the picture on the screen as Smithy proceeded to tap the components in turn with an insulated rod he had taken from his pocket.

"Nothing's happening," announced Dick after a while, "nothing's happening at all. That picture's absolutely steady. There's no judder, no shudder, no nothing!"

"That's funny," remarked Smithy, puzzled. "I've tapped every component there is in that oscillator circuit. I'll have another go."

Smithy repeated the process, tapping each of the components in turn. Then he tried again. And again. But there was no component or connection which, when tapped, had the slightest effect on the vertical stability of the picture on the tube.

"This is infuriating," snarled Smithy, as he put down the rod. "Let's just summarise

what's happening. The picture judders when the volume is turned high and there are loud sound peaks from the speaker. Silence the speaker and the judders stop. And yet I can't find a single microphonic component or connection in this vertical oscillator whatsoever!"

Smithy leaned his arms on Dick's bench and brooded as he glared malevolently at the receiver.

(And have you, dear reader, spotted a possible alternative cause of the picture judder which Smithy has completely missed? All the clues have been presented to you.)

"I'm going to try something crazy," said Dick suddenly, "just to see what happens."

"All right," said Smithy disconsolately. "I'll welcome anything which gives us a lead."

Dick turned down the receiver volume control and removed the jack plug. He then busied himself mysteriously as Smithy maintained his scowling gaze at the television set. About ten minutes passed before Dick gave voice again.

"What I've done," he stated, "is wire up an 8Ω speaker to this jack plug by way of a couple of yards of twin flex. I'm going to plug this into the earphone socket and then hold this second speaker right over the printed board. If I move it around above the board, it might show the location of the part which is causing the trouble!" (Fig.5.)

Smithy grunted and made no comment.


Dick placed the speaker on his bench, well away from the receiver, and plugged the jack plug into the earphone socket. He turned the volume control to full and the sound channel of the local transmission, tinny and high-pitched as reproduced by the un baffled 8Ω speaker, filled the air.

And the picture recommenced its judder.

"Hold it," called out Smithy excitedly. "Just hold things there!"

(Have you spotted it now? Hint: it's a single passive component, already mentioned by Smithy, which is the faulty one.)

"Hold it!" repeated Smithy. "Just hold things there!"

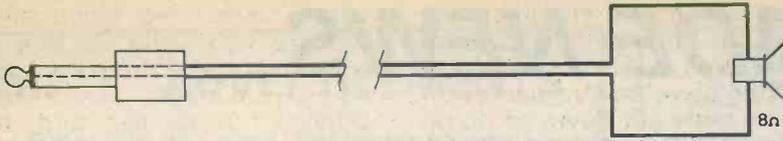

**Fig. 5.** In an attempt at fault location, Dick wired up an external 8Ω speaker to a jack plug which could fit into the television receiver earphone socket.

"Blimey, Smithy," spluttered a startled Dick, "what's eating you?"

"What's eating me," wailed Smithy in an agonised tone, "is that I'm an imbecile! The possible cause of this fault has been staring me in the face all along, and it has nothing to do with microphonic feedback from the speaker at all. Here, see if you can find me a 220μF electrolytic!"

Dick quickly obtained the required component from the spares cupboard and handed it to the Serviceman. Whilst the external speaker still produced its shrill eldritch sound, and whilst the picture still exhibited its vertical judder, Smithy located the 220μF supply bypass capacitor for the audio amplifier section (back to Fig. 1.) and, with trembling fingers, bridged it with the new 220μF capacitor Dick had given him.

The vertical juddering ceased.

### SUCCESS AT LAST

"Ye gods," commented a dazed Dick as he stared bemusedly at the now completely steady picture. "What's happening?"

"The 220μF supply bypass capacitor for the audio amplifier is open-circuit," pronounced Smithy. "The coupling from the audio output stage to the vertical oscillator section wasn't caused by an acoustic microphonic effect at all, it was caused by the heavy current demands of the output stage on sound peaks modulating the common 11 volt supply rail!"

"But there must have been some sort of acoustic coupling," argued Dick. "The vertical judder disappeared when I disconnected the set's speaker."

"What I'd forgotten," moaned Smithy, "is that, without an output load, the audio output stage draws hardly any current from its supply at all. It only draws heavy current

peaks when the speaker is connected to it. That's why the judder returned when you connected the external 8Ω speaker. The speaker was much too far away to give an acoustic coupling to the vertical oscillator components and so there had to be some other form of coupling."

"Blow me," said Dick slowly, as he considered this new state of affairs. "Now I wonder how the changing voltages on the supply rail were affecting the vertical scan."

"They were most likely varying the charging current for the shaping capacitor which follows the vertical multivibrator," said Smithy. He wiped his brow. "Phew, that was a hairy one. I thought I was really stymied for once with this fault."

"My crazy idea of wiring up an external speaker wasn't so crazy after all, then."

"It was," stated Smithy, slapping his assistant on the back, "the idea of a man of genius!"

Which seems to be a fitting moment for us to take our leave of the pair as they happily indulge in mutual congratulations. We are all of us human, with human frailties, and you can hardly blame Smithy for having an occasional off-day. Especially if, hopefully, you were able to decide what the possible fault was before he got round to finding it himself!

### POSTPONED

Due to the recent troubles in the printing industry Part 2 of the "General Purpose 8 watt amplifier" and No. 11 in the "Databuf" series have

both had to be postponed to our next issue.

We much regret the inconvenience caused to readers.

## Constructor's Crossword

Solution to the puzzle on page 611

**Across.** 1, Potentiometer. 8, Iota. 9, New. 10, Serial. 11, Transistor. 13, Iron. 14, Impede. 16, NAND gate. 19, Converge. 22, Insert. 25, Kerr. 26, Address-sees. 27, NOT AND. 28, G.C.A. 29, Eats. 30, Ratio detector.

**Down.** 1, Program. 2, Trainee. 3, Non-linear. 4, I.C.W. 5, Maser. 6, Turning. 7, Read-out. 12, Tin-lead. 15, Pan. 17, Noise gate. 18, Age. 20, One hour. 21, Variant. 23, Suspect. 24, Re-enter. 26, Audio. 28, Gee.

### Notes on the answers

Impedance can consist of resistance or reactance or a combination of the two. Insertion loss is the power loss given when a transducer is inserted in a transmission system. G.C.A. is the abbreviation for Ground Controlled Approach. I.C.W. is short for Interrupted Continuous Wave, and was used in the past by mechanically switching a c.w. transmitter on and off at an audio frequency. Maser is the acronym for Microwave Amplification by Stimulated Emission of Radiation. Working on a similar principle to the laser, the maser is not affected by random electron noise. Radio grade solder is an alloy of 60% tin and 40% lead. A noise gate in a sound studio cuts off any sound signal below a pre-set level.

# TRADE NEWS

## COMPUTER CATALOGUE

Latest catalogue of Electronic Brokers (who refer to themselves as "The Test Equipment People" and "The Mini-Computer People") has now come out. The full address of the company is Electronic Brokers Limited, 49/53 Pancras Road, London, NW1 2QB.

Electronic Brokers state that they are Europe's largest specialist in quality second user test equipment, mini-computers and associated peripherals.

One reason for their success is the company's policy of continually updating the type of equipment sold. Thus, from selling to private users the business has rapidly developed,

and today's customers include leading international companies, research establishments, universities, colleges and government institutions throughout the world.

The Electronic Brokers service laboratory checks each item that arrives at Pancras Road headquarters. Electronic test equipment is then thoroughly cleaned and a schedule prepared for any work which needs to be carried out to meet customers' requirements. Whether new test equipment or used, all items pass through the service laboratory where they are given final tests to ensure that they meet manufacturers'

specifications before delivery to the customer.

The catalogue has 62 large pages, of which 43 are devoted to test equipment of all types including, in particular, high grade laboratory measuring equipment. Very nearly all the remainder of the catalogue lists mini-computers and peripherals. Unless otherwise stated, all test equipment carries a 12 month warranty. There is a 90 days warranty for v.d.u.'s and teletypes, whilst computers are offered with on-site acceptance and diagnostic tests (which may qualify them for independent on-going maintenance).

## HOBBYIST SPRING KIT



The new Instrument Spring Kit for hobbyists, model-makers and do-it-yourself enthusiasts, from Lee Spring Ltd. It contains 16 cadmium-plated music wire springs in 108 different sizes.

For hobbyists, model-makers and do-it-yourself enthusiasts, a new Instrument Spring Kit containing 216 cadmium-plated music wire springs in 108 different sizes, has been introduced by Lee Spring Ltd. Packaged in a compact, pocket-size plastic box the kit comprises compression, extension and torsion springs, compartmentalised separately and instantly identifiable. On the inside lid of the box is a detailed specification-sheet with easy to read and locate data on each of the three types of spring. Springs in this list range from 0.006 to 0.026 inches and come in load-capacities of 0.3 to 6.75 pounds, outside diameters of 0.057 to 0.360 inches and free lengths

of 0.125 to 1.25 inches.

For those who do a lot of work in the home, these kits offer a cross-section of springs for every conceivable purpose with which to save time and avoid inconvenience in hunting high and low for springs that cannot be found when they are needed, or rushing off to the local shops in search of springs which they may or may not stock.

The Instrument Spring Kit from Lee Spring Ltd. costs £25.00.

Further information from Lee Spring Ltd., Cordwallis Estate, Maidenhead, Berkshire.

RADIO AND ELECTRONICS CONSTRUCTOR

## SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge  
£2.00  
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. (Replies to Box Numbers should be addressed to: Box No. —, Radio and Electronics Constructor, 57 Maida Vale, London, W9 1SN.

**BE PROFESSIONAL!** Use our P.C.B. equivalent to old-fashioned 8/way group boards. Incorporates locations for additional components if required. Pack of three in high-quality fibre-glass — includes special services catalogue and price list — only £2.00 post paid (Mail Order only). M. J. Evans, 7 Shap Drive, Warndon Estate, Worcester, WR4 9NY.

**COMPONENTS, Items, Bargains.** Various lists 15p or s.a.e. Sole Electronics (REC), 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

**MODULES:** Mullard LP1164 AM/FM I.F. Unused and guaranteed. £1.50. P.&P. C.W.O. BA screws, hardware, components, manufacturers' clearance. S.A.E. lists. Tennex Ltd., Stock Road, Southend-on-Sea, Essex, SS2 5QF.

**£5 OSCILLOSCOPE.** Standard junk box components plus approx. another £5 (Total components approx £12). This unit plugs into TV aerial socket and converts TV to oscilloscope. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL.

**FREE 1980 AMTRON CATALOGUE** with new range of kits and equipment cabinets. Send s.a.e. Amtron UK Ltd., 7 Hughenden Road, Hastings, Sussex, TN34 3TG. Telephone: Hastings 436004.

**FOR SALE:** "Challenge of the Stars" by Patrick Moore and David A. Hardy £2.00. "Destroyers" by Antony Preston £4.00. Box No. G376.

**ANY REQUESTED SERVICE SHEET £1** (Plus large s.a.e.). Full repair data any named TV £5.50 (with circuits, layouts, £7). Large s.a.e. brings newsletter, bargains, etc. Ausrec, 76 Church Street, Larkhall, Lanarkshire, ML9 1HE.

(Continued on page 629)

## MARCO TRADING

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a part of our range. (Our new list includes Tants, Electrolytics, Disc ceramics, etc.)

### 400m/w ZENOR DIODES

**Low Price**  
3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2,  
6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V,  
13V, 13V5, 15V, 16V, 18V, 20V,  
22V, 24V, 27V, 30V, 33V  
Price: 8p each 100 any mix £6.00

### RESISTORS

1W at 40°C 5% tol., 2.2 Ω  
to 2M2, E12 2p each.  
Resistor Pack — 2.2 Ω -2M2, 10  
each value (730 resistors) £6.00

1 watt

### ZENER DIODES

3V3 to 200V Full range  
Price 15p each 100 any mix £12.50  
8 DIL 10p 22 DIL 23p  
14 DIL 13p 24 DIL 24p  
16 DIL 15p 28 DIL 28p  
18 DIL 18p 40 DIL 40p  
20 DIL 22p

### VEROBOARD (Copper Clad)

Size Inch 0-1" 0.15  
2.5 x 1 20p N/A  
2.5 x 5 55p 56p  
2.5 x 3.75 46p 50p  
Vero Wiring Pen (including spool  
of wire) £2.84

### CONNECTING CABLE

Black. Blue. Green. Grey. Orange.  
Pink. Red. White. Violet. Yellow.  
Brown. Singles 5p per metre  
7/0.2mm 5p per metre  
16/0.2mm 8p per metre

### SPECIAL OFFERS

Power Amplifier Sanyo STK015 Brand New Full Spec, etc. 10 watts into 8 Ω  
Free Spec sheet with every order. Our price: £2.50 each.  
Radio Spares Edge Meter Type MR100 (259-562). All new and boxed. RS price  
over £4.00 each. Our Price: £2.50 each.

Send your orders to:

DEPT DP12, MARCO TRADING, THE OLD SCHOOL,  
EDSTASTON, Nr. WEM, SHROPSHIRE SY4 5RJ  
Tel: Whixall (094872) 464/465

Please add 30p postage and packing to each order and add 15% VAT to your total  
order. Export add NO VAT but add postage. Air/Sea at cost

### TANT. BEAD CAPS

0.1/35v 12p 4.7/35v 12p  
0.22/35v 12p 33/6.3v 25p  
1.0/35v 12p 47/10v 30p

### SUB. MIN. TOGGLE SWITCHES

SPST— 70p  
SPDT— 78p  
DPDT— 82p  
DPDT— 90p  
(C-OFF)



### BRIDGE RECTIFIERS

50V 32p 400V 50p  
400V 43p 6.0 Amp 50V 70p  
800V 58p 200V 78p  
2.0 Amp 50V 35p 400V 85p  
100V 42p

### 0.1W SUB. MINIATURE PRE-SETS

100 Ω to 1 Meg Vertical or Horizontal  
Price: 6p each. 100 any mix £4.50

AC128 20p BC125 10p BC184 9p  
AD149 58p BC147 8p ZN3055 48p  
BC107 10p BC153 10p BY127 12p  
BC108 10p BC172 8p IN4007 8p  
BC109 10p BC183 9p IN4148 2p

Full range of Panel Meters available  
£6.25 each



## Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLDS BEST  
CATALOGUE OF SPEAKERS, DRIVE UNITS KITS,  
CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER ●  
BOWERS &  
WILKINS ● CASTLE ● CELESTION ●  
CHARTWELL ● COLES ● DALESFORD ●  
DECCA ● EAGLE ● ELAC ● EMI ● FANE ●  
GAUSS ● GOODMAN ● HARBETH ●  
ISOPHON ● I.M.F. ●  
JORDAN ● JORDAN WATTS ● KEF ●  
LOWTHER ● MCKENZIE ● MISSION ●  
MONITOR AUDIO ● MOTOROLA ●  
PEERLESS ● RADFORD ● RAM ●  
ROGERS ● RICHARD ALLAN ● SEAS ●  
SHACKMAN ● STAG ● TANNON ●  
VIDEOTONE ● WHARFEDALE ●

**WILMSLOW AUDIO** DEPT REC  
SWAN WORKS, BANK SQUARE, WILMSLOW  
CHESHIRE SK9 1HF

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits,  
etc.,  
Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete  
speakers

# THE MODERN BOOK CO

## UNDERSTANDING MICROPROCESSORS Texas Ins. £4.25

For the newcomer to Microprocessors. An in-depth look at the magic of the solid-state chips that are affecting our lives. Written in everyday language. Ideal for self-paced individualised learning.

**ELECTRONIC FAULT DIAGNOSIS**  
By I. R. Sinclair Price £3.15

**ELECTRONIC PROJECTS IN AUDIO**  
by R. A. Penfold Price £2.50

**OP-AMPS THEIR PRINCIPLES & APPL.**  
by J. B. Dance Price £2.50

**PRINTED CIRCUIT ASSEMBLY**  
by M. J. Hughes Price £2.10

**ELECTRONIC SECURITY DEVICES**  
by R. A. Penfold Price £1.65

**UNDERSTANDING DIGITAL ELECTRONICS**  
by Texas Inst. Price £4.00

**UNDERSTANDING MICRO-PROCESSORS**  
by Motorola Price £4.30

**THE FIRST BK OF MICROCOMPUTERS**  
by R. Moody Price £3.35

**HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE**  
by F. G. Rayer Price £1.70

**THE OSCILLOSCOPE IN USE**  
by I. R. Sinclair Price £2.85

**AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR**  
by I. R. Sinclair £2.55

**REPAIRING POCKET TRANSISTOR RADIOS**  
by I. R. Sinclair Price £2.55

**MAKING & REPAIRING TRANSISTOR RADIOS**  
by W. Oliver Price £2.30

**WORLD RADIO TV HANDBOOK**  
by J. M. Frost Price £9.25

**PROJECTS IN RADIO & ELECTRONICS**  
by I. R. Sinclair Price £2.50

**ELECTRONIC PROJECTS IN THE HOME**  
by O. Bishop Price £2.50

**SIMPLE CIRCUIT BUILDING**  
by P. C. Graham Price £2.20

**110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR**  
by R. M. Marston Price £3.20

**HAM RADIO**  
by K. Ulliyett Price £5.00

**UNDERSTANDING SOLID-STATE ELECTRONICS**  
by Texas Inst. Price £3.95

**A SIMPLE GUIDE TO HOME COMPUTERS**  
by S. Ditlea Price £4.00

**HOW TO BUILD A COMPUTER-CONTROLLED ROBOT**  
by T. Loofbourrow Price £5.30

**THE CATHODE-RAY OSCILLOSCOPE & ITS USE**  
by G. N. Patchett Price £4.00

**HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER**  
by P. J. Guy Price £1.90

**A GUIDE TO AMATEUR RADIO**  
by P. Hawker Price £1.70

**RADIO CONSTRUCTION FOR AMATEURS**  
by R. H. Warring Price £2.80

**MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE**  
by R. H. Warring Price £2.90

We have the Finest Selection of English and American Radio Books in the Country

PRICES INCLUDE POSTAGE

**19-21 PRAED STREET (Dept RC) LONDON W2 1NP**

Telephone: 01-402 9176

## SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the . . . . . issue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 12p equals £1.80

ALL WORDING IN BLOCK LETTERS PLEASE

I enclose remittance . . . . . being payment at 12p a word, MINIMUM £2.00  
Box Number, if required, 30p extra.

NAME . . . . .

ADDRESS . . . . .

Copy to be received four weeks prior to publication.  
Published on the 3rd of every month, forward dated.

## SMALL ADVERTISEMENTS

(Continued from page 627)

**THE RADIO AMATEUR INVALID & BEDFAST CLUB** is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

**COLLECTORS' ITEMS.** Nearly 50 copies of Radio Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

**FREE!** 12" x 6" Veroboard, with first 50 orders for our compilation pack of components. Hundreds of common and exotic use devices plus pcb's thermistors, etc. This is really an offer not to be missed. Send P.O. or cheque for £8.20 immediately to: R.E. Norman, Portbuild Limited, 57 Amberwood Rise, New Malden, Surrey. Or send s.a.e. for list.

**PEN TYPE SIGNAL INJECTOR** available for £2.50 including air freight. Business Promotion Bureau, 376 Lajpat Rai Market, Delhi 110006, India.

**FOR SALE:** Wide angle 9.5mm cine equipment: camera, projector, screen, etc. Also several other 9.5mm cine cameras. S.A.E. for details Box No. G388.

**OSCILLOSCOPE FOR £12.** Easy build converter plugs into TV aerial socket and converts to large screen oscilloscope. Components cost approx £12. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL.

**FOR SALE:** Sinclair MK14 mini-microprocessor with power supply. £45.00 o.n.o. Box G389.

**FOR SALE:** 2000 diodes £2.50. 25 mixed voltage zeners £1.00. LCD 1/100 sec. stopwatch £12.00. LCD watch £7.50. Voice control ladybird toy £15.00. 3 dimensional hologram pendants £12.50. 10" x 8" holograms £30.00. S.A.E. for details. Damaged video tape recorders and CCTV cameras £25.00 to £75.00. Nicad battery chargers £1.50. Light powered calculator, needs no batteries, £20.00. Credit card calculator. C60 tapes 25p, 10 - £2.00, 100 - £15.00. Chess challenger 10 level £150, 7 level £100. Draughts, challenger 4 level £90. 2 level £75. Football table plans £5.50. Pair walkie talkies £15.00 J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

**INGENIOUS GAMES** to distract and tantalise - and to construct. Three original designs by me in kit form, pocket sized with a top quality finish to grace your coffee table and deceive your friends. From £4.25. Send s.a.e. for details of all three to: H. S. Houston, 12 Harlech Avenue, Leeds 11 Yorkshire.

(Continued on page 630)

## RADIO & ELECTRONICS Constructor Projects

We are pleased to announce the introduction of a new service to readers of this magazine.

We are now producing a kit of parts for projects appearing in this magazine. By the time this advert appears in print, we shall have completed a list of projects we are producing in this way.

Please send an S.A.E. for the list, and/or 30p in stamps for our full lists of other components and accessories.

All other services/components previously advertised are still available.

### SPECIAL OFFER

Low cost C60 cassettes — ideal for storing computer programs, or where high quality is not too important. Special price of 45p each.

Mail order only. All prices include VAT. Please add 30p for postage. Same day service on all orders. SAE with enquiries please.

**T & J ELECTRONIC COMPONENTS**  
98 Burrow Road, Chigwell, Essex. IG7 4HB

## A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

### CITY & GUILDS CERTIFICATES

Telecommunications Technicians'  
Radio TV Electronics Technicians'  
Electrical Installations Technicians'  
Electrical Installation Work  
Radio Amateurs'

MPT Radio Communications Cert  
**EXAMINATION STUDENTS —  
GUARANTEED COACHING  
UNTIL SUCCESSFUL**

### TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:  
Electronic Engineering & Maintenance  
Computer Engineering/Programming  
Radio, TV & Audio Engineering  
& Servicing  
Electrical Engineering Installations  
& Contracting

### COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in .....

Name ..... Age .....

Address .....

Occupation .....

**ICS**


Accredited  
by CACC  
Member of  
ABCC

To  
International Correspondence Schools  
Dept V278, Intertext House, LONDON  
SW8 4UJ or phone 01-622 9911 (anytime)

# Self-Binder
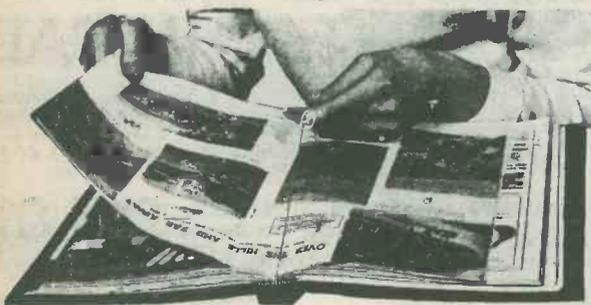
## for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine. Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.



**PRICE £2.25** P. & P. 50p  
including V.A.T.

Available only from:—

**Data Publications Ltd.**  
**57 Maida Vale London W9 1SN**

### SMALL ADVERTISEMENTS

(Continued from page 629)

**INTERESTED IN OSCAR?** Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

**BOOKS TO CLEAR.** "Solid State Design for the Radio Amateur" ARRL. £3.50. "The Radio Amateur's Handbook" by Frederick Collins, £3.00. "Amateur Radio Antennas" by Harry Hooton, £1.00. "Ham Antenna Construction Projects" by J. A. Stanley, 75p. "All about Cubical Quad Antennas" by W6SAI, £1.00. "Guide to Astronomy" by James Muirden, 40p. "Astronomy" by David Evans, £1.25. "Atomic Radiation & Life", Pelican Books, 40p. Box No. G390.

**FOR SALE:** Cassette tapes 6 – £5.00. Classical, rock, disco, country, party time or easy listening. J Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. – both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

**WANTED:** Service Manual circuit of R1155A receiver. To buy or borrow copy. All expenses refunded. Box No. G.391.

**ELECTRONIC COMPONENTS & ACCESSORIES:** We offer you a first class service at the right price, all orders processed the same day. Send now for 1980 catalogue 30p refundable on first order over £1.00 or return catalogue within 10 days for full refund to: Lightning Electronic Components (RE), Free post, Tamworth, Staffs., B77 1BR.

**FOR SALE:** Video Tape recorders, need attention. £25.00-£75.00. Also C.C.T.V. Cameras. Box No. G392.

**INTERESTED IN RTTY?** You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

(Continued on page 631)

## SMALL ADVERTISEMENTS

(Continued from page 630)

**SHACK CLEARANCE.** Large selection of good components. Everything must go so selling cheaply. S.A.E. for details. Box No. G393.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

**BOOKS FOR SALE:** *Master Transistor/I.C. Substitution Handbook*, by Tab Books, £1.75. *The Fabulous Phonograph 1877-1977* by Roland Gelatt, £2. *Linear I.C. Applications Handbook*, by George Clayton, £1. *John Logie Baird & Television*, by Michael Hallett, £2. *110 Semiconductor Projects for the Home Constructor*, by R. M. Marston, £1.20. *The Cat's Whisker - 50 years of Wireless Design*, by Jonothan Hill, £2.00. *Experiments with Operational Amplifiers*, by George B. Clayton, £3.75. *Digital I.C. Equivalents & Pin Connections*, by Adrian Michaels, £1.20. All prices include postage. Box No.G.394.

**WANTED:** FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ

### PERSONAL

**JANE SCOTT FOR GENUINE FRIENDS.** Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

**BROADLANDS RESIDENTIAL CLUB** for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

**SPONSORS** required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

**IF YOU HAVE ENJOYED A HOLIDAY** on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR8 85S.

### BUILD YOUR OWN

**P.A., GROUP & DISCO SPEAKERS** by R. F. C. Stephens  
Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

**THE INFRA-BASS LOUDSPEAKER** by G. Holliman  
(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

**THE DALESFORD SPEAKER BOOK** by R. F. C. Stephens  
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

**VAN KAREN PUBLISHING**  
5 Swan Street, Wilmslow, Cheshire




### Top Priority for every constructor - HOME RADIO CATALOGUE

- Over 2,000 items clearly listed
- Profusely illustrated throughout
- Over 100 A-4 size pages
- Bargain list included free

Send cheque or P.O. for £1.30

HOME RADIO Components LTD  
Dept. RC, P.O. Box 92, 215  
London Road, Mitcham, Surrey.  
01-648 8422

## REVOR OPTICAL & TECHNICAL

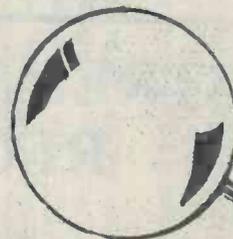

4" dia. lens

FLEXIBLE  
MAGNIFIER

WITH CAST IRON BASE,  
PRECISION GROUND AND  
POLISHED LENS, CHROME PLATED  
FRAME AND FLEXIBLE TUBE.  
IDEAL FOR HOBBIES, AND  
DETAILED WORK WHICH REQUIRES  
BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)


6 SICILIAN AVENUE  
LONDON W.C.1  
Tel. 01-836 4536

£14.91

POST  
FREE

# IN OUR NEXT ISSUE

## CAPACITANCE MEASURING ADAPTOR

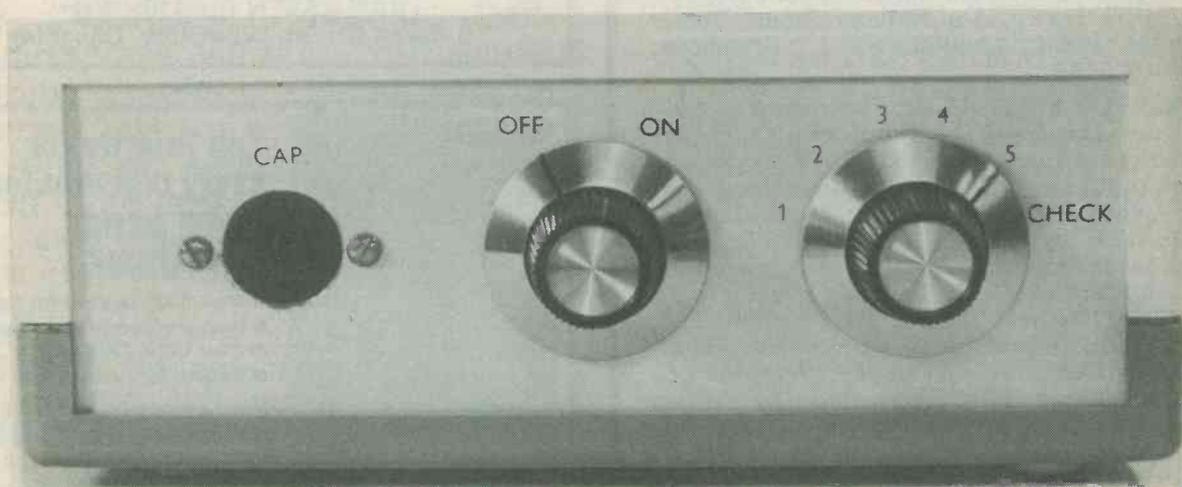

When used in conjunction with an analogue multimeter set to a  $0-50\mu\text{A}$  range, this simple device provides the following five ranges of capacitance measurement:  $0-2,500\text{pF}$ ,  $0-5,000\text{pF}$ ,  $0-0.05\mu\text{F}$ ,  $0-0.5\mu\text{F}$  and  $0-5\mu\text{F}$ . Most multimeters do not have provision for measuring capacitance and their usefulness will be considerably enhanced by the use of this add-on instrument.

## 80 METRE AMATEUR BAND RECEIVER

- Simple homodyne design for the beginner
- Expressly designed for s.s.b. and c.w. amateur signals
- Minimal alignment requirements



# PLUS MANY OTHER ARTICLES


## DIFFERENTIATION AND INTEGRATION

Differentiating and integrating circuits are most commonly encountered in television receivers, in which they appear in the synchronising circuits for the horizontal and vertical timebases respectively.

A differentiating circuit appears in (a), whilst in (b) the upper waveform shows a series of short horizontal sync pulses derived from the received signal by the sync separator. These pulses are applied to the differentiating circuit input and the leading edge of each pulse is passed almost unaltered to the output via the capacitor. The capacitor and resistor values are chosen so that the capacitor discharges into the resistor within the duration of the pulse, whereupon the trailing edge causes a negative excursion of the output. After this the capacitor discharges rapidly into the resistor again. The first positive-going output spikes can be used for synchronising the horizontal timebase.

The integrating circuit of (c) does not respond significantly to the short horizontal sync pulses. The vertical synchronising signal consists of a series of broad pulses, as in (d). The integrating circuit capacitor charges via the resistor for the duration of the first broad pulse, discharges for a brief period until the second broad pulse appears at the input, and so on. The output waveform from the integrating circuit consists of a large slowly rising pulse, and this is used to synchronise the vertical timebase.

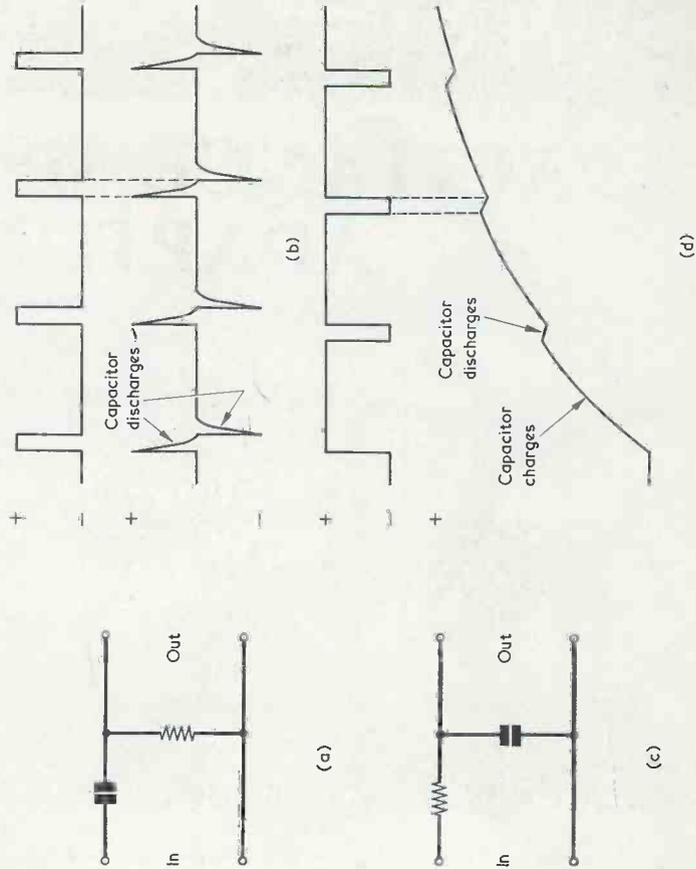The broad vertical sync pulses are at twice the horizontal sync pulse frequency. The differentiating circuit of (a) can still produce positive-going spikes from each leading pulse edge, thereby maintaining the horizontal timebase in synchronism on alternate pulses whilst the vertical sync signal is present.




# STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

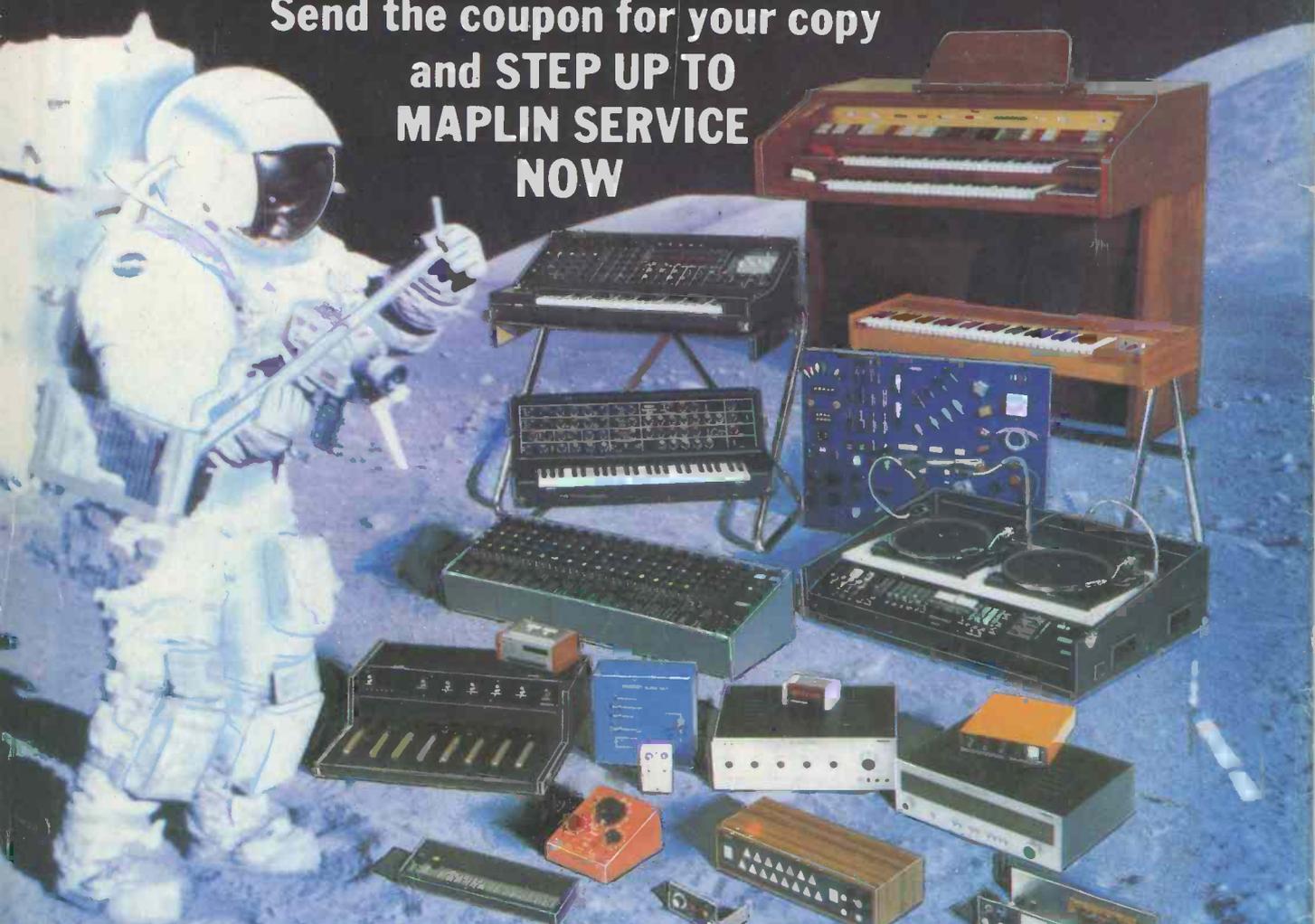Send the coupon for your copy  
and **STEP UP TO  
MAPLIN SERVICE  
NOW**




Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

R.E.C. 680

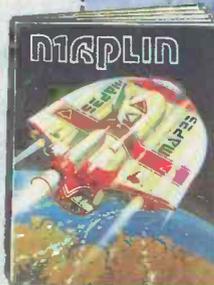

# MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).

Telephone: Southend (0702) 554000.

**Catalogue now available in all branches of WHSMITH  Price £1.00**