

Build Your Own Electronic Calculator

JUNE 1958

Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSTICK, Editor

Watch Your
Audio Levels

Common Servicing
Fallacies
In Color TV

Electronic
Boat Horn

Pocket Police
Transistor Radio


Build This
Electronic
Compass For
Land or Water

(See page 28)

35c
U.S. and Canada



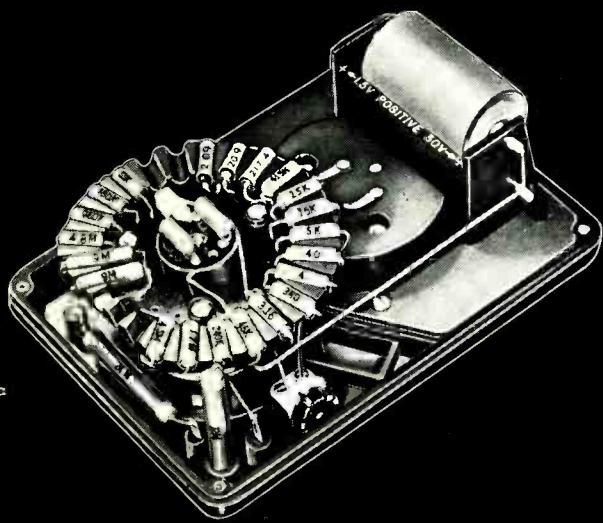CHICAGO 30 ILLINOIS
624C NO TRIPPE AVE
STEVEN WELSH 12-56



NEW TRIPLETT MODEL 630-PL | \$44.50 net


new... most easy to read



- Clear, unbreakable, shadowless front for instant wide vision.
- 5 to 500,000 cps on A.C.
- Continuous resistance reading from 0.1 ohms to 100 megohms.
- Polarity reversing switch.
- *Only one* (king-sized) switch selects both circuit and range—minimizes wrong settings, burnouts.

Only Triplett affords you such a wide choice of VOMs. Whatever your application—broad or limited—there is a Triplett VOM particularly suited for it.

the mighty nine + two


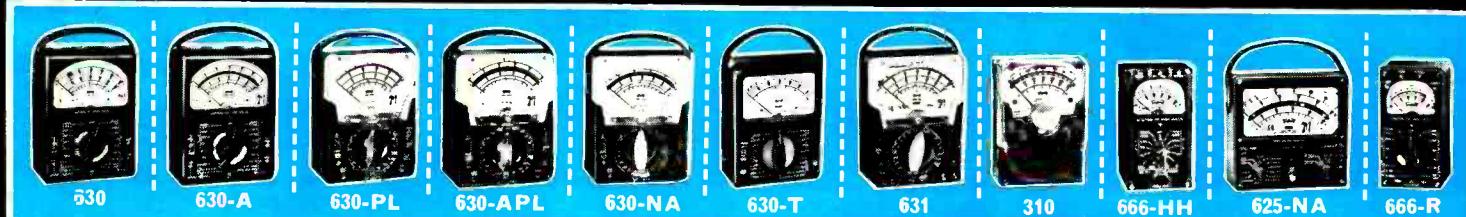


TRIPLETT ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO

Learn Radio-Television

Servicing or Communications by Practicing at Home in Spare Time

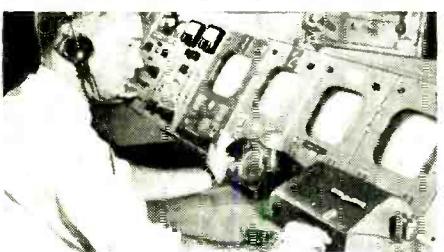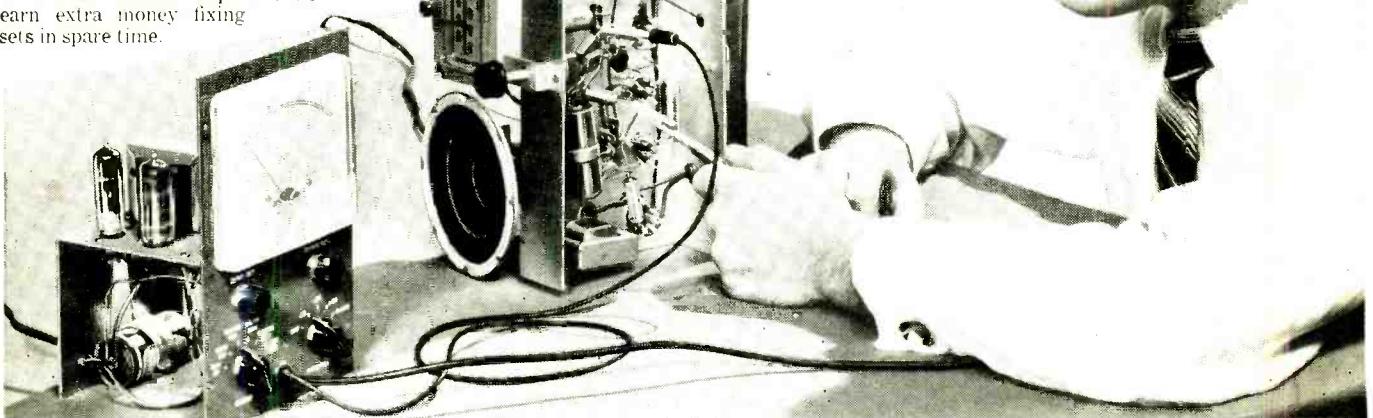N.R.I. SENDS kits with which you practice building circuits common to Radio and TV sets. You LEARN-BY-DOING to locate Radio-TV troubles. As part of N.R.I. Servicing Course, you build Vacuum Tube Voltmeter and AC-DC receiver. Use VTVM to conduct experiments. earn extra money fixing sets in spare time.



RADIO-TV BROADCASTING (see above) offers important positions as Operators and Technicians. RADIO-TV SERVICING Technicians (see below) needed in every community. Their services are respected, their skill appreciated.



N.R.I. TRAINED THESE MEN FOR SUCCESS



"I was repairing Radios by 10th lesson. Now have good TV job." M. R. LINDEMUTH, Fort Wayne, Ind.



"Doing spare time repairs on Radio and TV. Soon servicing full time." CLYDE HIGGINS, Waltham, Mass.



"There are a number of N.R.I. graduates here. I can thank N.R.I. for this job." JACK WAGNER, Lexington, N.C.

"I had a successful Radio repair shop. Now I'm Engineer for WHPE." V.W. WORKMAN, High Point, N.C.

VETERANS Approved Under G.I. Bills

JUNE, 1958



Fast Growing Field Offers You Good Pay, Success, Bright Future



J. E. SMITH
Founder

Bigger than ever and still growing fast. That's why Radio-TV has special appeal to ambitious men not satisfied with their job and earnings. More than 4,000 Radio and TV stations. More than 150 million home and auto Radios, 40 million TV sets. Color TV promises added opportunities. For the trained man, there are good jobs, bright futures in Radio-TV Servicing or Broadcasting.

Training PLUS opportunity is the ideal combination for success. So plan now to get into Radio-TV. The technical man is looked up to. He does important work, gets good pay for it. Radio-Television offers that kind of work. N.R.I. can supply training quickly, without expense of going away to school. Keep your job while training. You learn at home in your spare time. N.R.I. is the OLDEST and LARGEST home study Radio-TV school. Its methods have proved successful for more than 40 years.

Added Income Soon - \$10, \$15 a Week in Spare Time

Soon after enrolling, many N.R.I. students start to earn \$10, \$15 a week in spare time fixing sets. Some pay for their training and enjoy extra luxuries this way. Some make enough to start their own Radio-TV shops. N.R.I. training is practical—gets quick results. Easy to understand, well illustrated lessons teach you basic principles. And you LEARN-BY-DOING by practicing with kits of equipment which "bring to life" things you study.

Find Out What N.R.I. Offers

N.R.I. has trained thousands for successful careers in Radio-TV. Study fast or slow—as you like. Diploma when you graduate. Mail coupon now. Paste it on a postcard or mail in envelope. ACTUAL LESSON FREE. Also 64 page catalog that shows opportunities, shows equipment you get. Cost of N.R.I. courses low. Easy terms. NATIONAL RADIO INSTITUTE, Dept. 8FF, Washington 16, D. C.

SEND FOR BOTH FREE

National Radio Institute

Dept. 8FF, Washington 16, D. C.

Mail me Sample Lesson and 64-Page Catalog FREE. (No salesman will call. Please write plainly.)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

ACREDITED MEMBER, NATIONAL HOME STUDY COUNCIL





JUNE, 1958

Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION

EDITORIAL

- 27 Radio Signals to Venus—Hugo Gernsback

RADIO

- ✓ 28 Electronic Compass to Guide You Home—J. E. Pugh, Jr.
- 31 Communications in a Hurry
- 32 Three-Transistor Pocket Police Receiver—Edwin Bohr
- 34 Radio Runs on Low Voltage—Warren J. Smith
- 35 Identify That Chassis—Jack Darr
- 38 Slug-Tuned VFO Has Stable Output—Jack Gallagher, W5HZB

AUDIO—HIGH FIDELITY

- 39 Know Your Levels—Norman H. Crowhurst
- 43 New Discs and Stereo Tapes—Chester Santon
- 44 Remote Transistor Ear—F. J. Bauer, Jr., W6FPO
- 46 A PA Dummy Load—Richard H. Houston
- 48 Take Your Pick: Changer or Turntable—Herman Burstein

ELECTRONICS

- 50 More Jobs for Semiconductors, Part II—Paul Penfield, Jr.
- ✓ 52 Mr. Math—Forrest H. Frantz, Sr.
- 56 News from the IRE 1958 Meet—Eric Leslie

WHAT'S NEW

- 58 Pictorial Reports of New Developments

TELEVISION

- 59 Transistors in the TV Set, Part II—Louis E. Garner, Jr.
- 84 New Look in Indoor Antennas—Larry Steckler
- ✓ 86 Facts and Fallacies in Color TV Service—Robert G. Middleton
- 88 TV Dx—Robert B. Cooper, Jr.
- 90 TV Service Clinic—Conducted by Robert G. Middleton

TEST INSTRUMENTS

- 92 Square-Wave Generator—T. W. Dresser
- ✓ 96 Spot-O-Matic—I. Queen
- 99 An Inexpensive Scope Calibrator—Joseph Chernof

- | | |
|----------------------------------|-------------------------------|
| 124 Books | 112 Patents |
| 119 Business and People | 113 Radio-Electronic Circuits |
| 121 Corrections | 122 Technical Literature |
| 14 Correspondence | 110 Technicians' News |
| 104 New Devices | 117 Technotes |
| 101 New Tubes and Semiconductors | 115 Try This One |
| 6 News Briefs | 94 50 Years Ago |

RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index* (Formerly *Industrial Arts Index*)

RADIO-ELECTRONICS, June, 1958, Vol. XXIX, No. 6. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class mail privileges authorized at Mt. Morris, Ill. Copyright 1958 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions. **SUBSCRIPTION RATES:** U. S., U. S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$9.00 for three years; single copies 35¢. Pan-American countries \$4.50 for one year; \$8.00 for two years; \$10.50 for three years. All other countries \$5.00 a year; \$9.00 for two years; \$12.00 for three years. **SUBSCRIPTIONS:** Address correspondence to Radio Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 154 West 14th St., New York 11, N. Y. When requesting change of address, please furnish an address label from a recent issue. Allow one month for change of address. **GERNSBACK PUBLICATIONS, INC.** Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N. Y. Telephone Algonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary. **BRANCH ADVERTISING OFFICES and FOREIGN AGENTS** listed on page 125. **POSTMASTER:** If undeliverable, send Form 3579 to: RADIO ELECTRONICS, 154 West 14th St., New York 11, N. Y.

*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS

Average Paid Circulation
Over 195,000

GREATEST
ADVANCE IN
SHOP-METHOD
HOME TRAINING

EARN MORE MONEY...GET INTO TELEVISION ELECTRONICS-RADIO

Learn ALL 8 PHASES in ONE MODERN HOME-STUDY COURSE
At Home - In Spare Time

YOU GET ALL THIS NEWEST PRACTICAL EQUIPMENT

- Parts to build a modern TV set, including all tubes plus a large screen Picture Tube
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave
- Parts to conduct many experiments and build Continuity Checker, RF Oscillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator
- A Valuable Professional Multitester



**19 BIG KITS
YOURS TO KEEP**

YOUR NATIONAL SCHOOLS TELERAMA COURSE COVERS ALL 8 PHASES

- | | |
|------------------------------------|--------------------------------|
| 1. TELEVISION, INCLUDING COLOR TV | 5. PREPARATION FOR FCC LICENSE |
| 2. RADIO, FM AND AM | 6. AUTOMATION |
| 3. INDUSTRIAL ELECTRONICS | 7. RADAR AND MICRO WAVES |
| 4. SOUND RECORDING AND HI FIDELITY | 8. COMMUNICATIONS |

YOU ARE NEEDED IN THE TELEVISION-ELECTRONICS-RADIO INDUSTRY!

You can build a secure future for yourself if you get into Electronics NOW! Today's shortage of trained technicians creates tremendous opportunities. National Schools Shop-Method trained technicians are in constant and growing demand for high-pay jobs in Broadcasting and Communications, Electronic Research, Servicing and Repair, and many other branches.

Let National Schools, a Resident Technical School for over 50 years train you for today's unlimited opportunities in electronics! Our Shop Method trains you to be a MASTER-TECHNICIAN. Completely up to date, developed by experienced instructors and engineers, your Telerama Course will teach you all phases of the industry quickly, clearly and correctly. You can master the most modern projects, such as Color TV, printed circuits — even prepare for FCC License without taking a special

course. You can handle sales, servicing, manufacturing, or make good money in your own business. SEND FOR FACTS TODAY!

EARN AS YOU LEARN. Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning.

YOU GET EVERYTHING YOU NEED — Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects — all the valuable equipment shown above

— many other materials and services — consultation privilege with our qualified staff, and Graduate Employment Service. EVERYTHING YOU NEED for outstanding success in Electronics

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment—professionally installed—finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school—and part time job while you learn. Check box in coupon for full information.



FREE! Fully illustrated "Career" Book in TV-Radio-Electronics. PLUS actual sample lesson—yours at no cost, no obligation. CLIP COUPON NOW . . . MAIL IT TODAY!

APPROVED FOR G.I. TRAINING

NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF.



NATIONAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905
LOS ANGELES 37, CALIFORNIA

GET FAST SERVICE—MAIL NOW TO

NATIONAL SCHOOLS, DEPT. RG-68
4000 S. FIGUEROA ST.
LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Check if interested ONLY in Resident School training at Los Angeles
VETERANS Give date of Discharge _____



**Carefully
Balanced
Packaged Circuit
Inventory
with the**

NEW Centralab.[®]
PCK-40
Kit

With almost eighty million Centralab packaged circuits (identified by PEC*) already incorporated in TV chassis, packaged circuit replacement is getting to be bigger business for you all the time. Make it extra profitable by avoiding special trips and phone calls to your distributor.

The carefully balanced inventory of the new Centralab PCK-40 Kit covers 80% of your PEC* needs. You'll have the circuit you need, on hand, *when you need it*. The Kit contains 40 PEC*, divided among 14 of the most frequently used types, each in its individual rigid plastic package. They are conveniently arranged, for instant identification, in a rugged metal cabinet.

Ask your distributor to show you the new Centralab PCK-40 Kit now, with the FREE cabinet and handy guide. Price \$26.93 dealer net.

Centralab products are listed in PHOTOFACCTS, COUNTERFACTS, and THE RADIO-ELECTRONIC MASTER: PEC* Guide No. 4 available on request from your local distributor or direct from Centralab.

Centralab
*Trademark [®] Y-5832

**SWITCHES • PACKAGED ELECTRONIC CIRCUITS • CERAMIC CAPACITORS
CONTROLS • ENGINEERED CERAMICS • SEMI-CONDUCTOR PRODUCTS**

News Briefs



SEMICONDUCTORS MOVE into the regulation field with the announcement of a field-effect varistor developed by R. M. Warner, Jr., H. A. Stone and E. I. Douchette of Bell Telephone Laboratories. The unit has a constant-current feature which makes it ideal as a current regulator. It can also be used as a current limiter or pulse shaper and its high ac impedance makes it useful as a coupling choke or ac switch.

The device has a single diffused junction (see Fig. 1). Current passes parallel to this junction through a constricted area called the "channel."

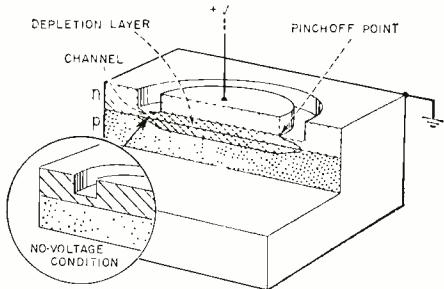


FIG. 1

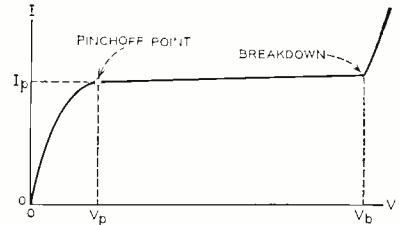


FIG. 2

As the voltage across the device is increased, current increases and a depletion area builds up which eventually reaches through the entire thickness of the channel. At this point, called the "pinchoff" point, a further increase in voltage does not increase current. As voltage is raised still higher, a breakdown point is reached, and current increases again. But between the pinchoff and breakdown points the current is essentially constant and this is the area used (see current curve in Fig. 2).

MASER AMPLIFIER BRINGS VENUS and other astronomical targets 10 times closer than previously possible, when coupled to a radio telescope. Now in use, the unit has been installed as part of the 50-foot radio telescope at the Naval Research Laboratory in Washington. The MASER (Microwave Amplification by Stimulated Emission of Radiation, see RADIO-ELECTRONICS, June, 1955) device operates on a 3-cm wavelength and was developed as a

**LET DEVRY TECH PREPARE YOU IN
SPARE TIME AT HOME AS AN**

ELECTRONICS TECHNICIAN



**NO PREVIOUS TECHNICAL EXPERIENCE
OR ADVANCED EDUCATION NEEDED!**

Laborers and bookkeepers, store clerks, shop men, farmers, salesmen — men of nearly every calling — have taken the DeVry Tech program and today have good jobs or service shops of their own in Electronics. You don't have to quit your present job. If you are 17 to 55, see how you may get yourself ready for a future in the fast-growing Electronics field.

Whether you prepare at home or in our well-equipped Chicago or Toronto Laboratories, you get sound, basic training in both principles and practice. At home, you use educational movies. You build actual circuits and test equipment. You read simple directions, follow clear illustrations. When you finish, you are prepared to step into a good job in an excitingly different field. You may even start a service shop of your own. Mail coupon for free facts today.


Live-Wire Employment Service



Puts you in touch with job opportunities—or helps you toward a better position in the plant where you are now employed.

Draft Age?

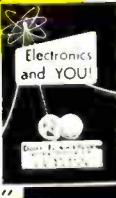We have valuable information for every man of draft age; so if you are subject to military service, be sure to check the coupon.



SAMPLE BOOKLET

We'll give you a free copy of an interesting booklet, "Electronics and YOU." See for yourself how you may take advantage of the opportunities in this fast-growing field.

FREE!

"One of North America's Foremost Electronics Training Centers"



Accredited Member
of National
Home Study Council

DEVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS

FORMERLY

DEFOREST'S TRAINING, INC.



**AN INDEX
to a
BETTER JOB,
A BRIGHTER
FUTURE**

Electronics

Radar

**Guided
Missiles**

Television

Micro-Waves

Communications

Radio

**Industrial
Electronics**

Computers

**Automation
Electronics**

**Remote Control
Systems**

Broadcasting

**Your Own
Service Shop**

MAIL TODAY FOR FREE FACTS

DeVry Technical Institute

4141 Belmont Ave., Chicago 41, Ill., Dept. RE-6-O

Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics as listed above.

NAME _____ AGE _____

STREET _____ Please Print _____ APT. _____

CITY _____ ZONE _____ STATE _____

Check here if subject to military training.

1090 DeVry Tech's Canadian Training Center is located at
626 Roselawn Avenue, Toronto 12, Ontario

NEWS BRIEFS (Continued)

Leading Set Makers
Specify Tung-Sol

High IN PERFORMANCE



Leading Independent
Service Dealers
Choose Tung-Sol

LOW IN CALLBACKS



TUNG-SOL®

Magic Mirror Aluminized

PICTURE TUBES

RECEIVING TUBES

ELECTRON TUBE DIVISION

TUNG-SOL ELECTRIC INC., NEWARK 4, N. J.

joint project of Columbia University and the Naval Research Lab.

It is a solid-state device that uses a synthetic ruby as the Maser amplifier. Freedom from electrical noise inherent in other types of amplifiers enables Maser devices to amplify signals much too weak to be handled by conventional amplifiers.

A similar device is slated for operation with Harvard University's radio telescope. Here, a potassium cobalticyanide crystal will be used with a 21-cm wavelength.

AN ELECTRONIC COMPUTER using punched cards and magnetic tape was used to index the Dead Sea scrolls, ancient Hebrew writings discovered in 1947 in a cave in Jordan, near the west coast of the Dead Sea. This system has saved many hours of tedious labor formerly done by hand. Each word was placed on a punch card. The information cards were then converted to tape by the machine. The 29,250 words took about 2 hours and 2 reels of tape. The final step turned out a printed alphabetical summary list in Hebrew at 150 lines a minute. The computer that did the job is the IBM 705 data-processing machine.

Calendar of Events

Armed Forces Communications and Electronics Association's Show, June 4-6, Sheraton Park Hotel, Washington, D. C.
National Symposium on Production Techniques, June 5-6, Hotel New Yorker, New York, N. Y.
Southwest High Fidelity Show, June 6-8, Shamrock Hilton Hotel, Houston, Tex.
National Convention on Military Electronics, June 16-18, Sheraton Park Hotel, Washington, D. C.
French Electronic Components Show, June 20-26, 23 Rue de Lubeck, Paris.

3,000 MILE RADIO NETWORK, using tropospheric forward scatter propagation (see RADIO-ELECTRONICS, October 1957, page 6; September 1956, page 37 and August 1955, page 39), has gone into operation in Alaska. The network, project White Alice, links the radar warning outposts of the Alaskan Air Command with the Alaskan portion of the DEW (Distant Early Warning) line spread across Alaska and Canada.

The system has been under construction since 1955. It was built by Western Electric and is operated by civilian employees of the Federal Electric Co.

INTEGRATED RADIO SYSTEM for San Francisco police, fire, civil defense and other local agencies brings the city's radio communications up to date. Under the new system, the Police Department will operate on four frequencies in the 40-50-mc band. A fifth frequency, in the 150-mc band, has been set aside for the use of affiliated law enforcement agencies.

Thoroughly covering the city, 17 base stations, including 10 located at police precincts, serve 185 cars and 164 motorcycles equipped with dual-channel

equipment.

The earlier net, which operated on 2466 kc, will be assigned to the telephone company for ship-to-shore use.

CITATION OF RECOGNITION for his contribution to the educational program of the College of Engineering has been awarded Hugo Gernsback by New York University. Among his efforts is Mr. Gernsback's annual award, through NYU's Electrical Engineering Department, of a \$1,000 scholarship to an outstanding student.

NEW YORK UNIVERSITY

COLLEGE OF ENGINEERING

In grateful recognition of his contribution to the educational program of the College of Engineering, particularly the scholarship assistance to students of electronics, the Department of Electrical Engineering proudly presents this

Citation of Recognition

Hugo Gernsback

April 14, 1958

Acting Dean,
Chairman, Department
of Electrical Engineering

HAVE YOU SEEN COLOR TV? RCA estimates that 75% of all Americans haven't. Of those who have color TV receivers, 91% are said to report complete satisfaction. And 80% of owners recommend buying a color receiver to their friends and two out of every three customers say they are buying a color receiver because of their friends' recommendations.

MEDICAL ELECTRONICS CONFERENCE, sponsored by the Council of International Organizations of the Medical Sciences (CIOMS), has been formed with the backing of UNESCO and the World Health Organization. The Medical Electronics Center of the Rockefeller Institute under the direction of Dr. V. K. Zworykin has undertaken the task of organizing the conference on an international scale.

The full-scale conference is tentatively scheduled for the spring of 1959. A preliminary meeting, to appoint the Conference Committee, will be held June 26, 27, 28, 1958, at the Grand Amphithéâtre, Commun de la Nouvelle Faculté de Médecine, Paris, France.

STEREO MUSIC from another station, WNBF in Binghamton, N. Y., is now on the air. The station transmits stereo tapes, using its AM and FM outlets. Listeners obtain the stereo effect by proper placement of their radio receivers. At present a 1-hour program is aired each week.

MAGNETIC FIELDS to keep missiles and spaceships cool when they hit the atmosphere has been proposed by Dr. Joseph L. Neuringer of Republic Aviation. It is a system of magnetohydrodynamic (or hydromagnetic) insulation.

When an object penetrates the earth's atmosphere at 13,000 mph, a shock wave forms ahead of it. Between this wave and the object is a stream of moving air, heated to about 12,000° F.

FREE from HOWARD W. SAMS!...valuable all-steel file cabinets with your purchase of **PHOTOFACt**— the world's finest TV-Radio Service Data

FREE! FOR REGULAR PHOTOFACt SUBSCRIBERS

You get your File Cabinets FREE if you are a regular subscriber to PHOTOFACt Folders and buy all new Sets as issued each month. Your Folders come to you in special envelopes, each including a "Bonus Certificate." Sixty (60) of these entitle you to a single-drawer File Cabinet ABSOLUTELY FREE...



FREE! FOR PHOTOFACt LIBRARY PURCHASERS

Get FREE File Cabinets as you complete your profit-building PHOTOFACt Library... here's how:



FREE!
Single-Drawer File Cabinet with your purchase of 60 Sets of PHOTOFACt Folders. Cabinets Worth \$895



FREE!
Two single-drawer File Cabinets with your purchase of 120 Sets of PHOTOFACt Folders. Cabinets Worth \$1790



FREE!
Three single-drawer File Cabinets with your purchase of 180 Sets of PHOTOFACt Folders. Cabinets Worth \$2685



FREE!
Four single-drawer File Cabinets with your purchase of 240 Sets of PHOTOFACt Folders. Cabinets Worth \$3580

NEW EASY-BUY PLAN

It's easy to complete your present PHOTOFACt Library or start a PHOTOFACt Library. Use the EASY-BUY PURCHASE PLAN:

- NO INTEREST
- NO CARRYING CHARGE
- AS LITTLE AS \$10 DOWN
- UP TO 24 MONTHS TO PAY

Get the world's finest TV-Radio Service Data... get FREE File Cabinets with your PHOTOFACt purchases... take advantage of the Easy-Buy Plan. See your Sams Distributor today, or write to Howard W. Sams for full details.

HOWARD W. SAMS & CO., INC.
2205 E. 46th St., Indianapolis 5, Indiana



Send details on your FREE File Cabinet offer and EASY-BUY Plan.

I'm a Service Technician: full time; part time

My Distributor is: _____

Shop Name: _____

Attn.: _____

Address: _____

City: _____ Zone: _____ State: _____

get the full details of the **HOWARD W. SAMS**
money-saving way to build your complete
profit-making **PHOTOFACt** Library!

NEWS BRIEFS (Continued)

About 2% of the air's atoms are ionized at this temperature. This mixture, called a plasma, is a conductor of electricity.

When an electrical conductor is pushed across a magnetic field, current flows through it and it is slowed down.

The idea behind the new system is to form a strong magnetic field on the front surface of the spaceship or missile. With ionized air flowing across it, the breaking action of the field will cause the air to pile up in a deeper, slower-moving layer and it will not transfer as much heat to the object's surface.

According to Neuringer, a magnetic field of about 3,000 gauss should reduce heat transfer 28%. A further reduction might be obtained by coating the nose of the object with a material that ionizes easily. Its ions mixed with those of the air would make a stronger conducting plasma that would be more effectively slowed by magnetism.

TWO NEW TV STATIONS

started programming since we last reported:

KVIQ, Eureka, Calif. 6
KGHL-TV, Billings, Mont. 8

The following new call letters were chosen:

KMSP, Minneapolis-St. Paul, Minn. 9
(formerly KMGK-TV)
KMOX-TV, St. Louis, Mo. 4
(formerly KWK-TV)
WNTA-TV, Newark, N. J. 13
(formerly WATV)

US operating stations now total 541 (446 vhf and 95 uhf), 31 of which are noncommercial.

Havana, Cuba, has opened its sixth outlet on a 14-hour (6:00 A.M. to 2:00 A.M.) daily all-color schedule from the Havana-Hilton Hotel. Its name is simply Canal 12.

CUTS IN TAXES AND IMPORTS are the aims the Electronics Industries Association (EIA) came up with at their recent Spring Industry Conference. Specific points the EIA wants are: lower excise taxes on radio and TV receivers and phonographs—5% instead of the current 10%; curbs on rising imports of Japanese-made components and radios, and steps toward going into the testing business by taking over the operation of a tube-testing laboratory formerly run by RCA.

A TRANSISTOR BURGLAR ALARM which uses an infra-red beam modulated at 55 cycles as its light source and a synchronous phase-sensitive demodulator pickup is now available. The all-transistor device, developed at Walter Kidde & Co., uses a different frequency than the standard 60-cycle line source to prevent intruders from using another light to keep the alarm from going off. Interruption of the 55-cycle beam or a change in its frequency keys the alarm.

The unit uses a transistor amplifier and oscillator, and a phototransistor to detect the light. A reference signal is compared with the 55-cycle light. Any variation sets off the alarm. END


new profits available in hi-fi servicing and **wal sco** **is Hi-Fi Service Headquarters**

Hi-Fi servicing is a booming new profit source for you, and WALSCO—always your completely dependable supplier for radio-tv service products—is ready with all the things you need to tap this growing field.

MOLDED-ON CABLES AND CONNECTORS



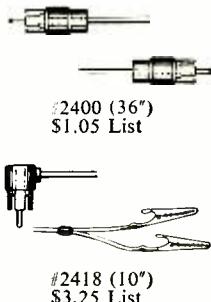Look for this WALSCO display at your distributor. A complete assortment for your every need. Dozens of tenite shielded cables with phono pin plugs, jacks, phone plugs and alligator clips in a wide variety of combinations—in lengths up to 72".



PHONO-RECORDER BELTS AND DRIVES



Webcor Drive Wheel
#1463—\$2.50 List

A complete replacement source for Ampro, Collaro, Crescent, Garrard, Pentron, Revere, RCA, VM, Webcor and every other standard changer and recorder.



RCA Idler Wheel
#1432—\$1.00 List

HI-FI CHEMICALS



"No-Slip" for cords
and pulley belts
#260-01—60c List

A full line of special chemicals for Hi-Fi servicing—to make your job easier and faster.



RH Recording
Head Cleaner
#93-01—95c List

WALSCO ELECTRONICS MFG. CO.

A division of Textron, Inc.

110 west green street
rockford, illinois

free!

The latest
WALSCO cata-
log . . . from
your distribu-
tor, or write for
it today.

HOW TO PASS Your FCC Commercial LICENSE EXAMS*

GET YOUR FCC LICENSE IN A HURRY!

Get your FCC Commercial License —or your money back

See Free Catalog for complete details

Cleveland Institute training results in success
with commercial FCC examinations
... easily . . . and quickly

"Investment in training really pays off"

"Thought you would like to know that in almost two years since I completed your course and obtained my first phone license, my pay has increased \$5 per week every six months. I don't believe any other investment could pay off as well as this one did."

Harold E. Phipps
North Augusta, S. C.

Cleveland Institute training results in job offers like these!

Electronic Technicians
RCA has positions for technicians, field engineers & instructor technicians to install, maintain, and teach military radar, communications, and fire control equipment. Usual locations at military bases throughout U.S., some overseas. Experience on recent military electronic equipment preferred. Company benefits.

Radio Operator
Capital Airlines (Ohio) is looking for a radio operator. A touch typing speed of 40 wpm is necessary. Must have at least a restricted operator's permit, but a radio-telephone 2nd or 1st class license is desirable.

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-18 4900 Euclid Ave. Cleveland 3, Ohio



Accredited by the National Home Study Council

Cleveland Institute of Radio Electronics

Desk RE-18, 4900 Euclid Ave., Cleveland 3, Ohio

We can train you to pass your License Exams if you've had any practical experience—amateur, military, radio servicing, or other. Our proven plan can help put you on the road to success.

• Your FCC ticket will be recognized by employers as proof of your technical ability.

**good training doesn't
cost . . . it pays!**

**Mail Coupon Now
and get both FREE**



Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below.

- Military
- Radio-TV Servicing
- Manufacturing
- Amateur Radio

In what kind of work are you now engaged?

- Broadcasting
- Home Experimenting
- Telephone Company
- Other

In what branch of Electronics are you interested?


Name. _____ Age. _____

Address. _____


City. _____ Zone. _____ State. _____

RE-18

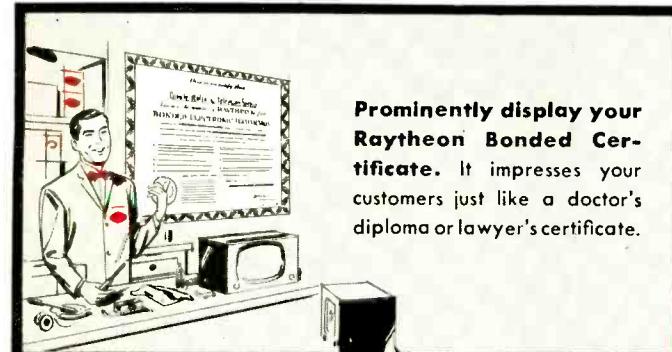
How to make more money as an independent RAYTHEON BONDED ELECTRONIC TECHNICIAN



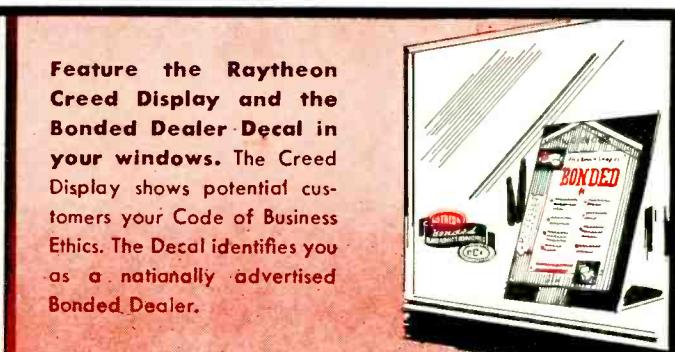Prominently display your Raytheon Bonded Certificate. It impresses your customers just like a doctor's diploma or lawyer's certificate.



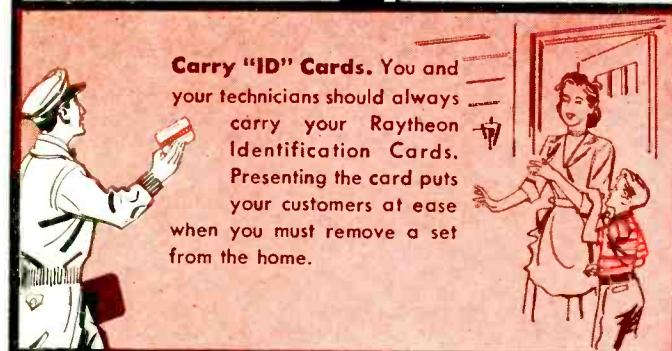Feature the Raytheon Creed Display and the Bonded Dealer Decal in your windows. The Creed Display shows potential customers your Code of Business Ethics. The Decal identifies you as a nationally advertised Bonded Dealer.




Carry "ID" Cards. You and your technicians should always carry your Raytheon Identification Cards. Presenting the card puts your customers at ease when you must remove a set from the home.



Advertise your Bonded Dealer standing. Use the newspaper mats Raytheon makes available to you for local newspaper advertising. Rates are low, results high. Scripts for radio and TV spots are also available to you at no cost.



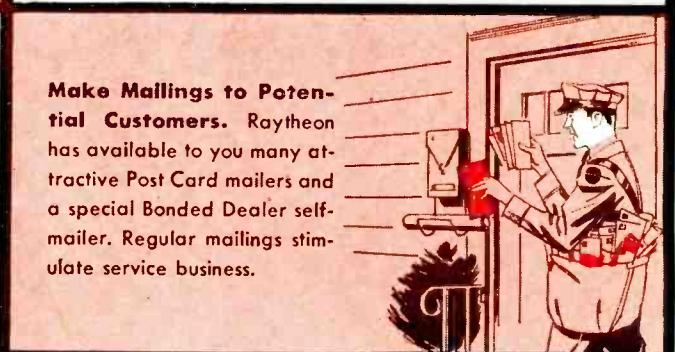
Use the Yellow Pages. List your shop as a Bonded Dealer shop in the Classified Telephone Directory — many customers select service dealers from this source.



Make Mailings to Potential Customers. Raytheon has available to you many attractive Post Card mailers and a special Bonded Dealer self-mailer. Regular mailings stimulate service business.



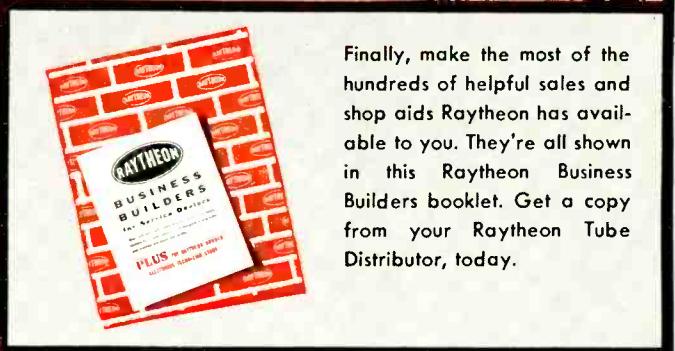Identify your shop. This traffic stopping metal sign will tell all passersby that you are the Bonded Dealer in your community — the Bonded Dealer that Raytheon is presenting to America as the top TV-Radio technician in the country.



Finally, make the most of the hundreds of helpful sales and shop aids Raytheon has available to you. They're all shown in this Raytheon Business Builders booklet. Get a copy from your Raytheon Tube Distributor, today.

P.S.

If you're not a Raytheon Bonded Dealer call the Raytheon Tube Distributor who sponsors the Bonded Program in your neighborhood. He'll tell you if you can qualify.



RAYTHEON MANUFACTURING COMPANY

Receiving Tube and Semiconductor Operations

NEWTON 58, MASS.
55 Chapel Street

CHICAGO 6, ILL.
9501 Grand Ave. (Franklin Park)

ATLANTA 6, GA.
LOS ANGELES 7, CALIF.
1150 Zonolite Rd. N.E.
2419 So. Grand Ave.

Raytheon makes all these

{ Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes,
Semiconductor Diodes and Transistors, Nucleonic Tubes, Microwave Tubes.



Excellence in Electronics

Dreams for some... but not for you when you get advanced CREI training in Electronic Engineering Technology

SERVOMECHANISMS


**GUIDED
MISSILES**

ASTRONAUTICS

COMPUTERS

RADAR

AUTOMATION

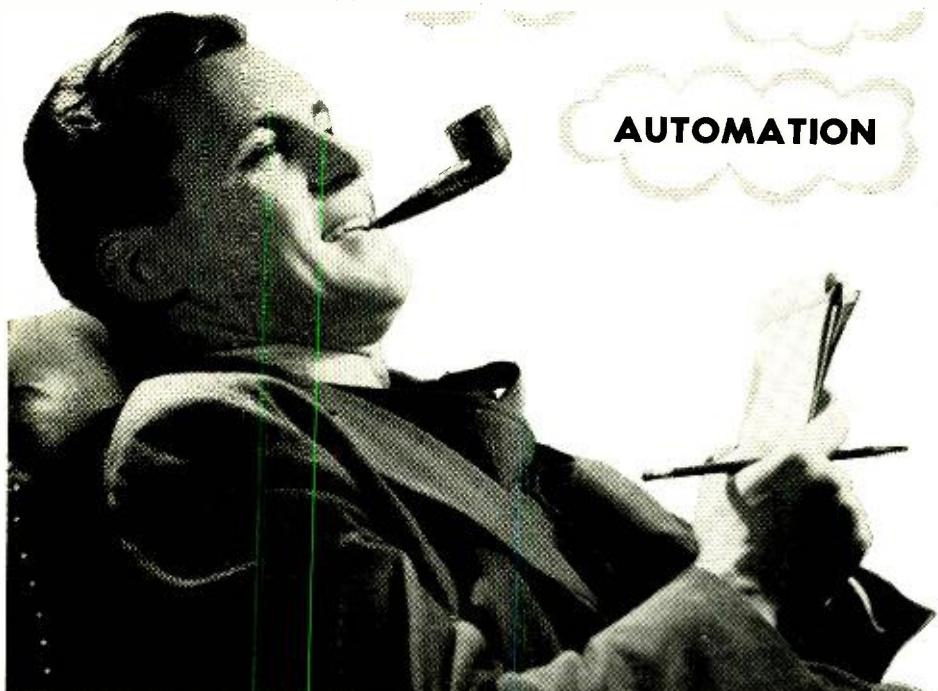

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical
Institute Curricula
Founded 1927
3224 - 16th St., N.W.
Washington 10, D.C.



MAIL THIS COUPON FOR FREE BOOKLET!

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula • Founded 1927

Dept. 146-E 3224 16th St., N.W., Washington 10, D.C.

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Electronics Engineering Technology.

CHECK FIELD OF GREATEST INTEREST

<input type="checkbox"/>	Radar, Servo and Computer Engineering Technology
<input type="checkbox"/>	Electronic Engineering Technology
<input type="checkbox"/>	Broadcast (AM, FM, TV) Engineering Technology
<input type="checkbox"/>	Television Engineering Technology
<input type="checkbox"/>	Aeronautical Electronic Engineering Technology

Name..... Age.....

Street.....

City..... Zone..... State.....

Check: Home Study Residence School Korean Veteran

NOT FOR BEGINNERS. If you have had a high school education, and experience in electronics—and realize the need of a high level technical knowledge to make good in the better electronic jobs—you can qualify for CREI home study training. (Electronics experience is not required for admission to CREI Residence School.) Please fill in the following information:

EMPLOYED BY

TYPE OF PRESENT WORK

EDUCATION: YEARS HIGH SCHOOL.....

YEARS COLLEGE.....

ELECTRONICS EXPERIENCE

The Tube-Tester that's always up-to- date!

- fast...
- fully automatic...
- pays for itself

**RCA WT-110A
Automatic Electron
Tube Tester**

\$199.50* includes 239 punched cards locked in sequence—covers 95% of active TV types...
USER PRICE (Optional) *Prices higher in Hawaii and Alaska

Plus—at no extra cost...

These bonus accessories... 24 additional punched cards, 24 unpunched cards, and sturdy new card punch!

With RCA's exclusive accessory punch and card kit, your WT-110A tester is always up-to-date as fast as new tube type punching information is announced. When you use the RCA WT-110A—the ultra-modern way to test tubes—you gain speed and accuracy for extra service income, and improved efficiency which pays for the tester in a very short time!

Remember, when you choose RCA's WT-110A Automatic Electron-Tube Tester, you also choose a brighter profit picture—now and in the future.

- Fully automatic! Sets up all socket connections and all operating voltages for heater, control grid, plate, screen grid, and bias.
- Checks for shorts and leakage between each element and all others consecutively—plate, screen, control grid, cathode. Multiunit tube sections checked individually.
- Checks amplifier tubes for transconductance—green scale indicates normal range of tube's transconductance.
- File capacity for 700 cards.
- High- and low-sensitivity ranges for gas and leakage tests.
- Automatically selects correct test conditions from 220 different heater voltages (from 0.1 volt to 120 volts) at currents up to 4 amps., 10 bias voltage, and 11 values of cathode resistance.
- Rectifier-type tubes tested for emission under heavy load currents (up to 140 ma per plate).
- 12-volt plate-and-screen supply for testing new auto-radio tubes.

See Your Authorized RCA Test Equipment Distributor!



RADIO CORPORATION OF AMERICA
Electron Tube Division

Harrison, N. J.

Correspondence



STANDS BEHIND THE OTL

Dear Editor:

As a proponent of the OTL (output transformerless) power amplifier I must take exception to some of the statements made by Herbert Ravenswood in his article "Is the Output Transformer Out" which appeared in the January, 1958, issue. It is evident that he is biased (way down to class C) against the OTL amplifier. The single-ended push-pull output stage has made the OTL power amplifier practical. To say that this configuration produces more distortion than the usual form of push-pull stage is not true. Provided the output tubes are matched and driven symmetrically, then they are both equally capable of low-distortion operation. This is so with triodes or pentodes, under class-A, -AB and -B, conditions.

Mr. Ravenswood also states that the single-ended push-pull output stage requires very unequal drive for its operation and this also is not true. As shown in Fig. 1 of the Peterson-Sinclair article, cited by Mr. Ravenswood, a push-pull driver transformer providing equal signal voltages, 180° out of phase, is used to drive each output tube; exactly as in the customary push-pull output stage. However, modern feedback amplifier design cannot tolerate a driver transformer and in the usual push-pull circuit it has been eliminated by various types of phase-inverter and phase-splitter circuits. These are well known in the art.

The single-ended push-pull output stage, however, when used with these circuits does not operate in true push-pull; hence the increased distortion cited by Mr. Ravenswood. Two circuit configurations have been developed that do operate the single-ended push-pull output stage in true push-pull under any and all conditions. These are the Peterson-Sinclair and the Futterman circuits.


Mr. Ravenswood is not impressed with the idea of eliminating the output transformer. Let me list briefly some of the advantages gained:

1. Elimination of notch distortion: This form of distortion shows up as a ragged treble response, usually blamed on the tweeter, and will occur, even with triodes when operated under class-AB or -B conditions.

2. More negative feedback can be used: With 40 db and more of negative feedback, entirely practical with the OTL power amplifier, distortion in the

FREE!

ALLIED'S 1958 CATALOG

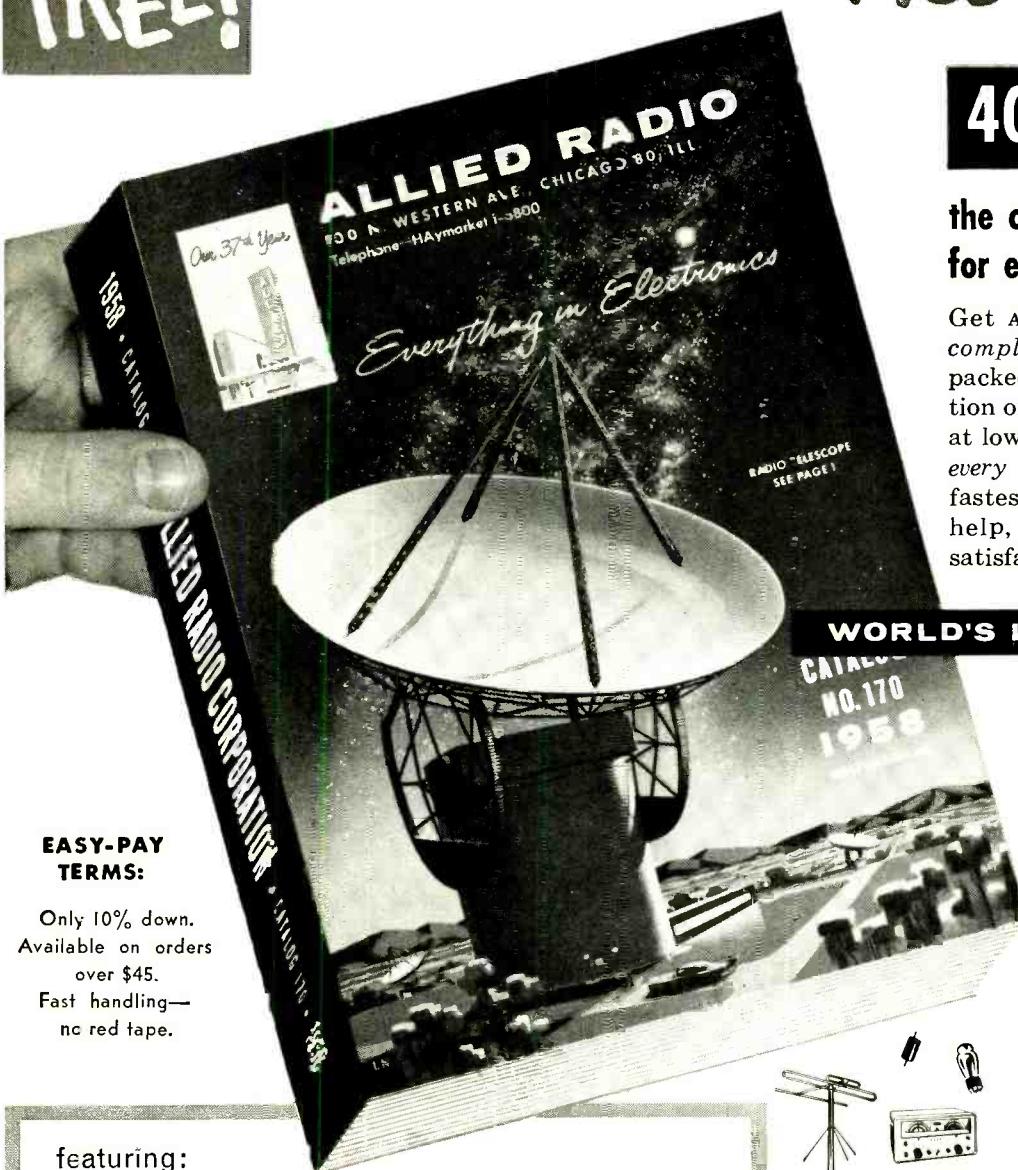

EASY-PAY TERMS:

Only 10% down.
Available on orders
over \$45.
Fast handling—
no red tape.

featuring:

ALLIED'S money-saving knight-kits:

Finest electronic equipment in money-saving kit form. Over 50 quality kits available—Hi-Fi amplifier, tuner and speaker kits, Hobby kits, Test Instruments, and Ham kits. ALLIED KNIGHT-KITS are easiest to build and they **SAVE YOU MORE!**

EVERYTHING IN HI-FI

World's largest selection of quality Hi-Fi components and complete music systems—available for immediate shipment from stock. Save on exclusive ALLIED-Recommended complete systems. Own the best in Hi-Fi for less!



Our 37th Year

ALLIED RADIO

World's Largest Electronic Supply House

404 value-packed
PAGES

the only **COMPLETE** catalog
for everything in electronics

Get ALLIED's 1958 Catalog—it's *complete*, up-to-date—404 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get every buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, guaranteed satisfaction...

WORLD'S LARGEST STOCKS

- Latest Hi-Fi Systems and Components
- Money-Saving, Build-Your-Own KNIGHT-KITS
- Recorders and Supplies
- Public Address Systems and Accessories
- TV Tubes, Antennas and Accessories
- Amateur Receivers, Transmitters, Station Gear
- Test & Lab Instruments
- Specialized Industrial Electronic Equipment
- Huge Listings of Parts, Tubes, Transistors, Tools, Books



send for the leading
electronic supply guide

FREE!

ALLIED RADIO CORP., Dept. 2-F8

100 N. Western Ave., Chicago 80, Ill.

Send FREE 404-Page 1958 ALLIED Catalog

Name _____

Address _____

City _____ Zone _____ State _____

CORRESPONDENCE (Continued)

amplifier does not have to be considered in the reproducing chain.

3. Better transient response: Large amounts of negative feedback, besides reducing all forms of distortion to negligible values, also greatly improves the transient response of the amplifier. This can be heard.

In conclusion I might add that I have designed and constructed OTL power amplifiers and they have been reproduced without difficulty or trouble by scores of amateurs. What is really needed in OTL amplifier design is an output tube made specifically for this. New York, N. Y. JULIUS FUTTERMAN

MR. RAVENSWOOD REPLIES

Dear Editor:

Mr. Futterman's letter, together with two received from different departments of the Philips' organization, reminds me of a reported conversation about the relative qualities of various social groups. Commented one, "There are good and bad among all of them." "He's prejudiced," said another, who was strongly imbued with the supposed superiority of his own group.

That I am not prejudiced against OTL amplifiers on principle, note my comments in the last paragraph of the article ("Is the Output Transformer Out," RADIO-ELECTRONICS, January, 1958): transistors do promise to make the OTL amplifier really practical. Mr. Futterman himself states that an output tube specially designed for it is really needed. So why do we not have such a tube type? Surely because the natural impedance ranges of tubes and dynamic loudspeakers differ so widely as to make it impractical.


The most logical impedance-matching device is the transformer. It does this job with less inherent distortion than a tube, and can be designed to avoid the deficiencies of its early prototypes. The cost aspect is answered by the recent twin-coupled design ("High Fidelity at Low Cost With Twin-Coupled Amplifier," RADIO-ELECTRONICS, November, 1957), to which I called attention in my penultimate paragraph. This design also solves the "impossible" situation relative to including the output transformer in the feedback loop.

To answer Mr. Futterman's points:

1. Notch distortion: (a) I acknowledge that notch distortion can occur with triodes—what I pointed out is that it is less likely; (b) it can also be eliminated using both pentodes and output transformers; vide McIntosh and twin-coupled.

2. Feedback: Mr. Futterman and the Philip's people apparently subscribe to the "more feedback the better" school. Demonstrations have repeatedly shown by subjective listening tests, that well-designed nonfeedback amplifiers, or ones with little feedback, are credited with giving "cleaner" reproduction than types using fabulously large amounts to achieve such wonderful specifications (0.1% or better).

(Continued on Page 20)

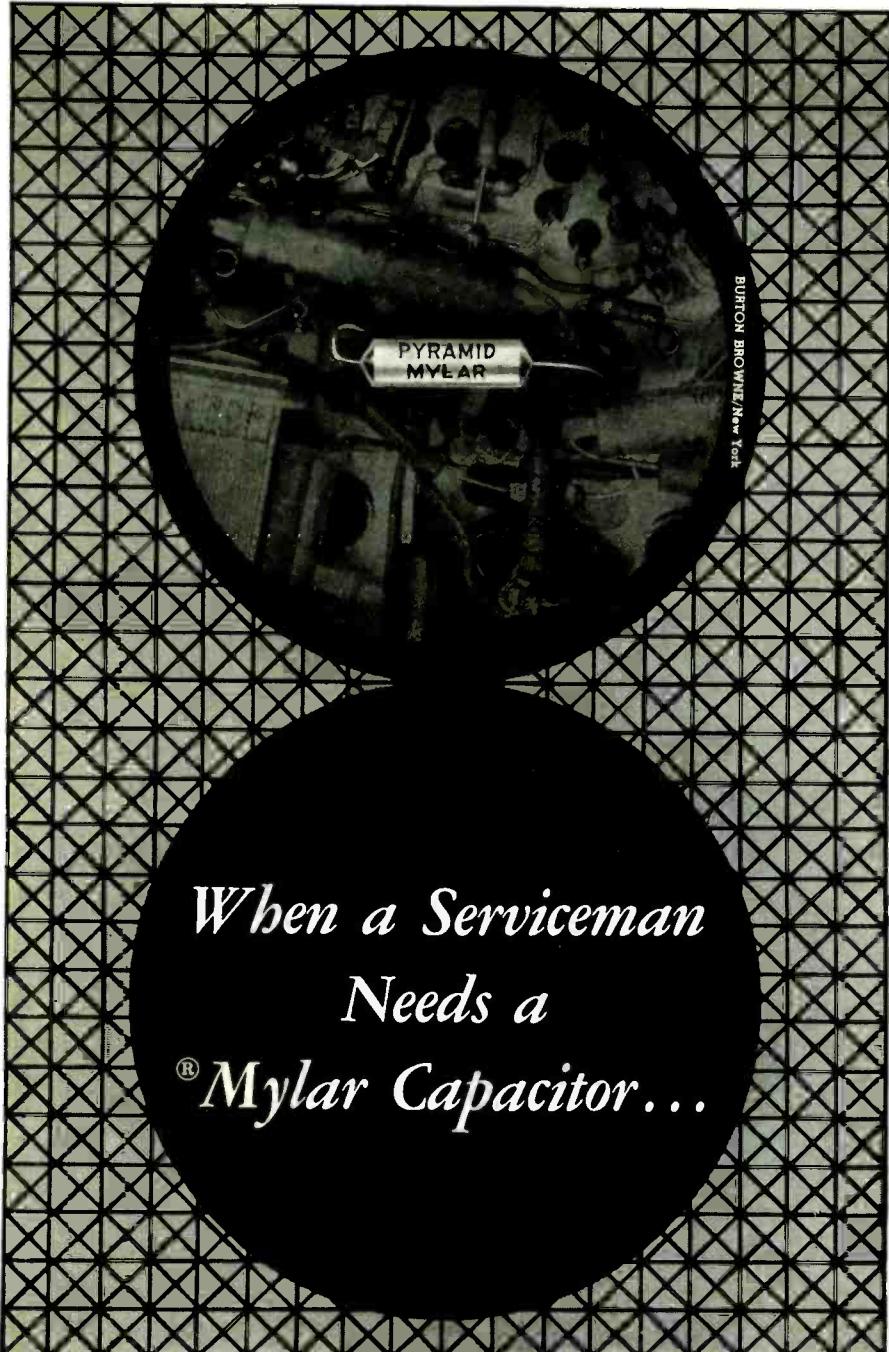

*When a Serviceman
Needs a
®Mylar Capacitor...*

When a serviceman needs a Mylar capacitor, he turns to Pyramid for the capacitor with high reliability, high resistance to moisture penetration and high insulation resistance.

Pyramid's Mylar capacitor guarantees the serviceman a highly dependable capacitor, designed for today's modern circuit requirements, at a price competitive with standard paper capacitors.

Available in standard capacitances and voltage ratings — Pyramid Mylar capacitors are ideal for use as by-pass and coupling capacitors.

Write today for complete information about Mylar capacitors or see your Pyramid distributor. Remember when a serviceman uses Pyramid, he uses the finest and eliminates costly call-backs.

CAPACITORS—RECTIFIERS
FOR ORIGINAL EQUIPMENT
AND REPLACEMENT

*DuPont Reg. trademark



PYRAMID

ELECTRIC COMPANY

North Bergen, New Jersey

Export: 458 Broadway, New York 13

Canada: Wm. Cohen, Ltd., 7000 Park Ave., Montreal

F.C.C. COMMERCIAL OPERATOR L I C E N S E

Training... for Jobs in Electronics

F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The THIRD CLASS radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The SECOND CLASS radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The FIRST CLASS radio telephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a *FIRST CLASS* F.C.C. license, and it does this by TEACHING you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand.

LEARN BY CORRESPONDENCE OR IN RESIDENT CLASSES

Grantham School of Electronics *specializes* in preparing students to pass F. C. C. examinations. Correspondence training is conducted from Washington and Hollywood; resident DAY and EVENING classes are held in both cities. Either way, we train you quickly and well—NO previous training required. A beginner may qualify for his *First Class* commercial F.C.C. license in as little as 12 weeks!

OUR GUARANTEE

If you should fail the F. C. C. exam after finishing our course, we guarantee to give additional training at NO ADDITIONAL COST. Read details in our free booklet.

HERE'S PROOF . . .

that Grantham students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Wks.
Edward Dahl, 7800 Old Chester Rd., Bethesda, Md.	1st	11
Griffin Kane, 3125 Wabash Ave., Los Angeles, Calif.	2nd	9
Beamon Meares, 1536 17th St., NW, Washington, D.C.	1st	11
Larry Pacifico, 65 Main St., Roseto, Pa.	1st	12
Tooru Iwahashi, Honohina, Hakalua, Hawaii	2nd	8
Basil D'Imperio, 2223 H St., NW, Washington, D.C.	1st	12
John Ward, 407 E. Cowden Ave., Midland, Texas	1st	10
Herbert Halbig, 315 Park St., Tupper Lake, N.Y.	1st	11
Vregh Godoshian, 312 E. Wilson St., Pontiac, Mich.	1st	11
Antone Mello, 68 Union St., Nantucket, Mass.	1st	10

Grantham School OF ELECTRONICS

Hollywood
Division

1505 N. Western Ave.
Hollywood 27, Calif.
Phone: HO 2-1411

for FREE Booklet CLIP COUPON and
mail in envelope or paste on postal card.

Washington D.C.
Division

821 - 19th Street, N.W.
Washington 6, D.C.
Phone: ST 3-3614

MAIL COUPON TO SCHOOL NEAREST YOU

Grantham Schools, Desk 84-G

821 - 19th Street N.W. OR 1505 N. Western Ave.
Washington 6, D.C. Hollywood 27, Calif.

Please send me your free booklet telling how I can get
my commercial F.C.C. license quickly. I understand there
is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes

YES! WE HAVE

STILL NO PRINTED CIRCUITRY IN CHASSIS




Even though Dr. Alexander Ellett, head of Zenith's research department, is recognized as the daddy of printed circuitry through his work on radio proximity fuses, still Zenith uses no printed circuitry in its TV chassis because it means more service headaches and often causes service delays.

LESS SERVICE HEADACHES FOR SERVICEMEN

Easier to service...more accessible

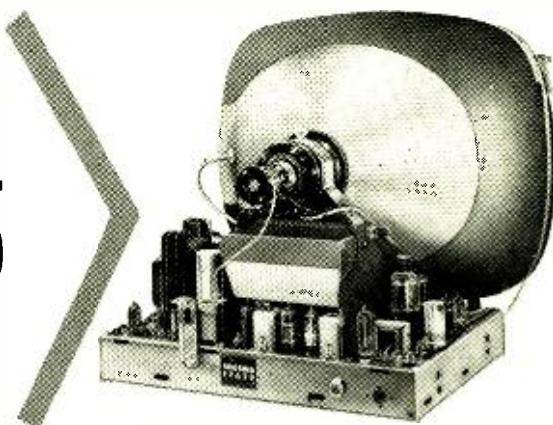**ZENITH'S HANDCRAFTED
SERVICE-SAVER HORIZONTAL
CHASSIS WITH NO PRINTED
CIRCUITS IN THE CHASSIS**



We think it's worth the extra cost of HANDcrafted standard circuitry to get the best performance and fewer service headaches and so do thousands of dealers who would sooner sell customer satisfaction than a price tag.



ZENITH RADIO CORPORATION, Chicago 39, Illinois

The quality goes in before the Zenith name goes on.


Backed by 39 years of leadership in radionics exclusively.

Also makers of Radio, High-Fidelity Instruments and fine Hearing Aids.

NO PRINTED CIRCUITS IN ZENITH TV CHASSIS

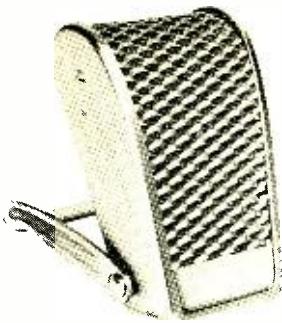**ZENITH HANDCRAFTED
STANDARD CIRCUITRY
COSTS MORE BUT IT MEANS MORE
SATISFIED CUSTOMERS FOR
ZENITH DEALERS AND SERVICEMEN**





NEW SUPER-CARDIOID ...and super value!

Difficult acoustic conditions are child's play for this sensational new super-cardioid microphone. Background noise, undesirable echo, and other unwanted sounds disappear when the ESL-SC403 is used for high fidelity broadcasting or recording of music and speech.

Excellent performance, inconspicuous size, and inexpensive price make this advanced moving coil microphone additionally suitable for lecture halls, churches, and conventions. A high impedance model is designated the ESL-SC403H. Write for details on other new ESL microphones.

ESL-SC403	ESL-SC403H
FREQUENCY RESPONSE: 50 to 12,000 cps ± 3 db	
DIRECTIONAL CHARACTERISTIC:	super cardioid
INTERNAL IMPEDANCE:	200 ohms 45,000 ohms
OUTPUT LEVEL:	-50 db 2.2 mv/ μ bar
REFERENCE LEVEL:	1 mw/10 dynes/cm ²
DIMENSIONS:	2" x 1 1/2" x 3 3/4"
NET PRICE:	\$25.50 \$28




FOR LISTENING AT ITS BEST

Electro-Sonic Laboratories, Inc.

Dept. E • 35-54 Thirty-sixth Street • Long Island City 6, N.Y.

BENCO

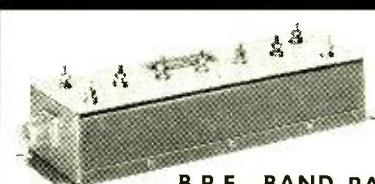UNMISTAKABLY—
THE FINEST NAME
IN COMMUNITY TV




B.P.F.—BAND PASS FILTER

A multi-stage HI-Q filter incorporating two HI-Q bridged T traps. Total attenuation in excess of 80 db on the trap frequencies. Will remove adjacent channel interference where other devices have failed. \$89.50

H. C. A. HIGH OUTPUT SINGLE CHANNEL AMPLIFIER

5 VOLTS R. F.

Maximum output

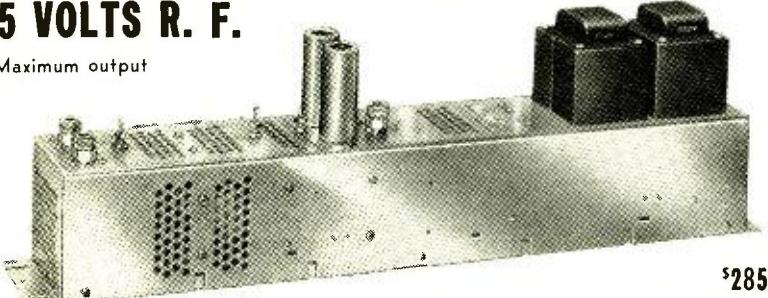

\$285.00

- * 20 db gain minimum
- * 6 mc/s bandwidth
- * Silicon Rectifier
- * Drives a low band signal thru 2 1/2 mi. of K-14 type cable

PRICES ARE SUGGESTED USER NET — SLIGHTLY HIGHER IN SOME U.S. AREAS

BENCO
TELEVISION ASSOCIATES LTD.
27 Taber Rd., Rexdale,
Ontario, Canada

SURE! Please send me full details on the B.P.F. H.C.A.
Name _____
Address _____
City _____ State or Prov. _____

CORRESPONDENCE (Continued)

3. *Transient performance:* Mr. Futterman's statement here requires qualification. Large amounts of feedback do serve to reduce transient distortion, but only one form of it. Often other forms are introduced by it. Although the latter forms may not be shown by standard measurement techniques, they can be very audible.

I would like to pass on a correction to Fig. 5 of my article, as noticed by Philips. The plate-coupling resistor for the ECC83 comes from the screen of the upper UL84, not the B-plus line, as shown. While this arrangement does give theoretical true phase inversion, similar to the Peterson-Sinclair circuit of Fig. 6, my basic point stands:

The audio voltage to ground, which is responsible for any stray electrical coupling that may occur, is still much greater from the plate than the cathode of the ECC83, and the circuit is of quite high impedance to make it susceptible to such transfer. This comes back to Mr. Futterman's point about tubes. Transistors provide us with much lower impedance circuits and make OTL design much more practical.

HERBERT RAVENSWOOD
New York, N. Y.

WHAT'S IT ALL ABOUT?

Dear Editor:

With reference to the discussion on Doppler effects by Messrs. Klipsch, Janszen, et al, it is puzzling to me, having listened with innocent pleasure to reproduced organ music on my Ultra-Linear and other devices for, lo, these many, to learn that the literature rates this effect at the same time as being both imperceptible and intolerable.

With a sincere desire to confuse the issue further, I (no electronics pundit) wonder if anybody has considered the relation between FM effects in reproduced music and possibly similar effects occurring in sound; for example, from an actual organ. In such a case, doesn't the varying velocity of the air in wave movements at, say, 60 cycles, carry with it, as wavelets on a tide, a complex, shifting pattern of frequencies as it strikes the ear? If so, who has complained? And if these FM effects are perceptible, or intolerable, is it not possible to determine the ratio of the effects in the reproduced music to those in the original? Or the ratio between mikeside and the middle of the hall?

How does all the above appear compared to an analysis of the wild and wonderful sound of a pipe organ in a cathedral with uncontrolled acoustics? The instruments of music are allowed to retain their ancient peculiarities; the air will not be denied its eccentricities as a conveyor of sound; the human ear is variable between individuals, times and places. Must the mind, itself fallible in its judgments, now be driven mad by an endless consideration of whether a thing is perceptible or not?

ARTHUR QUALEY
La Puente, Calif.

END

RADIO SIGNALS TO VENUS

... Radio to the Planets Is Now Assured ...

THE idea of bouncing radio signals from heavenly bodies is not new. It originated with the writer in an article entitled "Can We Radio the Planets?" in the February, 1927, issue of *Radio News*. It was then proposed to send a radio signal from the earth to the moon and back via short waves. The calculated elapsed time of the signal transit was 2.5 seconds to cover the two-way distance—twice 238,854 miles, or 477,708 miles, to and from the moon. Nineteen years later, on Jan. 10, 1946, Lt. Col. John H. DeWitt and associated scientists of the US Signal Corps first established actual radio contact with the moon. The elapsed time was 2.4 seconds. Our original predicted time was 2.5 seconds, an error of 0.1 second. In the article mentioned, we also spoke of signaling Mars and Venus, but refrained from giving elapsed signal time, because of the extreme complexity of the problem. In 1927, we had little practical knowledge of the penetration of short waves beyond the earth's atmosphere and into space, as well as eventual reflection of the returning high-frequency waves on the Heaviside layer.

It is gratifying to note that in the fall of 1959 man will at last attempt to signal the planets—Venus and Mars, not as a stunt but for serious astronomic and scientific purposes. British radio astronomers, using the world's largest radio telescope at the Jodrell Bank radio observatory, intend to radio-contact Venus first. The scientists state that they will have a power output 3,000 times greater than the average military or airfield radar installation! Many new and important facts will be learned from such a series of experiments in bouncing signals off Venus. One will be the rotation of Venus on its axis, not known now. Our closest sister planet is constantly shrouded in dense clouds. Hence man has so far not seen the surface of Venus. Its rotation period is thought to be 20 to 30 days—a guess at best. Radio astronomy via reflected signals may give us a clue to Venus' exact time of rotation.

Let us now consider how the scientists will "shoot" Venus at its inferior conjunction in the fall of 1959, when Venus will approach within 30,000,000 miles of the earth. (The closest approach was 26 million miles on Jan. 28, 1958.) At the speed of 186,000 miles a second, the radio signal will take 5.36 minutes to cover the distance out and back between the two planets (2.68 minutes to go to Venus, 2.68 minutes to return).

The inherent difficulty with the present-day state of the art of radio is our inability to concentrate a beam of radio-frequency signals—the diffusion is too great. The same is true of light. With the tremendous distances with which we have to work, the beam spreads. It is as if we aimed a high-pressure stream of water at a distant large football. Most of the water will not hit the object. A large part of it which hits will splash and reflect at different angles and only a comparatively minute amount will come back in the direction of the nozzle.

It is for this reason that the British scientists must use a large power output if they hope to get back an intelligible radio echo signal from Venus.

The Jodrell Observatory radio telescope, the largest known in the world today, has a great advantage in making these experiments. On account of its large size, it can concentrate the transmitter power output into a narrower beam and, again due to its large size, it concentrates the weak echo of the returned signal more effectively.

If in the future it should become possible to concentrate and narrow the radio beam further, much less power would be required to contact the various planets. Obviously, the greater the distance between earth and the outlying planets, the more difficult the problem of bouncing back signals.

It can be seen from the above that as earth and Venus pull apart, the distance between them increases rapidly, until at maximum separation—at superior conjunction—the distance is 161 million miles. Here it would take the round-trip signal 28.8 minutes to bridge the space. But now the sun would become an obstacle, partly blocking the path of the signal.

Would the signal be absorbed by the sun? Yes. Another interesting and perhaps far-reaching test would be the effect of the sun's gravitational attraction on the returning radio echo. This is known as the Einstein shift. If, before or after superior conjunction of Venus, we send a signal to Venus in such a manner that the return signal comes close to the sun, the signal should be bent toward the sun. The Einstein shift has been confirmed with light rays, but not with radio waves up to now. This, however, at the present time can only remain a theoretical consideration. The experiment could not possibly be conducted with present radio frequencies unless we had a radio-astronomical bowl transmitting and receiving antenna *at least 60 miles in diameter!*

In the future when we can produce super high frequencies of the electronoptical variety, which approach the frequency of light, it will be possible to record the Einstein shift electronically.

There will not be very much practical difference when we try to signal Mars, because the distances between our two planets are not too great at nearest approach—about 35 million miles for Mars, 26 million for Venus. We can therefore look forward to an early radio contact with Mars, too.



What about the further outlying planets? Possible, but increasingly difficult the further out we go. To bounce a radio signal off Jupiter will take 1 hour and 10 minutes for the two-way transit; 2 hours, 22 seconds for Saturn; 12 hours, 50 minutes for Pluto! To hit *squarely* such a distant planet, say Neptune, 2,677 million miles away at its closest, is in itself a difficult feat; for the signal to return to earth *without missing it altogether* would be an achievement of a high order—at least at the present state of the art.

—H.G.


Combining a 2-band transistor superhet radio and a marching compass gives you a compact, accurate, portable direction finder

ELECTRONIC COMPASS TO GUIDE YOU HOME

By J. E. PUGH, JR.

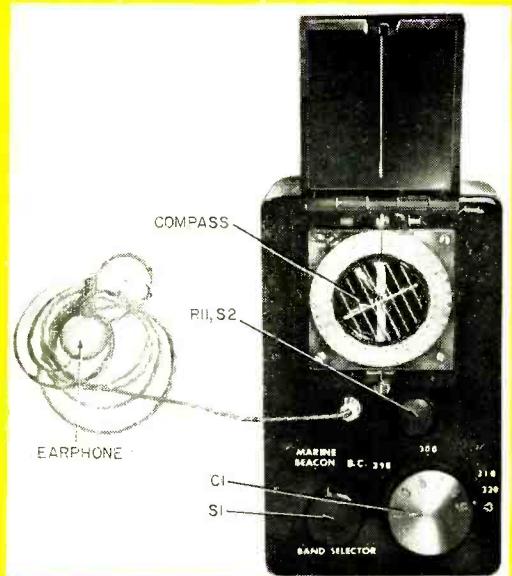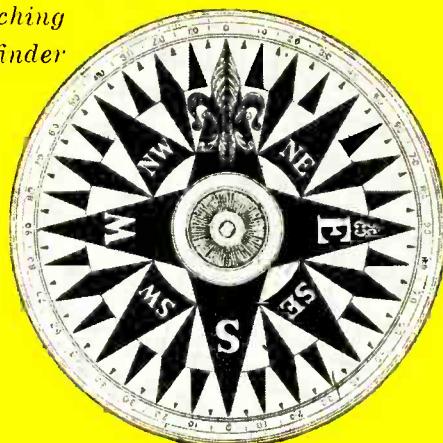

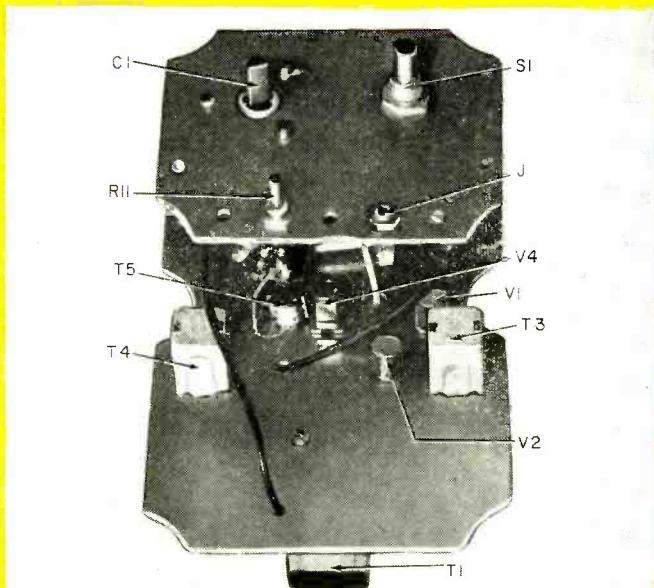Completed unit is small enough to slip into coat pocket.



Top view of the inside chassis assembly.

AN electronic compass is a worthwhile investment for people interested in outdoor activities such as motorboating, sailing, hunting, trapping, berry picking, camping, hiking or other activity where there is a possibility of getting lost.

The instrument described here was designed especially for uses where portability and ruggedness are important. It is housed in a strong Bakelite case that is easily waterproofed. It is small, lightweight, sensitive; has a sharp null point and incorporates a built-in magnetic compass. This combination of directional receiver and built-in compass is a true electronic compass and not just a radio homing device. It makes a rapid and accurate determination of actual position possible.

The superhet receiver

The receiver is a direction-sensitive superheterodyne using a class-B detector and a single audio stage. Two tuning ranges are used: the broadcast band (550 to 1,600 kc) and the marine radio-beacon band (285 to 325 kc). The broadcast band is used so bearings can

be taken from nearly any location and to provide entertainment while outdoors.

The radio-beacon band provides an extra degree of usefulness to boat owners. It is a desirable feature because many rivers, canals and harbors have radio beacons located near their entrances. Broadcast stations ordinarily will not permit such close work since they are seldom found in such a desirable location. If the electronic compass is used only for nonboating activities, the marine radio-beacon band can be eliminated.

A compact, flat ferrite loop antenna provides the directional properties needed for taking bearings on radio stations. It is mounted parallel to the length of the case to obtain the null point when the long axis of the receiver is in line with the station. The antenna has a high Q (about 450 to 790 kc) for maximum selectivity and sensitivity. A matching two-gang tuning capacitor tunes the antenna and local oscillator coil over the band.


The broadcast band is tuned with the BAND SELECTOR (S1) in position BC. When the switch is thrown to MARINE

BEACON, capacitor C4 is shunted across C1-a, C2 and T1 to drop the resonance range of this circuit to the radio-beacon band and at the same time restrict the tuning range so it fits this narrower band. Similarly C6 is shunted across C1-b, C3 and T2. And C5 is switched into the circuit to permit more accurate tracking of the oscillator circuit.

Although its value is not critical, C7 may have to be changed to a slightly different value in some instances. It must be large enough so the local oscillator functions properly at the lowest frequency in the marine band, but at the same time it must not be so large that feedback is excessive at the highest broadcast frequency. Too much feedback causes the oscillator to generate harmonics and reception of signals above the desired range will result.

Agc circuitry

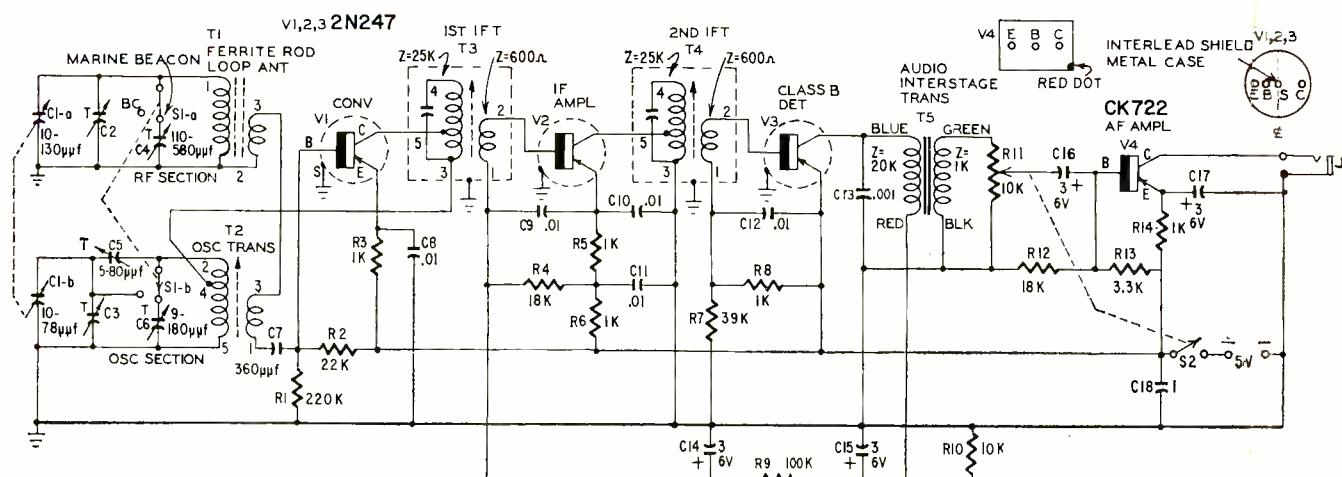The first three stages use 2N247 drift transistors. These transistors have high gain through the highest frequency used and, because of their very low base-to-collector capacitance, do not need neutralization. The converter and if stages are entirely con-



R1—220,000 ohms
 R2—22,000 ohms
 R3, 5, 6, 8, 14—1,000 ohms
 R4, 12—18,000 ohms
 R7—39,000 ohms
 R9—100,000 ohms
 R10—10,000 ohms
 R11—pot, 10,000 ohms, miniature, with spst switch S2 (Lafayette VC-28 or equivalent)
 R13—3,300 ohms
 All resistors $\frac{1}{2}$ -watt 10%
 C1—tuning capacitor; antenna section, 10-130 μf ; oscillator section, 10-78 μf
 Trimmers on C1
 C4—100 μf , trimmer (El Menco 467 or equivalent)
 C5—5-80 μf , trimmer (El Menco 462 or equivalent)

ventional, while the detector is a class-B type instead of the usual diode. This detector provides a worth-while gain and a dc collector voltage that can be used for avc, since its level is determined by the rf signal level.

Resistors R9 and R10 are part of the V2 base-biasing network and R10 is also in V3's collector circuit. The avc voltage developed across R10 is applied to V2's base to regulate its gain with variations in carrier level.

The audio transformer (T5) is a subminiature type well suited for this application. It as well as all other components must contain a minimum of iron to minimize errors in the magnetic compass. A larger transistor audio transformer will not be satisfactory unless it is mounted far from the compass.

The earphone is a high-impedance magnetic type and is satisfactory where the signal level is high and the noise level low. Sometimes, these conditions may be reversed, making a conventional pair of headphones more desirable.

A 5.0-volt mercury battery powers the unit. It has a 1,000-millampere-hour rating and should provide about 500 hours of service since receiver drain is only about 2 ma. When near the compass, this battery has a slightly greater influence on needle deflection than conventional flashlight cells but, when mounted as shown in the photos, its effect is not measurable. The battery is easily replaced when the bottom of the case is removed.

All stages use base-bias stabilization to minimize variations in performance caused by temperature changes since the electronic compass will normally

C6—9-180 μf , trimmer (El Menco 463 or equivalent)
 C7—360 μf , silver mica
 C8, 9, 10, 11, 12—0.01 μf
 C13—0.001 μf , ceramic
 C14, 15, 16, 17—3 μf , 6 volts, miniature electrolytic
 C18—1 μf , paper, miniature
 J—miniature phone jack (LaFayette MS-281 or equivalent and matching plug)
 S1—dpdt rotary (Centralab 1462 or equivalent)
 S2—spst on R11
 T1—ferrite-strip transistor antenna for 130- μf tuning capacitor (Miller 2005 or equivalent)
 T2—transistor oscillator coil for 78-100- μf tuning capacitor (Miller 2022 or equivalent)
 T3, 4—transistor if transformer, 455 kc; primary, 25,000 ohms; secondary, 600 ohms (Miller 2041 or equivalent)

Circuit of the four-transistor unit.

be used outdoors and frequently in the hot sun.

The magnetic compass is a small marching type. It has a rotatable scale for ease and accuracy of bearing determination. A notch and foresight on the compass let you select landmarks (when visible) in line with the desired course.

Let's put it together

All parts of the receiver are mounted on a long flat aluminum lower plate and a short flat aluminum upper plate as in the photos. The unit is fastened into the plastic instrument case with a second hex nut and lockwasher on the threaded switch bushing and with screws that run through the case into two threaded holes along the outer edge of the upper chassis plate.

The compass is mounted near the front end of the case with the needle pivot along the center line of the long dimension. Take your time while aligning the compass to insure the best possible accuracy. The rear mounting screw is a 6-32 flat head in a countersunk hole to permit the compass cover to be closed. The front mounting screw can be a round head but both must be brass with brass nuts. (Try them with a magnet.)

The aluminum chassis plates are shaped to fit the inside of the case with about 1/16-inch clearance on all sides. Make sure of this clearance after bolting to the tuning capacitor and switch but before the complete assembly of small parts is made. Otherwise, when the receiver is fastened in the case, pressure on one of these plates could upset the alignment by twisting the tuning capacitor.

T5—transistor audio interstage transformer; primary 20,000 ohms; secondary, 1,000 ohms (Merit A-2741 or equivalent)

V1, 2, 3—2N247 (RCA)

V4—CK722 (Raytheon)

Battery, 5-volt mercury type (Mallory TR-134R or equivalent)

Battery holder (Acme type 69 or equivalent)

High-impedance magnetic earphone

Tuning dial (Lafayette KN-26 or equivalent)

Knob for $\frac{1}{8}$ -inch shaft

Knob for $\frac{1}{4}$ -inch shaft

Bakelite instrument case, 2 x $3\frac{3}{8}$ x $6\frac{1}{4}$ inches (Lafayette MS-216 with matching cover)

Marching compass (Lafayette F-15 or equivalent)

Transistor sockets, 5-pin (4)

Miscellaneous hardware

One of the easiest ways to register the receiver parts with the case is to drill all necessary holes in the upper chassis plate. Then use this plate as a template for drilling the case from the inside. Be careful while drilling and avoid chipping. This problem can be minimized by backing each hole with a wood block while drilling and by making each hole somewhat undersize and bringing it to size with a tapered reamer.

The tuning capacitor is mounted with its trimmers facing the outer edge of the chassis for easy adjustment. The adjustment screws should be about $\frac{1}{8}$ inch from the outer edge of the chassis to provide adequate spacing between their heads and the plastic case.


One of the mounting holes on the rear of the tuning capacitor matches the corresponding front hole and the top chassis plate can be used as a template to locate this one. The other two must be located by measurement. If the same tuning dial is used as shown, the capacitor shaft will need to be flattened slightly on one side but its length will be satisfactory.

Final assembly


The oscillator coil can be fastened to the bottom chassis plate if desired but a better arrangement of terminals is possible if it is mounted on the top plate. To do this, remove the metal mounting clip and cement a threaded plastic plug in this end. A setscrew in a threaded hole in the top chassis plate is then used to hold the coil. A small hole is drilled in the lower plate directly below the coil for adjustment.

Mount the antenna by first cutting

RADIO

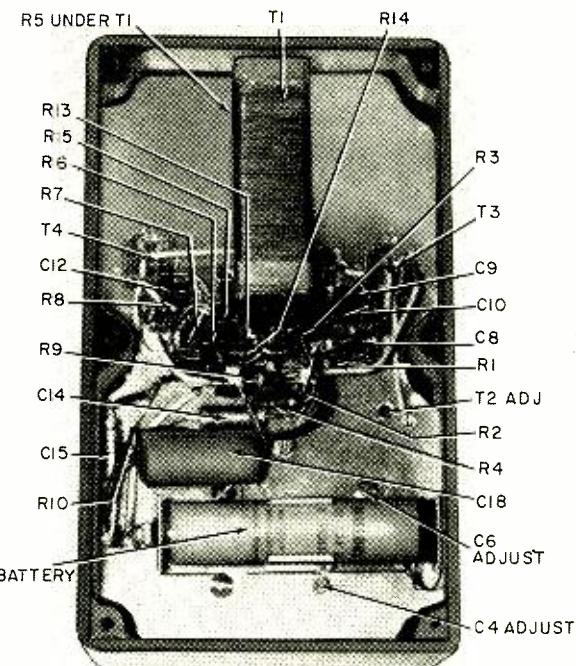

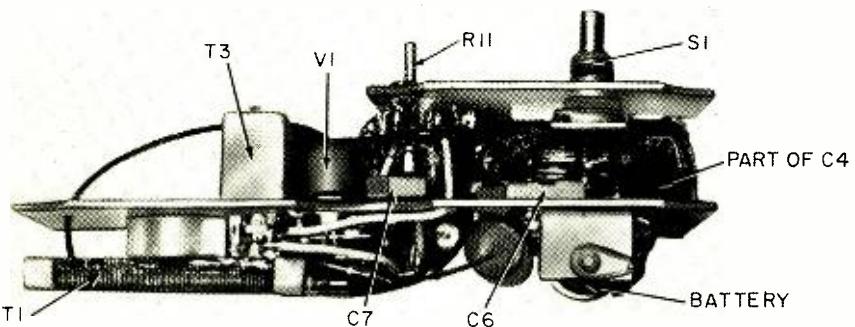Side view shows parts layout between the two chassis plates. In this model a small mica capacitor in parallel with C4 was needed.



its fiber mounting strip about $\frac{3}{8}$ inch shorter than the antenna. Then retape the antenna to this strip with their front ends flush and apply a small amount of coil dope along the joining edges. The undercut end allows room for some parts underneath. A $\frac{3}{8}$ -inch piece of $\frac{3}{8}$ -inch-diameter polystyrene rod is threaded for two $6/32 \times \frac{1}{4}$ -inch screws, and matching holes are drilled in the lower chassis plate. Mount this piece of rod on the plate and fasten the antenna to it with polystyrene coil dope, making sure that the antenna is parallel to the long side of the chassis.

Capacitors C4 and C6 are positioned so that their adjustment screws just clear the battery holder (see photos). These capacitors are mounted directly under the range switch with their outer plates making contact with the chassis. Their end terminals are soldered to the switch and their grounded terminals are bent over and soldered together for rigidity. Examine the ungrounded plates and rivets to be sure the "hot" ones are not grounded.

Both these capacitors should be set to within one-half to one turn from maximum capacitance before soldering. Capacitor C5 is mounted in the same way as C4 and C6, except that it is insulated from the chassis with a small

piece of $1/16$ - or $1/8$ -inch insulation.

The if transformers are mounted along the sides of the chassis to reduce their effect on the magnetic compass, and the audio transformer is mounted directly in front of the volume control with a couple of dabs of cement.

A two-terminal tie point is used for B-plus and for the R9, C14, T3 junction. A ground lug is located under the mounting screw and a No. 20 bare wire connected to it is used as a ground bus. This bus is connected to the shield terminals of the three 2N247's and various small parts are grounded to it along its length. Rubber feet are mounted on each corner of the case to prevent slippage if the weather gets rough.

Steps in weatherproofing

If the electronic compass is to be used in salt-water areas, some weatherproofing will be necessary. Even in fresh-water areas the possibility of wetting by rain, spray and high humidity and falling overboard will make such a step profitable. First obtain some sheet rubber, about $1/32$ inch thick, and cut a gasket about $1/8$ inch wider on all sides than the bottom cover. Now, with a file, trim the base plate to give a clearance of slightly

less than $1/32$ inch between all of its edges and the case, and chamfer its inner edge slightly. Glue the rubber gasket to the inner surface of the base plate and allow it to dry thoroughly.

Gaskets made of the same material can be placed under the compass securing nuts, under the switch shaft nut and under the upper chassis securing screws. The tuning control shaft, the switch shaft, the volume control shaft and the phone jack can be gasketed by splitting soft rubber grommets edge-wise. Use grommets with a $1/2$ -inch outside diameter and $1/4$ -inch hole for the three controls and $3/8$ -inch outside diameter with a $3/16$ -inch hole for the phone jack. In addition, it is advisable to spray the aluminum chassis and if transformer cans with clear plastic to provide an extra degree of protection.

Aligning the receiver

The first step is to align the if transformers for maximum output at 455 kc. An output meter or oscilloscope can be connected across the headphones, or a high-impedance dc voltmeter to V3's collector or the R10, C15, T5-red section for an output indicator.

After the if transformers have been peaked, turn the bandswitch to the broadcast-band position (BC) and adjust T2's core and C3 until the tuning range covers 550-1,600 kc. This is done by alternately adjusting T2's core at 550 kc and C3 at 1,600 kc until both ends of the range fit the dial. Next adjust C2 for maximum output at approximately 600 kc and check for satisfactory tracking at 1,400 kc. If C2 has to be decreased for maximum output at 1,400 kc, bend the slotted plates of C1-a outward and then readjust C2 for maximum output at 1,400 kc. Now adjust for maximum output at approximately 600 kc by simultaneously varying the tuning capacitor in very small steps and adjusting T2's core until the maximum is found. Alternately repeat the C2 adjustment at 1,400 kc and the T2 core adjustment at 600 kc until maximum output is obtained at both points.

The next step is to align the radio-beacon band. Throw switch S1 to RADIO BEACON and alternately adjust C6 at 285 kc and C5 at 325 kc until this range fits the dial. Next, adjust C4 for maximum output at approximately 290 kc and check for satisfactory tracking at 320 kc. When aligning this band, do not touch the core of T2, C2, C3 or the slotted C1-a plates, as these parts are adjusted only for the broadcast band. When alignment is completed, you can calibrate the dial.

How to use it

When the electronic compass is completed, check its accuracy by obtaining the null point on a visible station and at the same time checking to see that the station is directly in line by using the sights on the compass. If possible, check stations at various frequencies

in both bands. These checks should be made some distance from the station antenna and well away from any shore line, electric or telephone lines, metal buildings, or automobiles for maximum accuracy. In addition, hold the compass with the hands away from the antenna end of the case.

The overall accuracy of the electronic compass depends on antenna pattern, compass accuracy, compass alignment with respect to antenna, size and proximity of metal objects, and the nearness of a shore line and the station antenna. The compass error including alignment error should be very small. If any sizable error should be present, it can be compensated for by adding or subtracting a correction factor.

To use the electronic compass with the least amount of error and confusion, obtain a map of the area in which you will be operating. First mark a North-South line through the section of the map to be used and locate all the radio broadcast and beacon stations in your area on the map. Now set the North mark on the compass card under the red hairline, align one edge of the electronic compass case with the North-South line on the map, and rotate the map until the compass card North is aligned with the North end of the needle.

This orients the map so its North is pointed North. Now rotate the electronic compass (but not the map) to obtain a null on a station of known location, place one edge of the electronic compass to intersect with this station as located on the map while maintaining the null and draw a line through the station along the edge of the case. Do the same with a second station. The point where the two lines intersect is *your* location. Now that you know your location, it is a simple matter to get home either by following a plotted course to the desired point or by riding the null straight in if one of the stations is near your destination.

Satisfactory results can be obtained without the map. Simply use the compass to orient yourself with respect to North and then take compass readings on the null points of two stations of known location. The compass card is calibrated in degrees (0 to 360) and also has the usual N, E, S, W markings. Therefore, the readings on the two null points will immediately show you where you are with respect to the two stations. For greatest accuracy, keep your hands away from the antenna end of the case.

After making several trial runs using both methods, you will be able to decide which you prefer—with or without the map. However, try using the electronic compass each time you are engaging in your favorite outdoor activity, even in clear weather, to become completely familiar with it and to gain confidence in its usefulness.

For those who are interested, the US Coast Guard publishes lists of

lights for the US coastal and Great Lakes areas. These light lists include a chart and tables of the various radio beacons including their frequency, identification code and location. Write to the Superintendent of Documents, Washington 25, D. C., for information and prices.

Final notes

Sensitivity, on the broadcast band, will be adequate for nearly any condition, but the radio-beacon range may need a slight boost if there are no nearby stations. In such cases, try a 5- or 7-inch ferrite antenna instead of the 2½-inch one used in this model. This longer antenna will also increase the sharpness of the null point. A second if amplifier can also be added if so desired. This stage is identical with the V2 stage, except that the resistor corresponding to R6 should be about 3,300 ohms.

A speaker can be included by adding a pair of CK722's in a conventional

push-pull class-B output stage after V4. Also a null-indicating meter can be added to V3's collector circuit to obtain a sharper null reading. All of these changes will require a somewhat larger case and will cause a slight loss of portability.

(When adding a speaker or null-indicating meter to the direction finder, be sure to mount them in a place where their magnets will not disturb the magnetic compass. It might be advisable to install the meter and speaker in a separate box connected to the receiver by a cable.—Editor)

For some uses it may be desirable to attach a leather or plastic shoulder strap to two brass screws mounted on the sides of the case, below the compass but above the receiver chassis.

Where you want to eliminate the radio-beacon band, delete S1, C4, C5 and C6. The tuning capacitor shaft can now be aligned with the center of the chassis, or the extra space can be used for a speaker.

END

Communications In a Hurry

TENNESSEE stands ready to meet any emergency—flood, tornado, forest fire or explosion—with its unique mobile disaster communications bus.

Moments after arriving on the scene, the bus offers six radio sending and receiving sets which can operate simultaneously, first-aid equipment, a generator which can supply outside power and an emergency field kitchen.

The unit, operated by the Tennessee Highway Patrol and Civil Defense Organization, is available for use anywhere in the state and surrounding states.


The planning of Capt. P. E. Griffith, of Nashville, Tenn., made it possible to jam so many features into so little space. Captain Griffith heads the communications division of the Tennessee Highway Patrol which also handles communications for the State Highway Department and Civil Defense.

The bus is divided into three compartments, all in radio contact with each other. The front section houses the driver and six radio booths. From here, six radiomen can simultaneously direct operations of six service units.

The center compartment houses 10 transmitters which enable the center to use 40 frequencies, including those of public-service groups both in Tennessee and surrounding states. This section also contains the kitchen unit. Room was made for the field kitchen, Griffith noted, because frequently rescue workers at tornadoes and similar emergencies had gone 15 hours without food.

The rear portion holds first-aid equipment, including a respirator and generator. The generator can be rigged to supply power outside—to a hospital, for example.

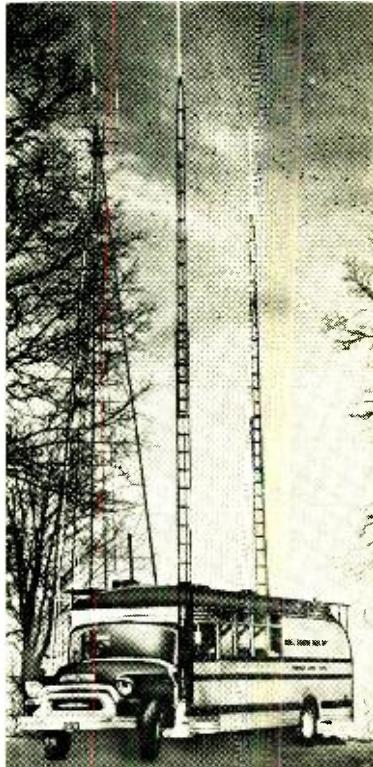The bus has two complete public-address systems and outside plugs to supply power to other electrical units.




Tele-Vue Towers, St. Petersburg, Fla.
This Tennessee Highway Patrol and Civil Defense mobile communications unit is equipped to handle any emergency.

Everything is geared to place units in operation almost instantaneously on arrival at the disaster scene. For example, the Tele-Vue aerial towers lie flat along the top of the bus while it is in motion. But as fast as cranks can be turned, they are hoisted to vertical positions and a second set of cranks swiftly telescopes them up to 45 feet in height. The bus cost \$14,442.

3-TRANSISTOR

Pocket Police Receiver

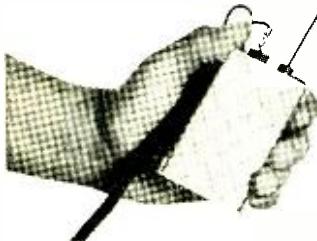

By EDWIN BOHR

THE idea of owning a police receiver is always intriguing. Interest spans all age groups from children to grandparents. There is a thrilling vicarious experience; listening to emergency broadcasts is exciting to all but the most blasé.

Added to this, we have an extra-special police receiver. It is hand- or pocket-size and completely transistorized. Its operating frequency range is about 30 to 45 mc.

The small size makes it ideal for auxiliary police, Civil Defense workers, merchant police, ambulance crews and the like. Also, it is just the thing for those who like to know what is going on.

The circuit is simple and there are few parts (see diagram). One of the transistors is a surface-barrier type. It is used just like a p-n-p fused-junction type. However, SB units can operate at very high frequencies.

The SB transistor is used as a high-frequency superregenerative detector. The other two transistors are audio amplifiers.

The receiver, as illustrated, is a fixed-frequency type. Tuning can be changed only by adjusting C1 through a hole in the case, and even the amount of superregeneration is set at a fixed value. These are desirable features, since they eliminate controls.

Receiver sensitivity

To appraise its performance, here is a report on the receiver in use. However, bear in mind that signal strengths vary tremendously in this type of service.

From experience, the audio output is strong and clear 5 miles from a central police transmitter. Reception is usually good, even without an antenna. Reception of patrol cars or utility-truck transmissions is another matter. Unless the vehicle is very close, audio is weak and garbled.

Miniature fixed-frequency superregenerative receiver that can be held in the palm of your hand. May be set for frequencies between 30 and 45 mc

This circuit has been used with a third audio stage and a small speaker. Still, earphone operation seems preferable for one-man listening. If a third stage is added for speaker operation, considerable audio decoupling is necessary to eliminate motorboating.

Detector circuit


The superregenerative detector is the receiver's nerve center. Superregeneration develops tremendous amplification in a single stage.

Inherently, the superregenerative detector is not very selective. Also, it has a natural automatic volume control action.

With rare exceptions, the stations in the 30-60 mc band are narrow-band frequency-modulated. The pocket police receiver picks up these stations by slope detection.

Because the detector is broadly tuned and the frequency swing is very small, audio output from the detector is low. This makes the two medium-gain audio stages necessary.

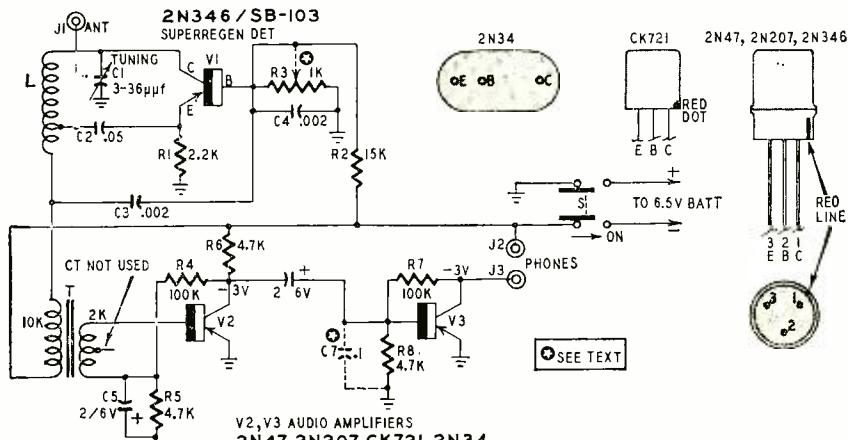The superregenerative detector's selectivity can be sharpened somewhat by setting the value of superregeneration carefully. In fact, it must be set for greatest selectivity for really good performance. This procedure requires a signal generator and is explained later.



R1—2,200 ohms
R2—15,000 ohms (see text)
R3—1,000 ohms (see text)
R4, 7—100,000 ohms
R5, 6, 8—4,700 ohms
All resistors 1/2-watt 10%
C1—3-36-μF trimmer (Bud MT-833 or equivalent)
C2—0.05 μF ceramic, subminiature type
C3, 4—0.002 μF, disc ceramic
C5, 6—0.002 μF, 6 volts, miniature electrolytic
C7—0.1 μF ceramic (see text)
J1, 2, 3-pin jacks

L—7 turns, tap at 2/4 turns (Barker & Williamson type 3003 Miniductor)
S—dpst slide
T—driver transformer; primary, 10,000 ohms; secondary, 2,000 ohms ct (Argonne AR-109 or equivalent)
VI—2N346/SB-103 (Philco)
V2, 3—2N47 (2N34, CK721, 2N207 may be substituted)
Battery, 6.5 volts (Mallory TR-165R or equivalent)
Terminal board
Case
Miscellaneous hardware

Circuit of the miniature receiver.

turns of a B & W No. 3003 coil, tapped at $2\frac{1}{4}$ turns. This coil is $\frac{1}{2}$ inch in diameter, with a pitch of 16 turns per inch.

Resistors R2 and R3 control superregeneration. I found that, with fixed frequency operation, fixed values of resistance can be used. For each individual receiver and frequency, however, these values will have to be changed for best performance. Either decrease R3 or R2. (Decreasing R2 has an opposite effect from decreasing R3.)

To make superregeneration variable, substitute a 1,000-ohm potentiometer for R3 and connect the center terminal of the control as indicated by the dotted lines in the schematic. Also, decrease R2 to 10,000 ohms.

Capacitor C2 should be a subminiature ceramic. The rather large value for C2 is necessary for superregenerative action.

Another essential is transformer coupling. The transformer characteristics have an effect on the detector's quench action. The Argonne AR-109 or something very similar should be used.

Only surface-barrier transistors will work properly in the detector circuit. The 2N346/SB-103 made by both Philco and Sprague is satisfactory (so are the military types 2N128 and 2N129).

The prices of surface-barrier transistors have recently been reduced. Now they do not cost much more than high-frequency junction types.


Audio amplification

The two audio transistors have medium beta (current-gain) figures—about 40 to 45. Any other p-n-p transistor with about the same gain is suitable. I used 2N47's, but as this transistor has been discontinued you may not be able to get any. The 2N202, 2N34 or CK721 can be substituted without making any circuit changes.


Direct-current feedback stabilization is used. While this is not as good as having emitter stabilization, it is sufficient and saves the space occupied by two emitter bypass capacitors.

The feedback does not compensate for individual transistor variations, but it does hold temperature changes of the collector current to a reasonable amount. The circuit works like this: If collector current tends to increase because of temperature effects, collector voltage decreases because of the drop across the collector load resistor. This, in turn, tends to decrease the base bias current and reduces the total change considerably. This bias method is infinitely better than just a single resistor from the base to the supply voltage.

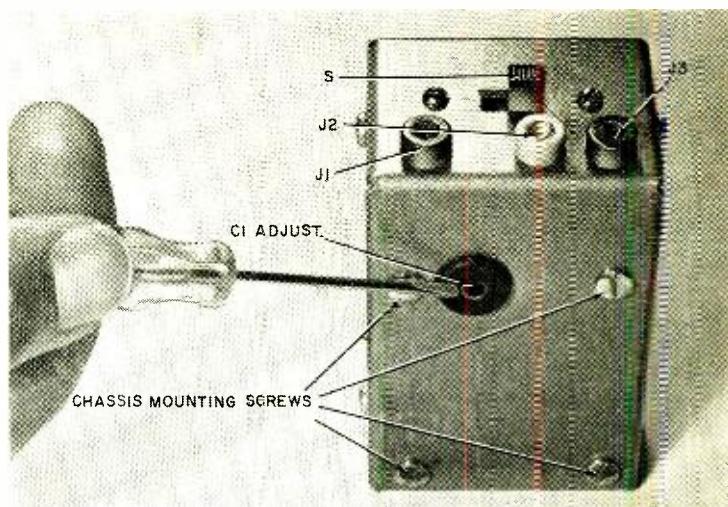
Collector voltage of transistors V2 and V3 should read -3 volts (± 0.5 volt) using a 20,000-ohms-per-volt meter. If higher, decrease the value of R4 or R7, as the case may be, to decrease the collector voltage and vice versa.



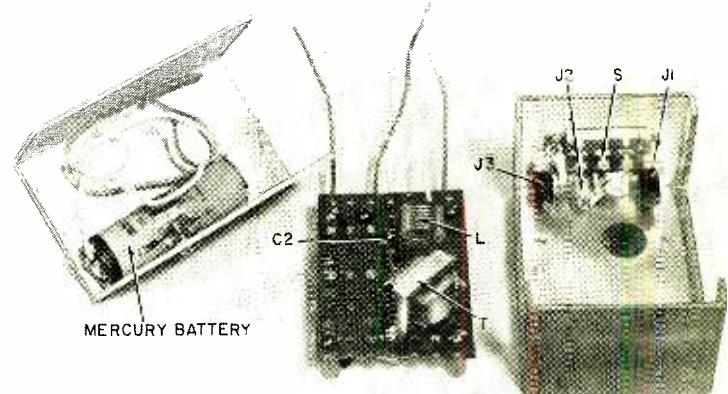The tuning adjustment can be reached through a hole in one side of the case.



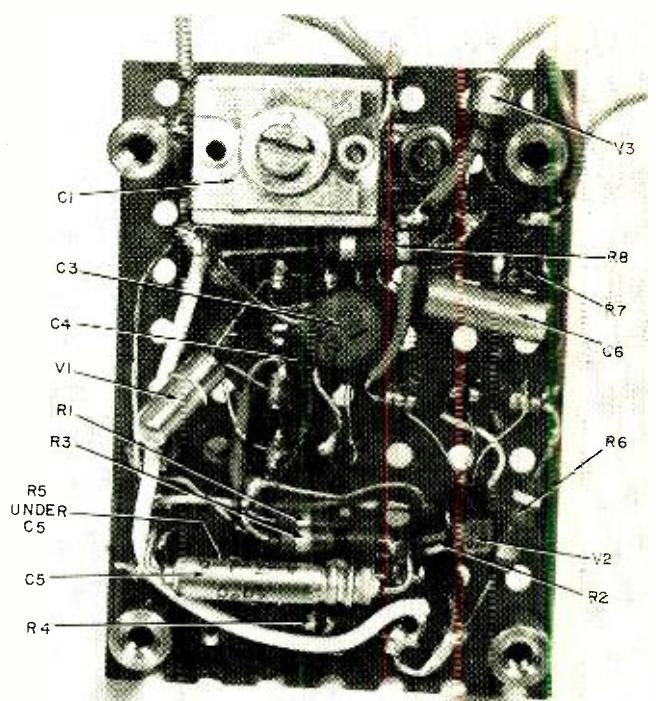Three subassemblies make up the completed receiver.



Most of circuit's components are mounted on a small phenolic terminal card.

RADIO

If a 2,000-ohm earphone is used, R7 may have to be reduced to about 47,000 ohms.

You may find that listening is more comfortable when the optional capacitor C7 is added. Capacitor C7 suppresses the ultrasonic quench frequency before it reaches the earphones or overloads V3.

A small terminal card simplifies construction. The components are wired to the card. Then the card is bolted into the case with four brass standoff spacers.

The TR-165R mercury cell is clamped to the case cover with a piece of strapping material. Of course, a capacitor clip or battery holder could also be used.

My antenna is a heavy piece of Copperweld wire, about 12 inches long, that plugs into the antenna jack. Increasing the antenna length does not seem to improve reception very much. Too much antenna length will load the oscillator and reduce the maximum working frequency.

Final check

For reception of narrow-band FM, detector superregeneration must be set for maximum selectivity. To do this, a signal generator is necessary. Assuming the set is working, a hiss or frying sound is heard when the detector is superregenerating. With the antenna connected, tune the receiver to the carrier frequency. This is found by setting the generator at the carrier with tone modulation. Now, rock the tuning capacitor C1 back and forth and adjust the value of R3 until the sharpest selectivity is obtained.

Turn off the generator and listen for a police carrier. The instant the carrier is heard, turn C1 *very slightly* for best reception. This is necessary to account for inaccuracies in the signal generator's calibration and because the detector must be tuned to one side of the carrier for slope detection. In other words, best audio will not be obtained with the detector tuned exactly to the carrier.

If the detector does not superregenerate, check the connections to the surface barrier transistor. It is easy to confuse the emitter with the base lead.

Next, check the transistor voltages. There should be about 6 volts from ground to collector and, very roughly, 0.1 volt from emitter to base. The base should be negative with respect to the emitter. Also, check to see that none of the parts have been omitted.

When the receiver is first connected to the battery, set R3 at maximum resistance. This protects V1 if the battery is inadvertently connected with wrong polarity.

The pocket police receiver gives the constructor a new project, but it is not something for the beginner. I recommend the circuit only to those who have had some previous experience with transistor circuits and vacuum-tube superregenerators.

END

Radio Runs on Low Voltage

By WARREN J. SMITH

With slight modifications, 3-way portable radios can be made to work on line voltage as low as 90

THREE-WAY portable radios often succumb to oscillator instability or failure when operated on the low line voltage in my locality (90 to 95 volts). These receivers almost invariably have a 1R5 or similar converter tube which is extremely sensitive to line-voltage fluctuation. The 1R5 cannot tolerate a drop in screen voltage of more than 10 to 15% without some ill effects. Filament voltage tolerance is even more critical. Although normally operated from 1.4 to the rated 1.5 volts, the tube functions erratically or not at all when filament voltage drops to 1.2 or 1.15. Many other portable radio faults not so readily apparent, such as low gain and poor sensitivity, can also often be attributed to low line-voltage operation.

To correct for inadequate supply voltage, I simply reduce the value of

where $E_{n\max}$ and $E_{n\min}$ are the measured maximum and minimum extremes of rectifier output voltages at point A, E_f the total voltage drop of the filament string.


Substituting actual values for line operation in our area (for the Emerson portable shown in the diagram):

$$R1 = \left(\frac{84.7 + 89.1}{2} \right) - 6.8 = 1,602 \text{ ohms}$$

.05

The closest standard resistance value, 1,500 ohms, is much too small. Therefore a series, a parallel or series-parallel combination of resistors must be made up. In this particular instance I used a series combination of standard values—1,500, 100 and 2.2 ohms for a total of 1,602.2 ohms.

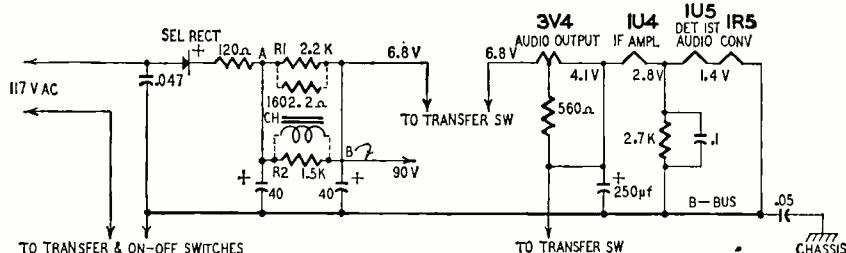In the portable used as an example, the dropping resistor in the B-plus line



Power supply circuit of an Emerson portable. Parts shown in dashed lines replace existing components.

the power supply's dropping resistors or eliminate them. Resistance changes, as illustrated in the diagram, let this particular portable operate satisfactorily, while previous operation was extremely unstable and erratic. Normal battery operation is not disturbed by this type of modification since the altered circuitry is switched out with the ac-dc rectifier circuit.

Use a Variac or similar variable ac source to determine the dc output voltage of the selenium or vacuum-tube rectifier (points A and B in the diagram) with a normal input voltage of 117. (This information usually appears in the manufacturer's service notes, but it is best to make your own tests.) Next, measure the rectifier output voltages with an ac input voltage equal to the minimum and maximum extremes of line-voltage variation in your particular area. Then, from the following formula, determine the total value of filament-dropping resistance (R1) needed.

$$R1 = \left(\frac{E_{n\max} + E_{n\min}}{2} \right) - E_f$$

$$R2 = \left(\frac{E_{n\max} - E_{n\min}}{R_n} \right)$$

where $E_{n\av}$ is the average of the low line voltage as determined from

$$\frac{E_{n\max} + E_{n\min}}{2}$$

$E_{n\max}$ is the normal voltage at point A and $E_{n\min}$ is the normal voltage at B with an input of 117 volts ac and R_n the original value of the B-plus dropping resistor (R2).

END

IDENTIFY THAT CHASSIS

A little detective work is all it takes to pin a model number on an unmarked chassis. Just follow the Old-Timer along as he shows you how



By JACK DARR

THE Old-Timer grunted loudly as he burned the tip of the finger he had unwisely poked into the small TV set he was working on. "Oww! Dad-burn it!" he grumbled. "I'll bet you I know what would be good useful equipment for a TV man—a set of asbestos fingers! Ouch!" and he sucked the damaged digit. The Young Ham, meanwhile, sat quietly at his end of the long bench, his crew-cut head bent over a car radio. Suddenly, he exploded.

"Darn it all!" he glared at the little chassis. "Why can't people put model numbers or somethin' on their radios! You'd think they were ashamed of 'em!"

"Well, some of 'em may be, and some of 'em ought to be," agreed the Old-Timer, looking up. "What's your trouble, Junior?"

"Aww, this little stinker!" growled the Young Ham. "No model number, no nothin'! This resistor's burned out, and I can't find anything on the set. How the heck do they expect us to fix 'em if you can't find out something about 'em?"

"Get out your crystal ball!" The Old-Timer grinned. "Let's see it." He got off his stool and ambled down to the end of the bench. "Ohh. That oughta be simple. I've seen several of them before."

"Well, I haven't!" burst out the Young Ham. "I can't tell beans from bones about it!"

The Old-Timer smiled at the young man's use of one of his own favorite expressions and studied the set closely. "Well, now, look here," he said, pointing into the upturned bottom of the set. "See that bypass? Says 'Bendix' on it, very plainly, don't it? Transformer does, too. Don't that tell you something?"

"OK, OK! So it's a Bendix, but what model? I've looked over the whole thing, case, lids and all, and I can't find anything on it at all!"

"Hang on, help's comin'," said the Old-Timer, reaching up to the well-filled bookshelf that ran the whole length of the shop. "You remember what kind of a car you got it out of, don't you?"

"Ford," said the Young Ham. "'53 Ford."

"Now, lessee; Chrysler, General Motors, Ford! Here we are," and he pulled a service manual down. "Now, look. Here's a Rider manual covering all the Ford radios from quite a ways back. '53 Ford, you say. Lessee. '52, '51. Here. See? Here's a picture of the front of the set. See? Looks somethin' like it, wouldn't you say?"

"Yeah! That's it!" said the Young Ham. "Now, let's see what that resistor was, before it burned up. Here it is. 1,800 ohms. Now, by golly!"

"Ah, Junior," said the Old-Timer quietly. "Ain't you a mite previous. Are you sure that's the same set?"

"Sure. Look at that front panel and the controls. Same set, see?" and the Young Ham pointed at the photograph.

"Well, that's true, but there might be one little difference. There was three people made Ford radios that year, Sylvania, Zenith and Bendix, according to the book. The one you're lookin' at happens to be a Zenith. Since when did Zenith start usin' Bendix capacitors and transformers? Huh?"

"Huh? Oh! I see what you mean," said the Young Ham sheepishly. "Got too previous, didn't I? Now, let's see in the Bendix set. Hmm. 1,000 ohms. Opps!"

"Yeah, you did get a mite quick," agreed the Old-Timer. "Now, you see what too much speed can do. It's a good idea to check up on everything before you make any rash moves, especially in a case like this!"

"Tell me, why in the world don't people put the model numbers and the maker's names on their radios and TV sets?" asked the Young Ham, as he replaced the resistor. "You'd think they were ashamed of 'em!"

"Junior, that's somethin' that'll never be known, I guess," opined the Old-Timer, as he replaced the cover on his little TV set. "That problem's puzzled radiomen since 1920, and it would have been before that, except they didn't begin to make sets until that year! Only way you can find out anything about 'em is by a long and painful process of deduction. Got that resistor in yet? I want

a coke, while I let my fingers cool off. Danged little tubes sure do run hot!"

Let's go for a coke

He was answered by a burst of rock and roll music from the car radio, and the Young Ham snapped it off. Leaping up, he announced, "I'm ready! Let's go!"

The pair trotted down the long hall and out the back door. As they crossed the alley and took their regular shortcut through the drugstore, the Young Ham said, "Gee, I wish I could find 'em that quick! I'd have been hunting all day, and you found it in just a second!"

"Hi, Hop!" said the Old-Timer, as they passed the pharmacist at his prescription counter. "How's the poison shop today?" Ignoring the rude reply, they passed on out the front door and across the street. When they were seated at a table in the soda shop, the Old-Timer got around to replying to the young man's question. "Well, Junior, it ain't so much a matter of genius as it is a combination of experience and patience," he explained. "Time you've had that button nose into as many of the things as I have, you'll be able to recognize 'em on sight, too. Main thing is, you gotta take advantage of every little clue you can find as to who made the thing and when."

"Maybe so, but what do you do when you find a set that hasn't got any clues as to who made it?" asked the Young Ham.

"They ain't no sich," said the Old-Timer, truthfully but ungrammatically. "I don't believe it's possible to build a set without leavin' some kind of a clue. Y'see, the only ones we'll have trouble with is the sets from the mail-order houses and other outlets like that. They don't build their own sets; they buy 'em from the manufacturers who make a business out of makin' sets just for such people. In fact, there used to be set makers who sold more sets under other people's names than they did their own—Wells-Gardner, for instance. Haven't seen one with their own name on it for more than 20 years, but there was more WG's than you could shake a stick at. Sears Roebuck, Mont-

RADIO

gomery Ward, Walgreen, Spiegel—everybody at one time or another sold Wells-Gardner sets, I reckon!"

"Well, what do you do then?" asked the Young Ham. "Hey, how about a coke over here?" He pounded the table, then ducked quickly as the waitress flung a water-soaked paper napkin at him.

"Well, Y'see . . . glupff!" said the Old-Timer, as the wet paper wad took him squarely in the mouth. "Hey! Phoo! How'd I git into this argument? I'm just an innocent bysitter!"

The waitress rushed over and mopped the Old-Timer's face with her apron, much to the delight of the Young Ham, then brought their cokes. The Old-Timer stirred his, then tasted it, gingerly. "Well, that takes the taste of that paperwad outa my mouth," he commented.

"Wow!" said the Young Ham. "They sure do make it cold!" and he ducked again. This sally was ignored by both waitress and proprietor, and the two finished their cokes in peace. Going out the door, they trotted back across the street, through the drugstore and back to the shop. Reaching up to the bookshelf, the Old-Timer took down a thick blue-backed book out of a set there. Opening it on the bench, he located a diagram.

"Here's a good example of what I mean, about some of those old-timers," he said. "See here? Here's a Sears Roebuck set listed under their trade name, Silvertone. Now, looky here," and he turned to the back of the book. "See? Under Wells-Gardner, here's the same set—Look at the tube lineup, the circuit and so forth."

"Yes, I can see that," said the Young Ham, "but how are you going to tell just who made the thing if you've never seen one like it before?"

"Well, that's the hardest part," admitted the Old-Timer, "but there's a kinda method you can use on all of 'em and find out what you've gotta know. It's a kinda combination of every little thing you can see: the cabinet, the chassis, the tube lineup, the general appearance of the set and everything else about it. If they all agree, then you're home free. Some people use a code in the model numbers, that's a big help. Montgomery Ward's Airlines, f'rinstance, since about—lemme see, 1939, I think. Yeah. See here?" and he pointed out a listing in the index.

"How can you tell anything by that?" asked the Young Ham. "Just looks like a mess of numbers to me."

"Nope; they're just full of information, if you know how to read 'em," said the Old-Timer. "Look at this model number here. '93BR508A.' Turn the first two numbers around and you've got the year it was made: 93—1939. Then the 'BR' tells you that it was made by the Belmont Radio Co. or, if it was 'WG,' by our old friend Wells-Gardner, and so forth. That'll help, if you can find the year it was made."

"Where do you go from there?" asked

the Young Ham. "Even if you do know the year, how do you find it in all that stuff," indicating the 20-foot bookshelf, filled with manuals.

Lots of service data

"Well, that's not too hard, either," said the Old-Timer. "All these Rider manuals are roughly numbered according to the year they came out, beginning with Vol. 1, which came out in 1930. So, if you wanted a set made in 1940, you'd be like to find it in Vol. 10, and so forth. Feller needs a pretty complete set of all the service data he can git his hands on, to do much of anything with this kind of work."

"Well, you've got that, I'll say that for you," said the Young Ham, eying the well-filled bookshelf and the stacks of assorted service information which covered nearly every flat surface in the shop.

"Yep, I have," admitted the Old-Timer. "And I use it all at one time or another too. Tell you what though. One of these days I'm gonna git in here and straighten out all of this stuff and file it like it oughta be! Lessee now, where were we?"

"You were talking about Airlines," said the Young Ham.

"Oh, yes. Now, look here. Here's another helpful soul—the Truetone sets sold by Western Auto Stores. They give you model numbers with codes in 'em, too. See this one? Model D-1191WG: 'Factory No. 6C18-3.' This means Wells-Gardner again. If it was BRC, Belmont; DRT, Detrola, and so on, just like the others. Then, you can look this up under Wells-Gardner and probably find it listed under model 6C18."

"Tube lineups are helpful, too," he continued, "especially on the older sets and once in a while on the new ones. Take this guy here, f'rinstance. Look. He's used a 12J5 as an oscillator and a 12SA7 as only a mixer tube, instead of using the 12SA7 as both. Well, all you have to do is look through your manuals until you find somebody else using the same circuit with the same tubes, and you've got him. Lots of other little peculiarities like that, if you take the time to look 'em up. Certain designers have certain habits and the chances are they'll use 'em over and over again, for several years, anyhow. If a certain guy uses a kind of trick circuit one year, you can be fairly sure that you'll find the same circuit in several sets, especially if it works fairly well!"

"You mean they use the same circuits in all the sets?" asked the Young Ham, with a bewildered look.

"No, not at ail," answered the Old-Timer. "What I meant was just certain parts of the circuit, like the if's, the oscillator stage, the front end and so on. Take Philco, for instance. One year they used an if stage with a little tertiary winding in the if amplifier screen circuit. Well, they used that same circuit for at least three years. So, if you

had if troubles and couldn't find the right diagram, you could look up the same circuit in another set, even if it was a year later. See?"

"Oh, I get it, now," said the Young Ham: "You can kinda make up enough information to get what you need, even if you have to use the diagrams of several different sets!"

"Now you're getting the idea." The Old-Timer applauded. "It's not where you find it, but what you find! There's a heck of a lot more service information available now than there was when I started, too. Why, they're even pasting schematics inside the cabinet on a lot of sets now, and that's a big help. TV sets, well, that's a different story. A TV set's a heck of a lot more complicated than a radio, and there's still a heck of a lot of variation between makes as to the different circuits. Thank goodness, they're beginning to settle down some by now, though. Different manufacturers are beginning to use the same circuits in the same places, with only minor variations here and there. Like the high-voltage supply—I guess about everybody uses the same general circuit by now. You don't find any more line-voltage supplies with the tremendous transformers, or rf power supplies with the separate oscillators and stuff like that, that we had in the early-day sets, and hurray for that!"

"No, sir, TV sets are not all alike, yet," agreed the Young Ham. "Not with all the funny tubes they're coming out with now."

TV set clues

"Well, that's sometimes a hindrance and sometimes a help," said the Old-Timer. "Some manufacturers have a habit of using certain tubes. That'll help you identify their sets, no matter what name they're under. For instance, Zenith used the 6BN6 tube as the sound discriminator for several years and no matter what set you had, if it had a 6BN6, chances are it was a Zenith. Now, we've got the same situation in



TV that we had in radio. Different makers are selling sets to chain stores, mail-order houses, and so on. The only way you can tell what kind of a set it is to give it the same treatment. Look it over carefully, check for brand names on the tubes, transformers and so forth. Look at this one here. This is an easy one." The Old-Timer indicated a small TV console in the finished-work department. "Says 'Truetone' on the cabinet, but look at it closely. What does it look like? We've had several of them in here lately, from ol' Walker's, down the road. Recognize it?"

"Why, it looks just like those—Oh, what was the name of that set—Oh, yes! Raytheon! That's what it is, a Raytheon!" said the Young Ham, excitedly.

"Kee-rect the first time," said the Old-Timer. "You'll also find that same set under Silvertone—had one the other day, out on 15th St. And, you know Ol' Dingbat's Stewart-Warner? The Gasman's? The 9300 series? I found one of them the other day, carrying a Silvertone nameplate, but it was a Stewart-Warner 9300 'cause the first thing I spotted was that characteristic heavy metal bridge over the yoke. That's another thing you want to remember. Look for characteristic construction features—like that bridge, or something distinctive. For instance, maybe some company always mounts their tuners way out to the side, actually off the main chassis. That's a trademark. Maybe they use a certain given kind of printed-circuit assembly—like Westinghouse or Admiral or G-E. Why, I even identified an Airline TV set one time by the dern knobs! It turned out to be a Bendix and they had those peculiar cutout knobs, with the inside shaft on the outside knob, and so on. Nobody used them that year but Bendix, and I spotted it that way!"

"Gosh, it'd take you a lifetime to learn all of the darn things," sighed the Young Ham in discouragement.

"No, not necessarily," said the Old-Timer. "All it takes is a pretty good memory for those little quirks and characteristics I've been talkin' about, and the ability to put 'em all together and make 'em spell out the name of the set. That, and somethin' you could use just a wee bit more of—patience!"

"Who, me?" said the Young Ham, aggrievedly.

"You," rejoined the older man. "In common with all kids, you want to git everything done today! Don't forget, there's always tomorrow, and you've got plenty of time! Take it slow and easy, and be sure you're right before you go ahead."

"But, back to the subject of identification. It's only once in a while you really need a schematic, especially since so many people got thoughtful and started puttin' tube layouts inside the cabinets on TV sets. Why, some actually put the heater string layout in the sets with series heater circuits and don't think that ain't handy! If they

ever stop doing that, we'll sure be up that well-known creek without any form of propulsion!

"Anyhow, like I said, the only time you've got to have a schematic is when something's burnt up, like a resistor or a coil and you can't get the identification from it. Although, come to think of it, coils, transformers, yokes and the like ain't too much of a chore. Look here." He dug a catalog from the file. "Here's a catalog put out by Merit that lists all kinds of TV sets and their components, especially yokes, transformers and stuff like that. Sets are listed by make and model number, and it's very little trouble to look up one and find out just what part you need. Thordarson, Sprague, Miller and several others put out similar catalogs. You can get 'em from your parts supply house or direct from the manufacturers. Sure are handy, too!"

"Do you know that you can even use these books backward? Instead of looking up the parts from the make and model of the set, you can look up the set from the make and part number of the part!"

"How's that again?" queried the Young Ham. "Run that by slowly, and let me get a better shot at it."

"All right, look. You've got a TV set. You know it's a Silvertone, say, but the model number's been scratched off or something. From the tubes, you've got a reasonable suspicion as to about what year it is, and—"

"How's that, now?" interrupted the Young Ham. "How can you tell from the tubes what year a set was made?"

"Well, you can't, too definitely, but you can get a general idea," admitted the Old-Timer. "Take the 3-volt series. When'd they come out, first? Last year, was it? Anyhow, if the set has 3-volt tubes in it, you know it was made sometime within the last 2 years, on account of they didn't make the tubes until then! Older sets, if they have tubes that haven't been in common use for several years, you know they aren't newer than a certain year, and so forth. Oh, just f'rinstance, if you find a 6AC7 in the video output, the set's apt to be over 3 years old because they haven't, as a rule, been using 6AC7's there since about that period. It's just a general hint, that's all."

"I see—I think," admitted the Young Ham.

"Now, where was I? Oh, yes. I was lookin' up sets by part numbers. Yeah. All right. First thing, you take the part numbers off two or three big parts, like the yoke, power transformer, fly-back transformer, vertical output transformer and so on. Copy 'em down on a piece of paper, and start lookin' through the catalog for a set, of the right make, which has *all* of those numbers! Chances are, when you find it, it'll be the right one. If it ain't, you can usually get so close that you can use the diagram of that set to find out what you want to know! Why? Because, if it uses all of the same parts,

there's bound to be a pretty good similarity between the two sets, see?"

"I think I'm beginning to get a glimmering of the idea," said the Young Ham.

"Well, it's usually a lot of dern trouble, any way you look at it," said the Old-Timer, "but sometimes that's the only way you can get the information you have to have. Guess the only way you could sum it up would be to compare it to a detective, lookin' for clues. You've got to take every little clue you can find. The cabinet, the shape and size of the chassis, the tubes, even the kind of parts, the type of construction used and every little detail. Why, I remember, a long time back, I even identified a radio because one part had a big long part number! Happened to think that the Colonial people had a fancy for great long part numbers, looked one up and there it was! So, if you take advantage of every clue, no matter how small, and add 'em all up right, you come up with the right answer, just like Friday. All you gotta do is get the facts, ma'am."

"Dum-di-dum-dum!" agreed the Young Ham.

"Yes, sir!" said the Old-Timer, leaning back on the bench, "that's gotta be your motto. No fact too small, no clue too insignificant!"

"Well, I can tell you one small insignificant fact you're overlookin' right now," said the Young Ham.

"Huh?"

"There," pointing to the clock. "It's 5 after 6, and I've got a heavy date. We're on overtime right now!"

"Ye Gawds, we can't afford that," cried the Old-Timer, leaping off the bench. "Let's git outta here. My wife's gonna kill me. I told her I'd be home early tonight, too!"

"Down scope, crash dive, all ahead flank," yelled the Young Ham, his voice fading rapidly as he dashed down the hall. "Night!" The Old-Timer grinned, pulled the master switch, looked around for cigarettes left burning and ambled after him.

END



RADIO

An easy-to-build oscillator without a tuning capacitor

slug-tuned VFO has stable output

By JACK GALLAGHER, W5HZB


THE difficulties which arise in the construction of a vfo can be reduced by proper choice of circuits. The Clapp oscillator—a very popular circuit because of its stability—is a good choice for a vfo if space is not a major consideration. Although it has good voltage stability, the output varies over the band unless gang tuning is used.

If space is to be considered, a circuit requiring low inductance will make large coils unnecessary. A circuit of this type will require a large amount of capacitance in the form of fixed and variable capacitors and would normally offset the space gained by using a small coil.

A high-C Colpitts oscillator whose frequency is between 1.7 and 2.2 me, and has a high degree of stability and uniform output over the band is shown in the diagram. To eliminate space-consuming variable capacitors, a slug-tuned coil (L1) is used for frequency variation. A total tank capacitance of some 2,320 μf is used across the coil in the form of two .001- μf silver mica padding capacitors (C1 and C2) and the series combination of the feedback capacitors of 470 μf and .001 μf .

Since the Q of a coil for use in a Colpitts circuit can be low compared to the Q required for the Clapp circuit, the Millen type 74001 slug-tuned form is a compact and easily adjusted coil to use with this oscillator.

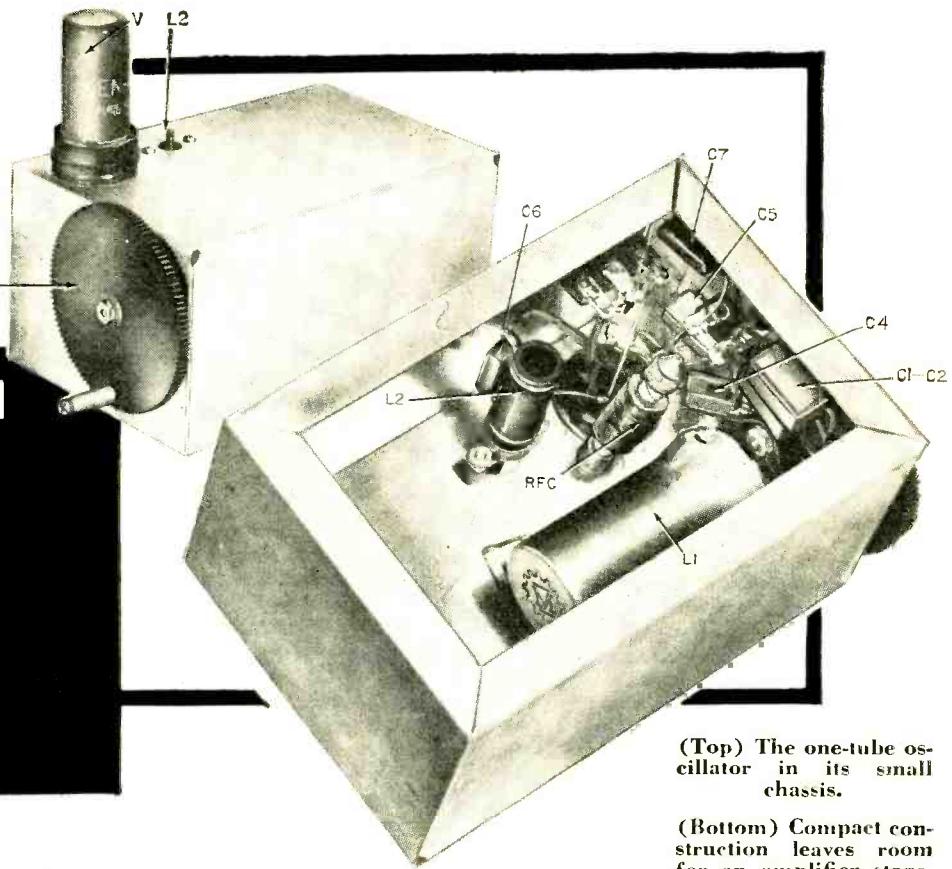To keep cost to a minimum, complicated and sometimes troublesome mechanical drive assemblies were re-




(Top) The one-tube oscillator in its small chassis.

(Bottom) Compact construction leaves room for an amplifier stage.

jected. The knob for the unit shown in the photographs was made from a bakelite gear removed from an old tuning capacitor. Since the travel of the slug screw is less than $\frac{1}{2}$ inch, it is easy to make fine adjustments with the tuning knob.

While the 6-40 screw threads on the slug screw provide smooth adjustment and about 40 kc of variation for one revolution of the shaft, almost any variation can be obtained by winding the coil in a different manner.

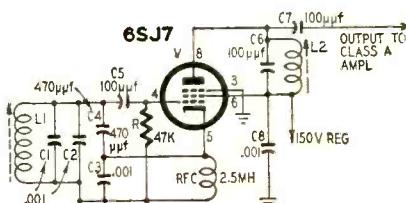The coil in this unit is wound with 18 turns of No. 20 enamel, spaced in a distance of $\frac{1}{8}$ inch. First, the slug was placed at the bottom of the form and the winding started at the top of the slug. The first 9 turns were spaced



R—47,000 ohms, $\frac{1}{2}$ watt
 C1, 2, 3—.001 μf , silver mica
 C4—470 μf , silver mica
 C5, 6, 7—100 μf , mica
 C8—.001 μf , disk
 L1—18 turns of No. 20 enameled spaced in $\frac{1}{8}$ inch (see text)
 L2—60 turns of No. 30 enameled closewound on a Millen No. 74001 $\frac{1}{2}$ -inch-diameter slug-tuned form
 RFC—2.5 mh
 V—6SJ7
 Chassis—4 x 5 x 6 inches
 Knob
 Miscellaneous hardware

Circuit of the slug-tuned vfo.

slightly greater than the wire diameter and the last 9 turns were closewound, ending about $\frac{3}{4}$ inch below the top of the form.

Although a similar winding method can be used to provide linear bandspread for slug tuning, it was not attempted in this case. The turns were spaced as described merely to cover the frequency range previously mentioned. After the range was checked, the coil was doped sparingly to hold the turns in place.

The construction of the oscillator is simple and straightforward with the exception of mounting the slug-tuned coil. It was mounted as shown in the photographs with a standard octal socket, which clears the aluminum box by $\frac{1}{4}$ inch, leaving ample room to remove the coil for adjustments. A $\frac{3}{8}$ -inch hole provides clearance for the slug screw.

The slug-tuned plate coil (L2) is mounted to the right of the 6SJ7 oscillator and is adjusted from the top of the chassis. The slug is set for maximum output. If the oscillator is set at 1950 kc, the output will be almost constant as the tuning is varied from 1.7 to 2.2 me.

Since the oscillator occupies about half the $4 \times 5 \times 6$ -inch chassis, there is room to add a class-A amplifier stage. This will help increase stability when a transmitter is keyed and also provides an ideal keying position. The plate supply of 150 volts should be regulated with a VR150 or an OA2. END

KNOW

YOUR

Both low- and high-level amplification have built-in complications. Discover what they are and how to beat them

LEVELS

By NORMAN H. CROWHURST

SOME things about designing or using amplifiers you can find in any textbook. But for some unexplainable reason other items of information that ought to be easy to find seem to get left out. For example, operating levels at various points in an audio system.

The amplifier user needs to know this so he can put the right items of equipment together and get the best performance out of the whole system. The amplifier designer needs this knowledge to select the right components for his amplifier.

A closely related piece of information—that of impedance matching—gets discussed in every second article on amplifiers. So it is common knowledge that a 50-ohm microphone must be connected to a 50-ohm amplifier input. A number of articles have shown how to make resistance pads to match one impedance to another.

I was called in recently on a case which aptly illustrates the lack of this knowledge. My job was to make a microphone-amplifier-loudspeaker combination work. The man who called me had paid careful attention to matching. The microphone was 50 ohms and the amplifier had a 600-ohm input, so he used a line transformer from microphone to amplifier. However, he was unable to get any output from the system.

Examination showed that the amplifier was designed to operate from an input level of 0.5 to 1 volt at 600 ohms. The microphone was one of the higher-sensitivity dynamic types which gives about 3-mv output across 50 ohms for normal speech. The matching transformer from 50 to 600 ohms stepped this voltage up about 3.5 times, delivering a little more than 10 mv to the amplifier. But 10 mv is not enough for an amplifier that needs an input of 0.5 volt (500 millivolts).

"You need more amplification," I told my caller.

"That's easy," he replied, "I have another of these amplifiers here on the shelf, and you know how to make a matching pad so I can work the 16-ohm output of one into the 600-ohm input of the other."

I explained that what he needed was not another power amplifier but a preamplifier for working at low level. This he did not seem to understand. He thought amplification was amplification, and between the two amplifiers there should be enough of it. So I explained briefly why this arrangement would not work.

But how many of us have had to find this out the hard way—by trying it—simply because there was no one on hand to tell us what would happen? Fortunately this job did not prove difficult, because he did have a comparatively high-sensitivity microphone and it wasn't too hard to find a preamp that would work successfully with this power amplifier.

If he had been trying to use a mike with a much lower output level, there would have been bigger problems in finding a satisfactory preamplifier. So let's start at the input end and see what it takes to make a good amplifier that will handle signals at all levels.

Low-level components

When we set out to build an amplifier for amplification at low levels, from insensitive microphones and pickups, particularly the ribbon type, we have to be very careful when selecting components. The first tube gets a maximum signal of only a few millivolts at its grid. It is expected to make these signals audible at the output. This is getting down to the level of tube hiss and the hum generated in a good many tubes.

The input circuit must be carefully

shielded to avoid hum pickup. This part of the story, though, has been well discussed elsewhere from time to time.

Tube hiss is due to plate current, which consists of electrons flowing from cathode to plate. Each electron transit is a separate event, so the plate current is made up of a random sequence of separate charges passing from cathode to plate. The average rate of transit determines the measured current. When amplifying low-level signals, changes in plate current due to the applied audio grid voltage are not much more than the fluctuation in rate of arrival of electrons at the plate due to the random nature of their departure from the cathode. Therefore, tube hiss is apt to be almost as loud as the audio signal we want to use.

Ways have to be found to minimize tube hiss. The noise a tube generates due to these effects is obviously proportional to the total current flowing—the proportion of fluctuation in electrons arriving at the plate is proportional to the average total number arriving. The noise voltage they develop at the plate is also proportional to the fluctuation in the velocity at which they arrive. The fluctuation in velocity is proportional to the actual velocity.

Therefore, halving the plate current will approximately halve the noise output of a tube and halving the plate voltage will also approximately halve the output. But halving the plate current or plate voltage does not necessarily halve the tube's gain.

Over a wide range of variation in plate current and voltage, a tube's amplification does not vary by too much. Operating the tube with low plate voltage and current gives almost the same amplification as a higher plate voltage and current, but considerably reduces noise introduced by the tube.

From the standpoint of noise, two things are required of an input stage:

AUDIO—HIGH FIDELITY

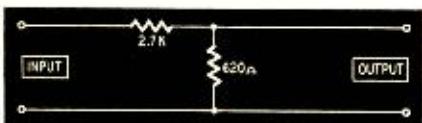


Fig. 2—Matching pad used between preamp and power amplifier permits best operation of overall system. The values suit the example given in the text. For other problems values should be worked out to suit the combination of equipment.

This means that a 12AU7, operated with its two triodes in push-pull, gives distortion and output comparable with a 6SN7, a considerable aid toward miniaturization.

A tube that may look tempting for some purposes is the 12AT7. It gives considerably more gain than either of the others just mentioned and its output is not too much less than theirs. While the 12AT7 has a very acceptable distortion figure at low levels—an input voltage of not more than 0.1—its distortion figures at higher levels do not compare favorably with the other tubes.

I could go on to discuss a whole range of tube types and their relative advantages and best modes of operation. The point I want to stress here is that in the design and use of amplifiers it is important to use the correct type for the purpose.

Other components in the circuit also have different requirements to meet for high-level operation than those at low-level operation. For low-level operation the important feature is reducing noise. At high-level operation the component must be able to handle maximum signal.

A point that can easily be overlooked is the dissipation of resistors. We may determine that a resistor has to drop 100 volts at 20 mA. Its value should be 5,000 ohms. A 4,700-ohm resistor looks like the nearest preferred value for this purpose. How often has the prospective amplifier builder dipped in his box of 4,700-ohm resistors (½-watt rating) and cheerfully put one into his circuit?

Had he stopped to do a little figuring he would have found that 100 volts at 20 millamps is a dissipation of 2 watts. This would have saved him from finding his voltage-dropping resistor burned out before the amplifier had been in service very long.

So it's a safe rule to check the dissipation of all resistors in high-level circuits. Allow a safe margin, remembering that signals on top of dc potentials *always* increase the resultant dissipation.

There is one more component to consider in high-level circuits—the output transformer. However, designing or selecting an output transformer that will work successfully in a power amplifier is a story in itself. The output transformer is the heart around which a power amplifier is designed. As this is the subject of another article I will not take up space discussing it here.

When putting a system together it is important to know what levels are so you can arrange to minimize both noise and distortion. For example, working a preamplifier into a power amplifier, the power amplifier requires a certain input to give the full power output of which it is capable—usually between 0.5 and 1 volt. The preamp may be capable of giving out as much as 4 or 5 volts before it runs into serious distortion.

If a direct connection is made between these two items of equipment, the gain control of the preamplifier will have to be set between 10 and 20 dB below the best operating level. As a result, the input fed to the power amplifier is likely to have more hum and noise than if the amplifier were designed to accept the full output of the preamplifier. The way to get the best performance out of this combination is to insert a resistance pad of the type shown in Fig. 2 so the preamp can deliver its full output of 4 or 5 volts while the power amplifier gets only the output of 0.5 to 1 volt that it needs.

Values can be calculated to suit the particular circuit in hand. Those shown in Fig. 2 suit a preamp with cathode-follower output, working into a power amplifier designed for a 600-ohm input. Although cathode-follower outputs are sometimes advertised as being 600-ohm or similar impedance, they work much better into an impedance higher than this, so it is well to build up the load impedance applied to the output of the

preamplifier rather than using the nominal value given.

Use the chart as an aid in calculating the various levels in a system, taking into account impedance changes. To illustrate how it is used, one microphone is listed as giving an output level of -56 dbm for 10 dynes/sq cm, impedance 50 or 50,000 ohms. Another is listed as -59 db referred to 1 volt per microbar. How can we correlate this information?

A microbar is the same as a dyne/sq cm, but some people prefer to use one or the other. And 10 microbars or 10 dynes/sq cm represents normal speech level.

The first microphone is listed with a power-level rating for both available impedances. Using the chart, you will find that -56 dbm corresponds to 350- μ v at 50 ohms, or -69 db referred to 1 volt. This form of reference is seldom used for low-impedance circuits. For 50,000 ohms, -56 dbm corresponds to 11 mv or -39 db referred to 1 volt.

The second microphone, being only high impedance, uses the voltage reference as being more direct. But it is quoted as -59 db for 1 microbar. Microbars being a unit of acoustic pressure, 10 times as many will induce 10 times the voltage. Since -59 db is 1.1 mv, 10 microbars will give 11 mv, or -39 db.

So the ratings mean both microphones have the same output, which we would never have known without this calculation!

END

**You
appreciate
him only
when you
need him . . .**

Cops can be (and frequently are) a pain in the neck. But when you really need one—they're nice to have around. That goes for advertising cops too. Maybe RADIO-ELECTRONICS mail-order tube policy is a nuisance to some people—certainly it is to the "fast buck" operators. But it's good to know it's working for you when you buy tubes by mail. Since January, 1956, the publishers of RADIO-ELECTRONICS have insisted



that mail-order tube advertisers state the condition of the tubes they sell—new or used, perfect or seconds, rejects, or surplus. It's no fun to play "cop"—but as long as it saves you from being gyped, we'll keep on doing it.



Reviewed by
CHESTER SANTON

Station WQXR, New York City

LAST month we looked into a special category of tape releases—individually made tapes designed to test the performance of tape machines. In general circulation these days are two other test tapes. These, however, are processed on duplicators: Westminster-Sonotape's 24-minute test extravaganza *Stereophonic Alignment Tape* (SWB-AL 101) at \$11.95 and Stereophony's 4-minute *Test Tape for Stereo Balancing* (T-50) at \$1.98. Containing more than test tones, both tapes have wide appeal. Playback in each case is 7.5 ips. At that speed, tape response today is reasonably flat to 10,000 cycles. Above that figure, frequency response falls off. For that reason, the Ampex and Livingston test tapes reviewed last month confine themselves to top test tones of 10 kc in the former and 12 kc in the latter.

Sonotape, by "strong-arm" tactics in gain boosting, manages a high-frequency tone labeled "15,000 cps for head alignment." The tone has audible intensity at normal listening level. The test frequencies are followed by an elaborate series of tests for balancing volume and equalization in the two channels. Perhaps the most useful of these is an excerpt from *Peter and the Wolf*. The music is switched several times from one channel to the other. With equalization controls of each channel in a flat position, this test is a good reference if further adjustments are necessary in the bass and treble setting on either channel. All told, the Westminster tape is quite a production. As a grand finale, the sounds of a subway train are merged with Tchaikovsky's *Fourth Symphony*.

The Stereophony tape performs its function without fuss or frill. Test tones of 3,000 cycles are alternately heard on each channel. The process is then repeated with tones of 100 cycles. In the final episode, the narrator moves from one microphone to the other. If the channels are in balance, he comes to a halt at a point midway between the two speakers.

If your system has separate volume controls, even the simplest tape for alternate-channel balancing can be useful in locating the "center of gravity" of the sound suspended between the speakers. Once located, its value is obvious, especially in the opening measures of classical music where one side of the orchestra provides most of the sound.

Stereophonic Recordings

Now that the stereo record is on the market, experiment in this medium has reached the consumer level. Audio Fidelity made this possible with its release in March of four Stereo-discs: *Dukes of Dixieland* (1851), *Railroad Sounds* (1843), *Music of the Bullring* (1835) and *Johnny Puleo and His Harmonica Gang* (1830)—all priced at \$6.95. Played with the Electro-Voice ceramic stereo cartridge, these records exhibit reasonable stereo effect when the recommended distance of 6 to 8 feet separates the loudspeakers. The audio quality is passable. In my opinion, cleaner sound was present on the first truly compatible stereo disc demonstrated by Columbia Records during the recent IRE convention. As in stereo records, the commercial releases will tell a more complete story.

Walter Schumann presents the Voices
RCA-Victor Stereo Tape APS-103
(7-inch; playing time, 15 min. \$6.95)

tion in the ensemble work in the classic *King Porter Stomp* with the brasses appearing several feet above and beyond the sax section. The disc version (Jazztone J-1285) offers far more music in equally straight-forward sound.

Modern Orchestral Textures

Willis Page conducting New Orchestral Society of Boston

Cook Stereo Tape 1068

(7-inch; playing time, 19 min. \$12.95)

Audiophiles familiar with the *Pacific* 221 performance on 10-inch LP will welcome the same Cook version on stereo tape. Honegger's orchestral portrayal of a locomotive demands a spatial medium for full impact. The mixing, unusually distant, dictates a moderate volume setting to stay below the noise level of that day. The tape includes Debussy's short, atmospheric *Danse* and a performance of Barber's *Adagio for Strings*, which I prefer to most other recorded versions.

Monaural Recordings

Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

BEETHOVEN: Piano Concerto No. 5 in E Flat (Emperor)

Rudolf Firkusny, Pianist

William Steinberg conducting

Pittsburgh Symphony Orchestra

Capitol PAO 8419

Capitol's time-tested mixing formula for the Pittsburgh hall contains a recent refinement. According to Frank Abbey, chief recording engineer at their sessions, the single Telefunken located in the first row of the concert hall's second balcony remains the basic microphone for overall pickup. All of the Pittsburgh recordings have utilized it. On stage, however, three Telefunkens have now replaced the ribbon mikes formerly used for solo passages in the orchestra. An extra Telefunken picked up the piano. The result—a true concert hall balance. The performance of Beethoven's greatest piano concerto is an excellent one.

London Microgroove Frequency Test Record

London FFRR 5343

London's new test recording is based on the RIAA curve. Its 25 tones range from 30 to 18,000 cycles. The separate frequency bands are arranged in groups of five. Frequencies above 10 kc are recorded 6 db below standard curve. Side 2 contains gliding frequencies with the same range and levels.

Espana, Vol. 9

Ataulfo Argenta conducting Orquesta de Camera de Madrid

London FFRR LL-1740

Orchestral interludes from the Spanish lyric theatre directed with smooth authority by the late Ataulfo Argenta. London's latest recording in *The Music of Spain* series enhances the reputation for sound established in previous volumes. This disc holds its richness of sound at all levels. A deluxe item.

Bagpipes and Drums

9th Regiment, New York State Guard Pipe Band

Audio Fidelity AFLP 1857

Giant Wurlitzer Pipe Organ


Leon Berry, Organist

Audio Fidelity AFLP 1844

On a good system, the low bass on these two records will jar loose the fillings in your teeth, so close is the pickup. Audio Fidelity has added to its microphone roster the Electro-Voice 667 with transistorized features. Their closest mixing to date does away with virtually all room acoustics. To reinstate some of them, try listening to these in an adjoining room. Traditional bagpipe music on the first record. The second offers rumpus-room fare on the Wurlitzer that Leon Berry has installed in the basement of his home.

END

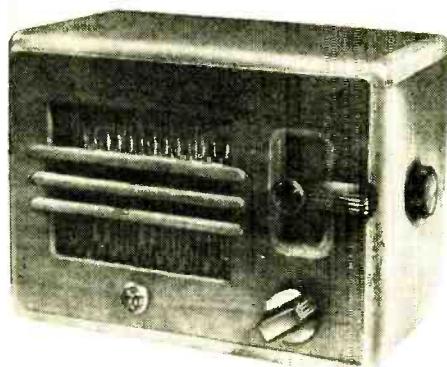Name and address of any manufacturer of records mentioned in this column may be obtained by writing *Records*, RADIO-ELECTRONICS, 154 West 14 St., New York 11, N.Y.



Remote Transistor Ear

This 3-transistor intercom has a 1/2-watt output

By F. J. BAUER, JR., W6FPO

NOW that low-priced power transistors are generally available, you can build transistor equipment with power output equal to that obtainable with vacuum tubes. The intercom described in this article is an all-transistor device which plugs into the 117-volt ac power line. It has an audio output of approximately 1 watt which is instantly available as no warmup time is required.

There are three transistor audio stages, and a selenium bridge rectifier for the power supply. The circuit is simple and conventional except for the input stage, which is connected as a common-base amplifier. This configuration does not require an input transformer since its input impedance is low enough to work directly as speaker voice-coil impedances. Eliminating the input transformer also reduces the possibility of hum pickup by the input stage and results in a quiet, high-gain amplifier. The .015- μ f ceramic disc capacitor connected across the amplifier's input eliminates broadcast-station interference when the intercom is used with a long remote-speaker line. The rest of the amplifier circuit is straightforward, employing transformer-coupled common-emitter stages.

All parts are standard and readily available, with the possible exception of output transformer T3. I used an Aeme Electric Corp. T-24041. If you cannot obtain this unit, you can use a Thordarson TR-61. The primary's et is not used and only the 3.2-ohm tap on the secondary is shown in the diagram. The power transformer is a 6.3-volt heater transformer with a 1-ampere rating.

No attempt was made to miniaturize the unit. Plenty of room was available for standard components on the 6½ x 4-inch chassis. Standard components also reduce the cost of parts.

The 2N255 power transistor is plugged into a nine-pin miniature tube socket with no heat sink for the collector. Its case must be insulated from

the chassis. A heat sink is not required because the power input to the 2N255 is limited to 1.25 watts, or half the transistor's maximum dissipation rating.

Hints for better construction

The parts layout is not particularly critical. In general, the amplifier follows a logical layout from left to right when viewed from the rear, with low-level components such as the small transistors and interstage transformers mounted at the left end. The output transformer, power transistor and selenium rectifier are mounted at the right end of the chassis, as shown in the photographs. When laying out the amplifier, pay particular attention to the following items to avoid possible feedback troubles:


A ½-inch separation between the

speaker frame and output transformer core is minimal, as shown in the photographs. If the transformer is too close to the speaker, you'll get audio feedback when the intercom speaker is used as a microphone.

The output transformer's secondary leads must be routed well away from the speaker, preferably below the chassis to prevent feedback. Shield this lead and ground it to the chassis.


Do not mount the power transformer on the chassis. The field from the transformer will induce a 60-cycle hum in the speaker when it is used as a microphone, no matter where the transformer is placed on the chassis.

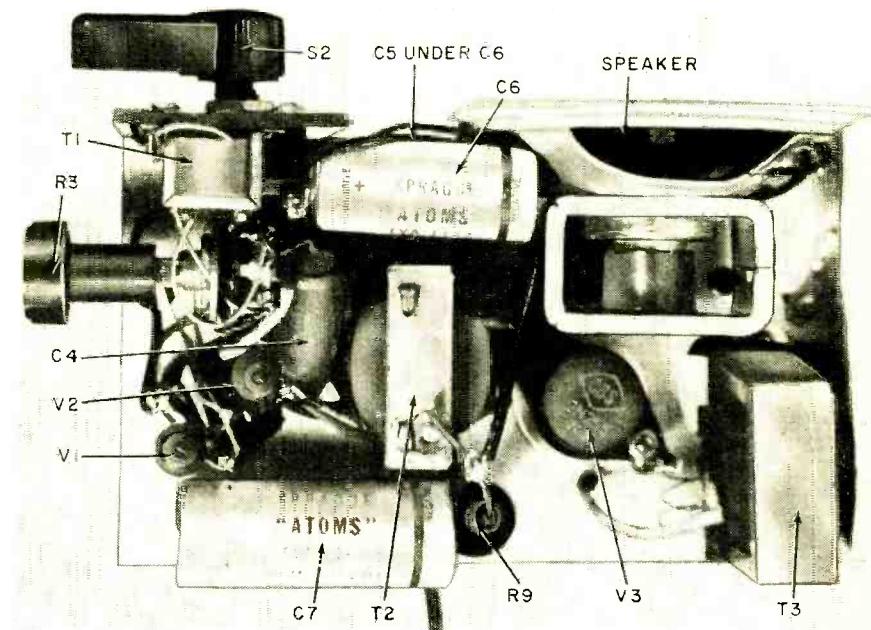This problem is solved by completely isolating the transformer from the intercom. The transformer is mounted in a small metal box which plugs directly into the ac outlet. The ac line running



Top view of the completed intercom. The remote speaker connects to terminals on the rear of the unit.

AUDIO—HIGH FIDELITY

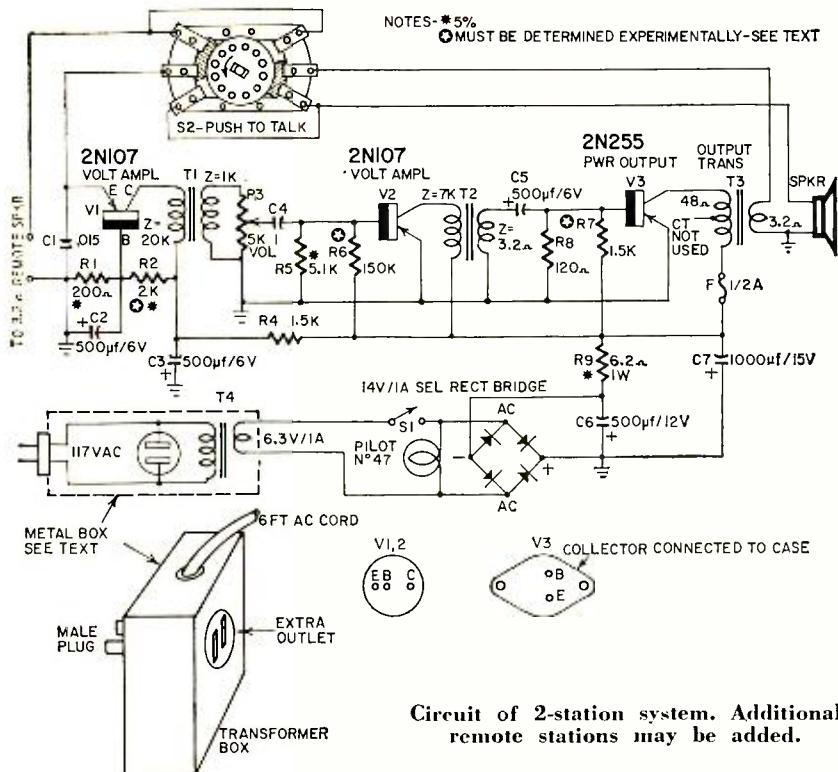

from the transformer box to the intercom unit carries 6 volts. During operation, the remote power transformer is left on continuously and the intercom switch is used to turn the unit on and off. The switch merely opens a lead to the bridge rectifier. This arrangement is practical since the transformer draws negligible power from the line, especially with the intercom switch in the off position.

I mounted some of the electrolytic capacitors above the chassis since they are bulky and chassis space is available. The capacitor leads are covered with insulating tubing and routed

through holes in the chassis as required.

Selecting the bias resistors

The unit should be completely wired except for the base bias resistors (R2, 6 and 7) and the push-to-talk switch (S2). Connect the intercom speaker to the output transformer temporarily and connect a remote speaker to the amplifier input. Be sure the remote speaker is placed so it does not cause acoustic feedback. Connect a 500-ma meter across the fuse holder with no fuse installed. The amplifier is now ready for bias adjustments of the various stages.

R1—200 ohms, 5%
R2—2,000 ohms 5%
R3—pot, 5,000 ohms, audio taper
R4—1,500 ohms
R5—5,100 ohms, 5%
R6—150,000 ohms
R7—1,500 ohms
R8—120 ohms
R9—6.2 ohms, 1 watt

All resistors $\frac{1}{2}$ -watt 10% unless noted
*Values shown for these resistors are the ones used by the author. However, the proper values for your unit must be determined experimentally. See text for details

C1—.015 μF, disc ceramic
C2, 3—500 μF, 6 volts, electrolytics
C4—1 μF, metallized paper
C6—500 μF, 12 volts, electrolytic
C7—1,000 μF, 15 volts, electrolytic
F—0.5-amp fuse

RECT—selenium-bridge rectifier, 14 volts dc, 1 amp (Barry Electronics Corp., 512 Broadway, New York 12, N.Y.)

S1—spst
S2—dpdt, spring-return wafer type (Cent-alab 1464 or equivalent)

T1—interstage transformer: primary, 20,000 ohms; secondary, 1,000 ohms (Argonne AR-104 or equivalent)

T2—output transformer for 50L6 or 50C5. Primary impedance 7,000 ohms; secondary impedance 3.2 ohms

T3—output transformer: primary impedance 48 ohms, ct not used; secondary impedance 3.2/16 ohms (Thordarson TR-61 or equivalent)

T4—heater transformer: primary, 117 volts; secondary, 6.3 volts, 1 amp (Thordarson 2JF08 or equivalent)

Speakers, 3.2-ohm; 3-, 4- or 5-inch

Fuse holder

Pilot-lamp assembly and No. 47 bulb

Chassis, $6\frac{1}{2} \times 4$ inches

Cabinet, $6\frac{1}{2} \times 5\frac{1}{2} \times 4$ inches

Transformer box, $4 \times 2\frac{1}{8} \times 1\frac{1}{8}$ inches

Male plug


Miscellaneous hardware

Connect a 5,000-ohm potentiometer in the circuit for R7 and make certain that the full potentiometer resistance is in the circuit before the power is turned on. Adjust the potentiometer for a collector current of 250 ma. Allow the 2N255 power transistor to reach full operating temperature by letting it run for about 20 minutes, meanwhile readjusting the potentiometer to keep the collector current at 250 ma. When the output stage has stabilized, as evidenced by no further change in collector current, check the potentiometer's resistance on an ohmmeter and install the nearest standard-value resistor permanently. Now check the collector current with the resistor installed and, if all is well, you can disconnect the milliammeter and put the 0.5-amp fuse in its holder.

Follow the same procedure to determine the proper bias resistor for the driver stage, starting with approximately 300,000 ohms for R6. Adjust the 2N107's collector current to 1 ma and again allow sufficient time for the stage to stabilize with respect to collector current.

If collector current cannot be limited to 1 ma, the 2N107 transistor should be replaced with another. Some experimental transistors, such as the 2N107, have a tendency to draw excessive current even with zero bias when operated near maximum ratings of 5 volts or so, due to the lack of uniformity in these low-priced units. Such transistors will still perform satisfactorily in low-level low-voltage applications.

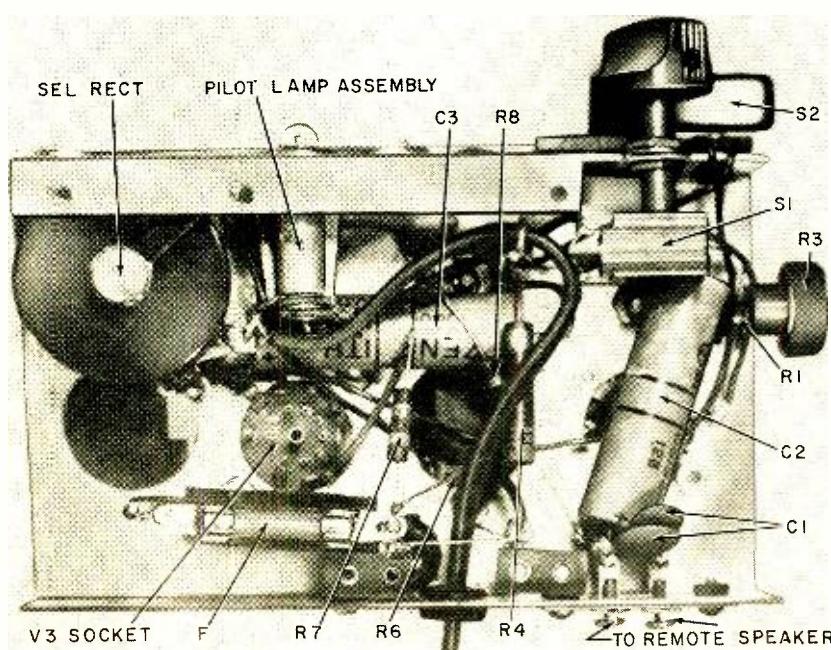When adjusting the bias of the common-base amplifier stage, use a 5,000-ohm potentiometer to determine the value of R2. You will find that the base voltage adjustment for a given trans-



Parts layout under the chassis.

sistor is fairly critical. Low emitter-base voltage will result in low collector current and noise with low amplification.

As the emitter-base voltage is increased, the thermal noise heard in the speaker is gradually reduced and amplification increases noticeably. If the bias adjustment is carried too far, the useful amplification will drop and the amplifier will cease to function. The proper adjustment for maximum gain is just below that point. I find that the easiest way to make this bias adjustment is to place the remote test speaker in a quiet location and use the ticking of an alarm clock as the signal source.

After adjusting the bias on the various stages and checking the amplifier for stability, wire in the PUSH-TO-TALK switch. If the amplifier tends to oscillate on talk-back, reroute the output transformer lead to minimize feedback. Careful routing of the output transformer's output lead is very important.

The routing of this lead is particularly critical where it connects to the push-to-talk switch, since it is close to the amplifier input at this point. The best procedure is to shield the lead and move it around until there is no feedback on talk-back with gain nearly wide open. During this test be sure that the remote speaker is far enough from the master unit so you will not be fooled by a case of acoustic feedback.

Most of the time electrical feedback cannot be completely eliminated with the gain wide open on talk-back.

Final steps

It will probably be necessary to treat the cone of the intercom speaker. If the speaker size is less than 5 inches, it tends to produce distortion when used as a microphone because of the thinner cone material used in such a small unit. If distortion is experienced on talk-back, give the speaker cone two coats of shellac to increase the diaphragm stiffness. Shellac the flat conical section only and leave the ribbed outer section near the frame untouched. This will give you a relatively stiff diaphragm with a flexible suspension. This way, performance as a microphone is greatly improved without impairing its performance as a loudspeaker.

No station-selector switching system was built into the unit because this feature was not desired. However, a regular station-switching system may be added if you want more than one remote station.

If excessive thermal hiss develops after the intercom has been in service for a while, it is an indication that the first stage has changed characteristics due to transistor aging. This may be corrected by determining a new value for bias resistor R2. Low-noise transistors are now available, so if you feel that the residual amplifier noise is objectionable, after bias adjustment, try a 2N106 or 2N189 in place of the 2N107.

END

a PA DUMMY LOAD

Lets you test your amplifier without raising the roof

By RICHARD H. HOUSTON

IN PA work, particularly on jobs other than the run-of-the-mill type, a dummy load is helpful. The amplifier builder finds a dummy load handy for testing purposes. An actual setup we used recently is an example. The job called for recorded music and live program material to be "broadcast" from the park in which the community Christmas tree had been set up. Since the programs were to continue during the entire Christmas season, I decided to establish a temporary studio in my home. The park was several hundred feet from the studio, making a volume indicator and aural monitor necessary. The wide variety of live program material presented the problem of auditioning each "act" in advance to determine correct microphone placement, gain settings, etc. A dummy load resistor to replace the speaker line solved the problem since the volume indicator, monitor, PA amplifier and other equipment operated just as though the speakers were connected.

When a dummy load is needed, the PA operator can connect an appropriate resistor across the amplifier's output, but this necessitates a certain amount of haywire and does not lend itself to rapid switching from load to speakers as is sometimes necessary. A far smoother program and a better impression on the customer will result if a neat, easily installed, quickly operated dummy load box is used.

Such a load box, capable of absorbing 40 watts of audio power, is shown in the photos and Fig. 1. Switch S2 connects either the speakers or the dummy load to the amplifier output. Switch S1 selects the load impedance to match the amplifier and speakers. Connections to the amplifier and speakers are made through sockets on the rear of the cabinet or a terminal strip mounted above the sockets.

Building the load box

Construction of the load box is simple. The entire unit is contained in a 6 x 6 x 6-inch steel box with removable panels

at the top and bottom. Input J1 has a separate terminal for each common PA output impedance. Each of these terminals is connected to a corresponding terminal on S1-a. When S2 is in the SPKR position, the rotor of S1-a is connected to the rotor of S1-c. When S2 is thrown to the LOAD position, the rotor of S1-a connects to the rotor of S1-b, which selects a dummy load resistor to match the amplifier impedance.

The impedances available are 2, 4, 8, 15, 200 and 500 ohms. Other values may be used if these do not match the speakers or amplifiers you use. The load resistances are made up of combinations of individual resistors in series and parallel. If single resistors of the desired resistance and power rating could be obtained the construction would be simplified, but some values are very difficult to find. However, it is not difficult to make up any required value from standard units. A more refined unit built with noninductive resistors would enable the experimenter to make precise measurements of output, distortion and other factors. For most PA purposes, ordinary wirewound resistors are adequate.

I made up the load resistances from my junkbox (Fig. 2). Four 500-ohm 10-watt resistors in series-parallel form the 500-ohm load. Two 400-ohm 20-watt units in parallel make up the 200-ohm load. The 15-ohm load is made from four 15-ohm 10-watt resistors in series-parallel.

The 8-ohm load is a combination of five 10-watt resistors in parallel (obviously a junkbox combination). I used 33-, 39-, 40-, 44- and 50-ohm resistors. Their actual resistance is 8.1 ohms, but this difference is negligible. The 4-ohm load is four 1-ohm 20-watt resistors in series with a tap to form the 2-ohm load. Each combination of resistors is secured to the rear wall of the cabinet by a threaded rod passed through the hollow core of two of the resistors.


It is a fairly simple matter to make up the required combinations of resistors from a well-stocked junkbox or from manufacturer's stock. The resist-

AUDIO—HIGH FIDELITY


(Right) The PA load box has only two controls.



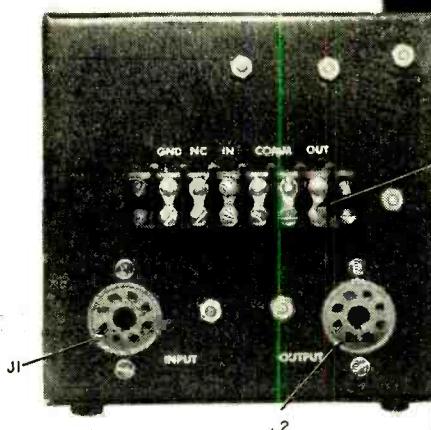(Below) Input and output connections are on rear of cabinet.



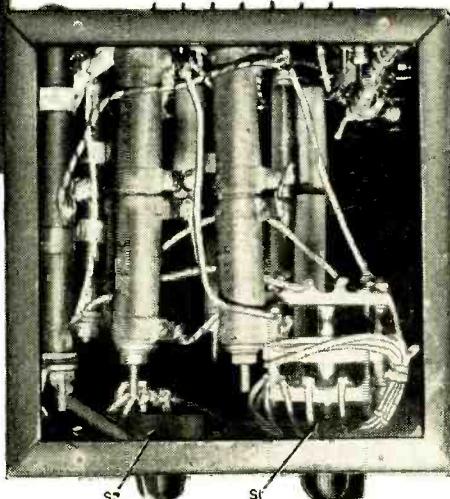(Below) Load resistors are fastened to rear of case.



R1—500 ohms
R2—200 ohms
R3—15 ohms
R4—8 ohms
R5, 6—2 ohms

All resistors 40 watts or more, wirewound. See text

J1, 2—octal sockets
S1—3-pole 6-position rotary
S2—spdt rotary

Terminal strip, 5 or more contacts (1)
Cabinet, 6 x 6 x 6 inches

Knobs
Miscellaneous hardware

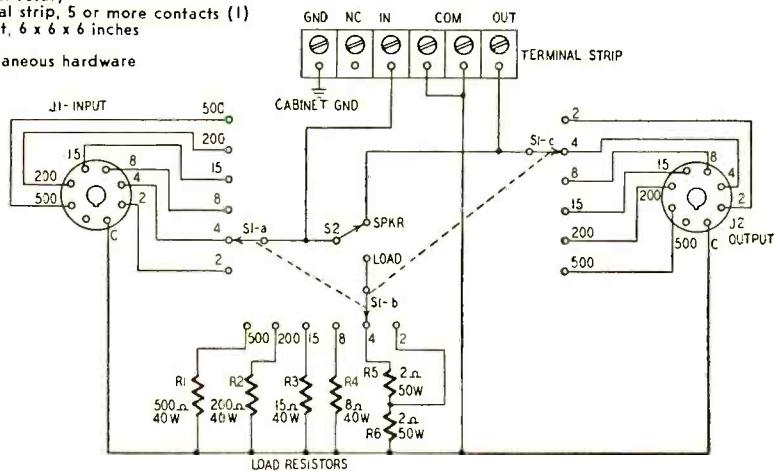


Fig. 1—Circuit of the PA dummy load.

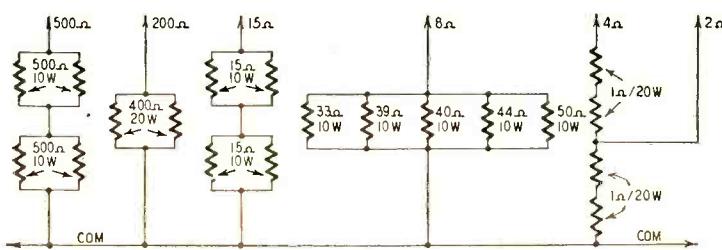


Fig. 2—Author used this method to obtain proper load impedances.

ance of a combination is calculated with the usual parallel- and series-resistor formulas. Keep a sharp eye on the wattage ratings to see that the total rating of the combination will equal or exceed the desired rating, which was 40 watts for this equipment. If identical resistors are used in series, in parallel or in a symmetrical series-parallel arrangement (as in the 500- and 15-ohm loads), the total wattage is the sum of the individual wattages. If dissimilar resistances are connected in any way or identical resistors are connected in a nonsymmetrical circuit (one resistor in series with a parallel combination of two others), the total wattage is a bit more difficult to calculate.

Wattage calculations

The easiest way to calculate the wattage of a circuit is to figure on the basis of the voltage across a parallel circuit or the current through a series circuit. For example, the 10-watt resistors used for the 8-ohm load are all in parallel, and the total power is easily calculated on a voltage basis. Since power is equal to E^2/R and the same voltage must of course appear across all resistors in a parallel combination, the lowest resistance unit will dissipate more power than any of the rest. In our case, the voltage is limited to that which will cause the 33-ohm resistor to dissipate its full 10 watts. This 10 watts equals $E^2/33$, so E , the maximum permissible voltage, is 18.2. This voltage across the entire combination, whose combined resistance is 8.1 ohms, corresponds to a total power rating of $(18.2)^2/8.1$, or 40.7 watts.

(Compare catalogs of various resistor manufacturers. Available resistances and wattages vary in different lines. It is possible to obtain all resistors except R4 in single units of either 40 or 50 watts, depending on the brand. R4 can be a series combination of 3 and 5 ohms or 4 and 4 ohms, each at 25 watts, or a parallel network of two 15-ohm 20-watt units. The selection depends on the brand or brands handled by your dealer.—Editor)

The input and output jacks are ordinary octal sockets since these connectors are standard in my equipment. Other types of connectors can be substituted to match any system. In any unusual or experimental situation where standard plug connections are inadequate, lines connected to the terminal board may be switched in exactly the same way as cables connected through the plugs. The SPKR-LOAD switch is a rotary switch, since switching may be necessary when silence must be maintained.

Probably few PA men have provided dummy loads for their work, but for the unusual job the convenience is well worth the effort of construction. Within a short time a flexible, easily used dummy load box will become an indispensable part of PA gear. END

TAKE YOUR PICK:

Some like changers, others prefer turntables—an outstanding one in each category is described here: the Glaser-Steers GS-77 changer and the Weathers ML-1 turntable

By HERMAN BURSTEIN



WHILE a transcription turntable is preferred for the utmost in high fidelity, the better record changers manage to keep only a step behind in performance. This step is so short that for many audiophiles the difference between a turntable and record changer is insignificant. Considering the numerous operating conveniences that changers offer and their generally lower price compared with a transcription turntable plus tone arm, it is easy to understand why changers are popular in high-fidelity systems.

Glaser-Steers GS-77

The Glaser-Steers GS-77 record changer is a newcomer that incorporates several novel and important features together with those that have become standard for changers in general. Despite its many features, the mechanism is relatively simple, as changers go, which is important from the viewpoints of reliability and ease of servicing.

The most striking innovation is the automatic speed change made possible when the speed-selector knob is in the Speed Minder position. Then 10- and 12-inch 33 1/3-rpm records can be intermixed with 45-rpm records, and the machine will change automatically from one speed to the other as necessary. The index finger (see photos) contacts each record to gauge its size and adjust the starting point of the pickup arm accordingly. The finger cannot contact a 7-inch 45-rpm disc. This actuates the speed-change mechanism. The automatic speed-change and intermix feature does not extend to the 16-rpm speed. The speed knob must be turned to the 16-rpm position.

Although 33 1/3- and 78-rpm records cannot be intermixed with an automatic speed change, the GS-77 in Speed Minder position shifts automatically to 78 rpm when a modified G-E VR-II cartridge, optionally available with the changer, has its 78-rpm stylus brought into position. A small arm on the cartridge strikes a lever on the rest post and causes the shift to 78 rpm. Piezoelectric cartridges frequently use a flipover arm for changing

from microgroove to standard stylus, and in some cases this arm can serve the same purpose as the special arm on the G-E. Glaser-Steers reports that a number of manufacturers of cartridges with dual styli are modifying them to incorporate such an arm. For cartridges without a flipover arm or with a specially attached one, the GS-77 comes with a clip which is mounted on the pickup arm to actuate the 78-rpm lever on the rest post.

The automatic change to 78 rpm, accomplished by changing from microgroove to standard stylus on a turnover cartridge, is not merely a convenience but also a matter of record safety. Many users of turnover cartridges have had the sad experience of accidentally playing a microgroove record with a 3-mil stylus and damaging the grooves. The automatic change to 78 rpm when the 3-mil stylus is brought into position provides an immediate alarm—Donald Duck sound—if a 33 1/3-rpm disc is played.

The change cycle is very brief, about 5 seconds, and remains the same at all four speeds as the change mechanism is independently driven by the motor rather than the turntable. During the cycle the turntable is stopped—by a brake against the inner rim—to prevent possible record abrasion as one disc drops onto another and so that the stylus will not cut across a moving groove as the arm comes down. Turntable motion resumes only after the stylus is in the lead-in groove, and full speed is reached in a fraction of a revolution.

For correct operation, three adjustments are readily accessible to the user at the pickup arm. One, to vary stylus tracking force; another to index the pickup arm so it will start at the proper point on the record, and the third to adjust the height at which the stylus stops above the turntable.

The tracking force remains within 1 gram from bottom to top of a stack of records. This is done by mounting the counter-tension spring of the arm as nearly horizontal as possible, so its length changes very little as the pickup arm moves up and down.

Resonance of the tone arm, always

a problem and more so in changers, is kept below 20 cycles by using an aluminum casting with reinforced ribbing, having no parallel surfaces and isolated from the deck by a rubber bushing.

The GS-77 can be operated manually if desired, and by placing the balance arm over the spindle the changer will shut off automatically when the record is over. The tripping mechanism that actuates the change cycle does not operate until the pickup arm reaches the last few grooves, so premature tripping due to cuing or groove irregularities is much less likely to occur. If the pickup arm is moved during a change cycle, the mechanism will not be damaged—frequently a bugaboo in record changers. The idler wheel, which drives the turntable rim, is automatically disengaged from both the motor pulley and turntable rim when the changer shuts off, preventing wow due to deformation of the rubber on the idler. Sound output is muted during the change cycle and when the tone arm is on the rest post. An R-C filter across the motor switch prevents a disturbing pop in the speaker when the changer shuts off.

In addition to quality of design, parts and assembly, performance of a product depends vitally upon adequate testing. After alignment and inspection for correct operation, every changer is checked for conformance with the following requirements: flutter (above 20 cycles) no more than 0.1% rms; wow (below 20 cycles) no more than 0.25% rms; rumble equivalent to at least 40 db below a 500-cycle signal recorded at 7 cm/sec peak (NARTB specifies rumble to be 35 db down); speed accurate within 2%. The inspected units are placed in racks of eight, and three of these eight are checked over again. If one of these three fails to meet standards, all eight undergo a complete check.

Weathers ML-1 turntable

The Weathers ML-1 turntable follows a design philosophy quite contrary to other professional units, yet comes up with truly professional specifications—wow 0.1%, flutter .01%, rumble 70 db below a recorded level of 7 cm/

AUDIO—HIGH FIDELITY

sec, and speed accurate within 0.25%.

The basic problems of a turntable are rumble, flutter and wow, which originate in motor vibration. Mr. Charles J. Gillies, a Weathers engineer, points out in a letter he wrote me that the vibration causes the rumble, while flutter and wow are due to shock-mounting of the motor and to the speed-reducing idler wheel used in many turntables.

In his words, the Weathers design philosophy is: "Why not use a very small precise motor which is practically free of vibration? This is exactly what we have done. The motor is a 12-pole synchronous type which rotates at only 600 rpm. It is so free of vibration that we can mount it solidly on the motor board. . . . The turntable can be driven directly from the shaft of the motor by a small rubber wheel of special shape which is made of very live pure gum rubber.* The bearing system is extremely free, and the platter itself is very light. Since the motor is very free of vibration, it is not necessary to use excessive weight to damp out the rumble."

Synchronous motors are known to have a tendency to hunt about their nominal speed and, partly for this reason, heavy turntables are used to provide a steady flywheel action. How does the Weathers unit get around the hunting problem despite use of a table weighing less than a pound?


Mr. Gillies replies: "Many manufacturers defeat some of the truly fine features of a synchronous motor by making it much too big. When the armature is heavy, it takes considerable power to turn it at this speed and there always is a tendency to hunt around the correct speed, due to the moving part of the motor. Our tiny motor has so little mass that this effect is mitigated. Also . . . you still get flywheel action from our turntable since its mass in relationship to motor mass is large. . . . The Weathers turntable will come from a dead stop to synchronous speed in three-quarters of a revolution and will not go beyond this synchronous speed. Thus, the hunting of the entire turntable as well as the hunting of the motor have been eliminated."

It is interesting to note that the ML-1 comes complete with base, and that resonance of the suspension system between turntable and base is kept low enough to minimize the effects of floor vibration, often a serious problem when the cartridge is operated with very low tracking force. The turntable pad is designed to suspend the record only at the outer rim, and a plastic disc around the center post supports the center, thereby preventing contact with the playing surface and resulting abrasion, pickup of dirt, etc. Although the ML-1 operates only at 33 1/3 rpm, an electronic control is optionally available to drive it at the other speeds in common use. END

* To isolate such little vibration as does exist.




The Glaser - Steers GS-77 ready to use.

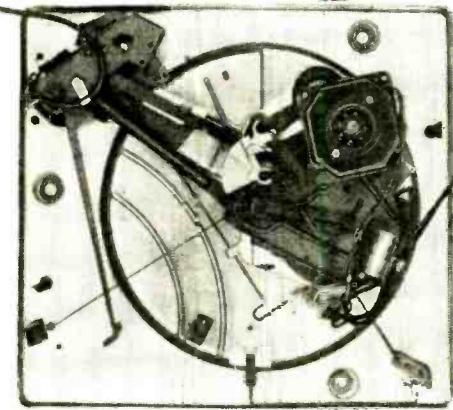

A bottom view shows the comparative mechanical simplicity of the GS-77 changer.



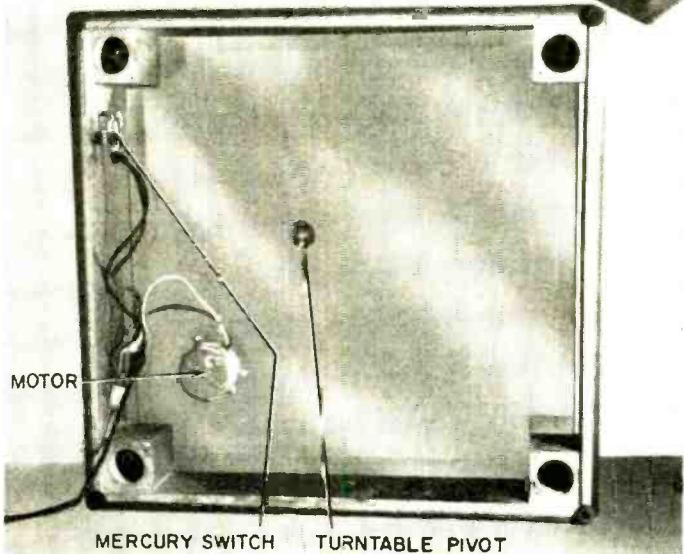The Weathers ML-1 turntable. The firm's FM capacitance pickup is shown.



The diminutive motor mounted under the motor-board presents an unusual appearance to the audiophile and represents a new approach to professional-type turntables.

more jobs for

SEMI CONDUCTORS

By PAUL PENFIELD, JR.

LAST month we saw how semiconductors could be used as voltage-variable capacitors and electronic switches or to measure magnetic fields. Now we will go on to photodiodes, phototransistors, photocells, thermistors and thermocouples.

Photosensitive devices

Many kinds of photosensitive semiconductor devices are possible. There are photoresistors, photodiodes, photovoltaic cells, phototransistors, PME photocells and lateral photocells.

The effect of light on a semiconductor is easy to understand. As you may know, light comes in small packets or photons. Each photon that hits a semiconductor makes an electron jump across the forbidden band—that is, it simultaneously creates an electron and a hole. Practical photocells use these electrons and holes.

Photoresistors are merely pieces of semiconductor, with two leads attached as in Fig. 5. A voltage is applied across the sample but only a small amount of current flows, since the number of holes and electrons available for conduction is small in a semiconductor. As soon as the photoresistor is exposed to light more electrons and holes are available and much more current flows.

Practical photoresistors can be extremely small. The recent cadmium sulfide and lead sulfide photocells are actually photoresistors. Germanium and silicon can also be used.

Another device is the photodiode. This is nothing more or less than an ordinary diode—either point-contact or junction. In operation it is reverse-biased, so very little current flows. But when the junction is illuminated, hole-electron pairs are formed. These pairs flow, forming current. Very high efficiencies are possible, and the photodiode is a widely used device.

You can get the same effect using ordinary diodes, but with less efficiency. Try it yourself on one of the diodes that come in a glass case. The circuit of Fig. 6 demonstrates this principle. Be careful about battery and diode

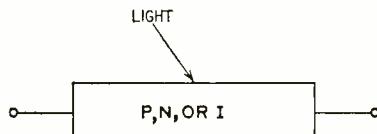


Fig. 5—Photoresistor made of p, n or intrinsic material.

Part II—They measure heat and light . . . make heat and light batteries . . . air-condition and refrigerate without moving parts

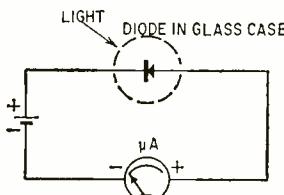


Fig. 6—Circuit for checking effect of light on diode. Use either point-contact or junction diode.

polarity, so that the diode is really reverse-biased. With a 100-watt bulb as a light source and using a 1N34-A you should get 20-30 μ A, easily read with a vomm.

A phototransistor is similar to a photodiode, except that it is physically identical to a transistor instead of a diode. Either p-n-p or n-p-n phototransistors are possible. In operation the base lead is not used, but the normal collector-to-emitter bias is applied. The current will be the normal cutoff current until light is applied to the collector junction. Then current rises sharply to a value about β times the equivalent photodiode current. Transistor action accounts for this amplification of the hole-electron pairs formed. The phototransistor can be considered a photodiode with a built-in amplifier.

Photovoltaic cells

A photovoltaic cell does not require a bias. Its physical structure is the same as the photodiode, and it can be used either way—as a photodiode or as a photovoltaic cell.

Strange as it may seem, if you shine light on an ordinary diode, you will develop a voltage across it. If the circuit is closed, current caused by the light will flow. For absolute proof of this effect you can try it yourself. Use any diode—point-contact or junction—that has a glass case. On bright illumination the output will be readable on a vomm. The same setup as Fig. 6 can be used, without the battery.

The so-called barrier-layer photocell is nothing but a photovoltaic cell. Again, the practical devices were in use long before the theory was well developed but, along with the theory, came improved techniques for making the devices, improved efficiencies, better materials, etc. The physical shape of present-day photovoltaic cells and the materials used differ from the early

models, but the fundamental process is the same.

Photovoltaic cells are used in photographic exposure meters and in many control applications. Practically any semiconductor can be used—typical cells use copper oxide, selenium, germanium, silicon, etc.

Because they require no bias, photovoltaic cells are useful for converting energy—they can be used as a battery. Shine light on the device, and the energy of the light is converted into electricity. The solar battery developed at Bell Telephone Laboratories is a photovoltaic cell designed specifically for energy conversion. Another similar device is one of the recently announced nuclear batteries. Instead of trying to convert nuclear energy directly into electrical energy, the inventors let the nuclear radiation hit a fluorescent material so it would glow, like a "radium" wristwatch dial. This light was used to power a photovoltaic cell.

Another type of photocell which is useful for converting energy, since it requires no bias, is the PME photocell, or the PhotoMagnetoElectric cell. This was developed simultaneously by two groups, one in England and the other in France, a few years ago. The principle is very simple.

Fig. 7 shows the device. It is similar to the Hall-effect devices (described last month) except that, instead of the current from left to right, the electrons and holes are supplied by light. Electrons and holes are formed right at the surface and they tend, because of their large numbers, to move away from the surface. As they diffuse back into the material, they get caught by the magnetic field and the holes are pushed up and the electrons down. Then a voltage appears across the two terminals—the PME voltage. Thus, the PME cell takes advantage of the Hall effect operating

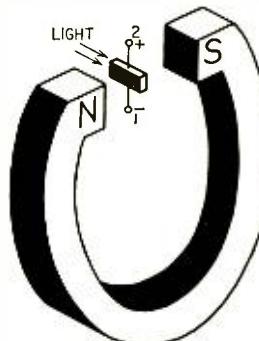


Fig. 7—PME photocell uses Hall effect acting on light-induced electrons and holes.

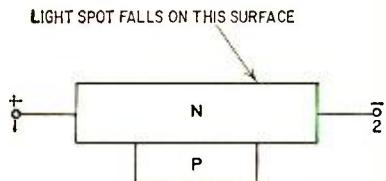


Fig. 8—The Wallmark lateral-effect photocell.

on the electrons and holes formed by the light.

The PME effect is used to measure certain properties of the semiconductor and is in less use as a practical photocell. It has certain advantages, however, and in the future will be used more, both as an indicating device and as a battery.

Just one more type of photocell, now—the Wallmark lateral-effect photocell. The theory here is a bit more complicated, but the device has some unique properties. As Fig. 8 shows, it consists of a p-n junction with two contacts to the n-material. If one of these contacts and a contact to the p-region were used, we would have an ordinary photodiode or photovoltaic cell. However, we prefer to use the two contacts to the n-region. The p-n junction then becomes a floating junction since no net current passes through it.

If the device is lighted with a small spot right at the center, nothing will happen except that a photovoltaic voltage will be generated. The two terminals (1 and 2) will be at the same voltage. However, if the spot is moved to one side or the other, the action of the floating junction is to cause a voltage between terminals 1 and 2. This lateral-effect photocell, developed by RCA, tells us the position of the spot of light—something none of the other photocells would do. Useful in many control applications, this photocell, not yet commercially available, will find many specialized applications.

Heat-operated devices

There are many ways to use the unique temperature properties of semiconductors. Thermistors or diodes can be used for reading temperature. For heating or cooling objects, we can use a Peltier refrigerator. We can use a thermocouple as a battery. All this is possible with semiconductors because the effects are more noticeable than with metals.

A thermistor is merely a piece of semiconductor with two leads on it. It is useful because its resistance depends on the temperature—the higher the temperature, the lower the resistance, *contrary to the way metals act*.

A thermistor can be used to "read" temperature, the same way a photoresistor is used to "read" light intensity. The action of these two devices is quite similar.

Thermistors are made in many sizes and shapes for all types of control purposes. They are useful, for example, in controlling the bias of a power trans-

sistor stage, to prevent the transistor's burning up at higher temperatures.

A diode also can be used as a thermometer. Diode reverse current is a very sensitive indication of the temperature. In this respect it is similar to a photodiode whose reverse current is a very sensitive indication of the light level.

Thermocouples have been known for some time. The basic circuit is in Fig. 9, showing two kinds of conductors (here copper and iron) connected together to form two junctions—one at the end on the left, and the other at the voltmeter. If the junctions are not at the same temperature, there will be a voltage generated by the thermoelectric or Seebeck effect. This effect has been used for many years to measure temperatures, since the voltage output depends only on the temperatures of the two junctions and on the type of material used.

For measuring purposes, the materials are usually metals and the output voltages run a few millivolts. The possible power output is so small that it would not be practical to use such a system as a battery. However, using semiconductors, the output voltages are hundreds of times larger, and it is quite practical to build semiconductor heat batteries which are really nothing more or less than simple thermocouples. Many such thermocouples can be connected in series or parallel to provide whatever current or voltage is needed.

More work is required to make such thermocouple batteries cheap enough to be practical. However, for the power-starved areas of the world, even expensive batteries are better than none, especially since these thermocouples require no maintenance and no charging. This type of battery, using semiconductors, has been developed in Russia and China to run small transistor radios. The higher temperatures are produced by a kerosene lamp. The thermocouples are mounted on the lamp's chimney to use the heat that would otherwise escape. It is only a matter of time before this type of battery can be made cheap enough to be useful throughout the world.

One more important device using semiconductors and heat is the Peltier refrigerator. The Peltier effect is the direct opposite of the Seebeck effect—instead of getting a voltage generated by a difference in temperature, now we get a difference in temperature caused by a current passing through a junction. The same device that works as a thermoelectric battery will also work as a refrigerator, although not too efficiently.

It is somewhat baffling to understand how passing a current through a junction will cool it, especially when all our experience tells us material heats when current is passed. The two processes, however, are different. With metals, ordinary I^2R heating is much more important. Even with semiconductors, special pains have to be taken to detect

the slight cooling that is possible. However, under the right conditions, with enough junctions and the right material, with the current set at just the right level, appreciable cooling is possible. Within a few years you can expect to see electric Peltier refrigerators, home freezers and air conditioners. The advantage is that there is no electric motor, no fluid or piping, nothing to wear out, and no maintenance required.

Other semiconductor devices

One other application for semiconductors should be mentioned because it is surprising that semiconductors should be used at all. We normally think of the transistor and the vacuum tube as competitors in some sense. Yet vacuum tubes use semiconductors in their construction.

Most modern vacuum tubes use an oxide-coated cathode, so the heater can be run at a lower temperature. The oxide used is a semiconductor—and the lower temperature comes from the un-

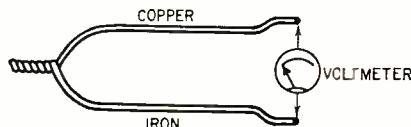


Fig. 9—A basic thermocouple. Its output can be used to indicate temperature or run transistor equipment.

usual properties of semiconductors. Here, they allow the electrons to escape more easily.

Among the devices used to detect *nuclear radiation* is the crystal counter whose resistance changes sharply when it is hit by a particle from a radioactive material. The action of this type of counter is similar to the action of a photoresistor when a light photon hits it—electron-hole pairs are formed. The material used is a semiconductor, and the electrons and holes formed after each hit are removed quickly. The pulses of current can then be counted, giving us a practical radiation detector.

If this last device is similar to a photoresistor, picture a device that is similar to a photovoltaic cell but uses nuclear radiation to form the electron-hole pairs, instead of light. This device can be used as a battery if a piece of radioactive material is placed near it. This then is a *direct* way to convert nuclear energy into electrical energy. In the future, special semiconductor materials will be used to give us nuclear batteries with very desirable properties.

Of all the devices described here, no one can predict which will become the most important. There is no doubt that the transistor has arrived. But remember it was only 10 years ago that the first crude transistor was made. Enough is now known about semiconductors to make many other devices possible, as outlined in this article. I wonder how many of these will become as common-place in the *next 10 years* as the transistor is now.

END

Simple electronic computer adds, subtracts, divides and multiplies



Analog Computer

By FORREST H. FRANTZ, SR.

INDUSTRY spends millions of dollars each year for computing instruments to free engineers, technicians and office workers from the labor of doing long computations by hand. Time that was spent doing this work is now used in more creative and productive pursuits.

Can this work for you as a service technician, ham, hi-fi enthusiast or experimenter? Yes, it can! With a modest calculator you can enjoy these benefits on a smaller scale. Mr. Math is just such an instrument. It will help you make accurate calculations for most electronic and electrical problems. Mr. Math opens the door to analog computing for you. You'll find math less laborious and more interesting. Your understanding and ability to use it advantageously will increase as you use Mr. Math.

What Mr. Math can do

What can you expect from Mr. Math in problem ability and accuracy?

Ability: Mr. Math can be used to work problems involving these commonly encountered formulas:

$$\begin{aligned} E &= IR, \quad I = E/R, \quad R = E/I, \\ P &= E^2/R, \quad P = I^2R, \quad e = E_m \sin \theta, \\ e &= E_m \cos \theta, \quad X_L = 2\pi fL, \\ X_C &= 1/(2\pi fC), \quad Z = \sqrt{R^2 + X^2}, \\ \tan \theta &= X/R, \quad \cos \theta = R/Z, \\ \sin \theta &= X/Z, \quad X = R \tan \theta, \\ X &= Z \sin \theta, \quad R = Z \cos \theta, \\ \text{Gain} &= E_{out}/E_{in}, \\ \text{Gain} &= \mu Z_L / (r_p + Z_L), \quad \mu = g_m r_p, \\ f_o &= 1/(2\pi \sqrt{LC}), \quad \text{and others.} \end{aligned}$$

Accuracy: 1% is usually considered adequate for engineering purposes. Mr. Math is accurate within 1% when carefully constructed, calibrated and used for most problems. With average construction, calibration and use, Mr. Math's error will be less than 3%.

Here's how Mr. Math is used:


Problem: You're fixing an old ac-dc radio that has a burned-out series-heater resistor. The total drop across the tubes must be 68 volts at 0.3 ampere. The line voltage is usually 120 in your locality. What should the resistance of the replacement be and how much power will it have to dissipate?

All you do to solve the problem is set four dials to obtain the resistance in ohms and readjust two of them to obtain the power in watts that the resistor will dissipate. Simple, isn't it?

Mr. Math's circuit is simple, but, before you become too involved with it, glance at Fig. 1-a. A battery of voltage E is connected to series resistors R_1 and R_2 . In a series circuit, the current through each resistance is the same and the sum of the voltage drops across the resistances is equal to the battery voltage. Therefore,

$V_2 = I R_2$. And, if R_1 plus R_2 equals 1,000 ohms and R_2 equals 200 ohms when E is 10 volts, V_2 will be 2 volts. Thus, V_2/E equals 0.2.

If resistances R_1 and R_2 of Fig. 1-a are replaced by a potentiometer as shown in Fig. 1-b, voltage V_2 may be varied by rotating the pot's shaft. R_1 plus R_2 is constant and is equal to the potentiometer's total resistance. R_2 is equal to the percentage of shaft rotation times total resistance. Total mechanical rotation possible with the potentiometers used in Mr. Math is 300° . But, the metal connector tabs on the ends of the resistance element take up 10° each. Therefore, the electrical rotation is only 280° . So a 28° rotation of the shaft corresponds to a 10% rotation, and V_2 will increase by 10% of E . If the potentiometer has a scale with ten 28° divisions, each marked from 0 to 10, and E is 10 volts, a

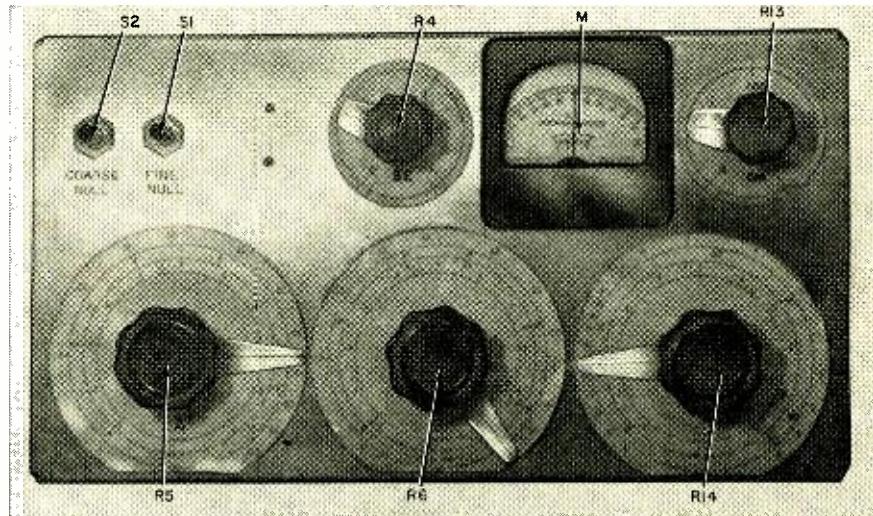

Mr. Math ready for use.

pointer knob on the potentiometer will indicate the magnitude of V_2 directly in volts. Thus we've generated the numbers between 0 and 10.

How can we multiply?

With a little thought, you will see that we already know one way to multiply. In Fig. 1-b we multiplied E by numbers between 0 and 1 and, when E equaled 10, generated the numbers between 0 and 10. This was done when the potentiometer input voltage was constant. If we add a second potentiometer with its outer terminals across V_2 as shown in Fig. 1-c, we can multiply V_2 by another number between 0 and 1. We can calibrate R_{TB} from 0 to 10 if we wish and increase E to 100 volts. Thus, with R_{TA} and R_{TB} set to 10, we have $10 \times 10 = 100$. However, there's no need to let the number 1 equal 1 volt. If we let it equal .01 volt, we can let E equal 1 volt and still graduate the potentiometers from 0 to 10. Thus, for 2×4 , V_3 equals .08 volt, or 8 units. A voltmeter with the proper

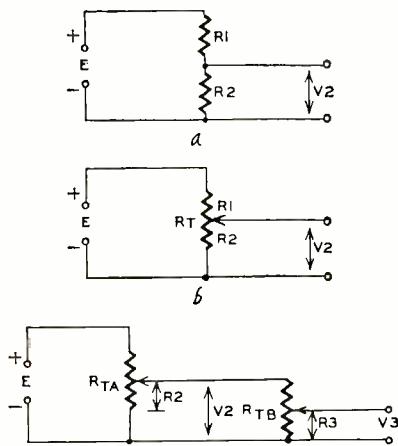


Fig. 1—Basic system of generating numbers and multiplying with cascaded potentiometers.

range could be calibrated to read directly in units from 0 to 10, and the meter range switch could be calibrated in multiples of 10.

To make the multiplication method of Fig. 1-c work properly, R_{TB} 's resistance should be at least 10 times R_{TA} if you want to use linear scales. Even then, there'll be some error (approaching 2% maximum) if you try to use linear scales. Furthermore, to multiply more than two-digit numbers with a string of cascaded pots, you run into the problems of using a large input voltage, a very low resistance for the first potentiometer to get a reasonably low resistance for the last pot and a very high-sensitivity meter for answer readout. Another disadvantage is that you cannot divide unless you provide a reciprocal scale (difficult to make and use) and multiply to divide. Thus, 3 divided by 7 would be 3 times 1/7.

But, there's another way to multiply and divide that is also handy for squaring and taking cube roots.

You can multiply by adding, and can

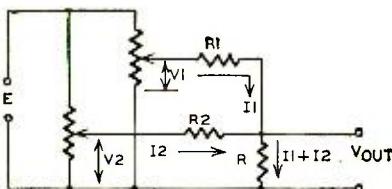


Fig. 2—Electronic adding with a mixing circuit.

divide by subtracting, logarithms. Recalling your high school math, let the letters A and B represent numbers. Then, the *log* of A times B is equal to the *log* of A plus the *log* of B . And the *log* of A divided by B equals *log A minus log B*. To use these principles in our analog calculator, we need only find a method for adding either voltages or currents.

Let's use a signal mixer

The circuit in Fig. 2 is familiar to most people in electronics. It's a simple signal mixer usually used to mix phono and mike inputs for a single-channel amplifier. The output voltage (V_{out}) is proportional to $V_1 + V_2$.

Now, to get back to multiplication and division. Granting that logarithms are to be used for multiplication and division, Mr. Math would have a limited value if we had to resort to log tables. To get around this, we provide the potentiometers with log scales for these tasks. With *log scales and linear scales* we can multiply, divide, add or subtract.

To simplify Mr. Math's design further, a simple bridge circuit is used. In this way, the need for a more expensive output meter is eliminated, and problem answers may be read from a 280° potentiometer scale instead of a 90° meter scale. Furthermore, division and subtraction may be done without reversing the voltages applied to the potentiometers. The multiplication scheme for Fig. 1-c is important though, and it is used in Mr. Math to square and to take square roots. The math principle involved is that *the log of A*

squared is equal to *two times the log of A*. Similarly, *the log of the square root of A* is one half the *log of A*.

Mr. Math's circuit


Now let's take a closer look at the circuit (Fig. 3) of this calculator we're going to build. The letters which identify the potentiometers correspond to the front-panel markings on the controls and dials. Pot A (R_5) furnishes a voltage output proportional to a dial-number setting as explained in conjunction with Fig. 1-b. Pot B (R_6) furnishes a voltage output proportional to a dial-number setting multiplied by the control pot BE (R_4) setting of $\frac{1}{2}$, 1 or 2. This circuit is similar to that of Fig. 1-c. The outputs of pots A and B add in the summing network consisting of R_7 , R_8 and R_9 . This is an application of the circuit of Fig. 2. The voltage representing this sum is introduced to one side of the meter. The sum of the output of pots C (R_{14}) and CM (R_{13}) connects to the other side of the null meter. This summation takes place in the summing network consisting of R_{10} , R_{11} and R_{12} . The output of pot C is proportional to the number set on the dial. The output of pot CM is proportional to 0, 1 or 2.

The numbers stated are for the linear scales on the dials (see Fig. 4). The calculator equation for meter null with these scales is:

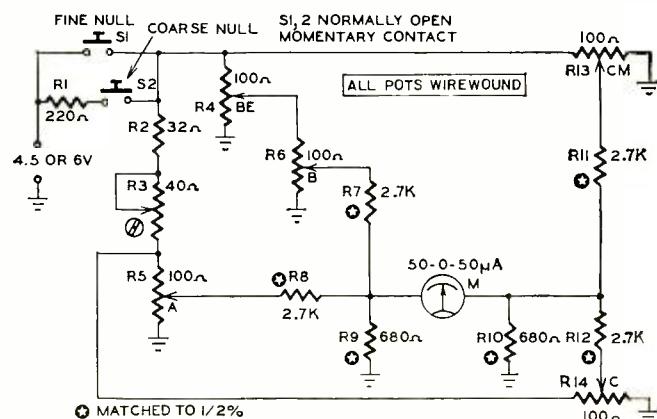(A) + (BM) (B) = (CM) + (C)
where BM = 0, $\frac{1}{2}$ or 2; CM = 0, 1 or 2 and A, B and C are continuously variable from 0 to 1.00 with dial scale divisions of .02.

This equation provides for adding and subtracting. But Mr. Math computes to only two significant figures. Since addition and subtraction can be performed rapidly with paper and pencil, principal calculator applications are in multiplication and division.

By assuming that the linear scales of pots A, B and C are the logarithms of numbers, new scales can be provided



R1—220 ohms
R2—32 ohms
R3—pot, 40 ohms, wirewound, screwdriver adjust (Mallory C40P or equivalent)
R4, 5, 6, 13, 14—pots, 100 ohms, wirewound (Claro-stat 58C1-100 or equivalent)
*R7, 8, 11, 12, 2,700 ohms, matched to $\frac{1}{2}$ %
*R9, 10—680 ohms, matched to $\frac{1}{2}$ %
All resistors $\frac{1}{2}$ -watt 10% unless noted

*Use 1% resistors if you do not have access to a Wheatstone bridge
M—50-0-50 μ A (Triplett 327-T or equivalent)
S1, 2—spst, normally open, momentary contact type (Cutler-Hammer 841I-K4 or equivalent)
Chassis, 2 x 13 x 7 inches
Knobs
Miscellaneous hardware

Fig. 3—Mr. Math's easy-to-build circuit.

ELECTRONICS


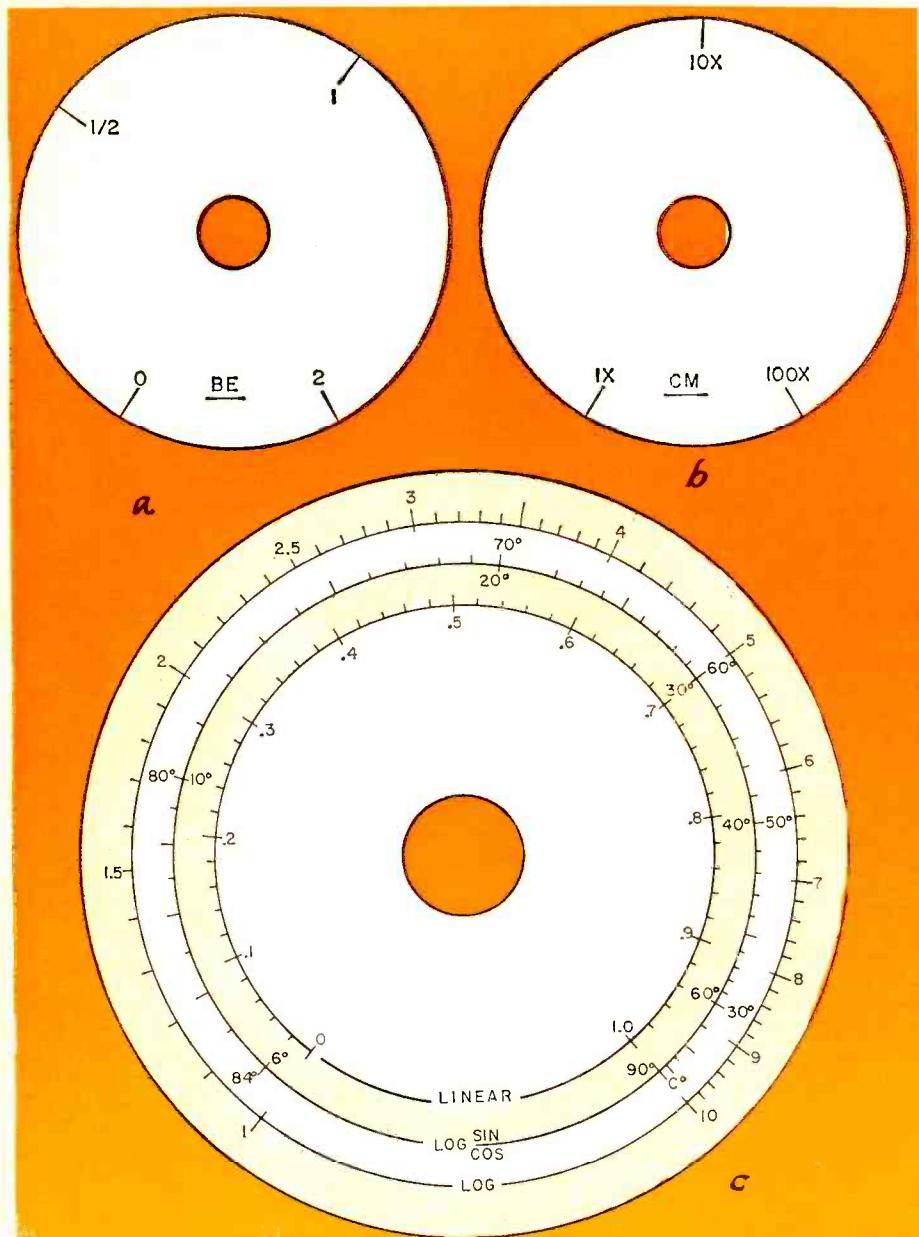


Fig. 4—Calibrated dials for Mr. Math: a and b—The end marks (0, 2, IX and 100X) are placed at the extremes of the mechanical rotation (300°). In use, these dial settings are not critical. The $\frac{1}{2}$, 1 (on BE) and the 10X (on CM) settings must be accurate. Do not ink in the $\frac{1}{2}$ mark on BE until calibration is completed.

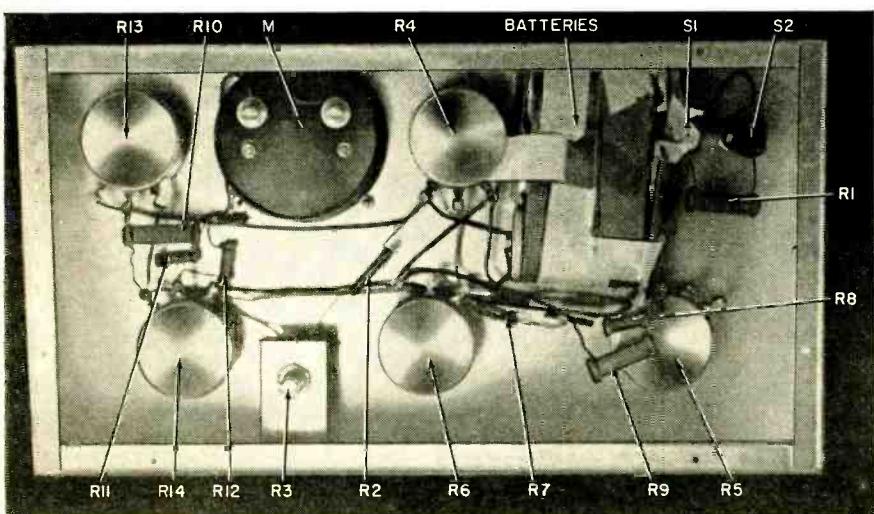c—Linear and log scales are marked off on all three main dials.



which are logarithmically related to the linear scale. Thus, with Mr. Math you can multiply, divide, square and take square roots. These are the most commonly required calculations in electronic work and they're the most time-consuming.

The calculator equation for Mr. Math using the log scales (outer scale in Fig. 4) is:

$$A \times B^{BE} = C \times CM$$

where $BE = \frac{1}{2}$ (for taking the square root of B),

$= 1$ (if B is not to be squared or its square root taken)

or $= 2$ (if B is to be squared)

$CM = 1, 10$ or 100 (to set the decimal point for the number on pot C)

A, B and C are continuously variable from 1 to 10. Trig scales and scales of numbers multiplied by commonly used constants (eg, 2π) may be laid out against the log scales to increase Mr. Math's memory.

The three large dial scales have a 4-inch diameter. These are prepared by first laying out a linear scale with a radius of $1\frac{1}{4}$ inches. The calibrated portion of the scale covers 280° and principal divisions are spaced 28° apart. The full-scale value is 10 and the 10 principal divisions are numbered from 0.1 to 1.0. After these are laid out, a $1\frac{3}{4}$ -inch radius circle is drawn for the logarithmic scale. The principal points for this scale were laid out using a log table or a slide rule. Remember that the inner linear scale corresponds to logarithms. There is enough space for an additional scale with a radius of $1\frac{1}{2}$ inches on each dial. My calculator has a log 2π scale in this space on the A pot dial, a log tangent-cotangent scale in this space on the B pot dial and a log sine-cosine scale in this space on the C pot. The explanation of these middle scales and their layout is difficult. Unless you've had a good bit of trigonometry, I suggest you wait to lay these out until you've become accustomed to Mr. Math's operation with the inner and outer scales. Mr. Math's scales are somewhat consistent with slide-rule scales. This allows you to use either without confusion if you know how to use a slide rule or learn how to use one in the future.

The calculator draws current from the battery only when the COARSE NULL or the FINE NULL button is depressed. The COARSE NULL switch is depressed first and an approximate null is established. Then the FINE NULL switch is depressed and fine null is established.

Calibrating Mr. Math

A series of adjustments of the pointer knobs and one semifixed pot is used to calibrate your calculator. The technique used is to set in several sample

Inside view shows location of parts. I taped the batteries to the case, but a battery holder could be used for a more secure mounting.

problems and adjust for the correct answer. You might call it an approximation method. Here's what to do:

1. Index knobs. Proper indexing is set when the hairline overrides the extreme clockwise and counterclockwise index marks by equal amounts.

2. Set controls so that (numbers given for A, B, and C are on linear scales)

$$A = 0, B = 0.5, C = 1.0,$$

$$BE = 2, CM = 1X$$

Adjust the 40-ohm screw-adjust pot under the panel (R8) for null with the fine-null switch depressed.

3. Set controls so that

$$A = 0, B = 0.5, C = 1,$$

$$BE = 2, CM = 10X$$

Check the null. If it is poor, adjust CM for null with the fine-null switch depressed. Loosen the knob setscrew on CM and move the knob until the hairline coincides with 10X again. Tighten the knob setscrew. Check to be sure that the null was not disturbed.

4. Set controls so that

$$A = 0, B = 1.0, BE = 1,$$

$$C = 1.0, CM = 1X$$

Depress the FINE NULL switch. If the null is not exact, turn BE for exact null, loosen the setscrew on BE and adjust the knob till the hairline coincides with 1. Tighten the knob setscrew. Check to be sure that the null was not disturbed.

5. Set controls so that

$$A = 0, B = 1.0, BE = \frac{1}{2},$$

$$C = 0.5, CM = 1X$$

Depress the FINE NULL switch. If null is not exact, adjust BE for exact null and place a new graduation line for $\frac{1}{2}$ on BE.

The dial indexing and calibration should be rechecked if error greater than 3% is noted on any calculation.

To use Mr. Math

The calculator is used as follows:

1. To add two numbers (3.5 + 4.5, for example) use linear scales.
 - a. set A at 0.35.
 - b. set B at 0.45.
 - c. set BE at 1.
 - d. set CM at 1X.
 - e. adjust C for meter null. read answer on C. C nulls at 0.80. (The answer is 0.80×10 . The multiple is used since the numbers were divided for entry.)

NOTE: If the sum of the numbers is greater than 10, set CM to 10X. The answer is 10 plus the number at which C nulls. Thus to add 7.2 and 8.7:

- a. set A at 0.72.
- b. set B at 0.87.
- c. set BE at 1.
- d. set CM at 10X.
- e. set C for meter null. read answer on C. C nulls at 0.59. [The answer is $10 \times (1 + 0.59)$ or 15.9.]

2. To subtract two numbers (8.3 - 4.1, for example) use linear scales.
 - a. set B to 0.41 (number to be subtracted).
 - b. set C to 0.83 (number to be decreased).
 - c. set BE to 1.
 - d. set CM to 1X.
 - e. adjust A for null. A nulls at 0.42

(The answer is 10×0.42 , or 4.2.)

3. To multiply two numbers (3.9×7.1) use log scales.
 - a. set A at 3.9.
 - b. set B at 7.1.
 - c. set BE at 1.
 - d. set CM at 1X.
 - e. attempt to adjust C for null. If null is not possible, set CM to 10X and adjust C for null. C nulls at 2.77. (The answer is 10×2.77 , or 27.7.)
4. To divide one number into another (26/3.1, for example) use log scales.
 - a. set C to 2.6.
 - b. set CM to 10X.
 - c. set BE at 1.
 - d. adjust A for null, and read answer on A. A nulls at 8.4. (This is the answer.)
5. To square a number (7.9, for example) use log scales.
 - a. set B at 7.9.
 - b. set BE at 2.
 - c. set A at 1 on log scale.
 - d. set CM at 1X and adjust C for null.
 - e. If no null can be obtained, set CM to 10X and adjust C for null.
 - f. C nulls at 6.22 with CM at 10X. (the answer is 6.22×10 , or 62.)
6. To take the square root of a number (8) use log scales.
 - a. set B at 8.
 - b. If number has odd number of places, set A at 1. If number has an even number of decimal places, set A at 0.16. Set A at 1.
 - c. set BE at $\frac{1}{2}$.
 - d. set CM at 1X.
 - e. adjust C for null. C nulls at 2.8. (This is the answer.)

Since the computer may have an error of 1 or 2%, answers should be read out to only two significant figures. Thus, 27.7 should be read as 28, 272 as 270.

Since the A, B and C log scales are scaled from 1 to 10, multipliers of 10, 100, etc. are used to represent numbers greater than 10. Thus to multiply 71×832 , the dial settings of A and B are the same as for 7.1×8.32 , and the result from CM and C is multiplied by 10, 100 or 1,000 to get the final answer.

The trigonometric scales (which I suggested you add later) are actually 10 times the respective functions which they represent. This requires the use of a scaling factor in the answer. Thus $5 \tan 45^\circ$ gives the result 50 on C and CM. This result must be divided by 10 to obtain the correct answer.

To get most accurate results from your construction work:

a. Match R7, R8, R11, and R12 within $\pm \frac{1}{2}\%$ with a Wheatstone bridge.

b. Match R9 and R10 within $\pm \frac{1}{2}\%$.

c. Use the potentiometers specified; others may not possess the linearity required.

d. Prepare dial scales accurately. Be sure knob pointers fit close to scale to prevent parallax errors.

e. Calibrate carefully according to the procedure outlined.

f. Set numbers into the calculator accurately when working problems.

Happy calculating!

END

NEXT MONTH

Horizontal Ringing Troubles

What to do when those vertical bars show up on the screen

Electronic Boat Horn

This useful device works as a low-power loud-hailer as well as a horn

Improving the Small Receiver


There are still more radios that TV's. Here are a few useful service hints

The JULY issue of Radio-Electronics

on sale June 24

Reserve your copy now

NEWS from the IRE 1958 meet

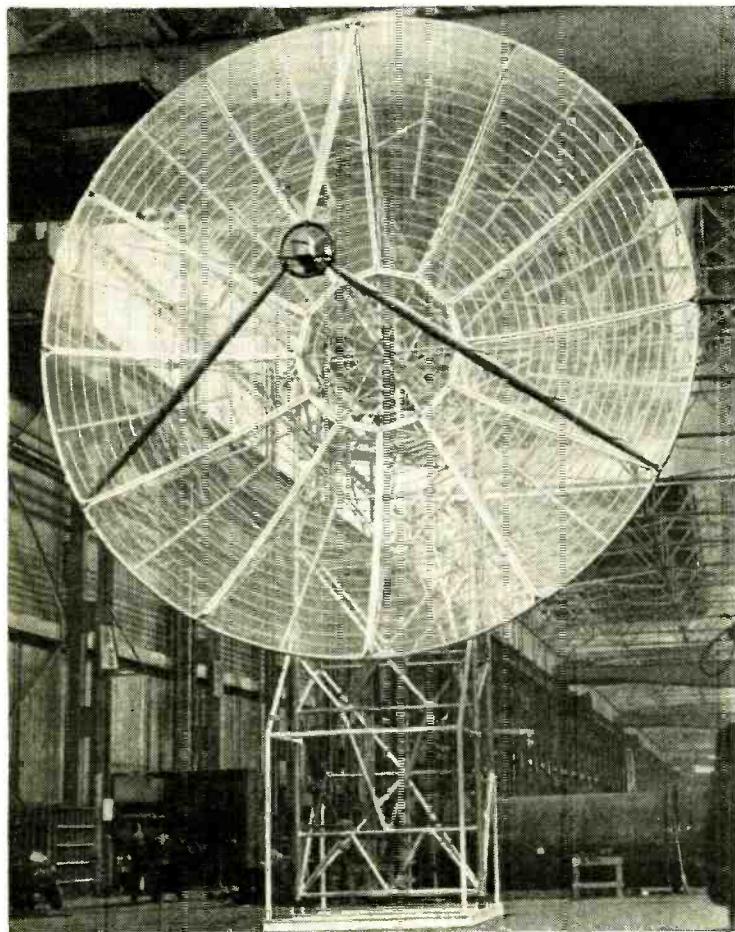


*55,000 electronic engineers
gather to discuss another year
of progress*

This mobile antenna stands
almost three stories high—
its radiation center is 24
feet above the ground.

By ERIC LESLIE

THE year's most striking example of how fast yesterday's wonders become commonplace was probably the 1958 convention of the Institute of Radio Engineers, held in New York City the third week of March. The engineers not many years ago had thrilled to the news that a radar message had been returned from the moon—now they talked calmly about shooting a manned rocket around it. Medical electronics was married to computer technology, and the old concept of gas tubes was expanded out of recognition. (Engineers talked of a plasma of electrons and ions at a temperature of 100 million degrees, carrying currents several times as great as could an equivalent bulk of copper, and held in an

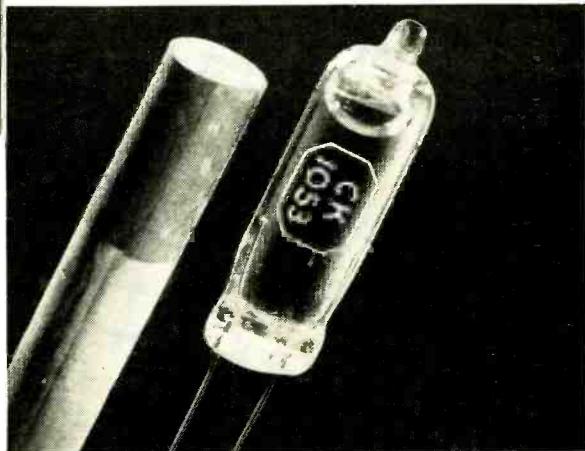The Raytheon operating-time indicator tube.



envelope consisting of a magnetic field that would constrict the plasma on itself.)

A complete session was in fact devoted to thermonuclear power. Another, a panel, was entitled Electronics in Space. A more mundane subject that would have been equally surprising to the old engineer was engineering education. Two sessions were devoted to

that subject, and another to a related one, engineering writing and speech. Devices that would read books and papers, then prepare engineering abstracts from them, were described, as well as an electronic Russian translator.

Another complete session was devoted to masers (microwave gas or semiconductor amplifiers) and atomic

clocks. One of these—a gas-cell clock described by Federal Telephone engineers—was visualized as “necessary equipment on any rocket ship.”

Luminescent panels for flat-tube television were discussed by Sylvania engineers, who pointed out avenues of research in that direction and reported on progress in producing moving pictures on such panels, but concluded that “major breakthroughs” would be needed before luminescent panels could be used as TV screens.

The field of sound

Audio was possibly the liveliest subject at the convention. One complete session was devoted to stereophonic disc recordings, and another to audio, amplifier and receiver developments. It was at that session that Dr. Peter Goldmark presented his surprise paper on the CBS compatible stereo-disc system.

It resembles the Westrex 45/45 system in general (Dr. Goldmark suggested that the 45/45 might be considered a special case of the CBS technique), but avoids some of the disadvantages of that system by putting most of the program into the lateral signal fed to the cutter. Only a few percent of the total signal remains for the vertical component. The record can be played back perfectly (as a monaural recording) with an ordinary long-play cartridge. As a stereo disc it can be played with any 45/45 setup, or even with a vertical-lateral cartridge. This last feature caused Goldmark to describe it as “compatible even with the incompatible!” Wear—either with a stereo or long-play pickup—was stated to be the same as with a regular long-play record.

[Stereo developments at the convention were sufficiently important to justify a complete article. This is being prepared by Mr. Norman H. Crowhurst, and will probably appear in an early issue.]

Computers and therapeutics

Biology was one of the important subjects. One session was devoted to medical electronics and one to biological transducers.

Top item on the medical-biological program was an infra-red spectrometer-computer for analyzing complex biochemical mixtures such as hormones. The instrument, developed by International Telephone & Telegraph Corp., is expected to be of great value in cancer research. In analyzing by chemical methods, one constituent is identified and removed from the compound, then the process is repeated for another—a time-consuming and laborious process. The new method, explained president Henri Busignies of Federal Telecommunications Labs (research division of IT&T), is to treat the absorption spectrum of the compound as a signal and to use the communications man's long experience with mixing and unmixing signals to discover not only

the components of the compound but also their relative quantities.

A pressure transducer, working on the strain-gauge principle, that can take measurements of blood pressure inside the human heart, at the same time bringing back blood samples from the heart's interior, was discussed by electronics researchers of the Ford Motor Co. laboratory.

Another paper described the use of a Nipkow disc in making biological microphotographic measurements, and still another covered the electronic evaluation of the condition of the unborn fetus.

An electronic postoffice

Experiments in electronic mail sorting had been started before last year's convention. This year a whole session was devoted to the method being tried at Ottawa, Canada. Each letter is readdressed by an operator, the new address being put on the back of the envelope in fluorescent ink. A simple code, easily learned by unskilled labor, is used. From this point, the various sortings for province, city and street address or carrier's route are entirely electronic.

An almost opposite system, which handles preliminary sorts only, is undergoing experiment at Washington, D. C. Letters fed to the electronic machine are sorted by states—and a few cities. The apparatus reads typewritten addresses in various sizes of type, but cannot as yet read handwritten addresses nor those written in all capitals.

Broadcast techniques

A new concept in the broadcasting field was presented by Leonard Kahn, developer of a compatible single-sideband AM transmission system. Described a year ago in the *Proceedings of the IRE*, the system has been tried out by several stations, including New York's WMGM and WABC. One sideband is greatly reduced in power without making special receiving techniques necessary, as in conventional types of single-sideband transmission. The reception in fringe areas is improved, since more power is concentrated in the single sideband, and fading—often due to interactions between the two sidebands—is not so marked. Interference can be reduced because of the smaller bandwidth of the single-channel signal.

Multiplex transmission received a couple of papers. Color TV was represented by a few scattered papers at different sessions.

The IRE show

The exhibition which is so impressive a part of the annual meetings was on a highly practical level, following last year's pattern of accenting improvements on existing practice rather than strange new equipment. One old-timer was heard to murmur that he could

remember when the bulk of the exhibits had to do with entertainment electronics—broadcasting and receiving equipment—but that now it had become practically a pure military-industrial setup. A number of striking things did however appear among the 17,000-odd pieces of equipment exhibited.

One of these was an elapsed-time tube exhibited by Raytheon. It looked like a miniature tube envelope with two terminals, filled with a bluish liquid. This liquid, a copper sulphate solution, gradually clears up as current passes through it, till—at the end of 20,000 microampere hours—it is entirely clear. If one wishes to find out how long a piece of equipment has been in operation while the tube still shows considerable color, a colorimeter indicates the number of microampere hours rather accurately. The device—if it reaches the popular market—should have a number of interesting applications. The high-fidelity enthusiast would be particularly interested. He could hook up one of these tubes in a circuit drawing 20 μ a dc, and at the end of 1,000 hours the clear liquid in the tube would tell him it was time to replace the diamond stylus.

A battery-operated TV set was another interesting exhibit. The battery consisted of 10 Yardney Silvercells and a solid-state converter manufactured by Interelectronics Corp. Viewers were informed that it would operate the set up to 6 hours and could be recharged overnight (at a low charging rate).

Inertial guidance systems were displayed by a number of exhibitors. Inertial guidance is a method of locating one's position on the globe by starting from a fixed known point with equipment that tells how far and in what direction one moves. It consists of a “stable table” that maintains its position with relation to the earth and to any change in the position of the vehicle carrying it. Three gyroscopes, one in each direction of motion, give it that stability. Accelerometers take note of any acceleration in any of these directions, and electronic devices record their output in terms of direction and distance. It is a system which might be called super dead reckoning, and can be used—for example—by a submarine traveling under Arctic ice, to indicate its position accurately.


A number of other displays were impressive in themselves, but revealed no startling advances in electronics. One, a portable antenna, brought back to the minds of old-timers the early days of portable radios, some of which were said to be best transportable by Mack truck. The antenna, exhibited by Kennedy Corp., was a parabola 28 feet across. It looked substantial enough for any permanent job, but two rubber-tired wheels were visible part way up the tower, and the whole job could be demounted and towed by a pickup truck. Probably it is the biggest piece of portable electronic equipment that is in existence.

END

what's new ?




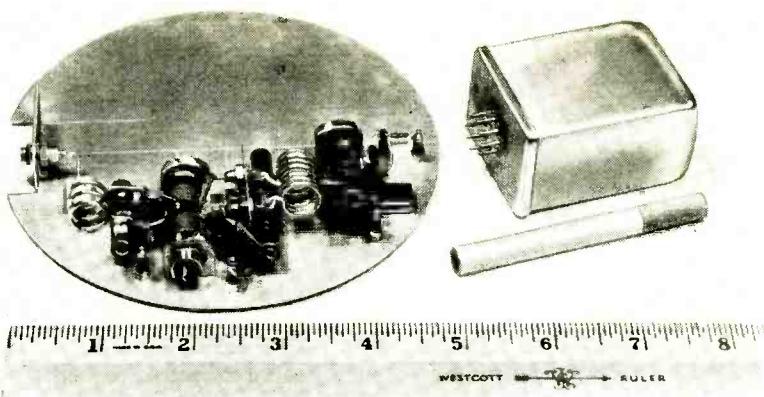GLASS TRANSISTOR HOUSING developed by G-E is the first in glass to meet the JETEC-recommended standard for low-power transistors. Eventually, mass-produced glass transistors may be much cheaper than those with metal cases.




SATELLITE TRANSMITTER with 500-mw output is smaller than a pack of cigarettes. It weighs less than 3 ounces and takes up less than 6 cubic inches of space. Operating at 108 me, the crystal-controlled transmitter uses three transistors. The unit, which operates 1½ to 4 times as long as existing transmitters, was constructed by engineers of the DuKane Corp., St. Charles, Ill., under contract to the Naval Research Laboratories.

GERMANIUM RESISTANCE THERMOMETER for measuring temperatures near absolute zero is dwarfed by a common pin. The heart of the unit is a tiny bridge of arsenic-doped germanium. The doped germanium presents a variable resistance to currents flowing through it. Temperature is measured by determining the potential drop when a small known current (approximately 10 μ a) is passed through the bridge. Developed at Bell Telephone Labs, the unit may be useful for accurately measuring temperatures in outer space, when mounted in a suitable carrier.

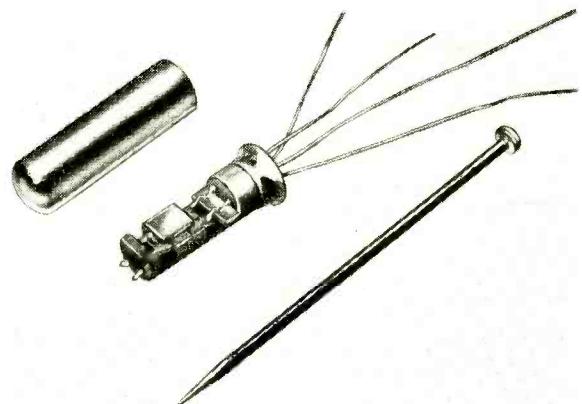

FIVE-STAGE MODULAR RADIO RECEIVER little bigger than an ordinary paper clip illustrates a new miniaturization technique. Using micro-modules (see photo insert), employing transistors and greatly reduced wiring, a typical missile guidance unit's size and weight could be reduced 90% or more. Developed by RCA, now under 2-year contract to the Army Signal Corps, the final aim of the project is to bring micro-module construction to the point where the weight of a 30-pound airborne radio system could be reduced to about 4 pounds.

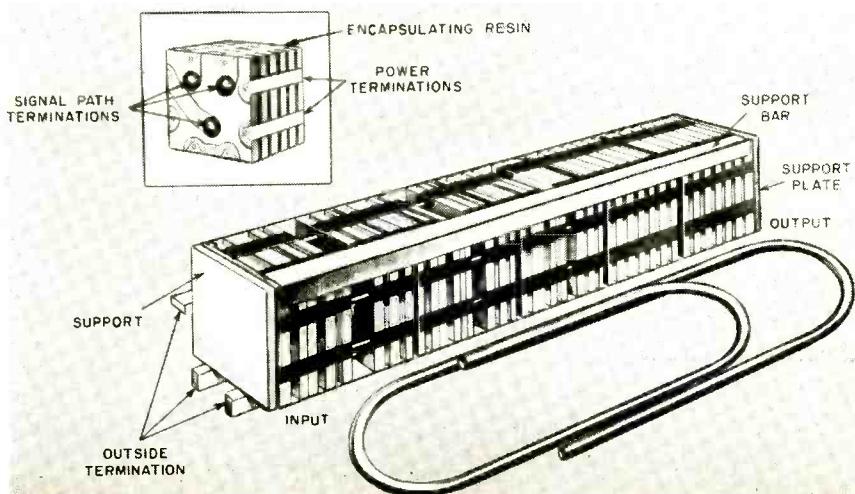

TRANSISTORS In The TV SET

By LOUIS E. GARNER, JR.

LAST month we examined the early stages of the transistor TV receiver. We discussed the front end, video if strip, video detector and video amplifiers. Now we will continue our first detailed look at an all-transistor TV set.

Audio if amplifier

A transistor TV receiver's audio if strip will probably consist of one or two stages, with the final stage driving a standard FM detector circuit modified to use semiconductor diodes in place of vacuum tubes. A deluxe receiver might use a three- or four-stage audio if amplifier, with the last stage or two serving as limiters, followed by a conventional discriminator type FM detector.

A two-stage 4.5-mc audio if amplifier and ratio detector circuit is shown in Fig. 5. Transistors V10 and V11 serve as common-emitter amplifiers. Rf transistors would be used in these stages, with suitable units including surface-barrier rf triodes, tetrodes and drift types. We have assumed the use of p-n-p rf transistors here.

The 4.5-mc signal obtained from the video amplifier is link-coupled to if transformer T10. A tap is provided on this unit's secondary winding to insure a good impedance match to V10's input circuit. Base bias current for the first stage is supplied by voltage divider R39-R40, bypassed by C31. Emitter resistor R41, bypassed by C32, establishes a small reverse bias for stage stabilization. R42 and C33 form a decoupling filter in V10's collector circuit.

Transformer T11 has a tuned prima-

ry winding and an untuned stepdown secondary. The primary-secondary turns ratio is chosen to provide a good impedance match to V11's base input circuit. A tap is provided on the transformer's primary to provide an optimum compromise between circuit Q and stage gain.

V11's base bias is furnished by voltage divider R43-R44, bypassed by C34. Unbypassed emitter resistor R45 introduces a small amount of degeneration to improve circuit stabilization. R46 and C35 form a decoupling filter.

The amplified audio if signal developed across transformer T12's primary is coupled to its center-tapped secondary and to coil L13. From here, the signal is applied to an FM detector which abstracts the audio modulation from the FM if carrier. The FM detector used in Fig. 5 is a modified ratio detector, with the customary vacuum-

tube diodes replaced by semiconductor diodes D1 and D2, shunted by resistors R47 and R48. C36 serves as the if bypass and C37 as the dc stabilizing capacitor. The audio output signal is obtained through filter R49-C39.

Audio amplifier

The audio signal obtained from the ratio detector is next fed to audio amplifier and output stages very similar to those used in present-day transistor radios. Standard audio transistors would be used in these circuits. However, chances are that the output stage will supply more power than a portable radio. To conserve operating power, the output stage may be operated as a class-AB or class-B push-pull amplifier, with medium-power transistors in portable sets and large multi-watt transistors in receivers intended

(Continued on page 76)

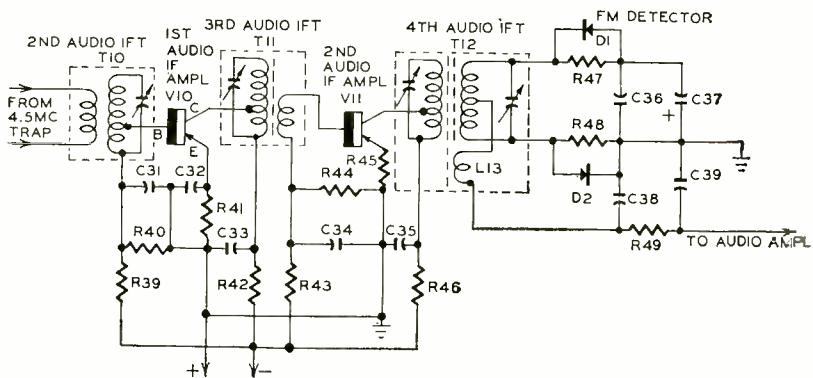


Fig. 5—The audio if strip. Two if amplifiers, and two diodes for FM detection are used.

"HEATHKITS®

gave me my start and I'm still sold!"


"...they are my lowest cost way to real quality and dependability in electronic equipment of any kind..."

...The clean, modern styling of HEATHKITS make me proud to own them. They make a handsome and useful addition to my workshop.

...Rigid quality standards of components used in HEATHKITS assure me of performance equal to or surpassing instruments costing many times more.

...after assembling a HEATHKIT myself, I know what "makes it tick"... I know that the thoughtful circuitry design and name-brand components used throughout guarantee me years of trouble-free service.

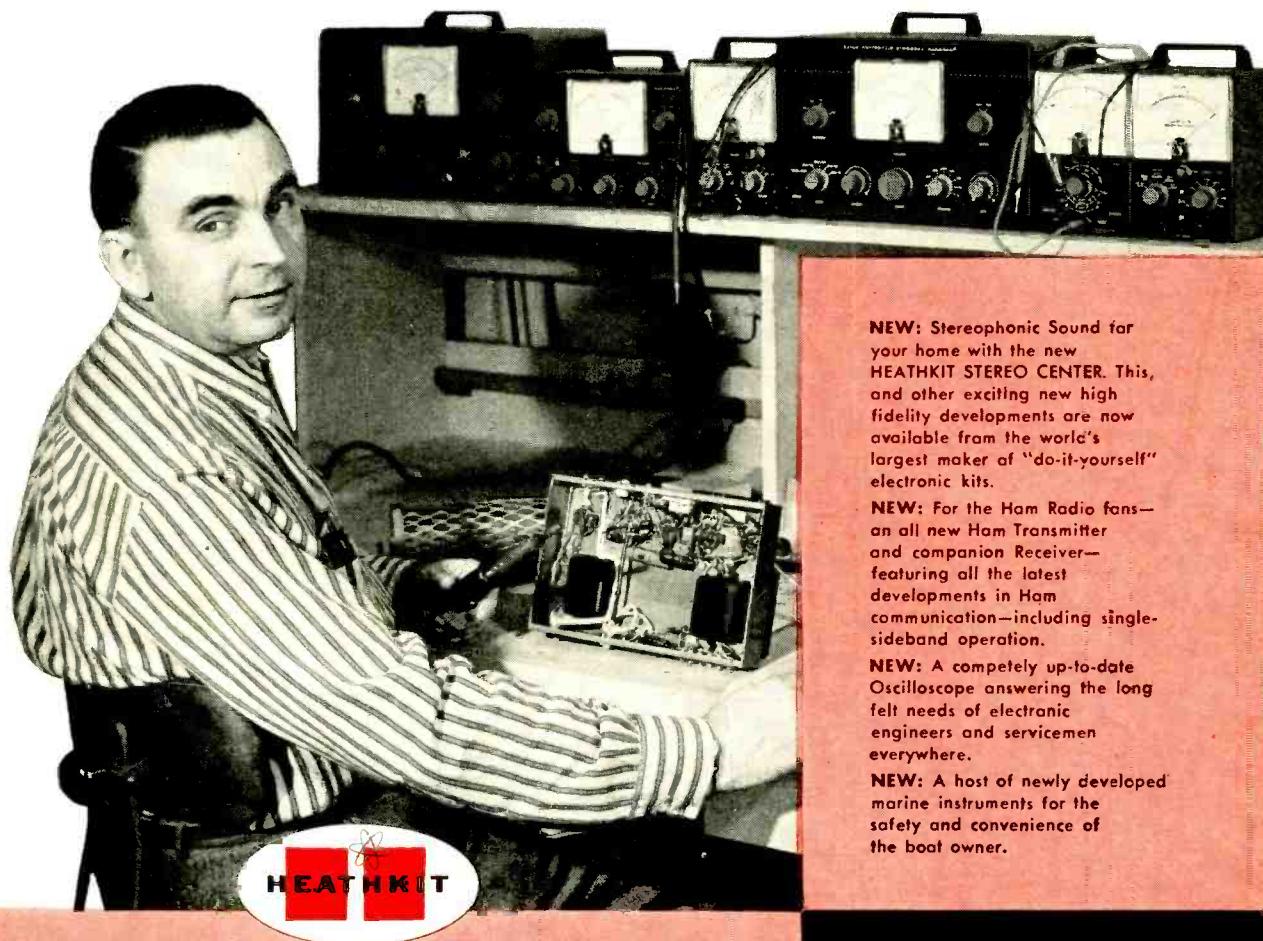...HEATHKITS cost me half as much as ordinary equipment... and I get so much more. In assembling my own instruments I am sure of the quality that goes into them. Plus the complete assembly and operating instructions as well as detailed schematics that are at my fingertips for future reference."



NEW: Stereophonic Sound for your home with the new HEATHKIT STEREO CENTER. This, and other exciting new high fidelity developments are now available from the world's largest maker of "do-it-yourself" electronic kits.

NEW: For the Ham Radio fans—an all new Ham Transmitter and companion Receiver—featuring all the latest developments in Ham communication—including single-sideband operation.

NEW: A completely up-to-date Oscilloscope answering the long felt needs of electronic engineers and servicemen everywhere.

NEW: A host of newly developed marine instruments for the safety and convenience of the boat owner.

The HEATH TIME PAYMENT PLAN allows you to outfit your whole workshop at one time with needed test instruments while you pay in easy monthly installments.

HEATH COMPANY Benton Harbor 20, Michigan



a subsidiary of Daystrom, Inc.

TELEVISION

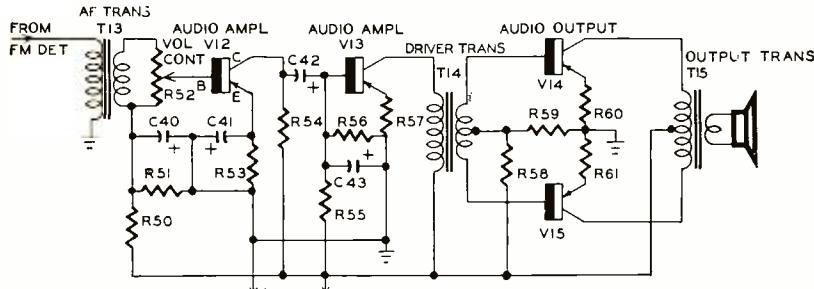


Fig. 6—Circuit of the audio amplifier and output stages.

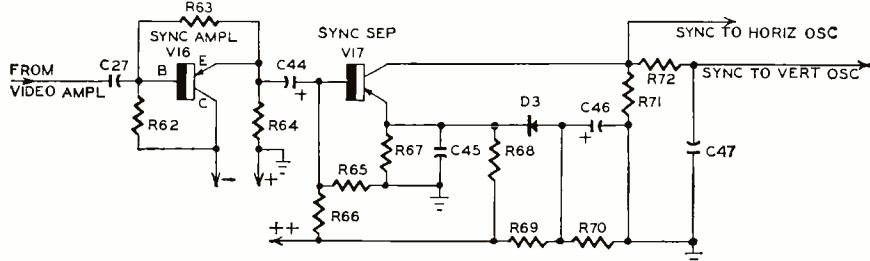


Fig. 7—The sync separator uses two p-n-p transistors and a crystal diode to do its job.

(Continued from page 59)

for home use (such as large consoles). The circuit of a typical audio amplifier section is given in Fig. 6. This amplifier consists of two common-emitter "gain" stages driving a common-emitter push-pull output amplifier which, in turn, drives a PM speaker. All transistors are p-n-p units.

In operation, the audio signal obtained from the ratio detector is coupled through impedance-matching transformer T13 to V12's input circuit. Potentiometer R52, across T13's secondary winding, serves as a *volume* control. Base bias for the first stage is supplied by voltage divider R50-R51, bypassed by C40. Emitter resistor R53, bypassed by C41, insures stable operation. R54 is V12's collector load.

The amplified audio signal appearing across R54 is coupled through capacitor C42 to V13's base. This stage's base bias current is supplied by voltage divider R55-R56, bypassed by C43. An unbypassed emitter resistor, R57, is provided to do a threefold job—it stabilizes stage operation, reduces distortion by introducing a small amount of degeneration and increases V13's input impedance. Driver transformer T14 matches V13 to the push-pull output stage. A stepdown turns ratio is used here.


Transistors V14 and V15, together, form the power output stage. Base bias current for these transistors is furnished by voltage divider R58-R59. Small unbypassed emitter resistors R60 and R61 minimize the effects of differences between V14 and V15 and thus insure balanced operation. Finally, the amplified output signal is coupled through output transformer T15 to the loudspeaker's voice coil.

Sync separator

Many types of transistor pulse-shaping, clipping and amplifying circuits

have been developed for use in military equipment and in electronic computers. Thus, the problem of sync-pulse separation is a relatively minor one. Chances are that a commercially manufactured TV receiver will employ a one- or two-stage sync separator, using high-speed switching or rf transistors in these stages. The schematic of a typical sync separator is given in Fig. 7. This circuit includes an impedance-matching common-collector amplifier (V16) and common-emitter sync separator (V17). Both stages use p-n-p's.

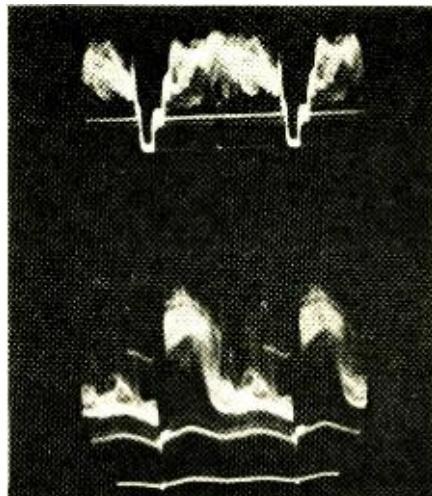In operation, the video signal obtained from the video amplifier is coupled through dc blocking capacitor C27 to V16's base circuit (waveform is shown in Fig. 8). Base bias current for this stage is provided by voltage divider R62-R63, with resistor R64 acting as the emitter load. The use here of a common-collector amplifier minimizes loading on the video amplifier. As the




Courtesy of Motorola, Inc.
Fig. 8—Waveforms at V16's base; (top) 60-cycle sweep; (bottom) 15,750-cycle sweep.

reader may recall, a common-collector circuit, in contrast to the more popular common-emitter configuration, has a *high* input impedance. The signal appearing across R64 (see Fig. 9) is coupled through dc blocking capacitor C44 to V17's base input circuit.


V17 is biased so that it is driven to collector-current saturation by the peaks of the applied video signal. This establishes the amplitude of the peak pulses developed across collector load resistor R71 at a relatively fixed value and, to some extent, clips off noise peaks of greater amplitude than the sync pulses. This saturating action is achieved, even with comparatively weak input signals, by using a combination bias voltage which includes fixed and variable components. A fixed bias is applied by voltage divider R65-R66, and a variable bias is developed in the emitter circuit, appearing across R67. The latter bias, in turn, depends on collector current and the ratio of bleeder resistor R68 and emitter resistor R67, R69, R70, C46 and D3 improve the circuit's immunity to noise signals while, at the same time, providing optimum separation of vertical sync pulses.

To see how this noise-immunity circuit works, let us first consider the circuit's operation when handling normal (noise-free) sync pulses. Under these conditions, emitter current biases diode D3 in its low-resistance (or conducting) direction, permitting R69, R70 and C46 to become part of the emitter-to-ground circuit. In effect, C46, a fairly large capacitor, is shunted across R67, and the emitter bias circuit has a fairly long time constant. This permits optimum separation of the broad, low-frequency vertical sync pulses.

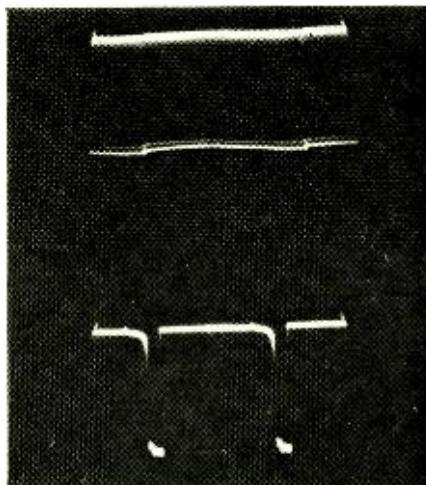If a high-amplitude noise signal is applied to the stage, D3 is still biased in its forward (conducting) direction and the action is as before. However, under these conditions, C46 can charge to a peak voltage higher than that to



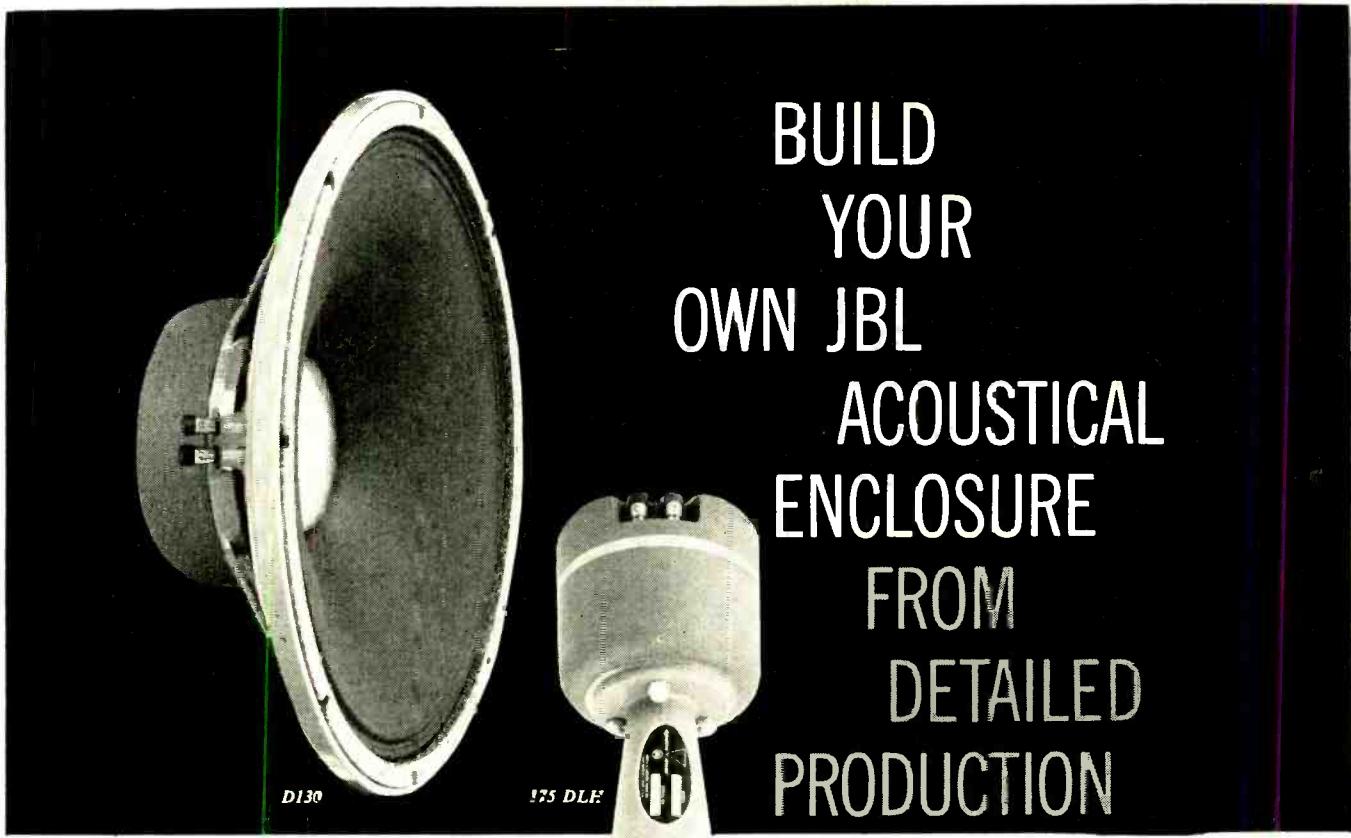
Courtesy of Motorola, Inc.
Fig. 9—In some transistor receivers, this waveform will be present at V16's base; (top) 60-cycle sweep; (bottom) 15,750-cycle sweep.




get the greatest thrill

high fidelity can give you...

THE HARKNESS Model C40

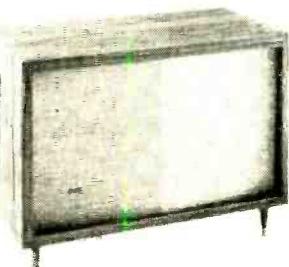

Model C34

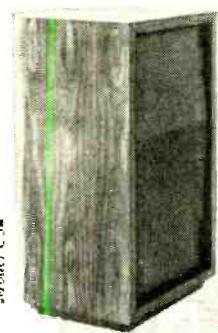

USE THIS FORM TO ORDER YOUR PLANS

Now you can build this most popular JBL enclosure from detailed production prints which include a complete list of materials, all dimensions, and instructions for assembly.

full range, rich, clean sound from precision JBL Signature loudspeakers mounted in an acoustical enclosure you make with your own hands. Reward your painstaking craftsmanship with speakers designed for the perfectionist. JBL Signature units, such as the Model D130, are acknowledged by foremost authorities to be the finest made. The D130 is the only 15" extended range speaker made with a 4" voice coil. It is unsurpassed in efficiency and transient-handling ability. The JBL Model 175DLH gives you smooth, crisp reproduction of frequencies above 1200 cps. The 175DLH is equipped with an acoustical lens, an exclusive JBL development, for even distribution of highs over a 90° solid angle. Any speaker, if it is to give you accurate bass reproduction, must be mounted in a properly engineered acoustical enclosure.

BUILD A JBL BACK-LOADED FOLDED HORN

Designed specifically for the JBL D130, the JBL back-loaded folded horn is probably the most widely-used enclosure of its type ever manufactured. The cabinet is relatively small—less than 40" in its greatest dimension—and yet, ingeniously folded within, is an exponentially tapered horn path with an effective length of six feet. The horn adds an octave of accurate, clean, deep down bass. There are two versions of the horn: Model C34 stands vertically and may be placed in a corner, although corner placement is not required. Model C40, the Harkness, is a low-boy folded horn that is independent of wall or corner for proper functioning. Prints are designed for direct, simple, clear instruction, and time-saving construction. Cost is three dollars per set.

JAMES B. LANSING SOUND, INC.

3249 Casitas Avenue, Los Angeles 39, California

Gentlemen:

Enclosed find \$_____ for

_____ Model C34 Production Prints @ \$3.00 per set.

_____ Model C40 Production Prints @ \$3.00 per set.


Please print clearly or type your name and complete address:

Name _____

Address _____

JBL

TELEVISION

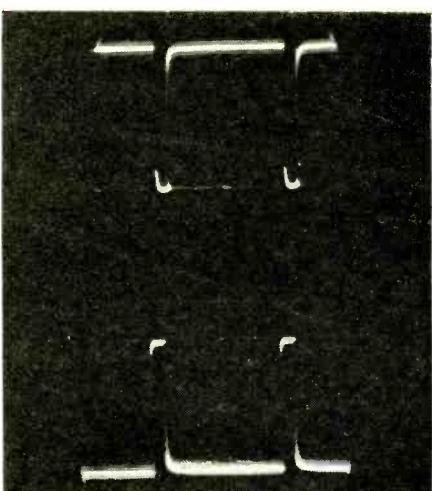

Courtesy of Motorola, Inc.
Fig. 10—Waveforms at V17's output; (top) at the collector, 15,750-cycle sweep; (bottom) at the emitter, 15,750-cycle sweep.

3 Million Transistor Portables

*Mean Big Battery Business
and Bigger Dealer Profits*

That's a lot of transistor portables that are going to be needing batteries this year... nearly three times as many as a year ago, and the figure is still growing.

For this skyrocketing new market, Mallory offers a complete line of transistor and portable radio batteries.

Mercury batteries, pioneered by Mallory, last longer, give steadier volume than ordinary batteries. Mallory Zinc-Carbon batteries are dependable and economical—meet all the requirements of today's modern portable radio sets, and flashlights as well.

Mallory Battery Company

A Division of

P.R. MALLORY & CO. Inc.
MALLORY

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

In Canada, Mallory
Battery Company of
Canada Limited,
Toronto 4, Ontario

- Capacitors • Vibrators • Resistors • Controls • Switches • Filters
- Rectifiers • Power Supplies • Mercury and Zinc-Carbon Batteries

which it is charged by the average sync pulses. When this occurs, the voltage across C46 is such as to place a reverse bias on D3, and C46 is effectively removed from the emitter-to-ground circuit. Thus, the time constant of the emitter biasing circuit changes from a large to a relatively small value (C45 is much smaller than C46). This lets the sync separator recover from noise pulses more quickly and allows a normal separation of horizontal sync pulses.

The stage continues to operate with a short time constant in its emitter biasing circuit until C46 discharges through R70. Then normal operation is resumed. This C46-R70 time constant is long enough to insure good noise immunity, but not so long as to interfere with the circuit's recovery in time to separate the next vertical sync impulse.

The sync pulses separated by V17 and appearing across R71 (see Fig. 10) are fed to the horizontal and vertical sweep oscillator circuits. R72 and C47 form an integrating network for the vertical sync pulses.

Sweep and high-voltage circuits

As in vacuum-tube TV receivers, the sweep oscillators may employ any of a variety of basic circuits—multivibrators, blocking oscillators, various types of relaxation oscillators and so on. In addition to the basic oscillator types available to vacuum-tube circuit designers, many specialized semiconductor oscillators suitable for use in sweep oscillator circuitry employ special-purpose devices such as G-E's Unijunction transistor, IBM's "thyatron" transistor and Shockley's bi-stable diode.

Transistor deflection circuits are, in a way, easier to design than vacuum-tube sweeps. For one thing, CRT deflection yokes are, in general, low-impedance devices. Vacuum tubes are high-impedance devices. Thus, considerable effort must be expended simply to match the output of a high-impedance

TELEVISION

tube to a low-impedance yoke winding. This problem is exemplified by the circuitry used in the horizontal output stages of most commercially available TV receivers. This stage alone generally requires a medium-power vacuum tube and may consume as much as 40 watts (three times as much as a complete transistor TV receiver may need). Theoretically, however, almost zero power is required to deflect a CRT's electron beam. The high power required of a typical horizontal output stage is used almost entirely to make up for circuit losses.

While we can expect much better efficiency from transistor deflection amplifiers, typical deflection circuits will probably use one or more power transistors. Such transistors are needed to supply the high peak deflection currents required, but probably will not be used at their maximum power ratings. In many cases, the deflection yoke windings may be direct-coupled to their respective sweep output stages; the output impedance of a power transistor and the input impedance of a yoke are on the same order of magnitude.

The high dc voltage needed for the CRT's anode may be obtained in much the same way as in vacuum-tube TV sets. That is, autotransformer action might be used to step up the pulse developed during the horizontal deflection circuit's retrace (or "flyback"), with this new pulse rectified by appropriate semiconductor rectifiers. Voltage-doubler or -tripler circuits may be used if necessary.

High voltage also can be obtained by using transistor rf or pulse type power supplies. In such circuits, one or more additional power transistors

would be employed in the receiver's circuit, together with a suitable oscillator transformer, and rectifier and filter components.

A typical horizontal deflection and high-voltage circuit is shown in schematic form in Fig. 11. This circuit includes a relaxation oscillator (V18), a common-emitter sweep amplifier (V19) and a voltage-doubler high-voltage rectifier (D5 and D6).

In operation, a Unijunction transistor, V18, is used as the oscillator. The circuit's basic repetition rate (frequency) is determined by the R-C time constant of R74, R73 and charge-discharge capacitor C49. Of these components, R74 is variable and acts as the horizontal hold control. The sync pulses from the sync separator are applied to V18's emitter circuit through dc blocking capacitor C48.

The negative-going pulses developed across load resistor R75 connected to V18's B2 electrode, are fed through coupling capacitor C50 to V19's base circuit. This p-n-p transistor is biased almost to cutoff by the small direct current delivered by voltage divider R77-R76 and acts as a switch, conducting heavily when pulses are applied to its base but remaining "off" at other times.

With a strong negative pulse applied to V19's base, this transistor conducts, charging C51 through the horizontal deflection yoke and starting the horizontal trace. At the same time, C52 is charged through T16, storing energy in both the transformer's winding and the capacitor. During this time, D4 is biased in its high-resistance (nonconducting) direction.

Once the initial pulse has passed, C52 can discharge through D4 and the

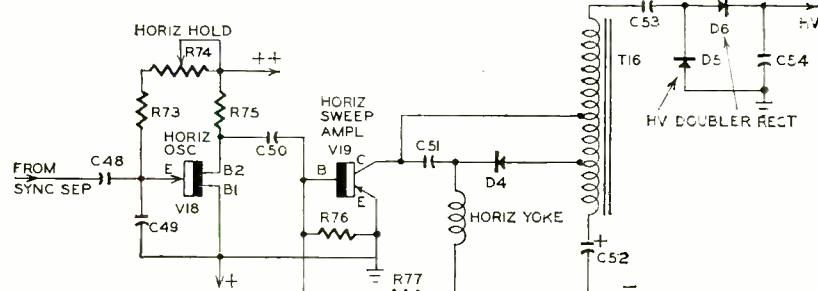


Fig. 11—Horizontal oscillator, horizontal output and high-voltage stages. A doubler rectifier and autotransformer are the major components in the high-voltage supply.


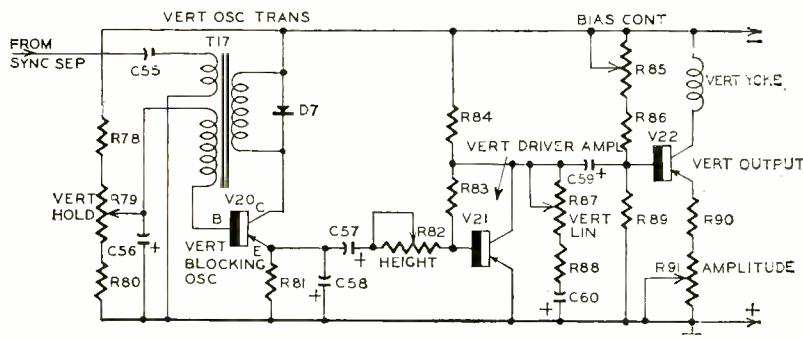


Fig. 12—The vertical sweep stages.

HOW TO BUILD A

Transistorized 40-watt supply

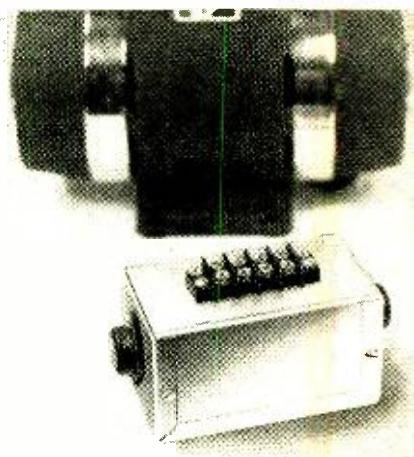

Easy to build, this modern power supply is as big in performance as it is little in size. Two CBS 2N256 power transistors, operating from a 12-volt battery, deliver 450 and 250 volts simultaneously. Combined output is 40 watts continuous service.

Features: compact and light . . . 85% efficient . . . instant-starting . . . cool-running . . . long-lived. No moving parts . . . vibrationless, noiseless and troublefree. You'll find this supply ideal for mobile or portable transmitter and/or receiver, sound system, etc.

Free Bulletin E-279 gives complete how-to-build-it details. Get it today with your 2N256 transistors from your CBS Tube distributor.



2N256...\$1.50

2N255...\$1.35

CBS-HYTRON

Semiconductor Operations, Lowell, Mass.
A Division of
Columbia Broadcasting System, Inc.

SHIPPED ON APPROVAL NO MONEY WITH ORDER NO C.O.D.



Model TD-55 — TUBE TESTER . . . Total Price \$26.95 — Terms: \$6.95 after 10 day trial, then \$5.00 per month for 4 months.



Model TW-11 — TUBE TESTER . . . Total Price \$47.50 — Terms: \$11.50 after 10 day trial, then \$6.00 per month for 6 months.



Model TV-12 — TRANSCONDUCTANCE TUBE TESTER . . . Total Price \$72.50 — Terms: \$22.50 after 10 day trial, then \$10.00 per month for 5 months.



Model 770-A — VOLT-OHM-MILLIAMMETER . . . Total Price \$15.85 — Terms: \$3.85 after 10 day trial, then \$4.00 per month for 3 months.

Superior's New Model TD-55 EMISSION TYPE TUBE TESTER

FOR { The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester.
The Professional Serviceman, who needs an extra Tube Tester for outside calls.
The busy TV Service Organization, which needs extra Tube Testers for its field men.
Speedy, yet efficient operation is accomplished by: 1. Simplification of all switching and controls.
2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

You can't insert a tube in wrong socket
It is impossible to insert the tube in the wrong socket when using the new Model TD-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

"Free-point" element switching system
The Model TD-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Checks for shorts and leakages between all elements

**Superior's
New Model
TW-11**

- Tests all tubes, including 4, 5, 6, 7, Octal Lockin, Hearing Aid, Thyratron, Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity Fuse Types, etc.
- Uses the new self-cleaning Lever Action Switches for individual element testing. All elements are numbered according to pin-number in the RMA base numbering system.
- Model TW-11 does not use combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.
- Free-moving built-in roll chart provides complete data for all tubes. Printed in large easy-to-read type.

**Superior's
New Model
TV-12**

- ★ Employs improved TRANS-CONDUCTANCE circuit.
- An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.
- ★ NEW LINE VOLTAGE ADJUSTING SYSTEM. A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.

Superior's New Model 770-A POCKET-SIZED

VOLT-OHM MILLIAMMETER USING THE NEW "FULL VIEW" METER 71% MORE SCALE AREA

Occupies exactly the same space used by the older standard 2 1/2" Meters, yet provides 71% more scale area. As a result, all calibrations are printed in large easy-to-read type.

USE APPROVAL FORM ON NEXT PAGE

We invite you to try before you buy any of the models described on this and the following page. If after a 10 day trial you are completely satisfied and decide to keep the Tester, you need send us only the down payment and agree to pay the balance due at the monthly indicated rate.

\$26.95
NET

Complete with carrying case.....

STANDARD PROFESSIONAL TUBE TESTER

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURE
SEPARATE SCALE FOR LOW-CURRENT TUBES
Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

Housed in hand-rubbed oak cabinet

\$47.50
NET

TRANS-CONDUCTANCE TUBE TESTER

*** SAFETY BUTTON**—protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

EXTRA FEATURE

Model TV-12 Also Tests Transistors!

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only" meter scale.

Housed in hand-rubbed oak cabinet

\$72.50
NET

Complete with test leads.....

NO INTEREST OR FINANCE CHARGES ADDED!

If not completely satisfied, you are privileged to return the Tester to us, cancelling any further obligation.

RADIO-ELECTRONICS

TRY FOR 10 DAYS

before you buy!
then if satisfactory pay in easy, interest free,
monthly payments. See coupon below.

Superior's New
Model 77

VACUUM TUBE VOLTMETER

WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price!

- ✓ Model 77 completely wired and calibrated with accessories (including probe, test leads and portable carrying case) sells for only \$42.50.
- ✓ Model 77 employs a sensitive six inch meter. Extra large meter scale enables us to print all calibrations in large easy-to-read type.
- ✓ Model 77 uses new improved SICO printed circuitry.
- ✓ Model 77 employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability.


AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN AC VOLTMETER: Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.

Model 77 comes complete with operating instructions, probe and test leads. Use it on the bench — use it on calls. A streamlined carrying case, included at no extra charge, accommodates the tester, instruction book, probe and leads. Operates on 110-120 volt 60 cycle. Only . . .

\$42.50
NET

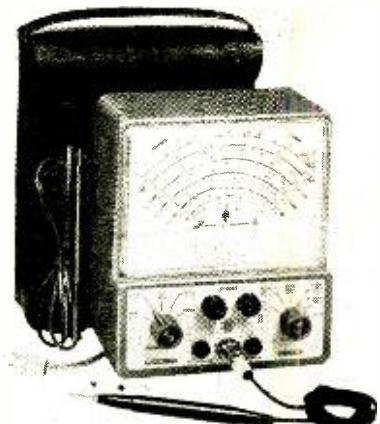

Model 77 — VACUUM TUBE VOLTMETER . . . Total Price \$42.50 — Terms: \$12.50 after 10 day trial, then \$6.00 per month for 5 months.

Superior's New

Model 76

ALL PURPOSE BRIDGE

A CONDENSER BRIDGE IT'S A RESISTANCE BRIDGE IT'S A SIGNAL TRACER IT'S A TV ANTENNA TESTER

Specifications

CAPACITY BRIDGE SECTION

4 Ranges: 00001 Microfarad to .005 Microfarad; .001 Microfarad to .5 Microfarad; .1 Microfarad to 50 Microfarads; 20 Microfarads to 1000 Microfarads. Will also measure the power factor of all condensers from .1 to 1000 Microfarads.

RESISTANCE BRIDGE SECTION

2 Ranges: 100 ohms to 50,000 ohms; 10,000 ohms to 5 megohms.

SIGNAL TRACER SECTION


With the use of the R.F. and A.F. Probes included

with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc.

TV ANTENNA TESTER SECTION

Loss of sync., snow and instability are only a few of the faults which may be due to a break in the antenna, so why not check the TV antenna first? Locates a break in any TV antenna and measures the location of the break in feet from the set terminals. Complete with R.F. and A.F. probes and test leads . . .

\$26.95
NET

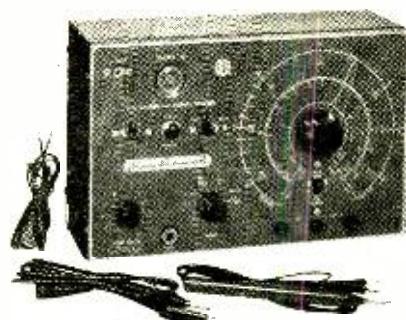

Model 76 — ALL PURPOSE BRIDGE . . . Total Price \$26.95 — Terms: \$6.95 after 10 day trial, then \$5.00 per month for 4 months.

Superior's New

Model TV-50

GENOMETER

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Color Dot Pattern Generator
- ✓ Cross Hatch Generator
- ✓ Marker Generator

R.F. SIGNAL GENERATOR: 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

VARIABLE AUDIO FREQUENCY GENERATOR: Provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

BAR GENERATOR: Pattern consists of 4 to 16 horizontal bars or 7 to 20 vertical bars.


CROSS HATCH GENERATOR: The pattern consists of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV): The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.

MARKER GENERATOR: The following markers are provided: 189 Kc, 262.5 Kc, 456 Kc, 600 Kc, 1000 Kc, 1400 Kc, 1600 Kc, 2000 Kc, 2500 Kc, 3579 Kc, 4.5 Mc, 5 Mc, 10.7 Mc, (3579 Kc is the color burst frequency.)

Complete with shielded leads . . .

\$47.50
NET

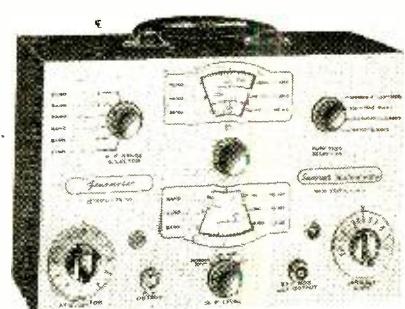

Model TV-50 — GENOMETER . . . Total Price \$47.50 — Terms: \$11.50 after 10 day trial, then \$6.00 per month for 6 months.

MOSS ELECTRONIC DISTRIBUTING CO., INC.

Dept. D-475, 3849 Tenth Ave., New York 34, N.Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

Name

Address

City Zone State

All prices net, F.O.B., N.Y.C.

Model TD-55 . . . Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00 monthly for 4 months.

Model TW-11 . . . Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00 monthly for 6 months.

Model TV-12 . . . Total Price \$72.50
\$22.50 within 10 days. Balance \$10.00 monthly for 5 months.

Model 770-A . . . Total Price \$15.85
\$3.85 within 10 days. Balance \$4.00 monthly for 3 months.

Model 77 . . . Total Price \$42.50
\$12.50 within 10 days. Balance \$6.00 monthly for 5 months.

Model 76 . . . Total Price \$26.95
\$6.95 within 10 days. Balance \$5.00 monthly for 4 months.

Model TV-50 . . . Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00 monthly for 6 months.

win a
dream
trip
for
two



BRUSSELS WORLD'S FAIR!

win other exciting prizes...
in the big, new Rek-O-Kut contest!

Rek-O-Kut's exciting, new contest is a music-lover's delight! You can win a trip for two to the Brussels World's Fair via Sabena Belgian World Airlines... magnificent Rondine turntables... and turntable arms... just by listening to a Rek-O-Kut demonstration. Simply stop in at your high fidelity dealer, ask him to demonstrate high fidelity reproduction on a Rondine turntable, and fill out an entry blank. There are no puzzles to solve — no jingles to write — no coupons to clip — nothing to buy! You'll be eligible for one of the big contest prizes... and you'll have enjoyed music reproduction at its finest — on a Rondine! Prices from \$59.95.

Selected for display at the American Pavilion, Brussels World's Fair!

For the high fidelity dealer nearest you, write:
REK-O-KUT COMPANY, INC.
38-19 108th Street, Corona 68, New York

TELEVISION

horizontal yoke, continuing the horizontal trace. The transistor (V19) is not conducting at this time and, for practical purposes, is no longer part of the circuit. Finally, as C52 is discharged, the energy stored in T16 is suddenly released as the magnetic field built up during the initial current surge collapses. This strong pulse, applied to the deflection yoke, develops the necessary retrace signal. The circuit then receives another pulse from V18 and the action is repeated.

The retrace pulse developed by T16 is stepped up by autotransformer action and fed through C53 to a voltage-doubling rectifier circuit consisting of high-voltage semiconductor diodes D5 and D6 and filter capacitor C54. The high dc voltage developed across C54 is, in turn, applied to the CRT.

The circuit for a vertical sweep circuit is given in Fig. 12. This section consists of a blocking oscillator (V20), a driver amplifier (V21) and a vertical output stage (V22). All three use p-n-p transistors in the common-emitter configuration.

In operation, T17 is the blocking oscillator transformer. Two windings provide feedback between collector and base circuits to start oscillation, while a third winding is used to inject the sync-pulse signal obtained from the sync separator. The vertical sync pulse is applied to the third winding through dc blocking capacitor C55.

The blocking oscillator's basic repetition rate is determined by its base bias current and by the R-C time constant in its base circuit. The circuit's time constant is determined by the setting of R79, by R80 and by C56. R79's setting also determines base bias and hence this potentiometer becomes the vertical hold control.


Diode D7, across T17's primary, bypasses the unwanted half cycle of the blocking oscillator's pulse.

A sawtooth signal is developed across C58 as this capacitor is charged rapidly through V20 and discharged slowly through R81. This signal is coupled through C57 and R82 to the base electrode of the driver amplifier (V21). R82 provides a basic amplitude adjustment and thus serves as a height control. Base bias for this stage (V21) is supplied through collector load resistor R84 and base resistor R83.


The amplified and inverted signal appearing across R84 is coupled through capacitor C59 to output amplifier V22. The network consisting of potentiometer R87, fixed resistor R88 and capacitor C60 is included to provide a linearity adjustment; R87 is the circuit's vertical linearity control.

Base bias for the output amplifier is furnished by a voltage divider made up of potentiometer R85 and fixed resistors R86 and R89. R85 can be adjusted to provide optimum bias for the output stage whenever it is necessary to replace the vertical output transistor (V22). Unbypassed emitter

THE
LINE
WITH
PROTECTION

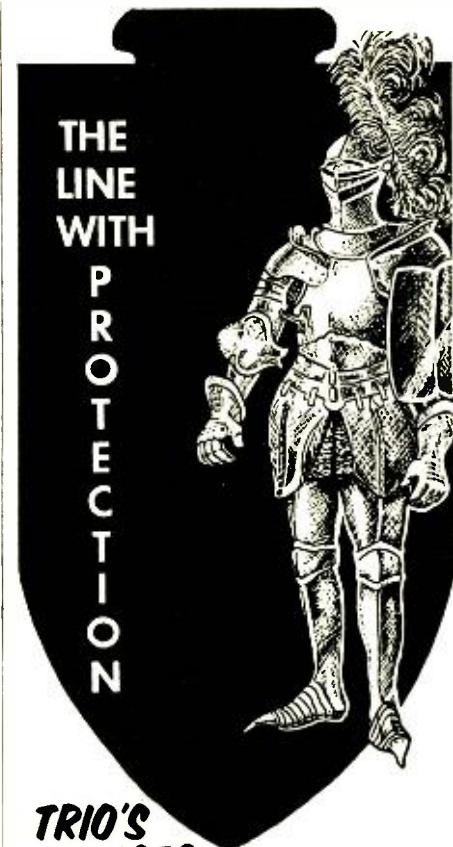


TRIO'S 1958 ZEPHYR FAMILY OF ANTENNAS

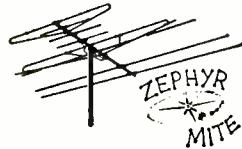

FOR DISTANCE



FOR EXTREME DISTANCE

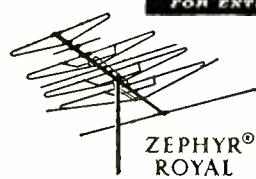

FOR THE MAXIMUM

U.S. PATENT No. 2,772,413
CANADIAN PATENT No. 541,670

EXTENDED "WING" DIPOLE
"WING" DIRECTOR
COLLINEAR DIRECTOR
STAGGER - TUNED

TRIO [®] Manufacturing Company
GRIGGSVILLE, ILLINOIS

Export Sales Div.,
Scheel International Inc.,
5909 N. Lincoln Ave., Chicago, U.S.A.
Cable Address: HARSCHEEL

TELEVISION

resistors R90 and R91 help stabilize circuit operation. One of these resistors (R91) is made adjustable and serves as an additional amplitude control.

The vertical deflection yoke is direct-coupled to V22 and is its collector load. In this application, V22 is operated as a class-A power amplifier. As a result, the vertical deflection signal includes a large dc component which would normally shift the CRT's raster far to one side. This shift is corrected by placing small ceramic recentering magnets longitudinally in the vertical yoke's window.

To sum up

The transistor TV circuits we have discussed are based on circuits which have been investigated theoretically, studied experimentally and, in some cases, used in experimental transistor television receivers. They do not necessarily represent the final circuits which will be used when such sets are in full production. The development and manufacture of new types of semiconductor devices could result in considerable changes in basic circuit philosophy.

For example, the invention of an extremely high-gain high-frequency transistor could reduce the number of stages needed in the video if and video amplifier sections. Similarly, the development and manufacture of a semiconductor picture-reproducing device which could be used in place of a cathode-ray tube would require entirely different sweep circuitry and probably would eliminate the need for a high-voltage supply.

Finally, there are the day-to-day changes in television broadcasting. With the increased interest in color television, there is the real possibility that the first commercially produced all-transistor TV receivers will be color sets. There is also the possibility that some manufacturer, taking advantage of the sales appeal and public interest in transistors, may introduce a partially transistorized (or hybrid) set well in advance of an all-transistor receiver.

END

Bibliography

Application Notes on the Surface Barrier Transistor, Sprague Electric Co., *Transistors I*, RCA Laboratories.

Joseph Chernof, "Design Features of a Transistor Sweep Circuit," *Electronic Equipment*, July, 1957.

Flory, Gray, Morgan and Pike, "Miniature ITV Camera Uses Drift Transistors," *Electronics*, January, 1957.

Louis E. Garner, Jr., *Transistor Circuit Handbook* (Sams).

Louis E. Garner, Jr., "Using the Unijunction," *Radio-ELECTRONICS*, July, 1957.

Walter B. Guggi, "CRT Deflection Circuit Has High Efficiency," *Electronics*, April 1, 1957.

D. W. Baker, "High-Frequency Circuits Use Meltsback Tetrodes," *Electronics*, June 1, 1957.

M. J. Hellstrom, "Design Considerations in Transistor Vertical Deflection," *Electronic Equipment*, June, 1957.

Lloyd P. Hunter, *Handbook of Semiconductor Electronics* (McGraw-Hill).

Richard B. Hurley, "Designing Transistor Circuits—Video Amplifiers," *Electronic Equipment*, May, 1957.

W. Palmer and G. Schiess, "Transistorized Vertical Deflection System," *Electrical Design News*, May, 1957.

Richard F. Shea, *Transistor Circuit Engineering* (Wiley).

Just 2 settings on the NEW

Model FC-2

FAST-CHECK TUBE TESTER

tests over 600
tube types
completely,
accurately
... AND IN
SECONDS!



SIZE:
H: 11 1/4"
W: 14 3/8"
D: 4 3/8"

NEW Special compartment
to accommodate line cord
and CRT Test Adapter cable

CANNOT BECOME OBsolete

Engineered to accommodate all
future tube types...new tube lists
furnished periodically.

TRY THE FC-2 BEFORE YOU BUY IT!

Shipped on approval for
FREE 10 day trial...No
obligation to buy

EASY TO BUY IF YOU'RE SATISFIED!

Pay in small monthly pay-
ments at net cash prices...
no financing charges

MODEL FC-2—housed
in rugged oak carrying
case complete with
CRT adapter, tube
listings.....only \$69.50 Net

GUARANTEED FOR 1 FULL YEAR

This extremely low price is
made possible only because
YOU ARE BUYING DIRECT
FROM THE MANUFACTURER

- NO MULTIPLE SWITCHING
- NO ROLL CHART CHECKING

The FAST-CHECK enables you to save valuable time and eliminate unprofitable call backs. You earn extra money and win confidence by showing your customer the actual condition and life expectancy of the tube on the large meter scale of the FC-2. The extra tubes you will sell each day will pay for the FAST-CHECK in a very short time.

WIDE RANGE OF OPERATION

- Checks quality of over 600 tube types...more than 99% of all TV and radio tubes, including the newest series-string TV tubes, auto 12 plate-volt tubes, OZ4s, magic eye tubes and gas regulators.
- Checks inter-element shorts and leakage.
- Checks for gas content.
- Checks for life expectancy.

IMPORTANT FEATURES

✓ Checks each section of multi-section tubes and even if only one section is defective the tube will read "Bad" ✓ 41 long lasting phosphor-bronze tube sockets accommodate all present and future tube types—cannot become obsolete ✓ Less than 10 seconds required to test any tube ✓ Large D'Arsonval type meter is extremely sensitive yet rugged—is fully protected against accidental burn-out ✓ Line isolated ✓ 7-pin and 9-pin straighteners conveniently mounted on panel ✓ Quick reference tube chart lists over 600 tube types ✓ Line voltage compensation

NEW A specially designed PICTURE TUBE ADAPTER cable is now part of the FC-2...making it a highly efficient CRT Tester-Rejuvenator. This feature eliminates the need of carrying extra instruments and makes the FC-2 truly an all-around tube tester. The adapter enables you to check all picture tubes including the new short-neck 110 degree picture tubes for cathode emission, shorts and life expectancy...also to rejuvenate and restore cathode emission of weak picture tubes.

"You've really made tube testing a snap" . . . "I've almost got the cost of the Fast-Check paid off

WHAT
with the extra money I've made, and it's . . . "It's
only 2 weeks since I received it" . . . "It's
easier to use than you said" . . . "I wouldn't
ever want to be without it" . . . "I use it in the
shop and take it along on every call".

*Names on request

MAIL COUPON NOW—NO MONEY REQUIRED WITH ORDER

CENTURY ELECTRONICS CO., INC.

111 Roosevelt Avenue

Dept. 106, Mineola, N.Y.

Please rush the new Model FC-2 FAST-CHECK TUBE TESTER for a 10 day trial period. If I am not completely satisfied I will return the instrument within 10 days without further obligation. If fully satisfied I agree to pay the down payment within 10 days and the monthly installments as shown. No financing charges are to be added. Should I fail to make payment when due, the unpaid balance shall become due and payable at once.

BUDGET TERMS: Pay \$14.50 within 10 days after receipt of instrument. Balance \$11.00 monthly for 5 months, plus shipping charges.


PREPAID TERMS: Enclose \$69.50 with coupon as payment in full and Century will pay all shipping costs. 10 day money-back guarantee.

Name.....

Address.....

City..... State.....

ABSOLUTELY NO RISK ON YOUR PART

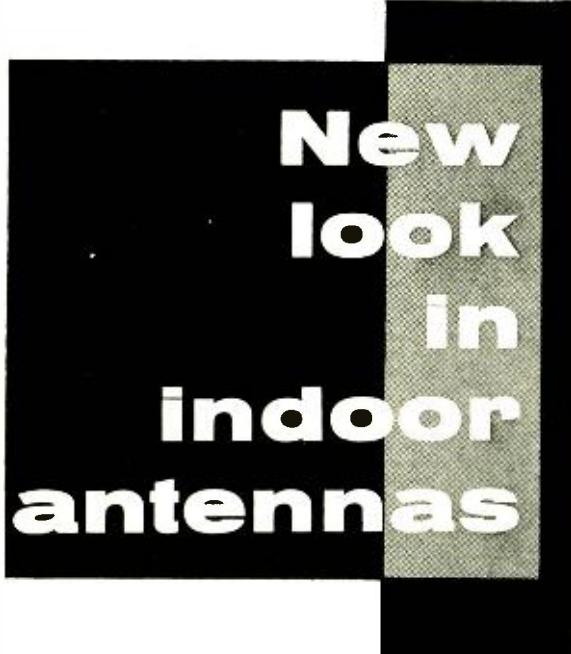

A NEW type of indoor TV antenna is now on the retailer's shelves. Called Vi-Fi (short for Video-Fidelity), it is different in both design and appearance—even has a flip-top box.

At the heart of this antenna are two coils wound on a common form and spaced about 3 inches apart. The inductances of these coils are simultaneously varied by an adjustable ferrite core. This electrically compensates for any variation from the theoretical element length. With previous types of indoor antennas, the length of the elements had to be adjusted or a multiple-position switch set to bring in the best picture.

The Slide Rule tuner (adjustable ferrite core) in the Amphenol Vi-Fi an-

tenna permits adjustment without touching the elements, a major problem with some types of indoor antennas. When you touch the elements, the added body capacitance may result in an improper adjustment of antenna length. When you remove your hand, the picture fades away or distorts in one way or another. None of this takes place with the Vi-Fi. Coil matching also allows shorter elements—only 27 inches when extended.

Another problem is matching the antenna to the set. The natural impedance of a dipole is approximately 72 ohms. The usual input impedance at a TV receiver's antenna-input terminals is 300 ohms. For best results the antenna's impedance must match the set's.

There are two ways to do this—either the dipole must be folded, increasing its impedance to 300 ohms, or some kind of matching network or transformer must be used. As a folded dipole is impractical and a matching transformer is bulky and expensive, a simple matching network is employed.

This network consists of a length of four-conductor ribbon line, which due to its construction transforms the dipole's 72-ohm impedance to 300 ohms. The actual wiring of this network is shown in Fig. 1 and the effective circuit in Fig. 2.

When tested in several metropolitan locations, the results were very satisfactory. It pulled in sharp, ghost-free

signals with a high signal-to-noise ratio. Simply adjusting the Slide Rule tuner cleared up ghosts and snow in many instances.

The primary or local area for television reception is rapidly expanding due to increased station power output and improved receiver sensitivity. In many areas, the outdoor antennas, which pioneered the way for television, are fast becoming old and dilapidated. In many of these instances the old roof antenna can be replaced by a new indoor unit with excellent results. The Vi-Fi was designed to fit these conditions.

Since the elements of an indoor antenna need be extended only when in use, the antenna housing is designed so that the elements can be collapsed and folded down into the case when not in use. A roll-up type dust cover (flip-top box) was added so the case could be closed, and the antenna takes on the appearance of a cigarette or jewelry box.

As an aid to orientation, the element sockets are the ball joint type, allowing 360° rotation. Two angle brackets, provided with the antenna, permit back-of-the-set installation. Since back-of-the-set mounting is not always feasible, plastic feet are fastened to the bottom cover so the antenna can also be used on top of the set. The housing comes in three decorative colors, one of which will blend with your color scheme. END

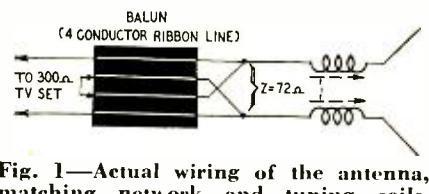


Fig. 1—Actual wiring of the antenna, matching network and tuning coils.


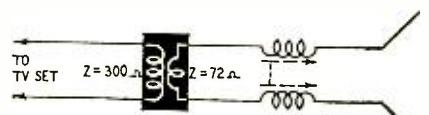


Fig. 2—Equivalent circuit shows impedance transformation from 72-300 ohms.

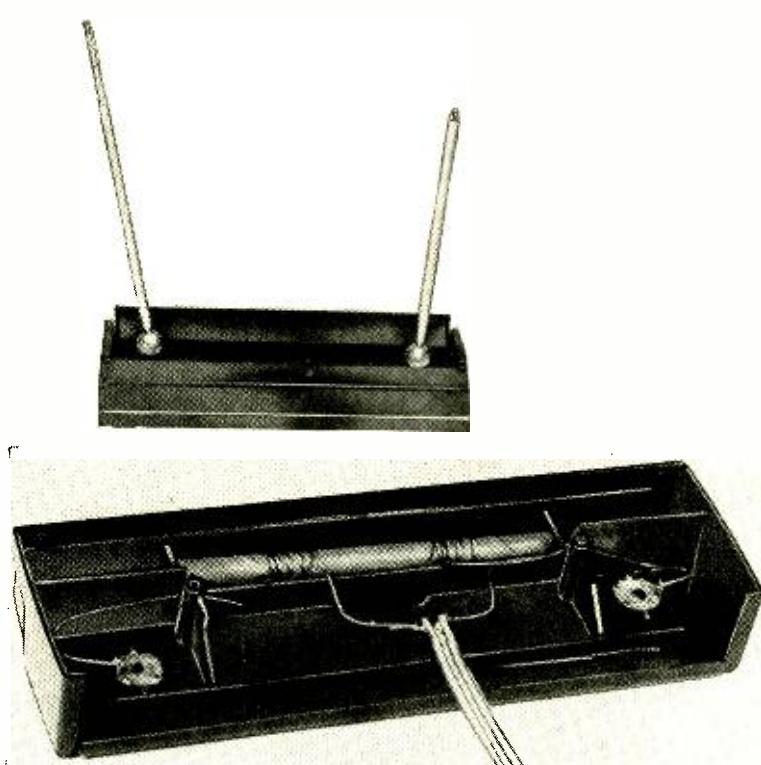

(Top) Antenna elements are partially raised after the case has been opened. Tuning is adjusted with the little lever in the front. Bottom view shows the tuned coils and four-conductor matching network.


To AVOID amplifier and speaker WASTE...choose from

University 4 WIDE-ANGLE SPEAKERS

For uniform dispersion of sound over a wide area

Only University gives you the choice of speakers you need to ensure greatest economy of amplifier power, equipment and installation costs. No wasteful, "cure-all, do-all" compromises here. Each speaker is designed to do its specific kind of job most efficiently and reliably, with plenty of room for future expansion. Each speaker incorporates many exclusive features to fulfill every possible application. The chart below graphically shows the relative differences between these four speakers in terms of sound output.

CHOICE OF 5 DRIVERS FOR CLH OR COBREFLEX

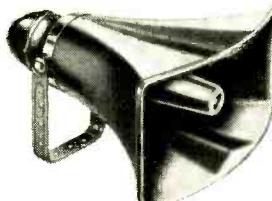


CLH 4½ ft. air column. Exclusive omni-directional bell and mounting bracket helps "tune out" reverberation and "dead spots." \$44.50 list.



COBREFLEX All die-cast aluminum one piece construction resists a life-time of physical abuse. 2½ ft. air column. \$38.33 list.



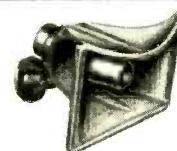CIB Built-in hermetically sealed driver. Excellent for "talk-back." Exclusive Positive-Lok omni-directional mounting bracket. \$42.00 list.



CMIL Smaller than CIB, perfect for voice. Built-in driver packs mighty wallop at low input power. Ideal for close quarter installations. \$29.75 list.



MA-25 \$27.50 list
85-6500 cps. 25 W.



SA-HF \$35.00 list
80-10,000 cps. 30 W.



SA-30 \$47.50 list
built-in matching trans.
80-10,000 cps. 30 W.




PA-HF \$47.50 list
70-10,000 cps. 50 W.




PA-50 \$57.50 list
built-in matching trans.
70-10,000 cps. 50 W.

put, input power, and low frequency response. Simply choose the intended application and determine the appropriate speakers. Or, depending upon existing operating prerequisites, select the speaker(s) capable of doing the job. That's all there is to it.

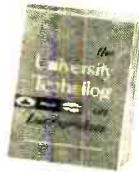NOW AVAILABLE—Free Product Catalog. Or send \$1 for the NEW 64-page University TECHNILOG, the complete speaker system planning manual. Desk J-4, University Loudspeakers, Inc., 80 S. Kensico Ave., White Plains, N.Y.



Background Noise Level in db	Average Typical Application	CHART A
50	FACTORY (Very Noisy)	
55	MACHINE SHOP (Average)	
60	PRINTING PRESS BALLROOMS RESTAURANT (Noisy) NOISY ASSEMBLY DEPT. FACTORY (Average)	
65	R.R. WAITING ROOM AUDITORIUM (Average)	
70	ASSEMBLY PLANT (Quiet)	
75	SHIPPING-REC. (Average)	
80	OFFICE (Busy)	
85	DEPT. STORE (Average)	
90	AUDITORIUM (Quiet)	
95	RESTAURANT (Average) STORE (Quiet) OFFICE (Quiet) GARAGE HOTEL LOBBY—HOSPITALS CHURCH—FUNERAL PARLOR	

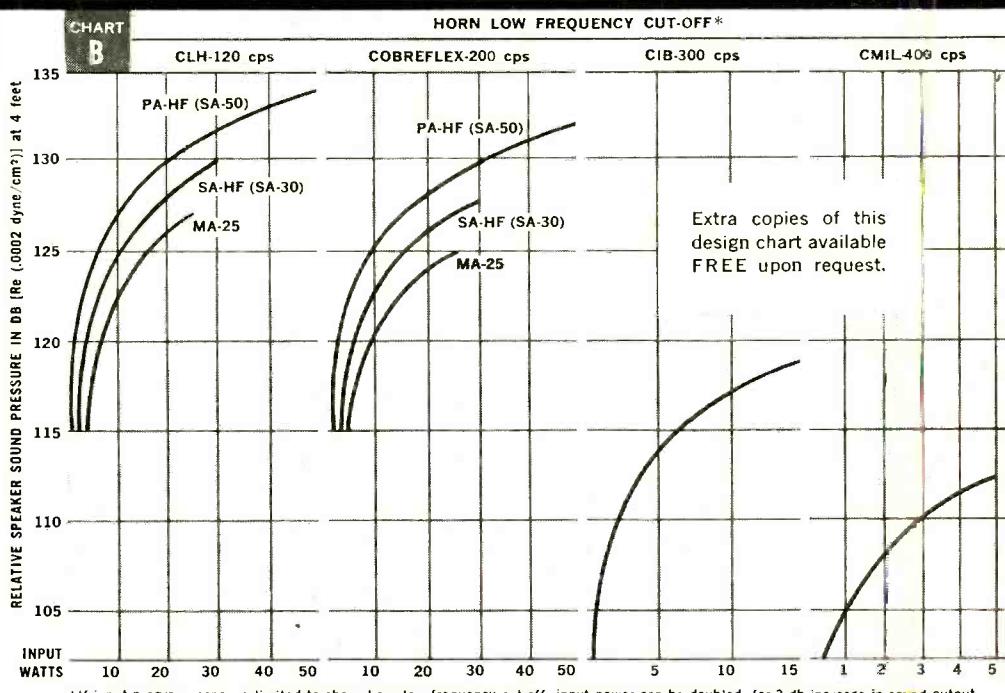

HOW TO USE THIS CHART

- Determine sound pressure needed by finding noise level from Chart A, add loss of db in Table C and add adjusting factor in Table D.
- Draw horizontal line across Chart B corresponding to the db figure just calculated. This now establishes which speakers can be considered.
- A vertical line drawn to the base of Chart B shows the input power needed for each qualifying speaker.
- Now, further selection may be based upon frequency

response necessary (see Horn Cut-Off, Chart B), initial cost, operating economy and reserve power desired.

5. The CIB and CMIL may also be used in high noise levels by employing several throughout the listening area.

Example: Factory — noise level 90 db, 320,000 cu. ft., live acoustics, music and speech

$$90 + 25 + 5 = 120 \text{ db required}$$

Qualifying speakers are CLH or Cobreflex, with any of the drivers. Final choice is determined by driver characteristics and installation problems. (Send for TECHNILOG or Product Catalog.)

ROOM VOLUME CU. FT.	INDOORS			OUTDOORS	
	LIVE	NEUTRAL	DEAD	FURTHEST DISTANCE FT.	DB LOSS
1,000	0	3	6	4	0
3,200	5	8	11	8	6
10,000	10	13	16	16	12
32,000	15	18	21	32	18
100,000	20	23	26	54	24
320,000	25	28	31	128	30
1,000,000	30	33	36	256	36

PROGRAM ADJUSTING FACTOR	SPEECH	INDOORS DB	OUTDOORS DB
	MUSIC	6	11
MUSIC & SPEECH	5	9	

LISTEN

University sounds better



FACTS FALACIES and in COLOR TV SERVICE



by ROBERT G. MIDDLETON

*Some things we have learned carefully just ain't so!***The Fallacy**

Color burst can be observed on a narrow-band scope if a demodulator probe is used.

The Fact

The burst signal is not displayed.

A scope is unsuitable for color TV service if it uses peaking coils in the vertical amplifier.

Individual cycles in the burst can be counted if a good scope is applied at the picture detector output.

Chroma waveform displays are unaffected by peaking coils.

Only a volt-ohmmeter is necessary for service in chroma circuits in a color TV receiver.

It is usually impossible to display the individual cycles of the burst signal at the output of the picture detector.

A volt-ohmmeter provides only preliminary test data. Good generators and scopes are essential for testing and adjusting chroma circuits properly.

A white dot generator must also provide cross-hatch output to be useful in convergence procedures.

An equally good convergence job can be accomplished whether cross-hatch output is available or not.

Good color reception can be obtained only if the antenna is very accurately oriented.

Extremely accurate orientation is not required. However, it is often helpful to use an antenna rotator if color programs are available on more than one channel.

in COLOR TV SERVICE**Discussion**

The test fails because the *demodulating capability* of conventional demodulating probes is limited. Such probes are OK for sweep-frequency tests of chroma circuits, in which the modulation envelope has a 60-cycle repetition rate. However, they fail in burst-signal tests in which the modulation envelope has a 15.750-cycle repetition rate and a low duty cycle. *Use a wide-band scope with a low-capacitance probe.*

Wide-band scopes which use series and shunt peaking coils in the vertical amplifier are much less costly than those using distributed amplifiers. The assumption that a scope which uses peaking coils is unsuitable for color TV tests arises from the fact that such a scope will ring on square-wave signals that have a *very fast rise*. All chroma waveforms have a relatively *slow rise time* and a *wide-band scope with series and shunt peaked amplifiers is completely satisfactory for color TV tests.*

The inability to display individual cycles of the burst signal at the output of the picture detector results from signal degradation by noise, cross-modulation with the sound signal, crosstalk with the sweep circuits and residual hum voltage. *Individual cycles of the burst signal can be counted only when the output from a color bar generator is viewed directly, prior to passage through the receiver signal circuits.*

Correct color reproduction depends greatly upon careful alignment of the chroma bandpass amplifier, burst amplifier, quadrature transformer and reactance tube circuits. For this purpose a good (crystal-controlled) color bar generator, wide-band scope, sweep generator with *flat* signal output and accurate (crystal-calibrated) marker generator are essential. The sweep generator must provide extended low-frequency output down to at least 40 kc, and preferably to 15 kc.

Cross-hatch output is a *convenience* in preliminary convergence adjustments. For example, it is somewhat easier to adjust the vertical columns into parallel lines, and the horizontal rows into parallel lines when cross-hatch is used, because incidental displacement of dots may be a confusing situation to the beginner. *Final convergence, however, must be accomplished upon the basis of a dot pattern. Cross-hatch complicates these final adjustments.*

The assumption that highly accurate antenna orientation is required for color reception arises from the fact that ghosts are more objectionable in color than in black-and-white. To the extent that an antenna rotator will minimize ghost signals, it will be found valuable in color TV reception.

The Fallacy

Impedance matching is mostly a joke and does not need to be considered in practical work.

Any antenna that provides good black-and-white reception is OK for color reception.

If there are standing waves on the lead-in, the line can be cut to a critical length to obtain color reception.

The bandwidth of the chroma bandpass amplifier in an (R - Y) (B - Y) receiver can be broadened beyond 0.5 mc to obtain more color detail in the picture.

If the color-phasing control is adjusted correctly for reception on one channel, it will not require readjustment on other channels.

The color picture tube is so sensitive to stray magnetic fields that setup adjustments must always be made if the receiver is moved to another place in the room.

Color TV is developing so fast that test equipment available today may become obsolete tomorrow.

It is so difficult to learn about color TV that it is best to have nothing to do with it.

You can save yourself a lot of headaches by talking down color TV to your customers.

The Facts

Impedance matching is often a serious problem in color reception and a poor match may result in complete loss of color.

Often untrue. If the black-and-white signal is analogous to the bass notes on a piano, the color burst and signal are analogous to the treble notes. Both low and high frequencies must be accommodated.

True for one channel. If more than one color station is to be provided for, this expedient often fails to give satisfactory reception on both channels.

The assumption is true but the adjustment is a compromise of conflicting factors. (See discussion.)

True only in special cases. In general, it is necessary to readjust the color-phasing control when the receiver is switched to another channel.

Sometimes true but not necessarily so. Whether purity is greatly affected depends upon local conditions.

True only for certain special types of instruments. No matter what receiver designs are adopted, 90% of present-day equipment will always be essential.

A very short-sighted attitude. Operators of horseshoeing shops sometimes took a similar attitude toward the automobile back in 1912.

This business practice is aptly termed "knocking yourself out." You might as well spend time each day tossing money out the window.

Discussion

Careless routing of the lead-in, branching of the lead-in to two or more receivers, faulty lightning arresters, a break in one side of the lead-in or faulty input circuits to the front end will often attenuate the color burst to such an extent that color sync drops out and color reproduction cannot be obtained.

Sharply tuned high-gain antennas, such as single-channel multi-element Yagis are least likely to provide good color reception although they are good for black-and-white. Broad-band Yagis, on the other hand, usually provide good color reception. Any antenna with flat response over the received channel, plus a noise-free signal, will deliver a good color picture.

When standing waves are present on the lead-in, causing the length of the line to become a critical factor, the proper procedure is to repair or replace the front end to obtain proper impedance match to the lead-in. Remember that discontinuities in the lead-in installation can cause the line length to become critical, in spite of the fact that the front end may be accurately matched to the line impedance.

When the response of the chroma bandpass amplifier is increased substantially beyond 0.5 mc in an (R - Y) (B - Y) receiver, it will be noted that although chroma detail improves the trailing edges of objects in the picture (during color reception) develop horizontal streaks or spikes. These spurious spikes are due to crosstalk between the Y and chroma channels.

Readjustment is usually required because the antenna may have an upward-sloping characteristic on one channel and a downward-sloping characteristic on another. Discontinuities in the lead-in and impedance mismatch to the tuner often cause a change in the standing-wave pattern on the lead-in from channel to channel. The frequency response of the tuner may also differ from channel to channel. These variations cause a phase shift in the chroma signal, which may require readjustment of the color-phasing control to compensate for the shift.

The amount of variation in stray magnetic fields about a room may be small or large in different situations. Some buildings contain extensive steel construction, while others have practically none. Stray magnetic fields are usually found in the vicinity of iron pipes, conduit, steam radiators and floor furnaces. No hard-and-fast rule can be laid down concerning stray magnetic fields in residences or shops.


The vast majority of test instruments are designed for the NTSC signal, which all receivers process in one manner or another. Accordingly, the wide-band (4-mc) scope, NTSC color bar generator and standard sweep alignment equipment cannot possibly become obsolete. However, the white dot generator could become unnecessary if a one-gun color picture tube is finally perfected.

It is no more difficult for a technician versed in black-and-white TV servicing to become proficient in color service than it was for radio technicians to master the new conceptions presented by black-and-white TV. Some who have cleared the new hurdle say that it is actually easier.

Color TV servicing is a new high-profit market. People expect to pay more for color service. They expect the receivers to require more frequent attention. And surprisingly enough, in the present market, customers are not highly critical of reception quality. The only headache is the time and effort required to learn the new technology. *Don't be a buggy-whip peddler in the automobile era.*

END

AEROVOX MICA CAPACITORS

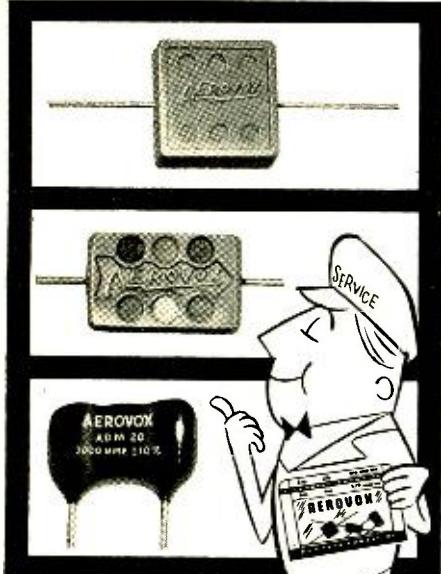

They're all
"TROUBLE-FREE"
CAPACITORS

Smart servicemen refuse to take risks... That's why technicians everywhere use and depend on Aerovox mica capacitors for "trouble-free" operation. Your local Aerovox Distributor stocks the complete line of Aerovox mica capacitors including all the popular types commonly used in service work.

POSTAGE STAMP MICAS

Types 1468LS and 1469 for those general applications are the smallest axial lead micas available. Ideal for critical applications such as horizontal or vertical oscillators. All units are color-coded and stamped with capacity value.

HIGH VOLTAGE MICAS

Types 1468LS-HV and 1467LS-HV are designed especially for TV and low power transmitters and power amplifier applications. These units feature the highest voltages available in these case sizes. Units are marked with capacity and working voltage and are tested at double the rated voltage to insure long-life.

PLASTIC-COATED, QIPPED-MICAS

Types ADM-15, 19 & 20 are superior in many instances to conventional molded units. High operating temperatures, excellent long-life characteristics, ideal for printed-wiring assemblies. Smaller physical sizes with unsurpassed performance and stability features.

AEROVOX
CORPORATION

DISTRIBUTOR DIVISION

NEW BEDFORD MASSACHUSETTS

TELEVISION



By ROBERT B. COOPER, JR.

It took a little while, but it finally happened. F2 skip made the big jump across the United States, bringing what is probably the first reception of this type ever recorded on a transcontinental basis. The period of Jan. 1-9, 1958, saw transcontinental skip between such places as Nova Scotia, Maine, New York, Montreal, Pennsylvania and the western United States—Washington, Oregon and northern California. Although most reception consisted of video only, channel 2, some northern California dxers did manage to sneak in a few minutes of audio at reception peaks.

Eddie Albright of Medford, Ore., reports his first F2 on Jan. 9, between 1100 and 1430 PST of what appeared to be CKCW, Nova Scotia. The audio portion of Eddie's channel 2 was completely obliterated by amateur 6-meter stations in Ohio, New York, Pennsylvania and New England. Some of the longest 6-meter TVI we have heard of!

James Scalvini of Ferndale, Calif., fared somewhat better, noting channel 2 reception like clockwork every day Jan. 1-9, excepting Jan. 2, between 0900 and 1100 PST. Reception would last 15 minutes to over an hour. Video reception was very distorted with multiple ghosting, continually changing phase relationships, all of which made viewing bad.


Going from West Coast observers to Nova Scotia, Canada, dixer Ronald Boyd of Truro, Nova Scotia, has had some very good luck in logging a Russian channel 2 station, BBC channel 3 (on our channel 2) and many tentatively identified stations from Germany, France, Italy and elsewhere. Dx was peaking nicely during the first three days of this year, but dropped off considerably around the middle of January. Such reception is gone for US and Canadian observers until next fall.

From the looks of current sunspot count information, the best F2 TV dxing for the current 11-year sunspot cycle should have occurred during November, 1957, and January, 1958. The peak average spot count appears to have been reached and a gradual descent is expected for the next few years. European reception should be very good again this fall, however. Skip is reported to have reached as high as 70 mc between Europe and parts of the Atlantic coast on two occasions this past fall, the highest values ever recorded (see chart).

Looking from the other end, we have on hand a report from Murilo Rodrigo Marques Lopes, employed at Radio Free

Europe, in Portugal. During the first weeks of November, 1957, Murilo reports strong but badly ghosted reception from what appears to have been WCBS-TV, New York; WGR-TV, Buffalo, and WGBH-TV, Boston, Mass. Dixer Lopes uses a dx setup worthy of the name, with complete switchable gear for all known world standards.

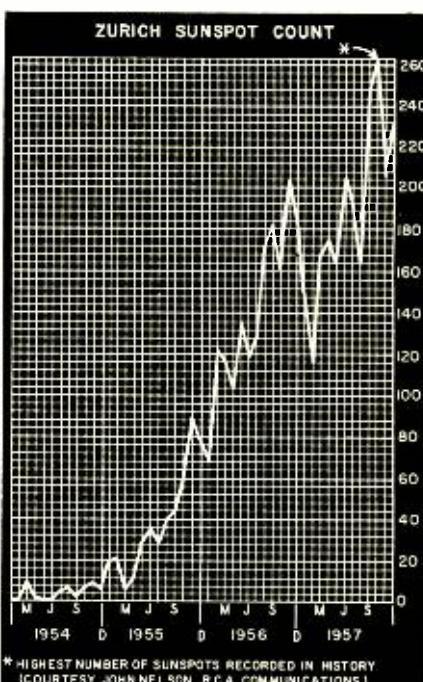During the summer of 1957, frequent daily reception was noted from many European countries (on E skip), lots of good tropes and now some F2. We hope to have Es reports from him this summer for a comparison between Es conditions on the two continents.



* HIGHEST NUMBER OF SUNSPOTS RECORDED IN HISTORY
(COURTESY JOHN NELSON, RCA COMMUNICATIONS.)

The Zurich number is compiled at the Federal Swiss Observatory and is a weighted figure representing the daily average number of sunspots observed each month.

E skip: Winter, 1958

Not to be left out, some E skip was reported during the first two months of this year, occurring for the most part during January. Jan. 3 appears to have been very good throughout the country. Dixer Ronald Boyd notes Jan. 3 as being on a par with anything seen at his location during the summer months. Es got as short as 430 miles for Ron (to Boston) while on the West Coast, KBOI-TV, channel 2, Boise, Idaho, was seen in Medford, Ore., by Eddie Albright, a short 330 miles for E skip. Such short skip is known as an occa-

TELEVISION

sional summer-time phenomenon, and is seldom noted in the winter.

February, 1958, has produced only one reported opening, occurring over a very southerly path from Malibu, Calif., to Harlingen, Tex., and Mexico City, Mexico. Mr. Jack F. Harris reports this skip during the evening of Feb. 8.

Although many brilliant auroral displays have been noted by visual observers, auroral dx on the television channels has been conspicuous by its absence. Again turning to Nova Scotia, Ronald Boyd of Truro notes identification of WSYR-TV, channel 3, Syracuse, N.Y., several times on Dec. 31, actually lasting all day from early morning (0630) till late evening. Another observation of daytime aurora (something which cannot be seen visually but must be tracked by radio reflection) occurred in the early morning of Jan. 1. CBFT, Montreal, was logged several times, with another patch of auroral skip around midnight. WBBM-TV, channel 2, Chicago, popped through on what appears to have been aurora-Es at midnight on the first. This picture was strong, although accompanied by violent fading and bad ghosting. We are still soliciting detailed reports of similar east-west hauls made during aurora.

A brilliant visual display on the evening of Feb. 10 and the morning of the 11th was reported as far south as Miami, Mexico, and Los Angeles. The same disturbance was also active in the southern hemisphere producing an Aurora Australis, seen over wide areas in the South Pacific. Dx reports for this period do not show any TV effects however.

Meteor-scatter dx

Ed Prond, Dolton, Ill., and John Cody, Middleton, Conn., are two dxers who don't quit just because E skip ceases to be a daily occurrence or tropes drop below par. Both managed to add to their station totals during January. Dxer Prond added 4 stations and Cody a whopping 11 new stations, all logged via meteor scatter. If you are new to the dxing game, we suggest you consult back copies of the TV DX column for more information on meteor-scatter dxing.

In our January listing of total number of stations logged by dxers, and the *Over 50 TV DX Club*, some confusion has been reported by readers. When first writing to this column, please include a list of your totals, broken down channel by channel, of every station logged by you in your dxing career. Dates and times of these back loggings are not required, although helpful to us. Your initial report, to which we add your monthly reports, is kept on file. If you keep your monthly reports coming in on schedule, listing all dx seen over the 30-day period, your totals will automatically appear up to date and be complete in the once-a-year-totals listing.

In counting a station which has changed call letters, channels, locations,

etc., we find the following method best. If the station in question changes channels (thus creating a new set of interference conditions), it is permissible to count the station as a new logging. Moving the transmitter location 10 miles or more also allows you to add the station to your log again. But mere changes in call letters, power increases, etc. do not constitute a new station.

Predictions

With the normal E-layer skip occurring in May and June, the chances for high-band burst reception (channels 7-13) is greatly increased when we have a strong E-skip opening coinciding with a strong meteor shower. With skip running as high as channel 6 (88 mc) over a 1,200-mile path, a meteor shower entering the E layer during the skip session may push burst reception into channels 7-13 with amazing frequency.

Before this reaches the newsstands, E-layer skip should be occurring on a fairly regular basis, providing dxers with frequent reception of low-band channels 500-1,500 miles distant. During the first two weeks of May, E skip is likely to occur from 1600-2100 local time. Moving on toward the end of May, Es follows no set pattern, occurring most anytime during the day and night. Watch vacant channels or those with fringe reception for signs of stations or interference from antenna headings not normally productive of a station. Reception via multihop E skip should be possible to Venezuela, Puerto Rico and Brazil during the second and third weeks of May, around 1700-2000 local time (channels 2-4). June and E skip are almost synonymous. Any time, any direction, any of the low-band channels the rule, not the exception.

Ground-wave reception increases greatly as the warmer months approach. With temperature inversions occurring almost daily, in the early morning and around sundown, general reception will probably increase 100 miles on low-band vhf, 150 miles on high-band vhf and 50-100 miles on uhf. Extra special long-range ground-wave conditions are usually signaled by approaching warm, moist fronts, moving eastward following a high-pressure area of dry air. Early morning and late evening are again the best periods of the day to try your hand at unusual extended ground-wave reception. East-west paths are normally most productive.

Report forms

This column, through RADIO-ELECTRONICS Magazine, provides free TV dx report forms or logging sheets to any observers requesting them. Your use of these forms will insure that we get all the essential information for each of your dx loggings. Simply address a 2-cent postcard to TV Dx Column, RADIO-ELECTRONICS Magazine, 154 W. 14th St., New York 11, N.Y. New report forms are sent upon receipt of completed monthly sets from you, the dxer.

THE PAUSE THAT PROTECTS YOUR RECORDS



exclusive feature of GLASER-STEERS GS-77 high fidelity changer

Now, the original brilliant performance of your records can be preserved for hundreds of additional plays. This requires an automatic record changer that handles records with a gentleness not yet achieved by any other changer on the market. The changer that accomplishes this... the new GLASER-STEERS GS-77.

TURNTABLE PAUSE is one dramatic reason why the GS-77 handles records more gently than any other automatic record playing mechanism. During the record-change cycle, the GS-77 turntable comes to a complete halt, and doesn't resume motion until the stylus has come to rest in the run-in groove of the next record. This completely eliminates the grinding action which occurs where records are dropped onto a moving turntable or disc.

The GS-77 TONE ARM affords further protection. Improved mass distribution and low pivot friction have so minimized arm resonance and tracking error that these flagrant causes of groove and stylus wear are now virtually eliminated. In addition, the arm has been so designed that stylus pressure between the first and top records in a stack does not vary more than 0.9 gram.

SPEEDMINDER goes still further — for by simply setting the appropriate stylus into play position, the GS-77 automatically plays at the correct record speed, and in the micro-groove position, intermixes 33½ and 45 rpm records regardless of their sequence in the stack.

The GS-77 is the perfect high fidelity record changer. It combines traditional turntable quality with modern automatic conveniences — and it does this with incredible mechanical simplicity. No wonder

... audiophiles are switching to the new
GLASER-STEERS GS-77
\$59.50 less cartridge and base
(base illustrated, \$9.60)

RE-6
GLASER-STEERS CORP.
20 Main Street, Belleville 9, N.J.

Please send me complete information on the
GS-77.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

TV Service
Clinic

conducted by
By ROBERT G. MIDDLETON
TELEVISION CONSULTANT

We are getting many requests for data on dc restorers and how to add one to a TV receiver. Because of the interest shown in this circuit, we are presenting the basic facts here.

There are two types of TV receivers. One has dc coupling from the picture detector to the picture tube. This type of receiver does not use a dc restorer. Dc restoration is inherent in dc coupling. Most receivers fall into the second category and are ac-coupled from the picture detector to the picture tube. These receivers require dc restorers for good reproduction of dark night and bright daylight scenes. Without dc restoration, night scenes appear too bright and day scenes too dark. Moreover, dark lettering on white backgrounds and light lettering on dark backgrounds appear with severe background distortion and smear.

A dc restorer clamps the horizontal sync tips to a preset level determined by the setting of the brightness control and reinserts the dc component of the composite video signal. It also does much more than this. It restores all ac frequencies in the video signal from dc to 15,750 cycles.

Hence, the name dc restorer is an ultra-conservative term. It is like saying that a rich man smokes 50-cent cigars. He also drives a Cadillac and drinks vintage wines. A better name for a dc restorer would be a low-frequency recovery device. Note that dc is a very low frequency (zero frequency, to be exact). Hence, if we call a dc restorer a low-frequency recovery device, we include its function of reinserting the dc component—moreover, we recognize the ac recovery function of this modestly named device.

A basic dc restorer is arranged as shown in Fig. 1. It holds the horizontal sync tips at some dc voltage value. It does this on the basis of the low forward resistance of the restorer diode, which conducts on the sync tips. The restorer charges capacitor C, which then discharges slowly. So, the capacitor always shows a charge which is practically the same as the horizontal sync voltage during vertical retrace time. At this time, the peak-to-peak

voltage of the sync pulses gives the actual dc level. Because the time constant of the R-C circuit is long, the horizontal sync does not "slump" or "grow" between vertical retrace intervals. This is clamp action. A "slump" or a "growth" in sync-tip level corresponds to distortion frequencies from zero to 15,750 cycles. Clamping eliminates this distortion.

The 100,000-ohm resistor in Fig. 1 reduces the restorer diode's load on the video signal lead. It works because it passes the 15,750-cycle sync pulses. The 100,000-ohm resistor works into the input capacitance of the diode. Accordingly, it gives a low-pass filter action where needed. The high video frequencies are not found across the diode. The restorer operates only on low video frequencies.

You will find elaborations of the Fig. 1 configuration, depending upon the

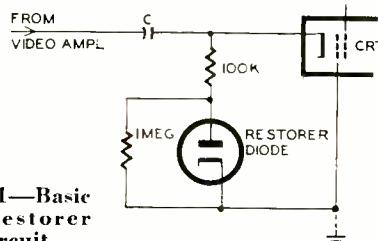


Fig. 1—Basic dc restorer circuit.

details of the picture tube input circuit. However, the basic principle is always as shown in Fig. 1. If you will take the time to understand its action, you will understand all dc restorer circuits.

Mixed-up colors

On an RCA CT-100 color receiver, large areas of red show as green, though small red objects appear OK. Afc and matrix are adjusted properly. Any suggestions will be appreciated.—J. H. C., Willowdale, Ont., Canada.

Your report does not describe the symptoms in detail. However, it would

seem that the picture tube is not tracking. Tracking means the adjustment of screen and background controls so that a neutral gray screen is maintained over the normal signal range of a black-and-white picture. A gray screen must be maintained at any usable settings of the brightness and contrast controls.

Here are the important rules:

1. To correct a highlight tint, adjust the blue and green background controls.
2. To correct a lowlight tint, adjust the blue and green screen controls.

Two-set coupling

Two receivers are being operated from a coupler which seems to be defective. Horizontal bar interference appears on one of the receivers.—R. N. S., Crystal City, Mo.

If a receiver radiates considerably, the coupler must have sufficient attenu-

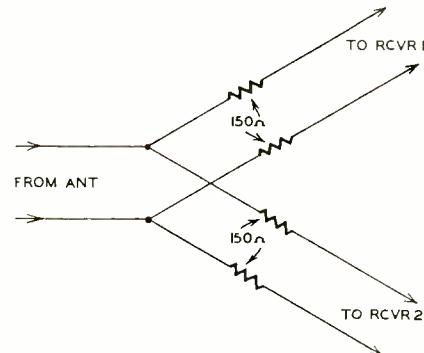


Fig. 2—This type of 2-set coupling reduces interference caused by radiation.

ation to kill the interference. A coupler made up from four 150-ohm resistors as shown in Fig. 2 is sometimes sufficient. However, if you still have noticeable interference, you must add H-pads in the receivers' lead-ins as in Fig. 3.

Vertical roll

A Zenith 23G22 has a tendency to roll vertically. I have replaced numerous components in the vertical oscillator and sync section, with no effect. The vertical hold is very touchy. What can you suggest?—B. S., Baltimore, Md.

Your report does not state whether the picture rolls up or down or both ways at different times. If the picture rolls down, the trouble is in the vertical oscillator. But, if the picture rolls up, the trouble can be in either the integrator section or the oscillator. When the oscillator drifts too far off frequency, even a strong vertical sync pulse cannot lock the sweep. On the other hand, a weak vertical sync pulse will not hold sync when the oscillator drifts slightly. This is a job for a scope. Check the vertical sync waveforms for

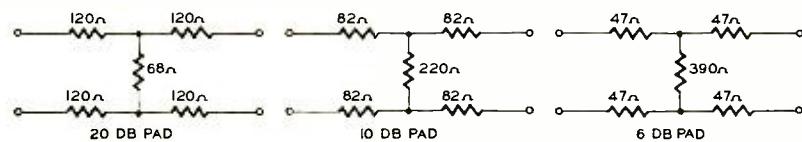


Fig. 3—H pads may be needed when coupling 2 sets to a single TV antenna to attenuate interference-causing radiation.

TELEVISION

peak-to-peak voltage. If these are correct, investigate the resistors and capacitors in the vertical-oscillator section—particularly those in the grid circuit.

Snowy picture

In a Philco 22B4002, code 140 TV receiver the picture is snowy on all channels. The antenna checks good, the tuner has been cleaned and appears to be normal, as well as the other stages in the receiver. Can you suggest the cause of this trouble?—D. S., Jr., College Park, Md.

There is a point in the early signal circuits at which the incoming signal is greatly attenuated and falls down to the noise level. Once this happens, subsequent amplification is useless, and all pictures become snowy. It is fairly easy to localize this type of trouble by pulling tubes and watching the picture. Start by tuning the receiver to a vacant channel. Turn up the contrast and volume controls to place considerable snow in the raster and noise in the sound. Then disconnect the lead-in. If there is little or no change in the noise level, the trouble is in the antenna. Try a pair of rabbit ears, or other antenna, for comparison. If there is a very noticeable drop in noise, the antenna is OK. Leave the antenna disconnected for the next tests. Pull the mixer. If there is a big drop in noise, the mixer is OK and the trouble is in the rf amplifier. But if there is little or no change in noise level, there is trouble in the mixer circuit. We know the oscillator is OK because you can get pictures. In exceptional cases, the trouble will be found in the first if amplifier stage.

Vertical instability

An Admiral 20X5B has intermittent vertical instability caused by a slight hum in the video which is not noticeable in the sound. Hum bars are noticeable only when the picture is momentarily off and carrier is on. Horizontal pulling varies from time to time. A scope shows 60-cycle hum as far back as the second if. I suspected that the lead-in cable might be picking up some ac, but another receiver works OK on the same cable. Overriding the age bias with battery voltage does not help. I have checked the power supply. I'm about out of ideas on this one.—H. E. S., Bryan, Tex.

Since the hum is at 60 cycles, we can go immediately to the heater system. This is a job which should be done with a scope at the output of the video amplifier, to check the hum level while unplugging tubes right down the line from the front end. This will probably localize the trouble and simplify location of the faulty circuit. However, if you can unplug all the tubes and still have the hum, the heater voltage is getting into the signal through a leak. It could be a leak across a socket from heater to grid. This can be localized by disconnecting the heater line step by step, leaving the scope at the output of the video amplifier.

END

FREE!

This Big Valuable Book Given
Just For Examining
Coyne's New 7-Volume Set

Applied Practical Radio-Television

ON 7 DAY
FREE TRIAL!

Yes, you get our big Diagrams book, absolutely FREE! It's like a valuable road-map that shows you the way to easier Radio-TV repair. Needed by every serviceman. Complete 11 x 22" Schematic Diagrams on many radio and television sets help cut your servicing time. Includes simple instructions on how to use the diagrams and picture patterns. This helpful book is yours FREE for asking to see Coyne's great new 7-book set, "Applied Practical Radio-Television!"

At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing!

Coyne's great new 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that is easy to understand, you'll find everything you want in volumes 1 to 5 which contain over 5000 practical facts and data. They cover every step from fundamentals to installing, servicing and trouble-shooting, all types of radio and TV sets. Includes COLOR TV, UHF and TRANSISTORS. All this plus Coyne's New TECHNICAL DICTIONARY with over 4000 definitions of latest terms, symbols and abbreviations.

EXTRA! 868-Page TV CYCLOPEDIA Included

For speedy on-the-job use, you get Vol. 6—famous Coyne CYCLOPEDIA. Quick answers to problems on servicing, alignment, installation in ABC order. **NEW!** Each book in the set has bright, modern, washable covers! Use this 7-volume TV-RADIO LIBRARY FREE for 7 days; get Servicing Book FREE!

SEND NO MONEY

Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$24.50 plus postage is paid. (Cash price \$22.50.) Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, the book of TV-Radio Patterns and Diagrams is yours FREE to keep! Offer limited. Act NOW!

COYNE ELECTRICAL SCHOOL
500 So. Paulina Street
Dept. 68-TI, Chicago 12, Ill.

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL, Dept. 68-TI
500 S. Paulina St., Chicago 12, Ill.
YES! Send 7-volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name _____ Age _____
Address _____ Zone _____ State _____
City _____
Where Employed _____
 Check here if you want library sent COD. You pay postman \$2.95 plus COD postage on delivery. 7-day money-back guarantee.

SQUARE-WAVE GENERATOR

Simple 2-tube instrument delivers square waves at all frequencies between 10 and 180,000 cycles

By T. W. DRESSER

THE quickest and easiest way to check the performance of any amplifier (video, scope or audio) is by squarewave analysis. The method is rapidly increasing in popularity, but has been held back by the relatively high price of a suitable generator.

While circuits for home-built instruments have appeared, they usually do not extend beyond about 20 kc, limiting their use to audio amplifiers. For scope or video amplifiers, a range extending to 100 kc or more is a must.

This inexpensive unit will cover from 10 or 12 cycles up to 180 kc and can be built by the average technician. It has four ranges: 12-180 cycles, 140-1,800 cycles, 1.4-18 kc, and 14-180 kc. The generated square wave has a rise time of slightly over 0.5 μ sec and a 12-volt peak-to-peak amplitude.

The circuit (Fig. 1) is essentially a cathode-coupled multivibrator. Components were chosen with a view to limiting the amplitude of the plate waveform. A dual triode is used rather

Take extra care while wiring and see that all capacitors are kept well away from the chassis to keep stray capacitance down. Leads should be as short as possible and well away from the chassis. Mount the time-constant capacitors (C1, C2, C3, C4) directly on switch S1. Use the smallest-size capacitors available and on no account use metal-cased units. The potentiometers are carbon or composition types.

When wiring is finished and the circuit has been checked for errors, you are ready to check the generator. Connect its output to the vertical input terminals of a good oscilloscope—one that has reasonably flat response at high frequencies and a fast rise time—otherwise it will be impossible to make accurate tests.

Switch on the generator and scope. Now vary the sweep until only 2 or 3 cycles are visible on the screen. Then adjust R1 until a balanced trace (see Fig. 2) is obtained. Then check at with the generator set at 50 cycles, 10 kc and 100 kc. At these points the square wave should be a perfect figure without tilt, rounding or overshoots.

In use, the generator's output is connected to the input of the amplifier under test and a scope is placed across the amplifier's output. Departures from a square wave at the output are noted and the cause found and repaired.

In video amplifiers, if there is a falloff of lower frequencies or phase

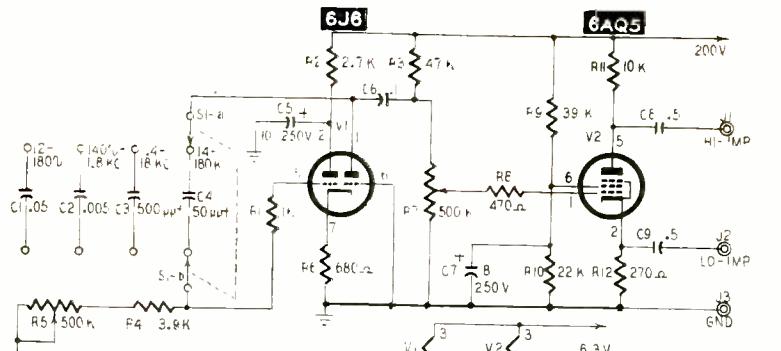


Fig. 1—Generator circuit. An external power supply is needed.

R1—1,000 ohms
R2—2,700 ohms
R3—47,000 ohms
R4—3,900 ohms
R5—7-pot, 500,000 ohms
R6—680 ohms
R8—470 ohms
R9—39,000 ohms
R10—22,000 ohms
R11—10,000 ohms
R12—270 ohms
All resistors $\frac{1}{2}$ watt 10%
C1—.05 μ f

C2—.005 μ f
C3—.500 μ f
C4—.50 μ f
C5—10 μ f, 250 volts, electrolytic
C6—0.1 μ f
C7—8 μ f, 250 volts, electrolytic
C8, 9—0.5 μ f
All capacitors 600 volts unless noted
J1, 2, 3—banana jacks
S1—2-pole 4-position rotary
V1—6J6
V2—6AQ5
Miscellaneous hardware

Square-wave generators can be divided into two types—those using a sine-wave generator followed by a clipper and amplifier, and the multivibrator type working as a relaxation oscillator. Any form of square-wave generator should have a balanced waveform—duration of pulses equal to time between pulses—so it can be used for beam switching on oscilloscopes and other purposes. Both types of generators will provide this, but a complicated circuit or carefully matched time-constant components are required.

than two separate tubes to obtain better symmetry of characteristics. The multivibrator's output is coupled to a 6AQ5 amplifier which provides both high- and low-impedance outputs.

I used a $10 \times 5 \times 2$ -inch chassis, but there is no reason why the unit could not be built into a small metal cabinet. A power supply delivering 200 volts dc at 50 ma and 6.3 volts at 2 amps is required. Calibration depends to some extent on the B-voltage and the unit's frequency range may vary if the B-supply voltage is different.

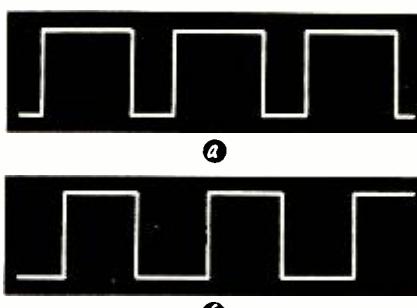


Fig. 2—Waveshapes at generator's output: a—unbalanced wave; b—balanced wave.

It's Newly Revised And Brought Up-To-Date!

Send for this **FREE** Booklet today!

- See what can be yours in the rapidly expanding field of . . .

ELECTRONICS

including: GUIDED MISSILES • RADAR

- INSTRUMENTATION • COMPUTERS
- AUTOMATION • ASTRONAUTICS
- SERVOMECHANISMS
- AERONAUTICAL ELECTRONICS
- TELEMETERING • COMMUNICATIONS
- MANUFACTURING • TELEVISION
- BROADCASTING

*Electronics
offers you a*


- BETTER JOB
- BETTER PAY
- PROMOTION
- GREATER SECURITY
- GREATER CONFIDENCE
- BETTER
LIVING FOR
YOU AND
YOUR FAMILY

All these benefits can be yours if you act now! Take that first step this minute—No obligation whatsoever! Write

**CAPITOL
RADIO
ENGINEERING
INSTITUTE**

Dept. 146-Y, 3224-16th St. N. W.
Washington 10, D.C.

JUNE, 1958

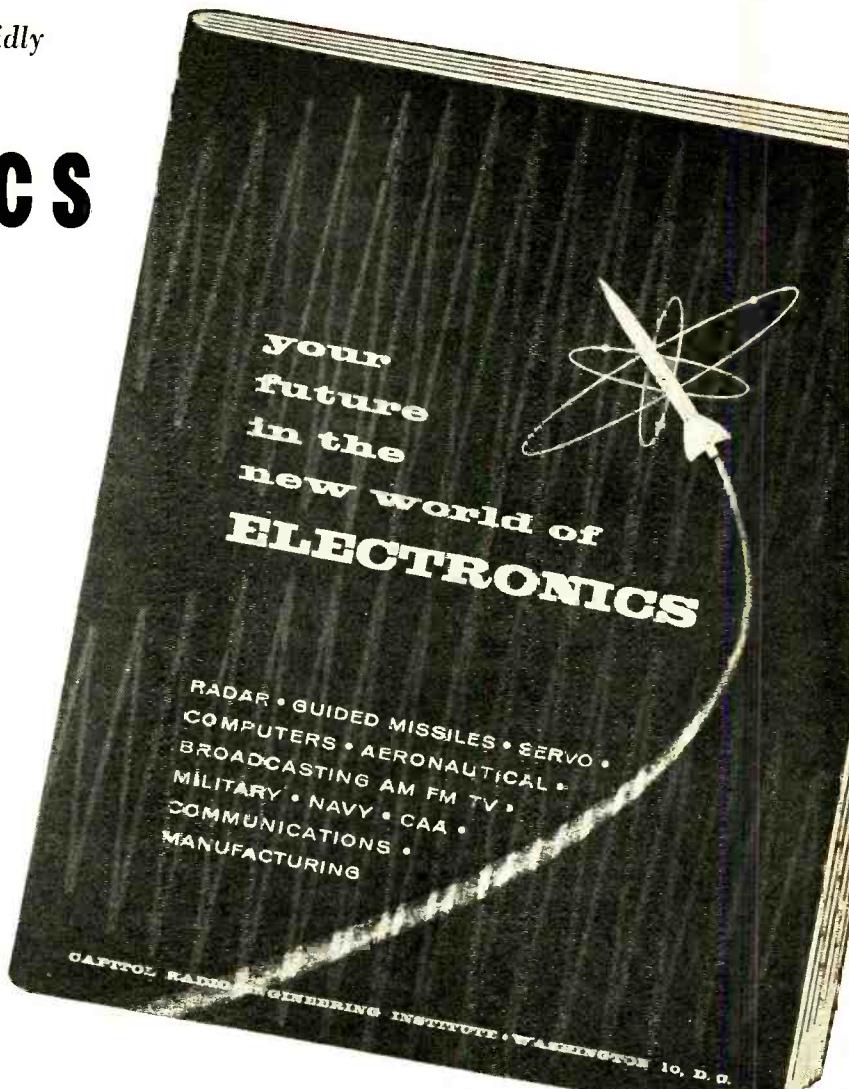

TAKE A MINUTE TO MAIL THIS COUPON FOR FREE BOOKLET!

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula—Founded 1927
Dept. 146-Y 3224 16th St., N.W., Washington 10, D.C.

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronic Engineering Technology.

HI

- CHECK Radar, Servo and Computer Engineering Technology
FIELD OF Electronic Engineering Technology
GREATEST Broadcast (AM, FM, TV) Engineering Technology
INTEREST Television Engineering Technology
 Aeronautical Electronic Engineering Technology

Name..... Age.....

Street.....

City..... Zone..... State.....

Check: Home Study Residence School Korean Veteran

NOT FOR BEGINNERS.

If you have had a high school education, and experience in electronics—and realize the need of high-level technical knowledge to make good in the better electronic jobs—you can qualify for CREI home study training. (Electronic experience is not required for admission to CREI Residence School).

Please fill in the following information:


EMPLOYED BY _____

TYPE OF PRESENT WORK _____

EDUCATION: YEARS HIGH SCHOOL _____

YEARS COLLEGE _____

ELECTRONICS EXPERIENCE _____

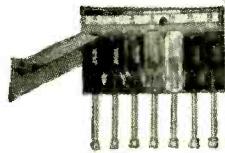

... Superbly made and designed for Radio, T.V. and Electronic Technicians. *See your Distributor* ... only one quality ... the finest — whether you choose individual items or the handy kits ...

Use the Tools the Professionals use!



XCELITE, INCORPORATED
ORCHARD PARK, NEW YORK
Canada: Charles W. Pointon, Ltd., Toronto

XCELITE
Quality Hand Tools
PREFERRED BY THE EXPERTS

Another Sencore Time-Saver

NEW IMPROVED SENCORE LC3 Leakage Checker

Check these outstanding New Features

Now — For the first time ...

Checks 130 different tube types — more than any other "grid circuit" type checker. Includes UHF and latest type tubes.

Checks picture tubes without removing tube from cabinet or chassis.

New Roll Chart prevents obsolescence — just dial the tube type and save time. Chart is easily replaced at no extra cost.

Dynamic Filament checks including heater to cathode leakage & shorts — no need for a second filament tester.

Two spare preheating sockets to cut down testing time.

Capacitor checks simplified.

The LC3 provides all these new improved features in addition to those employed in earlier leakage or "grid circuit" testers. A must for any TV service technician.

\$28.95
DEALER NET
Really Whips Tough Dogs

CUT OUT THIS AD NOW FOR FURTHER INFORMATION

LEKTRON
INSTRUMENTS CORP.
171 Official Rd • Addison, Ill.

BIGGEST BUYS OF '58!
Regency
ALL-TRANSISTOR
Vest-Pocket RADIO READY TO PLAY!
\$14.95 Including 1000-hour batteries and phone!

Lektron scoops the field with the "hottest" pocket transistor radio since the advent of the transistor! Designed and built by Regency, one of America's great names in radio. Uses an exclusive circuit with RF, DET and AMP stages. SMALLER THAN A PACK OF CIGARETTES — only 3 x 2 x 1". NO EXTERNAL MEXXANOID CABLE AND NO HANGING WIRES! Amazing sensitivity, volume and selectivity. Attractively designed two-tone styrene case. Variable tuning covers 540 to 1500 kc. READY TO PLAY when you receive it! 1000-hour batteries and ultra-sensitive phone included in this fabulously low price! Gift packed. Wt. 1 oz. Postpaid.

SATISFACTION GUARANTEED!
20,000 OHMS/VOLT MULTI-TESTER
LOWEST PRICE IN U.S.A.! **\$17.99**

Ready to go! 5 1/4 x 3 5/8 x 2 1/8". Test leads incl. Ranges: AC 0 to 1200, 600, 120, 30, 6, 20K ohms/volt DC, 10K ohms/volt AC; DC milliamps: 0 to 300, 120, 30, 10, 3, 1 milliamp; 0 to 1000 ohms; 0 to 100K ohms; 1 megohm; Diodes: 20 to -17; CAPACITANCE: .00005 to .01; INDUCTANCE: 30 to 3,000 henrys. Ship wt. 5 lbs. Please include postage with this item; excess returned.

WRITE FOR NEW SUMMER BARGAIN FLYER!

LEKTRON

131 EVERETT AVE. CHELSEA 50, MASS.

TEST INSTRUMENTS

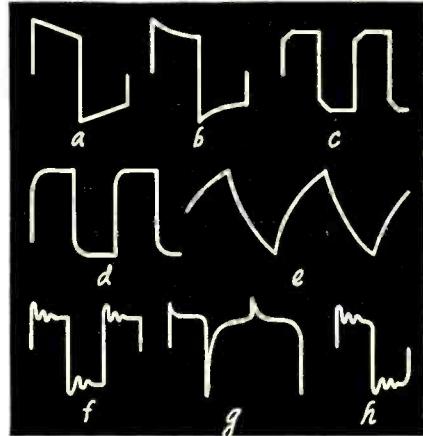


Fig. 3—Waveforms observed in amplifier troubleshooting: a, b, c—indicate a falloff of lower frequencies or phase shift with regard to higher frequencies; d—falloff in frequency response above 800 kc; e—falloff in frequency response around 200 kc; f, g, h—resonant peaks caused by misadjusted peaking coil, high wiring inductance or high-frequency leakage.

shift with regard to higher harmonics, the top of the wave, instead of being flat, will lean over and may even be concave as in Figs. 3-a, -b and -c. Fig. 3-d indicates a falloff in frequency response above 800 cycles and Fig. 3-e shows a similar condition at a lower frequency, around 200 cycles.

Resonant peaks result in the patterns shown in Figs. 3-f, -g and -h. This frequently indicates a misadjusted peaking coil, high wiring inductances or high-frequency leakages through gain controls or faulty capacitors.

While the unit is small and easy to build, don't think of it as a toy or something only for amateurs. It is intended for serious work and is probably as good for this purpose as many higher-priced more complicated equipment. It will have many uses in checking video and scope amplifiers and will prove just as valuable when that defective hi-fi amplifier comes into the shop.

END

50 Years Ago

In Gernsback Publications

HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.


In June, 1908, *Modern Electrics*
Modern Electric Tubes, by H. Gernsback.

The Poulsen Wireless Station at Lyngby.

A Silicon Detector, by A. C. Austin, Jr.
The Construction of a Tuning Coil, by A. C. Austin, Jr.

An Unusual Oscillation Detector, by John L. Hogan, Jr.

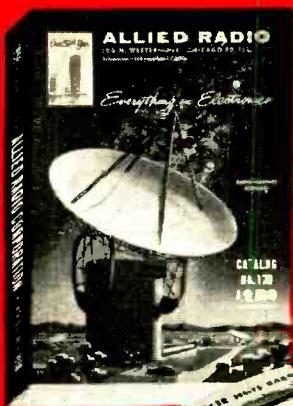Typesetting By Wireless, by the Paris Correspondent.



See The Best Before You Build!

SEE THE AMAZING

ALLIED knight-kits

IN THE WORLD'S LEADING ELECTRONIC SUPPLY CATALOG



FREE! send for it now

THERE'S A knight-kit FOR EVERY NEED

- LOWEST COST
- EASIEST TO BUILD
- LATEST DESIGN
- FINEST QUALITY

Do-It-Yourself: SAVE UP TO 50%



**knight-kits:
BEST BUY
HI-FI
KITS**

- 18-Watt Amplifier
- 30-Watt Amplifier
- 25-Watt Amplifier
- 20-Watt Amplifier
- 10-Watt Amplifier
- FM-AM Tuner
- FM Tuner
- Preamplifier
- 2-Way Speaker System
- 3-Way Speaker System




**knight-kits:
BEST BUY
HOBBY
KITS**

- 'Space-Spanner' Radio
- 'Ocean-Hopper' Radio
- 'Ranger' AC-DC Radio
- 2-Way Intercom
- Electronic Lab Kits
- Crystal Set
- Wireless Broadcaster
- 5-Transistor Portable
- 2-Transistor Pocket Radio
- Transistor Lab Kit
- 1-Transistor Radio
- Photoelectronic System
- Electronic Photoflash
- Phono Oscillator



**knight-kits:
BEST BUY
INSTRUMENT
KITS**

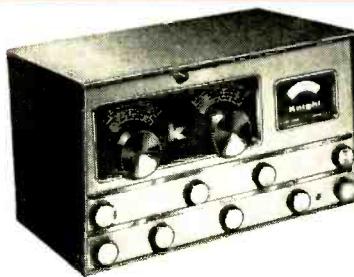- Capacitor Checker
- R/C Tester
- Transistor Checker
- Flyback Checker
- Battery Eliminator
- 5" Oscilloscopes
- Vacuum Tube Voltmeter
- Tube Tester
- VOM's
- RF Signal Generator
- Signal Tracer
- Audio Generator
- Sweep Generator
- R/C Substitution Boxes
- Voltage Calibrator



**knight-kits:
BEST BUY
AMATEUR
KITS**

- All-Band Ham Receiver
- Self-Powered VFO
- 100 kc Crystal Calibrator
- 50-Watt Transmitter
- RF "Z" Bridge
- Code Practice Oscillator

ALLIED RADIO

404-PAGE ALLIED CATALOG

FREE!

Send for this 404-page Allied Catalog featuring the complete ALLIED KNIGHT-KIT line, as well as the world's largest stocks of everything in Electronics. You'll want this valuable, money-saving Buying Guide.

WRITE FOR YOUR **FREE** COPY TODAY



ALLIED RADIO CORP., Dept. 122-F8
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1958 ALLIED 404-Page Catalog

Name _____

Address _____

City _____ Zone _____ State _____

SPOT-O-MATIC

With this signal generator, a flick of a switch spots the frequency you want—between 15 and 100,000 cycles

By I. QUEEN

EDITORIAL ASSOCIATE

THE R-C type of audio oscillator is well adapted to home construction because it is easily assembled and calibrated. This one has novel features not found in previous designs. Using only two tubes and no variable capacitors, it is easy to construct and takes up little space. It covers 15 cycles to 100 kc with plenty of output and low distortion. The most important feature is spot tuning, which makes many fixed frequencies available at the throw of one or more switches.

Fig. 1 is the complete circuit. V2 feeds back voltage to V1's grid through an R-C network. Oscillations occur at the frequency of the network. V2 is a cathode follower capable of high output at a low output impedance. Note how direct coupling eliminates components and, of course, improves frequency

response. V2's cathode is well above ground, but so is its grid and there is no bias problem. The power supply is conventional and needs no description. It is a full-wave type that delivers about 135 volts at 20 ma to the oscillator.

From TV receivers we know that switch tuning is quick and convenient and that it eliminates human error. If you have occasion to use several frequencies during a test run or hi-fi measurement, you will appreciate this feature. It means that you can switch from one frequency to others and always return to the precise value you originally had.

There are three frequency switches, for 15, 25 and 60 cycles. Fortunately we are not limited to a single frequency per switch. Actually, combinations of the three may be switched in, the

resultant being the sum frequency. For example, operating the first two switches (15 and 25 cycles) gives a 40-cycle output. With the three basic frequencies there are seven spot frequencies per decade. They are 15, 25, 40, 60, 75, 85 and 100 cycles, making a good distribution throughout the decade. The oscillator has a multiplying switch for $\times 1$, $\times 10$, $\times 100$ and $\times 1,000$; so you have a total of 28 spot frequencies, the highest being 100 kilocycles.

The frequency-coupling network is a bridged-T (see Fig. 2). Bridged-T oscillators generally have lower distortion than those based on the Wien bridge. Also, hum is lower because there is a common ground for both input and output.

Capacitors C_a and C_b control the

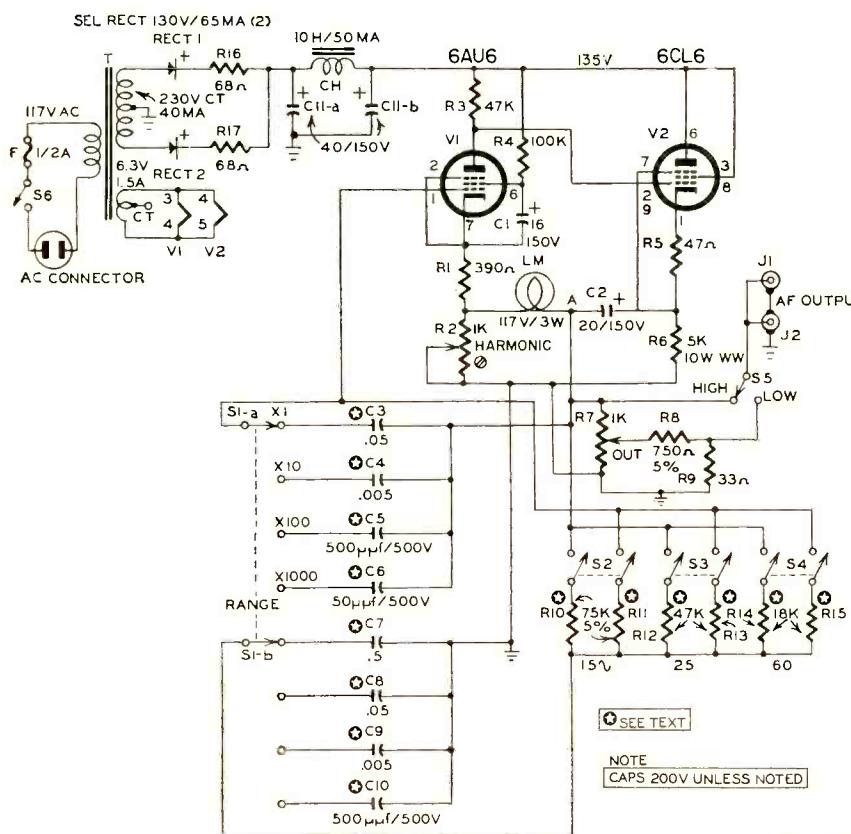


Fig. 1—Circuit of the two-tube Spot-O-Matic.

R1—390 ohms
 R2—pot, 1,000 ohms, screwdriver adjust
 R3—47,000 ohms
 R4—100,000 ohms
 R5—47 ohms
 R6—5,000 ohms, 10 watts WW
 R7—pot, 1,000 ohms
 R8—750 ohms, 5%
 R9—33 ohms
 R10, 11—750 ohms, 5%
 R12, 13—47,000 ohms
 R14, 15—18,000 ohms
 R16, 17—68 ohms
 All resistors 1/2-watt 10% unless noted
 C1—16 μ F, 150 volts, electrolytic
 C2—20 μ F, 150 volts, electrolytic
 C3, 8—.005 μ F, paper
 C4, 9—.005 μ F, paper
 C5, 10—500 μ F, mica, 500 v
 C6—50 μ F, mica, 500 v
 C7—.5 μ F, paper
 C11—40—40 μ F, 150 volts, electrolytic
 All capacitors 200 volts unless noted
 CH—filter choke, 10 h, 50 ma, 500 ohms (Triad C-3X or equivalent)
 F—1/2-amp fuse
 J1, 2—phono jacks
 RECT 1, 2—selenium rectifiers, 65 ma, 130 volts (Federal 1002 or equivalent)
 S1—2-pole 5-position rotary (1 position unused) (Centralab PA-1003 or equivalent)
 S2, 3, 4—dpdt toggle
 S5, 6—spst toggle
 T—power transformer: primary, 117 volts; secondary, 230 volts ct, 40 ma; 6.3 volts, 1.5 amps (Triad R-29A or equivalent)
 V1—6AU6
 V2—6CL6
 LM—3-watt 117-volt candelabra screw-base lamp (Allied Radio 52E354, GE type 3S6 or equivalent)
 Socket, candelabra screw
 Socket, 7-pin miniature with shield
 Socket, 7-pin miniature with shield
 Chassis, 2 x 7 x 7 inches
 Fuse holder
 Miscellaneous hardware

CHART OF CAPACITANCES USED BY THE AUTHOR

Capacitor	Value and connection
C3	.05 μf
C4	.022 μf in series with .005 μf
C5	500 μf
C6	47 μf
C7	0.5 μf
C8	.05 μf in parallel with .001 μf
C9	.005 μf
C10	500 μf in parallel with 36 μf mica trimmer adjusted for optimum

frequency range which may be $\times 1$, $\times 10$, $\times 100$ or $\times 1,000$. C_b is always 10 times larger than the corresponding C_a . When the switch is thrown to the next higher range, the respective capacitors are one-tenth the value of those for the previous range. For any given range, resistors R_a and R_b are equal, and they select the actual frequency.

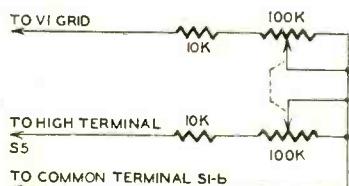


Fig. 2—The basic bridged-T frequency-determining R-C network.

A lower resistance means higher frequency. For the three spot frequencies we need three pairs of identical resistors.

Building the oscillator

The instrument is built into a 7 x 7 x 2-inch aluminum chassis. There is plenty of space for all components without crowding. The HARMONIC control is above the chassis, all others are on the front panel. The output jacks are mounted on the right of the chassis.


First mount the tubes, HARMONIC control, transformers, etc. Then assemble the power supply and check it.

Now you are ready for the frequency networks. Since the frequencies are fixed, it pays to spend a lot of time here to obtain accuracy. Commercial instruments are often rated at 5% maximum error but, if you have the time and patience, you can do much better. The plan is to go through your resistor and capacitor supplies and select the correct values by actual frequency measurement. The values designated on the schematic will provide the required frequencies quite closely, but if you have access to an oscilloscope, you can select components for higher precision.


Few experimenters have access to a good capacitance bridge, and it is not needed. Use paper or mica capacitors throughout, not ceramic or electrolytic. The resistor pairs should be checked with an ohmmeter.

For the $\times 1$ range, you need a 0.5- and a .05- μf capacitor. (At this stage of the game it is wise to connect all components with clip leads, leaving the soldering until you have made the final selection.)

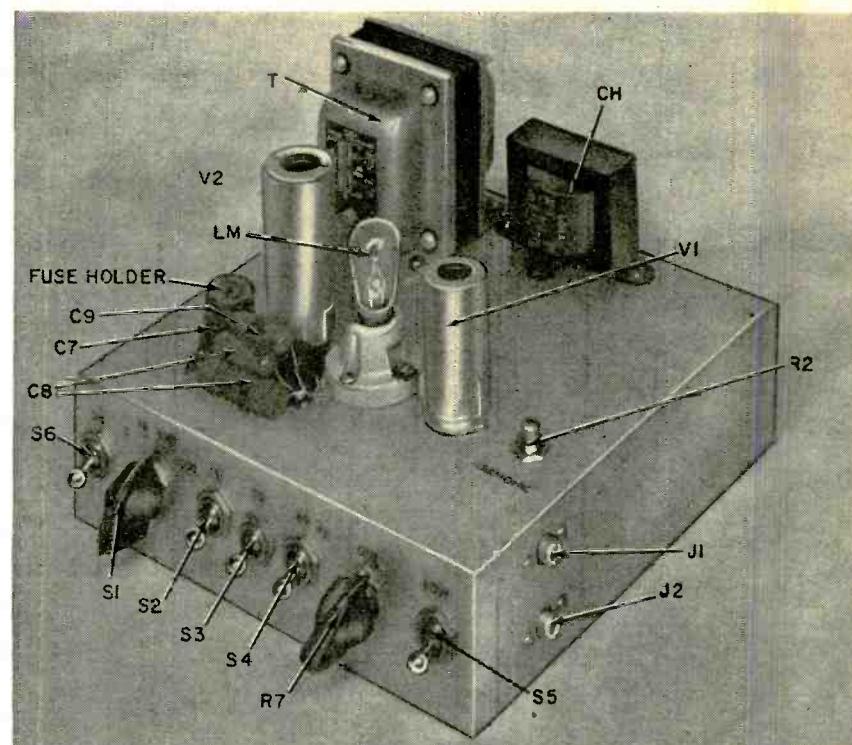Using your ohmmeter, select a matched pair of resistors of approx-



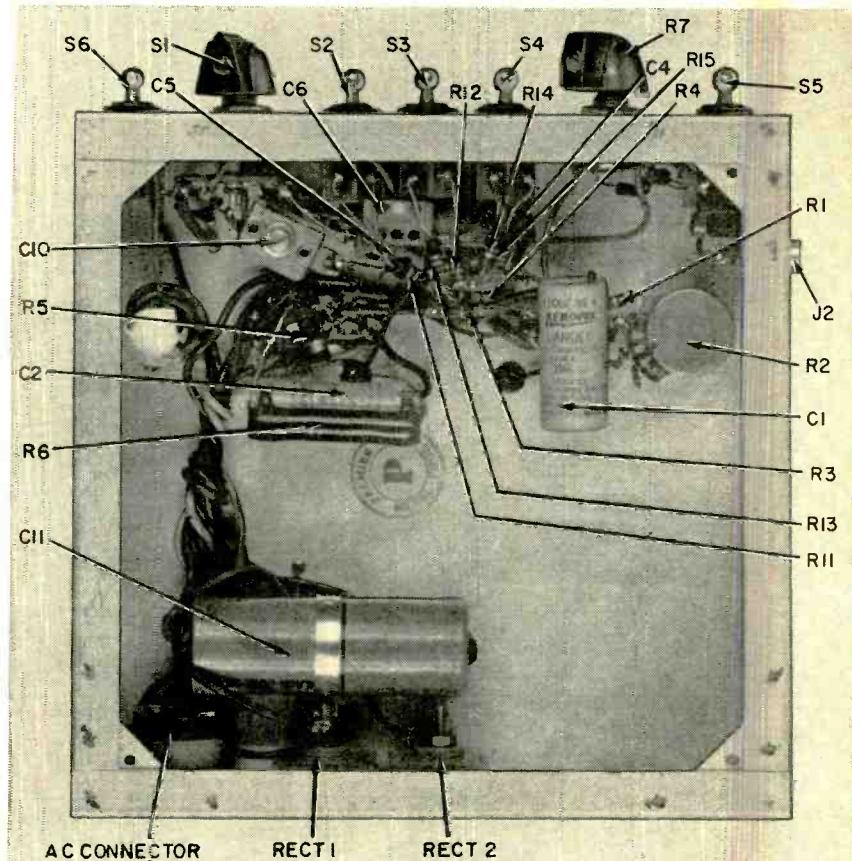All the Spot-O-Matic controls but one are mounted on the instrument's front panel.



imately 18,000 ohms. Upon completing the network and connecting it to the oscillator, your scope should show a

frequency of 60 cycles.* If the frequency is too high, larger resistors are needed or the value of the capacitors may be increased. That's why it is a good idea to have three or four capacitors and

*George Zwick, *Oscilloscope*, page 122 (Gernsback Library).


NOW...

stereophonic

HIGH FIDELITY *components*

by

Pilot

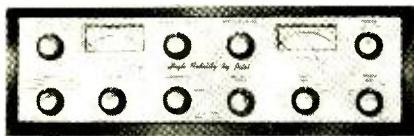

SP-215
Stereo Preamplifier
\$189.50



SM-244
Stereo Preamp
and Amplifier
\$189.50

PRICES SLIGHTLY HIGHER IN WEST

For complete details,
mail this coupon today.

Pilot Radio Corporation
37-06 36th St., L. I. C. 1, New York

Please send literature covering
Pilot Stereo Components.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Manufacturer in electronics
for over 39 years

TEST INSTRUMENTS

resistors of each indicated value on hand. Select the units that give greatest accuracy.

Now pick a matched pair of 75,000-ohm resistors. Try various units from those you have to get as close to 15 cycles as possible. Repeat this with 47,000-ohm resistors to obtain 25 cycles. If this frequency does not make an easily recognized pattern when compared with line frequency, try switching on 15 and 25 together. The 40-cycle pattern is easier to recognize. If the 15 and 40 networks are accurate, the 25 must also be.

Select a .05- and a .005- μ f capacitor for the $\times 10$ range. Don't forget that the larger unit is always C_b and connects to switch S1-b. With these capacitors the frequency must be 10 times larger and the amplitude must remain unchanged. Be guided by these facts: If one or both capacitors are too large, your new frequency will be lower than it should be. If the amplitude is too high, the ratio of C_b to C_a is too great.

Amplitude adjustments

For example, suppose we have completed the $\times 1$ range. Switch in any desired frequency in the band, say 40 cycles. Connect to the scope and set the sweep so that a single cycle appears. Thus, the sweep frequency is also 40 cycles. Now switch to the $\times 10$ range. You should observe 10 complete cycles on the scope. Furthermore, the amplitude of the range-2 pattern should be identical with range-1 signal.

Let us say that you are not too lucky (or perhaps you are very fussy). You feel that the range-2 amplitude is larger than that of the first. Furthermore, the frequency is a little too low and you want improvement. To raise the frequency we need lower capacitance (the resistors have been selected once for all ranges and should not be disturbed). The larger amplitude of range 2 shows that the ratio C_b/C_a is too large. Therefore, we select another (smaller value) for C_b . For extra-high precision you may even have to make a new selection for both capacitors.

Your labor can be eased with the help of another oscillator to compare frequency. Otherwise, simply set your scope for a complete cycle on one range, and look for 10 complete cycles on the next higher range. Use a minimum (preferably zero) sync signal during this measurement. For high accuracy, the patterns should remain stationary without aid of sync.

To arrive at the correct value of capacitance or resistance, you can add units in parallel or series as required. The chart shows the particular shunt and series capacitor arrangements I used. The same method applies, of course, to the resistors. I find that heat applied to a resistor can often raise its resistance several percent. If you have a resistor that is slightly low, apply a hot soldering iron to its leads. The resistance will rise appreciably, and in most cases will fall on cooling

but leave a net rise. For this reason keep hot soldering irons away from the resistors once you have the correct value.

Note that C7, C8, and C9 are mounted above the chassis. The other capacitors are below.

Final steps

After completing the instrument, connect its output to an oscilloscope. Note that J1 and J2 are tied together. Thus you may use one as signal source for an amplifier, and the other may be used for monitoring voltage or waveform. As the HARMONIC control (R2) is set toward zero resistance, no oscillation will occur. At maximum a distorted wave will be observed and, as the resistance is lowered toward midrange, the wave clears up. At about a 3-volt output, it should be a good sine wave but distortion will be still lower as R2 is decreased further.

S5 controls the output amplitude. In one position the maximum is about 3 volts (depending upon R2's setting). In the low position, the maximum is about 100 mv. R7 is a variable output control.

Because of low output impedance, the voltage does not drop much when a

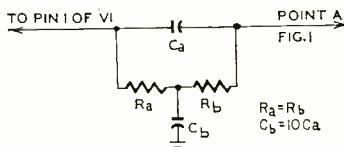


Fig. 3—A few additional parts and you've added a useful variable frequency circuit to the unit.

load is connected. For example, if you adjust for 2 volts open-circuit, a 600-ohm load will reduce it to 1.5 volts.

If you wish to add other basic frequencies or perhaps to substitute frequencies for those listed, the resistances must be changed. The required resistance may be calculated from the following simple formula:

$$\frac{f}{1,100} = R$$


where R is in thousands of ohms and f is the basic frequency (in the lowest range). Capacitors are as specified previously. Thus, for 55 cycles you need a pair of resistors, each 20,000 ohms. Of course this is the approximate value. The exact resistance is indicated by your oscilloscope as already described, and it requires careful selection of resistors.

Also, you may wish to add variable tuning. Since capacitance is fixed for any given range, the resistance must be varied. For the variable element use a dual potentiometer, each unit 100,000 ohms with logarithmic taper (see Fig. 3). The fixed resistors are limiting elements. To use the variable tuning, switch off all fixed frequencies and switch in the dual potentiometer instead. This feature was actually included in an earlier model of the Spot-O-Matic, but was abandoned in favor of greater simplicity. END

An Inexpensive Scope Calibrator

A range of .01 to 100 volts peak-to-peak with an accuracy of 5% makes this unit a valuable addition to your test equipment


By JOSEPH CHERNOF

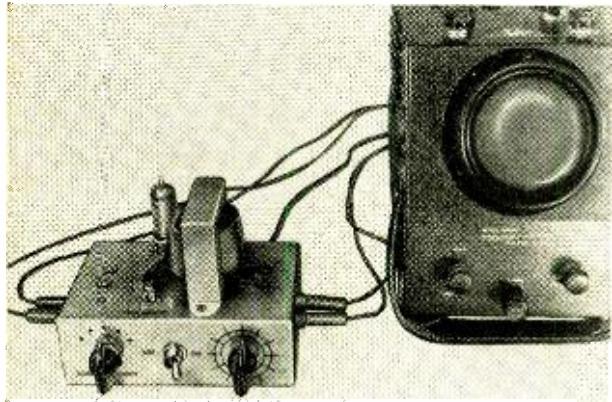


If amateurs and experimenters were polled as to what they consider the most important single difference between an inexpensive oscilloscope and its high-priced laboratory brother, the hands-down winner would probably be a built-in calibrator circuit. To be truly useful, the calibrator should provide a continuously variable output over a wide range with a reasonable degree of accuracy. It should also be small and compact so it can be used with a scope without increasing work-bench clutter. Such a unit is described in this article.

The scope calibrator operates from the 117-volt line. It has a useful output from below .01 volt to 100 volts peak to peak. With normal values of ac line voltage, output voltage accuracy should hold to within 5% after calibration. Accuracy depends on the care used in selecting the voltage-dividing resistors used in the COARSE OUTPUT switch network.

There are three front-panel controls. One, the COARSE OUTPUT switch, is a decade attenuator that provides four ranges of output voltage. The second, the OUTPUT VOLTS control, provides a continuous linear adjustment of the calibrator output voltage. The third control is an ON-OFF switch. Two pairs of banana jacks on the unit's side panels provide input and output terminals. The signal input terminals replace the scope's vertical input terminals for all test-lead connections. The signal output terminals are connected to the scope's vertical input terminals. For normal use of the scope, the fifth position of the output attenuator control provides a direct

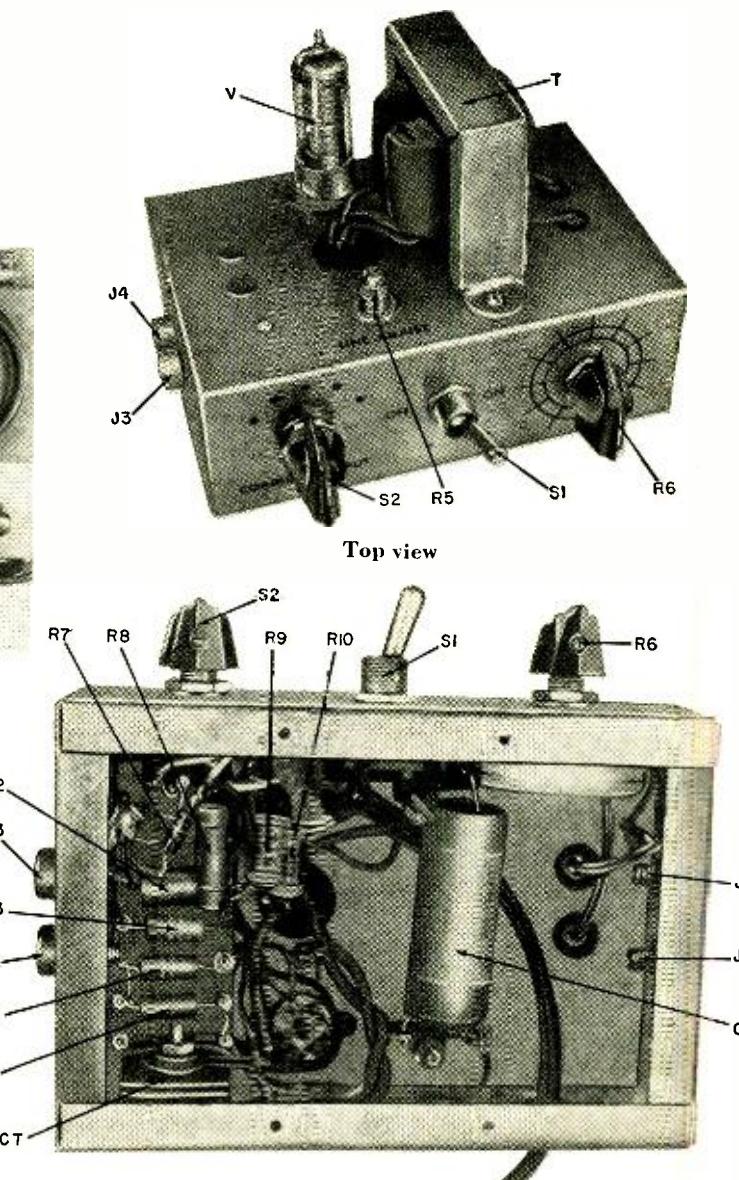


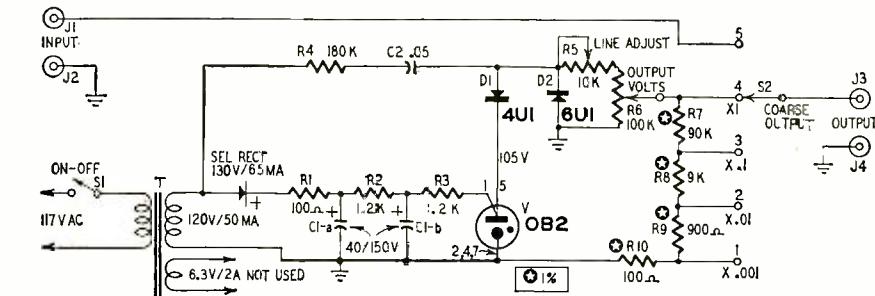With a little crowding size could be cut in half.



- R1—100 ohms
R2, 3—1,200 ohms
R4—180,000 ohms
R5—pot, 10,000 ohms, screwdriver adjust with locknut
R6—pot, 100,000 ohms, linear taper
R7—90,000 ohms, 1%
R8—9,000 ohms, 1%
R9—900 ohms, 1%
R10—100 ohms, 1%
All resistors $\frac{1}{2}$ watt
C1—40-40 μ F, 150 volts, electrolytic
C2—0.05 μ F
*D1—4UI, International Rectifier selenium diode
*D2—6UI International Rectifier selenium diode (D1, D2 mounted under terminal board.)
J1—4-Banana jacks
RECT, selenium 130 volts, 65 ma
S1—spst toggle
S2—1-pole 5-position rotary
T—Power transformer: primary, 117 volts, secondary 120 volts, 50 ma; 6.3 volts, 2 amps (Merit P-3045)
V—082
Case, 6 x 6 x 4 inches, socket, 7-pin miniature
miscellaneous hardware
* Available from: Radio Shack, 167 Washington St., Boston 8, Mass.

Circuit of the scope calibrator.

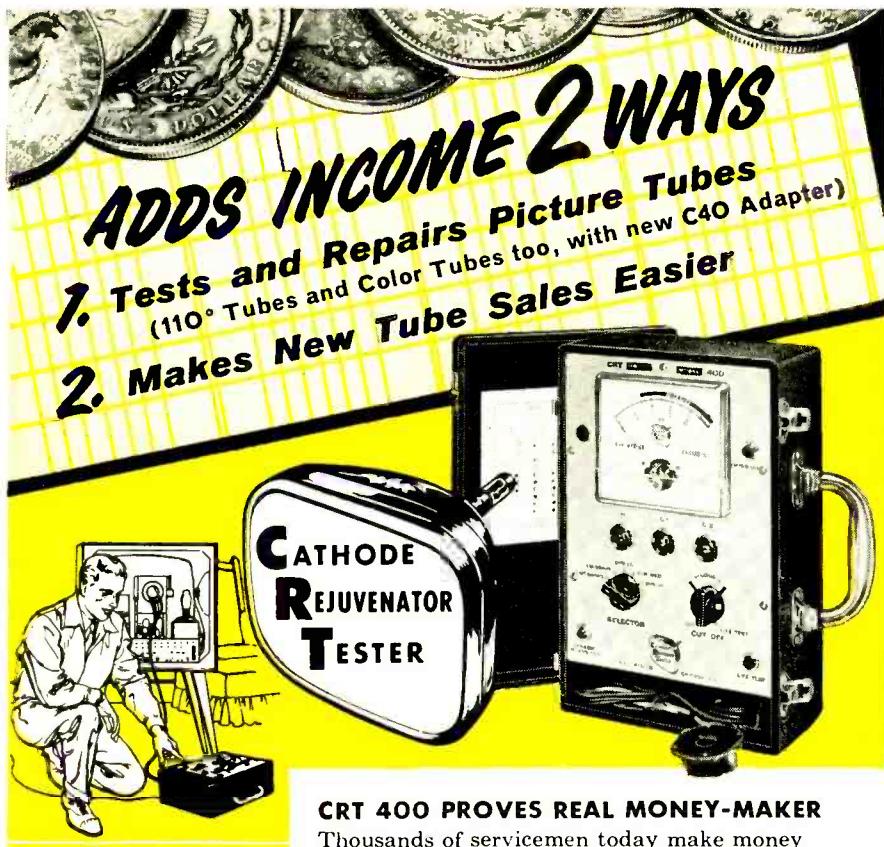

New C40 Adapter for
110° Tubes and Color Tubes



CRT 400 PROVES REAL MONEY-MAKER

Thousands of servicemen today make money and keep customer good-will by checking and correcting b&w picture tube troubles with the famous B&K CRT 400, right in the home without removing tube from set. Restores emission and brightness. Repairs inter-element shorts and open circuits. Checks leakage. Indicates picture quality customer can expect. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new picture tube replacement sales easier!

Model 400 (without adapter).....Net, \$59.95

NEW MODEL C40 ADAPTER DOUBLES VALUE OF B&K CRT

Designed for use with all B&K Models 400 and 350 CRT's. Makes it easy to test and rejuvenate TV color picture tubes and 110° picture tubes. Isolates and detects difficult color troubles. Tests and rejuvenates each gun of the color picture tube separately the same way as a black & white tube.

Model C40 Adapter.....Net, \$9.95

See your B&K distributor, or write for Bulletin AP12-E

Makers of CRT, DYNA-QUIK, DYNA-SCAN and CALIBRATOR

B & K MANUFACTURING CO.
3726 N. Southport Ave. • Chicago 13, Illinois



NEVER BEFORE AT THIS LOW PRICE!

Precision, battery-operated
transistorized portable

TAPE RECORDER

Weighs only 2 lbs. 8"x7"x2"
(imported from West Germany)

Precision-engineered—Records, plays back, erases. Variable speed controls. Operates on 4 ordinary C-batteries. Uses standard $\frac{1}{2}$ " 1-mill or $\frac{1}{2}$ -mill tape. Playback time about 15 min. Patented motor mount provides for forward and reverse winding; stopping with instantaneous braking action, taking up all slack tape; preventing tape from spilling. Voice can be dubbed and superimposed on music or other voice recording (and vice versa). Fine, durable, high-quality components. Complete instructions. Servicemen—Dealers! Every service call an easy sale after a simple demonstration. Renders same functions as machines costing many times as much.

Unconditionally guaranteed for 90 days against mechanical defects. 10-day money-back guarantee.

FILNOR PRODUCTS CO. Dept. RE-5 1 Park Ave., N.Y. 16, N.Y.

Your cost for sample, only \$29.95. Suggested retail selling price, \$39.95! On your re-order for two or more, earn an additional 10% discount. Hurry—be the first in your area with this sure-fire item! Everyone will buy! Rush order now!

TEST INSTRUMENTS

connection between the input and output terminals. This effectively removes the calibrator from the scope's input so a signal from a circuit under test can be observed. Additional utility and flexibility can easily be incorporated by adding an extra pair of input terminals connected to a sixth position of the output attenuator switch. (You would need a six-position rotary switch instead of the five-position unit used.) This would let you monitor two separate circuits without moving test leads around.

The unit's circuit is shown in the diagram. A rectified dc output voltage is filtered through R1, R2, R3, C1-a and C1-b. R1 is a current-limiting resistor, included to prevent damage to the selenium rectifier by the initial surge of charging current drawn by C1. Resistors R1, R2 and R3 are also used in conjunction with V1, an OB2, to provide a regulated 105-volt dc output.

Clipped output

The transformer's 120-volt output is also applied to the calibrator's voltage-dividing resistors. Diodes D1 and D2 limit the applied voltage to a 105-volt peak-to-peak value. D1's cathode is biased with 105-volt regulated dc from V1 so that it will conduct when voltages exceeding 105 are applied to its plate. Thus, peak voltages higher than 105 are effectively clipped. Likewise, D2's plate is connected directly to ground so that all negative values of instantaneous ac voltage will also be clipped. The output of these clipping circuits is a semi-square wave with a constant 105-volt peak-to-peak value.


This constant output voltage is applied to the output attenuating circuits, consisting of potentiometer R5, potentiometer R6, and the COARSE OUTPUT switch resistors R7, R8, R9 and R10. Values for these resistors have been chosen so that the variable output voltage from R6 can be multiplied by attenuation factors of 1, 0.1, .01 and .001. R7, R8, R9 and R10 should be held to tolerances of 1% for best calibration accuracy.

The initial calibration procedure is short and sweet. Connect an accurate vtv to output terminals J3 and J4, turn the calibrator unit on and set OUTPUT VOLTS potentiometer to the maximum voltage setting. Set COARSE OUTPUT switch to its $\times 1$ position. The vtv should indicate approximately 105 volts peak to peak. Vary R5 until the output voltage reads exactly 100 peak to peak. Tighten the shaft locknut.

The unit is now ready to use. It can be mounted on top of your scope or bolted to its side. The components will fit into a much smaller case if size and portability are important. If the unit is mounted on top of the oscilloscope, size would not be a major factor, and a 6 x 4 x 4-inch metal case, finished to match your oscilloscope, will provide an attractive housing for the calibrator.

END

New Tubes & Semiconductors

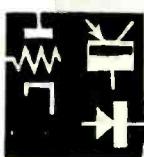


THIS month has turned out a large group of new units. Among them are two MADT transistors, a test picture tube for 110° deflection systems, a high-fidelity output tube and a group of 50-watt power transistors.

2N499

A micro-alloy diffused-base germanium transistor intended for use as a power oscillator or power amplifier at frequencies up to 100 mc. Polarities are similar to those of p-n-p transistors. Power gain is typically 10 db at 100 mc. Typical power oscillator output at 100 mc. is 35 mw.

The maximum ratings of this Philco transistor are:

V_{CE}	- 30
V_{CB}	- 18
V_{EB}	- 0.5
I_C (ma)	- 50
P_c (mw)	75

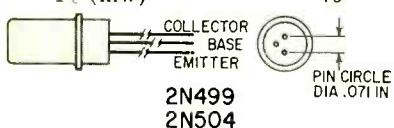

2N504


The 2N504 is a hermetically sealed germanium MADT (Micro-Alloy Diffused-base Transistor) field-flow transistor designed for use in if amplifiers. Its maximum frequency of oscillation is at least 50 mc. Polarities are similar to those of p-n-p junction transistors.

Maximum ratings of this Philco unit are:

V_{CB}	- 35
V_{CE} ($I_E = 0$)	- 25
V_{EB}	- 1
I_C (ma)	- 50
P_c (at 25°C) (mw)	50

8YP4

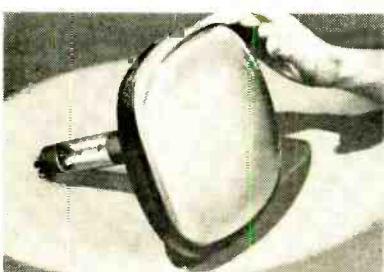This lightweight (2-pound) 8-inch rectangular picture tube is designed as a universal check tube for TV receivers



using 110° picture tubes. The tube has a conventional base and comes with an adapter to match the button base of most 110° tubes. It has a 6.3-volt 600-ma heater which is also designed to operate satisfactorily in 450 ma heater strings. It is made by Sylvania.

CORNELL-DUBILIER CAPACITORS



Thoroughbreds when the heat's on

Here are two types of C-D tubulars so thoroughly entombed in high-grade plastic that they're virtually unaffected by heat, cold and humidity. And, because they employ superior dielectrics, these capacitors have a 15%-25% greater voltage breakdown margin. That makes them the ideal replacement capacitors on all servicing jobs.

The C-D CUB, shown, is available with HT COMPOUND or DYKANOL "C" dielectric. The C-D PM utilizes the superior dielectric qualities of DUPONT "MYLAR." Both types maintain excellent electrical characteristics at high temperatures.


For a lasting service job, use C-D CUBS or PM'S. Your local C-D distributor carries complete stocks. For full data, ask for catalog 200D-3, or write Cornell-Dubilier Electric Corporation, South Plainfield, New Jersey, Dept. RE-6.



CORNELL-DUBILIER CAPACITORS

Old Hands at Dependability

CDR ROTORS

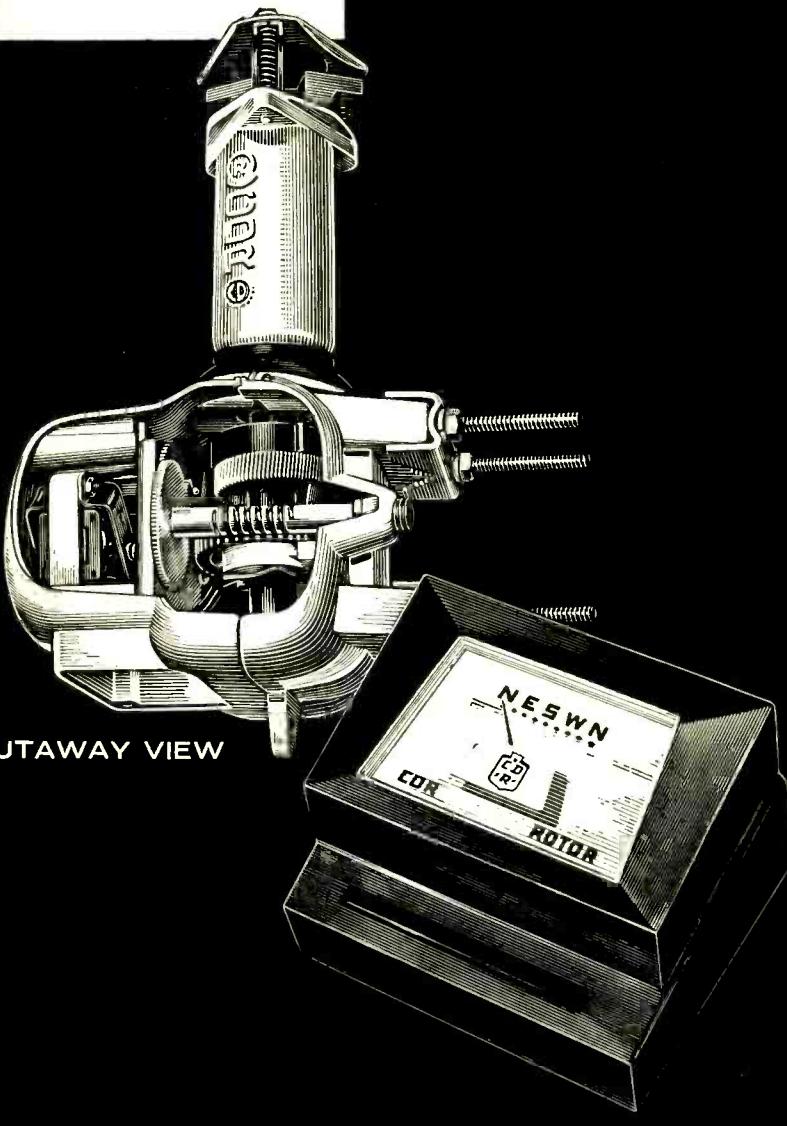

All new features

Completely designed from the ground up, CDR Model TR-15 and TR-16 Rotors have features never before available in the popular price range. Check these refinements and you'll see why: Quick mounting mast collet... speedy installation (no loose parts to assemble)... self-centering sawtooth clamps take masts up to 1½" O.D.... instant locking prevents drift... mechanical brake releases magnetically... instantly reversible... makes complete revolution in 45 seconds... meets JAN salt water test... great strength thrust bearing support... low weight... completely weather-sealed... fits standard towers... streamlined to reduce wind resistance... mahogany or blonde finish control box. Get full details today from your local CDR distributor.

CORNELL-DUBILIER ELECTRIC CORP.
South Plainfield, New Jersey

THE RADIART CORPORATION
Indianapolis, Indiana




CDR Antenna Rotors

Old Hands at Dependability

NEW TUBES & SEMICONDUCTORS (Cont'd)

2N623

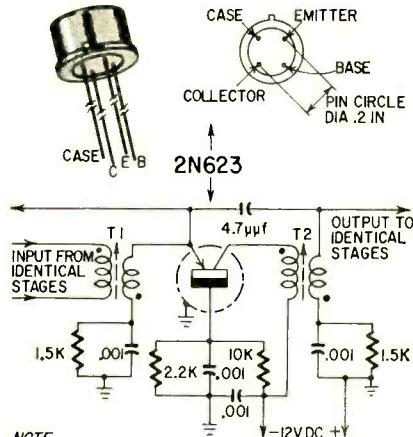A high-frequency diffused-base germanium transistor that enables high gain at frequencies ideal for television if amplifiers, radio rf amplifiers and vhf oscillators. Featuring a 200-mc typical maximum frequency of oscillation and a 90-mc typical alpha-cutoff frequency, this p-n-p transistor delivers



NOTE
T₁, T₂-PRI: 21 T N°30; SEC: 2-3/4 T N°30 WOUND OVER
BOTTOM END OF PRI ON 1/4 IN DIA FORM


50-db gain at 1 mc and 13-db gain at 50 mc. In the 43-mc if amplifier circuit (see diagram) the Texas Instruments 2N623 provides 15-db typical gain and 20-mw output.

Maximum ratings of the unit are:

V _{GRO}	- 30
V _{ERO}	- 15
V _{EBO}	- 1
P _{total} (mw)	40

7027

A high-perveance beam power tube designed specifically for use in push-pull power amplifier circuits of high-fidelity audio equipment. Featuring high power sensitivity and high stability, the 7027 can deliver high power at low distortion. Double-base pin connections for both grids 1 and 2 provide for flexibility of circuit arrangement and cool operation of the grids, which minimizes reverse grid current.

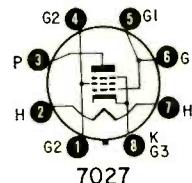

Typical operating values using this RCA tube in an Ultra-Linear output circuit are:

V _p	410
V _{g2}	see note
Cathode bias resistor (ohms)	220
Peak af (g1 - g1) (volts)	68
Zero-signal cathode current (ma)	134
Maximum-signal cathode current (ma)	155
Effective load resistance plate to plate (ohms)	8,000
Total harmonic distortion (%)	1.6
Maximum-signal power output watts	24


NOTE: g2 voltage is obtained from taps on the primary winding of the output transformer. The

NEW TUBES & SEMICONDUCTORS (Cont'd)

taps are located on each side of the center tap so as to apply 48% of the plate signal voltage to $\mu 2$ of each tube.

2N394, 395, 396, 397

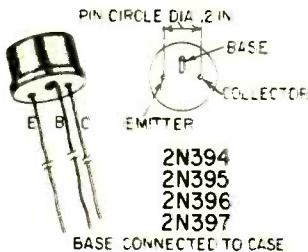These germanium p-n-p alloy-junction high-frequency switching transistors are intended for military, industrial and data-processing applications where




high reliability and extreme stability of characteristics are of prime importance.

Maximum rating of these General Electric transistors at 25°C are:

	2N394	395	396	397
V _{CE}	- 10	- 15	- 20	- 10
V _{CB}	- 10	- 15	- 20	- 10
V _{ER}	- 10	- 10	- 10	- 10
I _c (ma)	- 200	- 200	- 200	- 250
P _{across} (mw)	150	150	150	150
Alpha-cutoff				
freq (mc)	5.5	7	7	10

2N627, 628, 629, 630

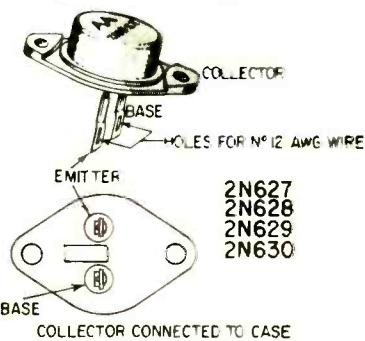Germanium p-n-p alloy junction power transistors capable of handling high wattages at high voltage. Collector electrode is connected to the case. Units are designed for high-current switching and audio applications.



Maximum ratings of these Motorola transistors are:

	2N627	628	629	630
V _{CB}	40	60	80	100
V _{CE}	30	45	60	75
I _c (dc) (amps)	10	10	10	10
P _c (base temp 30°C) (watts)	50	50	50	50
	END			



RADIART VIBRATORS



Consistently dependable power

Next time an auto-radio vibrator replacement is called for, try Radiart. There's a complete line for all 6-volt and 12-volt applications. And no waiting for the type you want, because your local Radiart Distributor maintains a full stock for your convenience. Ask him for your free copy of the Radiart Vibrator Replacement Guide, or write to Dept. S-1, The Radiart Corporation, Indianapolis 5, Indiana.




RADIART TOBE Vibrators

Old Hands at Dependability

new Devices




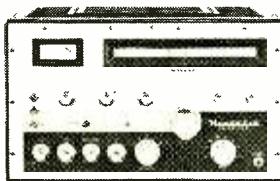HAM RECEIVER KIT, Mohawk model RX-1. Wide-band slide-rule type vernier tuning. Covers amateur bands from 160-10 meters. External receiver-powered converter accommodates cover 6 and 2 meters. Front end pre-assembled, wired and aligned. Double-conversion if at 1682



ke and 50 kc. 5 selectivity positions from 5 ke to 500 cycles. Bridged T-notch filter for maximum rejection. Built-in 100-ke crystal calibrator. 10-db signal-to-noise ratio at less than -1 μ u input. 15 tubes. Heath Co., Benton Harbor 20, Mich.

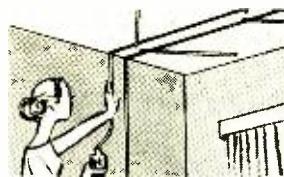INDOOR ANTENNA, Perma-Tena. Two continuous foil strips are glued to ceiling and connected to an antenna wall out-



let. Elements are extended from both sides of ceiling strips and secured with conductive cement. When painted over, antenna becomes invisible. Kit includes compass for proper orientation, conductive paint and materials, wall outlet, wall and conductive cement, applicator and other necessary material.—K & K Research Development Co., P.O. Box 925, Hawthorne, Calif.

FRINGE-AREA TV ANTENNA, Satellite-Helix. 28 elements. Front-to-back voltage ratios:



15 to 1 (low band), 18 to 1 (high band). 300-ohm impedance, balanced sleeve dipole system.—JFD Electronics Corp., 6101 16th Ave., Brooklyn 4, N.Y.

TV ANTENNA, Dura-Gold Corvette. Deep fringe-area, all-channel type (2-13). Metal ele-



ments covered with vinyl plastic to protect against corrosion.—Clear Beam Antenna Corp., Canoga Park, Calif.

ANTENNA TOWER, No. 25. General-purpose communications and heavy-duty TV type. 12 $\frac{1}{2}$ -inch equilateral triangular design. Uses 1 $\frac{1}{4}$ -inch heavy-gauge tubing for side rails and zig-zag solid steel cross bracing. Self-supporting to 50 feet or


used for switching between two antennas at receiver.—Techni-cal Appliance Corp., Sherburne, N.Y.

AUTO RADIO ANTENNA, model JA-7 Bullet. Chrome, die-cast swivels for vertical or 45° angle mounting. 3-section telescoping mast extends to 57



inches.—Tenna Manufacturing Co., 7580 Garfield Blvd., Cleveland 25, Ohio.

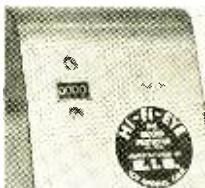STYLUS-USE TIMER, Hi-Fi-Eye. When connected in parallel with record changer or turntable, automatically indicates how many hours it has been in use. Lets you know when to



guyed to 150 feet. Hot-dipped galvanized or enamel finish.—Rohn Manufacturing Co., 116 Limestone, Bellevue, Peoria, Ill.

LOW-LOSS SWITCH, for antenna systems, TACO model 823. Miniaturized unit 1 $\frac{1}{4}$ x 1 $\frac{1}{4}$ inches. Mounted in gold anodized case. Slide switch presents 300-ohm impedance for maximum energy transfer. Dpdt type unit

change stylus.—Electronic Instruments Service, 8907 S. Vermont Ave., Los Angeles 44, Calif.

VARIABLE ATTENUATORS. Model AV-50 (illustrated) has

COYNE
TRAIN YOU
IN SPARE TIME
AT HOME
TELEVISION
RADIO-COLOR TV

COYNE QUALITY TRAINING AT LOWEST COST

Only from famous COYNE do you get this modern up-to-the minute TV Home Training. Easy to follow instructions—fully illustrated with 2150 photos and diagrams. Not an old Radio Course with Television tacked on. Includes UHF and COLOR TV. Personal guidance by Coyne Staff. Practical Job Guides to help you EARN MONEY QUICKLY IN A TV-RADIO SALES AND SERVICE BUSINESS—part time or full time. COSTS MUCH LESS—pay only for training—no costly “put together kits.”

SEND COUPON FOR FREE BOOK
SEND COUPON BELOW for Free Book and full details including EASY PAYMENT PLAN, NO COST OR OBLIGATION—NO SALESMAN WILL CALL.

B. W. COOKE, Jr., Pres.
COYNE
ELECTRICAL SCHOOL
A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT
500 S. Paulina, Dept. A8-H5, Chicago 12, Illinois

COYNE ELECTRICAL SCHOOL
Television Home Training Div.
500 S. Paulina St., Chicago 12, Ill., Dept. A8-H5
Send FREE BOOK and details of your Television Home Training offer.

Name _____
Address _____
City _____ State _____

NEW ULTRON UNIT PROVIDES SONIC REALISM

THE MODEL U-2 REVERBERATION UNIT

MAKES YOUR MUSIC SYSTEM REPRODUCE NATURAL QUALITIES OF LIVE SOUND



"PRESENCE" AT LOW COST APPLICATION OF REVERBERATION PRINCIPLES GIVES EFFECT OF STEREO WITHOUT REQUIRING MULTIPLE PROGRAM SOURCE

Ultron Company's Model U-2 Reverberation Unit will link any supplementary amplifier-speaker combination to your basic monaural system so as to provide realistic sound reproduction from a single source of program material. Music through a U-2 equipped system acquires a depth and sparkle known only to those accustomed to more expensive stereo installations. Hook-up is a simple matter covered in full by installation instructions accompanying each unit. Dimensions are approximately 2 x 3 x 5 $\frac{1}{4}$ inches.

ORDER NOW

OR SEND FOR FURTHER DETAILS

Purchase price will be refunded if unit is not as claimed and is returned undamaged within ten days of purchase.

ULTRON COMPANY

Dept. R-1, 7943 Haskell Ave., Van Nuys, Calif.

- Send free descriptive folder
- Send _____ U-2 Units @ \$18.75
(Calif. residents add 4% sales tax.)
- C.O.D. Postpaid (check enclosed)

Name _____

Address _____

City & State _____

**ALWAYS
SPECIFY**

HUSH®

Chemically engineered for tuners and switching mechanism

Hush comes in a 6 oz. pressure can with sufficient pressure to reach all contacts to wash away that dirt, leaving clean and positive contacts, protected with a lasting lubricant film.

Hush also available in 2 oz., 8 oz. and 32 oz. containers. Net \$2.25



EVER-QUIET®
Since 1949 the Original Volume Control and Contact Restorer EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning the contacts and leaving a safe protecting film.

2 oz. 79c Net
See your distributor or write to


**CHEMICAL ELECTRONIC
ENGINEERING, INC.**
Metawan New Jersey

NEW DEVICES (Continued)




50-ohm characteristic impedance; AV-75 has 75-ohm characteristic impedance. Both provide 0-62.5-db attenuation in 0.5-db steps. Operates from dc-500 mc.—**Jerrold Electronics Corp.**, 23rd & Chestnut Sts., Philadelphia 3, Pa.

UHF CONVERTER, model 99R. 3-section tuner with dual input section. Single-knob tuning of

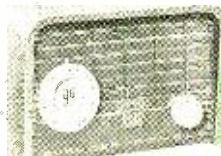


channels 14-83. 300-ohm impedance.—**Blonder-Tongue Laboratories Inc.**, 9-25 Alling St., Newark 2, N. J.

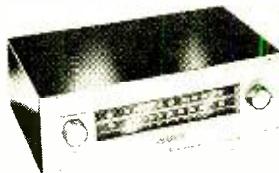AM-FM TUNER, model LT-25. FM section: response within 1 db from 20-20,000 cycles; output




level for 100% modulation is 2.5 volts; afc and afc defeat; Armstrong circuit with limiter and Foster-Seeley discriminator. AM response 20-5,000 cycles, within 3 db. Built-in AM and FM antennas.—**Lafayette Radio**, 165-08 Liberty Ave., Jamaica 33, N. Y.

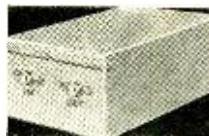REVERBERATION UNIT, model U-2. Used as link between basic amplifier output and input




of any auxiliary amplifier and speaker combination. Gives illusion of presence without necessity for two sources of program material.—**Ultron Co.**, 7943 Haskell Ave., Van Nuys, Calif.

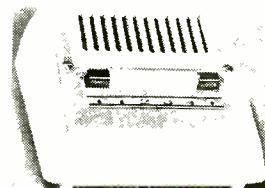TRANSISTOR INTERCOM, Centrum. Two 4.5-volt batteries power unit. Standard set consists of master station, substa-



tion and 20 yards of cable. Up to 3 additional substations may be added.—**Reeves Equipment Corp.**, 10 E. 52 St., New York.

HI-FI PHONO CARTRIDGE.

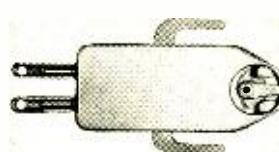


FLEXICONE. Helps improve speakers. Lowers cone resonance 10-40 cycles. Gives soft, permanently flexible, outer-edge cone suspension. Comes in do-




it-yourself kit with instructions.—**Howard Re-Cone Service**, 824 Kennedy St. NW, Washington 11, D. C.

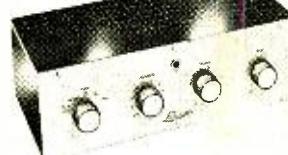12-WATT AMPLIFIER, model LA-22. Response 30-20,000 cycles



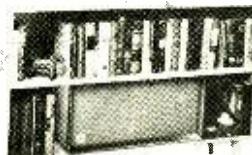SPEAKER ENCLOSURES. Model RJ/8 (illustrated), de-




signed for 8-inch speakers, fits in single shelf of standard bookcase. RJ 12-S: double-shelf model for 12-inch speakers. RJ 12-F: floor model for 12-inch speakers. RJ/Super 8: ready-to-play system consisting of RJ/8 enclosure equipped with Wharfdale Super 8/FS/AL speaker. Unfinished birch and finished in mahogany, walnut or blond.—**R-J Audio Products Inc.**, 80 Shore Rd., Port Washington, N. Y.

within 1 db at rated output. Less than 1½% IM distortion. Illum level 60-80 db below full output. 5 inputs including tape head. Equalization, loudness, treble and bass controls.—**Lafayette Radio**, 165-08 Liberty Ave., Jamaica 33, N. Y.

30-WATT AMPLIFIER, HF-32, kit or wired. Response within



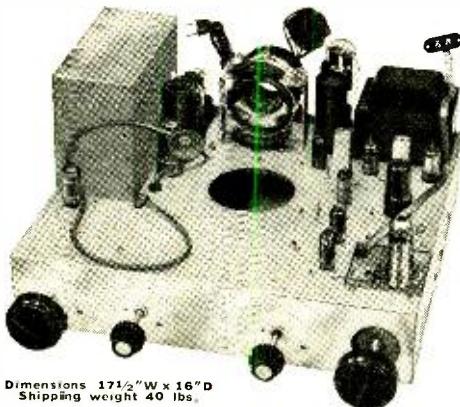DX-16 Super Deluxe TV KIT 70° or 90°—operating all 17", 21", 24" and 27" PICTURE TUBES



Dimensions 17½" W x 16" D
Shipping weight 40 lbs.

COMPLETE KIT
WITH SET OF


Westinghouse TUBES

NEW IN DESIGN—Mounts Horizontally, Vertically or Sideways.

- ★ Produces a Superior 16-Tube Chassis with 30-Tube performance.
- ★ Latest advanced Intercarrier Circuitry and Multi-section Tubes.
- ★ Standard Cascode Tuner for Selectivity and Fine Definition.
- ★ 5 Microvolts Video Sensitivity (20 volts peak to peak at CRT grid).
- ★ Fast Action AGC for Drift Free, Steady and Clear Pictures.
- ★ 3 Hi-gain Video I.F. Stages for excellent Contrast and Details.
- ★ AGC Level and Area Control, for adjusting reception to signal area.
- ★ All Video and I.F. Coils factory pre-aligned and tuned.
- ★ Horizontal Sweep Circuit is the famous RCA Synchroguide Network.
- ★ Large 250 ma Power Transformer.
- ★ Large 12" Concert-tone Speaker.

Sold on the Easy-Payment-Plan—\$2.49 starts you off. You receive LIFE-SIZE step-by-step Building Instructions . . . just buy a few dollars worth of parts at a time . . . or buy it complete at the low price shown below.

\$79.97

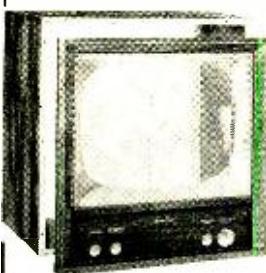

BUILD YOUR OWN TV CABINET FOR ANY TV CHASSIS

Comparable to the type that Top Mfrs. use on their higher priced TV sets.

CABINET KIT with 90% of the job done, includes—

FRONT SECTION complete as pictured in Solid Mahogany, Walnut or Blond Korina.

TOP, SIDES, BACK with **CRT CUP, MASK, SAFETY GLASS, ETC.** and Easy-to-follow Instructions.

Front, Top and Sides supplied in a beautiful Piano Finish • • • Knob panel undrilled (or drilled on receipt of your template) • • • For matching Mask specify type of CRT used. Same price for Mahogany, Walnut or Blond.

Worth \$60 when completed, only takes a few hours to assemble

Worth \$65 when completed, only takes a few hours to assemble

21" CABINET KIT 26" H. 25" W. 22" D \$24.95

24" or 27" CABINET KIT 30" H. 28½" W. 22" D \$36.47

(Also available for 17" CRT)

Maximum Shipping weight 48 Lbs.

FRONT SECTION for WALL INSTALLATIONS Includes Mask, Safety Glass, Decals and Illustrated Instructions. 21" .. \$17.45 | 24" or 27" .. \$22.97
(only) Same price on Mahogany, Walnut or Blond or in Natural (unfinished) for your own color application.

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y.

BUILD 16 RADIO

CIRCUITS at Home
with NEW DELUXE
1958 PROGRESSIVE
RADIO "EDU-KIT"

A COMPLETE RADIO COURSE

- * No Knowledge of Radio Necessary
- * No Additional Parts or Tools Needed
- * EXCELLENT BACKGROUND FOR TV
- * School Inquiries Invited
- * Attractively Gift Packed



\$22.95
Now \$22.95
Reg. U.S.
Pat. Off.

Now Includes

- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • HI-FI GUIDE
- QUIZZES • TV BOOK • FCC AMATEUR LICENSE TRAINING
- RADIO BOOK • PRINTED CIRCUITRY • PLIERS-CUTTERS
- ALIGNMENT TOOL • WRENCH SET

NO NEED TO SPEND
HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a reasonable price. You will learn how to build, repair and service radios. Therefore, you have the knowledge to operate electronic equipment, how to operate electronic equipment, how to build radios. You will receive a basic education in radio, worth many times the small price you pay, only \$22.95 complete.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specially prepared for any person who has desire to learn radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of

Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions and parts are included. Every step is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct your own radio, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learning the practical and theoretical aspects. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector units. These are new unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In addition, provides a thorough, well-integrated and easily-learned radio course.

The "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different advanced radio components, each guaranteed to operate. Our Kit contains tubes, tube sockets, variable, electrolytic and paper dielectric condensers, resistors, tie strips, coils, hardware, printed circuit board chassis, Instruction Manuals, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instruction and the progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book.

TROUBLE-SHOOTING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairing on the sets that you have built. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the Dynamic Radio & Electronics Tester. With your training in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Statius, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends and made money. The "Edu-Kit" paid for itself. I would like to spend \$200 for a Course, but I found your ad and sent for your Kit."

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND
CONDENSER KITS WORTH \$7.00

Send "Edu-Kit" Postpaid. I enclose full payment of \$22.95.
Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
Send me FREE additional information describing "Edu-Kit."

Name _____

Address _____


PROGRESSIVE "EDU-KITS" INC.

437 Union Avenue,
Dept. 141C, Brooklyn 11, N.Y.

NEW DEVICES (Continued)

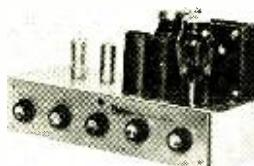0.1 db from 15-30,000 cycles at any level from 1 mw-and 30 watts. Harmonic distortion below 1% within 1 db of 30 watts. 4, 8 and 16-ohm outputs. Inputs for magnetic phono, tape head, mike, high level (TV, tuner, aux). Equalization, level, loudness, bass, and treble controls. Rumble and scratch filters.—
Electronic Instrument Co., Inc., EICO, 33-00 Northern Blvd., Long Island City 1, N.Y.

DUAL-CHANNEL AMPLIFIER, *Dual-Amp.* Input separated by electronic divider circuits into low-frequency and high-frequency components. Variable




crossover between 100 and 4,000 cycles. Low-end amplifier rated at 24 watts, high end at 6 watts. Separate volume controls for each.—
Transvision Inc., New Rochelle, N.Y.

HI-FI AMPLIFIER, *Mini-Fi model KN-510.* 10 watts. Response within 1 db from 20-20,000 cycles at full output. Harmonic distortion less than 2%. IM distortion less than 3%. Inputs for magnetic phono, crystal or ceramic phono, tuner,



auxiliary equipment and tape head. Bass, treble, volume, equalization selector and rumble filter. Outputs for 4-, 8- or 16-ohm speakers and high-impedance output for tape recorder.—
Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

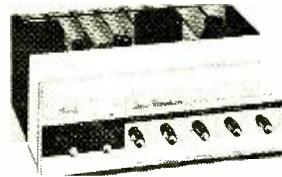STEREO AMPLIFIER, *model SR 17-17.* Combines 2 preamps and 2 power amplifiers on single chassis. Power output 17 watts each section. Harmonic distortion less than 0.5% at rated output. IM distortion less than 1.5% at rated output. Hum and noise 60-70 db below rated out-




put. Response within 1 db from 20-15,000 cycles. Inputs for tape decks, tape recorders, phono cartridges and auxiliary. Compensation, balance, bass, treble, volume and contour controls.—
Sargent-Rayment Co., 4926 E. 12th St., Oakland, Calif.

FM-AM TUNER AMPLIFIER, *model AT-130.* Sensitivity: FM, 5 µv for 20-db quieting; AM, 25 µv per meter. Selectivity: FM, 220 kc at 3 db point; AM, 9 kc at 6-db point. Hum level 60 db below maximum output. Amplifier response within 0.5 db from 20-20,000 cycles. Harmonic distortion: FM, 1%; AM, 2.5%. Built-in antennas. Treble, bass, loudness, function selec-



tor, and tuning controls. Tuning indicator. Inputs for tape or phone. Multiple speaker outputs.—
Granco Products Inc., 36-07 20th Ave., Long Island City 5, N.Y.

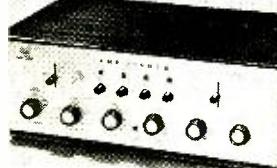STEREO MASTER CONTROL UNIT, *model 400:* 16 inputs, arranged in 8 pairs.—Low level, tape, mike, monitor, tuner, aux 1 and aux 2. 4 outputs. Push-button input selector, equalization and output selectors, volume, balance, loudness, bass and treble controls. Response uniform from 20-25,000 cycles.



Distortion less than 0.15% for 2-volt output. Crosstalk, 60 db down.—
Fisher Radio Corp., 21-21 44th Dr., Long Island City 1, N.Y.


ADJACENT-CHANNEL TRAP, *Filter Matic.* Hi-Q traps and bandpass filters remove adjacent-channel TV interference. Units for all vhf channels available.—
Benco Television



Associates Ltd., 27 Taber Rd., Rexdale, Ontario, Canada.


PANEL MOUNTING KIT. Accessory kit to be used with the Dynakit preamp. Includes brass escutcheon plate, pair of nickel-plated mounting brackets and hardware. Lets user mount preamp on panels up to 1½ inches thick.—Available from Dynikit distributors.

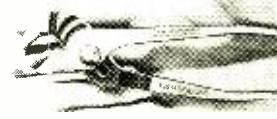MULTIPURPOSE PLIER, *Channellock No. 426.* 6½ inches long with thin jaws. For use in hard-to-get-at places. 5 adjustments with jaw capacity up to ¾ inch in parallel position. Drop-



forged; full-polished finish.—
Champion DeArment Tool Co., Meadville, Pa.

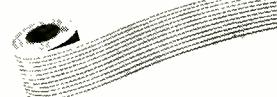POLYSTRIP CABLE, multiconductor flat cable for use in electrical and electronic equipment. Available in widths up to 51 conductors. Consists of flat copper ribbon .0015 inch thick and





NEW TO-5 TEL-OHMIKE® capacitor analyzer

measures all **4 . . . plus**

1 CAPACITANCE	2 POWER FACTOR	3 LEAKAGE CURRENT	4 INSULATION RESISTANCE	extra feature TURNS RATIO
Measures up to 2000 μ F in five overlapping ranges . . . including an accurate 1 to 100 μ F range, exclusive with Sprague.	Power factor of electrolytic capacitors is measured by the highly accurate bridge method. Reads up to 55% in three ranges for convenience in measurement.	Leakage current of electrolytics is measured directly on the meter, with exact rated voltage up to 600 v. applied from continuously adjustable power supply. Two ranges — 0-6-60 ma.	Insulation resistance of paper, ceramic, and mica capacitors is read directly on meter . . . up to 20,000 megohms.	In addition to its function as a complete capacitor analyzer, the TO-5 also measures the turns ratio of power and audio transformers.

The NEW TO-5 TEL-OHMIKE Capacitor Analyzer is one of the fastest and surest ways of measuring . . . capacitance, power factor, leakage current, insulation resistance, and turns ratio. This compact, easy-to-use instrument has the highest accuracy of any instrument of its type available to the service trade.

New jumbo dial makes meter reading easy. Special color-keyed pushbuttons permit instant range selection . . . and allow automatic safety discharge of capacitors after testing. Magic-eye tube simplifies bridge balancing for capacitance and power factor measurements.

SEE THE NEW TO-5 TEL-OHMIKE IN ACTION . . . AT YOUR DISTRIBUTOR!

This 4-in-1 test instrument is only 8 $\frac{1}{8}$ " high, 14 $\frac{5}{8}$ " wide, and 6 $\frac{1}{8}$ " deep . . . weighs a mere 12 $\frac{1}{2}$ pounds. The complete price for . . .

MODEL TO-5 (115 VAC/50-60 cy) . . . Only **\$83.90** net

Also available: Model TO-5X for 115-230 V/25-60 cy . . . \$89.90 net
Model TP-5RM for rack mounting . . . \$93.90 net

SPRAGUE®

world's largest capacitor manufacturer

SPRAGUE PRODUCTS COMPANY, DISTRIBUTORS' DIVISION OF SPRAGUE ELECTRIC COMPANY, NORTH ADAMS, MASS.



let RCA train you in Advanced Electronics

This is the college-level training you need to work with professional engineers on research, development or production projects in such fields as: automation, guided missiles, radar, television, computers and other advanced electronic applications. RCA Institutes Resident School in New York City offers this comprehensive course that prepares you for any field of electronics you may choose.

It's the blue ribbon course at RCA Institutes Resident School—among several to suit your inclination and ambition. Other courses in TV & General Electronics, Radio & TV Servicing, and Radio Telegraph Operating.

Classes start four times each year. Applications now being accepted. Approved for Veterans



RCA INSTITUTES, INC.
School of Television and Electronic Technology
A Service of Radio Corporation of America

RCA Institutes, Inc., Dept. RER-68
350 W. Fourth St., N. Y. 14, N. Y.

Please send me your FREE catalog of
Resident School courses in N. Y.

Name.....
Please print

Address.....

City..... Zone.... State.....

For Home Study Courses see ad on opposite page.

NEW DEVICES (Continued)


.030 inch wide encased in plastic insulation. Each conductor rated at 1 amp.—International Resistance Co., 401 N. Broad St., Philadelphia 8, Pa.

TUNABLE RF COILS. Encapsulated units cover a range of 0.1-10,000 μ h. Series 1, 13/32-inch diameter, $\frac{7}{8}$ inch long, 0.1




cm. Pre-wired terminal boards used for critical circuits.—Heath Co., Benton Harbor 20, Mich.

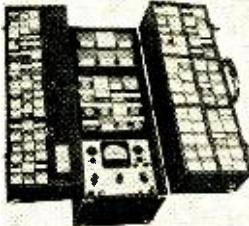CADDY TESTER has tube and rectifier checker built into tube and tool caddy. Leatherette-covered case with compartments




for tubes and tools.—Vis-U-All Products Co., 303 Fuller Ave. NE, Grand Rapids, Mich.

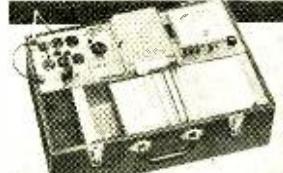AUTOMATED TUBE TESTER, Cardmatic model 121. Uses pre-punched cards to set up tester for tube to be tested. Checks



for mutual conductance, gas, grid emission, interelement shorts and leakages. Comes with cards for approximately 325 tubes.—Hickok Electrical Instrument Co., 10531 Dupont Ave., Cleveland 8, Ohio.

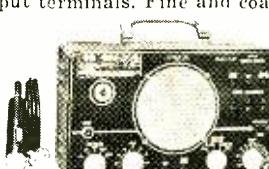
TUBE TESTER, Fast-Check model FC-2. Two controls to set. Checks for quality, interelement shorts and leakage, gas content



attenuators. Visual and audible signal indicators and output terminals for use with scope or vtv. Noise test, wattmeter and test amplifier circuits.—Paco Electronics Co., Inc. Div. of Precision Apparatus Co., Inc., 70-31 84th St., Glendale 27, N. Y.

DC SCOPE KIT, model OP-1.

De-coupled amplifiers and dc-coupled C-R tube unblanking. Triggered sweep circuit operates on either internal or external signals and may be ac- or dc-coupled. Sweep frequencies provided by switch-selected base rates of 2 and 0.2 msec/cm, and 20, 2 and 1 μ sec/cm in conjunction with continuously variable 10-to-1 multiplier. 5ADP2 flat-face scope tube. Edge-lighted grid screen. Vertical attenuator has 12 positions and is calibrated in volts per cm. Horizontal sweep calibrated in time per

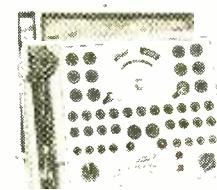


and life expectancy. 7-pin and 9-pin straighteners mounted on panel.—Century Electronics Co. Inc., 111 Roosevelt Ave., Mineola, N. Y.

POCKET TESTER, Electro-Probe. Checks for live outlets and determines if voltage is present at fuses, sockets, switches, lines and terminals. Use on all voltages between 110



and 500 ac or dc.—Superior Instruments Co., 2435 White Plains Road, New York 67, N. Y.

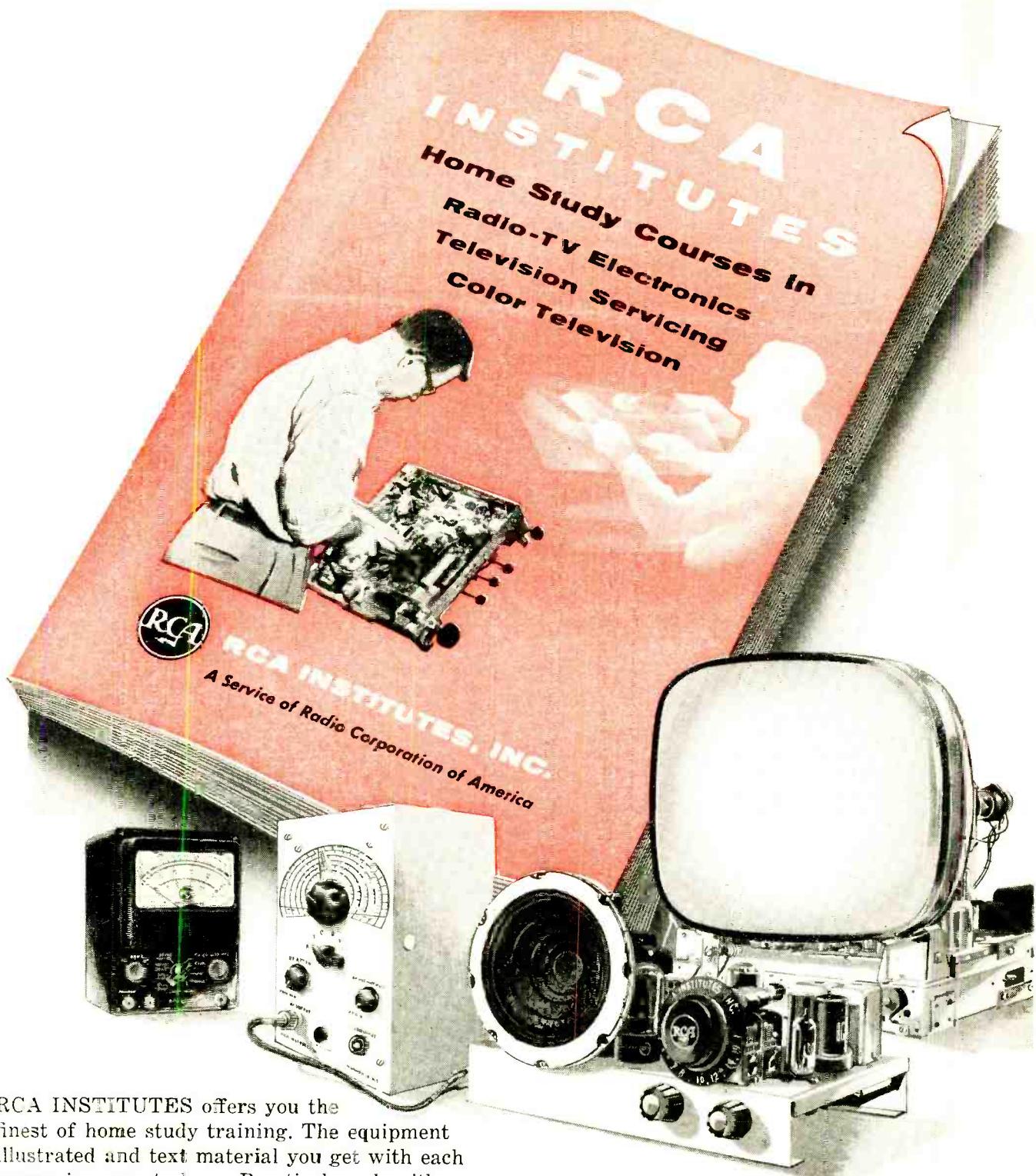All specifications given on these pages are from manufacturers' data.



RCA INSTITUTES offers you the finest of home study training. The equipment illustrated and text material you get with each course is yours to keep. Practical work with very first lesson. Courses for the beginner and the advanced student. Pay-as-you-learn. You need pay for only one study group at a time.

**Send for this
FREE Book Now**

[RESIDENT SCHOOL courses in New York City offer comprehensive training in Television and Electronics. Day and evening classes start four times each year.]

Detailed information on request

For resident school courses see ad on opposite page

RCA INSTITUTES, Inc. Home Study Dept. RE-68

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.

Without obligation, send me FREE 52 page CATALOG on Home Study Courses in Radio, Television and Color TV. No salesman will call.

Name please print

Address

City Zone State

Korean Vets! Enter discharge date

CANADIANS — Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to: RCA Victor Company, Ltd., 5001 Cote de Liesse Rd., Montreal 9, Quebec

To save time, paste coupon on postcard.



Whatever the choice may be — tape, record, or good old fashioned AM/FM radio, straight or multiplexed — Madison Fielding is the design center of any stereo system. Complete control and amplifier facilities for both monaural and stereophonic sound are built into the perfectly matched Series 330 AM/FM Stereophonic Tuner and Series 320 40-watt Stereophonic Amplifier.

Series 330 Tuner:

Two complete ultra-sensitive tuners on one compact chassis for either AM or FM reception individually, or, with a turn of a switch, both signals can be made available simultaneously. Multiplexed output is provided for by use of one adapter.

Series 320 40-watt Amplifier:

In addition to individual controls for each channel, the unit features a Master Volume Control, which controls both levels simultaneously for stereo. When used monaurally, it will serve as a complete electronic crossover system to feed separate woofer and tweeter.

For further information, write to:

Madison Fielding Corp.
5 Lorimer Street
Brooklyn, New York



The center of your stereo system.



NEW ASSOCIATION FORMED

A group of television technicians have banded together to form the Television Electronic Service Association of Central Missouri. Officers of the association are: Vernon Towner, Towner Radio & TV, Jefferson City, president; Al Idle, A & B Radio & TV, Jefferson City, vice president; John Reinsch, TV Service Center, Jefferson City, secretary-treasurer; Dennison Houghton, Peoples Radio Co., Columbia, director. Additional directors are to be appointed.

LESA FORMS

West Branch, Iowa, reports the organization and incorporation of the Linn Electronic Servicemen's Association (LESA).

The group plans to promote and maintain a high standard of ethics among retail electronic service technicians and dealers.

LESA officers are: Dick Reeder, president; Marvin Kirkpatrick, vice president; Tom Cours, secretary; George Rizzio, treasurer, and Louis Guetzko, Ralph Brink and Eugene Stick, directors.

LICENSE SUSPENDED

In the first action of its kind, the TV Board of Examiners of the City of Long Beach, N. Y., suspended the TV technician licenses of Norman Litman, Samuel Kaperstein and Bart Randazzo, operators of Melody Mart.

The board's decision states that these licensees had deceived and misled the complainant, Mrs. Harold Miller, by failing to give information to the complainant as to the condition of the TV set — warranting the set to be worth the expenditure for repairs, when in fact knowing that the cathode-ray tube was in poor condition and needed a booster, and by giving customer bill which did not reflect the true items of material used in repair.

The suspension was to have ended Feb. 28. However, an application for a new license to take effect on that date was denied.

TESA-MISSOURI VOTES

At a recent meeting in Columbia, Mo., of the Television Electronic Service Association of Missouri (TESA-Mo) a seminar on service business operations was conducted by Wayne Lemons and a technical discussion on servicing instrument development by David Doss.

New officers of the group are: Ed

"ONE DOLLAR" buys

As much as \$15 worth — Everything Brand New and sold to you with a money back guarantee.

DEDUCT 10% ON ANY ORDER OF \$10 OR OVER
Plus a FREE SURPRISE PACKAGE

100 - ASSORTED FUSES	popular sizes	\$1
100 - ASST. 1/2 WATT RESISTORS	Some 50%	\$1
70 - ASSORTED 1 WATT RESISTORS	\$1
35 - ASSORTED 2 WATT RESISTORS	\$1
50 - ASST. TUBULAR CAPACITORS	\$1
10 - 6' ELECTRIC LINE CORDS	with plugs	\$1
5 - TV CHEATER CORDS	with both plugs	\$1
4 - 50' SPOOLS HOOK-UP WIRE	4 colors	\$1
50 - STRIPS ASST. SPAGHETTI	best sizes	\$1
100 - ASST. RUBBER GROMMETS	best sizes	\$1
100' - TWIN LEAD-IN WIRE	300' heavy duty	\$1
50' - FLAT 4-CONDUCT. WIRE	many purposes	\$1
25' - INSULATED SHIELDED WIRE	\$1
1 - \$7 INDOOR-TV ANTENNA	big gain 3 Section	\$1
20 - ASST. TV KNOBS, ESCUTCHEONS, Etc.	\$1
3 - ASST. TOGGLE SWITCHES	spst, dpdt, etc.	\$1
6 - ASST. SLIDE SWITCHES	spst, dpdt, etc.	\$1
4 - BAKELITE KNOB SWITCHES	dpdt	\$1
15 - ASST. ROTARY SWITCHES	\$15 worth	\$1
100' - FINEST NYLON DIAL CORD	best size	\$1
200 - SELF TAPPING SCREWS	± 8 x 1/2"	\$1
35 - ASST. RADIO KNOBS	screws and push-on	\$1
100 - KNOB SPRINGS	standard size 3/8" x 1/2"	\$1
100 - ASSORTED KNOB SET-SCREWS	\$1
25 - ASSORTED CLOCK RADIO KNOBS	\$1
400 - ASST. H'DWARE	screws, nuts, rivets, etc.	\$1
50 - ASST. SOCKETS	metal, royal and miniature	\$1
20 - ASSORTED TUBE SHIELDS	best sizes	\$1
50 - ASST. MICA CAPACITORS	some in 5%	\$1
50 - ASST. CERAMIC CAPACITORS	\$1
10 - ASST. VOLUME CONTROLS	less switch	\$1
5 - ASST. VOLUME CONTROLS	with switch	\$1
100 - VOLUME CONTROL HEX NUTS	\$1
20 - ASST. PILOT LIGHTS	popular types	\$1
10 - PILOT LIGHT SKTS.	bayonet type, wired	\$1
50 - ASST. TERMINAL STRIPS	1, 2, 3, 4 lug	\$1
10 - ASST. RADIO ELECTRO. CAPACITORS	\$1
5 - ASST. TV ELECTROLYTIC CAPACITORS	\$1
15 - ASST. TV COILS	sync, peaking, width, etc.	\$1
25 - ASST. MICA TRIMMER CAPACITORS	\$1
50 - TUBULAR CAPACITORS	.001-.600V	\$1
15 - TUBULAR CAPACITORS	.047-.600V	\$1
50 - TUBULAR CAPACITORS	.01-.400V	\$1
2 - ELECTROLYTIC COND.	.40-.40-.450V	\$1
2 - ELECTROLYTIC COND.	.10/.10/.10-.450V	\$1
30 - FP CAPACITOR MOUNTING WAFERS	\$1
3 - ELECTROLYTIC COND.	.80-.150V	\$1
3 - ELECTROLYTIC COND.	.50/.30-.150V	\$1
15 - TUBULAR CAPACITORS	.015-.1600V	\$1
10 - HV TUBULAR CAPACITORS	.006-.1600V	\$1
10 - HV TUBULAR CAPACITORS	.001-.6000V	\$1
10 - HV TUBULAR CAPACITORS	.005-.6000V	\$1
35 - MICA COND.	20-100 mmf & 15-270 mmf	\$1
35 - MICA COND.	20-470 mmf & 15-680 mmf	\$1
35 - MICA COND.	20-820 mmf & 15-1000 mmf	\$1
35 - CERAMIC COND.	20-5 mmf & 15-10 mmf	\$1
35 - CERAMIC COND.	20-25 mmf & 15-47 mmf	\$1
35 - CERAMIC COND.	20-56 mmf & 15-82 mmf	\$1
35 - CERAMIC COND.	20-100 mmf & 15-150 mmf	\$1
35 - CERAMIC COND.	20-270 mmf & 15-470 mmf	\$1
35 - CERAMIC COND.	20-1000 mmf & 15-1500 mmf	\$1
35 - CERAMIC COND.	20-2000 mmf & 15-5000 mmf	\$1
50 - 1000 1/2 WATT RESISTORS	5%	\$1
75 - 470K 1/2 WATT RESISTORS	10%	\$1
50 - 15K 1 WATT RESISTORS	10%	\$1
50 - 470K 1 WATT RESISTORS	10%	\$1
25 - 2.2K 2 WATT RESISTORS	5%	\$1
25 - 100K 2 WATT RESISTORS	10%	\$1
10 - ASST. WIREW'D RES.	5, 10, 20 watts	\$1
3 - AUDIO OUTPUT TRANS.	.501.6 type	\$1
3 - AUDIO OUTPUT TRANS.	.6K6 or .6V6 type	\$1
3 - I.F. COIL TRANSFORMERS	.456 ke	\$1
3 - I.F. COIL TRANSFORMERS	10.7 mc FM	\$1
4 - OVAL LOOP ANTENNAS	asst. ht-gain types	\$1
3 - LOOPSTICK ANT.	new ferrite adjustable	\$1
12 - RADIO OSCILLATOR COILS	156 kc	\$1
3 - 1/2 MEG VOLUME CONTROLS	with switch	\$1
5 - 50K VOLUME CONTROLS	less switch	\$1
10 - SURE GRIP ALLIGATOR CLIPS	\$1
1 - GOLD GRILLE CLOTH	1 4/8" x 14" or 12" x 18"	\$1
1 - 5" PM SPEAKER	diafo. ± 5 magnet	\$1
5 - SETS SPEAKER PLUGS	wired	\$1
10 - SETS PHONO PLUGS and PIN JACKS	\$1
2 - \$2.50 SAPPHIRE NEEDLES	1000 playings	\$1
5 - DIODE CRYSTALS	2-1N21, 2-1N23, 1-1N61	\$1
2 - SELENIUM RECTIFIERS	1-65 ma & 1-150 ma	\$1
1 - TV VERT. OUTPUT TRANS.	10 to 1 ratio	\$1
5 - TV CRT. SOCKETS	with 180° leads	\$1
5 - HI-VOLT. ANODE LEADS	with 180° leads	\$1
1 - TV RATIO DETECTOR TRANS.	4.5 me	\$1
1 - SET TV KNOBS	standard type incl. decals	\$1
1 - LB SPOOL ROSIN CORE SOLIDER	40/60	\$1
6 - SPIN TIGHT SOCKET SET	3/16" to 7/16"	\$1
3 - TV ALIGNMENT TOOLS	5", 7", 12"	\$1
15 - "JACKPOT" TELEVISION PARTS	\$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (X in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for re-orders.

ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.

BROOKS RADIO & TV CORP.
84 Vesey St. Dept. A, New York 7 N.Y.

Engle, Crystal City, president; Dennison Houghton, Columbia, northeast vice president; M. C. Crane, St. Joseph, northwest vice president; W. A. Poyer, Mountain Grove, southwest vice president; E. Carroll, Cabool, southeast vice president; Carroll King, Lamar, secretary, and Carl Adcock, Aurora, treasurer. To the board of directors for two years: Robert Matteson, Florissant; Howard J. Freiner, St. Louis; Wayne Lemons, Buffalo, and Arrent Patterson, Springfield.

ATLANTA ELECTION

The Radio-Television Service Association of Greater Atlanta Inc., at their annual election meeting in Atlanta, Ga., elected Kermit M. Smith, Decatur Radio & Television Service, as their new president. L. J. Webber, Webbers Radio & Appliance Co., became first vice president; W. H. Steed, Radio Doctor, second vice president; M. Daniels, Fulton Appliance Service, third vice president; Pierce McGee, McGee's Television & Radio Service, secretary, and Joe Mull, Mull Television Co., treasurer.



Elected chairman of the board of directors was Red Tarsa, Riteway Television Co. Board members are Marvin Cochran, Atlanta Electronic Service; W. T. Edwards, Edwards Radio-Television Co., and Arthur Powell, Powell Electronics.

KCTSA MEETING

A program outlining how to avoid taking of "NSF" and "no account" checks was presented by the National Check Protection Service at a regular meeting of the King County Television Service Association Inc. (KCTSA). The meeting was held at the Stewart Hotel in Seattle, Wash.

At the annual meeting held earlier this year, Clayton Faller was elected president for the coming fiscal year. Other members voted to office were: Loyal Gudel, vice president, and Jim Humphrey, secretary-treasurer. Among the new directors are Connie Jenkins, Robert Kelly and Frank Shelton. Hold-over directors are Paul Morvee, Clinton Cox and Carl Pitman. Harold Hart, last year's president, will automatically serve on the board this year.

END

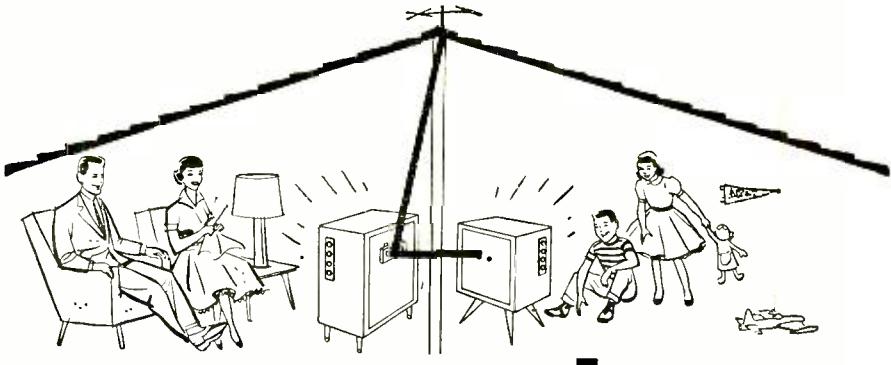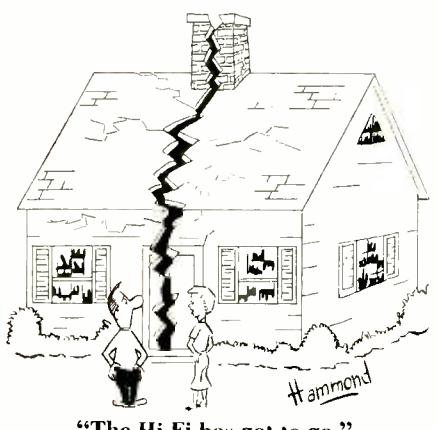


NOW!

sharper, clearer pictures on
1, 2 or 3 tv sets with 1 antenna

NEW  **B-23**

TWO-SET BOOSTER

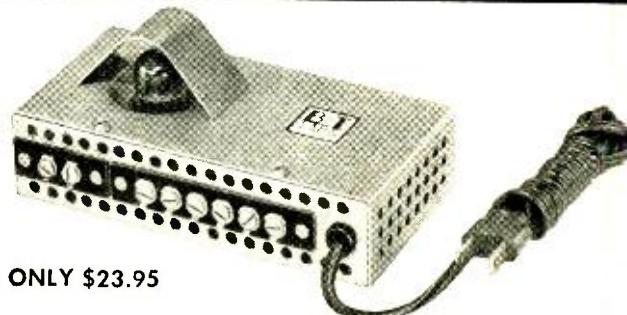

ONLY \$23.95

From B-T comes the most important step forward in better TV reception for 1958—a broadband TV amplifier that boosts signal strength on all VHF channels 2-13 and operates 1 or 2 or 3 TV sets with one antenna. No tuning is required.

combines two functions in one

A single B-23—

- **BOOSTS** signal strength on 1 or 2 or 3 TV sets—up to 6 db gain operating two TV sets from one antenna.

- **COPLES** 2 or 3 TV sets—using the present antenna. Outperforms non-powered couplers in any reception area by more than 2 to 1.

check these B-23 features:

- Ideal for color—add a color TV set and keep present black-and-white set, use the same antenna—the result, sharper, clearer pictures on both sets.
- Low noise figure—designed to work with new VHF sets.
- Reduces interference.
- Easily installed at antenna terminals of set. Can be mounted out of sight at the rear of the receiver.
- Automatically amplifies channels 2-13.
- Ideal small TV system (motels, multiple dwellings, TV showrooms).

FOR OPERATING 3 TO 8 TV SETS, USE THE B-T LABS DA8-B—MORE THAN 10 DB GAIN ON ALL VHF CHANNELS.

The DA8-B Distribution Amplifier is a broadband, all-channel unit that requires no tuning, impedance matching devices, pre-amps or other special fittings. Ideal for all small TV systems including garden apartments, motels, TV showrooms serving more than 3 sets. Approved for color, only \$94.50.

The B-23, the DA8-B, and a host of other B-T quality engineered products to improve television reception, are available at electronic parts distributors.

For further information, use coupon.

 **BLONDER-TONGUE LABS., INC.**
9 Alling Street, Newark 2, New Jersey

Please send me literature covering:

B-T B-23 B-T TV Accessories

Name _____

Address _____

City _____ Zone _____ State _____

RE-6

POWERING 4 OUT OF 5 of the world's greatest amplifiers



Amperex® 6CA7/EL34

HIGH-POWER OUTPUT PENTODE

High-fidelity authorities are not in agreement as to which is "best" among the handful of genuinely great power amplifier designs available today. But one thing they know for sure—at least 4 out of 5 of the contenders have 6CA7/EL34's in the output stage. No other comparable tube combines to the same degree the 6CA7's exceptional linearity, high power dissipation and low drive-voltage requirements. It is a true pentode design, with a separate suppressor grid that controls the space charge, resulting in greater linearity on reactive speaker loads than is possible with competitive beam-power tetrodes. A single pair of 6CA7's in push-pull has been successfully used in power amplifiers delivering up to 100 watts undistorted output.

OTHER Amperex TUBES FOR HIGH-FIDELITY AUDIO APPLICATIONS:

- EL84/6BQ5 9-pin power pentode; 17 W PP
- EF86/6267 Low-noise high- μ pentode
- ECC81/12AT7 Low-noise medium- μ dual triode
- ECC82/12AU7 Low-noise low- μ dual triode
- ECC83/12AX7 Low-noise high- μ dual triode
- GZ34 Cathode-type rectifier; 250 ma.
- EZ80/6V4 9-pin rectifier; cathode; 90 ma.
- EZ81/6CA4 9-pin rectifier; cathode; 150 ma.

At All Leading Electronic Parts Distributors

Amperex
ELECTRONIC CORP.

230 Duffy Ave., HICKSVILLE, Long Island, N.Y.


Patents



PASSIVE RESPONDER

Patent No. 2,812,428

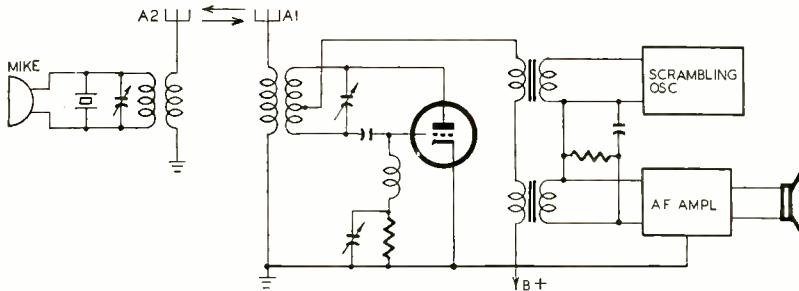Karl Rath, New York, N.Y. (Assigned to Radio Patents Co., New York, N.Y.)



A conventional radio transmitter needs power to operate it. However a remote station can be set up to pick up rf from another station, modulate it, then retransmit it, so no local power is

required. The master station is shown at the right of the diagram. It is a simple superregenerator, self-quenched at about 50 kc. The carrier may be 50 mc which is radiated from A1 to the remote antenna A2. The output of a superregenerator circuit is composed of pulses of rf.

The receiver tank is tuned to the same carrier and is shunted by a resonant quartz crystal. Like any vibrating device, the crystal absorbs power one instant, returns it the next. Thus, after a short delay, the crystal generates rf of the same frequency as that received, and power is radiated from A2. The microphone (when spoken into) modulates the rf. Due to time delay by the crystal, the pulses received at A1 arrive between intervals of superregenerator pulses.

When a modulated signal is picked up by a superregenerator, the receiver oscillations are similarly modulated. For that reason it is possible for an unauthorized listener to tune to A1 and receive the messages from A2. To avoid this possibility, a local scrambling oscillator is added as shown. The same scrambling process is also ap-

plied to the incoming audio signal to cancel out the interference. Therefore the reproduced signal is free of interference, yet secrecy is preserved so far as other stations are concerned.

AUTOMATIC TELEPHONE DIALING


Patent No. 2,813,931

Lev de Forest, Los Angeles, Calif.


nized by a rotary switch so it is in the circuit in sequence.

As R moves downward, the first finger moves beneath the card until it contacts the metal plate through the U perforation in the card (which is punched for UL 1-2345). At this time the dial has reached letter U also. The contact releases the gear mechanism through solenoid action. R flies back to its starting position, and the dial returns to its resting place. Then R advances again, this time with the second finger connected into the circuit. When this metal part reaches the perforation in letter L, contact is again made and the gear train returns to its starting position. Of course, L has now been dialed. In this way the five digits are dialed in turn.

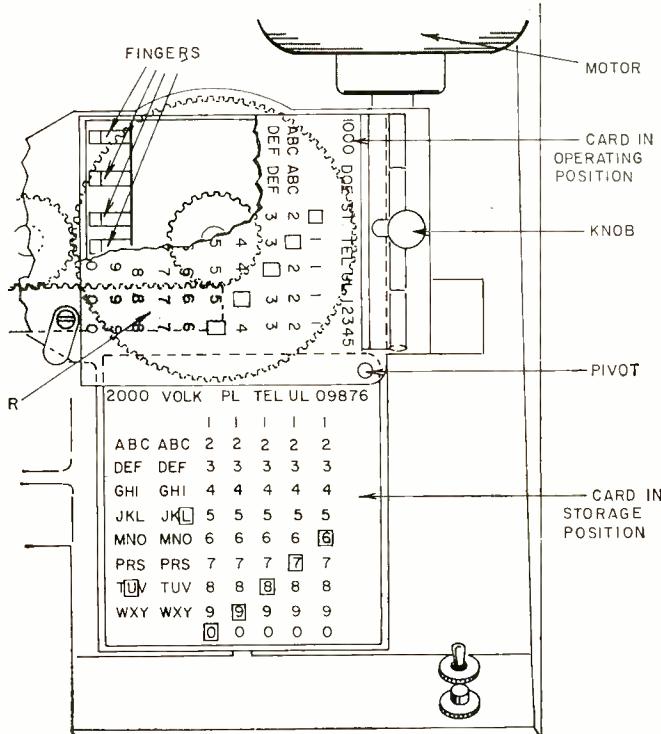Interested readers are referred to the patent specification for complete details. END




radio-electronic Circuits

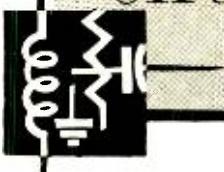

SPHERICAL TWEETER

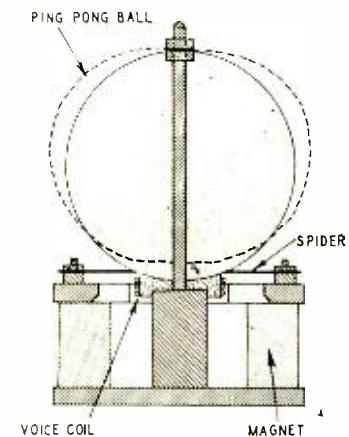The ideal pulsating sphere of all acoustics textbooks is cleverly approximated by K. H. Becker in an arrangement which appeared in *Funkschau*, 11-56.



all new edition

VOL. III, NO. 1



PLUS

up-to-date component prices
the quick easy way to figure service charges

Dave Rice's

OFFICIAL PRICING DIGEST



Flat rate and hourly service charges, based on and showing regional and national averages, plus up-to-date list or resale prices on over 63,000 components. Arranged alphabetically by manufacturers and products, numerically by part number. Compact, convenient size fits in tube caddy, toolbox or pocket. \$2.50 per copy from your distributor.

ELECTRONIC PUBLISHING COMPANY, INC.
180 N. WACKER DRIVE, CHICAGO 6, ILL.

The high-frequency directivity of the ordinary cone loudspeaker is very marked, and the usual remedies are diffusing contraptions or multiple-speaker arrangements.

The loudspeaker represented in the diagram replaces the cone by a spherical, ellipsoidal or ovoidal body. One pole or end is clamped and the other pole glued to the moving coil.

To improve its elasticity, it is recommended that slots be cut along the meridians between the two poles.

The displacement of the moving coil alternately expands and contracts the pulsating sphere. The sound is radiated toward the sides and upward.


The best practical results have been obtained using a ping-pong ball, with two diametrically opposed axial slots. The frequency range then extends from 2,000 to 15,000 cycles.—A. V. J. Martin

30-50-MC BOOSTER

Some of the less-expensive FM receivers for monitoring fire, police and similar radio services in the 30-50-mc band do not have enough gain for good quieting when receiving weak mobile stations. This low-noise cascode booster will improve these receivers.

L2 and L3 are Cambridge Thermionic Corp. (CTC) type LS3 30-mc inductors. L1 and L4 are antenna and output coupling coils. Each should be adjusted for maximum signal. Use hookup wire and start with about six turns around

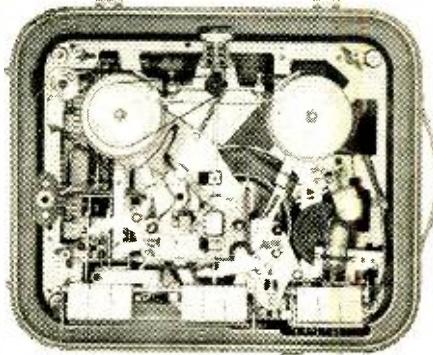THIS IS THE WAY
A GREAT
TAPE
RECODER
IS BUILT...



the
new
imported

NORELCO®

'CONTINENTAL'

*world's
most advanced
all-in-one
portable*

TAPE


RECORDER

Engineered by Philips of the Netherlands, world pioneers in electronics
Precision-crafted by Dutch master technicians

Styled by the Continent's top designers
Three speeds (7½, 3½ and 1½ ips)...
twin tracks...pushbutton controlled

Special narrow-gap (0.0002 in.) head
for extended frequency response
Built-in wide-range Norelco speaker
Also plays through external hi-fi set

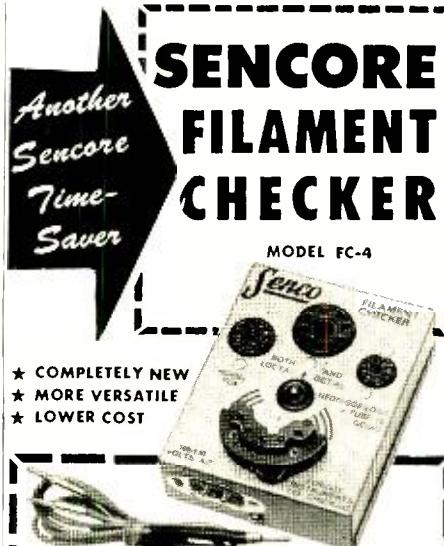For the name
and address
of your nearest
Norelco dealer,



Quickly finds any open filament. Especially handy for servicing series filament TV sets and radios; only checker that checks all octals, octalas, 7 and 9 pin miniatures automatically.

Continuity and voltage tester — no switches, merely plug in test leads.

AT LEADING DISTRIBUTORS
EVERWHERE

Mfg by
SENCORE
INSTRUMENTS CORP.
171 OFFICIAL RD., ADDISON, ILL.

Only
\$295
DEALER NET
WITHOUT LEADS
\$2.75

- POPULAR SENCORE PRODUCTS
• Transistor Tester
• Leakage Checker
• Filament Tester
• Voltage Regulator
• Bias Supply



NORELCO
NORTH AMERICAN PHILIPS CO., INC.
High Fidelity Products Division
230 DUFFY AVENUE, HICKSVILLE, L.I., N.Y.

DYNAKIT PREAMPLIFIER

ACCLAIMED AS THE FINEST AVAILABLE—
BY LABORATORY TEST OR CRITICAL LISTENING—IN MONEY-SAVING KIT FORM!



This handsome new control unit gives crystal clear, noise-free reproduction from *any* modern program source. Its unique all feed back design by David Hafler sets a new standard of preamplifier performance. The design of the Dynakit preamplifier is a synthesis of outstanding features which produce smoother, more natural sound. Compare these features with any other units regardless of price.

* Unequalled performance

Actually less than .1% distortion under all normal operating conditions. Response $\pm .5$ db 6 cps to over 60 kc. Distortion and response unaffected by settings of volume control. Superlative square wave performance, and complete damping on any pulse or transient test.

* Easiest assembly

All critical parts supplied factory-mounted on XXXP printed circuit board. Eyeleted construction prevents damage to printed wiring. This type of construction cuts wiring time by 50% and eliminates errors of assembly. Open simplified layout offers complete accessibility to all parts.

* Lowest noise

Integral dc heater supply plus low noise components and circuitry bring noise to less than 3 microvolt equivalent noise input on RIAA phono position. This is better than 70 db below level of 10 millivolt magnetic cartridge.

* Finest parts

1% components in equalization circuits to insure accurate compensation of recording characteristics. Long life electrolytic capacitors and other premium grade components for long trouble-free service.

* High flexibility

Six inputs with option of extra phono, tape head, or mike input. Four AC outlets. Controls include tape AB monitor switch, loudness with disabling switch, full range feedback tone controls. Takes power from Dynakit, Heathkit, or any amplifier with octal power socket.

* Outstanding appearance

Choice of bone white or charcoal brown decorator colors to blend with any decor. Finished in indestructible vinyl coating with solid brass escutcheon.

* Best buy

Available from your Hi-Fi dealer at only \$34.95 net (slightly higher in the West), and yet the quality of performance and parts is unexcelled at any price.

Descriptive brochure available on request.

Pat. Pending

The Dynaco Pre-Amplifier has been selected for display at the Brussels Worlds Fair as representative of highest quality American High-Fidelity equipment!


DYNACO INC.

617 N. 41st St., Philadelphia, Pa.
Export Division:
25 Warren St., New York 7, N.Y.

RADIO-ELECTRONIC CIRCUITS (Continued)

the bottom ends of L2 and L3. Neutralizing coil Lⁿ should be approximately 40 turns of No. 24 enameled wire wound on a $\frac{1}{4}$ -inch form. Vary the number of turns and the spacing for minimum noise.


The tuned circuits can be aligned

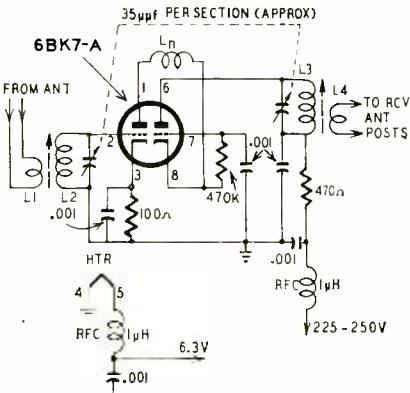

so they track reasonably well by carefully adjusting the slugs in L2 and L3. Tracking can be adjusted more precisely by connecting a small trimmer of around 5 μf across each section of the tuning capacitor and varying their settings along with those of the tuning slugs for optimum performance.

TRANSISTOR CODE OSCILLATOR

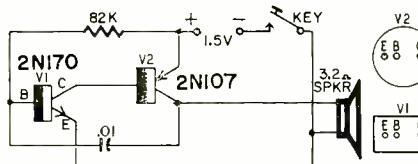Two transistors, a resistor, a capacitor, a loudspeaker, a telegraph key and a 1.5-volt penlight cell are all that are required for this simple and reliable code-practice oscillator. Volume is sufficient for classroom use, especially with an efficient loudspeaker. A direct-coupled positive-feedback circuit is used



with one n-p-n transistor and one p-n-p transistor.

Don't reverse the transistors or the voltage source polarity. The oscillator frequency can be lowered by using more capacitance, more resistance, or both. With the circuit constants given, the frequency is between 600 and 800 cycles. If one of the widely advertised 89c surplus telegraph keys and 99c manufacturer's surplus speakers are used, total cost will be less than \$5. Keying is clean and crisp if key contacts are not dirty. Total battery drain is less than 4 ma, low enough for obtaining many ham tickets before the first penlight cell is exhausted!—Harold Balyoz, W6YBP.

END

HEARING RANGE

By Jeanne DeGood

Since Hi-Fi gives me any tone
That any human hears,
What sounds are there I might have
known
If they'd improved my ears?

OPPORTUNITY ADLETS

Rates—50¢ per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for August issue must reach us before June 15, 1958.

RADIO-ELECTRONICS,
154 West 14 St., New York 11, N.Y.

"SHURE-TRAK" Liquid rubber-conditioner for phono drives, recorder belts, idler wheels. Cleans, restores, maintains traction. Unconditionally guaranteed. \$1. BROWN'S, Box 4124, Philadelphia 44, Pa.

HIGH-FIDELITY SPEAKERS REPAIRED. AMPIRE Speaker Service, 70 Vesey St., New York 7, N.Y. BA 7-2580.

CASH PAID! Sell your surplus electronic tubes. Want want clean transmitting, special purpose, receiving TV types; magnetrons, Elystrons, broadcast, etc. Also want military & commercial lab test and communications gear. We swap too, for tubes or choice equipment. Send specific details in first letter. For a fair deal write, wire or telephone: BARRY, 512 Broadway, New York 12, N.Y. WAVER 5-7000.

RECORDERS, Hi-Fi, Tapes, Free Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N.Y.

Ampeox, Concertone, Crown, Ferrograph, Presto, Tandberg, Ponton, Bell, Sherwood, Rek-O-Kut, Dynakir, Others. Trades. BOYNTON STUDIO, 10RE Pennsylvania, Yonkers, N.Y.

START A FAST GROWING, money making business. Operate a self-service tube tester route spare or full time. No selling. Stores make money for you every open hour. Send for FREE booklet describing this proven business. CENTURY ELECTRONICS, 111-J Roosevelt Ave., Mineola, N.Y.

LABORATORY QUALITY equipment and Military Surplus Electronics bought, sold. ENGINEERING ASSOCIATES, 434 Patterson Road, Dayton 9, Ohio.

DIAGRAMS FOR REPAIRING RADIOS \$1. Television \$2. Give make, Model. DIAGRAM SERVICE, Box 672-RE, Hartford 1, Conn.

DISCOUNTS up to 50% on hi-fi amplifiers, tuners, speakers, tape recorders; individual quotations only; NO CATALOGS. CLASSIFIED HI-FI EXCHANGE, RE 2375 E. 65 St., Brooklyn 34, N.Y.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING EQUIPMENT REPAIRED. HAZELTON INSTRUMENT CO., 128 Liberty Street, New York, N.Y.

TELEVISION Tuner Repairs. DAN'S TELEVISION LABORATORY, 619A Sunnyside Highway, Babylon, N.Y.

BUILD YOUR OWN printed circuits. Instructions, projects. \$1. CIRCUIT LABORATORIES, Box 52RE, Norwalk, Conn.

DEBTS COLLECTED everywhere or no charge. GRANT AGENCY, 34 Park Row, New York 38, N.Y.

WORLD FAMOUS Hartley Speakers now available to Dealers, Servicemen, custom installers lowest franchise requirements in High Fidelity industry write to HARTLEY PRODUCTS COMPANY 521 East 162nd St., New York 51, N.Y.

DISCOUNTS TO 50% recorders, tapes, hi-fi components, consoles, photograph equipment. Request specific prices only. LONG ISLAND AUDIO & CAMERA EXCHANGE, 3 Bay 26th St., Brooklyn 14-R, N.Y.

DELAYED LIGHT SWITCHES, home or automobile. For literature, KUHN & CO., 1212 Detroit St., Flint 3, Mich.

5-inch TV Test Tube, Model 5EP7. Brand-new, using an improved plug-in harness converter. See article "Economy Test Tube," Radio-Electronics, March, 1958, page 37. Essential for vertical chassis-non-ion. Guaranteed, \$3 postpaid. LION PRODUCTS, Box 205, Brooklyn 15, N.Y.

DIAGRAMS! Repair Information! Radios—Amplifiers—Recorders \$1. Televisions \$1.50. Give make, model, chassis. TV MINTIE, Box 101EA, Hicksville, N.Y.

SELF-SERVICE TUBE TESTERS, \$25 to \$50. Used—reconditioned complete with signs and floor model cabinets. Get into a profitable business with a minimum investment. Write, ED MOERKE, P.O. Box No. 264, Zion, Ill.

HIGH-PAYING JOBS, opportunities: foreign, USA. All trades. Companies pay time. For information, write Dept. J-11, National Employment Information, 1620 Broadway, Newark, N.J.

PROFESSIONAL Electronic Projects—Organs, Timers, Intercoms, Counter, etc. \$1 each. List Free. PARKS, Box 1665, Lake City Station, Seattle 35, Wash.

MIDGET radio kit \$1 plus postage. SMITH, Box 98, Frank, Pa.

SAVE MONEY! Get our price list on all types Radio and TV tubes at Mfrs. prices! 100% guaranteed, all brand new and unused, no mechanical or electrical rejects, not washed or rebranded! 24 hour service! Write United Radio Company, 58 Market St., Newark, N.J.

How Many Hours Have You Used Your Stylus? (Phono Needle)

HI-FI EYE—THE RECORD PROTECTOR—can answer this honestly, CAN YOU? A worn stylus WITH ONLY ONE PLAYING can wipe all the highs from your valuable records. A simple glance at HI-FI EYE tells you the total hours your stylus has been in use. Use this simple means to protect your valuable records. Easily installed. Operation automatic. Designed to sell for \$24.95. **SPECIAL INTRODUCTORY OFFER \$14.95.** Don't delay, order today. Guaranteed. 6 months warranty. No C.O.D.'s. California add 4%. Distributed by.

Hi-Fi Eye Co.
Box 44739 Hancock Station
Los Angeles 44, Calif.

Please mention

RADIO-ELECTRONICS

when answering advertisements

30 Watt Hi-Fi Super Lin Kit
AMP-PREAMP with
TRANSISTORIZED
FRONT END
FREQUENCY RESPONSE:
1-30, 10-100 cps.
TUBES: used (1) 6AU6,
(1) 12AU7, (1) 12AU7,
(2) EL311's, (1) 5V3-GB.
SHIPPING WEIGHT: 26
lbs. FL-30
Sale Price..... \$42.00
Send for Free Catalogue
CUTICK ELECTRONICS HI-FI RADIO TV PARTS
171 Washington St., (Dept. R-E), New York 7, N.Y.

TAPE RECORDERS

HI FI COMPONENTS

Tapes—Accessories

UNUSUAL VALUES

Send for Free Catalog

DRESSNER
69-02 RE: 174 St.
Flushing 65, N.Y.



TAPE RECORDERS

WHOLESALE PRICES

HI-FI COMPONENTS

NATIONAL BRANDS

WRITE FOR FREE CATALOGUE

CARSTON

215-TD E. 88 ST.
NEW YORK 28, N.Y.

July
RADIO-ELECTRONICS
on sale
JUNE 24

ENGINEERING

B.S. DEGREE
IN 27 MONTHS



Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. DEGREE IN 27 MONTHS in Aerospace, Chemical, Civil, Electrical or Mechanical Engineering; in 36 MONTHS in Mathematics, Chemistry, Physics. Intensive, specialized courses. Comprehensive training in electronics, television, advanced radio theory and design, math, nuclear physics and elec. eng. Engineering Science preparatory courses. Low rate. Graduates in demand. Spacious campus; 20 bldgs., dorms, gym, swimming pool. Earn part of your expenses in Fort Wayne, G.I. approved. Enter June, Sept., Dec., March. Catalog.

INDIANA TECHNICAL COLLEGE

1768 E. Washington Blvd., Fort Wayne 2, Indiana
Please send me free information on B.S. ENGINEERING
DEGREE IN 27 MONTHS as checked.

Electronics Chemical Aeronautical
 Civil Mechanical Electrical
B.S. DEGREE IN 36 MO. in: Math. Chem. Physics

Name
Address




SHOP HINTS

When more sensitive means aren't available, use a voltage regulator tube as a handy rf indicator. Tubes like the OB3/VR90 or OD3/VR150 serve well. For low power, touch terminal 2 or 5 to the rf source and the gas inside will glow. For higher power, hold the glass envelope in the rf field and the gas inside the tube will glow. The more rf, the brighter the glow in the tube, so that a resonance point is indicated by maximum glow—S. Clark

SOLDER AIDS DRILLING

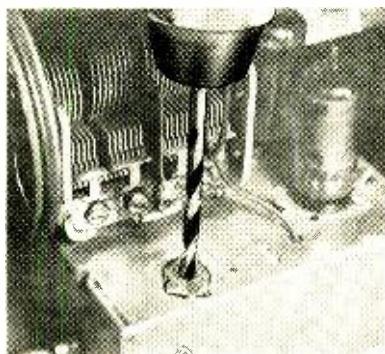To drill a hole in a metal radio or TV chassis, you must usually center-punch a pilot hole to give the drill an accurate start. The usually deforms the metal around the hole and gives the chassis and its many vibration-sensitive components a severe jolt.



To prevent this, form a thin layer or pool of solder over the spot where the hole will be drilled. The drill won't have any trouble eating into the soft solder and it will enter the chassis surface accurately without a center-punched pilot hole.—J. C. Alexander

DRINKING-STRAW SPAGHETTI

It recently occurred to me that wire insulating spaghetti is commonly sold for another purpose at the grocer and five-and-dime stores. Not only is it available at these stores, but it comes in a variety of colors and sizes! I'm referring, of course, to plastic drinking straws. They make ideal wire insulating spaghetti. I often pick up a pack of them right along with my weekly groceries. They're inexpensive too.—John A. Comstock

FUSE-CLIP BURNISHER

I clean and brighten the metal clips of tubular fuse holders with a 1½-inch wide strip of fine abrasive cloth wrapped around the ¼-inch shank of a screwdriver. The abrasive cloth is

DYNAKIT

Amplifier Kits

A great amplifier circuit of superb listening quality in money-saving kit form!



MARK III 60 watts **7995***
net

The new Mark III includes all the sensational attributes of the popular Mark II plus these outstanding deluxe features

- ★ 60 watts at less than 1% distortion. Instantaneous peak power of 140 watts. IM less than .05 at average listening levels.
- ★ Choke filtering and low noise circuitry reduce hum and noise to 96 db below 60 watts.
- ★ New rugged KT-88 tubes and other heavy duty parts used conservatively.

MARK II 50 watts **6975***
net

The Mark II is the best buy in high power high fidelity kits

- ★ Ease of assembly due to uniquely simple circuitry and printed circuit construction with factory-mounted parts.
- ★ Highest stability using patented stabilizing networks with minimum number of phase shifting stages. Suitable for all loud-speaker systems including electrostatic.
- ★ Dyna Biaster (patent pending) for simplified adjustment and complete freedom from effects of unbalanced components. No balancing adjustments required to meet published specifications.
- ★ Dynaco Super-Fidelity output transformer with patented para-coupled windings. This is the finest available transformer of its type for the most critical audio uses.

Available from leading Hi-Fi dealers everywhere *Slightly higher in West
Descriptive brochure available on request.

The Dynaco Amplifier has been selected for display at the Brussels Worlds Fair as representative of highest quality American High-Fidelity equipment!

DYNACO INC.

617 N. 41st Street, Philadelphia, Pa.
Export Div.: 25 Warren St., N.Y. 7, N.Y.

SATELLITES
ROCKETS
MISSILES
SPACE PROJECTS
ELECTRONICS -
AERONAUTICS -
TECHNOLOGY

**Prepare Now at
 NORTHROP**

for a brilliant career in the
 TECHNOLOGICAL WORLD
 of Today and Tomorrow!


This is the Technological Age — the time when men with Engineering Know-how can write their own ticket — pick their own field of specialization in Electronics and Aeronautics. YOU can EARN HIGH SALARY — and have an unlimited future — if you decide NOW to prepare for an ENGINEERING TECHNOLOGY CAREER.

AT NORTHROP INSTITUTE

— one of the country's leading institutions of technological education — you can complete your training in JUST TWO SHORT YEARS.

Recognized throughout the AVIATION and ELECTRONICS INDUSTRIES as an "industry" school, and with thousands of successful graduates now employed by Industry — you owe it to yourself to get complete information about what Northrop Institute can offer you.

Approved for Veterans

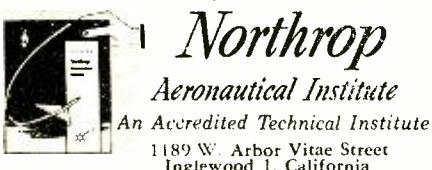

Mail Coupon for Complete Information

NORTHROP AERONAUTICAL INSTITUTE
 1189 W. Arbor Vitae Street, Inglewood 1, Calif.
 Please send me immediately the Northrop catalog, employment data, and schedule of class starting dates. I am interested in:


- Electronic Engineering Technology
- Aeronautical Engineering Technology
- Aircraft Maintenance Engineering Technology
- Master Aircraft and Engine Mechanic
- Jet Engine Overhaul and Maintenance

Name Age

Address

City Zone State
 Veterans: Check here for Special Veteran Training Information.

TRY THIS ONE (Continued)

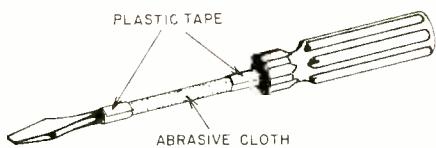

held in place with plastic tape. The fuse-size shank is an almost perfect fit and just a few turns of the handle makes fast work of burnishing the clip's inner surfaces. Since I came across a few really bad cases of high contact resistance due to slip corrosion, I've made it a habit to clean fuse-clip contacts every time I replace a tubular fuse.—Scott Mack


BATTERY TO SPEAKER CONNECTIONS

When discarding a dead portable battery, cut out and save any snap-on battery connectors. Many of these can be matched to each other. Next time you want to put connections onto a PM speaker just solder the snap-on clips to the speaker leads.—A. Von Zook

TIGHTENING DIAL CORDS

After considerable use, dial cables have a tendency to stretch and to slip on the tuning shafts. There are several ways to remedy slipping dial cables. You can apply nonslip compound to the cable where it goes around the shaft or, if possible, move the cable spring to a place on the drum where it puts more pull on the cable or shorten the cable

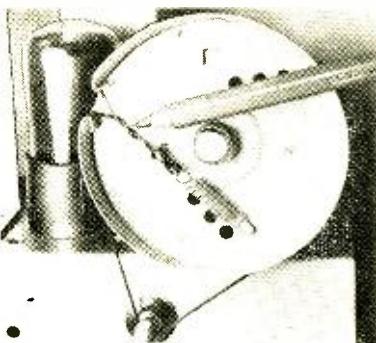or replace the old cable with a new one. However, I feel that my method is one of the simplest and most effective.



If the cable is in good condition, but simply slips on the tuning shaft, you can tighten it easily. Simply remove the bottom end of the cable spring from the lug of the drum, give the cable a few twists at the place pointed out in the photo, and hook the spring back on the drum lug again. The twists shorten the cable so the spring puts more tension on it. Experiment with the number of twists needed.—Art Trauffer

KEEPING THE IRON CLEAN

I keep the tip of my soldering iron clean and free of scale by occasionally holding it against a revolving wire brush. The stiff wire bristles of the brush remove all traces of scale and solder. Then the iron can be readily tinned.—John A. Comstock END

MAKE SURE IT FITS!

OXFORD SPEAKERS

You obtain the finest sound reproduction when you select the proper speaker for the specific application. Each OXFORD SPEAKER is "tailor-designed" to actually "fit the need."

Specify OXFORD when you next require quality speakers. Remember: Oxford quality has consistently been superior for over thirty years.

**RADIO &
TV SPEAKERS**

OXFORD Speakers are used by more original set manufacturers — find out why!

OUTDOOR SPEAKERS

For rugged, steady performance under any conditions, OXFORD Weather-proof speakers will meet the need.

**DUAL CONE HI-FI
SPEAKERS**

Oxford's newest development to provide maximum performance. For Hi-Fi and rear deck applications.

**PORTABLE RADIO
SPEAKERS**

More Oxford speakers are used in portable sets than ever before . . . there must be reason!

Our new catalog is available . . . write for yours NOW!

OXFORD

OXFORD Components, Inc.
 Subsidiary of Oxford Electric Corp.
 556 West Monroe Chicago 6, Ill.
 Export Agents: New York City
 In Canada: Atlas Radio Corp., Ltd., Toronto

Technotes




WATERLOGGED AUTO ANTENNA

Sometimes the insulation at the bottom of an auto antenna wears or breaks, allowing water to leak down the antenna, grounding it out. A fast, temporary remedy is to slip a boot from the end of an auto-brake master cylinder over the antenna and down to the cowl, forming an effective seal.—*E. Mayover*

DEFECTIVE BAR GENERATOR

This complaint concerned a color bar generator. When the generator was used to drive known good color TV receivers, only gray bars were produced, with no visible color.

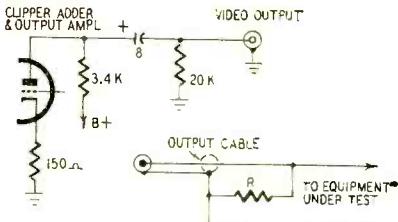It was a Telechrome generator, using the output circuit shown in the diagram. We started checking waveforms and found a normal signal at the grid of the tube. Evidently, high-frequency attenuation was taking place in the plate circuit.



It was apparent from the circuit diagram that the plate load (3,400 ohms) was much too high to obtain high-frequency output. However, the output cable is a branch of the ac plate load. We checked the cable and found no terminating resistor (R)—it had evidently been removed by someone who thought that it didn't make any difference or something. We connected a 75-ohm resistor across the cable's terminals and presto—we were back in the color business.—*Robert G. Middleton*

MOTOROLA TS-539

Symptom: No age, picture comes in momentarily after channel selection, then blanks out.

Measure the age voltage at the tuner's age terminal with no signal present. There should be 1 volt at this point. If no age is present and the 6AU6 age tube checks good, try replacing the 6DQ6 horizontal output. If this tube is shorted (and this has happened several times without noticeably affecting brightness or blowing the fuse), no age will be developed. On one particular receiver, the symptoms

NEW JUST OFF THE PRESS!

ELECTRONIC PUZZLES AND GAMES

By Matthew Mandl
Gernsback Library
Book No. 70
128 pages
Paper-cover edition
only \$1.95



More fun than a CIRCUS
Make your own ELECTRONIC PUZZLES and GAMES

You can make these games...

- Knife switch puzzle
- Double indicator puzzle
- Street light puzzle
- River crossing puzzle
- Little thinker
- Twenty one
- Hide-and-seek
- Trip to the Shore
- Jet plane game
- Cross-country race
- Space-travel game
- Mystery safe puzzle
- Adding machine puzzle
- Magic number puzzle
- Prospecting puzzle
- Hidden word puzzle
- Satellite game
- Tri-target game
- Basket-catch game
- Horse race game
- Plus a complete index

Now build, plan and play your own electronic games. Anyone from Cub Scout to engineer can do it and enjoy it. This new Gernsback Library book shows you how to make all of them—from a simple knife-switch to a complicated space-travel game. A wonderful book to start a boy off

on electronics. All you need is a soldering iron, wire, batteries, flashlight bulbs and a few simple tools. Layout drawings outline each puzzle or game and there are photographs of each basic type. Kids from 8 to 80 will love this book. It's more fun than a circus. Order your copy today!

SEE YOUR DISTRIBUTOR OR MAIL THIS COUPON TODAY

Gernsback Library, Inc. Dept. 68

154 West 14th St., New York 11, N. Y.

No. 70—Electronic Puzzles and Games

69 68 67 65 64 63 62 61 60

My remittance of \$..... is enclosed.
Please send me the books checked, postpaid.

Name.....

Please print

Street.....

City.....

Zone..... State.....

OTHER NEW GERNBSACK BOOKS

69—Electronic Hobbyists' Handbook	\$2.50
68—TV and Radio Tube Troubles	2.90
67—Elements of Tape Recorder Circuits	2.90
65—Servicing Color TV	2.90
64—Understanding Hi-Fi Circuits	2.90
63—Transistor Circuits	2.75
62—TV—It's a Cinch	2.90
61—Transistor Techniques	1.50
60—Rapid TV Repair	2.90

GET INTO ONE OF THESE TOP OPPORTUNITY FIELDS

ELECTRICITY

— Electronics or

TELEVISION

— Radio-Color TV

TRAIN IN THE GREAT SHOPS OF

COYNE

OLDEST, BEST EQUIPPED SCHOOL OF ITS KIND IN U.S.

Veterans and Non-Veterans—Prepare for a better job NOW that offers a real future, too! Get practical training in TELEVISION—RADIO—ELECTRICITY—ELECTRONICS (Refrigeration & Electric Appliance Repair can be included). Learn on real equipment—no advanced education or previous experience needed. Lifetime employment service to graduates.

Finance Plan—enroll now, pay most of tuition later. Part time employment help to students.

FREE BOOK Clip coupon for Big Free Illustrated Book. No salesman will call. Act NOW.

B. W. COOKE, JR.

President

COYNE FOUNDED 1899
ELECTRICAL SCHOOL

A TECHNICAL TRADE INSTITUTE OPERATED

NOT FOR PROFIT

500 S. PAULINA ST., CHICAGO, DEPT. A8-5C

ELECTRICITY • TELEVISION • RADIO • REFRIGERATION • ELECTRONICS

B. W. COOKE, JR., Pres., COYNE ELECTRICAL School
500 S. Paulina St., Chicago 12, Ill., Dept. A8-5C

Send FREE BOOK and details on:

- TELEVISION-RADIO
 ELECTRICITY-ELECTRONICS

NAME.....

ADDRESS.....

CITY..... STATE.....

NEW! IMPROVED! SENCORE TRC4 TRANSISTOR CHECKER

Another
Sencore
Time-
Saver

America's newest,
most popular test
instruments

NOW CHECKS:

★ Transistors
for opens, shorts,
leakage and current
gain. Includes new
gain test on
power transistors.

★ Crystal Diodes
checks forward to reverse
current ratio on all
diodes.

★ Selenium Rectifiers
checks forward and re-
verse currents.

Controls are accurately
set for each transistor
by referring to replaceable set-up chart on rear.
Test leads or socket provided for fast hook-up.

See your parts distributor.


ONLY \$17.95
Dealer Net
Cannot become
obsolete.
Approved by
leading
manufacturers.

Mfg. by SERVICE INSTRUMENTS CORP.

171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information

TRANSISTOR RADIO REPAIRS NOW EASY!

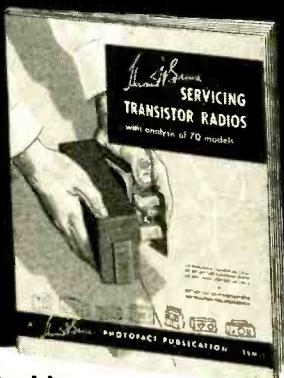


with this

NEW *Howard W. Sams* BOOK

"SERVICING TRANSISTOR RADIOS"

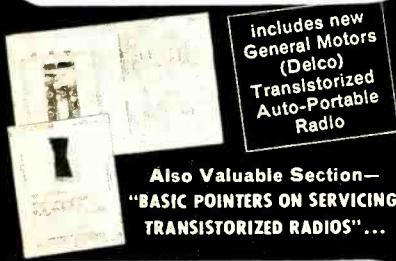COMPLETE ANALYSIS OF 70 POPULAR TRANSISTOR RADIO MODELS



COVERS LATEST MAKES AND MODELS

This book helps you earn big profits on Transistor Radio repairs—gives you complete, time-saving information—he helps you become an expert on transistorized radios! Complete data on 70 latest models is based on actual lab analysis of each set. You get the famous Sams Standard Notation schematics—accurate, big, legible; full photo views of each chassis, with all components identified; complete alignment instructions; complete parts lists with full replacement data—everything you need to be successful in fast-growing transistorized radio servicing. Here's a "must" book for your bench. Order it now!

152 pages; 8½ x 11" \$2.95
PRICE ONLY

SEE THIS BOOK AT YOUR SAMS DISTRIBUTOR OR MAIL COUPON

FREE TRIAL COUPON

Howard W. Sams & Co., Inc., Dept. 2-FFB
2201 E. 46th St., Indianapolis 5, Ind.

Send me Sams "Servicing Transistor Radios" for 10 days FREE examination. In 10 days I will pay for the book, plus few cents delivery cost, or return postpaid.

We pay delivery costs if you remit with this coupon; same return privilege.

Name _____

Address _____

City _____ Zone _____ State _____

(Outside U.S.A. priced slightly higher)

TECHNOTES (Continued)

did not point to a defective 6DQ6 because brightness and width were perfectly normal.—John B. Ledbetter

PHILCO 49-1002

Complaint was a wormy (grainy) picture. A clue to the trouble was found by moving a grounded metal plate around the chassis. The improvised TO VIDEO IF GRIDS 10K TO VIDEO OUTPUT CATH SHIELD


shielding wand showed feedback from the wire connecting the center arm of the contrast control (R300, 5,000 ohms) to the manual ave switch.

This video feedback was eliminated by running the lead in a shielded cable whose outer braid was grounded at both ends.—A. R. Clawson


MAGNAVOX CTA440AA

The set was suffering from critical vertical sync. To solve the problem, the sync pulse delivered to the PC integrator was increased by making the modification shown in the diagram.

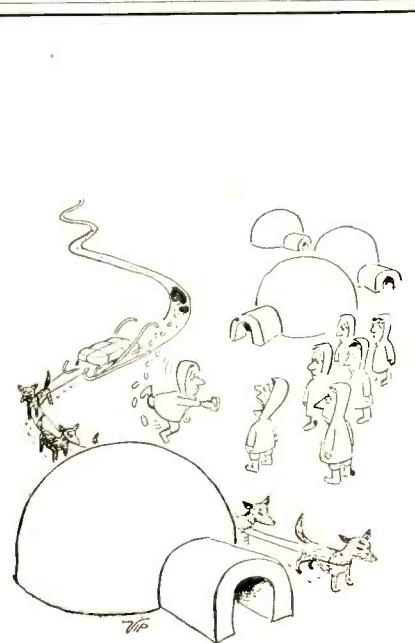
The vertical takeoff was across the 220-ohm portion of the cathode resistance (R311). This was changed to 470 ohms. The horizontal feed from the cathode of the phase splitter must be



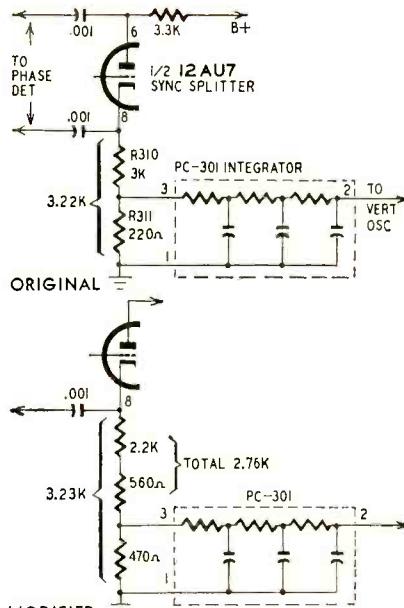"SERUM? Heck, we thought it was our order of JENSEN NEEDLES arriving."



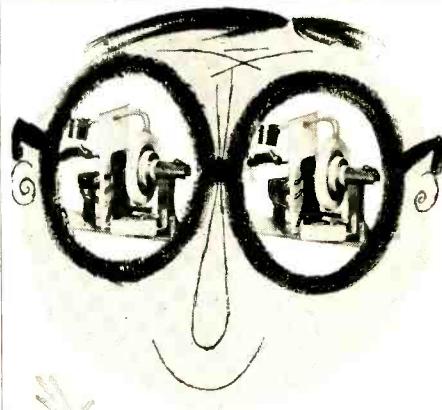about equal to that from its plate circuit. To make the cathode resistance nearly the same, R310 (3,000 ohms) was replaced with two resistors, 2,200 and 560 ohms. Total cathode resistance of the 12AU7 is now 3,230 ohms in place of the original 3,220 ohms. Locking and interlace are better.—Eugene Rollins. END



Seeing Double?

SURE . . . THEY LOOK ALIKE BECAUSE

THEY ARE EXACTLY ALIKE

Each Merit product of the same type is exactly the same as another—both in construction and appearance.

COMPARE IT WITH MERIT

Take a Merit product off the shelf. Compare it with any other similar product on the market. You'll find Merit is superior!



COMPARE IT WITH
MERIT
MERIT COIL & TRANSFORMER CORP.

MERIT PLAZA, HOLLYWOOD, FLORIDA

Business and People



J. R. Whiteside, executive vice president of Simpson Electric Co., Chicago, was named president.



P. R. Mallory where he was advertising and sales promotion manager.

Helen Staniland Quam of Quam Nichols Co., was elected president of the Association of Electronic Parts & Equipment Manufacturers Inc., the



first woman to head a major electronics industry trade group. Gail S. Carter (left) Merit Coil & Transformer Corp., was elected first vice president, and Robert E. Svoboda, Amphenol Electronics Corp., was elected second vice president. Kenneth Hathaway, Ward Leonard, was re-elected treasurer, and Kenneth C. Prince, executive secretary.

Victor Mucher, president of Clarostat Manufacturing Co., Dover, N. H., was honored on his 49th birthday by the Dover Rotary Club of which he is president. Friends, relatives and business associates surprised him in a takeoff of the TV program "This Is Your Life."



Photo shows Vic Mucher, seated, with his wife (right) and two sisters. Standing (left to right) are his two brothers, William and George; Austin C. Lescarboura, head of the agency which has handled Clarostat advertising for over 32 years, and Charles Golenpaul, vice president of Aerovox, an old friend.

INFRARED SNIPERSCOPE TELESCOPE & PARTS

See in the dark—without being observed. War surplus Sniperscope M-2. Contains the famous IP25A Image Tube. Govt cost about \$1200. Used for industrial plant security; research lab experiments; infrared photography; spectroscopy, etc. Instrument complete, ready to use. Includes Power Pack, infrared light source. Will operate from 6 V auto battery. Battery or transformer available.

Stock No. 85,053-EK.....Shipping weight approx. 12 lbs.....\$150.00
f.o.b. Barrington, N. J.

Send check or M.O.—money-back guarantee! Save still more money! Build your own Sniperscope! We will furnish instructions—parts, including: Power Packs, IP25A image tubes, light units, filters, etc. For details—request FREE Catalog "EK".



SPECIAL! SPECIAL!

INFRARED 1P25A IMAGE TUBE

Stock No. 70,127-EK.....\$9.95 pspd.
Send check or money order, money-back guarantee

COLOR TV TUBESCOPE

Saves time, effort in alignment of color dot pattern.
Stock No. 50,139-EK.....22 power.....\$24.50 pspd.
Send check or money order, money-back guarantee

GET FREE CATALOG "EK"

EDMUND SCIENTIFIC CO.
BARRINGTON, NEW JERSEY

SELF-SERVICE TUBE TESTER \$25 to \$50

Used-reconditioned complete with signs and floor model cabinets. Get into a profitable business with a minimum investment. Write, Ed Moerke, P. O. Box No. 264, Zion, Ill.

TELEVISION



AT HEALD YOU LEARN BY DOING IN MODERN ELECTRONICS LABORATORIES

HEALD
ENGINEERING COLLEGE

Established 1863
Van Ness at Post, RE
San Francisco, Calif.

Never before in American history has the need been so great for Trained Engineers and Technicians. No other type of training can compare with actual shop practice you get at Heald under expert instructors.

Bachelor of Science Degree, 27 Months

- Radio-TV Technician including Color TV (12 Months)
- Electronics Technician (12 Months)
- Industrial Electronics Technician (12 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans
DAY AND EVENING CLASSES

Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name _____

Address _____

City _____

State _____

the ALL NEW SENCORE Align-O-Pak TV BIAS SUPPLY



For
BLACK and WHITE
and COLOR

Just Dial any DC Voltage from 0 to 18 volts positive or negative—for AGC trouble shooting and alignment—Do away with messy bias batteries.

Completely isolated. Recommended by TV manufacturers. Wire wound control for calibration accuracy. For AGC trouble shooting, connect to AGC buss and vary voltage from 0 to 18 volts negative. If picture stabilizes at any voltage, AGC is defective. Complete with test leads.

MODEL BE3

\$7.85

Dealer Net
Leather Carrying Case...\$2.95

Mfg by

SERVICE
INSTRUMENTS CORP.

171 OFFICIAL RD. ADDISON, ILL.

POPULAR SENCORE PRODUCTS

- Transistor Tester
- Leakage Checker
- Filament Tester
- Handy "36"
- Vibra-Dapter

LEARN WHILE YOU SLEEP



100 page fact-filled illustrated instruction book—how to train while you sleep—results obtained...plus hundreds of time-saving hints. Price \$2.00. Satisfaction guaranteed. Sleep-Learning Research Assn. Box 24-H, Olympia, Washington.



CHRISTMAS IN JUNE!

**SEMI-ANNUAL
DOUBLE
BONUS
OFFER!**

BONUS #1

Your Choice
of any
POLY-PAK®
Listed Below

BONUS #2

Our Choice
\$5 WORTH
Assorted
RADIO PARTS

BOTH FREE WITH \$10 ORDER!

UNTIL JUNE 30

Our Usual \$1
POLY-PAKS®{ **88¢** EACH

<input type="checkbox"/> 100 CERAMIC CONDENSERS. 2 lbs.	<input type="checkbox"/> 6 TRANSISTOR SOCKETS. w/plate
<input type="checkbox"/> 30 DISC CONDENSERS	<input type="checkbox"/> 1000 PCS. HARDWARE. 2 lbs.
<input type="checkbox"/> 40 PRECISION RESISTORS. 1 lb.	<input type="checkbox"/> 6 SILICON DIODES.
<input type="checkbox"/> 10 TIMING MECHANISMS. 2 lbs.	<input type="checkbox"/> 8 GERMANIUM DIODES.
<input type="checkbox"/> WIRE STRIPPER-CUTTER.	<input type="checkbox"/> 10 POWER SWITCHES. asstd. 115 VAC
<input type="checkbox"/> 7 SCREWDRIVERS w/rack.	<input type="checkbox"/> 40 PRINTED CIRCUIT PARTS.
<input type="checkbox"/> 60 HI-Q RESISTORS. 1 lb.	<input type="checkbox"/> 60 COILS & CHOKES. 1 lbs.
<input type="checkbox"/> PIC TUBE BRIGHTENER. parallel.	<input type="checkbox"/> 2 SUB-MINI SOLENOIDS. 2 oz.
<input type="checkbox"/> 20 FERRITE TUNED COILS. 2 lbs.	<input type="checkbox"/> 20 VOLUME CONTROLS. 2 lbs.
<input type="checkbox"/> 5 BALLPOINT PENS. 1/2 lb.	<input type="checkbox"/> 15 ROTARY SWITCHES. 3 lbs.
<input type="checkbox"/> 50 FT. "ZIP" CORD. 2 ft. 10 in.	<input type="checkbox"/> 50 1/2" G.S. RECEP. JACKS. 3 lbs.
<input type="checkbox"/> 5 25' ROLLS "MICRO" WIRE.	<input type="checkbox"/> 6 FERRI-LOOPSTICK CORES. 1 1/2 lbs.
<input type="checkbox"/> 250 FT. HOOKUP WIRE. 3 lbs.	<input type="checkbox"/> SUN BATTERY. hundreds uses.
<input type="checkbox"/> 115/1/60 FAN MOTOR.	<input type="checkbox"/> 40 POWER RESISTORS. 2 lbs.
<input type="checkbox"/> SIGMA 10,000 ohm RELAY. 10,000 ohm	<input type="checkbox"/> 60 TUBULAR CONDENSERS. 1 lbs.
<input type="checkbox"/> MEN'S CIGARETTE LIGHTER.	<input type="checkbox"/> 60 TERMINAL STRIPS. BOARDS.
<input type="checkbox"/> 40 MOLDED CONDENSERS.	<input type="checkbox"/> 1 MINI-METER. 1 3/4 rd. 0-6 AMP. AC
<input type="checkbox"/> 150 RESISTORS. 2 lbs.	<input type="checkbox"/> 40 HI-Q CONDENSERS.
<input type="checkbox"/> 2 TRANSISTOR XFMRS.	<input type="checkbox"/> 8-PC. NUTDRIVER SET. 1 lb.
<input type="checkbox"/> 20 PRINTED CIRCUITS.	<input type="checkbox"/> TV MIRROR. 1 lb.
<input type="checkbox"/> 4 G-E IN69 DIODES.	<input type="checkbox"/> 50 ASSORTED KNOBS. 2 lbs.
<input type="checkbox"/> 6 AC-DC Cord sets	<input type="checkbox"/> 10 "POLY" BOXES.
<input type="checkbox"/> 5 DIAL-LITE ASSEMBLIES.	<input type="checkbox"/> 100 RADIO PARTS. 3 lbs.
<input type="checkbox"/> VEEDER-ROOT COUNTER. 0.9999.	<input type="checkbox"/> 75-PC. RESISTOR SPECIAL. 1 lb.
<input type="checkbox"/> 45 TUBE SOCKETS. 2 lbs.	<input type="checkbox"/> 2 PNP TRANSISTORS.
<input type="checkbox"/> MIDGET CRYSTAL MIKE.	<input type="checkbox"/> 65-PC. CONDENSER SPLC. 2 lbs.
<input type="checkbox"/> 4 POWER FILTER CHOKES. 2 lbs.	<input type="checkbox"/> 70 MICA CONDENSERS. 1 lb.
<input type="checkbox"/> "MICRO" MOTOR. 1 1/2 VDC.	<input type="checkbox"/> 15-PC. TWIST DRILL SET.
<input type="checkbox"/> 20 RAYTHEON KNOBS. 1 lb.	<input type="checkbox"/> 40 SUB-MINI RESISTORS.

AUTO SPEAKER KIT
Rear deck. 5 x 7 1/2" PM speaker. Switch. \$3.98
grille, hardware. \$3.98

6 x 9" SPEAKER KIT. only \$4.44

12" COAX HI-FI SPKR.
 range. 15,000 cycles
built-in extended range
tweeter & crossover. 6.8
ohm. v.c. Hwy Alinco mag.
Wt. 5 lbs. Reg. \$8.88
\$19.95

3-SPEED PICKUP
 With turnover cartridge. 2 sapphire needles. High output
hi-fi type. Reg. \$8.29

WORLD'S SMALLEST
RADIO
 KIT. 2 1/2 x 1 3/4 x 3/4" w/permability tuner,
diode. all parts, directions.
Reg. \$1.19
\$3.50

3-TUBE AC-DC AMPLIFIER
 Fully wired, ready for
use. Reg. \$5. Separate
volume and tone controls.
Lowest price \$2.99
ever!
TUBES. \$1.95 EXTRA

HOW TO ORDER Check items wanted. Return entire ad w/check or M.O. including sufficient postage; excess returned. C.O.D. orders. 25% down; rated net 30 days. Print name, address, amount money enclosed, in margin. (Canada postage, 45c 1st class, 28c ea. add'l. lb.) EXPORT ORDERS INVITED

"MICRO" METER SALE!

50-70% OFF!
In orig. boxes
EACH ONLY 1 1/8" SQUARE

<input type="checkbox"/> 0-15 VDC \$4.44
<input type="checkbox"/> 0-30 VDC 4.44
<input type="checkbox"/> 0-200 VDC 4.44
<input type="checkbox"/> 0-500 VDC 4.44
<input type="checkbox"/> 0-15 VAC 4.44
<input type="checkbox"/> 0-150 VAC 4.44
<input type="checkbox"/> 0-1 ma 4.44
<input type="checkbox"/> 0-100 ma 4.44
<input type="checkbox"/> 0-200 ma 4.44
<input type="checkbox"/> 0-500 ma 4.44
<input type="checkbox"/> 0-50 microamps	6.88
<input type="checkbox"/> 0-100 microamps	6.50
<input type="checkbox"/> 0-200 microamps	5.99
<input type="checkbox"/> 0-500 microamps	4.99

POCKET MULTI-TESTER

<input type="checkbox"/> 3 1/2 x 2 x 1 1/2" bakte	ite case. 100 ohms/volt. Zero adj. 0/15/150
<input type="checkbox"/> volt. 1000 ohms/volt. 0/1500 ohms/volt. 0/100,000 ohms. W/ test leads & battery. \$12 value	5 ohm, 10 watt resistor prevents TV circuit damage and simulates operating conditions.
	★ Two convenient current ranges — 0 to 2 amps and 0 to 10 amps. Test leads clip in place of fuse or fuse resistor.
	As Recommended by Leading Manufacturers

Mfg by **SENCORE** INSTRUMENTS CORP.

171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information

BUSINESS AND PEOPLE (Continued)

Joseph R. Owen was appointed manager of advertising and sales promotion for the General Electric Specialty Electronic Components Dept., Auburn, N. Y. He will be responsible for promotion activities on the department's high-fidelity audio components and specialized electronic materials and devices. He had been in charge of sales promotion in the G-E Television Receiver Dept.

Bob Mueller (left) and Leon Ungar (right), partners in Ungar-Mueller Sales Co., Southern California repre-



Business

Raytheon Manufacturing Co. Receiving Tube and Semiconductor Operations, Newton, Mass., was honored with the NATESA Friends of Service Management Award. In the photo, Frank Moch, executive director of NATESA, is shown



presenting the award to Norman B. Krim, vice president and general manager of Raytheon's receiving tube and semiconductor operations, while (left to right) F. B. Simmons, E. I. Montague, F. E. Anderson and J. A. Hickey, Raytheon executives look on.




sentatives for General Cement Manufacturing Co., Rockford, Ill., were presented with the Salesman of the Year Award by W. H. Dean (center), Western Sales Manager for General Cement, for outstanding achievement in total volume and largest percentage increase in distributor sales in the Western division.

**WILL YOUR REPLACEMENT
FUSE OR RESISTOR
BURN OUT AGAIN?**

Not if you use—
The NEW SENCORE
"FUSE-SAFE"
CIRCUIT TESTER

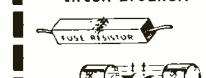Save costly call backs
by testing the circuit
before replacing
fuse, fuse resistor or
circuit breaker.



Individual scale for
each value fuse resis-
tor — no interpre-
tation, just read
in red or green area

★ Measures line current
and up to 1100 watts of
power at 115 volts using
line cord and socket.

★ Two convenient current
ranges — 0 to 2 amps and
0 to 10 amps. Test leads
clip in place of fuse or fuse
resistor.

★ 5 ohm, 10 watt resistor prevents TV circuit
damage and simulates operating conditions.

As Recommended by Leading Manufacturers

Mfg by **SENCORE** INSTRUMENTS CORP.

171 OFFICIAL RD., ADDISON, ILL.

Cut out this ad now for further information

STEREO LAYS AN EGG

Stereo can be wonderful but it just doesn't come naturally by the use of two of everything in sound. Unfortunately, this is what too many are realizing after substantial investments in this glamour child of high fidelity.

Stereo actually requires still higher fidelity than single channel systems due to the highly critical timing sequences which must be maintained until the separate signals reach each of the listeners' ears. Probably the most difficult problem in this regard is in the speaker system which now must reproduce and radiate these signals in the exact sequence required.

If this requirement is not met, and we have a virtual dissection of the input signals combined with random phasing and haphazard blending topped off by highly directive radiation, "stereo will most surely lay an egg," regardless of the cost involved.

With the use of a pair of the patented Karlson Enclosures and a couple of good wide range speakers, all these complicated requirements are automatically realized and you can have the very best in stereo at the most modest prices.

These enclosures are designed for 8, 12, 15 inch speakers and are available in kit, unfinished, and finished form at prices you can afford ranging from \$18.60 to \$174.00. Special models are also available for obtaining more optimum phasing with large multiple speaker systems.

Write to Karlson Associates, Inc., Dept. RE8X, 433 Hempstead Ave., West Hempstead, L. I., N. Y. for free catalog.

LEKTRO

131 Everett Ave.

CHELSEA 50, MASS.

BUSINESS AND PEOPLE (Continued)

Rek-O-Kut Co., Corona, N. Y., is offering a trip for two to the Brussels World's Fair and to Paris as the grand prize in a new dealer-consumer contest. In the photo, Cliff Shearer, marketing director of Rek-O-Kut, is being greeted



by Al Gross of Sabena Belgium Airlines and by Avery Yudin, Rek-O-Kut sales manager, on returning from Brussels where he arranged the trip.

Clark Gibb (right), president of The Paul Bunyan Chapter is welcomed back to The Representatives by Jules Bress-



ler, national president. The application of the Minnesota group was approved by the board of governors.

General Cement Manufacturing Co. purchased Microphone Division of Elgin

National Watch Co. and will move the operation to Rockford, Ill., where it will function as American Microphone Manufacturing Co., a division of GC-



Textron Inc. The present sales organization remains intact. Photo shows Stanley B. Valiulis (seated right), president of General Cement, signing the contract as Elgin and General Cement executives look on.

END

CORRECTIONS

In our *New Records* on page 129 of our February, 1958 issue, the line "Vox L-3 (16 2/3 rpm)" was misplaced; it should have appeared between "Borodin: Polovetsian Dances" and "Round the World, Round the Clock" and not at the top of the listing.

In the April issue (page 42) we announced a number of articles planned as features in the May Special Transistor Issue. Unfortunately, last-minute publishing difficulties and technical bugs prevented publication of all the articles. We deeply regret this and assure you these interesting articles on transistors will appear in early issues.

**Eliminate Battery Troubles
with the all new
BATTERY INSURANCE COMPUTER**

The revolutionary new electronic discovery—the BATTERY INSURANCE COMPUTER—attaches to the generator of your present car, controls your regulator and generator to give a quick charge or trickle charge to your present automotive battery automatically. Your present battery should serve you indefinitely with the aid of this all new concept of maintaining an adequate charge—

Computer controlled model \$7.50
Specify make and year of car—12 or 6 volt system

MacFARLANE INDUSTRIES
P.O. Box 33 Redondo Beach, Calif.


COLOR PRINTS 25¢
from your positive transparencies
2½ x 3½

Direct from laboratory to you—by mail
Custom quality—money back guarantee

COLOR FILM PROCESSING	COLOR PRINTS & DUPLICATES
Ansochrome, Ektachrome, 3½ x 5 \$.45 or Super Ansochrome— 8 x 10 2.00	
35mm 20 exp. 2/4, mtd \$1.25	35mm duplicates .25
Kodachrome-20 exp. 1.50	Sorry we do not ship COD

Write today for free mailer and complete price list!

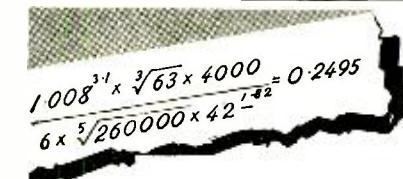Colorfax Laboratories • inc
1160-F Bonifant Street • Silver Spring, Maryland



A 66-inch Slide-rule for your pocket



The GENIAC® Calculator carries 66-inch spiral scales yet measures only ten inches fully extended and six inches when closed. Four to five figure accuracy can be relied on. It is indispensable to the scientist, research worker and student. Administrative staff and business men will find it of tremendous value for a host of estimating and checking calculations.

The GENIAC® Slide Rule solves multiplication, division, percentage calculation and gives 5 place logarithms.

You may use it for 30 days and if you are not satisfied repack and mail it back.

What our users say:

"It does all you claim—four or five figure accuracy without eyestrain or magnifiers. Half an hour's study is ample for its use." A.E.B.

"I use the GENIAC Calculator for all my slide rule work and need the extra digit which normal slide rules cannot give. I had to get one of my customers a GENIAC Slide Rule last month, after using mine in his office." E. & G.J. Textile Manufacturers.

Send for yours now—Only \$19.95 postpaid.

Oliver Garfield Co., Inc., RE-68

108 East 16th Street, New York 3, N.Y.



Slide Rule Closed

COMPLETE TRAINING FOR BETTER RADIO-TV SERVICE JOBS



Let these two world-famous Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Completely modern, prettily illustrated and written so you can easily understand every word, these books pave the way to fast, accurate service on any type of home radio-TV-electronic equipment ever made. Each book contains the latest data on the latest methods and equipment.

NOT a rehash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous *RADIO PHYSICS COURSE* and *MODERN RADIO SERVICE* were, for 20 years, more widely used for military, school and home study training than any other books of their type!

THE NEW Ghirardi RADIO-TV SERVICE LIBRARY

Almost 1500 pages and over 800 clear illustrations show step-by-step how to handle every phase of modern trouble-shooting and servicing.

1—Radio and Television Receiver TROUBLESHOOTING & REPAIR

A complete guide to profitable professional methods. For the novice, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs, to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable step-by-step service charts. 820 pages, 417 illus., price \$7.50 separately. See combination offer!

2—Radio and Television Receiver CIRCUITY AND OPERATION

This 669-page volume is the ideal guide for servicemen who want to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus., price \$6.75.

New low price... You Save \$1.25!

It is broken into lesson form and offers you as a "course." You'd regard these two great books as a bargain at \$8.00 or more. Together, they form a complete modern servicing library to help you work faster, more efficiently and more profitably.

Undoubtedly, this offer will buy them both for only \$12.00. You save \$1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them.

10-DAY FREE TRIAL

Dept. RE-68, RINEHART & CO., Inc.
232 Madison Ave., New York 16, N.Y.

Send books below for 10-day FREE EXAMINATION. In 10 days, I will either send price indicated (plus postage) or return books unpaid and owe you nothing.

Radio & TV Receiver TROUBLESHOOTING & REPAIR, price \$7.50 separately

Radio & TV receiver CIRCUITY & OPERATION, price \$6.75 separately

Check here for MONEY-SAVING COMBINATION OFFER... Save \$1.25.

Send both of above big books at special price of only \$13.00 for the two together plus postage. You save \$1.25. Payable at rate of \$4.00 plus postage after 10 days if you decide to keep books and \$8.00 a month thereafter until \$13 has been paid.

Name _____

Address _____

City, Zone, State _____

Outside U.S.A.—\$8 for TROUBLESHOOTING & REPAIR; \$7.25 for CIRCUITY & OPERATION; \$14 for both. Cash with order only, but same 10 day return privilege.

"TAB" Tubes Tested, Inspected, Boxed

New and used Gov't & Mfrs.
6 Mos. Guarantee! Surplus! No Rejects

	Receiving Color	Order No.	Part No.	Value
OA2	.80	68K10	.72	12AT6
OB2	.72	68K7	.95	12AT7
OC3	.84	6BL7	.95	12AU6
OD3	.80	6BN6	1.08	12AU7
OZ4	.50	6HQ6	1.19	12AX7
1AT	1.00	6G7	1.49	12AU6
1B5	.78	6C4	.49	12BA7
1RS	.78	6C5	.69	12BD6
1SA	.78	6BC6	.80	12BE6
1TA	.78	6CD6	1.40	12BF6
1U4	.69	6C7	.59	12BG6
1V4	.89	61S	.59	12BT7
1X2A	.68	616	.59	12BZ7
3Q4	.66	6K6	.59	12CU6
3QS	.86	6K7	.72	12CV6
3V4	.66	6L6	1.19	12D6
3V4	.99	654	.59	12SH7
SR4	1.25	658	.99	12SK7
SU4	.59	65A7	.69	12SK7
SV4	.89	65B7	1.19	12ST7
SZ4	.59	65C7	.89	12SG6
SAB4	.59	65G7	.79	1978
GAC7	.79	65H7	.69	258Q
GAG7	.85	65J7	.69	25L6
GAH6	.98	65K7	.72	25M4
GAJ6	.59	65L7	.72	25N7
GAL5	.59	65N7	2.51	2526
GAQ5	.66	65Q7	.74	EL34
GA57	3.00	65R7	.79	EL37
GAT5	.45	66A7	.59	25P6
GAU5	1.25	66B7	.89	25W4
GAU6	1.19	6V6	1.39	35Y4
GAX4	.79	6W6	.79	35Z5
GBA6	.59	6X6	.89	50A5
GBA6	1.00	6X5	.49	50C5
GBD6	.69	6Y6	.89	50L6
GBE6	.59	7N7	.89	KT66
GBG6	1.50	12A15	.59	75
GBH6	.79	12AQ5	.75	80

Write for Complete Tube List! Discounts to QTY. Buyers
TUBES WANTED! WE BUY! SELL & TRADE!

FINEST HI-FI RECORDING TAPE 1200 Ft.-7" Reel \$1.45 Lots of 3

Money Back Gtd. Highest quality controlled plastic base tape made by new "Erin" process. Precision coated & Slit. Grit. Constant output. Splicer Free. Fred. 7½ IPS No. 15Kc Oxide Wind In. Erin Quality "Mylar" 2400 Ft.—7" Reel Ferro S12.

NEW VRI "GE" PHONO CARTRIDGES

Postpaid 48 States!
160031/LP. OF 140617/78 DIAMOND \$16
160050/LP+78 TRI-PLAY SAPPHIRE \$6.59
160032/LP+78 TRI-PLAY DIAMOND & SAP \$18
160033/LP+78 TRI-PLAY DIAMONDS \$26

DIAMOND PHONO-NEEDLES! Postpaid 48 States! REGISTERED ONE YR. GUARANTEED BY THE MFG! ALL NEEDLES LISTED ARE MANUFACTURED BY TWO DIAMONDS: S14; DIAMOND & SAPPHIRE: S8. PLEASE SEND CARTRIDGE NAME & NUMBER

INFRARED RECEIVER ASSEMBLY USN/ U.S. Patent 2,441,441. Sewing Tech. ESCOPIC UNIT. CHANGES INVISIBLE INFRARED ENERGY INTO A VISIBLE IMAGE ON AN INBUILT SCREEN. INCLUDES INFRARED FILTER & RADIOACTIVE CHARGING SYSTEM. NO. 1000-8216 INCLUDES INST. CASE & DATA. SPECIAL \$21.

Write for BONUS CATALOG

NEW GTD RADIO & T.V. RECTIFIERS
35MA 40C @ \$2. For \$2: 65MA 45C @ .5 for \$2:
75MA 50C @ .5 for \$2: 125MA 55C @ .5 for \$4:
300MA 88C @ .8 for \$4: 350MA \$1.00 @ .8 for \$7:
400MA \$1.10 @ .5 for \$5: 550MA \$1.35 @ .4 for \$5:
65MA 260V \$1.10 @ .5 for \$5: 100MA 260V \$1.25
\$1.75 @ .55. Order 10. Postpaid 48 States!
MEGHRS. & DISTRS., WRITE FOR QTY. PRICES
NEW SILICON 500MA/100°C/140 V/400 PIV Rectifier Hmt Sealed with clip \$1.45. 8 for \$11.00. 25 for \$30.00.

NEW "TEKSEL" SELENIUM BRIDGE RECTIFIERS. ONE YEAR GTD!
FULL WAVE BRIDGE — WRITE for CATALOG
CURREN 18VAC 36VAC 72VAC 144VAC
CONT. 14VDC 28VDC 56VDC 118VDC
1AMP \$ 1.30 \$ 2.00 \$ 4.00 \$ 9.45
2AMP 2.15 3.00 6.20 16.50
3AMP 3.00 4.00 8.00 18.75
6AMP 4.15 6.00 18.75 36.15
10AMP 6.10 12.15 26.30 48.90
15AMP 9.90 19.00 40.00 66.60
24AMP 15.00 29.45 57.50 108.45

HAMS NEW TRANSISTORIZED "TABPAK"
D.C. Power Supply!!! Kit or Assembled. Filtered. Small in Size. Quiet Light Wgt. Input 12 to 14VDC. (Low Id Current). Output 450 & tap @ 250 VDC at up to 150 ma 65 watts.
"TABPAK" Assembled TR39CB \$35
"TABPAK" Kit TR39CK \$30

DC POWER for TRANSISTORS!
Transistors! Filtered Power Supply Kits used to power transistor circuits, amplifiers etc. Delivers 12VDC at 2AMPS. Filtered less than 0.5% ripple or 28VDC at 1A TPSK2 Kit \$18. TPSK2 Assembly w/ wire \$24.
1A 12VDC Transistor & Kit. W/ Bridge Rectifier for 12VDC @ 1AMPS or RECTRAN KIT RT1K \$4.50
RT1W Assembled & Wired \$8.50
RT2K Kit 12 or 18VDC at 6 AMPS \$9.00
RT2W Assembled & Wired \$14.75

KITS! "TAB" THE BEST KITS!

All Kits Contain Most Popular Values & Sizes
Kit 38 Precision Resistors
Kit 38 Switches
Kit 3 Transistor Transf.
Kit 150 Carbon Resistors
Kit 33 Panel Lamps
Kit 12 Electrolytic Cond's
Kit 15 Volume Controls
Kit 300 Sockets
Kit 500 Tubular Cond's
Kit 500 Lugs & Eyelets
Kit 10 Xmit. Mica Cond's
Kit 5 Lbs. Surprise Kit
Kit 10 Xmit. Mica Cond's
Kit 10 Encapsulated Plast. Fluid
Kit Volume Control Fluid
BUY 10 KITS GET ONE FREE EACH KIT 99¢

"TAB" TERMS: Money Back Guarantee!
Order 124th year and get one free
F.O.B. N.Y.C. Add shpg charges
or for C.O.D. 25% Dep. Prices
shown subject to change.
111JG LIBERTY ST. N. Y. 6 N. Y.
PHONE: RECTOR 2-6245
Write for Bonus Catalog



Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears.
UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

TELEVISION PICTURE TUBES, with complete physical and electrical specifications, are listed in this handy booklet. Monochrome, color and aluminized types are included.—Raytheon Manufacturing Receiving & Cathode-Ray Tube Operations, 55 Chapel St., Newton 58, Mass.

SILICON RECTIFIER HANDBOOK, catalog No. 67, deals exclusively with this manufacturer's line of silicon rectifiers. Theory of operation, manufacturing processes, characteristics and uses are shown.—Sarkes Tarzian Inc., Rectifier Div., 415 N. College Ave. \$1. Free to RADIO-ELECTRONICS readers.

ELECTRONIC COMPONENTS, 1958 catalog, 16-page 2-color booklet describes this

manufacturer's complete line of electronic test instruments and high-fidelity equipment in both kit and wired forms. Vtvm's, vom's, oscilloscopes, Geiger counter, preamplifier, amplifiers and speaker systems are included.—Electronic Instrument Co. Inc., EICO, 33-00 Northern Blvd., Long Island City, N.Y.

TEST INSTRUMENTS bulletin AP12 describes and illustrates the TV analyst, tube checkers and test instruments for in-the-home service and shop use.—B & K Manufacturing Co., 3726 N. Southport Ave., Chicago 13, Ill.

VARIABLE TRANSFORMER CATALOG, bulletin P258G. This 100-page book is filled with product information, engineering data, outline drawings, connections, ratings, and charts and illustrations of all standard 50/60-cycle Powerstats as well as some special-use types.—Superior Electric Co., Dept. P258G, Bristol, Conn.

HIGH-FIDELITY COMPONENTS are offered in an illustrated 12-page catalog. Tuners, amplifiers, speakers and speaker systems are presented.—Altec Lansing Corp., 1515 S. Manchester Ave., Anaheim, Calif.

REACTANCE SLIDE RULE solves problems such as resonant frequency, capacitative reactance, inductive reactance and coil Q, and dissipation factor. Useful for solving problems of filter design, oscillator tank circuits, trans-

What articles would you like to see published in RADIO-ELECTRONICS?
Maybe you're the man to write them. Ask for an author's guide.

RADIO-ELECTRONICS

154 West 14th Street

New York 11, N. Y.

SPECIAL INTRODUCTORY OFFER!

VACO

Red Cap
"At Your Service"

Screw Drivers

Here's your chance to get a beautiful 5-piece screw driver set at a true bargain price! All the most popular sizes (including No. 2 genuine Phillips) plus—a FREE tool hanger board complete with patented, adjustable hanger hooks for holding your most frequently used tools. Here's how:

FREE Tool Hanger Board
and Patented Hanger Hooks

Just mail in the coupon enclosed in the RC 15 Boxed Set and VACO will send you this 12" x 24" perforated masonite panel and set of hanger hooks at no charge.

See Your Jobber, Today!

VACO PRODUCTS CO., 317 E. Ontario St., Chicago 11, Ill.

In Canada: Atlas Radio Corp., Toronto 19, Ontario

TECHNICAL LITERATURE (Continued)

former and amplifier design.—Shure Brothers Inc., 222 Hartrey Ave., Evanston, Ill. 75c.

TERMINALS AND CONNECTORS for high-temperature applications are detailed in catalog section HT. Comprehensive specifications are presented for each type.—AMP Inc., Harrisburg, Pa.

SILICON RECTIFIER HANDBOOK, tells how they are made, gives theory of operation, engineering design notes, and basic rectifier circuits in the first section of an illustrated 64-page catalog 111. In the second section numerous types of these units with specifications and circuits are described.—Audio Devices Inc., Rectifier Div., 620 E. Dyer Rd., Santa Ana, Calif. \$1.

RECORDING TAPE. An illustrated folder "Which Tape Type are You?", offers general information on magnetic recording tape and helps you select the type tape that best suits your needs.—Minnesota Mining & Manufacturing Co., 900 Bush St., St. Paul 6, Minn.

CRYSTAL FILTERS. bulletin XT-455, is a 2-color 4-page brochure outlining a line of stock and special miniaturized quartz crystal filters. Technical data, typical and representative curves of the filters are shown. Symmetrical bandpass, wide-band, narrow-band, and asymmetric or single-sideband filters are described.—Burnell & Co. Inc., 10 Pelham Parkway, Pelham Manor, N. Y.

RADIO-ELECTRONICS pays \$3.00 for good cartoon ideas and \$15 and up for finished work.

RADIO-ELECTRONICS
154 West 14th St., New York 11, N.Y.

DIGITAL COMPUTER KIT



Build 100 transistor computer circuits and work with them! Basic units can be built within hours. Assemble them into computers and operate. The language of computers is explained and projects included. You will receive 22 transistors and 200 electrical parts. \$59.50 plus postage. Twelve other kits available.

Partial list of courses:

- C1 Elementary relay brains \$12.50
- C2 Elementary digital computers \$24.50
- C3 Elementary analog computers \$19.50
- C4 Computer Master 50 lessons and projects (digital voltmeter, digital ohmmeter)
- C15 Electronics, 40 lessons and 3 text books. \$22.50 down and \$10 for 5 months.
- Complete catalog.

EBE Inc., 1015 Atkin Ave.
Salt Lake City 6, Utah
 Send one transistor computer kit
 Enroll me in course.....
 Enclosed \$.....

Name and address attached

HI-FI TRANSFORMERS made by Partridge are presented in a 4-page leaflet. 20- and 30-watt models are offered. Complete specifications are included.—M. Swedgal, 259 Broadway, New York 7, N. Y.

APPLICATION NOTES for using silicon junction rectifiers to protect sensitive current devices are presented in Vol. 1, No. 1 of *Semi-conductor Application Notes*. This issue illustrates how the nonlinear characteristics of silicon diodes, in both the forward and Zener operating regions, make them ideally suited to protecting ac and dc measuring instruments.—Hoffman Electronics Corp., Semiconductor Div., 930 Pitner Ave., Evanston, Ill.

TRANSFORMERS AND COILS. catalog 630, lists the entire line of transformers, coils and components for radio TV, industry, amateur, transistor and military applications produced by this firm. Fully illustrated, 24 pages.—Thordarson - Meissner Manufacturing Co., 7th and Belmont, Mt. Carmel, Ill.

VHF-UHF EQUIPMENT including instruments and accessories for signal and pulse generation, impedance measurement, detection, modulation, attenuation and transmission through shielded coaxial lines detailed in this illustrated booklet.—General Radio Co., 275 Massachusetts Ave., Cambridge 39, Mass. END

Examine FREE



Prentice-Hall ELECTRONICS & UHF LIBRARY

Edited by
W. L. EVERITT

5 VOLUMES 1662 ILLUSTRATIONS

Pay Easy Installments If You Keep the Set

Turn to this new, up-to-date Library with complete confidence, for dependable facts on any phase of modern electronic theory and practice. These volumes, by outstanding authorities, give you thorough guidance—clearly written, logically arranged, profusely illustrated.

Electronic Fundamentals and Applications

By Prof. John D. Ryder,
Dean, College of Engineering, Michigan State University
Complete, logical, easy-to-follow treatment of (a) physical principles underlying electron tubes, (b) characteristics of vacuum tubes, (c) all basic tube circuits. Includes: Electron Ballistics, Cathode-Ray Tubes, Emission of Electrons, Space Charge in Vacuum Tubes, Diode Rectifiers, Triodes, Multi-Element Tubes, Small-Signal Amplifier Circuits, Audio-Frequency Amplifiers, Radio-Frequency Amplifiers, Oscillator Circuits, Modulation Systems, Wave-Shaping Circuits, Gaseous Conduction, Gas Diodes, Gas Control Tubes and Circuits, Photoelectric Cells, Solid-State Electronics.

Electromagnetic Waves and Radiating Systems

By Prof. Edward C. Jordan,
Head, Dept. Electrical Engineering, Univ. of Illinois
Covers entire field of electromagnetic engineering. Includes propagation as well as radiation and transmission. Full treatment of UHF transmission lines, wave guides, antennas, slot antennas, radiation and diffraction, ground-wave and sky-wave propagation.

Ultra High Frequency Engineering

By Thomas L. Martin,
Head, Dept. of Electrical Engineering, Univ. of Arizona
Theory and technique of ALL the new fields of electronic engineering: Radar, Telemetering, Electronic computing, Facsimile, Television, Blind landing systems, Pulse time modulation, Ionosphere measurements, and the others.

Networks, Lines and Fields

By Prof. John D. Ryder,
Dean, College of Engineering, Michigan State University
Network transformations and theorems, Resonance, Impedance transformation and coupled circuits, Filters, General transmission line, High-frequency line, Equations of the electromagnetic field, Radiation, Transmission and reflection of plane waves at boundaries, Guided waves between parallel planes, Wave guides.

Elements of Television Systems

By George E. Auner, University of Illinois
Complete basic theory, plus current practice, covering: Closed TV systems, Commercial Telecasting Systems, Color TV Systems. Gives clear exposition of all phases of picture transmission, including the new technique of dot interlace.

SEND NO MONEY—EXAMINE FREE

Just mail coupon below to get complete 5-Volume Set on 10 DAYS' FREE TRIAL. If not completely satisfactory, return in ten days and owe nothing. Or keep the set and pay only \$7.50 down and \$8 a month for five months until full price of \$47.50 is paid. Decide for yourself—without risk or obligation—just mail coupon to examine Library ten days free.

Prentice-Hall, Inc., Dept. 5744-H1
Englewood Cliffs, N.J.

Send me the Prentice-Hall ELECTRONICS & UHF LIBRARY (5 Volumes) for ten days' free examination. If fully satisfied in ten days I will send you \$7.50 plus few cents postage and then \$8 a month for five months until full price of \$47.50 is paid. Or I will return the Library in ten days and owe nothing.

Name.....

Address.....

City and State.....


NOW H. A. Hartley offers you a complete practical guide to audio design. . .

H. A. Hartley's new book -- AUDIO DESIGN HANDBOOK

saves you the time of wading through masses of technical data to ferret out the core of practical design information you're searching for. He steers you away from the shoals of tricky common mistakes and misconceptions. Hartley shows you how audio design can be done easily and simply! He tells you how to avoid blind alleys by first determining **WHAT YOU WANT**—and then building within the limits of your own goal. The book covers amplifiers, feedback, power supplies, speakers and enclosures, dividing networks, measurements and testing, plus a few salty personal observations on the wrong directions hi-fi has taken. Easily the most stimulating and helpful book on audio designing ever written!

You can get this deluxe, beautifully-bound \$5 book—the latest addition to the G/L Audio Hi-Fi Book Club—for only \$3.75! Read how you can join the club, get this book and save money.

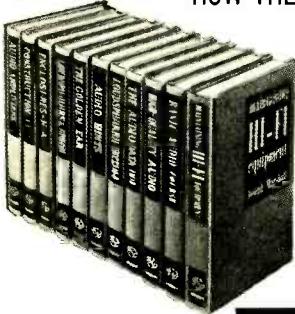HOW THE G/L AUDIO HI-FI BOOK CLUB CAN HELP YOU



- Shows you the way to more pleasure in hi-fi if it's your hobby—more profits if it's your profession.
- Offers you the benefits of the knowledge and experience of top writers like Crowhurst, Hartley, Dorf, Marshall and others.
- You can build a complete hi-fi library in easy stages—on the NO-RISK INSPECTION PLAN.
- You **SAVE \$1.25–25%–ON EACH BOOK YOU BUY!**

HOW TO ENROLL

- Select the book you want on the coupon below.
- SEND NO MONEY NOW—we send you the book on a NO-RISK inspection plan.
- If you like the book you keep it and pay—not the \$5.00 retail price—but the **SPECIAL MEMBER'S RATE OF ONLY \$3.75**—and we pay postage.
- If you don't want the book, simply send it back—no fuss, no obligation, no high pressure—**AND NO SALESMAN WILL CALL.**
- You receive a new book on the same NO-RISK INSPECTION PLAN every four months.
- You need take a minimum of only four books during the whole membership period. No time limit—no long term contract. You may cancel anytime after that.

Each book handsomely bound with a deluxe gold-leaf stamped cloth cover.

OTHER BOOKS ALREADY PUBLISHED

Order Audio Design Handbook or any other book.

ELEMENTS OF TAPE RECORDER CIRCUITS

By Herman Burstein and Henry C. Pollak
Answers all the questions a hi-fi fan would ask about tape recorder circuits. Includes a chapter on design for modifying your own equipment.

UNDERSTANDING HI-FI CIRCUITS

By Norman H. Crowhurst
Mr. Hi-Fi himself tells you how to get hi-fi tailored to your own needs. Tells you which type of components to choose for the system you want and can afford.

Other books are in preparation

NO-RISK COUPON

GERNBSACK LIBRARY, Inc., Dept. 68C
154 West 14th St., New York 11, N.Y.

Enroll me in the G/L Audio Hi-Fi Book Club. Begin my membership with the book checked below.

- AUDIO DESIGN HANDBOOK**
 UNDERSTANDING HI-FI CIRCUITS
 BASIC AUDIO COURSE
 MAINTAINING HI-FI EQUIPMENT
 ELEMENTS OF TAPE RECORDER CIRCUITS

Name _____

Street _____

City _____ Zone _____ State _____

MAIL THIS
COUPON
TODAY



SEND NO MONEY



H. A. Hartley
Popular author of articles
in RADIO-ELECTRONICS
and RADIO & TV NEWS.
Hailed on both sides of
the Atlantic as a brilliant
audio engineer.

Books



ALL ABOUT ELECTRICITY, by Ira M. Freeman. Random House, Inc., 457 Madison Ave., New York 22, N.Y. 7 x 9½ inches, 141 pages. \$1.95.

This is one of an "all-about" series that includes birds, flowers, stars, etc. It is intended for "readers of 10 to 15" but perhaps not for youngsters who already happen to experiment with transistors, build portable radios or operate ham stations.

With helpful illustrations, the book is simple, effective and as clear as possible for such a topic. Principles of the telephone, battery, electromagnetism, power transmission and radio are skillfully treated in a way to attract the interest of future scientists. Color TV appears briefly, and transistors are also mentioned.

For the benefit of young minds, the author has dramatized the basic discoveries of Franklin, Galvani, Oersted, Bell, Marconi and others. These stories introduce the reader to the principles and applications that follow.—IQ

SYLVANIA SERVICE INFORMATION, Vol. 2. Sylvania Electric Products Inc., Radio & Television Div., Service Dept., Batavia, N.Y. 11 x 17 inches, 138 pages. \$3.50.

A comprehensive manual of service information, schematic diagrams, production changes, test and alignment points and parts lists for Sylvania radio, TV and audio equipment produced between May, 1954, and December, 1957.—RFS

UNDERSTANDING ELECTRONICS, by John Lewellen. Thomas Y. Crowell Co., 432 4th Ave., New York, N.Y. 5½ x 8¼ inches. 213 pages. \$2.75.

This most recent of a series of books intended to give the nontechnical beginner an insight into some of the involved mechanics of the modern world presents a fascinating picture of electronics. Starting off with "Can you imagine anything changing its direction 500,000 times a second?" the author takes the reader through a tour of basic electricity, magnetic fields, how electrons behave, how the parts of radio work and even describes transistors. For the layman who wants to know what makes things tick.—LS

MOST-OFTEN-NEEDED 1958 TELEVISION SERVICING INFORMATION. Compiled by M. N. Beitman. Supreme Publications, 1760 Balsam Rd., Highland Park, Ill. 8½ x 10½ inches, 192 pages. Price \$3.

SCHOOL DIRECTORY


ENGINEERING DEGREES



E.E.
Option Electronics
or Power

Earned through
HOME STUDY

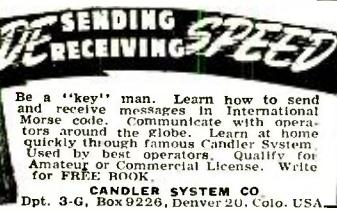Residence Classes Also
Available
**PACIFIC INTERNATIONAL
UNIVERSITY**
(Operating as a College of
Engineering only at present)
5719-M, Santa Monica Blvd.,
Hollywood 38, Calif.



Be a "key" man. Learn how to send and receive messages in International Morse Code. Communicate with operators around the globe. Learn at home quickly through famous Candler System. Used by best operators. Quality for Amateur or Commercial License. Write for FREE BOOK.

CANDLER SYSTEM CO.
Dept. 3-G, Box 8228, Denver 20, Colo. USA.

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, scientific investigators, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in electronics in 20 months. B.S. in electronic engineering obtainable. ECPD accredited. G.I. approved. Graduates in all branches of electronics with major companies. Start September, February, December. Complete school graduate or equivalent catalog.


**VALPARAISO TECHNICAL
INSTITUTE**

Dept. C Valparaiso, Indiana



ELECTRONICS

ENGINEERING DEGREE IN 27 MONTHS

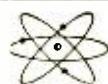

Prepare for unlimited opportunities in electronics! B.S. degree in 27 months, mathematics, electrical engineering, TV, advanced radio theory. Modern labs. Low tuition, earn board. Also Aero., Chemical, Civil, Electrical, Mech. Engineering. B.S. degree in 36 mos. in Mgmt., Chem., Physics, etc. prep courses. G.I. appro. 20 bridges, dorms, gym. Enter June, Sept., Dec., March. Catalog, *Keeping Pace With Progress*.

INDIANA TECHNICAL COLLEGE

1568 E. Washington Blvd., Fort Wayne 2, Ind.



... have higher incomes ... advance more rapidly. Grasp your chance for a better life. Share rewards awaiting college men. Important firms visit campus regularly to employ Tri-State College graduates. Start any quarter. Approved for Vets.

Bachelor of Science Degree in 27 months

Complete Radio Engineering courses (TV, UHF, FM, Electronics). Also Mechanical, Civil, Electrical, Chemical, Aeronautical Engineering in 36 months a B.S. in Business Administration (General Business, Accounting, Motor Transport Management Majors). Superior students faster. More professional class hours. Small classes. Enrollment limited. Beautiful campus. Well-equipped labs. Prep courses. Enter June, Sept., Jan., Mar. Earnest, capable students (whose time and budget require accelerated courses and modest costs) are invited to write Ivan McCarthy, Director of Admissions for Catalog and "Your Career in Engineering and Commerce."



2468 College Avenue, Angola, Indiana

Your choice of school
is highly important
to your career in



INDUSTRIAL
ELECTRONICS



RADIO-
TELEVISION



ELECTRONICS
COMMUNICATIONS

Become an
**ELECTRICAL
ENGINEER**
or an
**ENGINEERING
TECHNICIAN**
at

MSOE in Milwaukee

Choose from courses in:

ELECTRICAL ENGINEERING

Bachelor of Science degree in 36 months—

Communications of Electrical Power.

ENGINEERING TECHNOLOGY

Associate in Applied Science degree in 18 months—
Electronics Communications, Electrical Power, or Computers.

MSOE — located in Milwaukee, one of America's largest industrial centers—is a national leader in electronics instruction—with complete facilities, including the latest laboratory equipment, visual aid theater, amateur radio transmitter—offers 93 subjects in electrical engineering, electronics, radio, television, electrical power, and electricity.

Advisory committee of leading industrialists. Courses approved for veterans. Over 50,000 former students. Excellent placement record. Previous educational, military, and practical experience is evaluated for advanced credit.



QUARTERS BEGIN SEPTEMBER,
JANUARY, MARCH, JULY

Choose wisely—your future
may depend on it. Mail coupon today!

MILWAUKEE SCHOOL OF ENGINEERING

Dept. RE-658, 1057 N. Milwaukee St.
Milwaukee, Wis.

Please send free illustrated career booklet
(please print)

I'm interested in _____

Name _____ Age _____

Address _____

City _____ State _____

I am I am not eligible for veterans benefits

(discharge date) _____

STAN-BURN

CATHODE RAY TUBE SPECIALS

ONE YEAR GUARANTEE

G E	Type	STAN	BURN	G.E.	Type	STAN	BURN
S15-80	1GP1A	\$10.00	24.75	17AP1A	\$18.00		
19-10	1GP1A	13.95	37.00	10AP1A	24.00		
20-35	1GP1A	11.50	26.35	20GP1A	18.95		
20-75	1GP1A	13.75	33.00	20GP1A	25.00		
33-75	1GP1A	13.75	36.00	21GP1A	20.15		
33-75	1M4	14.50	29.75	21GP1B	23.25		
32-20	1GP1A	15.25	30.90	21GP1B	21.15		
23-50	1GP1A	15.75	29.75	21GP1	22.00		
28-40	1GP1A	16.75	34.85	21GP1A	25.00		
31-50	1GP1A	16.25	28.30	21GP1	21.00		
31-50	1GP1A	16.25	33.60	21ZP1B	26.00		
23-50	1GP1A	15.00	100.00	21GP1B	26.00		
28-40	1GP1B	16.75	34.85	(6 mos. quarr.)			
30-75	1GP1A	20.50	48.40	21GP1A	38.00		
33-90	1GP1A	21.50	50.00	21GP1B	39.00		

*ALUMINIZED—INQUIRE FOR ANY TYPE, TYPE NOT LISTED—STAN-BURN CRT TUBE, THE STAN-BURN CRT IS MADE BY LINCOLN. All orders of 6 or more STAN-BURN CRT are subject to additional 10% discount. PRICES SUBJECT TO CHANGE WITHOUT NOTICE.

WHY PAY MORE?

- HI-FI COMPONENTS • KITS
- RECORD PLAYERS • TAPE RECORDERS • TUNERS •
- AMPLIFIERS • SPEAKERS •
- ELECTRONIC PARTS & TUBES • Etc.

Top brand nationally adv. merchandise in this and other Radio & TV mags. is yours at low, low cost. Send us your list. Give Mfr's name and Model No. of item. Write for '58 catalogs to Dept. RE-6 today.

GENERAL ELECTRIC RECEIVING TUBES

Brand New—1 Year Guarantee—Boxed

024	.83	6K6GT	1.13	125A7	1.45
125GT	1.38	6S5GT	1.25	125K7	1.35
5U4GA	1.38	6S6GT	1.13	125K7	1.35
6AG5	1.25	6W4GT	1.15	35W4	.68
6AU6	1.00	12AU7	1.15	35Z5GT	.90
6BQ5GA	2.00	12BA6	.95	50C5	1.03
6BG6GA	3.10	12B6B	1.03	50L6GT	1.15

ADDITIONAL 10% DISCOUNT IN LOTS OF 10 ASSORTED!

WRITE FOR COMPLETE PRICE LIST

SAVE UP TO \$100 A YEAR ON TV REPAIRS

Amazing new book "How To Repair Your Own TV Set" gives you everything you have to know to spot TV trouble. Shows how to fix it "presto." Everything you need to understand and start fixing diagrams. Latest up-to-date information on tuner changes, antennas, tube location charts, trouble shooting guides, plus list of tube types and prices. Only \$1.00 plus 10¢ for postage.

HI-FI DIAMOND NEEDLES—1 Yr. Guar.

Diamond needles reduce record wear and needle noise thus retaining full frequency response and tonal qualities of your records for a longer period of time.

SINGLE DIAMOND needle.....\$7.95

DIAMOND SAPP dual needle.....\$8.95

Shipment F.P.D. (specify cartridge make)

RECORD CHANGERS

COLLARO TC-340 4 speed changer...\$36.75

COLLARO RC-440 4 speed changer...40.67

COLLARO TC-540 4 speed changer...45.57

GARRARD RC-88 4 speed changer...53.41

GARRARD RC-98 4 speed changer...66.15

FREE wood mounting base, record wiping cloth and 45 RPM spindle with all orders for Collaro and Garrard changers, with this ad.

VM 4 SPEED HI-FI CHANGER—Model 1210 with Ronette or Astatic flip-over cartridge.....\$22.95

MONARCH Model UABU 4 SPEED AUTO. INTERMIX CHANGER less cartridge...\$19.95

WEBCOR 4 SPEED CHANGER with turn-over cartridge.....\$23.95

RONETTE (phono fluid) cartridge flip-over type.....\$2.98

SONOTONE cartridge, flip-over.....\$2.98

45 RPM SPINDLE for V.M. or Monarch...\$1.98

WOOD MOUNTING BASE for V.M. or Monarch.....\$3.95

MOUNTING BOARD unfinished for V.M. or Monarch.....\$1.50

NEW GENERAL ELECTRIC HI-FI VARIABLE RELUCTANCE CARTRIDGE. Replaces discontinued RXP050 type. Full range reproduction 20-20,000 cycles. Four gram tracking force for minimum record and stylus wear.

4G050—Dual Sapphire needles.....\$8.77

4G052—Diamond, Sapphire needles...\$18.99

KITS!

We stock the following manufacturers' complete line of kits—see reference pages

EICO see pages 23-24
QUALITY see page 126
ARKAY
PRECISE
BOGEN
GARMINES

All domestic orders will be shipped prepaid. Send us your list. Order by Mfr. and Model No. of item.

\$20 WORTH OF ELECTRONIC PARTS IN GRAB-BAG consisting of: Porcelain sockets, coils, speaker, transformer, cond. ONLY.....\$1.98 (plus 50¢ postage)

YOU NAME IT—WE HAVE IT

Complete line of T.V. & Radio receiving tubes, coils, trans., controls, antennas & accessories—No Minimum Order—**DEALER DISCOUNTS!** Thousands of satisfied Hi-Fi enthusiasts and dealers will vouch that STAN-BURN GIVES THE BEST DEAL POSSIBLE!

EXPORT QUOTATIONS AND OFFERS INVITED.
Term: 10-30 days with order. Balance C.O.D. All prices F.O.B. NEW YORK Warehouse.

Write for our latest price list and Hi-Fi Catalog. RE-6. All Prices Subject to Change Without Notice.

STAN-BURN RADIO and ELECTRONICS CO.
558 CONEY ISLAND AVE. • B'KLYN 18, N. Y.

BOOKS (Continued)

A compilation of original manufacturers' service information covering nearly 520 models of television receivers produced by 11 firms.

TRANSISTOR ELECTRONICS, by David DeWitt and Arthur L. Rossoff. McGraw-Hill Book Co., Inc., 330 W. 42 St., New York 36, N. Y. 6 x 9 inches, 381 pages. \$8.

According to these authors, the purpose of this book is to teach. This it should do very well, for there is a good balance between basic theory and practical circuit design. The text is the result of a successful technical course, and it is written at the level of the senior student or graduate engineer.

The first chapters touch on crystal structure and junction theory. Following are discussions of transistors for low frequency, audio power, high frequency, switching, mixing, radio reception, etc. Chapters are divided into small sections with suitable subheadings for convenience in locating a desired topic.

The text is easy to follow if the reader knows his college math. Equivalent circuits and useful diagrams show how gain, power and impedance may be controlled and varied. The circuits are basic, leaving specific component values unlisted. Final chapters cover special transistor types, some not yet in wide commercial use, and the important subject of transistor noise.—IQ

COMMERCIAL RADIO OPERATOR'S LICENSE GUIDE, by Martin Schwartz. American Electronics Co., 1203-05 Bryant Ave., New York 59, N.Y. 6 x 9 inches. Elements 1 and 2, 18 pages, 75c. Element 3, 122 pages, \$1.75.

Study guides to prepare candidates for commercial radiotelephone first- and second-class licenses and radiotelephone third-class permits to pass Elements 1 (Basic Law), 2 (Basic Operating Practice) and 3 (Basic Radiotelephone) of the FCC examination. The guides contain study questions with clear simple answers to each. They present all diagrams and types of problems likely to be required on the exam. Each element concludes with a sample FCC type test with answers.

RADIO AMATEUR'S HANDBOOK. American Radio Relay League, Inc., W. Hartford, Conn. 35th Edition, 6 1/2 x 9 1/2 inches, 746 pages. \$3.50 in US, \$1 in possessions. \$4.50 elsewhere.

The radio bible has been brought up to date with new information on transistors, antennas, receivers and auxiliary equipment. Whatever your need—Conelrad device, optimum spacing for beam elements, help in learning the code, or review of theory—simply consult the index and turn to the indicated page.

As always, emphasis is on build-it-yourself apparatus. Photos, schematics, charts and detailed instructions all help to make it easier. A must for the engineer, technician and ham.—IQ END

BE QUALITY WISE...BUY QUAL-KITS!



HI-FI AMP. KIT

Complete 6 tube-10 watt beam power output, built-in pre-amp, 5 position selector switch, 3 position record equalization, LP, RIAA, Eur. Response 1/2 db. 20-20,000 cps. Output 10 watts at less than 2% IM. Low noise level and harmonic distortion.

\$28.50

Every kit complete with 28 page fully illustrated instruction and assembly manual. Cover and legs optional.

\$28.95*

Write for FREE catalog and name of nearest dealer carrying these remarkable units.

*Add 10 percent for new federal tax



HI-FI AM-FM TUNER KIT

Advanced 7 tube circuit plus Rectifier for full sensitivity and selectivity. Distortion less than 1%. Sensitivity is 5 uv for 30 db quieting on FM. 25 uv AM. Armstrong FM Circuit with limiter. Foster-Seeley Discriminator. 20-20,000 cps response. Full AFC control—no drift. Easy assembly.

\$28.95*

Write for FREE catalog and name of nearest dealer carrying these remarkable units.

QUALITY-ELECTRONICS

319 Church St. Dept. RE-6 New York 13, N. Y.

ORDER by MAIL and SAVE! TV PICTURE TUBES

10BP4	\$ 7.95	17BP4	\$10.95	21AMP4	\$19.95
12LP4	8.95	17CP4	17.00	21ATP4	20.95
11B-CP4	9.95	17GP4	17.60	21AP4	20.95
16DPA	14.95	17HP4	13.60	21EP4	14.95
16EP4	15.90	17LP4	13.60	21FP4	15.95
16GP4	15.90	17QP4	11.95	21WP1	17.30
16KP4	10.95	17TP4	19.30	21YP4	15.95
16LP4	10.95	19AP4	19.30	21ZP4	14.95
16RP4	10.95	20CP4	13.90	21CP1	23.95
16WP4	15.20	20HP4	17.95	21DP4	26.95
16TP4	10.95	21AP1	22.10	27EP4	39.95
17AVP4	15.20	21ALP1	20.95	27RP1	39.95

27"=4 month guarantee—all others 1 year. Aluminized Tubes \$5.00 more than above prices. These prices are determined to include the return of an acceptable similar tube under vacuum.

ALL PRICES FOR CHICAGO, ILLINOIS. Delivered F.O.B. Chicago. Old tubes are non-refundable. Inside Back Cover
Turned, refundable at time of return. 25% required on C.O.D. shipments. Old tubes must be returned prepaid. We ship anywhere.

WRITE FOR COMPLETE LIST.

PICTURE TUBE OUTLET

3032 Milwaukee Ave., Chicago 18, Ill.
Dickens 2-2048

CRYSTAL CONTROLLED CONVERTERS POLICE • FIRE • COMMERCIAL



✓ Precision—Stability

✓ Sensitivity

✓ Easy Installation

\$32.50

A compact converter supplied with commercial tolerance crystals, self contained automatic noise limiter. Also models with squelch. Ideal for mobile or home use.

TUNERS

Enjoy FM Programs
While You Drive.

- FM BROADCAST
- 30-50 MC
- 108-176 MC

from **\$22.50**

WRITE FOR LITERATURE



KUHN ELECTRONICS
20 GLENWOOD CINCINNATI 17, OHIO

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

- Aerovox Corp. 88
 Allied Radio Corp. 15, 95
 Amperex Electronic Corp. 112
- B & K Manufacturing Co. 100
 Barry Electronics Corp. 127
 Bell Telephone Labs. 21
 Benco Television Associates Ltd. 20
 Blonder-Tongue Labs. 111
 Brooks Radio & Television Corp. 105, 110
- CBS-Hytron. 22, 79
 Capitol Radio Engineering Institute. 13, 93
 Carston Studios. 115
 Centralab Div. of Globe Union. 6
 Century Electronics Co., Inc. 83
 Chemical Electronic Engineering Inc. 104
 Cleveland Institute of Radio Electronics. 11
 Colorfax Laboratories, Inc. 121
 Cornell-Dubilier Electric Corp. 101, 102
 Coyne Electrical School. 91, 104, 117
 Cutick Electronics. 115
- DeVry Technical Institute. 7
 Dressner. 115
 Dynaco Inc. 114-115
- EBE Inc. 123
 Edmund Scientific Co. 119
 Electro-Sonic Labs. 20
 Electro-Voice, Inc. Inside Back Cover
 Electronic Instrument Co. (EICO). 25, 26
 Electronic Publishing Co., Inc. 113
- Filnor Products. 100
- Garfield (Oliver) Co. 121
 Gernsback Library Inc. 117, 124
 Glaser-Steers Corp. 89
 Grantham School of Electronics. 17
- Heald Engineering College. 119
 Heath Co. 60-75
 Hi-Fi Eye Co. 115
- Indiana Technical College. 115
- Jensen Industries. 118
- Karlson Associates Inc. 120
 Kuhn Electronic Products. 126
- Lafayette Radio. 128-129
 Lansing (James B.) Sound Inc. 77
 Lektron Inc. 94, 120
- MacFarlane Industries. 121
 Madison Fielding. 110
- Mallory (P.R.) & Co. Inc. 78
 Merit Coil & Transformer Corp. 118
 Moerke (Ed). 119
 Moss Electronic Distributing Co. Inc. 80-81
- National Radio Institute. 3
 National Schools. 5
 North American Philips Co. Inc. 113
 Northrop Aeronautical Institute. 116
- Opportunity Adlets. 114
 Oxford Components, Inc. 116
- Philco Techrep Division. 130
 Picture Tube Outlet. 126
 Pilot Radio Corp. 98
 Prentice-Hall, Inc. 123
 Progressive Edu-Kits, Inc. 106
 Pyramid Electric Co. 16
- Quality Electronics. 126
- RCA Electron Tube Division Back Cover
- RCA Institutes. 108-109
- RCA (Test Equipment). 14
- Radiart Corp. 102, 103
- Raytheon Manufacturing Co. 12
- Rek-O-Kut Co. Inc. 82
- Rinehart & Co. Inc. 121
- Sams (Howard W.) & Co. Inc. 9, 118
 Service Instruments Corp. 94, 113, 117, 119, 120, 123
 Sleep-Learning Research Ass'n. 119
 Sprague Products Co. 107
 Sprayberry Academy of Radio Television. 23
- Stan-Burn Radio & Electronics. 126
- Tab. 122
- Trio Manufacturing Co. 82
- Triplet Electrical Instrument Co. Inside Front Cover
- Tung-Sol Electric Co. 8
- Ultron Co. 104
 University Loudspeakers Inc. 85
- Vaco Products Co. 122
- Walseo Electronics Manufacturing Co. 10
 Winegard Co. 24
- Xcelite Inc. 94
- Zenith Radio Corp. 18-19
- SCHOOL DIRECTORY PAGE 125
- Baltimore Technical Institute
 Canadian Institute of Science & Technology
 Candler System Co.
 Central Technical Institute
 Indiana Technical College
 Milwaukee School of Engineering
 Pacific International University
 Tri-State College
 Valparaiso Technical Institute

HQ for the 5 TOP NAMES in
 TV & RECEIVING TYPE

TUBES AT SENSIBLE PRICES!

Individually boxed. First quality only. Brand New

O2A2	.75	BB42	1.00	BB48	.75	BB50	.75	BB52	1.00
O2A3	.75	GN	1.00	B10	1.00	W10	.75	125-117	1.00
VR175	.75	BA6	1.00	B17	1.00	WB17	1.00	125-117	1.00
O162	.75	BR40-Y	1.00	B18	1.00	WB18	1.00	125-117	1.00
O163	.75	BR40-Y	1.00	B19	1.00	WB19	1.00	125-117	1.00
VR-50	.50	3141	1.00	B18A	1.00	WB18A	1.00	125-117	1.00
O2C3-VR	.75	BB40	1.00	B18B	1.00	WB18B	1.00	125-117	1.00
O2C4	.75	BB40	1.00	B18C	1.00	WB18C	1.00	125-117	1.00
O165	.75	BB40	1.00	B18D	1.00	WB18D	1.00	125-117	1.00
O166	.75	BB40	1.00	B18E	1.00	WB18E	1.00	125-117	1.00
O2A4	.75	BB40	1.00	B18F	1.00	WB18F	1.00	125-117	1.00
O2A5	.75	BB40	1.00	B18G	1.00	WB18G	1.00	125-117	1.00
O2A6	.75	BB40	1.00	B18H	1.00	WB18H	1.00	125-117	1.00
O2A7	.75	BB40	1.00	B18I	1.00	WB18I	1.00	125-117	1.00
O2A8	.75	BB40	1.00	B18J	1.00	WB18J	1.00	125-117	1.00
O2A9	.75	BB40	1.00	B18K	1.00	WB18K	1.00	125-117	1.00
O2A10	.75	BB40	1.00	B18L	1.00	WB18L	1.00	125-117	1.00
O2A11	.75	BB40	1.00	B18M	1.00	WB18M	1.00	125-117	1.00
O2A12	.75	BB40	1.00	B18N	1.00	WB18N	1.00	125-117	1.00
O2A13	.75	BB40	1.00	B18O	1.00	WB18O	1.00	125-117	1.00
O2A14	.75	BB40	1.00	B18P	1.00	WB18P	1.00	125-117	1.00
O2A15	.75	BB40	1.00	B18Q	1.00	WB18Q	1.00	125-117	1.00
O2A16	.75	BB40	1.00	B18R	1.00	WB18R	1.00	125-117	1.00
O2A17	.75	BB40	1.00	B18S	1.00	WB18S	1.00	125-117	1.00
O2A18	.75	BB40	1.00	B18T	1.00	WB18T	1.00	125-117	1.00
O2A19	.75	BB40	1.00	B18U	1.00	WB18U	1.00	125-117	1.00
O2A20	.75	BB40	1.00	B18V	1.00	WB18V	1.00	125-117	1.00
O2A21	.75	BB40	1.00	B18W	1.00	WB18W	1.00	125-117	1.00
O2A22	.75	BB40	1.00	B18X	1.00	WB18X	1.00	125-117	1.00
O2A23	.75	BB40	1.00	B18Y	1.00	WB18Y	1.00	125-117	1.00
O2A24	.75	BB40	1.00	B18Z	1.00	WB18Z	1.00	125-117	1.00
O2A25	.75	BB40	1.00	B18A	1.00	WB18A	1.00	125-117	1.00
O2A26	.75	BB40	1.00	B18B	1.00	WB18B	1.00	125-117	1.00
O2A27	.75	BB40	1.00	B18C	1.00	WB18C	1.00	125-117	1.00
O2A28	.75	BB40	1.00	B18D	1.00	WB18D	1.00	125-117	1.00
O2A29	.75	BB40	1.00	B18E	1.00	WB18E	1.00	125-117	1.00
O2A30	.75	BB40	1.00	B18F	1.00	WB18F	1.00	125-117	1.00
O2A31	.75	BB40	1.00	B18G	1.00	WB18G	1.00	125-117	1.00
O2A32	.75	BB40	1.00	B18H	1.00	WB18H	1.00	125-117	1.00
O2A33	.75	BB40	1.00	B18I	1.00	WB18I	1.00	125-117	1.00
O2A34	.75	BB40	1.00	B18J	1.00	WB18J	1.00	125-117	1.00
O2A35	.75	BB40	1.00	B18K	1.00	WB18K	1.00	125-117	1.00
O2A36	.75	BB40	1.00	B18L	1.00	WB18L	1.00	125-117	1.00
O2A37	.75	BB40	1.00	B18M	1.00	WB18M	1.00	125-117	1.00
O2A38	.75	BB40	1.00	B18N	1.00	WB18N	1.00	125-117	1.00
O2A39	.75	BB40	1.00	B18O	1.00	WB18O	1.00	125-117	1.00
O2A40	.75	BB40	1.00	B18P	1.00	WB18P	1.00	125-117	1.00
O2A41	.75	BB40	1.00	B18Q	1.00	WB18Q	1.00	125-117	1.00
O2A42	.75	BB40	1.00	B18R	1.00	WB18R	1.00	125-117	1.00
O2A43	.75	BB40	1.00	B18S	1.00	WB18S	1.00	125-117	1.00
O2A44	.75	BB40	1.00	B18T	1.00	WB18T	1.00	125-117	1.00
O2A45	.75	BB40	1.00	B18U	1.00	WB18U	1.00	125-117	1.00
O2A46	.75	BB40	1.00	B18V	1.00	WB18V	1.00	125-117	1.00
O2A47	.75	BB40	1.00	B18W	1.00	WB18W	1.00	125-117	1.00
O2A48	.75	BB40	1.00	B18X	1.00	WB18X	1.00	125-117	1.00
O2A49	.75	BB40	1.00	B18Y	1.00	WB18Y	1.00	125-117	1.00
O2A50	.75	BB40	1.00	B18Z	1.00	WB18Z	1.00	125-117	1.00
O2A51	.75	BB40	1.00	B18A	1.00	WB18A	1.00	125-117	1.00
O2A52	.75	BB40	1.00	B18B	1.00	WB18B	1.00	125-117	1.00
O2A53	.75	BB40	1.00	B18C	1.00	WB18C	1.00	125-117	1.00
O2A54	.75	BB40	1.00	B18D	1.00	WB18D	1.00	125-117	1.00
O2A55	.75	BB40	1.00	B18E	1.00	WB18E	1.00	125-117	1.00
O2A56	.75	BB40	1.00	B18F	1.00	WB18F	1.00	125-117	1.00
O2A57	.75	BB40	1.00	B18G	1.00	WB18G	1.00	125-117	1.00
O2A58	.75	BB40	1.00	B18H	1.00	WB18H	1.00	125-117	1.00
O2A59	.75	BB40	1.00	B18I	1.00	WB18I	1.00	125-117	1.00
O2A60	.75	BB40	1.00	B18J	1.00	WB18J	1.00	125-117	1.00
O2A61	.75	BB40	1.00	B18K	1.00	WB18K	1.00	125-117	1.00
O2A62	.75	BB40	1.00	B18L	1.00	WB18L	1.00	125-117	1.00
O2A63	.75	BB40	1.00	B18M	1.00	WB18M	1.00	125-117	1.00
O2A64	.75	BB40	1.00	B18N	1.00	WB18N	1.00	125-117	1.00
O2A65	.75	BB40	1.00	B18O	1.00	WB18O	1.00	125-117	1.00
O2A66	.75	BB40	1.00	B18P	1.00	WB18P	1.00	125-117	1.00
O2A67	.75	BB40	1.00	B18Q	1.00	WB18Q	1.00	125-117	1.00
O2A68	.75	BB40	1.00	B18R	1.00	WB18R	1.00	125-117	1.00
O2A69	.75	BB40	1.00	B18S	1.00	WB18S	1.00	125-117	1.00
O2A70	.75	BB40	1.00	B18T	1.00	WB18T	1.00	125-117	1.00
O2A71	.75	BB40	1.00	B18U	1.00	WB18U	1.00	125-117	1.00
O2A72	.75	BB40	1.00	B18V	1.00	WB18V	1.00	125-117	1.00
O2A73	.75	BB40	1.00	B18W	1.00	WB18W	1.00	125-117	1.00
O2A74	.75	BB40	1.00	B18X	1.00	WB18X	1.00	125-117	1.00
O2A75	.75	BB40	1.00	B18Y	1.00	WB18Y	1.00	125-117	1.00
O2A76	.75	BB40	1.00	B18Z	1.00	WB18Z	1.00	125-117	1.00
O2A77	.75	BB40	1.00	B18A	1.00	WB18A	1.00	125-117	1.00
O2A78	.75	BB40	1.00	B18B	1.00	WB18B	1.00	125-117	1.00
O2A79	.75	BB40	1.00	B18C	1.00	WB18C	1.00	125-117	1.00
O2A80	.75	BB40	1.00	B18D	1.00	WB18D	1.00	125-117	1.00
O2A81	.75	BB40	1.00	B18E	1.00	WB18E	1.00	125-117	1.00
O2A82	.75	BB40	1.00	B18F	1.00	WB18F	1.00	125-117	1.00
O2A83	.75	BB40	1.00	B18G	1.00	WB18G	1.00	125-117	1.00
O2A84	.75	BB40	1.00	B18H	1.00	WB18H	1.00	125-117	1.00
O2A85	.75	BB40	1.00	B18I	1.00	WB18I	1.00	125-117	1.00
O2A86	.75	BB40	1.00	B18J	1.00	WB18J	1.00	125-117	1.00
O2A87	.75	BB40	1.00	B18K	1.00	WB18K	1.00	125-117	1.00
O2A88	.75	BB40	1.00	B18L	1.00	WB18L	1.00	125-117	1.00
O2A89	.75	BB40	1.00	B18M	1.00	WB18M	1.00	125-117	1.00
O2A90	.75	BB40	1.00	B18N	1.00	WB18N	1.00	125-117	1.00
O2A91	.75	BB40	1.00	B18O	1.00	WB18O	1.00	125-117	1.00
O2A92	.75	BB40	1.00	B18P	1.00	WB18P	1.00	125-117	1.00
O2A93	.75	BB40	1.00	B18Q	1.00	WB18Q	1.00	125-117	1.00
O2A94	.75	BB40	1.00	B18R	1.00	WB18R	1.00	125-117	1.00
O2A95	.75	BB40	1.00	B1					

FREE LAFAYETTE CATALOG

A Must For
Every Hi-Fi
Enthusiast

New! Years Ahead!



NEW 180 PAGE ELECTRONIC CATALOG FEATURING THE BEST BUYS IN THE BUSINESS

The newest and largest assortment of Electronic, Radio and TV parts, Hi-Fi and Public Address Components and systems, Test Equipment, tubes, Transistor Kits and miniaturized components for transistor circuitry, Ham Equipment, Builders Kits, Tools, Books, Microscopes, Binoculars, Telescopes, Cameras, and Drafting Equipment.—**ALL AT LOWEST PRICES**—Catering to the economy minded dealer, serviceman, engineer, technician, experimenter and hobbyist. **CRAMMED FULL OF MONEY SAVING BUYS. SEND FOR YOUR FREE COPY TODAY.**

LAFAYETTE STEREO TUNER KIT

THE MOST FLEXIBLE TUNER EVER DESIGNED



ONLY 7.45 DOWN
7.00 MONTHLY

KT-500
IN KIT
FORM

74.50



KT-300
IN KIT
FORM

39.50

KT-400
IN KIT
FORM

69.50

ONLY 6.95
DOWN -
7.00 MONTHLY

- Multiflex Output for New Stereo FM • 11 Tubes (including 4 dual-purpose) + Tuning Eye + Selenium rectifier Provide 17 Tube Performance • 10KC Whistle Filter • Pre-aligned IF's • Tuned Cascode FM • Separately Tuned FM and AM Sections • Armstrong Circuit with FM/AFC and AFC Defeat • 12 Tuned Circuits • Dual Cathode Follower Output • Dual Double-Tuned Transformer Coupled Limiters.

More than a year of research, planning and engineering went into the making of the Lafayette Stereo Tuner. Its unique flexibility permits the reception of binaural broadcasting (simultaneous transmission on both FM and AM), the independent operation of both the FM and AM sections at the same time, and the ordinary reception of either FM or AM. The AM and FM sections are separately tuned, each with a separate 3-gang tuning condenser, separate flywheel tuning and separate volume control for proper balancing when used for binaural programs. Simplified accurate knife-edge tuning is provided by magic eye which operates independently on FM and AM. Automatic frequency control "locks in" FM signal permanently. Aside from its unique flexibility, this is, above all else, a quality high-fidelity tuner incorporating features found exclusively in the highest priced tuners.

FM specifications include grounded-grid triode low noise front end with triode mixer, double-tuned dual limiters with Foster-Seeley discriminator, less than 1% harmonic distortion, frequency response 20-20,000 cps $\pm \frac{1}{2}$ db, full 200 kc bandwidth and sensitivity of 2 microvolts for 30 db quieting with full limiting of one microvolt. AM specifications include 3 stages of AVC, 10 kc whistle filter, built-in ferrite loop antenna, less than 1% harmonic distortion, sensitivity of 5 microvolts, 8 kc bandwidth and frequency response 20-5000 cps ± 3 db.

The 5 controls of the KT-500 are FM Volume, AM Volume, FM Tuning, AM Tuning and 5-position Function Selector Switch. Tastefully styled with gold-brass escutcheon having dark maroon background plus matching maroon knobs with gold inserts. The Lafayette Stereo Tuner was designed with the builder in mind. Two separate printed circuit boards make construction and wiring simple, even for such a complex unit. Complete kit includes all parts and metal cover, a step-by-step instruction manual, schematic and pictorial diagrams. Size is 13 $\frac{3}{4}$ " W x 10 $\frac{1}{8}$ " D x 4 $\frac{1}{2}$ " H. Shpg. wt., 18 lbs.

The new Lafayette Model KT-500 Stereo FM-AM Tuner is a companion piece to the Models KT-300 Audio Control Center Kit and KT-400 70-watt Basic Amplifier Kit and the "Triumvirate" of these 3 units form the heart of a top quality stereo hi-fi system.

KT-500.....Net **74.50**

LAFAYETTE MASTER AUDIO CONTROL CENTER

with BINAURAL CHANNEL AND DUAL VOLUME CONTROL.

- Self-Powered • DC On All Filaments • 24 Positions of Equalization
- Tape Head Input, High Impedance • Dual Cathode Follower Output Stages

This is not only the finest hi-fi preamp characterized by unmatched features, but it has been functionally designed to keep pace with the conversion of your present hi-fi system to binaural (Stereophonic) sound. Incorporates an extra channel and dual volume control for binaural reproduction. Features include DC on all tube filaments, negative feedback in every stage, dual cathode follower output stages and latest printed circuit construction. Less than 0.09% IM distortion and less than 0.07 harmonic distortion at 1V. Hum and noise level better than 80 db below 3V. Uniformly flat frequency response over entire audible spectrum. 7 inputs for every type of phono, tuner or tape. Tasteful styling, brilliantly executed. Size 12 $\frac{3}{4}$ " x 9 $\frac{1}{8}$ " x 3 $\frac{1}{4}$ ". Shpg. wt., 10 $\frac{1}{2}$ lbs.

KT-300—Lafayette Master Audio Control Kit Complete with cage and detailed assembly instructions.....Net **39.50**

LT-30—Same as above completely wired and tested with cage and instruction manual. Net **59.50**

DELUXE 70 WATT BASIC AMPLIFIER

- Conservatively Rated At 70 Watts • Inverse Feedback • Variable Damping
 - Metered Balance And Bias Adjust Controls • Available In Kit and Wired Form
- Here's ultra-stability in a 70 watt basic power amplifier employing highest quality components conservatively rated to insure performance and long life. Features matched pair KT 88's and wire range linear Chicago output transformer, variable damping control, meter for bias and balance and gold finish chassis. Frequency response 10-100,000 cps ± 1 db. Hum and noise 90 db below full output. IM distortion less than 1 $\frac{1}{2}$ % at 70 watts, less than 0.3% below 30 watts. Harmonic distortion less than 2% at 70 watts from 20 to 20,000 cps ± 1 db. Output impedance 4, 8 and 16 ohms. Handsome decorative cage perforated for proper ventilation. Size 14 $\frac{1}{2}$ " x 10 x 7 $\frac{1}{2}$ " including cage and knobs. Shpg. wt., 40 lbs.

KT-400—Lafayette 70 watt Deluxe Basic Amplifier Kit complete with cage and detailed assembly instructions.....Net **69.50**

LA-70—Same as above completely wired and tested with cage and instruction manual. Net **94.50**

NEW! LAFAYETTE SCOOP!

DUAL WIDE-ANGLE TWEETER

Modernize Your Hi-Fi System

Modernize your high fidelity listening by adding this wide-angle dual-tweeter to extend treble range in a 2-way or 3-way speaker system. Mounts directly on any 12" speaker and converts it to a coaxial type. Response 2500 to 16,000 cps. Recommended crossover 2500 to 4000 cps. Heavy magnet for high efficiency. Dispersion angle approx. 125° horizontally. Impedance 16 ohms (2-8 ohm units in series). Will handle up to 20 watts program in 2 or 3-way systems. Incorporated specially designed chrome-plated steel bracket of rigid construction to prevent resonances. Measures 12" L x 2" D x 2 $\frac{1}{8}$ " H overall. Shpg. wt. 2 lbs. SK-100 Dual Tweeter.....Net **5.95**

Only
5.95

Lafayette Radio

DEPT
JF

P. O. BOX 511
JAMAICA 31, N.Y.

Send FREE LAFAYETTE Catalog 305

Name **CUT OUT**
AND MAIL

Address **TODAY**

City Zone.... State.....

LAFAYETTE PROFESSIONAL TURNTABLE

with AUTHENTIC HYSTERESIS SYNCHRONOUS MOTOR

Value 129.50 Only 64.50

SAVE OVER 50%

LAFAYETTE
MODEL
PK-225



PROFESSIONAL TURNTABLE WITH HYSTERESIS-SYNCHRONOUS MOTOR

The Lafayette Model PK-225 is a true hysteresis-synchronous motor and is free from speed variations due to fluctuations in line voltage, load and temperature. It is the smoothest type known, completely free from "cogging" (the minute variations of speed which show up as wow and flutter).

ONLY LAFAYETTE'S HYSTERESIS-SYNCHRONOUS MOTOR, in its price class, is made to extremely fine tolerances (on the order of .00001 inches). Only Lafayette's motor has 16 cores; a high permeability rotor magnet, ball thrust bearings, oilite sleeve bearings plus felt oil reservoir, cooling fins as an integral part of the rotor and a hollow rotor core for maximum efficiency and minimum heat. Only Lafayette's motor can be oiled from above, without disassembly, through a unique oil feed system. Only Lafayette's motor has a self-aligning armature.

Here's THE turntable—the last word in professional high-fidelity performance! A fine precision instrument in every sense. Just look at some of these OUTSTANDING FEATURES: • **WOW AND FLUTTER:** Less than 0.2% • **TURN-TABLE:** Heavy, diecast aluminum. Lathe-turned for perfect balance and concentricity. 12" diameter—weighs approx. 4 lbs., and provides amazingly constant speed; the extra-heavy rim acts just like a flywheel to prevent speed variations. • **TRUE-HYSTERESIS-SYNCHRONOUS MOTOR:** For smooth, low-noise, wow- and flutter-free operation • **RUMBLED: AND NOISE:** 50db below average recorded level • **INTEGRATED SPEED CONTROL:** For all 3 speeds—78, 45 and 33 1/3 rpm • **2 OVERSIZE, HEAVY DUTY IDLERS:** Precision-ground; provide positive constant-speed rim drive • **SINGLE BALL THRUST BEARING:** Turntable rides smoothly over ball bearing floating on thin film of oil • **FREE FLOATING, SHOCK-MOUNTED MOTOR • RUBBER CUSHION SHOCKMOUNTS** • **AUTOMATIC IDLER DISENGAGEMENT** • **CORK AND RUBBER MAT** • **STAINLESS STEEL PRECISION SPINDLE** • **POWER REQUIREMENTS:** For 105-130 volts, 60 cps AC; draws 16 V.A. • **ACCESSORIES SUPPLIED:** 45 RPM adapter, Strope disc • **SIZE:** 2 1/8" above and 4" below motor board; 14 3/4" deep x 12 1/4" wide • **SHIPPING WEIGHT:** 16 lbs.

LAFAYETTE MODEL PK-225

Deluxe Woodbase for PK-225 and 12" Tone Arm (Specify Finish). Shpg. wt., 13 lbs. Net 64.50
Deluxe Woodbase for PK-225 and 16" Tone Arm (Specify Finish). Shpg. wt., 15 lbs. Net 14.95
Net 15.95

VISCOUS DAMPED TRANSCRIPTION TONE ARMS



SPECIAL MONEY-SAVER COMBINATION

PK-225 Turntable, PK-90 12" Tone Arm, New GE VRII Series Triple-Play Cartridge Model 4G-052 with Genuine GE Diamond and Sapphire Styli. SPECIAL! Net 81.50

TINY 6 TRANSISTOR RADIO



• LIGHT • SMALL • SENSITIVE LOW PRICE HIGH PERFORMANCE

- PUSH-PULL AUDIO OUTPUT FOR FAITHFUL TONE QUALITY
- FULL TONE DYNAMIC SPEAKER
- BUILT-IN FERRITE BAR ANTENNA
- TROUBLE-FREE PRINTED CIRCUIT
- 6 ULTRA-MODERN TRANSISTORS PLUS GERMANIUM DIODE
- SUPERHETERODYNE CIRCUIT
- HIGHLY STYLED PLASTIC CASE
- EARPHONE JACK—BUILT IN—FOR PRIVATE LISTENING
- ECONOMICAL—USES ONLY ONE BATTERY

SIZE: 1 3/8" x 2 3/4" x 4 5/8" WEIGHT: 12 OUNCES

FS-110 — LAFAYETTE "TINY" TRANSISTOR RADIO COMPLETE with Battery, Carrying Case and Earphone Net 29.95

REGULARLY
48.50
29.95
Including Earphone,
Battery and
Carrying Case



NEW! POWER MEGAPHONE ... Portable Sound Broadcaster

- Uses 8 Flashlight Cells • Completely Self-Contained
- Weighs only 6 1/2 lbs. with Batteries • High Efficiency
- Horn Projects Sound 1000 Ft. • Shoulder Strap for Portability and Ease of Use • Microphone Detachable On 10-Foot Cord • For Construction, Auctions, Carnivals, Fire & Police Use • Also Ideal for Marine, Railroad, Civil Defense, Sporting Events

A power megaphone with many unusual features and many applications. Basically a highly efficient sound projector horn with a built-in microphone, capable of amplifying and projecting the voice with a range of 1000 feet. The microphone is a telephone-type element, easily replaceable, and may be detached and extended up to 10 feet from the horn. The reflex-type horn is extremely light-weight, rubber-rimmed, of strong, sturdy spun aluminum construction with 2 3/4" air column and is supplied with a strap for carrying or placing on the shoulder. A press-to-talk switch on the microphone provides for economy of power use—power is used only when actually talking. No warm-up time required—amplification is instantaneous. A patented non-linear current limiting device restricts current flow to safe levels for longest battery life. Uses 8 size "D" flashlight cells in series with an approximate life of about 10 hrs. of use. Battery housing serves as base for entire assembly. Battery compartment opens easily by means of 2 thumbscrews for battery replacement. Size 17" long overall; horn mouth is 12" diam. Shpg. wt., 8 lbs. less batteries.

PA-13 — Power Megaphone, Less batteries.....Net 29.50

BATTERIES FOR ABOVE—Burgess No. 2 or RCA

VS036—8 RequiredNet each .13

Reg. Value 69.50
ONLY 29.50



SHOULDER STRAP & DETACHABLE MIKE
JUST AIM & TALK

Self-Contained—
Only 6 1/2 lbs.
THROWS VOICE
1000 FT.



Lafayette Radio

165-08 Liberty Ave.
JAMAICA 33; N.Y.


INCLUDE POSTAGE WITH ORDER

NEW YORK, N.Y.	BOSTON, Mass.	BRONX, N.Y.	NEWARK, N.J.	PLAINFIELD, N.J.
100 6th Ave.	110 Federal St.	542 E. Fordham Rd.	24 Central Ave.	139 W. 2nd St.
RECTOR 2-8600	Hubbard 2-7850	Fordham 7-8813	MARket 2-1661	Plainfield 6-4718

LEARN SEMICONDUCTOR ELECTRONICS AT HOME

... prepare now for advancement in this growing, new technology!

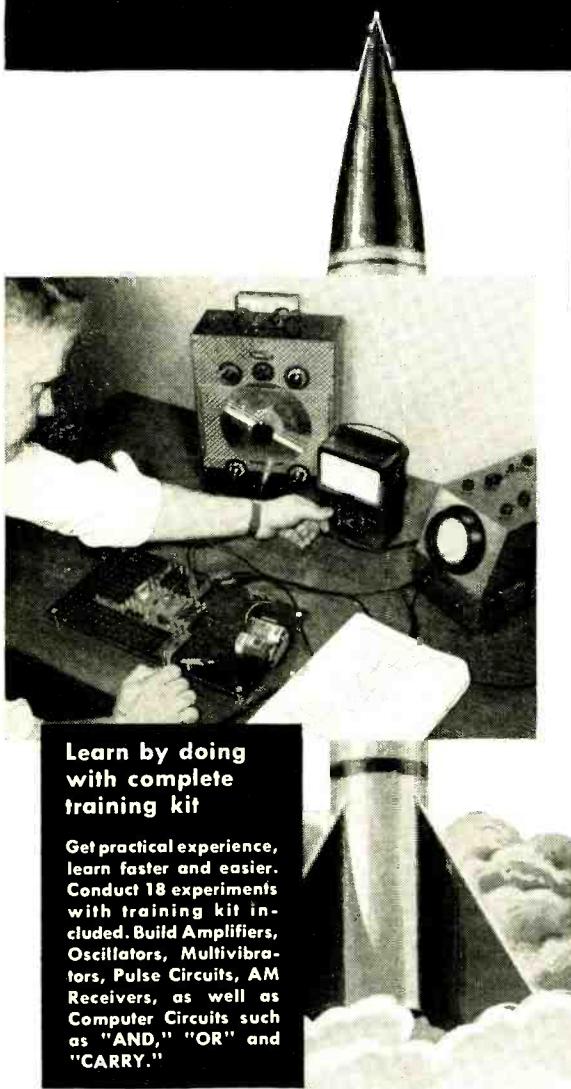GAIN VALUABLE KNOWLEDGE FOR A PROFITABLE CAREER IN ELECTRONICS WITH THIS SPECIALIZED CORRESPONDENCE COURSE ON TRANSISTORS THAT HAS BEEN SPECIALLY DEVELOPED BY THE PHILCO TECHNOLOGICAL CENTER



Learn by doing with complete training kit

Get practical experience, learn faster and easier. Conduct 18 experiments with training kit included. Build Amplifiers, Oscillators, Multivibrators, Pulse Circuits, AM Receivers, as well as Computer Circuits such as "AND," "OR" and "CARRY."

Prepare for a Career in Field Engineering with these Philco Correspondence Courses

BASIC RADAR—an introductory course.

ADVANCED RADAR—Comprehensive course on radar equipment and systems.

BASIC ANALOG COMPUTERS — an introductory course.

ADVANCED ANALOG COMPUTERS—Comprehensive coverage of systems and equipment.

Learn theory, construction and all important applications of all major types of transistors—Junction, Point Contact, Surface Barrier and many other related types—with this advanced Correspondence Course specially developed for engineers and experienced technicians now engaged in Design, Installation, Maintenance or Manufacture of electronics equipment or systems.

ELECTRONICS SPECIALISTS ARE URGENTLY NEEDED. Even during hard times and periods of high unemployment such as we are going through now, the newspapers are full of help-wanted ads for electronics technicians and engineers. And the pay is good, too! Of course, the more you know the better your chances for better jobs and bigger pay.

GET INTO THE SEMICONDUCTOR FIELD NOW. This field is growing fast. Industry can't find enough experienced technicians and engineers. Career opportunities are unlimited. Now's the time to get in on the ground floor.

THE PHILCO TECHNOLOGICAL CENTER IS A DEPARTMENT OF PHILCO TECHREP DIVISION, THE WORLD'S LEADING ELECTRONICS FIELD ENGINEERING ORGANIZATION. You benefit from Philco's 17 years of experience in providing electronics training and technical assistance to the Armed Forces and industry all over the world ... and from advanced training methods developed through these many years. You learn from proven courses that have been developed by experienced electronics training specialists to give you a complete and practical knowledge of semiconductors.

Mail Coupon Today for
Detailed Information of Course
Level and Materials!

(NO OBLIGATION)

PHILCO TECHNOLOGICAL CENTER
22nd and Lehigh Ave., Philadelphia 32, Pa.

TC-14

Please send free booklet and course information on subjects checked below:

- SEMICONDUCTORS
Transistor Principles
and Practices
 BASIC RADAR

- ADVANCED RADAR
 BASIC ANALOG COMPUTERS
 ADVANCED ANALOG COMPUTERS

NAME _____
ADDRESS _____
CITY _____ STATE _____

PHILCO
TECHNOLOGICAL
CENTER

22nd and Lehigh Ave.
Philadelphia 32, Pa.

Electro-Voice® DYNAMIC MICROPHONES

OUT-PERFORM ALL OTHERS for P.A. and RECORDING!

new acoustic principle — VARIABLE D acclaimed the most significant microphone development in 20 years!

Because of their durability and uniformity of response, dynamic microphones are almost universally used by recording studios. Electro-Voice dynamic microphones are a triumph of electro-acoustics in the recording, P.A. and general purpose fields. One of the many reasons for this is the Variable D principle which employs three distinct sound entrances, with acoustical filters; achieves flat response and excellent back cancellation while eliminating boominess caused by close talking—and susceptibility to shock. That's why those who want true fidelity, life-like recorded tape choose Electro-Voice dynamic microphones.



① E-V MODEL 664

Utilizing the revolutionary Variable D, this high-fidelity cardioid dynamic brings broadcast quality to tape recording and the P.A. and general purpose field. Proper placement of microphone stops unwanted sounds, gives accurate, natural pick-up of voice and music. Unprecedented ruggedness largely eliminates possibility of accidental damage.

Indestructible Acoustalloy diaphragm and precision manufacture assure long-life and dependable performance. Frequency response: 40 to 15,000 cps. Pressure cast case. Chrome finish. 18' cable. Size: 7 3/16" long, 1 1/8" diameter. Net weight: 1 lb. 10 oz. List price: \$85.00 (less stand).

② E-V MODEL 636


This model brings style and quality to the recording and public address fields. Slim and trim—only 1 1/8" in diameter x 10 1/4" long—it greatly reduces recording staging problems. Frequency response: 60 to 15,000 cps, essentially flat. Adjustable impedance. Gold or satin chrome finish. On-off switch standard equipment. Net weight: 15 oz. List price Chrome Finish: \$72.50 (less stand).

③ E-V MODEL 623

Excellent for both speech and music, its small, slim size makes it inconspicuous and easy to handle. Swivel mounting permits tilting microphone through a 57° arc toward the sound source. Acoustalloy diaphragm. Frequency response: 60 to 12,000 cps. Satin chrome finish. Net weight: 1 lb. List price: \$57.00 (less stand).

④ E-V MODEL 630

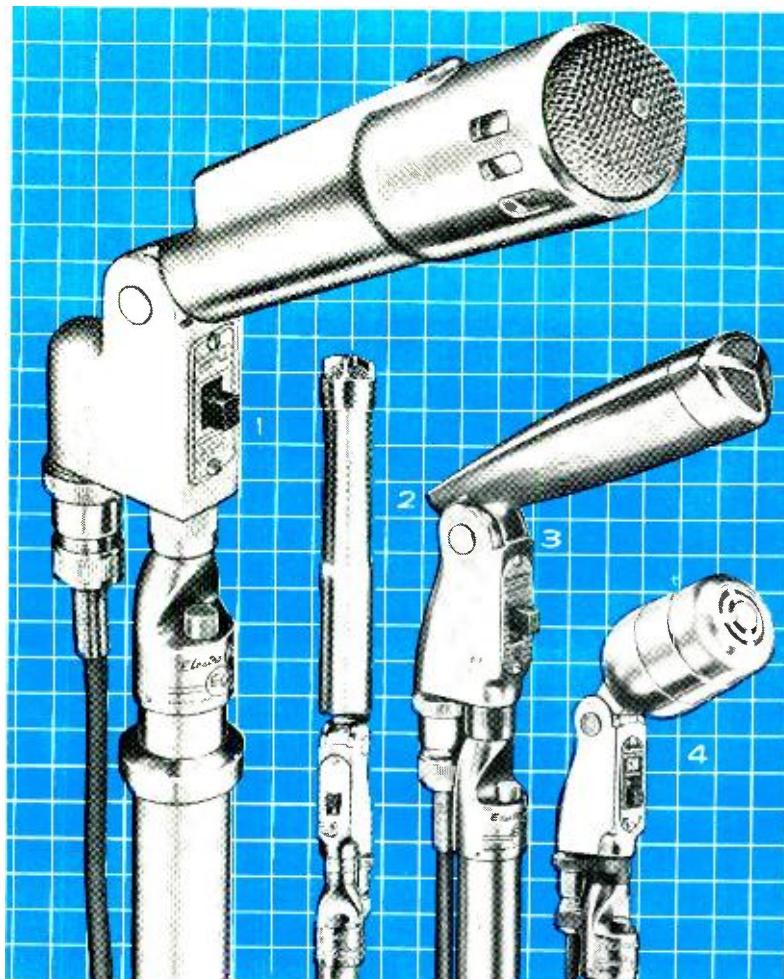This is similar to Model 623 in performance characteristics but is traditionally styled. Frequency response: 60 to 11,000 cps. Satin chrome finish. Net weight: 1 lb. List price: \$52.50.



Your tapes will have a new depth of realism when you record with Electro-Voice High-Fidelity Dynamic Microphones!




See your E-V hi-fi dealer today. Write for "The ABC's of Microphones," Booklet W-86

Electro-Voice®

**ELECTRO-VOICE, INC.
BUCHANAN, MICHIGAN**

anatomy
of the
tube...
LESSON #1

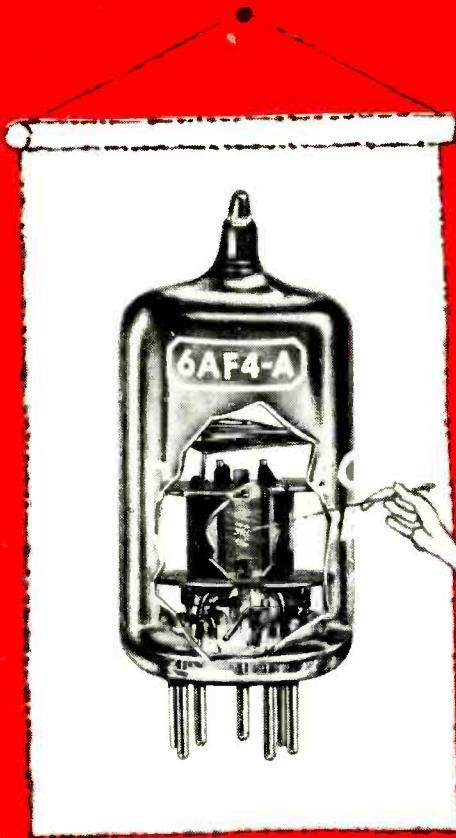

GRID

How RCA builds special
prescription grids...extends 6AF4-A life!

RCA's redesign of the 6AF4-A has resulted in minimized slump, product uniformity, and projected average life of *4,000 hours or more!*

Here are some of the materials RCA "prescribes" in manufacturing the new 6AF4-A. The grid is plated with Palladium, a rare metal capable of withstanding high temperatures. The use of this grid structure minimizes interelectrode leakage, prevents grid loading, and as a result, provides stable tube performance. The cathode, a nickel alloy, is specially selected to reduce interface resistance and thus minimizes slump. The use of pins which are silver-plated reduces skin effect at ultra high frequencies and improves tuner performance.

All these features, in addition to dynamic life tests, help to assure long and dependable performance. No wonder RCA's 6AF4-A is tops!

So, here's the #1 lesson in radio, phonograph, and TV service—when ordering tubes for replacement, specify "RCA Tubes only."



RADIO CORPORATION OF AMERICA
Electron Tube Division

Harrison, N. J.

