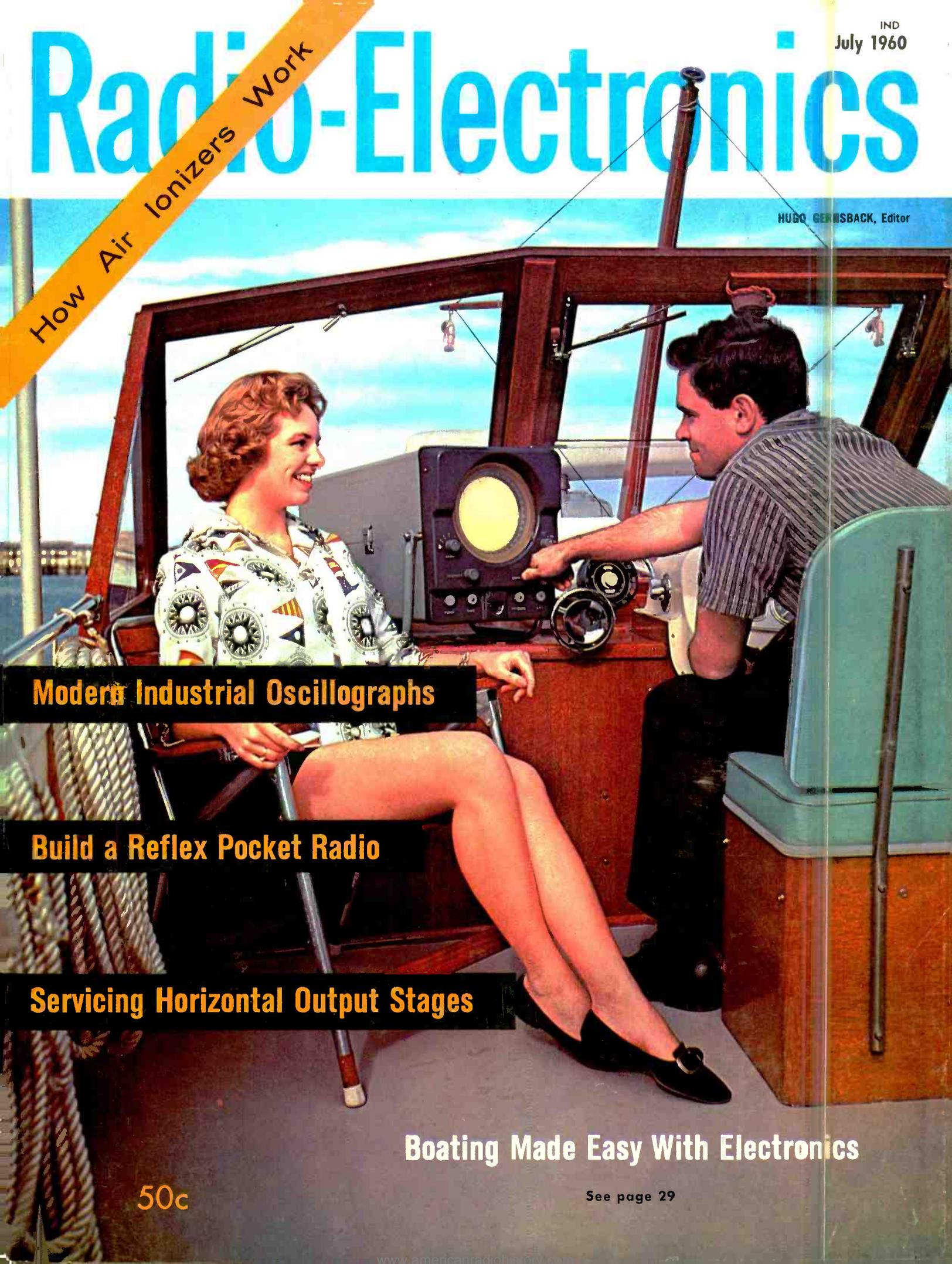


Radio-Electronics

IND
July 1960

How Air Ionizers Work

HUGO GERMSBACK, Editor



Modern Industrial Oscillographs

Build a Reflex Pocket Radio

Servicing Horizontal Output Stages

Boating Made Easy With Electronics

50c

See page 29



HERE'S A **COMPACT** DESIGN

*that's preferred among
all modern designs!*

IT'S THE SLIM, TRIM NEW
330 MICROPHONE SERIES
Dynamic, Ceramic and Crystal Models

BY **ASTATIC**

ACTUAL
SIZE

never before such quality of performance and
versatility of application at such low price

Yes, here's a classic design in modern, compact microphones—small, slender, unobtrusive, a beauty in simplicity. But the greatest achievement is in the magnificent performance quality of the Series among a great host of applications.

The Dynamic Models 335H (high impedance) and 335L (low impedance) operate with highest quality characteristics in TV and radio broadcast usage, in professional or home recording, public address, almost unlimited other lavalier, hand or stand applications.

The Ceramic Model 331 is a voice range unit specifically engineered for excellence in communications applications, 27 megacycle citizens' band use, and paging.

Ceramic Model 333 is a wide-range microphone offering a similarly high new level of perfection for tape recording, P. A. Systems, etc.

Crystal Model 332, with satin chrome body and cap, black grille, is already famous through widespread use. Performance throughout the series is of the highest order. **THUS, THE GREATEST NEWS OF ALL CONCERNING THESE NEW ASTATIC UNITS IS THEIR AMAZINGLY LOW COST!** Check out these new Astatic Microphones at your first opportunity.

Model	Type	Output	Frequency Range	Impedance	Finish	List Price
331	Ceramic	-56 db	300- 5,000	High	Black Body and Grille, Chrome Cap	\$17.90
333	Ceramic	-58 db	30-12,000	High		17.90
335H	Dynamic	-56 db	50-12,000	High	TV Grey Body, Chrome Cap and Grille	26.50
335L	Dynamic	-57 db	50-12,000	Low		23.50

NOTE: Model 331 has momentary-on, spring-return switch, is furnished with hang-up bracket. Cable provides for audio and relay connections. All other models have slide switch with "lock-on" position, are complete with lavalier and stand adaptor with 5/8"-27 thread.




GO BY BRAND . .
GO BUY ASTATIC

THE **Astatic** CORPORATION, CONNEAUT, OHIO
In Canada: Canadian Astatic Limited, Toronto, Ontario
Export Sales: Roburn Agencies, Inc., 431 Greenwich St., N. Y. 13, N. Y., U. S. A.



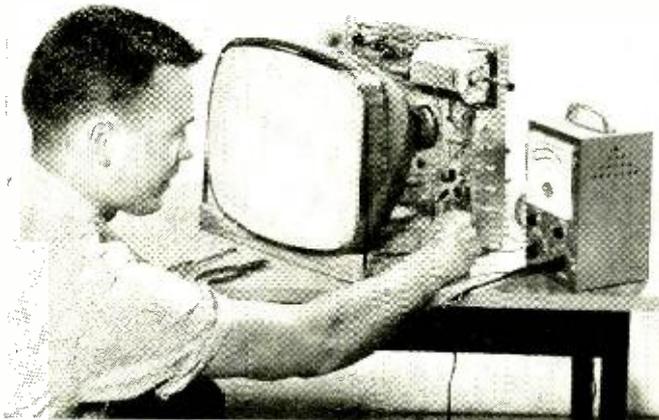Train at Home for Success in RADIO TELEVISION ELECTRONICS




You Learn at Home by Actual Practice

With NRI kits you build actual Radio-Television circuits and testing instrument. Practice locating and fixing Radio-Television troubles. Learn soon to earn extra money.



Good Jobs in Radio-TV Communications

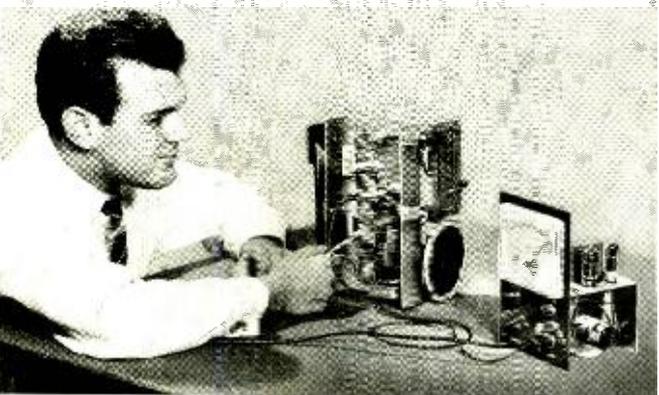NRI trained men hold good jobs as operators and technicians in Radio and Television broadcasting stations, with Police, Marine and Aviation stations. Interesting work, good pay.



There's Good Pay in Radio-TV Servicing

NRI trained technicians are needed, paid well, to help maintain 150 million home and auto Radios, 38 million TV sets. Color TV adding opportunities. Excellent field for spare time earning.

Join the thousands N.R.I. has trained for Successful Careers in Radio-TV

Get the benefit of NRI's 40 years experience training men for success in this field. Get personal attention of experienced instructors. Also get practice with Radio-TV equipment—learn by *doing*—with kits supplied as part of your course. Courses are easy to learn. Most successful NRI men start without any knowledge of Radio, many without a high school education.



J. E. Smith
founder

Find Out What Radio-TV Offers You

As trained Radio-TV Technician, you are prepared to supply much needed services. The technician is a respected and appreciated member of his community. Get Sample Lesson FREE. See how practical NRI has made learning at home. Mail the coupon. You also get 64-page Catalog telling about NRI, the lessons, equipment supplied, instruction services.

N.R.I. TRAINED THESE MEN FOR SUCCESS



"I am a police captain and have a good spare time Radio-Television service business. Just opened new shop." C. W. LEWIS, Pensacola, Florida.



"Received my License and worked on ships. Now Chief Engineer Station WAPA. Grateful to N.R.I." R. D. ARNOLD, Rumford, Rhode Island.



"Enrolled while meat market manager. Got serviceman job. In a year my pay increased 50%." C. CARTER, San Bernardino, California.



"Have a Radar job. Also do spare time Radio-Television servicing. Have my own amateur Radio Station." F. ZOWAKE, Scranton, Pennsylvania.


Added Income Soon—\$10, \$15 a Week in Your Spare Time

Soon after enrolling, many NRI students earn \$10, \$15 a week extra fixing sets in spare time. Vacuum Tube Voltmeter you build with parts we send helps you locate and fix troubles. Special lessons show you how. Many students use spare time earnings to pay for their training, and provide capital to start their own businesses when they get their National Radio Institute Diploma.

Color TV Making More Jobs

Radio-Television is an industry noted for continued and spectacular growth. Number of trained men employed has increased steadily. Color TV and other late developments are creating need for more technicians. The future is very bright for trained men. Find out how you can get ready at low cost, on easy terms. Send for FREE Sample Lesson and Catalog. Mail coupon today—National Radio Institute, Dept. OGF, Washington 16, D. C.

VETERANS—Approved under GI Bills

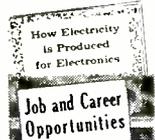

Send for Sample Lesson and Catalog FREE

MAIL COUPON TODAY

NATIONAL RADIO INSTITUTE
Dept. OGF, Washington 16, D. C.

Please send me sample lesson of your Radio-Television Training and catalog FREE. (No salesman will call.)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL



Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION*

EDITORIAL

25 Around the World in 80 Seconds—M. Harvey Gernsback

ELECTRONICS

- 26 The Tunnel Diode Story—R. L. Watters and J. V. Claeys
- 29 Electronics Goes Down to the Sea (in Small Boats)—Newell Garden
- ✓ 30 Underwater Metal Detector—Kenneth Richardson
- 31 Roundword Puzzle—Michael L. Nahrwold
- 32 Air Ionizers—Harold B. McKay
- 33 Electronic Camera Takes Movies
- 34 Principles of Modern Radar, Part II—Jordan McQuay
- 36 Automatic Recycling Timer—L. E. Fannon

TEST INSTRUMENTS

- 37 Troubleshooting Sweep Circuits—Val Sykes
- 39 An Audio Comparator—J. E. Pugh, Jr.
- ✓ 40 Test Adapters—Robert F. Scott
- 44 Capacitor Test Box—James A. Fred

WHAT'S NEW

45 Pictorial Reports of New Developments

INDUSTRIAL ELECTRONICS

- 46 Semiconductors for Industrial Controls—Tom Jaski
- 49 Oscillographs in Action—J. H. Thomas
- 52 Polyoptic Sealing Makes Better Tubes
- ✓ 53 Servomechanisms—How They Work—E. L. Safford, Jr.
- 55 New Secondary Time Standard

TELEVISION

- 56 Servicing Horizontal Output Stages—R. D. Jacques
- 59 TV Service Clinic—Conducted by Jack Darr
- ✓ 61 The Gibbons Substituter—Harold Davis

AUDIO-HIGH FIDELITY

- 68 High-Fidelity Test Panel—Herman Burstein and C. B. Graham
- 74 FM Multiplex in England
- 76 4-Track Stereo—Matchbox Size—Keith C. Johnson
- ✓ 81 More Bass from Smaller Loudspeakers—Norman H. Crowhurst
- 88 Mixing and Matching to Audio Inputs—Harold Reed

RADIO

- ✓ 92 Shirt-pocket Reflex for Local Listening—Alvin Mason
- 94 New Developments in Radio Circuitry—Henry O. Maxwell
- 96 Reserve Power for Survival—Sol D. Prensky
- 97 How Much Rf?—Irvin C. Chapel
- 98 Interference—Causes, Remedies and Location—Forrest H. Frantz, Jr.

- | | |
|----------------------------------|-------------------------|
| 116 Business and People | 6 News Briefs |
| 18 Correspondence | 110 Noteworthy Circuits |
| 120 New Books | 106 Technicians' News |
| 118 New Literature | 112 Technotes |
| 109 New Patents | 114 Try This One |
| 104 New Products | 113 50 Years Ago |
| 102 New Tubes and Semiconductors | |

ON THE COVER

(Story on page 29)

Sales and service of small-boat radio and electronic equipment are fast-growing fields. Photo shows 7-inch radar and miniature depth sounder on small power boat. Equipment may also include fuel-vapor detector, direction finder and radiophone.

Color original by Raytheon

- Hugo Gernsback
.....Editor and Publisher
- M. Harvey Gernsback
.....Editorial Director
- Fred Shunaman
.....Managing Editor
- Robert F. Scott
.....W2PWG, Technical Editor
- Larry Steckler
.....Associate Editor
- I. Queen
.....Editorial Associate
- Elizabeth Stalcup
.....Production Manager
- Wm. Lyon McLaughlin
.....Tech. Illustration Director
- Richard A. Giurlando
.....Art Director
- Fred Neinast
.....Staff Artist
- Lee Robinson
.....Director, Advertising Sales
- John J. Lamson
.....Eastern Sales Manager
- G. Aliquo
.....Circulation Manager
- Adam J. Smith
.....Director, Newsstand Sales
- Robert Fallath
.....Promotion Manager



Average Paid Circulation Over 174,000



RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index (Formerly Industrial Arts Index)*

RADIO-ELECTRONICS, July, 1960, Vol. XXXI, No. 7. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class postage paid at Mt. Morris, Ill. Copyright 1960 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.
SUBSCRIPTION RATES: U.S., U.S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$10.00 for three years. Pan-American countries \$5.00 for one year; \$9.00 for two years; \$13.00 for three years. All other countries \$5.50 a year; \$10.00 for two years; \$14.50 for three years.
SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.
GERNSBACK PUBLICATIONS, INC. Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N.Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.
ADVERTISING REPRESENTATIVES and FOREIGN AGENTS listed on page 123.
POSTMASTER: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS

NOW!
at a price
you can afford!

MAKE MORE MONEY in TELEVISION RADIO-ELECTRONICS

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of *Television-Radio-Electronics*.

LOWER COST... Other schools make several courses out of the material in our **ONE MASTER COURSE**... and you pay more for less training than you get in our course at **ONE LOW TUITION!**



These
two FREE books will
show you how!

You get all information
by mail... You make
your own decision... at
home! **NO SALESMAN
WILL CALL**

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough *Practical* training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up, that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how to earn extra money right from the start. Many of our students pay for their course—and more—while studying. So can you!

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles the world's TV capital, start **NOW** in our big, modern Shops, Labs and Radio-TV studios. Here you work with latest Electronic equipment - - professionally installed - - finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school - - and part time job while you learn. Check box in coupon for full information.

LESSONS AND INSTRUCTION MATERIAL ARE UP-TO-DATE, PRACTICAL, INTERESTING. Every National Schools Shop-Method lesson is made easy to understand by numerous illustrations and diagrams. All instruction material has been developed and tested in our own Resident School Shops, Laboratories and Studios.

SEND FOR INFORMATION TODAY... it can mean the difference between **SUCCESS** and failure for you! Send for your **FREE BOOK** "Your Future in Television-Radio-Electronics" and **FREE Sample Lesson**. Do it **TODAY**, while you are thinking about your future. It doesn't cost you anything to investigate!

GET THE BENEFITS OF OUR OVER 50 YEARS EXPERIENCE

Approved for
GI Training



NATIONAL SCHOOLS

Los Angeles 37, Calif.

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

SHOP-METHOD HOME TRAINING COVERS ALL PHASES OF INDUSTRY

1. Television, including Color TV
2. Radio AM & FM
3. Electronics for Guided Missiles
4. Sound Recording and Hi-Fidelity
5. FCC License
6. Automation and Computers
7. Radar & Micro-Waves
8. Broadcasting and Communications

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

MAIL NOW TO
NATIONAL TECHNICAL SCHOOLS, Dept. RG-70

4000 S FIGUEROA ST. LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Check if interested **ONLY** in Resident School training at Los Angeles.

VETERANS Give date of Discharge _____

men
17-55

**JOB OPPORTUNITIES!
EXCITEMENT!
MONEY!**

All this
can be
Yours as a trained

Electronics TECHNICIAN

**OVER 6,000 FIRMS HAVE EMPLOYED
DeVRY TECH GRADUATES!**

Thousands of companies in the United States and Canada who have employed DeVry Tech men prove two most important facts: (1) Electronics is one of the biggest, fastest growing opportunity fields of our time; and (2) DeVry Tech graduates are "WANTED" MEN.

Whether DeVry Tech prepares you in spare time at home or in its modern Chicago or Toronto Laboratories, your training is designed to get you ready to meet the exacting standards of industry. You get practical training that not only helps to fit you for a job or a service shop of your own—but also gives you a foundation for a career that can be profitable the rest of your life.

You work over 300 learn-by-doing experiments at home, using DeVry Tech's exclusive Electro-Lab method. You build and KEEP valuable equipment. With another DeVry Tech exclusive, you have the benefit of training movies that you can show over and over until basic points are crystal clear. Special texts guide you every step of the way as well.

HOW DeVRY TECH CAN "BLUEPRINT" YOUR CAREER!

DeVry's faculty not only know how to teach Electronics, but they also understand men. They most likely know the type of problems you face. From this staff you get help, advice and understanding. It is this "human" side of DeVry's program that has caused many of our graduates to say: "DeVry Tech not only trains you for a job, they actually help you blueprint a profitable future!"

NO ADVANCED EDUCATION NEEDED!

Why don't you write for FREE FACTS today? Learn how you TOO can be a member of the great fraternity of DeVry Tech graduates across the continent . . . men who were properly trained encouraged, appreciated and understood! SEND IN COUPON NOW!

EFFECTIVE EMPLOYMENT SERVICE


DeVry Tech's effective Employment Service is available to all graduates without additional cost.

2 FREE BOOKLETS Send Coupon TODAY!

"One of North America's Foremost Electronics Training Centers"



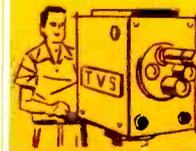Accredited Member of
National Home Study Council



TELEVISION



COMPUTERS



MICRO-WAVES



RADAR



BROADCASTING

**LET DeVRY HELP
YOU PREPARE
AND BLUEPRINT
A SOLID
CAREER IN
THIS
FAST-GROWING
FIELD!**



MAIL TODAY FOR FREE FACTS!

DeVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. RE-7Q

Please give me your 2 FREE BOOKLETS, "Pocket Guide to Real Earnings" and "Electronics in Space Travel," also include details on how to prepare for a career in one or more branches of Electronics.

Name _____ Age _____

Street _____ Apt. _____

City _____ Zone _____ State _____

Check here if you face military service.

2075 Canadian residents address: DeVry Tech of Canada, Ltd.
970 Lawrence Avenue West, Toronto, Ontario

**DeVRY TECHNICAL
INSTITUTE**
CHICAGO • TORONTO




for the money

circuit by

harman kardon

tubes by

Amperex*

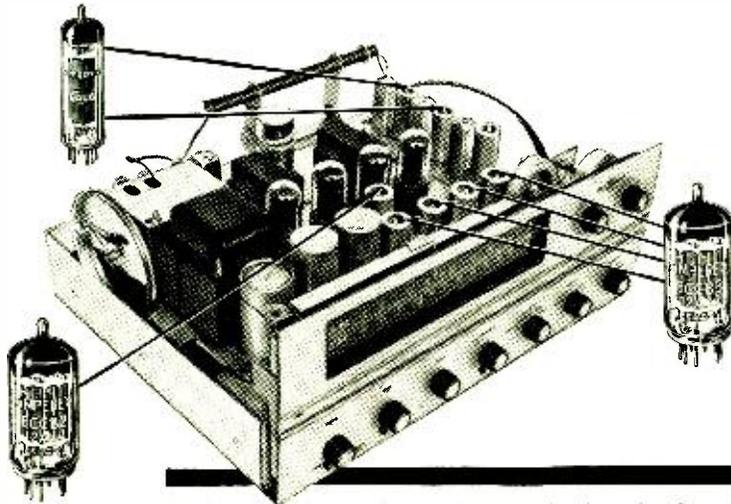

High gain...low noise...absence of microphonics...low distortion...reliability—these are the primary qualities circuit designers look for in electron tubes. Once again, Harman-Kardon engineers have found these qualities best exemplified in Amperex tubes. Small wonder, then, that the tube complement of the new Harman-Kardon "Stereo Recital" Model TA224 Integrated Stereophonic Receiver includes four Amperex 12AX7/ECC83's, one 12AU7/ECC82, and two 6AU6's.

These and many other Amperex 'preferred' tube types have proven their reliability and unique design advantages in the world's finest audio components.

Applications engineering assistance and detailed data are always available to equipment manufacturers. Write: Amperex Electronic Corp., Special Purpose Tube Division, 230 Duffy Avenue, Hicksville, L. I., New York.



ask Amperex
about hi-fi tubes
for hi-fi circuitry

OTHER AMPEREX TUBES FOR QUALITY HIGH-FIDELITY AUDIO APPLICATIONS

POWER AMPLIFIERS

6CA7/EL34: 60 w. distributed load
7189: 20 w., push-pull
6BQ5/EL84: 17 w., push-pull
6CW5/EL86: 25 w., high current, low voltage
6BM8/ECL82: Triode-pentode, 8 w., push-pull

VOLTAGE AMPLIFIERS

6Z6/EF86: Pentode for pre-amps
12A7/ECC81: Twin triodes, low
12AU7/ECC82: hum, noise and
12AX7/ECC83: microphonics
6BL8/ECF80: High gain, triode-pentode, low hum, noise and microphonics

RF AMPLIFIERS

6ES8: Frame grid twin triode
6ER5: Frame grid shielded triode
6EN7/EF183: Frame grid pentode for IF, remote cut-off
6EJ7/EF184: Frame grid pentode for IF, sharp cut-off
6AQ8/ECC85: Dual triode for FM tuners
6DC8/EBF89: Duo-diode pentode

RECTIFIERS

6V4/EZ80: Indirectly heated, 90 mA
6CA4/EZ81: Indirectly heated, 150 mA
5AR4/GZ34: Indirectly heated, 250 mA

INDICATORS

6FG6/EM84: Bar pattern
IM3/DM70: Subminiature "exclamation" pattern

SEMICONDUCTORS

2N1517: RF transistor, 70 mc
2N1516: RF transistor, 70 mc
2N1515: RF transistor, 70 mc
IN542: Matched pair discriminator diodes
IN87A: AM detector diode, subminiature

cylinder located behind the large white square on the left.

Power for the probe comes from 4,800 solar cells in four arms jutting from the 26-inch spherical package. The solar-cell output constantly charges 28 chemical batteries, the size and shape of standard flashlight cells only a great deal more powerful. These in turn power more than 40 pounds of electronics, a receiver, transmitters and associated logic units.

Stereo Disc Sales Up


A survey of a representative group of dealers in the New York area has revealed that sales of stereo discs for the first 4 months of the year average about 20% of total album sales. The percentage varies from dealer to dealer—5% to 45%.

For the same period last year, the average was about 14%, with no store having an individual average higher than 35%.

Translating Machine

A new high-speed translator has been translating Russian into English since June, 1959, according to International Business Machines Corp. IBM developed the machine under an Air Force contract.

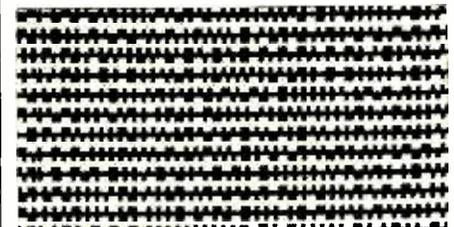The machine (or system) consists of an input Flexowriter, input register, dictionary and output Flexowriter. The dictionary is a 10-inch glass disc with about 50,000 words on it in the form of a black-and-white square-wave pattern on a set of circular tracks (see photos, one



shows disc, other shows 300x enlargement of tracks). The disc spins at 1,400 rpm, thus bringing each "bit" of information on it within quick reach of a beam of light from a cathode-ray tube (35 milliseconds average). A photomultiplier tube indicates whether the scanned spot on the disc is dark or light.

(Continued on page 12)

MOVING? MOVING? MOVING?

If you're moving please don't forget to send us your old address as it appears on your latest copy of the magazine. Include the numbers shown beside your name. If possible, send us the actual address label which is pasted on the lower right hand corner of the front cover. Be sure to include your postal zone number (if any) with your new address. If we receive this information before the 20th of the month, you will continue to get RADIO-ELECTRONICS without interruption.

Please send data to
Circulation Department

Radio-Electronics

154 West 14th Street • New York 11, N. Y.

2 Great *knigh-kit*® Citizens Band Transceiver Kits

A PRODUCT OF ALLIED RADIO

YOUR CHOICE OF THE FINEST VALUES IN 2-WAY RADIO EQUIPMENT



For Auto-to-Auto
or Auto to
Home or Office



For Farming
Operations



Local Trucking,
Delivery,
Construction Work



Boat-to-Boat,
Ship-to-Shore

YOU BE THE JUDGE OF
knigh-kit VALUE!
FREE Examination Privilege

We invite you to take advantage of our exclusive free examination offer. Order a Knight-Kit Transceiver. Examine it on arrival. Inspect the quality of the components, the circuitry, the easy-assembly manual. We're so confident you'll want the kit, we can make this offer: If you're not **COMPLETELY SATISFIED**, just return the kit for full refund!



Ultra-Selective
Super-Sensitive
The Very Finest

Lowest Cost
Quality
2-Way Radio

Citizens Band Superhet Transceiver Kit

Y-712L BEAUTIFUL STYLING... UNEXCELLED PERFORMANCE

\$79⁹⁵

\$5

Have dependable, economical 2-way radio communication with this top-rated, do-it-yourself transceiver. Has two crystal-controlled transmitting positions; operates at maximum FCC legal power input of 5 watts fully modulated. Superhet receiver is continuously tunable over the full 22 channel band; also has two optional crystal-controlled fixed frequency positions. Works just like press-to-talk intercom—speaker also serves as mike.

Ultra-selective, highly sensitive dual-conversion superhet receiver features built-in adjustable squelch and noise limiter. Sensitivity (manual) is better than 1 μ v for 10 db S/N; crystal, 1/2 μ v. Includes built-in AC power supply. Easy to assemble; has dependable printed circuitry and pre-aligned IF transformers. With distinctively styled high-impact case, 5 x 12 x 12". Complete with all parts, wire-type doublet antenna, and one transmitting crystal (available for any channel from 1 to 22—specify preference). FCC application form is included (license is available to any citizen over 18—no exams to take). See below for DC mobile supply, vertical antenna, etc. Wt., 20 lbs.

Model Y-712L. \$5 Down. ONLY **\$79⁹⁵**

- Y-729L. 3 Ft. Vertical Antenna. 2 lbs. NET **6.50**
- Y-714L. Mobile Mounting Bracket. 4 lbs. NET **5.35**
- Y-723L. 6-12 V. Mobile Power Supply. 6 lbs. NET **10.95**
- Y-769L. Optional Receiving Crystal (specify frequency) ... **1.99**
- Y-719L. Optional Hand-Held Mike. 1 lb. NET **9.50**

Manufactured and sold exclusively by **ALLIED RADIO**

Top Buy Citizens Band Transceiver Kit

Y-713L

\$39⁹⁵

\$2

Now have your own private 2-way radio system at an amazingly low cost! Consists of easy-to-assemble superregenerative receiver and 5-watt transmitter. Readily fits car, boat or desk. Single, one-switch operation permits talk or listen. Receiver tunes all 22 channels continuously. Built-in AC power supply. Handsomely styled case, 7x10x8". With mike, doublet antenna, and transmitting crystal (specify channel—1 to 22—if you have a preference). See below for antenna, mobile power supply, etc. Shpg. wt., 10 lbs.

Model Y-713L. \$2 Down. ONLY **\$39⁹⁵**

- Y-729L. 3 Ft. Vertical Antenna. 2 lbs. NET ... **6.50**
- Y-723L. 6-12 V. Mobile Power Supply. 6 lbs. **10.95**
- Y-724L. Mobile Mounting Bracket. 4 lbs. NET. **5.35**

ORDER NOW

ALLIED RADIO CORP., Dept. 68-G
100 N. Western Ave., Chicago 80, Ill.

Please ship: Y-712L Transceiver. Y-713L Transceiver.


Y-729L Y-723L Y-714L Y-724L
 Y-769L Y-719L \$_____ enclosed

Send latest catalog describing Knight-Kits.

Name _____

Address _____

City _____ Zone _____ State _____

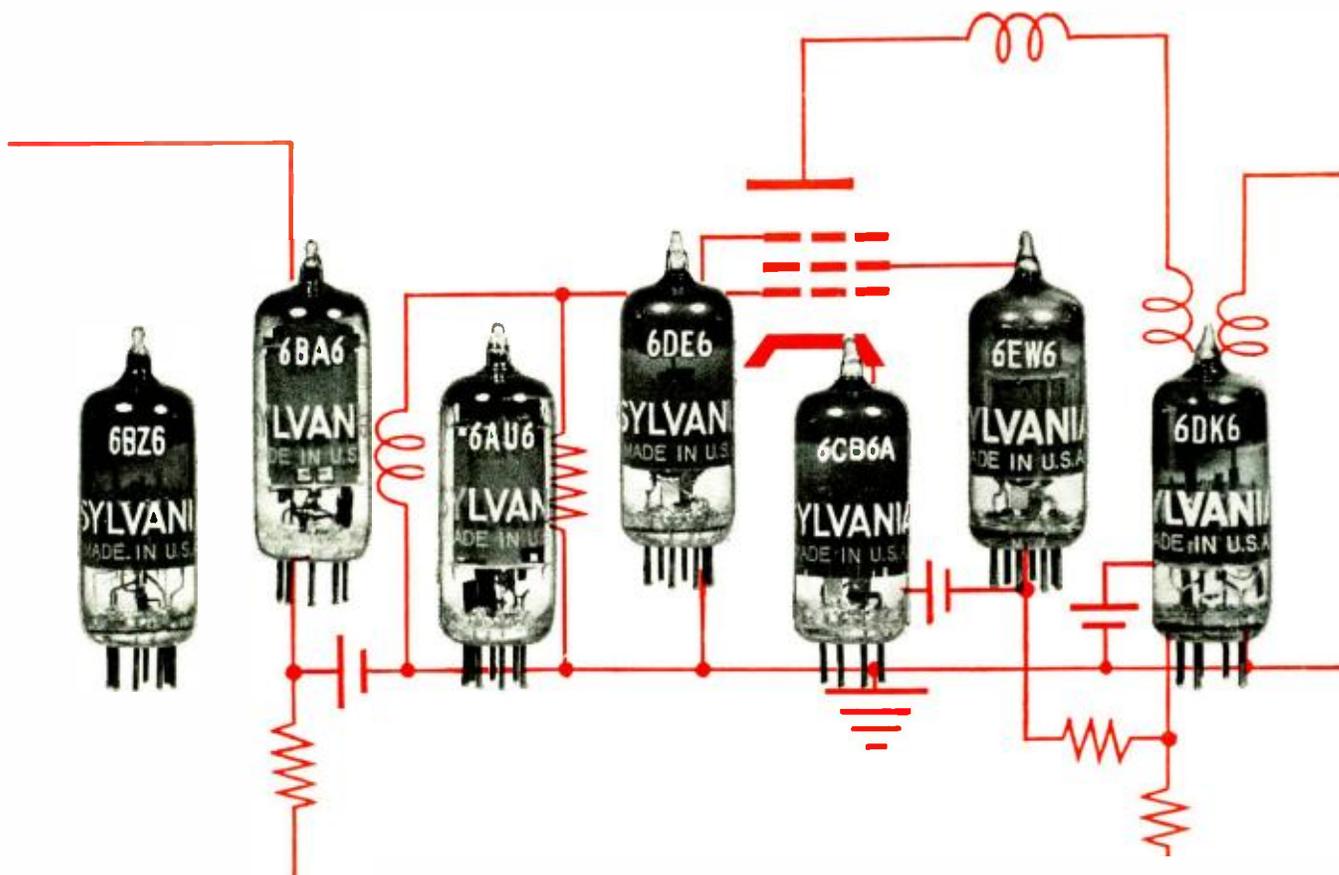

Why are SYLVANIA PENTODES so popular in TV sets?

Why, for example, are they so popular in video-if stages?

Video-if stages are critical with respect to over-all set performance. Must develop sufficient gain to "drive" the picture tube and to give effective agc. Have to deliver "clean" signals, free of hum modulation. When a TV set goes into quantity production, tubes used must be uniform in performance in their specific circuits. Tubes that are sent to the service dealer for that eventual replacement job must be just as good as those supplied to the set manufacturer.

Those are some of the reasons why you see SYLVANIA pentodes such as 6BZ6, 6BA6, 6AU6,

6DE6, 6CB6A, 6EW6, 6DK6 in TV set after TV set. They're reliable. And, because of the unique, automated techniques used by SYLVANIA in manufacturing those types, they feature exceptional uniformity from tube to tube, minimum interelectrode leakage and gas, thus a longer life expectancy.

Those are some of the same reasons why, for *original design* and for *replacement*, the popular tubes are SYLVANIA TUBES! Electronic Tubes Division, Sylvania Electric Products Inc., 1740 Broadway, New York 19, N. Y.

SYLVANIA

Subsidiary of **GENERAL TELEPHONE & ELECTRONICS** 

how to get a Commercial FCC LICENSE

We guarantee
to train you until you receive
Your FCC License
— or your money back


The Master Course in Electronics will provide you with the mental tools of the electronics technician and prepare you for a First Class FCC License (Commercial) with a radar endorsement. When you successfully complete the Master Course, if you fail to pass the FCC examination, you will receive a full refund of all tuition payments.

GET THIS HANDY POCKET ELECTRONICS DATA GUIDE

Free...

Puts all the commonly used conversion factors, formulas, tables, and color codes at your fingertips. Yours absolutely free if you mail the coupon in 30 days. No further obligation!

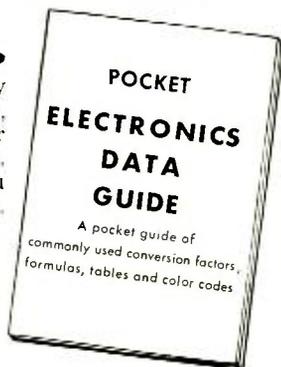**TO GET THIS FREE
GIFT, MAIL COUPON
Within 30 Days!**



“License and Good Job . . . Thanks”

“After finishing your Master Course, I passed the FCC exam for the 1st class license. I had my ticket for only one week and I got a job at WOC-TV, AM-FM. Incidentally, WOC is the oldest radio station west of the Mississippi. I sincerely feel that if it weren't for taking your Master Course, I would not have received my 1st class ticket. So I want to take this occasion to again thank you for such a fine preparation for electronics work.”

FRANCIS J. McMANUS
Davenport, Iowa

CLEVELAND INSTITUTE OF ELECTRONICS
Desk RE43A 4900 Euclid Avenue Cleveland 3, Ohio

Mail
Coupon
NOW!



good training
doesn't cost . . .
it pays!

get all three FREE!

We can train you to pass your License Exams if you've had any practical experience — amateur, military, radio servicing, or other. Our proven plan can help put you on the road to success.

- Your FCC ticket will be recognized by employers as proof of your technical ability.

Accredited by the National Home Study Council

Cleveland Institute of Electronics

Desk RE43A, 4900 Euclid Ave., Cleveland 3, Ohio

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below.

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other _____ |

In what kind of work are you now engaged?

In what branch of Electronics are you interested?

Name _____ Age _____


Address _____

City _____ Zone _____ State _____

RE43A

3 Great New Kits for Stereo by **PACO**

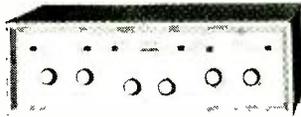
... with the famous specially-prepared giant-size diagrams and super-simple step-by-step instructions for fool-proof assembly and wiring. Crafted by PACO, Kit Division of **PRECISION Apparatus Company, Inc.**, world-famous manufacturers of laboratory electronic test equipment for over a quarter of a century.



The PACO SA-40 40 WATT STEREO PREAMP-AMPLIFIER The Last Preamp-Amplifier You'll Ever Have to Buy

Model SA-40—KIT, complete with gold and satin black cabinet. **Net Price: \$79.95**

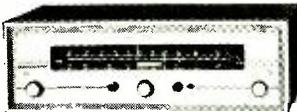Model SA-40W—FACTORY-WIRED, complete with gold and satin black cabinet. **Net Price: \$129.95**




The PACO ST-45 AM-FM STEREO TUNER A Truly Unusual Engineering Achievement in Stability and Sensitivity

AVAILABLE THREE WAYS:

Model ST-45—KIT, with factory pre-aligned transformers, complete with gold and satin black cabinet. **Net Price: \$84.95**

Model ST-45PA—SEMI-KIT, with both FM and AM tuner sections factory-wired and completely pre-aligned and calibrated for hairline sensitivity, complete with gold and satin black cabinet. **Net Price: \$99.95**

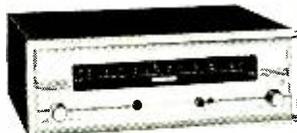Model ST-45W—FACTORY-WIRED, aligned, calibrated and assembled, complete with gold and black satin cabinet. **Net Price: \$134.95**



The PACO ST-35 FM TUNER

AVAILABLE THREE WAYS:

Model ST-35—KIT, with factory pre-aligned transformers, complete with gold and satin black cabinet. **Net Price: \$59.95**

Model ST-35PA—SEMI-KIT, with tuner section factory-wired and completely pre-aligned for hairline sensitivity, complete with gold and satin black cabinet. **Net Price: \$69.95**

Model ST-35W—FACTORY-WIRED, aligned, calibrated and assembled, complete with gold and satin black cabinet. **Net Price: \$89.95**



NEW PACO 2-WAY SPEAKER SYSTEM SEMI-KIT featuring Jensen Mid-Range Woofer and Horn-Type Tweeter

Model L2-U—SEMI-KIT, with unfinished, sanded cabinet. **Net Price: \$59.95**

Model L2-F—SEMI-KIT, with walnut-finished cabinet. **Net Price: \$69.95**



AVAILABLE AT LEADING ELECTRONIC PARTS DISTRIBUTORS & WHEREVER GOOD SOUND IS SOLD. You'll want much more data... the performance specifications will amaze you... write for complete, illustrated brochure to:

PACO ELECTRONICS CO., INC.
70-31 84th Street, Glendale 27, L. I., New York
Kit Division of **PRECISION Apparatus Company, Inc.**

NEWS BRIEFS (Continued from p. 8)

A typist copies the Russian to be translated on a special typewriter that converts the characters into holes on a tape, from which they are translated into the black-and-white language of the disc. A tape reader places a set of characters in the input register. A comparator compares them with whatever the beam is scanning, then indicates in what direction the beam should move to find the information desired. This is equivalent to an individual looking at any open page in a dictionary and then flipping pages in the right direction to get to the word he wants. The beam reads sections of each track (there are 700 of them) as it skips from one to the next. When it reaches the right track, the comparator stops it so it can read the whole track and find the word (or phrase) in the register. When the proper match is found, the English equivalent is read out and sent to the output Flexewriter. At the same time, a new set of characters is fed to the input register.

At the present time, the machine translates at about 30 words per minute. This limit is caused by the relatively slow input and output rates, not by the translator itself. By the end of the year, a special reading machine and high-speed output writers will extend the machine's speed to about 1,800 words per minute.

Since the machine translates on a word-for-word basis, the output is not grammatically correct. This is a sample from an article dated December 30, 1959 that appeared in *Pravda*:

"Let us note that addition to band visible light wave only one part radiospectrum led during the last decade to creation new science—radioastronomy with/from it truly phenomenal achievements. It allows investigators penetrate in region the most stormy nonstationary physical process, performing in celestial bodies." A word analyzer and lexical buffer now under development will allow much smoother future translations.

Radar Mapping


Thanks to a side-looking radar, it is now possible to get accurate aerial maps of thousands of square miles of terrain per hour in any weather in which man can fly. Developed by Texas Instruments for the Air Force, the new radar could also give near-photographic, up-to-the-minute information on troop and material movements well behind the enemy's front lines.

A sample radar map is shown in the photograph. It was made by a plane flying over Dallas, Tex. The white stripe across the center is the flight path of the plane and is a blind spot. For this picture, the sweep was 6 miles on each side of the plane. Thus an area about 12 miles by 15 1/4

miles can be mapped in the time it takes a plane to fly over it.

An advantage of the system for military use is that the radar map can be transmitted directly to headquarters and there need be no delay while waiting for the plane to return.

The side-looking radar, officially called the AN/APQ-55, has other advantages over ordinary photographic reconnaissance. It can isolate moving targets as a number of "radar maps" can be made of the same area in a short time. Radar maps also tend to be more accurate than standard photographic methods since the perspective of distance is adjusted electronically. Therefore, the items on the edge of the photo are in the same scale as those at the center. In an

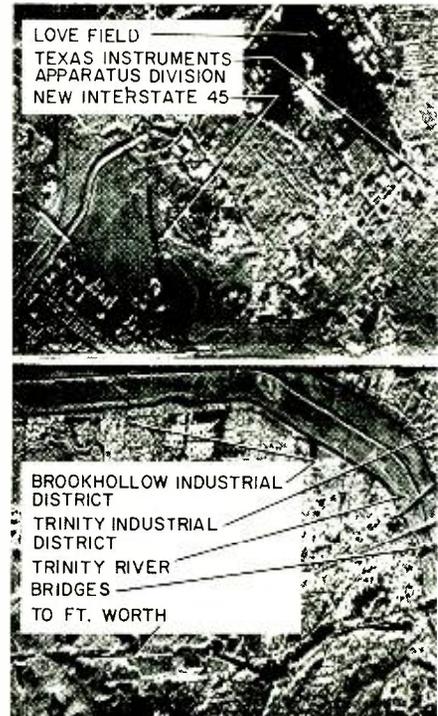

aerial photograph, ground distances are compressed as the distance from the camera increases. Also, an aerial camera scanning a fixed angle will map less area at low altitude. The side-looking radar mapping system scans a constant ground area independent of altitude.

In nonmilitary applications, the systems have already been used to detect icebergs in North Atlantic shipping lanes. Standard radar cannot differentiate between icebergs and fishing vessels which just drift with the current. Coast Guard personnel reported that the new radar identified icebergs, growlers and field ice. It also differentiated between bergs and other stationary targets even in foggy weather.

Astronaut—19-Inch Transistor TV

A 19-inch square-cornered picture tube backed up by 23 transistors and 12 diodes is the newest thing in
(Continued on page 16)

2 great **SPRAGUE DIFILM**® tubulars

are tops in their field . . . take your choice!

For maximum reliability
and performance
under toughest conditions

SPRAGUE DIFILM® **BLACK BEAUTY**®



Sprague Black Beauty tubulars are missile-type capacitors. Actually, they are low cost versions of the famous Sprague capacitors now being used in every modern military missile. Where positive reliability is important, make no mistake, use Black Beauty Difilm Molded Capacitors! You get the most for the least with Black Beauties!

Difilm Black Beauties are engineered to withstand the hottest temperatures to be found in TV or auto radio sets—in the most humid climates. Further, unlike straight polyester film tubulars, these capacitors operate in a 105°C environment—without derating!

Black Beauty tubulars are tough units, too—no fragile shell to break—you can't damage them in soldering. For your convenience, every capacitor is marked twice . . . no need to twist capacitor around to read rating.

For extremely small
size and exact
original replacement

SPRAGUE DIFILM® **ORANGE DROP**®



Sprague Difilm "Orange Drops" are a "must" for your service kit where only an exact replacement will fit. They are the perfect replacement for dipped capacitors now used by leading manufacturers in many popular television receivers. And when a dipped tubular is called for, you'll find that Orange Drops outperform all others, safeguarding your work and reputation for quality service.


Orange Drops are specially designed for easiest possible installation. Radial leads are crimped to assure neat mounting parallel to printed wiring boards . . . extremely small size makes them fit handily in tight spots. They'll beat heat and humidity because the solid, rock-hard capacitor section, double-dipped in bright orange epoxy resin, is well protected against moisture. A perfect team-mate for Black Beauty.

The heart of these Sprague Difilm Capacitors can't be beat! It's a dual dielectric combination of Mylar® polyester film and special capacitor tissue—resulting in capacitors which are superior to all other comparable tubulars. Sprague's rock-hard solid HCX® impregnant fills voids and pin holes in the film. Difilm capacitors have high insulation resistance, low power factor, and excellent capacitance stability and retrace under temperature cycling!

±10% CAPACITANCE TOLERANCE IS STANDARD AT NO EXTRA COST

Difilm Black Beauty and Difilm Orange Drops are packaged in sturdy, reusable rigid plastic Kleer-Pak® boxes. Your distributor is stocked in all the popular ratings. Order some today. You can count on Difilm.

SPRAGUE®
THE MARK OF RELIABILITY

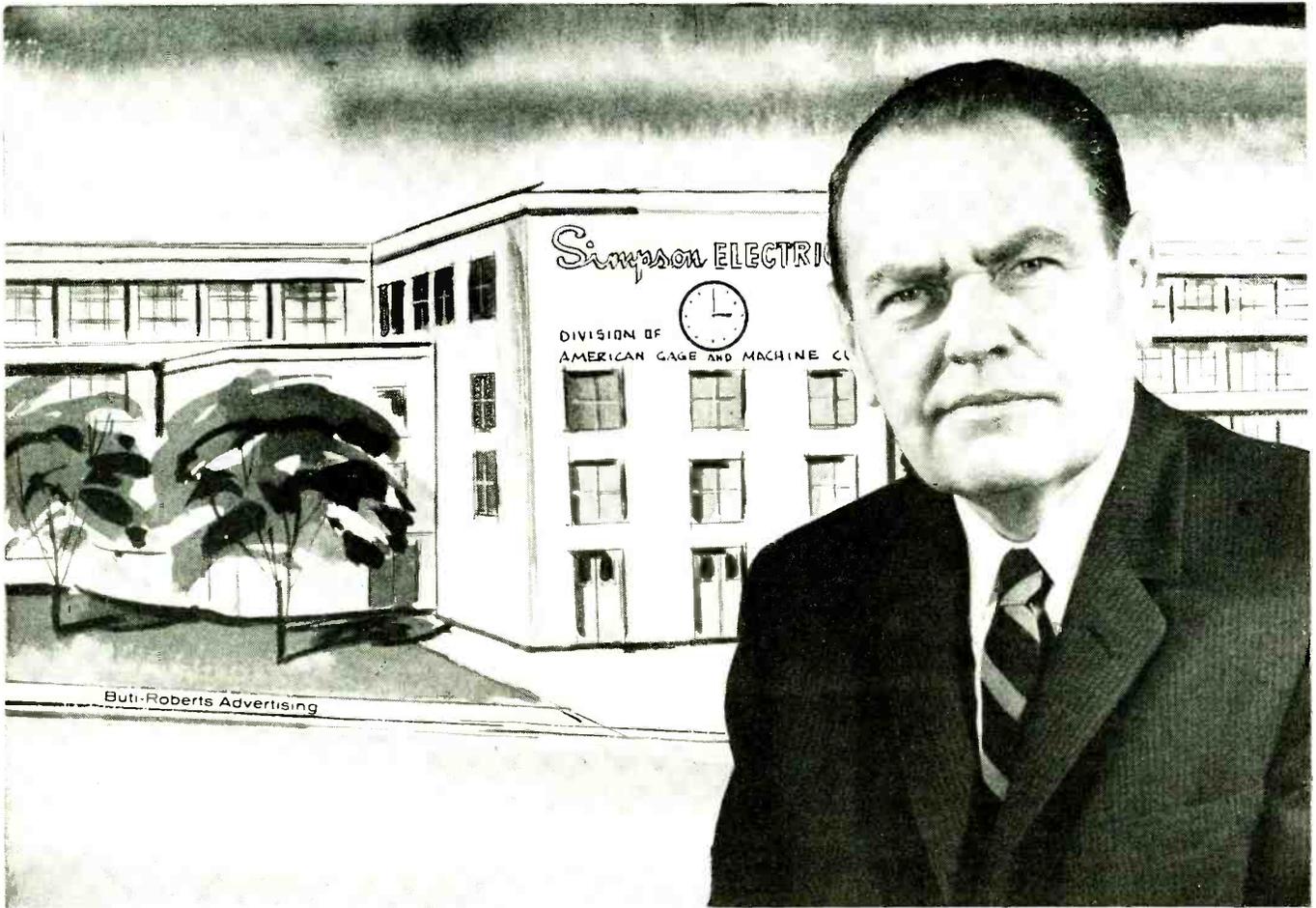

“We get the Simpson sales story across to jobbers by selling through independent electronic representatives”

Says Mel Buehring, Director of Sales, Simpson Electric Co.

“Merchandising, good customer relations, and product information are all a big part of the Simpson Electric Company sales picture. We’ve found that in 99% of the sales areas, the best way to be sure we’re getting through to the jobbers is to work with independent representatives. You can count on their knowing their jobs. These experts talk the jobber’s language and they know the ins and outs of the marketing and distribution problems peculiar to their particular area.

“And because he works his territory in-

tensively, the representative gets a friendly reception that is immeasurable in goodwill and reflected in gross sales.”


Whatever your line, you can benefit from the special talents and experience of the independent electronics Representative. And it’s easy to find Representatives especially suited to your particular sales requirements. One effective way is through the “Lines Available” columns in ERA’s publication, *The Representor*, distributed monthly to all member Representative companies. Write for complete details.



Electronic Representatives Association

600 So. Michigan Ave., Chicago 5, Illinois

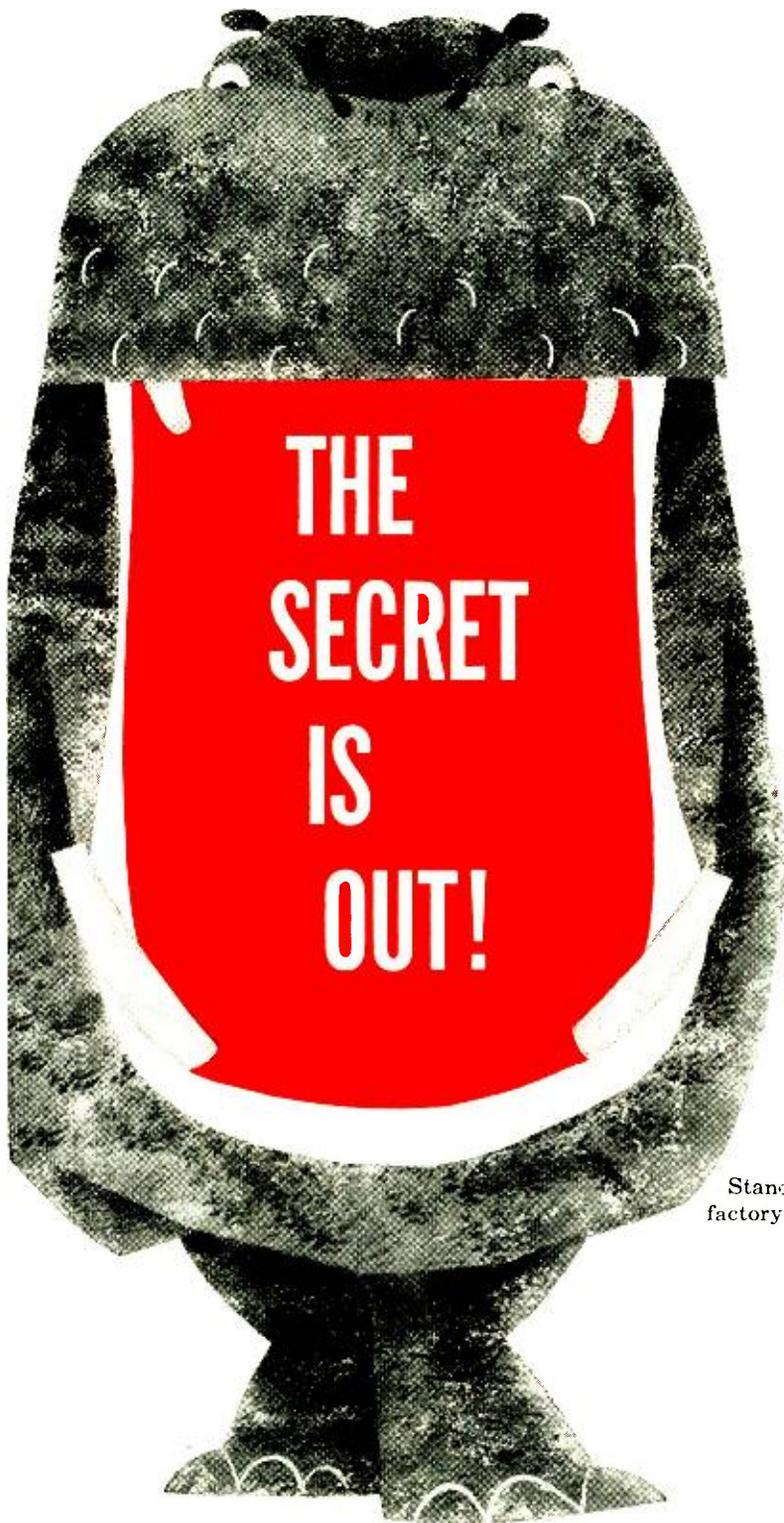Dedicated to improving and extending the role of the representative in electronics marketing.



Here is the new Standard Coil Tuner Replacement and Repair Program that enables you to offer better service to your customers at greater profit. Now Standard Coil Products provides the tools that will enable you to cash in on the profitable tuner repair and replacement market.

TUNER REPLACEMENT LISTING IN SAMS PHOTOFAC

Starting in January, Standard Coil tuner replacement listings will appear in all Sams TV Photofact. Tuner replacement information will be right at your finger tips. Standard Coil is the *only* manufacturer ever to provide this service.

NEW TV TUNER REPLACEMENT GUIDE

Lists original equipment TV tuners with the Standard Coil equivalent replacement for each. Also includes major mechanical replacement parts for all Standard Coil Tuners—those used in original equipment as well as the universal replacement. Eliminates all guesswork—minimizes your tuner repair and replacement problems.

48 HOUR FACTORY GUARANTEED REPAIR SERVICE

Standard Coil's special service department set-up assures factory guaranteed repairs—*on a 48 hour in-plant cycle!*

All repaired tuners carry a *six month warranty* on defective workmanship and parts failure (including tubes). Gives you more time for additional service calls—promptly returns your customer's set to like new operating condition.

DEFECTIVE TUNER TRADE-IN ALLOWANCE

Tuners which can *not* be repaired can be traded in against a new replacement tuner which carries a full *twelve month factory guarantee*. See your Standard Coil Distributor for complete details on how trade-ins can increase your tuner sales and profits—create greater customer satisfaction.

JUMP ON THE STANDARD COIL PROFIT WAGON TODAY!

For additional details, see your authorized Standard Coil Distributor or write to:

Standard

Coil Products Co., Inc.


2085 North Hawthorne Avenue, Melrose Park, Illinois

3 GREAT NEW PROFIT MAKERS

... Designed to help technicians achieve accuracy, speed and greater profits in their every day work.


OTHER MERCURY TEST INSTRUMENTS THAT HAVE WON THE UNANIMOUS APPROVAL OF TECHNICIANS EVERYWHERE

Model 300 COMBINATION TESTER

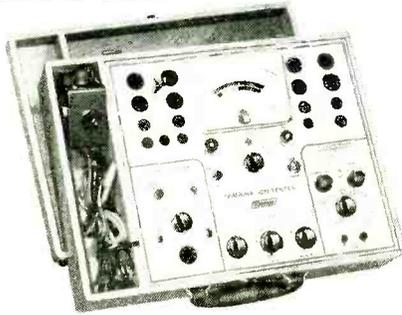

- ✓ A MULTIPLE-SOCKET TUBE TESTER
 - ✓ A CRT TESTER-REACTIVATOR
 - ✓ A 20,000 Ohms per Volt VOM and CAPACITY-TESTER
- ALL COMBINED IN ONE COMPACT UNIT!**

AS A TUBE TESTER... will check emission, inter-element leakage and gas content of over 700 tube types — AS A CRT TESTER-REACTIVATOR... will test, repair and reactivate all black and white and all color picture tubes — AS A VOM AND CAPACITY TESTER... sensitivity is 20,000 ohms per volt/DC and 5000 ohms per volt/AC... Capacity range: .001 mfd. to 80 mfd.... Housed in hand rubbed oak carrying case... Size, 17½x13¾x4½". DEALER NET **\$9975**

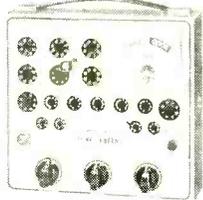


The speed of a multiple-socket tube tester at an economy price.

Model 101—DEALER NET **\$3995**



A deluxe tube tester that also tests diodes, rectifiers, fuses, pilot lamps, tube filaments.

Model 102-P—DEALER NET **\$5950**

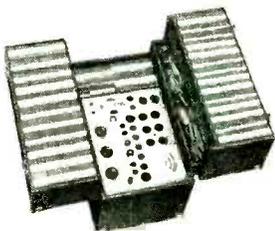

A deluxe tube tester and compact tube caddy... all-in-one.

Model 102-C—DEALER NET **\$7450**

A valuable assistant in the serviceman's shop.

Model 201-F Self-Service Tube Tester (floor model) DEALER NET... **\$15850**

Model 201-C Self-Service Tube Tester (counter model) DEALER NET... **\$10950**



Model 800 CRT TESTER-REACTIVATOR

TEST, REPAIRS, REACTIVATES ALL BLACK AND WHITE AND ALL COLOR PICTURE TUBES...


TESTS... emission, inter-element leakage and life expectancy — REPAIRS... shorts, and open elements — REACTIVATES... weak tubes with a controlled high voltage pulse (reactivation is seen and controlled on the meter as it takes place) — Tests the red, green and blue sections of color tubes separately... Also provides the newer 2.35 and 8.4 filament voltages... Hand rubbed oak carrying case... Size, 11½x9½x4½". DEALER NET... **\$4995**



Model 400 VOM—CAPACITY TESTER

- ✓ A 20,000 Ohms per Volt VOM
- ✓ AN ACCURATE CAPACITY METER

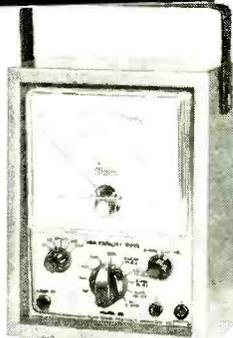DC VOLTAGE RANGES: 0 to 15/75/150/300/750/1500/7500 V... AC VOLTAGE RANGES: 0 to 15/75/150/300/750/1500 V... DC CURRENT RANGES: 0 to 75 microamps/7.5 ma./75 ma./750 ma./15 amps... CAPACITY RANGE: .001 mfd. to 80 mfd. RESISTANCE RANGES: 0 to 1,000/100,000 ohms/0 to 10 megohms... Sturdy hammer-tone finish steel case... Size, 5½x7½x3½". DEALER NET... **\$3995**



See Your Electronics Parts Distributors!



ELECTRONICS CORP.
manufacturers of quality electronic products

77 Searing Ave., Mineola, N. Y.

CANADA: Active Radio & TV Ltd., 58 Spadina Ave., Toronto 2, Ont.

portable TV. It puts a home receiver picture on the screen of a battery-powered portable. The 40-pound set is made by Motorola as the model 19P1 Astronaut. The set's sensitivity is 15 µv and its noise figure reaches a maximum of 10 db—both figures approximately the same as for conventional sets.

For portable operation, the Astronaut is powered by a 5-pound silver-cadmium battery. It will operate the



set between 5 and 6 hours before recharging is necessary. The battery can be recharged a minimum of 500 times and is not damaged by complete discharge. It is automatically recharged when the set is connected to ac line power. A built-in single-pole antenna folds out of sight when not in use. The set has a fiberglass carrying case, with a front cover to protect the picture tube.

Calendar of Events

- Congress of the International Federation of Automatic Control, June 25–July 9, Moscow State University, Moscow, USSR.
- National Convention on Military Electronics, June 27–29, Sheraton Park Hotel, Washington, D. C.
- New England Electronic Conference, June 27–29, Balsams, Dixville Notch, N. H.
- 1960 Music Industry Trade Show, July 10–14, Palmer House, Chicago, Ill.
- Conference on Medical Electronics, July 21–27, Olympia, London, England.
- Global Communications Symposium, Aug. 1–3, Statler Hotel, Washington, D. C.
- National Audio-Visual Association Convention and Exhibit, Aug. 6–9, Morrison Hotel, Chicago.
- Electronic Packaging Symposium, University of Colorado, Boulder, Colo., Aug. 18–19.
- Western Electronic Show & Convention, (WESCON) Aug. 23–26, Memorial Sports Arena, Los Angeles, Calif.
- British Radio & Television Exhibition, Aug. 24–Sept. 3, Earls Court, London, England.
- International Conference on Semiconductor Physics, Aug. 29–Sept. 2, Prague, Czechoslovakia.
- International Symposium on Information Theory, Aug. 29–Sept. 3, London, England.

**Through
HOME STUDY
or in
RESIDENT CLASSES**

ELECTRONICS

— field of opportunity —

the Grantham Communications
Electronics Course prepares you
for your first class commercial
F.C.C. LICENSE

The Grantham home study course teaches you principles of electronics in a simple "easy-to-grasp" manner. Each new principle is explained first in *everyday language* and then, after you understand it, is associated with the proper *technical language*. You learn and remember more, because the emphasis is on *understanding* rather than on memorizing.

This correspondence course is directed toward two major objectives — (1) to *teach* you a great deal about electronics, and (2) to prepare you to *pass* all of the F. C. C. examinations required for a first class commercial operator's license. We teach you step by step and have you practice with FCC-type tests which you send to the School for grading and comment. You prepare for your F. C. C. examinations under the watchful direction of an instructor who is especially qualified in this field.

Grantham training is the easy way to learn more quickly — to prepare more thoroughly — for F. C. C. examinations. And your first class license is the quick, easy way to prove to your employer that you are worth more money.

Get details concerning *how* we can prepare you for your F. C. C. license and *how* that license can help you advance in electronics. Mail the coupon below to the home office of Grantham School of Electronics in Hollywood, Calif., and our free catalog will be sent to you promptly.



offers

interesting and profitable careers in
RADIO AND TV BROADCASTING • TWO-WAY RADIO COMMUNICATIONS • RESEARCH AND DEVELOPMENT • RELAY STATION MAINTENANCE • AUTOMATION ELECTRONICS • TECHNICAL WRITING IN ELECTRONICS • INDUSTRIAL ELECTRONICS • ELECTRONIC COMPUTERS • MILITARY ELECTRONICS • INSTRUMENTATION • TELEMETERING • AERONAUTICAL ELECTRONICS • SPACE ELECTRONICS and many other

interesting and profitable fields of the present and future

To get ahead in electronics, you must have the proper training and your employer must know that you have that training. Your F. C. C. license is a "diploma" in communications electronics granted by the U. S. Government, and it is recognized as such by employers. Grantham School of Electronics specializes in preparing you to earn this diploma.

HERE'S PROOF... that Grantham students prepare for F. C. C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Edgar T. Phelps, 931 Hickory Street, Poplar Bluff, Mo.	1st	12
Wayne Hogg, 4830 San Fernando Rd., Glendale, Calif.	1st	20
Robert Watson, Star Route, Box 24, Renovo, Pa.	1st	12
William H. Patchin, 3865 Westview Ave., NW, Canton, Ohio	1st	12
V. Dean DeVore, 309 Bess Street, Washington, Ill.	1st	16
Edward T. Wall, Box 184, Kenly, N. C.	1st	12
James W. Wranich, 4236 Michigan Street, Kansas City, Mo.	1st	20
Robert E. Sullivan, 2475 E. Douglas, Des Moines, Iowa	1st	12
Nelson S. Kibler, 1413 Patrick Henry Dr., Falls Church, Va.	1st	18
Barry L. Ulrich, 1110 Chestnut Ave., Barnesboro, Pa.	1st	14
Jerry E. Milligan, 707 Ragsdale Dr., Milan, Tenn.	1st	12
Robert S. Davis, 2100 10 Ave., So., Apt. 12, Birmingham, Ala.	1st	13

If you are interested in details concerning our training, indicate in the coupon below whether you prefer home study or resident classes, and mail the coupon to the School's home office in Hollywood, California — to the address given in the coupon — for free details.

GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD

SEATTLE

KANSAS CITY

WASHINGTON

FIRST CLASS F.C.C. LICENSE IN 12 WEEKS

Grantham resident schools are located in four major cities — Hollywood, Seattle, Kansas City, and Washington, D. C. Regularly scheduled classes in F. C. C. license preparation are offered at all locations. New day classes begin every three months, and new evening classes begin four times a year. The day classes meet 5 days a week and prepare you for a first class F. C. C. license in 12 weeks. The evening classes meet 3 nights a week and prepare you for a first class license in 20 weeks. For more information about the Grantham resident schools, indicate in the coupon the city of your choice and then mail the coupon to the School's home office in Hollywood, Calif. Free details will be mailed to you promptly.

GRANTHAM SCHOOL OF ELECTRONICS
1505 N. Western Ave., Hollywood 27, Calif.

MAIL COUPON FOR FREE DETAILS — NO SALESMAN WILL CALL



(Mail in envelope or paste on postal card)

To: **GRANTHAM SCHOOL OF ELECTRONICS**
1505 N. WESTERN AVE., HOLLYWOOD 27, CALIF.

Gentlemen:

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.


Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study Kansas City classes
 Hollywood classes Seattle classes Washington classes

04-K

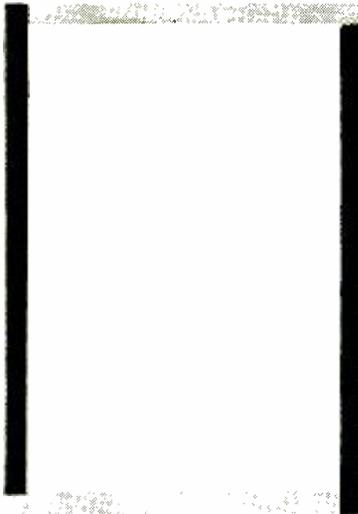

◀ *this*

is a picture of the technician who had a call-back on a Quam Speaker installation.

(You'll notice the space is blank. Servicemen who install Quam speakers can "sell 'em and forget 'em." You just don't get called back.)

this ▶

is a picture of a Quam speaker which was defective when received from the factory.

(This space is blank, too. Every Quam speaker is individually checked and tested before it leaves the factory.)




◀ *this*

is a picture of your bank book.

You'll notice how your deposits grow when you rely on Quam Adjust-a-Cone Speakers for every installation.

QUAM-NICHOLS COMPANY
238 E. MARQUETTE ROAD • CHICAGO 37, ILLINOIS

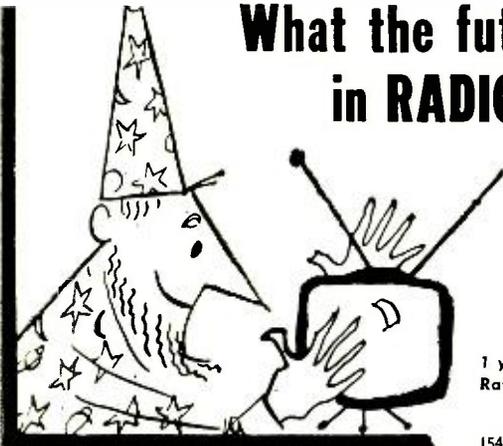What the future holds for you in RADIO-ELECTRONICS



- Radio Control with "Oomph"
- Industrial Applications of Infrared
- Design and Build the New Twin-Coupled Amplifier
- Servicing Sync Stages
- Transistor Paging Receiver
- Testing Electrolytic Capacitors

SUBSCRIPTION RATES

1 year \$4.00 2 years \$7.00 3 years \$10.00
Rates go up after October 31—Subscribe now and save.

RADIO-ELECTRONICS

154 West 14th Street New York 11, N. Y.

Correspondence



INDUSTRIAL SERVICING

Dear Editor:

Having been a reader of Gernsback publications since the days of the Electro Importing Co., on Fulton St., I must say I have gained a wealth of knowledge. However, the electronics industry is moving so fast, I decided to specialize.

I would like to see more articles on industrial servicing, and I would also like to hear from manufacturers in regard to servicing their equipment in the New Jersey area.

JOHN I. MEYER

Union City, N. J.

WANTED: LESS CONFUSION

Dear Editor:

In the dark ages (early 1900's), many companies made vacuum tubes. Fortunately for civilization, they got together and adopted a standard numbering system. Now, all 6SN7's are the same, no matter who makes them. This is progress.

What happened to this progress when it came to diode and transistor numbering? The other day I tried to find a particular transistor in a parts catalog. The transistors from 10 companies were listed with as many different numbering systems. Insanity, stupidity, chaos—what would you call it?

I thought this was a modern, intelligent generation. How about a movement to standardize diode and transistor numbering, basing and testing? Let's get organized!

KENNETH GREENBERG

Chicago, Ill.

WHAT ABOUT THE FUTURE?

Dear Editor:

I read your editorial ("Microelectronics") in the February issue with interest since my livelihood has been derived solely by repairs to radio and television receivers for the past 15 years.

If I correctly interpreted your editorial, it would seem that the present servicing business is to be tremendously reduced—possibly in 8 to 12 years—due to commercial use of micro-electronic techniques.

This brings me to the question of what program of preparation would be best for service technicians like myself—if the need for such a program exists.

I would appreciate any suggestions

IMPORTANT: for the man who wants to make big money in Radio-Television!

ONLY SPRAYBERRY TRAINING IN RADIO and TELEVISION

**OFFERS YOU ALL OF THESE VITAL NEW ADVANTAGES
TO HELP YOU EARN MORE MONEY FROM THE START!**

NEW BUSINESS BUILDERS

...through these practical proven plans and ideas we help you make plenty of extra money in spare time while training.

NEW TRAINING EQUIPMENT

...the famous Sprayberry Training kits have been newly engineered by our staff to offer you the latest in Radio-TV Service Techniques!

NEW TRANSISTOR COURSE

...literally millions of new transistor radios are being used. We show you how to make money fixing them!

NEW HIGH FIDELITY

...there's big money to be made installing and servicing Hi-Fi units. Your Sprayberry training now offers you this valuable and profitable preparation!

TRAIN AT HOME—SPARE TIME


WITH THESE **25 BIG COMPLETE KITS OF PARTS & EQUIPMENT**



You learn Radio-TV Servicing the best way... the practical way... testing and assembling these modern kits of equipment.


← The new Sprayberry Training Television Receiver, built and tested in 5 sections.

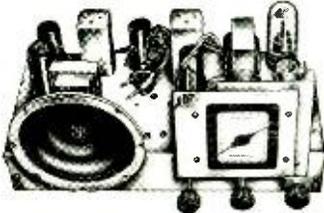Now offered... this fine modern oscilloscope.



← You build this powerful two-band super-heterodyne radio receiver.

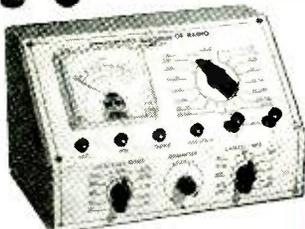You build the new Sprayberry tester — a complete 18-range Volt-Ohm-Milliammeter test meter.



FREE These two big new books are yours free! Find out what Radio-Television offers you... and let us show you how easily you can learn, even without previous experience of any kind. Rush COUPON today!

The field of Radio-Television Servicing is such a fast moving industry that the best jobs and biggest incomes always go first to the man with the most modern, complete and up-to-date training. Thanks to constant revision and improvement... Sprayberry Training helps you earn more from the start... and keeps you earning more in the months and years ahead!

Make no mistake! All radio-television training is not alike. The basic purpose behind Sprayberry Training is to prepare you as rapidly and as surely as possible... to make top money servicing Radio and Television sets and equipment. This is where the big money has been for years... and will continue to be in the years ahead.

It's important for you to know that for over 30 years... Sprayberry Training has been preparing ambitious men for success in this interesting and profitable kind of work. Our school has helped hundreds to qualify for the best jobs... or to get started in profitable businesses of their own. Today our student rolls are the largest in our school's history... because the need and demand for Radio-Television Service Technicians has never been more urgent.

Just \$6.00 Starts You

To encourage more men to enter Radio-Television at once... to help fill the great need for trained men... we're making it easier than ever before to start training. Just \$6.00 enrolls you. This liberal offer is naturally limited. Get the facts now


and consider enrollment while these favorable terms are available to you.

KEEP YOUR JOB ... while learning

Under the Sprayberry Plan you train entirely at home in spare time. You combine the most modern lesson training with fascinating and invaluable practical work with 25 big kits of parts and equipment that we supply. You get the equivalent of years of shop practice... and you can train as fast or as slowly as you wish. We help you make excellent spare time money while learning... and everything you receive—lessons, books, manuals, equipment—all yours to keep!

This is the Radio-Television industry's most modern and up-to-the-minute training. Sprayberry is the one school that gives you personalized attention and takes a real interest in your progress. Remember... just \$6 starts you! Mail the coupon today. Let the facts speak for themselves. Let us send you our new catalog and sample lesson... and prove the kind of opportunity that Sprayberry training can open up for you.

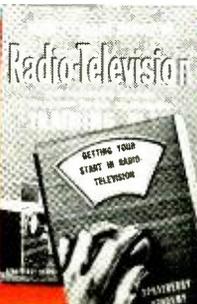SPRAYBERRY ACADEMY OF RADIO-TELEVISION
Dept. 20-N, 1512 West Jarvis Ave., Chicago 26, Ill.



MAIL COUPON - No Salesman Will Call

SPRAYBERRY ACADEMY OF RADIO-TELEVISION
DEPT. 20-N 1512 W. JARVIS AVE., CHICAGO 26, ILL.

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

NAME..... AGE.....

ADDRESS.....

CITY..... ZONE..... STATE.....

CORRESPONDENCE (Continued)

from you on this matter as you are intimately acquainted with the scope of the electronics field.

LAWRENCE A. HALEY

Wilmington, Del.

[During the next 10 years, micro-electronics is likely to be used in only such things as missiles and satellites. Micro-electronic techniques will not go into mass production until at least the early 1970's. TV screens must be large enough to see, so extreme miniaturization would not make much sense in home TV sets.

Radios the size of cigarette filter tips are interesting to think of, but are they necessary? How would you tune one?

As semiconductors come into more common use, set operating temperatures will drop. This will reduce the amount of service needed.

It seems to us that home servicing is not going to expand greatly over any extended period of time. That is why we have started our Industrial Electronics section—to alert technicians to this expanding field. Our advice is to learn as much as possible about the industrial servicing field as it will probably play a large part in the industry as a whole. —Editor]

MATCHBOX RADIO

Dear Editor:

I have a few additional comments to make about the "Matchbox Radio" (June, 1960, page 58):

1. The radio will operate a loudspeaker. [The test report indicated that it had not been tried with a speaker.—Editor] In general, if you can hear a station on a headset, you can hear it on a speaker.

2. The output can be taken from between the emitter and the positive battery lead. When the phones are unplugged, the battery is disconnected from the circuit. When using a speaker, the output transformer is not necessary because this emitter circuit is low-impedance. A 3.2-ohm speaker works well; higher-impedance speakers work better.

3. Battery voltage is noncritical one way. If you increase it, the volume goes up, but you increase the chances of a thermal runaway. *This occurs unfailingly at 9 volts.* If the voltage is reduced, the volume goes down. It drives a loudspeaker on strong local stations with as little as 1.5 volts.

4. Cheap, second-choice transistors can be used in this circuit.

5. Antenna coil L is a luxury. A suitable coil can be jumble wound on any mandrel, or an old video peaking coil can be used. Any value between 200 and 300 μ h will do.

A. V. J. MARTIN

Paris, France

ANTIQUÉ-RADIO COLLECTORS

Dear Editor:

Over the past year I have received more than 600 letters from antique-radio fans and collectors all over the country. Most of them would like to organize some sort of a club to help them reach other collectors. Also, many newcomers to the hobby would like to trade, buy or sell parts and sets, but don't know whom to contact.

I started a little over a year ago and have collected about 250 sets. This kept my typewriter (and myself) busy day and night whenever I had a spare minute. I would not like to see this happen to other collectors as it is very discouraging.

If you would like a club, *write and let me know.* A post-card is all I need.

I would like to put out a newssheet about every 2 weeks or every month, depending on how much (news and ads) there is to fill it. This means getting a mimeograph machine. For this I need *your* help. Cost of placing an ad in the sheet would be about 3 cents per word. (Of course the readership would be made up almost entirely of collectors.)

How about it fellows? If you are interested, write and let me know.

JAMES H. STEGNER

R. D. No. 1
Clearfield, Pa.

[If you are interested in forming an organization of antique-radio collectors, here is an opportunity. If any of you have an old (or new, for that matter) mimeograph machine

**RESIDENT SCHOOL COURSES IN
LOS ANGELES AND NEW YORK CITY**

**START YOUR CAREER
IN ELECTRONICS NOW
AT RCA INSTITUTES...
Choose from this list**

	Course	Qualifications	Length of Course
A	Advanced Electronic Technology (T-3)	High School grad, with Algebra, Physics or Science	Day 2 1/4 yrs. Eve. 6 3/4 yrs.
B	TV and General Electronics (V-7)	2 yrs. High School, with Algebra, Physics or Science	Day 1 1/2 yrs. Eve. 4 1/2 yrs.
C	Radio & TV Servicing (V-3)	2 yrs. High School	Day 9 mos. Eve. 2 1/4 yrs.
D	Transistors*	V-3 or equivalent	Eve. 3 mos.
E	Electronic Drafting (V-9)*	2 yrs. High School, with Algebra, Physics or Science	Eve. 3 yrs.
F	Color TV	V-3 or equivalent	Day 3 mos. Eve. 3 mos.
G	Audio-Hi Fidelity*	V-3 or equivalent	Eve. 3 mos.
H	Video Tape*	V-3 or equivalent	Eve. 3 mos.
I	Technical Writing (V-10)	V-3 or equivalent	Eve. 3-18 mos.
J	Radio Telegraph Operating (V-5)*	2 yrs. High School, with Algebra, Physics or Science	Day 9 mos. Eve. 2 1/4 yrs.
K	Radio Code (V-4)*	8th Grade	Eve. as desired
L	Preparatory Math & Physics (P-0)	1 yr. High School	Day 3 mos.
M	Preparatory Mathematics (P-OA)	1 yr. High School	Eve. 3 mos.

*Courses to be added to Los Angeles Curriculum

RCA Institutes is one of the largest technical institutes in the United States devoted exclusively to electronics. Coeducational Day and Evening classes. Free placement service. Applications now being accepted.



The Most Trusted Name in Electronics

RADIO CORPORATION OF AMERICA



--- Send to the school nearest you ---

RCA Institutes, Inc. Dept. RER-70
350 West Fourth Street Pacific Electric Building
New York 14, New York 610 S. Main St., L.A. 14, Calif.

Please send me your FREE catalog. I am interested in the courses circled below.

A B C D E F G H I J K L M

Name _____ (please print)
 Address _____
 City _____ Zone _____ State _____


For Home Study Courses See Ad On Opposite Page



RCA INSTITUTES



OFFERS YOU THE FINEST OF HOME STUDY TRAINING

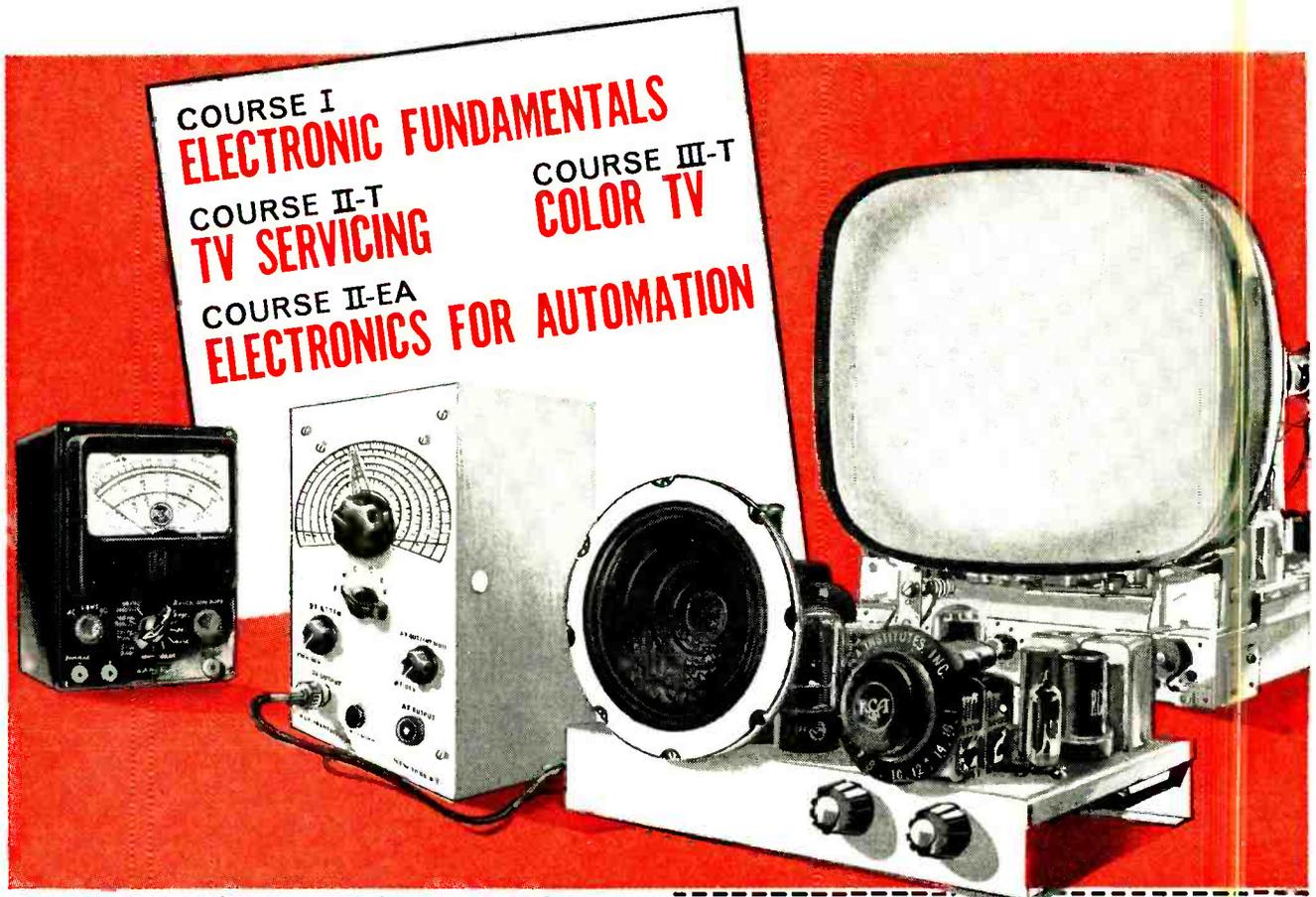


**COURSE I
ELECTRONIC FUNDAMENTALS**

**COURSE II-T
TV SERVICING**

**COURSE II-EA
ELECTRONICS FOR AUTOMATION**

**COURSE III-T
COLOR TV**

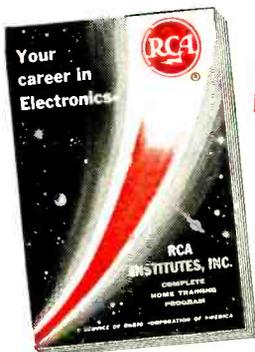The equipment illustrated and text material you get with each course is yours to keep. Practical work with very first lesson. Courses for the beginner and the advanced student. Pay-as-you-learn. You need pay for only one study group at a time.



**SEND FOR THIS
FREE BOOK NOW** 

For Resident School courses, see ad on opposite page.

RCA INSTITUTES, Inc. Home Study School Dept. RE-70

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.
Without obligation, send me **FREE 64-page CATALOG** on Home Study Courses. No salesman will call.

Name Age.....
Please print

Address

City Zone..... State

Korean Vets! Enter discharge date

CANADIANS—Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to:

RCA VICTOR COMPANY, LTD.
5575 Royalmount Ave., Montreal 9, Que.
To save time, paste coupon on postcard

Centralab[®] has the answer

to your *dual* control problems

FASTATCH Dual Radiohms[®]



No need to fence with dual concentric replacements . . . your problems are solved with CENTRALAB Model F and R controls. Just match front and rear units with proper resistance and taper—cut shafts to length (it's easy with the CENTRALAB SK-2 precision Shaft-Kut Tool)—snap together, and *touche*, you're ready to go.

You won't be foiled by switch problems, either. Just parry them by snapping on a Fastatch KR line switch if needed.

Fastatch Radiohms enable you to meet the demand for an immense variety of dual concentrics with a minimum of components. (The handy FDK-100 Kit provides coverage of 90% of your dual control requirements.) Ask your distributor for full information about CENTRALAB Model F & R controls.

CENTRALAB products are listed in PHOTOFACETS, COUNTERFACTS, and THE RADIO-ELECTRONIC MASTER.

Centralab

8-c-002

ELECTRONICS DIVISION OF GLOBE-UNION INC.
922G E. KEEFE AVE. • MILWAUKEE 1, WIS.
IN CANADA: P. O. Box 400, Ajax, Ontario

CONTROLS • ROTARY SWITCHES • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

CORRESPONDENCE (Continued)

and accessories, its use would be greatly appreciated. The question of dues or subscription is likely to come up shortly. Mr. Stegner will find that the cost in time and money of keeping in touch with several hundred collectors can be on the high side.—*Editor*]

BOB MIDDLETON REPLIES

Dear Editor:

I was somewhat surprised to see Mr. Mack's letter in the June issue because I have long doubted that anybody reads my articles, or, if they do—who gives a hoot anyhow?

If we *define* resistance as existing only in cylindrical packages with pigtail leads at the ends, I will agree with his objections. On the other hand, a 1N34 crystal diode is a semi-cylindrical package with pigtail leads, and it has *both positive and negative resistance*. If we wish to buy a negative resistance, we can ask the man for a 1N34, or, better, a 1N653 tunnel diode.

Now, a tunnel diode has positive resistance, as long as we use a low voltage. If we increase the source voltage, we arrive at a point where the diode has a negative resistance. When we apply *more* voltage, *less* current flows.

A type 24 tube has positive plate resistance (about 600,000 ohms) as long as the plate is operated at a higher voltage than the screen grid. But, if the screen is operated at a higher voltage than the plate, the plate resistance becomes negative. To put it another way, the negative resistance appears as *less* current if *more* plate voltage is applied.

I see no easy way to accept these positive resistances as "real" and then turn around and assert that the negative resistances are "unreal."

It actually makes little difference whether we allow positive resistance to a crystal diode and disallow its negative resistance, as long as we realize that it does exist and can make an electronic circuit work.

To my way of thinking, I must accept negative resistance of a crystal to be as real as its positive resistance. We connect a crystal diode across an L-C circuit, and bias the diode to make this negative resistance cancel the circuit's positive resistance. The circuit oscillates. Hence, I cannot agree that "—200 ohms has no significance to us whatever."

Sure, we took a few swipes at "Eggy." But we are TV technicians—not keepers of the keys to the ivory towers. Personally, I prefer to be told that "the cat ate the canary" rather than "the feline quadruped ingested a member of the genus *insula* Canaris."

Mr. Mack is right; "Eggy" has a real and vital part in industry today. So does Mr. Mack. I am only asking that more thought be given to the problem of communication. Life is too short to spend 90% of it consulting the unabridged dictionary while multiton sputniks circle over our heads.

ROBERT G. MIDDLETON
Birmingham, Mich. END

The specs prove it...your best buy is



B
TV-FM SWEEP GENERATOR
AND MARKER #368
KIT \$69.95 WIRED \$119.95



A
DYNAMIC CONDUCTANCE
TUBE & TRANSISTOR
TESTER #666
KIT \$69.95 WIRED \$109.95
Complete with steel cover & handle

C
RF SIGNAL GENERATOR #324
KIT \$26.95 WIRED \$39.95



D
PEAK-TO-PEAK
VTVM #232 &
UNIPROBE
KIT \$29.95
WIRED \$49.95



E
COLOR & MONOCHROME
DC TO 5 MC LAB & TV
5" OSCILLOSCOPE #460
KIT \$79.95 WIRED \$139.50
5" PUSH-PULL
Oscilloscope #425:
Kit \$44.95 WIRED \$79.95

A Tests all receiving tubes (picture tubes with adapter), n-p-n and p-n-p transistors. Composite indication of Gm, Gp & peak emission. Simultaneous selection of any one of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot.). Sensitive 200 ua meter. 10 six-position lever switches: freepoint connection of each tube pin. 10 pushbuttons: rapid insertion of any tube element in leakage test circuit. Direct reading of inter-element leakage in ohms. New gear-driven rollchart, CRA Adapter \$4.50.

B Entirely electronic sweep circuit with accurately-biased inductor for excellent linearity. Extremely flat RF output. Exceptional tuning accuracy. Hum and leakage eliminated. 5 fund. sweep ranges: 3-216 mc. Variable marker range: 2-75 mc

in 3 fund. bands, 60-225 mc on harmonic band, 4.5 xtal marker osc., xtal supplied. Ext. marker provision. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Narrow range phasing control for accurate alignment.

C 150 kc to 435 mc with ONE generator in 6 fund. bands and 1 harmonic band! $\pm 1.5\%$ freq. accuracy. Colpitts RF osc. directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. mod. amplifier: only 3.0 v needed for 30% mod. Turret-mounted, slug-tuned coils for max. accuracy. Fine and Coarse (3-step) RF attenuators. RF output 100,000 uv, AF output to 10 v.

D Uni-Probe — exclusive with EICO — only 1 probe performs all functions: half-turn of probe tip selects DC or AC-Ohms. Calibration without re-

moving from cabinet. Measure directly p-p voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v. with HVP probe, & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 meg. $4\frac{1}{2}$ " meter, can't-burn-out circuit. 7 non-skip ranges on every function. Zero center.

E Features DC amplifiers! Flat from DC to 4.5 mc, usable to 10 mc. Vert. Sens.: 25 mv/mm; input 2-3 megs; direct-coupled & push-pull throughout. 4-step freq.-compensated attenuator up to 1000:1. Sweep: perfectly linear 10 cps — 100 kc (ext. cap. for range to 1 cps). Pre-set TV V & H positions. Auto sync. lim. & ampl. Direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite screen with dimmer control; plus many more outstanding features.

FREE CATALOG shows you HOW TO SAVE 50% on 65 models of top quality professional test equipment. MAIL COUPON NOW!



New Transistor
Portable Radio RA-6
Kit \$29.95
Wired \$49.95
Incl. F.E.T., less 9V batt.
Prealigned RF, IF
xfmrs; push-pull
audio; 6" spkr.

*PAT. PEND.



NEW Power & Bias
Supply for
Transistorized
Eqt. #1020 *
Kit \$19.95
Wired \$27.95



NEW Tube &
CRT Fil.
Tester #612
Kit \$3.95
Wired \$5.95
Fast-checks
radio/TV tubes,
pilot lamps, etc.



Series/Parallel
R-C Combination
Box #1140
Kit \$13.95
Wired \$19.95



Tube Tester #625
Kit \$34.95
Wired \$49.95
• tests 600 mil
series string type
tubes
• illuminated
roll-chart
Pix Tube Test
Adapter..... \$4.50



6V & 12V Battery
Eliminator
& Charger #1050
Kit \$29.95
Wired \$38.95
Extra-filtered for
transistor equip.
#1050 Kit \$38.95
Wired \$47.95



20,000 Ohms/Volt
V-O-M #565
Kit \$24.95
Wired \$29.95
1000 Ohms/Volt
V-O-M #536
Kit \$12.90
Wired \$14.90



33-00 Northern Blvd. L. I. C. 1, N. Y.

Add 5% in the West. © 1959

TURN PAGE FOR MORE EICO VALUES



R-C Bridge & R-C-L
Comparator #950B
Kit \$19.95
Wired \$29.95
Reads 0.5 ohms-
500 megs,
10 mmfd-5000 mfd,
power factor



VTVM Probes
Kit Wired
Peak-to-Peak \$4.95 \$6.95
RF \$3.75 \$4.95
High Voltage
Probe-1 \$6.95
High Voltage
Probe-2 \$4.95
Scope Probes
Demodulator \$3.75 \$5.75
Direct \$2.75 \$3.95
Low Capacity \$3.75 \$5.75

EICO
33-00 Northern Blvd.
L. I. C. 1, N. Y.

C-7

Show me HOW TO SAVE 50% on Test Instruments
 Hi-Fi Ham Gear. Send free Stereo Hi-Fi Guide,
 Send free short course for novice license. Send me
FREE Catalog, name of neighborhood dealer.

Name
Address
City Zone State

Over 2 MILLION EICO Instruments in use throughout the world. Add 5% in the West.



IF YOU LOVE TO CREATE... BUILD **EICO** KITS

In **STEREO** and
Mono Hi-Fi...
 the experts say
 your Best Buy
 is **EICO**



Stereo Amplifier-Preamplifier HF81†



Stereo Preamplifier HF85††



**FM Tuner HFT90††
 AM Tuner HFT94††
 FM/AM Tuner HFT92††**



**100W Stereo Power Amplifier HF89
 70W Stereo Power Amplifier HF87
 28W Stereo Power Amplifier HF86**



Stereo Integrated Amplifier AF4††



**3-Way Speaker System HF53
 2-Way Bookshelf Speaker Systems
 HF55 and HF51**



**NEW!
 Stereo Automatic Changer/
 Player 1007**



- Exclusive advanced systematized engineering
- Latest and finest quality parts
- Exclusive "Beginner-Tested" easy step-by-step instructions
- Exclusive TRIPLE quality control
- Exclusive LIFETIME guarantee at nominal cost

IN STOCK — Compare, then take home any EICO equipment — right "off the shelf" — from 1500 neighborhood EICO dealers throughout the U.S. and Canada.

HF81 Stereo Amplifier-Preamplifier selects, amplifies, controls any stereo source & feeds it thru self-contained dual 14W amplifiers to a pair of speakers. Provides 28W monophonically. Ganged level controls, separate balance control, independent bass and treble controls for each channel. Identical Williamson-type, push-pull EL84 power amplifiers. "Excellent." — SATURDAY REVIEW. "Outstanding... extremely versatile." — ELECTRONICS WORLD. Kit \$69.95. Wired \$109.95. Incl. cover.

HF85 Stereo Preamplifier: Complete master stereo preamplifier-control unit, self-powered. Distortion borders on unmeasurable. Level, bass, & treble controls independent for each channel or ganged for both channels. Inputs for phono, tape head, mike, AM, FM, & FM-multiplex. One each auxiliary A & B input in each channel. "Extreme flexibility... a bargain." — HI-FI REVIEW. Kit \$39.95. Wired \$64.95. Incl. cover.

New HF89 100-Watt Stereo Power Amplifier: Dual 50W highest quality power amplifiers. 200W peak power output. Uses superlative ultra-linear connected output transformers for undistorted response across the entire audio range at full power, assuring utmost clarity on full orchestra & organ. 60 db channel separation. IM distortion 0.5% at 100W; harmonic distortion less than 1% from 20-20,000 cps within 1 db of 100W. Kit \$99.50. Wired \$139.50.

HF87 70-Watt Stereo Power Amplifier. Dual 35W power amplifiers identical circuit-wise to the superb HF89, differing only in rating of the output transformers. IM distortion 1% at 70W; harmonic distortion less than 1% from 20-20,000 cps within 1 db of 70W. Kit \$74.95. Wired \$114.95.

HF86 28-Watt Stereo Power Amp. Flawless reproduction at modest price. Kit \$43.95. Wired \$74.95.

FM Tuner HFT90: Prewired, prealigned, temperature-compensated "front end" is drift-free. Prewired exclusive precision eye-tronic® traveling tuning indicator. Sensitivity: 1.5 uv for 20 db quieting; 2.5 uv for 30 db quieting, full limiting from 25 uv. IF bandwidth 260 kc at 6 db points. Both cathode follower & FM-multiplex stereo outputs, prevent obsolescence. Very low distortion. "One of the best buys in high fidelity kits." — AUDIOCRAFT. Kit \$39.95*. Wired \$65.95*. Cover \$3.95. *less cover, F.E.T. incl.

AM Tuner HFT94: Matches HFT 90. Selects "hi-fi" wide (20-9000 cps @ -3 db) or weak-station narrow (20-5000 cps @ -3 db) bandpass. Tuned RF stage for high selectivity & sensitivity. Precision eye-tronic® tuning. "One of the best available." — HI-FI SYSTEMS. Kit \$39.95. Wired \$65.95. Incl. cover & F.E.T.

New FM/AM Tuner HFT92 combines renowned EICO HFT90 FM Tuner with excellent AM tuning facilities. Kit \$59.95. Wired \$94.95. Incl. cover & F.E.T.

New AF-4 Economy Stereo Integrated Amplifier provides clean 4W per channel or 8W total output. Kit \$38.95. Wired \$64.95. Incl. cover & F.E.T.

HF12 Mono Integrated Amplifier (not illus.): Complete "front end" facilities & true hi-fi performance. 12W continuous, 25W peak. Kit \$34.95. Wired \$57.95. Incl. cover.

New HF53 3-Way Speaker System Semi-Kit complete with factory-built 34" veneered plywood (4 sides) cabinet. Bellows-suspension, full-inch excursion 12" woofer (22 cps res.) 8" mid-range speaker with high internal damping cone for smooth response. 3 1/2" cone tweeter. 2 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest frequency & best transient response. 32-14,000 cps clean, useful response. 16 ohms impedance. HWD: 26 1/2", 13 7/8", 14 3/8". Unfinished birch. Kit \$72.50. Wired \$84.50. Walnut or mahogany. Kit \$87.50. Wired \$99.50.

New HF55 2-Way Speaker System Semi-Kit complete with factory-built 34" veneered plywood (4 sides) cabinet. Bellows-suspension, 5/8" excursion, 8" woofer (45 cps. res.), & 3 1/2" cone tweeter. 1 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest freq. & best transient resp. 45-14,000 cps clean, useful resp. 16 ohms,

HWD: 24", 12 1/2", 10 1/2". Unfinished birch. Kit \$47.50. Wired \$56.50. Walnut or mahogany. Kit \$59.50. Wired \$69.50

HF51 Bookshelf Speaker System complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps range, 8 ohms. HWD: 23" x 11" x 9". Kit \$39.95. Wired \$47.95

HF52 Omni-Directional Speaker System (not illus.) HWD: 36", 15 1/4", 11 1/2". "Fine for stereo" — MODERN HI-FI. Completely factory-built. Mahogany or walnut \$139.95. Blond \$144.95.

New Stereo Automatic Changer/Player: Jam-proof 4-speed, all record sizes, automatic changer and auto/manual player. New extremely smooth, low distortion moisture-proof stereo crystal cartridge designed integrally with tonearm to eliminate mid-range resonances. Constant 4 1/2 grams stylus force is optimum to prevent groove flutter distortion. No hum, turntable attractions, acoustic feedback, center-hole enlargement. Only 10 3/4" x 13". Model 1007D: 0.7 mil diamond, 3 mil sapphire dual styli, \$59.75. 1007S: 0.7 mil, 3 mil sapphire, \$49.75. Incl. F.E.T.

†Shown in optional Furniture Wood Cabinet WE71: Unfinished Birch, \$9.95; Walnut or Mahogany, \$13.95.

††Shown in optional Furniture Wood Cabinet WE70: Unfinished Birch, \$8.95; Walnut or Mahogany, \$12.50.

EICO, 33-00 N. Blvd., L.I.C. 1, N. Y. C-7

Show me how to SAVE 50% on easy-to-build top-quality Hi-Fi. Send FREE catalog, Stereo Hi-Fi Guide plus name of neighborhood EICO dealer.

Name.....

Address.....

City..... Zone..... State.....

Listen to the EICO Hour. WABC-FM, N.Y., 95.5 MC, Mon. to Fri. 7:15-8 P.M., Sat. 11-12 P.M. Ask dealer about EICO's Stereo Records Bonus.

© 1960 by EICO, 33-00 N. Blvd., L. I. C. 1, N. Y.

AROUND THE WORLD IN 80 SECONDS

... *The Strategic Air Command's Amazing Communications Net* ...

AS an editor, we are inclined to take electronics pretty much for granted. TV, color TV, radar, bouncing signals off the sun, we've heard about them all. You can't blame us for being a little bit hard-boiled and blasé.

But every once in a while something happens to restore our enthusiasm. Recently we were flying at 250 miles an hour 15,000 feet over Ohio in a plane of the SAC—*Strategic Air Command*. Our host picked up a microphone and called a ground station in Guam, in the Pacific. Guam answered immediately. He called another in Tokyo. Tokyo answered at once. Then in rapid succession he called Okinawa, Hawaii, Alaska, Greenland, Labrador, California, Louisiana, Massachusetts, Bermuda, Puerto Rico, England, Spain, Libya and Saudi Arabia. All answered their calls in seconds. We had talked our way around the world in less than 2 minutes.

Stunt? No—it happens regularly every day. This demonstration occurred aboard the military plane assigned to Lt. Gen. Francis Griswold, Vice Commander in Chief of SAC. (He is also an active ham, K0DWC.) We, together with a group of other editors, were en route to see SAC's remarkable world-wide communications headquarters and underground command post at Offutt Air Force Base, near Omaha, Neb.

The primary purpose of SAC's communications web is to get orders to its bombers and missiles in seconds, should this be necessary. Actually there are three separate communication networks, all converging on the underground command post in Nebraska. The first is a one-way telephone system with better than 99% reliability which connects Offutt with SAC's Air Forces around the world. It terminates at the famous "red telephone." The telephones in this system differ from conventional desk sets in one respect: They each have an acknowledgment button. In an alert, SAC headquarters may wish to pass frequent orders over the system. Yet it must be certain that the orders have been received by all. Upon receipt of a call, each station listens to the message and is asked to acknowledge it. This it does by pressing the acknowledge button. As each button is pressed, a corresponding light flashes on the central panel at the commander's desk back at Offutt.

It's impossible to describe adequately our feelings during a test. Within 10 seconds, we watched more than three score of tiny lights glimmer on one by one in acknowledgment. Lights turned on by the push of a button in Saudi Arabia, in Guam, in Greenland, in Spain!

Being primarily a wire system using commercial facilities, this network could be disrupted by sabotage or enemy action in an emergency. To backstop it, SAC has its *Commander's Net*. This is a single-sideband voice radio system, normally used as a ground-to-ground system interconnecting the commanders of the various segments of SAC. The air-to-ground demonstration mentioned earlier used this Commander's Net. Since SAC is on a continuous alert, commanders must be able to communicate instantly even when airborne. Hence commanders' planes are specially equipped with equipment similar to that at the ground stations. The performance of the single-sideband (SSB) equipment is remarkable, especially when one considers that 500 watts is the maximum power used. Despite this modest power, the system has a reliability of about 95%. It also provides almost instant world-wide communication. The Commander's Net is made up of stations at 26 locations throughout the world. Each station can operate on three different frequencies ranging from 2 to 35 mc simultan-

ously, if prevailing traffic should make it necessary.

One of the great advantages of the system is its relaying capabilities. Frequently, ionospheric conditions make it impossible to talk directly to some stations in the net. At the flick of a switch the operator at any one station can convert his equipment to a two-way relay station, picking up the signals from one station and retransmitting them instantaneously to another. In one demonstration we witnessed at Offutt, the operator could not reach Hawaii, although he could talk with Guam, a more distant point. He asked Guam to relay Hawaii. This was done instantly and Offutt talked with Hawaii via Guam. Except for a slight deterioration of clarity, it was impossible to know whether communication was direct or by relay.

The third and most important communications net operated by SAC is the ground-to-air Bomber Control net known as "Short Order." This is the net which would give the "go" order to SAC's bombers in the event of an enemy nuclear attack. Short Order is also SSB. The ground stations (two are in operation and two are in construction) consist of three 45-kw and six 10-kw transmitters at each location together with 16 directional and omnidirectional antennas. The associated receiving stations use essentially similar antennas and two receivers. Operating frequencies for the 45-kw transmitters and the receivers as well as individual antennas can be selected instantly by a telephone type dialing system in the underground command post. Complete system control can be taken over by any one of the stations on a moment's notice.

Another interesting feature of the SAC command post is a closed-circuit color TV system. This chain is used to transmit the status information displayed on the panels in the operations and intelligence centers to staff officers within the SAC headquarters. Five separate program channels are available. Color is used because much of the information displayed is color-coded. A separate black-and-white closed-circuit system connects the SAC command post with the Combat Operations Center of the North American Air Defense Command (NORAD) at Colorado Springs, Colo. Through this circuit, NORAD surveillance of North America is simultaneously displayed in front of the SAC controller.

Flexibility of control is the outstanding feature of the SAC nets. This requires complex control circuits. Maintenance and repair problems are compounded and skilled service technicians are of vital importance. Much of the test gear seen at the Short Order station sites would be strange to the average service technician, although familiar to the laboratory man. Precision frequency standards, laboratory type scopes and frequency counters are standard. The not-so-old cliché that modern armies (and air forces) are made up of technicians is nowhere better illustrated than at SAC.

A taxpayer's first reaction to SAC's installation is pride and satisfaction. But this is jolted aside by General Griswold's blunt complaint that communications development has not kept pace with missile and nuclear technology advances and that progress for many years has been primarily the result of improved technology rather than real breakthrough. One reason for this, in his estimation, is the relatively small amount of money devoted to communications research compared to that spent on atomic and missile research. He cited two relatively simple problems still crying for solution: Elimination of precipitation static interference on planes and development of really good antennas for planes.

—M.H.G.

THE TUNNEL DIODE STORY

By R. L. WATTERS* and J. V. CLAEYS*

THE tunnel diode reported in 1958 by Japanese scientist Dr. Leo Esaki, is an entirely new semiconductor device. It is like a diode because it has two terminals and like a transistor since it may be used to amplify power.

Although related to the transistor, the tunnel diode operates upon a different principle and offers advantages not found in transistors. Some of these are its very small size, extreme speed and stability under varying temperature conditions.

It is a new circuit element which may, with appropriate circuitry, function as a switch, amplifier and oscillator. Amplification and oscillation are possible well into microwave frequencies. At lower frequencies tunnel diode circuits may be simpler, smaller or more efficient than those of vacuum tubes or transistors. Let's see what this tunnel diode is and how it can be used in different circuit applications.

This new device gets its name from a mechanism called "quantum-mechanical tunneling" (until now of only theoretical interest) which describes the manner in which electrical charges move through the device. The combination of this "tunnel effect" and the fact that the device comprises a p-n junction between two regions of very heavily doped semiconductor material has led to the name tunnel diode.

Negative resistance

The property of the tunnel diode produced by the tunnel effect is the negative resistance which appears over a portion of its voltage range. A negative resistance may be defined as a circuit element in which current decreases with increase in voltage (or vice versa). This negative-resistance property is illustrated in Fig. 1, which shows the current-voltage characteristic of a typical germanium tunnel diode at room temperature. The negative-resistance region of the curve lies between points A and B.

The slope of this curve at any point is the resistance of the tunnel diode at that point. A vertical region (infinite increase in current), for example, would indicate zero resistance while a horizontal region (no increase in current)

would indicate an infinitely large resistance. In addition, a region which slopes upward to the right indicates a positive resistance while a region which slopes upward to the left indicates a negative resistance. An examination of the curve of Fig. 1 shows that the region from zero to A represents a positive resistance, the region from A to B represents the negative resistance and the region beyond B again represents a positive resistance. The current-voltage characteristic of the tunnel diode, therefore, has a region of negative resistance between two regions of positive resistance.

While the tunnel diode is related to the transistor, the semiconductive material used is much more heavily doped with impurity than that used for transistors. It is almost metallic, and no hermetic seal is necessary for protection from such things as surface contamination and moisture penetration.

A p-n junction formed between a heavily doped body of p-type conductivity and a heavily doped body of n-type conductivity semiconductive material is very narrow, about one-millionth of an inch or less. It is this combination, with the proper forward bias, that allows a "tunnel" current to flow and produces the negative resistance. All we need to know about this tunnel current is that *its transit time is so short that it does not affect the maximum operating frequency of the diode.* This frequency limit is set by the junction capacitance and negative resistance of

the device and the bulk resistance of the material from which it is made. A diode was recently made to oscillate at 10,000 mc. However, for known materials, the calculated maximum frequency of oscillation is 20,000 to 30,000 mc.

Now, how do we use the tunnel diode in a circuit? The current-voltage characteristic described above and shown in Fig. 1 is the key. Since the slope at any point of this curve is the resistance of the diode, this property of the diode may be conveniently determined from it. For example, the resistance at point D in Fig. 1 is $\frac{0.115}{-.00011} = -1045$ ohms.

Notice again that between A and B the diode is a negative resistance, that is, the current decreases with increase in voltage. At points A and B, however, the resistance is very high. We can see this on the curve itself. In the vicinity of A and B there is little or no change in current with changes in voltage.

The locations of points A and B of the curve are set mainly by the semiconductive material from which the tunnel diode is made. For germanium, the voltage at A is typically about .05 volt and at B 0.3. For silicon, on the other hand, the voltages are .07 and 0.4, respectively. Other materials have somewhat different values. However, all are in the forward voltage range of less than 1 volt.

Properties

To understand how to use the tunnel diode in various circuit arrangements,

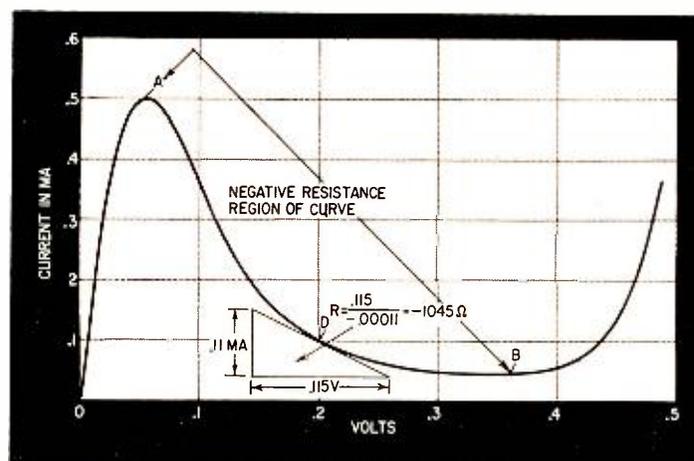


Fig. 1—Typical germanium tunnel-diode characteristic.

*General Electric Research Laboratory, Schenectady, N.Y.

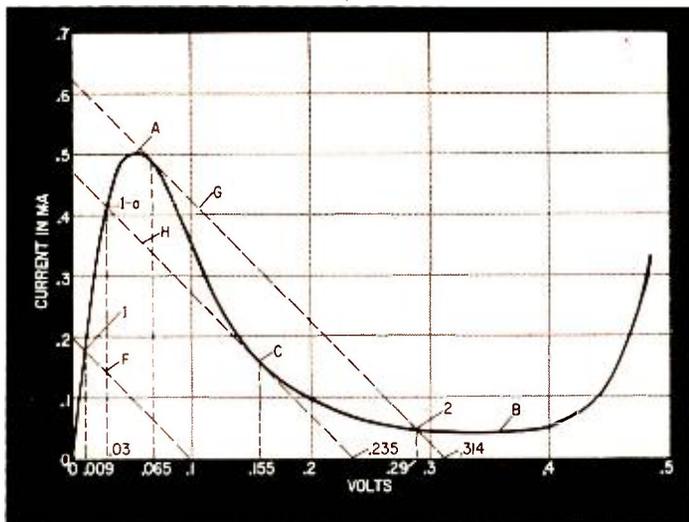


Fig. 2—Tunnel-diode characteristic with load lines for 500-ohm resistor in circuit of Fig. 3.

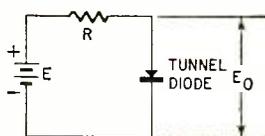


Fig. 3—Basic tunnel-diode circuit.


it will be useful to first explore some of its electrical properties. It will be convenient, therefore, to refer to the simple series circuit arrangement of Fig. 3. Then, in conjunction with Fig. 2, we will analyze the operation of the tunnel diode.

A current-voltage characteristic of a typical tunnel diode is shown in Fig. 2. The current through it is shown with respect to the voltage E_0 across its terminals. Since the circuit of Fig. 3 is a simple series arrangement, the voltage E_0 at any time is equal to the battery voltage E minus the voltage drop in the resistance R . It would be very useful, therefore, also to know the current flowing in resistance R with respect to the voltage drop in it. Load line F in Fig. 2 shows just this relation and a very useful tool is available from it. The intersection of line F with the voltage axis shows the battery supply voltage E while its intersection with the diode characteristic curve shows the voltage E_0 .

Load line F may be used to represent the resistance R in the circuit of Fig. 3. While the slope of this line is negative and it appears at first that there is a decrease in current with increase in voltage, it must be remembered that the load line F does not show the current flowing in the resistance with respect to the voltage supplied, as is the case for the diode characteristic. Rather, it shows the current flowing with respect to the voltage drop in the resistance. For this reason, this negative slope is not to be confused with the negative-resistance region ($A-B$) of the diode characteristic.

The slope of load line F is determined by resistance R so that, having drawn a particular load line on the diode characteristic, one can easily find the resistance (R) necessary to establish it.

Fig. 4—Tunnel-diode characteristic and load lines of switching property.

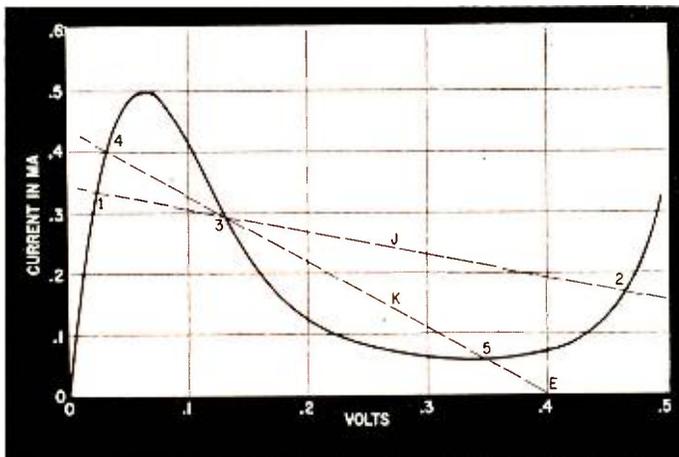

For example, to find the R necessary to get load line F in Fig. 1, the slope is found from the voltage and current values taken from the curve. Line F 's slope is equal to $\frac{0.1}{-0.0002} = -500$. The value of resistance R is $+500$ ohms since, as stated above, the negative slope does not concern us here.


For the condition shown, $E = 0.1$ volt, $E_0 = .009$ volt and the current is 0.18 ma. Therefore, with the above values, the point of operation of the diode (for the circuit of Fig. 3), will be as shown at 1 in Fig. 2. Although the slope of this load line is fixed by the resistance R in the circuit of Fig. 3, a change in the battery supply voltage will change its location with respect to the current-voltage characteristic.

Now, let us increase the battery supply voltage. As this is done the load line moves up along the branch 0-A. When the intersection (or E_0) reaches a point near A , as shown by the load line G , the intersection (E_0) jumps almost instantly to the point 2 between B and C . Point 2 represents

the new value of voltage E_0 .

If now we decrease the battery supply voltage E , the load line and its intersection will move toward the point C . Here it switches suddenly to the point 1-a on load line H and the lower value of voltage E_0 . Notice that the slope of the load line remains the same, since resistor R was fixed at 500 ohms and only the position of the line along the voltage axis changes with change in battery supply voltage.

Load lines G and H show the battery supply voltages as 0.314 and 0.235 at the respective switching points. This shows that, as the battery voltage E was increased from zero, E_0 increased to .065 volt and then very suddenly switched to 0.29 volt. This is an increase in voltage across the diode (E_0) of 0.225 volt. Reducing the battery voltage to 0.235 volt then caused E_0 to switch suddenly from a value of 0.155 to .03 volt. This is a decrease in voltage across the diode terminals of 0.125 volt. Thus, we see that near the switching points A and C a very small change in the battery voltage produced a relatively large voltage change across the diode.

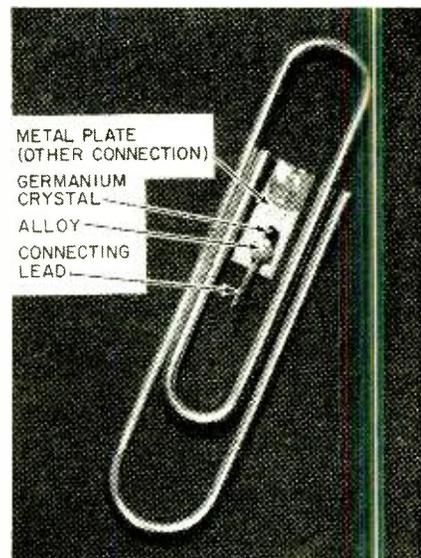

Laboratory style tunnel diode (original prototype). Semiconductor bodies are alloy and germanium crystal.

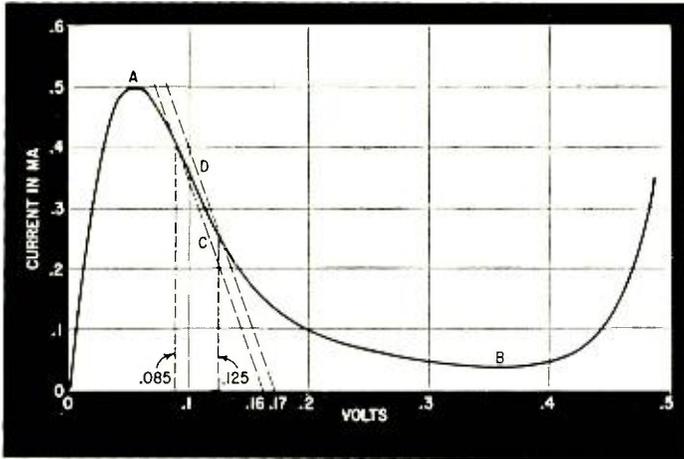


Fig. 5—Characteristic and load lines illustrating amplifying property.


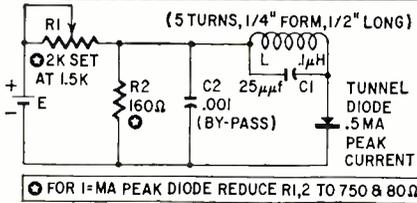


Fig. 6—Tunnel-diode oscillator circuit. Values given are for 100-mc operation. Unit may be frequency-modulated by 2,000-ohm headphone across R2.

Fig. 7—Characteristics and load lines illustrating oscillator operation.

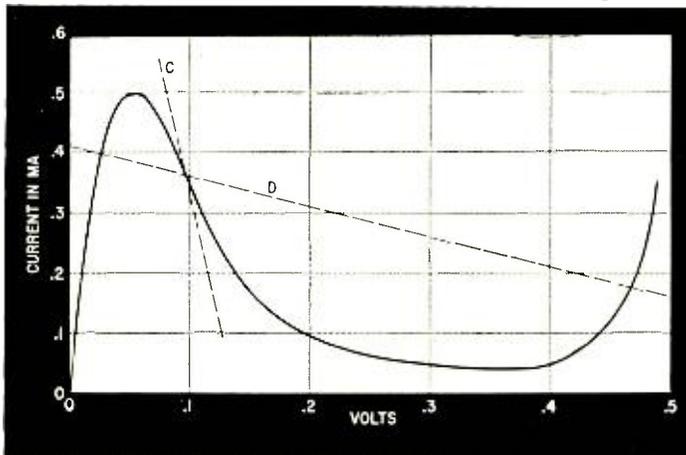

This property of the tunnel diode indicates one area of its usefulness.

Switching

Load line J in Fig. 4 (using the circuit of Fig. 3) represents a value of resistance much higher than the negative resistance of the diode. Notice that this load line intersects the characteristic in both positive resistance regions. Thus there are two stable operating points for a single battery voltage E. The voltage across the diode can be either that corresponding to point 1 or that corresponding to point 2.

To show that only points 1 and 2 are stable, look at Fig. 4 and load line J. Now imagine for a moment that the current and voltage have values corresponding to point 3. If, for any reason whatsoever (motion of electrons, heat or anything else), there is a very small increase in the current, then by looking at the characteristic curve we can see that there must be a decrease in the voltage across the diode.

A look at the circuit shows us that, if this happens, there is more voltage available to send current through the resistance which causes a further decrease in the voltage across the diode.

This action continues until point 1 is reached. At point 1, however, if there is to be any further increase in the current, there must also be an increase in the voltage across the diode since this is a positive resistance region. The only way the voltage across the diode can increase, of course, is for the voltage drop in resistance R to decrease. And this is possible only if the current becomes smaller. The operating point then must remain at 1 and be stable there.

The same thing would happen with any small decrease in current from that at point 3 so that the point would be then stable only at 2. This shows us that it is possible to provide a circuit arrangement which can be quickly changed from one impedance condition to another. For example, when the diode operates at point 1, it is in its low-impedance state and a relatively large current may flow. When operating at point 2, it is in a higher-impedance state and the current is limited to a relatively low value.

Selecting a load line such as K in Fig. 4 with its corresponding battery voltage E will indicate how this change may be made more significant. For

example, the current at point 4 on load line K for a germanium diode of about 0.5-ma peak current is 0.3 ma and the slope indicates an impedance of about 150 ohms. However, the current at point 5 is .055 ma and the slope indicates a very high impedance. Thus, the diode can be employed to switch impedances, currents or voltages if desired.

To use the tunnel diode as an amplifier or an oscillator, we must prevent it from switching. When we look at the diode characteristic curve we realize that, for this to be done, the value of resistor R must be less than the negative resistance of the diode. That is, the load line established by resistance R must have a steeper (more vertical) slope than the slope of the negative-resistance region between A-B (Fig. 1).

Such a load line is shown as C in Fig. 5. It always has only one intersection with the diode characteristic, making it possible to have an average bias in the negative-resistance region. The slope of region A-B for a typical germanium tunnel diode having a peak current at point A of about 1 ma is about -100. Hence its negative resistance will be 100 ohms.

If now we choose a tunnel diode with a junction area 10 times as large (so that the peak current is 10 ma), we find that the slope of the region A-B is steeper and the negative resistance is reduced to only 10 ohms. From this we can see that, as the diode's peak current increases, resistance R must decrease to prevent switching.

Amplification

Now how can the tunnel diode amplify? Refer to Fig. 3 again and assume that the diode is biased somewhere between the points A and B and has a load line such as shown at C on the characteristic of Fig. 5 so that it looks like a negative resistance. This negative resistance is indicated as (-R_o). Then:

$$(1) e_o = \frac{e(-R_o)}{R + (-R_o)}$$

$$\text{or gain} = \frac{e_o}{e} = \frac{(-R_o)}{R + (-R_o)}$$

where e is a small ac voltage in series with the battery and e_o is the ac voltage across the tunnel diode.

From equation (1) we see that the gain is 1 when R = 0 and increases to a very large value as R approaches (-R_o). This is shown graphically in Fig. 5. Lines C and D correspond to a resistance R of 150 ohms and battery voltages of 0.16 and 0.17 volts, or a change of .01 volt. At the same time we see that the voltage across the tunnel diode is .085 and 0.125 volt, respectively, or a change of .04 volt.

Therefore, the gain = $\frac{.04}{.01} = 4$. We also see that, as the slopes of the lines C and D approach that of region A-B of the diode characteristic, the gain increases.


Now let us consider the circuit of

ELECTRONICS GOES DOWN TO THE SEA (in small boats)

By NEWELL GARDEN*

Fig. 6. This arrangement can function as an amplifier or an oscillator, depending on the resonant impedance of the L-C circuit. Assume first that R_1 is adjusted so that the diode has a negative resistance, $-R_1$, and that R_2 is smaller than R_1 , so that we will prevent switching. If the resonant impedance of the L-C circuit is made greater than R_2 , then the circuit will oscillate. If, on the other hand, the resonant impedance is less than R_2 , the circuit will amplify. Fig. 7 shows the diode characteristic with the dc load line C established by resistances R_1 and R_2 and the ac load line D due to the resonant impedance of the L-C circuit in order for the circuit to function as an oscillator.

An important thing in regard to this is that the amplitude of the oscillation will build up until the average negative resistance of the diode just equals the positive resistance of the circuit at the operating frequency. For our purposes, it is sufficient to know only that this means that the diode still has a negative resistance while it is oscillating. We can make further use of this by adding another parallel-tuned circuit, tuned to

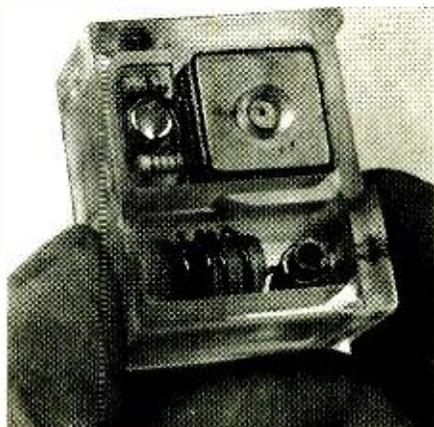

An FM transmitter built around a tunnel diode. The microphone is in the upper right corner and the battery is covered by it. The tunnel diode is to the left of the mike.

a different frequency, in series with the oscillator tank. This circuit "sees" a negative resistance. If its resonant impedance is slightly less than the impedance of the oscillator tank, it will amplify at this new frequency. We can add still another tuned circuit and use it as an amplifier also by following the same procedure. As an example, we have had a circuit operating, using a single tunnel diode, that was an rf amplifier (100 mc), an oscillator (110 mc) and a mixer and if amplifier (10 mc)!

A few of the successful applications of the tunnel diode are as quartz-crystal controlled oscillators, utilizing the series or parallel resonance of the crystal; frequency-modulated oscillators; regenerative frequency dividers; counters; logic elements; amplifiers and combination oscillator-amplifiers. The list is growing daily. END

THE outboard motor has made it possible for millions of Americans to find new recreation opportunities on the nation's waterways and oceans. Small, transistorized electronic navigation aids, either self-powered or operated with insignificant drain from the boat's 12-volt power mains, have given these boat owners new tools for enjoyment and protection.

Like the outboard motor, electronic depth sounders and radiotelephones are becoming common sights on boats in all parts of the country. Commenting on their growth in popularity, Capt. Joseph J. O'Connell of Fall River, Mass., one of the largest boat dealers in the country, notes that several years ago the prospective buyers used to ask if they really needed a depth sounder or a radiotelephone; now they raise an eyebrow if the boat they're looking at isn't electronic-equipped.

Although depth sounders have been around since the Fathometer was invented in 1924, they have been mostly styled and priced for commercial craft or large, expensive yachts.

The introduction of transistors and higher frequencies which made possible smaller components and equipment size has opened up an entirely new market for electronic depth sounders. Today more than 20 companies offer equipment specially made for the small-boat owner.

With a depth sounder, the boat owner can find a new measure of enjoyment in a fishing trip. The electronic lead line tells him accurately and continuously just how deep the water is—correct to the nearest foot. He gets a bonus in that the character of the flash on a flashing light unit or the trace on a recording unit can give him a good indication of the bottom characteristics. Knowing whether it is sand, mud or rock and just where the dropoffs and tables are is half the battle in game fishing. Commercial fishermen have used deep-water depth sounders for years.

Aside from fishing, the electronic depth sounder helps the boatman navigate in unmarked waters as well as known waters. He can determine his position by noting the depth of water under his boat and combining this information with his bearing from a light-house or known point ashore.

Radios, which according to Captain O'Connell, are specified more frequently by women than men, give the boatman the convenience of quick communication with the Coast Guard in case of emer-

gency. Although this safety tie-in is probably the real advantage of radiotelephone, the boatman can also use his radio to call the marine operator of the telephone company who can connect him with any shoreside phone. To the doctor or business executive who must be reachable for consultation, this means freedom to enjoy boating while maintaining his responsibilities.

Radio direction finders are an added convenience and safety factor for the boatman who ventures offshore or out onto the Great Lakes where night or fog might make navigation difficult. With a direction finder he can take a radio bearing on a lighthouse or light-ship to find his position or he can home on the signal of a lighthouse, aviation beacon or even the signal of a radio station near his home port.

Electronic gasoline-fume detectors are adding a safety margin to operators of inboard gasoline-engined boats. Gas fumes are heavier than air and, if there is even a small leak in the system or an overflow while fueling, the fumes settle in the bilges and engine compartment, from which they must be exhausted immediately and before the engine is started. The gas detector electronically sniffs the air in the bilges. If fumes are present, a platinum wire in the detector grows warm and an infrared cell triggers an alarm.


The newest electronic safety aid scaled down for small-boat use is radar, which has now been packaged in just two units. A transmitter and antenna unit is located on the cabin top or mast, and an indicator-receiver is installed in the wheelhouse. Using a 7-inch cathode-ray tube for an indicator, the new small-boat radars have good definition for navigation and collision prevention as they sweep the horizon for 12 miles. This month's cover shows how a Raytheon radar system looks in a small cabin cruiser. The new small depth sounder is also visible.

The low-cost radars for small boats take into account the shortage of power found in most pleasure craft. They can be operated from 12-, 24-, 32-, 110- or 220-volt lines. (Most of the earlier units required 110 or 220 volts.)

With all this electronic equipment available to boatmen and the boat owner adding more each year (20% more in fact), there are many new opportunities for professional electronic servicing in pleasure-boating centers to install electronic equipment and maintain it at its designed efficiency. END

*Raytheon Co., Waltham, Mass.

UNDERWATER METAL DETECTOR

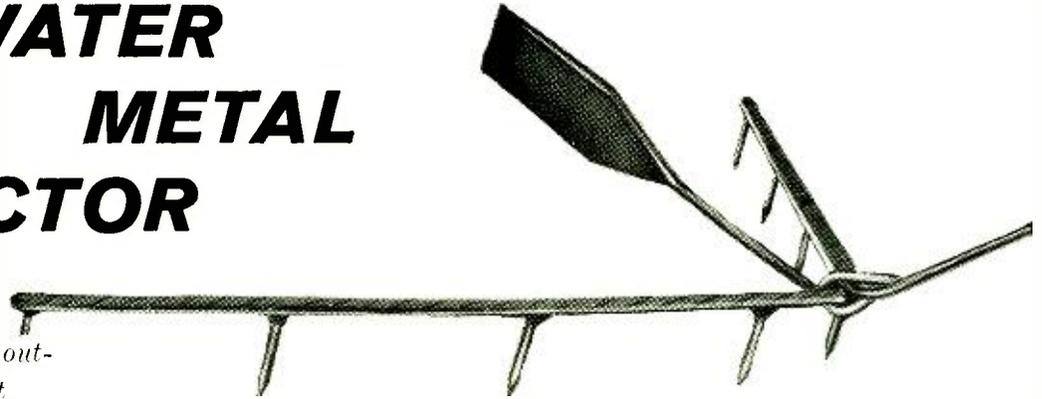

Now you can locate that out-board or anchor you lost

By KENNETH RICHARDSON

FOR centuries man's imagination has been stimulated—and his urge for sudden wealth aroused, by tales of buried and hidden treasure and its discovery. From sunken Spanish or English treasure fleets of the 16th and 17th centuries to gold-carrying ships sunk in World War II, there are hundreds of authentic or semi-authentic treasure troves, not counting the pirate hoards and other land-buried or hidden wealth.


With the invention of the Hughes induction balance in 1879, a practical means of searching for such buried treasure was introduced for the first time and Hughes balance devices are still in use. Since 1929, improved methods for locating buried treasure have been available. None of these is as well suited for locating metal underwater as the comparatively inexpensive electric-bridge instrument shown in the photo. It contains a battery, transformer, a sensitive meter and headphones. (The vibrator and associated parts were used in unsuccessful alternating-current experiments, and are not used in the instrument.)

Another photo shows the feeler, made of stainless steel, monel metal or copper, connected to the end of the insulated trailing cable.


The feeler may consist of either single or multiple elements, whichever the operator prefers, in the form of pointed spikes made of the selected metal. Each type of feeler has both advantages and disadvantages. The single-element feeler composed of merely a single spike will register the greatest percentage change of current flow on the meter upon contact with a metallic object. The multiple-element feeler with the spikes (arranged in the form of a

comb or rake, for example) will register proportionately less. The obvious advantage of the multiple feeler is that it covers a greater area. Personal experiment with feelers will assist the operator in determining the best type for his needs.

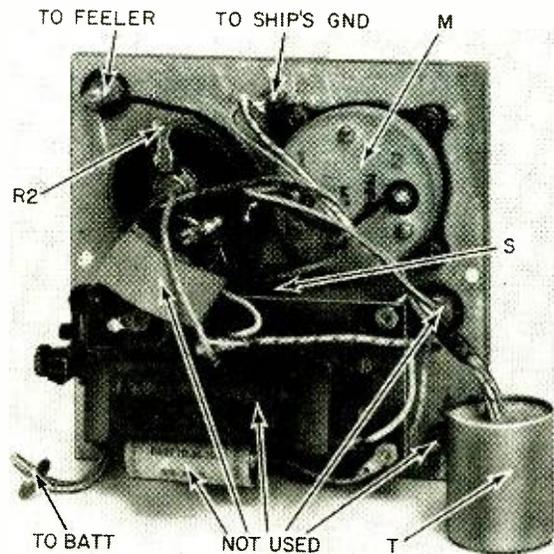In the photo of the multiple-element feeler, note that the two legs of the "rake" are angled to minimize snagging underwater. Also note the small vane, which acts as a rudder to assure that the feeler scours the bottom with its




Interior view of metal detector.

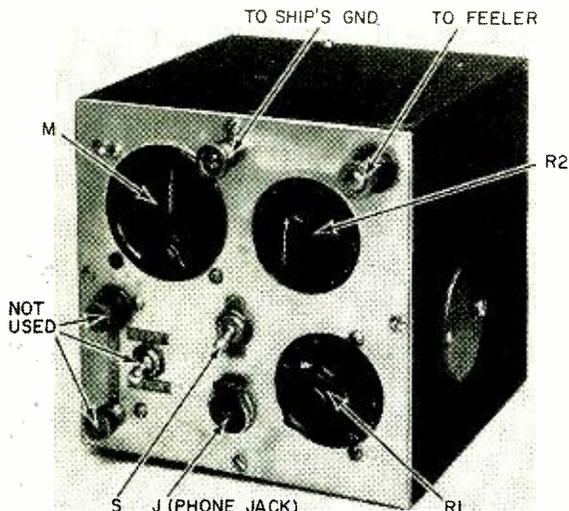

View of metal-detector control box.

spikes downward. A nylon rope is used to drag the feeler to relieve strain on the electric cable. As much of the feeler-frame surface as possible is insulated from contact with the water by tough plastic tubing and Vinylite tape. This will prevent loss of response due to leakage. Overall size may be anything from 2 feet to 6 or more, with the spikes spaced 6 to 12 inches apart.

To adjust the instrument, first drop the cable to the bottom while the boat is under way, to assure that the multiple feeler, if used, scours the bottom with its spikes downward. Next, ground the instrument to the ship's engines or to an overside seaplate. Turn on the switch and set R2 to its approximate center position. Then adjust R1 until the meter centers, readjusting R2 slightly if necessary to secure perfect centering.

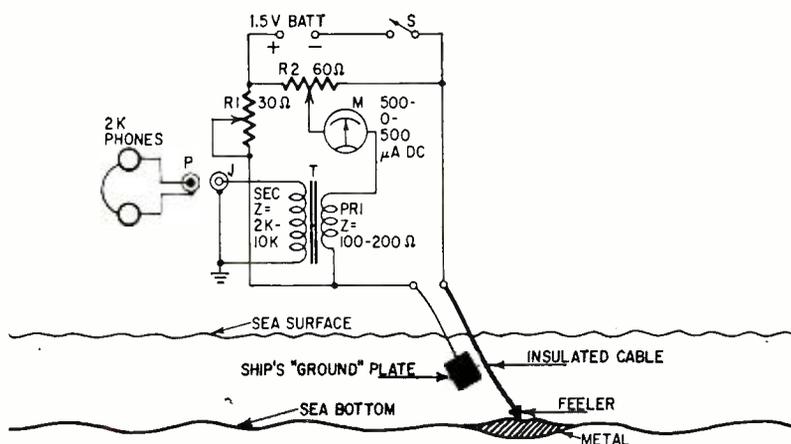

- R1—pot, 30 ohms
- R2—pot, 60 ohms
- M—zero-center meter, 500-0-500 μ a
- J—phone jack
- P—phone plug
- T—carbon mike to grid transformer, 100 or 200 to 2,000-10,000 ohms (Triad A-IX or equivalent)
- S—spst toggle
- Battery—1.5-volt cell (the larger the cell, the longer the battery life)
- Headphones, 2,000 ohms
- Battery holder
- Terminals for feeler and ground connections
- Case
- Feeler (see text)

Schematic of metal detector. If desired, an external shunt resistor may be used (15 to 30 ohms across R1) for salt-water use (since salt water has a lower resistance than fresh water, R1 should have a lower resistance).

In exploring any area, the operator maneuvers his boat back and forth, and the feeler sounds for metal along the sea bottom. As the feeler touches the surface of any metallic object, the meter reading will change, and a scraping sound will be heard in the headphones.

In areas of rocky bottom where the trailing method is more difficult, a weighted single spike is effective when repeatedly dropped vertically at short intervals as the boat maneuvers very slowly. These methods are suitable for locating sunken outboard motors and anchors, hundreds of which are lost annually, and also other metallic objects of value. Hulks of old wrecks containing valuable items repose in many of our bays, lakes and coastal areas. During his searching, the operator should be prepared to drop an

anchored buoy immediately on the site of any strike, because of the ever changing currents and winds. We will not go into a discussion of actual salvaging operations, which may range all the way from simple skin diving in clear water to the elaborate expeditions required in turbulent and muddy areas.

The approximate locations of a vast number of wrecks are actually known, and information can be obtained by writing to the United States Coast and Geodetic Survey, Washington 25, D. C. Numerous books on the subject are also available.

An active summer is assured the seeker of hidden underwater treasure, and the United States Government will permit him to retain all finds, after taxes. END

ROUNDWORD PUZZLE

By MICHAEL L. NAHRWOLD


ARE you tired of the old across-and-down type crossword puzzle? Well, then, here is the thing for you—a *roundword* puzzle. Simply start at No. 1 and print the words on the outside squares of the puzzle, always going in a clockwise direction. The first letter of each word is always the last letter of the word preceding it. The words on the lower half of the puzzle will read backward and the words on the left half will read from bottom to top.

For example, the answer to the first definition must be a 3-letter word that represents $\times 1,000,000$. Obviously, the correct answer is MEG and is placed in the first three boxes across the top of the puzzle—the M in the box numbered 1 and the G ending up in the box numbered 2. For our second answer we need a 7-letter word that starts with G and is a unit of magnetomotive force. GILBERT is such a word, but is it correct? As a check, is its last letter (T), which appears in the box numbered 3, the first letter of a 10-letter word that is the definition of a semiconductor? Try your luck and knowledge.

Answers on page 115.

1. $\times 1,000,000$ (prefix)
2. Unit of magnetomotive force
3. A semiconductor
4. Feedback
5. Narrow-band frequency modulation (abbreviation)
6. .000,001 ampere
7. Section of a beam antenna

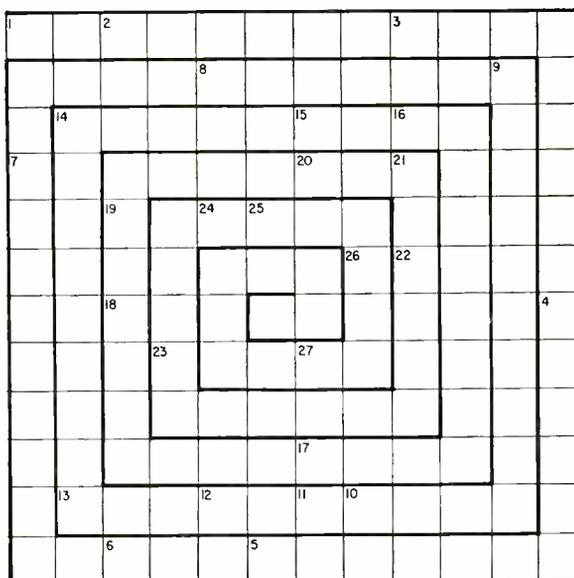8. 4 element tube
9. Type of tweeter
10. Code (abbreviation)
11. Radio station run by the National Bureau of Standards
12. Unit of electromotive force or potential difference
13. Grid-controlled rectifier
14. Lowest class ham ticket
15. Electron coupled oscillator (abbreviation)
16. Test instrument incorporating CRT
17. Flow of electrons from tube filament or cathode
18. Net control station (abbreviation)
19. Hi-fi using 2 channels
20. Unit of resistance
21. Unit of conductance
22. First stage of a CW transmitter
23. Electromagnetic switch
24. Unmarried lady amateur (slang abbreviation)
25. Antenna used in radio direction finders
26. Male connector
27. Type of diode



Why we want them, what they do, and how they work


AIR IONIZERS

By HAROLD B. McKAY

At one time, air conditioning meant filtering, cooling, dehydrating and circulating the air in a room. Placing the correct electrical charge on the air molecules must now be added to the list. The electronic repairman of the future may have to troubleshoot with the aid of sensitive instruments like the electrometer, or he may have to build an electroSCOPE to find out if an air conditioner is really "conditioning" the air.

Recent discoveries concerning the effect electrically charged air has upon animals and humans show that negatively charged air aids good health. Why ionized air affects humans and animals has been a matter of extensive study by doctors and other researchers.

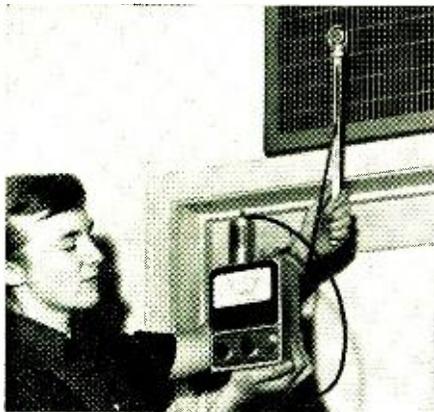Recently, the subject has been clarified by the work of two scientists, Albert Krueger and Richard Smith of the Department of Bacteriology, University of California. They conducted experiments in which sections of the




Electrometer and probe can be used to determine if an air conditioner is sending ionized air into a room.

windpipe were taken from rabbits, and the effects of the charged air noted.

The lining of the nasal passages, the trachea and bronchial tubes is surfaced with ciliary cells. These cells have tiny hairlike growths which constantly wave or beat. This action propels fluid upward toward the nose, and is nature's way of ridding our lungs of dust, bacteria, pollens and other irritants.

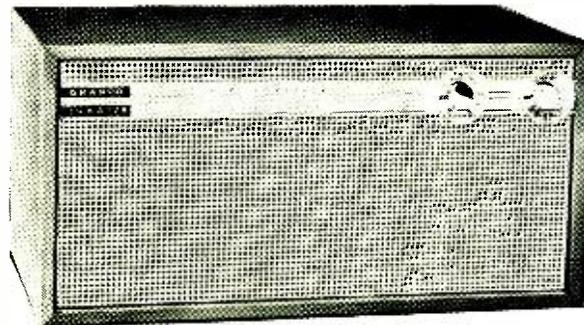The experiments showed that negative air causes the fluid of these cells to become less viscous, the cilia to beat faster and thus push particles away faster. Positive air caused the cilia to slow down, the fluid to dry and the specimens to die more quickly.



The Granco Ionator, a portable health appliance a foot and a half long by about ten inches high and deep that combines mechanical filtering, electrostatic precipitation and negative ionization. Particles as small as one micron in diameter are removed from the air sucked in, and the purified air is charged with negative ions as it is returned into the room.

Some manufacturers have been quick to note these developments, and already electric heaters and air conditioners which embody ionization equipment are on the market.

Normally, when air is ionized, both positive and negative ions are generated, but circumstances may alter the balance between the polarities. The ionization of the atmosphere is constantly changing in polarity.

Ions from heaters

The Wesix Electric Heater Co. became interested when the firm's president found that electric heaters could ionize air. He learned how electric heaters could be modified so they would take advantage of this and contribute a desirable surplus of negative ions to the air.

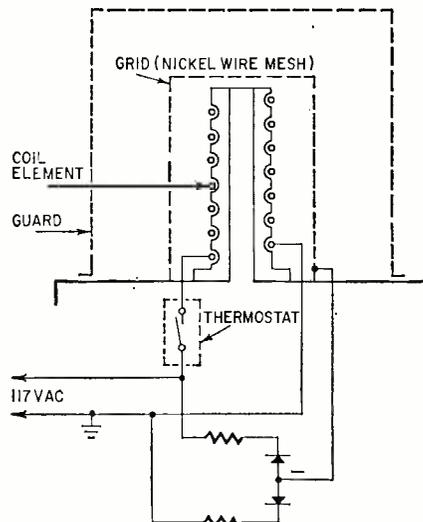


Fig. 1—Arrangement of an electric heater modified to deliver negatively ionized air.

This was done by placing a nickel wire-mesh grid around the ceramic tube on which the heating element is wound (Fig. 1). Under the heater a small rectifier is connected to the ac line. The negative side of the rectifier is connected to the grid which surrounds the heating element.

Operation is like that of a vacuum tube. The heater element, when it



This ionizer resembles a microphone. It is made by the Wesix Electric Heater Co.


reaches incandescence, generates both positive and negative ions. The positive ions are attracted to the negative grid and neutralized. The negative ions are repelled to the heater. When the ac goes through zero, the negative charge on the grid disappears. At this moment, both positive and negative ions pass through the grid. When the grid is again energized, the positive ions which got through are drawn back and neu-

ELECTRONIC CAMERA TAKES MOVIES

A NEW type of camera that is based on a combination of television and electronic printing techniques is now in the experimental stage. Developed by RCA scientists at developmental laboratories in Princeton, N. J., the electronic camera records its pictures on a strip of specially prepared reusable plastic tape.

A conventional lens system focuses the scene to be recorded on a tape made up of layers of conducting, photo-sensitive and insulating materials on a plastic base (see diagram). Before being exposed, the tape is given a uniform electric charge by an electron gun. When a picture is taken (one frame), the charge is driven from the tape according to the intensity of light in the scene. The result is an electrical charge pattern that corresponds to the light pattern of the image.

To view the pictures, the exposed tape is passed in front of a scanning beam from an electron gun which reads the electrical charge pattern to produce television type signals for transmission or recording on magnetic video tape. (The electrical charge will remain on the camera tape for about two weeks and can be scanned several times.) Final playback is on a TV screen. In the experimental version, the entire mechanism is enclosed in a vacuum.

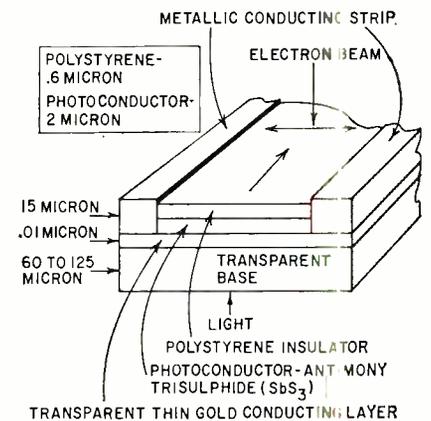


As used in space satellites (the original purpose of the device), the information would be transmitted to earth where it would be recorded on magnetic video tape. For home movies—a remote possibility for the future—the exposed film would be placed in a playback device that would record the signals on magnetic tape. Then through a video tape playback, the pictures would be viewed on a standard TV receiver. END

is connected to the plate electrode.

In addition to these devices, another manufacturer, Philco, now markets an air-conditioner which embodies an ion control device.

It consists of a power supply which

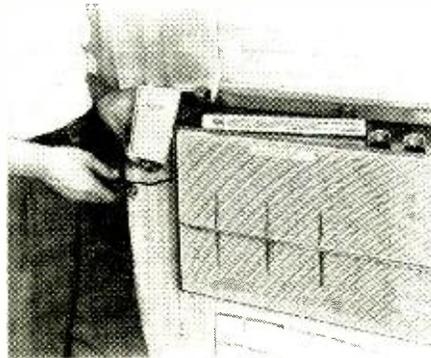

Philco's Ionitron being attached to an air conditioner.

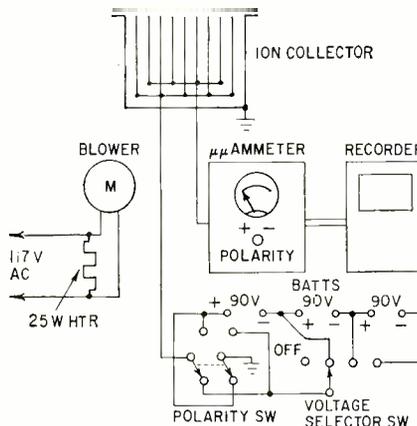


Fig. 4—Setup for measuring ion content and polarity of air.

delivers 4,000 volts dc to an ionizer tube located in the air stream (Fig. 3). The voltage is great enough to ionize the air, but not enough to form ozone or nitrogen oxides.

The polarity and count of atmospheric ions can be measured by apparatus which is fundamentally simple, but nevertheless quite delicate and expensive. All that is required is a set of plates, like an air capacitor, and a micromicroammeter. In principle, a charge from a battery is placed on one set of the plates. The ions in the air carry some of this charge to the other plates, from which it is drawn off through the ammeter and measured (Fig. 4).

An electrometer can check ions emerging from a suspected source. It is a sensitive vacuum-tube voltmeter type unit which reads in micromicroamperes when used with a shunt. It can be connected to a small probe consisting of a coin-sized disk surrounded by a ring (see photo on preceding page).

These are some of the units now on the market. More will be made and within a short time many more manufacturers will be turning out ionizers—another promising new field for the electronic technician. END

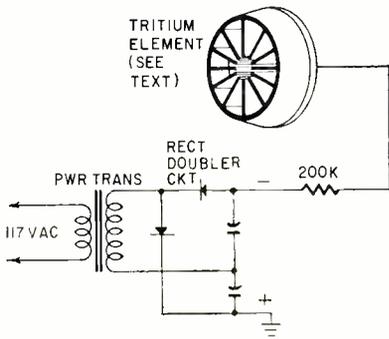


Fig. 2—Circuit for negative-ion generators.

trialized. The negative ions which are outside are repelled by the grid and pushed into the room. The ceramic tube which holds the heater and grid is slightly conductive when hot, and lets the grid charge leak off between ac cycles.

Heatless ionizer

You may not always want the heat on to get ions, so a gadget that looks like a desk microphone was developed for such cases (see photo). It consists of a small plastic disk containing a piece of titanium foil which has been impregnated with heavy hydrogen, tritium (H_3). This is a radioactive material which emits beta particles of .015 mev. It will ionize air, but the particles travel only a short distance, so there is no danger from radioactivity.

Behind the foil a flat plate electrode suppresses the positive ions and repels the negative ions into the room. The base of the desk unit contains a transformer and a voltage-doubling rectifier unit, with a circuit resembling that used in radio receivers (Fig. 2). About 900 volts of negative dc is obtained and this

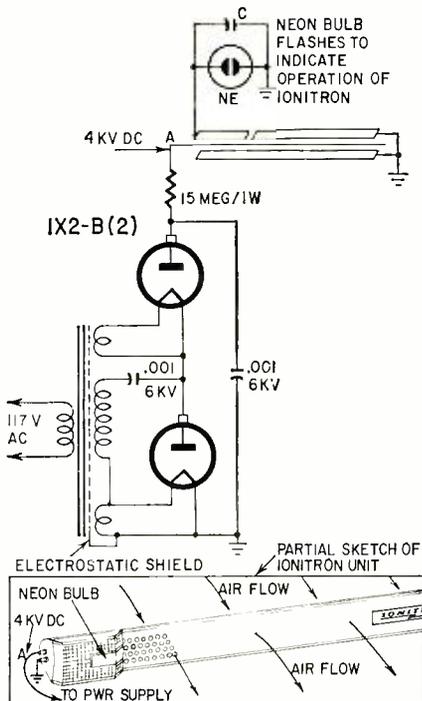


Fig. 3—Circuit of Philco's Ionitron.



PRINCIPLES OF MODERN RADAR

Part II—Pulse-Doppler systems eliminate many of the disadvantages of other radar systems in detecting and indicating moving targets

By JORDAN McQUAY

THE two basic kinds of radar discussed in the first part of this series were the pulse-modulated or PM and the frequency-modulated or FM. Although both provide accurate range and azimuth data, they depend on targets of fairly large size which do not move rapidly with respect to the range.

For example, PM radar is excellent for long-range detection and tracking of missiles and satellites in outer space. Although such targets may actually be traveling at high speeds, their rate of movement is not too consequential when compared to range distances of thousands of miles.

At very short ranges, ground-based PM and FM radar is ineffective in locating targets on or just above the ground—particularly when they are moving over the earth's surface.

A long-persistence PPI (*plan position indicator*) scope provides, with successive sweeps of the radar antenna, a series of repeating echoes from moving as well as fixed targets. Close scrutiny of slight changes in the position of these echoes on the scope screen gives some indication of movements of any target. But there is no highly accurate indication of moving targets on the PPI scope of a PM radar. It is even more difficult to see target echoes when they are submerged or partially covered up by echoes from fixed objects on the terrain.

This important requirement is met by a third kind of radar. Combining certain features of both the PM and FM, it is known as pulse-Doppler or PD radar because it uses the Doppler effect effectively.

The Doppler effect was named after the man who discovered it. It is simply an apparent change of frequency of any received signal by a moving object (the object can be stationary and the

signal source moving). A common example of this is the change in pitch of a whistle or bell on a train as it goes past a listener. The passengers on the train also experience this effect when listening to gate-crossing bells and such. The effect is not limited to sound or radio (or radar) signals: the light from a moving star seems to change in frequency (color). The light shifts toward the red region of the spectrum when the star recedes from us and toward the violet region when it approaches us.

Radar signals from a moving target are doubly affected by this effect. The target receives a signal that is changed in frequency and then reflects (or effectively retransmits) it to the original source. Since the target is moving with respect to the source, the frequency of the signal is changed again.

A PD radar can detect and locate all objects and targets within range—it sorts out *moving* targets with special data-processing circuitry and displays these *and only these* echoes on an indicator. A PD radar is sometimes called an MTI or *moving-target indicator*.

A single and important advantage of PD radar is that it defines moving objects and targets clearly at greater ranges—regardless of ground clutter and echoes from fixed objects or targets—than is possible with any other kind of radar.

Although developed primarily for military surveillance, PD radar will ultimately find commercial use for similar specialized applications.

Radar components

A PD radar (see block diagram) is similar in many ways to the PM type. The principal difference is in the receiving circuit.

At an operating frequency of several

hundred or sometimes thousand megacycles, the radar transmitter sends out *pulses* of microwave energy. These are directed by the antenna system toward the area being searched or scanned.

The number of such pulses per second—usually about 5,000—is called the prf (*pulse recurrence frequency*). The duration of each rf pulse is extremely short—less than 1 μ sec—to allow time for reflected echoes from objects or targets to be received by the PD radar.

The prf and the pulse duration are both controlled by the *timer*. It also provides trigger voltages to synchronize operation of the transmitter, receiver, indicator and other components of the radar system.

A *duplexer*—or TR switch—permits use of a single antenna for both transmitting and receiving.

Objects and targets within range of the radar and reached by the very narrow rf beam from the antenna will reflect very weak echoes—usually less than 1 μ v in strength. These reflected echoes are picked up by the antenna and pass directly through the duplexer to the microwave receiver, which is broadly tuned to the same operating frequency as the radar transmitter.

In the receiver, echo signals are mixed with a local-oscillator signal to produce an if of 30 mc (sometimes 60 mc), which then passes through several stages of broad-band (if) amplification. Automatic circuits in the receiver provide for frequency control of the local oscillator and for gain control of the incoming echo signals.

At the same time, a *coherent oscillator*—actually a second local oscillator—is operating continuously at the if (30 mc or 60 mc). It produces if control signals that have a fixed phase relationship (or phase coherence) with the if echo signals.

Both signals—if control and echo—are applied to a phase detector. It combines them into video signals having a polarity determined by the phase difference between the control signals and the echo signals.

Echoes received from stationary objects and targets produce video signals (at the output of the phase detector) with a fixed polarity. Echoes from moving targets produce video signals that change in polarity at a frequency proportional to the rate of movement of the objects or targets.

To sort out and eliminate the video



US Army

Antenna of giant PM radar used to detect and track missiles and satellites.


signals of fixed polarity (from fixed targets), the output of the phase detector is applied to a *Doppler filter*. This discriminates against all video signals of fixed polarity, but passes all video signals that represent moving targets. The Doppler filter is a complicated device. Something like a bandpass filter, that is extremely sensitive to signals of fixed polarity.

After suitable amplification, the video output of the Doppler filter can be utilized or displayed in several ways.

The video signals can be used to modulate an audio amplifier which produces an audible tone whenever the PD radar detects a moving object or target. A headphone enables an operator to zero in on such targets, and thus provides data for manual plotting of range and azimuth. The frequency of the audio tone is about 30 cycles per second for each mile-per-hour motion of a target. The faster the movement, the higher the pitch of the audio tone.

The same video signals can be used to activate low-frequency voltmeters or other similar indicating devices. Or they can be fed to a frequency-indicating meter or graph calibrated in miles per hour (commonly used to detect speeding automobiles).

Some types of PD radar use a PPI

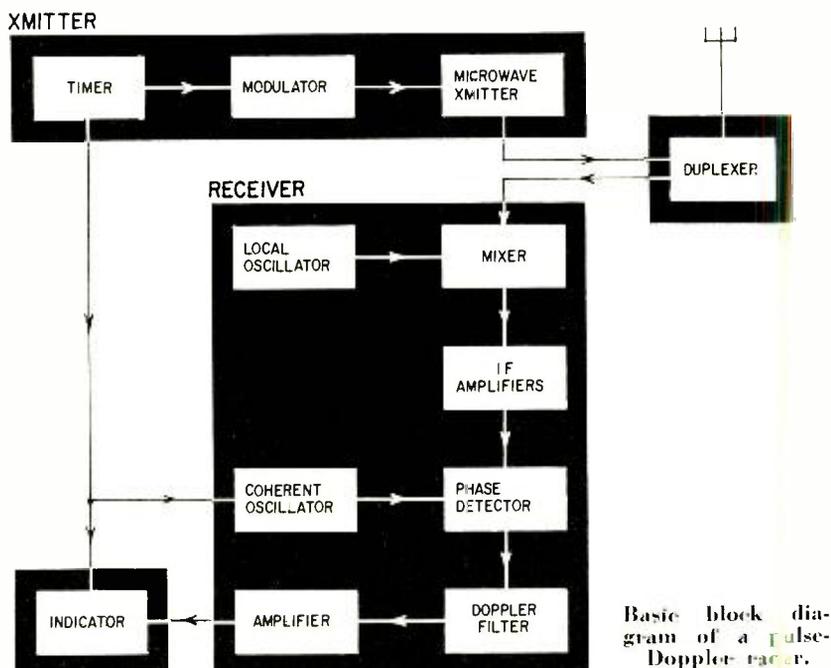

scope with a special intensifying circuit. Amplified video signals from the Doppler filter control a threshold detector. This, in turn, modulates or controls a low-voltage oscillator that intensifies a portion of the video signal in accordance with the video signal. Range and azimuth of each moving target are determined in the conventional manner for PPI scopes. But in this application, there are no interfering fixed echoes or ground clutter from fixed targets visible on the radar scope. Only echoes from moving targets

are visible on the scope face.

Other kinds of scopes may be used similarly, but require special locally controlled intensifying circuit.

Memory systems

Echo signals exhibiting Doppler-shift frequencies can be measured rapidly only with some type of memory system that accurately "remembers" the broadcast frequency of the transmitter and compares it quickly with the frequency of the echo signals.

The memory system just described



Hughes Aircraft

PPI scope (left) of long-range surveillance PM radar displays on approximate data on moving targets.

ELECTRONICS

is used for most ground-based PD radar where there is no appreciable change in frequency between successive signals. For this reason, it is called a *coherent* or "locked" system.

In the *noncoherent* system, a portion of the transmitted pulse power is stored electronically for comparison with echo signals. This comparison utilizes an echo signal reflected by a fairly large stationary target. Such an echo signal, which is not changing in frequency, is fed into a time-delay circuit prior to comparison with echo signals from moving objects and targets.

One example of a noncoherent PD radar is an airborne "side-looking" radar that scans downward, alternately, from each side of low-flying aircraft. Echo signals from stationary objects provide the reference required for frequency comparison. The radar provides a continuous picture map of the ground, about 30 miles in width, as the plane



US Army

Antenna system for medium-range military surveillance radar. Radiating element rotates beneath plastic housing.

flies along. For low-speed low-altitude aircraft, this provides an intimate view of all moving objects on the earth below it.

For comparable target reporting, PD radar, utilizing either type of memory system, is generally more effective than the PM or FM types.

The performance of PD radar is evaluated according to two parameters. One is the minimum strength of echo signal from a moving target that can be detected in the absence of any fixed objects. The second factor—called sub-clutter visibility—is the ratio of the maximum strength of echo signal from a fixed target to the minimum strength of echo signal obtained from a moving target. END

AUTOMATIC RECYCLING TIMER

By L. E. FANNON

SEVERAL articles have appeared describing transistor timers but all require discharging the charging capacitor with a manual reset switch to allow the timer to recycle. This timer was designed for automatic recycling through a relay network operation.

Using one transistor, it has a variety of applications in photography, portable industrial controls and airborne equipment.

Ruggedness, compactness and zero warmup time are the distinct advantages of this timer over vacuum tube units. While cold-cathode timers requiring no warmup time are common, they require a line-voltage source which is objectionable in portable and airborne equipment applications.

The timer's power requirements are met by a common 24-volt supply, making it especially adaptable to remote airborne switching operations. It can be miniaturized sufficiently for model control applications.

Circuit description


In the circuit (see diagram) when switch S is closed, capacitor C charges through R1 and R2 with R2 determining the desired time constant. Upon completion of the chargeup of C, current flows through R1, R2, R3 and the base-emitter paths, establishing the base bias. This results in a flow of collector current, closing the contacts of RY1 and connecting the supply voltage to the coil of RY2. This in turn momentarily connects the supply voltage to the controlled circuit. When the contacts of RY2 close, C is shorted and discharged, ending one cycle and starting another.

With values of R1, R2 and C as shown, time cycles ranging from 7 per second to 1 every 30 seconds are possible. The relay closure interval is not necessarily the R-C time constant of R2 and C, so actual measurement of the time is necessary. Resistor R3 holds base current to a minimum, aiding stability.

Total battery drain during the operation of both relays is 2.5 ma. Of course this will vary somewhat, depending on the sensitivity settings of the relays and the cycling time.

Because the coil of RY1 is in the transistor's output, the choice of collector voltage is influenced by that required for the relay's operation. Here the supply is 22.5 volts.

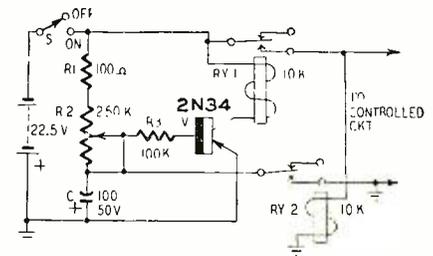A portable timer that needs no manual reset




R1—100 ohms, 1/2 watt
R2—pot, 250,000 ohms
R3—100,000 ohms, 1/2 watt
C—100 µf, 50 volts, electrolytic
RY1, 2—spst, 10,000 ohms
S—spst toggle
V—2N34

Battery—22.5 volts (Burgess XX15 or equivalent)
Chassis—approximately 2 x 4 x 5 inches
Terminal Strip—2 contacts

Circuit of the transistor timer.

Two 10,000-ohm spdt relays are used in this circuit. However, one dpdt relay could be used instead, with the second set of contacts serving the same purpose as RY2. This choice depends on the relay contact rating needed for carrying the controlled circuit current.

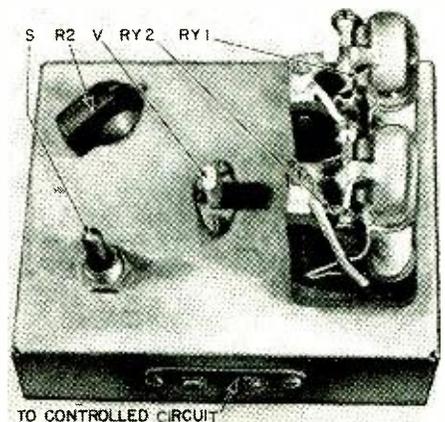The photo shows the relays and controls mounted on the chassis. The only controls required are the switch and time control. In this unit the time control is a 250,000-ohm potentiometer. If fixed, preset time intervals are required, a decade type switch with fixed resistors can be used to establish these settings in step series.



The portable recycling timer.

Although no effort was made to miniaturize this unit, it would be possible to decrease the size of the timer greatly by using a printed circuit and printed-circuit type components. Cost-wise, this is not practical unless space is at a premium. END

TROUBLESHOOTING

SWEEP

CIRCUITS

Faster and easier servicing with a low-priced instrument that substitutes vertical and horizontal oscillators.

By VAL SYKES*

HORIZONTAL sweep-circuit troubleshooting is still the "tough dog" of TV servicing.

With no raster visible, the non-technical user of a TV set will usually suspect the picture tube. However, a professional television technician can rapidly trace the trouble to the horizontal sweep circuits (if the trouble is there).

Most technicians attack horizontal troubles this way: First check the fuse and, if it is blown, replace it. (It is a good idea to replace the damper tube also). If the trouble is not in the damper circuit, the horizontal oscillator, discharge (if used), output and high- and low-voltage rectifier tubes are substituted. If no raster can be obtained by tube substitution, the trouble generally lies beneath the chassis.

At this point, the trouble must be tracked down to the defective stage before repairs can be made. Since any of the stages mentioned will prevent the appearance of a raster, it may not always be possible to pinpoint the trouble quickly. The Sencore Sweep Circuit Trouble Shooter was designed with such problems in mind.

The Trouble Shooter contains a stable 15,750-cycle sine-wave oscillator which uses half of a 12AU7-A dual triode. The oscillator stage is isolated from the TV set by the second half of the 12AU7-A, which reduces oscillator loading. A neon lamp on the front panel indicates that the oscillator in the Trouble Shooter is functioning correctly. The oscillator frequency depends on the L-C combination of T2 and C2 and stray capacitance (Fig. 1). Feedback to sustain oscillation is between the primary and secondary of the slug-tuned transformer, T2.

A sawtooth output signal (with a very rapid retrace period) whose amplitude is determined by R7 (the 50,000-ohm output control) is capacitively coupled to the output jack. A comparatively low-resistance control was selected to reduce variations in output signal amplitude due to the varying loads to which this unit is subjected. The output lead is safe to handle since it is isolated from B-plus by a .05- μ f capacitor (C6).

Oscillator substitution

To check the horizontal oscillator in

a TV set, apply the 15,750-cycle signal from the Trouble Shooter to the horizontal-output tube control grid (Fig. 2) and a raster will appear (if the set's oscillator is at fault). Working progressively backward toward the horizontal oscillator stage in the TV set will pinpoint the defective component. The Sweep Circuit Trouble Shooter should always be grounded to the TV chassis being checked. If the receiver's horizontal oscillator is normal and the trouble lies elsewhere, use of the substitute oscillator will produce no harmful effects.

Cathode-current check

The reason for measuring the cathode current of the horizontal output stage is to see if it is operating within its limits. An octal adapter socket (with test pins) is provided to make this test quick, simple and convenient. The test pins on the sides of the socket may be used for voltage measurements or for applying the oscillator output signal to the output tube's grid. The adapter automatically breaks the cathode circuit of the output tube. A three-position cathode selector switch, S1 (Fig. 1), selects the correct cathode pin for any horizontal tube used in present TV receivers. Selecting the wrong switch position will

not harm the Trouble Shooter or the TV set. The meter selector switch, S2, places a 0—3-ma meter (shunted by a 10-ohm resistor and .02- μ f bypass capacitor) in series with the cathode of the horizontal output tube, when it is in the cathode current position.

If the cathode current is higher than the average current for the particular tube (as indicated on the roll chart), a shorted coupling capacitor, grid resistor, horizontal output transformer or yoke may be the trouble. Lower than normal current is usually caused by bad screen components, an open output transformer or yoke. With the horizontal oscillator in the Trouble Shooter connected to the TV set and the cathode current reading high, trouble is definitely in the output section of the horizontal amplifier (if the coupling capacitor and grid resistors are good).

The cathode-current check can be used to make the proper adjustment on the horizontal linearity coil. With the Trouble Shooter set for cathode-current check, vary the setting of the linearity coil to the point where the cathode current dips. Linearity is best near the lowest cathode-current point.

Yoke substitution

If the trouble has not yet been isolated, the yoke should be checked with



Sencore SS105 Sweep-Circuit Trouble Shooter.

* Sencore design engineer.

TEST INSTRUMENTS

the deflection-yoke substitution coil (T3), a special slug-tuned coil designed to withstand high pulse voltages. The yoke substitution coil is connected in place of the suspected yoke through a thick lead (Fig. 3). This lead is connected to the top terminal of the tester. The bottom terminal of the tester must be connected to the TV chassis.

The inductance of the yoke substitution coil is adjustable between 6 and 40 millihenries with the slide knob on the front panel. This inductance range was selected because it covers prac-

tically all yokes in use. This approach to deflection-yoke troubleshooting is simple but effective. If a yoke is defective, the substitute yoke will produce a bright vertical line on the CRT and restore high voltage. The substitution-yoke inductance should be varied to obtain the above result. A vertical line is produced since only vertical deflection is applied to the TV yoke when making this check. The horizontal deflection component is applied to the substitute yoke coil, thereby producing no horizontal deflection on the TV screen. If a deflection yoke has a high-voltage short (under full load) between the vertical and horizontal coils of the yoke, the Trouble Shooter will isolate the coils and produce the vertical line, showing up the defective yoke.

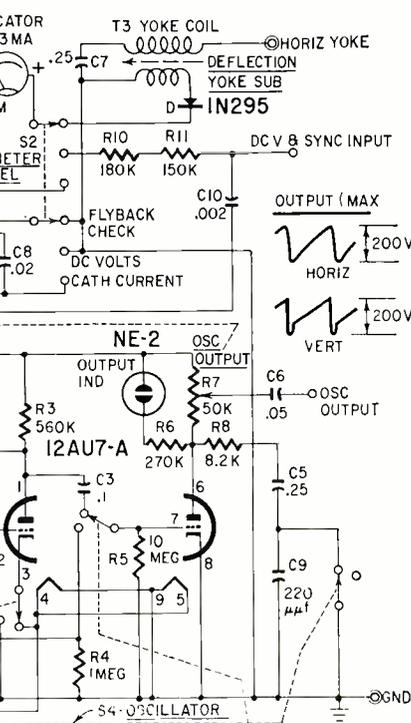


Fig. 1—Schematic of Trouble Shooter.

tically all yokes in use. This approach to deflection-yoke troubleshooting is simple but effective. If a yoke is defective, the substitute yoke will produce a bright vertical line on the CRT and restore high voltage. The substitution-yoke inductance should be varied to obtain the above result. A vertical line is produced since only vertical deflection is applied to the TV yoke when making this check. The horizontal deflection component is applied to the substitute yoke coil, thereby producing no horizontal deflection on the TV screen. If a deflection yoke has a high-voltage short (under full load) between the vertical and horizontal coils of the yoke, the Trouble Shooter will isolate the coils and produce the vertical line, showing up the defective yoke.

Voltage measurements

The sweep-circuit Trouble Shooter contains a voltmeter circuit intended for sweep-circuit voltage measurements. B-plus, screen-grid, bootstrap (B-plus boost) and cathode voltages can be measured with reasonable accuracy. Two heavy-duty multiplier re-

sistors totaling 330,000 ohms provide safe operation and indicate voltage correctly on the center scale of the meter. For this check, the meter is connected —by the meter-selector switch—through the multiplier resistors to the dc volts jack. Sweep-circuit voltages which should be measured and their approximate values are shown on the roll chart and in Fig. 4. B-plus at the damper stage should read within 10% of that at the low-voltage rectifier. Bootstrap voltage should be in excess of 100 volts over B-plus. If bootstrap volt-

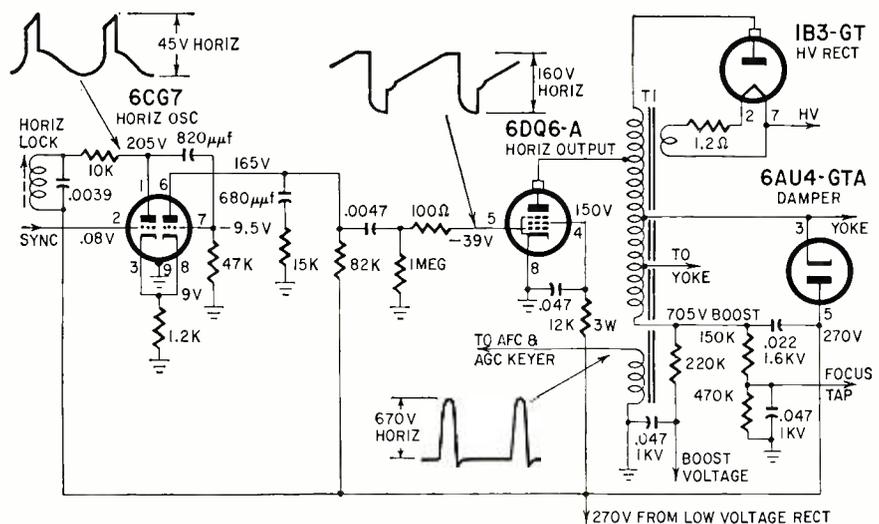


Fig. 4—Typical horizontal output stage showing voltages to be measured.

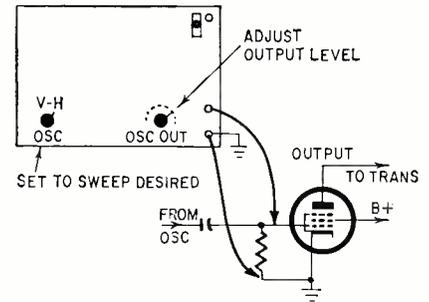


Fig. 2—Method of connecting tester to grid of output stage.

circuits fed by the bootstrap voltage temporarily and see if it returns to normal. This should be done before making the flyback check explained below. Nominal screen grid voltages are indicated on the roll chart for all horizontal amplifier tubes in use today. If screen voltage is too high, screen current may also be high, and the value of the screen resistor should be checked to prevent damage to the horizontal-output tube.

Flyback check

If the above substitutions and tests still have not isolated the trouble, a horizontal transformer output check should then be made with the Trouble Shooter. The meter-selector switch is set at the FLYBACK CHECK position and the substitute deflection yoke coil connected for this check (Fig. 5).

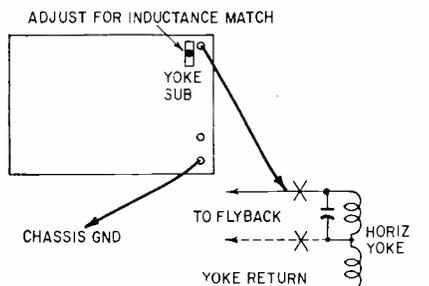


Fig. 3—Hot lead(s) to yoke are disconnected and the signal applied to the substitute yoke.

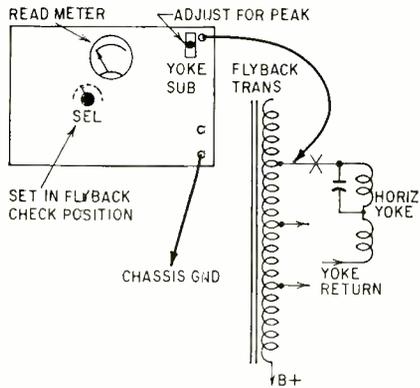


Fig. 5—Substitute yoke is connected and its inductance adjusted for maximum meter reading.

A small takeoff coil adjacent to the high-voltage yoke substitute coil picks up some of the energy from the larger coil, feeds it through a half-wave rectifier and then applies it to the meter. The amount of power fed to the yoke substitution coil from the horizontal transformer will be indicated on the flyback-check scale of the meter. Since the amount of power required to drive the yoke is dependent on the deflection angle being swept, the meter is calibrated in degrees of deflection.

It should indicate the deflection angle (or higher) of the set being checked

if the flyback is good. The yoke substitution coil is adjusted for a peak reading on the meter (if no peak can be obtained, the flyback probably has one or more shorted turns). If no reading can be obtained and the screen voltage, boost circuits and yoke are good, the flyback is bad.

Vertical substitution

An additional feature of this checker is a substitute vertical oscillator circuit. It is used in the TV set when only a thin horizontal line is seen on the CRT face or if sufficient height cannot be obtained. A thin horizontal line or insufficient height indicates trouble in the vertical oscillator or vertical output stage. The Trouble Shooter will isolate the trouble to the particular stage or component at fault.

The substitute vertical oscillator is connected to the vertical output tube grid in the same manner as the horizontal oscillator. The selector switch (S4) must be in the VERT position and the same output control is used. Height will be restored if the vertical oscillator in the TV set is inoperative. If there is no improvement, the trouble is in the output transformer, yoke or vertical output tube.

Remove the vertical output tube (or disconnect the plate lead). Connect the

output of the SS105 to the plate connection of the tube socket. If a picture approximately 2 inches high is visible on the screen (with oscillator output set at maximum), the output tube is bad. If there is still no height, apply the Trouble Shooter signal to the yoke. The appearance of a 1/2-inch-high picture shows the output transformer to be bad. No height indicates the yoke is defective.

The vertical oscillator circuit in the Trouble Shooter consists of the two sections of the 12AU7-A tube connected as an amplifier and clipper (Fig. 1). Therefore, in a sense, it is not an oscillator at all, but two amplifier-clipper and shaping stages making use of the 60-cycle line frequency for the required vertical signal. Because the output signal is locked to the line frequency, there will be no rolling (nor slipping) on the TV screen.

A novel feature of this unit is the roll chart indicating voltages, currents and pin numbering of all horizontal output stages used in present-day TV receivers. It will not become obsolete since any new tubes can be added to the chart.


The cathode-current check can also be used in balancing output stages in hi-fi amplifiers, a must for good performance of this equipment. END

AUDIO COMPARATOR


By J. E. PUGH, JR.

THIS simple, inexpensive instrument can be used to make rapid comparison tests on hi-fi tuners, phonographs, microphones, amplifiers, ac and dc voltage levels, the phasing of multi-speaker installations, or nearly any other use where it is desirable to compare levels or quality. It is useful in hi-fi sales and service and public address work. In addition, it can be used for switching between two or more turntables at dances or get-togethers.

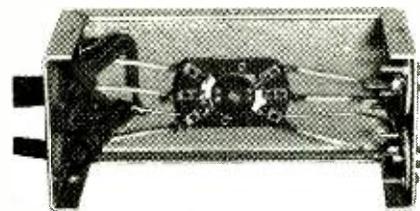A dpdt shorting type switch (Centralab 1462 or equivalent) is used in this model for comparing any two similar components. This will take care of most applications but, if you want to



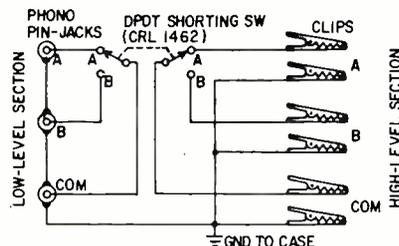Inside view of Comparator shows simple construction.



Circuit of the Audio Comparator.

compare a larger number of units, use a two-pole switch with more positions and a correspondingly greater number of connectors.


Phono pin jacks are used on the low-level section to minimize hum and noise pickup. This section of the comparator

is used where the signal level is low, such as at the input of an amplifier. The high-level section uses 5-foot lamp cords terminated in Mueller type 45 clips. It is used for tests on amplifier output and speaker systems.

The parts are mounted in a 2 1/4 x 2 1/4 x 5-inch aluminum box. Accessories include two 3-foot mike cables terminated with phono pin plugs and two 25-foot lamp-cord clip leads.

To compare high-impedance, low-level components such as microphones, phonographs or tuners connect one unit to jack A, the other to jack B and the indicator to the common jack. Amplifiers are compared by connecting the input and output of each amplifier to the corresponding A and B channels. Apply the input signal to the common jack and the speaker to the common clip lead. Compare speaker quality by connecting one unit to clip lead A, the other to clip lead B, and the amplifier output to the common clip lead.

Check speaker phasing by connecting the A and B clip leads to their voice coils and a type-C or -D flashlight cell with a 5.6-ohm resistor in series to Common. Switch between speakers to see that their cones move in the same direction for correct phasing. If this test is to be made often, such as when making PA installations, install the battery and resistor in the box and use a spst toggle switch to connect it between ground and the high-level switch arm when needed. END

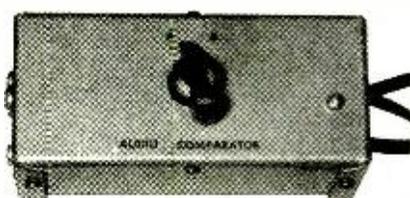

The completed unit, ready to use.

Test Adapters

By **ROBERT F. SCOTT**
TECHNICAL EDITOR

A series of adapters, using a multimeter as their indicating device, saves space and money

NOT so many years ago a service technician could tackle any radio or audio repair job with a tube checker and multimeter. The multimeter alone was enough to see him through a service call to a local factory or theater. Now, with TV, hi-fi audio, intercoms, transistorized equipment and electronic industrial controls—much of which must be serviced on the spot—a technician in the field may need a vtvm, battery and transistor testers and an ac ammeter. For audio servicing he may need a calibrated attenuator (microvolter) to obtain extremely low outputs from his af generator and an audio wattmeter for checking amplifiers and allied equipment.

Adding these to the normal shop complement of service equipment is a financial drain on many technicians. And the bulk puts a premium on space in the service truck.

One way to lick the space problem and reduce the financial outlay has been presented by Simpson with a new line of seven Add-A-Tester adapters for the famous 260 multimeters and the recently introduced model 270. The Add-A-Testers include an audio wattmeter, dc vtvm, audio microvolt attenuator, ac ammeter, and also temperature, battery and transistor testers. Each adapter measures 5-5/16 x 4-3/8 x 3-7/16 inches, and plugs into the bottom of the 260 or 270 vcm as shown in the photograph. Adapter weight ranges from 12 ounces for the transistor tester to 2 pounds for the vtvm and ac ammeter.

The model 260 is a popular multimeter that has been made in three versions. The series I cannot be used with the Add-A-Testers. It is identified by its flat, square-cornered panel. The Series II has a raised panel with rounded corners, uses pin jacks and has a 100- μ a dc range. The series III looks a lot like the series II and is distinguished by its 50- μ a dc range and banana jacks.

Inexpensive adapter case kits are available for using the series II and III 260's and the 270's produced prior to June 1, 1959. Adapter case kit model 401 is optional. It consists of a modified instrument case that permits latching

the Add-A-Testers securely to the underside of the multimeter. The 402 case kit for the series II 260's consists of a modified case and parts necessary for adding a 50- μ a dc range. This kit is necessary when using the series II instruments with the vtvm and temperature, transistor and battery testers requiring the basic 50- μ a movement.

The Add-A-Tester adapters have four banana plugs arranged along the top rear so they mate with jacks on the 260/270 multimeter. Four extra pin type plugs are supplied with each adapter so they can be used with series II 260's. All adapters have a switch (or special position on the function or range switch) that permits the multimeter to be used for its normal functions without detaching the adapter.

Model 650 transistor tester

The 650 Add-A-Tester provides beta and I_{co} measurements on general-purpose low- and medium-power germanium transistors. Power transistors and silicon junction types are checked by interpolation. Beta ranges are 0 to 10, 50 and 250 and the I_{co} range is 0 to 100 μ a.

The circuit of the 650 transistor tester (Fig. 1) is essentially a bridge that balances when collector current is 1 ma. The BAT ADJ control sets the voltage applied to the bridge for optimum accuracy. In the initial setup, it is set so the meter reads 25 on the 50-volt dc range. The ZERO ADJ control varies the base to provide 1-ma collector current and balance the bridge.

The basic bridge circuit for measuring beta is shown in Fig. 2. When the BETA switch is in the 250, 50 or 10 positions, predetermined values of resistance are switched into the base circuit, thus changing the base current and unbalancing the bridge. Beta is read directly from the scale corresponding to the setting of the BETA switch.

The transistor tester uses the 50- μ a movement of the 260/270. In use, the transistor is plugged in and the FUNCTION switch is thrown to NPN or PNP, depending on the transistor being tested. The BETA switch is set at BAT and the BAT ADJ control is set so the meter reads half-scale on the 50-volt



Model 260 multimeter and 650 transistor-tester adapter.



Model 651 dc vtvm adapter.



Model 652 temperature-tester adapter.



Ac ammeter adapter model 653.



Audio-wattmeter adapter model 654.



Model 655 microvolt-attenuator adapter.



Model 656 battery-tester adapter.

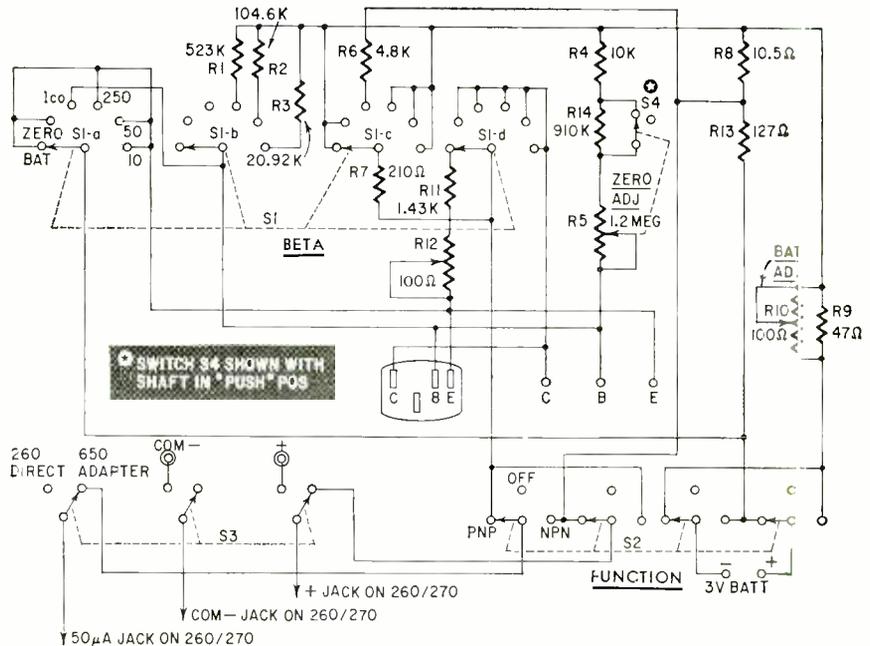


Fig. 1—Circuit of transistor-tester adapter, model 650. All adapters using 50- μ a meter range have plug on short lead to connect to 50- μ a jack on meter.

dc scale of the meter. The BETA switch is then set to ZERO and the ZERO ADJ control R5 is varied until the meter reads zero indicating bridge balance.

(The ZERO ADJ control is a combination pot, R5, and push-pull switch, S4. When pushed in, R14 is shorted out. The initial setup is made with the control pushed in. If the meter does not zero, the control is pulled out and the operation repeated.) If the meter still does not zero, the transistor is defective or has high leakage and must be checked as a power transistor.

When the BETA switch is advanced to 100, the emitter circuit is opened and the meter reads collector current. Read the 0-10 scale on the meter and multiply by 10 for leakage in μ a. Full scale is 100 μ a. Compare this reading to the transistor data sheet. It should be equal to or less than the manufacturer's data.

Throwing the BETA switch to 250, 50 or 10 causes the meter to indicate beta directly on the corresponding scale of the 260/270.

Silicon transistors are checked like germanium types but the beta reading obtained must be multiplied by 1.16 for accurate evaluation.

Power transistors have high values of I_{co} , so it is not always possible to zero the meter with the ZERO ADJ control. In this case, the control is set for the lowest reading. The BETA switch is then thrown to 250 and the first reading is subtracted from the second. The difference is the beta of the transistor. When I_{co} is more than 100 μ a, it is measured by switching the 260/270 to the 0-1 or 0-10-ma range and reading I_{co} on the corresponding scale.

Model 651 dc vtvm

This Add-A-Tester converts the 260/

270 multimeter into a completely portable dc vtvm that meets the needs of the modern radio and electronics service technician. Its sensitivity (0.5 volt full scale on the lowest range) makes it especially useful in checking transistor circuitry and age measurements. Its 10 full-scale ranges are 0-0.5, -1, -2.5, -5, -10, -25, -50, -100, -250 and 0-500 volts dc with an input resistance of 11 megohms. A FUNCTION switch turns the instrument on and off and selects polarity of the dc probe.

The vtvm uses a bridge type circuit with a triode-connected 1A4G subminiature pentode. The self-contained power supply consists of two Eveready 413 30-volt B-batteries and two Mallory ZM-9 1.34-volt mercury cells in parallel for the filament supply.

The complete circuit of the 651 is shown in Fig. 3, a bridge-circuit analogy in Fig. 4. The battery voltages are equal in adjacent arms of the bridge so it is balanced and the meter reads zero when the filament-plate resistance of the tube equals the value of R17.

Voltages to be measured are applied to the grid of the tube. This unbalances the bridge and the value of the applied voltage is read directly on the meter scale specified for the setting of the 651's range selector switch. When using the 651 with the 260 multimeter, the accuracy is $\pm 3\%$ full scale and $\pm 5\%$ of the reading. With the 270 multimeter, the accuracies are 2% and 4% respectively.

The FUNCTION selector should be set for the polarity of the voltage being measured. It is connected so the positive "side" of the voltage being measured is connected to the grid of the tube. The ZERO ADJ control should be set on each voltage range. It is adjusted so the meter pointer is exactly over the zero

TEST INSTRUMENTS

line with the dc probe connected to the ground terminal.

Model 652 temperature tester

This is a self-powered instrument for measuring temperatures from -50° to -250° F in two ranges. The low range goes up to 100° , the high from 100° to 250° F. Accuracy ranges from $\pm 2^{\circ}$ to $\pm 4^{\circ}$, depending on the temperatures covered. The model 652 handles up to three temperature probes and comes with one probe with a 15-foot lead. Other probes are available with 30-, 50-, 100- and 150-foot leads.

The temperature tester is a battery-powered bridge with a thermistor probe in one arm. The probe is placed in the location where temperature is to be measured. The circuit is shown in Fig. 5. The bridge uses the $50\text{-}\mu\text{A}$ movement of the 260/270 with readings taken on the 50-volt dc scale. A slide rule across the top of the 652 converts the meter readings to temperature.

The FUNCTION switch is marked OFF, ADJ, LO and HI. It turns the instrument on and off, sets up the bridge for balancing and selects the temperature range. In the ADJ position, the battery is connected across the bridge with the probe disconnected. The METER ADJ control (R3) is set so the meter reads 25. This is half-scale when set on the 50-volt range.

When measuring temperature, the thermistor probe is substituted for R9 and calibrate pot R11. Bridge sensitivity is changed for the two ranges by varying the resistances of the three arms. On the LO range, R1 is shorted out for measurements up to 100° . R2 and R12 are short-circuited for measuring temperatures ranging between 100° and 250° on the HI range.

The meter pointer deflects off scale on the right if the temperature is below -50° F and off scale on the left if it is above 100° F on the LO range. If the pointer deflects off scale to the left on the HI range, the temperature is above 250° and the probe must be removed from the high-temperature area to prevent damaging it.

Ac ammeter model 653

This instrument measures alternating currents in ranges of 0-0.25, -1, -2.5, -12.5 and 0-25 amps with frequency response essentially flat from 50 to 3,000 cycles to cover power-frequency requirements of military and commercial supplies. Insulation is for 600 volts rms maximum.

The ac ammeter (Fig. 6) is a current transformer with a tapped primary and a secondary loaded by a precision resistor. The primary is inserted in series with the circuit being metered. Current in the primary induces a proportional current in the secondary and the 4-ohm load resistor. The current in the primary circuit is obtained by taking a reading on the 2.5-volt ac scale of the 260/270 and multiplying it by the fac-

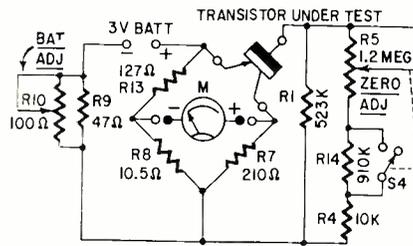


Fig. 2—Equivalent circuit of transistor tester with switch in Beta 250 position.

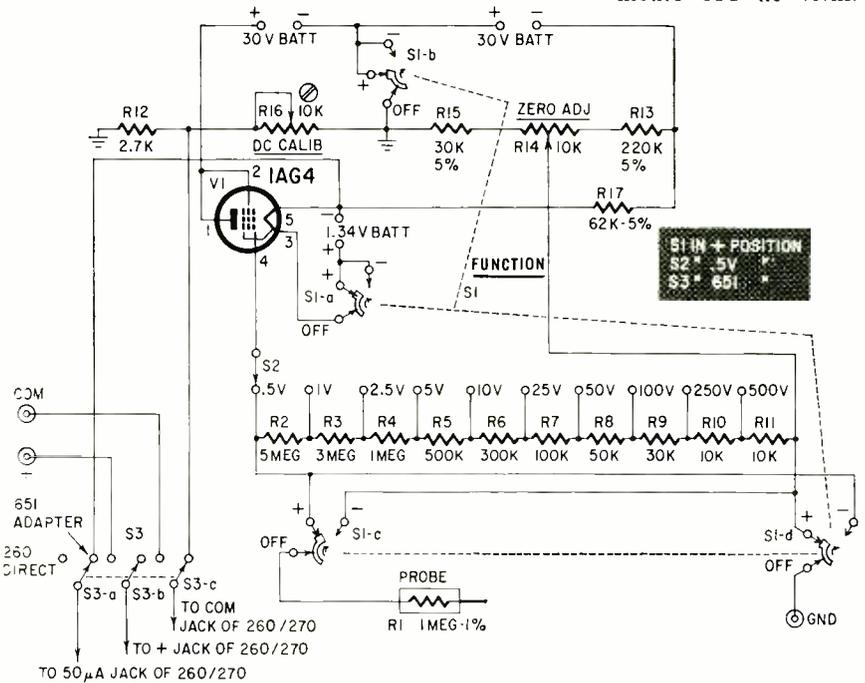


Fig. 3—Schematic of model 651 dc vtvm.

tor indicated above the range binding post used.

Model 654 audio wattmeter

The wattmeter is designed for use in installing and servicing audio equipment. It provides noninductive 4-, 8-, 16- and 600-ohm loads for circuits being metered. Frequency response is flat from dc to 20 kc. Maximum wattages (with ambient temperature of 77° F) are 50 watts continuous and 100 watts for $2\frac{1}{2}$ minutes with 4- and 16-ohm loads and 25 watts continuous and 50 watts for $2\frac{1}{2}$ minutes with 8- or 600-ohm loads.

The circuit diagram of the 654 audio wattmeter is in Fig. 7. The "+" and "-" INPUT terminals on the 654 are connected directly to the corresponding terminals on the 260/270 multimeter. When the five-position LOAD SELECTOR is in the 260 DIRECT position, the test leads are connected to the multimeter so it can be used for any of its normal functions without detaching the adapter. In the other four positions of the LOAD SELECTOR, one or more of the internal load resistors are bridged across the INPUT terminals and the 260/270.

When the 654 is being used, the normal equipment load—speakers, phones,

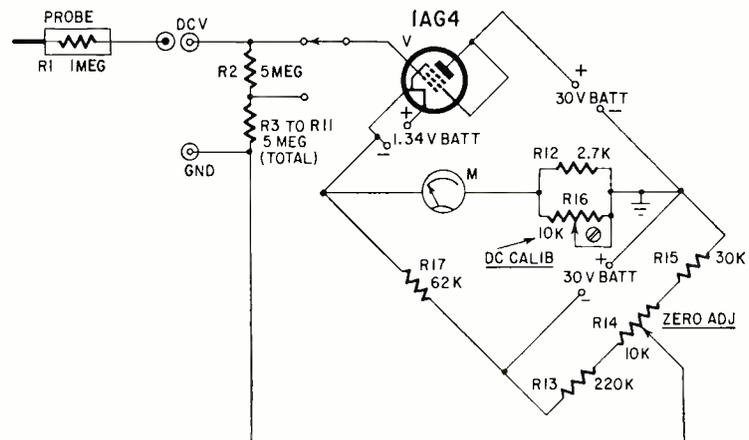


Fig. 4—Bridge circuit of 651 dc vtvm.

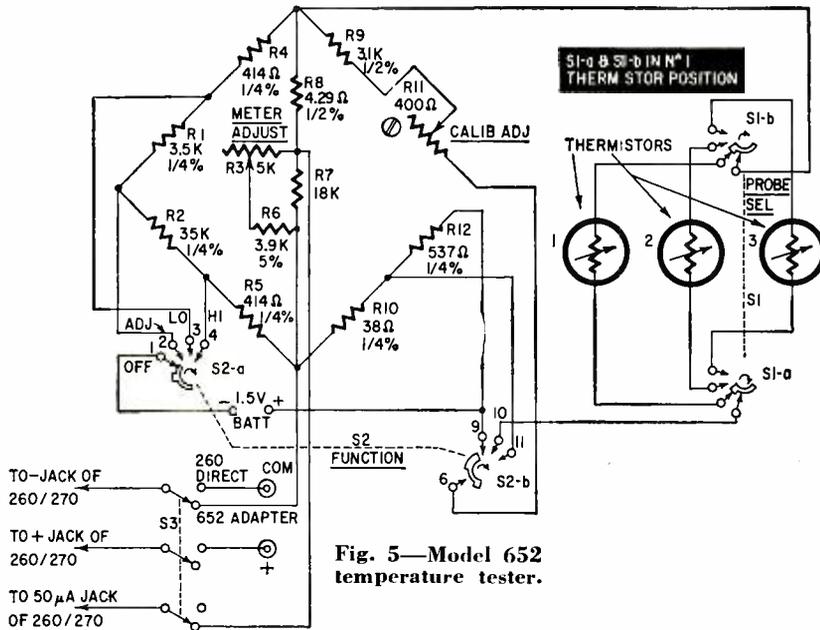


Fig. 5—Model 652 temperature tester.

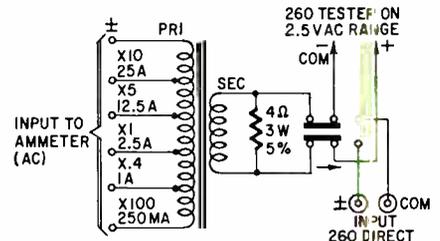


Fig. 6—Ac ammeter, model 653.

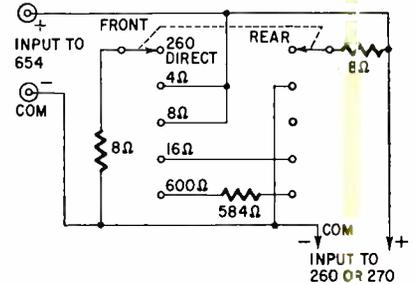


Fig. 7—Audio wattmeter model 654. Load-selector switch selects various load-resistor combinations.

lines, etc.—is removed from the output of the circuit or equipment being metered. The LOAD SELECTOR is set to the impedance matching the nominal circuit load. An audio voltage is fed into the unit being tested and the wattmeter measures the voltage across its load resistors on one of its ac voltage ranges. An attached slide rule converts the voltage reading to watts.

655 microvolt attenuator

This instrument provides calibrated low-level outputs ranging from 25 μ v to 250 mv from a 2.5-volt ac or dc source. Its frequency response, essentially flat from 0 to 20 kc, makes it an excellent source of precise low voltages. It consists of an input level control—METER ADJ—and a five-position 600-ohm ladder attenuator. Each section of the ladder reduces the signal 20 db or to one-tenth of its input level. The input impedance is 2,000 ohms. An internal 600-ohm load resistor can be switched in or out, depending on the resistance or impedance of the external load circuit.

The input voltage is applied across the 2,000-ohm METER ADJ control and the 260/270 multimeter measures the voltage applied to the ladder attenuator (Fig. 8). When the ladder's input is exactly 2.5 volts, the microvolter's output is 25 μ v, 250 μ v, 2.5 mv, 25 mv or 250 mv, depending on the range selector switch—marked FULL-SCALE OUTPUT. When the input to the microvolter is greater than 2.5 volts—maximum input is 33 volts—the output is equal to the meter reading multiplied by the attenuation factor corresponding to the range setting.

The 600-ohm internal load resistor is used when the microvolter's output is connected to a circuit with an input impedance of 60,000 ohms or higher. When the impedance is less than 60,000 ohms but greater than 600 ohms, the 600 Ω LOAD switch is thrown to OUT. An

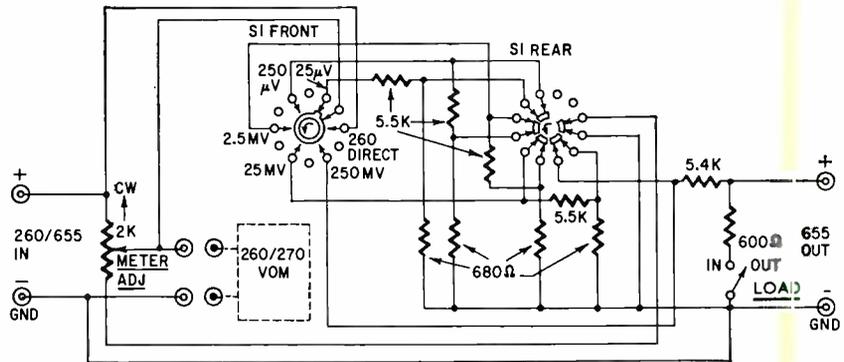


Fig. 8—Model 655 microvolter schematic.

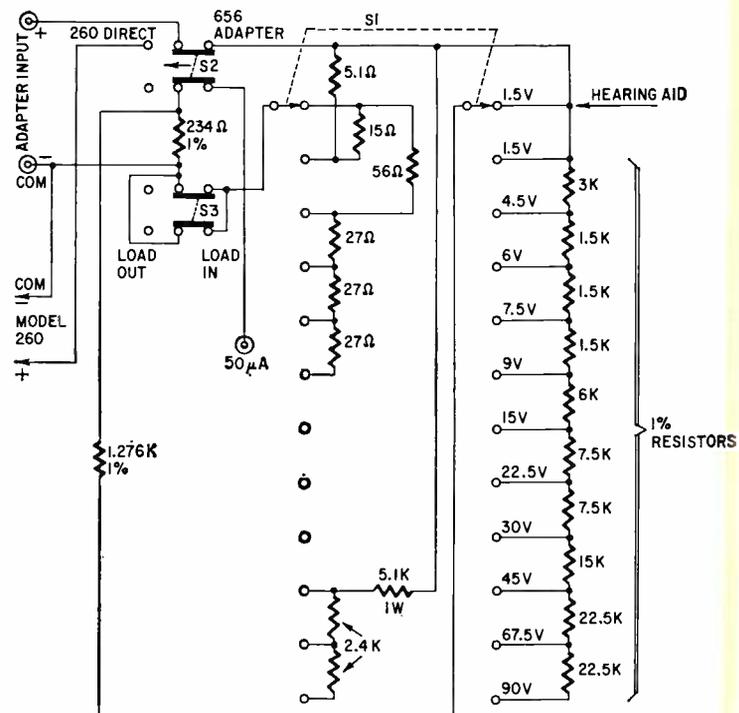


Fig. 9—Model 656 battery tester. Batteries checked under recommended load.

TEST INSTRUMENTS

external resistor is shunted across the circuit so the load on the microvolter appears as 600 ohms. The value of the external shunt resistor R_x equals $600 \times R/600 - R$, where R is the input resistance (or impedance) of the circuit being supplied.

When the input resistance (or impedance) of the external circuit is less than 600 ohms, the 655's internal load resistor is switched out and a resistance sufficient to bring the load impedance up to 600 ohms is inserted in series with one of the output leads. Voltage across the external circuit's input is proportional to the 655's output or $R \times E_o/600$, where R is the resistance of the load and E_o is the output voltage of the microvolt attenuator.

Battery tester model 656

This instrument tests, under suitable load, the batteries most commonly used in radio, hearing-aid and industrial service. The adapter has 12 voltage ranges. One for small 1.5-volt hearing-aid batteries and 1.5-, 4.5-, 6-, 7.5-, 9-, 15-, 22.5-, 30-, 45-, 67.5- and 90-volt ranges for A- and B-batteries.

The 656 (Fig. 9) has a slide switch which, when in the LOAD IN position, shunts the battery under test with the manufacturers' recommended load. In the LOAD OUT position, the shunt is disconnected and the battery can be tested under normal in-circuit operating conditions. The metering circuit draws a maximum of 1 ma.

The 656 uses the 50- μ a movement of the 260/270. The multimeter is set up for measurements on the 50-volt dc range and readings are made on that scale. A slide rule with three basic scales is mounted across the top of the adapter's case. The top is calibrated 0 to 50, the middle is marked BAD-WEAK-GOOD (for radio and hearing-aid batteries and all B-batteries). The bottom scale is calibrated from 0 to 110% (of the selector voltage range).

In testing a battery, the adapter's range-selector switch is set to the battery's terminal voltage and the meter is read on the 50-volt dc scale. The hair-line on the slide rule is placed over the meter reading on the top scale and the battery condition and percent of rated voltage are read on the middle and bottom scales of the rule. Actual battery voltage is found by multiplying the range-selector setting by the indicated percentage. END

AMATEUR CONVENTION

The Hudson Amateur Radio Council is holding its first annual convention at the Statler-Hilton Hotel in New York City. It will open at 10 am Saturday, Oct. 15 and close at 7 pm with a banquet. There will be technical talks, meetings, manufacturers' exhibits and prizes. The convention is being run entirely by the amateur clubs of the New York area and everyone within commuting distance is invited. For information write HARC Convention, PO Box 971, New Rochelle, N. Y.


CAPACITOR TEST BOX FINDS INTERMITTENTS

By JAMES A. FRED

IT'S hard to locate an intermittent electrolytic with in-circuit tests. If you try shunting the suspected unit with a good electrolytic, the charging current may temporarily heal the bad one. Then when you remove the test capacitor the set appears to work normally and you still don't know what's wrong.

After running into this problem a couple of times, I decided to build an electrolytic test box that would pick up bad capacitors without healing them. The unit I devised is shown in the diagram and photos.

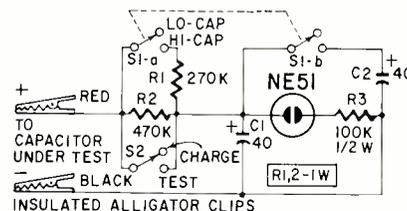A neon lamp and its series current-limiting resistor are connected across a test capacitor. The lamp lights when the capacitor is charged. Charging resistors are switched in and out of the circuit by S2, the CHARGE-TEST switch. Switch S1 gives you either a




Circuit of simple test unit.

40- μ f test capacitor (LO-CAP) or connects two 40- μ f units in parallel to form an 80- μ f unit (HI-CAP). At the same time, another section of S1 changes the value of the charging resistor—either R2 by itself (for 40 μ f) or R2 and R1 in parallel (for 80 μ f).

Using the checker is easy. Just set S1 for high or low—40 or 80 μ f and S2 to CHARGE. Then connect the tester to the capacitor under test with its insulated test clips—of course, you have already turned on the defective radio, hi-fi or TV. Wait for the neon lamp to light. Now slide S2 to the TEST position. If the capacitor under test is bad, the fault should vanish. If the fault remains, obviously the capacitor is good. Before going on to the next electrolytic, discharge the checker by shorting the red and black test leads. END




Completed electrolytic tester.

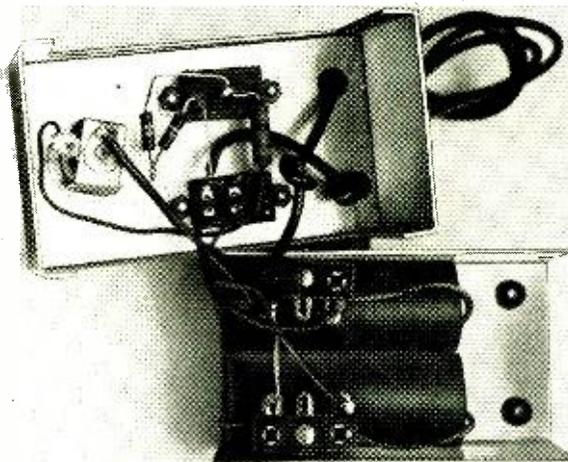

Parts layout inside checker.

WHAT'S NEW

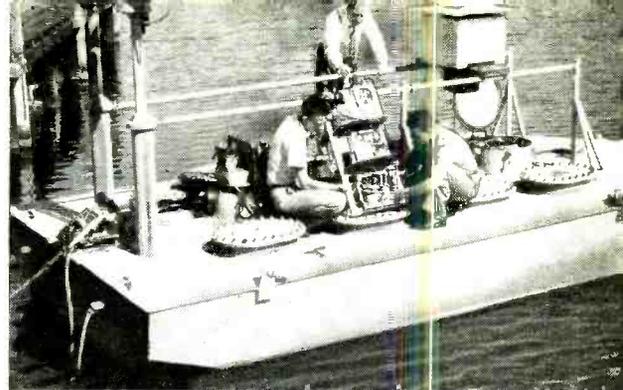


UNMANNED WEATHER STATION, developed by National Bureau of Standards for the Navy, transmits local data from remote ocean areas. Air and water temperature, wind speed and direction and barometric pressure are converted into three-letter groups in continental code and transmitted at 6-hour intervals on a frequency of about 6 mc.





NEW SWEDISH SYSTEM combines speakers and amplifier in one cannonlike enclosure. A seven-tube two-channel amplifier and six speakers are inside the enclosure. Woofer is at bottom in bass-reflex type of enclosure backed with sound-absorbent material which acts as partition between it and middle- and high-frequency speakers. Midrange speaker is seen at top and four high-frequency speakers are mounted around top perimeter. Both high- and low-frequency channels use single-ended push-pull with EL86's and direct drive to speakers, without output transformers. Power amplifier is mounted inside base panel. Elektron Lund of Malmo, Sweden.

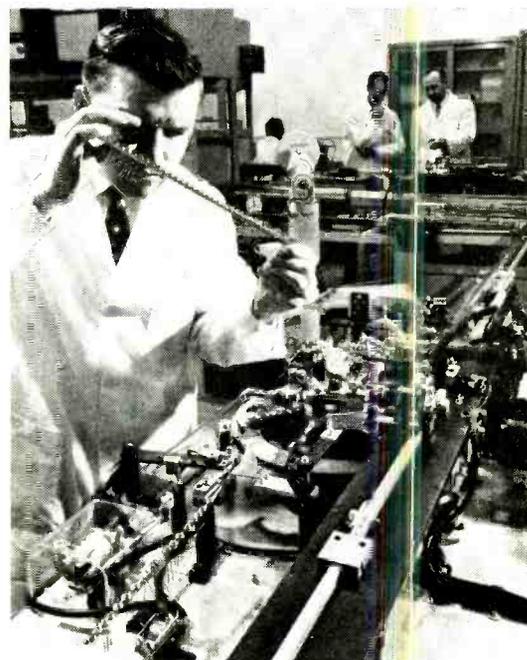SQUARE-NECKED PICTURE TUBE allows corners of picture to be seen. New tube bulb, developed by Kimble Glass Co., has four channels formed in neck to allow corners of picture to pass. This improves contrast because "corner clipping" in old tube bounced electrons off tube walls and bombarded screen in random fashion, reducing contrast. Deflection angle is 114°.



AUTOMATED ASSEMBLY SYSTEM produces 1,800 transistors an hour (higher than previous automated systems; see March, 1959 issue, page 6). Six turntables, two ovens (for alloying and bonding) and welding unit are primary components of IBM's unit. Entirely self-checking, photocell and mechanical devices reject any transistor-carrying "boats" (small carbon cylinders) that contain missing or poorly positioned parts.

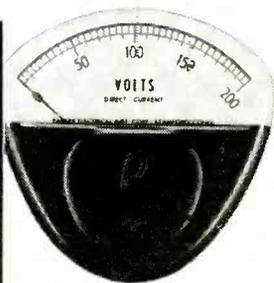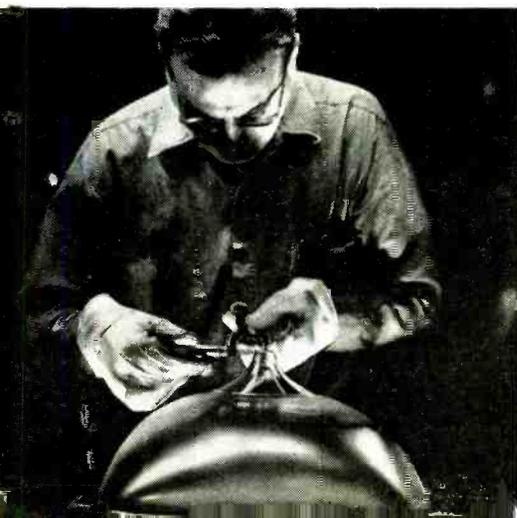


PANEL METER uses printed-circuit coils and thin ceramic ring magnet. Built-in shielding eliminates need to specify type of panel meter is mounted on. Two screws projecting from back serve as both termi-

nals and mounting screws. A 1,000% electrical overload for 1 second will not disturb accuracy. The Parker Electrical Instrument Corp. makes these very very thin units for use in a variety of circuits.

semiconductors for industrial controls

By TOM JASKI

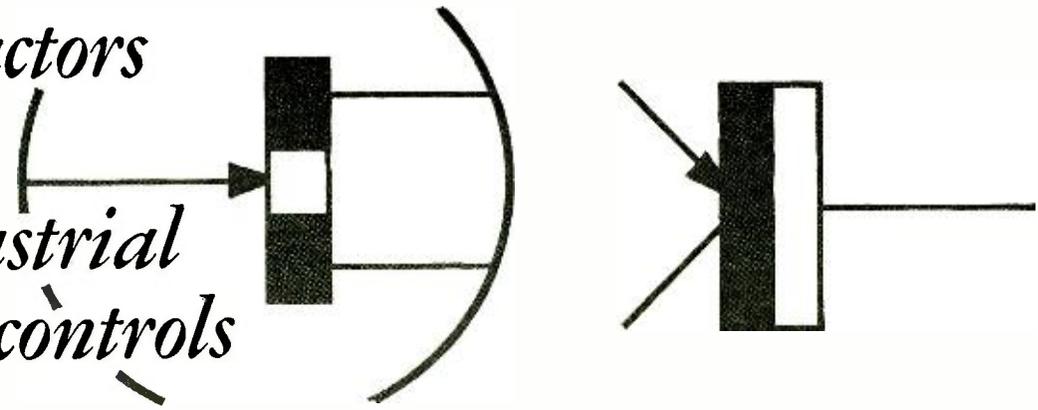Transistors, Unijunction transistors, avalanche diodes, Trigtors, silicon controlled rectifiers and cryostats are all usable as static switches



In the two previous articles we discussed magnetic amplifiers and the special control systems based on logic units developed from them. Much newer, and therefore not as widely applied, is an entirely different system, based on transistors.

To build logic units we need some kind of a switch or device with two states, conducting and nonconducting. A transistor fits in because we can recognize in its operation two greatly differing states, one of very high resistance and one of very low resistance. These two operating points are shown in Fig. 1. The transistor is off at A and on at B. Essentially, the only difference in circuit values responsible for these two states is the base current.

The quality of a transistor switch depends on how well we can reduce leakage current from collector to emitter. By providing a small amount of reverse bias, we can keep the transistor cut off. Fig. 2 shows the basic circuit of a transistor switch with reverse bias applied. There are other possible circuits, but the engineers who build industrial control systems consider reliability one of their most important criteria, and careful analysis has shown that the common-emitter switching circuit is the most reliable arrangement. Fig. 2 is the basis of a fundamental logic unit. Apply a signal to the input and the transistor presents a virtual short to its output (there is no output signal). This forms a logic unit we call a NOT circuit. If we add several inputs to this circuit so a signal applied to any one of them saturates the transistor, we can say that neither a signal on 1 nor a signal on 2 will provide an output, and we call this a NOR unit (any input prevents an output). An entire control system with logic units can be based on this NOR circuit. We can, of course, include one, two or more inputs, so long as we isolate them from each other with resistors as shown in Fig. 3. Generally speaking, we reach a limit when we have about 10 inputs.

Transistor Logic units

Fig. 4 shows the logic units we can build. Fig. 4-a is a simple NOT unit, which is the NOR with a single input.

If we make the units all alike and ignore some inputs, we waste some resistors, but the fact that we are making only one kind means that the units can be mass-produced. Fig. 4-b is the two-input NOR, and 4-c is an AND unit made up of two NOT units and one NOR unit. As long as no signal is applied to one of the NOT units, there is an output that prevents an output from the NOR unit. Both I and II must have an input to get an output from III.

Fig. 4-d shows a flip-flop which we can use as a MEMORY unit. Here we use a couple of 2-input NOR circuits, with the input of each one connected to the output of the other.

To examine the flip-flop's operation, let's start with a nonconducting state for both transistors, and no power on. As soon as power is applied, both transistors start to produce an output. But one will be very slightly faster, and its output will saturate the other and keep it saturated. So one stable state is intrinsic to the circuit. Assume that I is conducting, and II is nonconducting. If we apply a signal at input 2, transistor II saturates and its output stops, cutting off I. Alternate pulses at inputs 1 and 2 reverse the state of the memory unit at each pulse.

Fig. 4-e is an OR circuit made from a NOR unit followed by a NOT unit. A signal at either A or B keeps I turned off and no signal is applied to the NOT

unit, so we get an output at C. But with no signal on A or B we get an output from I which cuts off the NOT unit and prevents an output at C.

Another logic unit we have not previously encountered, but possible with the NOR system, is shown in Fig. 4-f. This is constructed from one NOT and one NOR unit. As long as there is no signal on the control, there will be an output from II but, as soon as a signal is applied to the control input, the output is "inhibited". This INHIBITING

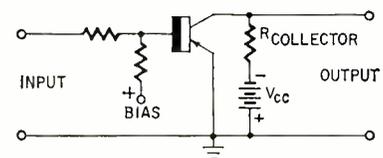


Fig. 2—Basic transistor switching circuit.

GATE is a very useful tool for connecting, disconnecting and controlling.

Time delay is important in logic systems. Fig. 4-g shows a time delay built around two NOR units. Normally unit I is cut off, producing an output which keeps II saturated. If we apply a short pulse to the input, both units

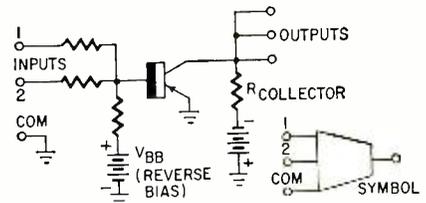


Fig. 3—Basic transistor NOR circuit and symbol.

momentarily saturate, but the charge stored in C2 quickly saturates II as soon as the pulse is removed and II never really gets a chance to conduct. Capacitor C1 saturates unit I until the charge on C1 leaks off, and all this time C2 holds II saturated until the job can be taken over by unit I again. Obviously, capacitor C1 in combination with the circuit resistances determines the time delay. Capacitor C2 must have the same value as C1 since it must keep II saturated until I produces a signal again.

This system of NOR circuit control

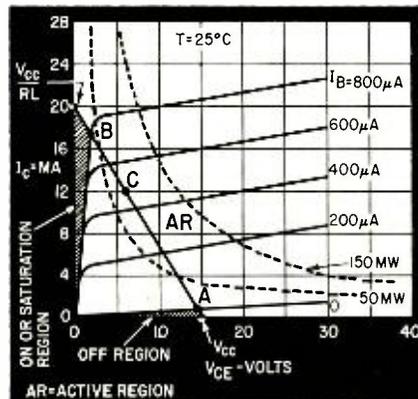


Fig. 1—Typical common-emitter characteristics of a transistor. Note the on and off regions.

is being marketed by Westinghouse. They have also built a computer, the NORDIC, based entirely on NOR circuits. Not as prevalent at present as the magnetic type circuits, control systems of NOR circuits have great possibilities, for they can obviously be built very economically.

There are many other switching and logic circuits we can build from transistors, but not many of them can be as universally applied as the NOR unit. We have all seen two- and four-transistor flip-flops which often use diodes as well. Obviously the two-transistor NOR flip-flop is more economical.

This may be the reason why many other excellent switching devices have not yet been extensively used as industrial control systems or even for logic units.

Some of these semiconductor devices have rather startling properties, but their cost is not low enough to compete with the common transistor.

Unijunction switches

One of the interesting semiconductor static switches is the Unijunction transistor. Its symbol and construction are shown in Fig. 5. It consists of a silicon bar with a base contact at each end. An emitter junction is on the bar, somewhat closer to base 1 than base 2. Fig. 5-b shows the basic Unijunction circuit. With no emitter voltage applied, the silicon bar functions as a resistor, and the field created in the bar by the current produces a small emitter-to-base voltage proportional to

the current through the bar. If the voltage applied to the emitter is less than this voltage, the junction is reverse-biased and emitter current is minimal. When the voltage applied to the emitter exceeds the intrinsic voltage, "holes" are injected into the bar. They reduce the resistance of the bar between emitter and base 1. This allows a sudden increase in emitter current. Once past this point we can decrease emitter voltage and still increase emitter current. This gives us a negative resistance effect. This is shown in Fig. 6, the characteristic Unijunction curve. It clearly shows the reversal of operating mode, which we exploit as a switching characteristic. Thus it is easy to construct a bi-stable circuit, such as a flip-flop, as shown in Fig. 7. The trigger signal at X must be positive, or we must apply a negative trigger at Y, to obtain the conducting state. A negative signal at X returns the unit to the nonconducting state. Conducting resistance runs as low as from 0 to 40 ohms, nonconducting resistance as high as 1 megohm.

Many Unijunction circuits have been developed, but no generally applied logic units have yet been marketed. Obviously, the competition of inexpen-

the increased voltage, succeed in knocking a large number of electrons out of a microscopically thin layer, creating a microplasma, which spreads rapidly throughout the layer. This special layer is an alloy formed by fusing a tiny speck of aluminum to a piece of silicon bar. The layer is estimated to be four millionths of an inch thick. The diameter of the junction is slightly over .001 inch!

The Trigristor

A third static switch is the Trigristor (see Fig. 8) a p-n-p-n device developed by Solid State Products Inc. The Trigristor has the unique characteristic that it can be turned on and off by a trigger,

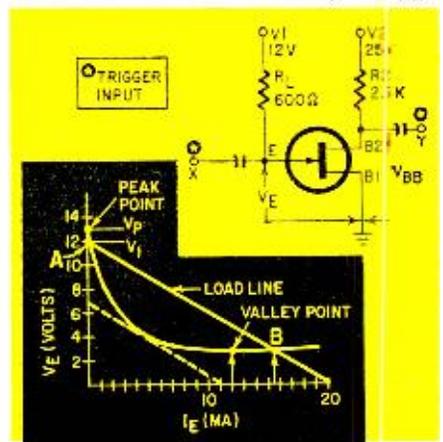


Fig. 7—Basic Unijunction transistor bistable circuit with typical emitter characteristic curve.

like any bi-stable circuit. A low-level positive trigger applied to its base turns the Trigristor on, and it remains on without base current. A negative trigger fed to its base turns it off, and it remains off without base current. This makes it possible to build flip-flops with very few components.

To understand Trigristor action we look at an analogy of two transistors, a p-n-p and an n-p-n transistor, as shown in Fig. 9. The collector of the n-p-n unit drives the base of the p-n-p unit and vice versa. The circuit has a gain which is the product of the betas of the two transistors. So long as these are both less than 1, the circuit is stable with no change in current. But once this product becomes greater than 1, regeneration keeps the process going until both transistors are saturated. When the negative trigger is applied, the gain product once again becomes less than 1, and the transistors cut off. In the Trigristor, the two transistors are fused into one device.

Silicon-controlled rectifiers

The next static switch which shows promise, particularly in the industrial electronics field, is the silicon-controlled rectifier. This device (Fig. 10) is more analogous to a thyatron but can also be operated as a switch, and a very good one at that. The silicon-controlled rectifier differs from the thyatron in that a current rather than a voltage

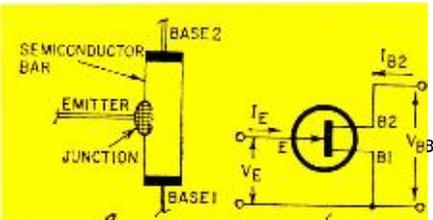


Fig. 5—Unijunction transistor: a—construction; b—schematic symbol.

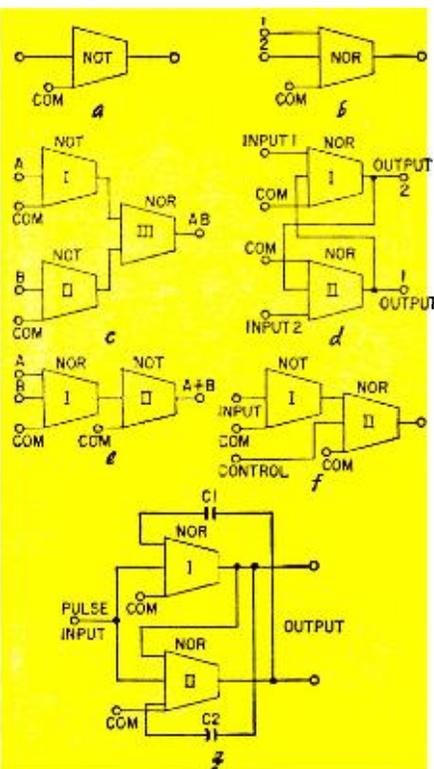


Fig. 4—NOR unit logic functions: a—NOT unit; b—NOR unit; c—AND unit; d—MEMORY unit; e—OR unit; f—INHIBITING GATE; g—TIME DELAY. Note that it uses a 3-input NOR unit.

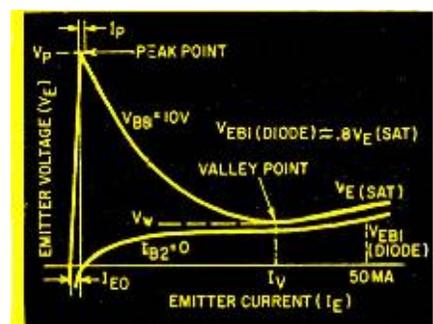


Fig. 6—Unijunction transistor's characteristic curve shows curve reversal that makes it usable as a switch.

sive transistors may hold up this development for a time.

Avalanche diode switching

We are still a long way from the bottom of the barrel. Another unusual and interesting static switch is the avalanche switch developed by Sperry Rand. It is a diode, which upon an increase of applied voltage switches (increases) the current through it so rapidly that we have no way of accurately measuring the transit time, which is on the order of a trillionth of a second. This switch uses the avalanche effect. Some electrons, speeded up by

in its control element causes conduction. Comparing the controlled rectifier with an ordinary rectifier (Fig. 11), we see that the normal rectifier has a silicon wafer forming the anode of the junction, while the controlled rectifier has an n-type silicon wafer with two p-layers diffused into its surface. This combination of p- and n-type silicon looks similar, in symbol at least, to the Trigistor. But the effect is quite different, partly because no base junction is formed and because the silicon wafer is just mounted on the stud.

Actually, the controlled rectifier is closer to the combination of an n-p-n transistor and a reverse-biased diode (Fig. 12). (Let me caution the reader that this is my own pet representation, not the manufacturer's official explanation.)

As long as the transistor is nonconducting, the voltage applied to the diode is low, because of the resistance provided by the cutoff transistor. But

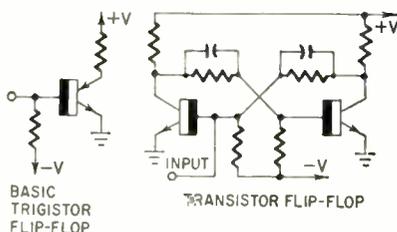


Fig. 8—Comparison between Trigistor and conventional transistor flip-flop circuit.

when a signal on its base makes the transistor conduct, even though the signal would be too small to cause the reverse breakdown of the diode, the fact that the conducting transistor now presents virtually no resistance in the circuit allows the full supply voltage to be applied to the diode, and breakdown occurs. Once this has happened, the voltage developed across the emitter junction would keep the transistor conducting and the reverse pulse required to turn the thing off would have to be as large as the supply voltage. This is almost true. To restore the controlled rectifier we must momentarily lower the supply drastically or bypass the rectifier. In my analogy, you can see this would also work, for if we momentarily allowed the diode to recover we would in effect remove the bias to the base.

The controlled rectifier has been made principally to deliver large currents. Although a number of circuits, such as flip-flops, are based on its action as a switch, their use in logic circuits is not immediately visualized. Where higher current possibilities are not important, other semiconductor devices such as the Trigistor and Unijunction transistor have definite advantages over the controlled rectifier in terms of parts required per logic unit. Nevertheless, it is an important type of static switch and may well find application as the final switching element in control systems where we have heretofore been

forced to use relays or contactors.

An electrochemical switch

A fifth static switch which we do not immediately associate with industrial control, because its development has been directed primarily in the direction of computer applications, is the Cryostat. In terms of construction, it is perhaps the simplest of all. But it has some severe environmental requirements, which may hold back even computer applications. The action of the Cryostat is based on the fact that a tantalum wire which has been supercooled will drastically change its resistance with a change in the magnetic field surrounding the wire. The Cryotron operates in an open bath of helium at approximately the boiling temperature of the liquid gas, and at room pressure, 4.2° K. The Cryotron gate consists of about 250 turns of 3-mil niobium wire wound on a tantalum wire, 9 mils in diameter and 1 inch long, a very small gadget indeed. The niobium wire remains superconductive over the range of magnetic-field change that affects the tantalum wire (a relatively small range—50 to 100 oersteds). The change in current in the niobium wire, from 0 to about 200 ma, represents the signal, and this changes the resistance of the 1 inch of tantalum wire from 0 to .008 ohm. To anyone thinking in terms of the industrial control systems we have been discussing, this may seem like an insignificant change, hardly enough to base a reliable control system on the word zero, which is not nearly as theoretical a word as it might seem. For superconductivity means that a wire with a current in the superconductive state maintains this current with no measurable decrease over a long period

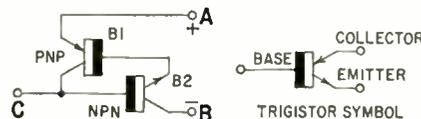


Fig. 9—Analogy between two transistors and a Trigistor.

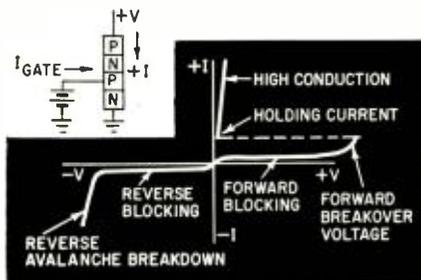


Fig. 10—Silicon controlled rectifier and its characteristic curve.

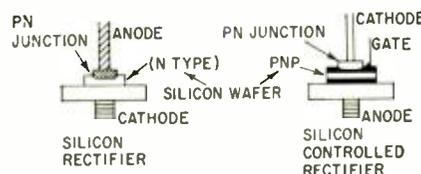


Fig. 11—Comparing standard and controlled rectifiers.

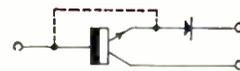


Fig. 12—The author's analogy for the controlled rectifier.

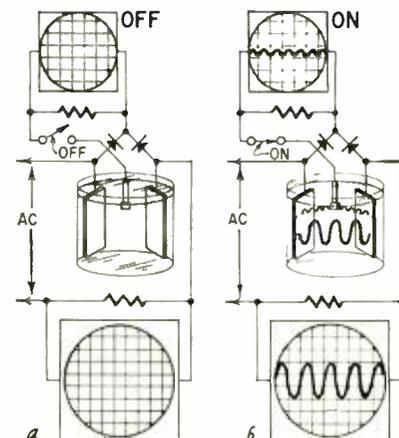


Fig. 13—Electrochemical static switch: a—off; b—on.

of time. Then the change of a fraction of an ohm becomes relatively enormous. Many logic elements have been built, and practical computer circuits tested. Again, the Cryostat earns its name as a static switch, but we will not see liquid helium flasks in a factory or steel mill for some time to come.

More likely to find application in these places is the electrochemical switch based on a discovery by Ovshinsky of the Ovitron Corp. Fig. 13 shows this switch diagrammatically in its off and on positions. The switch, with de on its firing electrode, passes an ac load, and without the voltage on the electrode presents a high resistance to the load current. No satisfactory theoretical explanation for the phenomenon has been found. Although not likely to be a candidate immediately for a series of ac logic circuits, this ac switch also has possibilities as the static equivalent of relays and contactors.

Here then, besides the well developed and widely applied static switching systems, you have seen a group of static switches, each of which may eventually come into its own in industrial electronics, and some which are on the doorstep right now. We have purposely avoided spending time on vacuum-tube and thyatron switching, since they are well known devices of yesterday as well as today. Static switching and control is today and the future. It represents a philosophy which will not only find its way into the control phases of industry, but also into the processes we use to produce machine parts. For example, electrolytic etching techniques are beginning to take the whirling lathe chucks and milling cutters out of the shop and into the museum. Not today, but certainly tomorrow, we may be producing entire machines without much more than a few streams of liquid electrolyte moving in the plant, and then the evolution of the process will allow us to do away even with them. END

OSCILLOGRAPHS IN ACTION

By J. H. THOMAS

THE modern oscillograph, though not an electronic instrument as such, is so often used with other electronic equipment in industry, in laboratories and on missile testing sites that it is important for the electronics technician to be acquainted with it. Far from being instruments of yesterday, oscillographs have their own area of application, sometimes overlapping that of cathode-ray oscilloscopes, but more often in applications where the oscilloscope is not the proper instrument to use. What is an oscillograph? What does it do? Where, why and how is it used? These are the questions we aim to answer.

Oscillograph history started with the basic D'Arsonval galvanometer. This is the well known moving-coil instrument, which you probably use daily. However, to label it as a galvanometer, we must think of the same instrument with a very small mirror in place of the pointer. When we direct a narrow beam of light at the mirror, the beam is reflected. As the coil turns, the reflected beam moves and we can then intercept it with a frosted-glass scale and make the instrument very sensitive by making our pointer (the beam of light) very long. Now if we use a film or light-sensitive paper in place of the scale and move it past the light beam, at right angles to the galvanometer deflection and at a constant speed, we add a time base and get a permanent record of the light-beam deflections as they occur in time. This is shown in principle in Fig. 1. In place of a moving film or paper, we can also add a second deflection to the light-beam by intercepting it again with a moving mirror, but this time moving the mirror at a constant speed at right angles to the beam deflection caused by the coil. Then we can record the trace on a still film shot such as a Polaroid camera produces. The principle is shown in Fig. 2. Here the time-base mirror is moved by a spring, while a dashpot assures constant speed.

Oscillograph advantages

The moving film (or paper) galvanometer can record long stretches of events or, by moving the film at great

The inside story on an important piece of industrial electronic test equipment. How it works; where it's used; what it does

speed, record them with great accuracy. Ordinary galvanometers could do this job, but they would be rather large and only a few could be used in one oscillograph. So the oscillograph has specially designed galvanometers, which are very slender. They consist of a very small coil pivoted on supporting spring wires (to avoid jewel pivots and provide torque at the same time), or even simply of a single loop of wire which functions as both coil and suspension. Both types are shown in Fig. 3.

Obviously the impedance of such coils is very low. Also we need a magnetic field hut, since the coil is so small we do not need the customary center core used in most D'Arsonval instruments to keep the field working on the coil homogeneous. And third, it will also be clear the stiffer the suspension (the greater the tension in the suspension wires), the harder it is to turn the coil, but also the faster the coil returns to zero position. In other words, the galvanometer can be made to respond to higher frequencies as we make it less sensitive.

Photo A shows a modern galvanometer from the Heiland oscillograph. When these units respond to fairly high frequencies, they must be damped or they may oscillate at their natural frequency when suddenly deflected. Sometimes the damping is done electrically (by shunt resistors) and sometimes by filling the galvanometer case with fluid. A large number (as many as 12) of these galvanometers are placed between the poles of a strong magnet, which provides the magnetic field normally provided (in a meter) for a single coil only. This is done to save space.

The response of these galvanometers is not high compared to the oscilloscopes you are used to. For example, a very sensitive galvanometer may have an impedance of about 300 ohms, respond to frequencies up to say 100 cycles, and deflect an 8-inch "pointer" light beam about 1 inch for 5 μ a. At the other end of the scale, we may find a galvanometer which deflects the beam an inch at the same arm length, but needs 30 ma to do it. However, this one may respond to as much as



Photo A—Subminiature Heiland galvanometer.

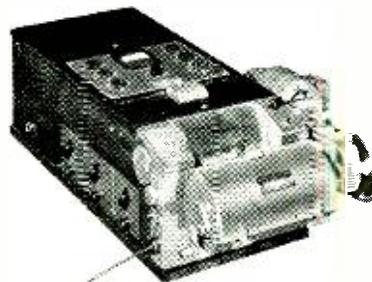


Photo B—Typical laboratory type oscillograph, the G-E PM-10-B2. Galvanometers are under small hood in center. Front part is camera film drum with its drive at right.

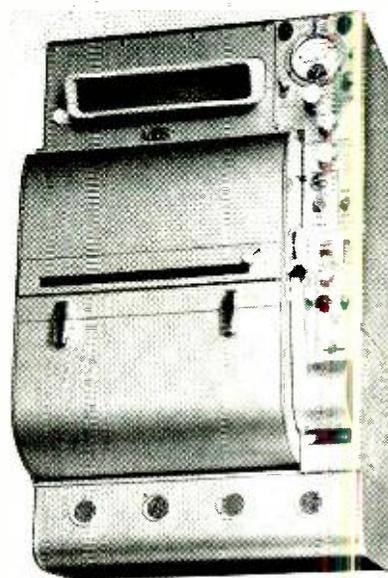


Photo C—Industrial type oscillograph. Slot at top is for viewing.

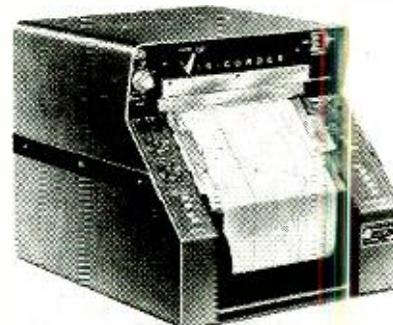


Photo D—Viscorder model 1103. Note pushbutton controls.

INDUSTRIAL ELECTRONICS

5,000 cycles. In between is a large selection of galvanometers of all kinds of sensitivities, frequency response and damping requirements.

How it works

Photo B shows a typical laboratory oscillograph. Here the film camera is up front, driven by the variable-speed drive at the right. The galvanometers are under the little cover in the top center, where they can be reached to adjust them. Adjustments are principally to position the trace on the film. This type of instrument can be made with as many as 24 galvanometers. The one shown has only 12.



During adjustment, the light-source lamp is in series with a resistor to lower its voltage. The lamp is a very-high-intensity incandescent lamp that delivers enough light to leave a clear trace on the film. We turn it on to full brightness only while recording—this is done automatically in the instrument. Projection type lamps are used. Some manufacturers make special lamps for their galvanometers, while others used the same kind of lamps used in sound-track systems for movie projectors. Lamp life runs between 100 to 500 hours, more likely the lower figure. Replacements should be kept on hand if the oscillograph is used frequently.

Photo C shows the form of oscillograph you are likely to encounter in industry. It has all the features of the laboratory instrument, but is enclosed in a more suitable case for permanent installation. Notice the slot near the top. It is for viewing the trace as it is being recorded or adjusted. This can be done quite simply as shown (Fig. 4). Of course we need a time base too. An angular mirror is rotated at high speed. As the mirror turns, your eye sees one flat side after another, and on each side the beam appears in different places as it moves. Viewing the sides rapidly is like seeing movies; you actually see a series of single shots but their sequential display tricks your eye into seeing movement. So here too you get the effect of a continuous time base.

Another feature of oscillographs is that we can readily add a time-calibration trace. This will simply be done with a special ac voltage source deflecting one of the galvanometers. The source is accurately calibrated for frequency and thus gives us a continuous check on the film or paper (as to the film-speed constancy). For very accurate work, the timing trace is sometimes made with a square wave.

Why, where and how

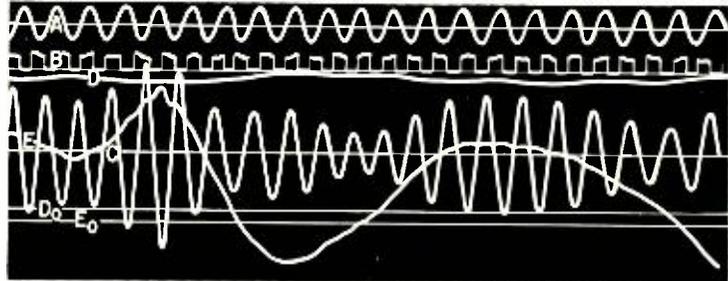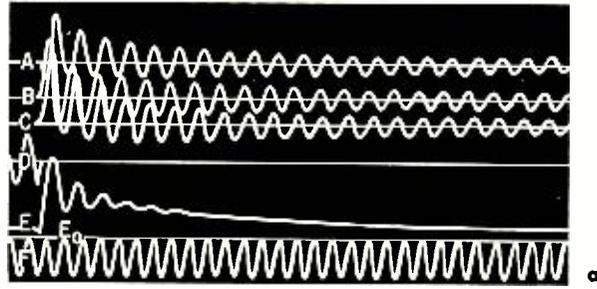Now let's see why, where and how oscillographs are used. Why is easy. We can build oscillographs which can record as many as 48 traces in a single instrument. This is almost impossible with an ordinary oscilloscope, even with electronic switches (getting 10 traces is doing quite well!).



Typical oscillograph traces: a—single-phase short circuit test on an ac generator; b—test on textile loom.

Second, as you know, scopes ("scope" = "seeing") are used most where we wish to *view* the trace, not necessarily record it. We can record from a scope screen with special cameras, but we are limited to either single shots of a few cycles or must use very special CRT's and special high-speed cameras to get a recording of any length. And then we usually end up with a single trace, or at best two or three. Not 48! Third, the oscillograph is used where the scope's extreme bandwidth is not needed or not desirable. We can set very high demands on the oscillograph galvanometers for linearity, but we cannot guarantee the same degree of linearity in scopes, particularly at lower frequencies or dc. These, principally, are the whys of oscillographs.

The next question is *where* do we use them. This is not so easy to answer, because they are used so widely. Generally speaking, oscillographs are used wherever we wish to record a number of signals simultaneously and continuously. We could use industrial recorders if we have a few signals, but not if we have very many. Also indus-

trial recorders generally record much slower variations than oscillographs.

We use oscillographs where the records must be simultaneous, where we must read data from a common time base. For example, we would use an oscillograph when flight-testing an aircraft or missile to record strain-gauge readings. The record gives a comprehensive picture of the strains the craft is subjected to.

Oscillographs are used when testing large circuit breakers to see if all the contacts (on three phases) break the current simultaneously, and how fast the current breaks. For example, modern high-speed circuit breakers should cut the arc of interruption in less than three cycles. To check how fast the breaker operates after we push the button, one trace is set up to show the current from the pushbutton. To check for bounce in the contacts and mechanism, the oscillograph is connected to a current source and transducers. In this way many things about a circuit breaker and *when* they happened in relation to time and each other can be studied.

This is a prime spot for the oscillograph. The low-frequency response and low impedance of galvanometers is of no consequence here, yet we would barely be able to see the event on a scope, let alone measure the variables!

An oscillograph can be set up to measure the flutter of aircraft trim tabs, the strain in the control cables, the temperatures of engine exhausts and the acceleration reached in a pull-out simultaneously. All these things can best be recorded with this instrument. These are just examples; we use them many other places where a large number of many variables must be recorded simultaneously.

We cannot do much about the galvanometer's low frequency response, although we can improve matters by using electronic amplification and the

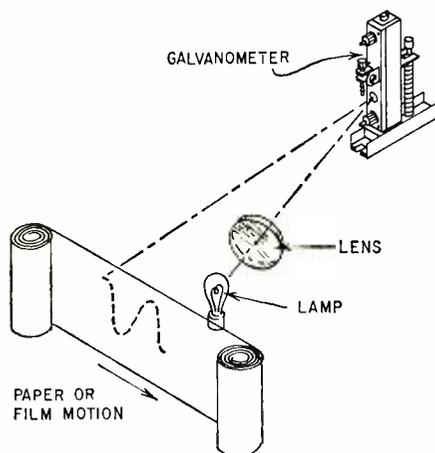


Fig. 1—Basic principle of the oscillograph.

"stiffest" galvanometers available. But it is easy to get around the low impedance with impedance-matching transformers or such electronic aids as cathode followers. And for remote recording, oscillographs are often used in conjunction with a "carrier" system where the variables modulate an audio carrier of a few thousand cycles, which is demodulated at the receiving end and fed to the galvanometer.

These are some of the how's about oscillograph applications. Now let's talk about some special disadvantages of oscillographs, and how a very modern instrument gets around these. First, the film or photosensitive paper used must be developed and fixed. This takes time, and we must sometimes wait a while before working with the records. Second, recording the time marker takes up a useful galvanometer, and a special device can be included to avoid this and keep one more active instrument available. Third, when we draw parallel lines on our record to mark off time points, for comparison of events, we may make errors by drawing the lines slightly at a slant. So if such lines can be recorded on the paper as we record the traces, another hazard is eliminated.

The Minneapolis Honeywell Visicorder (Photo D) is a modern instrument


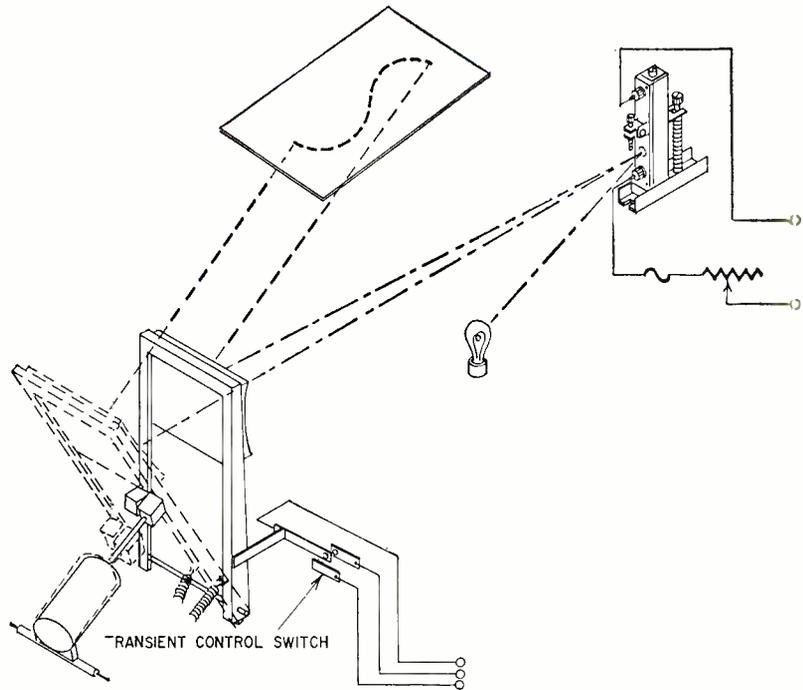
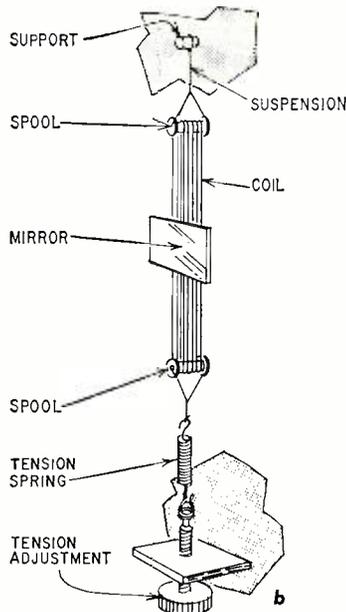


Fig. 2 (above)—Time base for single shots is obtained by moving the light beam at 90° from galvanometer deflection with a second mirror.

Fig. 3 (below)—Two types of galvanometers used in oscillographs: a—string; b—coil.

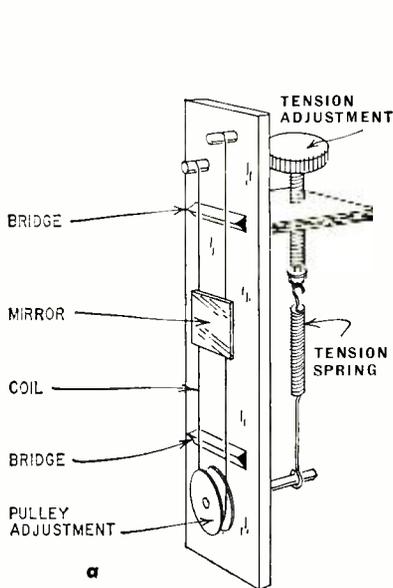

variations, connect a thermocouple directly to the galvanometer. To record pressures use a transducer that converts pressure into voltage. This could be a potentiometer moved by a Bourdon tube, a bellows (Fig. 5).

For example, to measure the contact opening time of the circuit breaker, connect an actual voltage and current that would be encountered in the field to the breaker from some high-voltage high-current source. The breaker has built-in current transformers to provide the instrument current used for the breaker (usually 5 amps at nominal rating). This can again be stepped down with an auxiliary transformer to the galvanometer rating. Thus the record shows the normal 60-cycle current through the breaker, and the instant

that gets around all these things. It uses a paper that is sensitive to ultraviolet light and immediately shows a trace on the paper recorder. This requires special optical systems, because ultraviolet does not normally pass through glass very well. Not only is the record immediately available, but a special shutter operated by the drive records a timing trace on the edge of the paper. In addition, thin timing lines, coinciding with the start of the time marks, are recorded all the way across the paper.

Setting up a test

Oscillographs are extremely simple

to use. We must have a source of low voltage representing the variable to be measured for direct connection to the galvanometer, a variable-gain amplifier, or we must use attenuators or impedance-matching devices. Other than that, any variable voltage which represents some factor we wish to measure and within the specifications of the galvanometers is the only requirement. Thus, to record position, we might use a voltage source and a potentiometer connected to the moving object.

The variable voltage from the potentiometer wiper would be the voltage to be recorded. For strain gauges use a bridge circuit. To measure temperature

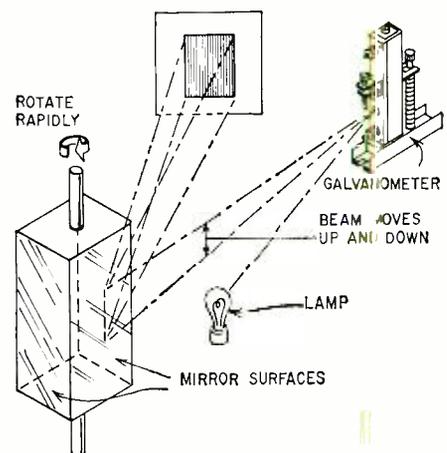


Fig. 4—Rotating mirror provides pseudo time base for viewing the trace from the galvanometer.

it ceases is the break point (Fig. 5-d). The galvanometers must be selected for the particular job. Contact bounce on the circuit breaker would be determined from the operating shaft of each section, with a potentiometer connected to the shaft, which would show then if the shaft vibrated after opening. (Most large circuit breakers rotate their contacts.) Or you could make a separate test with an accelerometer attached to the contact blade to show any reversal in movement of the blade. Remember, an oscillograph is simply a sensitive galvanometer that records whatever it measures. Use it as you would any other sensitive meter with low impedance and limited frequency response.

The oscillograph at present is an indispensable instrument for such applications as missile and aircraft tests, power-line tests, recording water levels in rivers, recording strains in giant dams or the twists in the frame of a locomotive as it rushes through a switch or poor section of rail. It is used in development of automobile bodies and frames, as a delicate instrument to record physiological variables (in EEG and EKG) and to record the shock waves from atomic bombs. It is something in the way of instrumentation you are bound to meet up with at some time or other. END

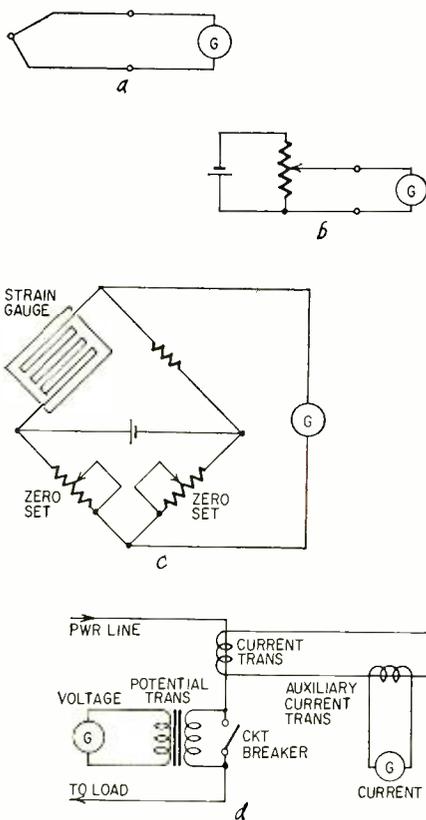


Fig. 5—Simple connections for oscillograph galvanometers: a—direct-connected thermocouple; b—position indicator with potentiometer; c—strain gauge connected in a bridge circuit; d—connections for current and voltage in a circuit-breaker test.

POLYOPTIC SEALING MAKES BETTER TUBES

A NEW, yet old method of joining the two glass parts of a vacuum tube (envelope and stem mount) has been demonstrated by the Chatham Electronics Division of Tung-Sol. It is based on the principle that if two glass surfaces are highly polished and mated they will hold together because of molecular attraction. Originally, some attempts were made to make airtight seals by using such accurately polished



and mated surfaces that true molecular bonding resulted.

The story goes that this process was first used by the French underground during World War II. They needed tubes for their radio equipment and had to make their own. However, gas for their Bunsen burners was difficult to get and they were forced to try optical polishing and mating to seal the parts of their tube envelope.

The process Tung-Sol has been working with was developed and is now used by the Compagnie Generale de Telegraphie sans Fil (CSF) of France. It is called polyoptic sealing. Briefly, the new technique calls for preparing the mating surfaces of the tube envelope and stem mount by optical polishing so the tube can be evacuated before the seal is made. This requires a polishing accuracy of a few millionths of an inch.

One step in the polishing process is shown in the first photo. Here the bulb is being given the precise contour it needs so it will mate with the polished button stem of the tube. It is done by applying the bulb to a rotating abrasive sphere coated with polishing rouge. This step is preceded by several grinding and lapping operations. The button stem is subjected to a series of similar steps.

After both bulb and stem have been polished they are checked under a monochromatic helium light to determine the exactness of the fit between

the mating surfaces of the bulb and stem. If inspection reveals unacceptable parts, they are returned for re-grinding and polishing. The inspection process consists of placing the surface to be checked against a standard and placing the pair under the helium light (see photo). Fringe patterns which reveal any defects appear as pink stripes (the color of helium light) separated by black bands (where the light waves interfere because of foreign particles between mating surfaces or surface irregularities).

After passing inspection, the two parts are joined and attached to an evacuation pump. Then the base is heat-sealed to the shell, the tube is sealed and the process completed.

The advantages of the process, though costly (In production, industrial tubes made by this process will cost 15% more than their conventional equivalents) are best demonstrated with a short set of figures: In tests conducted for the Signal Corps two groups of type 1288 thyratrons were made—38 by the polyoptic process and 50 by standard production techniques. Then both groups were life-tested. After 2,000 hours none of the standard-type tubes were working, but more than 55% of the polyoptic-sealed tubes were



still operating. Also, the yield of good tubes is higher under the polyoptic process—85% for polyoptic, only 60% for conventional types.

Based on the satisfactory results of the tests, Tung-Sol is continuing its study of polyoptic sealing. The results of the study are expected to reveal whether volume production using the polyoptic technique is warranted. END

SERVOMECHANISMS... how they work

Electronic circuits can control which way and how far an electric motor will turn or a piston will move



By E. L. SAFFORD, JR.*

SERVOMECHANISMS are electronic circuits that make electric motors run, open or close valves to control the amount of oil or air fed to a piston and serve in a myriad of other control and indicator applications. However, in this article we will deal only with motors and pistons that are connected to a load we want to move or position in some particular way.

The electronic circuit we use may be nothing more than a potentiometer, a couple of relays and a tube or two. Or it may be an amplifier which is just as complex as hi-fi or public-address types.

In audio work we want an amplifier to have little or no distortion. We also want plenty of power so we get excellent linearity when we operate at low power. And we want feedback to correct the response.

An ac servo amplifier has about the same requirements. It must furnish enough power to drive a motor or valve. It must have a linear response over a range of very low frequencies since its input may be only a few cycles per second. It must also have feedback, but with servos this feedback is a little different. It must indicate the *position* or *speed* of the motor gear-train output shaft or piston shaft, and not be a portion of the signal being amplified.

The input signal to a servo amplifier must identify the direction we want the motor or piston output shaft to move in and tell it how far to move. We do this with a dc signal by letting the polarity specify the direction and the amount of the voltage control the amount of movement. For an ac signal we let the phase, with respect to a reference voltage, tell the motor or piston which way to move, and again let the amount of voltage tell how far the output shaft is to be moved.

Fig. 1 shows how a simple linear potentiometer can be connected to a pair of batteries to form a bridge circuit. When the wiper is in the center, the voltage across terminals A and B is zero. If the wiper is moved to the right, A becomes negative with respect to B. If the wiper is moved to the left,

A becomes positive with respect to B. This could be an input circuit for a very simple motor control unit as shown in Fig. 2. We have not called this a servo, since it has no feedback.

With the wiper centered as shown there is no voltage on the grids of the tubes. R1 is set so RY1 remains open. R2 is set so RY2 just closes. Since both motor leads are connected to the positive battery terminal, it does not run. Now we move the wiper clockwise. The bridge is unbalanced and a positive voltage is placed on the grids. V2 is not affected since it is already conducting and its relay remains energized. V1 starts to conduct and closes relay RY1. This connects motor lead A to the negative line. Lead B is connected to the positive supply so the motor runs clockwise. It will keep running till we move the wiper back to its center position.

If we move the wiper counterclockwise, a negative voltage appears on the tube grids. V1 is unaffected (it is already cut off) but V2 stops conducting. This makes RY2 open and connect motor lead B to the negative line. Since

want in any kind of positioning servo-mechanism.

If we move the input wiper to the right, a positive voltage is applied to the tube grids. V1 conducts, closing RY1. The motor runs and turns the feedback wiper in the direction that brings it nearer the positive battery terminal. As soon as this wiper has moved the same distance from center that the input wiper was turned, the voltage difference between the two wipers is zero. The relay opens and the motor stops.

If we center the input wiper again, it is nearer the negative battery terminal than the feedback wiper. Now a negative voltage with respect to ground appears on the tube grids. This makes V2 stop conducting, and RY2 opens. Now the motor runs in the opposite direction until the feedback wiper reaches the center position and no voltage difference exists. The motor would, of course, have a gear train between its shaft and the object we want to position. This may be a rotary antenna, a hydraulic valve, sonar transducer or any similar device. The feedback pot would be attached to the shaft the *object* is connected to

The ac servo

Fig. 4 reveals the similarity between an ordinary audio amplifier and a servo amplifier. The values shown are only indicative of those in use and not the exact values used in any one amplifier. The idea here is to control the motion

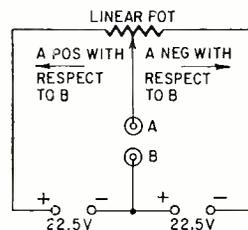


Fig. 1—Linear potentiometer and two batteries form a balanced bridge.

motor lead A is connected to the positive supply, the motor runs counterclockwise. Again, it keeps running until we center the wiper.

Position control

Fig. 3 shows how to add a second potentiometer, like the first, so it furnishes a position feedback signal to the tube grids. Now if we move the input wiper 10° clockwise, the motor output shaft also moves 10° clockwise and then stops. In other words, we can make the output shaft position correspond to the input shaft position at all times. This is basically what we

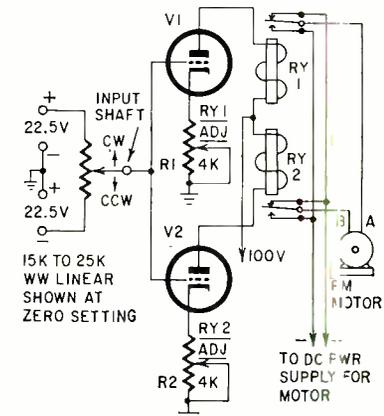


Fig. 2—Simple motor-control circuit.

* Author: *Model Radio Control*, Gernsback Library.

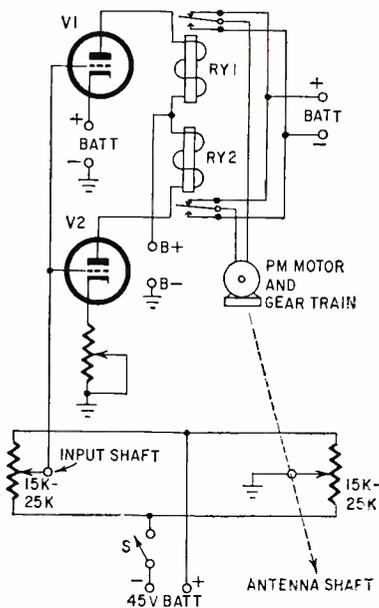


Fig. 3—Motor-control circuit with a position feedback potentiometer.

of a two-phase induction motor by controlling the phase to one winding.

If we use a synchro transformer for the input, we can provide a 60-cycle signal which can be in phase or out-of-phase with the line voltage. We can control the amount of ac voltage to the input tube grid by how far we move the input shaft from its zero position.

Note that we also have a feedback signal which will be provided by the same kind of device. The armature of the feedback synchro turns as the motor output shaft turns.

Here is how it works: With input and feedback synchros properly set in position, there is no signal to the input

tube grid. The motor has only its reference winding connected to the line and does not run. If we turn the input synchro shaft a little to the right, a 60-cycle signal appears on the tube grid. This is amplified, shifted in phase slightly (by the phasing network), amplified again by the power stages and applied to the second motor winding. The phase of this signal leads the reference by about 90° and the motor runs clockwise.

As the motor runs, it turns the feedback synchro and, if we have set it correctly, it will produce a signal exactly out of phase with the input. Thus when their voltages are the same, they cancel and the motor stops running since the amplifier no longer applies any voltage to it. The output shaft has been moved to the new position.

If we move the input shaft back to its center position, its signal vanishes. The signal now applied to the input tube is from the feedback synchro and is 180° out of phase with the one we used a moment ago. When this signal is amplified and fed to the motor winding, it is a voltage whose phase is lagging the reference. Thus the motor runs in the direction that moves the feedback synchro armature back to its zero position. The motor stops when the signal to the input tube vanishes.

The hydraulic system

Fig. 5 shows the basic elements of an electrohydraulic servo system. Examine the valve-piston arrangement first. The valve consists of a rod with three metal wheellike sections fastened or cut as a part of it—C, D, and E. The rod

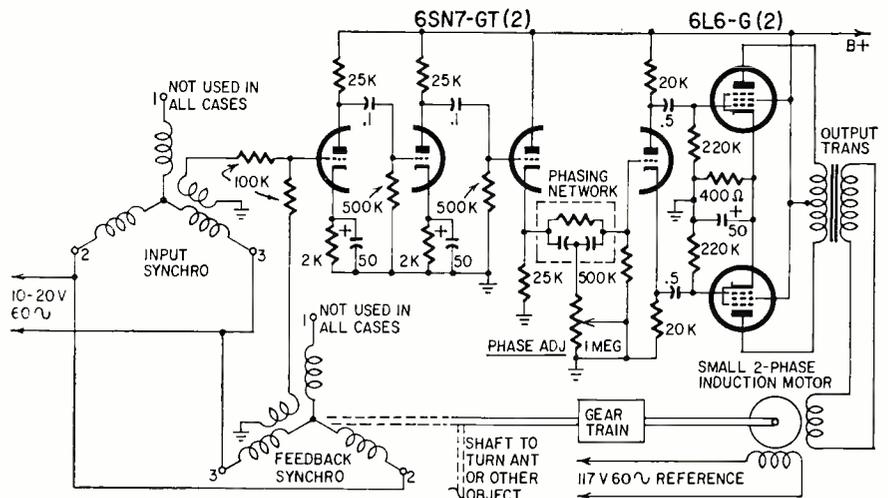


Fig. 4—A representative ac servo.


is held in place in the metal block by two centering springs. It can move up or down like a solenoid when either winding has current flowing through it.

Note that, as shown, the center part, E exactly covers the input hole where a pump, for example, is trying to force oil into the valve. C and D exactly cover the two exhaust lines so that oil in the piston cylinder cannot get out.

Now suppose the upper winding is energized, pulling the rod up. E opens the input line from the pump and also opens input B to the piston. Oil flows into the bottom of the cylinder and cannot get out since D still covers exhaust line B.

However, part C has uncovered exhaust line A and, as the oil flows into the bottom of the piston, the piston moves up, forcing oil from the top part of its cylinder out through exhaust line A. When the piston has moved enough to turn the feedback synchro enough to cancel the input signal, current to the top winding stops. The valve recenters and the piston stops moving. This same action takes place if the bottom winding is energized and the piston will move in the opposite direction.

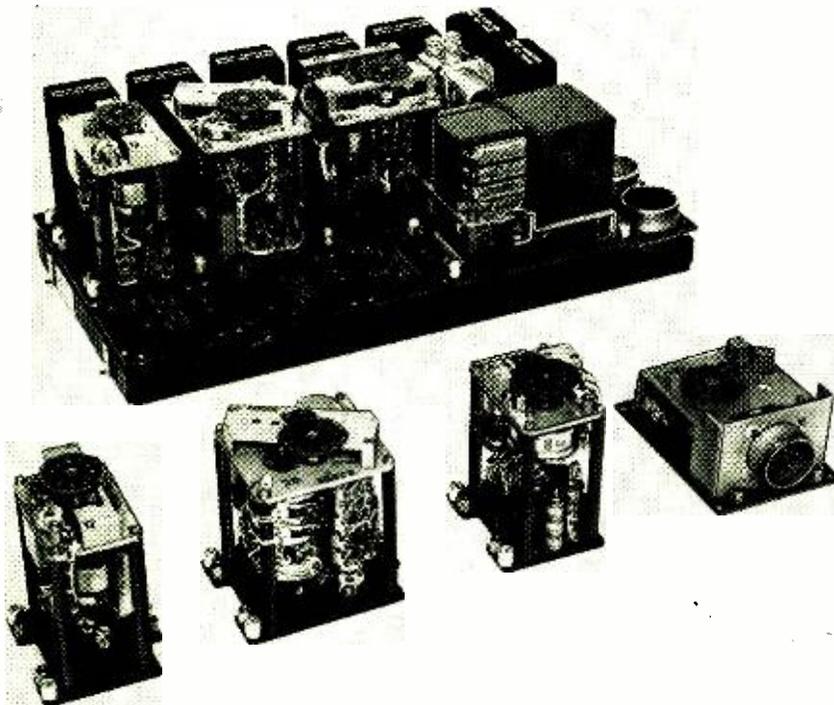Now let's see how we can energize one winding or the other by changing



Eight servos are used in this Air Data Computer.

Servomechanisms Inc.

the phase of the input signal as we did with the ac servo. A new output stage is required. The rest of the amplifier is the same as in Fig. 4 except that the cathode follower and phase inverter are replaced by V3 and transformer T2 of Fig. 5.

V1 and V2 in Fig. 5 are biased class-B and 117 volts ac is applied to their plates. T3 and T4 are small separate transformers.

Here's how these work: Since V1 and



Bellows-Air

Bellows Air Motor is a typical servo-controlled device.

V2 are biased class-B, normally no current flows in either output transformer. If we apply an input signal which is in phase with the plate reference, making V1's grid positive at the

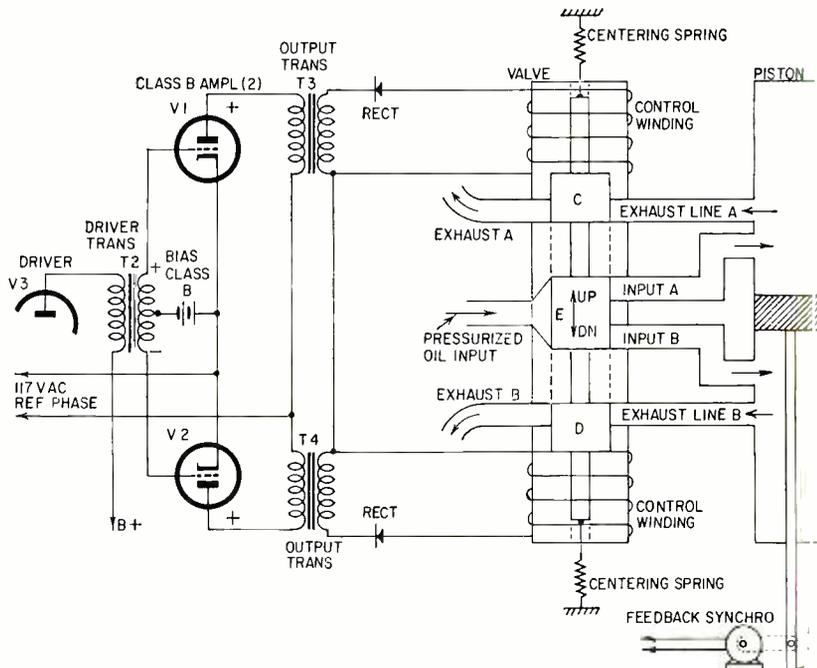


Fig. 5—Representative hydraulic servo.

same time as its plate, V1 conducts. The signal goes through T3, is rectified and causes a current to flow in the upper valve winding. V2 does not conduct with this signal because when its plate is positive, the grid is negative and, when its grid is positive, its plate is negative.

When we change the phase of the

input signal by 180°, V1 does not conduct but V2 will, since now its grid will be positive when its plate is. The lower valve winding will now receive current.

Remember, only two basic servo types have been discussed. There are many others. Some of them will be described in future issues. END

NEW PORTABLE TIME STANDARD

ZENITH Radio Corp. has announced the world's first portable secondary time standard, the WWV-1. This self-powered instrument is accurate to approximately ± 16 seconds per year.

The device contains a transistor receiver designed to pick up WWV or other sources of a one-second "tick." The receiver may be set at any of three switch-selected, crystal-controlled frequencies—2.5, 5 and 10 mc. Its output is fed to a decoder that removes all information except the one-second tick. The decoder includes circuitry to prevent false signals from disturbing the clock.

The tick is applied to a generator which supplies pulses of the required amplitude and duration to operate the clock.



With a set of contacts using the clock's hands and a special circuit board, the unit can switch external devices on or off at 15-, 30-, 45- and 60-second intervals. Longer intervals range from five minutes to an hour or any multiple of five minutes. The time combination desired is selected by inserting special shorting plugs into jacks on the panel.

The clock used in the standard was developed by the Hamilton Watch Co., Lancaster, Pa. Its balance wheel operates a set of contacts that pulse the timepiece twice per second. According to the manufacturer, it is waterproof, shock-resistant and not affected by extremes of temperature and altitude.

An audio amplifier and speaker provide an aural check of receiver performance, as well as a means of obtaining WWV voice and code signals.

Two standard batteries will operate the radio for several months. The clock runs as long as one year on a single, separate 1.5-volt battery.

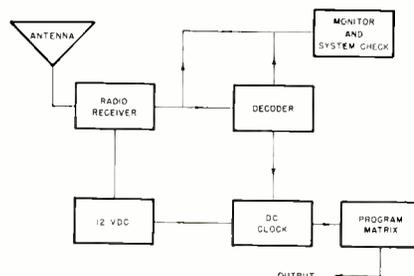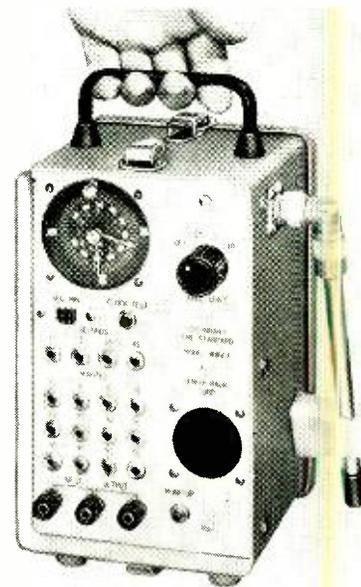Some of the uses for the WWV-1, as suggested by J. E. Brown, vice presi-



dent in charge of engineering, are to link instruments with metering equipment to record flow, viscosity, and temperature of oil or gas moving through pipelines. Several clocks could be used to simultaneously trigger a number of measuring or recording devices such as scintillation counters or cosmic ray measuring equipment at widely scattered locations. END

Servicing the

Horizontal Output Stage

By R. D. JACQUES

A professional full-time service technician tells how the horizontal output circuit works and how he goes about fixing it

LAST time we talked about horizontal oscillators (April, page 55). This month, let's work over horizontal output stage circuits. We may not get 'em all in, but we'll try.

The horizontal output stage of a TV receiver has two important functions. It generates the sawtooth currents that sweep the electron beam across the face of the picture tube, and it supplies high voltage for the picture tube. These happen simultaneously, but to make things a bit clearer we'll take them one at a time.

The horizontal output tube is always a power pentode, with a hefty current rating. It is biased to operate class-B or class-C, so that plate current flows for only a small part of the input cycle. The drive voltage (input signal) from the oscillator has a special shape. It is not a sawtooth, but a trapezoid (Fig. 1). This combination of a sawtooth and square wave is necessary because it causes a pure sawtooth wave of current to flow through the deflection yoke windings. This gives us the linear deflection we've got to have.

The plate load for this tube is a transformer which is coupled to the deflection yoke windings. The yoke is the load for the transformer secondary and the combination of the two (transformer and yoke) makes up the total load for the output tube. When the output tube is conducting, a pulse of current flows through the primary winding of the transformer. This generates a similar pulse in the secondary. Fig. 2 shows the waveform of the current pulse in the yoke. Notice the point on the waveform marked "output tube cutoff"? Right there, the peak of the sawtooth portion has been reached and the grid voltage has dropped below the operating point—the tube is cut off and plate current stops flowing.

The pulse stores energy in the form of a magnetic field in the transformer secondary. When the output tube is

cut off, the field collapses back through the winding, inducing another pulse of current *in the same direction*. Thus, when the pulse was applied, the magnetic field created in the yoke started the electron beam in the CRT moving from left to right (from a theoretical resting position in the center of the screen). When it reached the right edge, the tube stopped conducting. The resultant collapse of the field generated a sharp pulse in the windings that snapped the beam all the way across the tube. Then, the field still present kept the beam moving from left to right, until it reached the center again.

At this time the output tube takes over again and begins to conduct. The next pulse moves the beam the rest of the way across the screen. The combination of these two actions gives us a linear sweep.

When the stored energy in the transformer collapses, it induces a pulse of current in the primary. The rate of change of the current during this time is very fast and causes a high (pulse) current to flow in the primary. The pulse induces a very high voltage in the primary (it acts as an autotransformer) which is applied to the high-voltage rectifier, as in Fig. 3. The total time for a complete cycle is 63 μ sec. Of this, 56

back time) the collapse of the field shock-excites the whole system into oscillation. For reasons which we will get to in a moment, the whole system is designed to be naturally resonant at the fundamental frequency of the retrace time—70 to 72 kc.

To obtain the sweep we get these oscillations. We can't get rid of them so we do something useful with them. First, we get a rapid retrace. And second, by making the whole system resonant at the retrace frequency, we increase its efficiency tremendously and get a much larger pulse of current in the primary to be made into high voltage! If we let the oscillations die out normally, it would upset the sweep and the waveform would look something like

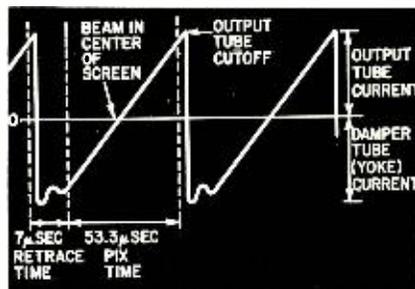


Fig. 2—Sawtooth current through yoke developed by the trapezoidal voltage.

μ sec is used for the sweep and 7 μ sec for retrace. The rest goes into the front and back porches. The inductive kick used to generate the pulse of high voltage has led to the name of *flyback* for these transformers.

Flyback-yoke system

The transformer-yoke system has inductance and, like any circuit having inductance, it also has a natural resonant frequency. During retrace (fly-

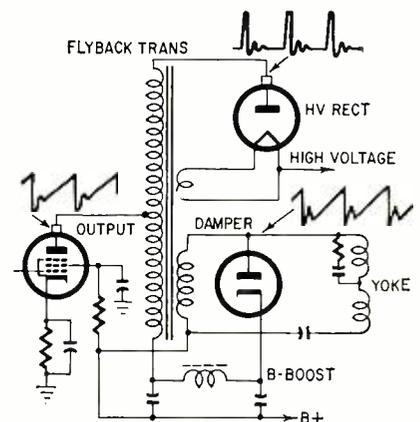


Fig. 3—How pulse from the plate of the horizontal output tube is applied to the plate of the high-voltage rectifier.

Fig. 4. This would cause ringing on the left side of the raster.

To get rid of the unwanted portion of these oscillations, we connect a half-wave rectifier across the yoke, as in Fig. 5. Now, during retrace, the pulse makes the cathode of this rectifier (the damper tube) positive, the tube does not conduct and, in effect, is not even there! After the pulse passes the zero line, it changes polarity. The next half-cycle applies a positive voltage to the plate of the damper, and it conducts heavily, shorting out the undesired halves of the pulses. This damps out the ringing and leaves us with an almost perfectly linear sweep.

So there's your circuit action. The

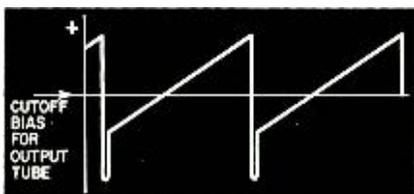


Fig. 1—Trapezoidal voltage on grid of horizontal output tube.

oscillator drives the output tube which in turn drives a tuned circuit, the flyback-yoke combination. You know what happens when a tuned circuit is thrown out of resonance—there's a drop in the stage's output. So, whenever we replace a component in the flyback or yoke circuit, we must use a replacement that will restore the whole circuit to its original resonant condition! This is the reason for using exact-duplicate yokes, flybacks, etc.

The most important sections of the circuit are the components that determine resonance—the flyback, yoke, and any capacitors which may be connected in the circuits. The high voltage generation is actually almost incidental. We can get high voltage by simply winding on more wire "above" the output tube plate, so we do!

The same thing applies to the boost voltage. When the damper tube conducts it acts like any half-wave rectifier and a positive voltage appears on its cathode. But the way the damper is set up, with the B-plus applied to its plate, the added voltage appears in series with the B-plus. This gives us a source of higher voltage (the boost voltage) used to furnish plate voltage for the vertical and horizontal output stages.

To get a dc voltage from the high-voltage pulse, we must rectify it. A special rectifier, with very wide spacing between its plate and filament, is used to prevent flashover. The filament must be above ground, so it is powered by wrapping a turn or two of wire (exceedingly well insulated wire!) around the core of the flyback. Output is taken from the filament, sometimes through a filter consisting of a large resistor and a 500- μ f capacitor. Many sets use the inherent capacitance between the conductive graphite (Aquadag) coating on the picture tube and the chassis as this capacitor.

Three flyback circuits

That's about all we need on the basic circuit. Now let's look at the three basic circuits used in commercial TV sets. They differ only in the yoke connections and you'll have to examine the schematic to see just which one you have.

1. The transformer circuit uses a separate secondary winding to drive the yoke (Fig. 6-a). B-plus is fed into the flyback through its secondary and the damper tube, and the high rf (the spike of voltage from the flyback action) is applied to the damper's plate. Boost voltage is developed at the damper's cathode and fed back through the linearity-coil circuit and the transformer's primary to the plate of the output tube.

2. The autotransformer circuit has only a single winding, and drives the yoke by connecting it across taps on that winding. B-plus is fed to the plate of the damper through the linearity coil. Boost voltage, of course, appears at the damper cathode and feeds the output tube plate through the flyback winding (Fig. 6-b).

3. The direct-drive circuit uses a simpler flyback that consists of only the plate and high-voltage winding as shown in Fig. 6-c. The yoke is connected in series at the lower end, back to the damper cathode and the boost voltage. Most of these can be identified by the flyback, which does not have an iron core, but either a plastic or paper form. You've noticed, of course, the identical nature of the high-voltage section of the winding on all of these circuits—all are autotransformers with the plate of the high-voltage rectifier connected to the top of the total winding.

Servicing tricks

Servicing any receiver, radio or TV should be handled back to front. Start at the output (speaker or picture tube) and work toward the antenna, repairing all troubles as you go. Servicing horizontal output stages demands a different approach. First, isolate the whole circuit in your mind—oscillator, output tube, flyback, damper, yoke and high-voltage rectifier. Now, think of this circuit as if it were a radio transmitter. Transmitter servicing is entirely different. We start with an oscillator, feed it into a power amplifier through a tuned circuit, then to an antenna. In this case, our "antenna" or load, is the yoke and the high-voltage rectifier, but the basic operation is just the same. So if we can think of the circuit as a

transmitter, it'll be easier to service!

We fixed the oscillator last time. From now on we'll assume it is working perfectly and any troubles lie in the output stage. Testing in this circuit is a process of elimination. You can use any of several places as your starting point. But practically everyone makes a routine examination of the set, noting which tubes are lit, checking the high-voltage fuse, measuring the B-plus voltage and checking to see just what symptoms the set shows. Once you discover there is no high voltage, you start eliminating the various things which could cause it.

The most common causes should be checked first—the tubes. All should be replaced, checking the set each time. A good order of replacement is: high-voltage rectifier, damper, horizontal output and oscillator. If this does not bring the raster back, leave the good tubes in until you're finished and proceed with the rest of the tests.

First, see if you can draw an arc from the plate of the high-voltage rectifier with the blade of a screwdriver. (I shouldn't have to tell you that the

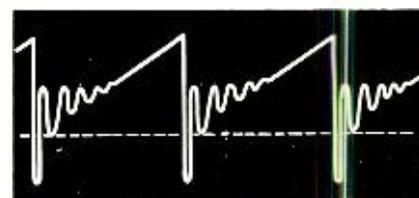


Fig. 4—Natural shape of waveform in yoke and flyback without a damper tube.

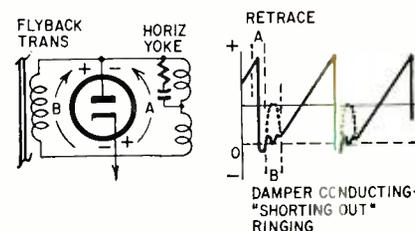


Fig. 5—Polarity of flyback pulse during retrace makes damper cathode positive so damper does not conduct. When ringing voltage starts, the damper cathode is negative and the tube conducts heavily, shorting out the ringing.

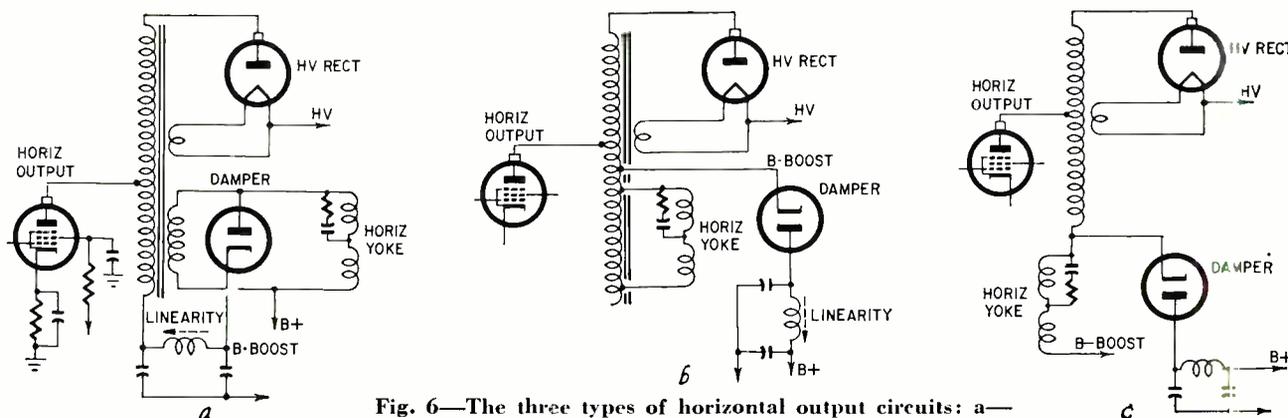


Fig. 6—The three types of horizontal output circuits: a—standard transformer; b—autotransformer; c—direct drive.

TELEVISION

screwdriver must be insulated. Anyway, you'll remember it the second time!) Normal arc here is about $\frac{3}{4}$ inch long and a bright blue. If the output tube plate cap is exposed, you should get a very short arc there. No arc at either plate means that there is no high-voltage pulse reaching the rectifier plate. At this point, disconnect the yoke and repeat the test. If a below-normal arc appears at the high-voltage rectifier plate, the yoke may be defective. Check it for shorts and leaky balancing capacitor-resistor networks. If possible, substitute another yoke of the same inductance (the horizontal section is all you need) and see if the high voltage comes up to normal. If it does, the yoke is definitely bad. If not, the trouble may be in the flyback or the output tube.

Weak output

In many of the newer sets, test points are easily accessible—oscillator plate, output tube grid and screen, etc. Measure voltages at these points and check them against the schematic. The scope is a valuable instrument for checking this circuit. By placing its probe *close to but not touching* the plate lead of the output tube you can see if there is any pulse voltage there and after a while get a pretty good rough idea of its normal amplitude.

Weak output may be caused by low drive, open coupling capacitors or incorrectly set drive adjustments. This can be quickly checked with the scope and a voltage calibrator. Measure the peak-to-peak amplitude of the drive signal at the output tube grid. For the

old 50° sets it should be about 50 volts, 65 volts for 70° sets, 75 volts for 90° and 90–105 volts for the 110° sets.

Measure the screen voltage of the output tube. A shorted tube, replaced some time before, may have damaged the screen resistor. Normal screen voltages for common tube types are: 6CD6, 175 volts; 6AU5, 6AV5, 6BQ6, 6CU6, 6DQ6, 200 volts, and the 6BG6, 350 volts. These are maximum values. In TV sets you'll find variations below this figure, but not too many. Screen voltage should never be more than the amount given or screen dissipation will be too large.

Cathode voltage should be checked if a protective resistor is used. Many circuits simply ground the cathode, but others use a small resistor (100–150 ohms) in the cathode to protect the tube against drive failure. Remember the radio transmitter? These tubes are just like final amplifiers—if operated without an input signal (drive), plate currents reach excessive heights and destroy the tube in a short while. So if you see the plate of the horizontal output tube turning red, turn the set off quick and check to see why the output tube isn't getting any drive signal!

Special testers

Several test instruments are made solely for checking flyback-yoke systems and all are worth their cost. Some are signal substitutes that provide signals which can be used on the output tube grid in place of the set's horizontal oscillator. Also, with the aid of a horizontal output tube in the in-

strument, they will drive the flyback and yoke without the set's output tube. This test tells you definitely whether there is trouble in the flyback.

Others test components out of the circuit. They detect shorted turns in flybacks and yokes by using the resonant-circuit principle we discussed earlier. (A winding with a shorted turn will not resonate at its proper frequency, and its output will be very low.)

One instrument can even be connected directly into the horizontal output circuit and reads all quantities concerned with it. Resistance readings can be taken in the B-plus and boost circuits, screen resistors and cathode resistors measured, and all voltages checked in actual operation, by merely turning switches.

Finally, by using test adapters or by opening the cathode circuit, the plate current of the output tube should be measured. This is the most important reading as far as tube life is concerned. Maximum plate currents should be 6AU5, 6AV5, 6BQ6, 6CU6, 6BG6—100 ma; 6DQ6—140 ma, and 6CD6—170 ma. If plate current is higher, tube life will be short indeed! Too-high plate current can be caused by incorrect screen voltage, low drive on the grid, improper bias in the cathode (if used) or by a severe mismatch in the yoke circuit. Leaky or open screen or cathode bypasses can also cause troubles. Whenever any major repairs are made to the flyback system, always measure the plate current of the horizontal output tube, too much means an inevitable callback! END

Remember—Check the Tubes

This set hurt my ego. I had reached that lofty stage of my career where I considered the tiresome routine of checking all tubes in troubleshooting


just a little superfluous. For a long time I had been making satisfactory, even spectacular, diagnoses by the mere use of my five senses and past years of experience. I could tell at a glance at the screen whether the tubes were good or not.

On this particular service call, I was confronted by a well banged up Sparton model 5107, looking a little disrobed with its back off and its high-voltage cage bared, left in that condition by a friendly neighbor the night before. This technically minded neighbor's opinion was that the flyback transformer was shot and, since it would take, among other things, a soldering iron to replace it, he had bowed out. There was no raster on the screen, but there was good sound. The small arc drawn from the cap of one of the 6BQ6's was about the same size as the one drawn from the 1B3, which fooled me into thinking the horizontal oscillator was working satisfactorily. I replaced all the tubes in the horizontal sweep section, and the 5U4, with no success. I examined the flyback as well as I could through its accumulation of sooty dust and finally I reluc-

tantly told the owner that I had to concur with her neighbor's opinion and the set would have to be taken to the shop.

On my bench a tester soon showed that the flyback and yoke were OK, and I began checking voltages. After turning the set on, the 130 volts on the plate of the horizontal oscillator, V23, slowly dropped to 40. I immediately suspected filter capacitor, C91-c, and unhooked it. No luck. There was only one place left to go, the plate of sync stripper V16, since it was tied through an 18,000-ohm resistor to the same capacitor. The voltage here dropped from about 400 when the set was turned on to practically nothing. Removing this tube restored the high voltage with a cheerful crackle. It also cracked my ego.

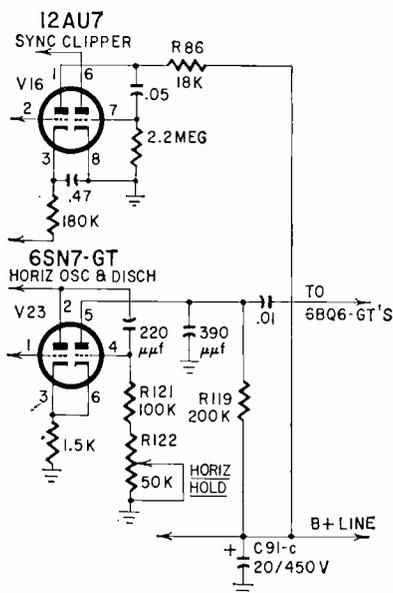I billed the customer for the 12AU7, an 18,000-ohm resistor, a service call and diplomatically discussed the weather instead of the flyback transformer! I also dug out the tube checker and put it back up on the front seat of my service truck, next to the tube caddy. It will be used early and often on future jobs.—*Klemm's Television*



MANY tests can be made on a TV set using only your eyes and powers of observation. For instance, the operating condition of the vertical oscillator and vertical sync stages can be checked out with remarkable accuracy.

Normal action on a TV set's vertical hold control should be familiar to all technicians (and set owners, too, for that matter!). When the hold control is moved in one direction, the picture should roll slowly downward until the blanking bar reaches a point about 2 inches or so from the bottom of the screen. There, it should snap out of sight, and another bar begin rolling down. Turning the control the other way should cause the picture to stand still until the critical point is reached. It should then break out and roll rapidly upward.

Unless these actions are as described, there is a possibility of trouble in the vertical oscillator, even though the set will hold a picture stationary on the screen. For instance, if the picture has no snap when rolling downward and can be rolled slowly upward, the vertical oscillator or sync stages are not working properly and will soon give trouble.

Loss of vertical sync (or weak sync pulses) can account for these symptoms as can weak tubes in the vertical oscillator or sync stages. Low oscillator supply voltages are another cause.

Antenna stacking

I have two TV antennas that I would like to stack. What are the mechanics of the problem?—R. C. J., Chapel Hill, N. C.

Efficient stacking requires stacking bars cut to a half wavelength of the desired channel. The lead-in is connected to the center point of the bars, as in Fig. 1. The length of the bars can be figured from a division of the channel frequency into 300×10^6 , which gives the wavelength in meters. A meter is 39.37 inches. Next, the spacing of the stacking bars must be adjusted to transform the impedance of each antenna to 600 ohms at the lead-in connection

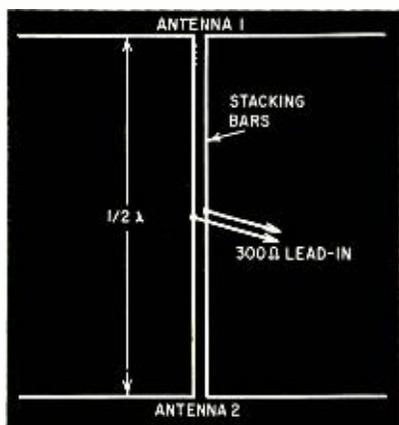


Fig. 1—A simple and effective stacking method is to use half-wave stacking bars, spaced for proper impedance transformation.



point. The two 600-ohm impedances are effectively connected in parallel, matching the 300-ohm lead-in. The spacing can be adjusted most accurately by using a sweep generator, as in Fig. 2.

Width-coil burnout

I found the width coil in a Sentinel 416 TV charred and burned, and replaced it with the type specified for this chassis. Some previous service technician had replaced the flyback with a type designed for the 419 chassis. Now, the width coil gets hot enough to burn your fingers. I've changed all the tubes and checked both flyback and yoke for shorted turns. I put a 4.7-ohm resistor in series with the width coil, and it burned up, too! Putting a meter in series with the width coil, I can read only about 10-μa. The coil controls the width of the picture as it should.—J. I. L., Niagara Falls, N. Y.

That flyback change is the villain here! Checking the specifications of both transformers. I found quite a perceptible difference in the sections of the windings where the width coil is connected. There is at least a 30% difference between the two!

A width coil must be matched to the portion of the flyback it is connected across, just as a yoke must be matched. Your overheating is due to the fact that this mismatched coil has set up a resonance here, and is carrying a very large circulating current! (When you disconnected one end and inserted the meter, it damped the circuit so that it could not oscillate; therefore you read only a harmless 10 μa.)

If the set will operate all right without the width coil, take it out entirely! Any excess width can be controlled by making a width-control sleeve out of foil and sliding it inside the yoke. If you want to replace the coil, a good rule of thumb is this: a width coil should have a minimum inductance equal (roughly) to one-half the inductance of the section of the flyback it is shunting. Maximum inductance should be three to four times this value. You may have to do a little "Cut and Try" engineering here, to find a suitable type. I should say that the inductance of this section in the Sentinel flyback is in the neighborhood of 0.7 to 1.0 millihenry.

Shifted channels

My problem is with a Bendix Model TS17DU TV which developed trouble in the front end. Channel 13 comes in on channel 8, channel 3 is on channel 2, and channel 8 is gone entirely. The uhf channel comes in OK. Can you tell me where to look for the trouble?—J. S. T., St. Petersburg, Fla.

The schematic I have for this model shows a Standard Coil turret tuner. In this tuner, such troubles would not be possible, as each channel has its own individual oscillator coil. Defects in one will not affect others. However, there is one peculiar difficulty, which is not uncommon. If the metal insert in a plastic channel-selector knob becomes loose and turns, you can get some extremely peculiar results!

However, from the symptoms you

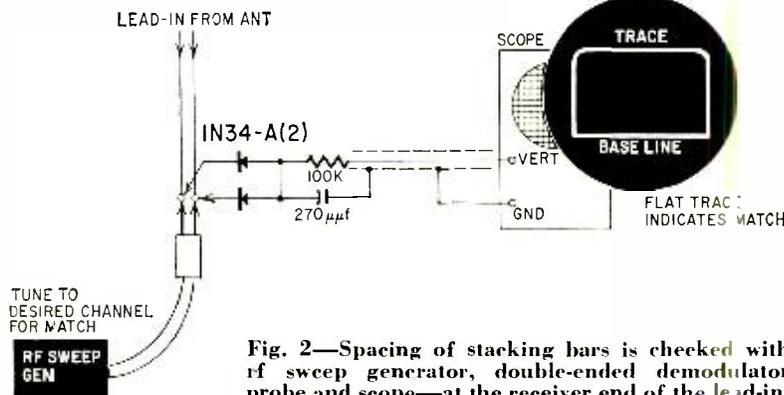


Fig. 2—Spacing of stacking bars is checked with rf sweep generator, double-ended demodulator probe and scope—at the receiver end of the lead-in.

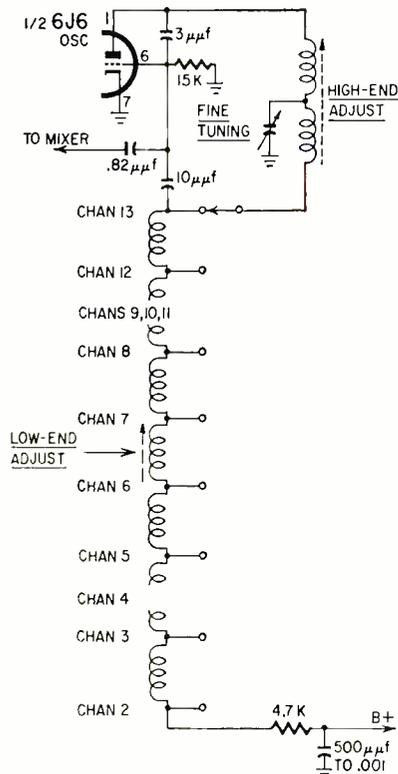


Fig. 3—Schematic of oscillator of incremental-inductance tuner. Switch (shown in channel-13 position) removes the unused coils. Fine-tuning control is effectively between grid and plate.

give, this must be an incremental-inductance tuner. Channel displacement in a Standard Coil tuner is always uniform. Each channel moves two, three, etc. channels one way or the other. You have a 210-mc channel 13 coming in on 180-mc channel 8, and 60-mc channel 3 coming in on 54-mc channel 2.

In the incremental-inductance tuners, the oscillator coils are arranged as shown in Fig. 3. Your local oscillator is far off frequency: 30 mc low on the high band, and 6 mc low on the low band. This would suggest a defective capacitor or coil. For example, if the fine-tuning capacitor were broken mechanically and jammed at maximum capacitance, the result would be somewhat similar. Other troubles might be found in the oscillator wafer of the switch. If the rectangular "drive hole" in the wafer is broken and enlarged, the wafer could get off calibration. A bad contact on the shorting portion of the switch would also leave too much inductance in the circuit (causing the oscillator to work on too low a frequency).

As you can see from the sketch, your coils are arranged in series. The total inductance of the portion left in the circuit determines the frequency of the oscillator. Therefore, either of the troubles mentioned would give you results like you observed—operation on too low a frequency.

Check all of the capacitors in the circuit. The values will be different in your tuner probably, but they will be

in the same locations. Either the 3- μf or the 10- μf capacitor in the grid circuit would affect the frequency. So would the adjustment of the tuning slug in the small coil labeled HIGH-END ADJUST. Check the setting and adjustment of these slugs.

I remember a very mysterious case in a different make TV set. Although the set worked perfectly in the store, when delivered at the house it was completely off on all channels. Investigation disclosed the low-frequency adjustment on channel 6 (an iron slug) had slipped and fallen out of the coil. This threw all channels off adjustment.

Critical horizontal hold

We have a General Electric 14T017 portable TV with a very critical horizontal hold. The set has always been this way, according to the owner. It runs with a black bar down the middle of the picture for a while, then falls completely out of sync.—G. M., Westville, N. Y.

There have been several production changes in this model, and they center around this circuit. The first version used a 5AN8 tube (the triode section) as a horizontal phase detector. Other versions used twin selenium diodes (Figs. 4, 5). If yours has the tube.

While these are the most frequent offenders, don't overlook C256, the .0047- μf capacitor across the stabilizer coil. If this is leaky, it will upset the hold action badly. If you replace it, be sure to use a very-high-grade capacitor which is not temperature-sensitive.

The shaping networks in the grid circuits are also worthy of attention: R256/C255 and their counterparts (not shown) in the remainder of the horizontal oscillator circuit. Measure the resistance of R253, the 5.6-megohm resistor from the plate of the 5AN8 or the left terminal of the comparer diodes, back to the 135-volt line. Quite often we all develop a human failing to check these very large resistors, feeling that they are so big that a little drift won't bother anything. Check them carefully; large though they are, they should be within their tolerance. Too much drift will upset this very sensitive circuit. This is especially true when selenium diodes are used.

Gassy replacements

Recently I changed a 27MP4 metal tube to a 27EP4 picture tube on an RCA 27D382 with a KCS-77C chassis. I used a rebuilt 27EP4 and in less than a month the tube became gassy. I returned the picture tube for another of the same brand, and the same thing

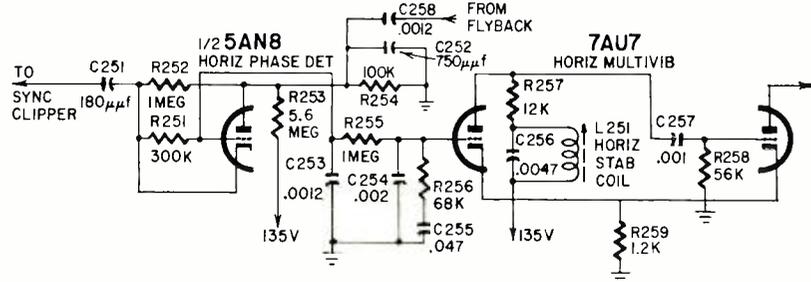


Fig. 4—Horizontal multivibrator with 5AN8 phase detector.

check plate resistor R252, R251, the grid resistor, the coupling capacitor C251, 180 μf , and the coupling resistor, R255, 1 megohm, to the grid of the 7AU7. Short out the horizontal stabilizer coil, L251, and see if the horizontal oscillator will "free-wheel" with any stability at all. (You'll probably have to increase R257, 12,000 ohms, to about 15-18,000 ohms to get it to do this. Replace the original resistor when through testing).

The circuit should be capable of holding a picture almost still, floating slowly across the screen, with the stabilizing coil out. Remove the short from the coil, and adjust the slug for a stable picture. If it will not free-wheel, check C257, .001 μf , for leakage, and the plate and grid resistors in the oscillator circuit. (The 5AN8 tube should have been replaced first, of course!)

If the set uses dual-diode phase comparers, check them or better, replace them, for a test. These units are the most common cause of horizontal instability in this set, in field experience.

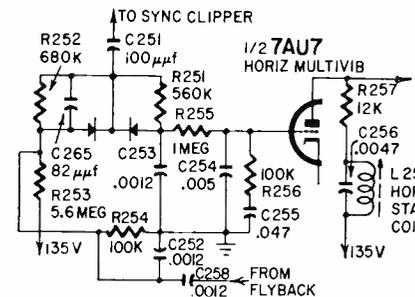


Fig. 5—Multivibrator with dual selenium diodes.

happened again. Is the picture-tube voltage too low?—J. J., Minneapolis, Minn.

The 27EP4 is one of the tube types which sometimes show a neck shadow that may be a little troublesome to work out. If the neck shadow is worked out with the ion trap, the beam will erode the aperture in the first anode and soon gas up the tube. Neck shadow should be worked out by eccentric *shimming* of the focus unit or by use of a thin pair of *centering magnets* mounted just behind the yoke. END

By HAROLD DAVIS

The Gibbons Substituter



Confucius say: Even the needle could be found in the haystack if one knew under what straw to look. Here's a quick way to prove where the needle isn't

I had been a hectic day and now we were relaxing, sipping hot coffee at the greasy spoon. "You know something," he said, "servicing television is simple."

Having just finished sweating the better part of a day on a set, this was indeed news. I just grunted.

"Sure enough. I mean it. It's simple. All you have to do to fix a TV set is find the defective part and replace it." He turned the palms of his hands up in a familiar gesture.

"Yes," I answered, "and I just spent a full day doing that very simple thing."

"Okay, let's get down to business. You're an average technician, why did it take you all day to find a shorted .001 capacitor?"

I got to thinking. It was a good question. Why did it take me all day to find a shorted bypass? After a moment's silence, I answered, "Well, for one thing I got sidetracked into believing the trouble was in another section."

"Ah-h-h!" he exclaimed, raising the proverbial finger. "In other words, you spent a day proving that nothing else was wrong with the set, correct?"

I had to admit that it was.

As we got started home, he said, "Come up to my place next week. I have something I want to show you."

I had been talking with "The Q," Quincy Gibbons, a graduate of Mississippi State in 1919 and one of the most refreshing and unpredictable fellows ever to come out of the Mississippi Delta. At the first opportunity I dropped in on The Q. "Guess you came up to see the gadget?" he inquired.

"I came up to see, period."

There it is

We went into one of the front rooms that contained the usual TV accumulations. "Here's what I wanted you to see," he said, picking up the contraption shown in Fig. 1 and placing it carefully on the table.

"My gosh! what a mess," was the best I could conjure.

"Mess! you say, and you haven't seen the back!" He turned it around, displaying what can be seen in Fig. 2.

"Just wait until you see what this thing can do," he promised.

"There's one thing I'm sure it can't do—work!"

"Ah-h me," he sighed, "to think all famous people have to go through this."

"Pull up you a chair and let me indoctrinate you. You can see that this was originally an RCA portable," he

announced, patting the front of the set. "Here's a block diagram that shows where I tapped into it (Fig. 3)."

"Yes," I confessed, "but Mr. Sarnoff would have a hard time recognizing it now."

"You sure die hard," he complained.

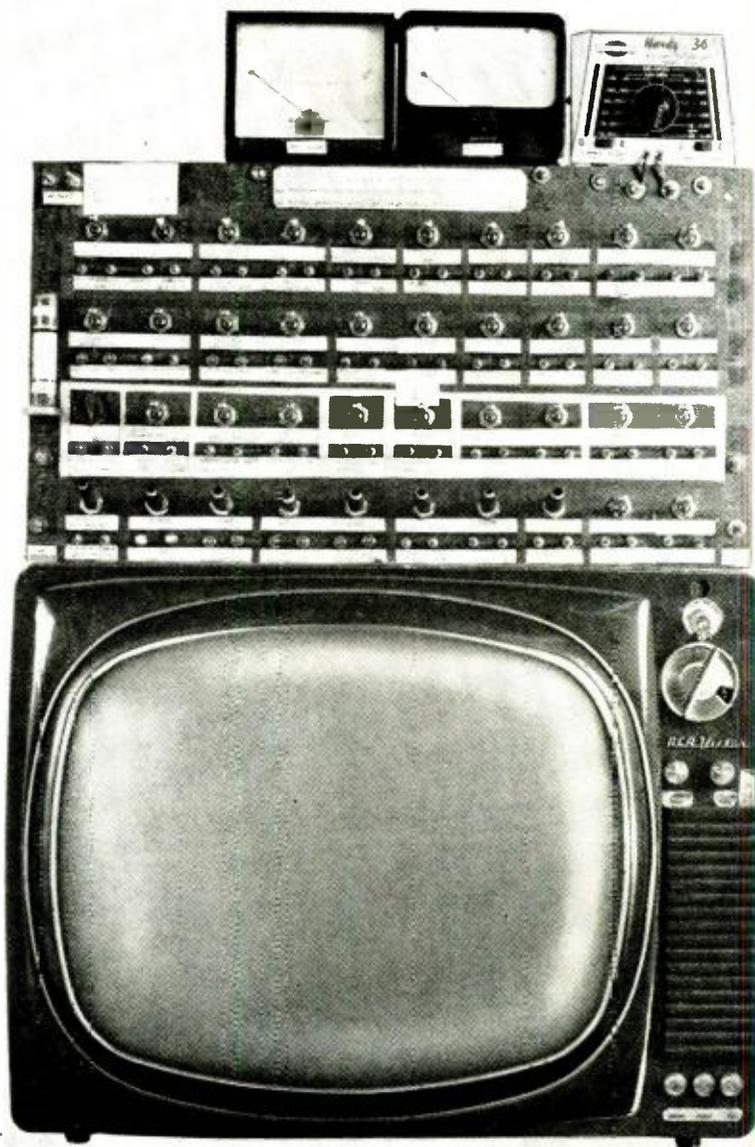


Fig. 1—"Mr. Sarnoff wouldn't recognize it."

TELEVISION

"I chose it for several reasons. For one thing, it's in a rugged metal cabinet and has a power transformer. Now I know we don't have too much trouble with power supplies, but we have all lost time wondering if low voltage or an improperly filtered supply was contributing to instability. To find out, I flick this switch down, attach a lead here, pull the 5U4 out of the defective set and drop this test lead into the No. 2 or 8 pin. In about the same time it takes to tell it I have eliminated power supply trouble. Savvy?"

What if it isn't there?

"Except for one minor detail. Just let's suppose that when you reach for that alleged 5U4 it isn't there."

"If the job has seleniums, we just move over into another department. In addition to the regular power supply, I built in a voltage doubler using silicons. By simply connecting leads to the proper terminals, I can bridge either rectifier, any capacitor, even the large ones, sometimes used in series with the line. Now would you say I have covered

the power supply rather thoroughly?" he asked.

"I concede you a point. Proceed."

"Now, let's go into something a little more difficult, the audio. By connecting here and throwing this switch I can drive the voice coil of the set under test, or I can make the test set drive this voice coil. How long would it take you to find out for sure that a voice coil was open without disconnecting it?"

"Well, I would have to screw the end off my flashlight, take out a battery, find something to use for leads and scratch the terminals. If I heard no scratch, the voice coil is open."

"But what if it were distorted? How would you show that up with a flashlight battery?"

"Okay, okay, you're building up points."

"Following the same procedure, I can substitute the output transformer—both ways, now mind you, and I can make the set under test drive this output and speaker or I can drive the output and speaker in the test set. Also, there are arrangements for two-way

substitution of signals from the input of the audio and the discriminator."

"All right, now let me see you kick that rf around a little, Smart Boy."

"Works the same way." Q shrugged confidently. "If you want rf to drive the discriminator, here it is. Or, you can take rf from the test set and drive this discriminator."

"Comes now the time when we must suppose that we have neither power supply or audio trouble. We have that very rare disease known as no pix. What would you prescribe to soothe that?"

"Listen, my friend, if you are planning on sticking me, you are going to have to dig deeper. Let's assume we have a trace of snow on the screen but no picture. My guess would be the tuner, but it would take a lot of work to prove it. With this gadget I simply attach a lead to the first if amplifier's grid, throw this switch and touch the other end of the lead to the grid of the first if in the test set. If I get a picture, the trouble is the tuner. Definitely! And as much as I hate to, I will have to tear into it."

Where do we go next?

"If the trouble hadn't been in the tuner, I would have tapped a signal off the if and fed it to the second detector. If I hadn't got a picture there, I would have kept going back tapping off the input to the video, the output of the video and finally the picture tube itself. In other words, I could have localized that trouble to an area small enough for me to make a minute search."

"Amen." I thought a minute and added, "But run a simple answer to this my way—why didn't those if's come uncranked when you were making like the AT&T with all those wires?"

"Well, Maestro, I regret that you brought up that subject, but I am prepared. Did you ever hear of the dandy art of 'doodling'?"

"Yes, that is exactly the thing we were always told not to do."

"Precisely. But this time I received a doodler's license by virtue of necessity."

"When I connected a lead that seemed to interfere with the picture or sound, I adjusted that particular stage to restore the quality."

"You may have restored the picture, but the quality part I doubt."

"Well, take a look for yourself." He snapped all the switches up, which is the normal operating condition, and sure enough he had a fair picture.

And the other switches?

"There seem to be a lot of switches you haven't wiggled yet, and we haven't talked any about high voltage, sync, vertical and horizontal, etc. For example, I see you have a terminal marked agc. What is it?"

"That's not really agc. It's a 45-volt battery hooked up through a pot so it can be varied down to .01 volt. And does that come in handy! The other day

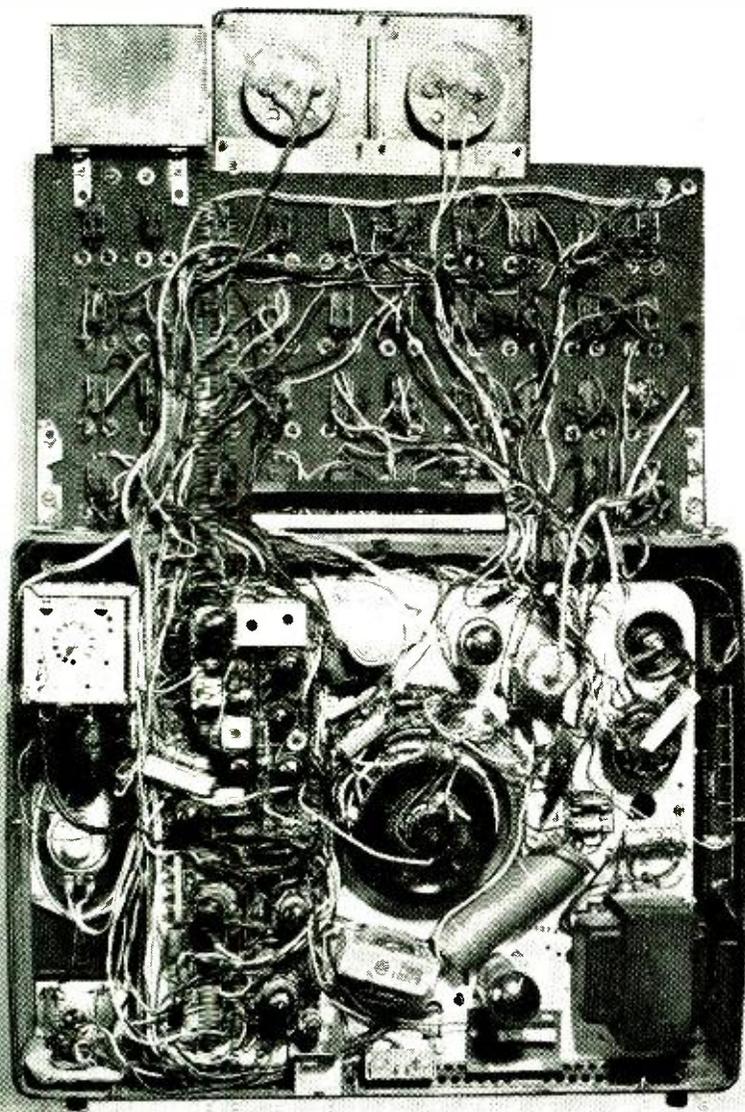


Fig. 2—"Mess! you say? Take a look at the back!"

I had a set that looked like two stations were coming in. I substituted a tuner signal and the trouble almost cleared up. When I fed a signal into the second detector, it did clear. I then substituted a battery bias and it also cleared. What do you think it was?"

"That's an unfair question for you, Q. It so happens that I have also been coached. It was the agc filter, usually a low-voltage electrolytic."

"That's right, but, why does it do it?"

"I thought you were supplying the answers, not the questions."

"Don't get me wrong," Q said. "I've never said I knew all about this business. In fact, I don't even know enough to quit." He laughed.

"Well, the reason you get double images or ghost effect when the agc filter capacitor is open or deteriorated is simple. It was put there in the first place to bypass anything that was moving on the age line, particularly hum and picture information. When it's not effective, picture information is fed back to the grids of the rf and if amplifiers where it is delayed or out of phase and appears on the face of the picture tube as a ghost, or interfering picture. . . .

"Along this same line, I had a rough one a while back. I was getting picture information in the sound. It was caused by a strong local overloading because of not enough bias. I see I could have found it much quicker with your device."

"Yep, agc can cause a lot of trouble. That's another reason why I selected this particular RCA for my substituter, it has keyed agc and I wanted the pulse that is fed back from the flyback transformer to the agc tube. That thing always did cause me trouble. Now," Q said, "I can supply that pulse to the line and remove another doubt. I can also supply the sync pulses. Here I have the composite sync right off the second detector, and these two terminals make available the vertical pulse after it has gone through the integrator, and the horizontal at the grid of the horizontal oscillator. You know, I can run these pulses along the line and actually find defective components? How many times have you wondered about the condition of this?" He tapped a printed-circuit integrator.

"Plenty," was my answer.

"I can tell you in a few seconds. If it passes my injected signal, it is good, and vice versa." Q demonstrated with good results.

Into the sync circuits

"The rest of the gadget is almost self-explanatory. I can feed a signal both ways from the input and output of the vertical and horizontal tubes. I can substitute both the vertical and horizontal output transformers. Also either section of the yoke."

"There are bound to be some variations in circuits that would keep you from substituting the vertical and horizontal outputs," I complained.

"Granted that there are," he an-

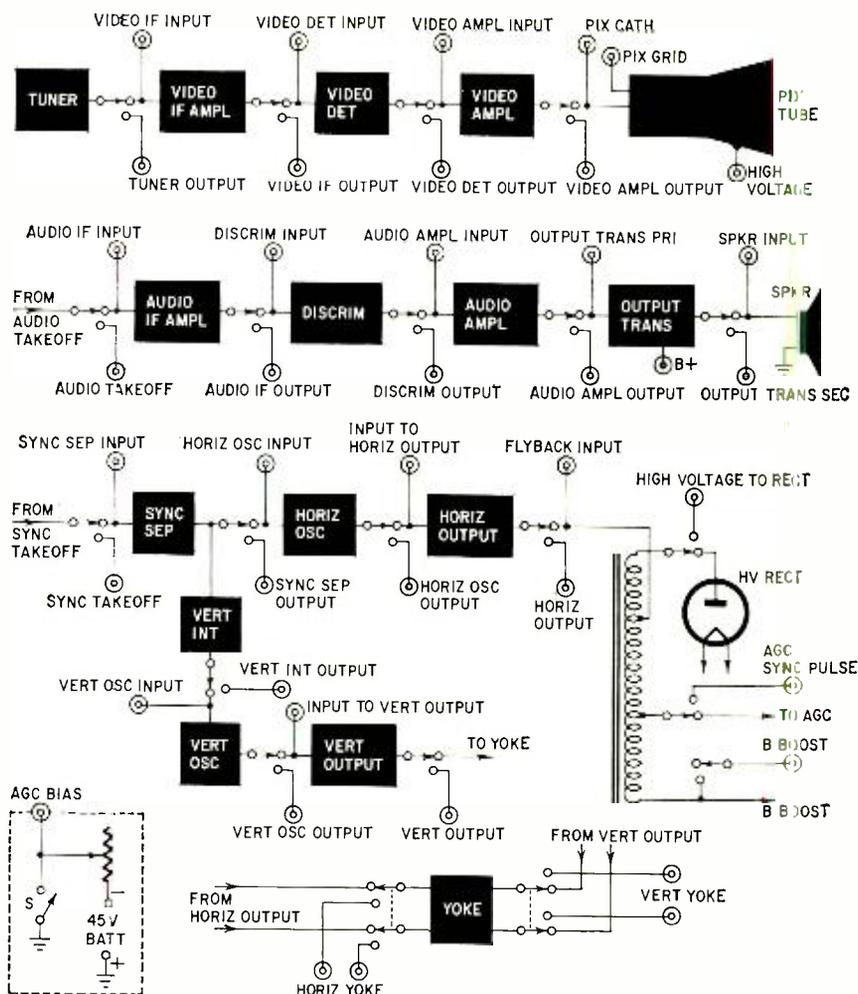


Fig. 3—Block diagram shows where taps are made to convert TV set into a Gibbons' Substituter. Some of the more obvious features (and harder to show in a diagram) such as a power supply are not indicated.

swered, "but I will still stick to my original statement and say that, by substituting both ways, I have always been able to localize the trouble. And, fortunately flybacks and yokes don't cause much trouble."

"No," I agreed, "I don't believe I ever replaced a flyback or yoke that wasn't obviously bad."

"Right! And that about wraps it up with the exception of mentioning the width coil I've brought out. Also I didn't mention that I brought out both the grid and cathode of the picture tube. B-boost, of course. And don't forget this high-voltage terminal. It can come in handy."

"Yes, I could have used that very nicely yesterday. I had an 8-inch Emerson that wouldn't light up. The high voltage at the input of the high-voltage rectifier seemed definitely low. The low voltage was off about a third, so I replaced the seleniums but it still didn't come up. After a couple of hours of checking, I decided to replace the flyback. Then I discovered that a pin had broken off from the lug on the high-voltage rectifier socket. This is one case I know your gadget would have saved me hours."

"Is there anything extra special you've learned to do with it?"

"Yes, in a way," Q answered. "You can detect hum in a circuit by connecting to the video amplifier input. Hum will show up on the screen just as it does with a shorted tube in the circuit."

"And by the same token," I added, "you should be able to detect contamination along an age line. By the way, what are those meters on top?"

"This one, of course, is simply an ac-dc meter across the line. The other is a high-resistance meter in the second-detector circuit. I can measure, relatively, the output of a tuner or the gain of an if by connecting the tuner in question to the first if in the gadget. Then I can go down the line measuring the gain of each if."

"I presume that it's sometimes necessary to use decoupling in the leads when interconnecting, like small capacitors or resistors?"

"Occasionally. It all depends on the situation."



"It's also necessary to ground the two sets, and that's the reason for not using a selenium job for a Substituter."

"It would be all right," Q said, "if you used an isolating transformer."

"I guess this gives me enough information to tell the boys about it. I guess I'll wrap things up and head for the post office." END

HEATHKIT

Presents 18 New Kits for

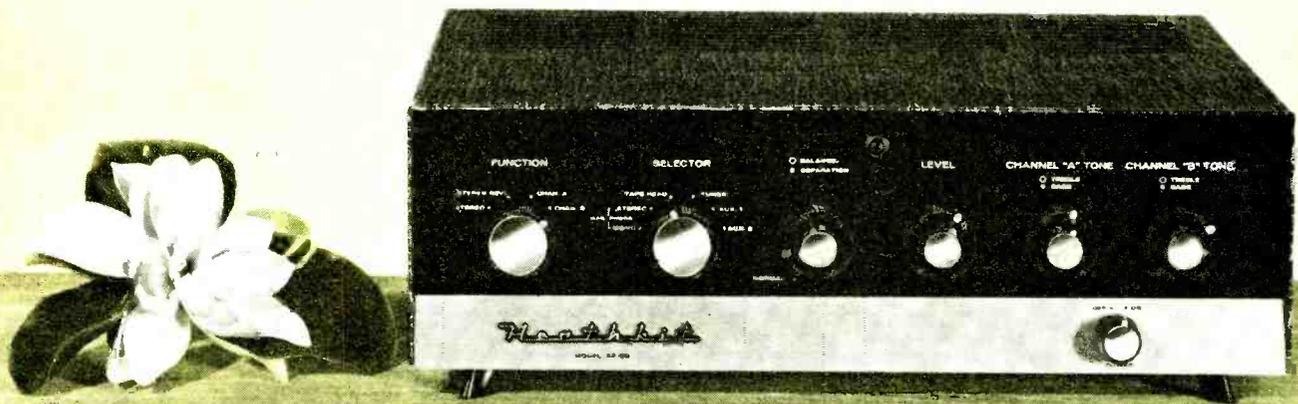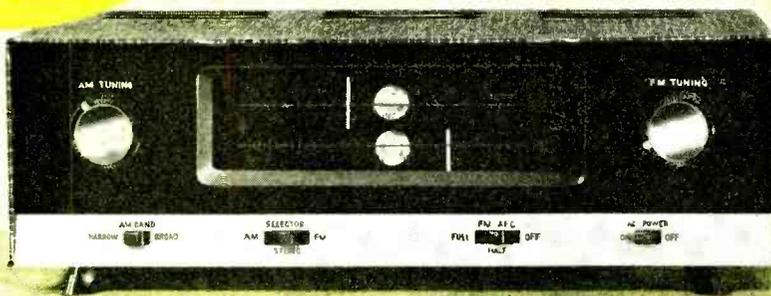

GO STEREO IN STYLE . . . WITH HEATHKIT® QUALITY AND ECONOMY!

ECONOMY STEREO AM/FM TUNER KIT (AJ-10)

Full fidelity AM and FM reception, plus up-to-the-minute design features are yours at minimum cost with this new Heathkit stereo tuner. Features include: 2.5 uv. sensitivity for 20 db of quieting; individual flywheel tuning; separate magic-eye tuning indicators for AM and FM; AM bandwidth switch; 3-position (off-half-full) automatic frequency control (AFC); FM multiplex adapter output; built-in FM rod antenna; terminals for external AM and FM antennas; "AM," "STEREO" and "FM" function selector switch. 14 lbs.

\$5995

AJ-10
\$6.00 dn., \$6.00 mo.

HI-FI RATED 25/25 WATT STEREO AMPLIFIER KIT (AA-50)

In one handsome package, you get both stereo power and control, with a host of deluxe features. Hi-fi rated at 25 watts per stereo channel (50 watts monophonic), this new Heathkit design includes channel separation control . . . new mixed center speaker output . . . stereo reverse and balance controls . . . separate tone controls for each channel with ganged volume controls . . . five switch-selected inputs for each channel (stereo "mag. phono," tape head, three hi-level). Extra input for mono "mag. phono." Special outputs for tape recording. 30 lbs.

\$7995

AA-50
\$8.00 dn., \$8.00 mo.

YOUR "BEST BUY" IS HEATHKIT® HI-FI!


FREE CATALOG

Send for your copy today! . . . describes over 150 Heathkit hi-fi, ham radio, test, marine and general products.




STEREO/MONO RECORD PLAYER KIT

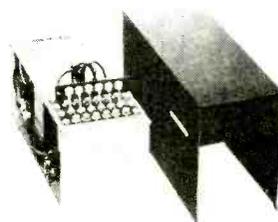Four speeds (16, 33, 45 and 78 RPM); Sonotone 8 TA4-SD ceramic stereo cartridge. 10 lbs.
AD-10 \$33.95



MIXED LOWS STEREO CROSSOVER KIT

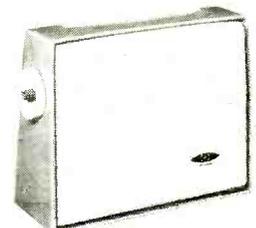Delivers stereo bass frequencies to single woofer; highs to individual wing speakers. 10 lbs.
AN-10 \$19.95




TRANSISTOR PORTABLE KIT

Tremendous value! 6-transistor circuits. Fun to build!
XR-2P (plastic)
6 lbs. **\$29.95**



Just 10% DOWN ON ORDERS OF \$55 OR MORE!

Your Summertime Enjoyment

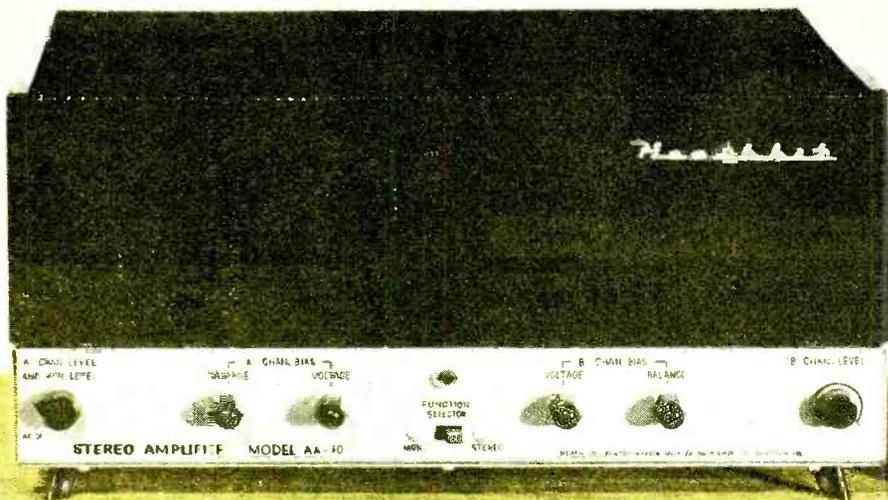

HEATHKIT® . . . FOR FLEXIBILITY and COMPATIBILITY!

ECONOMY STEREO PREAMPLIFIER KIT (AA-20)

A low-cost, versatile stereo preamplifier control center. Four inputs each channel accept magnetic cartridge, crystal or ceramic cartridge; and tuner, tape, TV, etc. Six position function switch gives flexible stereo or monophonic use. Features cathode follower outputs plus hi-level outputs for tape recorder drive, calibrated Baxandall-type tone controls for each channel, clutch-type volume controls, filament balance controls, and accessory AC sockets. Self-powered. Styled in black and gold. Shpg. wt. 8 lbs.

\$34⁹⁵
AA-20

PROFESSIONAL RATED 35/35 WATT BASIC AMPLIFIER KIT (AA-40)

Doubles as a superb dual 35 watt stereo amplifier or a full-fledged 70 watt monophonic amplifier. Features: mixed-channel center speaker output; individual level controls; "Stereo-Mono" switch (ties both amplifiers to one level control for monophonic use); dual outputs for 4, 8, 16 and 32 ohm speakers. Paralleling outputs for 70 watt monophonic use matches 2, 4, 8 and 16 ohm speakers. 41 lbs.

\$79⁹⁵
AA-40
\$8.00 dn. \$8.00 mo.

Now . . . a complete Mobile PA Sound System in easy-to-build, HEATHKIT® form!


MOBILE PA SOUND SYSTEM

Perfect for political campaigns, advertising, sporting events. The powerful amplifier operates from any 12 volt car battery. Features an all-transistor circuit; inputs for microphone and music source. Two channel mixing circuit "fade" auxiliary input when used with microphone supplied. Lets you override music with voice without changing control settings. Outputs for 8 and 16 ohm speakers. Mounts easily under auto dash. Mobile PA Amplifier Kit (AA-80). 7 lbs. . . . **\$39.95**

COMMERCIAL SOUND SYSTEM (CSS-1): consists of AA-80 Amplifier; microphone; plywood car-top carrier; one 16 ohm, 15 watt outdoor speaker. 24 lbs. . . . **\$84.95**

COMMERCIAL SOUND SYSTEM (CSS-2): same as above except with 2 speakers. 30 lbs. . . . **\$99.95**

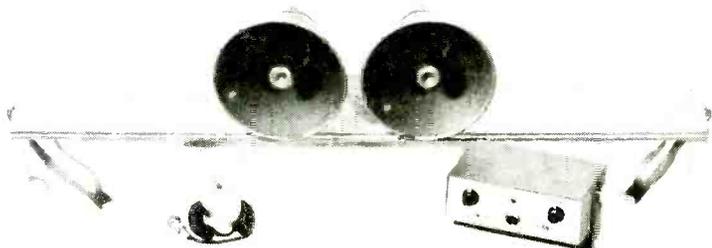EXTRA HORN SPEAKERS (401-38): As described above. 6 lbs. . . . **\$19.95**



SAVE 50% . . . ON THE WORLD'S BEST QUALITY KITS



First... With The Finest

a subsidiary of
DAYSTROM, INCORPORATED




Buy The Best in Quality At Half the Cost With Heath

**CITIZENS BAND TRANSCEIVER KIT
(GW-10 Series)**

Superb 2-way Citizens Band communication! Superheterodyne receiver may be switched to crystal control or continuous tuning. Featured are an automatic "series gate" noise limiter, to minimize ignition interference, etc.; and adjustable squelch control to silence receiver during "standby." Press-to-talk microphone features a coil-cord connection to the transceiver. Transmitter is crystal controlled on any one of 23 assigned channel frequencies chosen. Order model GW-10A for 117 v. AC operation, and GW-10D for 6 or 12 v. DC operation; both have self-contained power supply. 11 lbs.

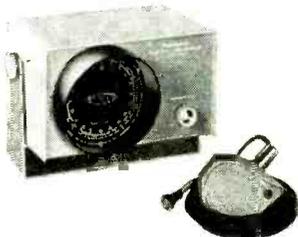GW-10A (117v. AC) or **GW-10D** (6 or 12 v. DC) **\$62.95** ea.
\$6.30 dn., \$6.00 mo.



**TRANSISTOR DEPTH
SOUNDER KIT**

Shows depth, type of bottom and submerged objects from 0-100 feet. Powered by 6 flashlight cells. 10 lbs.

DS-1 **\$69.95** (\$7 dn., \$7 mo.)



**6 & 10 METER HAM
TRANSCEIVER KITS**


Combined crystal controlled transmitters and variable tuned receivers. Operate fixed or mobile. 10 lbs.

HW-19 (10 meters) **\$39.95** ea.
HW-29 (6 meters) (less XTAL)

**3-BAND "MARINER" TRANSISTOR
DIRECTION FINDER KIT (DF-3)**

Priced far below pre-assembled units of comparable quality, the DF-3 includes such important features as: 9-transistor circuit; 6 flashlight battery power supply; pre-assembled, pre-aligned tuning section; new modern styling; rugged aluminum splash-proof cabinet. Covers broadcast band, beacon and aeronautical band, and marine-telephone band. Special "sense" antenna eliminates "double null" effect common in many direction finders. Circuit has high gain IF amplifier and audio output amplifier delivering up to 380 mw of audio power to the large 4" x 6" weatherproof speaker. 13 lbs.

\$99.95
DF-3
\$10.00 dn., \$9.00 mo.

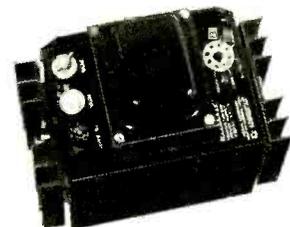

**TRANSISTOR MOBILE
POWER SUPPLY**

All-transistor! Provides plate, screen and bias voltages for mobile amateur equipment. 120 watts ICAS. 10 lbs.

HP-10 **\$44.95**



EDUCATIONAL KIT

First of a series . . . designed to teach, as you build, the basic "yardsticks" of electronics. Consists of kit and text-workbook. Finished volt-ohm-milliammeter has many uses. 4 lbs. **EK-1** **\$19.95**

TIME PAYMENTS!
Use Heath's convenient time payment plan . . . only 10% down on orders of \$55 or more.

in Easy-to-Build Electronic Kits



MUTUAL CONDUCTANCE TUBE TESTER KIT (TT-1)

An impressive list of electronic and mechanical features make this tube tester one of the finest values in the electronics industry. Tests Gm (amplifiers) from 0 to 24,000 micromhos, Emission, Leakage, Grid Current (1/4 microampere sensitivity), Voltage Regulators (built-in variable DC power supply), Low Power Thyatron and Eye tubes. Features 300, 450 and 600 ma constant current heater supplies. Life Test, Hybrid Tube test, built-in switch-operated calibration circuit. Large, easy-to-meter. Constant tension, free rolling illuminated chart. Kit includes 7 wiring harnesses. Assembly skill of technician or higher recommended; assembly time, 40 hours average. Black leatherette case with white trim, nylon feet, removable top. A specialized tool of unusual value that will pay for itself many times over! 27 lbs.

TT-1 **\$134⁹⁵**
 (\$13.50 dn., \$12.00 mo.)



WORLD-WIDE, ALL BAND RADIO RECEPTION

- Ceramic IF "Transfilters"
- Five Bands
- Flashlight battery power

10 TRANSISTOR "MOHICAN" GENERAL COVERAGE RECEIVER KIT

First kit of its kind uses ceramic IF "Transfilters." Covers 550 to 30 mc on 5 bands, with 5 separately calibrated bands to cover amateur frequencies (including 11 meter citizens band). Powered by 8 flashlight batteries.

Built-in 54" whip antenna, tuning meter, headphone jack. (less batteries) (20 lbs.) **GC-1** **\$109⁹⁵**
 \$11.00 dn., \$10.00 mo.

send today for Your FREE HEATHKIT® CATALOG

Over 150 items of hi-fi, marine, amateur, test and general equipment are illustrated and described in the complete Heathkit catalog.



HEATH COMPANY, Benton Harbor 20, Michigan

Please send the following HEATHKITS:

ITEM	MODEL NO.	PRICE

Ship via () Parcel Post () Express () COD () Best Way

() SEND MY FREE COPY OF YOUR COMPLETE CATALOG

Name _____

Address _____

City _____ Zone _____ State _____

B

Dealer and export prices slightly higher.

HIGH-FIDELITY

TEST

PANEL

By HERMAN BURSTEIN and CHARLES B. GRAHAM

TO capture a good share of the growing high-fidelity and tape-recorder service business, the service shop must have readily available test facilities at its front counter to check out any component quickly as soon as it's brought in. This is more complicated than preliminary checking of radio or television receivers which are all-in-one units and usually require only an ac socket and perhaps an antenna. Too, the typical audiophile will less often settle for "good enough" than will other service customers. With a well arranged checkout station, the progressive service shop will not only be set up to perform first-rate audio work quickly, but also to impress the customer.

The repair technician should be certain that the customer agrees with him as to the trouble when the equipment is brought in. If the technician checks the unit right before the owner's eyes (and ears) and they agree on what's wrong, serious misunderstandings which might otherwise come up later can be avoided.

If the front bench is not to be a clutter of components and cables, such a checkout station requires a carefully designed switching system through which components can be quickly connected in various combinations.

A flexible and time-saving approach to this problem has been developed by Sigma Electric Co.,* an experienced tape recorder and components servicing organization. Sigma has designed and installed a *test panel* out front at its customer service counter where sets are accepted for repair. They also have a *bench test panel* at each of three repair technicians' benches back in the shop. These audio-component test panels represent a careful approach which was worked out over a period of several years. Examination of the details of the test panels will suggest useful variations to many technicians doing test maintenance, and repair of tape recorders and audio components.

Fig. 1 shows the test panel behind the customer counter. It's a standard

*11 E. 16 St., New York 3, N. Y.

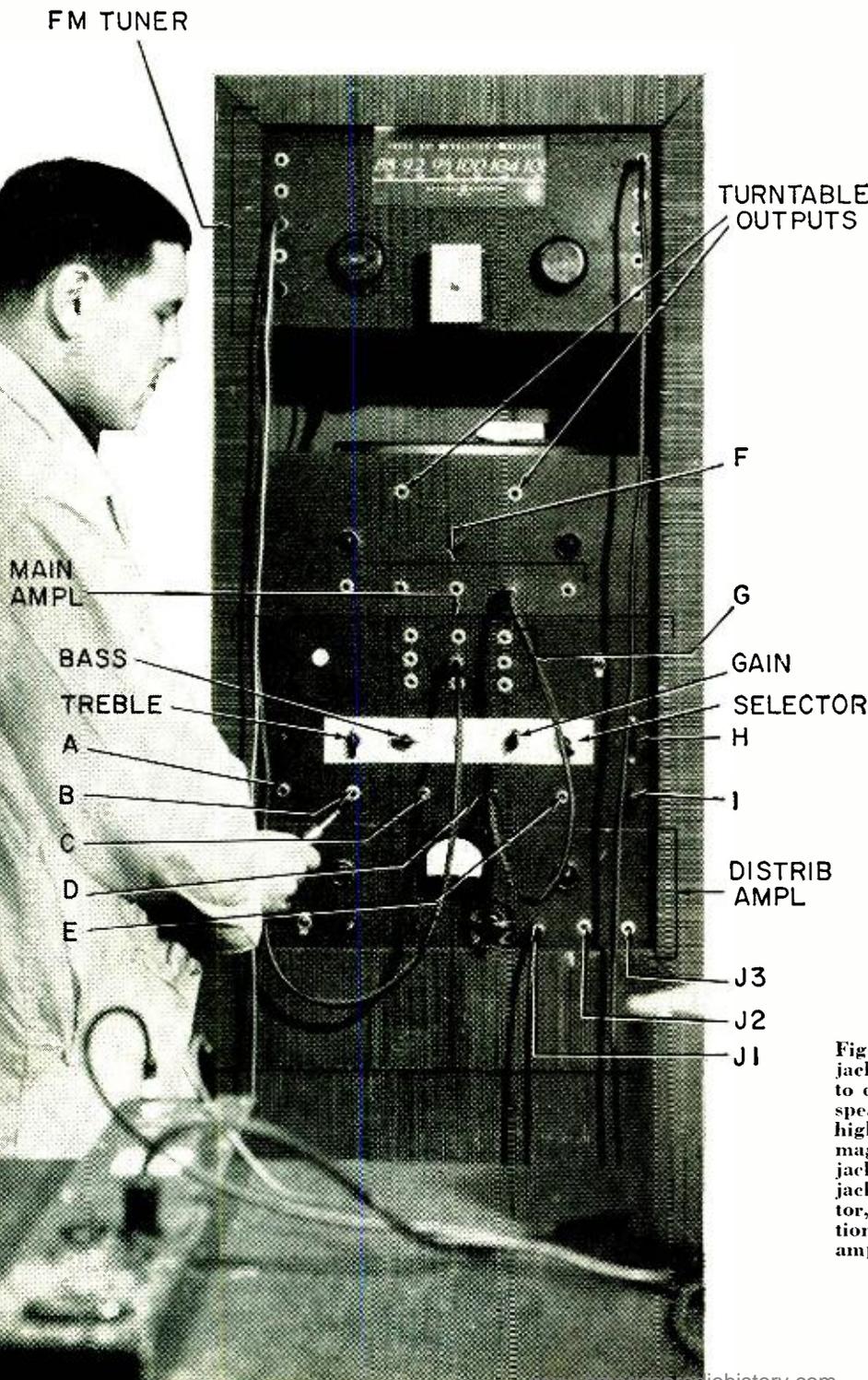


Fig. 1—Audio test panel at the counter. Counter jacks in box at lower left connect under counter to color-coded jacks on test panel. A—external speaker, B—external amplifier output, C—high-Z input, D—straight-through input, E—magnetic phono or tape input, F—color-coded jacks from counter, G—3 sets of paralleled jacks, H—tape head input, I—magnetic selector, J1—cathode follower output of distribution amplifier, J2—monitor, J3—distribution amplifier input.

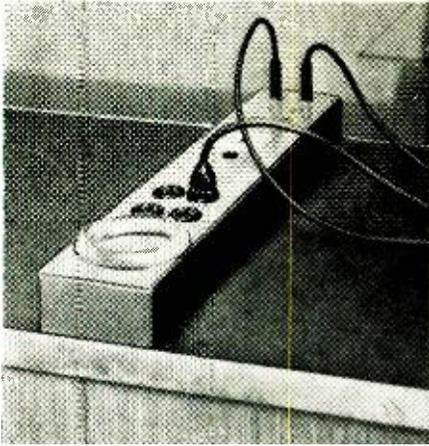


Fig. 2—Jack boxes (rear of counter unit) accept cables to connect gear for counter checking. Box jacks parallel test panel jacks behind counter.

19-inch rack holding four panels. The counter is clear except for three adjacent jack boxes (Fig. 2) wired so that each of the five color-coded jacks in each box is paralleled to corresponding jacks in the other box and connected to similar color-coded jacks on the test panel behind the counter with short runs of low-capacitance two-wire shielded cable. (Note that there are only 5, not 15 color-coded jacks on the test panel itself, since the three jack boxes are paralleled.)

When a piece of equipment such as an amplifier, tape recorder or preamp-control unit is brought in for repair, it is placed on the counter and plugged to one of the bench jack boxes with a patch cable. A number of these patch cables are always stored, loosely plugged into unwired storage jacks in the top section of the test panel. These patch cables have a standard telephone plug at one end, and either a telephone plug, RCA phono plug, or some other standard connector at the other end.

Since the jacks in the counter jack boxes, the jacks on the test panel (connected to counter jacks) and the phone plugs on the patch cables are all color-coded, the technician can use these colors as ready identification to keep connections straight. In addition, two (or, under some conditions, three) pieces of equipment can be counter tested at the same time.

Test panel

Fig. 1 includes labels for the parts of the test panel showing the jacks and facilities of each of the four rack sections. At the top is the FM tuner and two vertical rows of nonconnected storage jacks. These are simply holders for patch cables not in use.

The FM tuner is the main signal source for the shop and for the counter. The output of the tuner is fed throughout the shop via a distribution amplifier which is at the bottom of the test panel. Since this FM tuner runs continuously, it must be sturdy and drift-free.

The second rack panel from the top holds a phonograph turntable and the test panel jacks which connect to the jacks on the counter. These jacks are color-coded with spots of quick-drying enamel to match the ones on the counter.

The arm used with the turntable has a removable shell with a high-quality cartridge for playing LP's. Three extra shells are kept ready, one with a ceramic or crystal pickup, and two empty shells with small alligator clips for testing the occasional phono pickup cartridge which is brought in for checking.†

Two phonograph output jacks are paralleled out at the top of this second rack panel section. One makes the phono signal available for counter test of amplifiers; the other provides any desired phonograph material to the repair bench locations in the shop (by patching it to the input of the distribution amplifier), without taking the phonograph turntable out of front bench testing use. This panel section also includes pilot lights, fuse and switch for the turntable.

The third section of the test panel has nine jacks grouped so that three sets of three jacks each are paralleled. They are used to parallel outputs or inputs without using external multiple connectors.

†A test record made by Components Corp., Denville, N. J., has 1,000-cycle tone recorded at high level both at its outside and near its center. Playing this disc, "How's Your Stylus?" can reveal stylus condition. This material has also been released by Urania Records, Belleville, N. J., and Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.


The third panel section of the test panel also mounts a standard high-fidelity amplifier combining on one chassis the preamplifier, control unit, and power amplifier modified for this application.

The gain, treble, bass and high-frequency scratch filter controls are conventional, but the selector switch has been modified to allow choice of either of two high-impedance inputs or one of four (different equalization curves) magnetic phono positions. These modifications include wiring five phone jacks on the front panel. Independent access to the loudspeaker is through closed-circuit jacks wired as shown in Fig. 3.

The three lower right-hand jacks, C, D and E, are inputs for high impedance (medium level), "straight-through" (low gain and no tone controls) and magnetic phono (pickup) or tape head, respectively. The left-hand jack, A, is an output jack, making available the output of the amplifier for testing external speakers. The next jack, B, connects only to the system loudspeaker (not shown). Jacks A and B are closed-circuit jacks connected as shown in Fig. 3 so that the amplifier feeds directly to the system loudspeaker except when one of the two jacks, A or B, is plugged into.

The output transformer of the power amplifier has several output impedance taps which are selected by the switch above jack A.

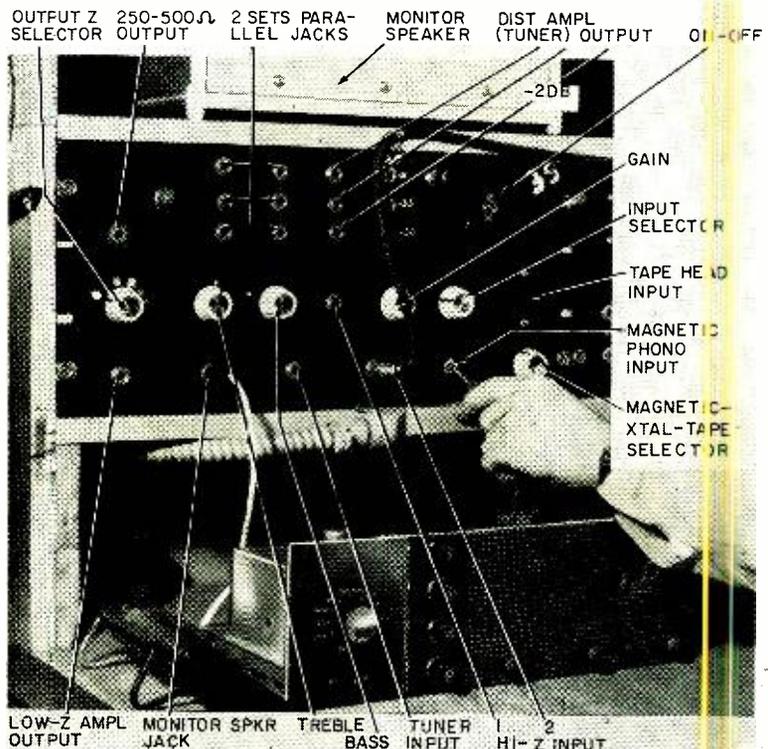The "straight-through" input is particularly useful for demonstrating that it is the equipment under check which



External amplifier and external speaker jacks shown in direct, normal position. Either a loudspeaker or an amplifier may be plugged into these jacks for rapid checking

FIND TUBE TROUBLES OTHERS MISS!



A New Dynamic Approach
 Check over 1300 tubes for

- Cathode Emission
- Grid Emission
- Leakage
- Shorts
- Gas

SENCORE "MIGHTY MITE" TUBE CHECKER


Answers the needs of the fast moving, profit minded serviceman who hates time consuming call backs. A "mite" to carry but a whale of a performer with more efficiency than testers costing much more.

New unique circuitry tests for grid emission and leakage as high as 100 megohms yet checks cathode current at operating levels. Special short test checks for shorts between all elements. The MIGHTY MITE will test every radio and TV tube that you encounter (over 1300!) plus picture tubes. Set up controls as easy as "A B C D" from easy to follow tube chart. New tube charts provided free of charge.

AND check these added Sencore servicing features: • Meter glows in dark for easy reading behind TV set • Stainless steel mirror in cover for TV adjustments • Rugged, all steel carrying case and easy grip handle • Smallest complete tester made.

Model TC109.....DEALER NET **59⁵⁰**

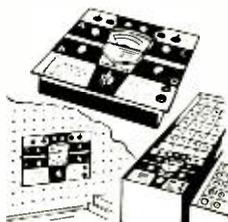Ask your distributor for the "MIGHTY MITE" with the mirror in the cover



Use it everyday in every way. Especially designed so you can transfer inner chassis to your tube caddy, bench or counter. Only 9" x 8" x 2 1/2".

ALL PARTS

SENCORE

ADDISON 2, ILLINOIS

STAMP OF APPROVAL



A mail-order tube advertisement in RADIO-ELECTRONICS is its own stamp of approval—your assurance that you will get what you pay for when you order. Since January, 1956, RADIO-ELECTRONICS has insisted that mail-order tube advertisers tell you that their tubes are new and unused, or, if they're not—that they are seconds, rejects or otherwise imperfect. Over the years this has cost us thousands of dollars in advertising—but it has protected you.

AUDIO—HIGH FIDELITY

is at fault, and not the test panel itself. This position also prevents cascading the panel tone controls after the controls on the amplifier or recorder.

The *distribution amplifier* serves a double purpose. First, it feeds the FM tuner to shop locations in such a way that shorts occurring at one bench in the shop will not short out the rest of the system. Second, it makes the FM signal available at the front counter for checking customer equipment. As shown in simplified form in Fig. 4, it consists of a stage of voltage amplification followed by eight cathode-follower outputs. Seven of these outputs feed the primary signal to the shop locations. The eighth is connected to output jack J1 on the front panel of the distribution amplifier. Output jack J2 (for phones) is permanently connected to the VU meter and eight-position switch for monitoring the signal going to each shop location. The eight-position switch allows checking each shop location from the front panel for proper audio. The indication that all is well is obtained on the VU meter, which is also used to set the outgoing signal to a predetermined satisfactory level. J3 is

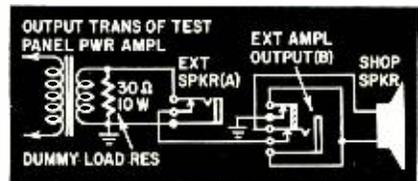


Fig. 3—Bench panel is one of three at repair benches for troubleshooting, repair, and calibration of recorders and components. Due to gradual development this panel has a few extra jacks not required in a new panel. Similar to main test panel at front of shop, repair bench panels allow more precise measurement and test procedures.

an input jack, which permits any other signal source to be fed into the distribution amplifier. This jack is a break type, so the insertion of a phone plug interrupts the normal connection from the FM tuner.

The distribution amplifier front panel also contains pilot lights, power switch and fuses for both ac and B-plus.

Bench panels

At each of three repair benches there is a bench panel (photo, p. 69) with a complete amplifier, including controls, preamplifier and a variety of jacks and switches for the convenience of the repair technician. This bench panel is capable of accomplishing most of the functions which the main test panel can, (out front at the customers' counter) and also provides several facilities not available at the front-of-the-store panel.

The bench panel has five controls. Four of them are conventional controls, bass, treble, volume and input selector (tape head, magnetic or crystal-ceramic discs pickup, tuner and other medium-level signals) while the fifth control is a selector for choosing various output transformer taps. There is a closed-

AUDIO—HIGH FIDELITY

circuit jack marked "speaker" which the technician may plug into should he wish to use the bench speaker which is normally driven by the bench panel amplifier. This would be useful in testing a customer's amplifier.

The bench panel has a jack which makes the output of the bench panel amplifier available for testing the customer's speaker or the built-in speaker of a tape recorder, portable phonograph or other complete unit.

The bench panel also has three jacks which make a pad available for reducing the line output by specific amounts (35 and 50 db) for checking low-level high-gain channels such as microphone or tape-recorder preamps. There are three paralleled jacks which are the output of the distribution amplifier (main test panel out front). They are paralleled so the technician may use that program for more than one purpose at a time.

Finally, there are two sets of paralleled jacks, three per set. These make

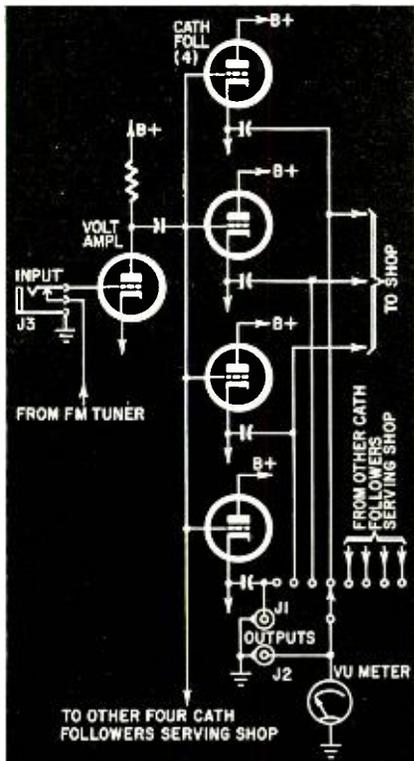


Fig. 4—Simplified schematic of distribution amplifier. Consult text.

it convenient to plug patch cords through the parallel jacks for making connections. This eliminates many of the universal adapter cords otherwise necessary for patching up temporary test setups, and provides a much neater way of plugging things together. It also helps keep the bench clear.

There's also a 1,000-cycle test tone signal at about 1.5 volts available at one of the jacks. This tone comes from the main test panel, too.

In addition to these controls and jacks, this bench panel has an on-off switch and a pilot light. In the photograph shown there are 21 jacks and 6 controls. Without sacrificing much flexibility, there could have been as few as

Transistor Radio Servicing CAN be Highly Profitable




The ONLY Complete Transistor Radio Service Lab Everything you need for less than \$50



Check Transistors, Diodes, Rectifiers . . .

SENCORE TRC4 TRANSISTOR CHECKER

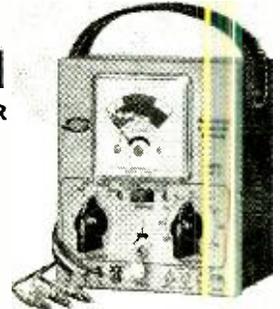
Accurately checks all transistors in hearing aids, radios and power transistors in auto radios. Tests for opens, shorts, leakage, current gain. Measures forward-reverse current ratio on all crystal diodes. Measures forward and reverse currents on selenium rectifiers. With set-up chart for accurate checking of each transistor. Size, 5x4½x2½". With batteries. DEALER NET..... **19⁹⁵**



Replace Batteries During Repair . . .

SENCORE PS103 BATTERY ELIMINATOR


All-new "Transi-Pak," twin to TRC4 Checker above. Provides variable DC voltage to 24 volts; 1.5-volt biasing tap (a "must" for servicing Philco and Sylvania radios). Metered current output, to 100 ma. Handles 200-ma peaks. Two 200-mfd electrolytics provide proper filtering and low output impedance. No hum or feedback problems. Ideal for alignment using station signal; adjust IF slugs for max. current, also ideal for charging nickel-cadmium batteries. Size, 5x4½x2½". DEALER NET..... **19⁹⁵**

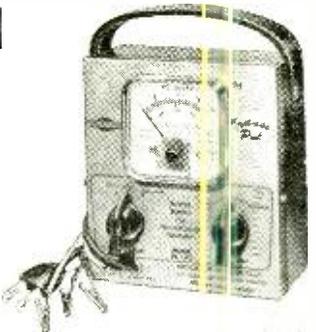

Find Defective Stage in a Minute . . .

SENCORE HG104 HARMONIC GENERATOR

New signal generator designed primarily for fast signal-tracing of transistor radio circuits. No need to unsolder all transistors. Provides RF, IF and audio signals *simultaneously*, drastically cutting service time. Traces from speaker to antenna. Clear 1000 cycle note signal is heard in speaker from all good stages. Signal weakens or stops at defective stage. Equally as effective for testing TV, hi-fi and other audio circuits also. Size, 3½x4½x1¾". With batteries. DEALER NET..... **9⁹⁵**

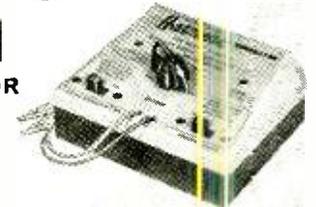

Turn page for other



ALL PARTS



MADE IN AMERICA

SENCORE

ADDISON 2, ILLINOIS

SERVICEMEN KNOW!

Here they pay less and get the best

HUSH®

Chemically-Electronically, engineered for Tuners and Switching Mechanisms.

When New HUSH is applied it will wash-away that dirt, leaving clean and positive contacts protected by a lasting lubricant. New HUSH is made from the finest solvents and it contains Electro-Silicone oils.

Also available—2 oz., 8 oz., 32 oz. containers 6 oz. Spray can **\$2.25 net**

EVER-QUIET®

Since 1949

VOLUME CONTROL AND CONTACT RESTORER

EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning the contacts and leaving a safe protecting film. Harmless to metals, wire or carbon.

Also available—32 oz. containers 6 oz. Spray can **\$1.59 net**

2 oz. Bottle & dispenser **79c net**



CHEMICAL ELECTRONIC ENGINEERING, INC. Matawan, New Jersey

AUDIO—HIGH FIDELITY

15 jacks and 5 controls. They are here because of special circumstances in the construction of this particular bench panel, and are not included in the other two panels.

Underneath the front bench are screw-in circuit-breaker type fuses for the ac lines. Although these cost a little over a dollar apiece, they save time and expense, considering the number of shorts occurring in customer equipment.

Cables

Two kinds of cables are used for access to the test panel, *patch* cables and *adapter* cables. The patch cables have a phone plug at each end and are used to make connections between the various jacks on the test panel. Five of these patch cables are color-coded to correspond with the colored counter and panel jacks, and one end of each patch cable is left in the panel jack of the same color.

The adapter cables allow the customer's equipment to be plugged into counter jacks. One end of each cable has a 3-circuit phone plug, while the other end may have any one of a number of connectors required to make connections to equipment brought in for service. Sigma's adapter cables include those terminating in an RCA type phono plug, in a Cannon plug such as used in certain professional tape recorders, in a pair of alligator clip leads, in banana plugs, in a five-prong speaker plug, in a six-prong speaker plug, in a plug fitting an octal socket and in pin tips. All unbalanced connectors have separate grounded shields available with alligator clips attached.

Miscellaneous other cables are kept on hand. These include a twin lead with a plug fitting the bench TV socket at one end and a clothespin connector (for screw terminals) at the other; an adapter cable for TV purposes, with a plug fitting the bench TV socket at one end and a socket matching a wall type TV antenna plug at the other; TV cheater cords; an ac extension cord with a small molded ac socket such as used in several brands of tape recorders, and an ac cord with a standard ac plug at one end and well insulated alligator clips on the other.

Typical test setups

To clarify the use of the test panel, the counter jacks and various cables, let's consider several typical instances in which a piece of audio equipment is to be checked.

Assume that a customer brings in a record changer which produces no sound. The cable from the changer terminates usually in an RCA phono plug. A Switchcraft adapter, combining a phono socket and phone plug, permits the cable to be plugged into one of the counter jacks, say the black one. The changer has a ceramic cartridge. The black patch cable is connected from the black panel jack to the input jack marked High Level 1 on the control power amplifier.

The technician makes certain that the




SENCORE ES102

ELECTRO-SUB

- What more can you ask for? The Electro-Sub not only saves time for any serviceman, engineer or experimenter but insures maximum protection too. Simply select the electrolytic, connect test leads and push surge protector switch.
- How many times have you reached for an electrolytic for substitution to find that value or voltage rating missing?
- How many times have you wanted a value just a little higher to see if you could knock out annoying hum?
- How many times have you had sets that blow fuses, fuse resistors or rectifiers and you did not check all electrolytics because it was too time consuming?
- Have you ever healed a suspected electrolytic by "bridging" it and made a call back that same week on the same trouble?
- Have you ever grabbed an electrolytic that you thought was discharged or watched a customer's dismay as you discharge one?
- Well, here is your answer . . . from the smallest electrolytics used in transistor radios to the largest used in costly Hi-Fi amplifiers . . . complete, safe substitution.

ES102.....DEALER NET **15⁹⁵**

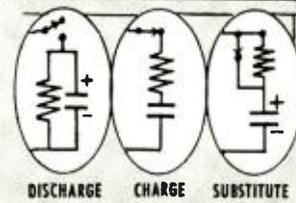AUTOMATIC SURGE PROTECTOR for you and the circuit



DISCHARGE CHARGE SUBSTITUTE
It does all this by merely pushing surge protector switch. Move it as fast as you want; it is smooth and returns automatically.

You'd pay more for just the parts than you would for the complete ES102 . . . amazed? See your parts distributor.

ALL PARTS
SENCORE
MADE IN AMERICA

SENCORE

ADDISON 2, ILLINOIS

What articles would you like to see published in

RADIO-ELECTRONICS?

Maybe you're the man to write them. Ask for an author's guide.

RADIO-ELECTRONICS 154 West 14th St. New York 11, N.Y.

FREE! CATALOG OF HI-FI, RADIO, TV PARTS & ACCESSORIES — yours for the asking!

Vidair ELECTRONICS MFG. CORP.
44 CHURCH ST. • BALDWIN, N. Y.

MAIL ORDER HI-FI

You can now purchase all your HI-FI from one reliable source and be assured of perfect delivery. Carston makes delivery from NY stock on most HI-FI. Recorders and tape within 24 hours. SEND US A LIST OF YOUR HI-FI REQUIREMENTS FOR OUR WHOLESALE QUOTATION and our FREE wholesale catalogue.

CARSTON STUDIOS 125-RD E. 88 St. New York 28, N. Y.

AUDIO—HIGH FIDELITY

function switch is in position 1, so that this input is operative. Thus the record changer is connected to the control power amplifier and, in turn, to the shop speaker. A record is taken from a rack, put on the changer, and the test is on. If there is indeed no sound, the technician makes a quick check of the cable connection by pulling out the Switchcraft adapter from the bench jack, which should produce a click.

Assume that a tape recorder is brought in, one of the usual home variety with a self-contained power amplifier and speaker. This requires only a signal source. One of the color-coded patch cables, say the white one, is connected from the white panel jack to output jack 1 on the distribution amplifier, which provides the FM tuner signal. In turn, an adapter cable is connected from the white counter jack to the radio (high-level) input of the tape recorder through a suitable cable, thus feeding in the FM signal. A reel of tape and an empty reel are taken from a rack and placed on the tape recorder, a recording is made, and the tape is then played back, providing a check of the machine's performance. If the complaint concerns only the playback performance of the recorder, then a pre-recorded tape is played on the machine. However, this does not involve the use of the test panel.

At this point it may be brought out that both customers just described could be served simultaneously inasmuch as the record changer is feeding a signal into the test panel and shop speaker, while the tape recorder is being fed a signal from the test panel. If a third customer came in with a tape recorder, he too could have his equipment checked at the same time without having to wait for the panel facilities to be released. Although this is an unlikely situation, it illustrates the versatility of the test panel. The third customer's tape recorder would receive the FM signal in the same manner as the other recorder, except that another set of counter and panel jacks, say red, would be used, and the FM signal would be picked up from output jack 2 of the distribution amplifier.

Assume that a customer brings in a professional tape recorder, one with separate record and playback heads and which does not have its own power amplifier and speaker. In this case, the testing requires both a signal fed into the machine and an amplifier for the signal fed out of it, bearing in mind that a three-head recorder permits simultaneous record and playback. A patch cable, say yellow, would connect the yellow panel jack to J1 (or J2) of the distribution amplifier to pick up the FM signal. The FM signal would then be fed from the yellow counter jack to the recorder by an adapter cable. The recorder output would go via an adapter cable to, say, the green bench jack, and then from the green panel jack via patch cable to one of the high-level inputs of the control power amplifier, say jack C, thereby feeding the

Spot in a flash... FAULTY CAPACITORS AND RESISTORS



A complete range of capacitors and resistors at your command.


SENCORE HANDY 36 SUBSTITUTION UNIT

Serviceman . . . Engineer . . . Experimentor . . . here's a unit that really saves you time. The Handy 36 provides the 36 most often needed capacitors and resistors for fast, on the spot substitution. The 12 position, 3 wafer switch individually selects one of the 36 components. You simply dial the value you want to the exact or closest reading. Substitution is still the only time tested method for determining whether or not a component is faulty while operating in circuit.

Eliminate time wasted in hunting for parts to use in testing. Say goodbye to the soldering mess created by substituting individual components. Put an end to the twisted wires and messy parts you've tossed in parts drawers.

The Handy 36 is simple to use. If a component is suspected of being shorted, open one end and substitute the Handy 36. Or, merely parallel any capacitor or resistor you think is open.

Model H36 DEALER NET **1275**

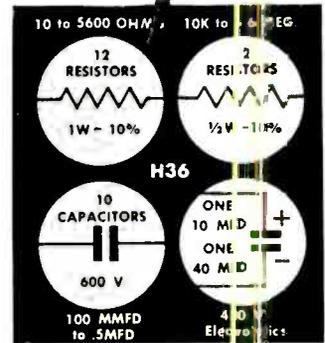

The Handy 36, with new improved circuitry, pays for itself in the first month by saving you hours of valuable minutes. The parts alone in the H36 would cost you more than the completed unit.

Ask any parts distributor for the "Handy 36", accept no substitute.


ALL PARTS
SENCORE
MADE IN AMERICA

SENCORE
ADDISON 2, ILLINOIS

TV TUNERS OVERHAULED

ALL MAKES AND MODELS **\$9.95** NET **30 DAYS WARRANTY** UHF VHF \$19.90

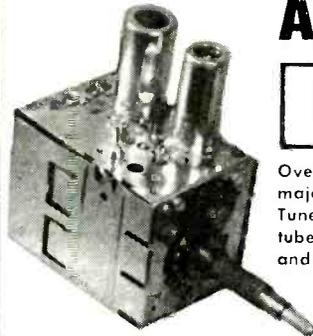SAME DAY SERVICE
ON POPULAR TYPES—48 HOURS ALL OTHERS



Overhaul charge includes labor and minor parts tubes and major parts are extra at net prices. Tuner to be overhauled should be shipped complete include tubes, shield cover and any damaged parts. Quote model and state complaint. Pack well and insure.

WE WILL SHIP C.O.D.—F.O.B. CHICAGO OR TO YOU


Castle TV Tuner Service

5710 N. WESTERN CHICAGO 45, ILL. U.S.A. • 136 MAIN ST. TORONTO 13 CANADA


Win with EMC



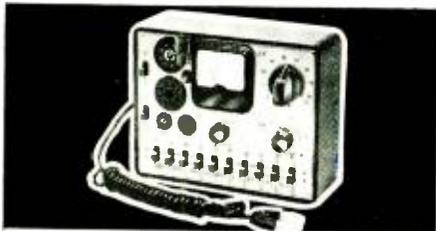By far the **BEST VALUE** obtainable in either wired or kit form . . . compare and you'll agree **"THE BEST BUY IS EMC."**




EMC Model — 211 Tube Tester — The smallest, lowest priced, domestic made tube tester on the market. It is completely flexible and obsolescent proof. It checks each section of multi-purpose tubes separately, checks all octal, loctal, 9 prong and miniature tubes for shorts, leakages, opens, intermittents as well as for quality. Quality is indicated directly on a two color meter dial using the standard emission test. Comes complete with instructions and tube charts in ring bound manual. Size 6 3/4" x 5 1/4" x 2 1/4" deep. Shipping weight: 3 lbs.
 Wired \$22.90 Kit \$14.90
 CRT Picture Tube Adapter \$ 4.50

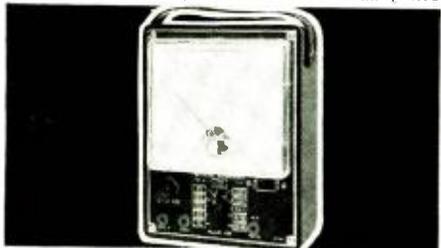

EMC Model 109 — Voltometer — Features 20,000 OHMS volts DC sensitivity and 10,000 OHMS per volt AC sensitivity. Uses a 4 1/2, 40 microampere meter, with 3 AC current ranges, and 3 resistance ranges to 20 megohms. 5 DC and AC voltage ranges to 3000 volts and 3 DC current ranges; also 5 DB range.

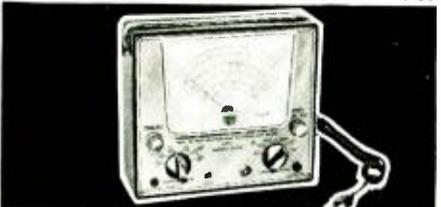Model 109 — With carrying strap, Weight 2 lbs. 5 ozs.; Size: 5 1/4" x 6 3/4" x 2 7/8" \$26.95
Model 109K — Kit Form 19.25
Model HVT — 30,000 Volt Probe for Model 109 7.95



EMC Model 107A — Peak to Peak Vacuum Tube Volt-Ohm Capacity Meter — 6" meter cannot burn out — entirely electronic. Measures peak to peak AC voltages to 2800 volts in 6 ranges. Measures capacity in 6 ranges from 50 mmfd to 5000 mfd. Measures resistance in 6 ranges from .2 ohm to 1000 megs. Measures DC volts to 1000 volts in 6 ranges. Input resistance to 16.5 megs. Wired \$51.40 Kit \$36.50

Yes, tell me more, send me **FREE** a detailed catalog of the Complete EMC Line. RE-76

NAME
 STREET
 CITY STATE

EMC Electronic Measurements Corp.
 625 B'way, New York 12, N. Y.
 Ex. Dept., Pan-Mar Corp., 1270 B'way, New York 1, N. Y.

AUDIO—HIGH FIDELITY

recorder's signal into the control-power amplifier and then to the shop speaker.

As a final example, let us say that a customer brings in a power amplifier for a checkup. Again this requires a signal and an amplifier. An adapter cable connects the input of the power amplifier to, say, the black counter jack, and the black panel jack is connected by patch cable to distribution amplifier output (J1). The output of the power amplifier is connected by an adapter cable to, say, the white bench jack, and the white panel jack is connected by the white patch cable to jack B of the control power amplifier, marked "loudspeaker." When the phone plug of the patch cable is inserted into jack B, the customer's amplifier replaces the test-panel power amplifier, as was shown at bottom of page 69.

This test panel has met the challenges of time and use. It has proven itself a rapid, flexible means of checking equipment both before and after repair. It

also impresses customers with the fact that they are dealing with an efficient, capable service organization.

Although the test panel is not over-elaborate in view of the volume of customer traffic handled, still it might well exceed the needs and budget of the small shop. However, there is much that can be done to cut down the test panel and associated elements in size and cost without losing basic advantages. A substantial reduction can be effected by eliminating the distribution amplifier and feeding signals directly from the FM tuner to the control power amplifier via one of the latter's high-impedance inputs. The number of bench panels can be reduced from three to one. The colored-coded bench jacks and panel jacks can be reduced from five to three. The phono outputs can be reduced from two to one. And so forth. Despite these economies, the test panel will prove itself a profitable tool for the high-fidelity service shop. END

FM MULTIPLEX IN ENGLAND

FROM the research laboratories of Mullard Radio in Great Britain comes another system for FM stereo multiplexing—putting two channels of audio information on one FM transmission channel. It claims one important advantage—the FM receivers used to pick up the program material are only slightly more complex than standard sets. Of course, they do require a second audio amplifier and speaker.

The Mullard system was developed by G. D. Browne and is completely compatible with existing FM transmission. A monaural set tuned in to the new system gets a first rate monaural FM program. On the other hand, a stereo FM receiver also gets a good monaural program when tuned in to standard broadcasts.

The stereo system is described as a two-channel pulse-amplitude time-multiplex arrangement. It works by coding the two channels of stereo information just before the transmitter is modulated.

A sampling oscillator produces a 32.5-kc sinewave which divides into two sine-wave outputs that are out of phase. These outputs are fed through a half-wave rectifier to produce two sets of pulses—one set for the right channel (A) the other set for the left channel (B). These pulses are modulated by the audio signal in their respective channels and give us the waveforms shown in Figs. 1-a and 1-b. Next these two sets of modulated pulses are combined to form the signal shown in Fig. 1-c. As a final step before being sent on to modulate the transmitter, sync pulses are added as in Fig. 1-d.


The receiver, of course, has the task of separating the two signals to form the two stereo channels. First, the incoming signal is detected in the usual manner, resulting in a signal that looks like Fig. 1-d again. The sync pulses

which were added to the signal just before transmission phase lock a 32.5-kc oscillator that separates the A and B signals and passes them on to their respective audio amplifiers.

The result of this process is a good stereo FM program. Crosstalk between channels is 45 db down, insuring complete separation between channels. This is especially useful in countries where the two channels might be used to carry the same program, but in different languages.

Existing receivers can be easily modified for use with the Mullard system. The set is used as is, up to the output circuit of the audio detector. At this point two tubes (a triode and a duopentode) are added. The triode is used as the receiver's 32.5-kc oscillator while the dual pentode forms the decoder circuit. The pentode outputs are connected to the audio amplifiers that drive the two stereo speakers.

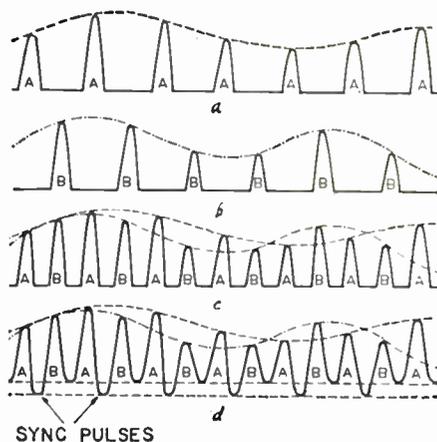Mullard claims clear-cut stereo with a frequency response up to 15,000 cycles in both channels, low cost, and most important, complete compatibility. END





Summertime is Reading Time . . .

enjoy it—and profit from it too,
with choice tidbits like these in

next month's Radio-Electronics

A treasure trove of electronica.

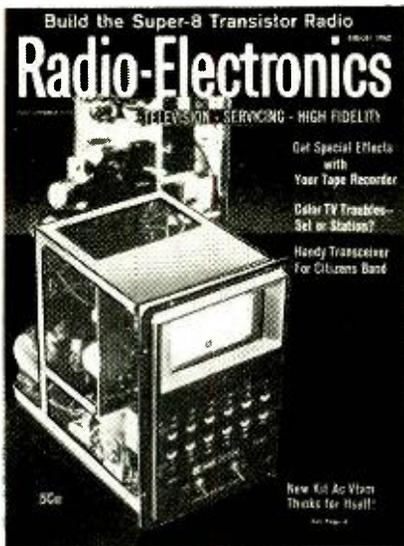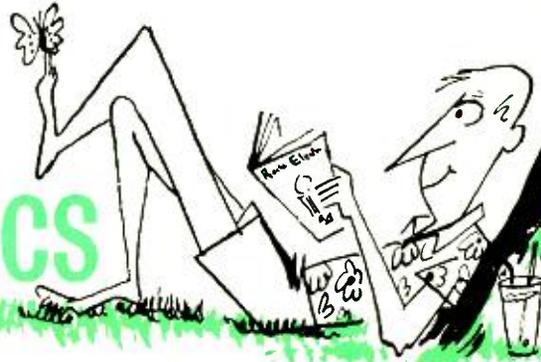

Building the Super Eight Receiver

How to build an 8-tube transistor receiver that's not a midget. This sweetheart uses a 6 inch speaker and will outperform most table sets. Good looking too—you'll enjoy reading about—and maybe building—it next month.


Handy Transceiver Covers Citizens' Band

Citizens' band communication is catching on like ice cream at a Sunday school picnic. Here's an ingenious little transmitter-receiver using transistors in receiver and audio portions—tubes in the transmitter. You'll love the simple switching arrangement.

There's something here for the service technician, the industrial technician, the engineer, the hi-fiteer, the serious experimenter, the student and the teacher. Articles to build from, articles to learn from, articles to work with, articles to think about, articles like...

Missile Control and Guidance —

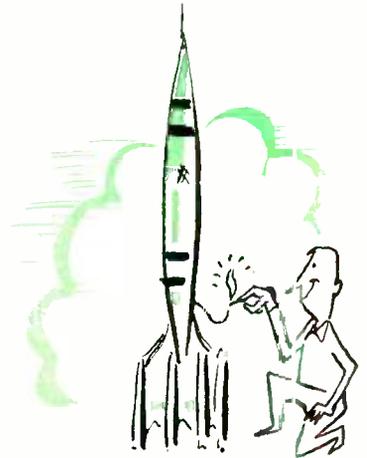By Marvin Hobbs. A thrilling and enlightening look at what goes on behind the launching pads. A countdown on the problems met in directing a missile to target. Explains several methods in detail including homing on heat or other radiation and direction by signals sent out from home base—or the missile itself. A fascinating feature you won't forget!



Special Effects with Your Tape Recorder

Raise your social batting average. One trick here will definitely make you the life of the party if not the most popular guy in the neighborhood. Gives you some inside tips on making multi-track recording, working with a slide projector and producing reverberations and echoes. Lots of fun.



Plus many, many more articles in addition to the standby regular departments:

WARNING! Subscription rates going up in October... better ACT NOW AND SAVE.

DON'T MISS THE AUGUST ISSUE — on sale July 26... Tell your dealer to save you a copy now or — make sure you never miss another issue, subscribe now.
\$4 one year \$7 two years \$10 three years

This new
BOGEN
GUIDE-BOOK
 tells you how
 to cash in on the
 profitable commercial
 sound market in
 PA and INTERCOM



"GETTING STARTED IN SOUND"

16 pages, packed with valuable information, advice, answers to all your questions—discusses qualifications required—how much capital it takes—costs of operation—and, most important, how to get started on a modest investment. This guide book also tells you how to obtain...

VALUABLE FREE SALES KIT TO HELP YOU IN THE FAST GROWING SOUND BUSINESS

FREE sound sales kit contains sales literature—sample solicitation letters—job quotation forms—technical and installation data—product specification sheets—merchandising ideas.

You will also receive additional free material from time to time. And if you are not already dealing with a Bogen Sound Distributor we will also put you in touch with one to serve as your local supply source.

This valuable sales kit will be furnished to you when you send in the special card included in each copy of "Getting Started in Sound."

THIS MAY BE the very opportunity you have been waiting for. Don't miss it! Visit your local Bogen Sound Distributor for your copy of "Getting Started in Sound." It will be the best 25c investment you ever made. If your distributor has not yet received his supply or is sold out, use this convenient coupon. Enclose 25c in coin, and a copy will be mailed to you directly.



BOGEN-PRESTO, PARAMUS, NEW JERSEY RE-7

Yes, I am interested in earning more money in sound systems, so please send me "Getting Started In Sound" by return mail. I enclose 25c in coin.

NAME _____


ADDRESS _____

CITY _____ ZONE _____ STATE _____

Look to Bogen-Presto for the big profit opportunities in sound

BP BOGEN-PRESTO PARAMUS, NEW JERSEY **RE-7**
 A Division of the Siegler Corporation

AUDIO—HIGH FIDELITY

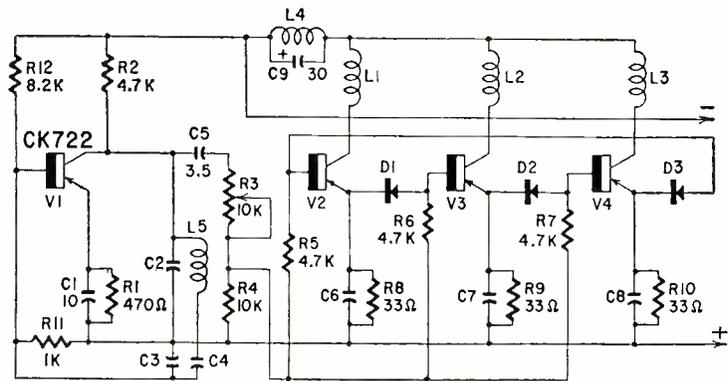

L1, L2, L3, L4—Selsyn windings: L4 is the field and L1, L2, L3 are armature windings (see text)
 C2, C3, C4, L5—Determine speed of motor. Common wire for L1, L2 and L3 is internal connection and selsyn must be disassembled to retrieve it.

Fig. 6—Three-phase power supply drives surplus selsyn.

C5 is adjusted for minimum ac voltage at V4's collector. Finally, when the amplifier is working, adjust C8 for bias according to the head manufacturer's specifications.

The oscillator transformer, which is hand-assembled, is a toroid wound on an Arnold A-066032-2 core obtainable from Arnold Engineering (610 E. Palisade Ave., Englewood, N. J.). Fig. 5-a shows how the coil is wound. Although it is very simple, be careful with the physical coil positioning. The close coupling of L1 to L2 and L3 is necessary and prevents distortion, and a coil modification may not produce an oscillator. Some 2N188-A's may require R17 to be larger than the value shown, whereas others would be burned up with this setting. If the bias oscillator is dead, check and recheck the coil polarities and then increase the value of biasing resistor R17.

At present, the toroidal core (89c each) is available only on a \$10 minimum order. If you would rather use a less expensive cylindrical core, use a Miller 22A000RB1 or a Miller 6210 TV horizontal oscillator ringing coil with the coil removed. This cylindrical configuration is difficult to wind and may lead to insufficient recording bias with some heads. However, it will work.

Before any adjustment is made to the completed amplifier, the record head must be properly biased according to the manufacturer's specifications. All three resonant circuits must be tuned to the same frequency if the amplifier is to work at all. If the bias is still low after the adjustments, L4 may be increased. Like the playback amplifier, C2, C4, C6, and R13 are matched to the head to get flat response. Fortunately, these adjustments are straightforward.

Selsyn motor and power supply

Small battery-operated recorders and phonographs have real motor problems. Small dc motors are not readily available, have low efficiency and do not operate at a constant speed. Often, hand-cranking the capstan will produce less wow and flutter than these motors. A few manufacturers are producing governor-controlled motors. General In-

dustries markets such a motor in their battery-operated turntable. Unfortunately, the governor plays havoc with the reproduce amplifier, causing much popping and static which must be filtered and shielded.


A very common war surplus Bendix Autosyn costing about \$3 is constructed like the huge three-phase industrial synchronous motors. It has a Y-connected armature winding, which is the stator, and a rotating field winding and is started like some induction motors by shorting the field winding. This motor easily pulls tape at 3.75 ips, drawing less than 40-ma current at 9 volts.

No special phase-shifting circuits are needed to get three-phase power. A simple trinary ring counter (Fig. 6) fed from an oscillator of three times the fundamental frequency powers the motor. Transistors V1, V2 and V3 in the three-phase supply circuit switch on in succession, simulating a three-phase square wave in motor windings L1, L2, and L3. Field winding L4 is in series with the collector supply and is excited by the motor current. V1 is in a standard Colpitts oscillator driving the ring counter.

Not all the component values for the three-phase supply are indicated. They depend upon the types of selsyns used and how they are loaded. They are easy to determine and their omission prevents beginners from running up a large transistor bill resulting from improper operating points. The emitter parallel R-C circuit has a time constant roughly one-fourth the period of the three-phase fundamental. The diodes steer the driving pulse from the transistor previously switched to conduction to the next one. Thus the voltage across the emitter resistor must be just high enough to let the following transistor switch on and not be blocked through the interconnecting diode. If you are moderately careful with the design, this synchronous motor configuration will behave like the costly ones, but will be more efficient.

The completed machine opens a new world of rallies, concerts, movie sound effects and fun almost impossible to enter with heavy machinery. **END**

More Bass from Smaller Loudspeakers

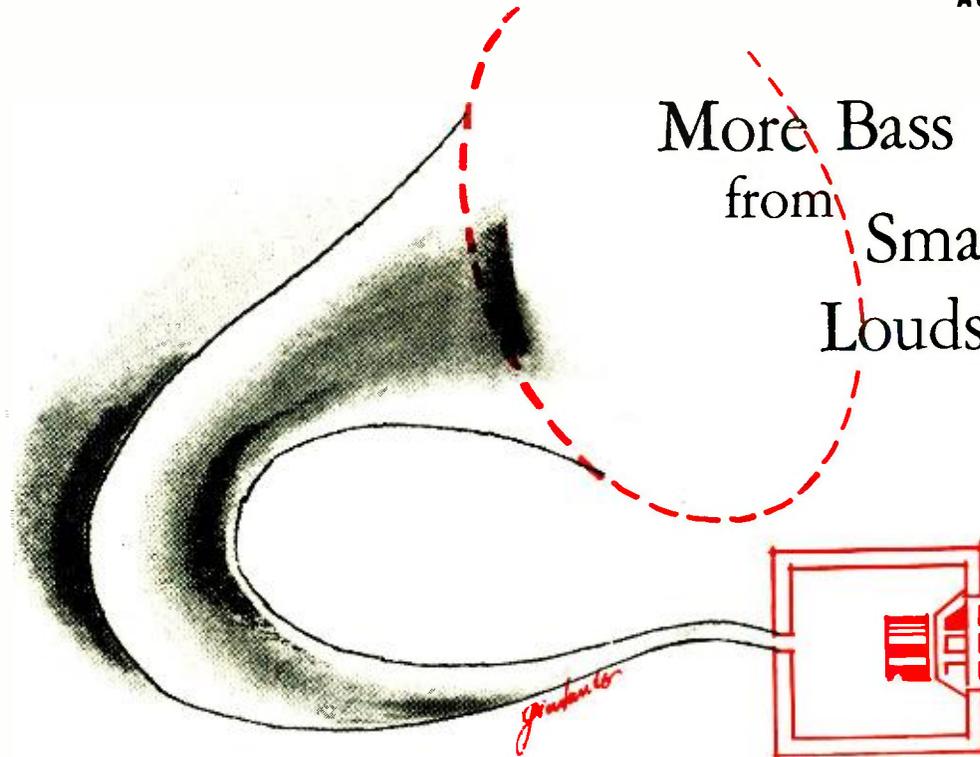

Part I—Don't be confused by the trend toward miniaturizing the loudspeaker and enclosure. This two-part article explains the operating principles of most of them

By **NORMAN H. CROWHURST**

THE popularization of hi-fi has made it increasingly desirable to get big bass from little speakers. But certain sound-propagation considerations indicate that a speaker must have a size inversely proportional to the lowest frequency it is expected to reproduce. However, the commercial urge has resulted in quite big-sounding bass coming from astoundingly small boxes.

There seem to be several ways of doing it, and the variety in the field has led to some confusion about the methods used. So here is an attempt to sort out this confusion. Three aspects of the problem appear:

1. Coupling the transducer so it can move enough air at these low frequencies without running into distortion.
2. Arranging for it to operate over a range of frequencies with as near as possible uniform efficiency.
3. Any moving diaphragm has two sides: do we utilize sound waves from both sides or only one of them?

Elaborating on these points a little: The first means we want to find a way, if possible, of moving a lot of air with a small diaphragm movement, because large mechanical movements are difficult to achieve without distortion. The alternative is to work from the other end, and get the big movement without distortion but obviously this is much more difficult.

It may be relatively easy to get large

air movement for a small drive, by using resonance, which is what an organ pipe does. But we do not want all low frequencies, regardless of original source, to sound like an organ pipe; all frequencies *within a range* should be reproduced accurately and uniformly.

Second, any diaphragm has a resonant frequency due to the compliance (or springiness) of its suspension acting with its mass (or weight). Without being enclosed in any way, it will move most readily at this frequency. But the acoustic loading that the enclosure provides can control this, rendering the radiation efficiency practically constant over a range of frequencies. The point to watch is how the method of enclosing it influences the frequency range of the complete loudspeaker, as compared to its free-air resonance.

The low frequencies are radiated by big waves—much bigger than most of the loudspeaker units used to reproduce them (although the complete enclosure may be big). When the diaphragm moves forward, it momentarily produces pressure at its front and rarefaction behind it. Something has to be done to stop these two effects from cancelling before a wave is radiated.

This is the third question: Some ways use only the radiation from one side of the speaker and “lose” the other, while others find a way of turning the “phase” of one so it augments the other, instead of cancelling (at low frequencies, where it is needed).

To get the clearest possible picture of how the different methods work, we will start here and see first how the well-tried types achieve their objective, following on with the newer smaller types to see what they do.

Horns

These work by carefully controlling the propagation of the sound wave for several wavelengths (of the lowest frequency) from the loudspeaker diaphragm until it reaches the air (Fig. 1). The horn allows an intense sound wave at its throat to develop gradually into a big-volume wave at its mouth. But to do this the horn's expansion has to be very gradual (following an exponential or some similar “law” or growth rate), and it has to finish up rather more than a half wavelength long across the mouth.

Because of the high intensity of the sound wave “loaded” onto the active side of the diaphragm, which has the property of an acoustic “resistance” (at all frequencies above horn “cutoff”), the free-air diaphragm resonance is well controlled and usually does not show up at all. Also the opposition to motion produced by the horn throat is much greater than that on the other side, so the speaker delivers practically all its work into the horn. Little sound comes from the free side, and it can be left open or protected by a cover with a vent in it.

But a horn for low frequencies gets
(Continued on page 86)

**CREI's Extension Division offers Engineering Technicians and Engineers a combination of courses in advanced electronic engineering technology.*

**The program is designed to meet your present and future employment requirements and to increase your professional status and earning power.*

-this CREI College-level Home Study Program in Electronics is Comparable in Technological Content to Advanced Residence Courses!!!!

The CREI home study program is the culmination of 33 years of working closely with leading companies and Government agencies in the critical field of electronics. This accredited program is designed for men already employed in a technical capacity in the electronics industry.

This CREI college-level program is comparable in technological content to advanced residence courses. You may complete the program in 2 to 4 years, depending on the amount of free time you can devote to study, and the courses you choose.

For several years the electronics industry has suffered a serious shortage of technical personnel with

modern advanced education, and there is every indication that this shortage will increase in the years ahead. New jobs are being created daily through the application of electronic developments in missiles, space exploration, automation, instrumentation, computers, telemetering and many other fields. These positions must be filled by men with modern advanced education, which fact is evidenced by the experience of the CREI Placement Bureau, where the demand for graduates and advanced students far exceeds the supply. It is of interest to note that Help Wanted ads frequently specify "CREI education or equivalent."

CREI is recognized by industry and government

Another reason why CREI men are respected and eagerly sought by industry and Government agencies alike is the accreditation and enthusiastic approval accorded the CREI home study program in advanced electronics. We co-founded the National Council of Technical Schools, and we were among the first three technical institutes whose curricula were accredited by the Engineers' Council for Professional Development. Further, the U.S. Office of Education lists CREI as "an institution of higher education."

Of equal importance, we believe, is the appreciation expressed by industry and government for the CREI programs. Dozens of major electronics organizations, ranging from industrial giants to the Government's Voice of America, have agreements with CREI for enrollment of students under company sponsorship. U.S. Navy electronic personnel in the number of 5,240 are enrolled in CREI extension programs. The British Royal Air Force, Army and Navy have approved CREI courses under their tuition assistance plan. The following companies comprise only a partial list of the organizations which not only recommend CREI study but actually, in many cases, pay all or part of the tuition for employees taking CREI courses:

National Broadcasting Company
Jerrold Electronics Corporation
Pan American Airways
Radio Corporation of America
Canadian Aviation and Electronics
Federal Electric Corporation
The Martin Company
Voice of America
Canadian Broadcasting Corporation
Northwest Telephone Company
Commercial Cable, Incorporated
Canadair Limited
Columbia Broadcasting System
All America Cable and Radio
Canadian Marconi
Mackay Radio
United Air Lines
Gates Radio Company
Mohawk Airlines
Florida Power and Light Company

RESIDENCE SCHOOL

... in Washington, D.C., for those who can attend classes. Day and evening classes start at regular intervals. Graduates earn AAS degree in 27 months. Electronics experience is not required for admission.

QUALIFICATIONS FOR CREI ENROLLMENT FACTS ABOUT TUITION, REGISTRATION

If you have a high school diploma or equivalent, basic electronic training and practical experience in electronics, you meet the minimum requirements for enrollment. Tuition is reasonable and may be paid monthly, if you wish. Veterans qualify for this program under the GI bill.

Over 20,500 CREI students find home study convenient and profitable

You can pursue the CREI program while you continue your regular full-time job. You study at home during hours chosen by you. You are not rushed and you have plenty of time to do your best.

The courses are prepared in easy-to-understand format, and the CREI staff of experienced instructors guides your progress all along the way. These instructors stand ready to assist you whenever you need help. You will find our personal assistance and guidance efficient and helpful, because 33 years of experience in home study teaching enables us to anticipate questions in our lesson material.

Many CREI students have learned that they do not have to wait until they have completed the program to realize significant improvement in their status and income. The very fact that you are ambitious enough to pursue this college-level program enhances your opportunities for rapid promotion. Project leaders and supervisors recognize the value of CREI education.

How you benefit from CREI program of home study

CREI students are electronic engineers and technicians engaged in every phase of electronics. They are in research laboratories and manufacturing plants. They work on the design, development and production of the latest computers; on the latest military and civilian aircraft; on the electronic equipment associated with the Nation's missiles and space exploration efforts; on communications equipment of all kinds; they maintain electronic equipment for the air lines, the Government and private corporations. You will find CREI students in all 50 States and in most foreign countries of the free world.

To the serious-minded and ambitious CREI student our home study program offers a series of important benefits:

1. You gain a solid college-level education in advanced electronic engineering technology; you keep abreast of continuous new developments in the field.
2. You can gain higher status and enjoy the increased respect of your associates.
3. You facilitate more rapid professional advancement with corresponding significant increases in pay.
4. You gain the personal satisfaction that comes from working and communicating intelligently with your technical colleagues and superiors.

WRITE FOR DETAILED 44-PAGE BOOK of curricula and other information about CREI, entitled "Insurance for Your Future in the New World of Electronics." USE POSTAGE-PAID CARD ATTACHED, or write to Dept. 1407-G.

The Capitol Radio Engineering Institute

*ECPD Accredited Technical
Institute Curricula
FOUNDED 1927*

3224 16th Street, N.W.
Washington 10, D.C.
Dept. 1407-G

AUDIO—HIGH FIDELITY

(Continued from page 81)

very big. True, it can be folded, so the narrower section is accommodated in space around the mouth area, but the mouth must still be big and the "development" requires considerable volume.

Another thing about horns: their smoothness of performance—which a good one invariably has—is dependent on the gradual expansion being continued right on after the sound leaves the horn. A horn in the middle of a room loses most of its smoothness, because of the abrupt change the wave finds when it leaves the mouth. To get the best out of a horn, it should be placed in a corner, so the room walls continue the effective horn mouth contour.

Even this is an idealization (for most listeners): the ideal corner should be the *only corner in the room*. The wave should leave the horn mouth and keep going, indefinitely. But most rooms have four sides, a floor and a ceiling, which block this indefinite progress of the wave. Even so, a horn takes a lot of beating in the larger rooms.

A horn has an acoustic cutoff frequency—related, not to any resonance effect, but to sound propagation—below which it fails to couple the sound waves from the diaphragm to the air at the mouth. This means the air load on the diaphragm disappears below this frequency, and some measure is advisable so that such low frequencies do not reach the speaker from the amplifier.

"Infinite" box baffle

This idea may seem rather crude to a horn man. It is simply a baffle, such as was originally used to extend the edges of the unit, brought around to enclose the back completely (Fig. 2). To be truly infinite, the box on the back needs to be infinitely large. In this hypothetical case, the loudspeaker unit radiates equally on both sides, but one side is totally enclosed in a box, while we listen to the other side. So only half the speaker's acoustic output is used.

A practical "infinite baffle" uses a box of *finite* size. The size chosen is such that the ideal is not departed from to any great extent. This has the effect of making the speaker do a little more work in compressing the air inside the box than it does in radiating sound from the front. Also the air in the box acts as an additional "spring" on the diaphragm, which raises the speaker's resonant frequency slightly.

The mechanical Q of the loudspeaker is determined by several contributing factors: amplifier damping; efficiency of the conversion of electrical into acoustical power; any mechanical resistance due to viscosity in the suspension (which has to be built in), and any acoustic resistance due to "stuffing" put into the box.

With a struggle, the resonant boom can just about be held down by all these means acting together. Then the low-frequency roll off occurs immediately below the resultant resonant

Fig. 1—The horn is relatively large compared to wavelength of lowest frequency it must radiate.


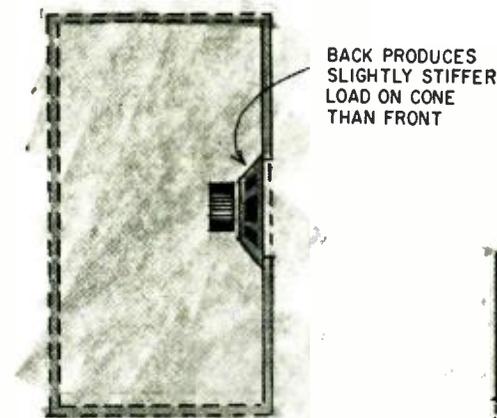
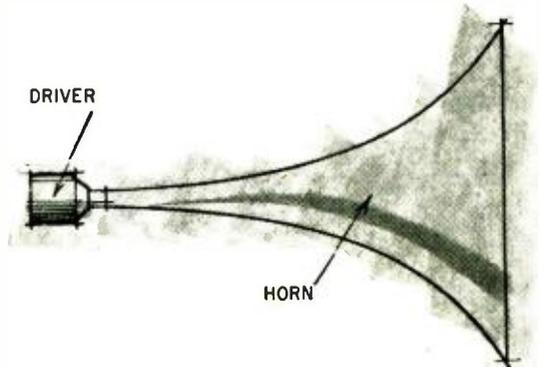


Fig. 2—An "infinite" baffle is merely a large box shutting in the speaker's rear.

Fig. 3—The air coupler's length is based on wavelength, rather than volume.

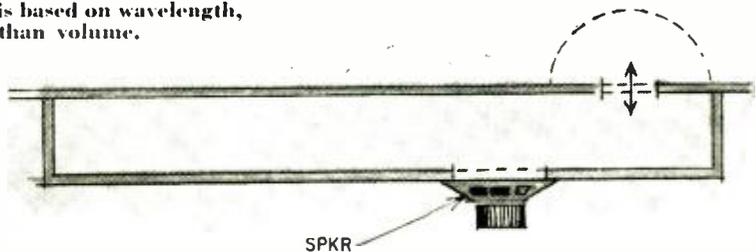

frequency (speaker unit *in its box*), at a rate that is basically 12 db per octave, like an L/C high-pass filter.

So if we start with a speaker resonance of 70 cycles and the enclosure pushes this up to 90 or 100, the complete system falls off at 12 db per octave below this; will be about 12 db down at 50 cycles, 24 db down at 25 and 28 db down at 20. How can we get the response down lower? More of this anon. But whereas the horn's range depends mainly on its "acoustical dimensions," the infinite baffle is basically limited by the resonance of the unit driving it.

Air coupler

Another development that appeared some years ago was the air coupler. This utilized propagation principles to change the characteristic acoustic

SOUND ABSORBENT BAFFLES

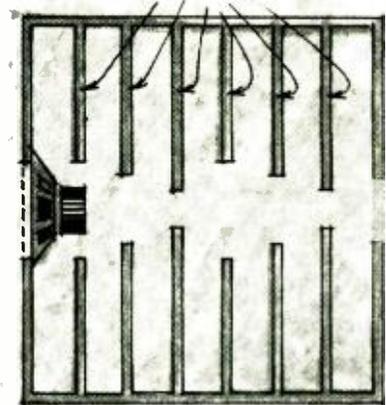


Fig. 4—Baffle is another way to eliminate back radiation.

impedance (Fig. 3). The back of the speaker was free. Without the coupler between, half the energy would be radiated from both sides. But at the lowest frequency the coupler is a quarter-wavelength long, so the "free" effect of the tube opening into the room is converted into a "stiff" mass of air at the speaker diaphragm. In this way, it uses all its energy pushing the air in the tube and very little gets out the back.

Setting the quarter-wavelength frequency at the speaker resonance effectively loads the resonance out of existence. Careful design is needed to avoid undesirable effects at higher frequencies, where the same tube is successively half, three-quarters and more wavelengths long. The principal limit to this idea's useful application seems to be that it is essentially a built-in type,

AUDIO—HIGH FIDELITY

not just simply a piece of furniture.

Baffle

Mr. Hartley's Baffle ("box baffle") achieves a similar objective by a different method (Fig. 4). The back of the speaker is basically free, but it differs from the horn or air coupler in that the front feeds sound out direct, while the back is "treated" so its sound is absorbed instead of coming around to cause interference. The back of the cone meets air that is rendered extra "free" in this case, allowing the work to be done in front.

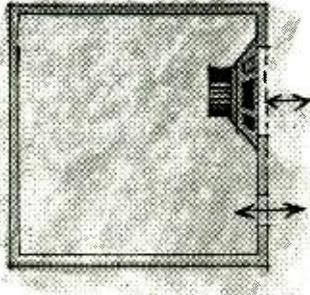


Fig. 5—Bass reflex is first attempt at radiation from front and back of cone.

The horn and air coupler use different kinds of loading on the front; the back is just normally free, by not being so loaded. The infinite baffle and the Baffle feed the wave directly from the front, in the first case loading the back with the box (which reduces efficiency) and in the second case making it extra free (which may slightly increase efficiency). In neither of them is motion of air from *both sides* used.

Bass reflex

This was the first type which attempted to use the motion at the back, instead of getting rid of it somehow. The enclosure contains a port (Fig. 5), of controlled dimensions, so the weight (technically called mass) of air moving back and forth in the port is about equal to that of the speaker diaphragm. This way, at resonant frequency, the air in the box is alternately compressing and rarefying, while the motion at both diaphragm and port is *in phase*.

This means, at this particular frequency (below which the system "drops dead" at about 18 db per octave), about twice as much air is moved to form a sound wave, for the same diaphragm movement. At higher frequencies, the air in the box absorbs the back radiation just like the infinite baffle. The common practice is to design the box and port dimensions to have about the same resonance as the speaker unit, so it loads down this primary resonance, much as the air coupler did.

This method produces two secondary resonance effects, rather like an over-coupled circuit in radio, resulting in a peak below and above the basic resonance frequency. Various methods have been adopted to level these resonances, such as the acoustic resistance unit introduced by Goodmans, which

improved the performance of the bass-reflex type, eliminating the boom from the "boom-box."

Back-loaded horn

Although the horn protagonists won't like this, there are certain similarities between the bass-reflex and the back-loaded horn that make the comparison useful. As in the bass reflex, the higher frequencies are radiated directly from the front, and their back radiation is absorbed in the box directly behind the cone (Fig. 6). Below a certain frequency set by the acoustic crossover, the volume of this box, coupling the

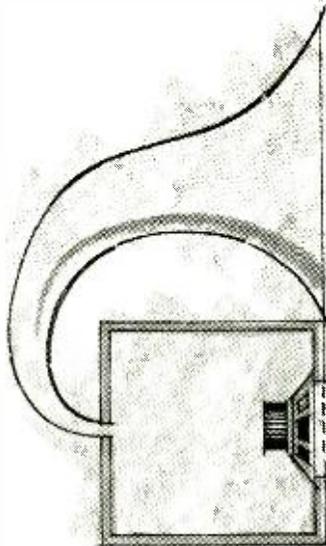


Fig. 6—Back-loaded horn radiates front of speaker for high end, horn for low end.

horn to the back of the diaphragm, ceases to absorb in this way and causes the horn to load the back more than the front. In this range the unit behaves like any other horn.

So the back-loaded horn radiates from the front above acoustic-crossover frequency and from the back below it. Its low-frequency cutoff is governed, as in the simple horn, by the horn's dimensions. It differs from the bass reflex in that the point where back and front both contribute is at the acoustic-crossover frequency, which is well above the lowest frequency radiated, and in that the speaker resonance is relatively unimportant.

Like any other horn, it needs placing in a corner. The corner location does help to camouflage the size of a horn. While the horn protagonist will tell you "you can always find a corner—or two for stereo," my experience with American living rooms says that corners are not always conveniently available. And the best of the alternative types, infinite baffle and bass reflex, can give good low-frequency performance in a practical comparison at an economy in size.

So far we have studied early steps toward smaller enclosures. Next month we will look at acoustic suspension, duct-loaded reflex, variable mass and other methods of reducing enclosure size.

TO BE CONTINUED



The Beautiful Schober CONSOLETYPE

—only small organ with two full 63 note key-boards and 22 stops. Requires only 2-3/2" floor space! Commercial value approximately \$1600 or more.

BUILD THIS SUPERB
Schober **ORGAN**
FROM SIMPLE KITS
and save over 50%

Give Your Family A Lifetime of Musical Joy With A Magnificent Schober Electronic Organ!

Now you can build the brilliant, full-range Schober CONSOLETYPE or the larger CONCERT MODEL with simple hand tools! No skills are needed; no wood-working necessary. Just assemble clearly marked electronic parts guided by step-by-step instructions. You build from kits, as fast or as slowly as you please . . . at home, in your spare time — with a small table serving as your entire work shop.

Pay As You Build!

Start building your organ at once, investing just \$18.94! The superb instrument you assemble is as fine, and technically perfect, as a commercial organ . . . yet you save over 50% on quality electronic parts, high-priced labor, usual store mark-up!

Free Booklet

Send for 16-page booklet in full color describing Schober organs you may build for home, church or school — plus articles on how easy it is to build your own organ and how pleasant it is to learn to play. Also available is 10" LP demonstration record (price \$2.00 — refundable on first order). Send for literature. No obligation and no salesman will call.

THE GREAT CONCERT MODEL meets specifications of American Guild of Organists

Mail This Coupon For FREE Schober Literature And Hi-Fi Demonstration Record TODAY!

The Schober Organ Corp., Dept RE-5
2248 Broadway, New York 24, N.Y.


Please send me FREE Color Booklet and other literature on the Schober organs.
 Please send me the 10" hi-fi Schober demonstration record. I enclose \$2.00 (refundable on receipt of my first kit order).

Name.....
Address.....
City..... Zone..... State.....


MIXING and MATCHING To AUDIO INPUTS

By HAROLD REED

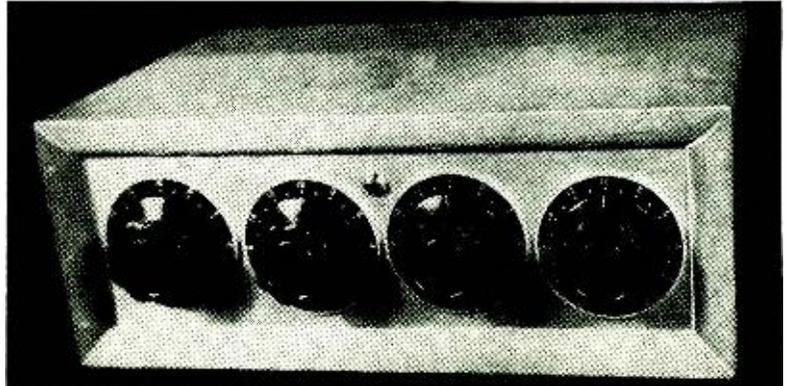Use the proper circuit and you can connect 500-600-ohm lines, low-impedance microphones and multiple low-impedance sources to an amplifier's or recorder's high-impedance input



The mixer diagrammed in Fig. 5.

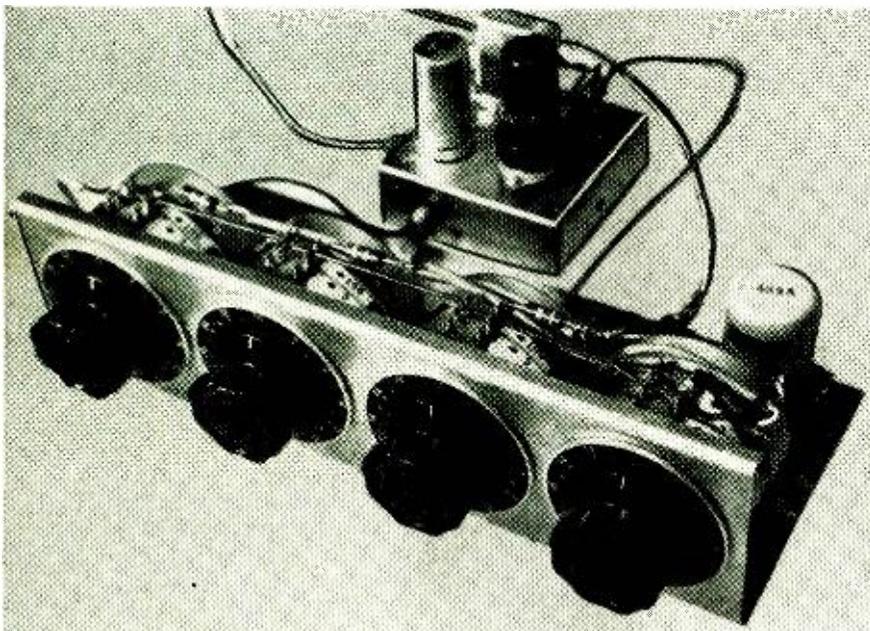

Four T-attenuators, a single transformer and four resistors are all you need inside the mixer's case.

MANY hi-fi enthusiasts and audio hobbyists have tape recorders and audio amplifiers that have only a single input channel for microphones, tuners, etc. This input channel is usually of unbalanced (one side grounded) high-impedance design.

You want to feed several audio sources into this recorder or amplifier simultaneously, or have it handle low-impedance inputs. Several useful methods for doing this are discussed in this article. First let us consider how we can use a low-impedance source such as a 50- or 250-ohm microphone with such an amplifier.

What we need is some kind of matching circuit between the two devices. An

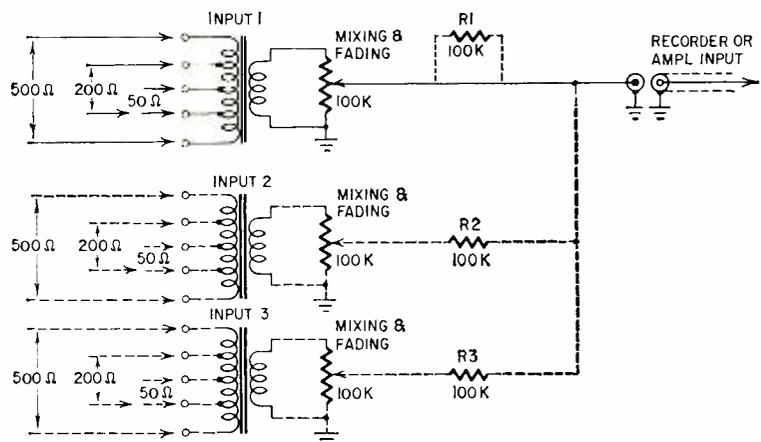


Fig. 1—Input transformers are best for matching low-impedance sources to a high-impedance input.

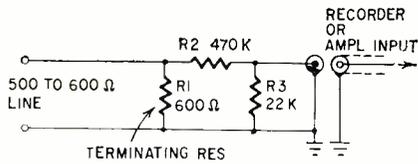


Fig. 2—Transformerless network matches 500-600-ohm line to amplifier input.

input transformer is best for this purpose, as shown in Fig. 1. Use a transformer that provides several input impedances. Miniature and subminiature transformers are also satisfactory. A volume control connected across the transformer's secondary provides mixing and fading facilities. Additional inputs with transformers and mixing-fading controls are shown in dashed lines and may be added as required. The 100,000-ohm resistors are isolating units and make interaction between the circuits negligible.

Line to high impedance

If you want to connect a 500-600-ohm line to the recorder's or amplifier's high-impedance input, try the transformerless circuit shown in Fig. 2. The line is terminated with a 500- or 600-ohm resistor, R1, which is then bridged with the resistive input R2, R3. Values for R2 and R3 are selected to provide the proper signal voltage to the input.

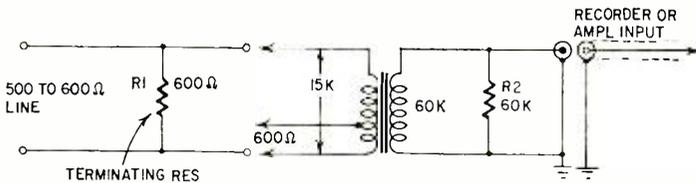


Fig. 3—For balanced matching of line to high impedance try this arrangement.

If R2's value is increased, there is a greater voltage drop across it and less voltage at the high-impedance input; decreasing R2 results in a lower voltage drop and greater signal voltage at the high-impedance input of the recorder or amplifier. If the signal voltage from the low impedance source is too low, R2 and R3 can be eliminated. This circuit, of course, unbalances the source.

Where the low-impedance line's balance must be maintained, a line-to-grid transformer should be used (see Fig. 3). The line may be terminated in an appropriate resistance and then bridged with the high-impedance tap of the transformer. This will allow several amplifiers, with high-impedance input transformers, to be bridged across the line without causing appreciable loading or mismatch. To get proper termination and correct matching for a single amplifier input, connect the line to the 600-ohm tap on the primary instead of the high-impedance tap. Of course, if you do this a 500-600 ohm terminating resistor is not needed.

To feed a 500-600-ohm line to the recorder or amplifier input without changing the signal magnitude appreciably or unbalancing the line, a 1-to-1 impedance ratio transformer provides isolation without attenuation. See Fig. 4 for the circuit.

Low-impedance mike

A convenient method for feeding a single, low-impedance microphone into a high-impedance input is to use a microphone cable transformer which has a primary tapped for 30-50 and 200-500 ohms and a secondary designed to work into a tube's grid circuit. Keep the cable on the transformer's secondary side as short as possible to minimize hum pickup. Any reasonable length of cable can be used on the low-impedance side. Use shielded cable with the shield carried straight through to the high-impedance input's ground.

Four-channel mixer

We would often like to feed several low-impedance microphones or lines to the audio system's high-impedance input and at the same time avoid the cost of the three or four input transformers used in Fig. 1. Several mixing circuits can be used, but one of the most satisfactory is the series-parallel system shown in Fig. 5. It lets you ground each channel, preventing hum pickup and cross-talk. Also the insertion loss for as many as four channels is only 6 db. The circuit shown is intended for

four 250-ohm inputs using T-attenuators. For other impedances, determine the proper component part values with the following formulas:

The value for resistors R2 is equal to $R(N-3)/N$, where R is the input impedance (250 ohms in Fig. 5) and N the number of inputs or channels (4 in Fig. 5). The output impedance, R_o, is equal to $4R(2N-3)/N^2$, where R and N are equivalent to the values in the foregoing formula and N² is the number of channels squared. Parts values are included in the circuit. These values are given as derived from the equations. They are not so critical that they must be exactly as shown. Some standard value close to these figures will do.

The transformer in Fig. 5 is a low-impedance line-to-grid type. Its voltage stepup helps make up for the mixer insertion loss and with some audio systems it may be possible to connect the mixer directly to the recorder or amplifier input.

If there is not enough output from the mixer, you can insert a voltage amplifier after transformer T. If you use a standard preamp for this, any phono equalizing resistors should be removed.

When laying out and wiring any of the circuits discussed in this article, follow the usual construction techniques for shielded cable and for proper grounding. END

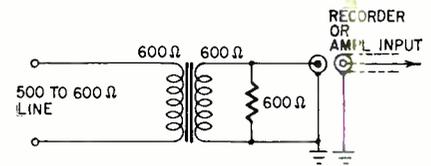


Fig. 4—Little attenuation and balanced matching are the features of this simple circuit.

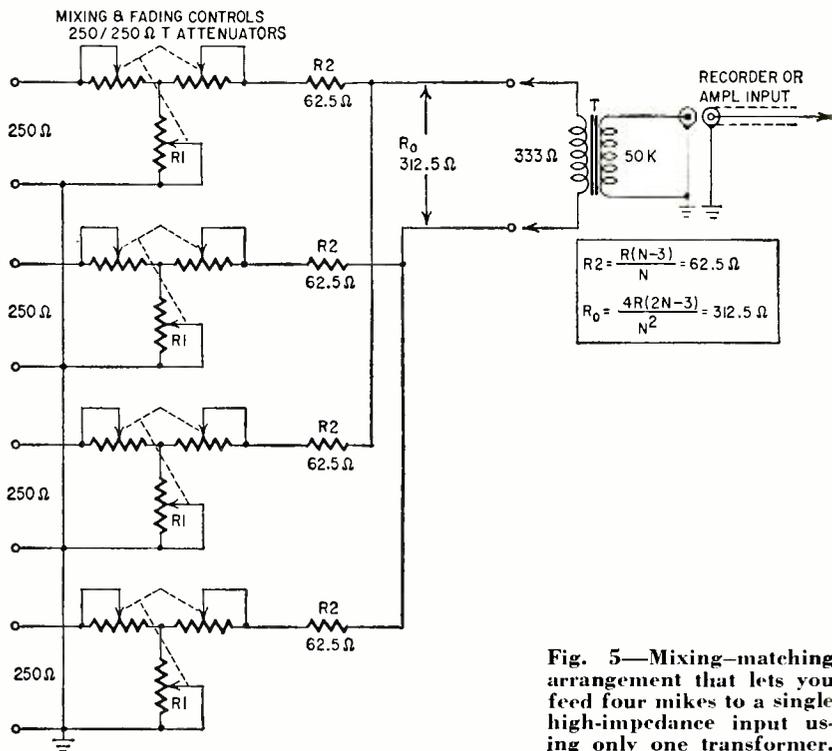


Fig. 5—Mixing-matching arrangement that lets you feed four mikes to a single high-impedance input using only one transformer.

SUPERIOR'S
NEW MODEL 77

VACUUM TUBE VOLTMETER

WITH NEW 6" FULL-VIEW METER

Compare it to any peak-to-peak V.T.V.M. made by any other manufacturer at any price



Model 77—VACUUM TUBE VOLTMETER
Total Price \$42.50—Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary!

- ✓ Model 77 completely wired and calibrated with accessories (including probe, test leads and portable carrying case) sells for only \$12.50.
- ✓ Model 77 employs a sensitive six inch meter. Extra large meter scale enables us to print all calibrations in large easy-to-read type.
- ✓ Model 77 uses new improved SICO printed circuitry.
- ✓ Model 77 employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability.

AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN AC VOLTMETER: Measures RMS values if sine wave, and peak-to-peak value if complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.

Model 77 comes complete with operating instructions, probe and test leads. Use it on the bench—use it on calls. A streamlined carrying case, included at no extra charge, accommodates the tester, instruction book, probe and leads. Operates on 110-120 volt 60 cycle. Only.....

- ✓ Model 77 uses a selenium-rectified power supply resulting in less heat and thus reducing possibility of damage or value changes of delicate components.
- ✓ Model 77 meter is virtually burn-out proof. The sensitive 400 microampere meter is isolated from the measuring circuit by a balanced push-pull amplifier.
- ✓ Model 77 uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

SPECIFICATIONS:

• DC VOLTS—0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance. • AC VOLTS (RMS)—0 to 3/15/75/150/300/750/1,500 volts. • AC VOLTS (Peak to Peak)—0 to 8/40/200/100/800/2,000 volts. • ELECTRONIC OHMMETER—0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms. • DECIBELS—10 db to + 18 db, + 10 db to + 38 db + 30 db to + 58 db. All based on 1 db = .006 watts (6 mw) into a 500 ohm line (1.73v). • ZERO CENTER METER—For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5 75/150/375 750 volts at 11 megohms input resistance.

\$42⁵⁰
NET

Superior's
New Model 80

20,000 OHMS PER VOLT ALLMETER

THE ONLY 20,000 OHMS PER VOLT V.O.M. SELLING FOR LESS THAN \$50 WHICH PROVIDES ALL THE FOLLOWING FEATURES:



Model 80—ALLMETER... Total Price \$42.50—Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary!

- ✓ 6 INCH FULL-VIEW METER provides large easy-to-read calibrations. No squinting or guessing when you use Model 80.
- ✓ MIRRORED SCALE permits fine accurate measurements where fractional readings are important.
- ✓ CAPACITY RANGES permit you to accurately measure all condensers from .00025 MFD to 30 MFD in addition to the standard volt, current, resistance and decibel ranges.
- ✓ HANDSOME SADDLE-STITCHED CARRYING CASE included with Model 80 Allmeter at no extra charge enables you to use this fine instrument on outside calls as well as on the bench in your shop.

NOTE: The line cord is used only for capacity measurements. Resistance ranges operate on self-contained batteries.

- A built-in Isolation Transformer automatically isolates the Model 80 from the power line when capacity service is in use.
- Selected, 1% zero temperature coefficient metallized resistors are used as multipliers to assure unchanging accurate readings on all ranges.

SPECIFICATIONS:

7 D.C. VOLTAGE RANGES: (At a sensitivity of 20,000 Ohms per Volt) 0 to 15 75/150 300 750 1500/7500 Volts.
6 A.C. VOLTAGE RANGES: (At a sensitivity of 5,000 Ohms per Volt) 0 to 15/75 150 300/750/1500 Volts.
3 RESISTANCE RANGES: 0 to 2,000/200,000 Ohms. 0-20 Megohms.
2 CAPACITY RANGES: .00025 Mfd. to .3 Mfd., .05 Mfd. to 30 Mfd.
5 D.C. CURRENT RANGES: 0-75 Microamperes, 0 to 7.5/75/750 Milliamperes, 0 to 15 Amperes.
3 DECIBEL RANGES: -6 db to +18 db + 11 db to + 38 db + 31 db to + 58 db

Model 80 Allmeter comes complete with operating instructions, test leads and portable carrying case. Only.....

\$42⁵⁰
NET



Model TV-50A—Genometer. Total price—\$47.50—Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary!

GENOMETER

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:

A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV

R. F. SIGNAL GENERATOR: The Model TV-50A Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

VARIABLE AUDIO FREQUENCY GENERATOR: In addition to a fixed 400 cycle sine-wave audio, the Model TV-50A Genometer provides a variable 300 cycle to 20,000 cycle peak wave audio signal.

BAR GENERATOR: The Model TV-50A projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

THE MODEL TV-50A comes absolutely complete with shielded leads and operating instructions.

CROSS HATCH GENERATOR: The Model TV-50A Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

DOT PATTERN GENERATOR (FOR COLOR TV) Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

MARKER GENERATOR: The Model TV-50A includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc. (3579 Kc. is the color burst frequency).

\$47⁵⁰
NET

EXAMINE BEFORE YOU BUY!
USE APPROVAL FORM ON NEXT PAGE

SUPERIOR'S NEW MODEL TW-11

STANDARD PROFESSIONAL TUBE TESTER



Model TW-11—Tube Tester
 Total Price\$47.50
 Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

★ Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Subminors, Proximity fuse types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.

★ The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURE


SEPARATE SCALE FOR LOW-CURRENT TUBES: Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a handsome portable saddle-stitched Texon Case. Only**\$47⁵⁰**

SUPERIOR'S NEW MODEL 82A

Multi-Socket Type

TUBE TESTER

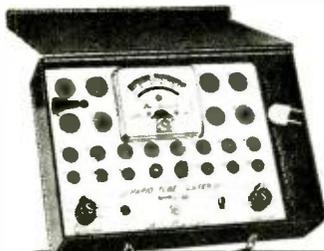

Model 82A—Tube Tester
 Total Price\$36.50
 Terms: \$6.50 after 10 day trial, then \$5.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

TEST ANY TUBE IN 10 SECONDS FLAT!

- ① Turn the filament selector switch to position specified.
- ② Insert tube into a numbered socket as designated on our chart (over 600 types included).
- ③ Press down the quality button—

THAT'S ALL! Read emission quality direct on bad-good meter scale.

SPECIFICATIONS

- Tests over 600 tube types
- Tests OZ4 and other gas-filled tubes
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence
- Dual Scale meter permits testing of low current tubes
- 7 and 9 pin straighteners mounted on panel
- All sections of multi-element tubes tested simultaneously
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82A will outperform similar looking units which sell for much more — and as proof, we offer to ship it on our examine before you buy policy.

To test any tube, you simply insert it into a numbered socket as designated, turn the filament switch and press down the quality switch — **THAT'S ALL! Read quality on meter.** Inter-element leakage if any indicates automatically.

Model 82A comes housed in handsome, portable Saddle-Stitched Texon case. Only**\$36⁵⁰**

SUPERIOR'S NEW MODEL 83

C. R. T. TESTER

TESTS AND REJUVENATES ALL PICTURE TUBES

ALL BLACK AND WHITE TUBES

From 50 degree to 110 degree types — from 8" to 30" types.

ALL COLOR TUBES

Test All picture tubes—in the carton—out of the carton—in the set!

• Model 83 is not simply a rehashed black and white C.R.T. Tester with a color adapter added. Model 83 employs a new improved circuit designed specifically to test the older type black and white tubes, the newer type black and white tubes and all color picture tubes.

• Model 83 provides separate filament operating voltages for the older 6.3 types and the newer 8.4 types.

• Model 83 employs a 4" air-damped meter with quality and calibrated scales.

• Model 83 properly tests the red, green and blue sections of color tubes individually—for each section of a color tube contains its own filament, plate, grid and cathode.

• Model 83 will detect tubes which are apparently good but require rejuvenation. Such tubes will provide a picture seemingly good but lacking in proper definition, contrast and focus. To test for such malfunction, you simply press the rej. switch for Model 83. If the tube is weakening, the meter reading will indicate the condition.

• Rejuvenation of picture tubes is not simply a matter of applying a high voltage to the filament. Such voltages improperly applied can strip the cathode of the oxide coating essential for proper emission. The Model 83 applies a selective low voltage uniformly to assure increased life with no danger of cathode damage.

Model 83 comes housed in handsome portable Saddle Stitched Texon case—complete with sockets for all black and white tubes and all color tubes. Only**\$38⁵⁰**



Model 83—C.R.T. Tube Tester
 Total Price\$38.50
 Terms: \$8.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary.

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Try any of the instruments on this or the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. **No Interest or Finance Charges Added!** If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC, INC.

Dept. D-779, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligations.

Model 77..... Total Price \$42.50
 \$12.50 within 10 days. Balance \$6.00 monthly for 5 months.

Model 80..... Total Price \$42.50
 \$12.50 within 10 days. Balance \$6.00 monthly for 5 months.

Model TV-50A..... Total Price \$47.50
 \$11.50 within 10 days. Balance \$6.00 monthly for 5 months.

Model TW-11..... Total Price \$47.50
 \$11.50 within 10 days. Balance \$6.00 monthly for 5 months.

Model 82A..... Total Price \$36.50
 \$6.50 within 10 days. Balance \$6.00 monthly for 5 months.

Model 83..... Total Price \$38.50
 \$8.50 within 10 days. Balance \$6.00 monthly for 5 months.

Export Division: Rocke International Corp., 13 East 40th St., New York 16, N. Y.


Name.....

Address.....

City..... Zone..... State.....

All prices net. F.O.B., N. Y. C.

Shirt-pocket Reflex for Local Listening

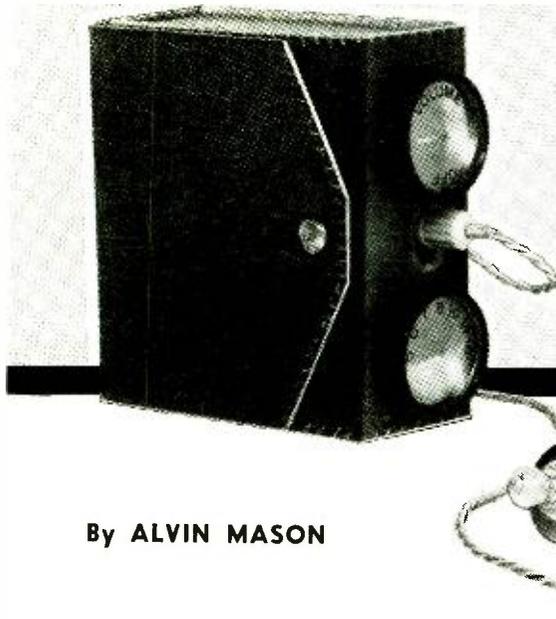

By ALVIN MASON

Tiny 2-transistor unit puts the local stations in your pocket, and it doesn't use an external antenna

HERE'S a simple, low-cost pocket reflex radio with a little different twist in circuitry and a big twist in performance. It has no external pickup leads and uses only two transistors.

The receiver measures only 3 x 3 x 1¼ inches and has low drain for longer battery life. The circuit is non-critical, with no rf feedback coupling to cause oscillations, yet sensitive to the very weakest signals.

Transistor V1 is a Philco rf type, chosen for its high cutoff frequency and low operating voltage.

V2 is another Philco transistor used for that extra punch in the audio output. It is a subminiature type specially selected for good performance at low voltage.

T2, also a Philco item, measures only about ½ inch square and has a shielding can to prevent stray rf coupling. Also, this shielding permits more flexible parts layout without fear of oscillations.

How it works

The receiver (Fig. 1) is a reflex type in which transistor V1 amplifies both the received rf signal and the detected af signal. Here's how it goes: C1 and L1 form a tuned circuit that picks up the desired rf signal. It is coupled to L2 and fed to V1 for amplification. The amplified rf signal


is fed through T2 and is detected by diode D. (The rf signal cannot pass through audio transformer T3.) The detected af signal developed across R2 is fed back to V1's base, where it is again amplified. This time it is passed through T2's primary (the rf coil presents negligible impedance to the audio signal) and on to T3's primary. From there it goes to T3's secondary and on to V2 for final

amplification. The amplified signal from V2 is fed to a headphone.

Construction

Construction is simple and straightforward. No special rules to follow, just good wiring practice. The set could be made smaller or larger if desired. However, if a smaller model is built, wiring may become more difficult.

A 3-inch-square piece of solid bake-

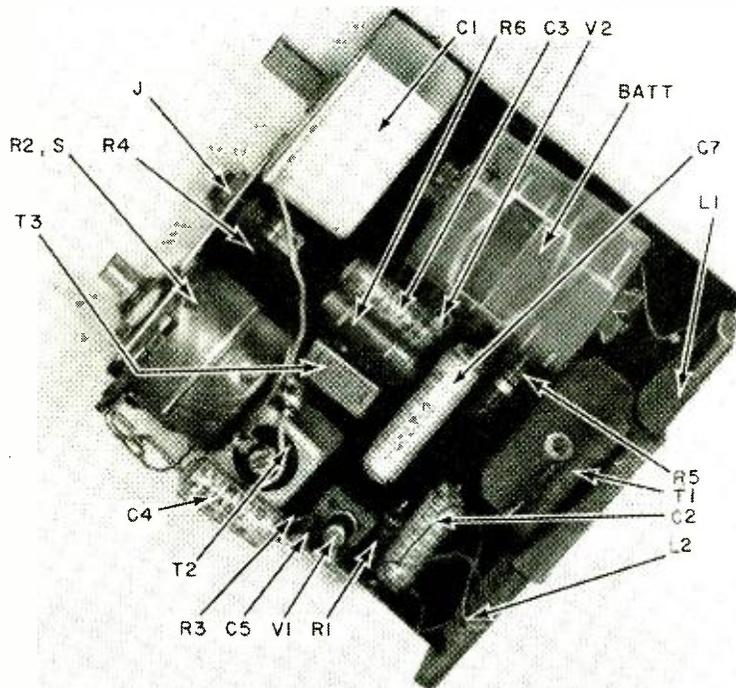


Chassis layout is compact, but not crowded.


- * 2-transistor reflex
- * simple construction
- * shirt-pocket size
- * no external antenna needed

Tests conducted by a member of the staff of RADIO-ELECTRONICS showed that the receiver has plenty of volume and picks up seven stations in Brooklyn, N. Y. There is some background hiss since af gain is high and rf gain relatively low. However, when the received station is loud enough, it overrides this interference. Conclusion: a set to build where the extreme gain and selectivity of a 2-stage if is not needed.

BENCH

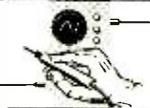

TESTED

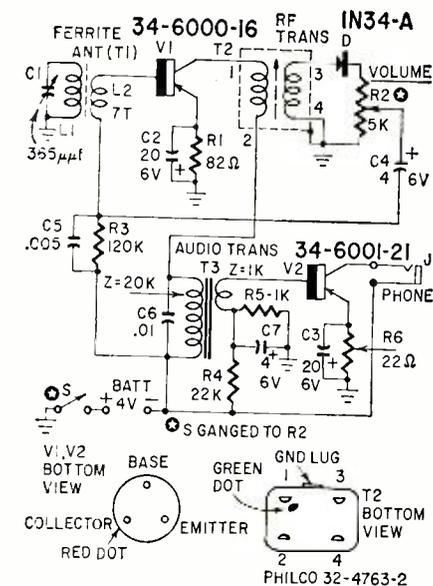

- R1—82 ohms
- R2—miniature pot, 5,000 ohms, with spst switch
- R3—120,000 ohms
- R4—22,000 ohms
- R5—1,000 ohms
- R6—22 ohms
- All resistors 1/2-watt 10% unless noted
- C1—miniature tuning capacitor, 365 μf (Lafayette MS-274 or equivalent)
- C2, 3—subminiature electrolytic, 20 μf, 6 volts
- C4, 7—subminiature electrolytic, 4 μf, 6 volts
- C5—.005 μf, disc ceramic
- C6—.01 μf, disc ceramic
- BATT—4 volts (RCA VS308 or equivalent)
- D—1N34-A
- J—miniature phone jack
- S—spst on R2
- T1—flat ferrite antenna (L1) (Miller No. 2004 or equivalent) with 7 turns No. 22 enameled wire (wound on ground end (L2)—see text)
- *T2—rf transformer (Philco 32-4763-2)
- T3—audio transformer: primary, 20,000 ohms; secondary, 1,000 ohms (Argonne AR-104 or equivalent)
- *V1—34-6000-16
- *V2—34-6001-21
- Transistor sockets (2) (Lafayette MS-395 or equivalent)
- Perforated bakelite board (Lafayette MS-304 or equivalent)
- Earphone (Telex type 18140 or Lafayette MS-368)
- Miscellaneous hardware
- *Available from authorized Philco distributors

Fig. 1—Circuit of the reflex receiver.

lite board is used for the chassis. Or a piece of perforated bakelite can be used to avoid drilling holes for each component. All parts are mounted on one side of this board, with their leads running through to the opposite side where they are connected "printed-circuit" style. That is, all leads and connections are close to the bottom of the chassis.

The tuning capacitor, volume control and phone jack are mounted on a 3 x 1 3/4-inch piece of light aluminum bent over and riveted or screwed to the bottom of the chassis board. In the final wiring this metal bracket will be grounded by the return side of the phone plug so all bare leads must be kept from contacting it.

The two transistor sockets are easy to mount. Simply run the solder prongs through holes in the bakelite board and bend flat against the underside.

The battery is mounted by simply anchoring two No. 18 solid wires at each end of it and soldering directly to the terminals. This is done because the battery will seldom have to be

changed. However, snap fasteners may be used to allow easier replacement.

Although wiring is simple with only two transistors, there is still the possibility of making errors. But you should have no trouble if you check each connection before proceeding to the next.

When connecting the diode, grip the leads with long-nose pliers to dissipate heat from the soldering iron. A black ring, the letter "k" or a "+" sign indicates the cathode end of the diode.

Antenna coil L1 comes with a Masonite mounting base which is considerably longer than the antenna itself. Remove this base by cutting away the cellophane-tape holders.

After the base is removed, tape up the tap that appears a few turns up from the ground end of the antenna. This tap is not used. Now wind 7 turns of No. 22 enameled wire from this spot to the ground end. Wind directly over and in the same direction as the an-

inch thick. Apply a thin coat of plastic resin cement to one side of the board; then press on a sheet of leatherette material of the design and color you desire. Work out all wrinkles and air bubbles. Now coat the other side of the cardboard with cement and leave standing till thoroughly dry—about 2 hours.

After drying, mark off each measurement according to Fig. 2. Cut out three holes for the controls, then fold along the dotted lines. Glue each section into place and clamp it by placing a small weight on top of the case.

When the case has dried, pull the lid flap down tightly and punch two holes with an icepick or punch at the points marked F. With long-nose pliers crimp each half of a stud fastener into these holes. And the case is finished.

Now use it

With all wiring completed and the battery in place you are ready for the

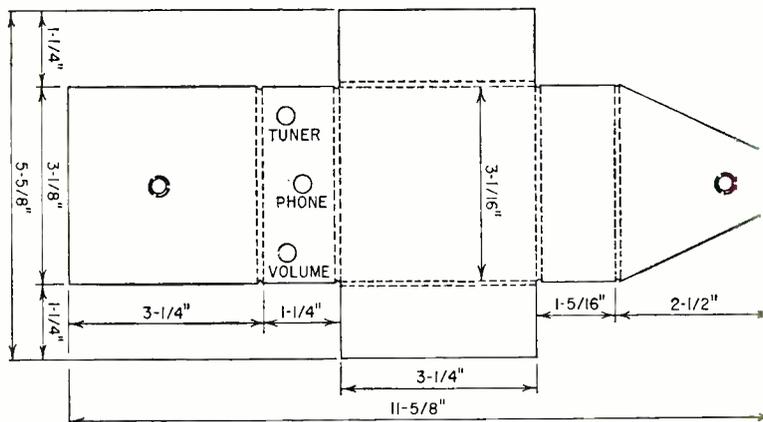


Fig. 2—Layout for the receiver's case.

tenna winding. You now have an antenna transformer, with the added secondary (L2) feeding V1's base.

The antenna is mounted by forming a cardboard loop about 1 inch wide around the center of the coil and fastening to the chassis.

Transformer T2 has five solder lugs which extend through holes in the chassis and are bent over. Before bending them, however, make a pencil mark on the top of the can to correspond with the green dot on its bottom. The green dot indicates proper hookup, and cannot be seen after the transformer is in place.

T3 is a subminiature audio transformer, 20,000 to 1,000 ohms impedance, with four color-coded leads. It is mounted with two twist prongs extending from its bottom. Position this transformer so that its primary and secondary windings are in proper relation to T2 and V2.

Making the case

A plastic box makes a good case. Or, if you wish to make a case like mine, simply follow the instructions in Fig. 2. This makes a very neat job and adds considerable class to the receiver.

Use a piece of cardboard big enough for the entire cutout and about 3/64

transistors. Cut the leads of each transistor to about 3/8 inch. Make sure each lead is plugged into its proper socket terminal.

Turn the switch on and advance the volume control to full power. Rotate the tuning knob. If all wiring is correct, stations should come in loud and clear.

If stations are not received satisfactorily or if no stations are heard try these tests: Touch your finger to V2's base connection. A loud pop should be heard in the earphone. Try the same test on V1's base. This time a loud squeal should be heard.

If both these tests give the listed effect, check the antenna hookup. New components are seldom defective, so these should be checked last.

In operation you will find that the antenna is somewhat directional and should be rotated slightly for best results. Also, transformer T2 has a tuning slug which may be adjusted to peak the receiver to a particular section of the broadcast band. Or this slug can be removed entirely for distributed gain throughout the band.

The unit is a great little receiver for only two transistors. And it should prove well worth the effort put into building it.

END

NEW DEVELOPMENTS IN RADIO CIRCUITRY

Several manufacturers have incorporated novel circuits in their equipment

By HENRY O. MAXWELL

ENGINEERING developments and innovations in modern audio and radio equipment tend to follow cyclic patterns. For fairly long periods, circuitry in new equipment will be static. Then suddenly new circuits blossom forth from nearly every chassis. This month we discuss some of the most interesting ones we've seen recently.

Unusual FM-AM detector switching

The detectors in AM-FM tuners and receivers have become pretty much standardized as two separate circuits. The FM detector is either a ratio detector or a Foster-Seeley discriminator. The AM detector and avc circuit invariably uses a half-wave diode which may be a germanium diode, a section of a multipurpose tube or the grid-cathode circuit in the FM limiter. The two detectors are generally completely isolated and easy to spot with one glance at the diagram.

Blonder-Tongue engineers have come up with a couple of novel innovations combining the functions of many of the components in FM-AM detector circuitry. Fig. 1-a is the detector circuit in the model R-98 FM-AM radio. When S3 is in the FM position, we have a completely conventional balanced ratio detector with diodes D1 and D2 developing an audio voltage at the junction of load resistors R15 and R14. Reservoir capacitor C31 swamps out voltages developed by residual AM on the FM if signal. R18 and C32 form the audio de-emphasis network. R13 and R17 compensate for minor differences in the characteristics of the detector diodes.

Switching to AM removes D1 from the circuit and converts D2 to a conventional half-wave AM and avc detector. Fig. 1-b shows the AM detector with all inactive components eliminated for simplicity. R19 is the diode load and C27 is the rf bypass capacitor. The FM de-emphasis network remains in the audio circuit but its effect is negligible on the average AM program.

Fig. 2-a is the corresponding detector circuit in the T-88 FM-AM tuner. The tuner has an ac-dc power supply with one side of the power line connected to the B-minus bus and the chassis so its output must be completely isolated from the chassis to prevent a shock hazard on the amplifier to which the

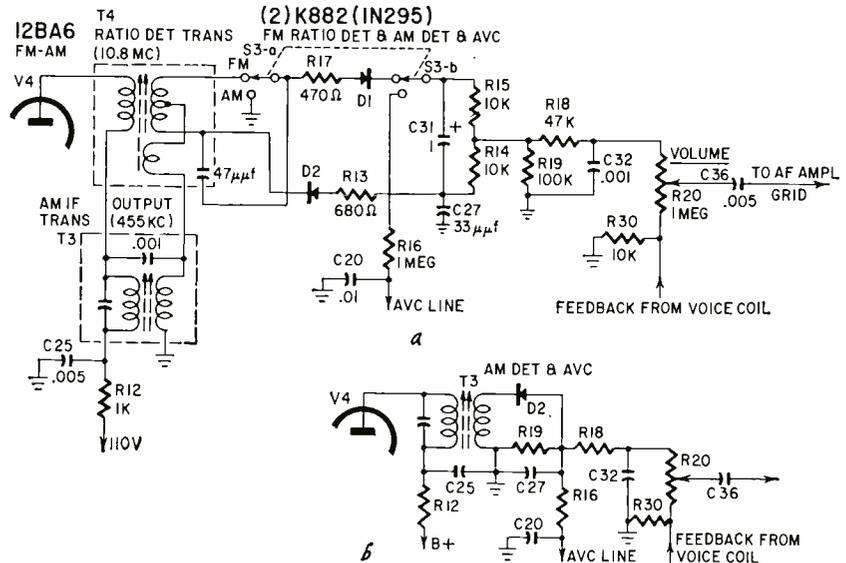


Fig. 1-a—Detector circuitry of the R-98 AM-FM radio with switch S-3 in FM position; b—simplification of circuit in AM position.

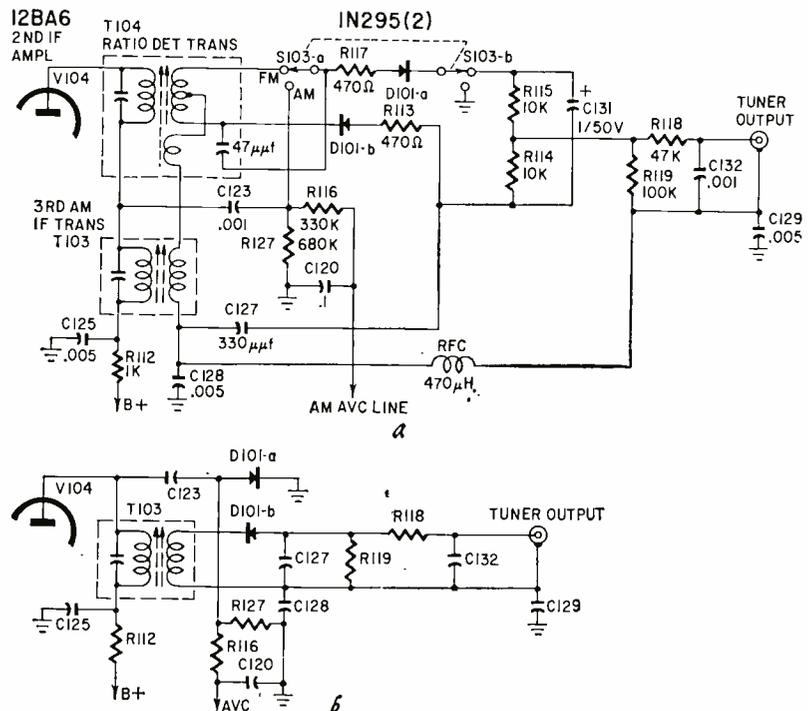


Fig. 2-a—Detector circuitry of T-88 AM-FM tuner with S103 in FM position; b—simplified AM circuit.

tuner might be connected. The ratio detector circuit is similar to that in the R-98 receiver but the low end of the tertiary winding of T104 is isolated from ground by C128 and C129 and is connected to the mid-point of the detector load resistors through an rf choke and R119. The audio output is taken from across R119.

Fig. 2-b is the simplified AM detector circuit. Diode D101-b is the AM detector developing an audio voltage across R119 which functions as the AM detector load. This circuit is isolated from the chassis and B-minus, so a separate source of avc voltage is required. D101-a is the avc diode coupled to the if amplifier plate through C123. It develops a dc voltage across R127 proportional to signal strength. This voltage is filtered by R116 and C120 and fed to the first and second if amplifier.

Novel tuning indicator

The RCA model TPM-13 AM-FM stereo combination uses the novel neon type tuning indicator shown in Fig. 3. The indicator is a NE-51 neon lamp in series with the plate of the triode section of the 19T8 operating as the indicator amplifier or control tube. (The diodes in the 19T8 are used as FM and AM detectors.)

The grid of the 19T8 is connected to the grid of the third FM if amplifier and limiter and to the AM avc line through 22-megohm isolating resistors. Under no-signal conditions, the tube draws enough plate current through the NE-51 to cause it to glow brightly. When a signal is tuned in, the negative avc voltage developed across the AM detector load (R14 and R15) or the FM limiter grid resistor (R7) reduces the plate current drawn through the NE-51 and decreases its brilliance. The tuning controls are adjusted for minimum brilliance. The 10-megohm resistor, R16, draws just enough "keep-alive" current through the NE-51 to keep it conducting at all times. At high volume levels, the neon indicator tends to oscillate at a frequency determined by the value of C10.

6-volt hybrid radio

The Motorola model 406 auto radio is the first hybrid set we've seen that operates from a 6-volt storage battery. This set, using a 6BE6 converter, 6BA6 if amplifier, 6CR6 detector, avc and first audio, 6BF6 driver and 2N176 transistor output stage, is easily mistaken for a 12-volt model. Unlike the 12-volt versions that have a maximum of 12-14 volts available for the tubes and transistors, this set has a transistor type 50-volt B-supply for the tubes while the audio and oscillator transistors operate from the 6-volt battery.

Fig. 4 is the diagram of the power supply and audio circuits in the model 406. The power supply oscillator is a conventional circuit using tickler feedback to the base. Approximately 60 volts ac is developed in the secondary

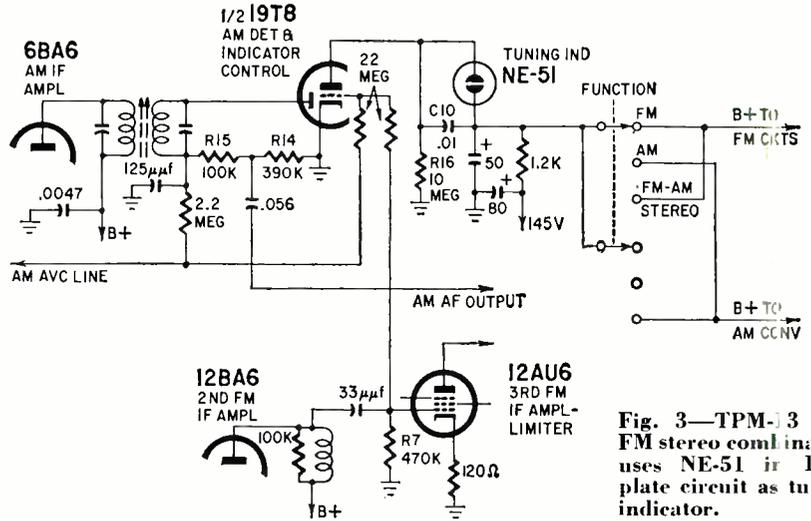


Fig. 3—TPM-13 AM-FM stereo combination uses NE-51 in 19T8 plate circuit as tuning indicator.

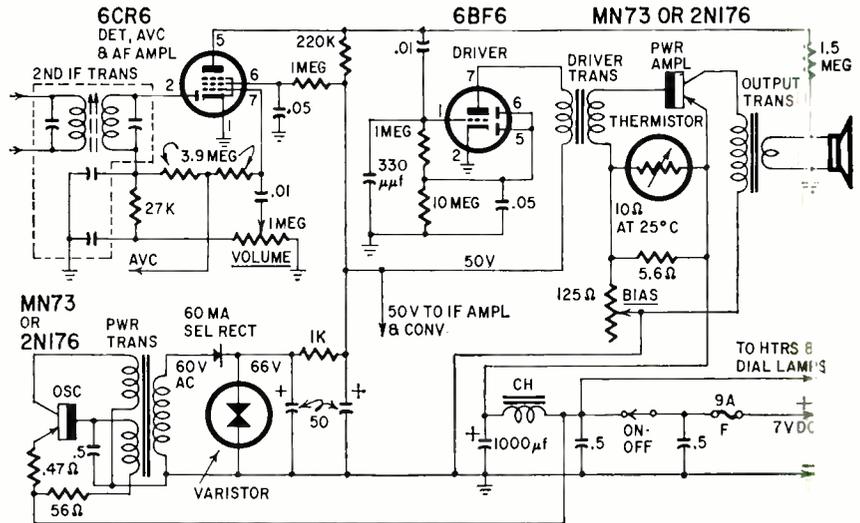


Fig. 4—Motorola 406 radio uses MN73 or 2N176 transistor to provide 50-volt B-supply.

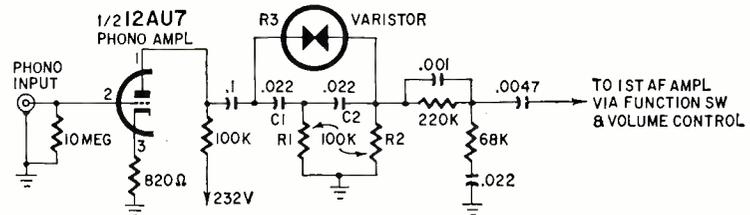


Fig. 5—Varistor short-circuits high-pass filter at high signal levels, allowing rumble filter to work only at low signal levels.

of the power transformer. It is rectified and filtered to deliver 50 volts B-plus to the tubes. This voltage is stabilized by the varistor across the rectifier.

The grid of the 6BF6 driver is biased by contact potential of the paralleled diodes (pins 5 and 6). This is a logical circuit development because cathode bias would reduce the effective plate voltage—which is already limited—and other forms of bias would be more expensive and likely to cause trouble.

Automatic rumble filter

Some of the new Zenith radio-phono combinations feature a phono rumble filter circuit that operates only during low-level passages when rumble is most noticeable. During high-level bass pas-

sages, rumble is masked by the program material so the filter is automatically bypassed to permit full-range bass to come through.

Fig. 5 is the circuit in Zenith's 11A21 chassis. The rumble suppressor consists of a two-section high-pass filter C1-R1, C2-R2 bypassed by varistor R3. (A varistor is a nonlinear semiconductive element whose resistance is determined by the voltage applied across it.) With no signal or with a low-level bass input from the record, the varistor's resistance is high and the signal takes the path of least resistance through the filter. During high-level passages the varistor's resistance is low, effectively shorting out the filter and allowing full bass to come through. END

DON'T WASTE MONEY
on instruments you don't need!
CUT TEST TIME IN HALF!



Down-to-earth training in
MODERN TEST INSTRUMENTS
and how to use them fast and right!

The most important factor in TV-radio or industrial electronic service is a complete working knowledge of instruments—which ones you really ought to have—which ones to use for specific jobs—how to substitute one for another—and how to follow professional time-saving procedures every step of the way. And that's exactly the kind of practical training these two Rinehart manuals bring you! 570 pages and over 300 clear pictures provide above-average instrument training that equips you for better, faster work and higher earnings.

1 A COMPLETE MANUAL OF MODERN INSTRUMENTS

A money-saving guide to every type in common use!

This 234-page BASIC ELECTRONIC TEST INSTRUMENTS is a complete working guide to practically every instrument in common use. Teaches you the advantages and disadvantages of various types; helps you get more for your instrument dollars and avoid buying those you don't really need; outlines instrument construction and operation; explains instrument features and the particular applications for each; tells how to calibrate and care for them, and how to select the ones most suitable for your particular needs. Price separately \$4.95.

2 New guide to TIME-SAVING TEST PROCEDURES

How to troubleshoot better, faster and more accurately!

BASIC ELECTRONIC TEST PROCEDURES Manual brings the kind of "brass tacks" training that helps you locate troubles in a jiffy. Teaches you exactly what instruments to use and exactly how, where and why to use them; how to substitute one instrument for another and how to develop time- and money-saving test methods all along the line. Subjects include Current Checks; making measurements of Power, Capacitance, Inductance, Resistance, A.P., R.P., Phase, Distortion and Modulation; checking Sensitivity, Frequency, A.V.C. Voltage, Operating Voltages, etc. Covers time-saving visual alignment techniques—even transmitter and industrial electronic test procedures. 216 pages, 190 how-to-do-it pictures and dozens of step-by-step troubleshooting procedures. Price \$6.50 separately.

SAVE \$1.45
on this complete 2 vol. instrument library!

PRACTICE 10-DAYS FREE!

Dept. RE-70, RINEHART & CO., INC.
232 Madison Ave., New York 16, N. Y.

Send books indicated below for 10-day FREE examination. In 10 days I will either remit price shown (plus postage) or return books postpaid and owe you nothing.

Basic Electronic TEST INSTRUMENTS, \$1.95 separately

Basic Electronic TEST PROCEDURES, \$6.50 separately

Check here for **MONEY-SAVING COMBINATION OFFER**. Send both manuals at special price of only \$10.00 for the two (regular price \$11.45 . . . you save \$1.45). Payable at rate of \$1.00 plus postage after 10 days if you decide to keep books and \$3.00 a month for 2 months until \$10.00 has been paid. (**EXTRA SAVINGS!** Send \$10 with order and Rinehart pays postage. 10-day return privilege with money refunded.)

Name

Address

City, Zone, State

OUTSIDE U. S. A.—\$5.45 for TEST INSTRUMENTS; \$7.00 for TEST PROCEDURES; \$11.00 for both. Cash only but money refunded if you return books in 10 days.

RADIO

RESERVE POWER FOR SURVIVAL

Be ready in an emergency. Keep mercury batteries on hand for your transistor radio

By **SOL D. PRENSKY***

EVERY owner of a transistor radio can have the added assurance provided by a survival-shelter radio by using mercury batteries as a reserve power source for the receiver. Using mercury batteries as a reserve, rather than a spare set of carbon-zinc batteries, instantly frees you from the bugaboo of poor shelf life that makes the ordinary (carbon-zinc) battery so unreliable.

The excellent shelf life of mercury batteries is not as widely known or appreciated as it should be. Instead of only the few months during which we can rely on unused carbon-zinc batteries, mercury batteries can sit on the shelf for 2 or 3 years or longer and still be usable.

To determine which mercury battery to use for a reserve, a simplified battery listing is provided. It classifies the more popular types of transistor batteries according to their general description, and avoids the confusion generated by a multiplicity of manufacturer numbers.

In the table, the General Description and NEDA No. columns list the 7 most popular zinc-carbon types. The next four columns give the manufacturer's number of each type. The final column shows the mercury equivalents available as direct replacements for the zinc-carbons.

The Mercury Equivalent column contains only four entries, indicating that only four of the seven zinc-carbon battery classes are directly replaceable by mercury batteries. However, these four replacements cover at least 92 transistor radios. (A list of these radios by manufacturer model number is avail-

able from the battery manufacturers listed.)

The photo shows two mercury types, the 1.4-volt penlight and the 9-volt oval-ended, that are stocked by most dealers. The other two mercury types, the 1.4-volt size D and the 22.5 volt, are available but may have to be ordered from the manufacturer.

For the three classes for which no exact mercury replacement is available, the same principle of reserve power still can apply. The set owner can keep a replacement set of zinc-carbon batteries on hand and check or replace them periodically, or he might fit the equivalent mercury battery with alligator clips to act as a more dependable reserve than the original carbon-zinc. Or perhaps, direct replacements for these three classes may become available shortly. In any case, the problem should not be too difficult for those who realize the importance of reserve power for survival. **END**



Two typical mercury batteries: right—mercury equivalent of the 1.5-volt penlight cell; left—mercury equivalent of the popular 9-volt zinc-carbon battery.

*Assistant Professor, Electrical Engineering, Fairleigh Dickenson University, Teaneck, N. J.

MERCURY REPLACEMENT BATTERIES FOR PORTABLE RADIOS

General Description	NEDA No.	Zinc-Carbon				Mercury		
		Mallory	Burgess	Eveready	RCA	Mallory	Eveready	RCA
1.5 volts, flashlight (standard size D)	13	M-13R	230	A100	VS336	RM-42R	—	—
1.5 volts, flashlight (medium size C)	14	M-14R	130	635	VS335	—	—	—
1.5 volts, penlight (size AA)	15	M-15R	930	1015	VS334	ZM-9	E-9	VS313
9 volts, cylindrical (snap contact, 1 x 1 x 1 3/32)	1600	M-1600	P6M	226	VS300A	—	—	—
9 volts, rectangular (snap contact, 1 3/8 x 1 3/8 x 2 3/4)	1602	M-1602	2M6	246	VS305	—	—	—
9 volts, oval (snap contact, 1 1/2 x 1 1/8 x 1 3/32)	1604	M-1604	2U6	216	VS312	TR-146R	E-146	VS312
22.5 volts, flat (flat contact, 1 1/2 x 3/8 x 2)	215	M-215	U15	412	VS084	RM-412R	—	—


RADIO

How Much Rf?

IS A radio signal coming off that antenna? When this knob is turned, is there more or less signal? Such questions are commonplace to the ham operator and mobile service technician. This little untuned field-strength meter answers them, and cheaply too.


Hook a pair of diodes to a short pickup antenna, place it where the rf is to be measured and connect the rectified signal (which is proportional to the incoming rf) to a meter. The indicating meter may be mounted at the operating table and the pickup head placed 50 feet or more away.

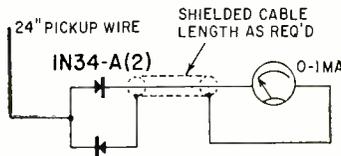The signal picked up by the head is rectified and carried to the indicating meter as direct current. Since the instrument performs one specific function,



determining the presence of rf, and since the cost of parts is low, there is no need of providing for plug-in features, calibration or removal of components, except the meter itself. It, of course, can be switched to other functions. Transistors, tubes and batteries are eliminated by using a diode pair. No resistors are necessary—unless a strong rf signal that might damage the meter is measured—then the usual shunting resistors for the meter should be used or a less sensitive meter connected. Capacitors are not mandatory, even on the output of the diodes. The capacitance of the shielded cable furnishes enough storage action for radio frequencies.

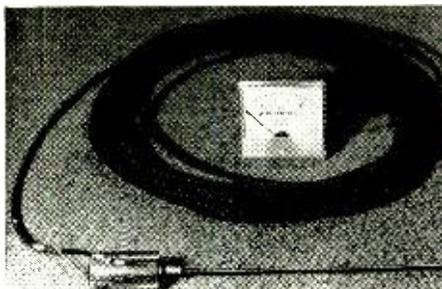When the pickup head was located about 100 feet from an aerial which was



connected to a 40-watt transmitter, the meter indicated 1 ma when the transmitter's output was properly adjusted, and zero when the transmitter was improperly adjusted or the antenna disconnected from the transmitter. By placing the pickup head in a location remote from the transmitter itself, the actual radiation from the transmitting antenna can be determined.—Irvin C. Chapel.




from stand



to hand . . . instantly

introducing the world's smallest cardioid dynamic microphone

UNIDYNE III
by
SHURE

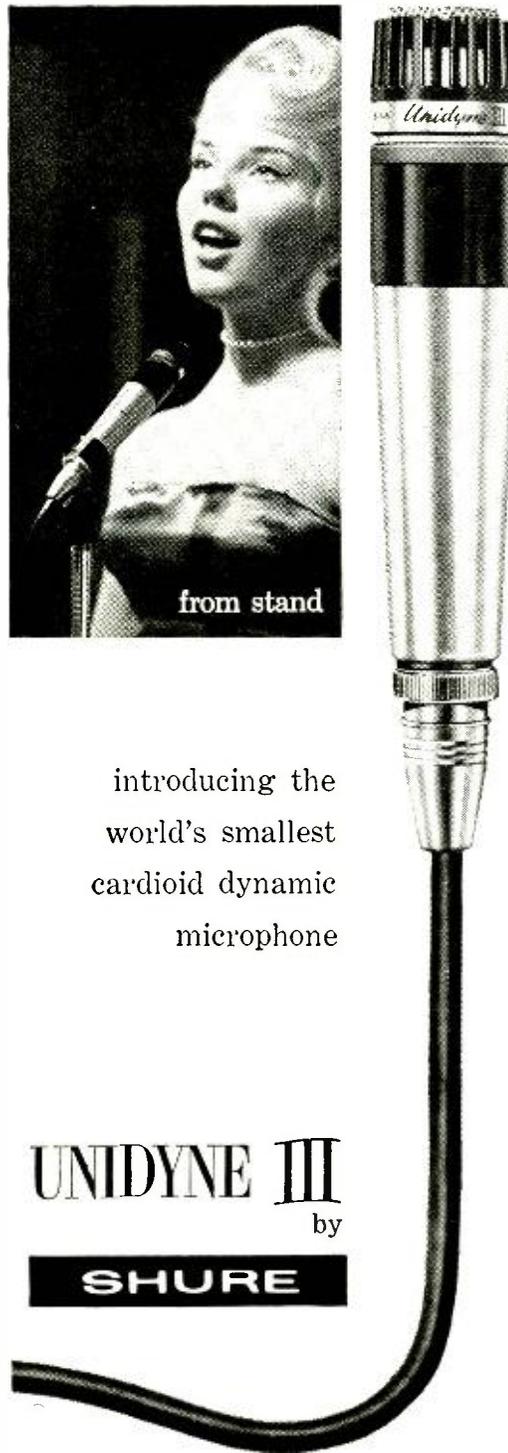

EVERYTHING YOU WANT IN A QUALITY CARDIOID MICROPHONE . . . AND THEN SOME!

Compact size . . . modern design . . . wide response . . . superior feedback suppression . . . uniform cardioid pattern . . . ruggedness . . . reliability; you name it, SHURE has designed it into the dramatic new Unidyne III.

50% SMALLER — Less than 6" x 1 1/4", 0.6 lb.!

PERFECTION IN PERFORMANCE — Moving coil design with truly uniform cardioid pick-up pattern. Response: 50 to 15,000 cps. Up to 75% greater distance from sound source. Impressive feedback suppression.

MAXIMUM VERSATILITY — unobtrusive size, dual impedance, light weight, instant change from stand to hand, and wide-range response make it ideal for faithful reproduction of voice or music, indoors or out, for P.A., tape recording . . . anywhere fine quality is required.

RUGGED AND RELIABLE — Famous SHURE quality. Takes 6-foot drop-tests and still performs according to specifications!

Literature available:

SHURE BROTHERS, INC.
222 Hartrey Ave., Evanston, Ill.

\$50.00

Professional Net

HELP WANTED?

—you'll get what you want if you advertise in RADIO-ELECTRONICS Opportunity Adlets. Rates as low as \$5. Write

RADIO-ELECTRONICS

154 West 14th Street

New York 11, N. Y.

INTERFERENCE— CAUSES, REMEDIES and LOCATION

Problems with TV sets and radios can generally be solved by finding out what causes the interference as the first step in eliminating it

By **FORREST H. FRANTZ, SR.**

ELECTRICAL interference is annoying to the broadcast listener, exasperating for the shortwave listener and frustrating to hams. Natural electrical interference cannot be controlled; man-made interference can. The effects can often be eliminated at the receiver, but in some cases interference must be eliminated at the source.

To cope effectively with electrical interference, it is important to understand how it's generated and transmitted. When the type is recognized, the source can be found and eliminated.

The causes of man-made interference fall into four general categories:

1. Switching
2. Discharges
3. Radio-frequency leakage
4. Harmonic generation

Switching noise occurs at electrical switches and commutators. Typical offenders are: light switches; thermostats on electric irons, heating pads and home heating systems; switches and flashers on advertising signs; commutators on electric motors, industrial equipment and home appliances, and poor electrical connections.

This interference is caused by arcing when an electrical circuit is opened or closed. Fig. 1-a shows the idealized waveform for switch operation, with its characteristic steep rise and fall. Fig. 1-b shows a practical waveform. The fall time is increased and current decay is irregular. The arc radiates a complex signal which contains many frequencies.

An intermittent break in a poor

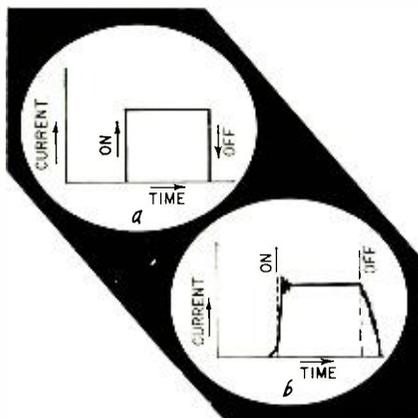


Fig. 1—Waveform of: a—ideal and b—practical switch operation.

electrical connection can be extremely harassing because arcs are continuously struck and extinguished in a haphazard way. Arcing is a type of electrical discharge that occurs at relatively high currents (generally 100 ma or more).

Glow discharges such as those associated with neon and fluorescent lamps occur at intermediate currents (generally a few microamperes to several milliamperes). Glow discharge tubes are ordinarily ac-operated. The ac voltage acts as a switch for the discharge. The resulting interference looks like the waveforms of Fig. 2. The voltage increases from zero to the glow striking voltage. The tube fires and the current drops in an oscillatory manner till the voltage reaches the extinguishing value. Again a series of harmonic-rich oscillations occur as the current drops to zero. The process is repeated during the negative half-cycle. A total of four oscillatory discharges occurs during each voltage cycle, or 240 times a second with a 60-cycle line voltage!

Corona discharges usually occur at extremely high voltages and are characterized by extremely low currents. Interference picked up on automobile radios while passing near high-voltage lines is due to corona discharge. This type of discharge occurs during the voltage peaks of the ac cycle. Fig. 3 shows the waveform. This interference may contain frequencies from the audio range up to several hundred megacycles.

Radio-frequency (rf) leakage interference is generally caused by inadequate shielding of rf generators such as induction heaters, diathermy machines and high-voltage power supplies which employ rf oscillators. Occasionally, it's an interfering radio station. Interference of this type differs from the others—it is tunable.

Harmonic interference is caused by generators of nonsinusoidal waveforms. Sawtooth and square waves contain many harmonics of the fundamental frequency. Thus, a 10-ke sawtooth signal might contain troublesome harmonics at frequencies as high as a megacycle.

Remedies at the receiver

A receiver picks up signals with power levels of considerably less than a billionth of a watt. Although inter-

ference may reach a receiver by conduction through the power lines, most interference is picked up by the receiver antenna. Interference conducted to the receiver through the power lines may be radiated within the set and picked up by the receiver input circuit.

Conduction of interference to the set via the power lines may generally be eliminated by connecting a capacitor of .01 to .05 μ f across the ac lines for ac-dc receivers (Fig. 4-a). The arrangement in Fig. 4-b, with a capacitor from each side of the line to ground, may be employed for ac receivers. A .05- μ f

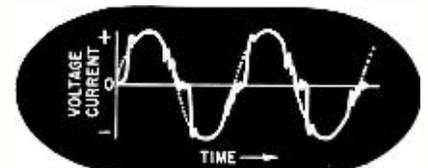


Fig. 2—Current in a glow discharge tube goes through several high-frequency oscillations each cycle.

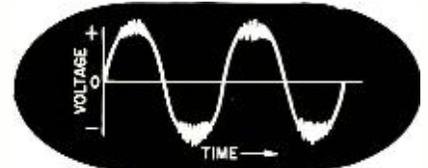


Fig. 3—High-voltage corona discharge normally occurs during voltage peaks.

capacitor has a reactance of 3.18 ohms at 1 megacycle and 0.318 ohm at 10 mc. This is a near short circuit to rf signals.

Interference introduced via the antenna is another matter. If the receiver uses a loop antenna, it may be possible to take advantage of the directional characteristics of the set. The other avenue open is to locate the noise and eliminate or suppress it at the source.

The external antenna in this age of high-sensitivity receivers is frequently a piece of wire strung inconspicuously around the room. If the wire is close to a household power line or within several feet of a fluorescent lamp (and it often is), interference may be reduced by relocating the antenna wire or resorting to an outside antenna with a shielded or twisted-pair lead-in. The shield or unused wire in the case of a twisted pair should be connected to the receiver ground (Fig. 5).

An outside antenna can become a

RADIO

source of noise in itself if the lead-in is not soldered to the antenna proper or if the lead-in is permitted to touch rain gutters or other metal objects.

Tunable rf signals may be reduced with a wavetrap. Two types of wavetraps and their connection modes are shown in Fig. 6. The inductance-capacitance combination is the same as you'd use in a receiver to tune to the interfering station. Set the wavetrap capacitor for minimum signal pickup. The trap of Fig. 6-a inserts a large impedance between antenna and receiver at the interference frequency. The trap of Fig. 6-b places a low impedance across the antenna and ground terminals at the interference frequency.

In a television receiver, interference signals below 50 mc may feed through the front end of the receiver and be amplified by the broad band if stages. High-pass filters which attenuate signals up to about 50 mc are available commercially. This type of filter is connected between the lead-in and the TV set's antenna terminals. The filter must be chosen to match the impedance of the transmission line—300 ohms for ribbon, 72 ohms for coax.

If TV interference is tunable, a wavetrap may be employed. A single series-resonant trap connected across the transmission line terminals as shown in Fig. 7 is preferable. (This arrangement will also work on FM receivers.) Symptoms of interference that a filter or a trap might cure are noise streaks, sound bars and herringbone patterns on the picture. TV picture pulling and FM receiver crosstalk between adjacent stations can often be eliminated with a wavetrap tuned to suppress the stronger station.

Locating the noise

If the suggested remedies applied at the receiver do not eliminate interference, you might as well get out your deerstalker and turn into a noise sleuth.

If the noise is the result of non-sinusoidal signal generation, the source is usually a piece of electronic equipment. Television receivers are primary suspects. Find out if your own TV set is causing your interference by observing if the noise exists with the set on and disappears with it off. Discharge interference will be apparent at rela-

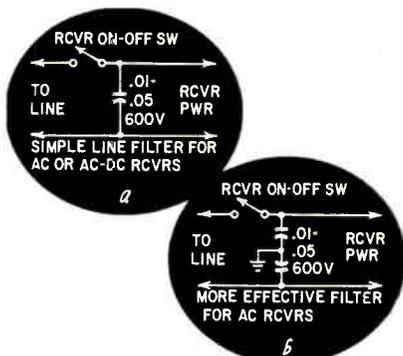


Fig. 4—Line filters for: a—ac and ac-dc and b—ac only receivers.

AMAZING DEMONSTRATION!

New H. H. Scott 72 watt Stereo Amplifier drives 20 KLH Speakers at once!



H. H. SCOTT proudly introduces the most powerful, most versatile complete stereo amplifier ever made. A recent demonstration at ELH Research and Development Corp., Cambridge, Mass., proved the 272's amazing capabilities. This powerful new unit simultaneously drove 20 KLH Model Six speakers to full room volume (with virtually unmeasurable distortion).

UNLIMITED VERSATILITY

The versatility of the 272 is unmatched. It has 25 separate controls. Its advanced features include such H. H. Scott exclusives as: electronic Dyna-ural Rumble Suppressor* which automatically removes annoying turntable and record-changer rumble without audible loss of music; unique Pick-Up Selector Switch; separate Bass and Treble controls on each channel; Center

Channel Output with front panel control; massive output transformers using EL34 output tubes. Total weight 47 pounds. Power Rating: 36 watts per channel (RMS rating); 0.8% Total Harmonic Distortion. \$269.95 (slightly higher West of Rockies. Accessory Case Extra.

H. H. SCOTT

H. H. Scott Inc., Dept. AE7
11 Powdermill Road, Maynard, Mass.

Rush me your new 1960 H. H. Scott Guide and Catalog.

Also include complete technical information on your powerful new 272 complete stereo amplifier.

NAME _____

ADDRESS _____

CITY _____ STATE _____

Export Telesco International, 25 W 40th St., N.Y.C.

* Covered by one or more of the following patents: 2,606,974, 2,606,975, 2,606,973.

Solve Rough Sweep Output Problems

**IN MINUTES
INSTEAD OF HOURS!**



NEW **B&K** DYNA-SWEEP CIRCUIT ANALYZER

1. Provides composite synchronizing signals (negative or positive) to inject directly in each sync stage.
2. Provides plate drive signal to check complete vertical output circuit, including V.O. transformer.
3. Provides vertical yoke test signal to determine if vertical yoke windings are defective.
4. Provides horizontal plate driving signal to directly drive TV horizontal output transformer circuit.
5. Provides 3+ boost indicator.
6. Provides unique high-voltage indicator.
7. Provides sensitive tests for each of the horizontal output components, including H.O. transformer and yoke. Immediately reveals their true condition, good or bad.

Quickly solves tough output servicing problems that have always plagued the TV serviceman. Provides horizontal and vertical sync and driving pulses that make it easy to check out every stage in the sync and sweep sections of a television receiver. Tracks down troubles in the horizontal and vertical output circuit, including defective output transformer and yoke. Checks for shorted turns, leakage, opens, short circuits, and continuity. Gives unique high-voltage indication. Eliminates trial and error replacements. Saves many hours of service work! Pays for itself over and over again.

Model 1070 Dyna-Sweep. Net, \$74.95

MODEL A107 DYNA-SWEEP CIRCUIT ANALYZER

for use with B&K Model 1075 Television Analyst

Functions like the Model 1070 above, but is designed as a companion unit for use only with B&K Model 1075 Television Analyst for driving source. Makes your Television Analyst more useful and valuable than ever. Net, \$54.95



See your B&K Distributor or Write for Bulletin ST24E

B&K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.



Canada: Atlas Radio Corp., 50 Wingald, Toronto 10, Ont. • Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

CARTOONS

RADIO-ELECTRONICS pays \$3.00 for good cartoon ideas and \$15 and up for finished work.

Radio-Electronics 154 West 14th St., New York 11, N. Y.

RADIO

tively high frequencies. Sources of thermostat are noises and appliance interference created in your home are usually obvious, since you know when these devices are being operated.

Assuming nothing this obvious, turn on a battery-operated portable radio and tune it off station. Pull the main fuse or switch on your house wiring panel. If the interference disappears

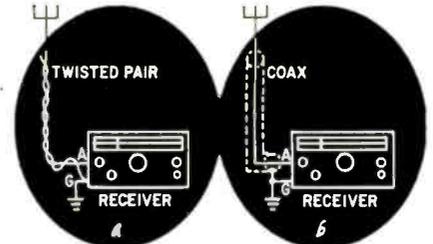


Fig. 5—Shielded and twisted-pair leads reduce noise.

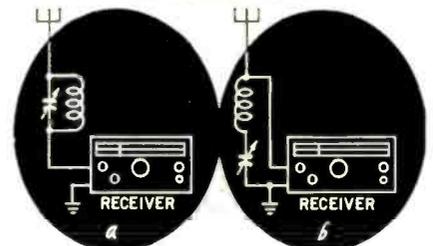


Fig. 6—Parallel-resonant wavetrap in series with antenna, b—series-resonant trap across antenna-ground terminals.

or drops significantly, the noise source is probably connected to the electrical circuit in your home. Now you can turn the main switch on and turn the other circuits off one at a time till the interference stops. From this point on, it's a matter of locating the offending appliance, lamp or defective wiring.

A battery portable radio may be useful in locating the source of the noise by actually homing in on it. For this type of work, a battery receiver with a highly directional antenna and a signal-level meter such as the Heathkit DF-1 radio direction finder is invaluable. If the noise is not being generated on your premises, scout the neighborhood with your battery-operated portable.

Remedies at the source

Remedies at the source depend, of course, on the type of interference. Noise due to motor commutator arcing may usually be suppressed with a 1- μ f 600-volt capacitor connected across the line terminals at the motor. A 0.1- μ f 600-volt capacitor is more practical for portable tool and vacuum cleaner motors. The motor frame should be grounded as a safety as well as a noise precaution. A .02- μ f capacitor connected from each side of the line to the grounded frame may reduce the interference further. In extreme cases, a commercial filter (a capacitor-inductor combination) may have to be used.

Contact arcing on switches, relays and thermostats where currents of less than 3 amperes are involved may be reduced with a 0.1- μ f capacitor connected across the contacts. To limit charge and discharge currents, a 100-

RADIO

ohm 1/2-watt resistor should be connected in series with the capacitor (Fig. 8-a). The voltage rating of the capacitor depends on the circuit inductance. If the contacts control a device for which timing is important, the R-C combination of Fig. 8-a cannot be used. Instead, two 1-millihenry rf chokes of adequate current rating for the load may be connected as shown in Fig. 8-b.

To suppress fluorescent fixture interference, connect a .05- μ f capacitor across the line and connect a .02- μ f capacitor from each side of the line to the metal frame of the fixture. The filter should be mounted inside the grounded fixture frame. Interference from neon signs may be minimized by removing protruding points in the wiring which might allow auxiliary discharges and by cleaning switch contacts periodically. High-frequency oscillations may be damped by placing a 47,000-ohm resistor in series with each of the transformer secondary leads to the tubing (Fig. 9).

Interference from automobile ignition systems to home receivers is rarely ever bothersome. But the ignition system will introduce noise to the automobile radio if it isn't suppressed. Ordinarily a resistive suppressor in the ignition coil lead to the distributor, and a 0.5- or 1- μ f capacitor from the ammeter to ground will suppress ignition noise. This, of course, assumes a properly shielded antenna lead with a good shield connection to the auto frame. A 0.5- or 1- μ f capacitor should be connected across the generator to suppress generator noise. In severe cases, particularly in older cars, additional measures may be required. END

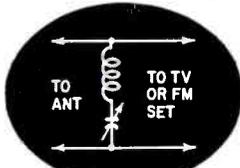


Fig. 7—Series-resonant wavetraps may be connected directly across transmission line.

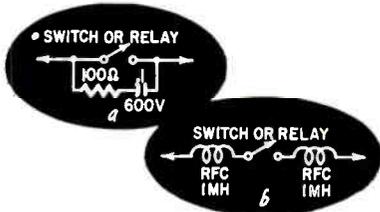


Fig. 8-a—R-C combination suppresses arcing, b—rf chokes can be used on device where timing is important.


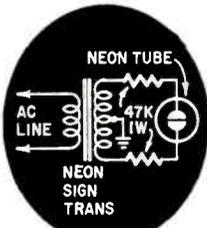


Fig. 9—Resistors damp oscillation in neon tubes.

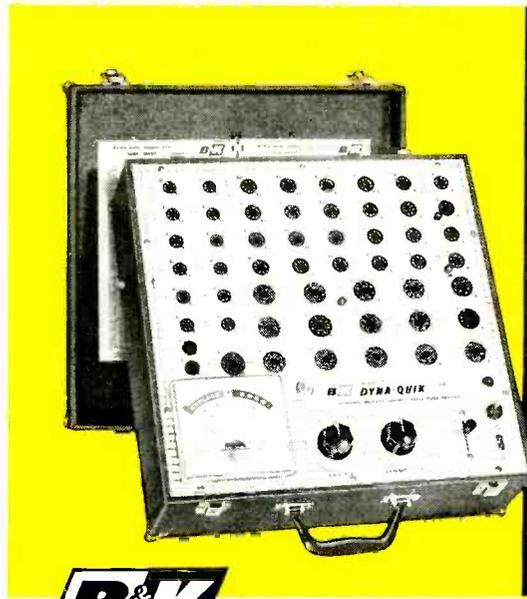

B&K MODEL 550 **DYNA-QUIK** DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

Greatest value for professional servicing! Provides 52 tube sockets to test more tubes faster, easier, with laboratory accuracy. Measures true dynamic mutual conductance. Quickly detects weak or inoperative tubes. Sells more tubes. Saves call-backs. Makes more money for you every day.


Tests Each Section of Dual-Section Tubes Separately
Completely tests each tube in seconds. Checks average TV set in a few minutes, in home or shop. Checks tubes for shorts, grid emission, gas content, and leakage. Shows tube condition on "Good-Bad" scale and in micromhos. No multiple switching. Quick-reference listings on socket panel and handy chart. New tube reference charts regularly made available. Patented automatic line voltage compensation. Phosphor bronze contacts. A real professional instrument for only **\$119⁹⁵** NET

See your B&K Distributor or Send for Bulletin ST24 E

B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont. • Export: Empire Exporters, 277 Broadway, New York 7, N.Y., U.S.A.

GET MORE FOR YOUR MONEY

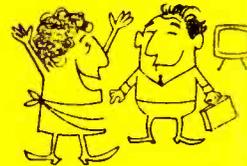

SAVE CUSTOMERS




SELL MORE TUBES



SUPER POWERED SINGLE CHANNEL AMPLIFIER

Minimum 20V—5 Watts on All Channels

This all new super powered unit has the highest output of any TV channel amplifier with sufficient power to cover large communities with ample signal voltage and deliver a strong signal thru many miles of cable. The unit was designed specifically for community television and is the only unit of its kind that does not produce power in fractions of a watt. For full rated output a high-powered commercial transmitting tube is used.

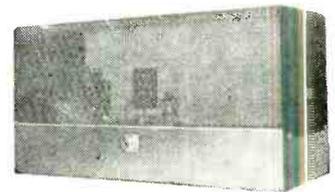

- C. C. S. Service
- 26 db min. gain
- 6-8 mcs. band width
- Channels 2-13 as specified
- Requires only 1 V input
- Co-axial input and output connectors for 75 OHM Line
- Linear class A operation
- Low Power Drain (1 Amp.)

MODEL SPA
\$350

Write for details today.


SEG Electronics • 1778-A Flatbush Ave., Brooklyn 10, New York

NEW TUBES and SEMI-CONDUCTORS

TUBES for audio dominate this month. Sprinkled throughout the releases are a hi-mu twin triode and two power pentodes for audio amplifiers. In between we have a TV horizontal oscillator and a group of germanium diodes.

6GH8

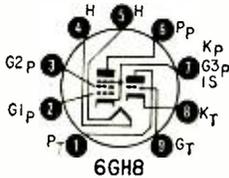A multi-unit tube in a 9-pin miniature envelope. A medium-mu triode and a sharp-cutoff pentode are enclosed in the envelope and are intended for use in multivibrator type horizontal deflection oscillators in TV receivers. The




6GH8 can also be used as an age amplifier or sync separator.

Characteristics of the RCA 6GH8 in class-A₁ amplifier service are:

	TRIODE	PENTODE
V_p	125	125
V_{G2}	—	125
V_{G1}	-1	-1
μ	46	—
R_p (k ohms)	5.4	200
I_{G2} (ma)	—	4.0
I_p (ma)	13.5	12
g_m (μ mhos)	8,500	7,500
V_{G1} (for 10- μ a plate current)	-8	-8

2N1501, -1502

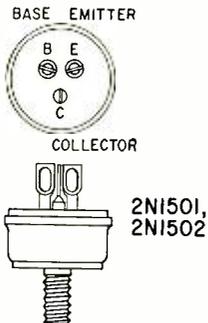These hermetically sealed germanium p-n-p transistors are designed for a



variety of uses including servo amplifiers, power conversion, voltage regulation, switching, etc.

Maximum ratings of these Minneap-

olis-Honeywell transistors are:

	2N1501	2N1502
V_{CB}	60	40
V_{CE} (active region) (emitter forward biased)	40	40
(Cutoff region) (emitter reverse biased)	60	40
V_{EB}	28	28
I_E (amps) (rms)	3.5	3.5
I_B (amps) (rms)	0.5	0.5

DC 7, 7A, 7B, 7C, 7D

These uhf germanium mixer diodes are designed and manufactured for 1,000-mc applications. Made by Semi-



Elements Inc., they replace two diodes that have been discontinued by G-E—the 4JB2E9 and the G7B.

All units have the following specifications:

$I_{average\ dc}$ (ma)	25
$I_{peak\ dc}$ (ma)	75
Operating frequency (mc)	1,000
P_{total} (mw)	250


The table breakdown shows variations between the units:

Type	Use	Peak Inverse Voltage	Minimum Rect. Eff.	IF Impedance
DC 7	Detector and Meter	15	75%	—
DC 7A	Uhf Mixer	10	—	250 ohms
DC 7B	Uhf Mixer	5	50%	250 ohms
DC 7C	High-level, high-efficiency Detector and mixer	10	60%	—
DC 7D	High-level, very-high-efficiency meter detector and mixer	15	70%	—
			85%	—

60FX5

This is a power pentode in a 7-pin miniature envelope that is designed for use in the output stages of inexpensive audio amplifiers. It is particularly suited for use in 2-tube series-string

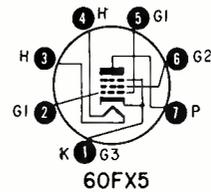stereo amplifier systems. Because of its high power sensitivity, the 60FX5 can be driven to full output by a ceramic or crystal phono cartridge.




Typical operating characteristics of the RCA 60FX5 in class-A₁ amplifier service are:

V_p	110
V_{G2}	115
R_K (ohms)	62
V_{G1} (peak af)	3
I_p (zero signal) (ma)	36
(max signal) (ma)	35
I_{G2} (zero signal) (ma)	10
(max signal) (ma)	12
R_L (ohms)	3,000
Harmonic distortion (%)	8
Power output (max) (watts)	1.3

6EU7

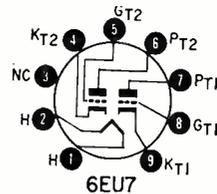A high-mu twin triode in a 9-pin miniature envelope especially designed for use in high-gain resistance-coupled



audio preamplifiers. The RCA 6EU7 has an amplification factor of 100, low hum, low microphonism, double helical heaters and a special basing arrangement that lets the circuit designer get good isolation between stereo channels.


Operating characteristics (per section) of the 6EU7 are:

V_p	100	100
V_G	-1	-2
μ	100	100
R_p (k ohms)	80	62.5
g_m (μ mhos)	1,250	1,600
I_p (ma)	0.5	1.2

35EH5

A power pentode in a 7-pin miniature envelope. It is intended for use in the

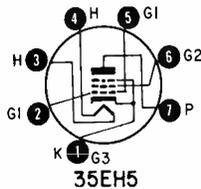audio output stages of FM or AM-FM radios and audio amplifiers operating from transformerless ac or ac-dc power supplies. Two 35EH5's, a 12AX7 and a 35W4 can make up the entire tube complement of a stereo amplifier system using a series heater string.




Typical operating characteristics of the RCA 35EH5 class-A1 amplifier service are:

V_p	110
V_{G2}	115
R_k (ohms)	62
V_{G1} (peak af)	3
I_p (zero signal) (ma)	32
(max signal) (ma)	32
I_{G2} (zero signal) (ma)	7.2
(max signal) (ma)	12
R_p (approx) (ohms)	14,000
gm (μ mhos)	12,000
R_L (ohms)	3,000
Harmonic distortion (%)	8
Power output (max) (watts)	1.2

CST-1744, -1745, -1746

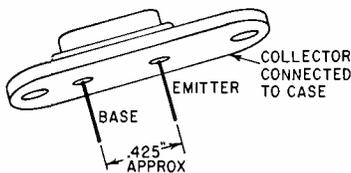These special-size germanium p-n-p transistors are designed for use in amplifier circuits where their improved frequency response leads to higher audio fidelity, in switching circuits where they provide faster switching and in



CST-1744, CST-1745, CST-1746

regulated power supplies where they deliver improved performance.

Maximum ratings of these Clevite Spacesaver transistors are:

V_{CE}	40
V_{EB}	45
I_C (amps)	3
I_B (amps)	2
P_{total} (watts)	12

Typical characteristics are:

	CST-1744, -1745	-1746
G_{PE} (power gain) (min) (db)	28	32
$f_{G_{PE}}$ (cutoff freq) (typ) (kc)	15	15
D (distortion) (typ) (%)	3	3
h_{ie} (input impedance) (typ) (ohms)	20	20

Semiconductor briefs


New low- and high-voltage military-type industrial transistors in 3-ampere ratings have been introduced by Motorola. The high-voltage types have collector-base voltage ratings of 120 volts and collector-emitter ratings of 100 volts. All of these new transistors are germanium p-n-p alloy junction units.

Tiny 1/2 x 1/2-inch photoconductive cells can dissipate up to 500 mw when mounted on a heat sink. Two types are available: the 504, a cadmium selenide unit that has a relatively high speed of response; and the 505, a cadmium sulphide unit. Both cells are made by Clairex. END

Now...from Sonotone-

4 Big Improvements

in the quality stereo cartridge

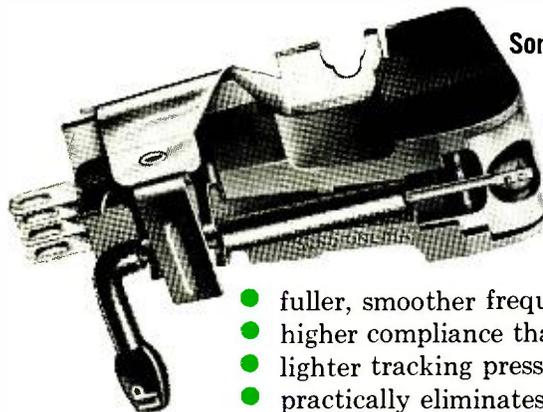

Sonotone 8TA cartridge replaces 8T as industry standard

The new Sonotone 8TA cartridge gives greater than ever stereo performance... has 4 big extras:

- fuller, smoother frequency response
- higher compliance than ever before
- lighter tracking pressure
- practically eliminates dust pile-up

ONLY \$14.50*

Sonotone 10T unitized stereo at lowest price ever

New 10T cartridge sells at record low price of \$6.45.* And it covers the complete high fidelity range. 10T's unitized construction makes it easiest to install, easiest to replace. Low price means more sales—more profits.



SPECIFICATIONS


	8TA	10T
Frequency Response	Smooth 20 to 20,000 cycles. Flat to 15,000 with gradual rolloff beyond.	Flat from 20 to 15,000 cycles \pm 2.5 db.
Channel Isolation	25 decibels	18 decibels
Compliance	3.0×10^{-6} cm/dyne	1.5×10^{-6} cm/dyne
Tracking Pressure	3-5 grams in professional arms 4-6 grams in changers	5-7 grams
Output Voltage	0.3 volt	0.5 volt
Cartridge Weight	7.5 grams	2.8 grams
Recommended Load	1-5 megohms	1-5 megohms
Stylus	Dual jewel tips, sapphire or diamond.	Dual jewel tips, sapphire or diamond.

*including mounting brackets

Sonotone makes only 6 basic ceramic cartridge models... yet has sold over 9 million units... used in over 662 different phonograph models. For finest performance, replace worn needles with genuine Sonotone needles.


Sonotone

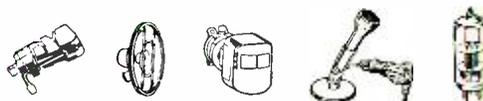Electronic Applications Division, Dept. C2-70
ELMSFORD, NEW YORK




Leading makers of fine ceramic cartridges, speakers, tape heads, microphones, electronic tubes. In Canada, contact Atlas Radio Corp., Ltd. Toronto

new PRODUCTS

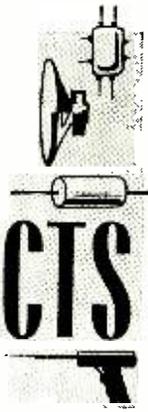

MOUNTING BRACKET, *Cardio master*, converts transistor radio to auto radio. Powerful permanent magnet and adjustable holding bracket holds radio near windshield. No additional wiring, antennas or motor suppressors required.—**R-Columbia Products Co., Inc.**, 305 Waukegan Ave., Highwood, Ill.

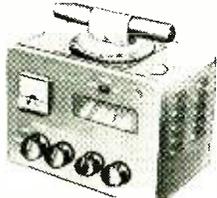RADIO DIRECTION FINDER operates on 4 size-D cells. Built-in compass. Easy-mounting




brackets for removal from boat for personal use. Superhet. Tunes broadcast and marine bands. Carrying strap.—**Alco Electronics**, 3 Wolcott Ave., Lawrence, Mass.

MICROPHONES for amateur, mobile and Citizens band use. Tough plastic case, coiled cord (5 feet extended, 11 inches retracted). *Model 350X* (crystal): response 60 to 6,500 cycles, level -48 db. *350C* (ceramic): same




response, output level of -54 db. *350R* (carbon): response 200 to 4,000 cycles, level -38 db. All models have hanger button and dash bracket. Wired for relay operation.—**Turner Microphone Co.**, 909 17th St., N. E., Cedar Rapids, Iowa.

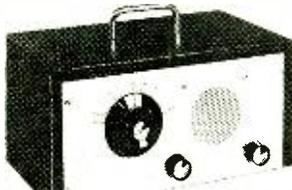FM RECEIVER kit *model 777-1* comes with all transformers; variable capacitor; 6 transistors; antenna, rf and oscillator coils; knobs. *Model 777-2*



similar to above, but metal case and panel. Completed receiver has 2.5- μ v sensitivity, afc, vernier tuning, push-pull output stage.—**J. W. Miller Co.**, 5917 S. Main St., Los Angeles 3, Calif.

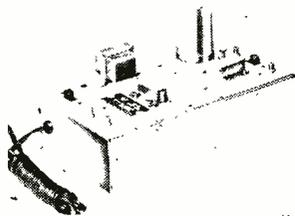TV-FM AMPLIFIER *model BT-3* fully transistorized. Low-channel gain 18 to 15 db. High-channel gain 19 db. FM-band



(88-109-mc) gain 15 to 9 db. Low noise, low cross-modulation. Minimum operating costs.—**Blonder-Tongue Laboratories, Inc.**, 9 Alling St., Newark, N. J.

ANTENNA covers 10-, 15-, 20-, 40- and 80-meter bands. *Hy-Tower* vertical antenna 24-foot steel tower topped by 26-foot aluminum mast. Hot-




dipped, galvanized, X-braced. No guy wires required. Vertical fed by 52-ohm coax. 90 pounds. SWR less than 2:1 on all bands.—**Hy-Gain Corp.**, 1135 N. 22 St., Lincoln, Neb.

OUTPUT TRANSFORMER for vertical deflection use covers more than 54 turns ratios.



2 x 3 1/4 x 2 inches.—**Chicago Standard Transformer Corp.**, 3501 Addison, Chicago 18, Ill.

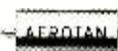SOLID TANTALUM Capacitors. Sintered tantalum anodes. Hermetically sealed in subminiature metal cases. Semiconductor electrolyte. Corrosion- and leak-free. *Aerotan's* available in insulated and uninsulated cases. Operate over range of from




-80°C to 125°C.—**Aerovox Corp.**, New Bedford, Mass.

SILICON RECTIFIER line for medium-power applications

handles up to 6 amperes. Available in 8 PIV ratings from 50 to 600 volts. Mounting styles 1/2-inch hex ceramic insulated and 7/16-inch hex.—**Cornell-Dubilier Electric Corp., Semiconductor Div.**, Norwood, Mass.

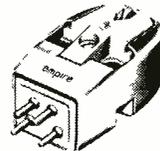STEREO CARTRIDGE *Empire 108*. Outputs balanced to within 1 db. Response 15 to




20,000 cycles \pm 2 db, usable output to 30,000 cycles. Channel separation 25 db, horizontal and vertical compliance 6×10^{-6} cm/dyne. Minute moving magnet assures low dynamic mass. Output 8 mv per channel.—**Dyna-Empire, Inc.**, 1075 Stewart Ave., Garden City, N. Y.

STEREO CARTRIDGES *C99* (shown) and *P99* fit *ESL-S310* professional tone arm and any standard changer or pickup arm, respectively. Response 18 to 20,000 cycles \pm 2 db. Channel separation 20 to 25 db, dynamic mass .0025 gram. Output per channel 1 mv at 10 cm/sec. Ver-




tical and lateral compliance 5×10^{-6} cm/dyne.—**Electro-Sonic Labs., Inc.**, 35-54 36th St., Long Island City 6, N. Y.

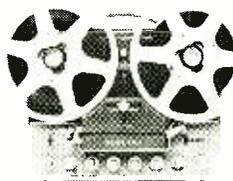STEREO RECORDER *model SM-310-4* 1/4-track version of *SM-310*. Records 1/4-track stereo or monophonic. Plays back 1/2- and 1/4-track tapes. All other




specifications same as *SM-310*.—**Newcomb Audio Products Co.**, 6824 Lexington Ave., Hollywood 38, Calif.

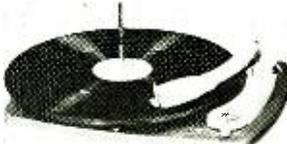RECORD CHANGER *model RC-1* mixes different-size records of same speed. 4 speeds. Kit or wired. Plug-in head. 45-



rpm record adapter and short spindle for manual use available. No stabilizer arm. Records slide gently rather than drop down spindle.—**Arkay International**, 88-06 Van Wyck Expressway, Jamaica, N. Y.

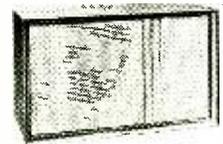SPEAKER SYSTEM. 12-inch woofer, 8-inch midrange and horn-loaded tweeter. Lower crossover frequency 200 cycles, tweeter takes over at 3,500 cycles. *Regal 300* in 25 x 14 x



13 1/2-inch bookshelf enclosure. Response 35 to 18,000 cycles. power-handling capability 70 watts program material, impedance 8 ohms. Midrange speaker in isolated chamber to prevent interaction with woofer rear-wave pressures.—**Electro-Voice, Inc.**, Buchanan, Mich.

SPEAKER SYSTEM for PA or stereo use. *Rocket* has approximately 20% efficiency. Response 80 to past 15,000 cycles. Impedance 8 ohms; power-



handling capability, 4 watts. Operates somewhat like horn, but has superior characteristics. Horizontal dispersion angle 140°, vertical 80°, eliminating necessity for "stereo seat." Place on furniture or hang upside down on wall.—**Karlson Associates, Inc.**, 433 Hempstead Ave., W. Hempstead, N. Y.

TONE-ARM LIFT clips onto pickup arms without tools. Spring steel with resilient plastic covering. Allows needle to




be placed in proper groove (or band) without fumbling.—**Clevite Walco**, 60 Franklin St., E. Orange, N. J.

AMPLIFIER CHASSIS *model M-2*. Flat design for low-clearance installations. Response 20 to 30,000 cycles. 3 inputs, 4- and 8-ohm outputs. Loudness



control, tone controls, program-selector switch. May be paired for stereo use. 12 watts.—**Model Engineering & Manufacturing, Inc.**, 56 Frederick St., Huntington, Ind.

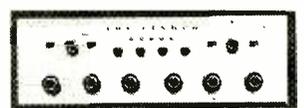AUDIO CONTROL has 10 high-level, 8 low-level inputs. Sonic null balancing for perfect stereo balancing without guesswork. *Model 400-CX*: channel blending eliminates "hole-in-middle." Center-channel output. Response 20 to 20,000 cycles \pm 1/2



NEW PRODUCTS (Continued)

db. Hum and noise more than 80 db below rated output for high-level input. Lights indicate mode of operation. Scratch and rumble filters. 10 tubes.—Fisher Radio Corp., 21-21 14th Drive, Long Island City 1, N. Y.

VOLTAGE REGULATOR adjusts for line-voltage changes. 4-position switch feeds line voltage direct, increases line




voltage 10%, decreases line voltage 10% and shuts off equipment. Model LR-10 handles up to 350 watts.—Vidaire Electronics Mfg. Corp., 44 Church St., Baldwin, N. Y.

SILICONE SPRAY in 6- and 16-ounce size. Nonvolatile liquid deposited by spray excellent lubricant for rubber, leather, canvas, metal surfaces, fishing




reels, etc. Stops sticking, squeaks. Repels water. Does not wash off readily. Colorless. No thickening with age.—Krylon, Inc., Norristown, Pa.

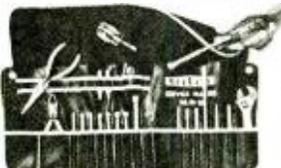TOOL KIT model 99NM has 99% of tools required by technicians on calls. High-carbon steel shafts, polished nickel




chrome finish. 23 pieces, screwdrivers, nutdrivers, reamers, pliers, extension blade and 6-inch wrench. Xcelite, Inc., Orchard Park, N. Y.

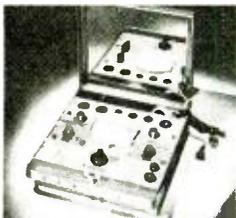TUBE TESTER Mighty Mite tests for cathode emission, interelement shorts, gas, grid emission and grid leakage as high as 100 megohms. Setups



are made with help of small attached booklet (new charts provided free). 3½-inch meter glows in dark for easier back-of-set servicing. Stainless-steel mirror in case lid. Separate inner chassis removable from case for caddy or counter mounting.—Sencore, Addison 2, Ill.

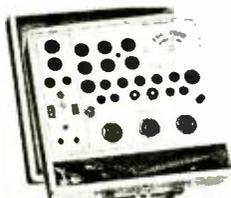TUBE TESTER checks quality of over 700 tube types. Model 102-P checks emission; for gas,




leakage and shorts. Multisection tubes each section checked separately. Tests crystal diodes, power rectifiers, pilot lamps and fuses. Oak carrying case, etched aluminum panel. New charts issued periodically. Model AD-1 available for testing monochrome and color picture tubes for emission, shorts and gas.—Mercury Electronics Corp., 77 Searing Ave., Mineola, N. Y.

TUBE TESTER TE-15 indicates shorts and quality. Slide




switches connect tube elements to respective circuits. Power switch for high or low line voltage. Slide-out tray contains tube charts. Meter scale calibrated 0 to 100 plus replace?—good scale. Separate scale for diodes.—Lafayette Radio, 145-08 Liberty Ave., Jamaica 33, N. Y.

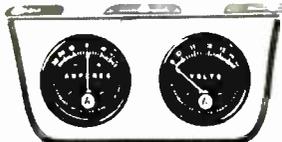AMMETER-VOLTMETER for car and boat electrical system monitoring Kit No. 83Y711, 12-volt systems only. Expanded-scale voltmeter reads 9 to 15 volts. Zero-center ammeter reads 30-0-30 amps. Illuminated



by vibration-proof pilot lamps. Supplied with cables and information on voltage-regulator adjustments.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

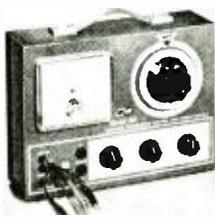TRANSISTOR TESTER model 160 measures beta (gain) directly within 3%, no interpola-



tions. Tests for leaky or open junctions. Automatically provides proper bias for 2nd base in tetrodes. Supplies metered dc for servicing transistor radios. Operates on 105 to 125 volts ac. Will not burn out transistor being tested.—B. & K. Manufacturing Co., 1801 W. Belle Plaine, Chicago 13, Ill. END

All specifications from manufacturers' data.

BECOME A RADIO TECHNICIAN for only \$26.95

BUILD 20 RADIO

CIRCUITS AT HOME

with the New Progressive RADIO "EDU-KIT"®

All Guaranteed to Work!

PRACTICAL HOME RADIO COURSE only \$26.95



Reg. U.S. Pat. Off.

NOW INCLUDES

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ AMPLIFIER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR
- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBERSHIP IN RADIO-TV CLUB • CONSULTATION SERVICE • HI-FI GUIDE • QUIZZES • TV BOOK • FCC AMATEUR LICENSE TRAINING • RADIO BOOK • PRINTED CIRCUITRY • PLIERS-CUTTERS • ALIGNMENT TOOL • WRENCH SET • CERTIFICATE OF MERIT • VALUABLE DISCOUNT CARD

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and layout radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay, only \$26.95 complete.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are twenty Receiver, Transmitter, Code Oscillator, Signal Tracer, Square Wave Generator and Amplifier circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our kits contain tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing punched metal chassis, Instruction Manuals, hookup wire, solder, selenium rectifiers, volume controls and switches. In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to the F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Testers Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

J. Statistis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a course, but I found your ad and sent for your kit."

UNCONDITIONAL MONEY-BACK GUARANTEE

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course. By popular demand the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc., has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7.00

- Send "Edu-Kit" Postpaid, I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."


Name.....
Address.....

Progressive "EDU-KITS" Inc. 1186 Broadway, Dept. 166-G
Hewlett, N. Y.

"PHOTOFACTS...most complete..."

"I have found PHOTOFACTS to be the most complete service information available on all makes and models of radios and television."

—Aaron F. Triplett
Flint, Michigan

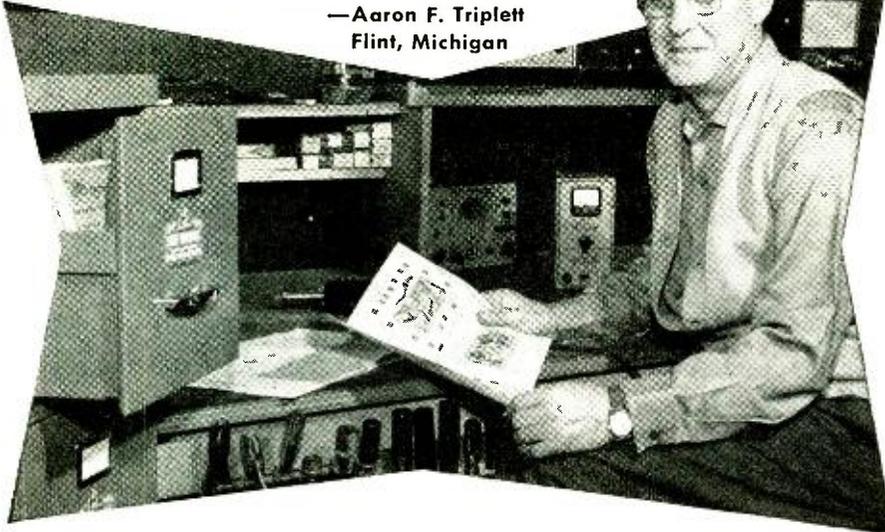

Service Technicians! YOU EARN MORE... YOU RATE with the public when you own the PHOTOFACT® service data library!

You enjoy maximum earnings as the owner of a complete PHOTOFACT Service Data Library! It's inevitable, because no matter how expert you are, you can always *save more time on any job, get more jobs done daily*—EARN MORE, DAY IN AND DAY OUT...

What's more—as the owner of a complete PHOTOFACT Library, you know your customers' sets *best*. You can actually show each customer you have the PHOTOFACT Folder covering his very own set. Result: You command public respect and acceptance which paves the way to more business and earnings for you.

HOW TO STAY AHEAD...

Yes, the truly successful Service Technicians are those who own the complete PHOTOFACT Library, who can meet and solve any repair problem—faster and more profitably. And these men *keep ahead* because they're on a Standing Order Subscription with their Distributors to receive all new PHOTOFACTS as they are released monthly. (They're eligible for the benefits of membership in PEET, too—see below!)

ONLY \$10 DOWN puts the complete PHOTOFACT Library in your shop—and you have up to 30 months to pay. See your Sams Distributor today, or write to Howard W. Sams

NOW IS THE TIME TO JOIN

"PEET"

THE POWERFUL NEW PROGRAM FOR QUALIFIED TECHNICIANS

If you now own a PHOTOFACT Library or plan to own one, you can apply for membership in "PEET." It's the first industry program really designed to build powerful public acceptance for the Service Technician who qualifies. Builds enviable prestige and business for its members. Benefits cost you absolutely nothing if you qualify. Ask your Sams Distributor for the "PEET" details, or mail coupon today.

HOWARD W. SAMS & CO., INC.
1726 E. 38th St., Indianapolis 6, Ind.

- Send me full details on the new "PEET" Program.
- Send full information on the Easy-Buy Plan and Free File Cabinet deal.
- I'm interested in a Standing Order Subscription.
 - I'm a Service Technician full-time; part-time

My distributor is _____

Shop Name _____

Attn: _____

Address _____

City _____ Zone _____ State _____

TECHNICIANS'

NEWS

NEW YORK DISTRIBUTORS FIGHT STATE LICENSING

Jobbers in Rochester, Buffalo and New York City were largely responsible for a drive to kill the proposed N. Y. State TV technician licensing law, according to an article by James C. Kinkaid, editorial director of *Jobber News* Magazine. In the April, 1960, issue of that journal, he said that the jobbers fighting the measure were confident that the State Legislature would adjourn without getting the legislation out of committee although it was supported by Gov. Nelson Rockefeller and State Attorney General Louis J. Lefkowitz. They were right, neither bill was reported out of committee when the Legislature adjourned.

The *Guild News*, organ of the Radio & Television Guild of Long Island, has published a list of the jobbers in the guild area that fought the bill and suggests that technicians not deal with these firms.

Jobber News had a list of the anti-licensing dealers throughout the state. More than 30 firms—most of them in New York City—were listed.

BBB LISTS CODE OF ETHICS

The Better Business Bureau of Greater St. Louis, Inc. (Ill.) has published "Standards of Advertising and Code of Ethics" for the service industry.

Some of the points covered in the code are:

Employ qualified (and adequately trained) personnel and use approved methods and equipment.

Advertise in a manner fair to both customers and competitors.

Render service promptly and proficiently.

Give an advance estimate and perform only authorized repairs.

Install parts of equal or better quality and performance rating. Return all parts and tubes to the customer on request, except parts in warranty or on an exchange basis.

Issue an itemized bill.

A few of the points covered in the Standards of Advertising are:

No firm shall represent itself as an authorized service company for a manufacturer when such is not the fact.

Offers of gifts or premiums shall not be used.

Bait advertising and selling practices shall not be used.

There shall be no quotation of a price or prices for service calls. It is permissible, however, to advertise prices for service contracts.

Exaggerated claims such as "Lowest prices in —" shall not be used.

Statements comparing the advertiser's service with a competitor shall not be used. An advertiser shall not attempt to discredit a competitor.

NEW LOCAL FORMED

Thirty TV service dealers in the Canton, Ohio, area have formed the Television & Electronic Service Association of Stark County (TESA Stark County).

Royal Lister has been named chairman; Bruce Sullivan, president; Robert Wood, vice president; Al Roberson, secretary, and W. O. Phillips, treasurer.

Directors are Ben Lowe, Horace Williams and Daniel A. Scipione.

The group has adopted a code of ethics including home servicing of sets where possible, service within 24 hours and presenting estimates before major repairs are made.

JOINS COUNCIL

The Radio Servicemen's Association of Trenton, N. J., has joined the Tri-State Council of TV Service Associations, according to the *Vanguard*, organ of the council. The Tri-State Council covers Delaware, New Jersey and Pennsylvania.

TESA MIAMI ELECTS

The Television & Electronic Service Association of Miami, Inc., has elected new officers. In order of their appearance in the photograph, they are: (left to right, back row) Charles D. Pierce, 2nd vice president; Roger Misleh, 1st



swered this statement in a letter to *Home Furnishings Daily*, pointing out among other things that the grandfather clause is a constitutional protection needed so that individuals cannot be legislated out of their livelihood.

PRESIDENT RESIGNS

Ken LaRue has resigned as president of the North Carolina Federation of Electronic Associations, Inc., according to *The Printed Circuit*. He explained that his business has recently been a great deal more inclined toward sales, instead of service, and he must correspondingly devote a large portion of his time toward sales.

As provided by their Constitution, the vice president, Charles McBroom,

took over the vacated office of president.

Secretary Ray Stanley also resigned. Garland Hoke, a Director, agreed to take over as acting secretary until September.

BILL TO BE RE-INTRODUCED

The Empire State Federation of Electronic Technicians Associations (ESFETA) expects to have a television-technician licensing bill re-introduced into the next session (starting in January) of the New York State Legislature, according to Robert Larsen, executive director of Radio & Television Technicians Guild of Long Island. The Legislature closed their last session without passing a previously introduced license bill. It caused considerable debate among technicians and their suppliers.

A group of 10 Buffalo, N. Y., electronic parts distributors, opposing the bill stated that it would cut down on the supply of future electronic technicians. They claimed the apprentice clause in the bill would restrict the entry of new technicians because apprentices cannot earn a living wage. A resolution drawn up by the dealers and sent to the State Senate and Assembly stated that the proposed law would not fulfill its objectives, and TV prices would rise because of the closed shop the legislation would produce. The resolution also hit the legally necessary grandfather clause, saying that it accepts technicians who may be cheats or incompetent and gives them an implied indorsement. John A. Wheaton, of the Guild, an-

swered this statement in a letter to *Home Furnishings Daily*, pointing out among other things that the grandfather clause is a constitutional protection needed so that individuals cannot be legislated out of their livelihood.

He went on to say that the argument against the apprentice clause actually admits "the present low level of income in the trade. The . . . license bill would provide a healthier TV service field, and a more attractive one for young people to enter".

NATESA DIRECTORS MEET

National Alliance of Television & Electronic Service Associations directors held their annual spring meeting

4 GREAT NEW SAMS BOOKS

"Tube Substitution Handbook"

Compiled by the engineering staff of Howard W. Sams & Co., Inc. Lists over 1500 American receiving tubes, including more than 300 which can be replaced by European receiving tube types. Also lists 400 picture tubes; 179 European types that can be replaced by American tubes, and 78 receiving tubes replaceable by industrial tubes. Includes helpful facts on tube substitution. Invaluable reference for technicians. Handy 5½ x 8½" size. Only \$150



"Practical Transistor Servicing"

by William C. Caldwell

The latest word on how transistors and transistor circuits operate—shows how to signal-trace and diagnose portable and auto-radio troubles. Tried and tested procedures are based on the premise that "time saved is money earned." Concentrates on the practical in 8 fact-filled chapters; tells clearly how transistors work; describes circuit components and their functions; shows how to isolate troubles; indicates normal transistor voltages and explains meanings of defective voltages; tells how to test transistors; shows how to troubleshoot auto radios; gives actual case histories. Profusely illustrated; 5½ x 8½" size. Only \$295



"Rapid Printed Circuit Repair"

by G. Warren Heath

Printed circuit boards, now being used in more and more electronic devices, can be a headache to the technician unless he understands their function and how to repair them. This practical book avoids complicated theory; it clearly describes and illustrates the fundamentals of printed circuitry and the components used by various manufacturers. Servicing and repair techniques and the various types of defects likely to be encountered are listed in alphabetical order for easy reference. 5½ x 8½". Only \$195



"Electronic Tips and Timesavers"

by John Comstock

Includes over 300 ingenious time- and money-saving tips—solving just about any problem the technician, engineer, builder or experimenter might face. Simply written and supported by illustrations, these bench-tested hints will save you much effort and frustration. You'll want to keep this book handy for constant reference use. Eight sections include tips on bench and field servicing, shop and truck equipment, soldering, tools, test equipment, construction and experimentation. 5½ x 8½". Only \$150



HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. G-20 1720 E. 38th St., Indianapolis 6, Ind.

- Send me the following books:
- "Tube Substitution Handbook" (TUB-1)
- "Practical Transistor Servicing" (PTC-1)
- "Rapid Printed Circuit Repair" (PC-2)
- "Electronic Tips and Timesavers" (TSC-1)

\$ enclosed. Send Free Book List

Name _____


Address _____

City _____ Zone _____ State _____

■■■■■ (outside U.S.A. priced slightly higher) ■■■■■

15,000,000

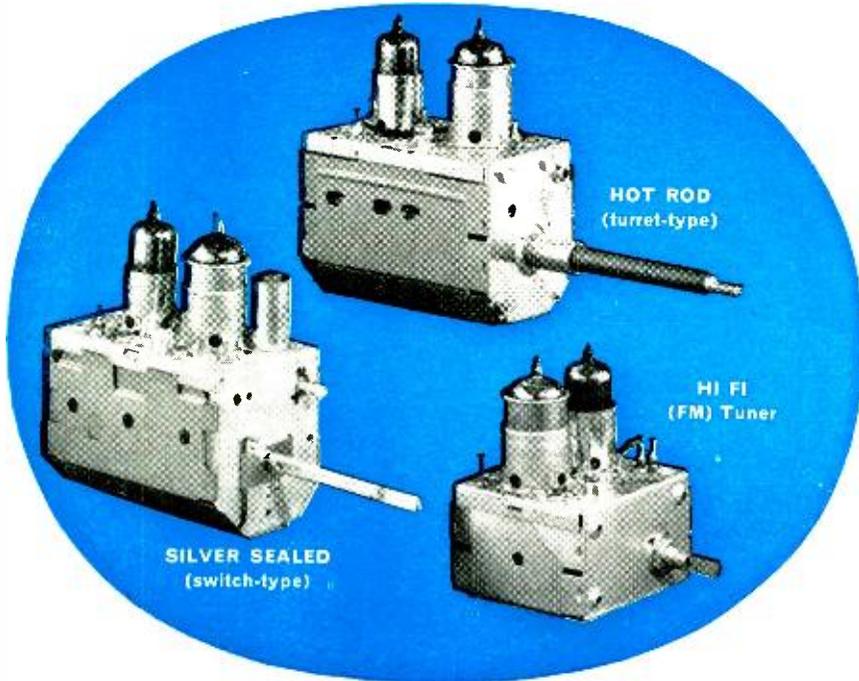is a lot of anything—
whether it's \$ dollars,
donuts , or...
TV and FM TUNERS




Since the early days of television, Sarkes Tarzian has turned out over fifteen million TV Tuners for the nation's leading manufacturers of receivers.

That's a lot of TUNERS in anyone's language.

The Tarzian technical "know-how"—combined with modern, automated production facilities—has led Tarzian to the position of *the world's leading manufacturer of tuners.*

And, only Tarzian offers both the HOT ROD (turret-type) and SILVER SEALED (switch-type) . . . as well as the newer Hi Fi FM Tuner. All with the built-in reliability that has helped make the Tarzian Tuners world famous.

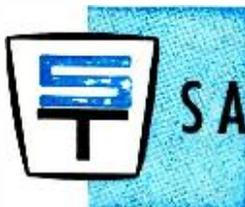For more information, write to: Sales Department
Tuner Division



SARKES TARZIAN INC

east hillside drive • bloomington, indiana

Manufacturers of Semiconductors, Air Trimmers and Broadcast Equipment

TECHNICIANS' NEWS (Continued)

at Tulsa, Oklahoma. As was promised by TESA Oklahoma president, H. O. Eales, a working oil well was given away. It was rolled into the room on a dolly, plugged in and presented to Vincent Lutz, past president of NATESA.

TESA's Chicago Director reminded all present that the general NATESA convention is to be held Aug. 19-21 at the Sheraton Towers Hotel in Chicago.

AREN'T YOU ON THE LIST?

RADIO-ELECTRONICS is publishing a list of known service associations in North America. Areas covered so far are: Pennsylvania, New York, Ohio, Iowa, North Carolina, Kansas, Arizona, Michigan, California, Ontario (Canada), Massachusetts, Missouri, Minnesota, Florida and Montana. The listings started in the August, 1959, issue, and can be consulted for the name of the Association nearest you. If you belong to an association that has not been listed, let us know about it.

States that seem reluctant to admit that they have any activity are Arkansas, Connecticut, New Hampshire, Oklahoma, Rhode Island and Texas. Alaska and Hawaii seem to have no activity at all.

To list an association or to find out the name of the one nearest you, write to: Associations Editor, RADIO-ELECTRONICS, 154 W. 14 St., New York 11, N. Y.

FLORIDA

TELEVISION & ELECTRONIC SERVICE ASSOCIATION OF MIAMI, INC. (TESA MIAMI)

James J. Ross, *corres. sec'y*

(M. Reiser, *acting corres. sec'y*)
119 N. W. 12 Ave.
Miami

TELEVISION & ELECTRONIC SERVICE ASSOCIATION OF ST. LUCIE COUNTY (TESA-St. Lucie County)

Leonard Appel, *secretary*
130 So. 4 St.
Fort Pierce

TELEVISION SERVICE DEALERS ASSOCIATION OF PALM BEACH (TSDA Palm Beach)

Roy Batton, *president*
407 Flamingo
W. Palm Beach

ELECTRONIC SERVICE ASSOCIATION OF BROWARD COUNTY (ESA Broward County)

Hamilton Boyd, *secretary*
901 N.W. 4 Ave.
Fort Lauderdale

TELEVISION SERVICE DEALERS ASSOCIATION OF ST. PETERSBURG (TSDA St. Petersburg)

Bud Fox, *president*
P. O. Box 2711
St. Petersburg

JACKSONVILLE ELECTRONICS TECHNICIAN SOCIETY (JETS)

Dale Andrews, *president*
906 San Marco Blvd.
Jacksonville

TALLAHASSEE TELEVISION & ELECTRONICS ASSOCIATION

Don Birch, *secretary*
213 College Ave.
(Ramm's TV Service)
Tallahassee

MONTANA

ELECTRONIC SERVICE ASSOCIATION OF BUTTE MONTANA (ESA)

Raymond G. Tuszynski, *president*

James Glase, *corres. sec'y*
Templars Hall
215 No. Main St.
Butte

RETAILERS' TAX

All "offerers of service" are required by law to register with the Illinois Department of Revenue as do retailers, according to *NATESA Scope*. They go on to say that the names of all known service offerers in the state have been turned over to the department for cross checking to see if they are registered. Anyone not found on the list will be advised to cease operations or register. After this, arbitrary bills for back taxes will be issued, followed by court judgments and levies. Serious offenders are being processed for criminal-violation prosecution.

END

new PATENTS


MAGNETIC AMPLIFIER

Patent No. 2,907,947

Stephan Steinitz, St. Louis, Mo. (Assigned to Vickers, Inc., Detroit, Mich.)

This amplifier's power windings serve for control as well. Power from the line flows for one half-cycle through D1 and L1. During the other half, D2 conducts flow through L2. The power is limited by the reactors.

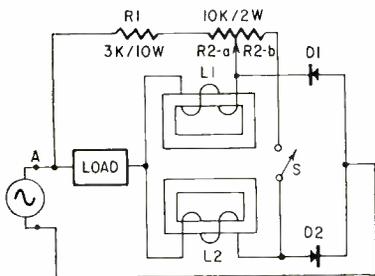Shunt circuit R1, R2-a acts to increase the power. This is accomplished by partly or fully



satürating the core of L1. To show this, assume that A goes positive. Current through the shunt circuit flows into both reactors in the saturating direction. Reducing R2-a permits greater current and therefore more power in the load. At the same time, R2-b must increase. Note that this resistor shunts both diodes, so permits current in the desaturating direction through the reactors.


The inventor notes that a 200-watt lamp can be dimmed with a 3,000-ohm 10-watt resistor for R1 and a 10,000-ohm 2-watt potentiometer R2. Power is reduced by adjusting the potentiometer arm to the right. This increases R2-a, which reduces saturation. It also decreases R2-b, which permits greater desaturation.

ELECTRONIC FLASHER

Patent No. 2,916,670

Helmer T. Pederson, Solana Beach, Calif. (Assigned to Bill Jack Scientific Instrument Co., Solana Beach, Calif.)

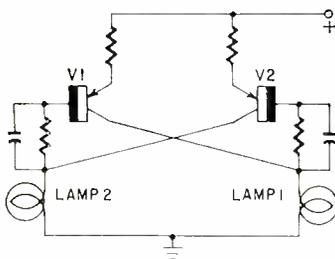This flasher is controlled by a multivibrator. As alternate transistors conduct, the correspond-



ing lights go on. For example, V1 corresponds to lamp 1, etc. The flasher can also operate with a single lamp, a resistor substituting for the other lamp.

DIODE COMPARATOR

Patent No. 2,912,582


James R. Davey, Franklin Township, N. J. (Assigned to Bell Telephone Labs, Inc.)

This circuit indicates when one signal (at A) matches another (at B). The gate is symmetrical so A and B may be interchanged. The signal may be either -1.5 or -13 volts.

When signals at A and B are equal, both diodes block and permit pulses to pass from input to output. When they are unequal, one diode conducts to short out the input. The following chart illustrates this point:

A	B	P	output
-1.5	-13	-13	no
-1.5	-1.5	-6.5	yes
-13	-13	-18	yes

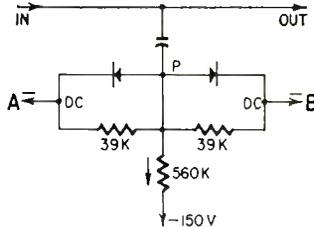When the bias at P is more negative than A or B, both diodes block and the input is transmitted.



Otherwise (see first case in previous chart) the pulse is shorted out through a diode.


An unknown quantity may be measured as follows. Using binary notation, a "zero" may correspond to -13 volts and a "one" to -1.5 volts, and we need as many gates (see diagram) as we have digits in the unknown number. The known number is applied at B (of each gate). To make the measurement automatic, the known is varied rapidly through all possible combinations. When it is equal to the unknown number (which remains constant), a light can flash or a relay can be energized to indicate that fact.

HIDDEN MICROPHONE

Patent No. 2,901,552


Giovanni Celoso, Milan, Italy

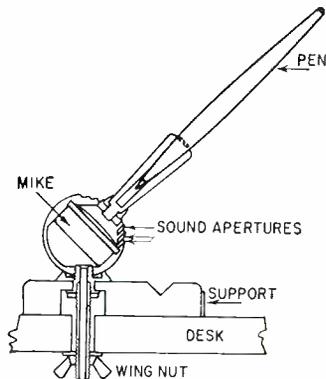Here is a novel way to camouflage a microphone: hide it in a pen holder. A real pen is




inserted into the holder to make it look real. The holder is tied down on a desk as illustrated. The cable for the mike may be passed through a hole in the desk. END

IT'S DRUGS

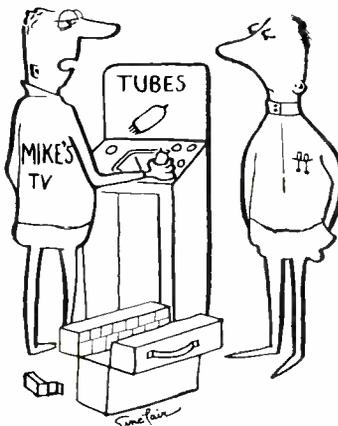

"Ours is broken."

RELIABLE

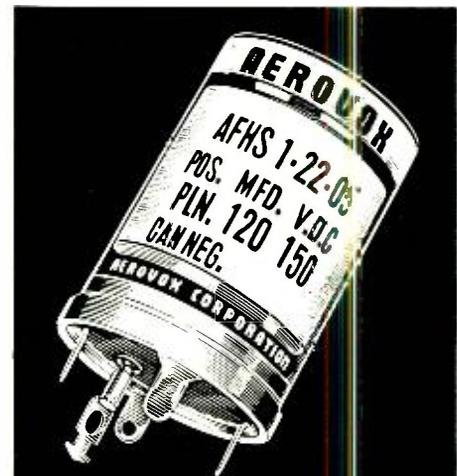

TWIST-PRONG ELECTROLYTICS

A satisfactory repair job means a satisfied customer. To keep your customer happy and to prevent costly call-backs you must depend on a reliable replacement. Aerovox AFH Twist-Prong Electrolytics can always be depended on to give long-life and excellent service because they're made better . . . high-purity aluminum foil construction throughout, 85°C operation, improved hermetic sealing and rugged prongs and mounting terminals.

Available in the widest selection of exact-duplicate replacements including printed-wiring and selenium rectifier types. Your local Aerovox Distributor stocks the replacement you need when you need it. Call on him today for all your capacitor requirements.

BUY THEM BY THE KIT . . .

Your Aerovox Distributor offers you special "Stack-A-Lytic" kits (AK-400 and AK-401) with a selection of 8 or 16 popular TV replacements with a FREE handy metal storage rack with stacking features.



AERVOX CORPORATION
DISTRIBUTOR DIVISION
NEW BEDFORD, MASS.

Ask By Name For
GENUINE "NO NOISE" PRODUCTS
 your assurance of brand name quality



NO-NOISE TUNER-TONIC with PERMA-FILM

- Cleans, lubricates, restores all tuners, including wafer type.
- Non-toxic, non-inflammable.
- For TV, radio and FM use.
- Economical—a little does a lot.

6 oz. Aerosol Can
\$3.25
 Net to Servicemen

NO-NOISE VOLUME CONTROL and CONTACT RESTORER

- Cleans
- Lubricates
- Protects
- Not a Carbon Tet Solution

2 oz. Bottle **\$1.00**
 6 oz. Spray Can **\$2.25**
 Net to Servicemen

FREE At your Jobbers
5" PLASTIC EXTENDER

- Push Button Assembly
- For Pin-Point Applications
- Does Not Cause Shorts

ELECTRONIC CHEMICAL CORP.
 813 Communipaw Avenue Jersey City 4, N. J.
 P.S. Be Sure To Ask For **NO-NOISE RUBBER COAT**
 6 oz. Spray Can **\$3.25**

ONE CENT SALE

BUY ONE AT OUR REGULAR LOW PRICE and GET the SECOND for ONLY 1c MORE

CITIZENS BAND TRANSMITTER (27 MC) 5 watt chassis, complete with crystal. \$14.49 each; two for \$15.00.

CITIZENS BAND RECEIVER chassis tunable through all 22 channels. Complete with audio amplifier. \$9.99 each, two for \$10.00.

AMATEUR BAND TRANSCEIVER (144-148 MC) chassis with dual VHF triodes for walkie-talkie radiophone. \$9.99 each, two for \$10.00.

TRANSCEIVER TRANSFORMER: Mike to grid input and plate to low impedance headphone output. Good for telephone handsets. \$1.99 pair, two for \$2.00.

SIGNAL BOOSTER chassis for 27 MC. High gain (20dB) double tuned RF pentode amplifier. Improves performance of any Citizen Band receiver. Complete with tube \$11.99 each—2 for \$12.00.

COILED CORD 4 conductor 11" telephone cord. Extends to over 4 ft. .39 each, two for \$1.00.

KIT OF PARTS for AM-FM VHF radio receiver. Tunable from 80-200 mc, which includes U.S. satellite frequencies. \$6.99 each, two for \$7.00.


TRANSISTOR AUDIO AMPLIFIER gives 50X voltage gain on low level signals. Operates on 1 1/2 volts. \$3.99 each, two for \$4.00.

CONVERTER (crystal controlled) for 27 MC Citizens Band. Adapts any standard broadcast radio to 27 MC band. Times all 22 channels. Complete with tubes and crystal. \$14.99 each, 2 for \$15.00.

ALL MERCHANDISE GUARANTEED LIMITED QUANTITY—NO LITERATURE OR CATALOG

Remit in full. Include sufficient postage.
 No C.O.D.'s.

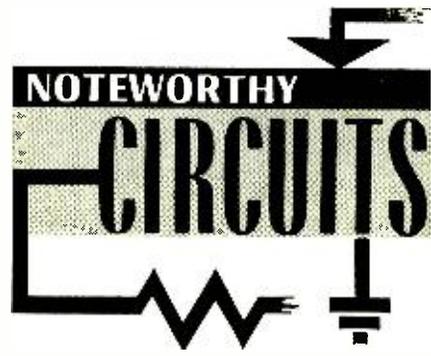
VANGUARD ELECTRONIC LABS
 Factory & Mail Order, 190-48 99th Ave.,
 Retail Store; 196-23 Jamaica Ave.
 Dept. RE-7 Hollis 23, N.Y.



BATTERY-OPERATED STROBOSCOPE

The diagram shows the circuit of a simple stroboscope operated from a 6-volt battery. Since no power-line connections are needed, this instrument will be useful in field applications for speed and rate measurements and for

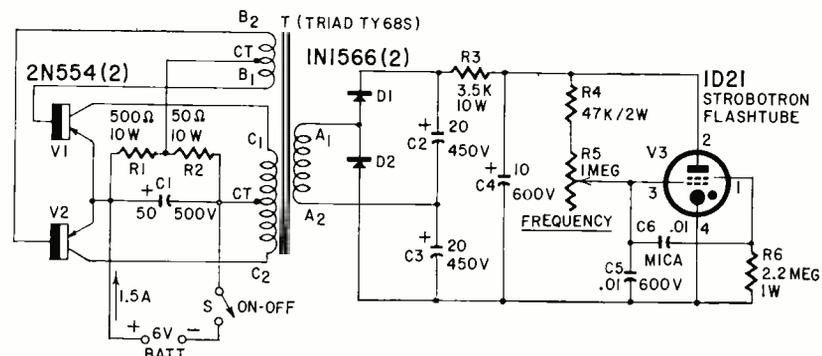transistor transformer (T) and a voltage-doubler circuit made up of two silicon diodes (D1 and D2, Motorola 1N1566), three electrolytic capacitors (C2, C3 and C4) and a filter resistor (R3). When the instrument is in opera-



- R1—500 ohms, 10 watts
- R2—50 ohms, 10 watts
- R3—3,500 ohms, 10 watts
- R4—47,000 ohms, 2 watts
- R5—pot, 1 megohm
- R6—2.2 megohms, 1 watt
- C1—50 μ f, 500 volts, electrolytic
- C2, 3—20 μ f, 450 volts, electrolytic
- C4—10 μ f, 600 volts, electrolytic
- C5—.01 μ f, 600 volts, paper
- C6—.01 μ f, 600 volts, mica
- BATT—6 volts
- D1, 2—1N1566
- S—spst toggle
- T—power transformer, toroidal; primary, 12 volts; secondary, 250 volts, 65 ma (Triad TY68S)
- V1, 2—2N554
- V3—1D21
- Chassis and case to suit
- Miscellaneous hardware

freezing machinery in motion. The strobe's flashing rate is continuously variable between 10 per second (600 per minute) and 112 (6,720 per minute). The power supply consists of a transistor chopper with two inexpensive power transistors (Motorola 2N554), a

tion, 1.5 amperes are drawn from the 6-volt battery. For short-term operation, a hot-shot battery (or some smaller type) may be enclosed in the stroboscope case. Bright orange-red flashes are obtained from the strobotron tube (Syl-

TOP-HAT SILICON RECT.

PIV/RMS 50/35 .20 ea. 10 for 1.90	PIV/RMS 300/210 .45 ea. 10 for 4.35
PIV/RMS 100/70 .30 ea. 10 for 2.90	PIV/RMS 400/280 .55 ea. 10 for 5.25
PIV/RMS 200/140 .85 ea. 10 for 3.40	PIV/RMS 500/350 1.00 ea. 10 for 6.25
PIV/RMS 600/420 .85 ea. 10 for 8.00	PIV/RMS 700/490 1.00 ea. 10 for 9.50
PIV/RMS 900/630 1.30 ea. 10 for 12.50	PIV/RMS 1000/700 1.75 ea. 10 for 17.00
PIV/RMS 800/560 1.10 ea. 10 for 10.50	PIV/RMS 1100/770 2.10 ea. 10 for 20.00

500 MA RECTIFIERS GUARANTEED
 Input Working Range RMS/ACV Res or Cap.
 Designed for Bridge or C.T. up to 750ma D.C.
SPECIAL!!! All Purpose Rectifier 400 piv @ 250ma
 .40 ea. 25 for 9.00

ELECTRONIC SPECIALS: 100 Different Pre. Res. Mepeco, Shalicon, etc. 1/2W, 1W, 2W, 1/2%, 1% Tol. Only \$1.90/c; JAN SWITCH, NEW ST42D S.P.D.T. A H-H C-H Bat Handle .25 ea. 10 for \$2.40 w/hdw; 100 Ass. RADIO & TV KNOBS Pushons \$1.90—all new Distributors O.E.M. Exporters. Write Quantity Prices All Material Guaranteed. \$2.00 min. order. Orders F.O.B. NYC. Include check or money order. Shpg. charges plus. C.O.D. orders 25% down.

WARREN DIST. CO.
 NYC 7, NY 87-89 Chamber St. WO 2-5729

OUT OF SPACE?

You bet we'd be... if we were to tell you all about AUDION'S 'Out of this World Hi Fi Values'!

Write for free Catalog

audion
 25-E Oxford Road
 Massapequa, New York

PACKAGE HI FI or SINGLE COMPONENTS

You'll find our prices low and service fast.

Write for our quotation

CENTER ELECTRONICS Co., Inc.
 74-R Cortlandt Street, New York 7, N.Y.

LOOK

no further... if you're searching for hi-fi savings. Write us your requirements now.

Key Electronics Company
 120-A Liberty St., N.Y. 6, N.Y.
 Cloverdale 8-4288


vania 1D21). This tube takes a four-pin socket and may be mounted in a flash-gun type reflector to intensify the

flashes. Potentiometer R5 is the frequency control. It regulates the flash rate of the stroboscope.—*Rufus P. Turner*

CATHODE-FOLLOWER AMPLIFIER

This cathode-follower amplifier is comparatively simple and inexpensive. Except for the oil-filled capacitors,

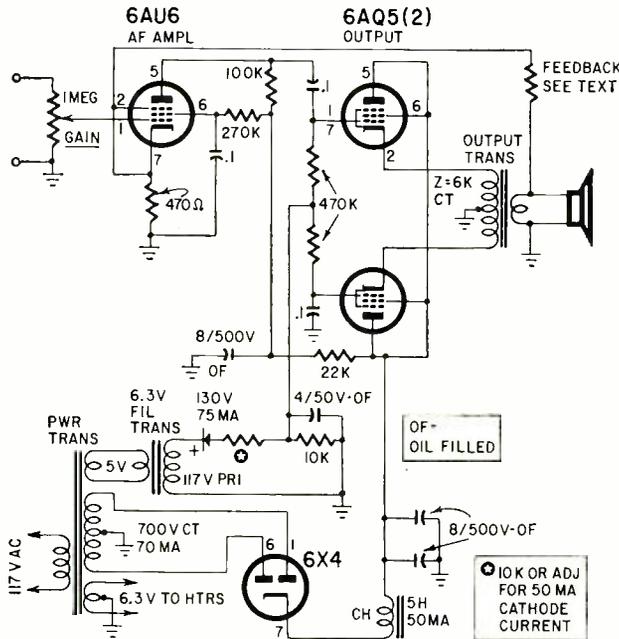if you use electrolytic capacitors in place of the specified oil-filled units, increase the capacitance somewhat. The




standard components are used throughout. The power supply may look a little unusual, but it insures safe operation by isolating the ac line from the bias supply. No hot chassis with this arrangement. Values are not critical, but

primary impedance of the output transformer is about half that used in a conventional triode output stage. If desired, feedback can be added. A little experimenting will show how much.—*Richard Youse*

FEEDBACK TONE CONTROL

A clever tone control is used on some Radialva TV receivers. The diagram

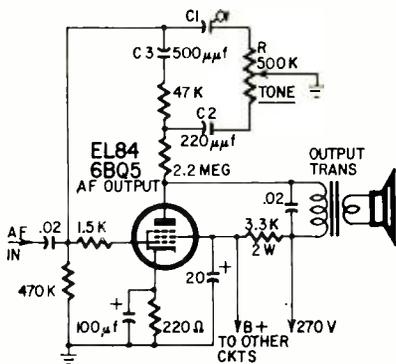shows the feedback network between the plate and grid of the audio output tube.



shows the feedback network between the plate and grid of the audio output tube.

Tone is controlled by potentiometer R. When its arm is turned fully counterclockwise, capacitor C1 is connected between grid and ground produces treble cut. C2 is ineffective because of the pot's high resistance.

When R is turned fully clockwise, capacitor C2 is connected between feedback and ground, thus reducing feedback at high frequencies and producing treble boost. This time C1 has no effect because of the pot's high resistance. The exact operation of the circuit is somewhat complicated since the feedback network is frequency-sensitive because of C3. This capacitor produces some medium cut.—*Martin de France*

HI-FI & STEREO COMPONENTS
Send us your list for a **SPECIAL PACKAGE DEAL QUOTE**
No sale too small. Trade-ins accepted. **BONAFIDE** offers biggest discounts on all standard brands. Expert advice and full guarantee are assured at
BONAFIDE ELECTRONICS
Dept. RE7, 89 1/2 Cortland St., N.Y. 7, N.Y.
WE WILL NOT BE UNDERSOLD

A NOTE TO THE HI-FI BUYER
AIR MAIL us your requirements for an **IMMEDIATE LOWEST PRICE QUOTATION**
Components, Tapes and Recorders
SHIPPED PROMPTLY AT LOWEST PRICES
WRITE TODAY FOR FREE CATALOG
AUDIO UNLIMITED 714-R Lexington Ave. New York 22, N. Y.

OPPORTUNITY ADLETS
Rates—50c per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for September issue must reach us before July 8, 1960.
RADIO-ELECTRONICS,
154 West 14 St., New York 11, N. Y.

ANNNOYED BY EXPENSIVE REPLACEMENT COSTS OF 9V TRANSISTOR RADIO BATTERIES? Save money with new rechargeable battery and charger set. Recharges up to 100 times by inserting into household outlet. Only \$1.95 postpaid. Guaranteed. **LITTLE FALLS IMPORT CO.,** Little Falls, N. J.

RADIO & TV TUBES at Manufacturers' Prices! 100% Guaranteed! Brand New! No re-brands or pull. **UNITED RADIO,** Box 1000-R, Newark, N.J.

LEARN WHILE ASLEEP. Hypnotize with your recorder, phonograph or amazing new Electronic Educator endless tape recorder. Catalog, details free. **SLEEP-LEARNING ASSOCIATION,** Box 24-10, Olympia, Wash.

SONGPOEMS and LYRICS WANTED! Mail to: **TIN PAN ALLEY, INC.** 1650 Broadway, New York 19, N. Y.

PROFESSIONAL ELECTRONIC PROJECTS — Organs, Timers, Computers, etc.—\$1 each. List Free. **PARKS,** Box 1665, Seattle 55, Wash.

RADIO & TELEVISION RECEIVING TUBES, brand new, first line name brands only. No rejects, no pull. Discounts up to 60% off list. **EDISON TUBE CO.,** 355 Main St., Meriden, N.J.

LEARN CIVIL and criminal investigation at home. Earn steady, good pay. **INSTITUTE APPLIED SCIENCE,** 1920 Stummside, Dept. 26B, Chicago 40, Ill.

COMEDY PARTY RECORDS. 45 RPM. \$1 each or 6 for \$1.95. **HOLLYWOOD JOKERS** Dept. B, P.O. Box 1986, Hollywood 28, Calif.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. **HAZELTON INSTRUMENT CO.,** 128 Liberty Street, New York, N.Y.

SEND DIME for surplus catalogue and **FREE GIFT.** **SMOS,** 1212 E. Fifth St., Charlotte 4, N. C.

DISCOUNTS UP TO 50% on HI-FI amplifiers, tuners, speakers, tape recorders, individual quotation only, no catalogs. **CLASSIFIED HI-FI EXCHANGE,** 2375 East 65th Street, Brooklyn 34, N.Y.

COMPONENTS, Recorders, Tapes. **FREE Wholesale Catalogue.** **CARSTON,** 215-T East 88th St., New York 28, N.Y.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean radio and TV receiving, transmitting, special-purpose, Magnetrons, Klystrons, broadcast types, etc. Want military & commercial lab/test and communications equipment such as G.R., H.P., AN/DPM prefix. Also want commercial receivers and transmitters. For a fair deal write **BARRY,** 512 Broadway, New York 12, N. Y. WAHler 3-7000.

AMPEX, Concetton, Crown, Magnecord, Scotch, Norplex, Bogon, Tandberg, Sherwood, Rek-O-Kut, Seeb, Shure, Dynakit, others... Trades. **BOYNTON STORE,** Dept. RE, 10 Pennsylvania Ave., Tuckahoe, N.Y.

RADIO & TELEVISION TUBES — Brand new — 1st quality, no rejects, top name brands in original boxes, 60% off list. **FREE BOXES** with orders. Prompt deliveries. **U T C,** Box 306, Syosset, New York.

PRINTED CIRCUIT LAYOUT KITS. Complete materials and instructions to make three Printed Wiring Boards \$3.95. State choice — Transistor Receivers, amplifiers, Power Supplies. **ADVANCE DESIGNS INC.,** 933 Lullaby Lane, Vienna, Va.

1000 BUSINESS CARDS, Raised Letters \$3.95 Postpaid. **FREE SAMPLES.** **JOHN H. TAYLOR,** Dept. J. R.D. 2, Box 215, West Middlesex, Pa.

Tube—TV and Radio tubes—Guaranteed. Save up to 80% — Brand new, no pullouts, some factory seconds. Write: **EMKAY ELECTRONICS,** P.O. Box 142, Blythesbourne Station, Brooklyn 19, N. Y.

TV PICTURE TUBES!
At Lowest Prices

10BP4 \$ 7.95	17BP4 \$ 9.95	21AMP4 \$15.75
12LP4 8.50	17CP4 17.00	21ATP4 15.75
14BCP4.... 9.95	17GP4 17.00	21AUP4 15.75
16DP4 12.00	17HP4 12.50	21EP4 13.50
16EP4 12.75	17LP4 11.50	21FP4 14.50
16GP4 14.50	17QP4 9.95	21WP4 14.00
16KP4 9.95	17TP4 17.00	21YP4 14.50
16LP4 10.95	19AP4 16.00	21ZP4 13.50
16RP4 9.95	20CP4 13.50	24CP4 23.50
16WP4 14.00	20HP4 14.50	24DP4 24.50
16PT4 9.95	21AP4 22.00	27EP4 39.95
17AVP4.... 12.50	21ALP4.... 15.75	27RP4.... 39.95

1 year warranty
Aluminized tubes \$3.00 for 21"; \$5.00 for 27" and 27" additional. Prices include the return of an equivalent similar tube under vacuum. These tubes are manufactured from reprocessed used glass bulbs. All parts and materials including the electron gun are brand new.
ALL PRICES FOR CHICAGO, ILLINOIS. Deposit required, when old tube is not returned, refundable at time of return. 25% deposit required on COD shipments. Old tubes must be returned prepaid. Tubes shipped Rail Express. Shipped only to Continental U.S. and Canada.
WRITE FOR COMPLETE LIST.
PICTURE TUBE OUTLET
2922 North Milwaukee Ave.
Chicago 18, Ill. Dickens 2-2048

If you are a career-minded engineer or technician . . .

RE-DIRECT your future aims to high standing in NUCLEAR ENGINEERING technology

Learn Nuclear Engineering Technology through an advanced home study program offered by CREI Atomics. Enrollment is limited.

ONLY A LIMITED NUMBER OF MEN will be accepted at this time for this program of home study offered by CREI ATOMICS, an expertly-staffed extension division of The Capitol Radio Engineering Institute.

U.S. Atomic Energy Commission states about the severe shortage of trained people in nuclear technology: "... the immediate goal is to retrain, through short courses . . . those already grounded in traditional disciplines." Through CREI Atomics you can now combine your present technical education and engineering experience with knowledge in nuclear engineering and technology. The result: increased career opportunities and corresponding income advantages as the nuclear field develops.

Program of study includes—

Nuclear Physics, Reactor Physics, Thermodynamics, Reactor Technology, Reactor Controls, Instrumentation for Reactor Control, Isotopes, Health Physics—many other subjects



USE THIS COUPON TO REQUEST DETAILED CATALOG


CREI Atomics
 3224 16th Street, N.W.
 Washington 10, D.C.
 Please send me complete information about CREI ATOMICS.

name _____
 street _____
 city _____ state _____
 job title _____



PHILCO 9H25U

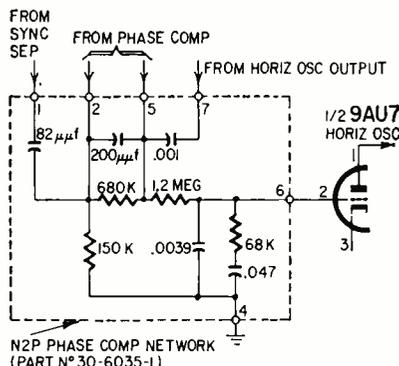The set came in with very critical horizontal hold. At times the picture would float (showing the horizontal blanking bar) and the horizontal sync would lock in, it was very jittery. Re-



sistance measurements showed more than 2 megohms between the chassis and pin 2 of the 9AU7—an abnormally large reading. Circuit checks revealed the cause, the 680,000-ohm resistor between points 2 and 5 of the N2P phase-

comparator network was open.—W. G. Eslick

BENDIX T20 CHASSIS

If you work on the tuner in these sets and when you are finished find that the set isn't working, check the two rear mounting screws on the tuner. Be sure that each one has a cup washer on it. If not, the mounting screws project too far into the tuner and sometimes short out a lead.—Ray Baum

MAGNAVOX CT257

Horizontal and vertical sync were both unstable. On some channels the picture would jitter horizontally and roll intermittently but for the most part the hold was almost uncontrollable.

The customer advised me that another technician replaced the picture tube recently and it was only since then that the set was behaving this way. I listened politely but quickly dismissed this explanation as another dissatisfied customer complaint.

When all else failed, the set was taken to the shop. The first point I tried to establish was whether the trouble lay in the sync circuits or the age circuit so I hooked up an external age bias supply. There was a slight improvement in sync stability but not enough to warrant further examination of the age system.

Therefore, I concentrated on the sync circuits. Every capacitor was checked by direct substitution and every resis-



PERFECT TOGETHER

Matched perfection of movement; the two shoes at dance time, and the ESL MICRO/FLEX cartridge in the ESL GYRO/BALANCE arm.† Such matchless stereo perfection can be yours!*

*only \$49.50 †only \$34.95



FOR LISTENING AT ITS BEST
Electro-Sonic Laboratories, Inc.

Dept E • 35-54 38th St • Long Island City 6, NY


tor was okayed. The waveform at the output sync stage was obviously distorted but I could find no apparent cause for it. The previous age test eliminated that part of the receiver as the source of trouble so I was in a quandary.

I stopped for a moment to reconsider what the customer had told me and wondered if she possibly could have been on the right track. Two points were noted: the picture tube had no Aquadag coating and the tuner shield was missing. Was it possible, I wondered, that the picture tube was radiating into the tuner and distorting the sync pulses without noticeably affecting the video quality. An old tuner shield immediately answered that one for me—as soon as it was clipped into place the sync pattern cleared up and the picture took hold.—*Frank A. Salerno*

LOOPSTICK TRACKING

Ferrite-core antennas are used almost exclusively in transistor radios. If one is replaced, it may need adjusting for satisfactory tracking.

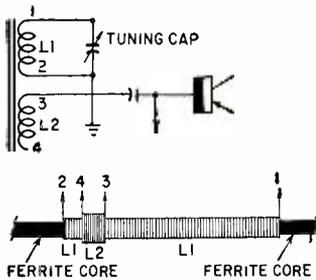The sketch shows the usual circuit and the physical connections to the antenna. Tracking is adjusted by removing turns from the long coil (L1) at the end away from the secondary coil (L2). Turns should not be removed



from terminal 2, since mutual coupling to the low-impedance transistor coupling coil (L2) may be upset. Take off turns at lead 1 a couple at a time.—*Lawrence Shaw* END

50 Years Ago

In Gernsback Publications

HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In July, 1910, Modern Electrics

- A New Franch Telephote [Television] Apparatus, by Frank C. Perkins.
- The Gernsback Detectorium, by A. C. Austin, Jr.
- Tabular Variable Condenser, by H. Linde.
- The Poulson System of Wireless Telephony and Telegraphy, by C. F. Elwell.
- High Frequency Oscillations, by Moore Stuart.
- An Ingenious Wireless Transmitter.
- Image Transmitting Devices, by A. C. Marlowe.
- Simple Detector, by L. L. Riley.
- Cleat Insulators, by Eugene Wulff.
- Automatic Break Switch, by Harold Peterson.

SALE PRICED FOR A SELL-OUT!
SENSATIONAL PRICE SLASHING
 "Many values a DOLLAR for a DIME" ... ALL BRAND NEW MONEY BACK GUARANTEE

Some ITEMS in THOUSANDS, others in limited quantities

Rush your order for desired quantities of each—Send 20% deposit with order

- 15000 - SELENIUM RECTIFIERS 65 ma. 16c
- SMALL HANDY SCREWDRIVER regular price 15c. 2c
- SPLINE WRENCH TOOL 1" blade. 5c
- FUSE #3AG 4 amperes 1 1/4" x 1/4" 1c
- LOCAL SOCKET mounting centers 1 1/2" 1c
- WHITE TUBE CARTONS SP. LP. GT. small G. 1c
- CONDENSERS .0022-.200v. .00082-.500v. 1c
- CERAMICS 1, 2, 5, 10, 25, 47, 68, 75, 120, 150 mfm 2c
- CERAMICS 220, 250, 330, 500, 560, 680, 829 1K mmf. 2c
- MICAS 5, 25, 75, 100, 150, 250, 330, 470, 1K, 10K mmf. 2c
- DISCS 5, 6.8, 10, 25, 50, 75, 100, 150, 220, 1K mmf. 3c
- TV PEAKING COILS 90 oh. 120 oh. 245 oh. 1c
- TOP BRAND CONDENSER .01-.500v list 35c. 2c
- CONDENSERS .047-.600v. 1-.600v. 25-.600v. 47-.400v. 5c
- CONDENSERS .001-1000v. .01-1000v. .039-1000v. 5c
- COND'S 1-1000v. .007-1600v. .03-1600v. .005-5000v. 5c
- CONDENSERS 1-50v. 1-100v. 1-150v. 2-450v. 4-500v. 5c
- CONDENSER 100/25-50v list price \$1.75. 10c
- CONDENSER FP type 10-150v list price \$2.25. 10c
- CONDENSER 50/30-150v with mounting strap. 25c
- WAFER SOCKETS standard octal. 7 pin. 9 pin. 3c
- MOLDED SOCKETS standard octal. 7 pin. 9 pin. 6c
- METAL TUBE SHIELDS miniature 3 1/4". novel 1". 3c
- PILOT LIGHTS top brand 41, 46, 47, 51. 5c
- PILOT LIGHT SOCKET bayonet, long leads. 5c
- LINE CORD 6' complete with plug. 8c
- LINE CORD 550Q 6' complete with plug. 8c
- TV CHEATER CORD 6' complete with both plugs. 14c
- 50' HOOK-UP WIRE red, white, blue, black ea. roll 15c
- RCA PHONO PLUG AND JACK SET. 10c
- SPEAKER PLUG SET wired long leads. 10c
- RESISTORS 1/2-W-10% 47, 100, 150, 270, 330, 470, 560Ω. 2c
- RESISTORS 1/2-W-10% 820, 1K, 1800, 2700, 4700, 6800Ω. 2c
- RESISTORS 1/2-W-10% 8200, 10K, 22K, 47K, 100K, 470KΩ. 2c
- RESISTORS 10% 470-1W, 1K-1W, 15K-1W, 180-2W. 2c
- OVAL LOOP ANTENNA standard type and size. 10c
- RADIO KNOB 1/2" acorn, brown, push-on. 2c
- TUNING SHAFT BRACKET handy for many mountings. 5c
- WIRE'ND RST'S -5W 250, 470, 650, 5K, 10K, 16KΩ. 8c
- WIRE'ND RST'S -10W 20, 50, 100, 220, 280, 525Ω. 8c
- WIRE'ND RST'S -10W 680, 1K, 1500, 2K, 2500, 3KΩ. 8c
- WIRE'ND RST'S -10W 5K, 7K, 10K, 15K, 22.5KΩ. 8c
- CONTROL 10K with switch 1/2" shaft above bushing. 10c
- CONTROLS less/sw 50K, 1/4 meg, 3/2 meg, 750K, lineg. 10c
- ION TRAPS single, double, new 110° type. 10c
- PHONO MOTOR 110v 78 rpm complete w/turntable. \$1.00
- PHONO ARM 78 rpm complete with cartridge. 1.00
- PHONO ARM 4-speed w/flipover cartridge. 2.19
- RONETTE STEREO CARTRIDGE 1-speed. 2.97
- SONOTONE CARTRIDGE dual sapphire #3T. 2.97
- G.E. DIAMOND STEREO CARTRIDGE #GC7. 9.46
- MONARCH STEREO CHANGER 4-speed complete. 16.49
- VM STEREO CHANGER 4-speed complete. 22.34
- GARRARD STEREO CHANGER #RC-121. 28.64
- AM RADIO TUNER connects on Phono or TV. 4.57
- \$25 GUARDIAN connects on Radio as Intercom. 6.90
- JEWEL RADIO AC-DC complete with 4 tubes. 8.99
- RADIO CHASSIS PAN 9 1/2"x5 1/2"x1 1/2" ind. 5 sockets.39
- RADIO CHASSIS PAN 10 1/4"x4 1/2"x2"19
- RADIO CHASSIS PAN 9 5/8"x3 1/2"x2"19
- VARIABLE CONDENSER 2-gang 420/102 mfd.29
- RADIO LOOPSTICK ANTENNA standard ferrite adjustable.29
- TOGGLE SWITCHES SPST-14c SPDT-24c DPDT-.14
- I.F. COILS 10.7mc FM 4.5mc 9.1mc29
- I.F. COIL popular 45mc for most Radios29
- I.F. COIL 262kc for Auto Radios.29
- RAMBLER 2-TRANSISTOR RADIO loud Spk. compl. 7.99
- RADIO BATTERY 9V same as Eveready 21629
- 2-STATION INTERCOM ready to operate. 15.97
- METAL SPEAKER GRILL 8"x5 1/2" for Radio, Phono, etc.19
- PM SPEAKERS 3"-88 4"-88 5"-90 6"- 1.28
- PM SPEAKERS 4"x6"-1.59 5"x7"-1.86 6"x9"- 1.99
- PM SPEAKER 8" with 6.8 oz. Alnico mag. & twin-cone. 3.86
- PM SPEAKER 12" with 6.8 oz. Alnico mag. & twin-cone. 5.97
- 12" UNIVERSAL HI-FI SPEAKER 20W, 50-15000cps 9.97
- AUDIO OUTPUT TRANS. 50L6-29 6K6-29 6V6- 38
- AUDIO OUTPUT TRANS. 3Q4-37; 6L6-48; 6V6pp. 58
- 3 1/2" TWEETER SPEAKER for HI-FI list price \$2.75. 88
- SELENIUM RECTIFIERS 65ma-16; 75ma-22; 100 ma. 28
- SELENIUM RECTIFIERS 150ma-32; 300ma-39; 450 ma. 59
- RCA SYNCHROGUIDE COIL #205R1.69
- SOUND TAKE-OFF COIL for TV Tuner.49
- RATIO DETECTOR COIL 4.5mc.49
- RATIO DETECTOR COIL 10.7mc.49
- TV SOUND I.F. COIL 4.5mc.49
- TV SOUND TRAP COIL49
- TV I.F. COIL for 2nd, 3rd & 4th video.49
- TV AGC COIL = 1R4AG standard for most TV's.49
- EM FOCUS COILS 247Q, 320Q.29
- EM FOCUS COILS 470Q, 1000Q, 4000Q.50
- FOCUS CONTROLS 4W 1500Ω, 2000Ω, 5000Ω.79
- #630 CONTROL 10K-1meg with switch list \$3.00 99
- #630 CONTROL 50K-1meg.48
- #630 ELECTROLYTIC CONDENSER 40/40/10-450v 1.19
- #630 ELECTROLYTIC CONDENSER 40/10/80-450v 1.24
- #630 POWER TRANSFORMER #201T6 list \$35.00 12.97
- TV PICTURE TUBE #17BP4B Top make, brand new 19.65
- TV PICTURE TUBE #21YP4A Top make, brand new 24.97
- TV PICTURE TUBE #21DP4A Top make, brand new 32.49
- TOP BRAND 104 TUBE also serves as 1T1. \$.07
- TUBES 1T4, 1L4D3, 1L4B3, 6C4, 6SH7, 6KT.19
- TUBES 5U4, 6AL5, 6AU6, 6AV6, 50C5, 6V6.62
- TUBES 6SN7, 6AC7, 6CB6, 6AX4, 6J6, 50L6.79
- TUBES 12BH7, 12BY7, 1B4, 6X4, 6CG8, 6A8.89
- DEFLECTION YOKES 60° standard type.25
- DEFLECTION YOKES 70° Incl. Instructions. 1.69
- DEFLECTION YOKES 90° Incl. Instructions. 2.28
- DEFLECTION YOKES 110° Incl. Instructions. 3.97
- FLYBACK TRANSFORMER 70° Incl. Instructions. 1.49
- FLYBACK TRANSFORMER 90° Incl. Instructions. 1.97
- FLYBACK TRANSFORMER 110° Incl. Instructions. 1.97
- TV 10KV CARTWHEEL CONDENSER.05
- TV 15KV CARTWHEEL CONDENSER.15
- TV 20KV CARTWHEEL CONDENSER.28
- TV 30KV CARTWHEEL CONDENSER.39
- TV CRT SOCKET with 18" leads.10
- TV ANODE LEAD with long lead and clip.18
- TV FILTER CHOKES 62Q, 250Q.79
- DIODE CRYST. 1N21, 1N23, 1N34, 1N60, 1N54, 1N69.19
- SILICON RECTIFIERS 500ma-59 750ma-.89
- S3 TV CRT BRIGHTENER 6 wire parallel.59
- S8 TV INDOOR ANTENNA 3-section hi-dip.79
- TV PM FOCALIZER adjusts for any obstar.84
- ELECTRONIC TESTER for TV & Radio pocket size 1.99
- WIRE CUTTER & STRIPPER finest made.65
- 1-LB. ROSIN CORE SOLDER 10/60.79
- S6 ELECTRIC SOLDERING GUN 1.30W. 3.98
- TV MASK 21E14 (Minimum Sold 20)39
- TV SAFETY GLASS 18"x22 1/2" (minimum sold 30) 2.68
- TV KEYED AGC KIT w/6AU6 tube & Instructions. 2.96
- TV POWER TRANSFORMER 250ma with Instructions. 3.97
- STAD'N NEUTRODE TUNER 21mc W/Instructions. 15.97
- 70° TV CONVERSION KIT Complete w/Instructions. 9.97
- 90° TV CONVERSION KIT complete w/Instructions. 11.98
- 110° TV CONVERSION KIT complete w/Instructions. 12.62
- DX-16 SUPER DELUXE TV KIT complete w/ tubes. 79.95
- 21" TV CABINET KIT mahog. walnut or blond. 22.78
- 24" TV FRONT PANEL mahog. walnut or blond. 19.98
- 1000 - RUBBER GROMMETS 1/2" OD, 3/8" ID 2.00
- 1000 - RADIO KNOB SET SCR. 1 1/2" long, 1/2" diam. 2.00
- 300 - RADIO KNOB SET SCREWS 1/2" long, 1/8" diam. 1.00
- 200 - PLATED SOLID WING NUTS #8 1/2". 1.00
- 600 - NUTS, SCREWS, WASHER, RIVETS, Etc. \$1
- 1000 - MICA CONDENSERS 820mmf-500v. 7.50
- 1000 - MICA CONDENSERS 10000mmf-500v top brand. 16.00
- 1000 - CERAMIC CONDENSERS 1mmf-500v. 7.50
- 1000 - CERAMIC CONDENSERS 2mmf-500v. 7.50
- 1000 - CERAMIC CONDENSERS 10mmf 500v. 7.50
- 1000 - CERAMIC CONDENSERS 120mmf 500v. 12.00
- 1000 - DISC CERAMIC CONDENSERS 10000mmf-500v. 15.00
- 1000 - TOP BRAND TUBULAR COND'S. #022-200v 7.50
- 1000 - ASST. 1/2W RESISTORS short leads. 3.00
- 300 - ASST. 1/2W RESISTORS short leads. 1.00
- \$15 - "JACKPOT" TELEVISION PARTS. \$1
- 15 - ASST. ROTARY SWITCHES \$15 worth. \$1
- 40 - ASST. PRECISION RESISTORS best sizes. \$1
- 100 - ASST. 1/2 WATT RESISTORS some 50c. \$1
- 70 - ASSORTED 1 WATT RESISTORS some 50c. \$1
- 35 - ASSORTED 2 WATT RESISTORS some 50c. \$1
- 50 - ASST. TUBULAR CONDENSERS. \$1
- 50 - STRIPS ASST. SPAGHETTI best sizes. \$1
- 100' - TWIN LEAD-IN WIRE 300Ω heavy duty. \$1
- 50' - FLAT 4-CONDUCT. WIRE many purposes. \$1
- 25' - INSULATED SHIELDED WIRE. \$1
- 20 - ASST. TV KNOBS, ESCUTCHEONS, Etc. \$1
- 100 - TV ESCUTCHEON RETAINING SPRINGS. \$1
- 100' - FINEST NYLON DIAL CORD best size. \$1
- 200 - SELF TAPPING SCREWS #8x1/2". \$1
- 35 - ASST. RADIO KNOBS screw and push-on. \$1
- 25 - ASSORTED CLOCK RADIO KNOBS. \$1
- 50 - ASST. SOCKETS octal, novel and miniature. \$1
- 100 - ASST. MICA CONDENSERS some in 50c. \$1
- 100 - ASST. CERAMIC CONDENSERS. \$1
- 10 - ASST. VOLUME CONTROLS less switch. \$1
- 5 - ASST. VOLUME CONTROLS with switch. \$1
- 50 - ASST. TERMINAL STRIPS 1, 2, 3, 4 lug. \$1
- 10 - ASST. RADIO ELECTRO. CONDENSERS. \$1
- 5 - ASST. TV ELECTROLYTIC CONDENSERS. \$1
- 25 - ASST. MICA TRIMMER CONDENSERS. \$1
- 2 - ELECTROLYTIC COND. 10/40-450v. \$1
- 3 - ELECTROLYTIC CONDENSERS 80-450v. \$1
- 35 - MICA COND. 20-100 mfm & 15-270 mfm. \$1
- 35 - MICA COND. 20-470 mfm & 15-680 mfm. \$1
- 35 - MICA COND. 20-820 mfm & 15-1000 mfm. \$1
- 35 - CERAMIC COND. 20-5 mfm & 15-10 mfm. \$1
- 35 - CERAMIC COND. 20-25 mfm & 15-47 mfm. \$1
- 35 - CERAMIC COND. 20-56 mfm & 15-82 mfm. \$1
- 35 - CERAMIC COND. 20-100 mfm & 15-150 mfm. \$1
- 35 - CERAMIC COND. 20-270 mfm & 15-470 mfm. \$1
- 35 - CERAMIC COND. 20-1000 mfm & 15-1510 mfm. \$1
- 35 - CERAMIC COND. 20-2000 mfm & 15-5000 mfm. \$1
- 12 - RADIO OSCILLATOR COILS 450 \$1
- 3 - 1/2 MEG VOLUME CONTROLS with switch. \$1
- 15 - ASST. TV COILS sync, peaking, width, etc. \$1
- 3 - TV ALIGNMENT TOOLS assortment #1. \$1
- 3 - TV ALIGNMENT TOOLS assortment #2. \$1
- 3 - TV ALIGNMENT TOOLS assortment #3. \$1
- 3 - TV ALIGNMENT TOOLS assortment #4. \$1
- 3 - TV ALIGNMENT TOOLS assortment #5. \$1

BROOKS RADIO & TV CORP., 84 Vesey St., New York 7, N.Y.

more

...so much more for everyone...for every application...in the complete line of Stanton Stereo Fluxvalves*.

Here is responsible performance...in four superb models...for all who can hear the difference. From a gentle pianissimo to a resounding crescendo—every movement of the stylus reflects a quality touch possessed only by the Stereo Fluxvalve.



STANTON Calibration Standard: Model 381—An ultra-linear professional pickup for recording, channel calibration, radio stations and record evaluation by engineers and critics...from \$48.00

Collectors Series: Model 380—A precision pickup for the discriminating record collector...from \$29.85

Pro-Standard Series: MK II—A professional pickup outstanding for quality control...from \$24.00

StereoPlayer Series: Stereo 90—A fine quality stereo magnetic pickup for the audiophile...\$16.95

LISTEN!...and you will agree Pickering has more for the best of everything in record reproduction—mono or stereo. **More Output—More Channel Separation—More in Response—More in Record Life!** In short...more to enjoy...because, there's more quality for more listening pleasure.

FOR THOSE WHO CAN HEAR THE DIFFERENCE

 PICKERING & CO., INC., PLAINVIEW, NEW YORK
STEREO FLUXVALVE, STEREOPLAYER, COLLECTORS SERIES, PRO-STANDARD SERIES, CALIBRATION STANDARD ARE TRADEMARKS USED TO DENOTE THE QUALITY OF PICKERING COMPANY, INC. PRODUCTS.

LISTEN!—Ask for a Stereo FLUXVALVE demonstration at your Hi-Fi Dealer today!
 Send for Pickering Tech-Specs—a handy guide for planning a stereo high fidelity system...address Dept. R-71
 * U.S. Patent No. 2,917,590

TARZIAN Offers 48-Hour, Direct Factory Service on Tuner Repairs

only \$8.50

Price Effective Jan. 1, 1960

That's right. Net, \$8.50 per unit and \$15 for UV combinations, including ALL replacement parts. 90-day warranty against defective workmanship and parts failure. Tuners repaired on approved, open accounts. Replacements offered at these prices* on tuners not repairable:

- VHF 12 position tuner \$22.00
- VHF 13 or 16 position 23.00
- VHF/UHF combination 25.00
- UHF only 15.50

*Subject to change

 Tarzian-made tuners are easily identified by this stamping on the unit. When inquiring about service or replacements for other than Tarzian-made tuners, always give tube complement . . . shaft length . . . filament voltage . . . series or shunt heater . . . IF frequency, chassis identification and allow a little more time for service. Use this address for fast, 48-hour service:

SARKES TARZIAN, Inc.
 Att.: Service Mgr., Tuner Division
 East Hillside Drive
 Bloomington, Indiana

FREE

Full Year's Subscription to **RADIO SHACK'S Sensational ELECTRONICS CATALOGS**

Send coupon today! See world's largest and best line of electronic equipment! Invaluable to pros, exciting for hobbyists. Over 100,000 items—stereo, hi-fi, ham radio, tapes — at money-saving prices. 15-day home trial on any item. Satisfaction Guaranteed.

TYPICAL RADIO SHACK VALUE!
 "Realistic" 2-speed Tape Recorder \$49.95

Radio Shack dual-track portable! Wt. only 17 lbs. Has separate record, playback, erase heads. Mike, 5" reel.

MAIL COUPON NOW
 Radio Shack Corp., 730 Commonwealth Ave. Boston 17, Mass. Dept. 60G10
 Without further request, send latest catalog plus every issue for year—all FREE.
 Name _____
 Address _____
 Post Office or City _____ Zone _____ State _____



SOLDERING-TOOL MAINTENANCE

In addition to keeping your soldering gun's tip tinned, check to see if the screws or nuts that hold the tip in place are tight. Loose screws or nuts mean a poor electrical contact and reduced tip temperature and soldering efficiency. If you work with an iron, do you ever take time out to unscrew the tip or loosen the setscrew (if yours has one) and remove the tip? If this isn't done occasionally, the tip may become frozen in place and very difficult to remove. Should that happen, soak the tip in ammonia to loosen it.—Charles A. Cunningham

BRIGHTEN METER SCALES

Meter and instrument scales ultimately get dull and dirty-looking. Cleaning is difficult because of soft easily scratched surfaces, and the printing or lithographing. We have found only one satisfactory way of cleaning meter faces, but it really does a good job. Obtain some drawing cleaning powder from a stationery store or one that deals in engineering drawing supplies. Then sprinkle the meter face with the powder and rub with a rotary motion using a soft cloth or piece of paper toweling. A second application may be necessary. The result will be a beautifully and uniformly clean instrument dial.—Edwin Bohr



der from a stationery store or one that deals in engineering drawing supplies. Then sprinkle the meter face with the powder and rub with a rotary motion using a soft cloth or piece of paper toweling. A second application may be necessary.

The result will be a beautifully and uniformly clean instrument dial.—Edwin Bohr

DUAL CONTROL ASSEMBLY


When replacing dual controls in a TV set with a unit assembled from a control kit, use a little lubricant between extension shafts before fastening the sections together. Some controls have a tendency to be rough when first put together. The lubricant corrects the condition.

TRY THIS ONE (Continued)

A moment's consideration before the control is assembled will prevent the time-consuming job of taking it apart again, or turning out a job with that scratchy feeling.—George D. Philpott

PHONE-TIP ADAPTER

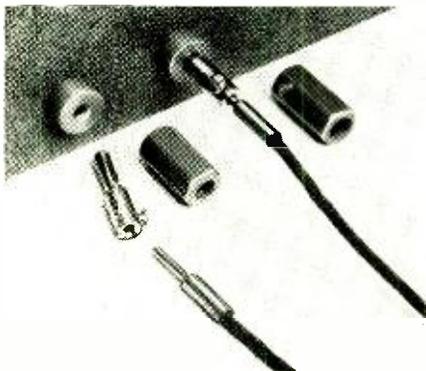
In electronic servicing and experimental work, we sometimes want to plug phone tips into banana jacks. To do this quickly and easily, some sort of adapter is needed. A simple solution



to the problem is to buy a couple of ICA solderless banana plugs and use them as adapters, as shown in the photo. You will find the openings on the back ends of the solderless banana plugs just the right size for phone tips which are locked in place with the setscrews on the banana plugs.—Art Trauffer

STAY-PUT TROUBLE LIGHT

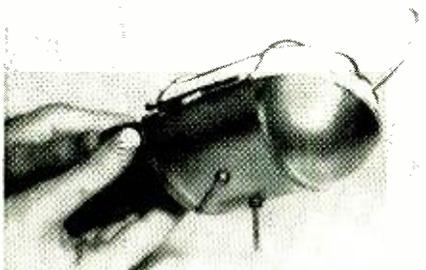
If you use a trouble light like the one shown, you know just how difficult it is to make it stay put on a flat sur-



face. Keep the light from rolling out of position by adding a couple legs. Drill two holes through the reflector and insert a 1/4-inch long machine screw in each as shown.—John A. Comstock

SOLDERING-IRON HOLDER

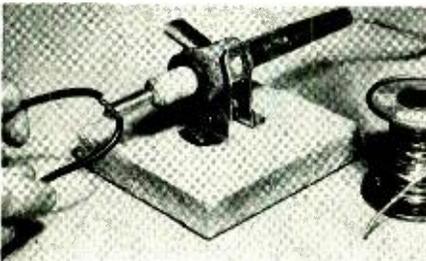When you need both hands free for a soldering job, this simple holder is good to have around. It consists of a




spring type broom clip fastened to a block of wood. A hole drilled in the base lets you hang the whole works on a nail driven into the shop wall, when the holder isn't in use.—John C. Alexander

TENT FOR LIGHTNING ARRESTER

The moisture that collects on a TV's lightning arrester during wet weather tends to short out the TV signal and impair reception. When it is mounted on the outside of a window sill or any other place where it is exposed to the weather, it's a good idea to tack a transparent plastic tent over it. Cut the tent from an old plastic bag or some other plastic material.—Clyde A. Compton

FUSE HOLDER FOR SPARES

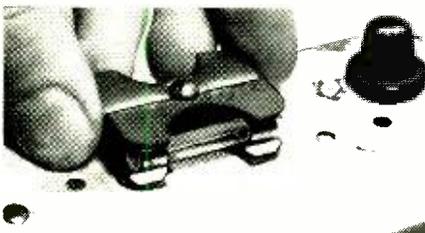A snap-on fuse holder, the kind used when replacing a pigtail fuse with an



ordinary tubular fuse, makes a good holder for a couple of spare fuses. Simply cement the holder to a vacant spot on the chassis and snap a couple of spares into it.—Alex Carlton

SHOCK-ABSORBING RIDE

When you have to deliver a TV to a customer over a rough country road, rest the set on a partly pumped-up inner tube placed on the floor in the back of your service truck. The inner tube will absorb all of those rough jolts that could otherwise jar something loose and cause trouble. Carry one of these TV cushions and you can be sure the set will still be in operating condition when you reach your destination. For console radio-TV-record player combinations, use two inner tubes.—Charles Abraham

Answer to "Roundword Puzzle," page 31

M	E	G	I	L	B	E	R	T	R	A	N
E	M	E	N	T	E	T	R	O	D	E	S
L	N	O	V	I	C	E	C	O	S	L	I
E	O	T	E	R	E	O	H	M	C	E	S
R	R	S	A	Y	L	O	O	H	I	C	T
E	T	C	L	A	N	I	P	D	L	T	O
P	A	N	E	M	M	U	L	S	L	R	R
M	R	O	R	R	E	G	U	C	O	O	E
A	Y	I	O	T	A	L	L	I	S	S	G
O	H	S	S	I	M	E	P	O	C	T	E
R	T	L	O	V	W	W	C	I	T	A	N
C	I	M	F	B	N	O	I	T	A	R	E



PRECISION INSTRUMENTS AND KITS

MODEL 221 VTM — large 4 1/2" meter with "can't-burn-out" circuit. Zero center for TV FM discriminator alignment. AC DC Vols: 0-5, 10, 100, 500, 1,000 (Up to 30,000 v, with HVP probe, up to 250 mc with PRF probe, and peak-to-peak with PTP probe). OHMS: 0-2 ohm to 1,000 megs. DB -30 to +55. Input R: 25 megs. 1% precision multipliers. Double triode bridge circuit. Three-color etched panel; steel case.

MODEL 221 VTM

Wired Ready to Use **\$39.95**

KIT - \$25.95

Leatherette Carrying Case - \$3.95

Almo RADIO CO.

Stores Throughout the Entire Delaware Valley Area

913 ARCH ST., PHILADELPHIA, PA.

ATLANTIC CITY
4401 VENTNOR AVE.

BUR HOLME
5801 RISING SUN AVE.

CAMDEN, N. J.
1133 HADDON AVE.

NORRISTOWN, PA.
530 MARKLEY ST.

TRENTON, N. J.
201 CALHOUN ST.

WILMINGTON, DEL.
1122 FRENCH ST.

VINELAND, N. J.
219 LANDIS AVE.

SALISBURY, MD.
317 PARK HEIGHTS AVE.

FREE



Fill in coupon for a FREE One Year Subscription to OLSON RADIO'S Fantastic Bargain Packed Catalog—Unheard of LOW, LOW, WHOLESALe PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and thousands of other Electronic Bargains.

NAME _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

If you have a friend interested in electronics send his name and address for a FREE subscription also.

OLSON RADIO CORPORATION

709 S. Forge St., Akron 8, Ohio

"TAB" Tubes Tested, Inspected, Boxed
Six Months Guarantee!! No Rejects!
NEW & Used Gov't & Mfgs. Surplus!

Orders \$10 or more, Receiving types only p.p.d. 48 states

0A2	.80	6B16	.60	12AT6	.50	18X1	1.00
0B2	.65	6B17	.60	12AV7	.84	17Z6	1.10
0C3	.69	6B17	1.25	12AU6	.69	4-65A	16.00
0D3	.35	6B16	.98	12AU7	.69	2D21	2/81
0Z06	.59	6B17	1.19	12AX7	.79	5Z23	3.95
1A7	.89	6B27	1.25	12BA6	.65	717A	5/81
1B3	.78	6C4	.43	12BA7	.99	4-125	25.00
1R5	.78	6C5	.49	12BD6	.59	4-250	35.00
1S4	.78	6C6	.84	12C6	.69	4E27	7.00
1T4	.78	6C6	1.49	12BF6	.50	4PR60	29.50

Sand Box for Catalog

1U4	3/51	6H6	3/81	12BH7	.99	4X150G	\$15
1U5	.73	6J5	.53	12BY7	.98	4X250	35.00
1X2A	.68	6J6	.48	12BZ7	.99	4X500	38.00
3Q5	.68	6K6	.59	12C6	1.45	5894	4.98
3Q5	.89	6K7	.64	12SA7	.94	58P4	4.98
3S4	.68	6L6	1.19	12SG7	.89	35T	4.00
3V4	.83	6SA	.59	12SH7	.89	100T	7.00
5R4	.98	658	.99	12SJ7	.73	318A	5/81
5U4	.59	6SA7	.69	12SK7	.94	388A	3/81
5V4	.89	6587	1.19	12SQ7	.84	4168	4.00

Wanted Surplus Literature

5Y3	.59	65C7	.80	198G6	2.15	450T	42.00
6B4	.79	65G7	.79	1978	1.16	807	1.00
6AC7	.79	65H7	.69	25BQ6	1.39	809	3.00
6AC7	.89	65J7	.89	25C7	.99	811	3.49
6AH6	.99	65K7	.72	25W4	.77	812	3.00
6AK5	.99	65L7	.89	25Z5	.63	813	3.00
6AL5	2/81	65M7	2/78	25Z6	.73	814	3.15
6AS7	.63	65Q7	.71	EL34	3.49	815	2.75
6A5	3.00	65R7	.79	EL37	2.49	826	.59
6AT6	.49	678	.80	75	.63	829B	8.00

Wanted 50¢ Tubes! Top \$ \$ Paid

6AU4	1.10	6U8	.98	35W4	.49	832A	7.00
6AU5	1.19	6V6GT	.70	35Y4	.69	866A	2.75
6AU8	.69	6W4	.74	50	.63	8781	3.00
6AX4	1.79	6W6	.88	50A5	.69	8146	4.00
6BA6	.59	6X4	2/81	50B5	.69	5879	.98
6BA7	1.49	6Y6	.97	50C5	.69	5879	2.79
6BD6	.69	6Y6	.97	50L6	.69	6550	3.00
6BE6	.59	7N7	.89	KT66	3.29	5654	1.00
6BG6	1.29	12AL5	.59	75	.63	829	12.00
6BH6	.2	12AQ5	.80	80	.59	7193	10/81

TUBES WANTED! WE BUY! SELL & TRADE!

NEW SILICON 750MA* DIODES TOP HATS

GENERAL PURPOSE SPECIAL 2 FOR \$1	400 PIV at 250 MA 25 FOR \$10		
rms/piv 35/50	rms/piv 70/100	rms/piv 140/200	rms/piv 210/300
.35c	.35c	.55c	.55c
rms/piv 280/400	rms/piv 350/500	rms/piv 420/600	rms/piv 490/700
.65c	\$1.00	\$1.26	\$1.35
rms/piv 560/800	rms/piv 630/900	rms/piv 700/1000	rms/piv 770/1100
\$1.50	\$1.70	\$2.00	\$2.50

* CAPACITOR INPUT DERATE 20% \$5 or more this item see ppg P.P./U.S.

***NEW "TEKSEL" SELENIUM RECTIFIERS**

FULL WAVE BRIDGE RECTIFIERS. ONLY YEAR GTD!

AMP.	18VAC	31VAC	44VAC
CONT.	14VDC	28VDC	56VDC
1AMP	\$ 1.30	\$ 2.00	\$ 4.90
2AMP	2.15	3.00	6.25
3AMP	2.90	4.00	8.50
6AMP	4.15	8.00	18.75
10AMP	6.10	12.15	26.30

Write for Complete Rectifier Catalog

NEW Selenium Radio & TV Rectifiers! GTD.

65Ma 45c. @ 6 for \$2; 100Ma 45c @ 12 \$5;
250Ma 65c. @ 10 \$6; 300Ma 88c. @ 10 \$8;
500Ma \$1. @ 10 \$8. 25 \$18
Orders this Item \$10 or More, Postpaid 48 States!

NEW POWER CONVERTER

12VDC to 500VDC up to 200MA 100 Watts; Tap at 250VDC Type C1250E \$35. Hi efficiency, low ripple, low standby current - Silicon rectifiers! Toroidal Hi-Eff! Mag-metal tape wound transformer. Tap-out & short circuit proof, small in size, Quiet! Light weight! 4 1/2 lbs. built, ready to go. Conservatively Rated. Delco Transistors, Heavy Copper-Heatsink. 12VDC to 250VDC up to 100MA Type C1225A \$30.

"TAB" KITS! "TAB" THE BEST KITS! "TAB"

- All Kits Contain Most Popular Tubes & Sizes
- | | |
|----------------------------|----------------------------|
| Kit 2 End Parallel Res. | Kit 5 Submini Tubes |
| Kit 35 Precision Resistors | Kit 40 Standoff Insulators |
| Kit 10 Switches | Kit 35 Power Resistors |
| Kit 75 Resistors 1/2 1/2W | Kit 75 Mica Condensers |
| Kit 150 Carbon Resistors | Kit 5 Crystal Diodes |
| Kit 25 Panel Lamps | Kit 100 Fuses, Assorted |
| Kit 12 Electrolytic Cond's | Kit 100 Ceramic Cond's |
| Kit 56 Tube Sockets | Kit 10 6-1/2" Tubes |
| Kit 65 Tubular Cond's | Kit 5 FT243 Xtal Holders |
| Kit 500 Lugs & Eyelets | Kit 8 Silicon Diodes |
| Kit 10 Bathub Oil Cond's | Kit 5 Microswitches |
| Kit 5 lbs. Surprise Pckg. | Kit 4 Asst Rectifiers |
| Kit 10 Xmttr Mica Cond's | Kit 2 PNP Transistors |
| Kit 3 Phone/Patch Xfms | Kit 4x50 Ft Hookup Wire |
| Kit 3 Searchlights | Kit 2 Vender Counters |
| Kit Circular Slide Rule | Kit 2-Computer Toroids |
| Kit 12 Algrt Clip Asst'd. | Kit High Gain XTAL Mike |

BUY 10 KITS - GET ONE FREE! EACH KIT 99¢

TRANSISTORS & ACCESSORIES

2N111	\$3.	2N442	\$4.50	2N277	\$4.	2N278	\$5.
2N125	\$1.39	2N176	\$1.80	2N177	\$1.	2N178	\$1.75
2N175	\$2.47	2N150	\$2.55	2N120	\$2.00	2N270	\$9.95
2N274	\$1.25	2N108	\$8.80	2N314	\$1.20	2N578	\$1.80
2N579	\$2.20	2N581	\$1.25	2N582	\$2.10	2N174	\$8.50
2N174	\$8.50	2N173	\$6.50				

DIAMOND BASE MICA MOUNTING KIT \$.30
DELCO ROUND BASE MICA MOUNTING KIT \$.30
DELCO POWER HEAT SINK WITH FMS \$.75

"VACDAC" SILICON TUBE REPLACEMENTS

WITH BUILT IN RF. SURGE & SERIES BALANCING PROTECTION

TYPE	VRMS/PIV	AMPS.	PRICE
ST866	5000/10400	0.3	\$20.00
ST816	1000/7000	0.6	\$16.00
ST584	1900/2800	0.5	\$15.00
ST504	1120/1600	0.6	\$ 8.00

SNOOPERSCOPE TUBE 2" \$5 @ .2 for \$9
4X150 HiTemp. CHIMNEY EZ Mtg. 69c. 2 for \$1
HC21 NEW ORIG. SHORPS RECALIB. RECORDING
TIONED OVSEAS PCRD NEW CALIBRATION BOOK
MINT CNDTN! \$1.10
NEW BULBS 26-39 to 3R-9 M's. TRANSIEVER WITH
6-12V SUPPLY & SPARES OVSEAS PCKO \$9.99
AN-ARRR RCVH GOOD COND less tubes. \$1.59
SEND FOR NEW CATALOG 25c.
CO-AX METERS IN ROUND OIA \$5 @ .5 for \$2
CO-AX CNDTRS PL250A. 45c @ .5 for \$2
HYT 14T 115V/60CY SELSYNS TWO for \$5
TSB44/WE/USN SCOPE 1.7N \$49.00

"TAB" TERMS: Money Back Guarantee! Order by 15th year. \$2 min. order F.O.B. N.Y.C. Add shpg charges or for C.O.D. 25% Dep. Prices shown subject to change.
111-KJ LIBERTY ST., N. Y. 6, N. Y.
Send 25¢ PHONE: RECTOR 2-6245 for Catalog

BUSINESS and PEOPLE

Blonder-Tongue Labs., Inc., Newark, N. J., launched the biggest advertising program in its history in support of its new 10th-Anniversary line of TV reception improving products. A special-ity designed symbol identifies products in the line and space ads will be run in trade and special interest magazines, including RADIO-ELECTRONICS. A consumer program supports the company's FM and FM-AM radio line.




Jensen Industries, Forest Park, Ill., is using a series of colorful 12 x 10-inch

United Catalog Publishers, Inc., Hempstead, N. Y., celebrates the 25th anniversary of *The Radio-Electronic*




Master this year. Arthur I. Rabb, general manager of the company, sets up a giant silver replica of *The Master* in the company's reception room as Samuel Roth, president, looks on.

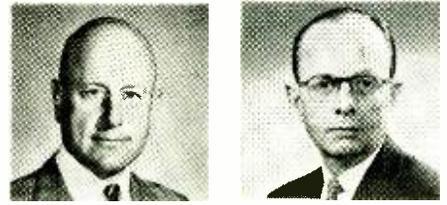Charles F. Adams (left) was elected chairman of the board of Raytheon Co., Waltham, Mass. Richard E. Krafve succeeds him as president. Krafve, former



vice president of Ford Motor Co., joined Raytheon in the spring of 1959 as group vice president, commercial. In September, he was elected executive vice president and a director.

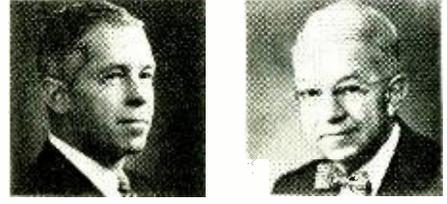G. Barron Mallory, administrative vice president of P. R. Mallory & Co., Inc., Indianapolis, Ind., was elected



president succeeding Joseph E. Cain. Philip R. Mallory was re-elected chairman of the Board of Directors. Cain was elected co-chairman of the Board of Directors and chairman of the Executive Committee, succeeding J. F. Riely who remains a member of the Executive Committee together with C. Harvey Bradley and G. B. Mallory.

Oden F. Jester joined Merit Coil & Transformer Corp., Hollywood, Fla., as general sales manager. He has been a sales executive in the electronic industry for many years, including such posts as radio sales manager of Stewart-Warner Corp., vice president and general sales manager of the original Utah Radio Products Co., and distributor sales manager of Standard Coil Products Co.

J. B. Farese was elected division vice

counter cards to introduce its new Perfectone phonograph needles in sapphire and diamond tips.

Vaco Products Co., Chicago, Ill., is offering electronic parts distributors a Walking Display attaché case for out-



side salesmen. It contains a series of speciality tools for electronic technicians.

Edward Crowley joined Jensen Industries, Forest Park, Ill., as assistant to the president. Previously he was executive vice president and director of Fidelitone.



BUSINESS AND PEOPLE (Continued)

president, Entertainment Tube Products Dept., for the RCA Electron Tube Div., Harrison, N. J., and C. E. Burnett, division vice president, Industrial Tube Products Dept., Lancaster, Pa. Martin F. Bennett was named vice president, distributor and commercial relations; Carl V. Bradford, staff vice president, Eastern distributor and commercial relations at Cherry Hill, N. J., Harold A. Renholm, staff vice president, Central distributor and commercial relations, Chicago; Harold R. Maag, staff vice president, Western distributor and commercial relations, Hollywood, Calif.

Theodore Lindenberg is now director of engineering for Astatic Corp., Conneaut, Ohio. He comes to the company from Pickering Co., Plainview, L. I., N. Y., where he served as chief engineer.



David B. Tolins was appointed manager of the newly consolidated advertising, sales promotion and merchandising activities of the Semiconductor Div. of Sylvania Electric Products, Inc., Woburn, Mass. He had been division advertising and sales manager.



Don Kirkendall was promoted to advertising manager of Electro-Voice, Inc., Buchanan, Mich., from assistant advertising manager.



Ira Molay (left), sales engineer for CBS Electronics Div., Danvers, Mass.,




was promoted to product manager, audio components. Kenneth A. Waldron, manager of Government sales, is now marketing manager for government and industrial products.

Stuart D. Cowan was elected vice president, commercial marketing and international services, of Raytheon Co. Waltham, Mass. He was formerly director of commercial marketing services. John E. Gagnon, Robert L. McCormack and Dr. Martin Schilling were also elected vice presidents of industrial relations, industrial components, and Government programs and planning, respectively. Gagnon had been director of employee relations; McCormack, general manager of the Industrial Components Div., and Dr. Schilling, assistant for program planning on the corporate staff.

END

NOW...enjoy your HI-FI OUTDOORS

PATIO, GARDEN, TERRACE, PORCH

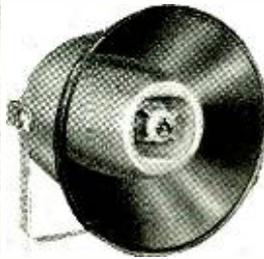

with the new WT-6

ATLAS HI-FI COAX-PROJECTOR

all-weather construction... install it, forget it!... or take it with you wherever you listen.

True HIGH FIDELITY TWO-WAY system — not just a "compromise" of two horns coupled to a single diaphragm. The WT-6 comprises a weather proof cone type driver (with 6-inch throat) coupled to its individual woofer horn; a separate pressure-type driver loaded to its separate tweeter horn. The built-in crossover electronic filter supplements the electro-mechanical frequency-limiting characteristics of the 2 individual reproducers — providing for smooth frequency division as each speaker functions within its engineered range of frequencies.

All-weather... high efficiency... compact... for all indoor and outdoor uses... universally adjustable "U"-type rugged steel mounting... finished in high temperature baked modern beige enamel.

POWER RATING 15 watts continuous **net**
 FREQ. RESP. 140-15,000 cps **\$34.50**
 IMPEDANCE 8 ohms. DISPERSION 120°
 DIMENSIONS bell opening 15", overall depth 12"

See the WT-6 at your local distributor. Send for catalog RE-7-

ATLAS SOUND CORP.
 1449 39th St., Brooklyn 18, N. Y.



all new edition

up-to-date component prices

PLUS

the quick easy way to figure service charges

EQUALS



Pure Riee's

OFFICIAL PRICING DIGEST

VOL. 4, NO. 1



Flat rate and hourly service charges, based on and showing regional and national averages, plus up-to-date list or resale prices on over 63,000 components. Arranged alphabetically by manufacturers and products, numerically by part number. Compact, convenient size fits in tube caddy, toolbox or pocket. \$2.50 per copy from your distributor.

ELECTRONIC PUBLISHING COMPANY, INC.
 180 N. WACKER DRIVE, CHICAGO 8, ILL.



TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.

Get practical training in New Shop-Labs of Coyne. Prepare for a better job and a successful future in a top opportunity field. Advanced education or previous experience not needed. Employment service to graduates.

Enroll NOW—Pay Later

Finance Plan and Easy Payment Plan. Also Part Time Employment help for students.

FREE BOOK Clip coupon or write to address below for Free Illustrated Book. "Guide to Careers"—Describes all training offered. No obligation and No Salesman Will Call. Act NOW.

B. W. Cooke, Jr., President

COYNE ELECTRICAL SCHOOL
 CHARTERED NOT FOR PROFIT
 Established 1899
 1501 W. Congress Pkwy., Chicago, Dept. 80-5C

COYNE Electrical School
 1501 W. Congress Pkwy., Chicago 7, Ill.
 Dept. 80-5C

Send FREE book "Guide to Careers" and details of all training you offer. However, I am especially interested in:

ELECTRICITY TELEVISION BOTH FIELDS

NAME.....

ADDRESS.....

CITY.....STATE.....

ALL THE CONVENIENCES OF HOME WILL TRAVEL WITH YOU WHEREVER YOU GO

NOW! FROM ARKAY

ARKAY 12 VOLT TRANSISTOR INVERTER



Model 2-120W
KIT

\$29.95

Factory wired \$35.95

use these and more from car or boat battery

Build it in a few short hours — install it in minutes! Transistorized circuit adapts any 12 Volt battery to 115 Volt AC.

- Portable TV
- Electric Razor
- Communications Receiver
- Amplifier
- Table Radio

ONLY ARKAY
Golden '60 components give a **LIFETIME GUARANTEE!**



FM TUNER KIT

\$39.95

Factory wired \$64.95

All delicate adjustments have been done at the factory on the completely pre-wired, prealigned front end. All the worry is removed — only the fun is left! Professional quality FM Tuner with AFC for drift-free reception, precision tuning indicator, 3 double-tuned IF stages. **FM-7 KIT**

arkay
88-06 Van Wyck Expressway Richmond Hill 18, N.Y.

Purchasing A HI-FI SYSTEM? NOW YOU CAN CHARGE IT!

If you are an International credit card holder. Up to 10 months to pay. No down payment.

Send Us Your List Of Components For A Package Quotation

WE WON'T BE UNDERSOLD!

All merchandise is brand new, factory fresh & guaranteed.

AIREX RADIO CORPORATION

64-RE Carlandt St., N.Y. 7, CO 7-2137

- Altec Lansing
- Electrovoice
- Jensen
- Hartley • Stephens
- University
- Acoustic Research
- Janszen
- Wharfedale
- Karlson Cabinets
- Viking
- Concertone
- Bell • G.E.
- Weathers
- Harman-Kardon
- Eico • Pilot
- Acrosound
- Quad Ampl & Spkrs
- Dual Changer
- Bogen • Leak
- Dynakit • Fisher
- H. H. Scott
- Uher Recorder
- Thorens • Sherwood
- (Fair Traded)
- Pentron • Roberts
- Ampex • DeWald
- Sony
- Challenger
- Wollensak
- Garrard
- Miracord
- Gisner-Steers
- Rek-O-Kut
- Components
- Norelco
- Fairchild
- Pickering • Gray
- Audio Tape
- Magnecord
- Full Line of
- Wellcor Cabinets

new LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

VOLTAGE REGULATOR of the tubeless magnetic-amplifier type supplies 10 to 25 amperes at 130 volts dc (or less) for field winding of ac generators. Input is taken from generator's output, making generator self-excited. *Bulletin 3300* describes this magnetic-amplifier regulator-exciter. — **Fidelity Instrument Corp.**, 1000 E. Boundary Ave., York, Pa.

SERVICING MANUAL that shows diagrams of all of the important 1960 TV sets is described in a 4-page folder. Also covered are radio servicing manuals and a TV service course. — **Supreme Publications**, 1760 Balsam Rd., Highland Park, Ill.

RECORDING SPECTROPHOTOMETER for measuring the color of materials is described in *Bulletin GEZ-3031*. Operating principles, accessories and specifications are given in 12-page booklet. — **General Electric Co.**, Schenectady 5, N. Y.

POWER SUPPLIES, transistor-type, are described in a 4-page folder. The company's ST series covers the range from 0 to 18 volts dc at up to 6 amps to 0 to 100 volts at up to 10 amps. — **Mid-Eastern Electronics, Inc.**, 32 Commerce St., Springfield, N. J.

MINIATURE LAMPS and who makes them are listed in *Miniature Lamp Data*. Drawings of bulb shapes, bases and filament styles are also shown. Voltage, current and life information is given in tabular form. — **Chicago Miniature Lamp Works**, 1500 N. Ogden Ave., Chicago 10, Ill.

COMPONENTS to help design engineers plan and package circuitry are listed in *Quick Order Guide*. Racks, sockets, indicators and hardware are among the components listed. — **Alden Products Co.**, Dept. QOG-96, 117 North Main St., Brocton 64, Mass.

AUDIO FILTERS AND TOROIDS are listed in a 4-page catalog. A new standard line of encapsulated toroids is described and illustrated. Typical performance curves are shown. Information is given on how to specify style and types of leads when ordering. — **Barker & Williamson, Inc.**, Canal St. and Beaver Dam Rd., Bristol, Pa.

PUSHBUTTON SWITCHES are available in single- and double-row assemblies of from 4 to 12 stations. *Bulletin No. 7000* gives detailed specifications,

photographs and dimension drawings. Switches have interlocking action and may be illuminated if desired. — **Donald P. Mossman, Inc.**, Brewster, N. Y.

FUSION-SEALED RESISTORS use tin-oxide film as resistive element and are completely moisture-proof. The film is fused to the surface of a glass rod, then the assembly is encapsulated in glass. Available in 1/8- and 1/4-watt sizes. Request data sheet *CE-2.02* on company letterhead. — **Corning Electronic Components**, Corning Glass Works, Bradford, Pa.

SEMICONDUCTOR HANDBOOK lists units by type (small-signal audio, low-speed switching, high-speed switching, etc.). Parameters of more than 750 semiconductors are given. Also covered are silicon capacitors. — **Radio Shack Corp.**, 730 Commonwealth Ave., Boston 17, Mass.

AMPLIFIERS, splitters and outlet wall plates for TV distribution systems are described in an 8-page catalog. — **Delta Electronics**, Queen Elizabeth Way, Clarkson, Ontario, Canada.

MECHANICAL FILTERS are listed on data sheet *CR-WD-1005*. Case styles are illustrated along with detailed dimensions. Frequency range covered is 250 to 500 kc. Single-sideband filters range from 60 to 455 kc. — **Collins Radio Co.**, Western Div., 2700 W. Olive Ave., Burbank, Calif.

APPLICATION GUIDE gives information on transistor use in chart and graph form. A typical graph shows transistor gain (in a practical circuit) plotted against frequency. — **Philco**, Lansdale Div., Lansdale, Pa.

MULTICOUPLER PERFORMANCE is the title and subject of this 17-page booklet. When feeding several communication receivers from a common antenna, a multicoupler is necessary to prevent mismatches and spurious signals. The problem of selecting the correct multicoupler for a particular system is covered in detail. — **Trak Electronics Co.**, Div. C. G. S. Labs., Inc., 59 Danbury Rd., Wilton, Conn.

SEMICONDUCTOR SUBSTITUTION for the practicing service technician is simplified by *Semiconductor Complement Manual*. It lists radios and audio equipment by brand name and model number, all the transistors, diodes, and rectifiers in them. Next to each semiconductor

the correct Sylvania replacement is listed (if one exists). The more popular European and Japanese makes are among the more than 60 brands of home and auto radios covered.—Sylvania Semiconductor Division, 100 Sylvan Rd., Woburn, Mass. 50c.


CLOSED-CIRCUIT TV equipment (cameras, lenses, monitors, control equipment, housings, and switchers) is described in a 112-page industrial catalog. Photographs of the units mentioned are shown. Write on company letterhead and request *ITV-93059*.—Radio Corp. of America, Closed-Circuit Television Dept., Camden, N. J.

REPLACEMENT NEEDLE chart for wall use is 22 x 24 inches. Shows several hundred common phono needles with drawing of each, grouped by manufacture of cartridge. Also shows model number of needle as indicated by cartridge maker, and list price of replacement.—Clevite Walco, 60 Franklin St., East Orange, N. J.

MICROWAVE WAVEGUIDE data are covered in a 14 x 21-inch wall chart called *Standard Waveguide Data Chart*. It shows military and EIA designation numbers, cutoff frequency, CW power rating, attenuation factors and mechanical dimensions. This chart can save engineers the time they formerly had to spend calculating this data.—Narda Microwave Corp., 118-160 Herriicks Road, Mineola, N. Y.

INDUSTRIAL INSTRUMENTS are described in a 12-page "briefalog" *No. 19-60*. Covered are high- and low-range ohmmeters, insulation testers, frequency meters, tachometers, dielectric testers, etc.—James G. Biddle Co., 1316 Arch St., Philadelphia 7, Pa.

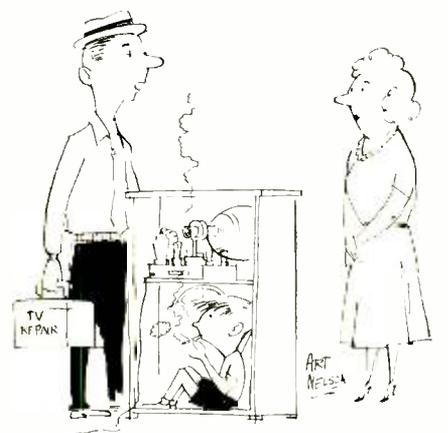ELECTRONIC KITS for use in school science programs are detailed in an illustrated 20-page catalog—*Electronic Equipment Designed for School Systems*. Detailed descriptions of all kits are included, and the age and technical skill needed by the builder are stated.—Arkay International, 88-06 Van Wyck Expressway, Jamaica, N. Y. \$1. END



"I've found out, ma'am, why your set's been smoking lately."

JULY, 1960

will increase their acceptability.
The Editor, RADIO-ELECTRONICS
 154 West 14th St. New York 11, N. Y.

JULY, 1960

LEARN ALL ABOUT THESE VITAL SUBJECTS
 EASILY . . . COMPLETELY . . . ECONOMICALLY

GYROSCOPES

VIDEO TAPE RECORDING

CARRIER TELEPHONY

TRANSISTOR PHYSICS

FOUR NEW RIDER TITLES

BASICS OF GYROSCOPES ('Pictured-Text' Course)

by Carl Machover — 2 Volumes

This book is written primarily for the non-specialist: not for the gyro engineer, but for the student, technician, or engineer who comes in contact with the gyroscope in his studies or work. The text is primarily descriptive and mathematics are kept to a minimum. Only a basic knowledge of algebra and trigonometry is needed for an understanding of the material. The material upon which this book is based has been proven successful in teaching engineers, technicians and technical sales people at one of the nation's leading gyroscope firms. Every effort has been made to keep the book technically accurate, while simplifying all ex-

planation. Much of the material in this book, such as the sections on stable platforms, and error sources has never appeared before in book form. It is up-to-date and some of it has only recently been declassified.

CONTENTS: VOL. I—What a Gyro is . . . How it works . . . Vertical Gyro . . . Vertical Gyro Components . . . Directional Gyro. VOL. II—The Rate Gyro . . . The Integrating Gyro . . . Stable Platforms . . . Inertial Navigation . . . Difficulties of Gyro Construction . . . Other Gyro Applications.

#257, 2 vols., soft cover, \$6.60; #257H, cloth, \$7.75.

BASICS OF CARRIER TELEPHONY ('Pictured-Text' Course)

by David Talley (radio engineer General Telephone Service Corp., div. General Tel. & Electronics)

This 'pictured-text' course clearly presents the fundamental principles of carrier telephone systems. It describes the basic equipment elements making them readily understandable to telephone technicians, maintenance personnel and engineering students. The book also will acquaint telephone and radio engineers and others in the communication fields with the carrier multiplexing technique as applied to microwave circuits.

CONTENTS: The Telephone System; Telephone Carrier Definitions; Wire Transmission; Principles; Telephone Transmission Practices; Carrier System Fundamentals; Modulation and Demodulation Process; Electrical Filters; Carrier System Operation; Carrier Transmission and Signaling Features; Cable Carrier Systems; Carrier Applications to Radio Systems. #258, 1 vol. soft cover, \$4.25; #258-H, cloth, \$5.75.

VIDEO TAPE RECORDING

by Julian Bernstein

Video tape recording has revolutionized the TV broadcasting industry. This book deals with all phases of video tape recording—techniques, equipments, and circuitry. The author has succeeded in providing a book that is most useful for all who have an interest in this growing field. The reader does not require an engineering background to benefit from this book.

CONTENTS: Introduction; Waveshapes and Signals; Electronic Photography; Mechanics of Recording; Electronics of Tape Recording; Video Recording; Servo Systems; The Video System; Color Correction Circuits; Servo Circuits; Video Circuits; Machine and Tape Operations. #254, cloth, \$8.95.

FUNDAMENTALS OF TRANSISTOR PHYSICS

by Irving Gottlieb, P.E.

An extremely thorough analysis of the action in transistors. While circuit operation is secondary, the book will generate a complete understanding of transistor operation in circuits. The book makes the subject crystal clear without depending upon mathematics for explanation.

CONTENTS: Atomic Physics; Electrical Conduction; Transistor Action; Transistor Structure and Materials; Biasing the Transistor; The Three Transistor Amplifier Circuit; Related Semiconductor Devices. #267, RE-7

There are more than 200 Rider titles covering every area of electronics from basic electricity to space age electronics. At your electronic parts distributor, bookstore or write direct:

JOHN F. RIDER PUBLISHER, INC. 116 West 14th Street, New York 11, N. Y.
 Canada: Chas. W. Pointon, Ltd., 56 Racine Rd., Rexdale, Ont.
 Europe & British Isles: Chapman & Hall Ltd., 37 Essex St., London India: Asia Publishing House, Bombay and other cities

ATTENTION . . . Service Technicians' Associations

CLUB MEMBERS • STUDENT GROUPS
 Special subscription rates to **RADIO-ELECTRONICS** are available to associations, clubs, schools, employee groups, etc. For information write—C. Aliquo

ENGINEERING DEGREE IN SCIENCE MATH
 27 or 36 MOS.

Accelerated year-round Program prepares for early employment in fields of Science and Engineering. Regular 4-year program for B.S. Degree completed in 36 months, special engineering degree program in 27. Classes start quarterly June, September, January, March. Quality education. Graduates employed from coast to coast. Government approved for veteran training. Students from 50 states, 40 countries, 20 buildings; dorms, gym, campus. Save time and money. Earn board while studying. Write for catalog and complete information.

1770 E. Washington Blvd., Fort Wayne 2, Indiana
INDIANA TECHNICAL COLLEGE

AT LAST! A home study course covering all phases of electric and electronic organ servicing.
A NEW COURSE An extensive course covering every make of organ—repair, regulating, and troubleshooting.

Electronic ORGAN SERVICING

Your Opportunity To Get Into A New, Rapidly Expanding Field At The Start. Don't Miss It!!

WRITE NOW FOR FREE BOOKLET
NILES BRYANT SCHOOL
 Dept. E., 3731 Stockton Blvd. Sacramento 20, California

NHSC Approved • The Pioneer School
 Established 1898

Industrial Electronics Sound Equip. Serv'g Profess'l Eng. (Elec.)
 Radio-TV Eng'g Electrical Eng'g Electrical Drafting
 Electronic Servicing Electrical Tech. Other _____

Name _____ Age _____
 Address _____
 City _____ State _____

Name _____ Age _____
 Address _____
 City _____ Zone _____ State _____
 I'm eligible for veterans education benefits.
 PE-123



best buy
GERNSBACK
BOOKS



new
BOOKS

JULY SPECIALS

- **RG8A/U Coaxial Cable.** Fresh stock. Latest non-contaminating type of RG8-U. 8 1/2 ft.
- **UG88/U Connectors** modern type BNC connector. Reg. price \$1.99, 60¢.
- **Hubbell Polarized Plugs.** Rated 20 A or 250 V. Order Hubbell "Twist-Lock". 1/2¢ each. Stock # B-207.
- **Ceramic crystal sockets** for modern miniature CR type crystals. 15¢ 80¢. # B-205
- **Silver Plated Buss Strips** for UHF wiring and plate connections. 4 1/2" Length. Width: 3/8". In 1/2" Length. 15¢. Stock # B-212 or .15¢ each. In 7/8" Length. Stock # B-213 or .25¢ each.
- **TS197/U Military Equivalent of Model 80 Sig. Generator.** 2 to 400 Mcs. in 6 bands. \$350.00.
- **SP-600 Hammarlund Super-Pro.** 54 to 54 Mcs. in 6 bands. Lab certified O.K. Reg. \$1200.00. Special \$150.00.
- **Just received new lot of transistorized power supplies.** I.P. Digital VTVM's Model 405AR. New. Write for details.
- **Oil Capacitor Special.** 2 Mfd @ 2,000 VDC \$2.00 (Bracket #200 for 10011)
- **Westinghouse Glass-Enclosed Overload Relay.** Adjustable from 500 Ma. 50 to 2 Amps. Coil: 115 VAC or 60 CPS. Type SC-1. \$4.95 each.
- **Mobile Transmitter.** Uses 5618 crystal oscillator into CBS 5516 amplifier. Modern design. Only 7 lbs. net wt., including built-in 6 V. vibrator pwr. supply. w/ 8 silicon rectifiers. Comp. enclosed in aluminum cabinet. Furnished w/ crystal that doubles near 10 meter band. Requires slight & easy modification for 10 meter operation. Unused w/ tubes \$15.95.
- **Raised Relief Map 28 1/2" x 18 1/2".** Beautiful colors in lifetime plastic. SPECIALLY MADE in World Map @ \$9.95 each (ready for hanging—self framed).
- **Ling Model 2050 TV Xmitr (demonstrator)** 420 to 150 Mc. Write for details.
- **Aero 9 Reed Freq. Meter.** Range: 58 to 62 Cy. 100-140 V. AC 27 Rd. \$11.00.
- **Cramer 15 Second Adjustable Timer.** Oper. on 7.5 VAC 60 CPS. Supplied w/ suitable xfm for 115 VAC use. SP4PT contacts. 10 Amps. Mounts in 3 1/2" Dia. hole. \$8.95.
- **Selen. Rectifier 130 V. RMS 300 Ma. .50¢ RG459/U** Coax cable .04¢ Ft.
- **Minimum order \$5.00. 50¢ service charge for orders under \$5.00.**
- **JUST OUT! NEW SUMMER 1960 GREEN SHEET CATALOG. WRITE FOR YOUR COPY TODAY!**

Walker 5-7000

BARRY ELECTRONICS

Dept. RE-7

CORPORATION

512 BROADWAY, NEW YORK 12, NEW YORK

Please mention
RADIO-ELECTRONICS
when answering advertisements

TAPE RECORDERS

HI-FI COMPONENTS
(SLEEP LEARN KITS)

MERITAPE
Low cost, high quality recording tape in boxes or cans. 1960 CATALOG

UNUSUAL VALUES FREE
1960 CATALOG

DRESSNER, 69-02RE 174 St., Flushing 65, N.Y.

**GRIPS THE SCREW!
DRIVES IT TOO!**

QUICK-WEDGE
SCREW-HOLDING
SCREW DRIVER

2" to 14" blades, 4 bit sizes. Available with shock-proof plastic covered tubing.

Ask For It At Your Dealer

KEDMAN CO., 233 S. 5th W., Salt Lake City, Ut.

NEW BOOKS (Continued)

diagnosis, electrotherapy and electro-surgery. Electronic readers will find the chapter on strip chart recorders and that on ultrasonics especially interesting.—FS

CLASS-D CITIZENS BAND CALLBOOK, 1960. International Crystal Mfg. Co., Inc., Oklahoma City, Okla. 9 x 11 in. \$3.95.

This register is for persons who operate class-D, who intend getting their permit to do so or who merely like to eavesdrop on the band. It gives calls in every district, with names and addresses, and includes a map, explanation of FCC rules, plus data on antennas, tuning and frequency measurement, etc.

An application for a Citizens band permit and the complete Part 19 of the FCC rules form part of the callbook. They will help you get your name in the next callbook.—IQ

PRINCIPLES OF TRANSISTOR CIRCUITS, by S. W. Amos. John F. Rider Publisher, Inc., 116 W. 14 St., New York 11, N. Y. 5 1/2 x 8 1/2 in. 167 pp. \$3.90.

This book is an excellent introduction to the theory and practice of transistors and circuit design. It discusses such factors as gain, power, impedance, stability factor, etc., and practical examples show how to determine them.

The book is suited for students and technicians who know basic algebra. It derives the exact formulas for circuits and their approximate values as used in practice. Small-signal and class-B amplifiers, radios and stabilizing networks receive special attention. Multivibrators, dc converters and the newer transistor types are discussed briefly.

INDUSTRIAL ELECTRONICS AND CONTROL, by Royce Gerald Kloeffer (Second Edition). John Wiley & Sons, Inc., 9 1/4 x 6 in. 540 pp. \$10.

A text for the advanced student, practicing engineer or technician interested in industrial electronics. Expanded and updated, the book covers many aspects of the subject. It starts off with nine chapters on electronic fundamentals, including transistors, electrical conduction in gases, and amplifier and oscillator circuits. The remaining nine chapters illustrate the operation of several types of industrial devices—servomechanisms, high-frequency heating, X-ray applications and computer principles.—LS

SILICON RECTIFIER HANDBOOK, Sarkes-Tarzian, Inc., Semiconductor Div., Bloomington, Ind. 5 1/4 x 8 1/2 in. 62 pp. \$1.

Here is the whole story of silicon rectifiers, from theory to practice. Manufacturing methods, test circuits and filter design are among the subjects. Charts, tables and formulas show how to get optimum results from rectifiers and circuits. The book ends with a list of rectifiers and their characteristics.—IQ

LOW FREQUENCY AMPLIFIER SYSTEMS, 70 pp. \$1.80.
VIDEO AMPLIFIERS, 80 pp. \$1.80.
RF AMPLIFIERS, 96 pp. \$2.40. Edited by

A. Schure. John F. Rider, Publisher Inc., 116 W. 14 St., New York 11, N.Y. 5 1/2 x 8 1/2 in.

These 3 volumes cover the frequency ranges from af through rf to the higher video frequencies. Readers should be familiar with algebra and radio theory. The books discuss design equations and show how to use them. Most of the material is on tube circuits, but two of the books include short chapters on transistors. All three are suitable for students of electronic technology.

TABULATION OF DATA ON RECEIVING TUBES. National Bureau of Standards Handbook 68. US Government Printing Office, Washington 25, D. C. 7 3/4 x 10 1/4 in. 110 pp. \$1.

This handbook makes it easy to locate the receiving tube you need. It lists types with less than 25 watts plate dissipation that are suitable for use at frequencies below 1,000 mc.


A numerical listing gives size and shape, use, manufacturer, as well as plate and filament ratings, gm, capacitance, etc. Also, tubes are listed under headings like double triode, pentode with triode, etc. Large, readable base diagrams appear at the end of the book.—IQ

ABC'S OF HAM RADIO by Howard S. Pyle. Howard W. Sams & Co. Inc., 1720 E. 38 St., Indianapolis, Ind. Bobbs-Merrill Co., 717 5th Ave., New York, N.Y. 5 1/2 x 8 1/2 in. 112 pp. \$1.50.

From this book you can learn all you need to know to become a Novice operator. It tells how to prepare for the exam and how to learn the code. Basic electricity, Q code, location of FCC offices are among the contents.

RADIO AMATEUR LICENSING HANDBOOK (Second Edition), by Jim Kitchin. Radiotelephone Directories of Canada Ltd., 119 W. Pender St., Vancouver 3, B. C., Canada. 5 1/2 x 8 1/2 in. 107 pp. \$2.

This one is for Canadians. It explains licensing and operating rules in Canada and gives typical exam questions. The Q code, time-conversion charts and other useful data are included. Canada has no Novice class and its radio exams are partially oral. Therefore, radio theory is particularly important to prospective hams. This is not a theory book, so the reader should arrange to study techniques from another source.—IQ

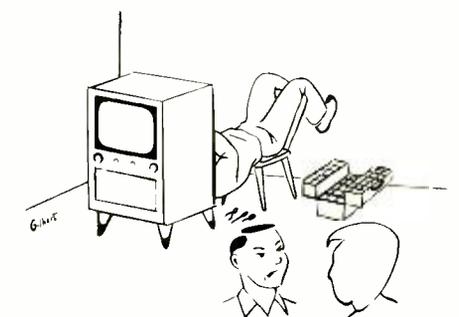

"Joe's been on car radios too long!"

RADIO-ELECTRONICS

the correct Sylvania replacement is listed (if one exists). The more popular European and Japanese makes are among the more than 60 brands of home and auto radios covered.—Sylvania Semiconductor Division, 100 Sylvan Rd., Woburn, Mass. 50c.


CLOSED-CIRCUIT TV equipment (cameras, lenses, monitors, control equipment, housings, and switchers) is described in a 112-page industrial catalog. Photographs of the units mentioned are shown. Write on company letterhead and request *ITT-93059*.—Radio Corp. of America, Closed-Circuit Television Dept., Camden, N. J.

REPLACEMENT NEEDLE chart for wall use is 22 x 24 inches. Shows several hundred common phono needles with drawing of each, grouped by manufacture of cartridge. Also shows model number of needle as indicated by cartridge maker, and list price of replacement.—Clevite Walco, 60 Franklin St., East Orange, N. J.

MICROWAVE WAVEGUIDE data are covered in a 14 x 21-inch wall chart called *Standard Waveguide Data Chart*. It shows military and EIA designation numbers, cutoff frequency, CW power rating, attenuation factors and mechanical dimensions. This chart can save engineers the time they formerly had to spend calculating this data.—Narda Microwave Corp., 118-160 Herricks Road, Mineola, N. Y.

INDUSTRIAL INSTRUMENTS are described in a 12-page "briefalog" *No. 19-60*. Covered are high- and low-range ohmmeters, insulation testers, frequency meters, tachometers, dielectric testers, etc.—James G. Biddle Co., 1316 Arch St., Philadelphia 7, Pa.

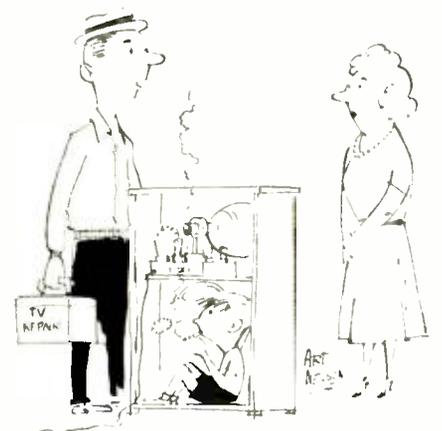ELECTRONIC KITS for use in school science programs are detailed in an illustrated 20-page catalog—*Electronic Equipment Designed for School Systems*. Detailed descriptions of all kits are included, and the age and technical skill needed by the builder are stated.—Arkay International, 88-06 Van Wyck Expressway, Jamaica, N. Y. \$1. END



"I've found out, ma'am, why your set's been smoking lately."

LEARN ALL ABOUT THESE VITAL SUBJECTS
EASILY . . . COMPLETELY . . . ECONOMICALLY

GYROSCOPES VIDEO TAPE RECORDING CARRIER TELEPHONY TRANSISTOR PHYSICS

FOUR NEW RIDER TITLES

BASICS OF GYROSCOPES ('Pictured-Text' Course)

by Carl Machover — 2 Volumes

This book is written primarily for the non-specialist; not for the gyro engineer, but for the student, technician, or engineer who comes in contact with the gyroscope in his studies or work. The text is primarily descriptive and mathematics are kept to a minimum. Only a basic knowledge of algebra and trigonometry is needed for an understanding of the material. The material upon which this book is based has been proven successful in teaching engineers, technicians and technical sales people at one of the nation's leading gyroscope firms. Every effort has been made to keep the book technically accurate, while simplifying all ex-

planation. Much of the material in this book, such as the sections on stable platforms, and error sources has never appeared before in book form. It is up-to-date and some of it has only recently been declassified.

CONTENTS: VOL. I—What a Gyro . . . How it works . . . Vertical Gyro . . . Vertical Gyro Components . . . Directional Gyro. VOL. II—The Rate Gyro . . . The Integrating Gyro . . . Stable Platforms . . . Inert Navigation . . . Difficulties of Gyro Construction . . . Other Gyro Applications.

#257, 2 vols., soft cover, \$6.60; #257H, cloth, \$7.75.

BASICS OF CARRIER TELEPHONY ('Pictured-Text' Course)

by David Talley (radio engineer General Telephone Service Corp., div. General Tel. & Electronics)

This 'pictured-text' course clearly presents the fundamental principles of carrier telephone systems. It describes the basic equipment elements making them readily understandable to telephone technicians, maintenance personnel and engineering students. The book also will acquaint telephone and radio engineers and others in the communication fields with the carrier multiplexing technique as applied to microwave circuits.

CONTENTS: The Telephone System; Telephone Carrier Definitions; Wire Transmission Principles; Telephone Transmission Practices; Carrier System Fundamentals; Modulation and Demodulation Process; Electrical Filters; Carrier System Operation; Carrier Transmission and Signaling Features; Cable Carrier Systems; Carrier Applications to Radio Systems. #258, 1 vol. soft cover, \$4.25; #258-H, cloth, \$5.75.

VIDEO TAPE RECORDING

by Julian Bernstein

Video tape recording has revolutionized the TV broadcasting industry. This book deals with all phases of video tape recording—techniques, equipments, and circuitry. The author has succeeded in providing a book that is most useful for all who have an interest in this growing field. The reader does not require an engineering background to benefit from this book.

CONTENTS: Introduction; Waveforms and Signals; Electronic Photography; Mechanics of Recording; Electronics of Tape Recording; Video Recording; Servo Systems; The Video System; Color Correction Circuits; Servo Circuits; Video Circuits; Machine and Tape Operations. #254, cloth, \$8.95.

FUNDAMENTALS OF TRANSISTOR PHYSICS

by Irving Gottlieb, P.E.

An extremely thorough analysis of the action in transistors. While circuit operation is secondary, the book will generate a complete understanding of transistor operation in circuits. The book makes the subject crystal clear without depending upon mathematics for explanation.

CONTENTS: Atomic Physics; Electrical Conduction; Transistor Action; Transistor Structure and Materials; Biasing the Transistor; The Three Transistor Amplifier Circuits; Related Semiconductor Devices. #267, \$3.90. RE-7

There are more than 200 Rider titles covering every area of electronics from basic electricity to space age electronics. At your electronic parts distributor, bookstore or write direct:

JOHN F. RIDER PUBLISHER, INC. 116 West 14th Street, New York 11, N. Y.
Canada: Chas. W. Pointon, Ltd., 66 Racine Rd., Rexdale, Ont.
Europe & British Isles: Chapman & Hall Ltd., 37 Essex St., London. India: Asia Publishing House, Bombay and other cities.

ATTENTION . . . Service Technicians' Associations

CLUB MEMBERS • STUDENT GROUPS

Special subscription rates to **RADIO-ELECTRONICS** are available to associations, clubs, schools, employee groups, etc. For information write—C. Aliquo

**ENGINEERING DEGREE IN
SCIENCE MATH** 27 or 36 MOS.

Accelerated year-round program prepares for early employment in fields of Science and Engineering. Regular 4-year program for B.S. Degree completed in 36 months. Special engineering degree program in 27. Classes start quarterly June, September, January, March. Quality education. Graduates employed from coast to coast. Government approved for veteran training. Students from 30 states, 40 countries, 20 hundred+ homes, 2 year Campus. Save time and money. Earn board while studying. Write for catalog and complete information.
1770 E. Washington Blvd., Fort Wayne 2, Indiana

INDIANA TECHNICAL COLLEGE

AT LAST! A home study course covering all phases of electric and electronic organ servicing. **A NEW COURSE** An extensive course covering every make of organ—repair, regulating, and troubleshooting.


Electronic ORGAN SERVICING

Your Opportunity To Get Into A New, Rapidly Expanding Field At The Start. Don't Miss It!!

WRITE NOW FOR FREE BOOKLET

NILES BRYANT SCHOOL
Dept. E., 3731 Stockton Blvd.
Sacramento 20, California

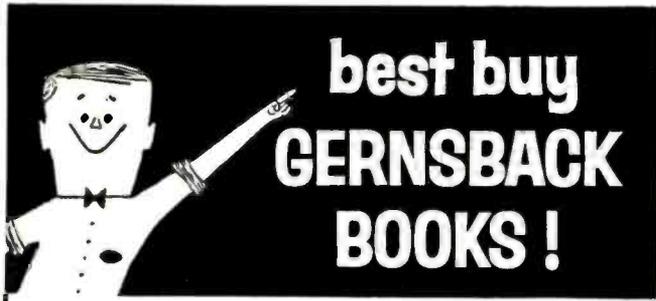NHSC Approved • The Pioneer School
Established 1898



best buy GERNSBACK BOOKS!

There's a Gernsback Book for everyone in electronics—beginner, serious experimenter, hi-fi fan, service technician, engineer. Gernsback books are technically accurate and fun to read. Page for page and dollar for dollar they give you more than any other technical books in the field. Read them and see.—You'll agree your best buy's GERNSBACK.

SERVICING

□ No. 85—How to Get the Most Out of Your VOM—By Tom Jaski. How to put this versatile instrument to new uses. \$2.90

□ No. 81—Printed Circuits—By Morris Moses. How they're made. How to work with them. \$2.90

□ No. 78—Rapid Radio Repair—by G. Warren Heath. Now you can find the toughest trouble in minutes. \$2.90

□ No. 76—Servicing Transistor Radios—By Leonard D'Airo. A specialist shows you how. \$2.90

□ No. 72—Oscilloscope Techniques—By Alfred Haas. How to use the scope for many new purposes. Hundreds of actual scope patterns illustrated. \$2.90

□ No. 68—TV and Radio Tube Troubles—By Sol Heller. How to spot tube troubles fast. \$2.90

□ No. 65—Servicing Color TV—By Robert G. Middleton. Color TV sales are up. Keep up with the industry, get this book now. \$2.90

□ No. 60—Rapid TV Repair—By G. Warren Heath. The ABC's of fast TV servicing. \$2.90

□ No. 59—Servicing Record Changers—By Harry Mileaf. It's easy and profitable to fix changers. \$2.90

□ No. 57—The VTVM—By Rhy's Samuel. How and why it works with hints on new uses. \$2.50

□ No. 55—Sweep and Marker Generators for TV and Radio—By Robert G. Middleton. You need this one for better servicing. \$2.50

□ No. 54—Probes—By Martin Clifford and Bruno Zucconi. All probe types and how to use them. \$2.50

□ No. 52—The Oscilloscope—By George Zwick. How to understand and use your scope. \$2.25

□ No. 50—TV Repair Techniques—Corner cutting hints to make servicing easier. \$1.50

□ No. 49—Radio & TV Test Instruments—Build 22 of the most practical. A steal at this price. \$1.50

SEMICONDUCTORS

□ No. 92—Fundamentals of Semiconductors—By M. G. Scroggie. A masterful study of the whole field. \$2.95

□ No. 89—Transistor Projects—A how-to-do-it that promises hours of happy building. \$2.90

□ No. 63—Transistor Circuits—By Rufus P. Turner. Over 150 "building blocks" and they all work. \$2.75

□ No. 61—Transistor Techniques—A work book on testing, performance, construction. \$1.50

□ No. 75—Transistors Theory & Practice (2nd ed.)—By Rufus P. Turner. Accepted as the standard work on the subject. It belongs on your bookshelf. \$2.95

HIGH FIDELITY

□ No. 90—Hi-Fi Made Easy—By Norman Crowhurst. Mr. Hi-Fi tells the layman what it's all about. Clever cartoons make learning more fun. \$2.90

□ No. 80—Stereo—How It Works—By Herman Burstein. If you want to know all about stereo get this one. \$2.90

□ No. 79—Designing and Building Hi-Fi Furniture—By Jeff Murkell. For the man who wants his system to look good, too. \$2.90

□ No. 73—Audio Measurements—By Norman Crowhurst. A complete manual for audiophile, technician, engineer. \$2.90

□ No. 71—H. A. Hartley's Audio Design Handbook—See—you don't have to be an engineer. \$2.90

□ No. 67—Elements of Tape Recorder Circuits—By Burstein and Pollack. Complete coverage of the electronic elements of a tape recorder. \$2.90

□ No. 66—Basic Audio Course—By Donald C. Hoefler. From the theory of sound to recording techniques. \$2.75

□ No. 64—Understanding Hi-Fi Circuits—By Norman Crowhurst. How audio circuits work and what to expect from them. \$2.90

□ No. 58—Maintaining Hi-Fi Equipment—By Joseph Marshall. What you have to know to service hi-fi systems. \$2.90

□ No. 56—High-Fidelity Circuit Design—By Norman Crowhurst & George Cooper. For the advanced hi-fi man. Cloth bound. \$5.95

□ No. 48—High Fidelity—Design, Construction, Measurements. \$1.50

All books paper bound unless otherwise stated

SEE THEM AT YOUR DISTRIBUTOR—OR ORDER DIRECT

In Canada: Len Finkler, 1794 Avenue Rd., Toronto 12, Ont.

Prices slightly higher in Canada



HOBBIES

□ No. 74—Model Radio Control—By Edward L. Saford. Revised and expanded basic book on theory and construction. \$2.65

□ No. 70—Electronic Puzzles and Games—By Matthew Mandl. Lots of fun for beginners. \$1.95

□ No. 69—Electronic Hobbyists' Handbook—By Rufus P. Turner. A grab bag of ideas for the electronic doodler. \$2.50

□ No. 53—Radio Control Handbook—By Howard G. McEntee. A practical construction book. \$2.25

FUNDAMENTALS— MISCELLANEOUS

□ No. 84—Marine Radio for Pleasure Craft—By Harold McKay. A primer for the growing navy of part-time skippers. \$2.95

□ No. 77—Guide to Mobile Radio—By Leo G. Sands. A close look at a growing new phase of electronics. \$2.85

□ No. 62—TV-It's a Cinch—By E. Aisberg. It is with this delightfully written (and cartoon-studded) book. \$2.90

□ No. 47—Radio & TV Hints—Hundreds of 'em—and only a buck. \$1.00

□ No. 45—Radio Tube Fundamentals—By George Christ. Tells the practical technician how and why tubes work. \$1.00

□ No. 44—Basic Radio Course—By John T. Frye. Manages to make the trip from Ohm's law to circuit analysis fun. Cloth bound. \$2.25



SERVICING HI-FI AND FM IN THE CUSTOMER'S HOME, by Milton S. Kiver. Howard W. Sams & Co. Inc., 1720 E. 38 St., Indianapolis, Ind. 8 1/2 x 5 1/2 in. 158 pp. \$2.95.

Service technicians will find this book helpful. A wide range of rapid tests are described for all kinds of hi-fi equipment. For example, Chapters 2 and 4 show the best way of using a vtvm and a small probe detector to troubleshoot amplifiers and AM-FM receivers in the home. Also covered are printed circuits, stereo units and transistor preamplifiers.—LS

MOST-OFTEN-NEEDED 1926-1938 RADIO DIAGRAMS and Service Information. Compiled by M. N. Beitman. (Reprint of book copyright 1941.) Supreme Publications, 1760 Balsam Road, Highland Park, Ill. 8 1/2 x 11 inches, 240 pages. \$2.50.

The rising interest in classic radios has prompted large numbers of inquiries for schematics of receivers manufactured before the '40's and going back to battery sets. These have been hard and expensive to obtain, being largely photocopied from out-of-print volumes. In view of the increasing demand, Supreme Publications has reprinted its Volume I, going from 1937 back to the early Atwater Kents.

The collector of ancient radios will find this work very useful, though he may be surprised to find that the manufacturers omitted values in some of the oldest schematics.—FS

CIRCUIT THEORY OF LINEAR NOISY NETWORKS, by Hermann A. Haus and Richard B. Adler. Technology Press of MIT and John Wiley Sons, Inc., 440 Fourth Ave., New York 16, N. Y. 6 x 9 in. 79 pp. \$4.50.

Much work is needed and is being done to minimize noise in radio circuits. To control anything, one must first understand and measure it. These authors have worked out methods for expressing the noise performance of networks and amplifiers, including those with negative resistance. A knowledge of higher mathematics is required.—IQ

MEDICAL ELECTRONICS, by Edward J. Bukstein. Frederick Ungar Publishing Co., 131 E. 23rd St., N. Y. 10, N. Y. 6 x 9 in. 168 pp. \$3.50.

Mr. Bukstein, known to readers of this magazine as the author of a number of articles, is an instructor of advanced electronics and approaches medicine from the electronic side of the fence. The book, therefore, pays most attention to things electronic, although it does describe in detail the recording of biological potentials and of non-electrical physiological phenomena, as well as devoting a chapter to electro-



GERNSBACK LIBRARY, INC., 154 West 14th St.
New York 11, N. Y.

SCHOOL DIRECTORY

ELECTRONICS

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION

TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS
OF VETERANS
BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE
BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

**SCIENCE
ENGINEERING**

BACHELOR'S DEGREE IN 27 OR 36 MONTHS
Accelerated year-round program: Aero., Chem., Civil,
Elec., Mech., Metal., Math., Chemistry, Physics. Modest
rate. Earn board. New classes start Sept., Jan., Mar., June.
Catalog, 1570 E. Washington Blvd., Fort Wayne 2, Indiana.

INDIANA TECHNICAL COLLEGE

**GET INTO
ELECTRONICS**

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 29 mos. B.S. in electronic engineering obtainable. ECPD accredited, G.I. approved. Graduates in all branches of electronics with major companies. Start September, February, Dorms, campus. High School Graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE
Dept. C Valparaiso, Indiana



engineering degree in 27 months

Grasp your chance for a better life. Rapid advancement. Better income. BACHELOR OF SCIENCE DEGREE IN 27 MONTHS in Elect., Electronics or Power majors. Mech., Civil, Aero., Chem., Engineering. IN 36 MONTHS in Business Administration (General Business, Acctg., Motor Transport Mgt. majors). Small classes. More professional class hours. Well-equipped labs. Campus. Dorms. Modest costs. Year-round operation. Founded 1884. Enter Sept., Jan., Mar., July. Write J. G. McCarthy, Director of Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.

TRI-STATE COLLEGE 2470 College Ave. Andola, Indiana

PHOTOGRAPHS

RADIO-ELECTRONICS can use good photographs of service benches, service shops, high-fidelity audio layouts, and any other interesting and original radio-electronic devices.

We will pay \$7.50 each for good professional photos or equivalent, suitable for reproduction.

Full information on subject photographed will increase their acceptability.

The Editor, RADIO-ELECTRONICS
154 West 14th St. New York 11, N. Y.

LEARN

LEARN RADAR MICROWAVES COMPUTERS—TRANSMITTERS CODE • TV • RADIO

Phila. Wireless Technical Inst. 1533 Pine St., Philadelphia 2, Pa. A Non-Profit Corp. Founded in 1908

Write for free Catalog to Dept. RE-7 Sept. classes now forming

Learn Transistor Electronics At Home!

Prepare now for a profitable career in this growing field. Learn theory, construction and applications of all types of transistors with this proven home-study course from the Philco Technological Center.

FOR FREE INFORMATION PLEASE WRITE TO:
PHILCO TECHNOLOGICAL CENTER
"C" and Ontario Sts., Philadelphia 34, Pa.

FREE! ELECTRONICS CAREER KIT

If you're interested in breaking into a good-paying job in Radio-TV-Electronics, I.C.S. will send you absolutely free a famous Career Kit with 3 famous booklets that have helped thousands of others — just like yourself — on the road to real success. Includes:

- 1 "HOW TO SUCCEED" Career Guide — 36-page gold mine of career tips and information.
- 2 "JOB CATALOG" of opportunities in your field of interest.
- 3 "SAMPLE LESSON" (math) to demonstrate the famous I.C.S. method.

Send today for your free I.C.S. Career Kit with these 3 famous booklets. There's no obligation. This may be the big break you've been waiting for. Mark and mail the coupon today.

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 37689F, Scranton 15, Penna.

Please send free Career Kit with 3 famous booklets

General Electronics Radio-TV Serv'g Practical Electrician
 Industrial Electronics Sound Equip. Serv'g Profess'l Eng. (Elec.)
 Radio-TV Eng'g Electrical Eng'g Electrical Drafting
 Electronic Servicing Electrical Tech. Other

Name _____ Age _____
Address _____
City _____ State _____

prepare for your career in

ELECTRICAL ENGINEERING ELECTRONICS COMPUTERS RADIO-TV

At MSOE, you can equip yourself for a career in many exciting, growing fields: MISSILES RADAR • AUTOMATION RESEARCH • DEVELOPMENT ELECTRICAL POWER AVIONICS • ROCKETRY

When you graduate from the Milwaukee School of Engineering, you are prepared for a dynamic career as an Electrical Engineer or Engineering Technician. Under a faculty of specialists, you gain a sound technical education in modern, completely equipped laboratories and classrooms. As a result, MSOE graduates are in great demand and highly accepted by industries nationally.

At MSOE you will meet men from all walks of life and all parts of the country — some fresh out of high school or prep school, others in their twenties — veterans and non-veterans.

You can start school in any one of four quarters and begin specializing immediately. Engineering technicians graduate in 2 years with an Associate in Applied Science degree. For a Bachelor of Science degree in Engineering, you attend 4 years. A 3-month preparatory course also is available.



FREE CAREER BOOKLET!
If you're interested in any phase of electronics, radio or television, be sure to look into the programs of study offered by the Milwaukee School of Engineering. Just mail the coupon.


MILWAUKEE SCHOOL OF ENGINEERING
Dept. RE-760, 1025 N. Milwaukee St., Milwaukee, Wisconsin

Please send FREE Career Booklet. I'm interested in Electrical Engineering; Electronics Computers Electrical Power Radio-TV Mechanical Engineering.

PLEASE PRINT

Name _____ Age _____
Address _____
City _____ Zone _____ State _____
 I'm eligible for veterans education benefits.

MS-123

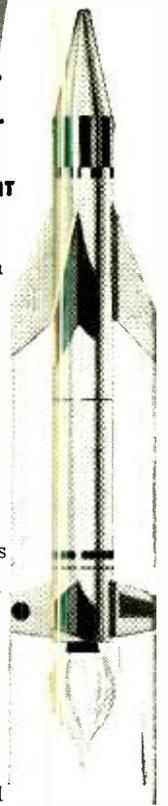

JULY SPECIALS

- **RG8A/U Coaxial Cable.** Fresh stock. Latest non-contaminating type of RG8 U. 8 1/2¢ ft.
- **UG88/U Connectors** modern type BNC connector. (Reg. price \$1,091.00).
- **Hubbell Polarized Plugs.** Rated 20 A @ 250 V. Order 1 Hubbell "Twist-Lock". 45¢ each. Stock #B-207.
- **Ceramic crystal sockets** for modern miniature CR type crystals. 15¢ Stk. #B-205.
- **Silver Plated Buss Strips** for UHF wiring and plate connections. 4 1/2" Length. Width: 3/8". In 1/2" Length. 15¢. Stock #B-212 @ .15¢ each. In 7/2" Length Stock #B-213 @ .25¢ each.
- **TS-197/U Military Equivalent of Model 80 Sig. Generator.** 2 to 400 Mcs. in 6 bands. \$350.00.
- **SP-600 Hammarlund Super-Pro.** 551 to 57 Mcs. in 6 bands. Lab certified O.K. Reg. \$1200.00. Special \$150.00.
- **Just received new lot of transistorized power supplies.** H.P. Digital VTVM's Model 405AR. New. Write for details.
- **Oil Capacitor Special.** 2 Mfd @ 2,000 VDC \$2.00 (Brackets .29¢ for a pair).
- **Westinghouse Glass-Enclosed Overload Relay.** Adjustable from 500 Mcs. 5/16 to 2 Amps. coil: 115 VAC @ 60 CPS. Type SC-1. \$4.95 each.
- **Mobile Transmitter.** Uses 5618 crystal oscillator into CBS 5516 amplifier. Modern design. Only 7 lbs. net wt., including built-in 6 V. vibrator power supply, w 8 silicon rectifiers. Comp. enclosed in aluminum cabinet. Furnished w crystal that doubles near 10 meter band. Rectifiers slight & easy modification for 10 meter operation. Fused w/ tubes \$12.95.
- **Raised Relief Map 28 1/2" x 18 1/2".** Beautiful colors in lifetime plastic. Specialty USA or World Map @ \$9.95 each (ready for hanging - self framed).
- **Ling Model 2050 TV Xmitr (demonstrator)** 120 to 150 Mcs. Write for details.
- **Aero 9 Reed Freq. Meter.** Range: 58 to 62 Cy. 100-140 V. AC 37 Rd. \$11.00.
- **Cramer 15 Second Adjustable Timer.** Oper. on 7.5 VAC @ 60 CPS. Supplied w suitable xfm for 115 VAC use. \$17.00 contacts 10 Amps. Mounts in 2 1/2" Dia. hole \$8.95.
- **Selen. Rectifier 130 V. RMS 300 Ma.** .50¢ RG50/U Coax cable .04¢ ft.
- **Minimum order \$5.00. .50¢ service charge for orders under \$5.00.**
- **JUST OUT! NEW SUMMER 1960 GREEN SHEET CATALOG. WRITE FOR YOUR COPY TODAY!**

Walker 5-7000

BARRY ELECTRONICS CORPORATION

Dept. RE-7

512 BROADWAY, NEW YORK 12, NEW YORK

Please mention
RADIO-ELECTRONICS

when answering advertisements

TAPE RECORDERS

HI-FI COMPONENTS SLEEP LEARN KITS

MERITAPE | **UNUSUAL VALUES**
Low cost, high quality recording tape in boxes or cans. | **FREE 1960 CATALOG**

DRESSNER, 69-02RE 174 St., Flushing 65, N.Y.

**GRIPS THE SCREW!
DRIVES IT TOO!**

QUICK-WEDGE SCREW-HOLDING SCREW DRIVER

2" to 14" blades, 4 bit sizes. Available with shock-proof plastic covered tubing.

Ask For It At Your Dealer

KEDMAN CO., 233 S. 5th W., Salt Lake City, Ut.

NEW BOOKS (Continued)

diagnosis, electrotherapy and electro-surgery. Electronic readers will find the chapter on strip chart recorders and that on ultrasonics especially interesting.—*FS*

CLASS-D CITIZENS BAND CALLBOOK, 1960. International Crystal Mfg. Co., Inc. Oklahoma City, Okla. 9 x 11 in. \$3.95.

This register is for persons who operate class-D, who intend getting their permit to do so or who merely like to eavesdrop on the band. It gives calls in every district, with names and addresses, and includes a map, explanation of FCC rules, plus data on antennas, tuning and frequency measurement, etc.

An application for a Citizens band permit and the complete Part 19 of the FCC rules form part of the callbook. They will help you get your name in the next callbook.—*IQ*

PRINCIPLES OF TRANSISTOR CIRCUITS, by S. W. Amos. John F. Rider Publisher, Inc., 116 W. 14 St., New York 11, N. Y. 5 1/2 x 8 1/2 in. 167 pp. \$3.90.

This book is an excellent introduction to the theory and practice of transistors and circuit design. It discusses such factors as gain, power, impedance, stability factor, etc., and practical examples show how to determine them.

The book is suited for students and technicians who know basic algebra. It derives the exact formulas for circuits and their approximate values as used in practice. Small-signal and class-B amplifiers, radios and stabilizing networks receive special attention. Multivibrators, dc converters and the newer transistor types are discussed briefly.

INDUSTRIAL ELECTRONICS AND CONTROL, by Royce Gerald Kloeffer (Second Edition). John Wiley & Sons, Inc., 9 1/4 x 6 in. 540 pp. \$10.

A text for the advanced student, practicing engineer or technician interested in industrial electronics. Expanded and updated, the book covers many aspects of the subject. It starts off with nine chapters on electronic fundamentals, including transistors, electrical conduction in gases, and amplifier and oscillator circuits. The remaining nine chapters illustrate the operation of several types of industrial devices—servomechanisms, high-frequency heating, X-ray applications and computer principles.—*LS*

SILICON RECTIFIER HANDBOOK, Sarkes-Tarzian, Inc., Semiconductor Div., Bloomington, Ind. 5 1/4 x 8 1/2 in. 62 pp. \$1.

Here is the whole story of silicon rectifiers, from theory to practice. Manufacturing methods, test circuits and filter design are among the subjects. Charts, tables and formulas show how to get optimum results from rectifiers and circuits. The book ends with a list of rectifiers and their characteristics.—*IQ*

LOW FREQUENCY AMPLIFIER SYSTEMS, 70 pp. \$1.80. VIDEO AMPLIFIERS, 80 pp. \$1.80. RF AMPLIFIERS, 96 pp. \$2.40. Edited by

A. Schure. John F. Rider, Publisher Inc., 116 W. 14 St., New York 11, N.Y. 5 1/2 x 8 1/2 in.

These 3 volumes cover the frequency ranges from af through rf to the higher video frequencies. Readers should be familiar with algebra and radio theory. The books discuss design equations and show how to use them. Most of the material is on tube circuits, but two of the books include short chapters on transistors. All three are suitable for students of electronic technology.

TABULATION OF DATA ON RECEIVING TUBES. National Bureau of Standards Handbook 68. US Government Printing Office, Washington 25, D. C. 7 1/4 x 10 1/4 in. 110 pp. \$1.

This handbook makes it easy to locate the receiving tube you need. It lists types with less than 25 watts plate dissipation that are suitable for use at frequencies below 1,000 mc.


A numerical listing gives size and shape, use, manufacturer, as well as plate and filament ratings, g_m , capacitance, etc. Also, tubes are listed under headings like double triode, pentode with triode, etc. Large, readable base diagrams appear at the end of the book.—*IQ*

ABC'S OF HAM RADIO by Howard S. Pyle. Howard W. Sams & Co. Inc., 1720 E. 38 St., Indianapolis, Ind. Bobbs-Merrill Co., 717 5th Ave., New York, N.Y. 5 1/2 x 8 1/2 in. 112 pp. \$1.50.

From this book you can learn all you need to know to become a Novice operator. It tells how to prepare for the exam and how to learn the code. Basic electricity, Q code, location of FCC offices are among the contents.

RADIO AMATEUR LICENSING HANDBOOK (Second Edition), by Jim Kitchin. Radiotelephone Directories of Canada Ltd., 119 W. Pender St., Vancouver 3, B. C., Canada. 5 1/2 x 8 1/2 in. 107 pp. \$2.

This one is for Canadians. It explains licensing and operating rules in Canada and gives typical exam questions. The Q code, time-conversion charts and other useful data are included. Canada has no Novice class and its radio exams are partially oral. Therefore, radio theory is particularly important to prospective hams. This is not a theory book, so the reader should arrange to study techniques from another source.—*IQ* END

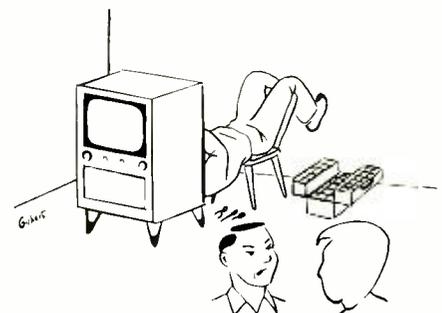

"Joe's been on car radios too long!"

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Aerovox Corp.	109
Airex Radio Corp.	118
Allied Radio	9
Almo Radio Co.	115
Amperex Electronic Corp.	8
Arkay International Inc.	118
Astatic Corp.	2nd Cover
Atlas Sound Corp.	117
Audion	110
Audio Unlimited, Inc.	111
B & K Mfg. Co.	100, 101
Barry Electronics Corp.	122
Bonafide Radio	111
Bogen-Presto	80
Brooks Radio & TV Corp.	113
Niles Bryant School	119
Capitol Radio Engineering Inst.	82, 85
Carston Studios	100
Castle TV Tuner Service	73
Center Electronics Co., Inc.	110
Centralab Div of Globe Union	22
Chemical Electronic Engineering, Inc.	71
Cleveland Institute of Radio Engineering	11
Cornell-Dubilier Electric Corp.	79
Coyne Electrical School	117
CREI Atomic	112
DeVry Technical Institute	7
Dressner	122
Electro-Sonic Labs.	112
Electronic Chemical Corp.	110
Electronic Instrument Co.	23, 24
Electronic Measurement Corp.	74
Electronic Publishing Co., Inc.	117
Electronics Representatives Association (ERA)	14
Gernsback Library	120
Grantham School of Electronics	17
Heald Engineering College	123
Heath Company	64, 65, 66, 67
Indiana Technical College	119
Jerrold Electronics Co.	3rd Cover
Kedman Co.	122
Key Electronics Co.	110
Lafayette Radio	124
Mercury Electronics	16
Moss Electronic Inc.	90, 91
National Radio Inst.	3
National Technical Schools	5
Ohmatsu Electric Co. Ltd.	123
Olson Radio Corp.	115
Opportunity Adlets	111
PACO Electronics	12
Piekering & Co., Inc.	114
Picture Tube Outlet	111
Progressive "Edu-Kits", Inc.	105
Quam-Nichols Company	18
Quietrol Co., Inc.	112
RCA Tube Div.	Back Cover
RCA Institutes	20, 21
Radio Shack Corp.	114
Rider Inc. (John F.)	119
Rinehart & Co., Inc.	96
Sams (Howard W.) & Co., Inc.	106, 107
Schober Organ Co.	87
Scott, (H. H.), Inc.	99
Seg Electronics	101
Sencore	70, 71, 72, 73
Shure Bros. Inc.	97
Sonotone Corp.	103
Sprague Products Co.	13
Sprayberry Academy of Radio TV	19
Standard Coil Products Co., Inc.	15
Sylvania Electric Products, Inc.	10
TAB	116
Sarkes Tarzian, Inc.	108, 114
Vanguard	110
Vidaire	72
Warren Distr. Co.	110

SCHOOL DIRECTORY PAGE 121

Baltimore Technical Institute
 Indiana Technical College
 International Correspondence School
 Milwaukee School of Engineering
 Phila. Wireless Technical Institute
 Philco Technological Center
 Tri-State College
 Valparaiso Technical Institute

ADVERTISING REPRESENTATIVES: Los Angeles: Barker-Hurst & Conditin, 609 South New Hampshire, Tel. DUmkin 7-2328. San Francisco: Barker-Hurst & Conditin, 111 Market St., Tel. GArlfield 1-2481. Chicago: 8631 East Prairie Road, Skokie, Ill., Tel. ORchard 5-3740.
FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bilde Lane, London E.C. 4.
 Printed in the United States of America

JULY, 1960

new "LEADER" test instrument

LAG-55 AUDIO GENERATOR SINE SQUARE

A multi-purpose generator for measurements on audio equipment - amplifiers, speakers, networks. Three waveforms: sine, square and complex for all types of measurements including response, distortion, transient and I-M distortion checks. Full range is from 20 to 200,000 cps, output 5 volts with minimum amplitude variation throughout whole range.



The LEADER test instruments are being used in the more than 36 countries, attesting their excellence in design, performance and usefulness.

OHMATSU ELECTRIC CO. LTD.

2596, 5-CHOME, KAMIMEGURO, MEGURO-KU, TOKYO, JAPAN
 Cable Address "OHMATSUELEC" TOKYO

ATTENTION

- Service Technicians' Associations
- Club Members
- Student Groups

Special subscription rates to RADIO-ELECTRONICS are available to associations, clubs, schools, employee groups, etc. For information write— G. Aliquo

Radio-Electronics 154 West 14th St., New York 11, N. Y.

ELECTRONICS Engineering-Technicians

Bachelor of Science Degree, 30 Months

Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Technician (12 Months)
- Industrial Electronics Technician (12 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans
DAY AND EVENING CLASSES

Write for Catalog and Registration Application.
 New Term Starting Soon.



Missile headed for outer space. Courtesy of Space Technology Laboratories, Inc.

U.S. Air Force Photo

HEALD'S ENGINEERING COLLEGE

Established 1863

Van Ness at Post, RE
 San Francisco, Calif.

Your Name

Address

City

State

NEW


LAFAYETTE HE-15 CITIZENS BAND 11 METER 2-WAY SUPERHETERODYNE TRANSCEIVER

MADE IN U.S.A.



**COMPLETELY WIRED
NOT A KIT!**

64.50

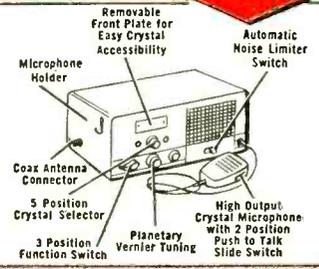


ONLY 5.00 DOWN

Not Superregenerative but SUPERHET!

The Lafayette HE-15 meets all FCC requirements and operates in much the same manner as police and other short wave communications systems. The Transceiver features 5 crystal controlled transmitting channels operating at a maximum legal power input of 5 watts fully modulated, RF stage in both transmitter and receiver. Any one of 5 transmitting frequencies may be instantly selected by the 5 position crystal selector on the front panel. These 5 crystals are readily accessible by means of a removable front plate and this may be easily interchanged with any 5 crystals of the remaining 22 allocated citizens band frequencies.

The Superheterodyne receiver is tuneable over the full 22 channel band with 3 watts audio output. Controls include a 3 position function switch (transmit, receive, and transmit with spring return), planetary vernier tuning plus squelch noise limiter control switch. All coils are ferrite tuned. Output impedance matches 52 and 72 ohm antenna with Amphenol type coax connector for operating into dipole, ground plane or rod antenna. Has large 4" PM speaker; input jack for crystal or ceramic microphone; power receptacle in rear for AC line and 6 or 12 volt external power supply. Transceiver is supplied with single transmitting crystal for channel 9. Complete high output with crystal microphone, and brackets for easy mounting of unit in auto, boat, etc. Operated on 115 volts AC. Addition of 6 or 12 volt power supply (separately supplied) adapts transceiver for mobile operation. Size 5 1/2"H x 6 3/8"D. Shpg. wt., 11 lbs.

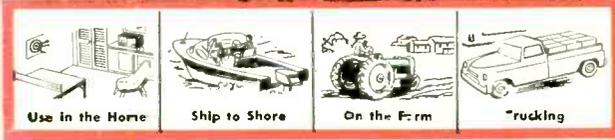HE-15 Factory Wired and Tested (Less antenna). 5.00 Down.....Net 64.50
 HE-19 Whip Antenna.....Net 3.95
 HE-16 Power Supply For 12 Volts.....Net 11.95
 HE-18 Power Supply For 6 Volts.....Net 11.95



- 5 CRYSTAL CONTROLLED TRANSMITTING POSITIONS
- SUPERHETERODYNE TUNEABLE RECEIVER OVER FULL 22 CHANNEL BAND
- 4 DUAL FUNCTION TUBES, PLUS 2 SINGLE FUNCTION TUBES, PLUS 2 RECTIFIERS FOR 12 TUBE PERFORMANCE
- PLANETARY VERNIER TUNING
- COMPLETE WITH TRANSMITTING CRYSTAL FOR 27.065MC
- MEETS ALL FCC REGULATIONS
- REMOVABLE FRONT PLATE FOR EASY ACCESSIBILITY OF CRYSTALS
- UNEXCELLED RECEPTION ON LAND AND SEA... COMPARES WITH UNITS COSTING 3 TIMES AS MUCH

NEW! LAFAYETTE TELESCOPIC CITIZENS BAND WHIP ANTENNA

3.95

- Chrome Plated
- Telescopes From 16 1/2" to 40"
- Mounts Vertically or Right Angle

An outstanding antenna value. This high quality three section telescoping antenna is designed for attachment directly to your citizens band transceiver. Ideal for point to point service over short distances. Molded base leading coil has a threaded stud with a PL-259 plug—connector for vertical or right angle mounting. Shpg. wt., 1 lb. HE-19.....Net 3.95



NEW! LAFAYETTE RADIO FIELD INDICATOR

A Must For Ham & Citizens Band Operators

7.95

- Provides a Continuous Indication of Transmitter Output • Rugged 200 ua Meter Movement • Completely Portable — Requires no Electricity, Batteries or Transmitter Connection.

With this rugged, new radio field indicator you can check performance of your marine, mobile or fixed transmitter... actually measures the RF field generated by any transmitter between 100KC and 250MC regardless of power. Features a 200 ua meter movement with a variable sensitivity control: Phone jack at rear of indicator accepts earphones thus providing an aural check of transmitter output. Antenna extends from 3 1/4" to 10 3/4". Powerful magnet on bottom plate allows easy mounting on car dashboard or metal surfaces. Use anywhere... requires no electricity or batteries. Dimensions: (less antenna) 3 1/4"W x 2 1/4"H x 2" D. TM-14.....Net 7.95



NEW! LAFAYETTE "Tiny"

6 Transistor Radio
SENSATIONAL PERFORMANCE
 In a Small Package!

19.95

- 6 Transistor Plus a Germanium Diode
- Superheterodyne Circuit • Vast Pocket Size
- Built in Earphone Jack For Private Listening
- Trouble-Free Printed Circuit

Engineered and constructed with the jewel like precision of a fine watch... true superhet circuit, with push-pull audio output powers either the built-in dynamic speaker or the personal-type earphone. Extremely sensitive... built-in ferrite—rod antenna brings in distant stations like locals. Employs standard 9 volt battery for economical service. Housed in smart black and gold rugged plastic case. Measures only 4" x 2 1/2" x 1 1/4" and weighs a mere 10 ounces. Complete with battery, carrying case and earphone. Shpg. wt., 2 lbs. FS-208 "Tiny" 6-Transistor Radio... Net 19.95



PLEASE RUSH ITEMS CHECKED!

- HE-15 CITIZENS BAND TRANSCEIVER
- TM-14 RADIO FIELD INDICATOR
- FS-206 "TINY" 6 TRANSISTOR RADIO
- HE-19 WHIP ANTENNA
- FREE 308 PAGE CATALOG 600

Enclosed Find \$.....(Please include postage to cover shipping)

FREE 308 Giant Size Pages!

Name.....
 Address.....
 City..... Zone..... State.....

Everything in Hi-Fi and Electronics

LAFAYETTE RADIO,
 P. O. BOX 222, JAMAICA 33, N.Y. Dept. **JG-6**

The Lid's Off!



JERROLD announces the all printed circuit antenna . . . the first new concept in TV-FM reception in 10 years!

Indoor Antenna—Outdoor Design! Jerrold's new Magic Carpet* is a flat, flexible all printed circuit antenna based on a broad-banded dipole design. Installed indoors in attic, crawl space, closet or any upper level location in the home, it offers performance comparable to a conical type outdoor antenna (mounted in the same location)** at a fraction of the cost.

A report on the Magic Carpet in the May issue of Electronics World states "Gain characteristics across all frequencies are very close to those of standard outdoor conicals." No more need for unsightly rooftop or indoor antenna (up to 30 miles from the TV transmitter). The Magic Carpet opens up a whole new antenna market for the TV and FM Serviceman.

9.95
LIST

Get the full story of the magic of its performance . . . the potency of its sales appeal, see your Jerrold Distributor or write today

JERROLD Electronics Corporation, Distributor Sales Division, Dept. IDS-34, Philadelphia 32, Pa.

Jerrold Electronics (Canada) Ltd., Toronto

Export Representative: CBS International, New York 22, N. Y.

↓ (illus. shows upper section of Magic Carpet)

*Trade Mark Patent Pending

**Data certified by American Electronic Laboratories Inc.



How do your customers rate you?



Your reputation is based largely on what happens *after* you leave the scene of each service call. For this reason the name on the tubes you install makes a world of difference. RCA tubes are designed and manufactured to assure customer confidence in you as well as in RCA.

RCA tube quality is your best insurance against call-backs due to premature tube failure.

RCA tube performance puts your workmanship in the best light and protects it through rigid quality control.

RCA's trademark symbolizes a name and reputation customers have respected for decades.

Your customers know that those red-white-and-black RCA tube cartons in your tube caddy represent the most trusted name in electronics. Remember, customer confidence is the cornerstone of your business.

To protect your service reputation before, during and after every service call, make sure your next tube order specifies... RCA TUBES.

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.



SIGN OF A SERVICE JOB WELL DONE



The Most Trusted Name in Electronics
RADIO CORPORATION OF AMERICA