

Have 310 • Will Travel...

Light!

Burton Browne Advertising

- Hand size, but with the features of a full-size V-O-M.
- 20,000 ohms per volt DC; 5,000 AC.
- EXCLUSIVE SELECTOR SWITCH speeds circuit and range settings. The first miniature V-O-M with this exclusive feature for quick, fool-proof selection of all ranges.
- SELF-SHIELDED Bar-Ring Instrument; permits checking in Strong Magnetic Fields.
- Fitting interchangeable test prod tip into top of tester makes it the common probe, thereby freeing one hand.
- Inbreakable plastic meter window.
- BANANA-TYPE JACKS—positive connection and long life.



MODEL 100



The most comprehensive test set in the Triplet line is Model 100 V-O-M Clamp-On-Ammeter Kit, now available at distributors. The world's most versatile instrument—a complete accurate V-O-M plus a clamp-on-ammeter with which you can take measurements without stripping the wires. Handsome, triple-purpose carton holds and displays all the components: Model 310 miniaturized V-C-M, Model 10 Clamp-On-Ammeter, Model 101 Line Separator, No. 311 extension leads and a Leather Carrying-Case, which neatly accommodates all the components. Model 101 literally makes it possible to separate the two sides of the line when using Model 10. Extension leads permit use of Model 10 at a distance from the V-O-M. Complete Model 100 is only \$59.50.




For full information see your Triplet distributor
or write

TRIPLETT ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO



PANEL METERS

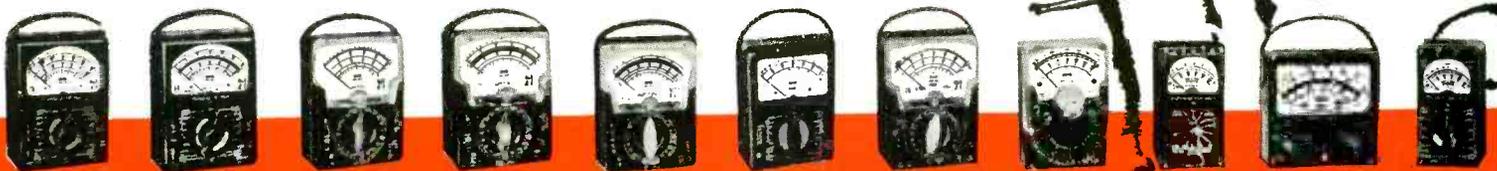AND A VOM FOR EVERY PURPOSE AND EVERY PURSE



530 530-A 530-B 530-C 530-D 530-E 530-F 530-G 530-H 530-I 530-J

www.americanlaboratory.com

If you have some knowledge of Radio or Television or Electronics now and want to **BECOME A PROFESSIONAL SERVICE TECHNICIAN**



you will want to investigate the special **ALL-PRACTICE TRAINING PLAN** developed for men like you by the **OLDEST AND LARGEST** home study **Radio-Television school**

Over 40 years ago, J. E. Smith, founder of the National Radio Institute, pioneered in teaching Radio by the home study method. Today, this magnificent building is completely devoted to NRI's Radio-TV Electronics training. Here up-to-date laboratory and research facilities are constantly testing new developments and improved methods of training men for Radio-TV Electronics careers.

All-Practice Method



NRI's Professional TV Servicing Training is practical, complete. You make tests and experiments to help thoroughly understand TV problems. You get equipment to build a 5" Oscilloscope, a 17" picture tube and all components for building a TV receiver. Comprehensive Color TV manuals also included. You learn how experts diagnose TV defects, get knowledge of professional techniques. Mail the coupon for free catalog now. **NATIONAL RADIO INSTITUTE, Washington 16, D. C.**

MAIL THIS TO NRI NOW

National Radio Institute, Dept. OKFT, Washington 16, D.C.

Accredited Member National Home Study Council

Please send me a **FREE** copy of your catalog "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name..... Age.....

Address.....

City..... Zone..... State.....

(Note: This training is NOT for beginners)



Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION*

EDITORIAL

33 Instructive Electronic Devices—Hugo Gernsback

AUDIO-HIGH FIDELITY

- 34 Build a High-Power Twin-Coupled Amplifier (Cover Feature)
—Norman H. Crowhurst
- 45 Add a Third Speaker the Easy Way—Herman Burstein
- 48 New Stereo Pickups, Part II—Julian D. Hirsch
- 78 Sound at the Cocktail Party

ELECTRONICS

- 38 How Live Is Your Nickel-Cadmium Battery?—Nathaniel Rhita
- 39 Better Photos With a Transistor Slave Flash You Can Make—Franklin T. Merkle
- 51 Duo-junction—I. Queen
- 54 Build a Transistor Capacitance Relay—Rufus P. Turner
- 55 Winding a Transistor-Power-Supply Transformer
—R. L. Winklepleck
- 58 The Tunnel Diode Really Works . . . Try These Circuits—I. Queen

RADIO

- 52 Assemble a One-Transistor Radio That Powers an 8-Inch Speaker
—William H. Grace, Jr.
- 82 Radio Control With Oomph—Make a 30-Watt Transmitter
—J. H. Thomas

INDUSTRIAL ELECTRONICS

- 68 Understanding Magnetrons, Industrial Power Generators—Tom Jaski
- 88 Injec-Check Industrial Equipment With This Home-Built Unit
—Wm. F. Kernin

TELEVISION

- 40 Troubleshooting the Vertical Oscillator and Output Stages
—R. D. Jacques
- 60 TV Service Clinic—Conducted by Jack Darr
- 84 Tube-Changing the Tough Ones—Jack Darr
- 92 TV Antennas Invite Lightning to Strike

TEST INSTRUMENTS

- 46 Construct This Practical Tester for Electrolytics—H. B. Conant
 - 76 Make Your Own Transistor Field-Strength Meter for the Citizens Band—Lyman E. Greenlee
- | | |
|-------------------------|-------------------------|
| 125 Business and People | 6 News Briefs |
| 21 Correspondence | 112 Noteworthy Circuits |
| 130 New Books | 114 Technician's News |
| 128 New Literature | 110 Technotes |
| 117 New Patents | 120 Try This One |
| 98 New Products | 124 50 Years Ago |
- 96 New Tubes and Semi-conductors

ON THE COVER

(Story on page 34)

The printed-circuit heart of the new RADIO-ELECTRONICS Twin-Coupled Amplifier described in this issue. The printed board was designed and executed by Electro-Technik Co., Detroit, Mich.

Color original by Habershaw Studios

- Hugo Gernsback
Editor and Publisher
- M. Harvey Gernsback
Editorial Director
- Fred Shunaman
Managing Editor
- Robert F. Scott
W2PWG, Technical Editor
- Larry Steckler
Associate Editor
- I. Queen
Editorial Associate
- Elizabeth Stalcup
Production Manager
- Fernando Martinez
Art Director
- Wm. Lyon McLaughlin
Tech. Illustration Director
- Fred Neinast
Staff Artist
- Lee Robinson
Director, Advertising Sales
- John J. Lamson
Eastern Sales Manager
- G. Aliquo
Circulation Manager
- Adam J. Smith
Director, Newsstand Sales
- Robert Fallath
Promotion Manager



Average Paid Circulation Over 163,000



RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index (Formerly Industrial Arts Index)*

RADIO-ELECTRONICS, October, 1960. Vol. XXXI, No. 10. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class postage paid at Mt. Morris, Ill. Copyright 1960 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.
SUBSCRIPTION RATES: U.S., U.S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$10.00 for three years. Pan-American countries \$5.00 for one year; \$9.00 for two years; \$13.00 for three years. All other countries \$5.50 a year; \$10.00 for two years; \$14.50 for three years.
SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscriber Service, 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.
GERNSBACK PUBLICATIONS, INC. Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N.Y. Telephone AIGonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary.
ADVERTISING REPRESENTATIVES and FOREIGN AGENTS listed on page 130.
POSTMASTER: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS

NOW!
at a price
you can afford!

MAKE MORE MONEY in TELEVISION RADIO-ELECTRONICS

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of *Television-Radio-Electronics*.

LOWER COST... Other schools make several courses out of the material in our **ONE MASTER COURSE** . . . and you pay more for less training than you get in *our course* at **ONE LOW TUITION!**



These two **FREE** books will show you how!

You get all information by mail . . . You make your own decision . . . at home! **NO SALESMAN WILL CALL**

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough *Practical* training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up, that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how to earn extra money right from the start. Many of our students pay for their course—and more—while studying. So can you!

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start **NOW** in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment . . . professionally installed . . . finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school . . . and part time job while you learn. Check box in coupon for full information.

LESSONS AND INSTRUCTION MATERIAL ARE UP-TO-DATE, PRACTICAL, INTERESTING. Every National Schools Shop-Method lesson is made easy to understand by numerous illustrations and diagrams. All instruction material has been developed and tested in our own Resident School Shops, Laboratories and Studios.

SEND FOR INFORMATION TODAY . . . it can mean the difference between **SUCCESS** and failure for you! Send for your **FREE BOOK** "Your Future in Television-Radio-Electronics" and **FREE Sample Lesson.** Do it **TODAY**, while you are thinking about your future. It doesn't cost you anything to investigate!

GET THE BENEFITS OF OUR OVER 50 YEARS EXPERIENCE

Approved for
GI Training



NATIONAL SCHOOLS

Los Angeles 37, Calif.

YOU GET...

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

SHOP-METHOD HOME TRAINING COVERS ALL PHASES OF INDUSTRY

1. Television, including Color TV
2. Radio AM & FM
3. Electronics for Guided Missiles
4. Sound Recording and Hi-Fidelity
5. FCC License
6. Automation and Computers
7. Radar & Micro-Waves
8. Broadcasting and Communications

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

MAIL NOW TO

NATIONAL TECHNICAL SCHOOLS, Dept. RG100
4000 S. FIGUEROA ST. LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

Check if interested **ONLY** in Resident School training at Los Angeles.
VETERANS: Give date of Discharge _____

News Briefs


Echo Satellite Opens Way To New Communications System

The successful transcontinental telephone conversations via the Echo satellite may be only the beginning of a complete system of telephone and TV relay communications via satellites. This is the opinion of scientists both of the National Aeronautics and Space Administration (NASA) and of the Bell Telephone Laboratories, who collaborated to put Echo into space.

The first satellite is a sphere 100 feet in diameter, making a circuit around the earth in a little over 2 hours, and traveling roughly 1,000 miles above the earth on a course angled 47° from the equator. Two tiny transmitters 180° apart on the sphere's equator help the ground stations to track it. Otherwise Echo is a complete passive reflector.

A number of satellites, either three or four at great heights, as proposed by Hugo Gernsback in RADIO-ELECTRONICS, March, 1958, or a system of 50 traveling at about the same height as Echo, could carry a fantastic number of messages and provide reliable communication at all hours of the day.

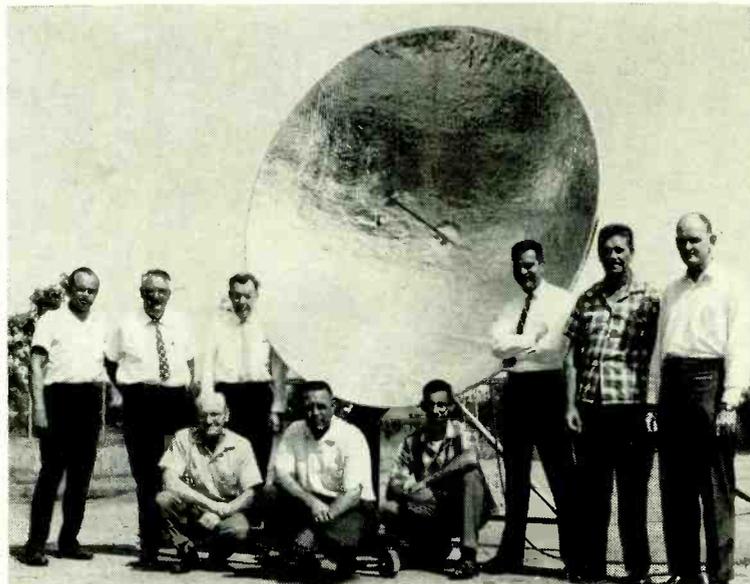As a rehearsal for Echo, phone messages were exchanged between Holmdel, N. J., and Goldstone, Calif., using the moon for a reflector. Reception, as witnessed by a large group of reporters, was completely intelligible, though much more noisy than the later Echo transmissions. The same receiving equipment was



used later to track and receive Echo.

In transmissions between the Bell station at Holmdel and Jet Propulsion Laboratories at Goldstone, power in the order of 10 kw for the transmitters was used at both ends, the West Coast station operating at 2390 mc and the Bell Labs transmitter at Holmdel using 960 mc. The receiver is a ruby maser type, which, in conjunction with the special horn antenna, reduces noise to a negligible level.

Hams Bounce Signals Off Moon

The first amateur radio moon-bounce contact was made July 21

between the Eimac Radio Club in San Carlos, Calif., and Sam Harris of the Rhododendron Swamp VHF Society, Medfield, Mass. The frequency used was 1,296 mc. At both ends of the circuit, a 1,000-watt (maximum allowable power) klystron was used in the transmitter and a sensitive Microwave Associates MA2-1000 parametric amplifier in the receiver.

The contact took place between 7:30 and 8:00 am, PDT.

The photograph shows some of the members of the Eimac Radio Club who participated in the moon-bounce project. They are, left to right, standing: W6OUV, Robert Sutherland; W6HB, O. H. Brown; W6UF, Bill Eitel; W6RXW, George Badger; W6MUC, Al Clark; K6GJF, Bob Morwood; sitting, W6KEV, Ray Rinaudo; W6IVZ, Charles Anderson and K6GSO, Allan Beer. Not shown are Bill Orr, W6SAI, and Mike Krivohlavak, K6AXN.

Underground Radio

A teletyped radio message has been sent through 4½ miles of the earth's substrata by Developmental Engineering Corp. The message was sent on a frequency of 150 kc, but anything between 30 kc to 3 megacycles is suitable.


The transmitter was placed 1,000 feet below the surface in a mine near Carlsbad, N. M. The receiving equipment was in a second mine 4½ miles away.

The Lithocom system is not suitable for general broadcasting as the

(Continued on page 10)




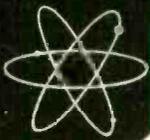Space-relay terminal at Holmdel, N.J. Transmitting antenna is at left, the receiving horn at the right of the photo. Receiving equipment is in shack at horn's end.



**The Man
who works with
His Hands..**

MEN 17-55

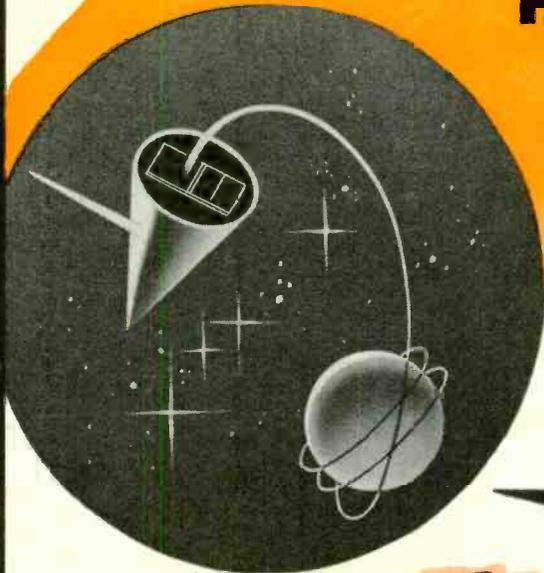

Has a Real Advantage When Preparing for
MONEY! EXCITEMENT! JOBS!
in
Electronics


**FROM RADAR—TV . . . TO GUIDED
MISSILE CONTROL
ETC.**



Machine Operator



Gas Station Attendant

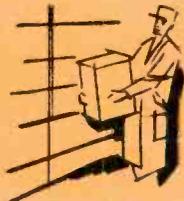

Stock Clerk



Soda Clerk



Laborer



Farmer

IS YOUR PRESENT JOB LIKE THESE?
You may have just the skill needed to train for a real job in Electronics!

"One of North America's Foremost Electronics Training Centers"
Accredited Member of National Home Study Council



EMPLOYMENT SERVICE
Helps graduates get started toward a good job or their own service shop.

DeVRY TECHNICAL INSTITUTE
CHICAGO • TORONTO

You run a punch press, drive a tractor, work at a gas station. Or, maybe you can make home repairs, wire an electric appliance, or tune your car. You work with your hands. So did Thomas Edison and many other famous men. Artists, engineers, surgeons—all "work with their hands"—and so do Electronics Technicians! So, by all means, be proud of your "hand skills!"

DeVry Tech readily prepares men who use their hands for good-paying careers in the fast-growing Electronics field by sending 16 shipments of quality parts for building their own valuable test equipment. They work over 300 projects with these parts while they learn important basic theory. They learn in spare time at home, or in our well-equipped training centers in Chicago or Toronto. Many earn money part time repairing TV and radio sets while still training! When they finish, we help them get started.

NO ADVANCED EDUCATION NEEDED!

DeVry Covers What You'll Need to Know

2 FREE Booklets

Send coupon TODAY!



If you can understand clearly-written instructions, work with equipment, run training movies in your home, you surely can train for a profitable future in Electronics. ACT NOW to find out. Send for two fact-filled booklets that have helped so many men get started toward the kind of careers they wanted.

DeVRY TECHNICAL INSTITUTE
4141 Belmont Ave., Chicago 41, Ill., Dept. RE10Q

Please give me your two FREE booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel." Also, include details on how to prepare for a career in one or more branches of Electronics.

Name _____ Age _____

Please Print

Street _____ Apt. _____

City _____ Zone _____ State _____

Check here if you face military service.



Canadian residents address: DeVry Tech of Canada, Ltd.
2072 970 Lawrence Avenue West, Toronto 19, Ontario

✓ Check THEN SELL THE COMPLETE ROHN LINE FOR BIGGER-BY-FAR PROFITS!


In addition to one-stop shopping, the full line of ROHN Towers and accessories mean more sales! **Check and see!**

- ✓ **The Most Complete Line**—The complete ROHN line of towers, masts, roof towers and accessories means you get everything you need from one dependable source!
- ✓ **Proven, Advanced Design**—Revolutionary self-supporting, guyed, and "Fold-Over" towers with "Magic Triangle" and "Zig-Zag" tower construction are proven designs that have outlasted all others.
- ✓ **Highest Quality**—Only the finest materials are used. Everyone knows you can trust ROHN products for quality and performance.
- ✓ **Foremost in Service**—The ONLY manufacturer with complete coast-to-coast service... instant and dependable service—when you need it—wherever you are.
- ✓ **More Exclusive Sales Features**—Hot-dipped galvanized after fabrication, complete accessories, exclusive and advanced designs—bring you more profits!
- ✓ **Universal Customer Acceptance**—Thousands of installations prove the ROHN line is FIRST in customer acceptance. More profits for you because you're selling the line that moves best.

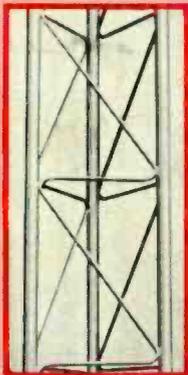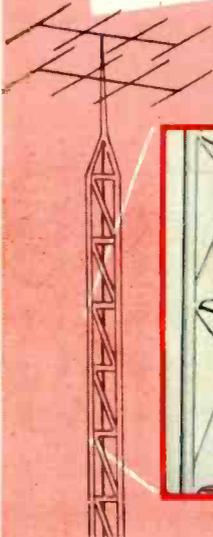The Full Line of ROHN Towers Fills Your Every Need!




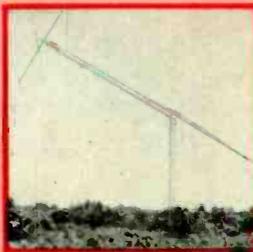ROHN TV TOWERS—The finest available for television reception. Install the No. 25 (illustrated) with amazing "zig-zag" design, self-supporting to 50 feet or, when properly guyed, to 280 feet. Or sell the popular No. 6 tower with the famous "Magic Triangle." Both are fully **HOT-DIPPED GALVANIZED THROUGHOUT AFTER FABRICATION** and come in handy 10 foot sections.




ROHN "FOLD-OVER" TOWERS—Specially designed to "fold-over" so the amateur radio operator can do his work on the ground. In sizes to handle all amateur antenna needs, ROHN "Fold-Over" Towers have won highest acclaim for design, performance and dependability.

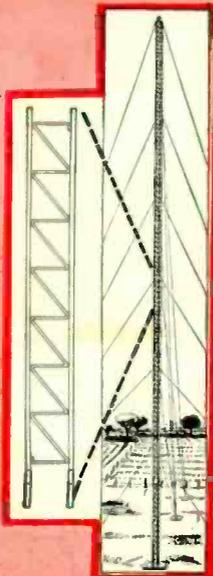ROHN COMMUNICATION TOWERS—Rugged, sturdy towers to meet EVERY communication requirement. Illustrated is the new and now available No. 55. Available are self-supporting towers to 150 feet... 7 full lines of towers in all for guyed heights up to 630 feet! All are **HOT-DIPPED GALVANIZED** after fabrication.



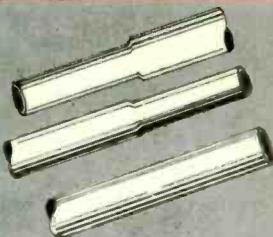
The Finest in Masts, Tubing & Accessories



Tubing—Just what you need. Six-inch expanded or swaged end, both $\frac{1}{2}$ " taper to form a solid locking joint. High carbon steel. The $\frac{1}{4}$ " tubing is available in 16 or 18 gauge, and in 5 and 10 ft. lengths; in $\frac{1}{2}$ ", in 16 gauge, with expanded or plain end, and 10 ft. lengths.



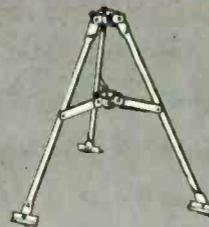Telescoping Masts—Unexcelled in design, structure and sales appeal. All popular sizes, heights and weights—in the exact specifications that are demanded today.



Roof Towers—A big profit item—very popular and easily shipped. Heights of 10, 5, 3, and $2\frac{1}{2}$ feet, ideal to use. **ALL HOT-DIPPED GALVANIZED.**

Shop quick and easy... shop the complete ROHN line of towers and accessories for bigger profits.

ROHN Manufacturing Company

6718 West Plank Rd.
Peoria, Illinois

BE SURE TO MAIL THIS COUPON NOW

ROHN Manufacturing Company
6718 West Plank Rd.
Peoria, Illinois

Send me complete literature on the following ROHN Products:

TV Towers Amateur Towers
 Communication Towers ROHN Accessories

Name _____
Firm _____
Address _____
City _____ State _____

Announcing a \$3.05 Pre-Publication Saving on This Long-Needed...

INTERNATIONAL DICTIONARY OF APPLIED MATHEMATICS

At Last! Over 8,000 Math Applications, Methods, Terms, Now in One 1,215-Page, Quick-Reference Book!

HERE'S an important achievement — the first comprehensive single volume that brings together for every use, defined and explained, the terms and methods of application of mathematics to 32 great fields of science and engineering.

This massive *International Dictionary of Applied Mathematics* contains some 8,165 entries. All those basic definitions and methods from pure mathematics, as well as from science and engineering, so necessary to an understanding of the mathematical applications are included. Each term is so clearly defined that many listings take up half a column, some require a page or more. Equations are included and their derivations explained.

World-Famous Specialists in Their Fields Make This Book Unique as a Reference

From the United States and abroad, noted mathematicians, physicists, chemists and engineers have prepared each entry to ensure authoritative selection and most careful presentation covering these fields:

- Acoustical Engineering
- Acoustics
- Astronomy
- Automatic Control
- Differential Geometry
- Electromagnetic Theory
- Mechanics
- Network Topology
- Nuclear Science
- Optics
- Quantum Mechanics
- Relativity
- Spectroscopy and Interpretation of Spectra
- Strength of Materials
- Chemical and Physical Thermodynamics
- Vector Analysis
- Aerodynamics and Hydrodynamics
- Atomic Structure
- Chemistry
- Elasticity
- General Mathematics
- Molecular Structure
- Nuclear Engineering
- Numerical Analysis
- Probability and Statistics
- Relativistic Quantum Mechanics
- Solid State Physics and Chemistry
- Statistical Mechanics

Structural Analysis and Design
Engineering Thermodynamics
Tensor Analysis
Visco-Elasticity and Plasticity

In this dictionary you will find those concepts and approaches which are most widely used in applied mathematics and which prove most fruitful in their results. Every article is *cross-referenced*: the section on "Hole Theory," for example, mentions Dirac equation. This is in bold type to refer you to its listing for a more complete understanding of the entire subject. A number of the articles in applied mathematics, especially in numerical analysis, refer you to the great 4-page entry on methods of computing eigenvalues and eigenvectors of matrices.

Important Foreign Language Indices

You bridge language barriers to pursue original reading by means of the four — German, Russian, French, Spanish — foreign language indices in this big book. Helpfully lists all terms with their English equivalents.


Every scientist, every engineer, every student, teacher, researcher needs this book. Whether you're checking data, looking for methods of application, interpolating an equation, writing a paper, clarifying technical articles — this book will give you the answers you need quickly, correctly, without wasted time or effort.

Pre-Publication Offer

A work of this scope (1,215 pages, 315 illustrations) would ordinarily sell for \$35 or more. However, the publishers plan an unusually large first printing to bring the retail price down to \$25.00. To build up this first printing, we are accepting advance reservations now. In return for helping us increase this printing's size, we will send you the Dictionary at the special pre-publication price of only \$21.95.

Send No Money

When the *International Dictionary of Applied Mathematics* comes off the press, a copy will be sent to you at the pre-publication price of only \$21.95. Simply fill out and mail reservation certificate at right. Browse through it, use it for *ten days free*. Then, if you're not convinced it will be the most used reference work on your desk, return it and owe nothing. Mail certificate today to: **D. Van Nostrand Company, Inc., Dept. 1810A, 120 Alexander Street, Princeton, N. J. (Established 1848).**

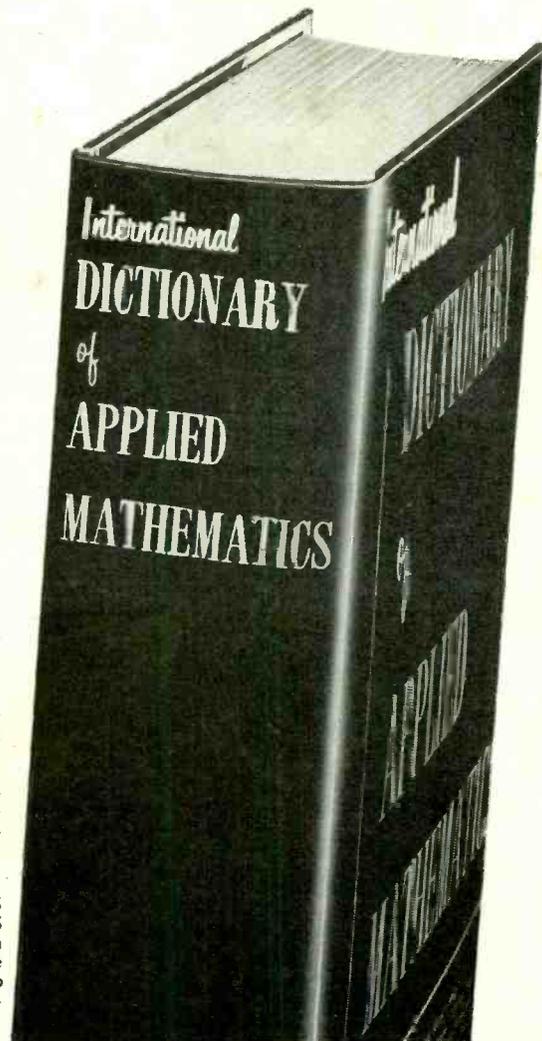

RESERVATION CERTIFICATE: SAVE \$3.05

D. Van Nostrand Company, Inc., Dept. 1810A
120 Alexander Street, Princeton, N. J.

Please send me, as soon as it is published, the *International Dictionary of Applied Mathematics*. If, after looking it over for 10 days, I am not delighted, I'll return it and owe nothing. Otherwise I will remit \$5.95, plus small shipping charge, and \$4.00 a month for 4 months.

Name.....
(please print)

Address.....

City..... Zone..... State.....

SAVE! Enclose \$21.95 with this certificate and shipping costs will be prepaid. Money-back guarantee.

(In Canada: 25 Hollinger Rd., Toronto 16. Prices slightly higher.)
Foreign and A.P.O. — please remit \$21.95 with reservation.

TAX DEDUCTIBLE if used in your work!

AMPHENOL TV PRODUCTS

help you serve your market better!

ANTENNAS

Complete line of VHF, UHF, VHF/UHF and FM antennas. Famous Inline (re-issue U.S. Pat. 23,273) is considered by impartial authorities as the finest broadband VHF antenna ever built.

ACCESSORIES


Antenna or set couplers, arrestors, other important products—all carefully engineered to highest quality standards.

TWIN LEAD


Both receiving and transmitting types are made by AMPHENOL, including the "hottest" twin lead on the market—AMPHENOL MARINE CORE, super low-loss Polyfoam.

COAXIAL CABLES

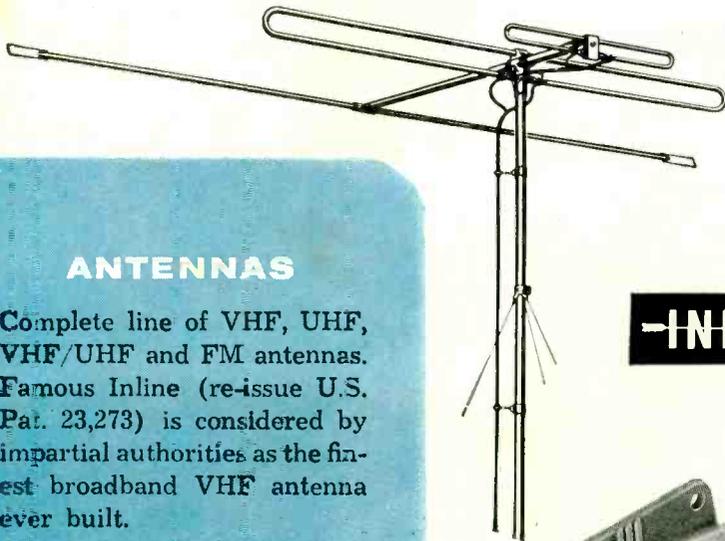AMPHENOL's Cable-bility is famous: More types of RG-/U (Polyethylene and Teflon), more experienced engineering, most modern production facilities.



—INLINE*

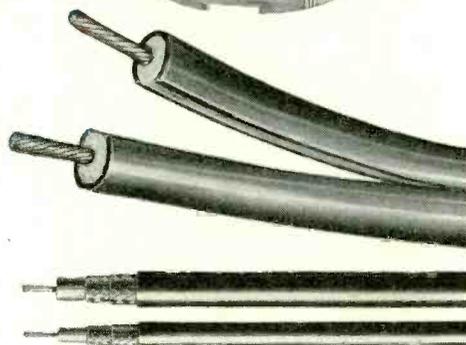

stock the finest—stock

AMPHENOL!

AMPHENOL

DISTRIBUTOR DIVISION
BROADVIEW, ILLINOIS

Amphenol-Borg Electronics Corporation

NEWS BRIEFS (Continued from page 6)

signals do not go above ground. The main value of the system lies in the fact that it is very difficult to jam. It can be used as an emergency means of communications. In a war, the enemy could not listen in (the expected maximum range is 100 miles).

Russian Artificial Hand

A man with an artificial hand "powered by bioelectricity generated in his own arm muscles" was presented to delegates of the First International Congress for Automatic Control, held in Moscow. The man wrote: "Welcome Congress Delegates" on a conference room blackboard in legible handwriting.

A paper presented on the subject by Soviet Professor Abram Kobrin-ski gave credit to Professor Norbert Wiener's work on bioelectrics 12 years ago. Dr. Wiener, of the Massachusetts Institute of Technology, said he was pleased that the Russians had developed "a bioelectrical artificial limb based on transistorized amplification of currents generated by the human body."

Reflecting Ring to Orbit Earth?

A plan to ring the earth with billions of tiny antennas is to be tested by the Air Force. Each antenna will be about half as thick as a human hair. Their length will depend on the frequencies to be used.

The ring will be used to relay signals from point to point by reflecting them off the ring in a manner similar to bouncing signals off the Project Echo balloon.

It is planned to place a small number of antennas in orbit by a vehicle with a different main mission. The vehicle may be launched within a month or two.

One objection to the plan is that the ring might block signals used in other space projects.

The ring would not be as likely to be damaged by meteorites or space debris as would balloons or "active" (receiver-amplifier) satellites.

Electronic Elevators Direct Passengers

"Talking elevators" installed at the Hess department store in Allentown, Pa., not only tell customers what they may find on the various floors, but also give instructions to help the passengers preserve their own safety and improve elevator service.

Completely electronic in operation, down to the pushbutton that summons the car, the elevators have a capacitance-operated door-safety device that detects a person in the way and opens the doors again to let him get in. If the passenger lingers, the elevator addresses him: "Kindly step back in the car, so that service may continue." After repeating the message a few times, if the passenger is still obstructing the entrance,

RADIO-ELECTRONICS

**do you know
what an FCC License**

Really Can
do for you in electronics


1. If you want to get into electronics . . . ?

2. If you are now employed in electronics . . . ?

See what this leading employer **Burroughs Corporation** has to say:

"An FCC License is a job asset . . .

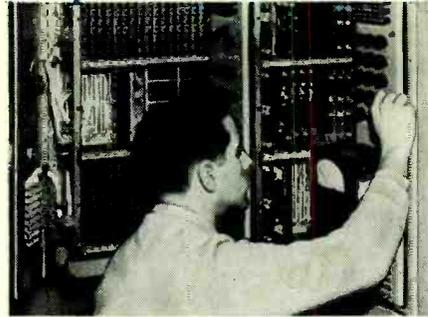to any man looking to enhance his career in the field of electronics. At Burroughs Corporation, a licensed man is well regarded because an FCC license attests to his knowledge of electronic theory. The licensed man at Burroughs will be called upon to handle many challenging assignments."



Employers are good judges of the value of an FCC License.

Cleveland Institute

announces a

New and Dynamic Technician Training Program

**in Computers, Servo Mechanisms,
Magnetic Amplifiers and others**

Other advanced fields covered include Basic Math, A. C. Circuit Analysis, Pulse Circuitry, Color TV, Radar, Advanced Measuring Techniques, Industrial Electronics, Instrumentation, Automation, Radio Telemetry. Send for information today.

Accredited by the National Home Study Council

Cleveland Institute of Electronics
Desk RE-46B

4900 Euclid Avenue

Cleveland 3, Ohio

GET ALL 3 VALUABLE BOOKLETS



free!

JUST MAIL THE
COUPON BELOW

Cleveland Institute of Electronics
Desk RE-46B, 4900 Euclid Avenue, Cleveland 3, Ohio

Please send Free Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below.

- | | |
|---|---|
| <input type="checkbox"/> Military | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing | <input type="checkbox"/> Telephone Company |
| <input type="checkbox"/> Amateur Radio | <input type="checkbox"/> Other |

In what kind of work are you now engaged? _____

In what branch of Electronics are you interested? _____

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

RE46B





BRIGHT NEW VIEW

for Multi-set TV-FM
Home Operation...




...and a
Bright Profit Outlook for YOU with

NEW JERROLD HSA-43

Amplified 3 SET COUPLER

Here's a new precision-perfected amplifier that provides 5 DB min. gain across all TV-FM channels on two outputs and no loss in the third output. Housed in a rugged, compact and handsome case. The HSA-43 features single tube operation (6DJ8), A.C. interlock and no-strip twin lead terminals. Its excellent isolation and match prevents set interaction and ghosting. IDEAL FOR FEEDING ONE FM AND TWO TV SETS FROM THE SAME ANTENNA.

\$29.95 list

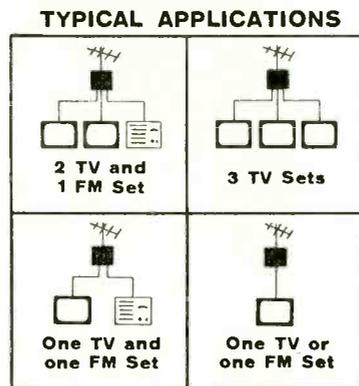

Write Jerrold today for full details on this new Profit Outlook!



ELECTRONICS CORPORATION, Distributor Sales Division
Dept. IDS-83, Philadelphia 32, Pa.

Jerrold Electronics (Canada) Limited, Toronto

Export Representative: CBS International, New York 22, N.Y.

LEADER AND LARGEST MANUFACTURER OF TV DISTRIBUTION SYSTEM EQUIPMENT

NEWS BRIEFS (Continued)

the elevator registers mild annoyance by starting a buzzer while continuing to urge the obstructor out of the way, and the doors close slowly but politely, nudging the customer into (or out of) the car. This capacitance system is considered superior to photocell methods of controlling doors, since it acts only if the customer is close to the door's edge. It also protects the smallest child, since the whole edge of the door, from ankle to shoulder height, forms part of the sensing element.

FM Increasing

FM stations are developing faster than AM stations, according to the latest count. Of course, AM stations still outnumber the FM's (3,484 AM's, 741 FM's), but percentage-wise, FM is ahead.

From 1958 to 1959, the number of operating FM stations increased from 571 to 677 (19% based on 1958 figures), while in the same period AM stations increased from 3,318 to 3,456 (4%).

In the period from Jan. 1 to June 30 of this year, 64 new FM stations went on the air (an increase of approximately 10% in just half a year), while 28 AM stations went on the air (approximately 1% in half a year).

And Now—Underwater Stereo

Submerged stereo in a swimming pool was heard for what is believed the first time in a joint demonstration by three audio companies at the famed Grossinger resort in New York State. Records were played through a dual 65-watt stereo amplifier to two specially designed underwater speakers. Bathers reported that the sound could be heard underwater across the whole pool.

Three companies took part in the demonstration of stereo sound, which was also carried on in more conventional style in a special listening room at the resort. Bogen-Presto supplied the amplifiers, University the special MM2-UW underwater speakers and United Audio the Dual stereo record changer.

Underwater Distance Record

Underwater explosions set off near Australia were picked up by Columbia University's Seismic and SOFAR (Sound Fixing And Ranging) station in Bermuda. The sound waves traveled 12,000 miles in 3 hours and 43 minutes.

The shots—weighing 50 pounds—were fired in a deep channel off southern Australia by the Vema, Columbia's research vessel. There were three of them, spaced 5 minutes apart.


John I. Ewing (staff member and brother of Dr. Maurice Ewing, director of Columbia's Lamont Geological Observatory, Palisades, N. Y.) said recording the shots was remarkable

(Continued on page 16)

ALLIED value-packed 1961

444-PAGE ELECTRONICS CATALOG

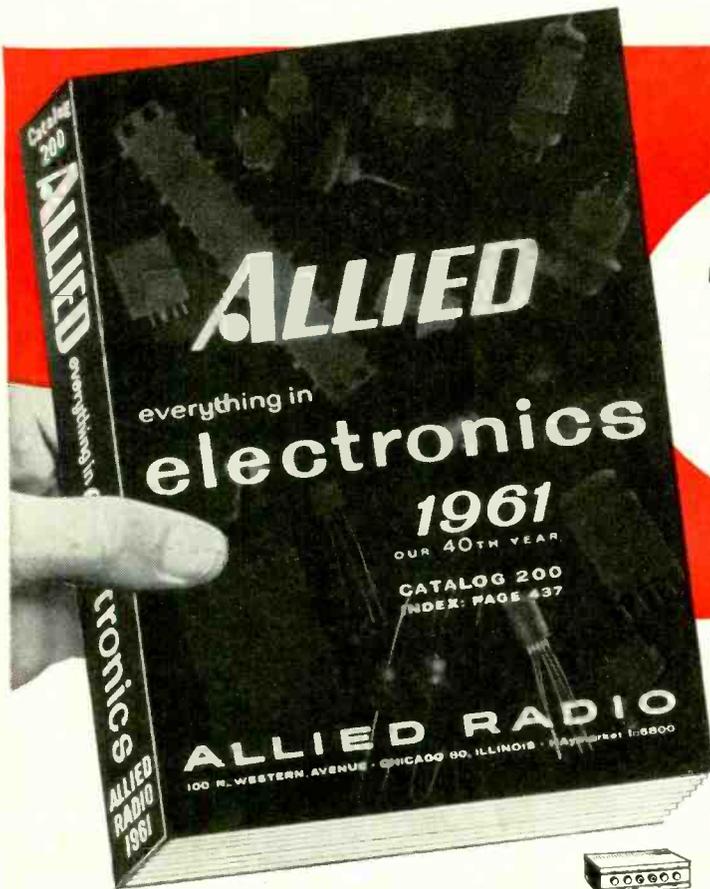including products available only from Allied



complete
up-to-date

free
send for it today!

SAVE MOST ON EVERYTHING IN ELECTRONICS

- Newest Stereo Hi-Fi Systems—Everything in Hi-Fi Components
- Money-Saving, Build-Your-Own KNIGHT-KITS® for Every Need
- Best Buys in Recorders & Supplies
- Newest Public Address Systems, Paging and Intercom Equipment
- Amateur Receivers, Transmitters, and Station Gear
- Citizen's Band 2-Way Radio
- Test and Laboratory Instruments
- TV Tubes, Antennas, Accessories
- Huge Listings of Parts, Tubes, Transistors, Tools, Books



BUY ON EASIEST TERMS ONLY \$2 DOWN

Yes, only \$2 down on orders up to \$50; only \$5 down on orders up to \$200; only \$10 down over \$200. Up to 24 months to pay.

ALLIED Exclusives:

MONEY-SAVING KNIGHT-KITS®—truly the very best in build-your-own electronic equipment—designed to save you money, easiest to assemble—the only kits offered with Free Inspection Privilege. See the complete selection of Stereo hi-fi kits, Hobbyist kits, Test Instrument and Amateur kits. KNIGHT-KITS are an exclusive ALLIED product.

KNIGHT® STEREO HI-FI—comparable to the best in quality and performance, yet priced far lower in cost. Select super-value KNIGHT components or complete systems and save most. Also see the largest selection of famous-name hi-fi components and money-saving ALLIED-recommended hi-fi systems.

ALLIED RADIO

our 40th year **SATISFACTION GUARANTEED
OR YOUR MONEY BACK**

World's Largest Electronic Supply House

free the most complete
electronics catalog!

ALLIED RADIO, Dept. 2-K
100 N. Western Ave., Chicago 80, Ill.

Send FREE 1961 ALLIED Catalog.

Name _____

Address _____

City _____ Zone _____ State _____



2 great SPRAGUE DIFILM[®] tubulars

are tops in their field . . . take your choice!


For maximum reliability
and performance
under toughest conditions

SPRAGUE DIFILM[®] BLACK BEAUTY[®]



For extremely small
size and exact
original replacement

SPRAGUE DIFILM[®] ORANGE DROP[®]

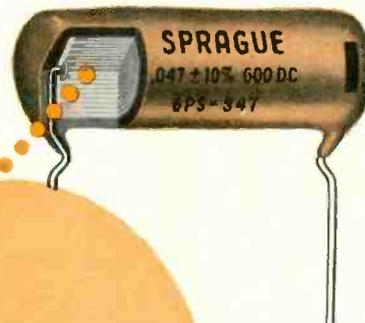

Sprague Black Beauty tubulars are missile-type capacitors. Actually, they are low cost versions of the famous Sprague capacitors now being used in every modern military missile. Where positive reliability is important, make no mistake, use Black Beauty Difilm Molded Capacitors! You get the most for the least with Black Beauties!

Difilm Black Beauties are engineered to withstand the hottest temperatures to be found in TV or auto radio sets—in the most humid climates. Further, unlike straight polyester film tubulars, these capacitors operate in a 105°C environment—without derating!

Black Beauty tubulars are tough units, too—no fragile shell to break—you can't damage them in soldering. For your convenience, every capacitor is marked twice . . . no need to twist capacitor around to read rating.

The heart of these Sprague Difilm Capacitors can't be beat! It's a dual dielectric combination of Mylar[®] polyester film and special capacitor tissue—resulting in capacitors which are superior to all other comparable tubulars. Sprague's rock-hard solid HCX[®] impregnant fills voids and pin holes in the film. Difilm capacitors have high insulation resistance, low power factor, and excellent capacitance stability and retrace under temperature cycling!

Sprague Difilm "Orange Drops" are a "must" for your service kit where only an exact replacement will fit. They are the perfect replacement for dipped capacitors now used by leading manufacturers in many popular television receivers. And when a dipped tubular is called for, you'll find that Orange Drops outperform all others, safeguarding your work and reputation for quality service.

Orange Drops are specially designed for easiest possible installation. Radial leads are crimped to assure neat mounting parallel to printed wiring boards . . . extremely small size makes them fit handily in tight spots. They'll beat heat and humidity because the solid, rock-hard capacitor section, double-dipped in bright orange epoxy resin, is well protected against moisture. A perfect team-mate for Black Beauty.

±10% CAPACITANCE TOLERANCE IS STANDARD AT NO EXTRA COST

Difilm Black Beauty and Difilm Orange Drops are packaged in sturdy, reusable rigid plastic Kleer-Pak[®] boxes. Your distributor is stocked in all the popular ratings. Order some today. You can count on Difilm.

SPRAGUE[®]
THE MARK OF RELIABILITY

MAKE MORE MONEY



TRAIN FOR ELECTRONICS . . .

In RESIDENT CLASSES

Grantham *resident* schools are located in four major cities—Hollywood, Seattle, Kansas City, and Washington, D. C. Regularly scheduled classes in F. C. C. license preparation are offered at all locations. New *day* classes begin every three months, and new *evening* classes begin four times a year. The day classes meet 5 days a week and prepare you for a first class F. C. C. license in 12 weeks. The evening classes meet 3 nights a week and prepare you for a first class license in 20 weeks. For more information about the Grantham resident schools, indicate in the coupon the city of your choice and then mail the coupon to the School's home office in Hollywood, Calif. Free details will be mailed to you promptly.

Through HOME STUDY

Grantham training is the easy way to learn more quickly—to prepare more thoroughly—for F. C. C. examinations. And your first class license is the quick, easy way to prove to your employer that you are worth more money.

This correspondence course is directed toward two major objectives—(1) to *teach* you a great deal about electronics, and (2) to prepare you to *pass* all of the F. C. C. examinations required for a first class commercial operator's license. We teach you step by step and have you practice with FCC-type tests which you send to the school for grading and comment. You prepare for your F. C. C. examinations under the watchful direction of an instructor who is especially qualified in this field.

GET your first class commercial F. C. C. LICENSE

To get ahead in electronics—first, you need the proper training; then, you need “proof” of your knowledge. Your first class commercial F. C. C. license is a “diploma” in communications electronics, awarded by the U. S. Government when you pass certain examinations. This diploma is recognized by employers. Grantham School of Electronics specializes in preparing you to earn this diploma.

Grantham training is offered in resident classes or by correspondence. Our **free** booklet gives complete details. If you are interested in preparing for your F. C. C. license, mail the coupon below to the School's home office at 1505 N. Western Ave., Hollywood 27, California—the address given in the coupon—and our free booklet will be mailed to you promptly. No charge—no obligation.


Get your First Class Commercial F. C. C. License by training at

GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD SEATTLE KANSAS CITY WASHINGTON

This booklet **FREE!**

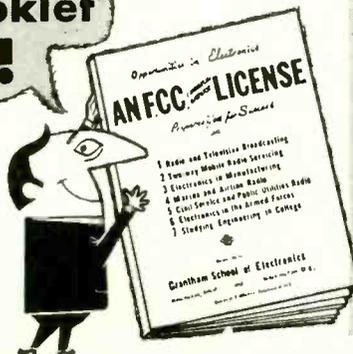This free booklet gives details of our training and explains what an F. C. C. license can do for your future. Send for your copy today.



for **FREE** Booklet **CLIP COUPON** and mail in envelope or paste on postal card.

for **FREE** Booklet **CLIP COUPON** and mail in envelope or paste on postal card.

To: GRANTHAM SCHOOL OF ELECTRONICS
1505 N. Western Ave., Hollywood 27, Calif.

Please send me your free booklet telling how I can get my commercial F. C. C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Kansas City classes, Q4-R
 Hollywood classes, Seattle classes, Washington classes

**NOW!
one Britener
for ALL
series string
heaters**

New **Perma-Power** unit
guards against
picture tube
damage
caused by
excessive power
boost



MODEL C412 VU-BRITE
110° Button Base—Series
ALL Filament Voltages
\$1.75 net

MODEL C403 VU-BRITE
Duodecal Base—Series
ALL Filament Voltages
\$1.12 net

MODEL C411 VU-BRITE
110° Button Base—Parallel
ALL Filament Voltages
\$1.49 net

MODEL C311 UNIVERSAL
110° Button Base—6.3 Volts
Series or Parallel
\$2.98 net

all available from your
Perma-Power Distributor

When you're trying to brighten a 110° button base picture tube, watch those series heaters! Many of the newer sets have controlled warm-up filaments with ratings of 2.34 and 2.68 volts. (Older sets are usually rated at 6.3 volts.)

These new tubes use finer heater wire and closer element spacings—which makes them more efficient, but more fragile. *Too much power boost will "blow" these low voltage filaments!*

On these newer tubes, you can not safely use a Britener made for older sets. But you can use the new Perma-Power Model C412 on these and older style tubes. For the first time, here's one Britener for all 110° button base series string heaters—the only Britener that works properly for 2.34, 2.68, 4.70, 6.3 and 8.4 volt filaments! No switching necessary—no adjustments required.

The Model C412 Vu-Brite is one of four new Perma-Power Briteners, all engineered to fit properly and work properly. Without excessive inventory, Perma-Power—and only Perma-Power—can now assure you of complete coverage—a Britener that's right for every picture tube in general use today.

Perma-Power COMPANY

3106 NORTH ELSTON AVENUE • CHICAGO 18, ILLINOIS


LOOK what's coming along in Radio-Electronics future issues

- Build a 6DZ7 Amplifier
- Servicing TV Distribution Systems
- Zener Diodes Simplified
- Simple Transistor Gain Checker
- Professional Picture Tube Testers
- Electronic Timer for Guns
- Technicians—Avoid Legal Pitfalls!


On sale September 27

Last chance to subscribe now
at these low rates

1 year \$4	2 years \$7	3 years \$10
On October 31st rates go up to		
1 year \$5	2 years \$9	3 years \$12

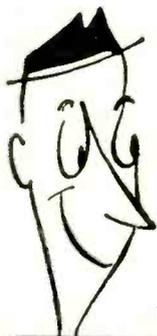

154 West 14th Street

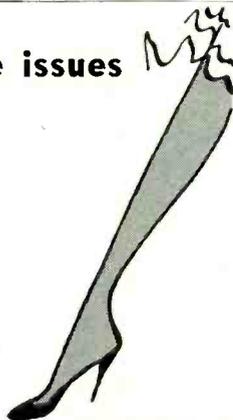

New York 11, N.Y.

both because of the distance and the small probability that there is a clear path between the firing point and Bermuda.

"Sound waves traveling through the water between those two points may have to feel their way around islands and through shallow areas," he said. The sound traveled near the surface in the south and then dropped to depths of around 2,600 feet near the Equator. It followed a Great-Circle path past the Cape of Good Hope.

The instruments in Bermuda are located in water about 2,600 feet deep. Scientists believe that an underwater atomic blast could be picked up if it was fired near the sound channel.

Party Lines Next?

Two widely separated computers can now exchange information with each other over a telephone system at the rate of 150 characters or numbers per second, the International Business Machines Corp. reported recently. The system requires a pair of IBM 1009 data-transmission units, one at each end of the line.

Information from a core storage unit, punched cards or magnetic tape may be sent.

Language Labs for Schools

The Board of Education plans to install language laboratories in 38 schools in New York City beginning this fall. The labs will be placed in 27 high schools, 7 junior high schools and 4 elementary schools.

In a language laboratory, the student listens to model speech through a pair of headphones and replies to or imitates it. His reply (and the master) are recorded on tape. By playing back the tape, the student can compare his answers with the master and see how well he is doing. Each student is in an acoustically treated booth. The instructor can monitor any of the booths (for more details, see "Electronic Labs Help Teach Languages," RADIO-ELECTRONICS, June, 1960, page 33).

Telephone Service Expanded

Two-way air-to-ground telephone service is now available in the New York, Washington and Pittsburgh areas. The service was previously available only on an experimental basis in the air corridor between Chicago and Detroit.

In making an air-to-ground call, a passenger pushes a button on the phone. An "aviation" switchboard operator answers via the nearest base station. The customer gives the operator the number he wants and she makes the connection.

Ground-to-air calls are made by dialing the telephone company and asking for the aviation operator in the area where the plane is known to be flying.


Equipment will be furnished to

ANOTHER FACTOR IN
"INTEGRITY IN MUSIC"

does your
amplifier
CHANGE
the
music?



FOR INTEGRITY IN MUSIC . . .

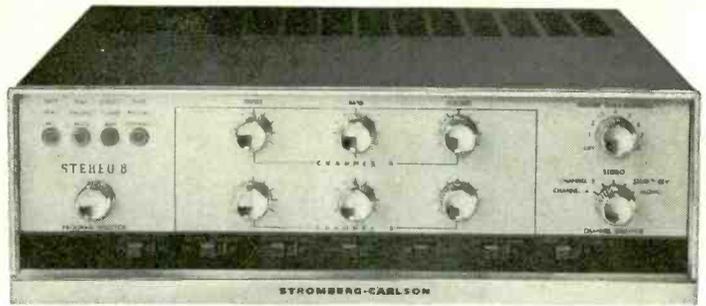

ASR-8-80 Stereo Amplifier

When your amplifier adds or subtracts not one nuance of sound . . . you enjoy Integrity in Music. This concept of pure, unadulterated reproduction has been manifested most recently in Stromberg-Carlson's 8-80 stereo amplifier. Its combination of features, performance and price—its control versatility and listening quality—make it the most unusual value ever offered in high fidelity.

ASR-8-80 Specifications: *Power:* 64 watts (2-32-watt channels); *Response:* 20-20,000 cps ± 0.9 db; *Distortion:* Harmonic: less than 0.6% at full output; IM: less than 1% at program level; Hum & Noise: down 70 db. A plus B output for center speaker system; *Price:* \$199.95, Zone 1, gold and white finish, top cover extra.


Another amplifier featuring Stromberg-Carlson integrity is the dual channel ASR-433. Each channel provides 12 watts of exceptionally clean, balanced power. The control and performance are excellent.

The deliberately conservative specifications include: frequency response 20-20,000 cps; harmonic distortion less than 1% at full output; IM distortion less than 1% at program level; hum and noise 63 db down. Top cover available in gold and white or black and brushed chrome. ASR-433 . . . \$129.95.*

Stromberg-Carlson now offers 16 equipment cabinets in a wide variety of styles and finishes. They are designed to house complete Stromberg-Carlson stereo component systems and are factory assembled. They reproduce as faithfully as separately mounted components because of a unique mounting method that isolates the speaker systems from the other sensitive components.

See your dealer (in Yellow Pages) or write for a complete component and cabinet catalog to: 1478-010 North Goodman St., Rochester 3, New York.

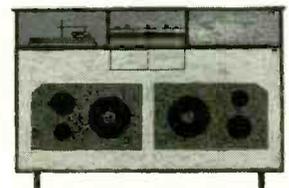*Prices audiophile net, Zone 1, less base, subject to change.



"There is nothing finer than a Stromberg-Carlson"

STROMBERG-CARLSON
A DIVISION OF **GENERAL DYNAMICS**

private planes and airlines by the participating telephone companies. The 450-mc band will be used.

Ground stations, antennas and other equipment are operated by the New York Telephone Co., Chesapeake & Potomac Telephone Co., Bell Telephone Co. of Pennsylvania, Michigan Bell Telephone Co. and Illinois Bell Telephone Co.

Calendar of Events—October 1960

National Communication Symposium, Oct. 3-5, Hotel Utica and Utica Municipal Auditorium, Utica, N.Y.

Conference on Radio-Interference Reduction, Oct. 4-6, Chicago, Ill.

EIA Conference on Value Engineering, Oct. 5-6, Disneyland Hotel, Anaheim, Calif.

National Electronics Conference, Oct. 10-12, Hotel Sherman, Chicago.

The Southwest Area Reliability Training Conference, Oct. 10-15, Lake Texoma Lodge, Kingston, Okla.

Audio Engineering Society 1960 Convention and Exhibit, Hotel New Yorker, New York City, Oct. 11-14.

More than 80 papers, on subjects ranging from psychoacoustics to public address, will be read and discussed in the 13 technical sessions of the Audio Engineering Society convention at the Hotel New Yorker, Oct. 11-14. An exhibit of audio equipment will be included.

Engineering Writing and Speech Symposium, Oct. 13-14, Bismarck Hotel, Chicago, Ill.

Symposium on Adaptive Control Systems, Oct. 17-19, Garden City Hotel, Garden City, N.Y.

Symposium on Space Navigation, Oct. 19-21, Deshler-Hilton Hotel, Columbus, Ohio.

International Congress & Exhibition for Instrumentation and Automation, Oct. 19-26, Dusseldorf, Germany.

East Coast Aeronautical and Navigational Electronics Conference, Oct. 24-26, Lord Baltimore Hotel, Baltimore, Md.

Conference on Non-Linear Magnetics and Magnetic Amplifiers, Oct. 26-28, Bellvue-Stratford Hotel, Philadelphia, Pa.

1960 Electron Devices Meeting, Oct. 27-28, Shoreham Hotel, Wash. D.C.

Conference on Electronic Techniques in Medicine and Biology, Oct. 31-Nov. 2, Sheraton Park Hotel, Washington, D.C.

IRE-EIA Radio Fall Meeting, Oct. 31-Nov. 2, Syracuse Hotel, Syracuse, N.Y.

Conference on Magnetism & Magnetic Materials, Nov. 14-17, New Yorker Hotel, New York, N.Y.

Mid-America Electronics Conference (MAECON), Nov. 15-16, Muehlebach Hotel, Kansas City, Mo.

Northeast Research & Engineering Meeting (NEREM), Nov. 15-17, Commonwealth Armory and Sheraton Plaza Hotel, Boston, Mass.

Northwest Hi-Fi Show, Nov. 25-27, Leamington Hotel, Minneapolis, Minn.


EIA Winter Conference, Nov. 29-Dec. 1, Fairmont Hotel, San Francisco, Calif.

US Cites Inventor

Dr. Otto Halpern was awarded the Department of Defense medal for distinguished public service for an invention that helps ships and planes evade enemy radar detection.

Last year, Dr. Halpern accepted \$340,000 from the Government in settlement of his 18-year fight for a patent. The Government had refused a patent, saying that it would make public the details of an invention that was still a military secret.

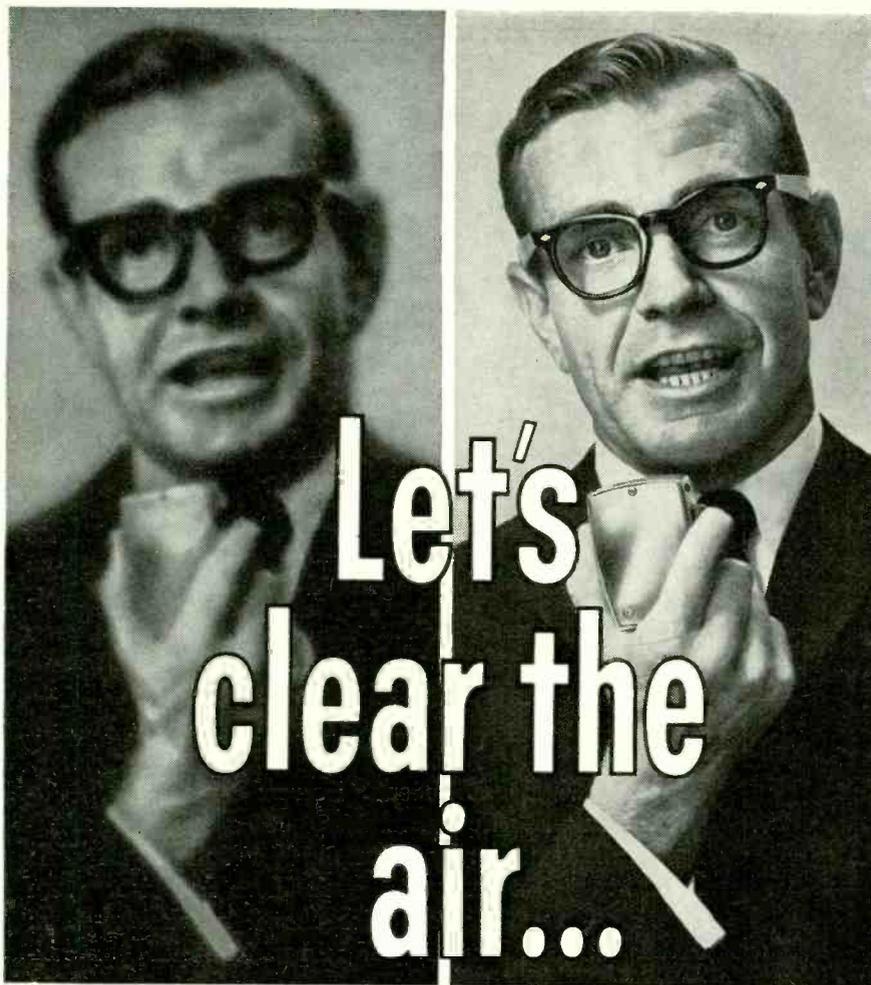The invention is a rubberlike material containing metallic flakes that absorb radar waves. **END**



Let's
clear the
air...

WITH VOCALINE 4-CHANNEL COMMAIRE ED-27M CITIZENS BAND RADIO

Ranked first for
dependability
distance • clarity



Also available in single channel model — Commaire ED-27M — proven as the world's finest-performing class D Citizens Band Radio! Only \$179.50 each, list.

\$189.50
each, list.

Citizens band radio can be no more effective than the equipment you use! In fact, no judgment on the subject can be valid until one has heard the type of performance possible when properly engineered; truly superior equipment is utilized. Example: the Vocaline Commaire ED-27M, the finest citizens band radio available anywhere today! The difference between Vocaline Commaire ED-27M and ordinary Citizens band radios can be as substantial as the difference between the two photos above. For distance, reliability, flexibility and uniform clarity on the entire 22 channel citizens band . . . you have only to hear the Commaire to convince yourself that this is the

one unit that is unmatched by any other in its class.

Specifications and features: Finished to pass U.S. Navy 500 hour salt spray test! "Silent-Aire" squelch with exclusive noise suppression. Double conversion superheterodyne single crystal receiver—accepted as the finest. Transistorized power supply. 5 watts input — 3 watts output. 6 and 12 VDC — 115 VAC. Only 5 1/4" x 9 1/4" x 8 1/4".

VOCALINE
COMPANY OF AMERICA
123 Coulter Street
Old Saybrook, Conn.



Send complete literature to:
Name _____
Address _____
City _____ Zone _____ State _____


Learn RADIO, TELEVISION AND ELECTRONICS by Practicing at Home in Your Spare Time

At No Extra Cost you get specially developed Electronic Training Kits for practical experience. Shop and laboratory practice at home make learning easier, interesting, faster. You do not need a high school diploma or previous experience.

Increasing Demand for Trained Men


This is the Electronics age. Men with Electronic know-how are in demand. They enjoy high pay and growing opportunities for advancement. Satellites, Radar, Automation in Industry, Missiles, Rockets, Planes, Stereo, TV, Radio, Two

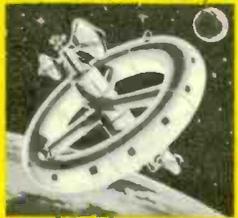Way Communications for transportation are a few of the fantastic developments in the fast growing Electronics industry. If you are not completely satisfied with your work; if you are doubtful about your future, investigate Electronics.



High Pay, Prestige, Bright Future

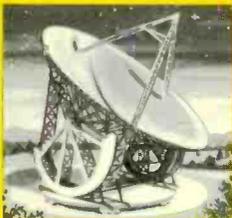What branch of Electronics interests you? Thousands of successful NRI graduates prove that NRI's learn-by-practice method is the way to success. You start in your chosen career way ahead of the man who only learns from books. You do not need to give up your job. You do not need to go away to school. You learn at home, get practical knowledge from training kits NRI provides.




Train With the Leader

NRI is the world's oldest and largest home study Electronics school. You benefit from the experience NRI has gained from training men for 45 years. NRI offers you proven courses of home study in Electronics; Principles, Practices and Maintenance—Radio Television Communications—Radio Television Servicing.

Start Soon to Earn More

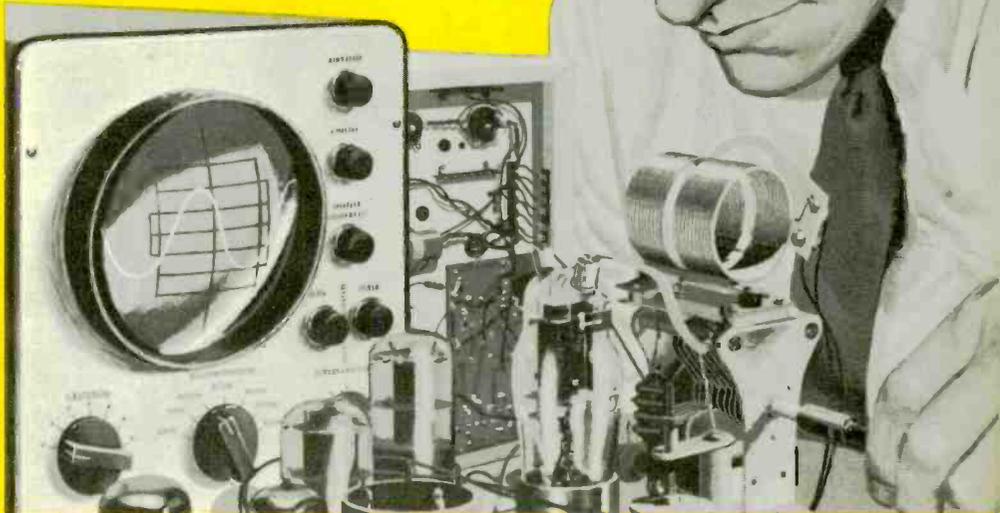Soon after enrolling NRI shows you how to apply your knowledge to earn extra money doing Electronics repairs or servicing Radio and Television sets for friends and neighbors. Take the first step toward success now. Find out what NRI offers you. Mail the postage-free card. No obligation. Cost of NRI training is low. Monthly payment plan available. NATIONAL RADIO INSTITUTE, Washington 16, D.C.



NRI Has Trained Thousands for Success



"I get over twice the salary I made before enrolling. NRI training gave me a thorough understanding." H. ATKINSON, Austin, Tex.



"I started with station CjIC, now in charge of sound effects for CBC. NRI opened doors to greater opportunity for me." F. TUDOR, Toronto, Ontario



"Averaged \$150 a month spare time before I graduated. Now have my own full time business and employ 2 men." F. W. COX, Hollywood, Cal.

NEW COURSE IN ELECTRONICS TURN PAGE

Cut Out and Mail—No Stamp Needed

64-PAGE CATALOG FREE

No Salesman will call. (Please PRINT) Z


Name _____ Age _____

Address _____

City _____ Zone _____ State _____

OLDEST & LARGEST HOME STUDY RADIO-TV SCHOOL
National Radio Institute
WASHINGTON 16, D. C.

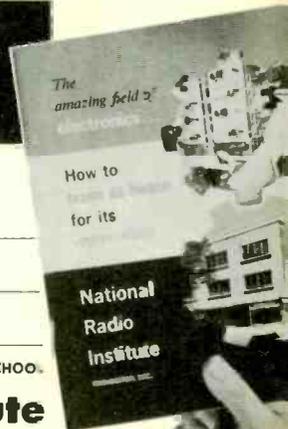ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL





JOB COUNSELORS ADVISE LEARN ELECTRONICS

NEW Home Study Course in **ELECTRONICS** Principles-Practices-Maintenance **NOW READY**

This is the Electronic Age. Electronic equipment is already being used to count and control flow of liquids, solids, gases. Electronics is employed to search for oil, make surveys, control traffic, machine complex parts and in atomic installations. Military uses of Electronics are great and expanding rapidly. In business, Automation with Electronics plays an important part, prepares payrolls, calculates engineering formulas.

Learn More to Earn More

Now, to meet the growing demand for trained Electronic Technicians NRI has developed a comprehensive, complete course in Electronics Principles, Practices, Maintenance. This training stresses fundamentals. It is a course specially prepared for beginners and for Technicians. You get both theory and practical experience in an interesting, exciting way.

Ten Special Training Kits Give Practical Experience

You get practical experience with Thyatron Tube circuits, Multivibrators, build a D'Arsonval type Vacuum Tube Voltmeter (Kit 2); work and experiment with pentode tubes, selenium resistors, oscillators, transistors, magnetic amplifiers; and get practical experience in telemetry circuits as used in earth satellites, digital and analog computers (Kit 9).

NRI—Oldest and Largest School

Wishing for success won't bring success. You must act. Get FREE 64-page Catalog from America's oldest and largest home study Electronic-Radio-Television school. It gives facts, opportunities in Industrial and Military Electronics careers, also shows what you learn, tells about NRI's other courses in Radio Television Servicing and Radio Television Communications. Monthly payments plan. Mail Postage Free Card for 64-page Catalog.
NATIONAL RADIO INSTITUTE, Washington 16, D.C.



SPECIAL TRAINING KITS NO EXTRA COST

PRACTICE WITH
17" TV RECEIVER

PRACTICE WITH
LOW POWER TRANSMITTER

PRACTICE WITH ULTRA
HIGH FREQUENCY OSCILLATOR

PRACTICE WITH
D'ARSONVAL TYPE VOLTMETER

PRACTICE WITH
AC-DC RECEIVER

← **SEE OTHER SIDE** →

FIRST CLASS
Permit No. 20-R
(Sec. 34.9, P. L. & R.)
Washington, D.C.

BUSINESS REPLY CARD

No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY

National Radio Institute
3939 Wisconsin Avenue
Washington 16, D.C.

**POSTAGE FREE CARD
MAIL NOW**

Correspondence



SUPPRESSORS NEEDED

Dear Editor:

With regard to the article by F. H. Frantz, "Interference—Causes, Remedies and Locations," in the July issue, several points should be clarified.

The reactance alone of a capacitor at a given frequency will not establish its attenuation characteristics. The degree of attenuation can be made to vary 12 to 15 db by adjusting the capacitor's lead length.

With regard to automotive suppression, it will almost invariably be necessary to install 10,000-ohm suppressors in series with each spark plug. Further, it should be noted that the generator can be suppressed at the armature. Bypassing the field coil may prove quite costly.

L. G. JAKUBEC, JR.

Reseda, Calif.

WHERE TO GET THEM

Dear Editor:

In at least two issues of RADIO-ELECTRONICS within the past year, the question has been raised as to the availability of spare parts for Natco projectors. Parts are available from several sources: First of all, Natco, 4401 W. North Ave., Chicago 39, Ill. Also parts for some models are available from Sears, Roebuck. Some models were marketed under the Sears Tower brand.

If the drive chain needs replacing, it is available from DeVry Corp., 4141 Belmont Ave., Chicago 41, Ill. DeVry's projector uses a drive chain that is almost identical with Natco's. If gears are needed, they can be cast or ground by Boston Gear Works, Quincy 71, Mass. LaVezzi Machine Works, 4635 W. Lake St., Chicago 44, Ill., is a good bet for reproduction of parts for almost all projectors.

The only electrical trouble that is likely to occur would be the 6V6 oscillator coil (for the excitor lamp) burning out. Simply use a universal oscillator coil available from most parts houses.

HERSHEL D. PARKER

Gaisden, Ala.

IMPROVING DETECTOR

Dear Editor:

Looking over the July issue of RADIO-ELECTRONICS, I came across the article "Underwater Metal Detector" by Mr. Richardson. This looks like a good thing for the small-boat people. It seems to me that R2 could be eliminated and, at the same time, increase the sensitivity. Since R2 is in parallel with the battery, it is also an extra drain. Remove R2

(Continued on page 26)

NEW! Kit-Pak Container®
Opens to a self-contained work area you can use anywhere.

NEW! Part-Chart®
Speeds your work. All parts are mounted on Kit-Pak cover in numerical sequence. And every part meets H.H. Scott's tough test standards.

NEW! Ez-A-Lign System®
Requires no extra equipment. You align this tuner using the meter on the tuner itself! All needed alignment tools are included.

NEW! Pre-Stripped, Pre-Cut Wire
Every piece of wire is included. And each piece is pre-cut to proper length, stripped and tinned.

LT-10 Laboratory Tuner Specifications
• Usable (IHFM) sensitivity 2.5µV
• Signal: noise ratio 60 db below 100% mod. • Harmonic distortion 0.8% • Drift 0.02% • Frequency response 30 cps—15Kc ± 1 db. (IHFM measurements are made only in the range 30-15,000 cps. The LT-10 actually has far wider frequency range than shown here.)

The new LT-10 Tuner Kit will work as well as factory units, yet it can be aligned without expensive equipment. You align this tuner using the meter on the tuner itself. All needed alignment tools are included. This is the first kit to use H. H. Scott's Wide-Band circuitry. This results in greater selectivity and sensitivity than possible with any other kit on the market.

The exclusive H. H. Scott silver plated front end is completely pre-assembled and pre-aligned. All parts are mounted in sequence of assembly. All wires are pre-cut to proper length and stripped. Parts such as tube sockets and terminal strips are already riveted to the chassis. Here's a kit that's fun to build, and that you'll be proud to own.


* Prices slightly higher west of Rockies. Accessory case extra.



WORLD'S LEADING COMPONENT MANUFACTURER

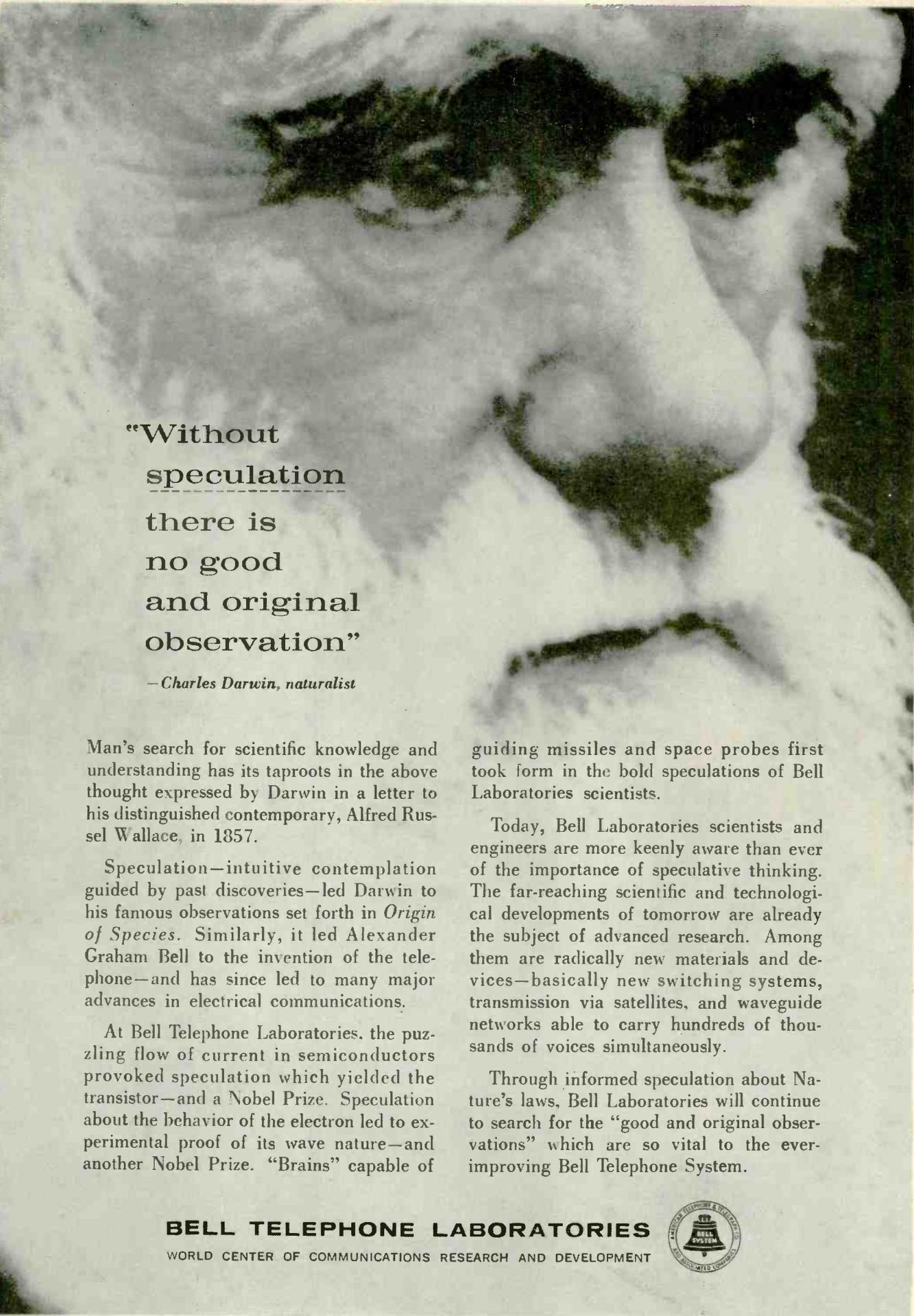H. H. SCOTT INC., 111 Powdermill Rd., Maynard, Mass.
Please send me FREE the following booklets: RE-10
 Colorful new 1961 catalog and hi fi guide.
 Complete technical specification sheets on your new products, including your new LT-10 Tuner Kit.

Name _____
Address _____
City _____ Zone _____ State _____
Export: Telesco International Corporation, 36 West 40th Street, N. Y. C.



**“Without
speculation
there is
no good
and original
observation”**

—Charles Darwin, naturalist

Man’s search for scientific knowledge and understanding has its taproots in the above thought expressed by Darwin in a letter to his distinguished contemporary, Alfred Russel Wallace, in 1857.

Speculation—intuitive contemplation guided by past discoveries—led Darwin to his famous observations set forth in *Origin of Species*. Similarly, it led Alexander Graham Bell to the invention of the telephone—and has since led to many major advances in electrical communications.

At Bell Telephone Laboratories, the puzzling flow of current in semiconductors provoked speculation which yielded the transistor—and a Nobel Prize. Speculation about the behavior of the electron led to experimental proof of its wave nature—and another Nobel Prize. “Brains” capable of

guiding missiles and space probes first took form in the bold speculations of Bell Laboratories scientists.

Today, Bell Laboratories scientists and engineers are more keenly aware than ever of the importance of speculative thinking. The far-reaching scientific and technological developments of tomorrow are already the subject of advanced research. Among them are radically new materials and devices—basically new switching systems, transmission via satellites, and waveguide networks able to carry hundreds of thousands of voices simultaneously.

Through informed speculation about Nature’s laws, Bell Laboratories will continue to search for the “good and original observations” which are so vital to the ever-improving Bell Telephone System.

BELL TELEPHONE LABORATORIES

WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT



The greatest beauty of
Thorens famous quality...
you can afford it!

No need to hesitate, you *can* afford Thorens famous quality. You *can* have music as it's meant to be heard. You *can* relax with Thorens *unique* one year guarantee. There's a Thorens model that fits handily into any budget.

Whether you know a lot or a little about high-fidelity equipment, you'll particularly enjoy the courteous and knowledgeable way a Thorens franchised dealer *earns* your confidence. Each Thorens dealer is carefully selected for knowledge, ability and integrity. They'll make buying *your* Thorens almost as much fun as owning it. Shop around this page for a few of the outstanding features and then stop in and *see* all of them for yourself. O.S

Guaranteed for one full year. Sold only through carefully selected franchised dealers.



THORENS

SWISS MADE PRODUCTS

MUSIC BOXES • HI-FI COMPONENTS
SPRING-POWERED SHAVERS • LIGHTERS
New Hyde Park, N. Y.

MATCHLESS!

TD-124. All four speeds. Plays any record. Easy-to-use lighted strobe sets exact speed for best musical reproduction. Completely silent. Many more exclusive features... only \$99.95 net.



TD-184

TD-124



MORE ECONOMICAL!

TD-134. The finest 4-speed manual turntable you can buy. Includes tone arm. Elimination of semi-automatic feature saves you another \$15. You can also save up to \$30 on the tone arm. Look at TD-134... only \$59.95 net.

MARVELOUS!

TD-184. Includes tone arm and simple dialing system that lets you select records and start turntable. All 4 speeds. Save \$20 on turntable, up to \$30 on tone arm. Look at TD-184... only \$75.00 net.

TD-134



TDK-101

MOST ECONOMICAL!

TDK-101. You can assemble this Thorens turntable yourself. The superb quality of the components makes all your work worthwhile. Look at Thorens TDK-101... only \$47.50 net.

“THE CITATION SOUND”

“... FOR THE SAKE

“Over and above the details of design and performance, we felt that the Citation group bore eloquent witness to the one vital aspect of audio that for so many of us has elevated high fidelity from a casual hobby to a lifelong interest: the earnest attempt to reach an ideal—not for the sake of technical showmanship—but for the sake of music and our demanding love of it.”

A truly remarkable commentary about a truly remarkable group of products—the Citation Kits by Harman-Kardon.

Mr. Reid's eloquent tribute to Citation is one of many extraordinary reviews of these magnificent instruments. We are proud to present a brief collection of excerpts from Citation reviews written by outstanding audio critics.

“When we first heard the Citations our immediate reaction was that one listened through the amplifier system clear back to the original performance, and that the finer nuances of tone shading stood out clearly and distinctly for the first time . . . bass is clear and firm, and for the first time we noted that the low frequency end appeared to be present even at low volumes without the need for the usual bass boost . . . The kit is a joy to construct.” C. G. McProud, Editor, Audio Magazine

“The unit which we checked after having built the kit, is the best of all power amplifiers that we have tested over the past years . . . none have had distortion that was quite as low as we found in this new Citation II . . . the amplifier should provide the very finest in hi-fi stereo reproduction . . .”

William Stocklin, Editor, Electronics World


PRESENTING THE 1961 CITATION LINE FEATURING



**The CITATION I
Stereophonic Preamplifier
Control Center**

Here is the first brilliant expression of the advanced design concepts which sparked the new Citation Kit line—the incomparable Citation I, Stereophonic Preamplifier Control Center. The Citation I consists essentially of a group of circuit blocks termed “active” and “passive” networks. The “active” networks are treated as one or two stage amplification units, flat over an extremely wide frequency range and each is surrounded with a feedback loop. This results in levels of distortion so low as to prove unmeasurable. The “passive” networks provide precise equalization with no phase shift.

The use of professional step type tone controls overcome the limitations of continuously variable potentiometers. Each position on a step control is engineered to perform a specific function—which is absolutely repeatable when necessary. The many professional features and philosophy of design expressed in Citation I permit the development of a preamplifier that provides absolute control over any program material without imparting any coloration of its own. Citation I—\$159.95. Factory Wired—\$249.95. Walnut Enclosure, Model WC1—\$29.95.

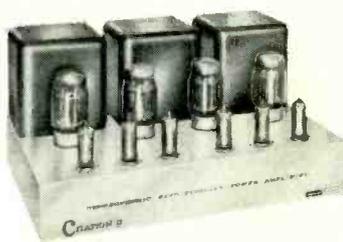

**The CITATION II
120 Watt Stereophonic
Power Amplifier**

This remarkable instrument has a peak power output of 260 watts and will reproduce frequencies as low as 5 cycles virtually without phase shift, and frequencies as high as 100,000 cycles without any evidence of instability or ringing. At normal listening levels the only measurable distortion comes from the laboratory test equipment.

Video output pentodes are used in all low level stages for exceptional wide frequency response and low distortion. Multiple feedback loops for increased degree of usable feedback (30 db overall) result in lower distortion without sacrificing stability. The power supply consists of four silicon diode rectifiers, choke, heavy duty electrolytics and potted power transformer for precise regulation and long life. The use of rigid component boards, heavy duty components, special Cable Harness assure the kit builder that the unit he constructs will be the exact duplicate of the factory built instrument. Because of its absolute reliability and exceptional specifications the Citation II has gained widespread acceptance among professionals as a laboratory standard. The Citation II—\$159.95. Factory Wired—\$229.95. Metal Enclosure, Model AC11—\$7.95.



**The CITATION III
Professional FM Tuner**

Citation III is the world's most sensitive tuner. But more important—it offers sound quality never before achieved in an FM tuner. Now, for the first time Harman-Kardon has made it possible for the kit builder to construct a completely professional tuner without reliance upon external equipment. To meet the special requirements of Citation III, a new FM cartridge was developed which embodies most of the critical tuner elements in one compact unit. The cartridge is completely assembled at the factory, totally shielded and perfectly aligned—eliminating the difficult problems of IF alignment, oscillator adjustment and lead definition.

The Citation III's front end employs the revolutionary NuVlster tube which furnishes the lowest noise figure and highest sensitivity permitted by the state of the art. A two-stage audio circuit patterned after the Citation II is employed. By utilizing a high degree of feedback and providing a frequency response three octaves above and below the range of normal hearing, the Citation sound quality is maintained and phase shift is eliminated. The Citation III is styled in charcoal brown and gold to match all the other Citation instruments. Citation III—\$149.95. Factory Wired—\$229.95. Walnut Enclosure, Model WC1—\$29.95.

OF MUSIC AND OUR DEMANDING LOVE OF IT."

"Its listening quality is superb, and not easily described in terms of laboratory measurements. Listening is the ultimate test and a required one for full appreciation of Citation . . . there is a solidity, combined with a total ease and lack of irritation which sets this amplifier apart . . . The more one listens to the Citation II, the more pleasing its sound becomes . . . Anyone who will settle for nothing less than the finest will be well advised to look into the Citation II."

Hirsch-Houck Labs, High Fidelity Magazine

"At this writing, the most impressive of amplifier kits is without doubt the new Citation line of Harman-Kardon . . . their design, circuitry, acoustic results and even the manner of their packaging set a new high in amplifier construction and performance, kit or no."

Norman Eisenberg, Saturday Review

"Specifications published by the manufacturer are so astonishing that our sister publication, Electronics World, has subjected them to critical examination and found performance wholly consistent with claims . . . Nothing can faze it . . . we have heard this particular amplifier loaded with four big speaker systems glide over the steepest orchestral hurdles without the slightest trace of strain . . . The realism of the virtually distortion-free music was nothing less than startling. Our initial amazement soon gave way to an easy, relaxed enjoyment that was sustained for hours without a trace of that tension known as "listening fatigue." Here was a sound system that fulfilled the most difficult of all high fidelity requirements: to provide an awareness only of music, and oblivion of technicalities."

Herbert Reid—Hi Fi Stereo Review


THE NEW CITATION III PROFESSIONAL FM TUNER



**The CITATION IV
Stereophonic Preamplifier
Control Center**

The new Citation IV is a compact stereophonic preamplifier designed in the best Citation tradition. It offers performance and features rivaled only by Citation I. Square wave tracings at 20 and 20,000 cycles reveal no difference between the response of the Citation IV and the signal generator.

The Citation IV provides separate bass and treble tone controls for each channel which may be switched out of the circuit completely to eliminate phase shift and transient distortion inherent in all tone controls. D.C. on all heaters and the use of low noise resistors in critical places reduce thermal agitation and hum. A zero to infinity balance control allows complete cut-off for either speaker. Military type terminal boards make for rigid, professional appearance and facilitate construction. The control over program material provided by the new Citation IV enables the user to perfectly recreate every characteristic of the original performance. The Citation IV is handsomely styled in charcoal brown and brushed gold. The Citation IV — \$119.95. Factory Wired — \$189.95. Walnut Enclosure, WCI—\$29.95.

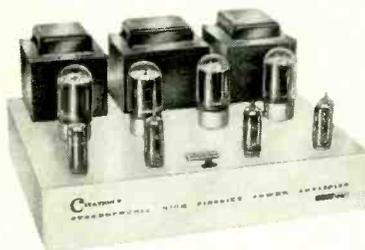

**The CITATION V
80 Watt Stereophonic
Power Amplifier**

The Citation V is a compact version of the powerful Citation II. Designed with the same lavish hand, it is conservatively rated at 40 watts RMS per channel with 95 watt peaks at less than 0.5% distortion.

The availability of rated power at the extreme ends of the frequency range enables the amplifier to effortlessly drive any of today's most inefficient speakers. It clips clean without breakup. The output stage consists of two 7581's per channel operating conservatively in a fixed bias, ultra-balance circuit. A bias meter is provided to statically and dynamically adjust each pair of output tubes. The power supply consists of four silicon diodes (hermetically sealed) and heavy duty electrolytics for excellent B+ regulation and long life. This results in instantaneous recovery time and superb transient response.

Here is an all new power amplifier which truly reflects The Citation approach to audio design: no compromise in quality regardless of cost. The Citation V is styled in charcoal brown and brushed gold. The Citation V — \$119.95. Factory Wired — \$179.95. Metal Enclosure, ACV—\$7.95.

CITATION KITS by

harman kardon


INCORPORATED
PLAINVIEW, NEW YORK

For complete information on the new Citation Kits, including reprints of independent laboratory test reports, write to: Dept. 100, Citation Kit Division, Harman-Kardon Inc., Plainview, New York.

All prices slightly higher in the West.

STEREO QUALITY SOARS TO NEW HEIGHTS...

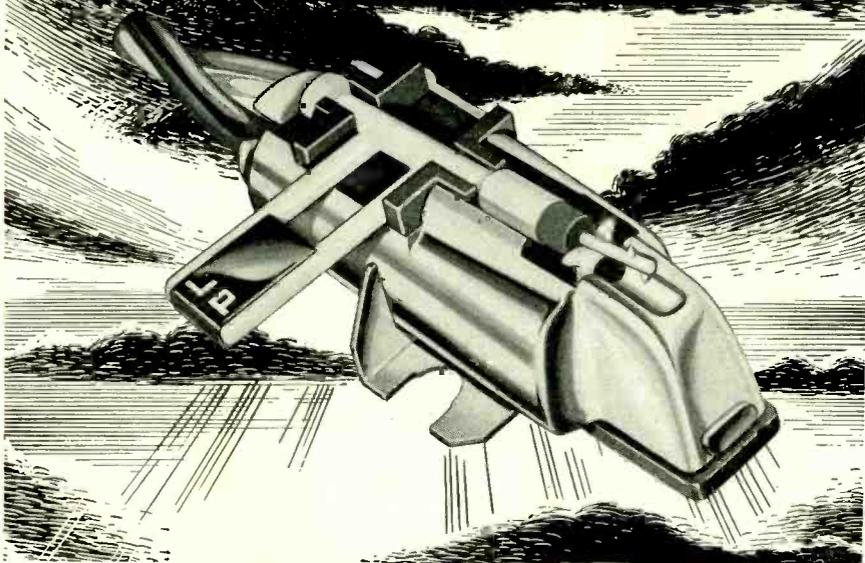Presenting the
finest ceramic stereo cartridge
ever perfected by Sonotone



THE "PROFESSIONAL QUALITY" 9T!

Now, the ceramic cartridge proved in independent A-B listening tests to perform as well as the highest-priced "professional" types. It's Sonotone's revolutionary new 9T. So superior, you can expect faithful reproduction from the most robust musical passages to the most subtle overtones. Sonotone's new 9T series stereo cartridge:

GUARANTEES performance equal to cartridges costing up to 3 times as much—as proven in A-B listening tests.

GUARANTEES highest compliance—allows major reduction of tracking force.

GUARANTEES more than adequate channel separation.

GUARANTEES crisp definition.

GUARANTEES superior, more compact mechanical design—including revolu-

tionary new needle design with instant "snap-in, snap-out" replacement needle feature and built-in jewel tip protector.

ELIMINATES distortion—incredibly flat response of ± 1 db from 20 to 17,000 cps—cuts listening fatigue.

ELIMINATES dust pile-up—at recent trade show the 9T ran 4 straight hours, collected no dust.

ELIMINATES most record groove noise or hiss—no "needle talk".

Imagine, the 9T boasts all these "professional" features...yet sells for less than half the price of the least expensive "professional" cartridge. Simplify your inventory...cut call-backs—increase sales and profits—with Sonotone's great new 9T cartridge...unsurpassed for performance—and for value.


LIST PRICE:	9T-S...\$16.50 (0.7-mil and 3-mil sapphires)	9T-S77...\$16.50 (Two 0.7-mil sapphires)	9T-SD...\$19.50 (Sapphire-Diamond)
-------------	---	---	---------------------------------------

Sonotone[®]

ELECTRONIC APPLICATIONS DIVISION, ELMSFORD, N. Y. DEPT. C2-100

IN CANADA, CONTACT ATLAS RADIO CORP., LTD., TORONTO

LEADING MAKERS OF

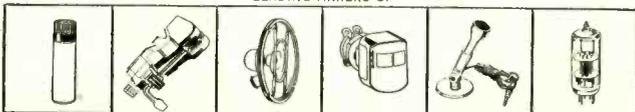

BAITERIES • CARTRIDGES • SPEAKERS • TAPE HEADS • MIKES • ELECTRONIC TUBES

CORRESPONDENCE (Continued from p. 21)

and connect the meter lead to the slider of R1.

On page 18 of the same issue, "Wanted: Less Confusion," Mr. Greenberg is sooooo right.

THOMAS L. BARTHOLOMEW
Washington, D. C.

METER LIMITATIONS

Dear Editor:

In the August issue, Robert G. Casey described a method of making an audio wattmeter from a vtvm. His method appears simple, but there are two limitations to be kept in mind when using the meter.

First, the method is good when working with sine waves only. This is a rarely encountered waveform in audio work (except when using a sine-wave generator for testing). Most vtvm's respond to either peak-to-peak voltage or to the average value of the waveform. The indicated rms voltage is correct only when the waveform is sinusoidal. For all other waveforms, the meter reading will probably be too high or too low. When the erroneous reading is squared to get the power, the error becomes relatively much greater.

Second, the suggested circuit makes use of the meter's 0-to-3-volt range. Here, most of the simple peak-responding meters become relatively inaccurate. For example, two Heath V-7A meters were calibrated to read correctly on sine waves above 6 volts. Both read about 14% low on a 1.4-volt rms sine wave and 14% high on a 2-volt (peak-to-peak) square wave.

Considering the above points, Mr. Casey's system will be quite satisfactory if it is restricted to sine-wave measurements and if a vtvm that is accurate on the low ranges is used. (The latter restriction will eliminate most of the simple peak-responding meters.)

KENNETH E. STONE

Iselin, N. J.

ELECTROSTATICS

Dear Editor:

In Norman Crowhurst's article "More Bass From Smaller Loudspeakers" (August, 1960), he makes certain statements concerning wide-range electrostatics which I believe are not completely fair.

"this new field is only beginning."

The truth of the matter is that Quad full-range units have been publicly demonstrated for more than 5 years and have been available for more than 3. It is true, of course, that competitive units will be introduced only this fall, but that does not subtract from the fact that the Quad has been available for some time.

"one way to use it is to just stand it by the wall, in which case the whole unit acts as its own air coupler."

Actually, the Quad works best away from walls and other room divisions which tend to upset frequency relationships, no matter what kind of speaker is used. The walls are no part of the

RADIO-ELECTRONICS

AT LAST!

RADIO-TV and ELECTRONICS TRAINING ... AT A PRICE YOU CAN AFFORD!



***21 INCH**
Receiver Kit included

Yes, this great course costs far less than any training of its kind given by other major schools! Radio-Television Training School will train you for a good job in Television or Industrial Electronics — AT HOME IN YOUR SPARE TIME.

Think of It—a complete training program including over 120 lessons, Fourteen Big Radio-Television Kits, Complete Color-TV Instruction, Unlimited Consultation Service . . . ALL at a really big saving to you. How can we do this? Write to us today . . . and find out!

And what's more — you can (if you wish)

OPEN YOUR OWN RTS-APPROVED AND FINANCED RADIO-TV SERVICE SHOP

We Want Many More Shops This Year


This 38 year old training organization — called RTS, that's Radio-Television Training School — wants to establish a string of Radio-TV Repair Shops in principal cities throughout the U. S. So far, a great many such shops are NOW IN BUSINESS AND PROSPERING. We are helping and training ambitious men to become future owners and operators of these shops in all areas.

FOR UNSKILLED INEXPERIENCED MEN ONLY — WE TRAIN YOU OUR WAY!

We must insist that the men we sign up be trained in Radio-TV Repair, Merchandising and Sales by our training methods—because WE KNOW the requirements of the industry. Therefore, we will TRAIN YOU . . . we will show you how to earn EXTRA CASH, during the first month or two of your training period. YOU KEEP YOUR PRESENT JOB. TRAINING TAKES PLACE IN YOUR OWN HOME, IN YOUR SPARE TIME!



YOU BUILD THESE AND OTHER UNITS!

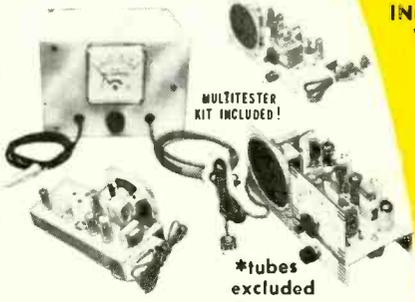


MULTITESTER KIT INCLUDED!

*tubes excluded

RADIO-TELEVISION TRAINING SCHOOL

815 E ROSECRANS AVENUE
LOS ANGELES 59, CALIFORNIA

Est. 1922

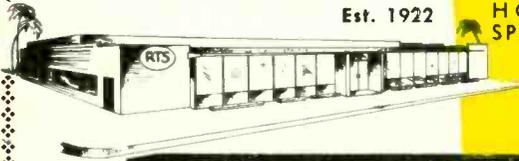

ACT NOW!


Get your free book on the **FAMOUS RTS BUSINESS PLAN** find out how you can open **A REPAIR SHOP OF YOUR OWN**

We supply and finance your equipment

When you are ready and qualified to operate one of our RTS-Approved TV Repair Shops **WE WILL SUPPLY AND FINANCE EVERY BIT OF EQUIPMENT YOU NEED TO GET STARTED** plus an inventory of parts and supplies. In other words we will stake you . . . **AN OFFER NEVER MADE BEFORE BY ANY TRAINING ORGANIZATION.** Under the RTS Business Plan you receive:

- | | |
|---|--|
| 1. An electric sign for the shop front. | 6. Plans for shop arrangement. |
| 2. Complete laboratory of test equipment. | 7. Instructions on how to go into business. |
| 3. Letterheads, calling cards, repair tickets, etc. | 8. Continuous consultation and help. |
| 4. Basic inventory of tubes, parts, supplies. | 9. The right to use RTS Seal of Approval, and the RTS Credo. |
| 5. Complete advertising and promotional material. | 10. The right to use the Famous Trade Mark |

ACCREDITED MEMBER

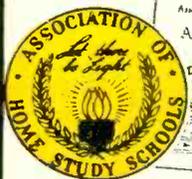

RTS' Membership in The Association of Home Study Schools is your assurance of Reliability, Integrity, and Quality of Training.

ALL THESE FREE!



CUT OUT AND MAIL — TODAY!

RADIO-TELEVISION TRAINING SCHOOL

815 EAST ROSECRANS AVENUE Dept. RE100
LOS ANGELES 59, CALIFORNIA

SEND ME FREE — all of these big opportunity books — "Good Jobs in TV-Electronics," "A Repair Shop of Your Own" and "Sample Lesson." I am interested in:

- Radio-Television Industrial Electronics (Automation)

Name _____ Age _____

Address _____

City & State _____

302

Mail This Coupon Now—No Salesman Will Call

Stancor. n.

Synonym for
quality and
dependability
in coils and
transformers

It makes good sense for you to choose replacement parts from the manufacturer who is the world's largest supplier of electronic transformers to the original equipment market. The complete Stancor line includes the unit you need, at the fine performance level you expect. For quality and dependability in transformers and coils, always specify Stancor.

The Stancor TV Guide

gives you always up-to-date replacement information—through regular mailings of loose-leaf pages direct to you from Stancor. Register with your distributor to get the Stancor TV Guide.

STANCOR

CHICAGO STANDARD TRANSFORMER CORPORATION
3501 WEST ADDISON STREET • CHICAGO 18, ILLINOIS

CORRESPONDENCE (Continued)

Quad transmission system. Indeed, the response, out of doors and hung in the air, is flat to at least 40 cycles—the only known speaker that does not require room reinforcement for flat bass.

"dramatically different impedance—high and capacitive."

The Quad impedance curve is essentially resistive—actually lying between 15 and 30 ohms between 40 and 8,000 cycles (falling above that frequency).

"something will have to be done about its directional effects."

If you will read Mr. Briggs' chapters on electrostatic loudspeakers (in *Loudspeakers*, the most recent edition), he points out that directionality is the same problem with electrostatics as with dynamics, no more, no less. The following generalizations must apply (no matter what kind the speaker) and may mean that the electrostatic is the answer.

An electrostatic can be designed with any dispersion angle required. Design parameters are infinitely variable. Any design is completely predictable, whereas the design of dynamic speakers must be a bit more empirical since masses and interactions are much less precise.

More important than the actual dispersion angle (theorists vary on the requirements) is what speaker engineers call "acoustic ratio"—the congruence of dispersion angles at all frequencies from deep bass to high treble. It can be shown, analytically, that only a full-range electrostatic can be designed for a "proper" loudspeaker-room relationship.

Interested parties can read about these matters in Mr. Peter Walker's articles on electrostatics in *Wireless World*, 1955.

IRVING M. FRIED, president
Electronics of City Line Center, Inc.
Philadelphia, Pa.

Mr. Crowhurst Comments

Mr. Crowhurst was asked to comment on the above. His remarks follow:

When I wrote the article, I anticipated that some manufacturer might write in and complain that I had not been fair. After all, one cannot find good reason to pronounce every competitive product better than the rest! But Mr. Fried's letter, about the *wide-range electrostatic* came as a surprise.

He complains of my remark that this is a new field, just beginning, yet acknowledges that there has been only the QUAD so far. The rest of my remarks, about change in proportions, as compared with dynamic, about different impedance (where he quotes only part of my sentence—the rest of it refers to adaptation to integration techniques, for which the electrostatic is basically well suited) and about tailoring the directional response, only serve to confirm this first remark to which he takes exception.

On placement, I did *not* recommend placing it against a wall. I am well aware that an open-backed unit such as the electrostatic is least likely to suffer interference effects if it is away from walls. But if Mr. Fried insists on his customers hanging QUADS in the air or leaving them in the middle of the room, I don't think he'll sell many. Far more people need to place the speaker against a wall. My comment was that it *can* be used that way.

Unfortunately some makers of dynamic units act as if wide-range electrostatics are a joke—they'll never work! It seems as if Mr. Fried adopts the reverse attitude and ignores any comparison with dynamics. Trying to convey the impression that his speaker—of whichever type—is the only one that works, does not help anyone. Articles like mine try to put things in perspective to enable the purchaser to judge realistically.

There is no disagreement between Mr. Briggs and myself on this subject. In particular, Mr. Briggs conducts thorough investigations and makes realistic observations, letting "the chips fall where they may." Doubtless Mr. Briggs, too, gets accused occasionally of being "unfair."—*Norman H. Crowhurst*

END

this is the "500th"

SAMS PHOTOFACT SET

500
SEPTEMBER - 1960

marking a milestone in the history of the Electronic Servicing Industry

- ★ over 20,000,000 PHOTOFACT Sets now In use
- ★ over 50,000 listings ... complete ... authoritative

THE WORLD'S FINEST TV-RADIO-ELECTRONICS SERVICE DATA

"Bonus" Features Now in PHOTOFACT Schematics At No Extra Cost

Following is a partial list of the more than 60 features now included:

- Voltage on schematic
- Wiremarks on schematic
- "Circuit Tracer" for printed boards
- Values of resistors and capacitors
- All tube types and tube data indicated
- Same numbers listed to parts list and printed
- Ratings of special components
- Warnings on up of resistors over "Wet"
- Call and identification terminal diagrams of color coded indicators
- Paper "Lamps" "Outlets"
- Total B + current
- Call resistance over one ohm
- Test points located
- Electrode location coding
- Cathode current for horizontal and vertical output tubes
- Screen current for horizontal output tube
- Tube ratings
- and many more.

INAUGURATING
A NEW SERVICE
 WITH THIS SET

NOW - keep current on new tube setup data for popular tube testers. See **TUBE TESTER DATA Folder** inside.

FOR CONTENTS OF THIS SET SEE "SERVICER" INSIDE

HOWARD W. SAMS & CO., INC. • Indianapolis 6, Indiana

PUBLISHED AND PRINTED IN U.S.A.

THIS IS PHOTOFACT SET NO. 500

truly a milestone in the history of the Electronic Servicing Industry

over **20,000,000** PHOTOFACT Sets are now in use the world over
 over **50,000** listings of TV, Radio and allied equipment are covered
 over **23,000** Service Technicians subscribe to every new PHOTOFACT Set
 over **75,000** Service Technicians refer to PHOTOFACT daily

PLAIN FACTS: PHOTOFACT owes its universal acceptance and success to its unquestioned ability to help *earn more money for any Service Technician.* The man

who owns a PHOTOFACT Service Data Library knows his customers' sets best. **HE EARNS MORE... HE RATES** with the public because he's **PHOTOFACT-EQUIPPED.**



**BE AMONG THE FIRST IN
 YOUR COMMUNITY TO DISPLAY
 THIS POWERFUL SYMBOL**

If you now own a PHOTOFACT Library or plan to own one, you can apply for membership in "PEET"—the first industry program to build truly effective public acceptance for the Service Technician who qualifies. Membership helps you win public respect and confidence, builds more business for you. Benefits cost you absolutely nothing if you qualify. Ask your Sams Distributor for the "PEET" details, or mail coupon today.

HOWARD W. SAMS & CO., INC.

OCTOBER, 1960

WRITE TODAY FOR VALUABLE INFORMATION

HOWARD W. SAMS & CO., INC.
 1724 E. 38th St., Indianapolis 6, Ind.

Send me full details on how I can qualify for membership in the "PEET" Program. Include details of Easy-Buy Plan and Free File Cabinet offer.

I'm a Service Technician full-time; part-time

My distributor is _____

Shop Name _____

Attn.: _____

Address _____

City _____ Zone _____ State _____


SELECT THE BLONDER-TONGUE TV/FM SYSTEM DESIGNED TO BRING IN THE BEST RECEPTION IN YOUR AREA

NEW BLONDER-TONGUE ALL-CHANNEL TV/FM AMPLIFIER MODEL HAB




Provides high gain ($23 \text{ db} \pm 1 \text{ db}$) on all VHF channels including the FM band. Ideal amplifier for home systems or pre-amplifier for large or small master systems. 69.50 list.

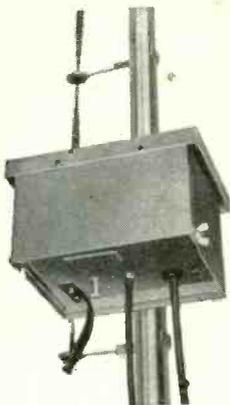NEW BLONDER-TONGUE SINGLE-CHANNEL ANTENNA MOUNTED TV AMPLIFIER MODEL CB






Enclosed in a weather-proof housing, this versatile performer can be used in the home as a pre-amp or booster to increase signal strength for a single weak channel, or in conjunction with other CB amplifiers to make an economical and powerful multi-channel system. 17 db gain, CH. 2-6; 15 db, CH. 7-13. 52.50 list.

NEW BLONDER-TONGUE B-24 POW-R BOOSTER

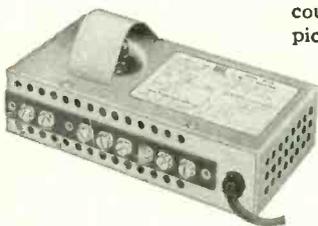

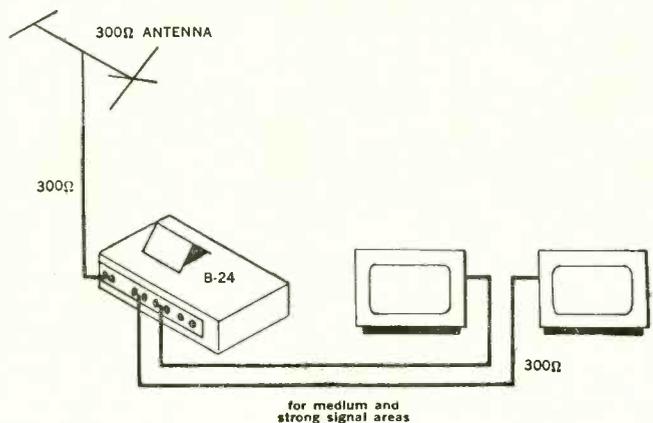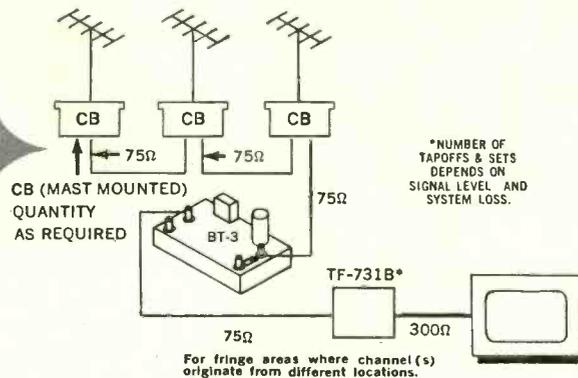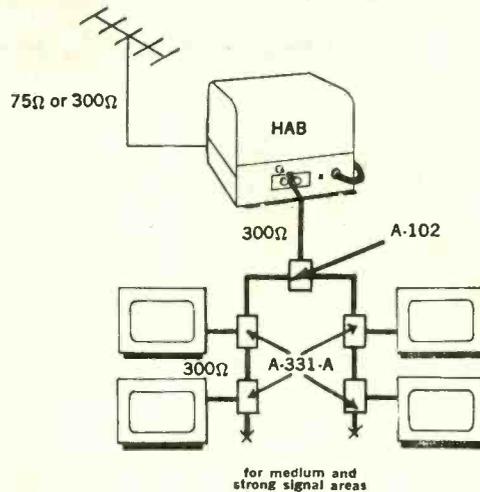Powerful booster or amplified coupler provides sharp, clear pictures on 1, 2 or more TV sets with only one antenna. 10 db gain as 1-set booster, 5 db gain per set as amplified 2-set coupler. No-loss 4-set distribution system with B-T A-104 4-set coupler. 24.95 list.



Available at parts distributors. For further information write Dept. RE-10
BLONDER-TONGUE LABORATORIES, INC.

9 Alling St., Newark 2, N. J.

Export: Morhan Export Corp., N. Y. 13, N. Y.

hi-fi components • UHF converters • master TV systems • industrial TV cameras • FM-AM radios



IF YOU LOVE TO CREATE... BUILD **EICO** KITS

In **STEREO** and

**Mono Hi-Fi...
the experts say
your Best Buy
is EICO**

Over 2 MILLION EICO instruments in use throughout the world. Add 5% in the West.



Stereo Amplifier-Preamplifier HF81†



Stereo Preamplifier HF85††



FM Tuner HFT90††
AM Tuner HFT94††
FM/AM Tuner HFT92††



100W Stereo Power Amplifier HF89
70W Stereo Power Amplifier HF87
28W Stereo Power Amplifier HF86



Stereo Integrated Amplifier AF4††



3-Way Speaker System HFS3
2-Way Bookshelf Speaker Systems
HFS5 and HFS1

NEW!



Stereo Automatic Changer/
Player 1007



- Exclusive advanced systematized engineering
 - Latest and finest quality parts
 - Exclusive "Beginner-Tested" easy step-by-step instructions
 - Exclusive TRIPLE quality control
 - Exclusive LIFETIME guarantee at nominal cost
- IN STOCK — Compare, then take home any EICO equipment — right "off the shelf" — from 1500 neighborhood EICO dealers throughout the U. S. & Canada, most of whom offer budget terms.

HF81 Stereo Amplifier-Preamplifier selects, amplifies, controls any stereo source & feeds it thru self-contained dual 14W amplifiers to a pair of speakers. Provides 28W monophonically. Ganged level controls, separate balance control, independent bass and treble controls for each channel. Identical Williamson-type, push-pull EL84 power amplifiers. "Excellent" — SATURDAY REVIEW. "Outstanding... extremely versatile." — ELECTRONICS WORLD. Kit \$69.95. Wired \$109.95. Incl. cover.

HF85 Stereo Preamplifier: Complete master stereo preamplifier-control unit, self-powered. Distortion borders on unmeasurable. Level, bass, & treble controls independent for each channel or ganged for both channels. Inputs for phono, tape head, mike, AM, FM, & FM-multiplex. One each auxiliary A & B input in each channel. "Extreme flexibility... a bargain." — HI-FI REVIEW. Kit \$39.95. Wired \$64.95. Incl. cover.

New HF89 100-Watt Stereo Power Amplifier: Dual 50W highest quality power amplifiers. 200W peak power output. Uses superlative ultralinear connected output transformers for undistorted response across the entire audio range at full power, assuring utmost clarity on full orchestra & organ. 60 db channel separation. IM distortion 0.5% at 100W; harmonic distortion less than 1% from 20-20,000 cps within 1 db of 100W. Kit \$99.50. Wired \$139.50.

HF87 70-Watt Stereo Power Amplifier. Dual 35W power amplifiers identical circuit-wise to the superb HF89, differing only in rating of the output transformers. IM distortion 1% at 70W; harmonic distortion less than 1% from 20-20,000 cps within 1 db of 70W. Kit \$74.95. Wired \$114.95.

HF86 28-Watt Stereo Power Amp. Flawless reproduction at modest price. Kit \$43.95. Wired \$74.95.

FM Tuner HFT90: Prewired, prealigned, temperature-compensated "front end" is drift-free. Prewired exclusive precision eye-tronic® traveling tuning indicator. Sensitivity: 1.5 uv for 20 db quieting; 2.5 uv for 30 db quieting, full limiting from 25 uv. IF bandwidth 260 kc at 6 db points. Both cathode follower & FM-multiplex stereo outputs, prevent obsolescence. Very low distortion. "One of the best buys in high fidelity kits." — AUDIOCRAFT. Kit \$39.95*. Wired \$65.95*. Cover \$3.95. *Less cover, F.E.T. incl.

AM Tuner HFT94: Matches HFT 90. Selects "hi-fi" wide (20-9000 cps @ -3 db) or weak-station narrow (20-5000 cps @ -3 db) bandpass. Tuned RF stage for high selectivity & sensitivity. Precision eye-tronic® tuning. "One of the best available." — HI-FI SYSTEMS. Kit \$39.95. Wired \$65.95. Incl. cover & F.E.T.

FM/AM Tuner HFT92 combines renowned EICO HFT90 FM Tuner with excellent AM tuning facilities. Kit \$59.95. Wired \$94.95. Incl. cover & F.E.T.

AF4 Economy Stereo Integrated Amplifier provides clean 4W per channel or 8W total output. Kit \$38.95. Wired \$64.95. Incl. cover & F.E.T.

HF12 Mono Integrated Amplifier (not illus.): Complete "front end" facilities & true hi-fi performance. 12W continuous, 25W peak. Kit \$34.95. Wired \$57.95. Incl. cover.

HFS3 3-Way Speaker System Semi-Kit complete with factory-built 3/4" veneered plywood (4 sides) cabinet. Bellows-suspension, full-inch excursion 12" woofer (22 cps res.) 8" mid-range speaker with high internal damping cone for smooth response, 3 1/2" cone tweeter. 2 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest frequency & best transient response. 32-14,000 cps clean, useful response. 16 ohms impedance. HWD: 26 3/8" x 13 7/8" x 14 5/8". Unfinished birch. Kit \$72.50. Wired \$84.50. Walnut or mahogany. Kit \$87.50. Wired \$99.50.

HFS5 2-Way Speaker System Semi-Kit complete with factory-built 3/4" veneered plywood (4 sides) cabinet. Bellows-suspension, 5/8" excursion, 8" woofer (45 cps. res.), & 3 1/2" cone tweeter. 1 1/4 cu. ft. ducted-port enclosure. System Q of 1/2 for smoothest freq. & best transient resp. 45-14,000 cps clean, useful resp. 16 ohms.

HWD: 24" x 12 1/2" x 10 1/2". Unfinished birch. Kit \$47.50. Wired \$56.50. Walnut or mahogany. Kit \$59.50. Wired \$69.50.

HFS1 Bookshelf Speaker System complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps range. 8 ohms. HWD: 23" x 11" x 9". Kit \$39.95. Wired \$47.95

HFS2 Omni-Directional Speaker System (not illus.) HWD: 36" x 15 1/4" x 11 1/2". "Fine for stereo" — MODERN HI-FI. Completely factory-built. Mahogany or walnut \$139.95. Blond \$144.95.

New Stereo/Mono Automatic Changer/Player: Jam-proof 4-speed, all record sizes, automatic changer and auto/manual player. New extremely smooth, low distortion moisture-proof crystal cartridge designed integrally with tonearm to eliminate mid-range resonances. Constant 4 1/2 grams stylus force is optimum to prevent groove flutter distortion. No hum, turntable attractions, acoustic feedback, center-hole enlargement. Only 10 3/4" x 13". 1007S: 0.7 mil, 3 mil sapphire, \$49.75. Incl. F.E.T. and "Magnadaptor."

†Shown in optional Furniture Wood Cabinet WE71: Unfinished Birch, \$9.95; Walnut or Mahogany, \$13.95.


††Shown in optional Furniture Wood Cabinet WE70: Unfinished Birch, \$8.95; Walnut or Mahogany, \$12.50.

EICO, 33-00 N. Blvd., L.I.C. 1, N. Y. C-10
Show me how to SAVE 50% on easy-to-build top-quality Hi-Fi. Send FREE catalog, Stereo Hi-Fi Guide plus name of neighborhood EICO dealer.

Name.....
Address.....
City..... Zone..... State.....

Listen to the EICO Hour, WABC-FM, N. Y. 95.5 MC, Mon.-Fri., 7:15-8 PM.

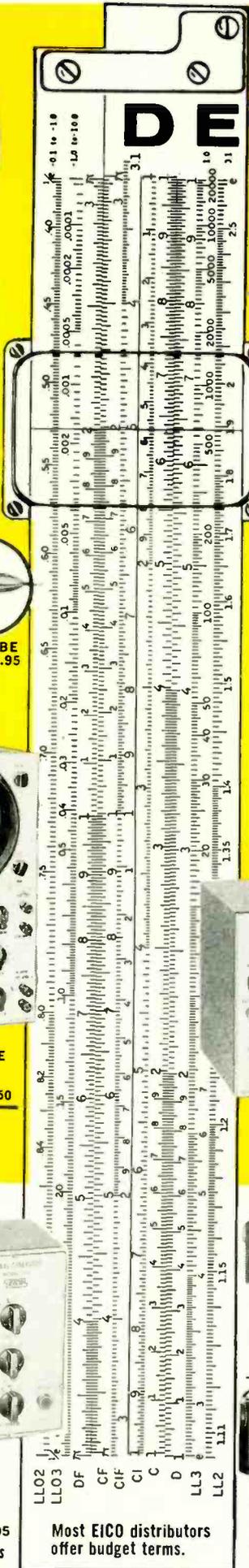© 1960 by EICO, 33-00 N. Blvd., L. I. C. 1, N. Y.



DESIGNED

AS YOU WOULD DESIGN IF YOU WERE AN ELECTRONICS ENGINEER...

Praised by the experts as Best Buys... **EICO**



A PEAK-TO-PEAK VTVM #232 & UNI-PROBE KIT \$29.95 WIRED \$49.95



B COLOR & MONOCHROME DC TO 5 MC LAB & TV 5" OSCILLOSCOPE #460 KIT \$79.95 WIRED \$129.50

Also available:
5" Push-Pull Oscilloscope #425
Kit \$44.95 Wired \$79.95



C RF SIGNAL GENERATOR #324 KIT \$26.95 WIRED \$39.95
Turn Page For More EICO Values

Most EICO distributors offer budget terms.

A By far the best professional VTVM value in electronics; nobody but EICO brings you such outstanding instrument performance for so low a price! Calibration without removing from cabinet. Measure directly p-p voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 volts with HVP probe, & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 4 1/2" meter, can't-burn-out circuit. 7 non-skip ranges on every function. Zero center. Features EICO's exclusive UNI-PROBE: your terrific time-saver, performs all functions: a half turn of probe-tip selects DC or AC-Ohms!

B An engineering achievement unmatched in the industry! EICO-designed for laboratory precision and EICO-priced for lowest cost. Features DC amplifiers. Flat from DC to 4.5 mc, usable to 10 mc. Vert. Sens.: 25 mv/in.; input 2 3 megs; direct-coupled & push-pull throughout. 4-step frequency-compensated attenuator up to 1000:1. Sweep: perfectly linear 10 cps - 100 kc (ext. cap. for range to 1 cps). Pre-set TV V & H positions. Auto sync limiter & amplifier Direct or C coupling; balanced or unbalanced inputs; edge-lit engraved lucite screen with dimmer control.

C More features and versatility, more range and accuracy than in generators costing three to four times as much. 150 kc to 435 mc with ONE generator in 6 fundamental bands and 1 harmonic band! ±1.5% frequency accuracy. Colpitts RF oscillator directly plate-modulated by K-follower for improved modulation. Variable

depth of internal modulation 0-50% by 400 cps Colpitts oscillator. Variable gain external modulation amplifier: only 3 volts needed for 30% mod. Turret-mounted, slug-tuned coils for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv, AF output to 10 v.

D Provides more ranges, greater ease and accuracy, and better performance than any competitive unit. Entirely electronic sweep circuit with accurately-biased inductor for excellent linearity. Extremely flat RF output. Exceptional tuning accuracy. Hum & leakage eliminated. 5 fundamental sweep ranges: 3-216 mc. Variable marker range: 2-75 mc in 3 fund. bands, 60-225 mc on harmonic band. 4.5 mc crystal marker osc. crystal supplied. Ext. marker provision. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Narrow range phasing control for accurate alignment.

E Speedy, simple operation, unexcelled sensitivity and accuracy; superb electrical and mechanical design. Tests all receiving tubes (picture tubes with adapter), n-p-n and p-n-p transistors. Composite Indication of Gm, Gp & peak emission. Simultaneous selection of any one of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot.). Sensitive 200 ua meter. 10 six-position lever switches: freepoint connection of each tube pin. 10 push-buttons: rapid insert of any tube element in leakage test circuit. Direct reading of inter-element leakage in ohms. New gear-driven rollchart. CRA Adapter \$4.50.



D TV-FM SWEEP GENERATOR & MARKER #368 KIT \$69.95 WIRED \$119.95



E DYNAMIC CONDUCTANCE TUBE & TRANSISTOR TESTER #666 KIT \$69.95 WIRED \$109.95
Complete with steel cover and handle



All Transistor Portable RA-6 Kit \$29.95 Wired \$49.95 less battery



Power & Bias Supply for Transistorized Eqt. #1020 Kit \$19.95 Wired \$27.95



DeLuxe Multi-Signal Tracer #147 Kit \$24.95 Wired \$39.95



Tube Tester #625 Kit \$34.95 Wired \$49.95 Pix Tube Test Adapter \$4.50



6 & 12V Battery Eliminator & Charger #1050 Kit \$29.95 Wired \$38.95 #1060 Kit \$38.95 Wired \$47.95



V-O-M #565 Kit \$24.95 Wired \$29.95 V-O-M #536 Kit \$12.90 Wired \$14.90



R-C Bridge & R-C-I Comparator #950B Kit \$19.95 Wired \$29.95

EICO 33-00 Northern Blvd., L. I. C. 1, N. Y. C-10
Show me HOW TO SAVE 50% on Test Instruments
 Hi-Fi Ham Gear. Send free Stereo Hi-Fi Guide. Send me FREE Catalog, name of neighborhood dealer. Send free Short Course for Novice License.

Name.....
Address.....
City..... Zone..... State.....

© 1960 EICO 33-00 N Blvd. L. I. C. 1, N. Y. Add 5% in the West

INSTRUCTIVE ELECTRONIC DEVICES

. . . *There Is a Big Market for Educational Devices Today* . . .

IN an age when our survival as a nation depends upon the electronic progress of our next generation, the thoughtful observer is being continually shocked to note how little is being done today to strike a responsive spark in our youngsters and to awaken them to present-day electronic-scientific wonders.

Make no mistake, electronic engineers don't fall from the sky ready made. In some way they all are indoctrinated at a very early age, usually before they are 6. Some magnetic or electric toy usually catches the child's fancy, lighting the flame of scientific knowledge. Thereafter the youngster slowly progresses to more interesting devices, learning and absorbing the mysteries of the various branches of physics, few of which he ever forgets as he grows up.

The despair of the average father nowadays is how little is offered on the market to start off a youngster on the road to electronic adventures. Outside of a few interesting magnetic toys in our stores, there is a vast vacuum when it comes to simple, low-priced, electric instructive devices.

At the turn of the century, the present writer was responsible for bringing to a previously nonexistent market dozens of simple, low-priced items, all of which found ready acceptance. Many were imported from Europe; others were made by his pioneering firm, the Electro Importing Co. (E. I. Co.); still others were manufactured at his behest by enterprising farseeing manufacturers.

Let us name only a few: telephone receivers (50¢); sturdy electric motors (from 60¢ up); household medical coils (weak electric induction shocking machine) (90¢); electric whistle (\$1); electric luminous scarf pins (to operate from pocket battery) (45¢); 6-volt dynamo (\$3.80); spark coils, giving a ¼-inch spark (\$2.20); dozens of types of fascinating colorful Geissler tubes to work from spark coils (from 38¢ up); static-electric machine (3-inch spark) (\$3.50); 4-inch X-Ray tubes* (\$4.30) that worked well with a fluoroscope (\$3.75); Fun With Electricity set (static) (50¢); microvolt meter (compass with coil winding) mounted with binding posts (50¢); rheostats (50¢)—just a few items from a long list.

Where can you buy such devices today? Particularly educational devices that a young boy can operate himself *before he can read*—the critical age.

More important, some of the few items that can be bought in stores today are all too often shoddy and a goodly percentage do not work.

Item: For two of our grandsons, below age 6, we bought a set of hand telephones (intercommunicating). Made of red plastic, the set looked attractive. It had, however, no binding posts or any device for clamping the connecting wires. Each handset instead had two metal strips with a tiny hole into which you stuck the wires—impossible to obtain a good contact. Upon testing the phones, they were found to be inoperative—dead. Since it was electromagnetic, no batteries were required to work the set, but there was an open circuit, so we returned the outfit. What about the complete frustration to the children? The less said the better. A week later, a new set arrived—also dead! Then the factory in New Jersey closed for vacation. Finally, a month later, an operable outfit arrived, but the functioning was so poor that the voices came through in whispers. Yet the shoddy set's cost was close to \$8!

It has been our experience over the past 15 years that a large percentage of present-day instructive electronic devices sold in toy stores are so skimpy, so poorly engineered that it is a wonder they work at all. Mass-produced, they

are often not properly tested or, if they are, they fall apart during shipping.

This usually is not the case with most of the similar European devices, which are much better made and far sturdier, a necessity for inquisitive and impatient little fingers.

In a number of cases, after ransacking toy stores to no purpose, we had to design and make a number of devices ourselves for the youngsters. One—a combination electric set mounted on a block of wood 8½ x 5½ inches—included: a sturdy standard buzzer, a small neon bulb, several colored flashlight bulbs, a few pushbuttons, two metal handles and several binding posts. The buzzer had its vibrator "blocked" in such a way that it became a high-frequency type. Its self-inductance built up sufficient voltage to light a neon bulb that normally required at least 40 volts, although we used only a 3-volt battery. The buzzer also had sufficient electric "kick" to operate as a miniature shocking coil when the metallic handles were connected to it. Everything worked by means of pushbuttons, all wiring being concealed under the base.

We constructed a number of other projects—all simple for youngsters to operate. One with a few electromagnets, springs and half-inch steel balls proved very successful. These examples are mentioned only to give some idea of the hundreds of devices that can be evolved with a bit of ingenuity and planning nor is a large capital investment necessary.

When mass-produced, with correct engineering and good workmanship, such devices can satisfy a huge market. The sales prices can be kept surprisingly low, even today. Plastics in countless shapes, electro- and permanent magnets, when produced in large quantities are still not expensive per unit, due to recent advances in mass production and automated machinery. Hence there is no reason why many instructive electronic devices should be out of reach of any youngster, even the ones in the most modest circumstances.

Parents, too, should learn that it is not always the most elaborate or costly outfit that makes the greatest hit with a given child. Often the very complexity proves frustrating because it's over his head—he's too young for it and cannot read and digest the technical instructions.

For example, such an outfit costing over \$20 was given a 6-year-old boy. He turned away from it dejectedly after a few useless attempts to make some of the pieces work. He then played for hours with a device costing less than \$2, which we assembled for his birthday: a small toy electric motor mounted vertically on a board. On top of the rotating shaft, you could place a number of specially colored disks, which were constantly changed into surprising color combinations if you interleaved them with other disks.

Another variety of devices, which are also mostly inexpensive and comparatively easy to make, can be created for older youngsters. They are *electronic games and puzzles*. Practically none of these are on the market. Yet none of them need to contain expensive parts—they use neither vacuum tubes nor transistors. Many of these devices are begging to be launched on the market by enterprising manufacturers looking for a steady, lucrative market.†

We were happy to learn that for youngsters, age 8–14, one of our great electronic kit manufacturers is launching a new line this fall in the country's *toy stores*. The list includes broadcast wireless mikes, experimental board, transistor kits and others.

—H.G.

*In 1907, it wasn't known that they were dangerous.

†For further information on this subject, see *Electronic Puzzles and Games* (Gernsback Library).

COVER STORY

HIGH POWER

FOR THE

TWIN-COUPLED AMPLIFIER

Design a twin-coupled amplifier for tubes you like to use or build this 35-watt unit using EL34's

By **NORMAN H. CROWHURST**

MANY readers have asked, "How can we design a twin-coupled amplifier around the output tubes we like using?" This article answers that question by showing a high-power twin-coupled circuit you can build and how to design one to suit your own tubes, ideas or requirements.

The original twin-coupled circuit was designed to give high fidelity at low cost.* It used EL84's in its output, and inexpensive output transformers would in the simplest possible manner to get adequate performance. This, unfortunately, resulted in unequal resistance for the primary halves. While the inequality is not important in the plate-screen-coupled transformer, it does result in slightly different bias on each of

* "High Fidelity at Low Cost With Twin-Coupled Amplifier," November, 1957. "Updating the R-E Twin-Coupled Amplifier," June, 1960.

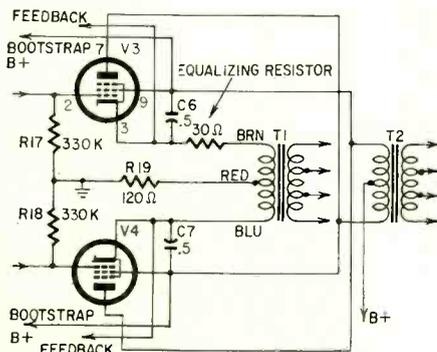


Fig. 1—A variation that equalizes cathode circuit resistance in the output tubes.

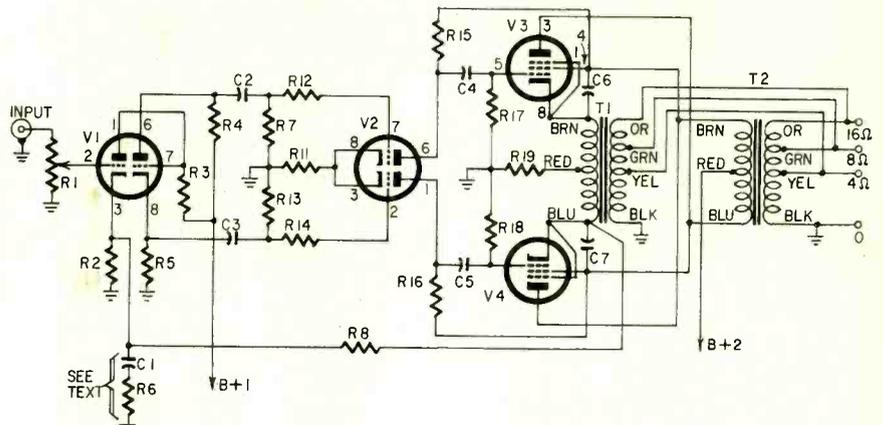


Fig. 2—Basic circuit of a more powerful twin-coupled amplifier.

the output tubes—because of the different dc drop across the cathode-connected primary.

Some readers have rectified this difference and increased output 1 or 2 watts, by inserting a 30-ohm equalizing resistance in series with the half primary that measures only 70 ohms, to make its total resistance equal to the other half (Fig. 1).

To design your own circuit, use the same configuration as the original, or the variation shown in Fig. 2. As far as possible, the same component numbering is used on both to avoid confusion. But don't look for R9 or R10 in Fig. 2, because they aren't there. Which ever circuit you use, keep the arrangement and wiring of V2, V3, V4, R15, R16, C4, C5, R17, R18, C6 and C7 physically compact. They carry high audio voltages that should be kept away from the input circuits.

To go about the design, first decide what output tubes (V3, V4) you want to use and the operating conditions.

If you want to go to more than 20 watts, you should use the larger transformer—Chicago Standard A-8098. It has balanced primary halves, more handling capacity and better mixing for high-frequency response. Its primary impedance is 2,000 ohms center-tapped, intended for use with tubes having a normal plate-to-plate load requirement of 4,000 ohms.

With slight variations, almost any output tubes can be used, with the suitable output transformer. To show how to figure circuit values, we will take EL34's as an example. The Mullard tube manual lists a condition using 375 volts B-plus with cathode bias, to give 35 watts output. The plate-to-plate load is given as 3,500 ohms for this condition. With a 4,000-ohm plate-to-plate load (using two A-8098 output transformers), these tubes should give better than 30 watts, assuming we get the same voltage swing with the higher load value.

To deduce the available output volt-

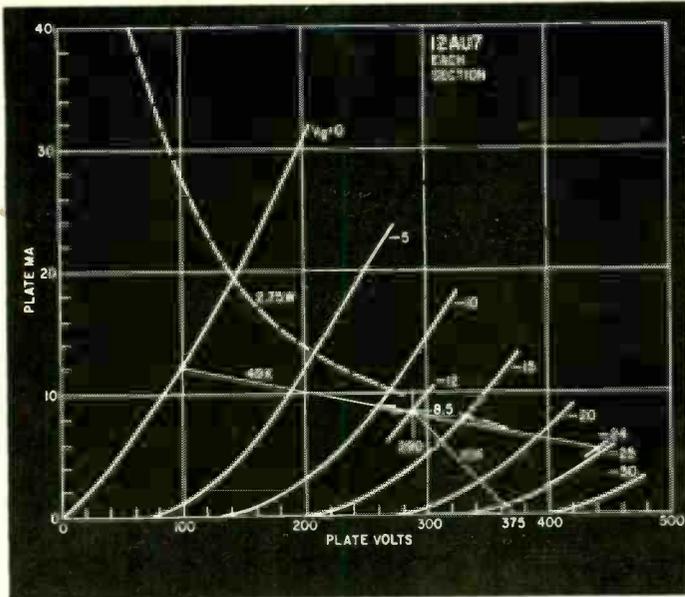


Fig. 3—Construction showing operation of a 12AU7 as a driver. Swing does not have sufficient margin.

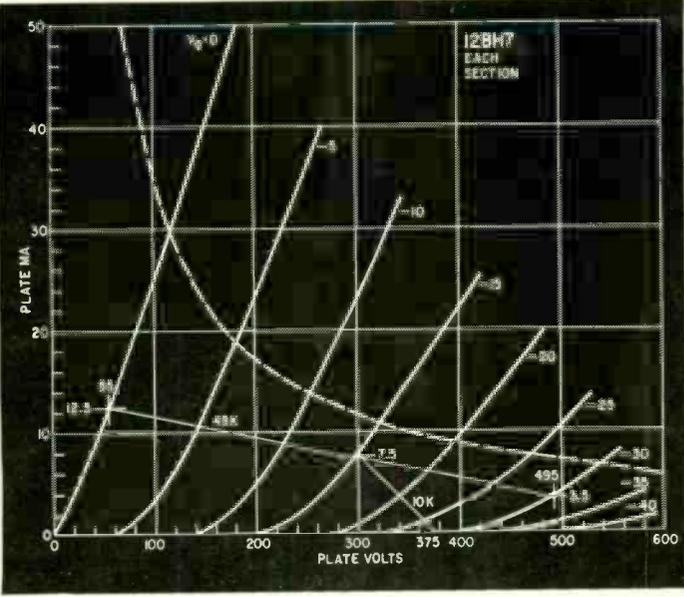


Fig. 4—12BH7-A gives plenty of swing as a driver.

age swing in the plate circuit, from which we work out all the other swings, use the condition indicated in the Mullard tube manual tables: 35 watts output with a 3,500-ohm plate-to-plate load. This works out to 350 volts rms, using the formula $V = \sqrt{WR}$. We are interested in swing. Peak voltage will be 500, and peak-to-peak, which is swing, will be 1,000. Of this, 500 volts will appear across each primary, and 250 volts across each half primary.

Don't forget, while we figure out operation in terms of swing or peak-to-peak, a meter measures rms (on a sine-wave test signal). So when you check operation, divide the swing value by 2.83 to get the reading you should expect on an audio voltmeter.

To get the output swing we have just figured, the tube manual says the grids need an input of 40 volts rms, grid to grid. This will be 20 volts rms per grid, or 56 volts swing per grid. But this 56-volt swing is required from grid to cathode, and the cathode swings 250 volts because of the output voltage. So each driver stage has to deliver $250 + 56 = 306$ volts swing to its output tube grid.

The driver stage

Now we look for a driver stage. First let's try a 12AU7. The only way is by drawing the load line on the curves. First we put in the maximum voltage and dissipation (Fig. 3).

If we use 10,000-ohm resistors in the plates (R15 and R16) and about 12 volts bias, the operating point is about 290 volts, 8.5 ma (from the 375-volt supply). For a 56-volt swing, measured grid to cathode of the output stage, the grid swings 306 volts. So this 10,000-ohm resistor has only 56 volts (audio) across it, although the plate is delivering 306 volts audio. This means the effective value of the 10,000-ohm resistor for plate coupling, in the

dynamic sense, is multiplied by $\frac{306}{56}$ or

about 5.5, which makes it look like 55,000 ohms.

The grid resistors (R17, R18), which should not be higher than 470,000 ohms to satisfy operating requirements of the output tubes, do not get multiplied in this way because they have to be returned to ground. So the effective ac plate load is 55,000 ohms in parallel with 470,000 ohms, or about 49,000 ohms.

Laying a 49,000-ohm load line through the operating point and estimating a 24-volt swing (twice the bias voltage), plate swing is from 100 to 440, or 340 volts. To use this dynamic operating point, one tube passes 12 ma (at 100 volts) while the other passes 5 ma (at 440 volts). The total current is 17 ma on dynamic swing, or 18 ma in quiescent condition, and we require 12 volts bias. So the cathode resistor (unbypassed) must be 680 ohms.

This is just enough, but it allows too little margin for comfort. To be sure of getting enough swing, let's try a 12BH7-A (Fig. 4). Again using a 10,000-ohm plate resistor (R15, R16), this time with 15 volts dynamic bias, we get an operating point of 300 volts, 7.5 ma, which is within the rating of the tube.

With the same 49,000-ohm dynamic plate load, the swing is now from 55 volts, 12.5 ma to 495 volts, 3.5 ma. The voltage swing is much more adequate: $495 - 55 = 440$ volts. The cathode resistor (R11) needs to give 15 volts bias with a total current of $12.5 + 3.5 = 16$ ma. Probably 1,000 ohms is close enough, in view of the reserve.

This will give close to the same quiescent operating point, because each tube passes 7.5 ma with 15 volts bias.

For the EL34 bias, the Mullard tube manual lists 260 ohms per tube. Each half primary of the A-8098 transformer measures 55 ohms, so an additional 205 ohms per tube is needed. For two tubes, this value is halved. A 100-ohm resistor (R19) is close enough. Total maximum signal plate and screen current is 227 ma ($2 \times 94 + 2 \times 19.5$), which will give a 22.7-volt drop and dissipate $22.7 \times 0.227 = 5.15$ watts. A 10-watt resistor should be used.

The driver plate resistors (R15 and R16) drop 75 volts with 7.5 ma, a dissipation of a little more than $\frac{1}{2}$ watt, so at least 1-watt resistors should be used here. A $\frac{1}{2}$ -watt resistor is plenty for the driver bias (R11) and other resistors in these stages.

Phase splitter and voltage amplifier

The driver stage will need 30 volts swing on each grid (twice the bias voltage). This a 12AX7 will do easily with either circuit (Fig. 5). Using the arrangement of Fig. 2, with 100,000 ohms in both cathode and plate of the phase-splitter section (R4, R5), the load line is 200,000 ohms. Supplying 300 volts B-plus to this point, the minimum tube drop is about 60 volts. With the dynamic load line, due to paralleling the following-stage grid resistors (R7, R13), the minimum tube drop is somewhat greater, so allow 75 volts. This will be the minimum bottom swing from the operating point, with 15 volts in each load, plate and cathode. So the tube operating voltage should be 105.

PRINTED CIRCUIT AVAILABLE

RADIO-ELECTRONICS is pleased to announce that the printed-circuit board used in the Twin-Coupled Amplifier can be purchased by the constructor. By special arrangement, you can get a Twin-Coupled Amplifier circuit board for \$2, postpaid, from RADIO-ELECTRONICS, 154 W. 14 St., New York 11, N.Y., or Electro-Technik Co., 19456 Meyers Rd., Detroit 35, Mich. Both sides of the board you will receive are shown in Fig. 9 of this article. In future issues, printed-circuit boards for other construction projects will also be made available.

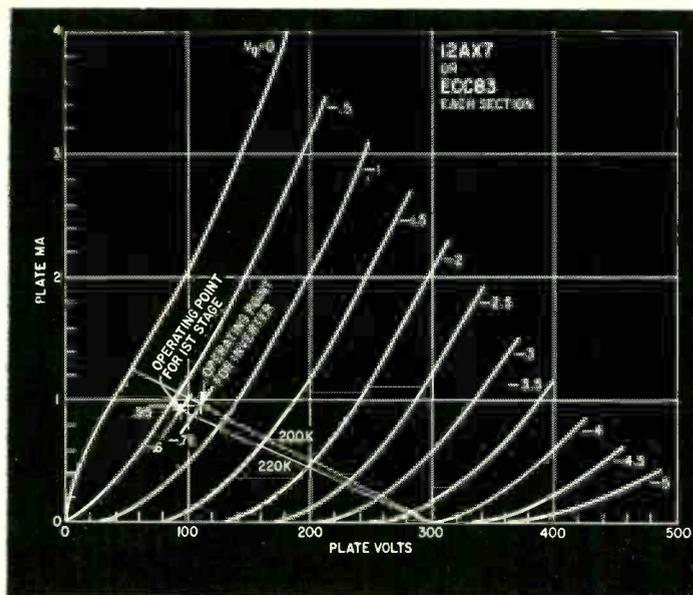


Fig. 5—Finding values for circuit in Fig. 2 using a 12AX7 or ECC83 voltage amplifier and phase inverter.

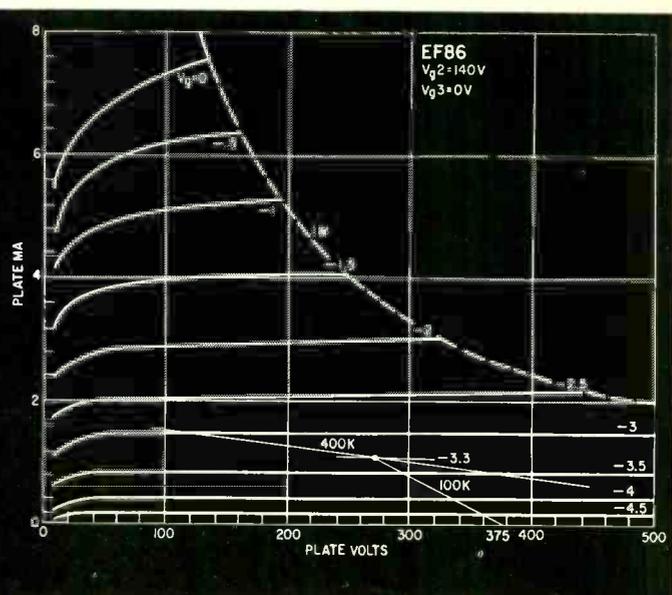


Fig. 7—Characteristics of an EF86 showing operation as a bootstrapped driver with a gain of about 500.

Make it 110 volts to give a slight margin. This leaves a 190-volt drop to the dc load resistor, 95 volts in the cathode and 95 in the plate.

Now the other half of the tube has to provide a direct-coupled grid voltage of 95 positive (strictly this should be less the bias of the second stage, which would make it 94.3 volts). Using a 220,000-ohm plate resistor (R3), this needs a bias of 0.6 volt with 0.9-ma plate current. So the input stage bias resistor (R2) must be about 680 ohms. This is also the bottom leg of the feedback network.

The phase splitter and voltage amplifier operate from a 300-volt source (B+ 1) so a series resistor is needed to reduce the available voltage (B+ 2) to this level. A 39,000-ohm ½-watt resistor passing 1.85 ma will develop the required 75-volt drop.

The stage has a gain of about 70, so the 30-volt output swing needed for the phase-inverter input (the phase-inverter gain is very nearly unity from input to each output) is obtained with about 0.43 volt input. If we use 14 db of feedback, the input has to be about

5 times this, or 2.15 volts swing, which is 0.76 volt rms. To get this feedback, the voltage across R2 has to be about 4×0.43 , or 1.72 volts swing. The swing on V4's cathode, from which this is derived, is 250 volts. So resistor R8

$$\text{must be } 680 \times \frac{250}{1.72} = 100,000.$$

Coupling capacitor values follow the original circuit. Also R12, R14 and R13 (with R7 made the same—270,000 ohms). If a 400-0-400-volt power transformer is used, total current is 227 ma for output tubes, 15 ma for the driver stage and almost 2 ma for the input stages: a total of 244 ma. A 5U4 with capacitor input filter will take care of power requirements. Using a 10- μ f input capacitor, the output voltage is about 470. So the smoothing resistor must drop about 95 volts at 244 ma, requiring 370 ohms at 23 watts. A 350-ohm 25-watt resistor will serve. C8 must be rated at 500 volts.

Those are the calculations. But after building the amplifier, check the operating voltages, both quiescent and with power. The plate voltage of the 12BH7 should be 300 (assuming the B-supply

ends of R15 and R16 get 375 volts). The cathode and plate of the second half of the 12AX7 should be 95 and 205 volts, respectively (again assuming the supply point is 300 volts). If not, the bias resistors (R11 or R2) need changing to get the voltages right. Don't forget, if you change R2, R8 needs changing in the same ratio to maintain correct feedback.

Network C1-R6, from V-1a's cathode to ground, levels off the response to around 20 kc when working into an open circuit or a resistive load. If the speaker system includes an electrostatic tweeter, this R-C network produces a 6- to 8-db boost at around 20 kc. This boost can be minimized by eliminating C1 and R6 when using an electrostatic tweeter.

If you use the original first-stage circuit (See RADIO-ELECTRONICS, June, 1960, for full schematic, or November, 1957, for original article), adjust R9 and R10 with signal passing and feedback connected, until signal voltage on both driver grids is equal. This is more easily done experimentally than by calculation.

Transformer input

Another variation requested was a surprise to me—a circuit to use transformer input. To do this effectively, much more gain is needed from the driver stage, so two stages (drive and output) are sufficient. This is done by using a pentode driver and taking the bootstrap feedback a little further, to include the output stage grid resistors. Fig. 6 shows the circuit.

The output stage is the same as the one we have just worked through and requires a 306-volt swing per grid, of which 250 volts appears at the cathode. The driver uses two pentodes, which can be EF86's. Using a 100,000-ohm plate resistor (R15, R16), coupled to a 470,000-ohm following grid resistor (R17, R18), and 3.3 volts bias, the gain is approximately 500 (using a dynamic


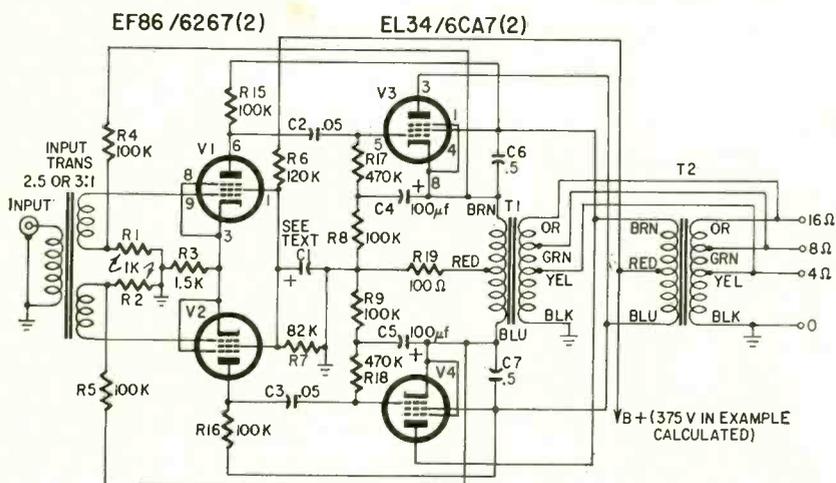


Fig. 6—Circuit using bootstrapped pentodes for drivers.

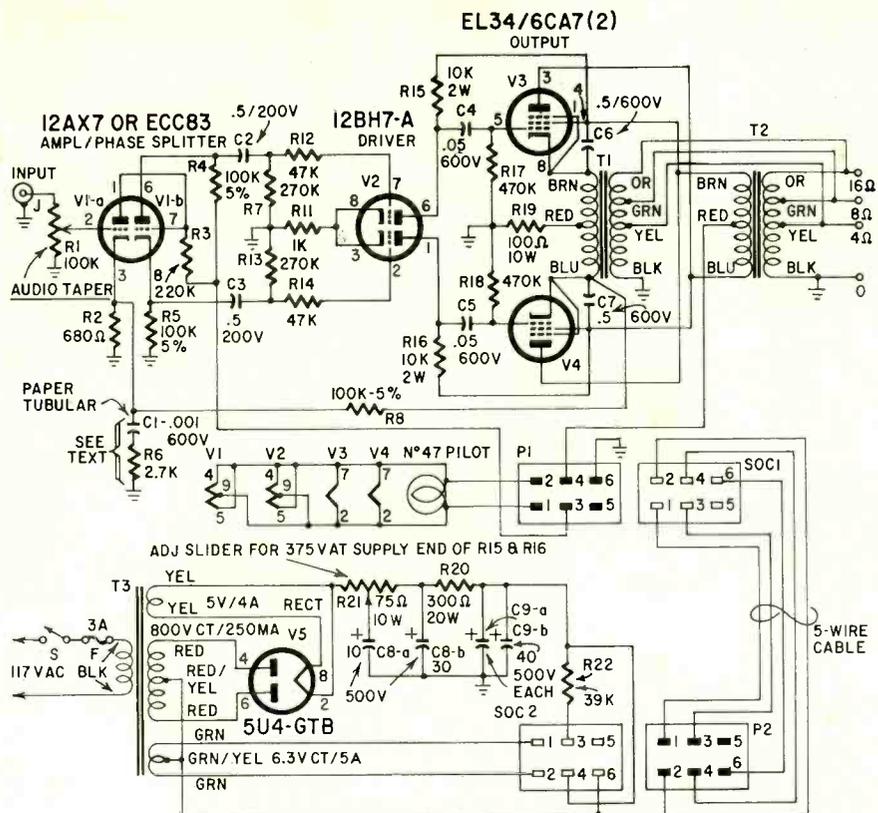

- R1—pot, 100,000 ohms, audio taper
 - R2—680 ohms
 - R3—220,000 ohms
 - R4, 5, 8—100,000 ohms, 5%
 - R6—2,700 ohms
 - R7, 13—270,000 ohms
 - R9, 10—not used, see text
 - R11—1,000 ohms
 - R12, 14—47,000 ohms
 - R15, 16—10,000 ohms, 2 watts
 - R17, 18—470,000 ohms
 - R19—100 ohms, 10 watts
 - R20—300 ohms, 20 watts
 - R21—75 ohms, 10 watts, adjustable
 - R22—39,000 ohms
- All resistors 1/2-watt 10% unless noted
- C1—.001 μ f, 600 volts, paper tubular
 - C2, 3—.05 μ f, 200 volts, paper tubular
 - C4, 5—.05 μ f, 600 volts, paper tubular
 - C6, 7—.05 μ f, 600 volts, paper tubular
 - C8—30, 10 μ f, electrolytic, 500 volts minimum
 - C9—40, 40 μ f, electrolytic, 500 volts minimum
- F—fuse, 3 amp
 - J—phono jack
 - SOC1—connector, female, 6 prongs, cable type
 - SOC2—connector, female, 6 prongs, chassis type
 - P1—connector, male, 6 prongs, chassis type
 - P2—connector, male, 6 prongs, cable type
 - S—spst
 - T1, 2—output transformers: see text
 - T3—power transformer: primary 117 volts; secondaries 800 volts, ct, 250 ma; 5 volts, 4 amp; 6.3 volts, 5 amp (Stancor PC8413 or equivalent)
 - V1—12AX7 or ECC83
 - V2—12BH7-A
 - V3, 4—EL34/6CA7
 - V5—5U4-GT5
- Chassis—see text
- Sockets, (2) 9-pin shielded top-mounting type for printed circuits
- Sockets, (2) top-mounting octal type for printed circuits
- Fuse extractor post
- Barrier strip, 4 terminals
- Tie strips (3), lug-type; 3 terminals
- Grommets, miscellaneous hardware

Fig. 8—Schematic of the complete 35-watt twin-coupled. B-plus voltage is adjusted by varying R21's slider.

load line of $5.5 \times 80,000$, or 440,000 ohms (Fig. 7).

This means the grid input swing for the EF86's must be about $\frac{306}{500} = 0.6$ volt. Inserting 2.4 volts (4×0.6) in the return of the input transformer's grid windings gives 14-db feedback. The input swing per grid winding must be 3 volts, or about 1.06 volts rms. One of the stock line/plate to push-pull grid transformers, with a stepup ratio of 2.5 or 3 overall, will permit driving this amplifier from a cathode follower output delivering 1 volt rms.

The feedback resistors can be 1,000 ohms (R1, R2) and 100,000 ohms (R4,

R5), to provide the 100-to-1 reduction from 250 volts to 2.4 (approximate). The only remaining details are the bias and screen voltage arrangements and the output-stage grid decoupling, to permit bootstrapping the grid resistors.

The EF86's need 3.3 volts bias with a total plate current of 2 ma, plus about one-sixth of this as screen current. A 1,500-ohm resistor should be right for this. Screen voltage must be 140, to use the operating point the curves were based on. Estimating screen current (two tubes) as 0.3 ma (one-sixth plate current) and swamping it five times with the potentiometer feed,

the top part (R6) has to drop $375 - 140 = 235$ volts with 1.8 ma, requiring a resistance of 130,000 ohms. The bottom part (R7) needs to drop 140 volts with 1.5 ma, requiring 93,000 ohms. Preferred values of 120,000 and either 91,000 or 82,000 ohms should serve.

A large capacitor (C1) is needed to decouple the screen because of the high stage gain, which means the screen will be susceptible to the amplification of any hum voltage fed to it. Try a 100- μ f 150-volt electrolytic.

The output-stage grid decoupling requires full cathode swing voltage to be coupled to the bottom end of the grid resistors. There is a dc voltage across the capacitors used for this (C4, C5) equal to the bias of the output stage (22.7 volts). So a 50-volt electrolytic can be used, say 100 μ f. The resistors

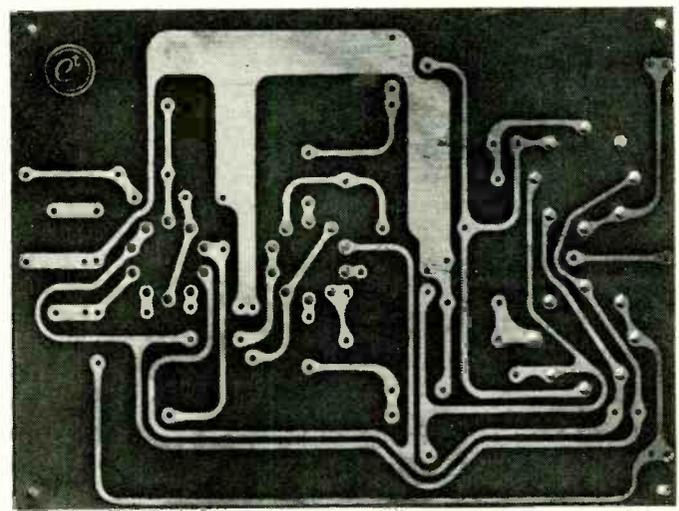
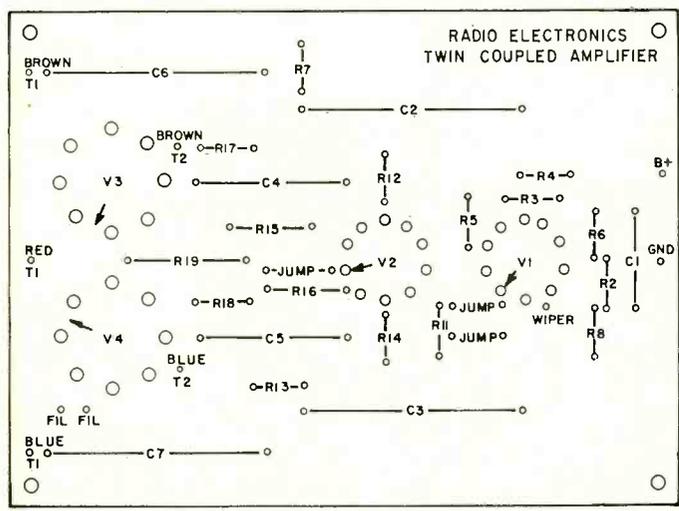


Fig. 9—Top and bottom views of the printed-circuit board. Drawing and photo are almost exactly half size. Board used measures $7\frac{1}{8} \times 5\frac{1}{4}$ inches. If you make your own, add about $\frac{1}{4}$ inch along each side to simplify mounting. Drill an additional mounting hole in the center of each long side to reduce flexing.

(R8, R9) absorb a small portion of the output power (as do feedback resistors R4 and R5, which at each cathode "see" a 1,000-ohm load resistance (one-fourth the total plate to plate). Making them 100,000 ohms means that only 1% of the proportion of power coupled by the cathodes will be fed to these resistors. The total grid-circuit resistance is now about 600,000 ohms (470,000 + 100,000).

In setting this circuit up, as with the others, check all dc voltages and then see that the signal voltages are also what they should be.

A practical circuit

Following the design procedures outlined in this article, the staff of RADIO-ELECTRONICS developed the 35-watt twin-coupled amplifier shown in Fig. 8

must be oriented carefully before mounting. Mount sockets for V3 and V4 so the arrows on the mounting fall between pins 1 and 8. Mount V1 and V2 sockets so the arrows point to the space between pins 1 and 9. The arrows on the V1 and V2 mounting locations point to extra holes used for ground leads for the tube shields.

The prototype audio section of the amplifier was built on a 7 x 11 x 2-inch chassis. But, since B-plus voltage appears on some points on the top of the printed-circuit board, we recommend that you build this section on an amplifier foundation kit (a chassis with a matching ventilated cover) such as the Bud CA-1751 or ICA 3966.

The power supply, connected to the audio chassis through a five-wire cable, fits nicely on a 5 x 7 x 2-inch chassis.

HOW LIVE IS YOUR NICKEL-CADMIUM BATTERY?

By NATHANIEL RHITA


THE voltage of a mercury or nickel-cadmium cell remains nearly constant throughout its life span; then the cell goes dead suddenly. At normal discharge rates, for example, NiCd cell voltage varies as follows:

discharge	voltage
10%	1.28
40%	1.24
70%	1.19
95%	1.15

Thereafter, the voltage drops sharply. The small voltage variations during its useful life are not easy to measure on a 3- or even a 1.5-volt scale.


A better method is shown in the diagram. The NiCd cell under test is connected in series (opposing) with a mercury cell. The latter voltage is about 1.35. Thus the voltage difference between cells will vary between approximately zero and 0.2 volt.

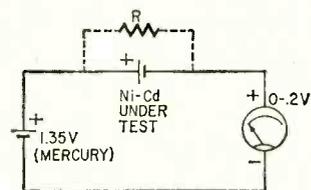Sensitive dc meters generally measure about 0.2 volt without multipliers.



For example, a 100- μ a meter may have an internal resistance of 2,000 ohms, and thus measure 0.2 volt. My own meter is a 40- μ a instrument with resistance of 5,000 ohms. When connected as shown, such a meter measures the voltage between the 1.35 volts of the mercury cell and 1.14 volts from the NiCd cell. To simulate actual conditions, add a load (R) across the measured battery. Select R to have about the same current drain as the equipment on which the cell is used.

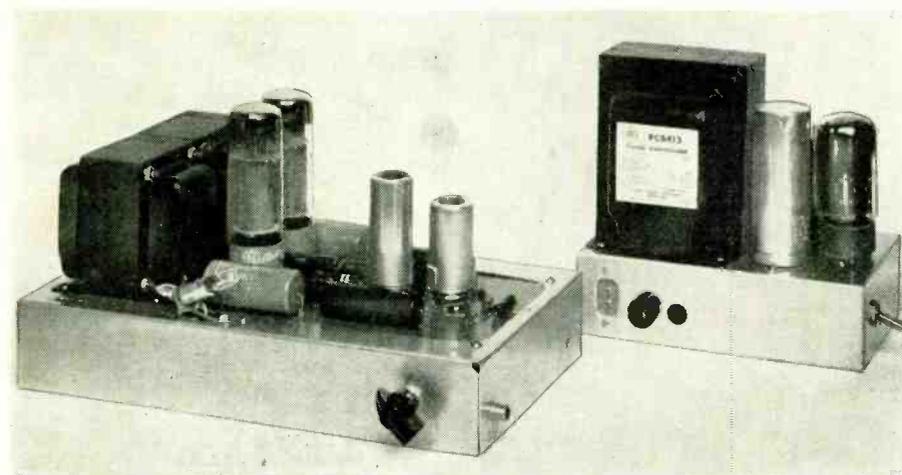This method can indicate whether a cell is fully charged, half-charged or exhausted so it can be put back on charge. It may prevent the embarrassment of trying to operate from a cell that has little life left.




Top of the twin-coupled amplifier. Printed-circuit board makes all parts readily accessible.


and the photographs. The amplifier was constructed as a two-chassis unit with printed-circuit wiring in the audio section.

The sockets for V1, V2, V3 and V4

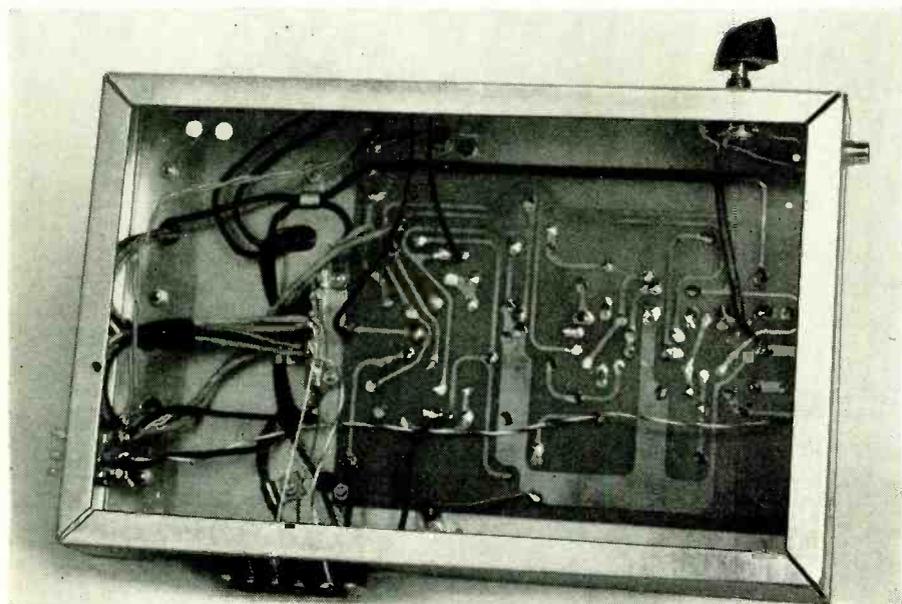Input filter resistor R21 has its adjustable slider connected to the positive end of C8-a. The slider is adjusted for 375 volts at the B-plus ends of R15 and R16 (blue and brown leads of T2). END



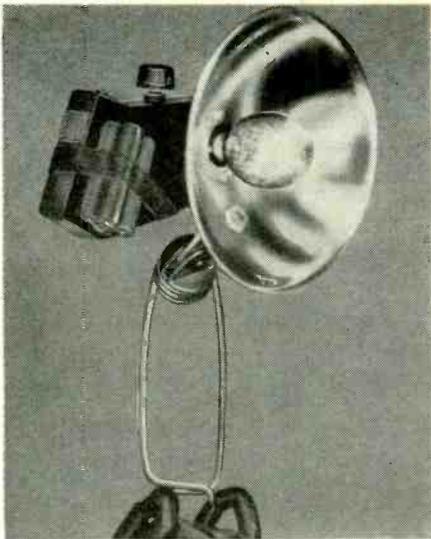Under-chassis view of the 35-watt twin-coupled amplifier.



The finished unit. A clamp stand is attached to the reflector so the remote unit can be mounted almost anywhere.

By FRANKLIN T. MERKLER

EACH year thousands of flash bulbs are fired to produce thousands of flat portraits to paste into the family album. The villain is the flash bulb anchored to the top, side or bottom of the camera. It is needed to provide enough light for a proper exposure, but the direction and quality of this light never varies—it is always head-on.

Twenty years ago, I went through this critical phase of picture taking and soon tired of the flat prints, the glassy-eyed look, the ash-white faces. The flash gun was taken off the camera and two or more flash bulbs were set off at the ends of extension cords. These pictures were excellent, but the dangling wires which would sometimes appear in the picture and the nuisance of carrying some 20 feet of wire soon ended this experiment. Slowly the camera fell into disuse, except for the usual birthday and Christmas shots.

What I needed was an extension flash synchronized with the flash bulb on the camera. Such units could be made with the help of vacuum- and photo-tube circuits, but the disadvantages of providing a high-voltage supply ruled them out. I needed a unit that would be small, mobile, self-contained and keyed by the flash of light originating at the camera-mounted gun. Transistors could make such a unit possible.

Circuit requirements


Before a design could be worked out, I had to find out how much voltage and current a flash bulb requires. A typical M-class bulb (No. 5, Press 25, etc.) could be fired with 3 volts or more, but the current requirement was critical—300 to 350 ma minimum. To do the job, I designed a transistor switch that applies 6 volts at 500 ma to the flash

Better Photos with a Transistor Slave Flash

bulb. The sensing unit is an International Rectifier Co. solar battery. Its output is too low to trigger the transistor switch directly, so some dc amplification is needed.

The circuit worked, but stray light would key the unit and flash the bulb. To make the unit more reliable, I added a 10,000-ohm potentiometer to the dc amplifier's base circuit and made up a test light to fit the flash socket. When the added pot is set so the test lamp does not light, it is safe to plug in the flash lamp. Any setting that lights the test lamp will fire a flash bulb. So when room lighting is bright enough to light the test lamp, the pot is turned down until the test light goes out.

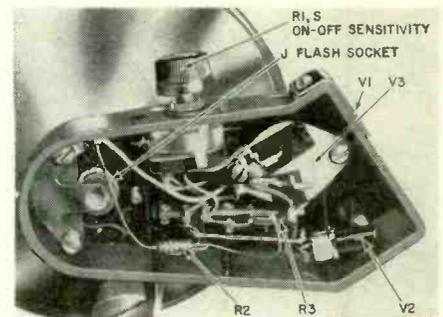Now I had a practical circuit (see schematic), but would it fire a flash bulb in sync with the one on the camera? At this stage, a professional photographer friend, Mr. Dale Watson, was asked to test the unit. He used a Speed Graphic with a Compur Synchro shutter. My slave flash was set up 12 feet away and aimed directly at the camera. The shutter was set at 1/25



Parts layout inside the slave-flash case.


second for the first exposure, subsequent tests were made at 1/100 to 1/400 second. Each time the slave flash unit keyed and fired its bulb when the camera bulb fired.

The breadboard setup was run through its paces in other ways too. One test had the flash bulb at the camera completely shielded from the subject. The light from the camera-mounted flash could only hit the slave-flash unit which was aimed to light the subject. This test was a complete success, the picture was perfectly exposed.

Building and using the unit

The finished unit (see photos) was built around a surplus flash unit. The reflector, socket and plastic body were used, but all internal wiring and the mounting shoe were discarded. Four penlight cells were needed to power the slave unit and they wouldn't fit into the case. Instead they are wired in series to provide 6 volts and are taped to the plastic case under the reflector. The 10,000-ohm potentiometer and its ganged switch are mounted in a hole drilled in the side of the case. Parts layout is not critical. The only vital point is to make sure all components are fastened securely in place.

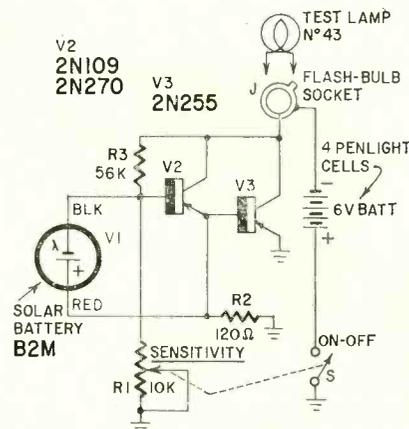The slave flash makes an effective portrait light when placed off to one side and above the subject so its light falls at about a 45° angle on the subject. Use the electronic slave flash to light your way to lively color slides and flash pictures with quality and punch.



- R1—pot, 10,000 ohms, with spst switch S
- R2—120 ohms, 1/2 watt
- R3—56,000 ohms, 1/2 watt
- BATT—6 volts (4 penlight cells in series)
- J—flash-bulb socket
- S—spst on R1
- V1—B2M solar battery (International Rectifier)
- V2—2N109 or 2N270
- V3—2N255
- Chassis to suit (surplus flash unit)
- Miscellaneous hardware

Circuit of the 2-transistor unit.

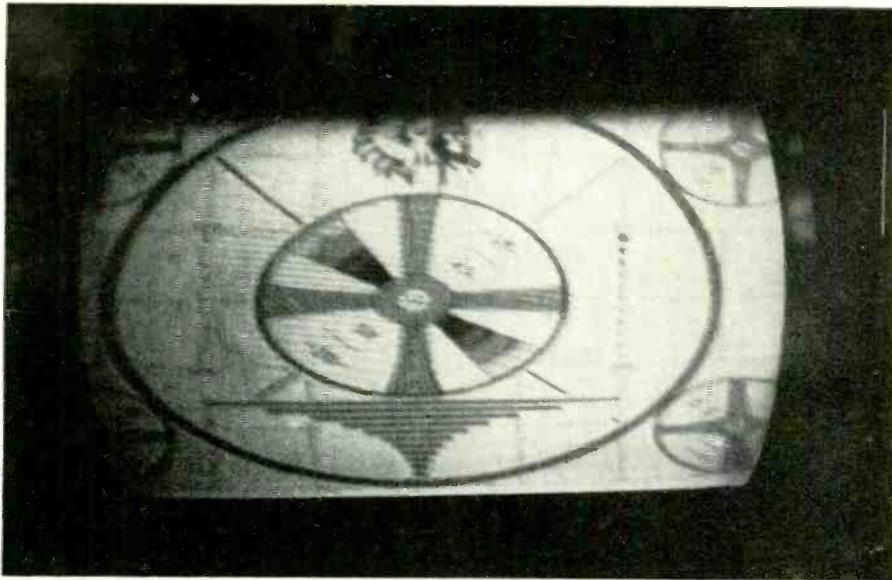


Fig. 1—Picture set up for vertical adjustments. Height and linearity controls turned down to leave 1 to 2 inches of space at top and bottom.

Much can be learned about the condition of the vertical stages just by observing the picture

THE vertical oscillator and output stages of a modern TV set shouldn't be too hard to troubleshoot. You can get a good idea of what shape they are in just by looking at the picture! A test pattern is always helpful (either off the air or from a pattern generator). And you can use a scope in one place (checking vertical sync), but even here you can find out what's going on just by watching the way the picture acts when you move the vertical hold control. You can get a pretty good idea of the condition of the whole circuit, in fact, by just checking the picture and raster (actually, you don't even need the picture, but it's easier!).

There are three things to check about the vertical circuit: height, linearity and "holding ability." The first two can be checked out pretty quickly by looking at the picture. If it doesn't fill the screen, find out why.

Height and linearity controls are used to compensate for tube aging. The first step should be to set up the picture correctly. Turn height and linearity controls down until you have a linear picture that lacks about an inch of filling the screen (top and bottom, as in Fig. 1). Center it with the centering magnets on the yoke until it is the same distance from both top and bottom edge. Now, using both controls, see if you can pull it up (and down) until it fills the screen with about a 1/2-inch overscan at top and bottom. If the picture will not cover the screen or isn't linear (crowded or stretched at the top), then you've found the first trouble.

Height lack is usually due to a weak tube or low B-plus voltage. In most cases, low B-plus will cause a narrow picture too. A weak tube in either oscillator or output stage will usually result in the picture being nonlinear at the same time. In any case, if the picture is too small, replace the tubes first; it's the easiest! (Note:

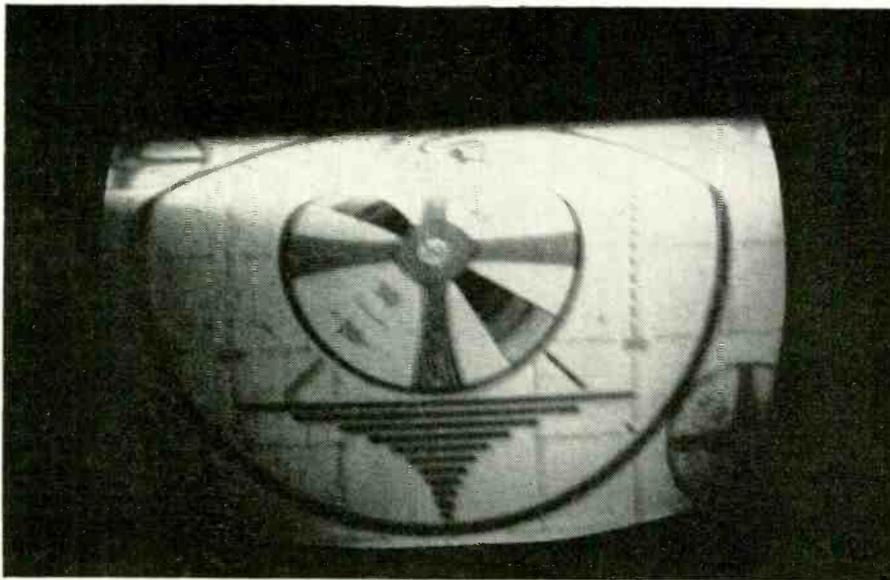


Fig. 2—Compression at top of picture is example of nonlinearity.

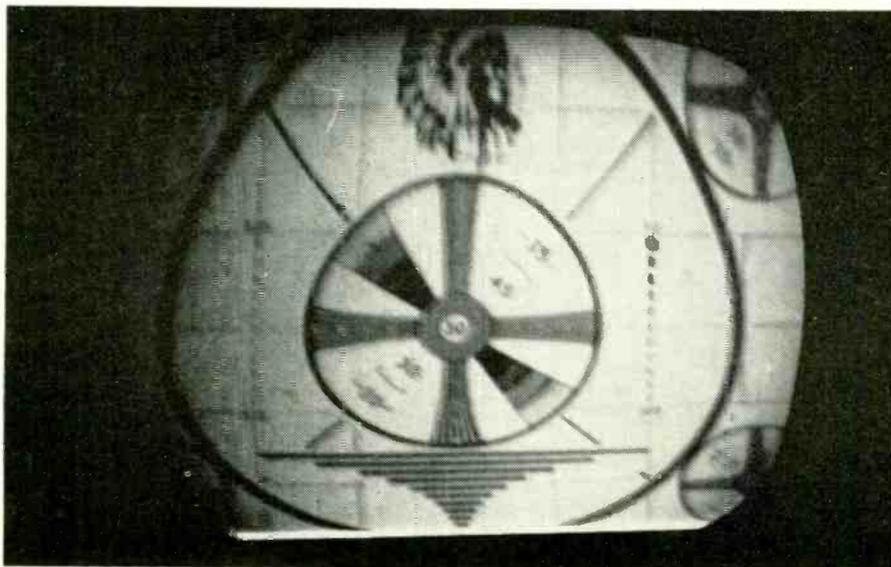


Fig. 3—Another example of nonlinearity is stretching of picture top.

TROUBLESHOOTING the VERTICAL OSCILLATOR AND OUTPUT STAGES

By R. D. JACQUES

you'll find a few cases where the picture *will* have enough height, but will be stubborn about being linear. Change the tubes first; this is often the cause!

While adjusting the height and linearity controls, check them for noise and roughness. Carbon controls will develop dirty or worn spots and cause trouble. These carry some dc in most circuits and are prone to troubles like this. You may find that the picture suddenly disappears as you move either control, leaving a thin white line across the screen. If this happens, the control is bad; replace it before going any further.

Linearity check

To check the linearity of the picture, look at the scanning lines. If they're evenly spaced all the way from top to bottom, fine. If not, the linearity is bad. A quick check for linearity is to roll the picture slowly downward with the vertical hold control. Watch the blanking bar as it travels down the screen. If it stays the same width all the way, good; if it comes into view very wide, then shrinks as it comes down, bad linearity. The opposite is also true: if it comes into sight narrow, then widens

or if it changes in width at all as it goes down, the linearity is off and must be adjusted. Poor linearity will also show up in the picture: Fig. 2 shows compression at the top; Fig. 3, excessive stretch at the top.

Vertical oscillator

Now let's look at a typical vertical oscillator output stage used in many TV receivers (Fig. 4). The older sets used blocking oscillators with a separate output stage, usually a pentode. However, the multivibrator has almost taken over in sets made in the last few years. The first versions used two tubes (sometimes) as in one series of Bendix chassis, half of a 6SN7 and a 6W6. Later sets use a single specially designed triode. These tubes are double triodes, but the two "halves" are different. The oscillator section is a voltage-amplifying type with a fairly high μ ; the output half is a power amplifier. The 6CM7, 6CY7 and 6DR7 are typical of this class.

The two tubes are connected as a simple multivibrator. There are variations of this circuit, of course, but each version can be traced out as a multivibrator. Note the feedback paths from

the plate of each section to the grid of the other. These R-C networks determine the time constants of the circuit, so that it will operate near the correct frequency of 60 cycles per second when free-wheeling.

The height control (sometimes labeled VERT SIZE) is usually found in the plate supply of the oscillator section. It will be a large resistor, common values being from 3 to 8 megohms. The vertical linearity control is most often found in the cathode of the output section. It will be a smaller control, running from 250 to 2,000 ohms. In this location, it regulates the output-stage bias so that the tube operates on the most linear (straightest) portion of its curve. A variation of this is used in Westinghouse and other sets with the linearity control connected in the grid-return circuit of the first and second stages. It is part of the grid leaks of both and also part of the coupling network. A higher resistance control is used here, around 500,000 ohms (Fig. 4).

In almost all circuits, the vertical hold control will be found in the grid circuit of the oscillator section where it will be a part of the R-C network. By varying the resistance in the grid cir-

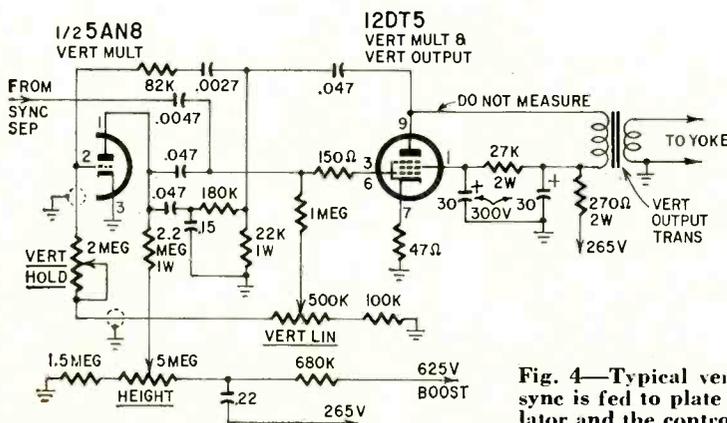


Fig. 4—Typical vertical multivibrator. Notice that sync is fed to plate of the first section of the oscillator and the control is in the common grid return.

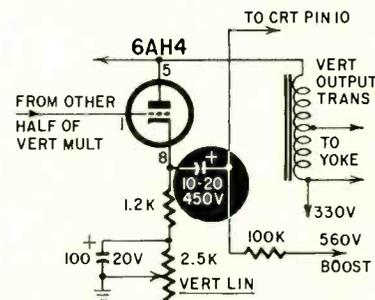


Fig. 5—When cathode-to-B-boost capacitor (circled) is leaky or open, linearity troubles may develop.

cuit, we alter the time constants and change the operating frequency of the oscillator.

There is a sort of general rule that applies to these circuits: The height control affects the bottom half of the picture, while the linearity control works mainly on the top half. Like all generalizations, this one is false, as it won't work in all cases. But it is pretty close.

Common troubles

The most common defect is loss of height or linearity. Weak tubes cause most of the trouble (as in all other circuits), and low operating voltages are next. As you can see from the schematics, some multivibrators are supplied from B-plus, while some are fed from the boost voltage. A few feed the oscillator from B-plus and the output stage from B-boost. Check the schematic for the set you're working on to see just what comes from where.

You'll find some high-value resistors in the supply circuits. These should always be checked carefully. If the trouble seems to be thermal (showing up only after the set is thoroughly heated up) you can suspect a shift in the value of one of the resistors in the B-plus circuits. Connect an ohmmeter across the resistor (after disconnecting one end) and hold the tip of a soldering iron close to the resistor. Watch for any resistance rise. If it changes more than 5%, replace it. Incidentally, while we seldom suspect variable resistors—such as height controls—of varying in total resistance, this *has happened!* So, don't overlook them when you're hunting for the

cause of a height loss.

If the oscillator is fed from the B-boost voltage, a drop in boost voltage (due to a weak damper tube and so on) can cause trouble. Check the boost voltage first to make sure it's up to snuff. If the boost voltage is OK but the voltage at the output tube's plate is suspiciously low, check the output transformer for a high-resistance joint in the winding. A leaky coupling capacitor between oscillator and output stage can also cause this trouble although this will usually upset the linearity badly, causing foldover at the bottom of the screen.

Linearity troubles

Linearity troubles are almost always found in the output stage. While it is theoretically possible for it to originate in the oscillator circuit, in practice it is seldom found there. If the VERTICAL LINEARITY control is in the cathode of the output stage, it will always be bypassed with a large low-voltage electrolytic capacitor, 100 μ f or more. If this value falls off or the capacitor opens entirely, linearity will be very bad.

High power factor in this capacitor is usually the cause of the mysterious "wrinkle" that shows up about a quarter of the way down from the top of the screen. The best test for this is to disconnect the original and substitute a known good unit of equal or larger size. You can use a larger capacitor but never a smaller one than that shown in the schematic.

Electrolytic capacitors elsewhere in the power supply can be responsible for vertical troubles. Some sets use an electrolytic of about 10 to 20 μ f connected from the boost voltage to the vertical output tube's cathode. Obviously trouble in this unit can give you all kinds of assorted headaches! Leakage through it upsets the output tube bias; an open will allow all sorts of wild

waveforms to float around the circuit and so on. So, if all of the "standard" parts seem to be OK, look for a capacitor connected in this manner (Fig. 5).

In a few cases, the last filter capacitor in the boost circuit will cause the same kind of trouble. This will be connected from B-boost line to chassis and may be far removed, physically, from the vertical circuits. If it opens up, it may allow high-level horizontal pulses to leak into the vertical output circuits where they will cause trouble.

The last common cause of vertical nonlinearity is found in the output transformer. Short of substituting a new one, these transformers are hard to test unless a winding happens to be completely open, in which case even I could find the trouble pretty easily! However, if everything else in the circuit is OK as far as you can tell and the picture still refuses to be linear (or have sufficient height), then there is room for a logical suspicion that the output transformer has a shorted turn(s) somewhere. Substitution is about the only quick check for this.

A lot of technicians have a tendency to suspect the vertical section of the yoke when this happens. However, you'll find that very few of these troubles are actually caused by defective yokes. There is one sure sign of vertical yoke trouble: that well-known trapezoidal raster (much narrower at top than bottom, or vice versa) which you'll find in every book. If you see this, there is only one thing that can cause it, and that's a bad yoke. In case of doubt, reduce picture width and look at the edges of the raster. If they are trapezoidal, you'll see it then. (There is one more possibility: If the vertical output transformer is *not* the original part, check up on the part number, just to be sure that whoever replaced it put in the right one. It *has happened!*)

Instability, sync troubles

Poor vertical stability is about the most common customer complaint, it seems. (It's rolling!) This can be due to two things: weak vertical sync or trouble in the oscillator. A weak oscil-

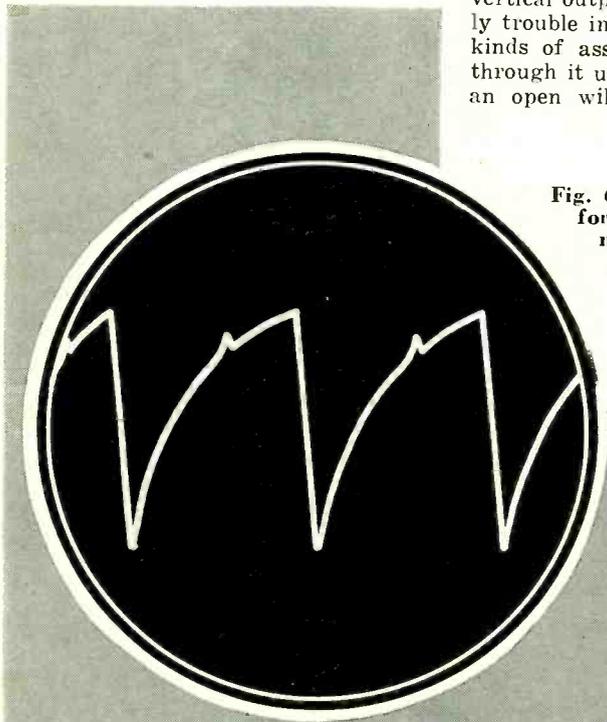


Fig. 6—Vertical oscillator waveform with sync pulse. Picture must be rolling slowly downward to make pulse visible.

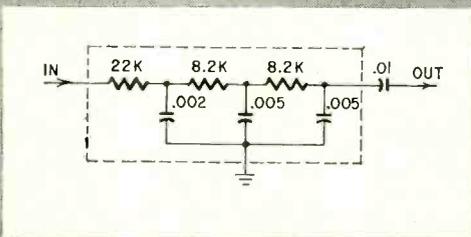


Fig. 7—Typical vertical-integrator network.

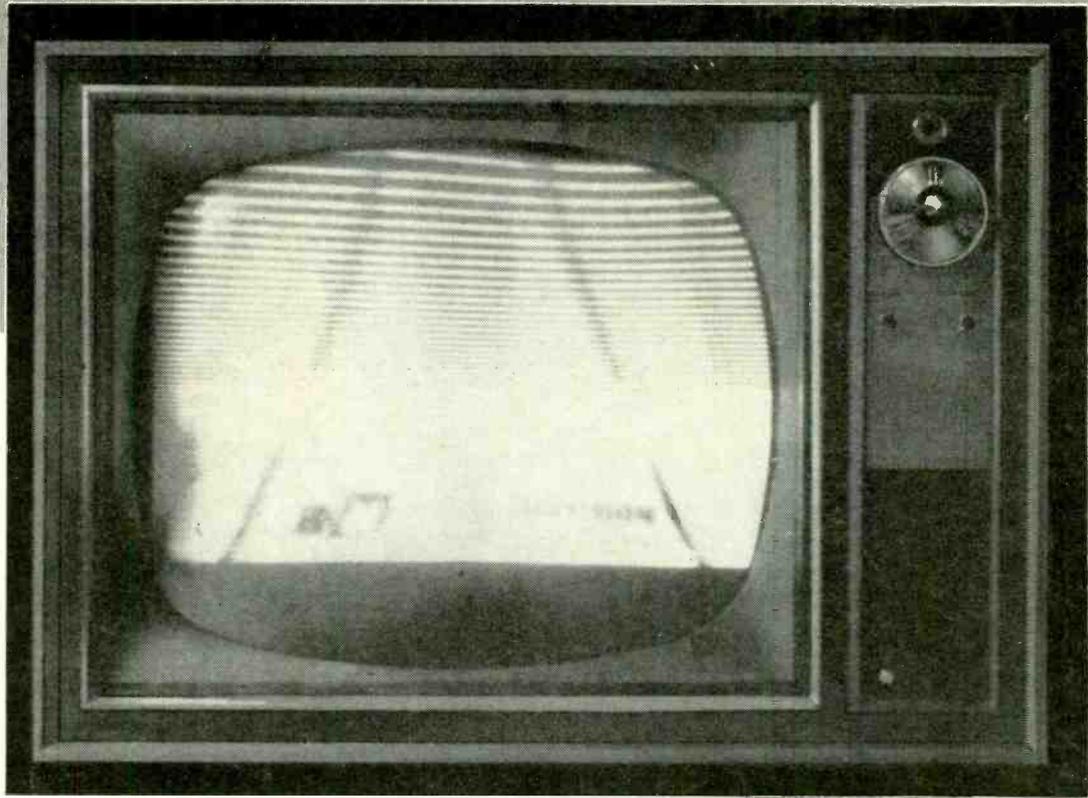


Fig. 8—Heater-to-cathode leakage in oscillator produces extreme non-linearity.

lator tube can account for a lot of it so always change it first. If replacing the oscillator tube doesn't help, then change the sync tube immediately preceding it, just to find out.

A good check of the sync or holding action can be made from the front of the set. Simply roll the picture downward by turning the vertical hold control. This control can tell you a lot about the condition of the vertical stages. The picture should roll *slowly downward* when the control is turned one way, with the blanking bar rolling smoothly down until it gets to a point about 3 to 5 inches from the bottom in a large-screen set. It should then suddenly snap out of sight and the picture lock momentarily in place. When the control is turned in the other direction, the picture should remain stationary, then "break out," rolling *upward very rapidly!* If you can roll a picture *slowly upward* by turning the hold control, then there's something very definitely wrong with the sync or oscillator circuits!

The snap at the bottom of the picture is the point where the vertical sync pulse grabs the oscillator and forces it to lock in. On a scope, this looks like Fig. 6. Here, the picture has been rolled part way down so that the vertical sync pulse may be seen. It is the tiny notch just below the top of the waveform. This is about the minimum amplitude for the sync pulse. If it is smaller than the one shown, it won't be

able to control the oscillator as it should. Low sync is usually caused by weak sync tubes, incorrect plate voltage on sync tubes or leaky capacitors in the vertical integrator network (Fig. 7). This is often a printed-circuit type (the parts values shown are the ones most commonly used) although there are others found in some sets that will differ from these. Zenith, for example, uses a small Rescap network which is actually only a single capacitor and resistor.

This is the one place where a scope can be used to real advantage. Connect it (through a low-capacitance probe) to the sync input of the vertical oscillator, roll the picture slowly down with the hold control and check the amplitude of the sync pulse. If you have hold trouble, the sync pulse may be so small that you can't see it at all or show up as a mere wiggle on the oscillator waveform. If there is any doubt, kill the vertical oscillator by removing the tube or grounding the grid (turn the brightness down to prevent burning the picture-tube screen) and check the amplitude of the sync pulse all by itself. In the multivibrator circuit of Fig. 4, the sync is fed into the plate of the vertical oscillator. This may appear strange to some hard-headed old-timers who insist that sync should always be applied to the grid.

Before checking for holding action, be sure that the picture is adjusted to normal height and linearity with the proper controls. If the picture is not

set up right, there will be a change in the waveshape which may make sync action improper. Too much stretch at the top, for instance, can flatten the top of the wave so much that the sync pulses will have a hard time locking the oscillator at the right instant.

Foldover

Foldover at the bottom of the picture is caused by the oscillator running too fast. The beam has reached the bottom of the screen and started back up again before the whole picture has been scanned. Therefore, the bottom part of the picture is folded up over itself, making a wide white line (customer's description) at the bottom. This is usually caused by leaky coupling capacitors, defective grid resistors or improper bias on the oscillator tube.

Another cause of foldover, this one quite different, is heater-cathode leakage in the oscillator tube. This results in a 60-cycle sinusoidal voltage being applied, in effect, to the grid instead of the sawtooth and results in a picture looking like that of Fig. 8. This is easy to cure; just replace the tube. Characteristic symptoms: very bad non-linearity and severe foldover so that the picture covers only about half the screen.

two business primers

Fig. 9—Vertical integrator used in some General Electric sets.

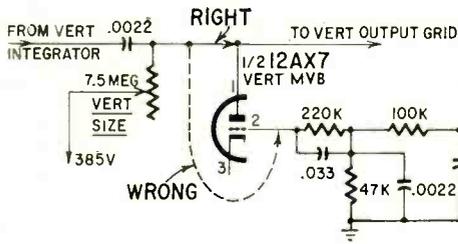
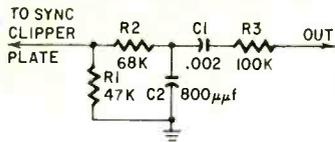


Fig. 10—Partial schematic of a Zenith vertical multivibrator circuit. Feeding sync to grid instead of plate causes faulty vertical lock.

Some odd troubles crop up as in all other stages. If there are two full pictures on the screen and the hold control has very little effect, look for a shorted capacitor in one of the time-constant R-C networks. For instance a shorted capacitor may change the time constant to only half of what it should be, and you will be able to get a double picture on the set. For a reliable test, one end of the capacitor must be disconnected. You can see the numerous parallel paths in the circuit which would foul up any resistance measurements taken with parts still connected.

Some tubes will give trouble, even though they test OK. For example, the 12B4 used as vertical output amplifier in certain Zenith TV sets will cause poor linearity, even though the screen is completely filled. Replace the tube for a quick test. In a Bendix T17 (with half of a 6SN7 and 6W6), the picture would hold fairly well. The "stop" action was almost normal. But, as the picture stopped, it would bounce up and down with a peculiar, slow rubbery bounce, almost as if it were suspended on springs! The cure? Replace the 6W6 output: apparently this tube had a wee gas content.

In some sync circuits you'll find parts values which might seem a bit strange, especially in a circuit handling 60-cycle pulses. An example of this is seen in

Fig. 9. If you find vertical sync troubles in sets with similar values, try rebuilding the integrator. Reduce R3 to about 27,000 ohms and increase C1 to about .01 to .02 μ f. This will increase the amplitude of the sync pulses applied to the oscillator and improve the hold action tremendously. Do not use too small a resistor for R3, or too large capacitor for C1. This will upset the time constant of the vertical oscillator, making the action jerky.

One final case history before we go. This was in a Zenith TV, using a multivibrator similar to Fig. 4. After replacing a leaky sync-coupling capacitor, the picture would roll up normally, lock in beautifully and was most exceedingly linear. There was only one small hitch: the point at which the picture locked so firmly in place was slightly off center (photo below). Try as we would, it would not lock where it was supposed to! (Remember, we just said that to some hard-headed old-timers all sync must be fed to the *grid* of a tube?) In desperation, we checked the circuit we should have checked first: the one we were working on. Sure enough, there was the sync-coupling capacitor, firmly soldered to the *grid*! (Fig. 10—Should have been on the plate!) Moral: when in doubt, always check the job *you just did*, before searching for more obscure troubles!

END



Feeding sync pulses to the grid instead of the plate (Fig. 10) locked in the picture with the blanking bar visible.



"Charlie says these speaker plans almost have him baffled."

THREE-speaker stereo is gaining in popularity. A center speaker, driven by the combined signal of the left and right channels, is added to the left and right speakers. This is in contrast to *three-channel* stereo, not yet available for the home, in which the center speaker is fed by a separate channel.

Several reasons have been advanced in favor of a center speaker:

▶ If the left and right speakers are angled wide to the listener's left and right, the center speaker tends to fill the hole in the middle.

▶ Center sound is a combination of the left and right channels. Combining them and feeding them to a center speaker serves to re-create center sound.

▶ The listener's position has less effect upon the stereo illusion when a center speaker is used. That is, he may sit closer to or farther from the speakers, or he may sit more distant from the center line between the end speakers, without losing the stereo illusion, as contrasted with the optimum position when only two speakers are used.

Whether these arguments are good or not, the fact remains that many stereophiles are incorporating or at least experimenting with center speakers. To save the cost of a third power amplifier, they often connect the center speaker across the stereo power amplifier as in Fig. 1.

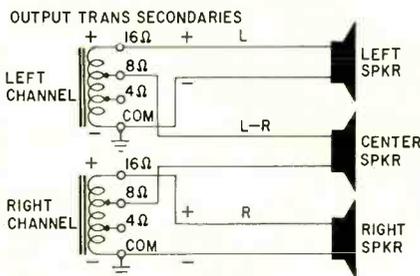


Fig. 1—Connecting center speaker to conventional power amplifiers can result in difference signal.

Unfortunately, this setup feeds a *difference* signal instead of a *sum* signal to the center speaker. Sometimes the difference signal produces results just as satisfactory as those we get from a sum signal. Often, however, the difference signal is unsatisfactory. This is apt to happen when a center microphone is used in recording and its output is fed in equal amounts to the left and right channels. Then the difference signal cancels the center sound.

To circumvent this problem, a number of stereo power amplifiers are now wired as in Fig. 2. The 4-ohm tap of each output transformer is connected to ground. Electrically, the 4-ohm terminal is the center tap of the secondary winding, so the output transformer is operated as a push-pull device. By connecting the center speaker to the 16-ohm tap of one output transformer and the common tap of the other, we get a sum signal.

It is possible to rewire conventional

add a THIRD SPEAKER the easy way

A few minutes will show you whether a third speaker will make your stereo system sound better

power amplifiers to operate as in Fig. 2. However, the values of the feedback network have to be adjusted to maintain the same amount of feedback as before the rewiring. This must be done on the basis of keeping the amplifier's gain

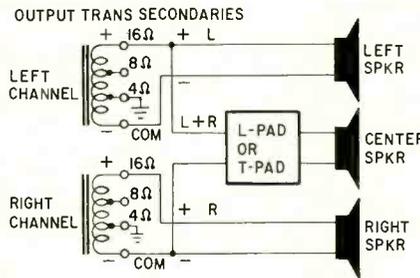


Fig. 2—Wiring a stereo power amplifier to produce a sum signal for the center speaker.

the same as it was prior to the changes. An audio oscillator and a vtvm are needed to measure gain.

For those using conventional power amplifiers for stereo, there is a much easier solution than rewiring the amplifiers, if their stereo preamplifier has a phase-reversal switch, as many do nowadays. This solution is illustrated in Fig. 3.

The phase reversal is only in one channel, let us assume the right one. When the phase switch is in its reverse position, the output of the right power amplifier is out of phase with that of the left. Therefore a sum signal is obtained when the center speaker is

connected to like terminals on the two power amplifiers (for example, to the 8-ohm taps).

Because the right amplifier is out of phase, the leads to the right speaker must be reversed, as shown in Fig. 3.

If the left and right speakers are connected to the 16-ohm terminals, it is advisable to connect the center speaker to the 8-ohm taps to get reduced output from the center speaker. If all three speakers have the same efficiency, the center one will have 3 db less output than the others, which is just about right for three-speaker operation. Operating the center speaker at a slightly lower level than the end ones maintains sound at the left and at the right, instead of tending to focus it all toward the center.

In a similar fashion, if the end speakers are operated from the 8-ohm taps, connect the center speaker across the 4-ohm taps.

If the center speaker's efficiency is not the same as that of the end speaker's, adjust the relative volume of the center speaker by operating it through an L-pad or T-pad.

The "easy solution" presented here requires only a few minutes to hook up a center speaker. Quite possibly you have an extra speaker in the house. Or you may be able to borrow a bookshelf type speaker for several hours from a friend. With this speaker, a few feet of wire and an investment of a little time, you can find out for yourself whether three-speaker stereo enhances your enjoyment. END

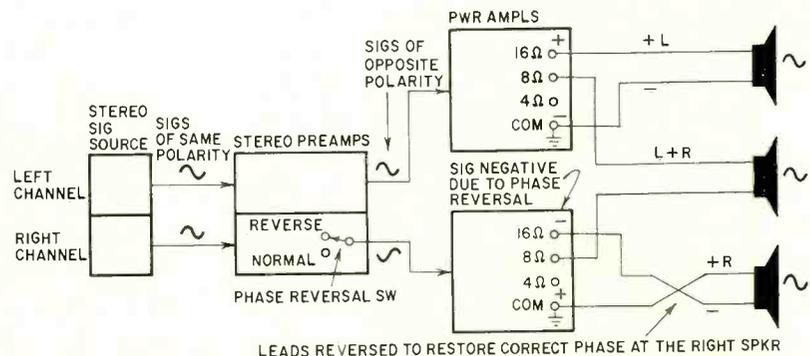


Fig. 3—An easy way to get a sum signal from conventional power amplifiers.

A

practical tester

FOR ELECTROLYTICS

THE best test for any product is one which evaluates its ability to do the job for which it was intended.

Therefore any good test method must simulate some typical operating condition of the product under test.

In its most common function as a power supply filter, the electrolytic capacitor receives current pulses from a rectifier. It stores these for delivery to the dc load circuits during the intervals between rectifier pulses. The rectified ac is thus smoothed to a continuous direct current—if the capacitance is large enough, or if several filter sections are used.

If there is too little capacitance, some of the rectifier pulses remain superimposed upon the dc output of the filter and produce what is known as "ripple." (Ripple is proportional to current drawn by the dc load and inversely proportional to the capacitance of the filter capacitors.)

The test circuit shown places the capacitor under test in typical service where it receives current pulses through the 1N2069 silicon rectifier. Between pulses it partly discharges through the 30,000-ohm load resistor or through about 1,400 ohms when the 1,500-ohm resistor is switched in parallel. With no capacitance connected to the test terminals, ripple voltage is 100% so the meter is set to 100% or full scale with potentiometer R4.

Any capacitance across the test terminals will tend to filter the rectifier output, thereby reducing the ripple voltage and the meter reading.

The 30,000-ohm load resistance provides a range of .03 to 6 μf and with the 1,500-ohm load in parallel, the range is 0.3 to 60 μf . Obviously, an open capacitor will not drop the meter reading; with a shorted capacitor, the meter will read zero. The reading will also be zero if an electrolytic is connected backward. The capacitor can also be damaged. Therefore mark the test terminals prominently to indicate polarity.

Circuit considerations

The meter circuit shown is a full-wave bridge rectifier type ac voltmeter fed through a .04- μf capacitor so that it reads only the ripple voltage. A 100- μa meter was used although any meter up to 1 ma can be used by changing values of capacitance and resistance to suit. The meter rectifier is a Conant catalog No. 1101 selenium bridge, selected both for economy and relative freedom from temperature effects, plus its suitability to this kind of circuit.

Transformer T is principally used for isolation from the line to avoid "fire-works." It is a small power transformer, rated at 117 volt primary and 125 or 150 volts secondary, and is attached with the secondary to the line. Its secondary (original primary) may deliver anything between 75 and 125 volts and should be rated 50 ma or more. If secondary voltage is greater than 75, the silicon rectifier should be a 1N2070.

Control R4 should be of the lowest resistance which in combination with fixed resistor R5 will permit setting the meter to full-scale on either range and on all line voltages likely to be present. As a suggestion, a 1,000-ohm control

By

H. B. CONANT *


may be tried, with 1,000 ohms for the value of R5. If the meter won't come up to full scale, increase the value of R5. Reduce it if the meter can't be brought down to full scale. [Note that .01 μf was used for C and 470 ohms for R5 in making the measurements for the table shown here.—*Editor*]

Calibrating the meter


Calibration will be simplified if the meter scale is calibrated 0-100, representing for calibration purposes 0-100% ripple. As there is a broad capacitance tolerance in commercial electrolytic capacitors, they cannot be used to give precise calibration, but may be close enough for practical use. Exact percentage of ripple depends upon the exact values of the load resistors.

After the tester is built, if possible borrow a pair of precision capacitance standards, say 1 and 10 μf , and find where they read on the two respective ranges. Assuming that each reads 30%

* Conant Laboratories, Lincoln, Neb.

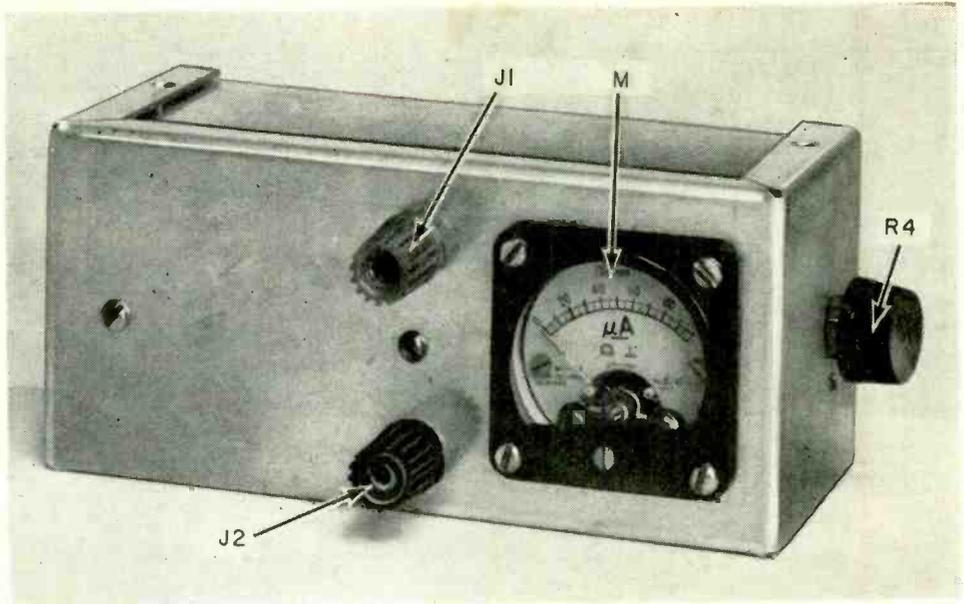

The practical capacitor tester.

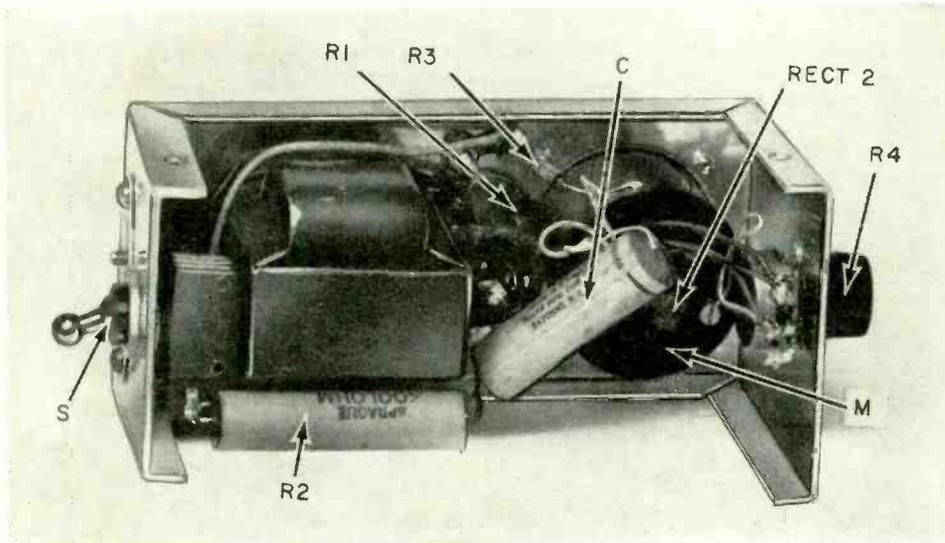

Capacitor checker, internal view.


The tester measures ripple voltages. Thus the larger capacitances read lower on the meter scale.

ripple on their respective ranges, then 0.5 μf and 5 μf will read 60%, 4 and 40 μf will read 7½%. Doubling the capacitance halves the ripple voltage. The response of the ac meter is essentially linear except at the extreme low end of the scale, so calibrations at the very low end will be only approximate.

Quality control

While this tester measures capacitance in terms of ripple voltage, its indications do tell whether a given capacitor is good or bad. For example, let us say an 8- μf capacitor reads 4 μf . Obviously it does not reduce the ripple voltage as well as 8 μf should, so it should be replaced.

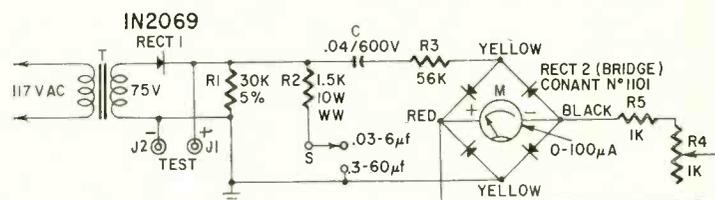Subject to small errors introduced by associated circuitry, this tester is practical for in-circuit testing. But don't try testing capacitors rated at less than 150 volts. And don't put it into transistor gear unless you want to ruin low-voltage components. END



METER READING vs CAPACITANCE

High Range		Low Range	
Meter	μf	Meter	μf
4	60	6	8
12	20	10	4
25	10	33	1
70	4	58	0.5
88	2	72	0.25
95	1		

The above readings were made by Mr. Queen of the *Radio-Electronics* staff. C was .01 μf and R5 470 ohms in his setup.

- R1—30,000 ohms, 5%, ½ watt
- R2—1,500 ohms, 10 watts, wirewound
- R3—56,000 ohms, ½ watt
- R4—1,000 ohms, pot (see text)
- R5—1,000 ohms, ½ watt (see text)
- C—.04 μf , 600 volts paper (see text)
- RECT1—IN2069 or equivalent, see text
- RECT2—meter rectifier, bridge type (Conant No. 1101, or equivalent)
- S—spdt toggle switch
- M—meter, 0-100 μa , see text
- T—transformer, see text (Stancor PA-8241 or similar type)
- J1, 2—jacks or binding posts
- Case, cord, miscellaneous hardware.

BENCH

Specifications: Checks all capacitors from approximately .05 to 60 μf . Can be used for in-circuit testing in many circuits. Performance data: Tested by a RADIO-ELECTRONICS staff member, this capacitance checker was found to work reliably, and to be a simple, accurate and useful instrument.



TESTED

NEW stereo PICKUPS

In pre-stereo days, many of the finest phonograph cartridges used a moving coil as their generating element.

Although moving-coil cartridges in general have lower output voltages and tend to be more fragile than other types, their lower impedance makes them relatively immune to induced hum (from nearby phono motors or power transformers) as well as to the shunting effects of cable capacitance at high frequencies.

At present, there are few moving-coil stereo cartridges. Two of these, both of very high quality, are the Grado and the Neumann.

Grado

The original Grado stereo cartridge (now called the Master) was described in *RADIO-ELECTRONICS* (November, 1958, page 88). Current production models of the Grado Master, though similar in construction to the unit described in the earlier article, have been further refined. The two coils, each of 1,000 turns of extremely fine wire, are wound on a hollow plastic cube approximately 1/16 inch square, which is molded in one piece with the stylus arm (Fig. 1). The coil assembly is mounted in a special rubber grommet which provides uniform compliance in all planes.

The coils are located in a uniform field supplied by a powerful permanent magnet. When the coil structure rotates, a voltage is generated in each coil (proportional to the recorded velocity in the corresponding channel).

The new Master cartridge has an output of 6 mv at 10 cm/sec. The effective stylus mass has been cut in half, from 0.8 to 0.4 milligram, which, in turn, extends the high-frequency response of the cartridge. The manufacturer's specifications for frequency response are 10-50,000 cycles (with no tolerance specified).

In other respects, the present Grado Master cartridge is identical to the earlier models. The two outputs are balanced to within 0.5 db over the audio range. Recommended tracking force is 3 grams and the load resistance is non-

Part II—The Grado Master, Neumann DST Dynaco TA-12, G-E VR-22, London-Scott 1000

By JULIAN D. HIRSCH

critical so long as it is greater than 5,000 ohms. Channel separation is greater than 25 db. A tiny radioactive element embedded in the case of the cartridge behind the stylus ionizes the air in the vicinity of the record surface. Static charges are reduced and so is the amount of dust that accumulates on the record.

The Grado Custom stereo cartridge is a less expensive version of the Master for use in record changers. Its coils are wound with more turns of slightly heavier wire. The output, therefore, is greater than that of the Master series—approximately 7 mv at 10 cm/sec.

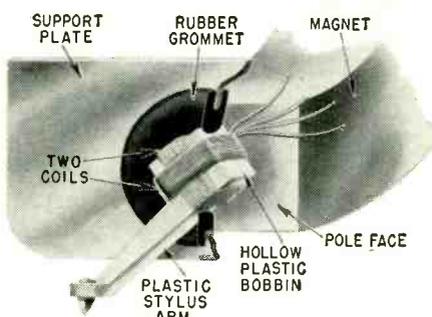


Fig. 1—The coil bobbin and stylus arm of the Grado Master are one piece.

The effective mass at the stylus is 0.6 milligram (reducing the claimed upper limit of frequency response to 40,000 cycles). Channel separation is in excess of 20 db. In all other respects, the Grado Master and Custom cartridges are similar.

The Grado Master cartridge is priced at \$49.50 and the Custom at \$32.50.

Neumann DST

The Neumann DST stereo cartridge is the product of a West German manu-

facturer of professional-quality microphones (sold in this country under the names of Telefunken and Neumann). It is imported by Gotham Audio Sales Co., 2 W. 46 St., New York 36, N. Y.

The Neumann cartridge is a moving-coil type with a tubular torsion bar mounting the stylus at one end and the two generating coils at the other end. The entire stylus bar is covered by a thin rubber membrane (visible in the photo). This membrane serves a triple purpose: It keeps dust and foreign matter from entering the cartridge, protects the delicate moving system from damage and provides a slight amount of stylus damping. Only the stylus jewel protrudes from the rubber membrane.

The impedance of the DST cartridge is extremely low—about 18 ohms—and it will work satisfactorily into any load impedance greater than 50 ohms. The output is correspondingly low, 1.05 mv at 7 cm/sec. This makes a stepup input transformer a virtual necessity. Gotham offers the Beyer TR147C transformer which has a 15-to-1 stepup ratio and a response from 30 to 20,000 cycles within 1 db. Two are needed for stereo operation.

The frequency response of the Neumann DST cartridge is 30 to 15,000 cycles ± 2 db. Channel separation exceeds 30 db at mid-frequencies (1,000 to 3,000 cycles) and is better than 12 db at 10 kc. The stylus-system compliance is 3.6×10^{-6} cm/dyne. The recommended tracking force is 4 grams and the stylus is a diamond with a 0.6-mil tip radius.

The DST is designed to fit arms having the plug-in connection used on some professional European equipment. Typical arms are the Neumann TA-2 or the Danish Ortofon (known in this country as the ESL Professional).

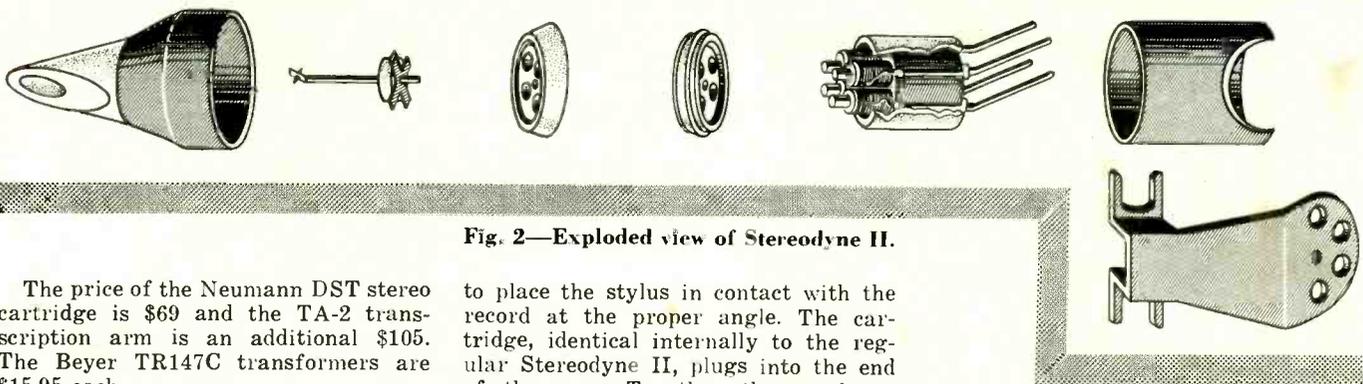


Fig. 2—Exploded view of Stereodyne II.

The price of the Neumann DST stereo cartridge is \$69 and the TA-2 transcription arm is an additional \$105. The Beyer TR147C transformers are \$15.95 each.

Variable reluctance

The variable-reluctance principle (pioneered by General Electric in its early monophonic pickups) is still widely used in stereo cartridges. In a variable-reluctance cartridge, a fixed magnet supplies a magnetic field which links two or more fixed coils (in a stereo cartridge). An air gap is built into the magnetic circuit and the stylus moves an iron armature to vary gap width. This causes a change in *reluctance* (the magnetic equivalent of electrical resistance). The flux variation through the coils generates a voltage proportional to the stylus velocity. Thus, the name—variable reluctance.

Dynaco TA-12

The Dynaco B&O Stereodyne II cartridge is virtually identical to the one described in *RADIO-ELECTRONICS*, March, 1959, page 83. It has four coils and four pole pieces arranged to form a square (Fig. 2). The stylus moves an X-shaped armature, varying the flux to the two coil sets.

The chief changes in the present Stereodyne models have been to improve the stylus-system damping. The same basic cartridge, however, has been incorporated into an interesting integrated pickup design known as the TA-12.

The arm is tubular with the front portion angled downward and inward

to place the stylus in contact with the record at the proper angle. The cartridge, identical internally to the regular Stereodyne II, plugs into the end of the arm. Together they make a strange-looking combination.

The pivot design of the Dynaco arm resembles the gimbals used to support the rotor of a gyroscope. The inner ring is pivoted at top and bottom to allow lateral arm motion while the arm itself is pivoted from the sides of the inner ring for vertical motion.

The counterweight at the rear of the arm exactly balances the cartridge and is offset to the side opposite to the head offset. As a result, the arm (being fully balanced) is not affected by a turntable that is jarred or is not level. The downward tracking force is derived from a spring whose tension is adjusted by sliding a plastic collar along the arm. Calibration lines indicate stylus force (from 1 to 4 grams). The manufacturer recommends a force of 2 to 3 grams, which is enough for most installations.

The cartridge leads run through the pillar supporting the pivot assembly and are fully shielded. Since the cartridge is encased in Mu-metal, the result is a very low hum level.

The frequency response of the Dynaco TA-12 is rated at 30 to 15,000 cycles ± 3 db. The output voltage is 7 mv per channel at 5 cm/sec. The compliance is 5×10^{-6} cm/dyne in all directions due to the symmetrical design of the cartridge. The moving mass is less than 3 milligrams. Recommended load resistance is 47,000 ohms.

Price of the Dynaco TA-12 integrated stereo pickup is \$49.95.

G-E VR-22

The VR-22 is the improved version of the G-E model GC-5 and GC-7 stereo pickups (*RADIO-ELECTRONICS*, October, 1958, page 49). In all fundamental respects, the new cartridge is identical to the original version.

The VR-22 series is available in two models, the VR-225 with a 0.5-mil diamond stylus for quality pickup arms and the VR-227 with a 0.7-mil stylus for record-changer operation.

The stylus assembly of the VR-22 cartridge has been improved—a new damping-block design improves tracking of high-level passages. Mu-metal shields around the top and front of the cartridge, as well as the coil assembly, minimize hum pickup.

Most of the performance specifications of the VR-22 are identical to those of the original Golden Classic cartridges. A notable improvement has been made in channel separation (which is as great as 30 db at mid-frequencies) and in channel balance. The outputs of the two channels are within 1 db of each other at 1,000 cycles and are closely matched over the entire frequency range.


The response of the VR-225 is rated at 20 to 20,000 cycles ± 3 db, and the VR-227 at 20 to 17,000 cycles ± 3 db. The output of both cartridges is 6 mv per channel at 5 cm/sec. The lateral and vertical compliances of the VR-225 are 4×10^{-6} cm/dyne and 2.5×10^{-6} cm/dyne respectively. For the VR-227, the compliances are 3×10^{-6} cm/dyne and 2×10^{-6} cm/dyne. Recommended tracking forces are 2 to 4 grams for the VR-225, and 5 to 7 grams for the VR-227.

The price of the VR-225 is \$27.95; the VR-227, \$24.95.

London-Scott 1000


In an earlier article (*RADIO-ELECTRONICS*, November, 1958, page 83), the London-Scott 1000 integrated pickup was described briefly. It had just been introduced and only sketchy information was available. This British unit is unique in being a true vertical-lateral pickup instead of the 45-45 type we are accustomed to.

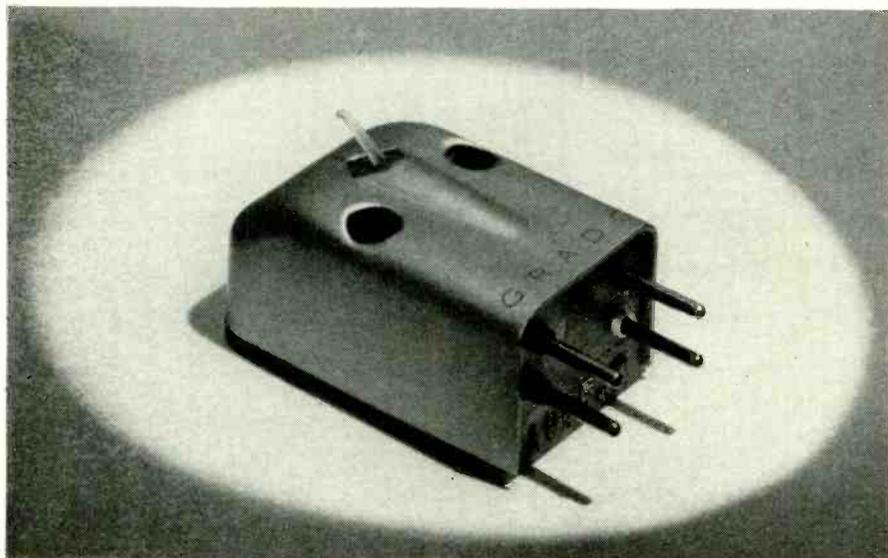The arm is anodized aluminum with needle type pivots in the vertical and




The Grado Custom.

Dynaco Stereo-
dync TA-12.

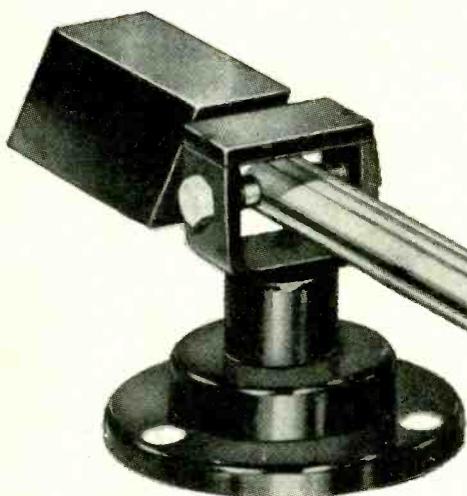

London-Scott mounted
on its arm.

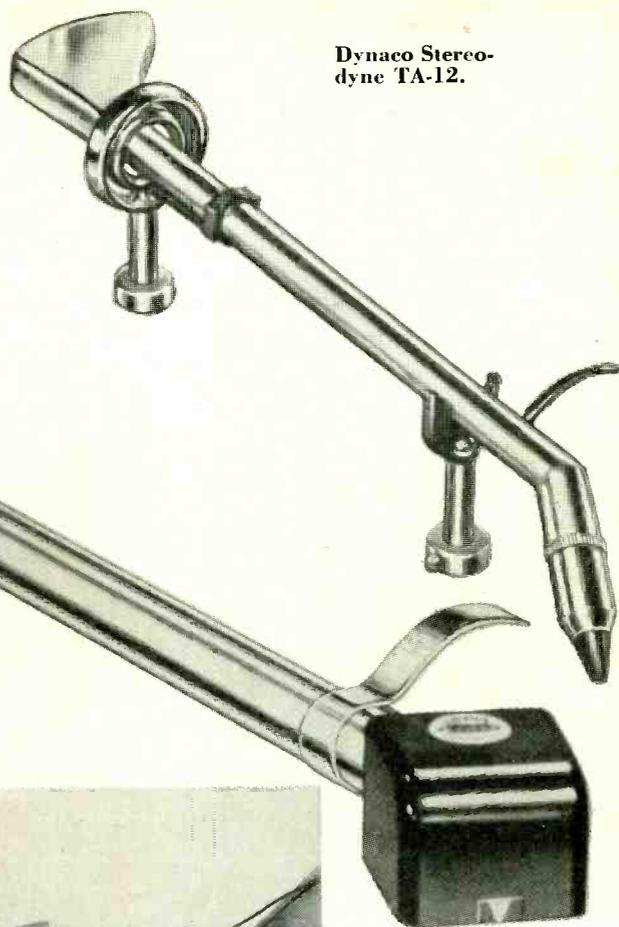

ball bearings in the lateral plane. Its height can be adjusted to accommodate various turntables. The counterweight is factory-set for a 3.5-gram tracking force. A small amount of viscous damping is used in the arm to damp its low-frequency resonance (which occurs at 14 cycles). The cartridge clips on to the arm.

The London-Scott 1000 is a variable-reluctance pickup. Two sets of coils are linked by the cartridge's magnetic field. The L-shaped armature is of magnetic material and forms a part of the magnetic circuit for both sets of coils.

Fig. 3 is a simplified sketch of the pickup. The complete magnetic structure, including pole pieces, is not shown. The single lateral coil and two vertical coils are identical, so that a given


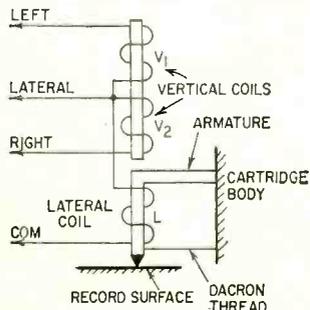


Fig. 3 — Interior of the London-Scott 1000 showing coil connections.

stylus velocity in the appropriate plane will generate the same voltage in its corresponding coil. The two vertical coils are connected in opposition with their junction connected to one side of the lateral coil. The other end of the lateral coil serves as a common output lead for all signals.

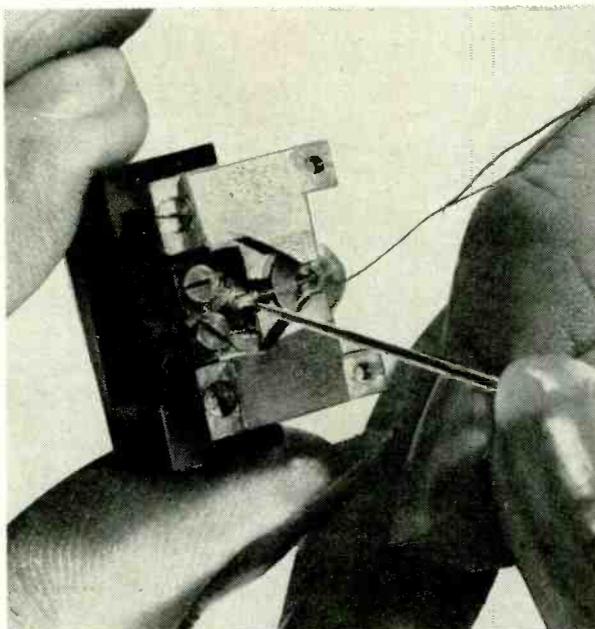A purely lateral motion of the stylus will induce a voltage in the lateral coil, but not in the vertical coils. Under these conditions, the same output voltage will appear at all three output terminals (LEFT, RIGHT and LATERAL). On the other hand, a purely vertical stylus motion will not generate a voltage in the lateral coil, but will develop equal and opposite voltages in the two vertical coils.




Drop of cement is used to fasten the Dacron thread to the London-Scott cartridge body.



General Electric VR-22.

In stereo operation, with the 45-45 system of recording, modulation of one groove wall will generate equal voltages which may be called L, V_1 and V_2 . Measured between the common lead and the left-channel output (assuming common and right-channel outputs will appear $(L - V_2)$ or zero volts. This electrical matrixing converts the vertical-lateral coil outputs into equivalent channels of a 45-45 system.

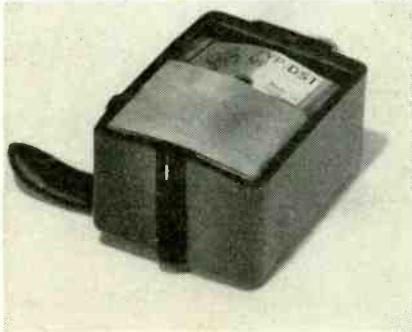In this type of cartridge, it is not necessary to parallel the left and right outputs to cancel vertical output when playing monophonic records. The output is taken from the lateral coil only and the vertical output is ignored.



Neumann DST showing membrane.

A Dacron thread is shown in Fig. 3. This is needed to restrain the stylus motion on the longitudinal axis (due to frictional drag on the record surface). It has no effect on the vertical or lateral motion of the stylus.

A bottom view of the cartridge, uncased, is shown in one of the photographs. The lateral coil is visible and the two vertical coils are hidden. The pole pieces direct the magnetic field through the coils, via the armature, which can be seen protruding (tip down) through the coil bobbin. The Dacron thread can also be seen.

The stylus-assembly compliance is in the order of 3.5×10^{-6} cm/dyne. The moving mass has been reduced to a very low value, less than one milligram. This places the high-frequency armature resonance well above the audio range and results in smooth response from 20 to 20,000 cycles. Output is 4 mv per channel. Channel separation is better than 25 db at mid-frequencies. The stylus has an 0.5-mil tip radius.

The London-Scott 1000 stereo pickup sells for \$89.95 complete with arm rest, cables and hardware. TO BE CONTINUED

"TRIPLETS, MADAME"

Doctors can now say it will be triplets or twins, or just a single baby, if encephalographs are taken during the expectant mother's fifth, sixth or seventh month. Research described in the *Journal of the American Medical Association* revealed that accurate diagnosis of the number of tiny hearts beating can be made during that period, with less certain determination earlier. Naval doctors C. A. Novotny, W. K. Hass and D. A. Callagan did not say they could tell if the babies would be boys or girls!

DUO-JUNCTION

By I. QUEEN
EDITORIAL ASSOCIATE

If you read Garner's article* on the G-E Unijunction transistor or other literature on this remarkable device, you know how useful and versatile it is. On the other hand, if you read the latest parts catalogs, you probably know that the Unijunction sells for about \$15. Though well worth its price (it's made of silicon and dissipates nearly 500 mw), it is beyond the financial reach of many experimenters.

It is not generally known that 2 junction transistors can be directly coupled to show results like those of the Unijunction. For want of a better name, I have dubbed it the "duo-junction." For more theory and schematics on the two-transistor combination, consult *The Junction Transistor and Its Applications* (The Macmillan Co.),

plementary pair of transistors—one p-n-p and the other n-p-n. A recently announced pair, the 2N217 and 2N647, is suitable. After considerable experiment, I found Fig. 2 an efficient circuit for square-wave generation. Waveform is excellent. With a .01 unit for C, the frequency is about 1,200 cycles. With a larger capacitor, the frequency drops. Use about 0.2 μ f for 40 cycles.

For the transformer I used a tiny SSO-9 (UTC). A 6V6 output transformer also served well here.

In Fig. 2, R1 limits the emitter current. Potentiometer R2 adjusts the wave's symmetry and stability, and also varies frequency to some extent. R3 is variable and adjusts amplitude. If R3 is set too high or R2 too low, oscillations tend to cease abruptly. They resume when these controls are reset properly or if the battery circuit is opened and closed again.

For pulse generation, a simpler circuit is sufficient. The transformer may be shorted out since it is not needed. The same output terminals (A-A) are used as before. The waveform is now identical with that shown in Fig. 3. Pot R2 controls frequency over a very wide range.

For sawtooth generation, again short out T, but use the B-B output terminals. The resulting waveform will be identical with that shown in Fig. 4.

The experimental square-wave generator is assembled on a 2 1/4 by 4 3/4-inch baseboard of heavy perforated plastic (made by Vector). Both transistors are plugged into the same seven-pin in-line socket. The center pin is not used.

The duo-junction seems to be a good substitute for the Unijunction in many respects. Of course, it is not equal in power dissipation or temperature tolerance. Why not connect up one of these circuits and give it a try? END

Fig. 1—Unijunction operating curve.


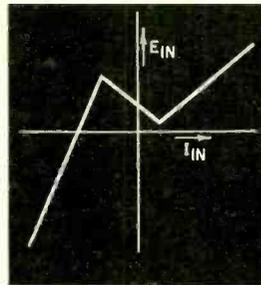


Fig. 2 (below)—Two-transistor duo-junction circuit.

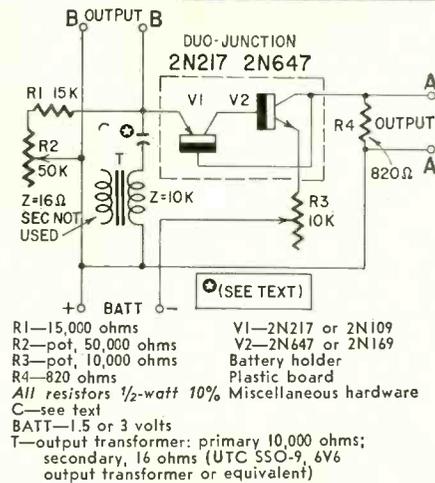

edited by E. Wolfendale, page 292. Also refer to the patent column, page 117 of this issue.

Briefly, the Unijunction is a three-lead transistor with a negative-resistance N-shaped characteristic (Fig. 1). Thus it is a natural oscillator and requires few parts to generate pulse, sawtooth or square waves. Not having a Unijunction here, I set up the two-transistor "duo-junction" and found it gives excellent results.

The duo-junction requires a com-

*July, 1957, page 91.

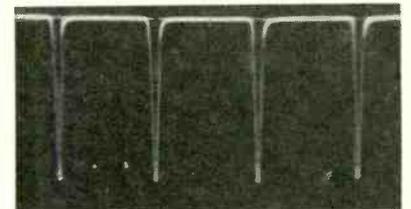



Fig. 3—Pulse generator waveform.



Fig. 4—Sawtooth generator waveform.

SINGLE TRANSISTOR

OPERATES EIGHT-INCH SPEAKER

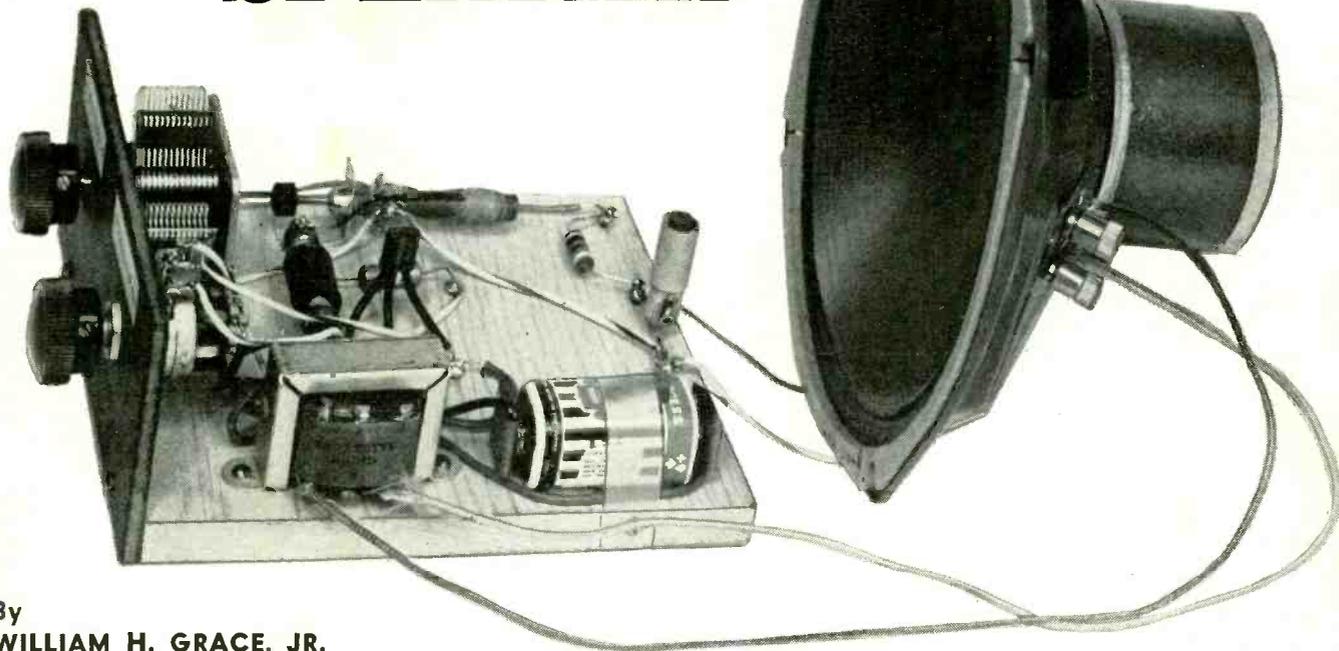

By
WILLIAM H. GRACE, JR.

Breadboard model of receiver next to 8-inch speaker.
Unit is quite small even though parts are spread out.

THERE is no gimmick in the title—this simple little single-transistor radio has been tested in various localities and has repeatedly given a good report of itself. Tone quality is excellent and volume is truly surprising for the few components employed.

An efficient outside antenna and a good low-resistance ground *must* be available for loudspeaker results as there is no provision for rf amplification in the circuit. An antenna about 75 to 100 feet long plus a waterpipe ground makes a combination that gives adequate volume for a large-sized room (within about 15 miles of local broadcasting stations). Actual antenna size will depend upon location and the field strength of signals in a given area. For example, 18 miles north of New York City, a 60-foot flattop brings in eight locals with fine quality and volume. In the uptown region of the city, a 45-foot length of lamp cord dropped out a window of a tall apartment house picked up 10 stations. Reports on the basic circuit from Richmond,

One transistor and a diode using Interflex principle result in good tone quality and volume

Va., and the Chicago area were also favorable.

Circuit history

The schematic shows the two parts of the circuit. The first is the tuned or resonant section; the second is the detector-amplifier or output section. There is only a single connection, a small coupling capacitor, between them. No ground return is provided as none is required. While this system may appear unconventional to some readers, it is not a new idea and was often used in the days of spark in standard wave-meters and receiving circuits. It is a most effective method of coupling and was chosen in this case for simplicity.

The detector-diode is connected direct to the base of the transistor without any series capacitor. This is not a new idea either. The Interflex principle was introduced by Hugo Gernsback, the editor of this magazine, some 35 years

ago. He suggested in 1925 that a crystal detector be substituted for the conventional grid-leak-and-capacitor combination used in De Forest tube circuitry for improved quality and superior gain over that of existing circuits. He developed the ingenious Interflex receiver which many of the old-timers will recall building in the early 20's. The writer himself built such a receiver in 1926 and was favorably impressed with the results obtained with a single tube.

Shortly after the debut of transistors, the Interflex was adapted to use with both the point-contact and junction type transistors and the August, 1955, *RADIO-ELECTRONICS* (page 54) printed an article on it. The circuit became a popular one and is widely used today in various applications—receivers, field-strength meters and, in modified form, in certain TV video-detector-amplifier circuitry. All present transistor circuits in which a diode


replaces the usual base series capacitor are, of course, merely transistor adaptations of the original Interflex idea.

Construction

The receiver may be assembled in any way the builder elects. The author has constructed both breadboard and miniature versions with equally good results. It is easy to house the small number of parts in a case whose dimensions are slightly less than those of a postcard. No socket is required for the transistor because the adjacent parts provide sufficient support. Wiring is done with No. 18 copper wire, either solid or stranded. The soldered joints must be made with care so that cold joints will not cause trouble later.

Parts assembly is not difficult; the order closely follows that shown in the circuit diagram. The front panel is drilled for mounting the volume control and tuning capacitor (and output jacks if desired). The first rf choke (RFC1) is soldered directly to the antenna and ground terminals. If the set tunes broadly after all other adjustments have been made, reverse RFC1's connections. On the breadboard model (shown in the photographs), the battery is held in place by a plastic strap and a piece of sponge rubber.

Try different values for C1 to find the best compromise between good volume and desired selectivity. Somewhere between 15 and 30 μf would be a good working value to try out first. If you have a small air trimmer on hand, wire it into the circuit to give an approximate idea of the value required. Substitute a fixed capacitor of the same size in the finished rig. C3, also a very small capacitor, serves as the only coupling link between the resonant section of the receiver and the detector-amplifier section. The exact value is again a compromise between volume and selectivity—too large a value will broaden the tuning; too small a value will diminish volume. A starting value of about 5 to 10 μf is a good beginning to work from. I solved the problem by twisting together about 2 inches of No. 18 solid enamel-covered wire and

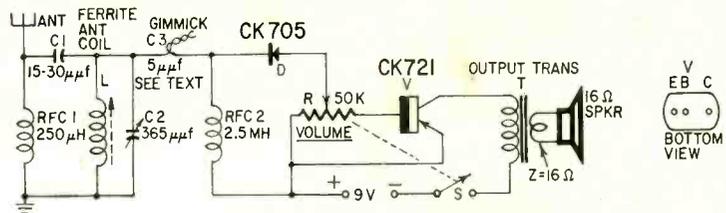

Schematic of single-transistor receiver.
A good external antenna is required.

- R—pot, 50,000 ohms with switch
- C1—15 to 30 μf , ceramic, see text
- C2—365 μf , variable
- C3—5 μf (approximately), see text
- L—loop antenna, ferrite core
- RFC1—250 μh , see text
- RFC2—2.5 mh
- D—CK705 (or 1N34 or equivalent)

- V—CK721
- T—output transformer, see text
- S—spst switch on R
- BATT—9-volt battery (Burgess P6M or equivalent)
- Speaker, 8 ohms, see text
- Miscellaneous hardware, knobs (case or board and panel, depending on size desired)

then clipping off $\frac{1}{4}$ -inch lengths until the best value was found. This completes the front end.

One end of the second choke RFC2, is connected to the lower end of the volume control; the other end to the junction of C3 and the diode. Various diodes were tried, but the CK705 did as good a job as any tested. A 1N34 is also suitable. The volume control may be of almost any value between 25,000 and 200,000 ohms, but be sure it has an attached switch to turn off the battery when the set is not in use. If you are in an area of low field strength, the volume control may not be needed. But, as this receiver is designed to function in areas of medium to high field strength, the volume control is an asset.

The transistor is a Raytheon p-n-p junction type, the CK721. Many others (2N106, 2N109 and 2N64) were found satisfactory with the exception of the CK722. An n-p-n transistor may also be employed in this circuit, but the polarity of the diode (and battery) must be reversed. If the diode polarity is not correct, the circuit will not function.

In the miniature version, the output transformer was mounted inside a separate speaker case to reduce the space needed in the receiver case.

Speaker selection

Naturally, the actual output of a single-transistor receiver is but a few


milliamps. Therefore it is very important to use a good output transformer and sensitive PM speaker. The very small output transformers are not suitable for use with this circuit and much better results will be obtained from one of the universal types such as the Stancor A-3856 or the Lafayette TR-12.

Proper impedance matching is most important for both volume and voice quality. The speaker should have a heavy magnet and high efficiency in converting the available electrical energy into sound. Several high-quality units were tested with excellent results when installed in an acceptable enclosure, but good PM units and baffles are expensive. After a search for a combination that would deliver the goods without being too expensive, the Lafayette SK-130 was chosen. Mounted in a Karlson 8-inch enclosure, it gave results equal to some units costing several times as much. This is a British speaker with a magnetic flux density of 13,000 gauss and a 1-inch-diameter voice coil. Its impedance is 16 ohms and could be well matched with either output transformer mentioned above. The Karlson baffle is one of the better enclosures tried by this author. However, any good PM unit in a correctly designed baffle should produce good quality and volume with this tiny receiver.

It being a very simple circuit, not many things can go amiss, but any experienced builder knows that errors do creep in once in a while. It often takes as much know-how to get the most from a very simple receiver as it does from much more complicated rigs. A small loss of efficiency in complicated jobs is seldom apparent but, in receivers with low audio output, even a little loss is too much.

It is a wise move to place a meter in the collector circuit when a strong signal is being received and check the current drain. Readings of 10 to 20 ma are common, but it is desirable to limit the current to about 10 or 15 ma with the volume control under average operating conditions. The set has been run for periods well over an hour at better than 20 ma with no damage to the transistor.

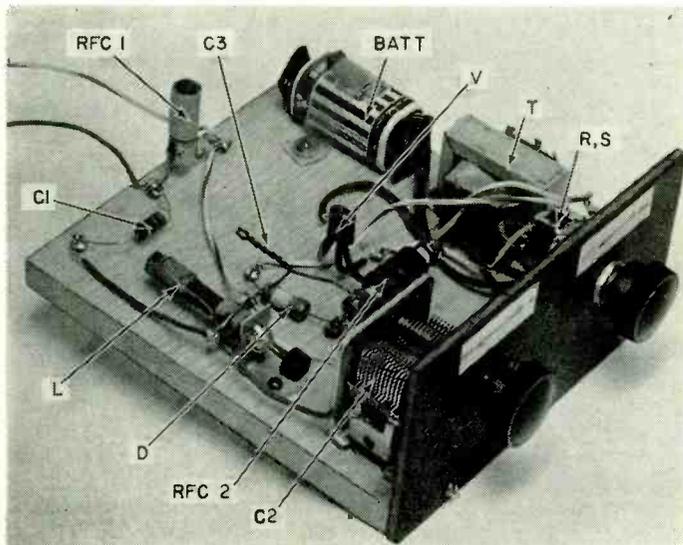The constructor may experiment with voltages higher than the 9 volts used by the author as long as the transistor specifications are not violated. I used 15 volts in some tests with an increase in volume, but transistors can be ruined



Breadboard model of single-transistor unit. Notice the "gimmick" capacitor, C3.

WINDING A

TRANSISTOR-POWER-SUPPLY

TRANSFORMER

By R. L. WINKLEPLECK

TRANSISTOR converters of low-voltage dc to high-voltage ac (or dc) have many obvious advantages over the conventional vibrator type power supply. They're compact, have no moving parts and nothing to wear out. They introduce little or no noise into associated circuitry since the square-wave output is easy to filter, and they are very efficient when properly designed.

The wide selection of power transistors which combine relatively high alpha under load with comparatively low cost is rapidly sounding the death knell for vibrator power supplies.

The only serious drawback is the high cost of transistor power transformers, which must be correctly designed for high efficiency. This cost bottleneck can be eliminated by rewinding an old transformer from the junk-box. It is not claimed that such a re-wound transformer is the full equal of the expensive commercial units. But it is possible to get fairly high efficiencies (with good design). This makes the home-rolled version very attractive if the thickness of your pocketbook is an important consideration.

Basic circuit

Fundamentally, a transistor power converter resembles a blocking oscillator or a multivibrator. The collectors of two transistors are connected to a center-tapped transformer primary. A feedback winding is connected to the two bases in such manner that the conducting transistor is biased forward and the nonconducting one cut off as long as current through half the primary winding continues to rise. This bias is maintained until the transformer saturates and can no longer supply the drive signal. At the instant of saturation, the base currents reverse. The conducting transistor now cuts off, and the other one is driven into conduction. This action is continuous and repetitive, producing an essentially square waveform. The secondary output voltage is proportional to the winding ratio. The frequency depends on the supply voltage, the primary inductance of the transformer and peak collector current. If the saturation flux of the transformer core material is known, it is possible to design for a specific frequency.

In the absence of this information,

The high cost of special transformers need no longer stop you from building your own transistor power supply

it is still possible to design an efficient power supply. It can be made to fit the transistors available and the input and output voltages and currents desired, but the frequency will "fall where it may." This is not too important if you plan to rectify the output.

Saturation test

First, an old transformer must be selected. The larger the transformer, the higher its potential power output. The frequency will be relatively high, however, and good results are possible

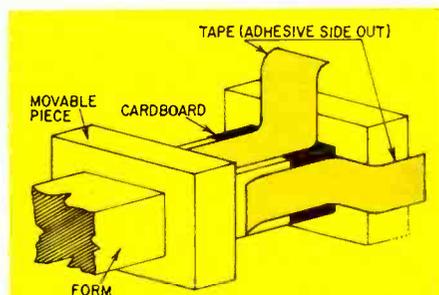


Fig. 1—Place strips of tape (sticky side out) on form before winding any coils.

with almost any old filament or audio transformer with a core area of at least $\frac{1}{2}$ square inch. Dismantle the laminations, remove the old windings and make a matching winding form. This may consist of a 4- to 6-inch strip of wood with the same cross-section as the transformer core. A small square of thin wood is nailed across one end. Prepare a second piece with a square hole. This can be slid onto the core form and fastened in position to provide a winding area just the height of the window in the core (see photo). A strip of light cardboard (the width of the coil) is wrapped around the form and held in place with a piece of tape.

Three temporary coils wound on the form will be used to get information on core properties. Scramble-wind a 30-turn winding on each end of the form with enameled wire (which may be salvaged when the transformer is disassembled). The wire size used in these coils is not important. The center of the

core area is wound with 30 turns of heavy enamel wire—No. 20 or larger is suitable. The completed three windings are now removed from the form and the transformer laminations re-assembled around them. If a couple of strips of tape are laid across the form sticky side out (Fig. 1) and then folded across the completed windings, they will be much easier to handle.

Now for the tests! You'll need a storage battery (or other heavy-duty source) of the voltage which you plan to use with the power supply, a heavy-duty rheostat and a dc ammeter. These are connected in series to the heavy center test winding so the current to the winding can be varied and measured. A low, 60-cycle voltage is connected to one of the end windings. This should be 1 volt or less, otherwise it will confuse the reading. The 0.75-volt filament tap of a tube tester may be used or a suitable voltage divider may be temporarily hooked across the output of a spare filament transformer. The vertical leads from an oscilloscope are attached to the third coil and a horizontal scope lead is attached to either end of the ac winding (Fig. 2). Set the scope for horizontal input and apply the ac voltage.

Adjust the horizontal and vertical gain controls to produce a rectangular trace similar to Fig. 3-a. The figure may be reversed but this isn't important. This trace is the first cousin of the transformer's hysteresis loop. Now apply and gradually increase the dc. Notice that the height of the scope pattern shrinks as in Figs. 3-b and c. Increase the direct current until the almost-horizontal lines meet and cross as in Fig. 3-d. Note the meter reading. This is the current required to saturate the core. With this information it's time to start a little pencil work.

Calculating windings

Now we have to decide what transistors to use. When the switching capabilities of a transistor are not known, they can be assumed to be approximately five times their class-A amplifier ratings. The collector voltage

should be rated at $2\frac{1}{2}$ times the supply voltage you plan to use.

Divide the ampere-turns for saturation (determined by the test) by the collector-current rating of the transistor chosen. This gives the number of turns for each *half* of the collector winding since each transistor operates into half the winding. The wire size required may be determined from a reference source such as the wire table in the *ARRL Handbook*.

The center-tapped base-bias winding should consist of one-fifth the turns of the *total* collector winding. Very little current flows in this coil, so No. 26 or 28 wire may be used.

To get the number of turns for the output winding, multiply total collector turns by the desired output voltage, then divide by twice the supply voltage. This gives the open-circuit output voltage. The number of turns must be increased by from 20% to 50% if this voltage level is to be reached under heavy load. Wire size for the secondary may be quite small. In fact, it *must* be small if the windings are to fit the transformer window. You can determine the secondary wire size from the wire table. Pick out the smallest wire that will carry the load.

Winding the coils

The coils are wound on the wooden form which has first been prepared with the cardboard strip and the short lengths of binding tape placed adhesive-side out (Fig. 1). Enameled wire is used for all windings. It should be laid on in smooth layers; this way it will occupy far less space than if scramble-wound. The secondary goes on first. If some kind of winding jig can be fashioned from a hand drill or a lathe, winding the coils will be a lot easier. Leave plenty of wire for leads. Wrap the secondary with a layer of tape and then do the center-tapped base bias winding. The collector coil is wound last. The tape strips are then pulled tightly across the windings, a

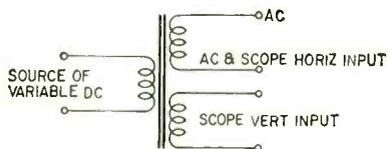


Fig. 2—Test circuit used to determine transformer's saturation point.

final protective layer of tape is applied and the completed winding is slid off the form. Reassemble the laminations around the new winding.

If you intend to experiment with the number of secondary turns (to find what is required to put out the needed secondary voltage *under load*), the secondary may be wound last. However, the efficiency is reduced somewhat by this arrangement.

When you take the trouble to prepare an accurate winding form and wind the coils neatly, there should be no difficulty in keeping the overall size of the windings small enough to fit the window of the transformer core. It's always a good idea, however, to use the smallest

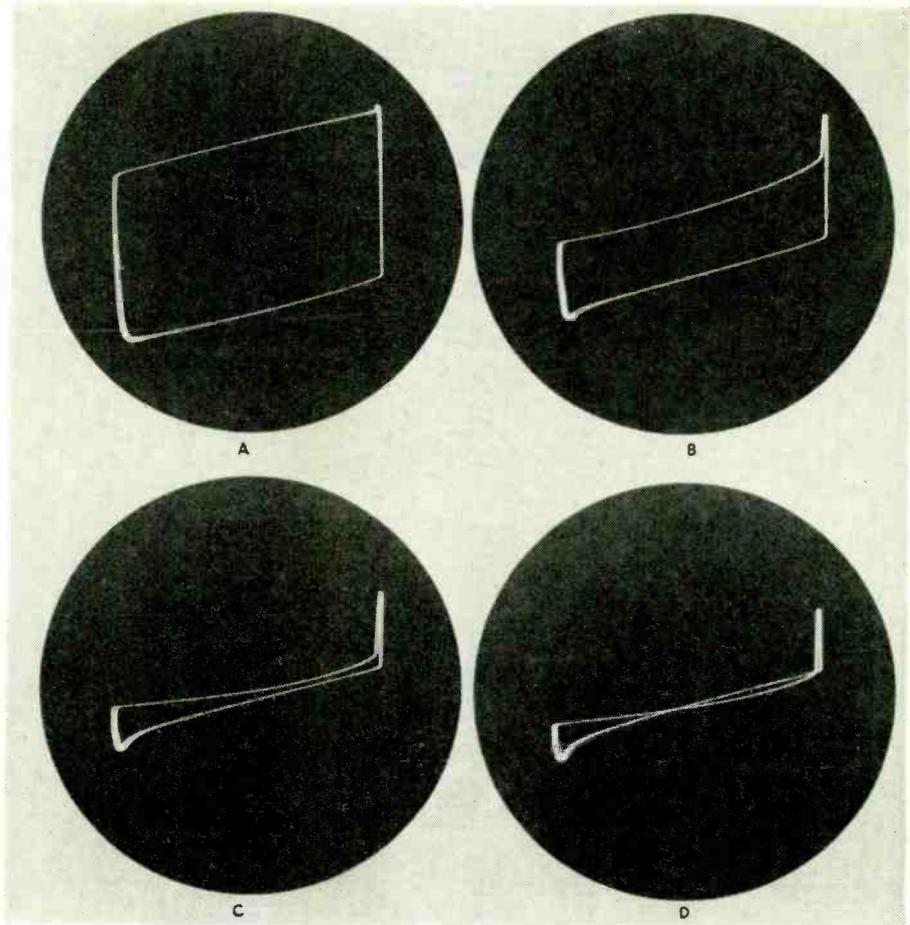


Fig. 3—a, b, c—scope patterns obtained as the transformer nears the saturation point; d—when lines cross, transformer is saturated.

wire which will carry the calculated current using the wire tables as your guide. Furthermore, place each turn tightly against its neighbor and keep the layers orderly.

Try it out

There are many transistor power supply circuits but the one shown in Fig. 4 is simple and dependable. It uses two resistors in a voltage-divider arrangement to assure easy starting under load. The high-voltage capacitor (C1) across the secondary is to reduce spikes which might damage the transistors. A high-capacitance low-voltage capacitor across the supply voltage will eliminate hash in associated equipment (if any is noted). The ratings of the rectifiers and the capacitors are determined by the output voltage and current.

Connect the transformer as shown and apply 1 or 2 volts. It should start to oscillate immediately. Use a scope or voltmeter across the secondary to check. If nothing happens, reverse the feedback leads (to the transistor bases), re-apply power and you should be in business.

Examples

These directions have purposely been given without examples so that you might use them to build a power supply to fit exactly your needs with the materials at hand. A couple of "for-instances," however, are helpful: A

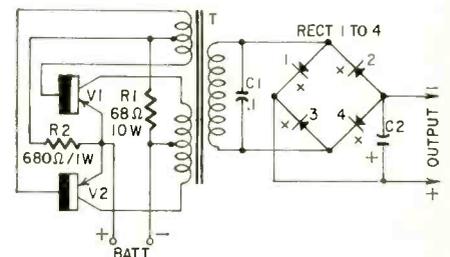


Fig. 4—Typical transistor power supply. The voltage and power rating of the supply will determine the ratings of the rectifiers and capacitors.

burned-out Stancor filament transformer is salvaged. A coil form is prepared to match its $\frac{3}{4}$ -square-inch core area and the test coils are wound as described. With a 6-volt supply, 1.5 amperes are required to pull the scope trace together (indicating core saturation). This is 45 ampere-turns. Two CBS 2N256 transistors on hand are rated at 2 amperes (approximately) collector current in switching service. Dividing 45 by 2 indicates that each half of the collector winding should consist of $22\frac{1}{2}$ turns. This winding will carry 2 amperes and the wire table suggests a size between Nos. 18 and 19. Either No. 18 or 20 will be satisfactory and the smaller size is used because the power supply won't be in steady use, current flows through each half of the winding alternately and a roll of No. 20 is on the shelf. The base-bias winding will have one-fifth the collector turns

and there's some No. 28 wire available for it. Figuring a secondary voltage of 150 open-circuit, we multiply 45 (the collector turns) by 150 and divide by 12 (twice the supply voltage). This rounds out to 560 turns. While No. 40 or smaller would be OK, this isn't a big winding so a convenient spool of No. 32 is used. The coil form is chucked in the lathe and "away we go."

Even though a much larger secondary wire size was used than needed, the cross-sectional area of this winding is comfortably smaller than the window. If we'd decided on a much higher secondary voltage (requiring many more turns), it would then have been important to use the smaller wire so the windings would fit the window area.

When completed and hooked up in the multivibrator circuit, the output is 150 volts, no load, just as figured. A 60-milliampere load is applied which pulls the output down to 100 volts. This is an output of 6 watts. The 6-volt input is supplying 1.7 amperes (or a bit less) or 10 watts. Thus the efficiency is 60%.


By reducing the size of R1 and 2, but still retaining their 10:1 ratio, the output can be raised to 10 watts or even more—still at 60% overall efficiency. With these transistors, however, the base current must not exceed 100 ma. Any adjustment of the resistors must keep base current within this value.

Next, a small audio output transformer with a core area of $\frac{1}{2}$ square inch from a junked ac-dc radio was rebuilt. It required only 20 ampere-turns to close the hysteresis loop. It was decided to lower the battery drain, so a center-tapped 50-turn collector winding was calculated to produce only 0.8-ampere collector current. This and the 10-turn bias winding were applied on top of the original transformer high-impedance winding. A test showed that it pulled just under 1 ampere, about as expected. The no-load output was 500 volts. It charged a 500- μ f photoflash capacitor to 450 volts in 25 seconds and would make a fine power supply for an electronic photoflash outfit. Incidentally, the laminations in some small audio transformers are placed all one direction. For power purposes these laminations, when reassembled, should be alternated.


In instances where it is possible to salvage and use the old transformer secondary or primary intact, most of the work is eliminated. The collector and base windings go on fast and easily, occupying far less space than the original primary.

These two examples show the flexibility possible with this design procedure.


Your power supply can be designed for your car radio, for mobile equipment or for an electronic photoflash. Just remember that the transistors are working hard in some of these applications. They give off quite a bit of heat and must be mounted on a metal surface to help dissipate this heat. Check their operating temperature, if it goes over 150°F you'd better arrange a larger heat sink, a cooler location or perhaps a small fan to cool them. END

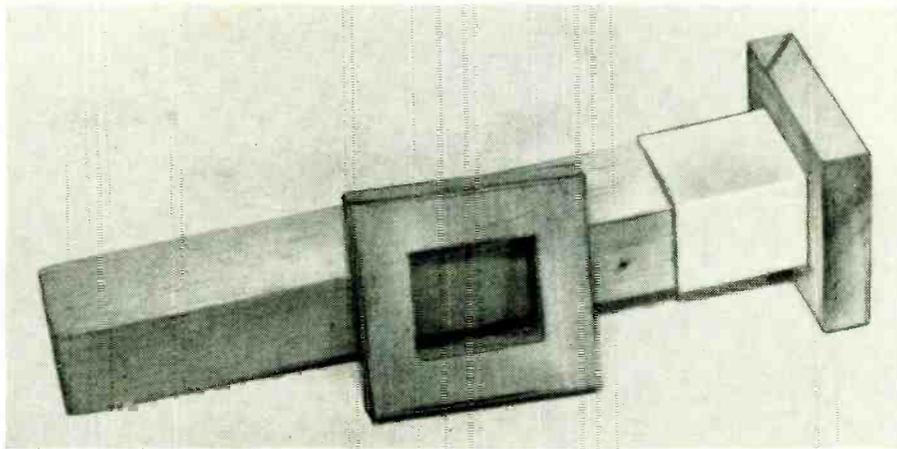

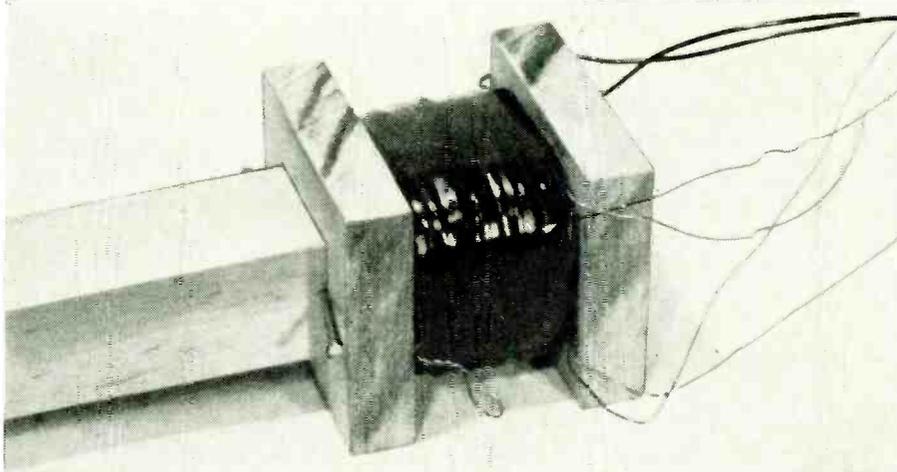
The winding form with cardboard collar mounted.



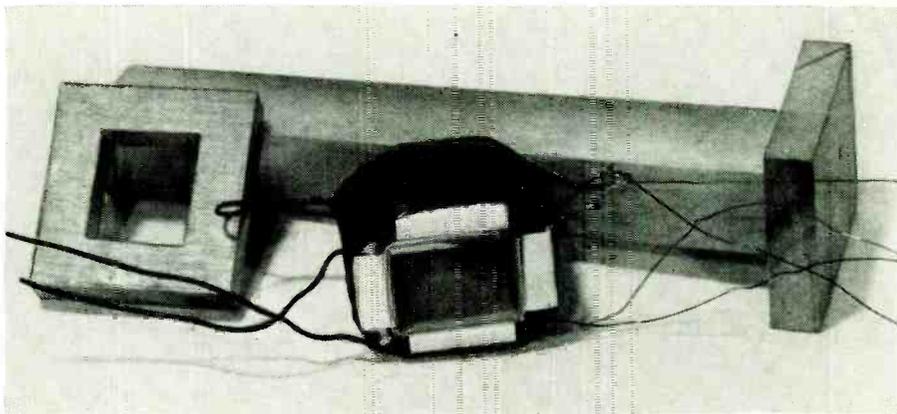Completed windings are covered with protective layer of tape.



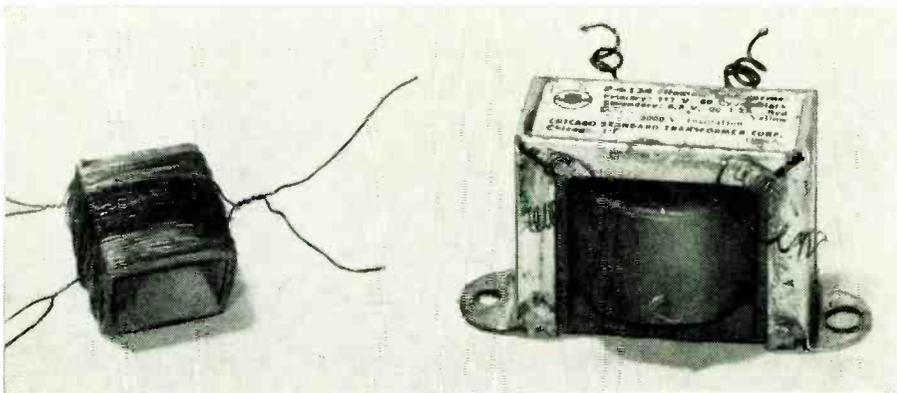Windings removed from form and ready for assembly.



A completed transformer and the test coils.

THE TUNNEL DIODE REALLY WORKS

These two practical circuits can be duplicated by the average experimenter

By I. QUEEN
EDITORIAL ASSOCIATE

THE tunnel diode is an amazing semiconductor. Articles on it and its applications have appeared in periodicals, but have often been too theoretical for readers who like to experiment. Exact voltage and component values are often missing, making it hard to duplicate the stated results. (The operating bias for a tunnel diode is generally very critical.)

The July issue of this magazine, page 26, carried an excellent discussion of basic principles of the diode. It showed that this device has a *negative* resistance sandwiched between regions of *positive* resistance. Fig. 1 shows a highly simplified form of the familiar tunnel diode curve. Current increases as voltage is increased up to about 0.1 volt, then *decreases* as voltage increases from 0.1 to a little less than 0.5 volt, when it again starts to rise with increasing voltage. Voltage and current values are typical for a 1N653 (Texas Instruments). Circuit theory indicates that such a device must be an excellent *oscillator* and *switch*. This article will give full details on a crystal oscillator for 27–30 mc and a switch that is triggered by light.

The oscillator

The negative resistance region means that the tunnel diode is a ready oscillator. As explained in the July issue, the load line must intersect the region of negative resistance (Fig. 2). This

load resistance is *smaller* than the negative resistance of the diode, specified as -40 ohms for a 1N653. E_i , the circuit voltage, is a small fraction of a volt.

No battery with such low voltage is generally available, so a divider is needed. Fig. 3 illustrates the crystal oscillator. Note the low value for R3 (which determines circuit resistance). Oscillations occur when the voltage across the diode is about 0.2. Start with a 100-ohm pot for R1. To set it, vary R1 (and R2 for fine adjustment) and listen for the signal on a nearby receiver tuned to the crystal frequency. Tune C2 for maximum output. For 27–30 mc, L is 16 turns of No. 18 wire, $\frac{1}{4}$ -inch diameter, close-wound.

You may also adjust this oscillator and observe circuit operation by measuring voltages. Start with maximum resistance at R1 and R2, then raise the voltage across the diode. (R2, the 20-ohm pot, is rather critical. Use 10 ohms for ease of control.) At about 0.17


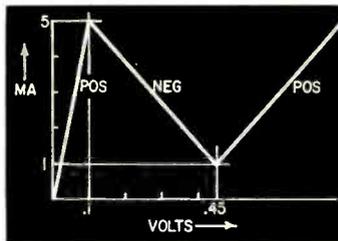


Fig. 1—Tunnel diode characteristic in an idealized—or cubist—form.

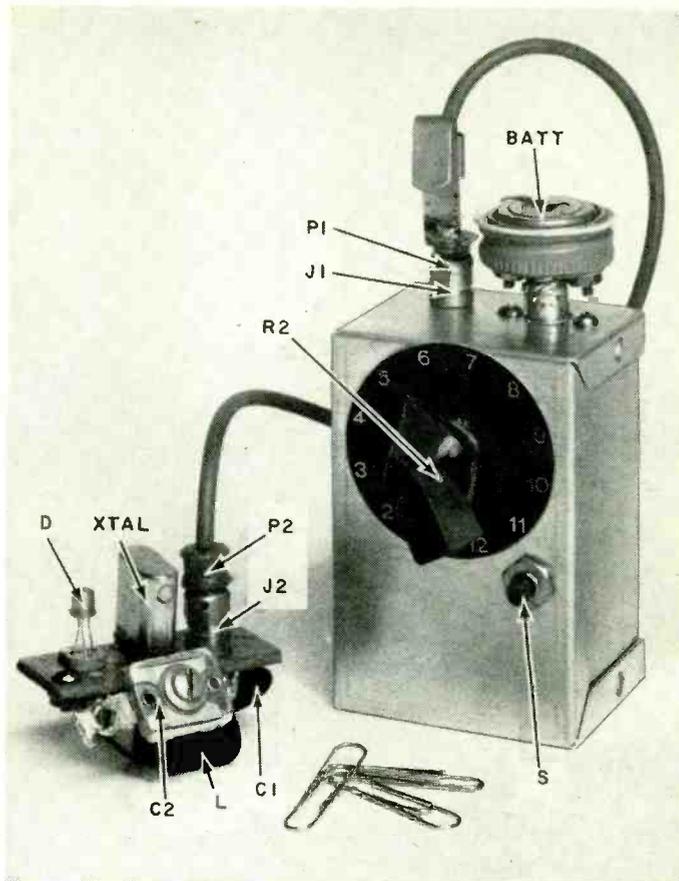

Simple tunnel-diode oscillator.

volt (as measured with a 20,000-ohms-per-volt meter) you will note a sudden jump (to about 0.2 volt) and oscillations will begin.

This circuit will work with any overtone crystal from 27 to 30 mc without retuning. This is hardly the upper frequency range of a tunnel diode. With smaller tanks you should have no trouble pushing the range higher. If you remove the crystal, the circuit will self-oscillate with a rough and unstable signal.

Once R1 has been determined for your particular diode and circuit, it may be replaced with a fixed resistor. A 47-ohm unit is just right for my oscillator.

For safety, limit diode current to a maximum of about 6 ma till you determine the current value for R1.

Construction is uncritical. In my unit, a battery and voltage-divider unit already on hand was used. That portion of the circuit could, of course, be mounted on the board with the other components.

Trigger switch

When the load line intersects the diode characteristic in three places (as load 1 does in Fig. 4) we have a switch. As an example, suppose the circuit voltage is E_i , about 1.2 volts. Load line 1 resistance is about 250 ohms. When the circuit is switched on, it stabilizes at point A.

Now if a weak positive pulse is applied to the diode, the operating point will rise over the peak. It will move along the downward slope quickly (due to negative resistance) and arrive at C. (Point B is an unstable position, and is of little importance in this explanation). All this takes place instantaneously. Thus even a very weak pulse will trigger the circuit from A to C. In a 1N653 these points correspond to about 5 and 2 ma, respectively. (This is terrific amplification, if you want to look at it that way.)

The triggering push may be an externally applied voltage or it may be just a reduction in circuit resistance. To show this, refer to Fig. 5. Starting with maximum R1, lower the resistance. At about 5 ma the meter will suddenly deflect *downward* to 2 ma, although we are *reducing* R1. The operating point

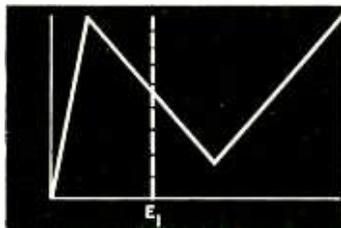


Fig. 2—Operating point for tunnel diode oscillator.

(Fig. 4) has moved up the curve till it reached the peak of the characteristic. At that instant (when it reaches the peak) it snaps to C. R2 (Fig. 5) is a limiting resistor.

Now increase R1. The slope of the load line becomes more horizontal until it coincides with load 2, at which instant the current will snap upward. For the 1N653 this occurs when the total series resistance is about 1,250 ohms. The current will snap from a low of 0.6 ma to 1.2 ma.

The circuit may be triggered by light falling on a photocell (Fig. 6). A low-resistance Hoffman S1-A solar cell is shown in series with the winding of a relay RY to be energized. Light falling on the solar cell increases the circuit voltage and triggers the circuit. The higher voltage corresponds to changing the load line from 2 to 3 (Fig. 4). When

- R1—47 ohms, see text
- R2—20 ohms, pot (see text)
- R3—10 ohms
- All resistors 1/2-watt 10%
- C1—.001, ceramic
- C2—25- μ f trimmer
- L—16 turns No. 18 enameled, 1/4-inch diameter, closewound
- XTAL—see text
- S—push-button, normally open
- D—tunnel diode, 1N653 or equivalent
- BATT—1.2-volt, nickel-cadmium rechargeable. (The one shown was mounted in a metal screw cap with a phono plug.)
- Miscellaneous hardware, jacks, boards or other housing as desired



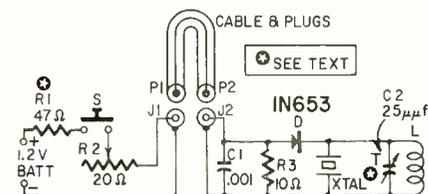



Fig. 3—The tunnel-diode oscillator on the right; power supply on the left.

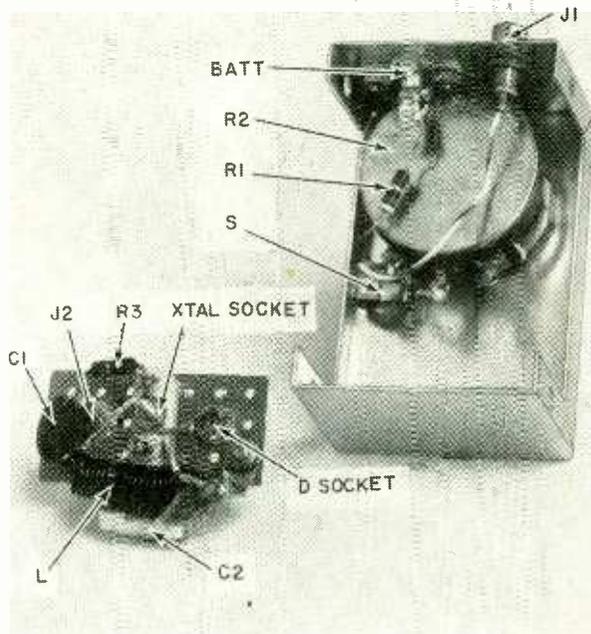

A look inside the oscillator.

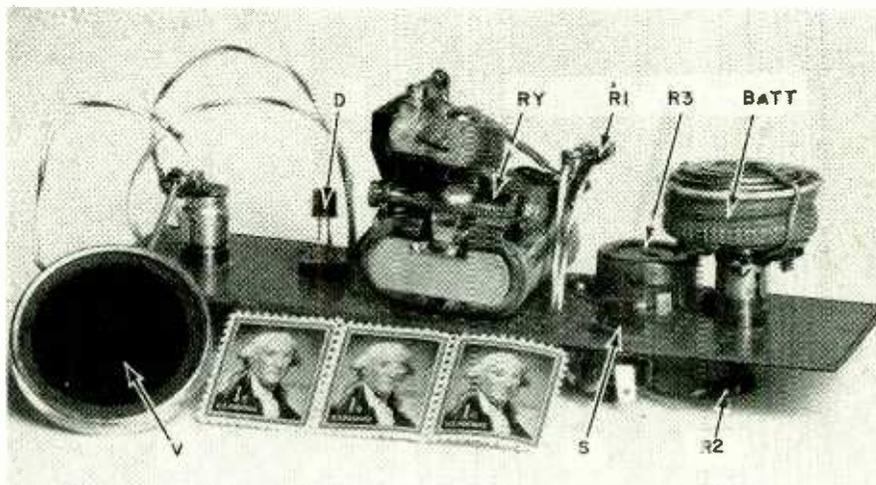

Switching circuit uses a tunnel diode.

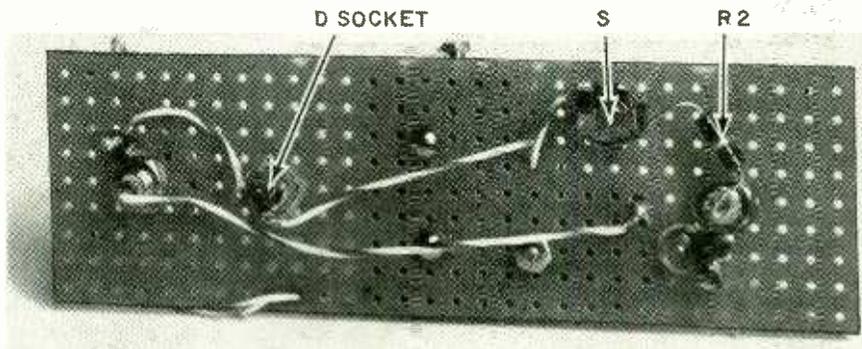

One resistor sits under the chassis of the switching circuit.

the new line touches the peak point on the characteristic, the circuit triggers and the relay drops out.

The photo shows an actual switching circuit based on the above experiment. The relay must have a low-resistance winding. Being unable to find a suitable unit, I modified a Sigma 5F-1000, which has two coils in series, for a total of 1,000 ohms. They are reconnected in parallel to cut resistance to 250 ohms. Observe polarity of windings. The yellow lead of each coil is soldered to the black of the other. A 470-ohm resistor is shunted across the windings. This lowers the resistance and the sen-

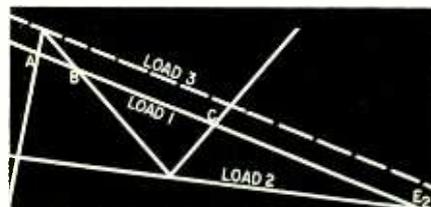


Fig. 4—How the tunnel-diode characteristic is used in switching.

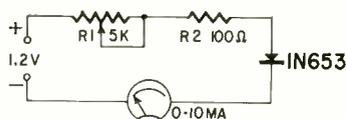


Fig. 5—Tunnel-diode switching circuit.

sitivity of the relay. Now the relay should be adjusted to pull in at 4.6 ma, release at 2.3 ma, approximately. Prime the circuit by pressing the RESET button, then lower R3 gradually until you are just below the trigger point. If triggering occurs, note the point and start over again, this time not advancing the control so far.

When properly set, the illumination from a 40-watt lamp at about 18 inches is sufficient to trigger the circuit and release the relay. Note that the solar

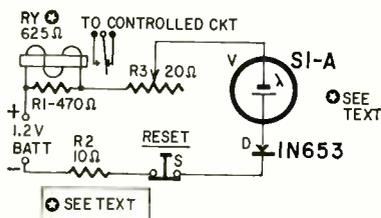


Fig. 6—Practical tunnel-diode switch.

- R1—470 ohms
- R2—10 ohms
- R3—20-ohm pot
- RY—Relay, Sigma 5F-1000, modified, see text
- S—push-button, normally closed
- D—tunnel diode, IN653 or equivalent
- V—photocell, Hoffman SI-A or equivalent
- Miscellaneous hardware, perforated board, jacks, etc., as desired

cell is in series *aiding* with the battery.

This circuit may be made so sensitive that it can be triggered by switching on or off a nearby soldering iron or other appliance. The magnetic field of the ac does it.

If you reverse the polarity of the solar cell, you can prime the circuit with illumination *on* the cell. Then you can trigger the circuit by interrupting the light falling on the cell, even for a brief instant.

END

TV Service CLINIC

conducted by

JACK DARR

CONVERGENCE has been made a great deal easier in the later-model color sets, for which we are duly grateful. RCA, for example, has mounted all the convergence controls on a separate board which can be set up on bolts above the back of the set so that it is accessible from the front.

Control circuitry in this department has changed too. RCA and others have adopted a very useful device, the "combination" control (Fig. 1). These are the ones marked R-G-1, R-G-2, etc. They work on both red and green at the edges of the screen, the most difficult place to get good convergences.

Some of these are inductance controls, some resistive pad types. They are found mainly in the horizontal dynamic-convergence circuits and their operation is exactly the same as the older types. The details vary from manufacturer to manufacturer, of course, so go by the detailed setup instructions furnished with each set.

Before we leave this circuit, there's one point I'd like to mention: watch that contrast! We recently installed a late-model set. The color was beautiful, no fringing or contamination, and we were very pleased. A few days later, the owner called, complaining about fringing, impurity and several other things including loss of focus. We rushed over to the house in time to catch a color program.

Sure enough, there were all the symptoms she had mentioned.

It was quite by accident that I happened to turn the contrast control. Immediately, the picture cleared up and all the objectionable symptoms dis-

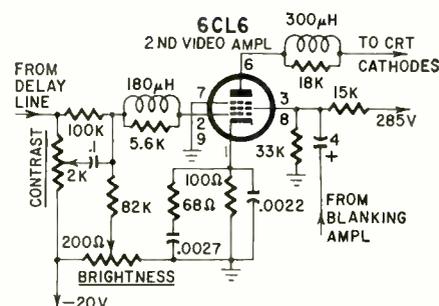


Fig. 2—Both the contrast and brightness controls are in the second video amplifier grid circuit.

appeared! The contrast control had been "opened wide." This gave us something of the same effect you'd get on a sensitive black-and-white set: smearing, loss of fine detail, excessive brightness, and, in this instance, slight misconvergence (probably due to a bit of blooming). In this particular set and in many others of the same vintage, I think you'll find that picture quality is best with the contrast control turned all the way down (counterclockwise).

While this may seem strange to those accustomed only to black-and-white circuitry, in the average color set it is quite normal. The controls labeled CONTRAST and BRIGHTNESS are found in quite a different place on color TV's. The contrast control on black-and-white receivers is usually located in the video amplifier cathode; in color sets it may be in any of several circuits. It is often located in or around the *grid* circuit of the second video amplifier (Fig. 2). However, in later chassis, you may find it back in the cathode (Fig. 3). Brightness controls are *not* found on the picture-tube grid or cathode, but in the


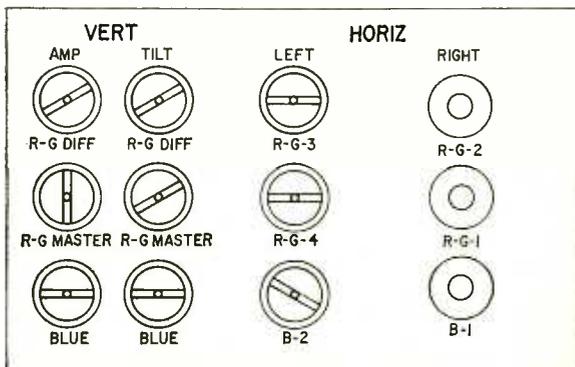
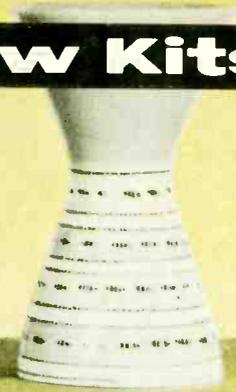


Fig. 1—Convergence board used by RCA in CTC10 sets. It is similar to the board in the August, 1960, issue, page 83.

HEATHKIT

Presents 18 New Kits for

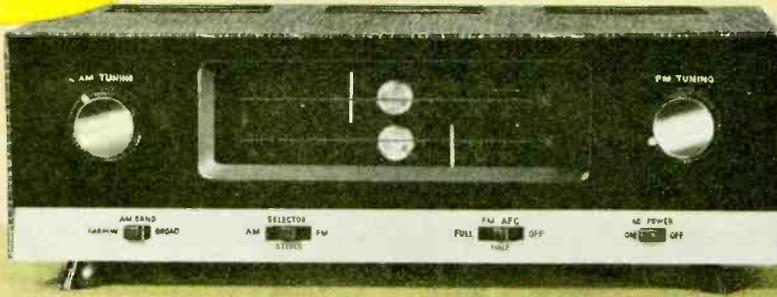

GO STEREO IN STYLE . . . WITH HEATHKIT® QUALITY AND ECONOMY!

ECONOMY STEREO AM/FM TUNER KIT (AJ-10)

Full fidelity AM and FM reception, plus up-to-the-minute design features are yours at minimum cost with this new Heathkit stereo tuner. Features include: 2.5 uv. sensitivity for 20 db of quieting; individual flywheel tuning; separate magic-eye tuning indicators for AM and FM; AM bandwidth switch; 3-position (off-half-full) automatic frequency control (AFC); FM multiplex adapter output; built-in FM rod antenna; terminals for external AM and FM antennas; "AM," "STEREO" and "FM" function selector switch. 14 lbs.

\$59⁹⁵
AJ-10
\$6.00 dn., \$6.00 mo.

HI-FI RATED 25/25 WATT STEREO AMPLIFIER KIT (AA-50)

In one handsome package, you get both stereo power and control, with a host of deluxe features. Hi-fi rated at 25 watts per stereo channel (50 watts monophonic), this new Heathkit design includes channel separation control . . . new mixed center speaker output . . . stereo reverse and balance controls . . . separate tone controls for each channel with ganged volume controls . . . five switch-selected inputs for each channel (stereo "mag. phono," tape head, three hi-level). Extra input for mono "mag. phono." Special outputs for tape recording. 30 lbs.

\$79⁹⁵
AA-50
\$8.00 dn., \$8.00 mo.

YOUR "BEST BUY" IS HEATHKIT® HI-FI!


FREE CATALOG

Send for your copy today! . . . describes over 150 Heathkit hi-fi, ham radio, test, marine and general products.



STEREO/MONO RECORD PLAYER KIT

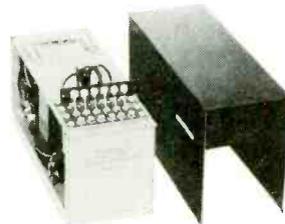Four speeds (16, 33 1/3, 45 and 78 RPM); Sonotone 8TA4-SD ceramic stereo cartridge. 10 lbs.
AD-10 **\$33.95**



MIXED LOWS STEREO CROSSOVER KIT

Delivers stereo bass frequencies to single woofer; highs to individual wing speakers. 10 lbs.
AN-10 **\$19.95**




TRANSISTOR PORTABLE KIT

Tremendous value: 6-transistor circuits. Fun to build!
XR-2P (plastic)
6 lbs. **\$29.95**

Just 10% DOWN ON ORDERS OF \$55 OR MORE!

Your Summertime Enjoyment

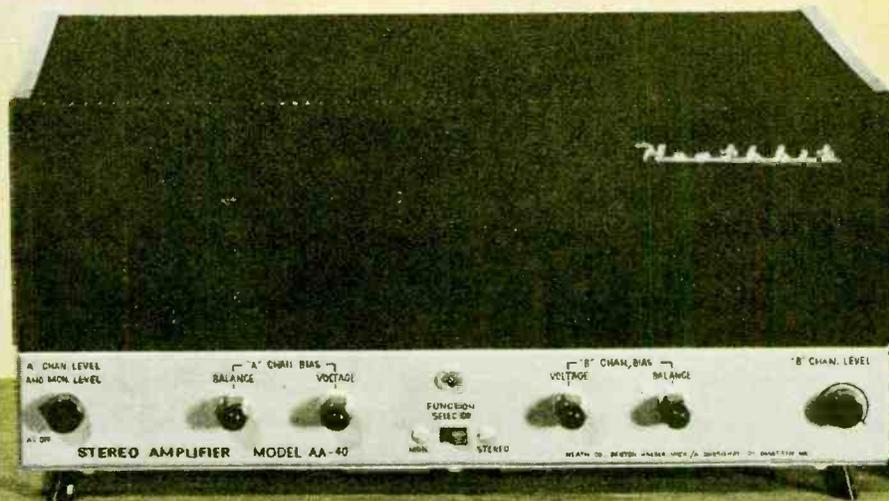

HEATHKIT® . . . FOR FLEXIBILITY and COMPATIBILITY!

ECONOMY STEREO PREAMPLIFIER KIT (AA-20)

A low-cost, versatile stereo preamplifier control center. Four inputs each channel accept magnetic cartridge; crystal or ceramic cartridge; and tuner, tape, TV, etc. Six position function switch gives flexible stereo or monophonic use. Features cathode follower outputs plus hi-level outputs for tape recorder drive, calibrated Baxandall-type tone controls for each channel, clutch-type volume controls, filament balance controls, and accessory AC sockets. Self-powered. Styled in black and gold. Shpg. wt. 8 lbs.

\$34⁹⁵

AA-20

PROFESSIONAL RATED

35/35 WATT BASIC AMPLIFIER KIT (AA-40)

Doubles as a superb dual 35 watt stereo amplifier or a full-fledged 70 watt monophonic amplifier. Features: mixed-channel center speaker output; individual level controls; "Stereo-Mono" switch (ties both amplifiers to one level control for monophonic use); dual outputs for 4, 8, 16 and 32 ohm speakers. Paralleling outputs for 70 watt monophonic use matches 2, 4, 8 and 16 ohm speakers. 41 lbs.

\$79⁹⁵

AA-40

\$8.00 dn., \$8.00 mo.

Now . . . a complete Mobile PA Sound System in easy-to-build, HEATHKIT® form!


MOBILE PA SOUND SYSTEM

Perfect for political campaigns, advertising, sporting events. The powerful amplifier operates from any 12 v. car battery. Features an all-transistor circuit; inputs for microphone and music source. Two channel mixing circuit "fades" auxiliary input when used with microphone supplied . . . lets you override music with voice without changing control settings. Outputs for 8 and 16 ohm speakers. Mounts easily under auto dash. Mobile PA Amplifier Kit (AA-80). 7 lbs. . . . **\$39.95**

COMMERCIAL SOUND SYSTEM (CSS-1): consists of AA-80 Amplifier; microphone; plywood car-top carrier; one 16 ohm, 15 watt outdoor speaker. 24 lbs. . . . **\$84.95**

COMMERCIAL SOUND SYSTEM (CSS-2): same as above except with 2 speakers. 30 lbs. . . . **\$99.95**

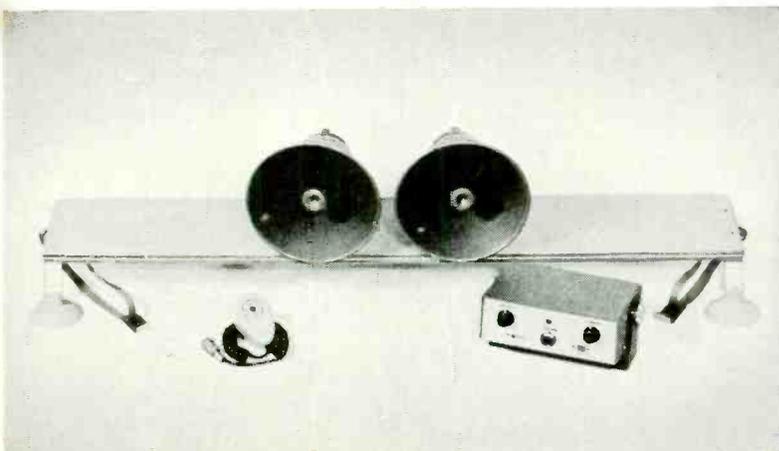EXTRA HORN SPEAKERS (401-38): As described above. 6 lbs. . . . **\$19.95**



SAVE 50% . . . ON THE WORLD'S BEST QUALITY KITS!



First... With The Finest

a subsidiary of
DAYSTROM, INCORPORATED



Buy The Best in Quality At Half the Cost With Heath

**CITIZENS BAND TRANSCEIVER KIT
(GW-10 Series)**

Superb 2-way Citizens Band communication! Superheterodyne receiver may be switched to crystal control or continuous tuning. Featured are an automatic "series gate" noise limiter, to minimize ignition interference, etc.; and adjustable squelch control to silence receiver during "standby." Press-to-talk microphone features a coil-cord connection to the transceiver. Transmitter is crystal controlled on any one of 23 assigned channel frequencies chosen. Order model GW-10A for 117 v. AC operation, and GW-10D for 6 or 12 v. DC operation; both have self-contained power supply. 11 lbs.

GW-10A (117 v. AC) or **GW-10D** (6 or 12 v. DC) **\$62⁹⁵** ea.
\$6.30 dn., \$6.00 mo.



**TRANSISTOR DEPTH
SOUNDER KIT**

Shows depth, type of bottom and submerged objects from 0-100 feet. Powered by 6 flashlight cells. 10 lbs.

DS-1 **\$69.95** (\$7 dn., \$7 mo.)



**6 & 10 METER HAM
TRANSCEIVER KITS**

Combined crystal controlled transmitters and variable tuned receivers. Operate fixed or mobile. 10 lbs.

HW-19 (10 meters) **\$39.95** ea.
HW-29 (6 meters) (less XTAL)




EDUCATIONAL KIT

First of a series... designed to teach, as you build, the basic "yardsticks" of electronics. Consists of kit and text-workbook. Finished volt-ohm-milliammeter has many uses. 4 lbs. **EK-1** **\$19.95**

**3-BAND "MARINER" TRANSISTOR
DIRECTION FINDER KIT (DF-3)**

Priced far below pre-assembled units of comparable quality, the DF-3 includes such important features as: 9-transistor circuit; 6 flashlight battery power supply; pre-assembled, pre-aligned tuning section; new modern styling; rugged aluminum splash-proof cabinet. Covers broadcast band, beacon and aeronautical band, and marine-telephone band. Special "sense" antenna eliminates "double null" effect common in many direction finders. Circuit has high gain IF amplifier and audio output amplifier delivering up to 380 mw of audio power to the large 4" x 6" weatherproof speaker. 13 lbs.

\$99⁹⁵
DF-3
\$10.00 dn., \$9.00 mo.

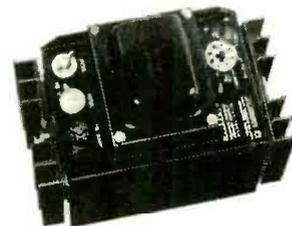

**TRANSISTOR MOBILE
POWER SUPPLY**

All-transistor! Provides plate, screen and bias voltages for mobile amateur equipment. 120 watts IC.A.S. 10 lbs.

HP-10 **\$44.95**

TIME PAYMENTS!

Use Heath's convenient time payment plan... only 10% down on orders of \$55 or more.

in Easy-to-Build Electronic Kits



MUTUAL CONDUCTANCE TUBE TESTER KIT (TT-1)

An impressive list of electronic and mechanical features make this tube tester one of the finest values in the electronics industry. Tests Gm (amplifiers) from 0 to 24,000 micromhos, Emission, Leakage, Grid Current ($\frac{1}{4}$ microampere sensitivity), Voltage Regulators (built-in variable DC power supply), Low Power Thyatron and Eye tubes. Features 300, 450 and 600 ma constant current heater supplies, Life Test, Hybrid Tube test, built-in switch-operated calibration circuit. Large, easy-to-meter. Constant tension, free rolling illuminated chart. Kit includes 7 wiring harnesses. Assembly skill of technician or higher recommended; assembly time, 40 hours average. Black leatherette case with white trim, nylon feet, removable top. A specialized tool of unusual value that will pay for itself many times over! 27 lbs.

TT-1

\$134⁹⁵

(\$13.50 dn., \$12.00 mo.)



WORLD-WIDE, ALL BAND RADIO RECEPTION

- Ceramic IF "Transfilters"
- Five Bands
- Flashlight battery power


10 TRANSISTOR "MOHICAN" GENERAL COVERAGE RECEIVER KIT

First kit of its kind uses ceramic IF "Transfilters." Covers 550 to 30 mc on 5 bands, with 5 separately calibrated bands to cover amateur frequencies (including 11 meter citizens band). Powered by 8 flashlight batteries. Built-in 54" whip antenna, tuning meter, headphone jack. (less batteries) (20 lbs.) **\$109⁹⁵**

GC-1 \$11.00 dn., \$10.00 mo.

send today for Your FREE HEATHKIT® CATALOG

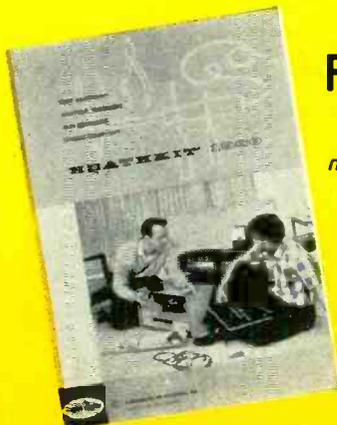Over 150 items of hi-fi, marine, amateur, test and general equipment are illustrated and described in the complete Heathkit catalog.



HEATH COMPANY, Benton Harbor 20, Michigan

Please send the following HEATHKITS:

ITEM	MODEL NO.	PRICE

Ship via () Parcel Post () Express () COD () Best Way

() SEND MY FREE COPY OF YOUR COMPLETE CATALOG

Name _____

Address _____

City _____ Zone _____ State _____

Dealer and export prices slightly higher.

B

(Continued from page 61)

Now Completely SELF-CONTAINED

For Testing & Rejuvenating
BLACK AND WHITE and COLOR including 110° TUBES

NEW CRT 440






TESTS AND REJUVENATES

all black & white and color picture tubes at correct filament voltage from 1 to 12 V.

TESTS AND REJUVENATES

110° tubes with 2.34, 2.68, 6.3 and 8.4 volt filaments.

TESTS AND REJUVENATES

color picture tubes. Checks each color gun separately same as black & white tubes.

*Used by Thousands of Professional Servicemen
MAKES NEW PICTURE TUBE SALES EASIER*

Gives you more value than ever—all-in-one. Quickly checks and corrects most TV picture tube troubles in a few minutes right in the home without removing tube from set. Gives new useful life to weak or inoperative tubes. Checks leakage. Restores emission and brightness. Repairs inter-element shorts and open circuits. Life test checks gas content and predicts remaining useful life of picture tube. Completely self-contained in leatherette-covered carrying case. Net, \$74⁹⁵

ACCESSORIES for USE ONLY with FORMER B&K Models 400 and 350 CRT



Model C40 Adapter. For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates TV color picture tubes and 6.3 volt 110° picture tubes. Net, \$9.95

Model CR48 Adapter. For use only with all previous B&K Model 400 and 350 CRT's. Tests and rejuvenates 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. Net, \$4.95



See your B&K Distributor
or Send now for Bulletin AP15-E



B & K MANUFACTURING CO.
1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

work properly (Fig. 5). At this point, the horizontal oscillator should be able to float a picture across the screen, if all of the parts are good! If the oscillator will not work now, you have a defective part. A leaky capacitor or an off-value resistor will throw the time constant of the circuit far out of the correct range.

After getting the oscillator circuit to the point where it will work without the ringing coil, remove the shunt and replace the original plate resistor. Don't move the horizontal hold control. Turn the slug on the ringing coil until the picture locks in (perhaps not entirely steady, but much better than without it). (Remember, the sync input is still grounded.) Now remove the short from the grid. If the picture immediately goes far out of sync, there is trouble in the phase comparator.

Sound troubles

In a Philco E2006-11 portable TV the sound will not come on when the picture does. About 5 minutes later it comes in, or both show up at the same time, then the audio gradually dies away, to come back with a "pop" in about 5 minutes. After it's warmed up, nothing short of hitting it with a sledge hammer will make it cut out. Of course, out of the cabinet, it works beautifully.
—C. S., Wilmington, Calif.

I hate to say this, but it looks as if you have a good case of printed-circuit trouble! It seems to be thermal in nature, from the description: the "loose wire" that is causing the trouble seems to be closing tightly once the set has heated up sufficiently.

There is one fairly good remedy for this. Using a medium to small iron, resolder all of the joints associated with the sound circuit, including the printed-circuit board!

If this drastic step fails, then replace the discriminator transformer. This trouble could also be caused by a defective base assembly, if one of the tiny built-in capacitors should be intermittent.


As you say, this set is used on ship-board quite a lot, you might check the 4.5-mc trap in the video output circuit. Salt-air corrosion could have caused one of the fine wires on this coil to be weakened. The same thing could account for the trouble in the discriminator transformer. After the trouble is located, spray the whole section with a good grade of acrylic plastic coating to prevent future corrosion.

Boost high voltage

Can the high voltage in a Transvision A41 be increased by using a 6CD6 instead of a 6BG6 in a flyback circuit that has a Merit HV-10 transformer and matching yoke? I would like to obtain about 1-kv increase.—H. H. G., Lansdowne, Pa.

There is more than one way to approach this problem. I would suggest checking the 6BG6's screen voltage. If it is less than 350 volts, the screen resistor can be reduced in value to

* RECORDING TAPE

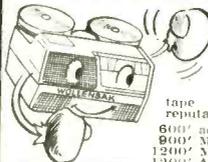

*Oxide guaranteed not to rub off or squeak — or money back. Compare ours with other "Bargain" tape. You'll find it's more than just "price" when you deal with us. We are original pioneers in the tape recorder business and our reputation means everything to us.

600' Acetate (plastic), 5"	.75
900' MYLAR (Polyester), 5"	.95
1200' MYLAR, 1/2 mil, 5" reel	1.28
1200' Acetate (plastic), 7"	1.29
1200' MYLAR, 1 1/2 mil (strong)	1.95
1800' Acetate (plastic), 7"	1.79
1800' MYLAR 1 mil thick, 7"	2.29
2400' MYLAR, untensitized, 7"	2.69
2400' MYLAR, tensitized, 7"	3.49

2400' MYLAR, tensitized. 7" 3.49
Studios. Large Users Even Lower

NORELCO SPEAKERS

Famous 9710M (twin-con 8" speaker, original list \$9.95, usual NET \$8.97. NOW, while they last 1/2 off net — 11.98 plus postage. (discontinued model). Frequency 40-20,000 cy. Other SENSATIONAL Speaker reductions on a first come, first served basis. SEND FOR SPEAKER SPECIFICATION SHEET.



COMMISIONED ELECTRONICS CO.
1776 Columbia Road Washington, D. C.

WHAT ARTICLES

would you like to see published in

Radio-Electronics ?

Maybe you're the man to write them.

Ask for an author's guide.

Radio-Electronics
154 West 14th St., New York 11. N. Y.

obtain additional high voltage. Do not operate the screen over 350 volts, however, as tube life could be impaired. A high-voltage doubler will give a big stepup, which can in turn be reduced to desired value by using a suitable series resistance in the high-voltage lead. A 6CD6 output tube does give an advantage over a 6BG6. This requires circuit rewiring. In any case of raising the high voltage, the flyback transformer can become a limiting factor. If you are unable to scan the picture tube fully when the high voltage is increased, a larger flyback is required.

Agc-width coil

I have lost a lot of sleep over this one. In a Stromberg-Carlson TC-19, the width coil, (which also supplies the agc keying pulse) was defective. All the replacement coils I can find have proved ineffective. The pulse at the keyer tube plate is correct in polarity, but I can't get the agc line to go more than 2 volts negative. An external bias of 6 volts restores the set to normal operation. I haven't been able to obtain an exact duplicate replacement part for this anywhere. Can you help me out?—B. C., New York.

The coil you refer to is *not* the width coil with an agc winding, but a special transformer which supplies only the keying pulse for the agc tube. The width control is in another circuit.

This is a very special transformer; so special, in fact, that I have been unable to find it listed (as an exact replacement, that is) in any of the multitude of catalogues I have. However, I have located a coil which, I think, will do the job.

The original coil (T in Fig. 6) has an 0.2-ohm primary resistance and a

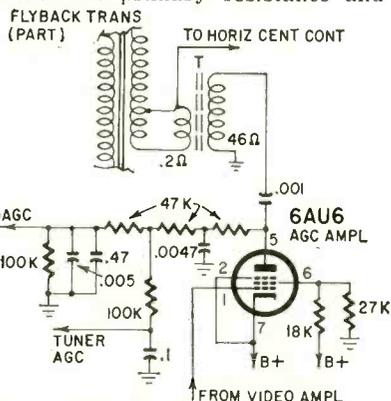


Fig. 6—Transformer T supplies high pulse voltage to agc amplifier's plate.

46-ohm secondary resistance. This would give it a tremendous stepup ratio.

Triad lists a coil which should do the trick: it is their WLC-29, with a primary inductance variable from 0.1 to 0.9 millihenry, and secondary from 4 to 28 millihenries. Because it has an adjustable core, you should be able to match the flyback tapping with the primary and get enough voltage out of the secondary to give you the correct pulse amplitude on your keyer tube.

As a precaution, you might check the signal level applied to the grid. Ordinarily this runs around 60 to 70 volts peak to peak. **END**

NOW TEST ALL TUBES

with Models 500, 550, or 650 DYNA-QUIK
SIMPLY BY ADDING THIS
NEW MODEL 610 TEST PANEL



TESTS OLD AND NEW TUBE TYPES
Measures Genuine Dynamic Mutual Conductance


Also Tests Thyratrons, Voltage Regulators,
Auto Radio Hybrid Tubes, Battery Radio Tubes,
European Hi-Fi Tubes, and most Industrial Types

Merely by adding the new "610" to your Dyna-Quik, you have all the advantages of fast, multiple-socket testing, *plus freedom from obsolescence*. Makes your B&K Model 500, 550, or 650 Tube Tester *more useful and more valuable than ever!* Enables you to test all present plus future TV, radio and other tube types for all shorts—gives highly sensitive grid emission and gas test—checks for leakage and life—*with laboratory accuracy*.

Speeds complete tube test, sells more tubes on-the-spot, saves call-backs, insures your professional reputation, and brings more servicing profit. *It pays to invest in B&K professional equipment.*

Model 610 Test Panel comes completely wired, ready to install and connect. **Net, \$4995**

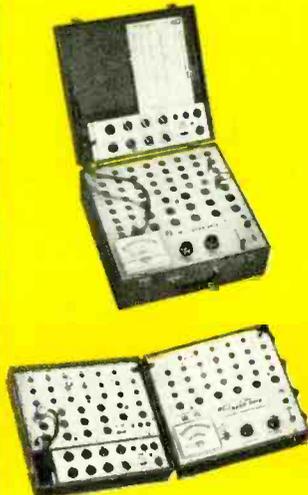Issues of helpful new tube information 4 times a year available on subscription



Photos above show how easily the new Model 610 Test Panel fits into the B&K Models 550 and 650 Dyna-Quik Tube Testers.

See Your B&K Distributor
or write for Bulletin AP16-E

B & K MANUFACTURING CO.

1801 W. BELLE PLAINE AVE • CHICAGO 13, ILL.
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.
Export: Empire Exporters, 277 Broadway, New York 7, U.S.A.

TAPE RECORDERS

**HI-FI COMPONENTS
SLEEP LEARN KITS**

MERITAPE
Low cost, high quality recording tape, in boxes or cans.

**UNUSUAL VALUES
FREE 1961 CATALOG**

DRESSNER, 69-02RE 174 St., Flushing 65, N.Y.

LOOK
no further . . . if you're searching for hi-fi savings. Write us your requirements now.


Key Electronics Company
120-A Liberty St., N.Y. 6, N.Y.
Cloveverdale 8-4288

ENGINEERING DEGREE IN SCIENCE 27 or 36 MOS. MATH



Accelerated year-round program prepares for early employment in fields of Science and Engineering. Regular 4-year program for B.S. Degree completed in 36 months, special engineering degree program in 27. Classes start quarterly—January, March, June, September. Quality education. Graduates employed from coast to coast. Government approved for veteran training. Students from 50 states, 40 countries. 20 buildings; dorms, gym. Campus. Save time and money. Earn board while studying. Write for catalog and complete information.
17100 E. Washington Boulevard, Fort Wayne 2, Indiana

INDIANA TECHNICAL COLLEGE

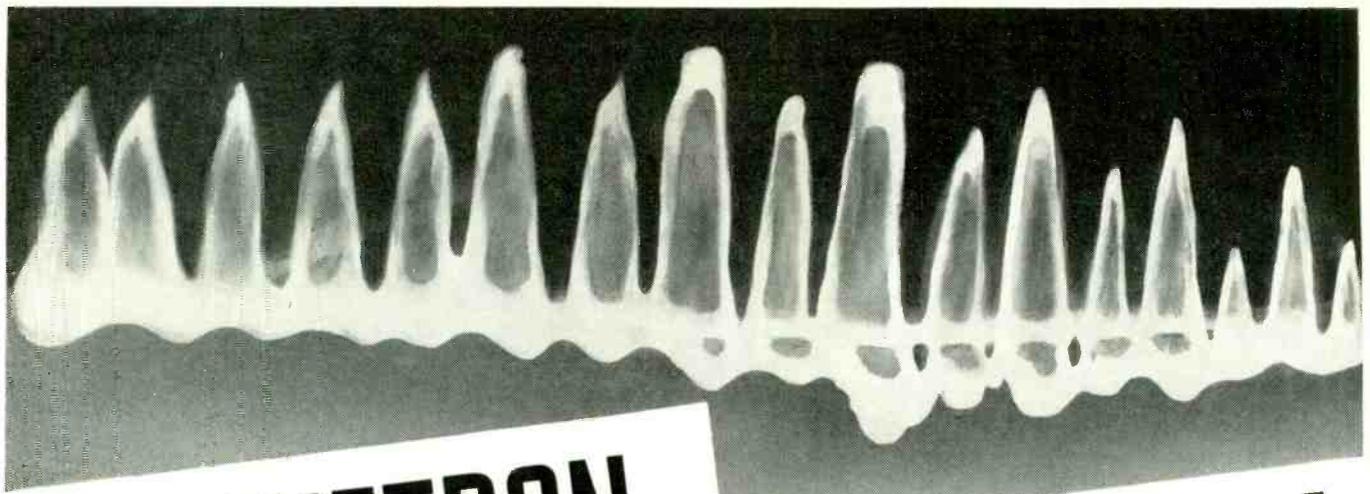

MAGNETRON industrial power generator

Able to supply great power for short periods at ultra-high frequencies, the magnetron's chief non-radar application at present is in cooking foods

By TOM JASKI

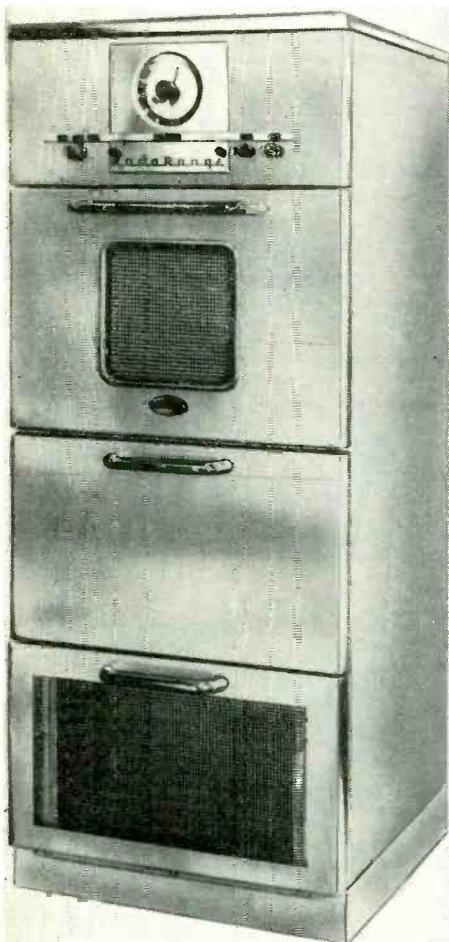


Fig. 1—The Raytheon Radarange, used in restaurants to cook food speedily.

YOU may not know it, but you have probably eaten food cooked by radio waves so thoroughly and rapidly that you couldn't tell it had been hard frozen *minutes* before. Modern electronic ranges can cook steaks in less than half a minute or turn out a piping hot frankfurter in seconds. The modern electronic way gives the restaurant diner foods that have been freshly cooked rather than wilted all day on a steam table, and it especially does away with hours of defrosting. One of the electronic marvels that can do this is the Raytheon Radarange, shown in Fig. 1.

Radio-frequency heating has been used in industry for many jobs during the past 30 years, but electronic cooking has not been around that long, and few are familiar with the equipment. While most industrial heating takes place at 13.8 mc, cooking ranges operate in the microwave regions. The frequency band of 2,400–2,500 mc has been assigned to industrial heating services by the FCC.

Heart of the Radarange and similar electronic cookstoves is the magnetron, powerful microwave generator, more familiar in radar installations. The magnetron in the range (Fig. 2) is mounted above the dish, and sprays high-energy radio waves with hundreds of watts of power directly at the food cooking it from the *inside out*.

The magnetron is a simple-looking tube, but the theory of its operation is

rather complex. It can be understood if some very simple principles of electron motion are kept in mind. For example, an electron can be deflected in its flight by a magnetic field. Of course you know this, for the electron beam which lights the screen in your TV picture tube is deflected magnetically. Fig. 3 shows how an electron is deflected, a little by a weak magnetic field, and a great deal by a strong one. The amount of deflection depends, of course, on how long we leave the electron in the magnetic field and on how much momentum it has—in other words, how fast the electron moves. Since an electron always moves from a negative to a positively charged body (one with a shortage of electrons), the amount of positive charge (the potential) determines the speed of the electron, and thus the amount of deflection in a given magnetic field. To make the electron path curve more, we can either strengthen the magnetic field, slow down the electron, or do both at the same time!

Simple magnetron theory

An electron moving within a cylindrical anode with a cathode at the center and a magnetic field along its axis (Fig. 4) can be made to take different paths to the anode after leaving the cathode. The shape of the path depends on the strength of the magnetic field and the voltage on the anode. It

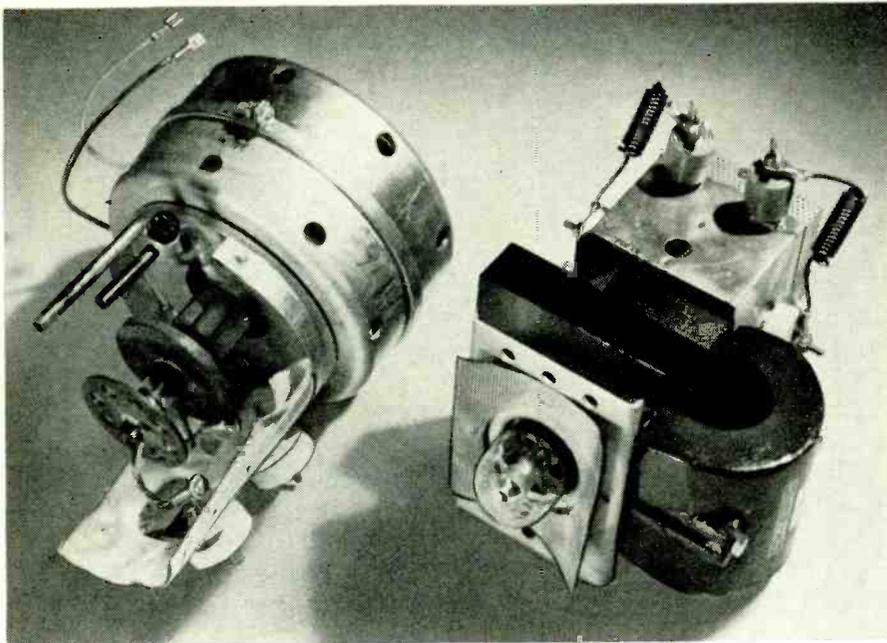


Fig. 2—Typical magnetrons. Left, a liquid cooled unit; right, air cooled type.

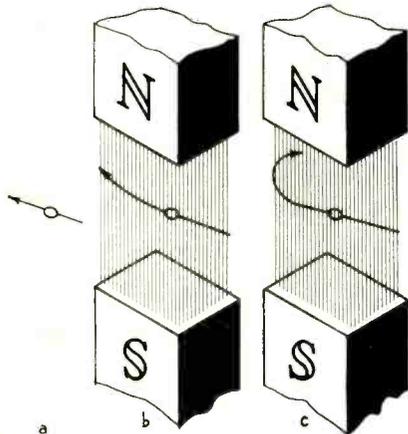


Fig. 3—How a magnetic field deflects electrons: a—no field, electron goes straight; b—weak field, path curves; c—strong field, path curves strongly.

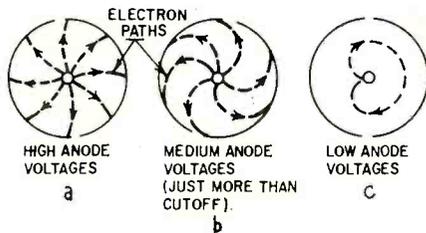


Fig. 4—How electron path varies in constant magnetic field: a—high anode voltage; b—medium voltage, just above cutoff; c—low voltage, cutoff condition.

will be almost straight if the field is weak and the potential high, curve more if the magnetic field becomes stronger or the potential lower, and so on, until we reach what is known as the "cutoff" condition, where a lot of electrons that leave the cathode will never get to the anode. Now cutoff is not an absolute condition, and a few electrons will travel to the anodes anyway, but very few. The great majority will travel around the cathode for a time in what we can call a rotating electron "cloud."

We will need this rotating cloud later in our explanation, so keep it firmly in mind.

We can operate a magnetron in two ways. One is called *negative resistance* and the other *transist time* or *dynatron* operation. We will discuss the former first, although few magnetrons operate that way now. But understanding it is fundamental.

Fig. 5 shows a split-anode magnetron, with an external resonant circuit and the supplies needed. If the tube is not oscillating, we have here the situation which has been redrawn in Fig. 6-a, where the anodes have the same voltage. The magnetic field is perpendicular to the paper, with the North pole above and the South pole below the paper. If, in such a tube, we could measure the potential (voltage) between plate and cathode, we would find that there is a gradual decrease of potential as we approach the cathode. If we jot down the location of our measurements and the potential measured and then connect points with the same potential, we find that the "equipotential lines" as they are called form neat circles (Fig. 6-a). The number in each circle represents the potential at that "layer" of the cylinder.

If we send an electron from the cathode in Fig. 6-a and we have a fairly strong magnetic field, the path of the electron will be as shown. This is the cutoff condition. As the electron travels, it crosses regions of higher potential and is attracted to plate A. But before it can gain enough momentum to get to the plate, the magnetic field curves the electron away from plate A. It then crosses weaker field regions progressively, and the magnetic field keeps the path nearly circular.

But now let us see what happens if we reduce the voltage on one anode and increase it on the other. Now the equipotential lines no longer are nice circles but are badly distorted as shown

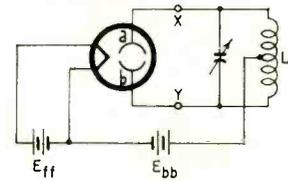


Fig. 5—Split-anode magnetron. Drawing is symbolic—filament is actually centered in the cylinder formed by the two anodes, and resonant circuit is composed of distributed instead of lumped elements.

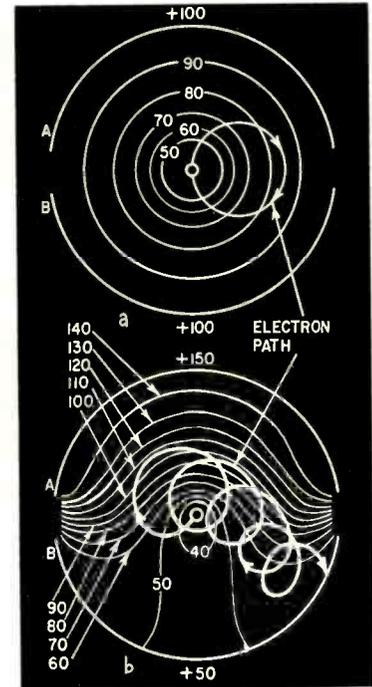


Fig. 6-a—Path of electron in cutoff condition, both anodes at same voltage; b—path with lower voltage on one anode. Lines show points of equal voltage.

in Fig. 6-b. What does this mean to the electron setting out from the cathode? As the electron starts out, it will meet conditions approximately like those in Fig. 6-a. But the change in potential region is much faster, and the electron gains somewhat more momentum from the field, but not enough to travel to plate A. Now it will curve back in a larger sweep, missing the cathode. And as it curves around the cathode, it will again pick up momentum in the rapidly differing field conditions encountered, and take another turn around. And again and again the field conditions the electron meets will cause it to take another turn (under the influence of the magnetic field) to travel the spiral path shown. Finally, after this long travel, the electron has lost a lot of its kinetic energy and is attracted to the nearest anode, which now is plate B. We have then the curious phenomenon that most of the electrons travel to anode B, the one with the *lower* voltage. Lowering the voltage on this plate has increased the current to it,



FREE!

Olson Radio Catalogs FOR ONE YEAR

- ★ 8 Different Issues
- ★ All Bargain Packed



FREE One Year Subscription to OLSON RADIO'S Fantastic Bargain Packed Catalog—Unheard of LOW, LOW WHOLESALE PRICES on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and other Bargains.

Another OLSON Bargain!

CEILING SPEAKER

★ Mounts Flush Without Cutting Hole



NEW!

No. S-394
3 for
\$15.00

\$5.49

Mounts on wall or ceiling. Perfect for built-in systems, built-in Hi-Fi systems, and adding extensions to your present system. For the Hi-Fi music enthusiasts who enjoy their music in the air. Specially designed to handle up to 15 watts. Response, 60 to 13,000 CPS. Voice coil 8 ohms. Overall depth is only 3". 6" speaker factory mounted. Finished in dull gold to blend with any surroundings.

MAIL COUPON TODAY

Fill in coupon below for your FREE one year subscription to Olson's Bargain Packed Catalog. To order Ceiling Speaker, simply check quantity desired and send remittance along with coupon. (Include enough for postage or parcel post shipment. Send \$2.00 deposit for C. O. D. orders.)

- FREE Olson Catalogs for One Year
- 1-S-394 Ceiling Speaker.....\$5.49
- 3-S-394 Ceiling Speakers.....\$15.00

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

OLSON RADIO CORPORATION

712 S. Forge St., Akron 8, Ohio

and we have a clearly negative resistance characteristic.

How do we use this to oscillate? Well, look again at Fig. 5. If we already had a voltage across the resonant circuit, this would provide the plates with the difference in voltage we show in Fig. 6, wouldn't it? Suppose now that we start the tube by warming the filament and then suddenly turn on the plate power. Nothing is symmetrical and so, in the first instant, one of the plates will get a little more current than the other. This will lower the voltage on this plate a little (through the coil impedance) and thus it will first attract more electrons, and we're off. The capacitor will charge until the voltages are even. Then the voltages through the inductance-stored energy will reverse, beginning to raise the voltage on the other plate, as in any other resonant circuit, and the tube is oscillating.

Of course at this high frequency (in the microwaves), the resonant circuit will probably not be the coil and capacitor we show but instead a resonant

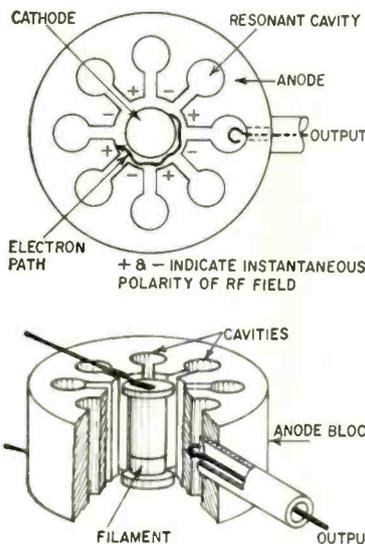


Fig. 7—Two views of multicavity magnetron, the type commonly used in industry.

cavity, with distributed capacitances and inductances instead of lumped ones.

This, basically, is negative-resistance operation of a magnetron, specifically the split-anode magnetron. Notice that essentially the magnetron was in the cutoff condition before it started to oscillate, but that the distortion introduced by the voltages on the plates did something to the field so that the electrons started flowing anyway and to the plate with the lower voltage.

Dynatron operation

Now remember the rotating cloud of electrons we could create in the magnetron in the cutoff condition. Assume we have created such a cloud. We will presently look at one of the electrons in it, but first let us look at an anode in which we have built cavities of the proper size for the microwave frequency at which we wish the magnetron to operate. Such a magnetron with cavities is shown in Fig. 7. (This is

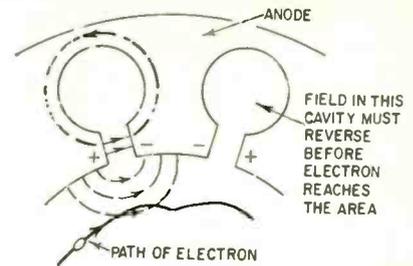


Fig. 8—Electron expends energy as it moves toward a negative point, absorbs energy when drawn toward a positive one.

appropriately called a *multicavity magnetron*.) Notice that we have a coupling loop in one cavity to take the energy out. Now look at Fig. 8, where we have stretched out two cavities of the anode in an enlarged view to help us explain the action.

When we have a cavity excited in some way by radio-frequency energy, we can have a difference of potential at the two walls of the cavity. This is indicated as "+" and "-" in Fig. 8. The arrows show (by convention) the direction in which an electron would be slowed down. Thus, an electron approaching the heel of the arrow is being decelerated, and an electron approaching the point of an arrow is being accelerated.

In Fig. 8 we have also drawn one of the electrons in the whirling cloud we spoke of before. This electron approaches the heel of an arrow—in other words enters a retarding field as it approaches the "-" segments, and loses some of its kinetic energy. This energy is imparted to the field in the cavity. How? Consider it in the following way: If the electron enters the field between the "+" and the "-", it will repel one electron charge from the field toward the "cathode" ("-") of that cavity. That charge will flow around the outside of the cavity to the "+" , as indicated by the dashed lines. When the electron is past, the charge will flow back and re-establish the equilibrium in the field. The traveling electron loses kinetic energy and is then deflected from the cavity entrance by the magnetic field (which is here again perpendicular to the paper), and we show the path curved that way. The charges flowing back and forth on the inner surface of the cavity constitute an oscillatory current.

But the electron travels on past the next cavity. If we make sure now that the electron will also find a retarding field there, the action will be repeated as at the first cavity, and the electron will lose some kinetic energy again. Eventually, after passing a number of cavities, it will lose enough energy to be attracted to one of the anode segments between the cavities, because, you may remember, a stationary positive voltage is still applied to the entire anode.

This is the mechanism by which we obtain energy from the electron cloud in the dynatron operation of the magnetron. It is, as you can see, very similar to the method used in traveling-

wave tubes (see RADIO-ELECTRONICS, December, 1959).

Between cavities, the electron obtains some energy from the positive voltage on the anode. If we now arrange our anodes and cavities and our electron speed so that the electron passes each cavity at the time when there is a retarding field, the electron will deliver energy to each cavity in turn. Since the cavities are adjacent, the field in these cavities will be 180° (half a cycle) out of phase. (The anode of one cannot be the cathode of the next one!) The time the electron must spend between cavities is exactly a half-cycle of the radio frequency. The path of such an electron is also indicated in Fig. 7. We have here, as in the traveling-wave tube, taken advantage of the transit time of the electron, which is the reason we also call this the *transit-time* method of operation.

Of course we must again get the thing started. But this is very easy, for once we get the cloud of electrons rotating by adjusting the plate voltage on the multi-cavity anode and the magnetic field (which most often is steady, supplied by a strong permanent magnet), the electrons passing the cavities will start to excite them and build up the rf field on them, which we had shown in Fig. 8 with the "+" and "-". These symbols of course indicate a momentary condition. We cannot keep the electron whirling around indefinitely; it would then begin to take up more energy than it would deliver. There is some optimum value for each type of magnetron.

Several other matters enter into magnetron operation. For example, there is the matter of *strapping*. The tendency of the cavities to get out of phase (because the electron which is losing energy might start to slow down) must be prevented. This we do by connecting each alternate anode segment with a heavy copper strap. This tends to equalize any voltage differences (rf, that is) on the anode segments, and the cavities are thus kept in phase. Obviously we must have an even number of cavities.

The magnetron can be made to deliver enormous power for very short periods of time. Even then the maggie must be cooled. As you saw in Fig. 2, air or liquid cooling can be used. But even so, the "duty cycle" of the magnetron (the portion of each second during which it is putting out power) must be short for maximum efficiency of radiated power without burning up the tube. So we *pulse* the magnetron—supply plate power to it 120 times per second in the Radarange. Fig. 9 shows the complete circuit of one of these ranges.

Most of the diagram is devoted to safety and control devices. T1 is the filament transformer and cathode connection. We bring this cathode to a high negative voltage 120 times per second (so that we can keep the plate nearest

* For safety, in case an interlock should fail or food particles reach the plate, shorting it to ground.

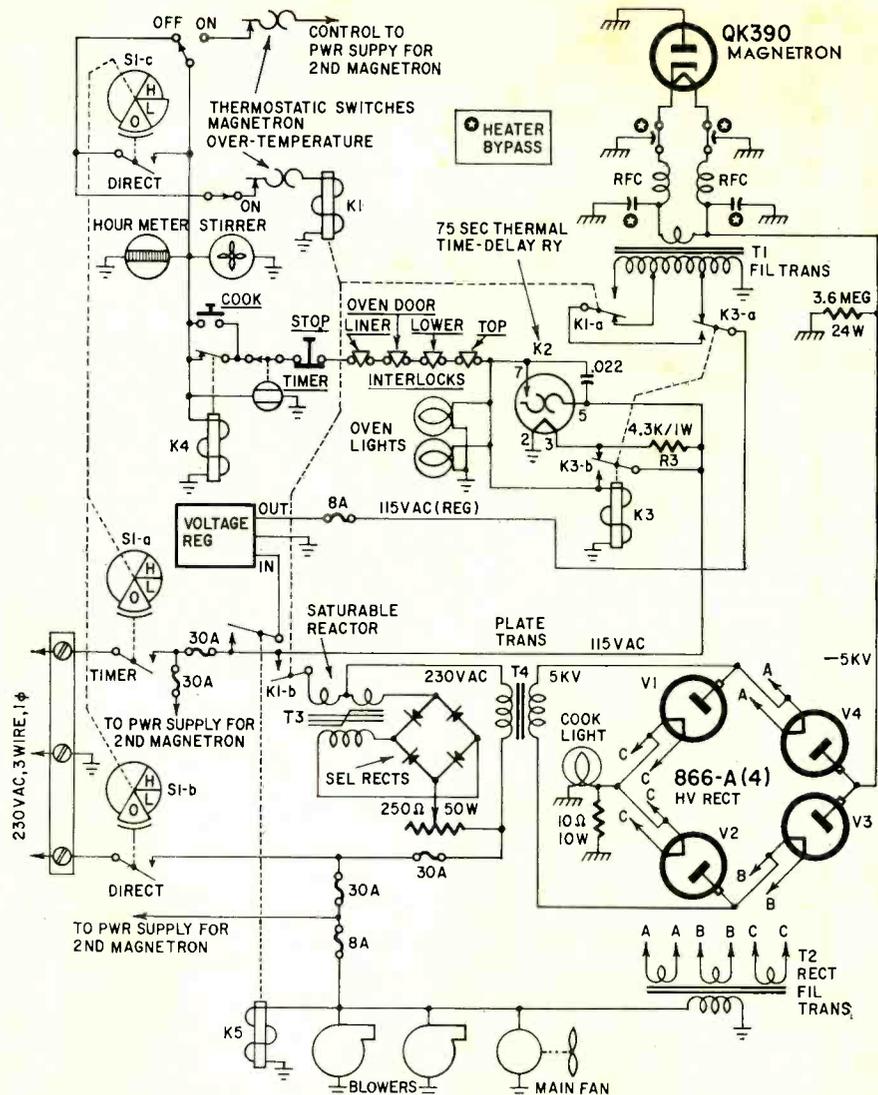


Fig. 9—Circuit of Raytheon Radarange. Not shown are a second magnetron and power supply, for full and half heat.

to the food grounded)*. This voltage is supplied by rectifiers V1, 2, 3, 4. These form an *unfiltered* full-wave bridge supply, providing the 120 pulses per second. The primary voltage of power transformer T4 is carefully regulated by magnetic amplifier T3. As you now know, the magnetron is very sensitive to voltage fluctuation.

Each Radarange contains two magnetrons. With switch S1 the operator can select OFF, LOW (one magnetron on) and HI (both on). He can preset the cooking time on the timer. Relays K2 and K3 provide a time delay, preventing the application of high voltage to the magnetrons until the filaments are warmed up. In the standby condition, when only the filaments are warm, they receive a *higher* voltage than when the plate power is on. As you will remember, some of the electrons return to the cathode, and these have additional heating effect.

To prevent the cathode from overheating, we must *reduce* the filament supply while the power is on. Relay K3 inserts R3 in series with the heater to apply a lower voltage to the thermal contacts of time-delay relay K2 after that relay has provided the necessary

time delay. However enough current passes to keep K2 energized. At this point contacts K3-a of relay K3 switch the 115-volt line to a higher tap on T1 to reduce the voltage applied to the magnetron filament to 9. This voltage is again reduced by K1 when that relay is energized by the cook button, and when it applies plate power to the magnetron.

The Radarange is the restaurant version. Industrial units are similar but some of them much larger. The 2,400–2,500-mc range of frequency is used because it is one of the most efficient *available* frequency bands for heating of foods. Actually 1,800 mc (10 cm) would be more efficient, but that frequency is occupied by other services.


This is the one industrial application of magnetrons, a microwave oscillator quite familiar from radar and other microwave applications. But you can be sure more and more of them will be used in industry as time goes by, particularly in the food industry, where they have the tremendous advantage that they can cook a large amount of food not only in a very short time, but also without discoloring it or changing its flavor. END

SENCORE *Most Popular Time Savers for Servicemen, Technicians, Engineers, Maintenance Men, Hobbyists!*



"MIGHTY MITE" TUBE CHECKER

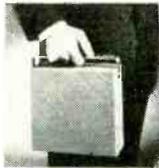Smaller than a portable typewriter . . . yet will outperform testers costing hundreds of dollars.



\$5950

A new dynamic approach to tube testing. Check over 1,300 tubes for cathode emission, grid emission, leakage, shorts and gas. A "mite" to carry but a whale of a performer that outperforms testers costing much more. New unique "stethoscope" approach tests for grid emission and leakage as high as 100 megohms yet checks cathode current at operating levels. Special short test checks for shorts between all elements. The Mighty Mite will test every radio and TV tube that you encounter (over 1,300!) plus picture tubes. Set up controls as easy as "ABC" from easy to follow tube chart. New features: • Meter glows in dark for easy reading behind TV set. • Stainless steel mirror in cover for TV adjustments. • Rugged, all steel carrying case and easy grip handle. • Smallest complete tester made. Measures only 9" x 8" x 2½" and weighs just seven pounds.

It's a real money-maker

LC3 LEAKAGE CHECKER

Provides grid emission and leakage checks with the same sensitivity as the famous Mighty Mite but checks critical tubes only; 172 types

\$2895



Ask any serviceman who owns one . . . or try one for just one day of servicing. You'll see for yourself how much time the LC3 can save you. Checks for leakage between all elements, whether caused by gas, grid emission or foreign particles. Also checks leakage on all capacitors with voltage applied — including electrolytics. Provides instant filament checks in "Fil-Check" position—no need for a second filament checker. One spare pre-heating socket and new roll chart prevent obsolescence. New charts provided free. For 110-120 volts, 60 cycle AC.

SENCORE SS105 SWEEP CIRCUIT TROUBLE SHOOTER

The Missing Link in TV Service . . .

IT'S A . . . UNIVERSAL HORIZONTAL OSCILLATOR. For direct substitution. No wires to disconnect in most cases. Traces trouble right down to the defective component. Variable output from 0-200 volts, peak-to-peak. Oscillator will sync to TV sync signal giving check on sync circuits.

HORIZONTAL OUTPUT CATHODE CURRENT CHECKER. A proven method that quickly checks the condition of the horizontal output tube and associated components. Adaptor socket prevents breaking wires. Easily replaceable Roll Chart gives all necessary pin, current and voltage data. New Roll Charts are Free.

UNIVERSAL DEFLECTION YOKE. A new, simple way to determine yoke failure accurately—without removing yoke from picture tube. Merely disconnect one yoke lead and substitute. If high voltage (also bright vertical line) is restored, TV yoke is defective.

DYNAMIC FLYBACK TRANSFORMER CHECKER. Merely flip switch to "Flyback Check" and meter will indicate condition of flyback transformer, in degrees of horizontal deflection. Extremely sensitive and accurate: even shows up one shorted turn on flyback.

VOLTMETER. For testing bootstrap, screen and other voltages. Direct-reading voltmeter, 0-1000 volts.



\$4295



HORIZ. OSC.	VERT. OSC.
HORIZ. O.P. STAGE	VERT. O.P. STAGE
HORIZ. FLYBACK XFORMER	VERT. O.P. XFORMER
HORIZ. DEFLEC. YOKE	VERT. DEFLEC. YOKE

UNIVERSAL VERTICAL OSCILLATOR. Checks oscillator, output transformer and yoke. Merely touch lead to component and check picture on screen. **SS105 is completely self-contained, nothing else is needed.** *New, improved Circuit.*

FC4 FILAMENT CHECKER

The ideal tool for servicing series string filaments.

\$275



Purposely works off your cheater cord to give you a positive check on line voltage. Prevents checking all tubes to find that your trouble was no line voltage. Only checker that checks all tubes automatically and has no batteries to replace. Cost half that of battery operated testers. Patented.

FC4 with test leads for checking continuity or AC or DC Voltage . . . **\$295**

VB2 "VIBRA-DAPTOR"

Checks 3 and 4 prong Vibrators Faster and Easier . . .

Plugs into any tube checker; ideal for use with LC3 or the Mighty Mite. To check 6v. vibrators, set for 6AX4 or 6SN7; for 12 v. vibrators, set for 12AX4 or 12SN7. Two No. 51 lamps indicate whether vibrator needs replacing. Instructions on front panel. Steel case.



\$275

"FUSE-SAFE" CIRCUIT TESTER FS3

Instantly tells you whether or not it is safe to replace fuse resistors, fuses, or circuit breakers. Separate red and green scale for each commercially available fuse resistor used in radio and TV. Eliminates guesswork, wasted time. Also handy for wattage checks up to 1100 watts at 115v.

\$895



Time Savers for America's ALL PARTS



Radio, TV and Electronic Minit-Men MADE IN AMERICA

See your Parts Distributor Now or Mail Coupon on Opposite Page

SENCORE


You can own all these popular Time Savers for less than some Mutual Conductance Tube Testers!



For TRANSISTOR RADIO SERVICING

Everything you need for less than \$50.00

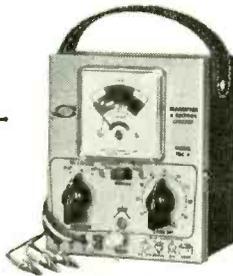
SENCORE TRC4 TRANSISTOR-RECTIFIER CHECKER



\$1995

Checks Transistors, Diodes, Rectifiers . . .
A transistor tester that is used by over 50,000 servicemen, engineers and experimenters from Coast to Coast. Recommended by TV and Radio manufacturers; used by such leading companies as Sears Roebuck, Bell Telephone and Commonwealth Edison. Tests indicate that the TRC4 will outperform testers costing many times more. The TRC4 tests all transistors for gain, leakage, and open or shorts. Simple to operate without set-up chart for service work and with set-up chart for more accurate checks. With batteries.

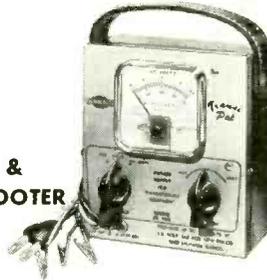SENCORE PS103 BATTERY ELIMINATOR & TROUBLE SHOOTER



\$1995

Replaces Batteries During Repair . . .
Replaces batteries during repair time of transistor radios and helps trouble shoot, too. For transistor radio servicing, experimenting and to charge nickel cadmium batteries. Dial output voltage from 0 to 24 volts DC and read on meter. Low ripple insures no hum or feedback problem. Meter reads from 0 to 100 MA. Shorted stage will cause current to read high as indicated on PF schematics; open stage will cause current to read low. To align transistor radio, tune in station signal and adjust IF slugs for maximum current. The PS103 is the only supply that will operate radios with tapped battery supplies; such as Philco, Sylvania, Motorola, etc.

SENCORE HG104



HARMONIC GENERATOR

\$995

Finds Defective Stage in a Minute . . .
Believe it or not. Just touch the output leads of the HG104 to inputs and outputs of transistors and a clear 1000 cycle note from speakers will tell you whether or not the stage is defective. Here is an unexcelled time saver, not a "pencil" gimmick. It actually works every time from speaker to antenna. Two leads and calibrated output (not found on pencils) are a must for speaker connection, grounding to prevent RF spray and front end checks. Also saves time when servicing HiFi, TV and radios. With life-time batteries.

Get all 3 **COMPLETE TRANSISTOR RADIO SERVICE LAB**
All 3 Time Savers shown above in handsome display carton carrying case


MODEL TL107 \$4985



For SUBSTITUTION SERVICING

Goodbye to messy parts . . . the mess of soldering and unsoldering in testing.


SENCORE H36 "HANDY 36"

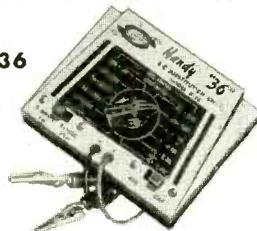

\$1275

Substitute for Capacitors, Resistors . . .
Provides the 36 most often needed resistors and capacitors for experimenting, substituting or testing. Eliminates searching for replacement components, unnecessary soldering and unsoldering and the mess it creates. Says goodbye to crumpled parts. Flick of a switch instantly selects any of: 24 Resistors from 10 ohms to 5.6 meg-ohms, 10 Capacitors from 100 mfd to .5 mfd, 2 Electrolytics, 10 mfd and 40 mfd at 450 Volts. All components are standard American brand.

SENCORE ES102 ELECTRO-SUB

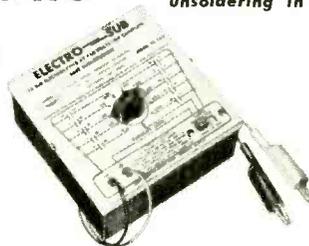

\$1595

Substitute for Electrolytic Capacitors . . .
Complete, safe substitution . . . from the smallest electrolytics used in transistor radios to the largest used in costly Hi-Fi amplifiers. Contains 10 electrolytics from 4 to 350 mfd. Select correct value with the flick of a switch. Features automatic discharge, surge protector circuit. Prevents accidental "healing" of capacitor being bridged. Completely safe—no arc or spark when connecting or disconnecting. Usable from 2 to 450 volts, DC.

SENCORE RS106 RECTIFIER TROUBLE-SHOOTER



\$1275

Locate faulty Rectifiers, Diodes . . .
This unique substitution unit simplifies trouble shooting rectifiers and diodes, gives you a positive check every time. Substitute for suspected rectifier or diode, watch picture or listen to sound and you'll know in seconds whether or not the rectifier or diode should be replaced. No guess work, soldering mess or time lost. The RS106 costs less than having loose rectifiers and diodes in the shop for testing and is worth many times more. A must for servicing voltage doubler circuits. Protected by a 1/2 amp. Slow Blow Fuse.

All 3 Time Savers shown above in handsome display carton carrying case **MODEL SL108 \$4145**

See your Distributor . . . if he cannot help you, Pat will . . .

SENCORE BE3 "ALIGN-O-PAK"

Eliminates messy batteries in TV service work. Handy for alignment, AGC troubleshooting or checking gated sync circuits. Dial the voltage you need, 0-18 volts, positive or negative. Completely isolated DC supply, less than 0.1% ripple. Covers all voltages recommended by TV set manufacturers and in Photo Fact schematics. For 110-120V, 60 cycle AC.



\$785



SENCORE, ADDISON 3, ILLINOIS

Dear Pat: Will you please . . .

Send me _____ Time Savers
(Model Numbers)

PAT RUDE, Customer Service Check or M.O. enclosed (PP Prepaid.) Send C.O.D.

Distributor's Name (if any) _____

Your Name _____

Street _____


City _____ Zone _____ State _____

ALL UNITS FULLY GUARANTEED OR MONEY BACK WITHIN 10 DAYS


TRANSISTOR

FIELD-STRENGTH METER for the CITIZENS BAND

- R1—pot, 500,000 ohms, screwdriver adjust
 R2—100,000 ohms
 R3, 6—pot, 5,000 ohms, linear
 R4—1,000 ohms
 R5—100 ohms
 All resistors 1/2 watt 10%, unless noted
 C1—10 μ f, ceramic, NPO (Centralab TCZ-10 or equivalent)
 C2—50 μ f, 6 volts, electrolytic
 C3—.005 μ f, ceramic
 BATT—3 volts (2 penlight cells in series)
 D—1N34-A
 J1—coaxial connector (to match antenna)
 J2—closed circuit phone jack
 M—0.500 μ A
 S—spsst toggle
 T—antenna transformer: secondary, 12 turns No. 28 enameled wire; primary, 3 turns plastic-covered hookup wire: both wound on CTC coil form PL55B
 V1—2N229
 V2—CK722
 Battery holder
 Flea clips
 Base-loaded whip antenna for 27-mc band
 Miscellaneous hardware

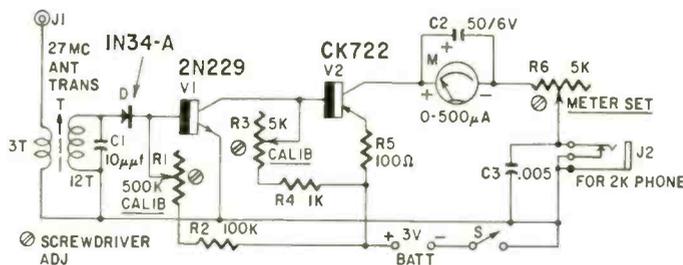

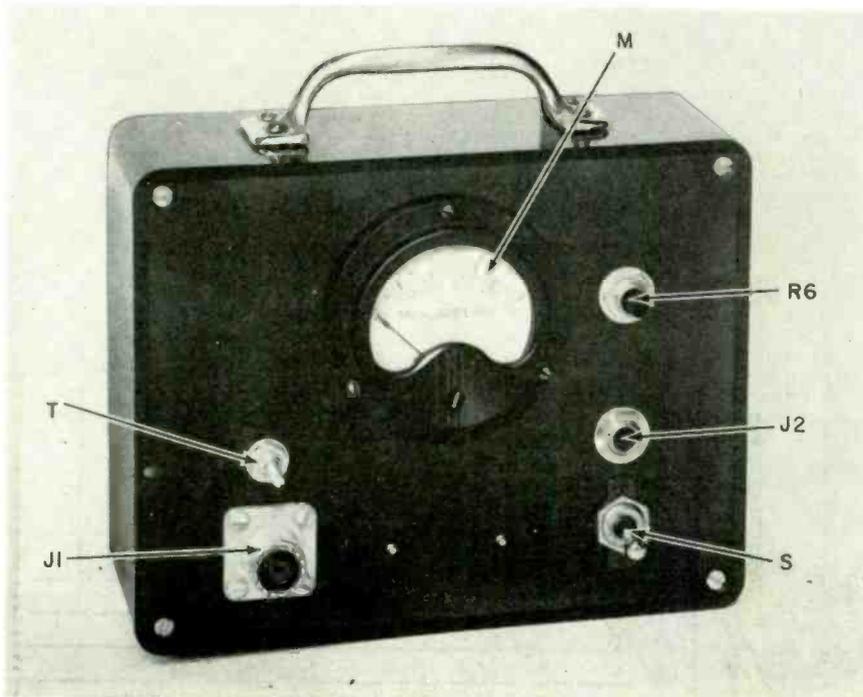Circuit of the two-transistor field-strength meter.




A bakelite case houses the unit.

By LYMAN E. GREENLEE

MEASURING the field strength of a transmitter's radiated signal is an excellent way to evaluate the efficiency of any antenna or transmitter. The best way to do this is with a field-strength meter. Most Citizens-band transmitters are limited to 5 watts input. Therefore, they require the maximum antenna efficiency to make full use of the available power. The latest FCC rulings permit the operator to adjust the antenna tuning on Citizens-band transceivers. The only adjustments not allowed are those affecting the transmitted frequency, which must be held to within a tolerance of .005%. But without accurate equipment for measuring field strength, it is not easy to tell whether antenna or transmitter adjustments are for better or worse.

This direct-coupled two-transistor field-strength meter is simple and requires few parts (see schematic). A 27-mc base-loaded whip antenna feeds through a coaxial connector to antenna transformer T. A 10- μ f fixed capacitor (C1) and the slug in the coil form allow tuning over all 23 Citizens-band channels. The diode detector feeds V1's base. This n-p-n transistor is direct-coupled to V2, a p-n-p unit. The meter is any 0-500- μ A unit and is bypassed by C2 to avoid sudden pointer swings on signal peaks. A pair of 2,000-ohm headphones can be plugged into the phone jack to monitor speech from the transmitter. This is a very convenient way to check speech quality. Power is furnished by two penlight cells.

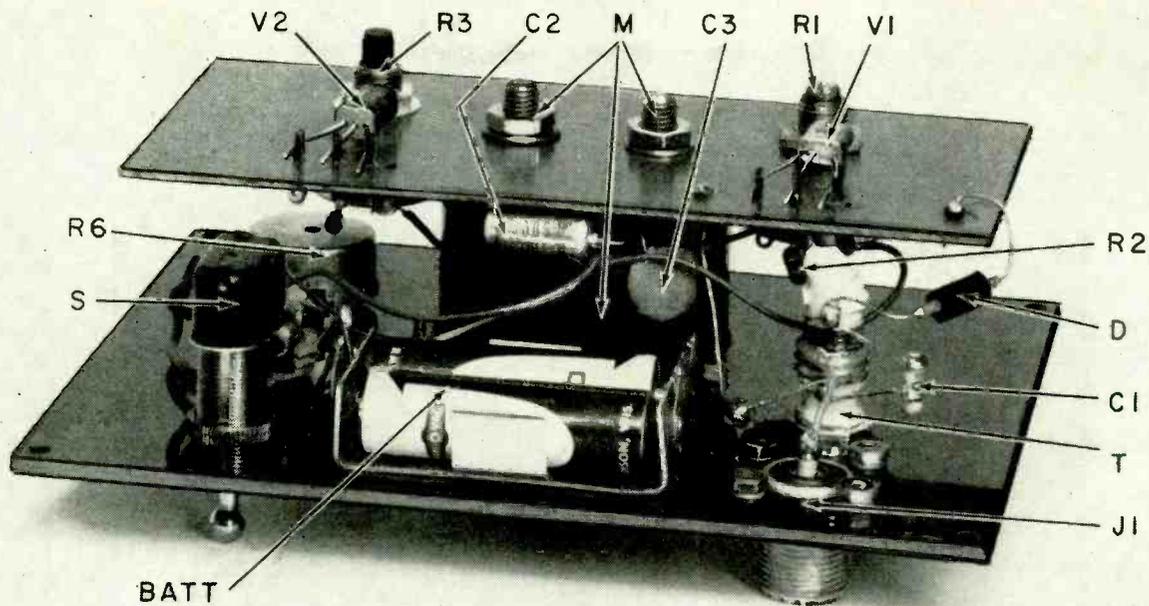Operating procedure is straightforward: Set R6 at half-scale (about 2,500 ohms) and adjust R3 (inside the meter case) for a full-scale meter reading. Make this adjustment with no signal.



The phenolic chassis is fastened to the meter. This gives firm yet simple mounting.

Now adjust T and R1 for maximum meter deflection with a 27-mc signal. The meter reads full scale with no rf signal, and R6 which is on the front panel is used to set the meter to full scale. R1 and R3 inside the case are adjusted once and left alone unless transistors are changed.

The circuit is temperature-sensitive (like all transistor circuits of this type) so R6 has to be adjusted each time the switch is turned on. If this full-scale meter adjustment is beyond the range of R6, reset R3 inside the case. In measuring field strength, we are primarily concerned with tuning the transmitter for maximum output, so we adjust for maximum meter *swing* regardless of the no-signal setting of the meter. Plugging in the phones will alter the meter reading, but this is of no consequence because field-strength measurements are normally made with the phones disconnected. The undistorted audio output is low, current through the phones being limited to 500 μ a at 3 volts, but it is adequate for checking hum and modulation difficulties with a small transmitter. If the field-strength meter is being operated within 10 feet of the transmitter, the audio output will be distorted because of overloading. If it is necessary

to work very close to the transmitter, remove the whip antenna. The easiest way to reduce the signal is to move away from the transmitter until a point is found where speech is clean and the circuit no longer overloads.

To evaluate different antennas, proceed as follows: Set up the field-strength meter at a known fixed distance from the antenna to be checked out. Set the meter to full scale with R6 and then turn on the transmitter, tune it to the antenna and take a field strength reading. In this way, various antennas, locations and transmitters can be compared. Use a tape measure and choose a convenient distance such as 25 or 30 feet for all measurements. By keeping the distance from the antenna constant, the relative meter reading will show antenna and transmitter efficiency and may be used as an accurate basis for comparing equipment. The rf output from the antenna can frequently be doubled or tripled with careful tuning and adjustment, and this is certainly worth while when we consider the low power and limited direct range of a Citizens-band transmitter.

The direct-coupled meter circuit has proved rugged and dependable in actual use. By reversing the polarity of the

diode, the meter can be made to swing in the opposite direction with an rf signal and, if a transistor with low leakage is selected for V2, the no-signal "zero" reading on the meter will be small.

With diode polarity reversed, R1 and R3 should be adjusted for a low initial meter reading, rather than a full-scale reading. This field-strength meter will give a satisfactory indication either way; the one you use is a matter of choice. When the diode polarity is reversed, set R6 for a full-scale meter reading with the maximum signal normally encountered.

Any of several base-loaded whip antennas can be used with the field-strength meter. Listed in order of best performance for this unit they are:

- International Crystal CRA 208
- Lafayette HE17
- Radio Shack 29D672 (I used this)
- Allied Radio 83YX729
- Philmore AA59

Mount the meter, S, J1, J2, T, the batteries and R6 on the front panel. The rest of the parts should be mounted on a small 1/8-inch linen bakelite subpanel which is held in place by the meter as shown in the photograph. Layout is not critical and all the parts to be used may be placed on the undrilled panels and outlined with pencil to locate the mounting holes. The transistors are mounted with six flea clips, three per transistor. Parts on the subpanel, including the flea clips, should be wired before it is attached to the meter. Be sure to observe correct polarity when connecting the transistors, diode, electrolytic capacitor, and battery. Be sure to install the transistors correctly and remember one of them is an n-p-n while the other is a p-n-p. If you install them the wrong way, both will be ruined. END

BENCH




TESTED

Specifications: Must for tuning up Citizens'-band transmitters • Completely portable • Very sensitive direct-coupled transistor circuit.

Performance Data: Tests conducted by a member of the staff of RADIO-ELECTRONICS showed operation substantially follows author's specifications. Unit is excellent for 27 mc, yet does not react to high power at 21 mc (50 watts). Sensitive enough to give a reading from a 250-mw transmitter. Components are comparatively inexpensive.

For Push-Pull AND Push-Push Switch Type Controls

it
all
adds
up
to
Centralab

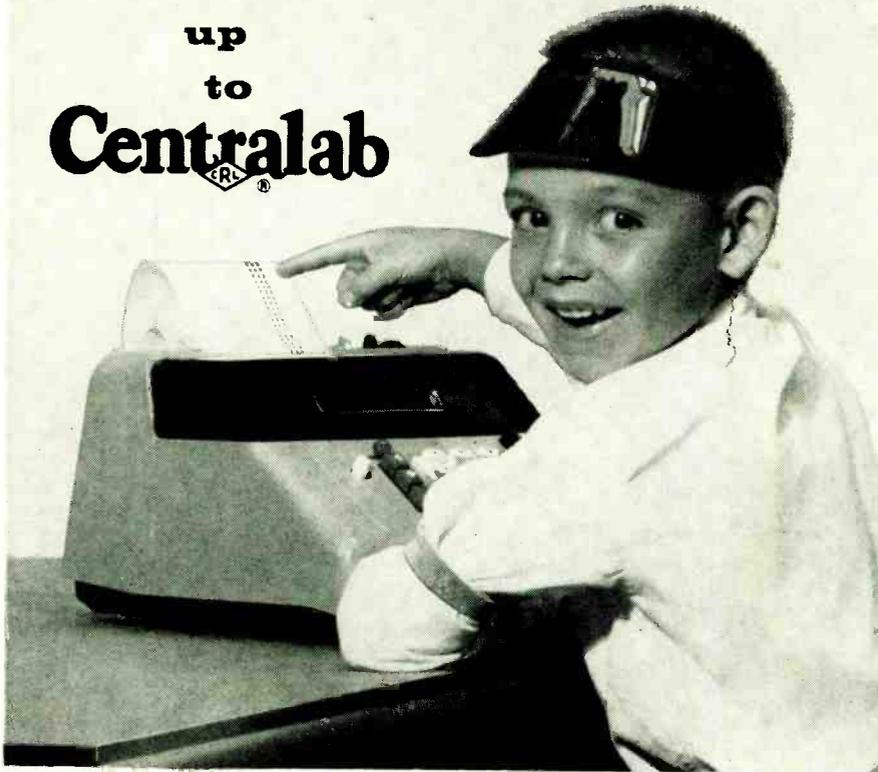

Look at the figures—78% of the TV, radio and hi-fi sets now being produced utilize push-pull or push-push controls! Only CENTRALAB gives you a *complete* line of replacements for them—35 push-pulls, plus the *only* push-push units available! To multiply your choice, these CENTRALAB switch-type controls are divided into 4 types—Adashaft, Universal Shaft, Fastatch or dual concentrics, and Twin types for stereo. Whatever kind you need, you can be sure your CENTRALAB distributor has it. For a complete accounting on these push-pull and push-push controls, ask your distributor for Bulletin 42-936 or write us for your free copy.

Centralab

THE ELECTRONICS DIVISION OF GLOBE-UNION INC.
922K EAST KEEFE AVENUE • MILWAUKEE 1, WISCONSIN
CENTRALAB CANADA LIMITED—AJAX, ONTARIO

B 6034

ELECTRONIC SWITCHES • VARIABLE RESISTORS • CERAMIC CAPACITORS
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS


SOUND AT THE cocktail party

HUMAN hearing is amazing. Ever notice how you can be in a crowded room filled with people all talking at the same time and still be able to concentrate on a specific voice and separate it from all other sounds even though it may be no louder than the surrounding noise level?

This "cocktail-party effect" works so well that any two-eared listener can enhance the effective intensity of the desired voice by 5 to 15 db simply by mentally suppressing the background noise level.

All this is well and good, but can it be duplicated electronically? Yes, it can and has been done. The way to do it was described by E. E. David, Jr. and J. F. Kaiser of the Bell Telephone Laboratories at a meeting of the Acoustical Society of America.

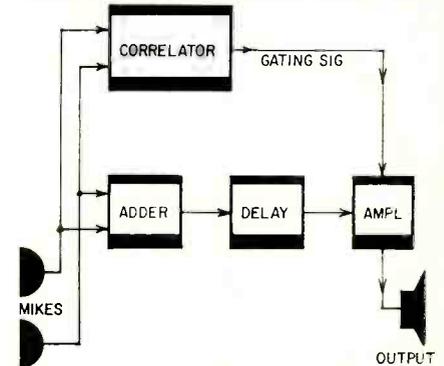The device these scientists use takes the output of two microphones (see dia-



gram), compares them and cross-correlates them to generate a gating signal which is applied to the combined output of the two mikes. The gating raises the intensity of the combined signal only when energy from the desired voice arrives simultaneously at both microphones. At all other times the gate suppresses the combined signal. Noise or interfering speech is passed through the gate only if it occurs at the same instant as the desired speech signal.

Subjective tests with a prototype unit showed enhancements of 9 db in effective signal levels against an interfering single-talker background. A smaller enhancement, 5 db, was measured when two extra talkers interfered. END



RADIO-ELECTRONICS


Mercury offers you **MORE** for your TEST EQUIPMENT DOLLAR!

NEW




Model 700
TRANSISTOR TESTER
Dealer Net **\$2425**

NEW

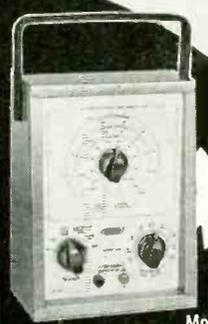

Model 500
COMPONENT SUBSTITUTOR
Dealer Net **\$2995**

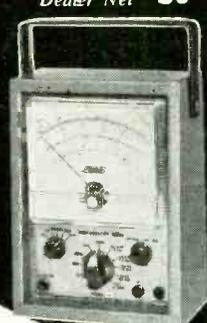
Model 400
VOM-CAPACITY TESTER
Dealer Net **\$3995**



Model 600 IN-CIRCUIT
RECTIFIER TESTER
Dealer Net **\$2750**



NEW

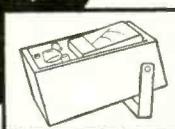

Model 700—Tests all transistors and diodes quickly and accurately • Checks all transistors (RF, IF, Audio, Power Output, Industrial) for leakage and gain • Checks all diodes for forward-reverse current ratio • *No time consuming reference to data charts necessary* • *Positively cannot become obsolete* as the Model 700 will accommodate new transistors as they are introduced • Sturdy hammertone finish steel case • Size, 5 7/8 x 7 3/4 x 3 1/2".

Model 500 — Actually substitutes for 44 different values of resistors, condensers, electrolytics, power rectifiers, crystal diodes, power resistors and bias voltages. Substitutes: 20 values of resistors from 33 ohms to 10 megohms • 10 values of condensers .0001 mfd. to .5 mfd. • 10 values of electrolytics from 4 mfd. to 330 mfd. • Power rectifiers up to 500 ma. • Crystal diodes • Power resistance, continuously variable up to 5000 ohms • Voltages, continuously variable up to 15 volts either polarity • Sturdy hammertone finish steel case • Size, 5 7/8 x 7 3/4 x 3 1/2".

Model 400—A 20,000 ohms per volt VOM and an accurate capacity meter. DC VOLTAGE RANGES: 0 to 15/75/150/300/750/1500/7500 V. • AC VOLTAGE RANGES: 0 to 15/75/150/300/750/1500 V. • RESISTANCE RANGES: 0 to 1,000/100,000 ohms/0 to 10 meg-ohms • RANGES: 0 to 75 microamps/7.5 ma./75 ma./15 amps. • CAPACITY RANGE: .001 mfd. to 80 mfd. • Sturdy hammertone finish steel case • Size, 5 7/8 x 7 3/4 x 3 1/2".

Model 600—Checks all power rectifiers *in-circuit* (whether SELENIUM, GERMANIUM, SILICON, COPPER OXIDE, etc.) rated from 10 ma. to 500 ma. • Checks with 100% effectiveness for quality, fading, shorts, opens, arcing, life expectancy • Simple to use: just clip test leads across rectifier under test *without disconnecting rectifier from circuit*. Press test switch and get an instant indication on the 3-color metal scales • Checks all power rectifiers out-of-circuit with equal effectiveness • Sturdy hammertone finish steel case • Size, 5 7/8 x 7 3/4 x 3 1/2".

New Mercury design projects meter forward . . . metal handle swings back to serve as rest so that instrument can be used in tilted position

Model 300 COMBINATION TESTER



NOW also available in KIT form!

Model 101 TUBE TESTER



Model 800 CRT TESTER-REACTIVATOR




✓ A multiple-socket tube tester ✓ A CRT tester-reactivator ✓ A 20,000 ohms per volt VOM and capacity tester **ALL COMBINED IN ONE COMPACT UNIT!**
 • AS A TUBE TESTER . . . will check emission, inter-element leakage and gas content of over 700 tube types • AS A CRT TESTER-REACTIVATOR . . . will test, repair and reactivate all black and white and all color picture tubes • AS A VOM AND CAPACITY TESTER . . . sensitivity is 20,000 ohms per volt/DC and 5000 ohms per volt/AC . . . Capacity range: .001 mfd. to 80 mfd. • Unbreakable mirror for TV adjustments inside detachable cover • Handsome wood carrying case.
 Size: 17 1/2 x 13 1/8 x 4 1/2".
 Dealer Net **\$9975**

A versatile economy priced tube tester
 • Checks quality (emission, shorts and gas) of over 700 tube types, including the newest series-string TV tubes, OZ4s, gas regulators, hi-fi and foreign tubes • Checks each section of multi-purpose tubes • Easy-to-read 3 color meter scales • 17 long lasting phosphor bronze tube sockets • Positively cannot become obsolete. New tube listing furnished periodically to all registered owners • Sturdy-gray hammertone steel case • Size: 9 x 8 1/2 x 2 3/4".
 KIT — WIRED —
 Dealer Net **\$3195** Dealer Net **\$3995**


✓ TESTS ✓ REPAIRS ✓ REACTIVATES all BLACK and WHITE and all COLOR picture tubes
 • TESTS . . . emission, inter-element leakage and life expectancy • REPAIRS . . . shorts and open elements • REACTIVATES . . . weak tubes with a controlled high voltage pulse (reactivation is seen and controlled on the enter as it takes place)
 • Tests the red, green and blue sections of color tubes separately • Also provides the newer 2.35 and 8.4 filament voltages • Unbreakable mirror for TV adjustments inside detachable cover • Handsome wood carrying case •
 Size 11 x 9 1/2 x 4 1/2".
 Dealer Net **\$4995**

Model 102-P TUBE TESTER

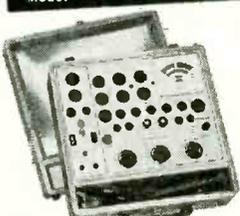

Same specifications as the Model 101 • Also tests picture tubes, all diodes, rectifiers, fuses, pilot lamps • Unbreakable steel mirror for TV adjustments inside detachable cover • Handsome wood carrying case.
 Dealer Net **\$5950**

Model 102-C CADDY TUBE TESTER

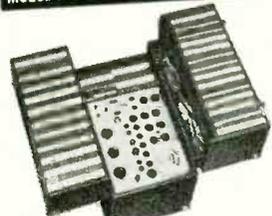


Tube tester has same specifications as Model 102-P • Tester is removable • Extra storage compartment under tester • Drawer for tools and test leads • Unbreakable mirror mounted under tester case for TV adjustments.
 Dealer Net **\$7450**

SELF-SERVICE TUBE TESTERS

Cannot become obsolete as new tube types are introduced!

Model 201-F (floor model)
 Dealer Net **\$15850**

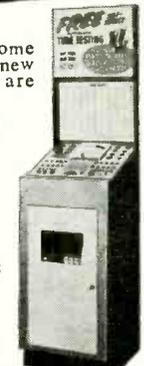Model 201-C (counter model)
 Dealer Net **\$10950**



SOLD ONLY THROUGH PARTS DISTRIBUTORS

FREE The instruction manual for any instrument shown is available upon request . . . use coupon below:

MERCURY ELECTRONICS CORP.
 77 Searing Avenue, Mineola, N. Y. E-10

Please send me instruction manuals of the test instruments I have checked.

<input type="checkbox"/> Model 700	<input type="checkbox"/> Model 101
<input type="checkbox"/> Model 500	<input type="checkbox"/> Model 800
<input type="checkbox"/> Model 400	<input type="checkbox"/> Model 102-P
<input type="checkbox"/> Model 600	<input type="checkbox"/> Model 102-C
<input type="checkbox"/> Model 300	<input type="checkbox"/> Model 201

Name.....
 Address.....
 City..... State.....

MERCURY ELECTRONICS CORP. 77 SEARING AVENUE, MINEOLA, NEW YORK
 West Coast Office: 4306 W. Victory Blvd., Burbank, Calif.

see the exciting **1961**

knight-kits[®]

A PRODUCT OF ALLIED RADIO


in this value-packed **ALLIED** catalog

free

444 pages
most complete

send for it!

use coupon
on next page

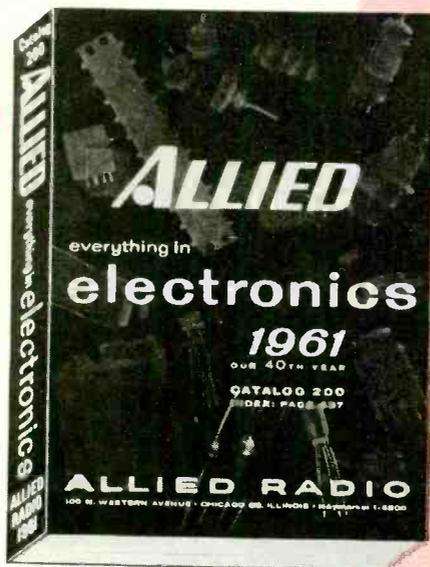

knight-kits — Best by Design

FUN TO BUILD Building it yourself is always satisfying fun—it's fun at its best when you build Knight-Kits—they're so beautifully engineered, so much easier, more pleasurable to work with...

YOU SAVE You save substantially because you buy direct from Allied at our money-saving big-volume-production prices—and because you do the easy building yourself...

YOU OWN THE BEST You'll be glad you built a Knight-Kit, because you'll own and enjoy with pride a true custom-built product, professionally engineered and styled—designed for superior performance...


EASIEST TO BUY **only \$2 down** on orders up to \$50; \$5 down up to \$200; \$10 down over \$200—up to twenty-four months to pay...

exclusive knight-kit **MONEY BACK GUARANTEE**

Every Knight-Kit is unconditionally guaranteed to meet our published specifications for performance or your purchase price is refunded in full.

Buy Any Knight-Kit!
...Build and Use It!
It Must Perform
Exactly as Claimed!

Your Satisfaction is Guaranteed

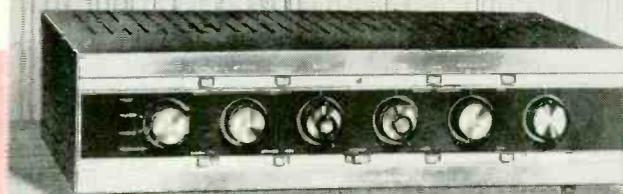

70-Watt
Super-Power
Stereo!

DELUXE 70-WATT STEREO AMPLIFIER

Super-power to drive any of today's speakers; the ultimate in control flexibility and functions. 83 YU 934 **\$119.95** only **\$5** down

see many more great **HI-FI KITS**

Stereo Preamp	18-Watt Amplifier
60-Watt Stereo Amplifier	12-Watt Amplifier
Stereo Control	FM Tuner
25-Watt Amplifier	Speaker Systems



ALL-BAND SUPERMET RECEIVER

Covers 540 kc to 36 mc, plus 6 meters; general coverage tuning and calibrated Amateur bandspread tuning. 83 YU 935 **\$67.50** only **\$5** down

see many other **HOBBYIST KITS**

"Space Spanner" [®] Receiver	Transistor Radios
"Ocean Hopper" Radio	Intercom Systems
Radio-Intercom	Electronic Lab Kits
Clock-Radio	Photoelectronic System



BEST VTVM VALUE

High sensitivity general-purpose VTVM; 11 meg input resistance; balanced-bridge circuit; 4½" meter. 83 Y 125 **\$25.75**

only **\$2** down



only **\$2** down

From original concept to final design, each Knight-Kit is produced by and comes directly to you from **ALLIED**

sold exclusively by


ALLIED

knight-kits: best in build-your-own electronic equipment



STEREO TAPE RECORD/PLAY PREAMP

Professional quality; permits tape monitoring, sound-on-sound and echo effect; use with any tape transport. 83 YX 929 (less case) **\$79.95**

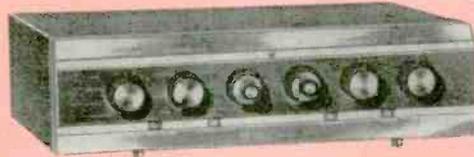

DELUXE 40-WATT STEREO AMPLIFIER

Full frequency center channel. Finest amplifier available anywhere in this price range. 83 YU 774.....**\$76.95**




SUPER-VALUE STEREO HI-FI AMPLIFIER

20-Watt Stereo Hi-Fi Amplifier, with special clutch-type dual-concentric level control; biggest bargain in Stereo hi-fi. 83 YX 927.....**\$39.95**

Only \$39.95 For Full 20 Watts Stereo!

DELUXE FM-AM STEREO HI-FI TUNER

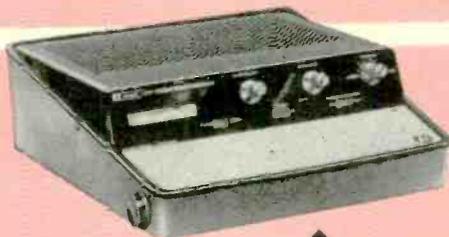Dynamic Sideband Regulation, variable AFC, "Magic Eye" slide-tuning, multiplex add-in. 83 YU 731.....**\$87.50**



SUPERHET CITIZENS BAND TRANSCEIVER

Dual-conversion receiver for highest sensitivity and selectivity; 2-channel crystal-controlled 5-watt transmitter. 83 YX 712-2.....**\$79.95**



TOP VALUE CITIZENS BAND TRANSCEIVER

Lowest-priced complete Citizens Band Transceiver. Tunable 22-channel super-regenerative receiver; 5-watt transmitter. 83 Y 713-2.....**\$39.95**

\$39.95 For This Citizen's Band Transceiver



FM-AM HI-FI TUNER BUY

Outstanding FM-AM Hi-Fi Tuner; with AFC and tuned RF stage on FM; includes multiplex jack. 83 YX 928.....**\$49.95**



32-WATT STEREO AMPLIFIER VALUE

Money-saving 32-Watt Stereo Hi-Fi Amplifier; high power at low cost; full frequency center channel. 83 YU 933.....**\$59.95**

SENSATIONAL 4-BAND "SPANMASTER" RECEIVER

For thrilling world-wide reception; exciting Short-wave and Broadcast; band-switching, 540 KC to 80 MC. With cabinet. 83 YX 258.....**\$25.95**



"600" TUBE CHECKER

Checks over 700 types; illuminated roll-chart; obsolescence-proof design. 83 YX 143...**\$32.95**

RF SIGNAL GENERATOR

Output to 112 mc on fundamentals; 400-cycle modulation. 83 Y 145.....**\$19.75**

full selection of INSTRUMENT KITS

- 5" Oscilloscopes
- AC VTVM
- Tube Checkers
- Signal Tracer
- Audio Generator
- Sweep Generator
- Battery Eliminator
- Capacity Checker
- Transistor Checker
- R/C Tester,
- plus many others*



free

SEND FOR THE 444-PAGE 1961 ALLIED CATALOG

Write today for the world's biggest electronics catalog, featuring the complete KNIGHT-KIT line. See the big news in quality electronic kits—save on everything in Electronics. Send for your FREE copy.

send for it today!

**ALLIED RADIO, Dept. 162-K
100 N. Western Ave., Chicago 80, Ill.**

Send FREE 1961 ALLIED Catalog


Name _____

Address _____

City _____ Zone _____ State _____

RADIO

Pioneer in electronic kit development

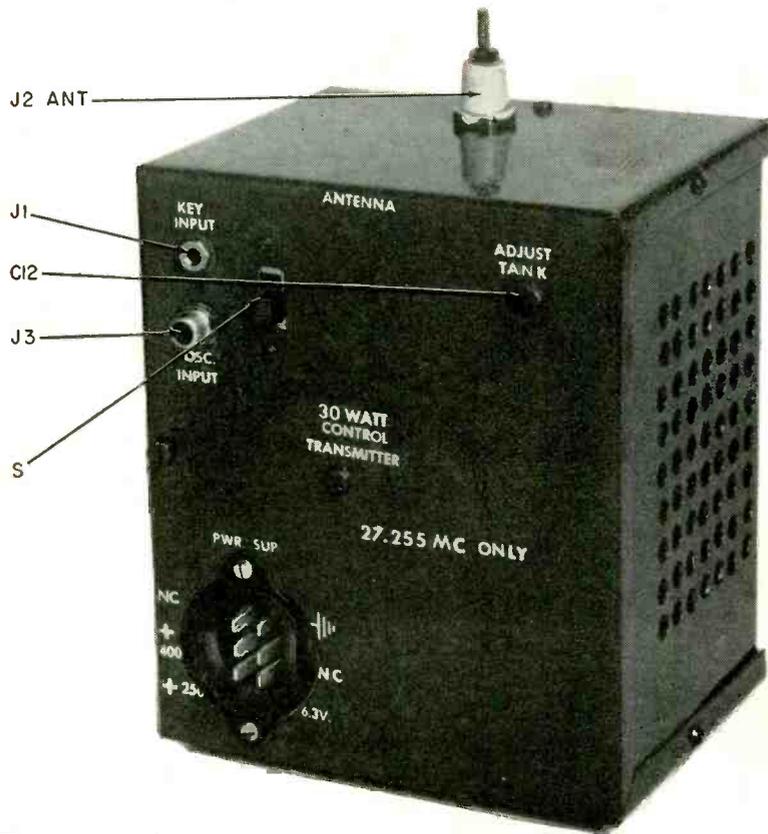

radio control with

OOMP

30 watts of remote-control power in a 4 x 5 x 6-inch package

The completed unit. Author used a 6-terminal Jones plug to connect the separate power supply.

By J. H. THOMAS

IN the excitement over the Citizens-band communications many may have overlooked the simultaneous change in the control channels, which allows 30 watts input on one of them, channel 23 (27.255 mc). Most radio control transmitters were designed for the earlier 5-watt maximum input. But here is a compact, powerful transmitter which can take advantage of the new regulations for class-C transmission.

The unit (Fig. 1) has a 30-watt input and can be keyed (for carrier control) or modulated for control by audio tones. The modulator is included in the unit, but the power supply (Fig. 2) is separate. Fig. 1 shows the complete schematic of the transmitter and modulator. Half of a 12AV7 is the crystal oscillator. Here you should note that for 30-watt input the FCC requires .005% frequency control (for less than 3-watt input .01% is permitted). Make sure that the crystal you buy has the proper frequency tolerance. The second 12AV7 section is an amplifier driving the 6BQ6 final.

The 6BQ6 final amplifier is screen-modulated. This is one of the most economical ways of modulating, but you can't use it and get 100% modulation—about 80% is the best that can be expected. This can be obtained with less than 1-volt signal at the modulator's input. (For 100% modulation, the screen would have to be driven negative.)

Switch S enables the operator to select modulated or unmodulated opera-


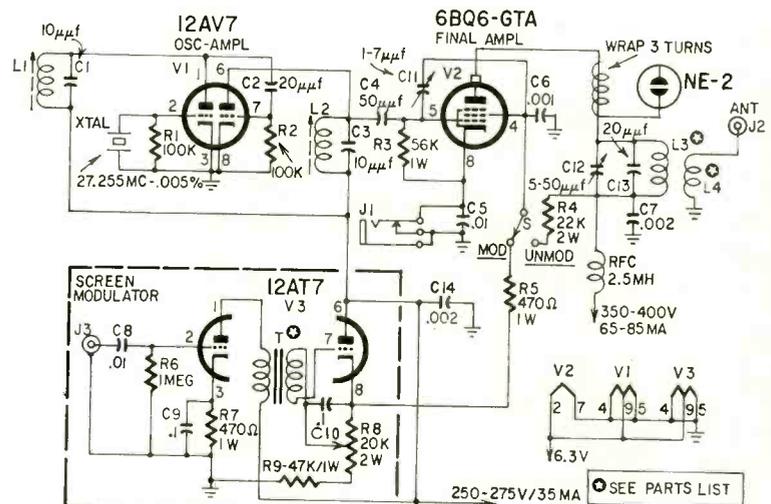



Fig. 1—Circuit of the radio control transmitter.

- R1, 2—100,000 ohms, 1/4 watt
- R3—56,000 ohms, 1 watt
- R4—22,000 ohms, 2 watts
- R5, 7—470 ohms, 1 watt
- R6—1 megohm, 1/4 watt
- R8—pot, 20,000 ohms, 2 watts or more, wirewound
- R9—47,000 ohms, 1 watt
- All resistors 10% tolerance
- C1, 3—10 μ f, disc ceramic
- C2, 13—20 μ f, disc ceramic
- C4—50 μ f, disc ceramic or mica
- C5, 8—01 μ f, disc ceramic
- C6—001 μ f, disc ceramic
- C7—002 μ f, disc ceramic
- C9, 10—0.1 μ f, paper
- C11—1-7 μ f, trimmer
- C12—5-50 μ f, trimmer
- All capacitors 600 volts
- J1—phone jack, normally closed

- J2—standoff insulator
- J3—phono jack
- L1, 2—15 turns No. 24 DCC on 1/4 inch slug-tuned coil form (Miller C-1 or equivalent)
- L3—11 turns No. 14 bare copper wire. Wind into coil 1/2-inch ID, 1 1/4 inches long, supported on C12.
- L4—2 turns No. 14 bare copper wire. Wind 3/4 inch ID, supported on standoff insulator.
- Leave one end long enough to reach chassis ground. Mount surrounding cold end of L3.
- S—spdt slide switch
- T—4:1 audio interstage transformer
- V1—12AV7
- V2—6BQ6-GTA
- V3—12AT7
- Case, 4 x 5 x 6 inches
- Socket, octal
- Sockets, 9-pin miniature (2)
- Neon lamp (NE-2)
- Miscellaneous hardware

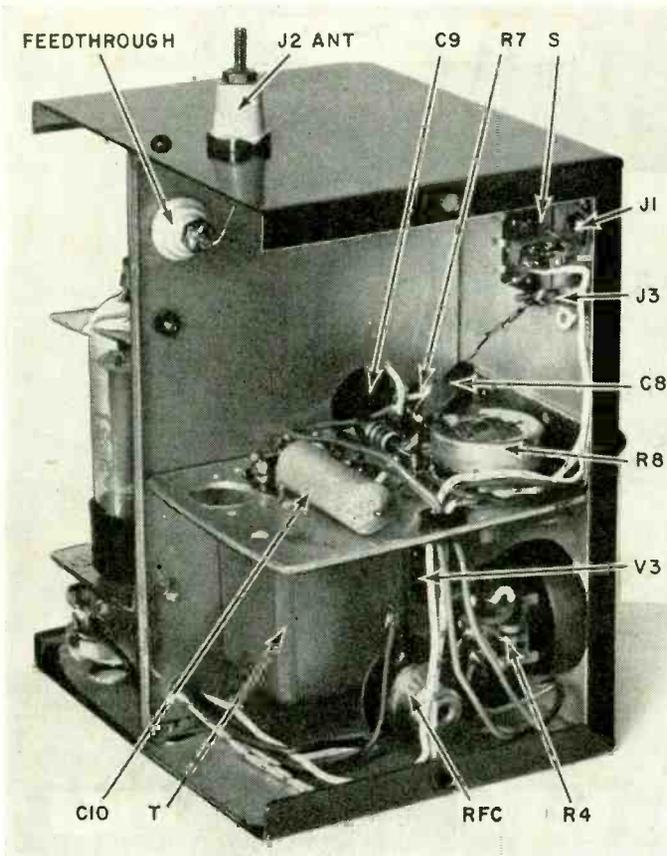

A look inside the transmitter's case.

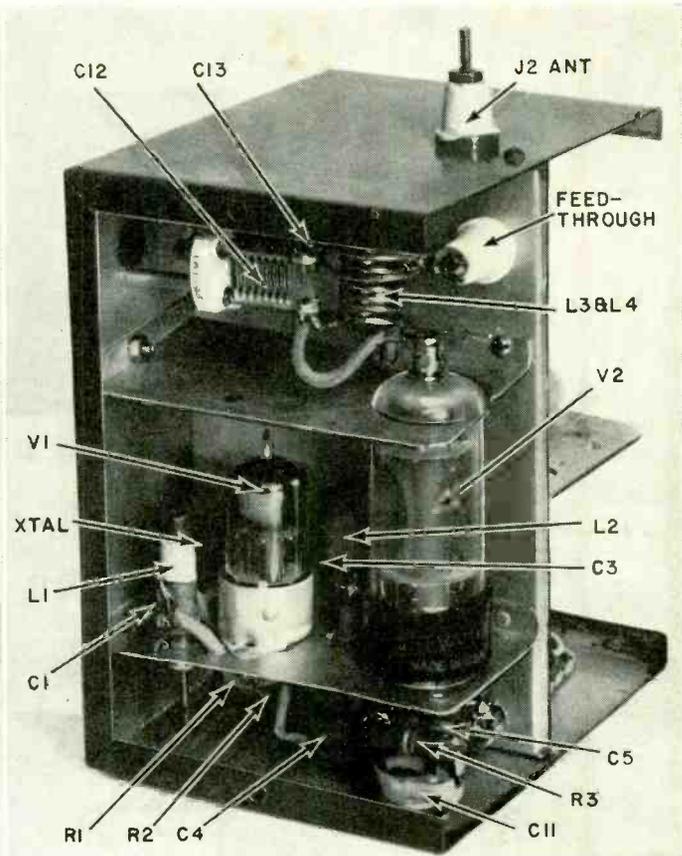

Another view of the transmitter's interior.

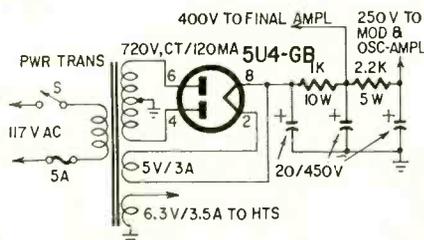


Fig. 2—Simple power supply for the transmitter.

tion. In one position, UNMOD, the screen is directly connected to the plate supply through R4. The transmitter is then operated with a key or switch connected to J1.

Adjusting the unit is easy. Hook up a dummy load, two No. 31 bulbs in parallel, across J2 and ground. Next tune the resonant circuits, L1-C1 and L2-C3, with a grid-dip oscillator to a frequency slightly higher than 27.255 mc. This must be done with the tubes in place since their input and output capacitances contribute to the total circuit capacitance. Then apply power and tune the bulbs in the dummy load for maximum brightness. Lack of signal will show up immediately as a sudden increase in plate current to the final. When the transmitter is lighting the bulbs, slowly increase the inductance of L1 and L2 a bit at a time, again increasing the bulb's brightness. Suddenly you will reach a point where no signal is generated. Back off a quarter of a turn on both L1 and L2, and turn the power off and on to shock the crystal into operation. If the bulbs light

each time you turn on the power, L1 and L2 are properly tuned. A final tank adjustment is necessary to match to the antenna you'll be using.

This kind of power can effectively shut down communication on the upper Citizens-band channels for miles around, if the communicators are using broadly tuned superregenerative receivers. So use the transmitter sparingly. The FCC permits the radio control transmitter to be on only when actually controlling objects.

In the modulator, with no modulation applied, R8 is adjusted for an antenna current of about 30% of the UNMOD position. However, this is difficult to judge with only a lamp load. Using a grid-dip oscillator as a detector may help, and it should show a reduction of about 50% with the modulator in the circuit.

What can you do with such a powerful transmitter? Well, for one thing you can consider control operations which would have had no margin of safety with low-power transmitters. The usual reliable range of ½ mile can now be increased to many miles. If you are a rocket fan, you can control missiles with it. If you just want to open


the garage door, you can now make sure that the door is fully open before you get there. Or you can use this transmitter to call people with a paging receiver. Voice transmission is not permitted, but calling is. In the words of the FCC (Part 19, paragraph 19.34c) "... for the remote control of objects or the remote actuation of devices used solely as a means of attracting attention."

Many other new uses will crop up. Controlling agricultural machines and devices over considerable distances and turning irrigation pumps on and off are a few farm applications. Industrial uses would include opening and closing doors, guiding carts and loading devices, etc. A friend of mine uses his to anchor his boat a considerable distance from the pier. A special pelican hook disconnects the mooring line from a buoy after a control impulse starts the engine. Control of engine and rudder then brings the boat alongside, saving the owner an arduous rowing trip.

The station must be licensed by the FCC. Such a license is not hard to get if the equipment is crystal-controlled and meets other specifications as set forth in part 19 of the rules. END

- Operates on Citizens band
- Long-range radio control
- 30-watt input
- Tone or carrier type operation

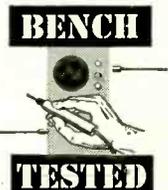Unit meets author's specifications. Transmitter has high output and seems to show no signs of frequency drift. If unit is stable—and this one is—it can be tuned to proper frequency. Transmitter must be on frequency. (Allowable tolerance is .005%.)



Tube-Changing The Tough Ones



By JACK DARR

RADIO-ELECTRONICS TELEVISION CONSULTANT

Changing a tube is often only the start of a repair job. It can indicate burnt-out resistors, shorted capacitors or other damaged components.

"THAT finishes Ozz-wald," said the Old-Timer, laying down his soldering gun. "Now we'll let him sit and cook for a while. Make sure his horizontal sweep is back in order. So, Junior, with the work out of the way for a while this looks like a good day for me to do a little lecturin', so get ready."

The Young Ham tore off a couple of pieces from the filthy cloth which was referred to as "the shop's clean rag" and pretended to stuff them in his ears. The Old-Timer made threatening motions at him and resumed.

"Well, sir, there's more to 'tube-changing' than just pluggin' in new tubes. For instance, if you open up a set and find the B-plus fuse blown, you might just put a new fuse in and go on, but if you do, you'll probably be back pretty soon. You oughta check the damper tube. Here." He pointed to it in the set on the bench. "See? Better check it for shorts by flipping it pretty hard with your finger, like this." He snapped his middle finger against the tube base. "If there's any shorts in it you'll notice it arcin' and sparkin' right down here at the base of the elements. You may short it out and blow a fuse, but better blow it now than after you leave. Lots of guys replace the damper tube anyhow, whenever they find that fuse blown, just for luck."

"How about the high-voltage rectifiers?" asked the Young Ham. "They give a bit of trouble too, don't they?"

"Yes, but not as much," replied the

Old-Timer. "They're pretty easy to spot. If you can draw a fairly good arc from the plate cap, but haven't got any high voltage on the picture tube, change the rectifier. But don't assume the rectifier's good if you can't get an arc; I've found several of 'em that must have been shorted. If they're weak you'll get 'blooming.' The picture will get a lot bigger when you turn up the brightness control. Generally goes out of focus at the same time."

"Can't you get the same symptoms from the horizontal output tube?" asked the Young Ham.

"Nope, just the opposite," said the

Old-Timer. "Usual sign of that is a narrow picture. Weak tube don't have enough poop to swing the beam all the way across. Also, a weak oscillator tube will narrow the picture. Look out though; I found one once that bloomed just like a bad 1B3—turned out to be a bad 6SN7 in the horizontal oscillator! Those are pretty scarce though. Y' want to look out for two-tube troubles. If the oscillator gets weak and don't drive the output tube and it's run for some time, the output tube may get weak from being underdriven and drawing too much plate current."

"Oh," said the Young Ham, "just like the final in my transmitter!"

"Pree-cisely," said the Old-Timer. "Same identical thing, in fact. These horizontal output tubes operate just exactly like your finals. Horizontal linearity control works kinda like your plate tuning. It 'tunes' the output of the stage so it will work most efficiently. So if you lose the drive on one of these hard-workin' little tubes, the chances are you'll weaken it considerable. Now, then! Here's somethin' you've got to do every time you change the horizontal output tube or oscillator. Check to see that the output tube has the proper amount of drive on its grid. Unless you do that, the chances are the new tube won't last too long!"

"How you gonna check that without taking the set out of the box?" asked the Young Ham. "The grid's on the bottom, pin 5, isn't it?"



Checking tube-element voltages from the top of the chassis. All it takes is a test-socket adapter.



SYLVANIA-6AU4-GTA

WITH

SARONG CATHODE

HELPS YOU

"WRAP-UP" PROFITS!

NEW life-giving, profit-building features are built into every SYLVANIA-6AU4-GTATV-damper tube. Consider, for one feature, the SYLVANIA SARONG CATHODE and how it adds dependability to tube life. SARONG provides uniform spacing between cathode and plate—reduces possibility of plate-to-cathode arc-over. SARONG prevents the build-up of “whiskers” inside the cathode sleeve that can develop during other types of coating processes—reduces possibilities of cathode-to-heater arc-over.

Consider, too, the “pigtail” heater in SYLVANIA-6AU4-GTA. Welded securely to the stem-lead, it reduces heater “hot spots” and the possibilities of heater burnout. More . . . rectangular top and bottom micas with exceptionally wide slots increase the resistance of dc leakage paths, further reduce the possibilities of internal arc-over and breakdown.

There's extra profit assurance, too, with SYLVANIA-6AU4-GTA. Every one of them is tested for shorts, emission and the ability to withstand arc-over at 5000-volts peak inverse on the anode.

So, “wrap up” the profits you make by putting a “damper” on call-backs. When you ask your distributor for 6AU4-GTA's, always specify SYLVANIA.

Electronic Tubes Division, Sylvania Electric Products Inc., 1740 Broadway, New York 19, New York.



SYLVANIA

Subsidiary of **GENERAL TELEPHONE & ELECTRONICS** 

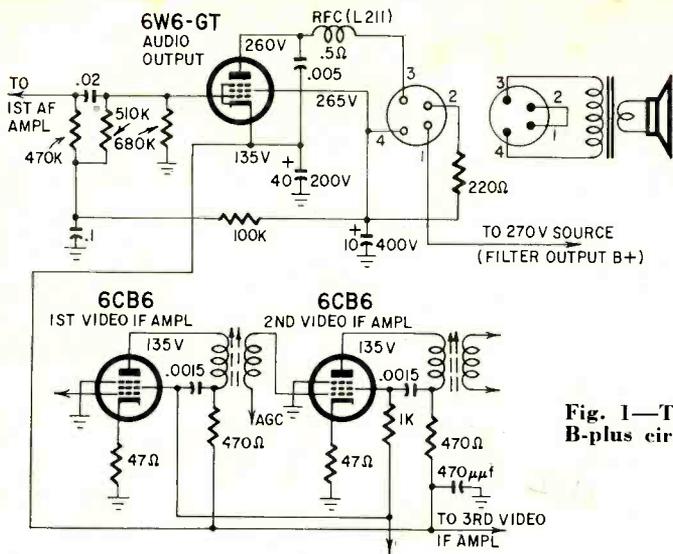


Fig. 1—Typical series B-plus circuit.

"On the 6BQ6, 6CU6 and some others it is," answered the Old-Timer. "Here's the answer to that problem." He reached a long arm up to a little shelf over the bench, and brought down an adapter. Turning the set off, he removed the 6BQ6, plugged it into the adapter and replaced it in the set. Turning the set on, he reached for a vom lying nearby. "See? The grid comes out to these little studs on the side here. Measure it with that little vom we keep in the tube caddy. There's one of these adapters in the tool kit too. See here? 28 volts negative. That's about what it should be. For this tube and this set, that is. There's some variation, but not too much. Now if that'd been down around 15 volts, we'd have had to check the oscillator, the setting of the horizontal drive, or something. If you don't get enough drive, you'll notice the plate showing a little color and that ain't right. Shouldn't run red-hot, like the tubes in your transmitter sometimes do."

"Aww, they were only a little pink," said the Young Ham. "That just means they're good tubes!"

"Yep, rf output and heat the ham shack, all for the same price, huh?" said the Old-Timer. "But we ain't interested in heatin' the house here; we just want a good picture."

"Yeah, and how about some of these tight-fitting doghouses? If you raised the tube that much, the plate cap would short to the shield or at least arc over!" argued the Young Ham.

"Simple. Use some of that amateur ingenuity. Looky," and the Old-Timer pulled the tube, removed the adapter and slipped a short piece of solid in-

sulated wire over the grid pin, after bending a loop on both ends and sliding the insulation back a bit. Replacing the tube, he clipped the voltmeter lead to the loose end. "Verstehen sie das, kinder?" he grinned. The Old-Timer had worked in South St. Louis long enough to pick up a smattering of "commercial German" and never tired of showing it off.

"Jawohl, Grossvater!" said the Young Ham, who hadn't been listening to him all year for nothing.

"'Nother thing," continued the Old-Timer, "you always oughta check your horizontal hold for proper range. In the average set with a good strong signal, you should be able to hold the picture over the entire range of the hold control. Of course, this means only the standard carbon-pot type of hold control, not some of them sets like the RCA's and the Stewart-Warner 9126 where the hold control knob was actually the end of the slug in the horizontal oscillator coil and you could keep turning it as long as you wanted to, almost. If your picture falls out with only a little turn of the control, chances are you've got a weak oscillator tube. Change it and see if your hold range doesn't go back to normal."

Combination troubles

"Now you get to the combination troubles. Stuff that's caused by one tube, but shows up like it was another one! Look here," taking a schematic from the file and spreading it on the bench. "What's going to happen if you get a heater-cathode short in this audio tube?"

"I don't know. Let's see . . ." and

the Young Ham bent over the schematic (Fig. 1).

"I'll give you a hint. Follow the cathode circuit and see where it goes."

"It goes to . . . the if plate?"

"Yep. That's a series-B-plus circuit. They've got around 300 volts in the power supply, so to save makin' a voltage divider they connect the audio output and the video if's in series, for their plate supply. If you'll check the voltages you'll see that each one runs about 150 volts from plate to cathode. Now, you see they show the audio plate 260 volts, the cathode 135 volts, and the if plates 135 volts. This is from ground, of course. Now, what happens if you get a heater-cathode short in that 6V6 audio output?"

"You'd have the 260 volts on the if plates," said the Young Ham.

"Hello? Where'd you get the 260 volts?" said the Old-Timer.

"Well, it'd go right through the audio stage and to . . . Oh! I see. You said heater-cathode short! You'd have 260 volts on the audio plate and no voltage on the if's at all!"

"Now you're gettin' better," approved the Old-Timer. "Wouldn't get much picture, would you? Nor much sound, on account of you'd lose the sound signal at the same time in the if's. So you might be lookin' for trouble there instead of in the sound tube where it actually was. If that audio tube gets too gassy or its coupling capacitor gets leaky, you got troubles too. That upsets the bias, also the current drain of the audio tube, and fouls up the plate voltages on the if stages."

"This gets more and more complicated as we go along," sighed the Young Ham.

"You ain't been anywhere yet," said the Old-Timer. "Another place where heater-cathode shorts'll really get you is in the series-heater TV sets (Fig. 2). Half your tubes will be lit, the other half dead. Whenever you see that condition, you can generally find a heater-cathode short somewhere. If you've only got three or four tubes burning, chances are they'll be burning real bright, on account of they're tryin' to use up all the current that should have supplied the whole string! Way to catch that is to look for the last tube in the string that's burning. Lot of people now are putting diagrams of the filament string inside the cabinets, bless their little hearts. Remember that Westinghouse we checked yesterday? Had a 3AL5 shorted out, and we looked on the diagram, traced it right down, and there it was. Sure appreciate the guy that put that there!"

"Yeah, that's helpful," agreed the Young Ham.

"And we can use all the help we can get!" said the Old-Timer fervently. "Here's another dandy. There's nothing these things would rather do than lead you up the garden path with a lot of false symptoms. You got a set with all the symptoms of agc trouble: weaving, buckling and, if you check the voltage at the agc test point, there ain't any. Ah ha! Agc trouble, you say. You

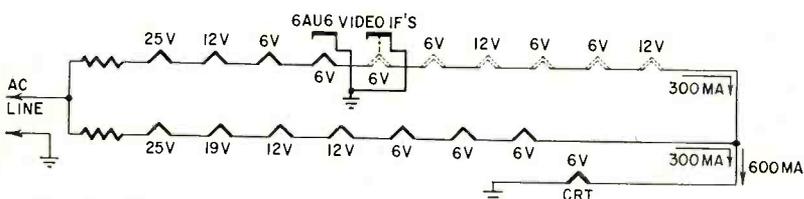


Fig. 2—Old-style series-heater circuit with two major branches. Each string carries 300 ma. If either 6AU6 in the upper string develops a heater-cathode short, the remainder of that string will go out.

change the age tubes; no help. Finally you come up with a grid-cathode short in the second if tube! It's lowering the signal and shorting out the age in the if stages, and there you are."

"That's what was the matter with that Philco last week, wasn't it? I remember what you called it!" laughed the Young Ham.

"All right, I'm ashamed of myself. Another case where you can get troubles, even after you replace the bad tube, is a tuner like the one we had last Tuesday. Remember? 6BZ7 shorted out, so we replaced it. Still had snow, so we had to take out the tuner and replace the two little resistors in the plate circuit that had burned to a crisp when the tube shorted. That's the one where the 'BZ7 plate was red-hot!

"Now you take color sets, you'll find all of the same symptoms in 'em, just like the black and white. Only thing, you've got a few more circuits in 'em. Now if you've got a good picture, but no color or the color won't hold, you start lookin' for some tube that handles the whole color signal—the burst amplifier, color killer, bandpass amplifier, and so on. Now if only one color was missin', say you didn't have any red in your picture, you'd start lookin' for a tube that handled only red signals—a dc restorer, or red amplifier, or somethin' like that. Simple, see?"

"Yeah, simple," agreed the Young Ham, dubiously. "I can imagine!"

"Now you can also get intermittents from tubes and lots of 'em! Take that set last week. Three other guys had worked on it without finding the trouble. I turned it on and the trouble showed up right away. I had to pull it out of the cabinet and check it with a scope, though, to be sure. It would play along perfectly and then blam! White-out! Scope showed no signal at the plate, but plenty at the grid. Nothin' between the two points except tube, so I replaced it. Took my high-power magnifyin' glass to the thing and, sure enough, you could see it then. The cathode ribbon was loose where it was welded to the tube pin! When she got hot, away she went, pulled loose. Like I say, I was just luckier than those other guys. It showed up for me."

"Aw, that wasn't luck, that was superior technical ability," said the Young Ham. "You're just smarter than they are. How about a raise?"

"I'll raise you, young squirt," said the Old-Timer. "Well, Ozz-wald," addressing the TV set which had been playing perfectly throughout all this discussion, "I reckon you're all right, so we can bundle you up and take you to your owner. Rain's stopped and it's about time to choose up sides an' go home." As he reached for the cheater cord, the picture gave a couple of wiggles, bowed in the center, and quietly faded out. The Old-Timer stared at it in amazement, while the Young Ham roared with laughter. Peering into the back of the set, the Old-Timer shrugged and reached for a 5U4. "Guess the dern thing musta been listenin'." He grinned. "Got a bad tube!"

END

the ultimate in
a dynamically-
balanced
tonearm
NEW

REK-O-KUT

*Micropoise*TM

STEREO TONEARM

with superb new features for higher playback quality and installation ease:


Model S-220
12" arm

\$29⁹⁵
net


PLUS THESE EXTRA FEATURES...

- Acoustically isolated counterweight.
- Exclusive precision low friction Sili-cone damped horizontal bearing — eliminates horizontal oscillation.
- Exclusive gimbal assembly incorporates individual double sets of 5 ball, 1 mm. bearings — provides freest lateral and vertical motion and assures perfect tracking.
- Plus many other exclusive Rek-O-Kut features.
Model S-260.....16" arm.....34.95 net
Extra Stereo Shell—
Model PS-20L.....5.95
Still available—
Model S-120. 12" arm. Now 24.95 Net
Model S-160. 16" arm. Now 27.95 net

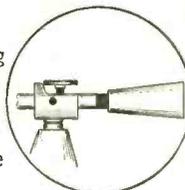
MICROPOISE DYNAMIC BALANCE CONTROL—By dialing the cushioned, spring-tension Microscope Balance Control, the arm is dynamically balanced and set for accurate stylus pressure:



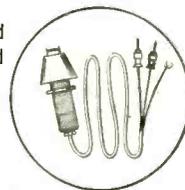PERMANENTLY ATTACHED PLUG-IN CABLE—fully shielded single-jacket cable is anchored to the arm—includes two color-coded plug-in leads, 2 shields and a ground wire. No soldering! No hum problem! Fast, correct installation assured!



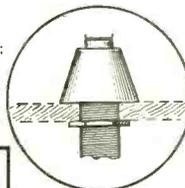FAST SINGLE-HOLE MOUNTING: Arm base mounts through single hole by tightening of single locknut.



Revolutionary automatic control accommodating the S-220 will soon be announced!



Rek-O-Kut Company, Inc., Dpt. RE 10
38-19 108th St., Corona 68, N. Y.

Please send me free brochure:

Name _____

Address _____

City _____ Zone _____ State _____

Export: Morhan Exporting Corp. 458 Broadway, N. Y. 13.
Canada: Atlas Radio, 50 Wingold Ave., Toronto 19.

INJEC-CHECK

INDUSTRIAL TEST UNIT

One-transistor instrument is a measuring device, continuity checker, signal injector and audio generator

By WM. F. KERNIN


HERE is a device, originally designed to handle a measurement problem in industrial electronics, that proved to have numerous practical uses in the radio and TV service business as well as on the home experimenter's workbench. To list some of its uses to date: a preset level or temperature indicator, a tube filament checker, a continuity checker, an af-if-rf signal injector. It is simple and efficient—completely self-contained, battery-powered and compact enough to fit into your tool box.

Originally, an instrument to indicate when the solution in a tank had reached a given level was needed. Visual indication was desired. Cords from the electric line were taboo, for safety reasons; economical, long-life battery operation was required. For a sensing element, two probes were to be used, so that when the solution touched both at the set level, the indicator light would go on. One difficulty—any voltage on the probes must be ac. Direct current would decompose the solution. And this ac must present no shock hazard.

The schematic diagram shows the circuit that fulfilled all those needs. A transistor blocking-oscillator power supply provides the high voltage for the NE-51 indicator light. It is patterned after the high-voltage GM counter supply presented by Thomas G. Knight, RADIO-ELECTRONICS, September, 1956. Bias resistor R is much lower than normal to "beef up" the output of the generator. Capacitor C determines primarily the frequency or pulse repetition rate. The radio-frequency choke—RFC—is included to improve the efficiency of the oscillator by blocking the oscillator energy from the dc power supply. Jacks J1 and J2 are the input terminals for the sensing probes. An UTC H-1 miniature transformer was used because of its rugged construction, improved terminals and better mounting system. However, the less expensive O-1 or O-2 may be used.

The output potential in this unit lights the NE-51 to full brilliance when the probes are shorted. However, there is no shock hazard even if one should grab the bare probes in both hands.

Power for the unit is supplied by

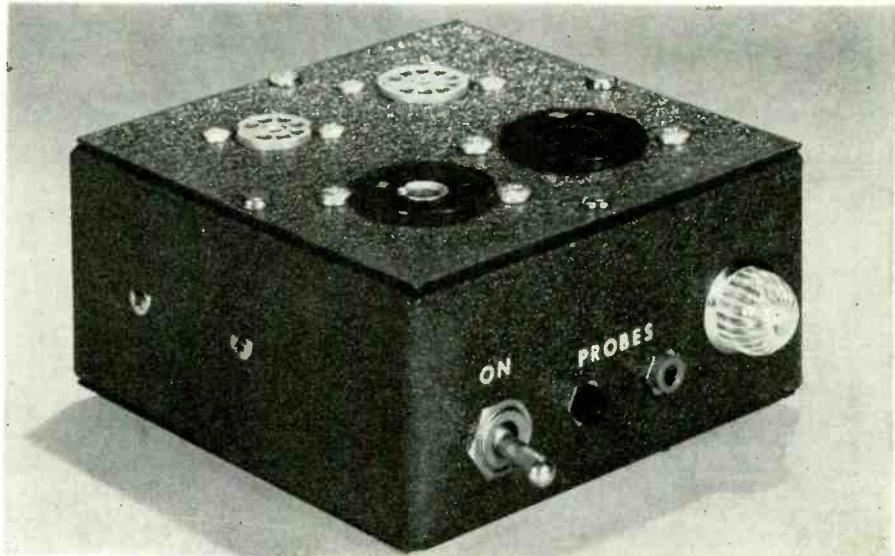

The Injec-Check has sockets for quick filament checking

two inexpensive penlight cells. Current drain averages 4 ma.

A level indicator

In operation, the probe tips are set at the desired height in the tank or vessel. Filling of the tank may begin as soon as the unit is turned on—no warmup time is needed. When the solution contacts the probes, NE-51 lights. When the level falls, the contact path between probes is broken—and the light goes out.

The unit may be used as a *minimum* level indicator. Here the light would stay lit until the solution fell below the preset level of the probes.

As a checkout feature for the unit, a momentary shorting switch may be connected between J1 and J2. To check the condition of the device when turned on, the switch is closed and, if all is well, the light should go on.

Proper operation depends upon a fair degree of conductivity of the solution. No attempt was made to use it with volatile or turbulent liquids.

Also a thermometer

As a set-temperature monitor, the unit is used with a mercury contact thermometer as the sensing element. This type of thermometer—particularly the delicate, precision ones—requires a low-potential low-current indicating

device to avoid contaminating the mercury. The NE-51 draws only 90 microamperes to glow at full brilliance in this unit. Hence it works well with the mercury contact thermometer.

And a continuity checker

Now for the bonus. By adding the tube sockets shown by the broken lines in the diagram, the original unit can be used as a go-no-go tube filament and continuity checker.


The NE-51 indicator light brilliance is not affected by normal filament resistance. Lowest current filament may be tested as surely as the highest.

The photographs show the layout used for a typical unit. A 4 x 4 x 2-inch utility box is the basic package. The choice of tube sockets shown covers most of the common tube types found in service work. To handle CRT and odd tubes as well as continuity checks, a pair of external test probes such as those used with the typical vom may be plugged into J1 and J2.

Operation as a filament continuity checker is simple. The unit is turned on; the tube is inserted in the proper socket. If the light lights, the filament is good. The same holds true using probes—continuity lights the light.

Or a signal injector

This device combines in one package

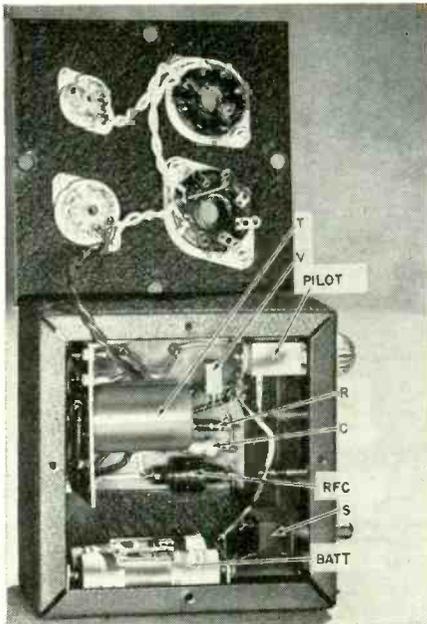


Inside view of Injec-Check

several features that are particularly handy in servicing the series-string ac-dc type of radio. Besides its use as a tube filament and continuity checker, it provides a signal source for injection into the radio under test. The waveform at jacks J1 and J2 is rich in harmonics, producing strong af, if and rf signals simultaneously. Thus, signal injection can begin right at the antenna and be applied to any and all stages. The output, or audio component, is

heard as a distinctive "growl" or buzz from the set's speaker, if all is well.

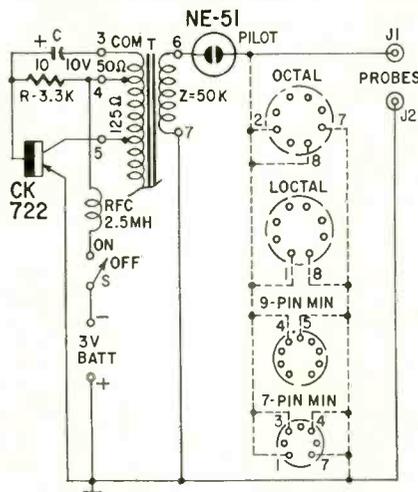The technique of signal substitution in servicing is fairly well known and need not be discussed here. To couple the signal into a set, one probe from the hot jack—J1—is all that is normally required. The ground return—J2—may be used for a stronger signal. END



The instrument is basically a transistor oscillator and neon-tube indicator

- R—3,300 ohms, 1/2 watt
- C—10 μ f, 10 volts
- T—transformer, UTC H-1, O-1, O-2 or equivalent
- V—CK722
- RFC—rf choke, 2.5 mh
- S—spst switch
- BATT—1.5-volt penlight cells (2)
- PILOT—NE-51, bayonet socket, clear jewel
- J1, J2—tip jacks (H. H. Smith 1505 or equivalent)
- Tube sockets (octal, loctal, 9-pin miniature, 7-pin miniature), battery holder, 4 x 4 x 2-inch box
- Miscellaneous hardware

Ask By Name For
GENUINE
your assurance
of brand name
quality

"NO NOISE"
PRODUCTS



**NO-NOISE
TUNER-TONIC**
with PERMA-FILM

- Cleans, lubricates, restores all tuners, including wafer type.
- Non-toxic, non-inflammable.
- For TV, radio and FM use.
- Economical—a little does a lot.



**NO-NOISE
VOLUME CONTROL
and CONTACT
RESTORER**

- Cleans • Lubricates
- Protects • Carbon Tet Solution

2 oz. Bottle \$1.00
6 oz. Spray Can \$2.25
Net to Servicemen



FREE At your
Jobbers
**5" PLASTIC
EXTENDER**

- Push Button Assembly
- For Pin-Point Applications
- Does Not Cause Shorts

ELECTRONIC CHEMICAL CORP.
813 Communipaw Avenue Jersey City 4, N. J.
P.S. Be Sure To Ask For
**NO-NOISE
RUBBER COAT** 6 oz. Spray Can \$3.25

TV-RADIO Servicemen or Beginners...

Send for *Coyne's*
7-Volume Job-Training Set
on 7-Day **FREE TRIAL!**



The First
Practical
TV-RADIO-
ELECTRONICS
Shop
Library!

Answers ALL Servicing Problems QUICKLY...
Makes You Worth More On The Job!

Put money-making, time-saving TV-RADIO-ELECTRONICS know-how at your fingertips—examine Coyne's all-new 7-Volume TV-RADIO-ELECTRONICS Reference Set for 7 days at our expense! Shows you the way to easier TV-Radio repair—time saving, practical working knowledge that helps you get the BIG money! How to install, service and align ALL radio and TV sets, even color-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick". No complicated math or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home. Over 3000 pages; 1200 diagrams; 10,000 facts!

SEND NO MONEY! Just mail coupon for 7-Volume TV-Radio Set on 7-Day FREE TRIAL! We'll include the FREE BOOK below. If you keep the set, pay only \$4 in 7 days and \$4 per month until \$27.25 plus postage is paid. Cash price only \$24.95. Or return set at our expense in 7 days and owe nothing. Either way, the FREE BOOK is yours to keep. Offer limited, so act NOW!

"LEARNED MORE FROM THEM THAN FROM 5 YEARS WORK!"

"Learned more from your first two volumes than from 5 years work."
—Guy Bliss, New York
"Swell set for either the serviceman or the beginner. Every service bench should have one."
—Melvin Masbruch, Iowa.

FREE DIAGRAM BOOK!
We'll send you this big book, "150 Radio-Television Picture Patterns and Diagrams Explained" ABSOLUTELY FREE just for examining Coyne's 7-Volume Shop Library on 7-Day FREE TRIAL! Shows how to cut servicing time by reading picture-patterns, plus schematic diagrams for many TV and radio sets. Yours FREE whether you keep the 7-Volume Set or not! Mail coupon TODAY!



Like Having An Electronics Expert Right At Your Side!

- VOL. 1—EVERYTHING ON TV-RADIO PRINCIPLES!** 330 pages of practical explanations; hundreds of illustrations.
- VOL. 2—EVERYTHING ON TV-RADIO-FM RECEIVERS!** 403 pages; fully illustrated.
- VOL. 3—EVERYTHING ON TV-RADIO CIRCUITS!** 335 pages; hundreds of illustrations, circuit diagrams.
- VOL. 4—EVERYTHING ON SERVICING INSTRUMENTS!** How they work, how to use them. 368 pages; illustrated.
- VOL. 5—EVERYTHING ON TV TROUBLESHOOTING!** Covers all types of sets. 437 pages; illustrations, diagrams.
- VOL. 6—TV CYCLOPEDIA!** Quick and concise answers to TV problems in alphabetical order, including UHF, Color TV and Transistors; 868 pages.
- VOL. 7—TRANSISTOR CIRCUIT HANDBOOK!** Practical Reference covering Transistor Applications; over 200 Circuit Diagrams; 410 pages.

ALL 7 BOOKS HAVE BRIGHT, MODERN, VINYL CLOTH WASHABLE COVERS

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
1455 W. Congress Parkway, Dept. AO-TI, Chicago 7, Illinois

Yes! Send me COYNE'S 7-Volume Applied Practical TV-RADIO-ELECTRONICS Set for 7-Days FREE TRIAL per your offer. Include "Patterns & Diagrams" book FREE!

Name Age

Address

City Zone State

Check here if you want Set sent C.O.D. Coyne pays shipping charges. 7-Day Money-Back Guarantee.

Coyne ELECTRICAL SCHOOL 1455 W. Congress Parkway Dept. AO-TI, Chicago 7, Illinois

SUPERIOR'S NEW MODEL TW-11 STANDARD PROFESSIONAL

TUBE TESTER



★ Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Subminars, Proximity fuse types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.

★ The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

EXTRAORDINARY FEATURE

SEPARATE SCALE FOR LOW-CURRENT TUBES: Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a handsome, portable Saddle-Stitched Texon Case. Only

\$47⁵⁰

Model TW-11—TUBE TESTER . . . Total Price \$47.50—Terms: \$11.50 after 10 day trial, then \$6.00 per month for 6 months if satisfactory. Otherwise return, no explanation necessary!



Superior's
New Model 80

20,000 OHMS PER VOLT ALLMETER

THE ONLY 20,000 OHMS PER VOLT V.O.M. SELLING FOR LESS THAN \$50 WHICH PROVIDES ALL THE FOLLOWING FEATURES:

- ✓ 6 INCH FULL-VIEW METER provides large easy-to-read calibrations. No squinting or guessing when you use Model 80.
- ✓ MIRRORED SCALE permits fine accurate measurements where fractional readings are important.
- ✓ CAPACITY RANGES permit you to accurately measure all condensers from .00025 MFD to 30 MFD in addition to the standard volt, current, resistance and decibel ranges.
- ✓ HANDSOME SADDLE-STITCHED CARRYING CASE included with Model 80 Allmeter at no extra charge enables you to use this fine instrument on outside calls as well as on the bench in your shop.

- A built-in Isolation Transformer automatically isolates the Model 80 from the power line when capacity service is in use.
- Selected, 1% zero temperature coefficient metalized resistors are used as multipliers to assure unchanging accurate readings on all ranges.

SPECIFICATIONS:

- 7 D.C. VOLTAGE RANGES: (At a sensitivity of 20,000 Ohms per Volt) 0 to 15/75/150/300/750/1500 Volts.
- 6 A.C. VOLTAGE RANGES: (At a sensitivity of 5,000 Ohms per Volt) 0 to 15/75/150/300/750/1500 Volts.
- 3 RESISTANCE RANGES: 0 to 2,000/200,000 Ohms. 0-20 Megohms.
- 2 CAPACITY RANGES: .00025 Mfd. to 3 Mfd. .05 Mfd. to 30 Mfd.
- 5 D.C. CURRENT RANGES: 0-75 Microamperes, 0 to 7.5/75/750 Milliampers, 0 to 15 Amperes.
- 3 DECIBEL RANGES: -6 db to +18 db +14 db to +38 db +34 db to +58 db

Model 80 Allmeter comes complete with operating instructions, test leads and portable carrying case. Only

\$42⁵⁰ NET

Model 80 — ALLMETER . . . Total Price \$42.50—Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months if satisfactory. Otherwise return, no explanation necessary!

NOTE: The line cord is used only for capacity measurements. Resistance ranges operate on self-contained batteries.



Model TV-50A—Genometer. Total price—\$47.50—Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months if satisfactory. Otherwise return, no explanation necessary!

GENOMETER

7 Signal Generators in One!

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:

A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV

R. F. SIGNAL GENERATOR: The Model TV-50A Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

VARIABLE AUDIO FREQUENCY GENERATOR: In addition to a fixed 400 cycle sine-wave audio, the Model TV-50A Genometer provides a variable 300 cycle to 20,000 cycle peak wave audio signal.

BAR GENERATOR: The Model TV-50A projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

THE MODEL TV-50A comes absolutely complete with shielded leads and operating instructions.

CROSS HATCH GENERATOR: The Model TV-50A Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines interlaced to provide a stable cross-hatch effect.


DOT PATTERN GENERATOR (FOR COLOR TV) Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

MARKER GENERATOR: The Model TV-50A includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc. (3579 Kc. is the color burst frequency).

\$47⁵⁰ NET

EXAMINE BEFORE YOU BUY!
USE APPROVAL FORM ON NEXT PAGE

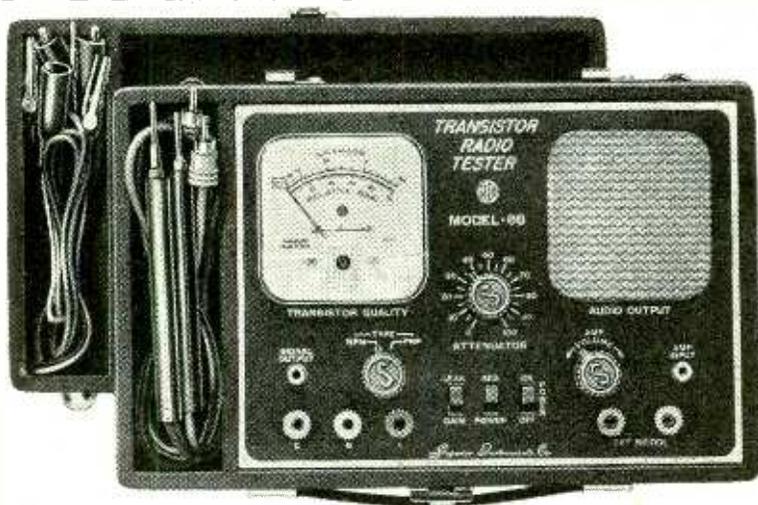The Model 88....A New Combination TRANSISTOR RADIO TESTER and DYNAMIC TRANSISTOR TESTER



The Model 88 is perhaps as important a development as was the invention of the transistor itself, for during the past 5 years, millions of transistor radios and other transistor operated devices have been imported and produced in this country with no adequate provision for servicing this ever increasing output.

The Model 88 was designed specifically to test all transistors, transistor radios, transistor recorders, and other transistor devices under dynamic conditions.

AS A TRANSISTOR RADIO TESTER

We feel sure all servicemen will agree that the instruments and methods previously employed for servicing conventional tube radios and TV have proven to be impractical and time consuming when used for transistor radio servicing. The Model 88 provides a new simplified rapid procedure — a technique developed specifically for transistor radios and other transistor devices.

An R.F. Signal source, modulated by an audio tone is injected into the transistor receiver from the antenna through the R.F. stage, past the mixer into the I.F. Amplifier and detector stages and on to the audio amplifier. This injected signal is then followed and traced through

the receiver by means of a built-in High Gain Transistorized Signal Tracer until the cause of trouble whether it be a transistor, some other component or even a break in the printed circuit is located and pinpointed. The injected signal is heard on the front panel speaker as it is followed through the various stages. Provision has also been made on the front panel for plugging in a V.O.M. for quantitative measurement of signal strength.

The Signal Tracing section may also be used less the signal injector for listening to the "quality" of the broadcast signal in the various stages.

AS A TRANSISTOR TESTER

The Model 88 will test all transistors including NPN and PNP, silicon, germanium and the new gallium arsenide types, without referring to characteristic data sheets. The time-saving advantage of this technique

is self-evident. A further benefit of this service is that it will enable you to test new transistors as they are released!

SPECIFICATIONS:

✓ Model 88 operates on a self-contained 4½ volt battery and is always ready for instant use on the bench or in the field.

✓ Signal Injector:

The signal injector used in the Model 88 is a new departure in signal source design. Previously, signal sources were provided by signal generators operating on a single frequency and requiring retuning. The Signal Injector of the Model 88 employs a transistor in a grounded emitter self-modulating blocking oscillator generating a low R.F. frequency providing stable harmonics to 30 megacycles. A power output of over 2.5 volts peak to peak is provided. An attenuator prevents overload of the receiver or the amplifier under test.

✓ Signal Tracer:

Two high-gain grounded emitter transistors are utilized in a high gain amplifier with sufficient output to operate the built-in 4½" Alnico V Speaker. A diode is used as a "clamp" to prevent overloading of the output stage. A volume control permits attenuation of strong signals. Provision is also made on the front panel for the addition of a meter or an oscilloscope for quantitative evaluation of the signal strength.

✓ Transistor Tester:

The transistor tester used in the Model 88 measures the two most important transistor characteristics needed for transistor servicing; leakage and gain (beta).

The leakage test measures the collector-emitter current with the base connection open circuited. A range from 50 ohms to 100,000 ohms covers all the leakage values usually found in both high and low power transistor types.

The gain test (beta) translates the change in collector current divided by the base current. Inasmuch as the base current is held to a fixed value of 50 microamperes, the collector current calibrated in relative gain (beta), is read directly on the meter scale.

The Model 88 will test all transistor types, including NPN or PNP, germanium, silicon, gallium arsenide and the newer diffused junction and mesa types.

Model 88 comes housed in a handsome portable case. Complete with a set of Clip-On Cables for Transistor Testing, an R.F. Diode Probe for R.F. and I.F. Tracing, an Audio Probe for Amplifier Tracing and a Signal Injector Cable. Complete—nothing else to buy!

\$38⁵⁰

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Try any of the instruments on this or the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. No Interest or Finance Charges Added! If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC, INC.

Dept. D-813, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligations.

Model 88.....Total Price \$38.50
\$8.50 within 10 days. Balance \$6.00
monthly for 5 months.

Model TW-11.....Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.

Model TV-50A.....Total Price \$47.50
\$11.50 within 10 days. Balance \$6.00
monthly for 6 months.

Model 80.....Total Price \$42.50
\$12.50 within 10 days. Balance \$6.00
monthly for 5 months.

Name.....

Address.....

City.....Zone.....State.....

All prices net, F.O.B., N. Y. C.

Export Division: Rocke International Corp., 13 East 40th St., New York 16, N.Y.

If you're among the thousands who think that an ordinary television antenna atop the roof is safe from lightning, you're wrong, says the Lightning Protection Institute.

Studies of some 1,500 lightning-fire and damage losses, reported in newspapers during a 3-month period, reveal that upward of 4% of them involve television sets and their antennas. That's no small matter—\$4,800,000 annually.

Those facts pointedly illustrate that an unprotected antenna *actually invites lightning to strike*. There are more than 40,000,000 television masts in this country, and it is inevitable that this forest of high-rising metal towers will help to increase the losses suffered from lightning strikes—unless the masts are protected.

Total annual lightning losses in the US are placed at 600 persons killed, more than 1,500 injured, along with \$120,000,000 in property losses. Lightning is the biggest single cause of fires in rural and outlying suburban areas, being responsible for 37% of all such fires.

Tying the TV antenna into the home's lightning-protection system is one means of helping to reduce losses. Where a building does not have a complete lightning protection system, grounding the TV mast properly will only partially protect it. To ground a TV antenna adequately, in addition to a 10-foot ground rod, tie-in should be made to the water system, electrical and telephone grounds and any metallic bodies within 6 feet of the down conductor. Ordinary TV installations in themselves are inadequately grounded, and the antenna is not a lightning-protection device.

Basic information

Lightning will most likely strike the highest object in an area. Because of its height above surrounding objects, the antenna becomes this most likely lightning target.

A TV antenna, even though grounded according to most set manufacturers' recommendations (and with a lightning arrester), does not offer sure lightning protection for the set. It is not connected with a heavy enough cable nor does it provide the proper paths to earth to function as an efficient lightning rod.

Most antennas, contrary to popular belief, do not have lightning arresters. And an arrester is not full protection in itself—the mast must also be tied in with the correct conductor cable to a ground rod sunk 10 feet deep in moist earth.

When lightning does hit an ungrounded antenna, its path is most likely to be down through the house. It may leap over to the wiring system or water pipes, or follow the antenna lead. At the least, you can expect damage to whatever mechanical equipment the bolt passes through (Many TV sets have ended in a ruined tangle of wires) and at the worst, injury or death to occupants.

TV ANTENNAS INVITE LIGHTNING TO STRIKE

Scores of lightning losses involving TV antennas lead the Lightning Protection Institute to endorse strongly this requirement in the Underwriters' Laboratories code:

"Radio and television masts of metal, regardless of location on building, shall be bonded with standard conductor and fittings to the main conductor of the lightning protective system. It is also recommended that a lightning arrester be installed on the lead-in wire, tape, or cable."

Where a television antenna is installed on a building provided with lightning protection (a lightning-rod system), the metal mast or supporting tower should be connected to the system. If the tower rises appreciably above the building, it should also have a down conductor connecting it directly to ground to conform to National Bureau of Standards requirements.

Alternate method

Where a building is not provided with a complete lightning protection system, and safety with economy is the watchword, the institute advises *full protection* of the TV antenna and set. This will partially protect the building

proper. This is recommended on the premise that some protection is better than no protection at all.


If the TV antenna is centrally located, grounding the mast can be tied in with complete lightning protection for the home by continuing the cable in both directions (and adding terminals at 20-foot intervals if the building is 40 feet or longer) from the TV mast along the roof ridge and down to ground on two sides of the building. This is not a job for the usual TV installation man. Considering the danger to life and property, the importance of trained engineering skill becomes even more vital. Don't hesitate to seek professional help or advice in all instances, whether for protecting a TV set and antenna or for a complete lightning-protection system. However, if the antenna is at either end of the building, the TV mast alone is comparatively simple.

The drawing illustrates how the lightning arrester is connected to the TV lead-in and then fastened to the mast with an approved pipe clamp (which generally comes with the arrester). Many good arresters are on the market; the important thing to

An increasing number of TV-related lightning fires occur each year. Most could be prevented if proper grounding techniques were used



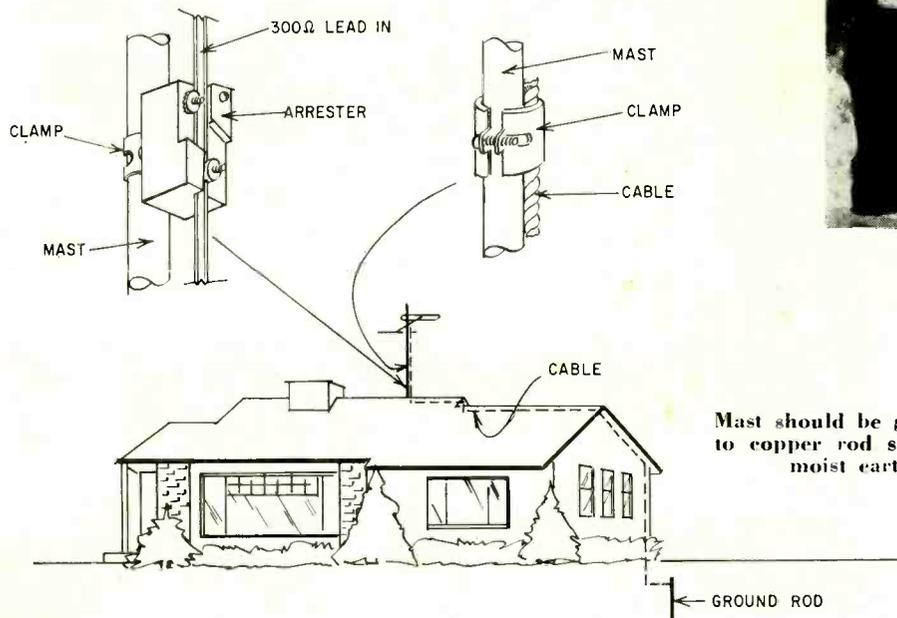Lightning traveled "down" a TV lead-in and made a new entrance for this kitchen.



Mast should be grounded to copper rod sunk into moist earth.

watch for is the Underwriters' Laboratories label.

The drawing also illustrates how the ground cable is connected to the TV mast, using a UL-approved cable clamp.

The ground cable is run from the connection at the mast, along the roof ridge (hidden by placement along ridge rolls), down the gable side (hidden under eave), then down the building side.

There are several rules governing cable installation. The cable shall have no bends sharper than 90°. The radii of all curves should be at least 8 inches. Lightning, with its sudden rise time, will not travel through a cable that has sharp bends if it can find a shorter path to ground (a jump across several feet to a water pipe is not uncommon). The cable is to be supported every 3 feet on open-air runs, and maintain a horizontal or downward course, free from down and up (V or U) pockets.

The cable is connected to an approved ground rod with a standard ground-rod clamp. The ground rod is driven 10 feet into permanently moist soil, at least 2 feet away from the house foundation.

Standard materials

Copper and aluminum are acceptable materials for lightning-protection systems, but should never be used together without special connectors. Aluminum parts must be larger than equivalent copper parts for equal conductivity.

The copper cable should weigh at least 187.5 pounds per 1,000 feet (individual wires making up the cable should be at least of No. 17 gauge). This cable is three times the size of a No. 6 cable which most manufacturers and installers recommend. Aluminum cable should weigh at least 95 pounds for the same length.

Ground rods, solid copper or copper-clad, should be at least ½ inch in diameter and 10 feet long.

Connectors and fasteners must be of the same material as the cable. Galvanized or plated-steel nails, screws or bolts are not acceptable on copper or aluminum installations.

Service available


The Lightning Protection Institute, a non-profit Chicago organization, offers its help whenever it is needed by any-

one—home owners, plant engineers, organizations or individuals. Sponsored by reputable, long-established lightning-equipment manufacturers, the institute was set up to promote the science and improve the methods of lightning protection (and to advise and give information).

Another of its purposes is to formulate and press for the practice of ethical standards in all phases of the lightning-protection industry. In this role, it works toward the goal of full inspection and official approval of all lightning-protection systems, new or old.

While the institute does not take any part in actual equipment testing or field inspections of installers and their work, the group works closely with Underwriters' Laboratories.

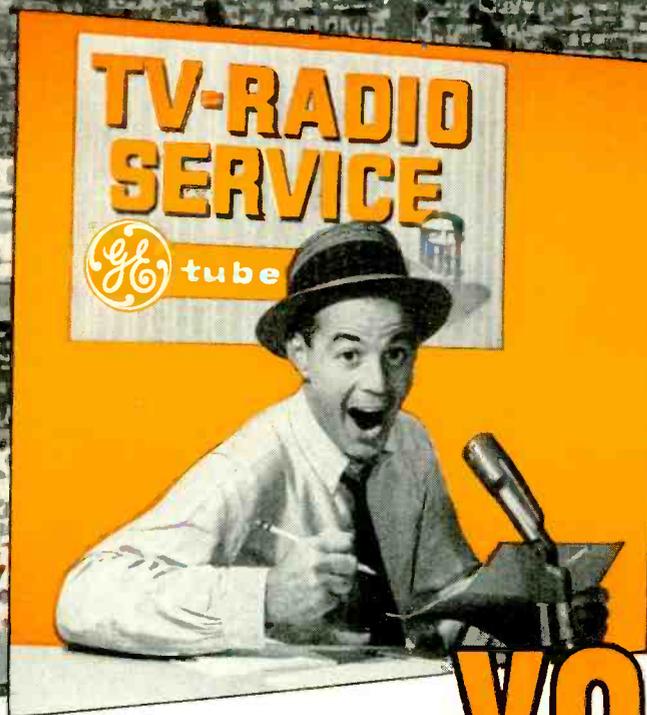If you plan to protect your TV antenna and set, entire home or plant against lightning and there is any question regarding materials or installation, the best way to get the answer is to write to the Lightning Protection Institute, 53 W. Jackson Blvd., Chicago 4, Illinois, for *Lightning Facts and Figures*. END




YOU WILL SCORE G-E WORLD SERIES

Spotlights you for quality TV service right when demand hits its peak! The year's top business, profit-builder for technicians!

All 55 million TV owners will want their sets to be in first-class condition when the umpire calls "Play ball!" The neighborhood technician whom owners know best will be the one to benefit. Don't miss this profit opportunity! General Electric is going all-out to help you—by telling World Series fans whom to call, where to go for fast, reliable TV check-up. *To the technician who installs G-E tubes! He's the best! And just around the corner!*

Long before the first day's pitchers have been named, G-E displays and promotions will be pulling customers into your shop. Once play starts, fans in most large cities will receive frequent radio reminders that you are ready to serve them fast and well. Go World Series with General Electric! Get ready for a B-I-G two weeks of business! See your G-E tube distributor! *Distributor Sales, Electronic Components Div., General Electric Company, Owensboro, Ky.*



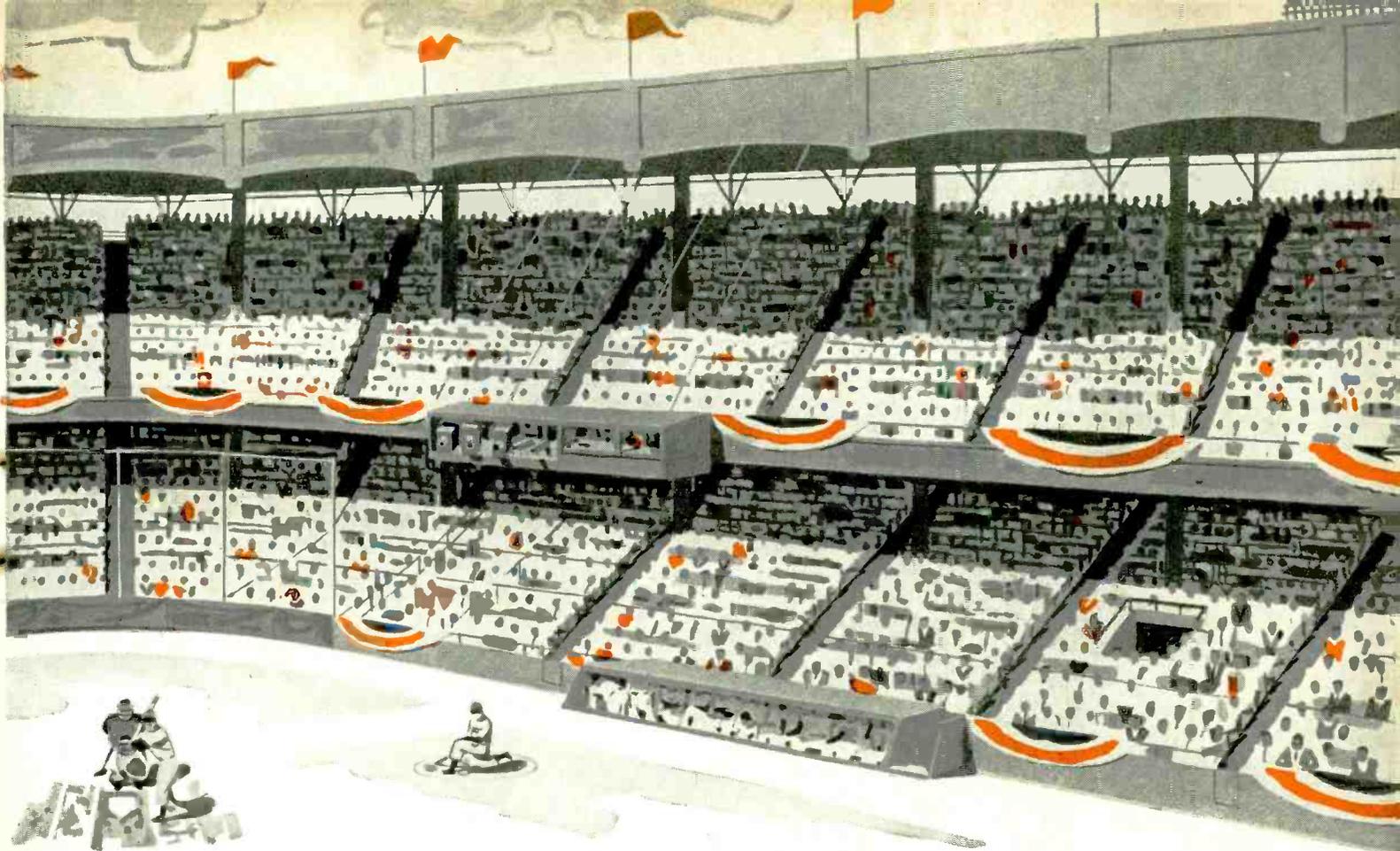

IN EVERY INNING WITH PROGRAM!

GO WORLD SERIES
to ring up
service dollars!

Timely, high-impact display items like these will draw more customers to your shop, pay off in stepped-up income. General Electric has ready for you many other World Series displays, advertising helps, and novelties, all new and exciting. See them today at your General Electric tube distributor's!

Don't miss
a play
in the

**WORLD
SERIES**

call us for our *SPECIAL WORLD SERIES TUNE-UP*
use **GE** tubes

*SPECIAL
WORLD SERIES
TUNE-UP*
with **GE**
tubes

Progress Is Our Most Important Product


GENERAL  ELECTRIC

311-403

Maximum ratings for these Texas Instruments transistors are:

	2N734	-735	-736
V _{CE}	60	60	60
V _{EB}	5	5	5
h _{fe} (V _{CE} =5, I _E =5 ma, f=1 kc)	50	100	200


The diagram shows a simple cascaded

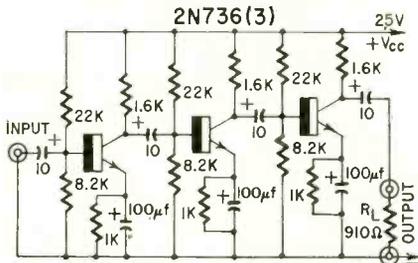

audio amplifier using the 2N736. It has a typical current gain of 92 db at 1 kc.

10-Pin Tubes

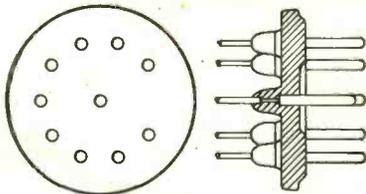
A new construction in miniature receiving tubes is the 10-pin envelope announced by Sylvania. The unit uses the regular 9-pin arrangement (like the 12AX7 or 12AU7) with an additional pin centered in the pin circle. The first tubes to use the new design are a double



tetrode for use as an rf amplifier, oscillator-mixer in FM tuners and receivers. Another unit will be a triple triode for use as an rf amplifier, oscillator-mixer and afc.

7262-A

A 1-inch camera tube (vidicon) intended for use in small, compact, transistorized television cameras. It can be used for televising black-and-white or color scenes in industrial and other closed-circuit TV applications. The high sensitivity of the tube makes possible high-quality pictures under normal room lighting conditions. The sensitivity of the 7262-A can be expressed as equivalent to a photographic film with an ASA exposure index of 600.

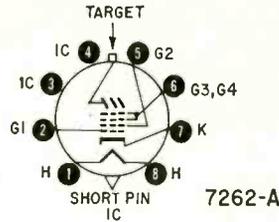

Characteristics under typical operating conditions for this RCA tube are:

V _{G4} (decelerator) & V _{G3} (beam-focus)	300
V _{G2} (accelerator)	300
V _{G1} (for picture cutoff)	-45 to -100
Visual equiv signal-to-noise ratio	300:1
V _{blanking} (min peak-to-peak) (when applied to G1)	75
(when applied to cathode)	20
	END

how often could you have used...

an Xcelite "Seizer"?

Handy as an extra hand or helper. Clamps lightly or tightly ... for moments or minutes.

two-position snap-lock

slim, serrated jaws

Outreaches, out-holds needle-nose pliers. Hardly a spot too small for it. Approx. 6" long. Dozens of uses: Holds and positions wires for soldering, retrieves small parts from inaccessible places, it's a heat sink. Two-position snap-lock won't slip, yet releases with a twist of the fingers. All stainless steel — precision machined and tempered for smooth action and years of service.

2 Models: No. 43H curved nose and No. 42H straight — Ask your distributor to show you Xcelite Seizers today.

MOVING?

If you're moving please don't forget to send us your old address as it appears on your latest copy of the magazine. Include the numbers shown beside your name. If possible, send us the actual address label which is pasted on the lower right hand corner of the front cover. Be sure to include your postal zone number (if any) with your new address. If we receive this information before the 20th of the month, you will continue to get RADIO-ELECTRONICS without interruption.

Please send data to
Subscriber Service

Radio-Electronics
154 West 14th Street • New York 11, N. Y.

Special Offer 25¢

Hear these authentic recordings of dramatic events from

"The Amazing World of Short Wave Listening"
narrated by Alex Dreier, Radio-TV "Man on the Go"

- President's voice from outer space!
- Actual capture of a desperate criminal!
- Radio amateur at Little America!
- Ships at sea . . . aircraft in action!

S-38E
receiver
\$59.95

3 short wave bands plus standard broadcast. Built-in speaker, headset output.

MAIL COUPON TODAY!

hallicrafters
DEPT. 23, CHICAGO 11, ILL.

Gentlemen: Please rush by return mail my recording, "The Amazing World of Short Wave Listening." I enclose 25¢.


NAME _____

ADDRESS _____

CITY _____ STATE _____

XCELITE

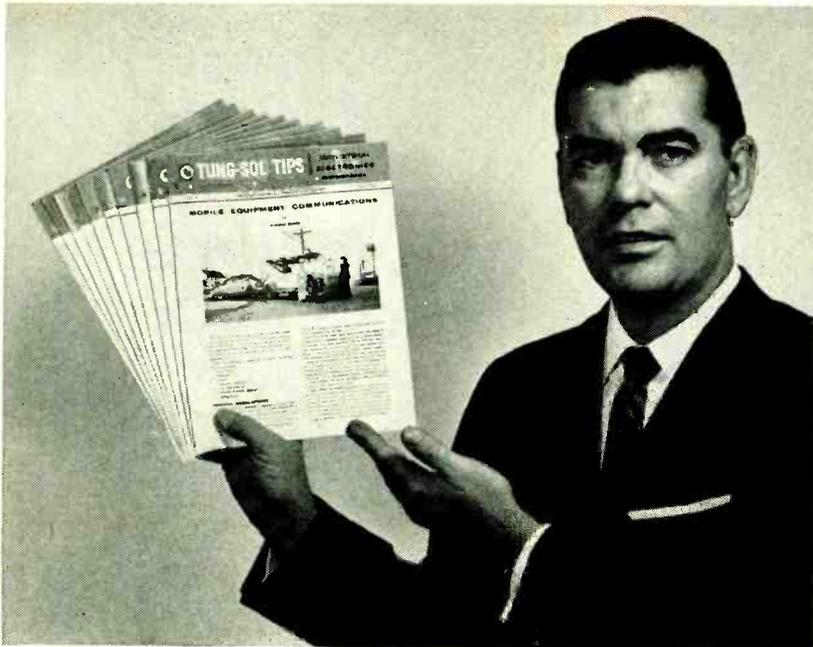XCELITE, INC. • ORCHARD PARK, N. Y.
Canada: Charles W. Pointon, Ltd., Toronto, Ont.



Is Your Library of Tung-Sol Tips Up To Date?

So far there have been ten issues in Tung-Sol's free monthly series of Tung-Sol Tips. Each one contains important technical information for servicemen who want to get more of the lucrative industrial electronics service business. If your library is not complete here is your opportunity to bring it up to date. Or perhaps you have not yet subscribed to Tung-Sol Tips. If that's the case this is the time to get your name on the mailing list. The service is free, the only cost is the 4¢ stamp you'll use to send us your name. New subscribers will get all back issues.

Tung-Sol Tips is edited to give servicemen a broad understanding of electronic components and their

use in industrial equipment. Everything from theory of operation to application, installation and maintenance is covered. Tips is another of the many services which Tung-Sol offers to help servicemen expand their businesses.

So if you are not yet on the mailing list or if you have missed out on any of the first issues get in touch with your Tung-Sol distributor or write directly to Tung-Sol Electric Inc., Newark 4, N. J.

Sales Offices: Atlanta, Ga.; Columbus, Ohio; Culver City, Calif.; Dallas, Texas; Denver, Colo.; Detroit, Mich.; Irvington, N. J.; Melrose Park, Ill.; Newark, N. J.; Philadelphia, Pa.; Seattle, Wash. Canada: Toronto, Ontario.

These 10 Important Subjects Should Be In Your Tung-Sol Tips Library


1. Semiconductor Rectifiers
2. Gas-Filled Rectifiers
3. Theory of Thyatron Operation
4. Practical Applications of Thyatrons
5. Photo-electric Theory and Operations
6. AC Amplifiers
7. Practical Applications of AC Amplifiers
8. DC Amplifiers and Choppers
9. Mobile Equipment Communications
10. 11-Meter Band Citizen's Communications

Back copies are available, write for those you want.


Soon to be on its way to subscribers, No. 11 is devoted to DC Power Supplies.

 **TUNG-SOL®**

new PRODUCTS

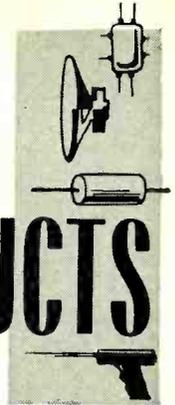


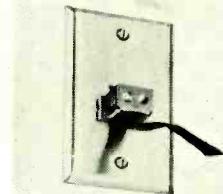WALL OUTLETS for TV antenna systems. Flush-mount (shown) and surface-mount styles. Come with plugs




with no-strip terminals. 300 ohms. Flush-mount type in brass, ivory, chrome. Surface-mount type in ivory.—Winegard Co., Burlington, Iowa.

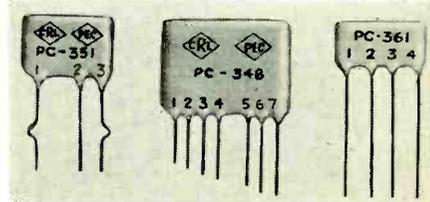PACKAGED CIRCUITS (27) for TV and hi-fi use have been added to PEC line. Included: balanced dual capacitor,



loudness contour networks, phase detector, diode-triode *Couplate*.—Centralab, 900 E. Keefe Ave., Milwaukee 1, Wis.

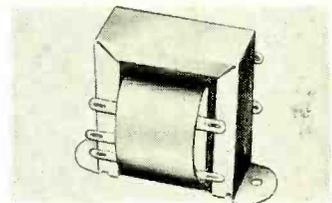REPLACEMENT PARTS for TV. Deflection yokes *DY-35A*, *DY-36A* replace Philco 76-9173-13/14 and Emerson 708353, respectively. Horizontal output



transformers *HO-312*, *HO-313*, *HO-314* replace Emerson 738160, 738162, 738169, respectively. Filter choke *C-2343* (0.75 henry at 300 ma). 70.7-volt output transformers (shown); A-8080 (1—5 watts), A-8081 (6—10 watts), A-8082 (11—15 watts). All have five power ranges in 1-watt steps. 8- and 16-ohm secondaries.—Chicago Standard Transformer Corp., 3501 Addison, Chicago 18, Ill.

TRANSCEIVER model *GW-30* for low-power unlicensed or licensed Citizens band use or 10-meter ham band. Fixed-tuned superregenerative receiver, crystal-controlled transmitter. Volume



REACH

UP TO FOUR TIMES THE WORKING DISTANCE OF CARDIOID TYPES* with the Electro-Voice model 644 sound spot

Of all the audio problems confronting sound engineers, one of the most difficult to overcome is the use of microphones in spacious areas. Churches, auditoriums and amphitheatres present formidable problems in room acoustics and reverberation which degrade audio quality. Consequently, microphones cannot be placed at conventional distances from the source of sound. Under such conditions, loss of level and "presence" further add to the enigma of proper pick-up. The Model 644 Sound Spot is the answer. Here is a microphone providing acceptance within an included angle of 90° at high frequencies, high axial sensitivity, wide frequency response extending from 40 to 12,000 cps and excellent wind noise cancelling characteristics. Its highly directional feature permits unusual microphone working distances as well as startling flexibility in loudspeaker placement. Effective cancellation of sound at the rear and sides for unparalleled rejection of random noise, reverberation and feedback without frequency response loss. See Polar Pattern, Stop at your Electro-Voice distributor today and let him demonstrate the Model 644.

*Depending on Acoustical conditions.

Other features: Output level—53 db. 150 ohm and high impedance. Impedance changed by moving one connection to connector. Low impedance only: line balanced to ground and phased. Acoustalloy diaphragm, shielded from dust and magnetic particles. Non-welded circuit with Alnico V and Armco magnetic iron. Pressure cast case. 5/16"-27 thread. Satin chrome finish. 18 ft. cable with MC4M connector. ON-OFF switch. Size: 2 3/16" diam. 16" length. Net Wt.: 2 lb. 9 oz. less cable. List Price \$110.00. Desk stand available (extra).

Polar
Pattern



Electro-Voice®

Commercial Products Division
ELECTRO-VOICE, INC.
Dept. 90T Buchanan, Michigan

RCA KITS

FOR VALUE, QUALITY AND PERFORMANCE!



RCA WV-38A (K) VOLT-OHM-MILLIAMETER

only **\$29.95*** (includes batteries, probe and cable with slip-on alligator clip, ground lead and clip, assembly and operating instructions) (available factory-wired and calibrated—only \$43.95*)

Exclusive features make this RCA VOM kit the buy of a lifetime! Extra 1-volt and 0.25 volt (250 mv) ranges for wider usage in transistor servicing—new handle clip accommodates probes and test leads for extra carrying convenience. Assembles in a breeze!

FEATURING: ohms-divider network fuse-protected • easier-to-read scales • extra-large 5/4 inch meter • polarity reversal switch • excellent frequency response • full-wave bridge rectifier • low circuit loading • standard dbm ranges.

SPECIFICATIONS: Input Resistance—20,000 ohms per volt on DC; 5,000 ohms per volt on AC • Accuracy—± 3% DC, ± 5% AC (full scale) • Regular Scales—2.5, 10, 50, 250, 1000, 5000 volts, AC and DC; 50 μ a 1, 10, 100, 500 ma, 10 amps (DC) • Extra Scales—250 mv. and 1 volt (dc) • Frequency Response—AC-flat from 10 cycles to 50 Kc (usable response at 500 Kc) • Ohms—3 ranges: Rx1—(0-2,000 ohms); Rx100 (0-200,000 ohms); Rx10,000 (0-20,000,000 ohms) • Dimensions—W. 5 1/4", H. 6 7/8", D. 3 1/8"

RCA WO-33A (K) 3-INCH OSCILLOSCOPE

only **\$79.95*** (complete with Low-Cap, Direct Input Probe and Cable) (also available factory-wired and calibrated—only \$129.95*)

The first 'scope kit with "get-up-and-go!" Use it for practically everything—video servicing, audio and ultrasonic equipment, low level audio servicing of pickups, mikes, pre-amps, radios and amplifiers, troubleshooting ham radio, hi-fi equipment, etc.—and you can take it with you, on the job, anywhere!

FEATURING: voltage-calibrated frequency-compensated, 3 to 1 step attenuator • scaled graph screen and calibrating voltage source for direct reading of peak-to-peak voltages • "plus-minus" internal sync... holds sync up to 4.5 Mc • shielded input cable with low capacitance probe included • weighs only 14 pounds • includes built in bracket to hold power cord and cables.

SPECIFICATIONS: Vertical Amplifier (Narrow Band Position)—Sensitivity, 3 rms mv/inch; Bandwidth, within -3 db, 20 cps to 150 Kc • Vertical Amplifier (Wide Band Position)—Sensitivity, 100 rms mv/inch; Bandwidth, within -3db, 5.5 cps to 5.5 Mc • Vertical Input Impedance—At Low-Cap cable input... 10 megohms, 10 μ f (approx.); At Direct-cable input... 1 megohm, 90 μ f (approx.) • Sweep Circuit—Sawtooth Range, 15 cps to 75 Kc; Sync, external, \pm internal; Line Sweep, 160° adjustable phase.



RCA WV-77E (K) VOLT OHMYST®

only **\$29.95*** (also available factory-wired and calibrated only \$43.95*)

Think of it—an RCA VoltOhmyst Kit at this low, low price! You get famous RCA accuracy and dependability, plus the easiest to assemble kit you've ever seen!


FEATURING: ohms-divider network protected by fuse • ultra-slim probes and flexible leads • sleeve attachment on handle stores probes, leads, power cord • separate 1 1/2 volts rms and 4 volts peak-to-peak scales for accuracy on low ac measurements • front-panel lettering acid-etched.

SPECIFICATIONS: Measures: DC Volts—0.02 volt to 1500 volts in 7 overlapping ranges; AC Volts (RMS)—0.1 volt to 1500 volts in 7 overlapping ranges; AC Volts (peak-to-peak)—0.2 volt to 4000 volts in 7 overlapping ranges; Resistance—from 0.2 ohm to 1000 megohms in 7 overlapping ranges. Zero-center indication for discriminator alignment • Accuracy—± 3% of full scale on dc ranges; ± 5% of full scale on ac ranges • Frequency Response—flat within ± 5%, from 40 cycles to 5 Mc on the 1.5, 5, and 15-volt rms ranges and the 4, 14, and 40-volt peak-to-peak ranges • DC Input Resistance—standard 11 megohms (1 megohm resistor in probe).

*User Price (Optional)



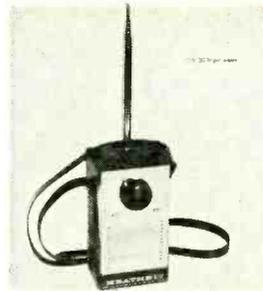See them all at your local RCA Test Equipment Distributor!
RADIO CORPORATION OF AMERICA
ELECTRON TUBE DIVISION
HARRISON, N. J.



control, push-to-talk button, telescoping antenna. Kit or wired, carrying case and shoulder strap.—Heath Co., Benton Harbor, Mich.

TRANSCEIVER for 27-mc Citizens band. 22-channel transmitter and receiver. Pretuned sealed oscillator. Up to



5 watts input. 5 tubes. Supplied with tubes, crystal, antenna, microphone.—Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass.

ALL-CHANNEL TUNER for crystal-controlled Citizens-band receivers. Plugs into receiver in place of crystal.



No batteries or power source needed. 2-inch vernier dial. 2 x 4 x 4 inches—Crown Electric Products Co., PO Box 171, Orange, N. J.

AUDIO-GENERATOR, model 605. Sine-, square-wave output. 20 to 200,000 cycles. Pushbutton range selection. Schmitt trigger circuit supplies square wave. Output voltage: sine wave 0 to 5



(rms), square wave 20 mv to 7 (peak to peak). Less than 1% distortion on sine wave. Square-wave rise time 0.2 μ sec.—Jackson Electrical Instrument Co., 124 McDonough St., Dayton, Ohio.

AC VTVM model 715, 10 ranges up to

NEW PRODUCTS (Continued)

300 volts full scale. Low range 10 mv full scale. Accuracy 5% of full scale.



Response 10 to 400,000 cycles ± 1 db. Db markings on scale, range switch.—Simpson Electric Co., 5200 W. Kinzie St., Chicago 44, Ill.

CAPACITOR ANALYZER, *Transcap model TCA-1*, for low-voltage low-leakage tantalum and aluminum electrolytic capacitors as well as other low-voltage units. 5 ranges cover 1 μf to 2,000 μf .




Meter reads insulation resistance from 50 to 20,000 megohms and leakage current down to fractional microamps. Power factors measured by Wien bridge from 0 to 50%—Sprague Products Co., 335 Marshall St., North Adams, Mass.

REACTANCE RULE solves resonant - frequency, inductive - reactance, capacitive-reactance, coil-Q and dissipa-




tion-factor problems. Frequency range 5 cycles to 10,000 mc. Re-issued.—Shure Brothers, Inc., 222 Hartrey Ave., Evanston, Ill.

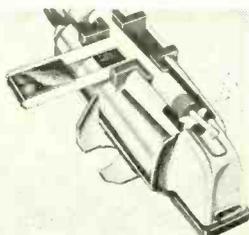STEREO CARTRIDGE model 9T. Turnover ceramic type. Smooth distortion-free response. Response 20 to 17,000 cycles ± 1 db. Compliance 3.5 x



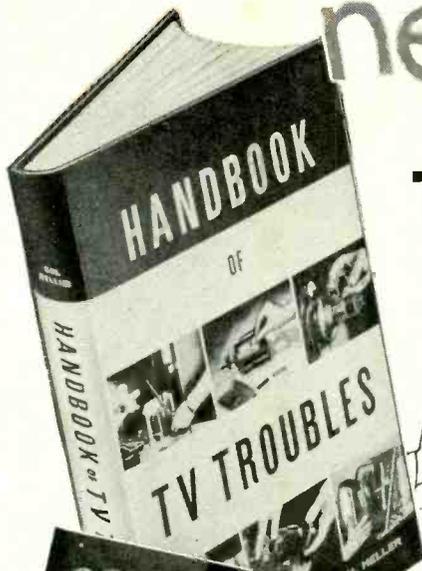10⁻⁶ cm/dyne. Low tracking force (2 grams for pickup arms, 3 grams for changers) reduces stylus wear, in-
(Continued on page 106)




This "automatic teacher" TAKES THE GUESSWORK OUT OF TV TROUBLE-SPOTTING AND REPAIR!

Covers all causes of practically every trouble you are likely to be called on to fix including:

- BRIGHTNESS TROUBLES—CONTRAST TROUBLES—PICTURE DISTORTION—UNSATISFACTORY PICTURE DETAIL—LINE OR BARS IN PICTURE—SYNCHRONIZATION TROUBLES—MISSING PICTURE—SIZE AND CENTERING TROUBLES—SOUND TROUBLES—TELEVISION INTERFERENCE, ETC.

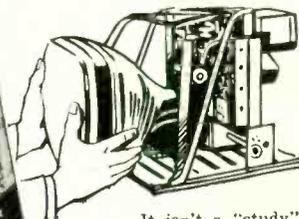new MASTER GUIDE TO TIME-SAVING TV SERVICE



A modern manual for fast, "symptomatic trouble analysis" and servicing of TV receivers.

It isn't a "study" book! From beginning to end, this big new manual is designed for daily use *right at the bench* as an outstandingly complete, easily understood guide to practically any job on any TV receiver.

Just turn to the Index. Look up the trouble symptoms exhibited by the TV you're working on. The **HANDBOOK OF TV TROUBLES** then tells you exactly what and where to check. Outlines time-saving short cuts. Explains puzzling details. Eliminates guesswork and useless testing. More than 150 test pattern, wave form and circuit illustrations explain test results and procedures so clearly you can hardly fail to understand.

LOOK! LISTEN! Then Follow This Easy Guide!

Almost regardless of set make or model, this remarkable new 302-page Handbook helps you track down TV troubles from the symptoms they produce in the set itself—screen intermittently dark; "blooming"; abnormal contrast in spots; "snow"; poor detail; sync troubles; sound troubles—and all the many other symptoms that indicate something is wrong. Then it explains how to make needed adjustments or parts replacements.

HANDBOOK OF TV TROUBLES is printed in large type and has sturdy, varnished covers for "on the job" use. Its **QUICK GUIDE TV TROUBLE INDEX** helps you find what you want in a jiffy. Throughout, the Handbook is a real time-saving money-maker for beginners and experienced service men alike! Try it for 10 days **AT OUR RISK**. Price \$7.50.

TRY IT 10 DAYS—See for Yourself!

Dept. RE-100, HOLT, RINEHART AND WINSTON, INC., Technical Div., 383 Madison Ave., New York 17, N.Y.

Send new 302-page **HANDBOOK OF TV TROUBLES** for 10-day FREE trial. If I decide to keep book, I will then send you \$7.50 in full payment. If not, I will return book postpaid and owe you nothing.

SAVE: Send \$7.50 with order and we pay the postage. Same 10-day return privilege with money promptly refunded.

Name.....

Address.....

City, Zone, State.....

OUTSIDE U.S.A.—Price \$8.00 cash only. 10-day return privilege with money refunded.

SERVICEMEN KNOW!

Here they pay less and get the best

HUSH®

Chemically-Electronically, engineered for Tuners and Switching Mechanisms.

When New HUSH is applied it will wash-away that dirt, leaving clean and positive contacts protected by a lasting lubricant. New HUSH is made from the finest solvents and it contains Electro-Silicone oils.

Also available—2 oz., 8 oz., 32 oz. containers 6 oz. Spray can \$2.25 net

EVER-QUIET®

Since 1949

VOLUME CONTROL AND CONTACT RESTORER


EVER-QUIET is a free-flowing liquid that leaves no powder residue. Scientifically designed to seep around the shaft and penetrate the control or potentiometer, cleaning the contacts and leaving a safe protecting film. Harmless to metals, wire or carbon.

Also available—32 oz. containers 6 oz. Spray can \$1.59 net

2 oz. Bottle & dispenser 79c net



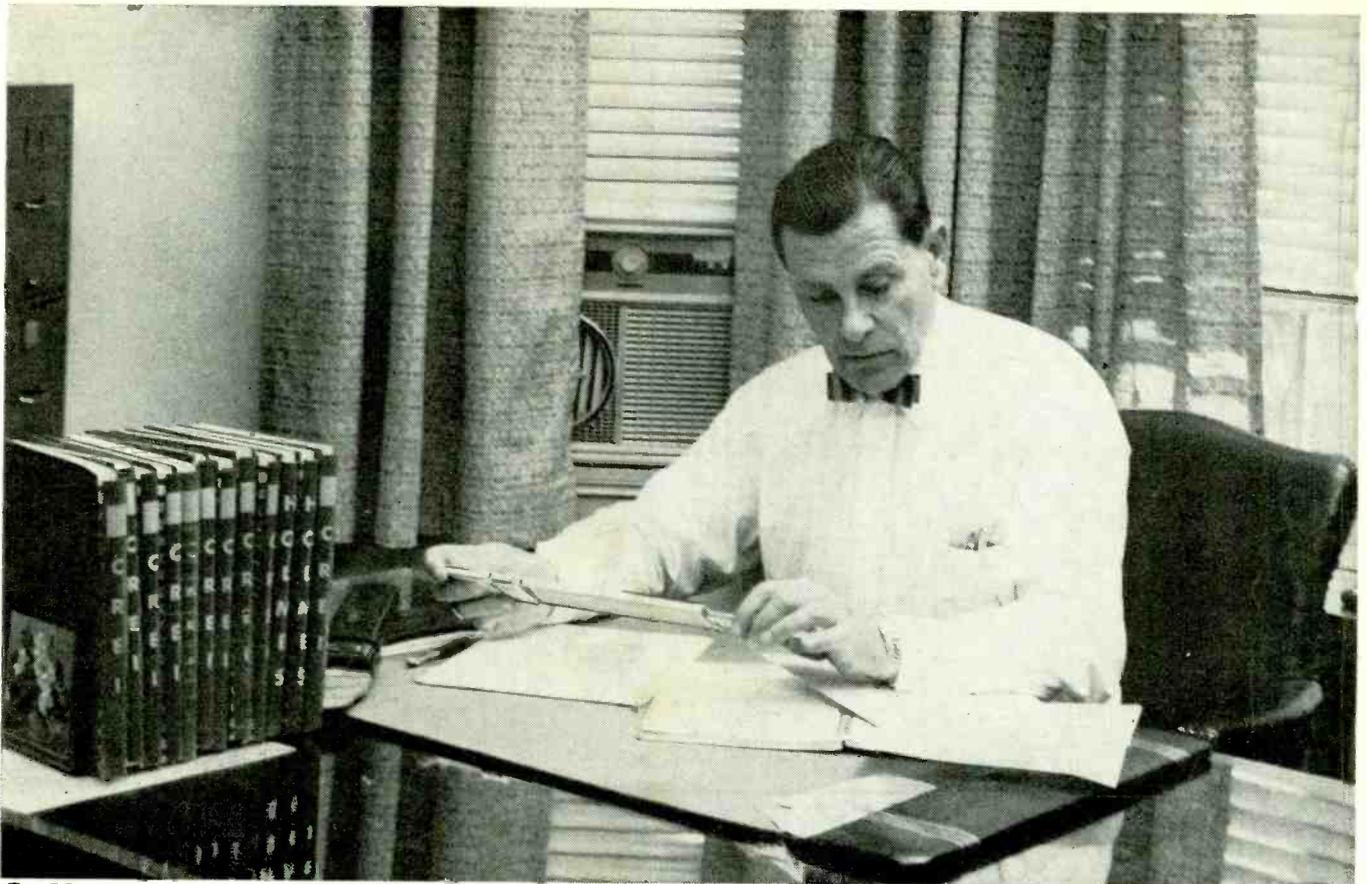CHEMICAL ELECTRONIC ENGINEERING, INC. Matawan, New Jersey



A Home Study Program for Engineering Technicians and Professional Engineers Comparable in Technological Content to College-Level Electronics Residence Courses.

CREI's Extension Division offers combinations of courses in advanced electronics engineering technology to meet present or future employment requirements, and step up your earning power.

A CREI program, the product of 33 years experience, is neither short-cut nor magic formula. It is an accredited home study curriculum which may take as little as 18 months, or as much as 3 years, depending upon the course selected and amount of stick-to-itiveness brought to bear. The program is designed specifically for men employed in a technical capacity in the electronics industry, where a shortage of manpower with advanced technical education not only exists, but shows every likelihood of increasing.

Now fifth in volume among American industries, the elec-

tronics industry offers almost unlimited employment and advancement opportunities. Applications of new electronic developments in automation, instrumentation, industrial electronics, aeronautical electronics, guided missiles, servomechanisms, computers, astronautics and telemetering create new jobs every day. Yet, paradoxically, industry growth does not always mean individual growth. Companies actively seeking men with modern, advanced technological knowledge are simultaneously firing mediocre men who lack this knowledge.

CREI students (more than

20,400 are currently enrolled) keep pace with the needs of the ever-advancing electronics industry and are eagerly sought by employers who offer solid opportunities for rapid promotion.

Since 1927 we have directed the technical education of students in advanced electronics engineering technology. We developed the prototype civilian electronics course for the Army Signal Corps in 1941, supplied 300,000 texts to the U. S. Navy in a special course for radio technicians in the South Pacific in 1943, trained hundreds of technicians during World War II for the Signal Corps. We co-founded

the National Council of Technical Schools, which first established scholastic and business standards for the technical school field. We were among the first three technical institutes whose curricula were accredited by the Engineers' Council for Professional Development. In 1946 we instituted the group training programs used by companies representing the cream of the electronics and aviation industries. CREI courses are widely employed today in company-sponsored educational plans by companies throughout the U. S. and Canada.

What does this record of achievement mean to you as a CREI student? It means that industry and the Armed Services alike respect CREI men. It means that your CREI diploma is a door-opener. Significantly, Help Wanted ads often specify "CREI education or equivalent required." Our Placement Bureau, which helps graduates and advanced students find more desirable positions, is always available to CREI men. While no placement guarantees will be made by CREI or any other reputable institution, for many years the demand for CREI graduates and advanced students has far exceeded the supply.



CREI HOME STUDY ADVANTAGES.

This advanced technical education is accomplished on your own time, during hours chosen by you. You waste no time in travel. You have plenty of time to do your best. Your work is under the supervision of a regular staff instructor who guides your progress step by step. Courses are prepared and taught by men experienced both in teaching and in electronics, presented in easy-to-understand form, kept up to date by periodic revision. Experience in more than three decades of home-study teaching, during which time we have corrected and commented on many hundreds of thousands of examinations, en-


ables us to anticipate questions in our lesson material.

CREI STUDENTS are professional electronics engineers and technicians, all over the world and in every phase of electronics, about one-third military, the rest civilian. Their median age is 28. In 1958 they devoted approximately 1,572,400 hours to 104,831



lesson texts, answered and were individually graded upon 1,048,310 searching questions and engineering problems. They studied advanced electronics engineering technology associated with transistors, microwaves, forward scatter, computers, servomechanisms, radar, electronic navigational devices and the entire field of modern electronics. New students enrolled during the year are on the missile ranges of

Vandenburg AF Base and Cape Canaveral. They are at Alamogordo and China Lake, at SAC bases around the world. They are in the research laboratories and manufacturing plants where the latest electronic equipment is designed and produced. They maintain electronic equipment for United Air Lines, and Trans-Canada Air Lines. They share in electronics at All America Cables and Radio, Inc., and The Martin Co. They work for USIA (Voice of America) and Columbia Broadcasting System, for Gates Radio and Federal Electric, to name but a few. All of the firms mentioned offer their personnel CREI education under company sponsorship. CREI men are found by the hundreds among field engineers of major electronic manufacturers. They're across the world and across the street. They're men you'll compete with—to gain or hold your place in the electronics profession.

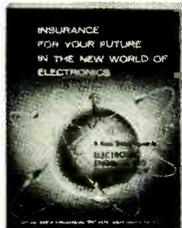

If ambition is part of your make-up—if you

want to convert interest and energy into dollars of income—if you want to convert your spare evening hours into material benefit and the personal satisfaction that comes with advancement and respect of your associates—then CREI's home study education assures you of:

1. A solid foundation of college-level, advanced technical electronic engineering knowledge.

2. A means of keeping abreast of the complex developments in electronics.

3. The ability to communicate intelligently with your engineering associates and superiors.

4. The best preparation for professional advancement in electronics as the industry demands more qualified personnel.

QUALIFICATIONS FOR CREI. College degree is not essential. If you have had basic electronic education, practical experience in electronics and a high school education, you can probably qualify. A good way to find out: Use the postage-paid card. It will bring you the free 54-page book which has launched thousands on their advanced careers: "Insurance for Your Future in the New World of Electronics." Tuition is reasonable and may be paid monthly. It takes just one \$10-a-week raise to repay your investment in CREI education and leave you a substantial bonus the first year. Available to veterans under GI bill.



RESIDENCE SCHOOL in Washington, D. C. for those who can attend classes. Day and evening classes start at regular intervals. Qualified graduates earn AAS degree in approximately 27 months. Electronics experience not required for admission.

CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula. Founded 1927

Dept. 1410-G
3224 16TH ST., N.W.
WASHINGTON 10, D. C.

EE

If you are a career-minded engineer or technician . . .

RE-DIRECT your future aims to high standing in NUCLEAR ENGINEERING technology


Learn Nuclear Engineering Technology through an advanced home study program offered by CREI Atomics. Enrollment is limited.

ONLY A LIMITED NUMBER OF MEN will be accepted at this time for this program of home study offered by CREI ATOMICS, an expertly-staffed extension division of The Capitol Radio Engineering Institute.

U.S. Atomic Energy Commission states about the severe shortage of trained people in nuclear technology: ". . . the immediate goal is to retrain, through short courses . . . those already grounded in traditional disciplines." Through CREI Atomics you can now combine your present technical education and engineering experience with knowledge in nuclear engineering and technology. The result: increased career opportunities and corresponding income advantages as the nuclear field develops.

Program of study includes—

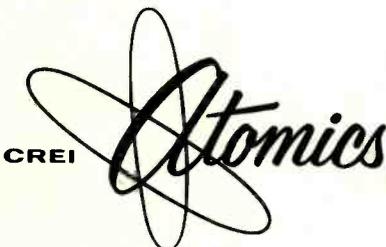Nuclear Physics, Reactor Physics, Thermodynamics, Reactor Technology, Reactor Controls, Instrumentation for Reactor Control, Isotopes, Health Physics—many other subjects




USE THIS COUPON TO REQUEST DETAILED CATALOG

CREI Atomics 1410-G
 3224 16th Street, N.W.
 Washington 10, D.C.
 Please send me complete information about CREI ATOMICS.
 name _____
 street _____
 city _____ state _____
 job title _____

NEW PRODUCTS (Continued from page 101)

creases record life.—Sonotone Corp., Elmsford, N. Y.

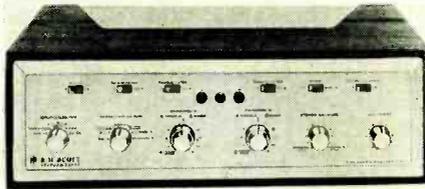STEREO AMPLIFIER model 299B improved version of 299. Monitoring for recording. Power increase to 50 watts



(IHFM standards). Extra-high-level input for electronic organs.—H. H. Scott, Inc., Dept. P., 111 Powdermill Rd., Maynard, Mass.

ORGAN TUNER uses spinning stroboscopic disc. Autotuner tunes most elec-




tronic organs in minutes. 6¾ x 5¼ x 2¼ inches. Microphone included.—Schober Organ Corp., 43 W. 61 St., New York 23, N. Y.

SUPER TWEETER T-202. Response 3,000 to 40,000 cycles (to 22,000 cycles ±2 db). Dispersion 120° in all direc-




tions. Power 30 watts. Built-in crossover and brilliance control. Impedance 8 ohms.—University Loudspeakers, Inc., 80 S. Kensico Ave., White Plains, N. Y.

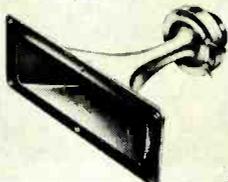HORN TWEETER, Tempo High Note. 2 x 6-inch horn loaded compression type.




Shielded magnetic circuit, wide-angle sound dispersion.—Oxford Components, 556 W. Monroe St., Chicago 6, Ill.

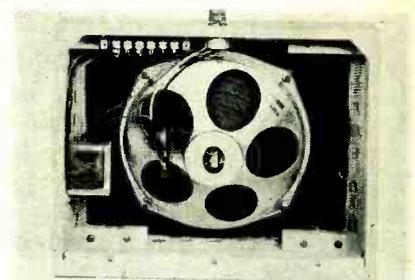SPEAKER - BAFFLE combination uses Magni-Magic inverted speaker. 4 series: (1) speaker and baffle; (2) speaker, baffle, volume control; (3) speaker, baffle, control, 70-volt transformer; (4) speaker, baffle, transformer. Blond, mahogany, walnut. 8-inch, 5-watt, 8-ohm speaker. Screw ter-




minals.—Utah Radio & Electronic Corp., 1124 E. Franklin St., Huntington, Ind.

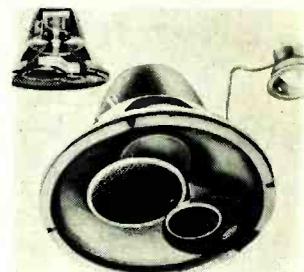TRIHELIX SPEAKER SK-180. 3 independent speakers on single frame. To minimize interaction, smaller speakers mounted off center. Built-in crossover network with brilliance control. Overall response 20 to 20,000 cycles (30 to 12,-




000 cycles ±3 db).—Lafayette Radio Corp., 165-08 Liberty Ave., Jamaica 33, N. Y.

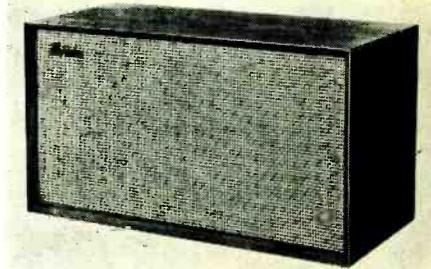SPEAKER SYSTEM model XP-2. Two 8-inch woofers, 5-inch tweeter. Response 35 to 15,000 cycles. Built-in crossover network. 22 x 12 x 11¼ inches. High compliance plus high efficiency. Enclosure filled with Acoustiglas to eliminate panel resonance. Birch,



cherry, walnut, mahogany. — Fisher Radio Corp., 21-21 44th Dr., Long Island City 1, N. Y.

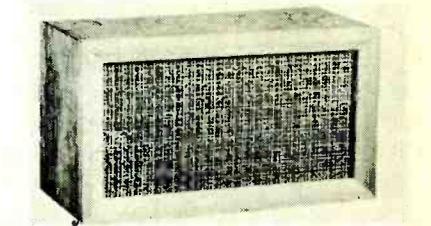
SPEAKER ENCLOSURE model 6. Unfinished. Cutout for 8-inch speaker, sound-reinforcing ports. 10 x 16 x 9



inches. ½-inch plywood, sanded on top and sides. Damping material installed.—Homewood Industries, 26 Court St., Brooklyn, N. Y.

NEXT MONTH

LOOK FOR THESE FEATURE ARTICLES IN

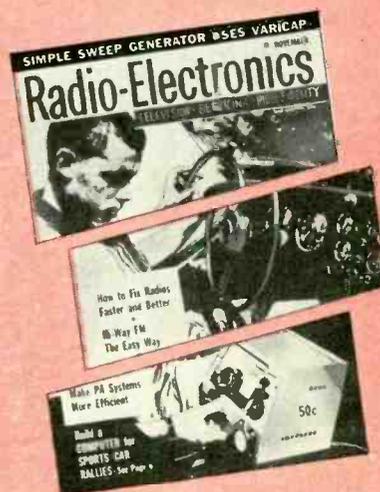

Radio-Electronics

HI-WAY FM — THE EASY WAY

You can buy an FM radio for your car—but the monthly payments for some of them come pretty high. There's an easier way—do it yourself. You can build this sensitive and selective FM car tuner, using a low-priced commercial set or an FM kit as the basic unit.

HOW TO FIX RADIOS FASTER AND BETTER

The Old-Timer insists he can diagnose the trouble in any radio receiver in five minutes—and he proves it! He says, "The only way to make money in radio repair is to fix 'em fast, but good!" You can learn—and earn a lot from the tips he gives you.

MORE EFFICIENT PA SYSTEMS

Listen as an old PA man tells how a few tricks can make amplifiers sound better and increase their power-handling ability. This one will make your PA work—a lot easier—and more profitable.

SIMPLE SWEEP GENERATOR USES VARICAP

Make your old sig gen into a sweep generator. It's easy using one of the new variable capacitance diodes. You can combine varicaps and inductances to give any desired deviation up to 600 kc.

**LAST CHANCE
TO SUBSCRIBE
AT PRESENT
LOW RATES**

**ALL THIS AND MORE IN RADIO-ELECTRONICS NOVEMBER ISSUE
ON SALE OCTOBER 20 • RESERVE YOUR COPY NOW.**

1 year \$4 • 2 years \$7 • 3 years \$10

**ON OCTOBER 31st RATES GO UP TO
1 year \$5 2 years \$9 3 years \$12**

Radio-Electronics

154 WEST 14th STREET • NEW YORK 11, N. Y.



... the world's standard wherever sound quality and dependability are paramount

The prime purpose in the design of every Shure microphone is faithful sound reproduction. All are painstakingly designed, developed, manufactured and tested for flawless performance coupled with longest possible trouble-free service. Regardless of price, they will perform according to specifications and will operate for years without deviation from their original standards.

MICROPHONES FOR EVERY APPLICATION—IN EVERY PRICE RANGE



NEW UNIDYNE III
World's most compact probe-type microphone with truly cardioid unidirectional pick-up pattern. Only 5/8" long! Dual impedance, superb response. Can be transferred from stand to hand instantly—without tools. \$51.00 Net.



UNIDYNE
World-famous dynamic microphone. Most widely used indoor-outdoor uni-directional microphone. Specified by leading sound engineers, and most requested by celebrities. \$49.80 to \$81.00 Net.



COMMANDO
Controlled-Magnetic omnidirectional. A significant achievement in quality sound at nominal cost. Can be hand-held, worn around neck, put into stand or withdrawn instantly, without tools. \$16.50 to \$23.10 Net.

Shure Brothers, Inc., 222 Hartrey Avenue, Evanston, Illinois

A NEW SERVICE AID

The versatile MULTI-PROBE DOES THE WORK OF 4 PROBES!

DC Probe AC/Ohms Probe RF Probe Lo-Cap Probe

Model MP-1 \$975 Dealer Net

Now for the first time — exclusive with MERCURY — a MULTI-PROBE that does all the work of 4 different probes. Functions: DC position . . . matches for VTVM input impedance • AC/Ohms position . . . for all low frequency, low impedance, voltages and wave forms • RF position . . . a demodulator for checking RF voltages, wave forms and signals and TV/radio RF and IF stages • Lo-Capacity position . . . a must for high impedance, TV sync and radio circuits where regular probes overload the circuit.

Available only through parts distributors

MERCURY ELECTRONICS CORP. 77 SEARING AVENUE, MINEOLA, NEW YORK
West Coast Office: 4306 W. Victory Blvd., Burbank, Calif.


NEW PRODUCTS (Continued)

TAPE RECORDERS, model 101 (shown) plays, records half-track monophonic. Response 50 to 12,000 cycles at 7½ ips. 5 transistors, 2 tubes. **Model 262-SL** plays 4-, 2-track stereo; records ¼-track monophonic. Response 30 to




18,000 cycles at 7½ ips. **Model 262-D** deck same specifications as 262-SL. All 117 volts, ac-operated. — Superscope, Inc., 8150 Vineland Ave., Sun Valley, Calif.

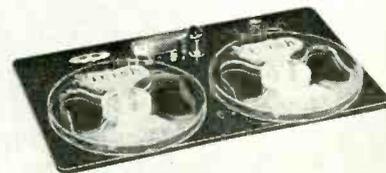TAPE-PLAYER KIT model AD-70 for prerecorded 4-track stereo tapes. For use with separate stereo preamplifier. Single control selects stop, play,



rewind, fast-forward. Mounts vertically or horizontally. Flutter and wow below 0.35%, harmonic distortion less than 2%. Finished, unfinished bases available.—Heath Co., Benton Harbor, Mich.

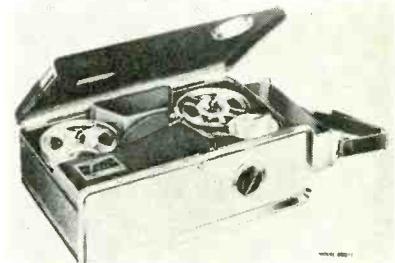PORTABLE RECORDER model MR511 works on 7 AA-size cells, house current or 12-volt auto systems. Plays 1½ hours at 1½ ips. 3-inch reels. Tran-



sistorized. 7 pounds, 3 x 6½ x 10¾ inches. '61 line ranges from stereo recorder-players to monophonic models for home use.—Telectrosonic Corp., 35-18 37 St., Long Island City 1, N. Y.

TURNTABLE AND ARM Realistic



NEW PRODUCTS (Continued)


Mark VIIIa. Hysteresis motor, 4 speeds. Noise level 50 db below average record level. Stereo pickup arm pivot-mounted with ball-bearing races to minimize friction. Mounting board, two 3-foot cables supplied.—Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass.

HIGH-FIDELITY pickup arms and turntables. *ST-33* turntable (shown): hysteresis-synchronous motor, 4 live-




rubber shock absorbers, polyurethane drive belt. 1/8-inch steel mounting plate has hole for pickup arms. *PK-33* turntable similar in kit form. *212 series* arms dual-viscous-damped. Kits available.—Gray Manufacturing Co., 16 Arbor St., Hartford 1, Conn.

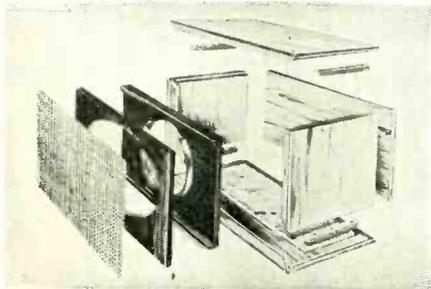CABINET KIT model *CK-14*. Elliptical port broadens frequency response.




No source separation between high, middle, low frequencies.—Lafayette Radio Corp., 165-08 Liberty Ave., Jamaica 33, N. Y.

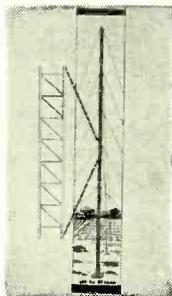ANTENNA TOWER No. 55. Rigidity and strength in heights up to 450 feet. 10-foot hot-dipped galvanized sections




constructed on 18 1/2-inch triangular pattern.—Rohn Manufacturing Co., 6718 W. Plank Rd., Peoria, Ill. **END**

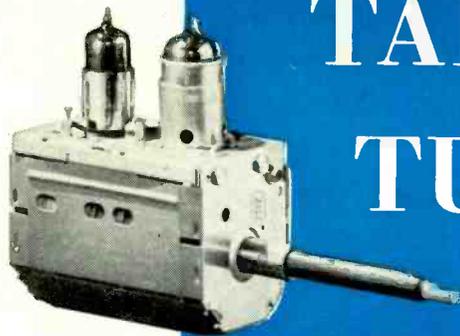All specifications are from manufacturer's data



HOT ROD
(turret-type)

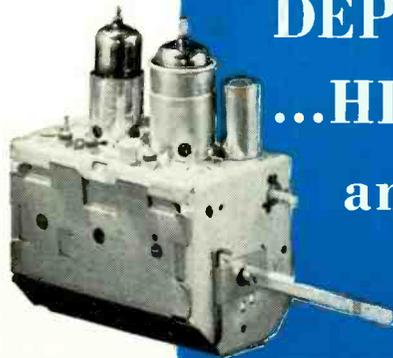

SILVER SEALED
(switch-type)



HI FI
(FM) Tuner

TARZIAN TUNERS

Noted for their
DEPENDABILITY
...HIGH QUALITY
and **LOW COST**

That's why the world's leading set manufacturers rely on the trouble-free TARZIAN TUNER for the excellent performance of their receivers.

Today TARZIAN TUNERS are backed up by more than 15 years of experience in the design . . . development . . . and production of more than 15 million TV Tuners.

And, Tarzian is the only commercial manufacturer offering both the HOT ROD (turret-type) and SILVER SEALED (switch-type) . . . as well as the newer Hi Fi FM Tuner.

All embody the high standards of QUALITY . . .

DEPENDABILITY . . . and PERFORMANCE that have made Tarzian a leader in the field.

For more information, write to: Sales Department
Tuner Division



SARKES TARZIAN INC

east hillside drive • bloomington, indiana

Manufacturers of Semiconductors, Air Trimmers and Broadcast Equipment

BECOME A RADIO TECHNICIAN

for only \$26.95

BUILD 20 RADIO

CIRCUITS AT HOME

with the New Progressive

RADIO "EDU-KIT"®

Reg. U.S. Pat. Off.

All Guaranteed to Work!

PRACTICAL only
HOME RADIO COURSE \$26.95

NOW INCLUDES

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ AMPLIFIER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR



TRAINING ELECTRONICS TECHNICIANS SINCE 1946

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • HI-FI GUIDE • QUIZZES • TV BOOK • FCC AMATEUR LICENSE TRAINING • RADIO BOOK • PRINTED CIRCUITRY • PLIERS-CUTTERS • ALIGNMENT TOOL • WRENCH SET • CERTIFICATE OF MERIT • VALUABLE DISCOUNT CARD

WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and lay out radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay, only \$26.95 complete.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are twenty Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector, Square Wave Generator and Amplifier circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, job, or professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hookup wire, solder, selenium rectifiers, volume controls, switches, knobs, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator. In addition to the F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

J. Statulis, of 2 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

UNCONDITIONAL MONEY-BACK GUARANTEE

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc., for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7.00


- Send "Edu-Kit" Postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name.....

Address.....

Progressive "EDU-KITS" Inc.

1186 Broadway, Dept. 169G
Hewlett, N. Y.

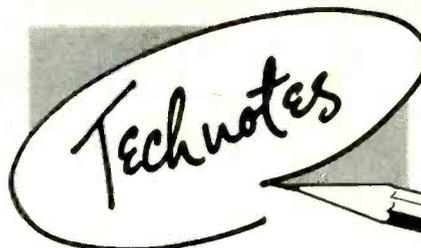


SILVERTONE 7140-A

Complaint was color fringing obviously caused by poor horizontal dynamic convergence. When an attempt was made to adjust convergence, no response was obtained from the red or green horizontal phasing controls. The control circuit is shown in the diagram.

A scope check showed drive voltage was being applied to the circuit, but that very little voltage was developed across the coils and trimmer capacitor. There was evidently a short or open in the circuit.

An ohmmeter check indicated no shorts or opens. Yet the 900-volt sine waveform refused to appear when the receiver was turned on. After a bit of wasted time, we discovered that the 25-280- μ f trimmer would short under the applied ac voltage, though it checked out OK at the 1.5 volts applied by an ohmmeter.

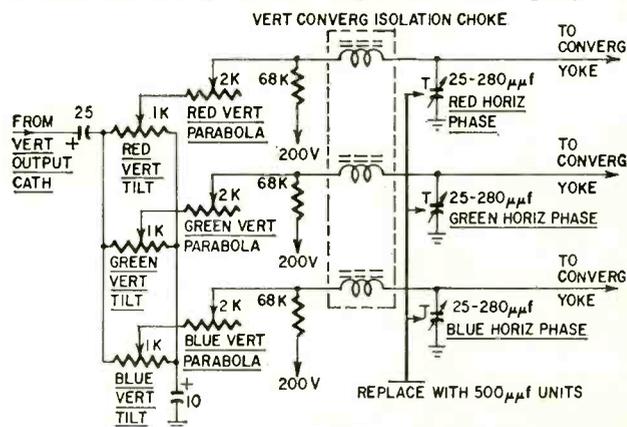The faulty trimmers were replaced, using units having a top range of 500 μ f. This corrected the difficulty. We found that the top value of 280 μ f in the original trimmers necessitated turning the adjusting screw down tightly to set



the phase correctly. Because of the high compression force, the trimmers failed to hold up under stress of the high ac voltage.

Using replacement trimmers with a top value of 500 μ f permitted correct phase adjustment without excessive compression.—Robert G. Middleton

PIX STREAKS AND FLASHES

Streaks and flashes in a television picture are often caused by a minor defect in the tuner—a dirty switch contact or wiper. This can usually be cured by spraying the contacts and wipers with a contact cleaner. Use a perfume atomizer to get a fine penetrating spray or try one of the new spray cans.—W. C. Warren

PHILCO MODEL UG3052-BL

This model often has a very noisy and defective tuner. The channels will not hold on station, sound is intermittent and, in extreme cases, there is no picture. A cursory examination of the tuner may lead the technician to diagnose the trouble as contact oxidation, or just plain dirty contacts and springs—but beware. Close inspection reveals that the tuner will not be repaired so easily. In fact, several jobs that crossed the bench led me to believe that the tuner was ready to fall apart. Anything in it you touched caused the set to cut out, with loss of most of the sound, and snow. You decide the tubes are defective or that a portion of the printed circuit, down underneath, is unsoldered but, regardless of the steps taken to find the trouble, as soon as these receivers are plugged in and the station selector is turned to one of the local channels—the same old trouble!


TECHNOTES (Continued)

In every case checked, the trouble turned out to be in the contact rivets on the shaft discs. Apparently the strain on these contacts, caused by turning from channel to channel, breaks the solder joint where they are solder-dipped to the thin printed wiring on the back side of the disc. The break cannot be seen and will not appear to be at this point. But, by very carefully touching up these soldered spots with a small iron, the trouble usually will be corrected. This condition, if not isolated at once and corrected, may cause several discouraging callbacks. If the job is approached with deliberation along the lines mentioned here, it should take no longer than a few minutes to satisfy the customer completely.—*George D. Philpott*

CORONADO 15TV4

Complaint: No raster.

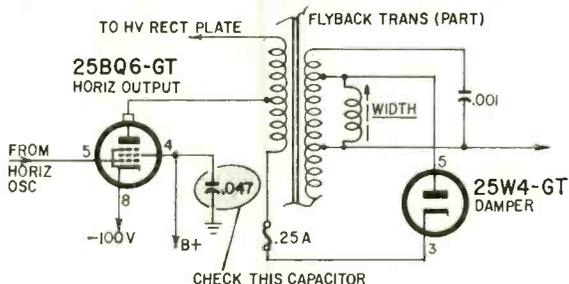Cure: Check B-plus at pin 3 of the 25W4 damper. If it reads about 220 volts instead of the recommended 280, check for an open .047- μ f capacitor from the screen grid of the




25BQ6 (the horizontal output tube) to ground. In one set with this trouble, both the horizontal oscillator and output

transformers were singing and would have been suspect. However, a quick check showed normal voltages and waveforms in their circuits.—*John B. Ledbetter*

G-E 17P1329

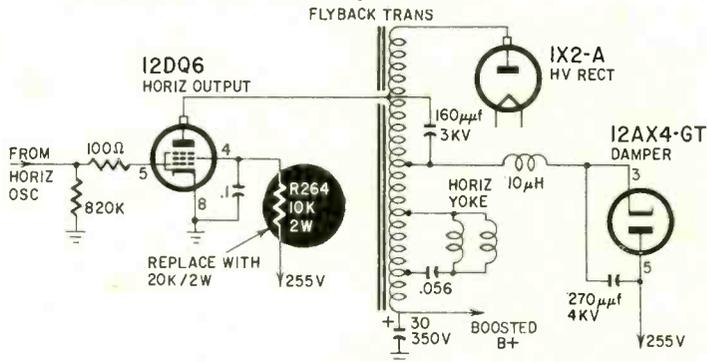Complaint: Too much width. The sides of the picture extend past the edges of the picture tube.



This problem can be cured by increasing the value of R264 from 10,000 ohms to 20,000 ohms. Use a 2-watt resistor.—*George Warren*

FORD 74BF

A stubborn case of distortion in this auto radio hybrid was solved when we discovered the transistor bias control was set at maximum resistance. As emitter current was normal at this setting, it indicated an unusually sensitive transistor. When a more normal transistor was substituted and the bias readjusted, the distortion disappeared.—*Chase Bass* END



Replace improper equipment with the only microphone designed specifically for citizen's band **THE TURNER 350C**

This reasonably priced, mobile-type ceramic microphone is the perfect replacement for the many improper, tape recorder-type microphones now being used on CB equipment. Has DPST switch wired for relay operation with easily reversible terminals to allow modifications (if necessary); wiring diagram enclosed with each microphone; hanger button and standard dash bracket for mobile rig mounting; and an 11" retracted (five foot extended), plastic-jacketed, coiled cord. Response: 80-7,000 cps. Output: -54 db. List price: \$16.50 complete. See your Turner Distributor, listed below, he has the 350C in stock.

THE TURNER MICROPHONE COMPANY
933 17th St. N.E.
Cedar Rapids, Iowa

- ARKANSAS**
Little Rock: Southern Radio Supply
Texarkana: Lavender Radio & T.V. Sup.
- CALIFORNIA**
Downey: Net Electronics
Hemet: Gil Sevens
Hollywood: Pacific Radio Exchange
Los Angeles: Radio Product Sales
The Sound Foyer
- Oakland: Elmor Electronics
Sacramento: Selectronics
San Francisco: Market Radio Sound Dept.
San Pedro: Marine Radio Service
- DISTRICT OF COLUMBIA**
Washington: Electronic Wholesalers
- FLORIDA**
Miami: East Coast Radio & TV
Tampa: Kinkade Radio Supply
- GEORGIA**
Atlanta: Specialty Distributing
- ILLINOIS**
Chicago: Nationwide Radio
La Salle: La Salle Electronics
- INDIANA**
Anderson: Seybert's Radio Sup.

- Bloomington: Stansifer Radio Co.
Evansville: Hutch and Son, Inc.
Ohio Valley Sound
- Fort Wayne: Pembleton Laboratories
Indianapolis: Brown Distributing Co.
Graham Electronic Sup.
Van Sickle Radio Supply
- Kokomo: George's Electronic Sup.
- Michigan City: Tri-State Electrical Sup.
- Portland: Buck's Hi-Fi
Richmond: Fox Electronics Company
Terre Haute: Midwest Supply Company
- IOWA**
Cedar Rapids: Iowa Radio Supply
Des Moines: Radio Trade Supply Co.
- KANSAS**
Topeka: Acme Radio Supply
- KENTUCKY**
Lexington: Radio Equipment Co.
Louisville: Arby Electronics
P. I. Burks Company
- LOUISIANA**
Baton Rouge: Davis Electronics Sup.
New Iberia: Brooks Electronics

- MASSACHUSETTS**
Boston: A. W. Mayer Company
Radio Shack Corp.
- Lawrence: Alco-Electronics
- MICHIGAN**
Ann Arbor: Purchase Radio Supply
Detroit: High Fidelity Workshop
Lansing: Offenauer Company
- MINNESOTA**
Minneapolis: Schaak Electronics
- MISSOURI**
St. Louis: Radonics
- NEW JERSEY**
Berlin: Midstate Radio Supply
Jersey City: Nidisco-Jersey City
Mountainside: Federated Purchaser
- NEW YORK**
Buffalo: Radio Equipment Corp.
Farmingdale, L.I.: Gem Electronics
Forest Hills: Beam Electronics
Mt. Vernon: Davis Electronics
New York: Harvey Radio Company
Acme Electronics
- OHIO**
Cleveland: Pioneer Electronic Sup.

- Columbus: Whitehead Radio Company
Mansfield: Wholesaling, Inc.
Toledo: Lifetime Electronics
- OKLAHOMA**
Oklahoma City: Johnson Wholesale
- OREGON**
Portland: United Radio Supply
- PENNSYLVANIA**
Lancaster: George D. Barbey Co.
Lebanon: George D. Barbey Co.
Philadelphia: Radio Electric Service Co.
Pottstown: George D. Barbey Co.
Reading: George D. Barbey Co.
Wilkes-Barre: General Radio & Electronic
York: Radio Electric Service Co.
- TEXAS**
Houston: Sound Equipment Inc.
- VIRGINIA**
Arlington: Rucker Electronic Products
Falls Church: The Television Workshop
- WISCONSIN**
Chippewa Falls: Bushland Radio Spec.
Eau Claire: Bushland Radio Spec.

ALL NEW!



EMC advances in Audio and Test Equipment—by far the Best Values obtainable in Wired or Kit form.

EMC Model 801 RC Bridge and In-Circuit Capacity Checker

A new comprehensive resistance and capacity checker. It measures condensers for actual value, leakage and power factor. In addition it measures condensers while still connected in their original circuits for opens, shorts or intermittents.



Model 801 Wired\$38.95 — Model 801 Kit\$24.95


EMC Model 802 Signal Tracer and Generator

Generates its own audio, IF and RF signal for tracing. Uses both a magic eye tube and a speaker for signal detection. Checks noisy components. Checks and compares magnetic, ceramic and crystal cartridges. Supplied with two shielded audio probes and RF crystal demodulator probe. Model 802 Wired\$38.95 Model 802 Kit\$24.95



EMC Model 107A Peak to Peak Vacuum Tube Volt-Ohm Capacity Meter

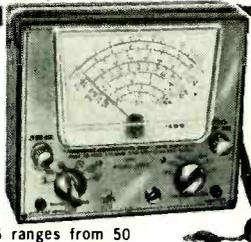6" meter cannot burn out — entirely electronic. Measures peak to peak AC voltages to 2800 volts in 6 ranges. Measures capacity in 6 ranges from 50 mmfd to 5000 mfd. Measures resistance in 6 ranges from .2 ohm to 1000 megs. Measures DC volts to 1000 volts in 6 ranges. Input resistance 16.5 megs. Model 107A Wired\$51.40 — Model 107A Kit\$36.50



EMC Model 214 Stereo Amplifier

A compact, highly attractive dual 14W amplifier with built in preamplifiers having 56 watts peak power output. Has rumble filter and contour control switch. Extremely low distortion and noise level. It can be used as a 28 watts (56 watts peak) monaural amplifier or as a monaural amplifier so arranged that one pre-amplifier is used to drive the internal amplifier while the other preamplifier is used to drive any existing monaural amplifier. Model 214 Wired\$106.80 — Model 214 Kit\$68.90

NOTEWORTHY CIRCUITS

TWO POWER MEGAPHONES

Of the circuits shown, the 1-watt unit (Fig. 1) will be adequate in most uses. The input load impedance is the primary of an output transformer. The 4-8-ohm secondary is not used. The 6-watt megaphone (Fig 2) is very powerful and can be considered a deluxe model. Wiring and parts layout are not critical and both amplifiers are de-

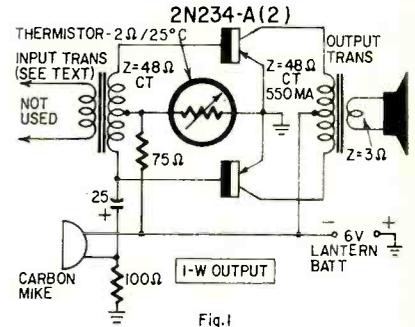


Fig. 1


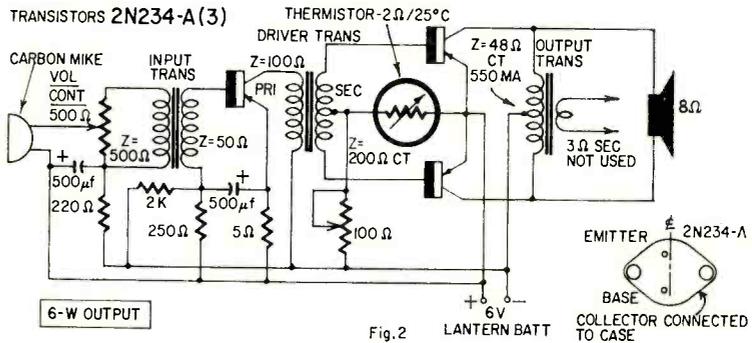


Fig. 2

TUBE REPLACEMENT GUIDE

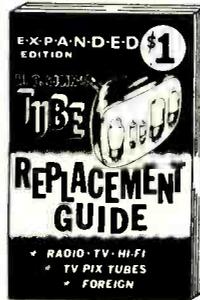EVERYONE who uses vacuum tubes NEEDS this new 1960 Expanded Edition TUBE GUIDE!



Contains over 4600 direct substitutions, including radio & TV receiving tubes, tubes used in Hi-Fi & Stereo, foreign tubes and TV picture tubes.

All tubes suggested for substitution have characteristics similar to those they are to replace. FIT INTO SAME SOCKET & NEED NO WIRING CHANGE.

Two chapters cover complete listing of 738 TV Pix tube replacements including newest 110° tubes.

Substitutes given for over 414 foreign tubes. also lists 415 transistor substitutes. The only complete GUIDE featuring all receiving tube SUBSTITUTIONS WITHOUT SOCKET CHANGES OR REWIRING.

This valuable book will save you TIME & MONEY and permit operation even though original tubes are unavailable.

Guaranteed Money Back in 5 days if Not Satisfied. Order from your Parts jobber or RUSH COUPON NOW!

\$1 Post-paid

Superior Instruments Company, Dept. 102
2435 White Plains Road, New York 67, N.Y.
Enclosed find \$1. Rush TUBE REPLACEMENT GUIDE.

Name

Address

City Zone State

Purchasing A HI-FI SYSTEM?

Send Us Your List Of Components For A Package Quotation

PARTIAL LIST OF BRANDS IN STOCK

- Jim Lansing*
- Altec Lansing
- Electrovoice
- Jensen
- Hartley • Viking
- University
- Acoustic Research
- Janszen
- Wharfedale
- USL Citizen Band
- Gonset • Hallicratter
- Texas Crystals
- Concertone
- Bell • G.E.
- Weathers
- Harman-Kardon
- Eico • Pilot
- Acrosound
- Quad Ampl & Spkrs*
- Dual Changer
- Bogen • Leak
- Dynakit • Fisher
- H. H. Scott
- Thorens* Sherwood*
- Pentron • Roberts
- Amplex • DeWald
- Sony • Tandberg*
- Challenger
- Wallensak
- Garrard
- Miracord
- Glaser-Steers
- Rek-O-Kut
- Components
- Norelco
- Fairchild
- Pickering • Gray
- Audio Tape
- Magnecord*
- Artizan Cabinets
- Rockford Cabinets

WE WON'T BE UNDERSOLD!

All merchandise is brand new, factory fresh & guaranteed.

AIREX RADIO CORPORATION

64-RE Cortlandt St., N.Y. 7, CO 7-2137

RE 106

Yes, tell me more, send me FREE a detailed catalog of the Complete EMC Line.

NAME

STREET

CITY STATE

EMC Electronic Measurements Corp.
625 B'way, New York 12, N. Y.
Pan-Mar Corp, 1270 Broadway New York, N. Y.


signed for use with standard 6-volt lantern batteries. The transistors in the

6-watt version must be mounted on a heat sink.—*Bendix Semiconductors*

MORE ON THE SNITCHER

After building the Snitcher described in the November 1959 issue (page 35), I decided to make a couple of changes.

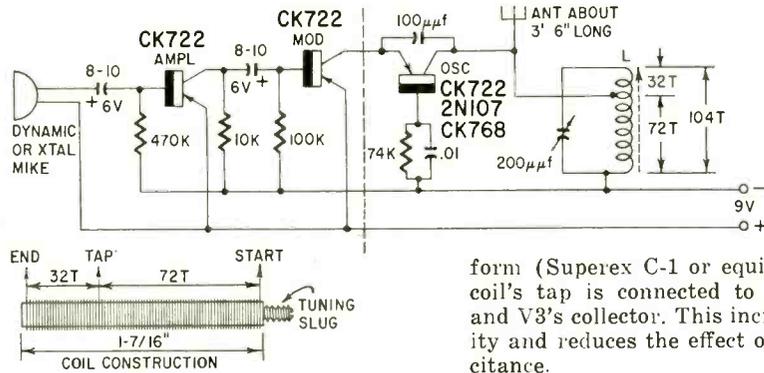put considerably. I also wound a new coil with 104 turns of No. 36 cotton-covered wire close-wound on a 1/4-inch




First I substituted a simplified amplifier-modulator unit. Then I decreased the value of R3, the oscillator base resistor, to 74,000 ohms. This increased out-

form (Superec C-1 or equivalent). The coil's tap is connected to the antenna and V3's collector. This increases stability and reduces the effect of body capacitance.

The hookup is shown in the diagram, and the operating frequency is in the upper part of the broadcast band.—*Karl Sperber*

- VOLTAGE-LIMITED SUPPLY -

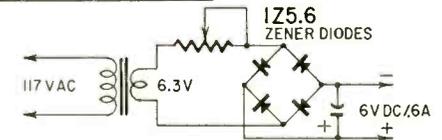The diagram shows a simple regulated dc supply. The Zener diodes both rectify and limit the supply's output voltage. They are selected to act as clippers in combination with the potentiometer. This limits the voltage to which the capacitor can be charged. The arrangement provides control of more power than could ordinarily be handled by



these Zeners and can be used wherever extreme regulation is not vital.—*International Rectifier News*

GERNSBACK LIBRARY
Low-cost, paper-covered books on all phases of TV, radio, audio-high fidelity and practical electronics ON SALE AT ALL BETTER PARTS DISTRIBUTORS.

TV PICTURE TUBES AT LOWEST PRICES

NEW TUBES	14RP4 \$16.95	21CEP4 \$22.95
ALL ALUMINIZED:	14W/ZP4 16.95	21DEP4 22.95
	17BJP4 19.95	24AEP4 26.95
	17BZP4 19.95	24AHP4 26.95

1 year warranty
Aluminized tubes \$3.00 for 21"; \$5.00 for 24" and 27" additional. Prices include the return of an acceptable similar tube under vacuum. These tubes are manufactured from reprocessed used glass bulbs. All parts and materials including the electron gun are brand new.

ALL PRICES FOR CHICAGO, ILLINOIS. Deposit required, when old tube is not returned, refundable at time of return. 25% deposit required on COD shipments. Old tubes must be returned prepaid. Tubes shipped Rail Express. Shipped only to Continental U.S. and Canada.

WRITE FOR COMPLETE LIST

—PICTURE TUBE OUTLET—
2922 MILWAUKEE AVE., CHICAGO 18, ILLINOIS
Dickens 2-2048

DON'T WASTE TIME MAKING CONNECTING CORDS

There is a SWITCHCRAFT INTERCONNECTING CORD FOR EVERY JOB

Before you take time to make up a special cord to connect 2 units, check or write for Switchcraft Catalog S-590. Over 190 Molded Cables with different type connectors and lengths.

Stocked by Electronic Parts, Musical and Photo Distributors.

SWITCHCRAFT
5579 N. Elston Ave., Chicago 30, Ill.
Canadian Rep.: Atlas Radio Corp., Ltd., 50 Wingold Ave., Toronto, Ontario.

Special Microammeters
4 Inch Sq. 50-0-50 Microamps. Ea. \$6.90
0-50 Microamps. Ea. \$7.90

EIMAC TRANSMITTING TUBE
4507L—Brand New—Fully Guaranteed **\$39.45**
Each

DYNAMOTOR SPECIAL
12 Volts Input-Output 440V. @ 200Ma., 12 Volts Input-Output 225V. @ 100Ma. All in one Dynamotor. BRAND NEW. Ea. **\$7.90**

BRAND NEW CARTER DYNAMOTOR
INPUT 5.9 VOLTS, OUTPUT 405 V. Ea. **\$4.90**
270 MA. SMALL SIZE

COAX CABLE
RG8U—52 Ohm Impedance—Fresh Stock—500 feet on sealed wooden spools. Each **\$32.45**
RG62A/U—92 ohm impedance—Fresh Stock—1000 Foot Spools. Ea. **\$38.45**
Smaller quantities 7 1/2¢ per ft. Min. order 25 ft.

NEW VACUUM CAPACITORS

50 MMF-5KV	\$ 90
25 MMF-10KV	2.20
EIMAC VC 12 MMF-32KV	6.90
EIMAC VC 25 MMF-32KV	7.90
EIMAC VC 50 MMF-32KV	8.90
JENNINGS 100 MMF-20KV	12.90
JENNINGS JHC-150 MMF-50KV	24.90

POWER TRANSFORMER
Primary 110V, 60 cy. Sec 445-0-445V. @ 150 Ma. 6.3V. @ 6 Amps. 5V. @ 3 Amps. Fully shielded. Ea. **\$3.90**
Write for quantity prices

CHOKE—FULLY CASED

4 HENRY 1 AMP	\$13.90
5 HENRY @ 200 Ma	1.90
5 HENRY @ 250 Ma	2.20
4-12 HY (Swinging) @ 300 Ma	3.90
10 HENRY 300 Mil	3.45
4 HENRY 400 Mil	3.90
12 HENRY 500 Mil	8.90
4 HENRY 900 Mil	12.90
6 HENRY 600 Mil	8.90

BRAND NEW OIL CONDENSERS

3 MFD 600 VDC .55	4 MFD 2000 VDC 3.45
4 MFD 600 VDC .70	6 MFD 3000 VDC 4.90
5 MFD 600 VDC .75	8 MFD 2000 VDC 5.90
6 MFD 600 VDC .80	2 MFD 2500 VDC 2.45
8 MFD 600 VDC .90	1 MFD 3000 VDC 1.80
10 MFD 600 VDC 1.14	2 MFD 3000 VDC 3.45
12 MFD 600 VDC 1.45	1 MFD 4000 VDC 3.20
15 MFD 600 VDC 1.65	2 MFD 4000 VDC 6.20
3x8 (24 MFD) 600 VDC 2.45	3 MFD 4000 VDC 8.90
1 MFD 1000 VDC .55	4 MFD 4000 " 12.90
2 MFD 1000 VDC .80	15 MFD 5000 " 39.45
4 MFD 1000 VDC 1.30	2 MFD 15000 " 2.90
8 MFD 1000 VDC 1.90	1 MFD 7500 " 17.90
10 MFD 1000 VDC 2.45	2 MFD 15000 " 42.45
12 MFD 1000 VDC 2.90	1 MFD 12500 " 19.90
15 MFD 1000 VDC 3.45	2 MFD 12500 " 34.45
1 MFD 1200 VDC .40	1 MFD 15000 " 42.45
2 MFD 1500 VDC .70	5 MFD 25000 " 64.90
2 MFD 1500 VDC 1.05	1 MFD 25000 " 39.90
4 MFD 1500 VDC 1.90	2 MFD 330 AC 1.90
8 MFD 1500 VDC 2.90	20 MFD 330 AC 2.90
1 MFD 2000 VDC .80	8 MFD 660 AC 2.90
2 MFD 2000 VDC 1.45	2 MFD 600 VDC .45

RELAYS

GUARDIAN 110V AC, 2 Pole Single Throw (1 N.O. & 1 N.C.) Repl. BC-610	\$2.45
Potter-Brumfield SM5LS 5000 ohm, 4 Ma. Sens.	\$2.20
Hermetically Sealed Relay Coil 110V AC 60 Cy SPDT Contacts 5 Amps.	\$1.45
6 Volt DC DPDT H.S.	94¢
12 Volt DPDT Relay	\$1.30
SIGMA type 22RJc 8,000 ohm SPDT, small sealed relay	\$2.44
Sealed Relay, SPDT, 6,000 ohm coil	\$1.90
G.E. Relay control, contains 8000 ohm relay, sensitivity 2 mils 10 for 59.25. ea.	\$1.05
SIGMA SF—16,000 ohm SPDT, operates on 500 Microamperes or less.	\$3.90

PANEL METERS 3" METERS

STANDARD BRANDS	100-0-100 Micro Amps
0-1 Mil	DC \$5.90
0-100 Micro	0-1 Mil DC 3.90
	0-10 Mills DC 3.90
	0-100 Mills DC 3.90
	0-150 Mills DC 3.90
	0-500 V. DC 3.90
2" METERS	0-1 Amp RF 4.45
100-0-100 Micro	0-15 Amps RF 4.45
0-50 Micro (0-5 scale)	0-12 Volts AC 3.90
0-10 Amps DC	0-15 Volts AC 3.90
0-20 Volts DC	REED Pres. Meter
15-36 Volts DC 1.94	110V. AC 57
0-150 V. AC	63 cy 9.90

MISCELLANEOUS SPECIALS


JOHNSON Var. Cond. 250 MMF 3500 V.	\$2.45
SPERTI Vacuum Switch used in ART 13 ea.	\$1.45
36 OHM 50 Watt Globar Non-Ind. Rec.	55¢ ea. 2 for \$.95
3-12 MMF Eric Ceramic Trimmers	16¢
FULL WAVE SELENIUM RECTIFIERS—20 Plates per section—Output 320V. @ 4 Amps.	\$4.90
Ea.	
MAGNETIC PICK-UP TOOL gets Nuts, Bolts, Tacks etc. out of difficult places.	74¢
Each	
CUTLER-HAMMER TOGGLE SWITCH SPDT (S742D) 4 for 5.95.	24¢
WILLARD STORAGE CELL—2V, 28 Amp hrs. Clear plastic case. Shipped dry.	\$2.45

Write for quantity prices on all special items

All merchandise sold on a 10 day money back guarantee
Min. Order \$3.00—25% with Order—F.O.B. New York

PEAK
ELECTRONICS COMPANY
66 W. Broadway, New York 7, N. Y., WO-2-2370

"I've never been without PHOTOFACT.."

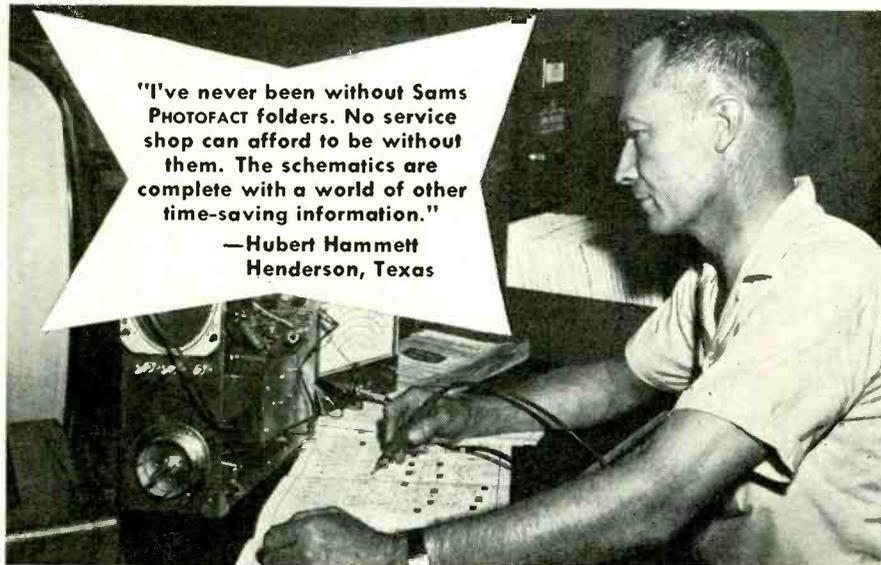

"I've never been without Sams PHOTOFACT folders. No service shop can afford to be without them. The schematics are complete with a world of other time-saving information."

**—Hubert Hammett
Henderson, Texas**

Service Technicians! YOU EARN MORE... YOU RATE with the public when you own the PHOTOFACT® service data library!

You enjoy maximum earnings as the owner of a complete PHOTOFACT Service Data Library! It's inevitable, because no matter how expert you are, you can always *save more time on any job, get more jobs done daily*—EARN MORE, DAY IN AND DAY OUT...

What's more—as the owner of a complete PHOTOFACT Library, you know your customers' sets *best*. You can actually show each customer you have the PHOTOFACT Folder covering his very own set. Result: You command public respect and acceptance which paves the way to more business and earnings for you.

HOW TO STAY AHEAD...

Yes, the truly successful Service Technicians are those who own the complete PHOTOFACT Library, who can meet and solve any repair problem—faster and more profitably. And these men *keep ahead* because they're on a Standing Order Subscription with their Distributors to receive all new PHOTOFACTS as they are released monthly. (They're eligible for the benefits of membership in PEET, too—see below!)

ONLY \$10 DOWN puts the complete PHOTOFACT Library in your shop—and you have up to 30 months to pay. See your Sams Distributor today, or write to Howard W. Sams

NOW IS THE TIME TO JOIN

"PEET"

THE POWERFUL NEW PROGRAM FOR QUALIFIED TECHNICIANS

If you now own a PHOTOFACT Library or plan to own one, you can apply for membership in "PEET." It's the first industry program really designed to build powerful public acceptance for the Service Technician who qualifies. Builds enviable prestige and business for its members. Benefits cost you absolutely nothing if you qualify. Ask your Sams Distributor for the "PEET" details, or mail coupon today.

HOWARD W. SAMS & CO., INC.
1726 E. 38th St., Indianapolis 6, Ind.

- Send me full details on the new "PEET" Program.
- Send full information on the Easy-Buy Plan and Free File Cabinet deal.
- I'm interested in a Standing Order Subscription.
 - I'm a Service Technician full-time; part-time

My distributor is _____

Shop Name _____


Attn: _____

Address _____

City _____ Zone _____ State _____

TECHNICIANS'

NEWS

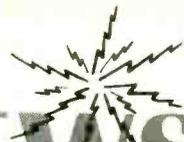

NEW KC LICENSE LAW

The City Council of Kansas City (Mo.) passed a new ordinance regulating TV and radio servicing after the old one had been declared void in a suit brought against the city by The Electronic Association of Missouri (TEAM). The Honorable Tom J. Stubbs, presiding judge, had ruled that the old law was altogether too broad and unreasonable.

Judge Stubbs also said: "I think the ordinance is bad for a further reason . . . the Board of Examiners are directed to take into account the character and reputation of the applicant for a license and, as I construe the ordinance, may refuse to recommend an applicant for a license if the board concludes that his character is such that he shouldn't have a license." The new ordinance makes no mention of character.

The old law applied to all electronic devices containing tubes, transistors or both. The new law pertains to "radio and/or TV receiving apparatus and associated components."

Service dealers and technicians are divided into three groups—Class One for both radio and TV servicing, Class Two for TV only and Class Three for radio alone. License fees are \$10 annually for a technician and \$25 for a service dealer.

The law also provides that customers must receive a copy of a bill showing the date(s) when work was performed; make, model and serial number of the set; full name and serial number of the licensee; name and address of the customer and the charge computation. The computation must specify what work was done and the amount charged for each part replaced. The dealer must keep his copy of the bill for 2 years.

WANT ASSOCIATION?

Those interested in forming a service association in Great Falls, Mont., are asked to contact LeRoy Peck, Peck's Radio-TV, 1010 First Ave. South, Great Falls.

OFFICERS RE-ELECTED

Raymond G. Tuszynski was re-elected president of the Electronic Service Association of Butte, Montana. Harry Carroll was re-elected recording secretary; Kenneth Venner, treasurer; and Al Laurick, trustee. New officers are Mrs. Eileen Giese, corresponding secretary and Bjarne Johnson, trustee.

CLOSED-CIRCUIT INSTRUCTION

Closed-circuit TV was used by General Electric Co. for instructing a class of television technicians at Buffalo,

N. Y. One camera was used to bring into view intricate assembly operations and to scan meters, charts and oscilloscopes. One 17-inch set was used as a monitor and six 21-inch sets were used for the technicians. All service technicians in the Buffalo, N. Y., area (independent and G-E) had been invited to attend.

Audience reaction was very favorable, according to Steven R. Mihalic, television service manager. "Giving each person a closeup view, even of waveforms and meter readings, established a close relationship between student and instructor and greatly facilitated an exchange of information," he said.

HESTER INJURED

Robert W. Hester, past president of NATESA, was seriously injured in a fall from a ladder while installing an air conditioner, according to *The Hoosier Test Probe*. His shop is located in Mission, Kan.

LICENSING CAMPAIGN

The California State Electronics Association is behind a massive signature campaign for state licensing. The program centers around a dummy ballot which is offered to technicians around the state. They are asked to indicate that they would vote for a state license bill and then sign their names. The

6810 **BALLOT**

<p>PROPOSITION NO. 1</p> <p>To license radio and television technicians in the STATE OF CALIFORNIA</p>	YES		
<p>As a registered voter of the STATE OF CALIF. I would support with my vote, the licensing of radio and television technicians in the STATE OF CALIFORNIA</p>	NO		

NAME _____

ADDRESS _____

CITY _____

ballots are then forwarded to State Legislators.

The ballot has the statement "As a registered voter of _____ county I would support with my vote, the licensing of radio and television technicians in the State of California" printed on it. Extra copies are available for technicians to give to their customers.

IOWA OFFICERS

The Television Electronic Service Association of Iowa (TESA) elected Henry Gulliver as its new president, states the *T.E.S.A. Beacon*. Bob Norman was elected vice president; Don Price, secretary; Ed Vilimek, treasurer. Members of the Board of Directors are Howard L. Bonar, Gene Wierson, George Rizzio, Jim Yordy, George Miller, Leland Scott, J. R. Jackson and Jack Betz.

PUBLICATIONS LIST

Below is a list of most of the magazines, folders and newsletters published by service associations around the country. A complete list of associations is planned for a forthcoming issue.

One of the most important things an association needs is publicity. If you make the public aware of you and what you stand for, you have taken the first step toward eliminating the doubt with which much of the profession is regarded. We do not make this statement lightly. Association publications from all over the country agree that a major problem to the industry is the fringe group of dishonest operators. What good does it do to set high standards of ethics, conduct, etc., unless the public knows about it? Publicity is a powerful weapon in the fight to upgrade the profession!

Yet some associations seem to be almost ashamed to admit they exist. Many groups have not answered our letters inquiring as to the name of the secretary or president. Some associations will not even reveal their address. We get letters and cards from individuals wanting to know the name of their nearest association. We send what information we have, but often we do not know the name of an officer to contact or even if the association is still active.

For information, write to: Associations Editor, RADIO-ELECTRONICS, 154 W. 14 St., New York 11, N. Y.

ARTSD NEWS
Don Hamill, editor
 Associated Radio & TV Service Dealers
 2552 N. High St.
 Columbus 2, Ohio

CINTI TESA NEWS
Harold J. Gruber, editor
 TESA of Cincinnati
 4365 Kalama Ct.
 Cincinnati 36, Ohio

CSEA DIGEST
Chet Spink, editor
 California State Electronics Association
 Orbit Publications
 Rm. 467A Porter Bldg.
 San Jose 13, Calif.

ETAT NEWS
Vern LaPlante, editor
 Electronic Technicians Association of Toledo, Inc.
 1952 Sylvania Ave.
 Toledo 13, Ohio

E. T. G. NEWS
Donald A. Ciccolini, editor
 Electronic Technicians Guild, Greater Boston Chapter
 PO Box 124
 W. Somerville 44, Mass.

GUILD NEWS, THE
Jack Wheaton, editor
 Radio TV Guild of Long Island, Inc.
 464 Sagamore Ave.
 E. Williston, N. Y.

HOOSIER TEST PROBE, THE
Frank J. Teskey, editor
 Indiana Electronic Service Association
 PO Box 23125
 Indianapolis 23, Ind.

IPET (for the Independent Electronics Technician)
Arnold J. Meyer, editor
 Society of Radio & TV Technicians, Inc.
 PO Box 126
 Van Nuys, Calif.

NATESA SCOPE
Albert C. W. Saunders, president
 National Alliance of TV & Electronic Service Associations
 5908 S. Troy St.
 Chicago 29, Ill.

PRINTED CIRCUIT, THE
Jim Hornaday, editor
 North Carolina Federation of Electronic Associations, Inc.
 1228 Montlieu Ave.
 High Point, N. C.

RASTER, THE
Benton Linder, editor
 Electronic Service Council of the Ozarks
 854 S. Glenstone
 Springfield, Mo.

RTA MAGAZINE
Chet Spink, editor
 Santa Clara Valley and Santa Cruz Chapter—CSEA (Old RTA)
 Orbit Publications
 Rm. 467A Porter Bldg.
 San Jose 13, Calif.

SUPREME EFFORT, THE
Harry H. Moore, editor
 TV Service Engineers, Inc.
 2114 E. 39 St.
 Kansas City 9, Mo.

T. E. A. TIMES
Leonard R. Smith, editor
 Texas Electronics Association, Inc.
 1105 May St.
 Fort Worth 4, Texas


TEAM NEWS
W. C. Pecht, editor
 The Electronic Association of Missouri
 718 Goodfellow
 St. Louis, Mo.

TESA BEACON
Frank Gronert, editor
 TV Electronic Service Association of Iowa
 5000 Urbandale Ave.
 Des Moines, Iowa

TESA MIAMI NEWS
A. Edward Stevens, editor
 TESA-Miami
 35 Almeria Ave.
 Coral Gables 34, Fla.

TESA NEWS, DAYTON AREA
Harry Hansen, editor
 TESA-Dayton Area
 6855 N. Dixie Dr.
 Dayton 14, Ohio

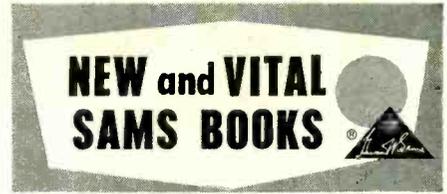TESA NEWS
Ken Garthe, editor
 TESA-St. Louis, Inc.
 5609 Riverview
 St. Louis 20, Mo.



101 Key Troubleshooting Waveforms for Horizontal AFC—Oscillator Circuits
 by Robert G. Middleton

First in a brand-new series by the author of the best-selling "101 Ways" books. Shows 101 abnormal waveforms (obtained when various circuit components become defective), accompanied by circuit symptoms, tests and evaluations of results. Supplementary notes provide background information. Covers the three most popular horizontal AFC-oscillator configurations: the multivibrator and blocking oscillator with pulse-width AFC, and the multivibrator with duo-diode AFC. With this book by your side you need never be puzzled by an abnormal waveform! 150 illustrations; 128 pages; 5 1/2 x 8 1/2". Only... **\$200**

Servicing Transistor TV Receivers
 by Milton S. Kiver and Charles R. Gray

Only book of its kind on this subject, timed with the appearance of the first transistor TV models. The authors introduce you to the transistor and to basic transistor circuits. Then, you are shown, one by one, how transistors are used in the tuner, video-IF amplifier, video-detector, video-amplifier, AGC, sound, sync-separator, and horizontal and vertical deflection sections. Includes data on the application of tube-set techniques; servicing differences between tube and transistor TV's; handling, testing and replacement of transistors; checking operating points, shorted and open transistors; plus special servicing pointers on specific sections, emphasizing horizontal-deflection systems. Illustrated; 272 pages; 5 1/2 x 8 1/2". Only... **\$450**

Experiments in Industrial Electronics
 by Melvin Whitmer

You learn how more than a dozen industrial devices work by actually sitting down and building them—the best way to learn a new skill. Projects are simple enough to appeal to the beginner, yet meaty enough to satisfy the most bench-hardened veteran. You'll build a photoelectric doorbell ringer, garage-door opener, burglar alarm, electronic time-welder control, electronic oven, flame detector and strain gauge, proximity detector (burglar alarm, store window novelty, thickness tester, etc.) that harnesses capacitance, DC motor control (including one for a portable turntable steady enough to satisfy even the wildest hi-fi fan) and a servo system. This valuable book can be your gateway to a profitable future in the fast-growing field of industrial electronics. 5 1/2 x 8 1/2". Only... **\$195**

JUST OUT

HOWARD W. SAMS REPLACEMENT GUIDE FOR TV & AUTO RADIO CONTROLS

Vol. 3. Greatly expanded—covers 27,000 TV and over 1,000 auto radio models. Lists recommended replacement controls of Controlab, Clarostat, IRC and Mallory. **\$100**
 8 1/2 x 11". Only.....

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. K-20 1720 E. 38th St., Indianapolis 6, Ind.

Send me the following books:

- "101 Key Troubleshooting Waveforms" (WFM-1)
- "Experiments in Industrial Electronics" (IEW-1)
- "Servicing Transistor TV Receivers" (KST-1)
- "Replacement Control Guide" (RGC-3)

\$.....enclosed. Send Free Book List

Name _____


Address _____

City _____ Zone _____ State _____

(Outside U.S.A. priced slightly higher)

with **DYNAKIT**
you know
you have the **BEST!**

COMING!
The New
DYNATUNER

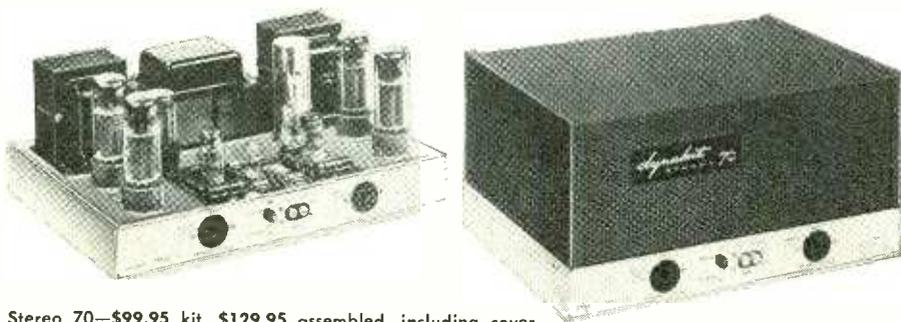

Stereo 70—\$99.95 kit, \$129.95 assembled, including cover

The DYNAKIT STEREO 70 is in a class by itself among high quality stereo power amplifiers, and no others can approach its unique combination of quality, reliability, simplicity and sheer listening pleasure for the discriminating audio buyer.

BEST IN EVERY WAY

Whether you purchase a kit, or prefer a factory wired and tested STEREO 70, you can be sure performance specifications will be met or exceeded in all respects. The basic DYNAKIT amplifier circuit, utilizing DYNACO's patented output transformers (worth one-half the cost of the kit) and other top quality components, yield an amplifier of uncompromised performance.

The two 35 watt amplifiers provide sufficient power for any need, in a compact, attractive package which you can assemble in one enjoyable evening. DYNAKIT's heavy duty pre-assembled etched circuits save you more than 2/3 of the effort, and provide an added measure of reliability for years to come. Detailed step-by-step instructions and large pictorial diagrams enable the kit builder to construct this amplifier with complete confidence even without previous experience.

It is not necessary to spend a lot of money to have the best sound available. DYNAKITS are designed to be the finest and to be used by those who are not satisfied with less than the best. The ultimate economy lies in sustained performance of equipment whose quality makes changes needless. We invite you to visit your high fidelity dealer and compare the DYNAKITS with the most expensive alternatives. Send us a postcard for complete specifications.

★ Finest Performance

35 watts continuous (80 watts peak) each channel at less than 1% distortion. Frequency response ± 0.5 db from 10 cps to 40 KC. Power response within 1 db of 35 watts without exceeding 1% distortion. Hum and noise more than 90 db below 35 watts (below audibility) due to choke filtered power supply. Superior square wave performance at any test frequency demonstrates its outstanding transient response and unconditional stability under any load. Perfect results are obtained with any dynamic or electrostatic loudspeaker. 1.3 volt sensitivity enables use with any preamplifier. Close tolerance components provide accurate stereo balance.

★ Most Conservative Operation

Output tubes operated at only 65% of capacity and filter capacitors at less than 85% of rated voltage. Highly efficient operation allows cooler running. Traditional DYNAKIT design makes possible a one-year guarantee, unique in the kit field, and seldom found on the most expensive amplifiers. In the words of one reviewer:

"This amplifier's components are operated more conservatively than those in any other commercial amplifier we have tested. . . Its power and distortion ratings are completely conservative. Its listening quality is unsurpassed."—H.H. Lab Report, *High Fidelity Magazine*, December, 1959.

★ Highest Quality Components

Matched EL34 output tubes, XXXP etched circuit boards, highest quality plastic molded capacitors and all premium grade resistors assure utmost reliability. Critical components are pre-assembled on the etched circuit board. Heavy plated 18 gauge bright nickel steel chassis for unparalleled structural rigidity. The cover, which is included, is finished in abrasion-resistant charcoal brown baked vinyl.

★ Patented Dynaco Circuit

The DYNACO-developed pentode-triode phase-inverter-driver and advanced-design feedback output stage minimize the number of phase-shifting stages, providing improved overload and stability characteristics by virtue of its implicit simplicity. Fewer stages mean lower distortion. Exclusive Dyna Biaset eliminates need for critical adjustments.

DYNACO, INC., 3916 POWELTON AVENUE, PHILA. 4, PA.
 CABLE ADDRESS: DYNACO, PHILA.

TECHNICIANS' NEWS (Continued)

TESA NEWS
Helen S. Bessert, editor
 TESA of Wisconsin
 PO Box 6091
 Milwaukee 7, Wis.

TSA-DV NEWS
Roy Fink, editor
 TV Service Association of
 Delaware Valley
 7819 Rugby St.
 Philadelphia 50, Pa.

TSA NEWS
Harold Chase, editor
 TV Service Association
 of Mich., Inc.
 8225 Woodward Ave.
 Detroit 2, Mich.

TSA SERVICE NEWS
Clinton W. Cox,
president
 King County TV Service
 Association, Inc.
 500 E. Pine
 Seattle 22, Wash.

TV SERVICE NEWSLETTER
Jack Massecar, editor
 Independent TV Service
 Dealers Association of
 Los Angeles County, Inc.
 213 S. Coronado St.
 Los Angeles 57, Calif.

VANGUARD, THE
Tony DeFranco, editor
 Tri-State Council of TV
 Service Associations
 4616 Westfield Ave.
 Camden, N. J.

ADVICE TO SET OWNERS

TV owners can save themselves trouble by carefully studying repair contracts before signing them, Attorney General Louis J. Lefkowitz of New York State believes. Mr. Lefkowitz, in an article in *TV Guide* magazine said that America has the finest technicians in the world, but there will always be "business sharpshooters." He advised set owners to do the following:

Don't permit your set to be taken from your home for repairs without receiving a written estimate of the repair cost.

Obtain written assurance that no additional repairs will be made unless you agree and that, if you do not wish the extra repairs, the set will be returned immediately.

Never sign a contract without reading it carefully.

Never sign a repair contract which contains blank spaces. Hundreds of people are victimized in this way every day.

Never sign a statement that work is done when it is not. You may have to pay for an unfinished job.

When dealing with an unknown repair service, check with your Chamber of Commerce, Better Business Bureau or technicians' association.

Mr. Lefkowitz cites one New York firm that victimized set owners of more than \$1,000,000 before being driven out of business. The company advertised that TV repair costs could be paid for with as little as 50 cents per week. Once the sets were in the shop, however, the customer was notified that a new picture tube was needed and a down payment of at least \$35 was required. The customer had no choice but to pay, without knowing if the tubes were really needed.

REFUSED MEMBERSHIP

The Electronic Service Association of Butte, Mont., voted to deny membership to a probationary member, Stuart A. Mayo. Grounds were price advertising in violation of the association's code of ethics, and violation of a membership resolution establishing a minimum service charge for house calls.

AD GIMMICK

TESA News of Wisconsin reports an interesting advertising gimmick being tried in Kansas City. The shop buys standby time from a local station. Whenever the station goes off the air because of technical troubles, it says (or words to this effect): "Don't call Ace TV, it's just TV station trouble." The shop has a flat rate, no matter how many times the station goes out.

[How much trouble does this station have?—Editor] END

new PATENTS

REGENERATIVE TRANSISTOR PAIR

Patent No. 2,864,062

Johannes S. Schaffner, Syracuse, N.Y. (Assigned to General Electric Co.)

This invention is a way of making a pair of junction transistors behave like a point-contact transistor. Readers probably know that the point-contact is an easy oscillator and can generate sine, square, pulse and sawtooth waves. A junction type is more rugged, efficient and easier to manufacture than the point-contact.

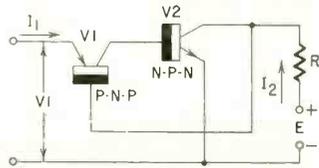


Fig. 1

Fig. 1 shows a p-n-p transistor (V1) directly coupled to an n-p-n unit (V2). Its input characteristic is drawn in Fig. 2. This idealized "curve" has three distinct regions.

With negative input current (I_1) V1 blocks and no current flows into V2's base. The input resistance is that of a reverse-biased diode (V1 emitter-base) which is positive and large. See region I.

Both transistors conduct when I_1 is positive. Note that V2's collector current (I_2) is greater than I_1 and is opposite in direction. V1, which is

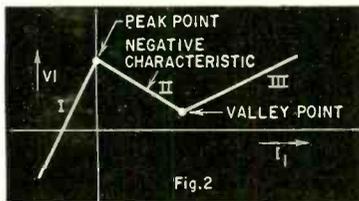


Fig. 2

equal to $E - I_2R$, goes down as I_1 rises. This is negative resistance as shown in region II.

Very large I_1 results in a large voltage drop across R. Due to the low potential difference between V2's collector-emitter, this transistor ceases to function. The input resistance is now

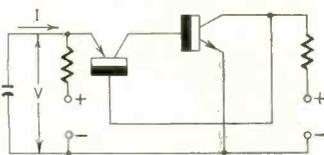


Fig. 3

that of a positive biased diode (V1 emitter-base) and is positive and small. Refer to region III.

Fig. 3 shows a free-running oscillator. The operating point is chosen so that the negative-resistance region corresponds to zero input current. For more data see story on page 51.


DEFLECTION CORRECTION

Patent No. 2,936,400

Thomas H. Tatham, Jr., San Diego, Calif. (Assigned to General Dynamics Corp., Rochester, N.Y.)

When an oscilloscope is used for precise measurement or display, its deflecting plates must be positioned accurately. If they slant (see diagram), the resulting display will slant likewise. If the plates are distorted, the error may be corrected by this external circuit.

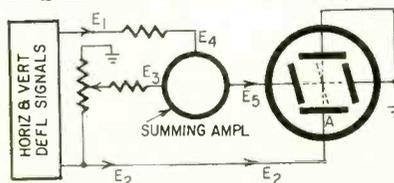E_1 is the horizontal deflecting voltage, E_2 the



OXFORD
... the Leader

WALTZ ME AROUND AGAIN, WILLIE!

A phase aimed for increasing your profits. Since the original equipment manufacturer demands speakers to the most exacting electrical characteristics . . . and demands OXFORD . . . WHY DON'T YOU? Oxford, major suppliers for original equipment provides the finest replacement speakers for any and every application. A complete line for your every need.

OXFORD SPEAKERS
... Preferred for original equipment,
Proven for replacement.
Our catalog is available upon request.

OXFORD Components,
A Division of Oxford Electric Corp.
556 West Monroe St., Chicago 6, Illinois

Oxford Speakers are available from recognized electronic parts distributors.

FREE

ask your
hi-fi
dealer


for



audio empire
STEREO/BALANCED HIGH FIDELITY COMPONENTS DYNA-EMPIRE, INC.
1075 STEWART AVE., GARDEN CITY, N. Y.
EXPORT: EMEC, PLAINVIEW, N. Y.
CANADA: ACTIVE RADIO & TV LTD., TORONTO 2, ONT.

all new edition
up-to-date
component prices

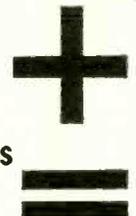PLUS
the quick easy way
to figure service charges
EQUALS



Pure Riee's
OFFICIAL PRICING DIGEST



VOL. 4, NO. 1

Flat rate and hourly service charges, based on and showing regional and national averages, plus up-to-date list or resale prices on over 63,000 components. Arranged alphabetically by manufacturers and products, numerically by part number. Compact, convenient size fits in tube caddy, toolbox or pocket. \$2.50 per copy from your distributor.

ELECTRONIC PUBLISHING COMPANY, INC.
180 N. WACKER DRIVE, CHICAGO 6, ILL.

WORLD FAMOUS
MOHAWK MIDGETAPE PROFESSIONAL 500
HIGH SPEED
POCKET TAPE RECORDER



Used by NBC - CBS
and numerous radio and TV
stations, for recording
in the field.

Records anything it hears and
plays it right back in
unbelievable broadcast quality.

Special built-in "VU Meter".
Weighs only 3 lbs.

**THE PEER OF POCKET
TAPE RECORDERS...
MIDGETAPE IS
AMERICAN MADE.**

"Scienca Fiction" accessories
available for confidential
recordings.

For literature on model 300...400...500
write Dept. RE.

ALL TRANSISTORIZED

Mohawk...
business machines corp.
944 halsey street brooklyn 33, new york
manufacturers

NEW PATENTS (Continued)

vertical. A fraction of E2 is combined with E4 at the amplifier. E5 is the corrected horizontal deflection voltage.


Consider the display of a vertical line which, due to plate misalignment, will slant. When the trace is at the top, plate A must be negative with respect to ground. Therefore E3 is also negative, and E5 must be more negative than E1. Thus the beam is repelled toward the right.

When the trace is at the bottom, A is positive. This means that E5 will be more positive than E1, and the beam will be attracted more to the left. It is obvious from this discussion that the display will be more vertical than it would otherwise be. R is adjusted as required for complete correction.

ELECTRIC BLANKET COOLS
Patent No. 2,938,356

Howard O. McMahon, Lexington, Mass. (Assigned to Arthur D. Little, Inc., Cambridge, Mass.)

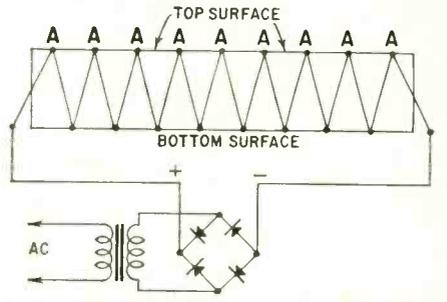According to this invention, blankets, flying suits, apparel or bedding can be used to cool the body. It utilizes junctions of dissimilar metals or semiconductors passing direct current. These junctions are cooled when current flows



in one direction, heated when the current is reversed. The principle is known as the Peltier effect.

The diagram shows how junctions (A) terminate at an upper surface made of nonconducting material such as fiber. This surface will be cooled. The other surface, contacted by the remaining junctions, will be heated.


The inventor recommends that the junction be made of a metal and a semiconductor, and he lists several suggested junctions in the patent.

TRIPLE TRANSISTOR
Patent No. 2,936,384

John R. White, Westbury, N. Y. (Assigned to Hazeltine Research, Inc.)

Here are three transistors formed of a single crystal. There are five layers, with a slot cut across the top. The lower p-n-p transistor is labeled V1. V2 is at the upper left, V3 at the upper right. V1's collector is also emitter for V2 and V3, for direct coupling.

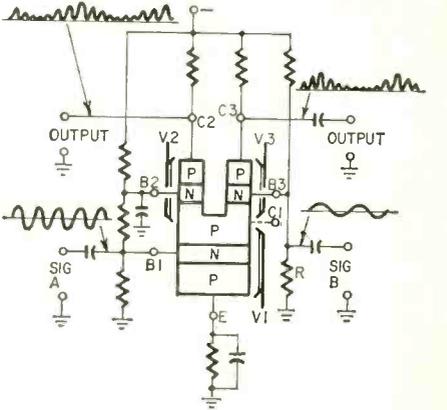A modulator using this unit is shown. The bases of V1, V2 are biased from a voltage divider. V3's base returns to ground through R. Output may be taken from the collector of V2 or V3.



Assume that the output is taken from V3. The output frequency is that of signal A, while signal B controls its amplitude. As B goes negative, it biases V3 for greater conduction and output. V3's emitter potential follows the potential of its base. Since V2's base voltage is held constant and its emitter has gone more negative, it is evident that V2's output goes down when B goes negative.

The inventor likens this device to a 6AR8 double-plate sheet-beam tube. Both are suitable for various switching and gating applications and permit push-pull output.

AT ELECTRONIC PARTS JOBBERS



2 FOR 1
DC
POWER SUPPLY

1... operates ALL auto radios
—transistor, hybrid, tube—

2... operates miniature radios
—transistor portables—

... also operates experimental transistor circuits, relays, use it for electroplating, laboratory work.

- Transistor protection.
- EPL patented cooling.

2 OUTPUT RANGES

VOLTS	CURRENT	RIPPLE
0-16	5 amps.	0.5%
0-20	75 ma.	0.15%

Compare and you'll
buy Model PS-2 **\$4995**

Also—Kit Model KPS-2...\$43.50

Send for FREE literature, name of your jobber!

Electro Products Laboratories
4501-R Ravenswood, Chicago 40, Ill.

Name _____
Address _____
City _____ Zone _____ State _____

Television
RADIO-ELECTRONICS
Electricity
ELECTRONICS
IN NEW SHOP-LABS OF **COYNE**

**TRAIN QUICKLY! OLDEST, BEST
EQUIPPED SCHOOL of ITS KIND in U.S.**

Get practical training in New Shop-Labs of Coyne. Prepare for a better job and a successful future in a top opportunity field. Advanced education or previous experience not needed. Employment service to graduates.

Enroll NOW—Pay Later

Finance Plan and Easy Payment Plan. Also Part Time Employment help for students.

FREE BOOK Clip coupon or write to address below for Free Illustrated Book. "Guide to Careers"—Describes all training offered. No obligation and No Salesman Will Call. Act NOW.

B. W. Cooke, Jr., President

COYNE
ELECTRICAL SCHOOL
1501 W. Congress Pkwy.
Chicago, Dept. 6C


Use this coupon to get our free book
"GUIDE TO CAREERS"

COYNE ELECTRICAL SCHOOL training at Coyne
1501 W. Congress Pkwy.
Chicago 7, Ill. Dept. of Electronics 6C training at home

NAME _____
ADDRESS _____
CITY _____ STATE _____

Unlike most other schools, we do not employ salesmen.

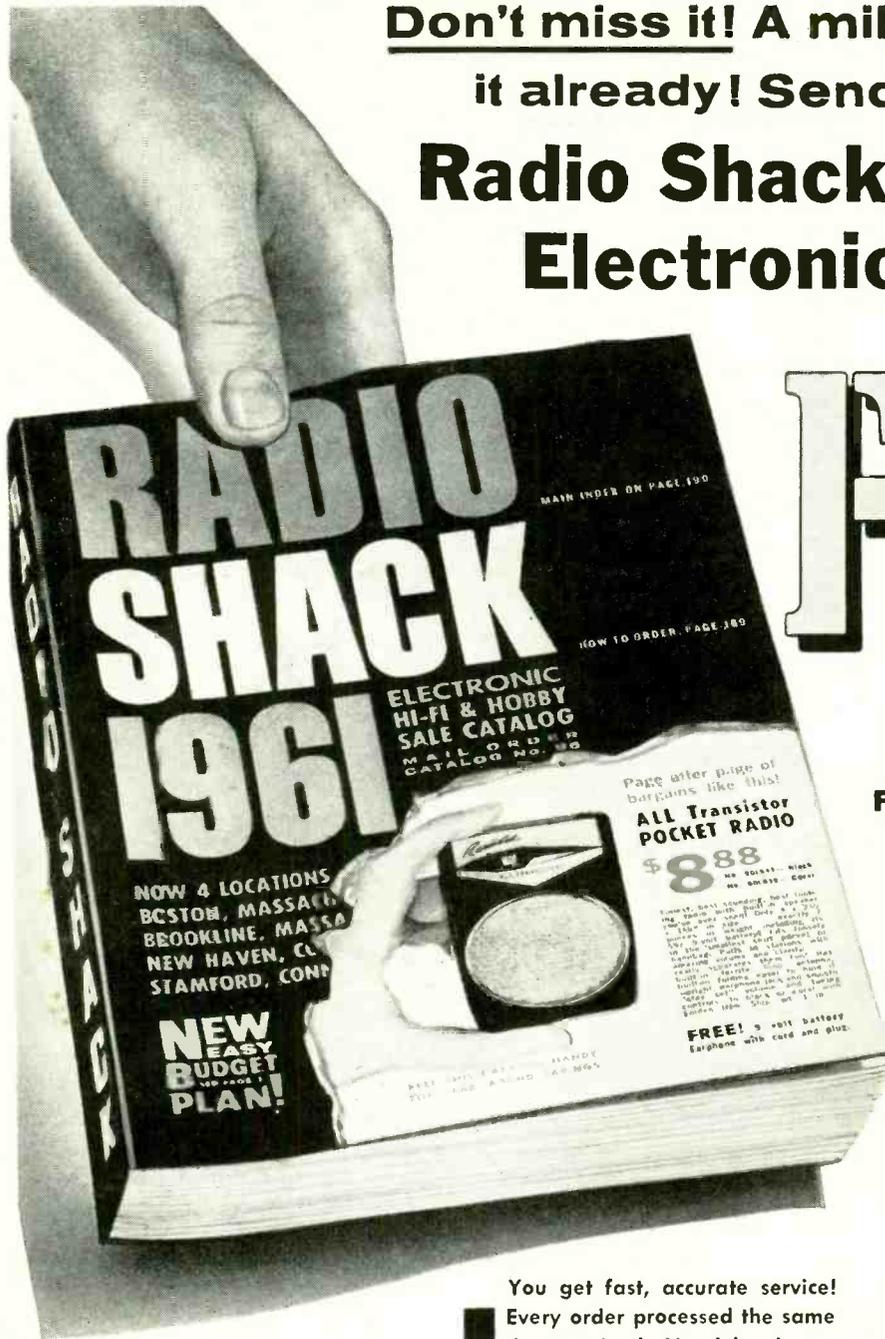Don't miss it! A million have sent for it already! Send for your copy of Radio Shack's new 1961 Electronics CATALOG



FREE

Plus a full year's FREE SUBSCRIPTION to all other Radio Shack Catalogs as issued

Save up to 50% all year long on the latest and best items in the whole fascinating field of Electronics.

See the world's biggest line of Stereo, Hi-Fi, Ham Radio, Transistors, Test Equipment, Kits and Parts, scores more.

You get fast, accurate service!
 Every order processed the same day received. No delays!

You can pay as you earn on Radio Shack's Easy Budget Plan. Low as \$2.00 down.

You can open a convenient Monthly Charge Account. "Add-on" orders are easy.

GUARANTEE: Radio Shack guarantees you must be satisfied with any item you order or your money back. 15-day no-risk home trial on any item!

RADIO SHACK

Corporation

730 Commonwealth Avenue
 Boston 17, Massachusetts



MAIL COUPON TODAY

RADIO SHACK CORPORATION Dept. 60K10
 730 Commonwealth Ave., Boston 17, Massachusetts


Without obligation, please send me FREE AND POST-PAID, your latest giant Electronics Catalog plus every new issue for one full year.

Name _____

Address _____

Post Office _____ Zone _____ State _____
 or City _____

V. H. F. TELEVISION TRANSLATORS

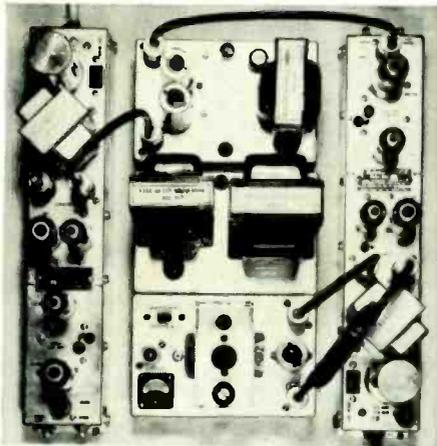

Complete — aligned and assembled. Ready to install on your new system or as a replacement for older systems. A complete high output amplifying system with conversion. The RX-17A uses two BT proven quality MCS Amplifiers with M.A.R.S. Converter CX-30A and Metered Final (F-17A). The system is capable of one watt PLUS output with as little as 50 microvolts input. The usual range of automatic gain control enables complete pre-adjustment to accommodate ANY useable signal level.

Metered output eliminates guesswork for fast — efficient operation. Automatic Cut Off (available). Code Identifier (available).

AVERAGE VALUE SPECIFICATIONS:

Gain: 110-120 DB.
Conversion Accuracy: Up to .0025%.
AGC: 40 DB plus.
Input Range: 50 to 5000 Microvolts.
Output: One Watt Plus.
Power: 115 Volts AC 60 Cycle (140 Watts).
Cables: Low loss input and output cables and baluns to match 300 OHM are included.

**For Full Information Write
Mid America Relay Systems, Inc.**

*Serving the Television World
from the Heart of America*

GENERAL SALES
601 Main Street

Rapid City, South Dakota

INTERNATIONAL DIVISION
Rocke International Building
13 East 40th Street

New York 16, N. Y., U. S. A.
Cables "ARLAB" N. Y. All Codes



LOOP OILER


A small narrow loop of thin wire makes an excellent oiler for carrying a small amount of oil into a tight spot and not elsewhere. Such a device may be made from a strand of stranded wire soldered to a heavier piece of wire. The loop should be rather small—not more than about five wire diameters across or the oil will not form a film.

In practice, the loop picks up a drop of oil from the nozzle of an oil can. It is touched to the point to be lubricated and twisted slightly so the oil flows on the part from the loop.—*L. Shaw*

SOLDERING-IRON CLEANER

A piece of fine screening tacked to a scrap piece of wood makes a fine scratchboard for a soldering iron.

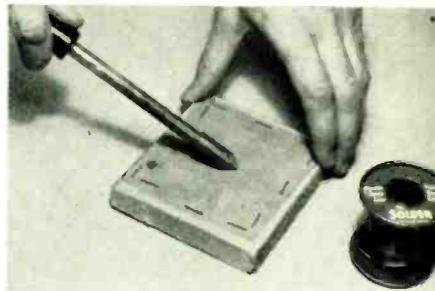Wiping the iron's tip across the screen occasionally removes excess drops of



solder and crust from the tip efficiently.
—*Charles A. Cunningham*

TESTING AT TOP OF SOCKET

The tips of ordinary test prods won't fit into the pin holes of miniature tube sockets. This is a definite handicap when you want to check voltages from the top of the chassis rather than from underneath. To overcome this handicap, file or grind the ends of your prods to fit. You'll have to make them smaller and more pointed.—*Albert Mason*

NEW FLOCK FOR TURNTABLE

Have you ever tried to pry the C washer off the spindle on a record player only to have the screwdriver slip and run a gash across the face of the turntable? With a little time and patience such an accident can be remedied with no one the wiser.


For An Important
Message Concerning
Your Career
In Electronics
See Page 69

Write for complete details about the Gernsback Technicians' and Hi-Fi Book Club Plans.

Gernsback Library, Inc.
154 West 14th St. New York 11, N. Y.

DX-16 Super Deluxe TV KIT

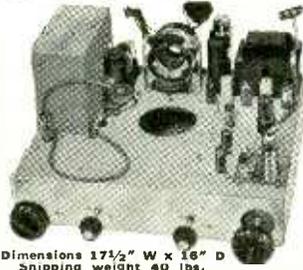70° or 90° — operating all 17", 21", 24" and 27" PICTURE TUBES



Dimensions 17 1/2" W x 16" D
Shipping weight 40 lbs.


- ★ Produces a 16-Tube Chassis with 30-Tube performance.
- ★ Latest Inter-carrier Circuitry and Multi-section Tubes.
- ★ Standard Neutrode Tuner for Selectivity & Fine Definition.
- ★ All Video and I.F. Coils factory pre-aligned and tuned.
- ★ Large 250ma Power Transformer for dependable service.
- ★ 12" Speaker or Twin-cone 6" x 9" Speaker.

Includes **LIFE-SIZE** step-by-step Building Instructions
Most Up-To-Date and Practical Course in Television

COMPLETE KIT
with SET of WESTINGHOUSE TUBES \$93.49

4-6CB6, 6U8, 6T8, 6T4, 12BH7, 6SN7, 6B06, 6W4, 6K6, 1X2B, 5U4. 6BN4, 6GC8, incl. in the Tuner (CRT)

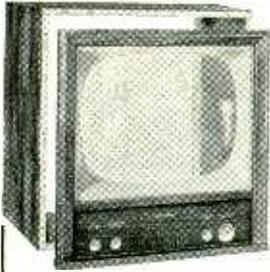Also sold on **EASY-PAYMENT-PLAN** Buy LIFE-SIZE Instructions—\$2.49—and buy PARTS as you build.



23" TV Cabinet Kit . . \$28.47 24" or 27" TV Cabinet Kit . . \$38.47 24" or 27" Front Panel Assembly . . \$24.97

BUILD YOUR OWN CABINET FOR ANY TV CHASSIS

Comparable to the type that Top Mfrs. use on high priced TV sets.

CABINET KIT with 90% of the job done, includes—
FRONT SECTION in Solid Mahogany, Walnut or Blond Korina. **TOP, SIDES, BACK, MASK, SAFETY GLASS, ETC.**
And **EASY-TO-FOLLOW ASSEMBLY INSTRUCTIONS**

Front, Top and Sides supplied in a beautiful Piano Finish • Knob panel undrilled • For matching Mask specify type or number of CRT used. Same price—Mahogany, Walnut or Blond. (Shipping weight 36 lbs.)

21" CABINET KIT 26"H, 25"W, 22"D \$26.97

"ONE DOLLAR" Buys

As much as \$15 worth — Everything Brand New and sold to you with a money back guarantee.

DEDUCT 10% ON ANY ORDER OF \$10 OR OVER

(ON DOLLAR BUYS)

Plus a **FREE SURPRISE PACKAGE**

- 100 — ASST. 1/2 WATT RESISTORS some 5¢ . . \$1
- 70 — ASSORTED 1 WATT RESISTORS \$1
- 35 — ASSORTED 2 WATT RESISTORS \$1
- 50 — ASST. TUBULAR CONDENSERS \$1
- 50 — ASSORTED FUSES popular sizes \$1
- 50 — 100Ω 1/2 WATT RESISTORS 10% \$1
- 75 — 470KΩ 1/2 WATT RESISTORS 10% \$1
- 100 — ASST. CERAMIC CONDENSERS \$1
- 10 — ASST. WIRE'ND. RES. 5, 10, 20 watt \$1
- 100 — MICA CONDENSERS 1000mmf-500v \$1
- 10 — HV TUBULAR CONDENSERS .005-6000v \$1
- 35 — ASST. DISC CERAMICS best numbers \$1
- 50 — ASST. MICA CONDENSERS some in 5¢ \$1
- 6 — ASST. SLIDE SWITCHES \$1
- 4 — BAKELITE KNIFE SWITCHES \$1
- 3 — ASST. TOGGLE SWITCHES \$1
- 15 — ASST. ROTARY SWITCHES \$15 worth \$1
- 100' — FINEST NYLON DIAL CORD best size \$1
- 200 — SELF TAPPING SCREWS #8 x 1/2" \$1
- 35 — ASST. RADIO KNOBS screw and push-on \$1
- 100 — ASSORTED KNOB SET-SCREWS \$1
- 25 — ASSORTED CLOCK RADIO KNOBS \$1
- 600 — ASST. H'DWARE screws, nuts, rivets, etc. \$1
- 35 — ASST. SOCKETS octal, noval and miniature \$1
- 25 — ASST. PRINTED CIRCUIT SOCKETS \$1
- 10 — ASST. VOLUME CONTROLS less switch \$1
- 5 — ASST. VOLUME CONTROLS with switch \$1
- 20 — ASST. PILOT LIGHTS popular types \$1
- 10 — PILOT LIGHT SKTS. bayonet type, wired \$1
- 50 — ASST. TERMINAL STRIPS 1, 2, 3, 4 lug \$1
- 10 — ASST. RADIO ELECTRO. CONDENSERS \$1
- 5 — ASST. TV ELECTROLYTIC CONDENSERS \$1
- 25 — ASST. MICA TRIMMER CONDENSERS \$1
- 15 — TUBULAR CONDENSERS .47-400v \$1
- 15 — TUBULAR CONDENSERS .1-600v \$1
- 6 — TV ION TRAPS standard for all CRT's \$1
- 15 — TUBULAR CONDENSERS .047-600v \$1
- 2 — ELECTROLYTIC COND. 40/40-450v \$1
- 3 — ELECTROLYTIC COND. 50/30-150v \$1
- 25 — ASST. PEAKING COILS popular types \$1
- 1 — ELECTRIC PHONO MOTOR 78rpm 110v \$1
- 1 — RCA FLYBACK TRANSFORMER #21111 \$1
- 300 — ASST. 1/2W RESISTORS short leads \$1
- 4 — TV CENTERING RINGS \$1
- 35 — DISC. CERAMIC CONDENSERS 500mmf \$1
- 25 — ASST. RADIO DIAL POINTERS \$1
- 8 — ASST. LUCITE CASES handy for parts \$1
- 100 — MICA CONDENSERS 820mmf-500v \$1
- 3 — ASST. SIZES RADIO CHASSIS PANS \$1
- 3 — VARIABLE CONDENSERS super 420, 162mf \$1
- 4 — OVAL LOOP ANTENNAS ass't hi-gain types \$1
- 3 — LOOPSTICK ANT. new ferrite adjustable \$1
- 3 — 1/2 MEG VOLUME CONTROLS with switch \$1
- 5 — 50K VOLUME CONTROLS less switch \$1
- 5 — ASST. 4 WATT WIREWOUND CONTROLS \$1
- 5 — 1/2 MEG VOLUME CONTROLS with switch \$1
- 5 — 1 OR 2 MEG VOLUME CONTROLS 1/switch \$1
- 100 — VOLUME CONTROL HEX NUTS \$1
- 10 — SURE GRIP ALLIGATOR CLIPS \$1
- 1 — GOLD GRILLE CLOTH 14"x14" or 12"x18" \$1
- 5 — SETS SPEAKER PLUGS wired \$1
- 10 — SETS PHONO PLUGS and PIN JACKS \$1
- 2 — \$2.50 SAPPHIRE NEEDLES 4000 playings \$1
- 5 — DIODE CRYSTALS 2-IN21 2-IN22 1-IN64 \$1
- 3 — DIODE CRYSTALS 1-IN60 1-IN64 1-IN69 \$1
- 4 — DIODE CRYSTALS IN34A \$1
- 35 — MICA COND. 20-50 mmf & 15-68 mmf \$1
- 35 — MICA COND. 20-100 mmf & 15-270 mmf \$1
- 35 — MICA COND. 20-470 mmf & 15-680 mmf \$1
- 35 — MICA COND. 20-820 mmf & 15-1000 mmf \$1
- 35 — MICA COND. 20-2200 mmf & 15-2400 mmf \$1
- 35 — MICA COND. 20-6800 mmf & 15-10000 mmf \$1
- 35 — CERAMIC COND. 20-5 mmf & 15-10 mmf \$1
- 35 — CERAMIC COND. 20-25 mmf & 15-47 mmf \$1
- 35 — CERAMIC COND. 20-56 mmf & 15-82 mmf \$1
- 35 — CERAMIC COND. 20-100 mmf & 15-150 mmf \$1
- 35 — CERAMIC COND. 20-270 mmf & 15-470 mmf \$1
- 35 — CERAMIC COND. 20-1000 mmf & 15-1500 mmf \$1
- 35 — CERAMIC COND. 20-200 mmf & 15-3000 mmf \$1
- 4 — KENRAD TUBES #65H7 \$1
- 2 — TOP NAME #65Q7 TUBES \$1
- 2 — TOP BRAND TUBES #35W4 \$1

TOP NAME TUBES 024, 1B3, 1X2B, 5U4, 6AC7, 6AX4, 6CB6, 6J6, 6K6, 6U8, 6V6, 6SN7, 6X8, 12AU7, 12AX7, 50L6 Each \$1

3 — TV ALIGNMENT TOOLS assortment = 1 . . . \$1

3 — TV ALIGNMENT TOOLS assortment = 2 . . . \$1

3 — TV ALIGNMENT TOOLS assortment = 3 . . . \$1

3 — TV ALIGNMENT TOOLS assortment = 4 . . . \$1

3 — TV ALIGNMENT TOOLS assortment = 5 . . . \$1

EACH ALIGNMENT TOOL is different and valued at over \$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (X in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for re-orders.

ON SMALL ORDERS—Include stamps for postage, express will be refunded. Larger orders shipped express collect.

TECH-MASTER for 1961 ★ "GOLD MEDAL" #2430-B

WORLD'S MOST POWERFUL TV CHASSIS

COMPLETE ready to operate (less CRT) 90° \$175.85 • 110° \$182.60 *Catalog on request*

TUBULAR CONDENSERS—85°C TOP QUALITY—Equally as good for Radio or TV work
.0047-400v, .01-400v, .02-400v, .047-400v, .001-600v, .0047-600v, .01-600v, .02-600v, .03-600v 5¢ ea.
.1-400v, .25-400v, .47-400v, .047-600v, .1-600v, .25-600v, .001-1000v, .0047-1000v, .01-1000v, 8¢ ea.
.039-1000v, .047-1000v, .1-1000v, .007-1600v, .03-1600v, .05-1600v, .005-3000v, .001-6000v, 14¢ ea.

ELECTROLYTIC CONDENSERS—85°C 1-50v, 1-150v, 2-350v, 25-50v, 8-150v 19¢ ea.
20/20-150v, 50/30-150v, 40-150v, 10-450v, 20-450v, 30-450v, 40-450v, 60-450v, 80-450v 34¢ ea.

CARBON RESISTORS—Regular factory stock in Stackpole, Speer, etc.
1/2 WATT 10% 10, 39, 47, 100, 120, 150, 270, 330, 390, 470, 560, 680, 820, 1k, 1800k 2¢ ea.
1/2 WATT 10% 2700, 3300, 3900, 4700, 5600, 6800, 8200, 10k, 15k, 18k, 22k, 27k, 33k 2¢ ea.
1/2 WATT 10% 39k, 47k, 50k, 56k, 68k, 82k, 100k, 120k, 150k, 180k, 220k, 270k, 330k 2¢ ea.
1/2 WATT 10% 390k, 470k, 560k, 680k, 820k, Ω 1, 1.2, 1.5, 2.2, 6.8, 10, 15 MEGΩ 2¢ ea.
1 WATT 10% 3.3, 10, 39, 100, 120, 150, 330, 470, 560, 680, 820, 1k, 1800, 2700, 4700 3¢ ea.
1 WATT 10% 6800, 10k, 15k, 18k, 22k, 27k, 33k, 39k, 47k, 68k, 82k, 100k, 150k, 470k, 680k 3¢ ea.
2 WATT 10% 18, 22, 82, 100, 180, 2200, 3900, 4700, 6800, 8200, 18k, 22k, 100k, 470k 4¢ ea.

WIREWOUND RESISTORS 5-5w, 16-10w, 20-10w, 47-5w, 100-5w, 140-5w, 220-5w. 16¢ ea.
280-10w, 390-5w, 470-5w, 500-10w, 680-10w, 820-5w, 1K-5w, 1K-10w, 1500-5w, 2K-10w 16¢ ea.
2500-5w, 3K-10w, 4700-5w, 5K-10w, 6K-10w, 7K-10w, 8200-5w, 10K-5w, 15K-5w, 22.5K-12w 16¢ ea.

CERAMIC CONDENSERS 1, 2, 3, 5, 6, 10, 22, 25, 47, 50, 51, 56, 82, 100, 120, 150 mmf 3¢ ea.

CERAMIC CONDENSERS 220, 250, 270, 330, 470, 1k, 1200, 1500, 2k, 5k, 6800, 10k mmf 3¢ ea.

MICA CONDENSERS 5, 25, 50, 60, 68, 75, 100, 120, 150, 220, 270, 330, 470, 510 mmf 3¢ ea.

MICA CONDENSERS 560, 680, 820, 1k, 1500, 2k, 2500, 3300, 4700, 6k, 6800, 8k, 10k mmf 3¢ ea.

- 1 — 5" PM SPEAKER alnico #5 magnet \$1
- 1 — 4" PM SPEAKER alnico #5 magnet \$1
- 1 — 3" PM SPEAKER alnico #5 magnet \$1
- 1 — 3 1/2" TWEETER SPEAKER for HI-FI \$1
- 3 — AUDIO OUTPUT TRANS. 50L6 type \$1
- 3 — AUDIO OUTPUT TRANS. 6K6 or 6V6 type \$1
- 3 — I.F. COIL TRANSFORMERS 456 kc \$1
- 3 — I.F. COIL TRANSFORMERS 10.7 mc. FM \$1
- 3 — I.F. COIL TRANSFORMERS 262 kc (auto) \$1
- 40 — ASST. PRECISION RESISTORS best sizes \$1
- 5 — SELENIUM RECTIFIERS 65ma list \$1.50 ea. \$1
- 4 — SELENIUM RECTIFIERS 75ma \$1
- 3 — SELENIUM RECTIFIERS 150ma \$1
- 3 — SELENIUM RECTIFIERS 250ma \$1
- 2 — SELENIUM RECTIFIERS 300ma \$1
- 2 — SELENIUM RECTIFIERS 1-450ma 1-65ma \$1
- 10 — TV CARTWHEEL CONDENSERS 10kv \$1
- 3 — TV CARTWHEEL CONDENSERS 20kv \$1
- 2 — TV CARTWHEEL CONDENSERS 30kv \$1
- 1 — TV RATIO DETECTOR COIL 4.5mc \$1
- 1 — TV RATIO DETECTOR COIL 10.7mc \$1
- 1 — TV SOUND I.F. COIL 4.5mc \$1
- 3 — HV RECTIFIER SOCKETS 1B3 m'nted \$1
- 3 — HV RECTIFIER SOCKETS 1X2 m'nted \$1

10-TUBES #104..\$1

- 1 — LB. SPOOL ROSIN CORE SOLDER \$1
- 4 — 50' SPOOLS HOOK-UP WIRE 4 colors \$1
- 10 — 6' ELECTRIC LINE CORDS with plugs \$1
- 5 — TV CHEATER CORDS with both plugs \$1
- 5 — TV CRT. SOCKETS with 18" leads \$1
- 5 — HI-VOLT. ANODE LEADS with 18" leads \$1
- 50 — STRIPS ASST. SPAGHETTI best sizes \$1
- 100 — ASST. RUBBER GROMMETS best sizes \$1
- 100' — TWIN LEAD-IN WIRE 300Ω heavy duty \$1
- 50' — FLAT 4-CONDUCT. WIRE many purposes \$1
- 25' — INSULATED SHIELDED WIRE \$1
- 32' — TEST PROD WIRE deluxe (red or black) \$1
- 1 — 57 INDOOR TV ANTENNA hi-gain 3 section \$1
- 20 — ASST. TV KNOBS, ESCUTCHEONS, Etc. \$1
- 1 — RCA 70° FLYBACK TRANS. #75240 \$1
- 1 — TV VERT. OUTPUT TRANS. 10 to 1 ratio \$1
- 15 — ASST. TV COILS sync, peaking, width, etc. \$1
- 15 — ASST. STANDARD TUNER VHF STRIPS. \$1
- 6 — ASST. STANDARD TUNER UHF STRIPS. \$1
- 2 — SILICON RECTIFIERS 500ma \$1
- 1 — SILICON RECTIFIER 750ma \$1


BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y. TELEPHONE: COrtland 7-2359

Now! SOLVE CIRCUIT PROBLEMS FAST!

Goodbye to trial-and-error methods. Every circuit calculation you need can now be done accurately with

THE ALGEBRA OF ELECTRONICS

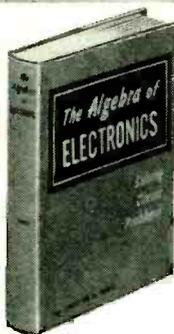YOU'LL BE AMAZED at how easy it is to figure resistances, load inductances, impedances, etc. for ANY part of ANY electronic circuit. With this new book, THE ALGEBRA OF ELECTRONICS, you will quickly gain the tools, techniques and shortcuts needed.



Three Great Books in One!

First, it's a textbook. All practical mathematical techniques explained clearly step-by-step; easy to follow by those with no more math training than high-school algebra and simple differential calculus.

Second, it's a handbook. Graphs and tables answer common electronic problems for those not wishing to work out complex derivations themselves.

Third, it's a review. Every equation is discussed, along with its practical on-the-job applications. 100 problems are shown with methods and answers provided.

THE ALGEBRA OF ELECTRONICS was written by Chester H. Page, Consultant to the Director of the National Bureau of Standards. Dr. Page discusses basic laws and fundamental principles, practical method of solving simultaneous equations. He develops elementary Fourier wave-form analysis, shows effects of frequency selectivity, modulation, and analyzes tubes, transistors and power supplies.

Try It FREE for 10 Days

Whether you're a repairman, technician, or engineer, you'll find THE ALGEBRA OF ELECTRONICS both profitable and interesting. Send coupon for a FREE 10-DAY EXAMINATION. No obligation — unless you want to keep the book. Mail coupon today to

Van Nostrand
Dept. 1810A, Princeton, N.J.
Established 1848

127 TOPICS


- 340 Pages
- 252 Illustrations
- Nonlinear Resistance
- Network Topology
- Mesh Currents
- Kirchoff's Law
- Voltage Variables
- Triangularization
- Simultaneous Equations
- Kramer's Rule
- Thevenin's Theorem
- Wheatstone Bridge
- Conjugacy
- Black-Box Variables
- Image Impedances
- Attenuators
- Capacitance
- Dielectrics
- Sinusoidal Voltage
- Energy Storage
- Series-Tuned Circuits
- Series Resonance
- Complex Phasors
- Mutual Inductance
- Transformers
- Critical Coupling
- F-M Discriminator
- Impedance Matching
- Hyperbolic Functions
- Diodes
- Amplifiers
- Transistors
- Thermal Noise
- Demodulation — many more

TRY THIS ONE (Continued)

First scrape some flocking off the rim of the turntable with a penknife. In most cases the turntable is set down in a well and the rim is out of view. Next, carefully apply some general-purpose cement to the gash and brush on some of the flocking. If this is done neatly, once the cement is set you will never know the difference.—Frank A. Salerno

TRANSISTOR LIFE SAVER

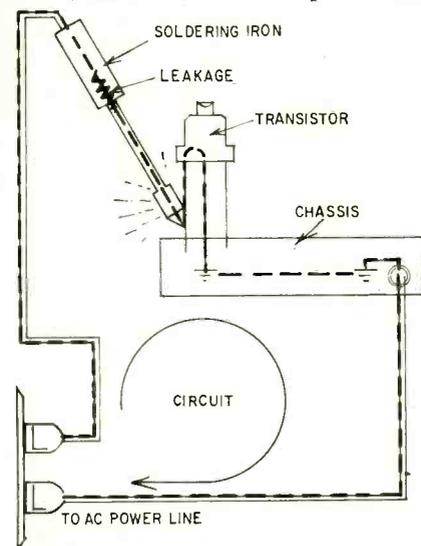Before you start to solder a transistor into a radio-TV or other electronic device, disconnect the set's power cord.




If the set is connected when you touch the tip of your iron to the transistor lead, you may ruin the component. This happens if there is leakage from the tip to the power line inside the iron or gun. The current path is from the power line, through the iron's tip, through the transistor, to chassis ground, and back to the power line. Though the diagram shows an ac-dc set, the same type of thing can also ruin transistors in sets that have a power transformer.—J. C. Alexander

PLASTIC TV KNOBS

The TV technician installing a chassis in the cabinet after an initial repair job often finds the plastic knobs so worn that they refuse to stay on the knurled shafts. Attempts to shrink the plastic with a soldering gun usually result in a messy, loose knob. At best, some technicians jam the knobs on the shafts, using wood or plastic tape to provide the necessary grip. These methods are sometimes effective, but not very permanent. An alternative method that works calls for simply slipping the proper type of insulating spaghetti tubing into the oversize knob hole, using a little cement to hold it in place, then fitting the knob on the shaft.

Walsco Flexitube spaghetti, a polyethylene type, or Alphlex PVC-105 seem best for this purpose. Either may be purchased in various sizes.—George D. Philpott

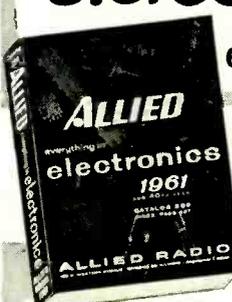SAVE on everything in stereo hi-fi and electronics



send for the 1961

ALLIED CATALOG

free

444-PAGES • VALUE PACKED. Write today for the leading Electronics Catalog. World's largest selection, including products and values available only from ALLIED. SAVE ON:

- Everything in Hi-Fi Music Systems & Components
- Biggest Selection of Hi-Fi Cabinetry
- Exclusive Knight® Super-value Stereo
- Knight-Kits®—Best in Build-Your-Own Hi-Fi
- Tape Recorders and Phono Equipment
- Everything in Electronic Parts, Tubes, Transistors, Test Equipment, Amateur Gear, P.A. Systems, TV Accessories, Tools, Books.

Save most at ALLIED. Write for FREE 1961 Catalog today!

ALLIED RADIO

100 N. Western Ave., Chicago 80, Ill.

Send FREE 1961 ALLIED Catalog.

Name _____

Address _____

City _____ Zone _____ State _____

CITIZENS BAND EQUIPMENT

Check Power Output, Standing Waves Cosco Transcheck. Gives meter indication of power output. VSWR. Ideal for transmitter tuning. Specify auto splice or PT-259 type coax connector. **\$20.95** Postpaid

Eliminate Generator Whine Cosco Generator Filter. Eliminates generator whine in mobile installations. Tunable for maximum attenuation. Most effective generator noise filter made. Also available for other frequencies. **\$3.00** Postpaid

Duopole Groundplane Base Antenna Rugged, tuned CB antenna with 1 to 1 VSWR. High gain, non-directional. All elements at DC ground potential for maximum lightning protection. Also available for other frequencies. **\$29.95** Shipped Express Collect

THE STOTTS-FRIEDMAN CO. Dept. R
108 North Jefferson Street, Dayton 2, Ohio

D. VAN NOSTRAND COMPANY, INC.
Dept. 1810A, Princeton, N.J.

Send for free examination—THE ALGEBRA OF ELECTRONICS. If I don't feel it can make electronic calculations clearer, easier, and faster, I may return it within 10 days; owe nothing. Otherwise, I will pay \$2.75 down, plus small delivery cost, and \$3 per month for 2 months.

Name _____ (Please Print Plainly)

Address _____

City _____ Zone _____ State _____

SAVE! Enclose \$8.75 WITH coupon and we will pay ALL shipping costs. Same ten-day money-back privilege. (Foreign and APO—please send \$8.75 with order.)

(In Canada: 25 Hollinger Rd., Toronto 16)
(Price slightly higher)

HI-FI RECORDING TAPE


*made by world famous manufacturer. Sold with 10-day money-back guarantee.

	3-	12-	24-
*1200' 7" acetate	\$1.29	\$1.16	\$1.10
*1800' 7" mylar	2.02	1.88	1.78
*1800' 7" acetate	1.79	1.59	1.49
2400' 7" mylar	2.31	2.75	2.70
2400' 7" Tensitized mylar	4.25	3.95	3.75

Can be assorted. Add 15¢ postage per reel 10¢ for 24+ reel orders.

MAIL ORDER HI-FI. You can now purchase all your HI-FI from one reliable source and be assured of perfect delivery. We deliver from NY stock most components, recorders & tape within 24 hours. SEND US A LIST OF YOUR HI-FI REQUIREMENTS FOR OUR WHOLESALE QUOTATIONS and our FREE wholesale catalog.

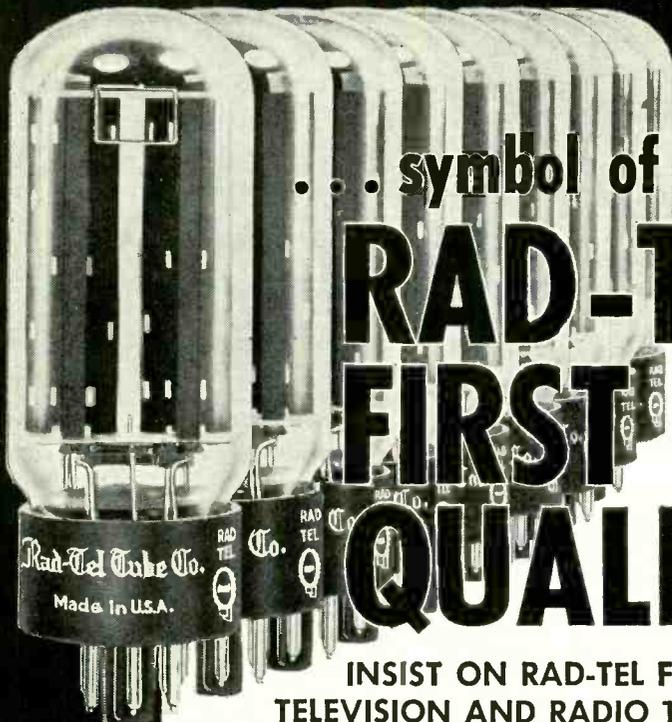CARSTON 125-RO E. 88 Street
New York 28, N.Y.



... symbol of
RAD-TEL
FIRST
QUALITY

INSIST ON RAD-TEL FOR EVERY
 TELEVISION AND RADIO TUBE NEED

Super-Special!

KIT OF 100
Bi-Pass
CONDENSERS

Over 50% Are 600V
 Others 400V And 200V

at
LESS
THAN
 4¢ each

\$ 3.95

Goodall
Semi-Molded
Paper
and
MYLAR

Values .001 to 1 mf

Up to 75% OFF on BRAND NEW TUBES

GUARANTEED ONE FULL YEAR!

You Can Rely On Rad-Tel's Speedy One Day Service!

Not Used — Not Pulled Out Of Old Sets • Each Tube Individually and Attractively Boxed!

Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price	Qty.	Type	Price							
—	024M	.79	—	30T6	.50	—	6AB4	.45	—	6B16	.62	—	6E08	.79	—	12A4	.60	—	12BD6	.50	—	12EG6	.54	—	198G6	1.39	
—	1AX2	.62	—	3Q5	.80	—	6AC7	.95	—	6BK7	.85	—	6E8A	.79	—	12AB5	.55	—	12BE6	.53	—	12E26	.53	—	19T8	.80	
—	1B3GT	.79	—	3S4	.61	—	6AF3	.73	—	6BL7	1.00	—	6HG8T	.58	—	12AC6	.49	—	12BF6	.44	—	12F5	.66	—	21EX6	1.49	
—	1DN5	.55	—	3V4	.58	—	6AF4	.97	—	6BN4	.57	—	6J5GT	.51	—	12AD6	.57	—	12BH7	.73	—	12F8	.66	—	25B06	1.11	
—	1G3	.73	—	4BC5	.56	—	6AG5	.65	—	6BN6	.74	—	6J6	.67	—	12AE6	.43	—	12BL6	.56	—	12FM6	.45	—	25C5	.53	
—	1J3	.73	—	4BC8	.96	—	6AH6	.99	—	6BD5	.65	—	6K6	.63	—	12AF3	.73	—	12BQ6	1.05	—	12K5	.65	—	25CA5	.59	
—	1K3	.73	—	4BN6	.75	—	6AK5	.95	—	6BQ6GT	1.05	—	6S4	.48	—	12AF6	.49	—	12BY7	.73	—	12SA7M	.86	—	25C06	1.44	
—	1L6	1.35	—	4BQ7	.96	—	6AL5	.47	—	6BQ7	.95	—	6SA7GT	.76	—	12AJ6	.46	—	12BZ7	.75	—	12SK7GT	.74	—	25C06	1.11	
—	1LN5	.39	—	4BS8	.98	—	6AM8	.78	—	6BR8	.78	—	6SK7	.74	—	12AL5	.45	—	12C5	.56	—	12SN7	.67	—	25DN6	1.42	
—	1R5	.62	—	4BU8	.71	—	6AN4	.95	—	6BU8	.70	—	6SL7	.80	—	12AL8	.95	—	12CA5	.59	—	12SQ7M	.73	—	25EH5	.55	
—	1S5	.51	—	4BZ6	.58	—	6AN8	.85	—	6BY6	.54	—	6SN7	.65	—	12A05	.52	—	12CN5	.56	—	12U7	.62	—	25L6	.57	
—	1T4	.58	—	4BZ7	.96	—	6A05	.55	—	6BZ6	.54	—	6SQ7	.73	—	12AT6	.43	—	12CR6	.54	—	12V6GT	.53	—	25W4	.68	
—	1U4	.57	—	4C56	.61	—	6AR5	.55	—	6BZ7	.97	—	6T4	.99	—	12AT7	.76	—	12CU5	.56	—	12W6	.69	—	25Z6	.66	
—	1U5	.60	—	4D6E	.62	—	6AS5	.60	—	6C4	.43	—	6U8	.78	—	12AU6	.50	—	12CUG	1.06	—	12X4	.38	—	35C5	.57	
—	1X2B	.42	—	4DK6	.60	—	6AT6	.43	—	6CB6	.54	—	6V6GT	.54	—	12AU7	.60	—	12CX6	.54	—	17AX4	.67	—	35L6	.51	
—	2AF4	.66	—	4DT6	.55	—	6AT8	.79	—	6CD6	1.42	—	6W4	.57	—	12AV5	.97	—	12D85	.69	—	17BQ6	1.09	—	35W4	.52	
—	3AL5	.42	—	5AM8	.79	—	6AU4	.82	—	6CF6	.64	—	6W6	.69	—	12AV6	.41	—	12DE8	.75	—	17C5	.58	—	35Z5GT	.60	
—	3AUG	.51	—	5AN8	.86	—	6AU6	.50	—	6CG7	.60	—	6X4	.39	—	12AV7	.75	—	12DL8	.85	—	17CA5	.62	—	50B5	.60	
—	3AV6	.41	—	5A05	.52	—	6A07	.61	—	6CG8	.77	—	6X5GT	.53	—	12AX4	.67	—	12DM7	.67	—	17D4	.69	—	50C5	.53	
—	3BA6	.51	—	5AT8	.80	—	6A08	.87	—	6CM7	.66	—	6X8	.77	—	12AX7	.63	—	12DQ6	1.04	—	17DQ6	1.06	—	50DC4	.37	
—	3BC5	.54	—	5BK7A	.82	—	6AV6	.40	—	6CN7	.65	—	7AU7	.61	—	12AZ7	.86	—	12D57	.59	—	17L6	.58	—	50EH5	.55	
—	3BE6	.52	—	5BQ7	.97	—	6AW8	.89	—	6CR6	.61	—	7A8	.68	—	12B4	.63	—	12DZ6	.76	—	17W6	.70	—	50L6	.61	
—	3BN6	.73	—	5CG8	.79	—	6AX4	.65	—	6CS6	.57	—	7B6	.69	—	12BA6	.50	—	12EL6	.50	—	19AU4	.83	—	117Z3	.61	
—	3BU8	.71	—	5CL8	.76	—	6AX7	.64	—	6CU5	.58	—	7Y4	.69	—												
—	3BY6	.55	—	5EA8	.80	—	6BA6	.49	—	6CU6	1.08	—	8A08	.83	—												
—	3BZ6	.55	—	5E08	.80	—	6BC5	.54	—	6CY5	.70	—	8A08	.93	—												
—	3CB6	.54	—	5J6	.68	—	6BC7	.94	—	6CY7	.71	—	8B05	.60	—												
—	3CF6	.60	—	5T8	.81	—	6BC8	.97	—	6DA4	.68	—	8C07	.62	—												
—	3CS6	.52	—	5T8	.81	—	6BD6	.58	—	6DB5	.69	—	8CM7	.68	—												
—	3CY5	.77	—	5U4	.60	—	6BE6	.55	—	6DE6	.58	—	8CN7	.97	—												
—	3D6	.60	—	5U8	.81	—	6BF6	.44	—	6DG6	.59	—	8C8	.93	—												
—			—	5V6	.56	—	6BG6	1.66	—	6DQ6	1.10	—	8E88	.94	—												
—			—	5X8	.78	—	6BH6	.65	—	6DT5	.64	—	10DA7	.71	—												
—			—	5Y3	.46	—	6BH8	.87	—	6DT6	.53	—	11CY7	.75	—												

Not a Kit, but Completely Wired

STEREO AMPLIFIER

CHASSIS \$4.95

- Single, \$5.95 ea.
- Set of tubes: 2-35C5; 1-12AX7; 1-35W4 \$1.15
- Set of 3 grey 1/2" knobs 30c



SEND FOR FREE TROUBLE SHOOTER GUIDE AND
 NEW TUBE & PARTS CATALOG.

NOT AFFILIATED WITH ANY OTHER MAIL ORDER TUBE COMPANY.

RAD-TEL TUBE CO.

55 Chambers St
 Newark 5, N. J.

TERMS: 25% deposit must accompany all orders — balance C. O. D.
 \$1 HANDLING CHARGE FOR ORDERS UNDER \$5. Subject to prior sale.
 Please add postage. No C. O. D.'s outside continental U. S. A.

RE-1060

For 1960. It's...


"COMPACT"

tools by VACO®

for the Electronics Service Trade

- "Compact" in Size: they fit the pocket
- "Compact" in Price: they fit your pocketbook too

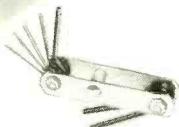Ask Your Parts Jobber or Your Jobber Salesman



HK-17 Hex Key Set \$1.00 net



DE-810 Double Nut Driver \$.79 net



AN-2 Tester \$.79 net



PK-8 Nut Driver \$.48 net



ND-141 Combination Screw & Nut Driver \$.79 net



SP-19 Probe \$.96 net



A-86 Pencil Type Driver \$.60 net

VACO PRODUCTS COMPANY, 317 E. Ontario St., Chicago 11, Illinois

In Canada: Atlas Radio Corp., Toronto 19, Ontario

PACKAGE HI FI or SINGLE COMPONENTS

You'll find our prices low and service fast.

Write for our quotation

CENTER INDUSTRIAL, Inc.

74-R Cortlandt Street, New York 7, N.Y.

TARZIAN Offers 48-Hour, Direct Factory Service on Tuner Repairs

only \$8.50

Price Effective Jan. 1, 1960

That's right. Net, \$8.50 per unit and \$15 for UV combinations, including ALL replacement parts. 90-day warranty against defective workmanship and parts failure. Tuners repaired on approved, open accounts. Replacements offered at these prices* on tuners not repairable:

- VHF 12 position tuner \$22.00
- VHF 13 or 16 position 23.00
- VHF/UHF combination 25.00
- UHF only 15.50

*Subject to change

Tarzian-made tuners are easily identified by this stamping on the unit. When inquiring about service or replacements for other than Tarzian-made tuners, always give tube complement . . . shaft length . . . filament voltage . . . series or shunt heater . . . IF frequency, chassis identification and allow a little more time for service. Use this address for fast, 48-hour service:

SARKES TARZIAN, Inc.

Att.: Service Mgr., Tuner Division
East Hillside Drive
Bloomington, Indiana

ALWAYS NEEDED



ALWAYS THERE

HERE'S HOW TO GET YOUR START in Radio-Electronics!



The most important training of all!

Now you'll really understand circuits—components—equipment! No matter what you want to do in radio-electronics, this big 396-page BASIC ELECTRICITY manual brings you the kind of down-to-earth training you absolutely must have. Backed with it, you'll read technical articles with new understanding. You'll know what's what about circuits, components, and equipment. Every detail of electric-electronic procedure and operation will be far clearer to you than ever before. BASIC ELECTRICITY covers the entire field—from circuits and currents to polyphase and 'phone principles . . . from tubes to transistors . . . from batteries, instruments and measurements to motors, generators, transformers and all the rest. More than 300 pictures and set-up diagrams make things doubly clear. Then, to top off your basic training, it includes an easily understood 61-page INTRODUCTION TO ELECTRONICS. Read it for 10 days at our risk!

10-DAY FREE EXAMINATION

Dept. RE-100, Technical Division
HOLT, RINEHART & WINSTON, Inc.
383 Madison Ave., New York 17, N.Y.


Send BASIC ELECTRICITY training manual for 10-day free examination. If I like book, I will then send you \$6.25 (plus postage) in full payment. Otherwise I will return book and owe you nothing. (Save! Send \$6.25 with order and we pay postage, 10-day money-back guarantee.)

Name _____
Address _____
City, Zone, State _____
OUTSIDE U.S.A. \$6.75 cash. 10-day money-back guarantee.

TRY THIS ONE (Continued)

GOODWILL KINK

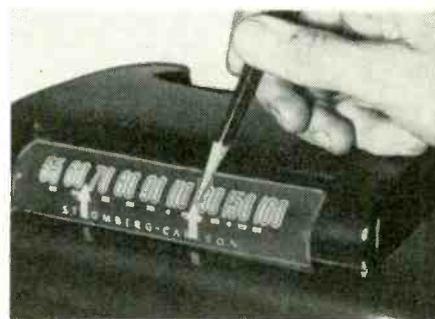As an extra service to the customers that bring older model radios to our



shop for repair, we mark the set's dial at 640- and 1240-ke (Conelrad alert frequencies) with arrows cut from red plastic tape. Customers seem to appreciate the interest we show in their welfare. To determine the exact location of each arrow, we just set up the signal generator to each frequency, calibrate the set's dial and stick the arrows in place.—Allen C. Johnson END

50 Years Ago

In Gernsback Publications


HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.

In October, 1910, Modern Electrics

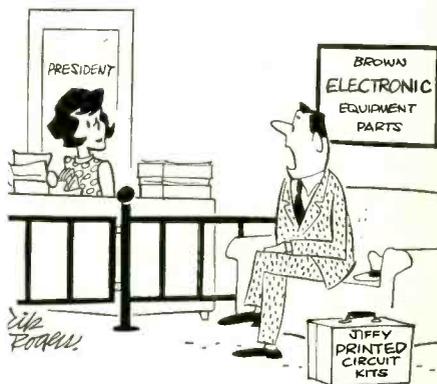- Radiotelephony, by Wm. E. Smith.
- A Variable Slide-Plate Condenser, by Richard Baker.
- New Electrolytic Detector.
- Helices, by D. E. McKisson.
- 90 Miles With a One-Inch Coil, by Chas. D. Herrold, E.E.
- How to Construct a Non-Inductive Potentiometer, by William Klaus.
- Construction of a Hot Wire Ammeter, by Donald R. Johnson.



"Pardon me, do you have a scrap of paper? There's a radio program I don't want to miss."

BUSINESS and PEOPLE

RCA Electron Tube Div., Harrison, N. J., launched a new advertising and sales promotion campaign, the biggest of its kind in its history, for its all-new



premium Silverama TV picture tube. Newspapers, trade and consumer magazines, radio and TV, direct mail and outdoor advertising will be used.

Electronic Instrument Co., Inc., Long Island City, New York, is offering distributors of its line of Eico hi-fi equip-



ment, test instruments and other electronic equipment, in kit or wired form, colorful neon and clock neon signs for window and interior display.

CBS Electronics, Danvers, Mass., again received an award from NATESA for outstanding service in creating better customer relations. A. L. Chapman, CBS Electronics president



(center) accepts the award from Mac Metoyer, NATESA president. J. H. Hauser, CBS Electronics sales manager; Frank J. Moch, executive director of NATESA, and R. V. Bontecou, CBS Electronics vice president of marketing, look on (left to right).

H. H. Scott, Inc., Maynard, Mass., has

FREE

GIANT 1961 204 PAGE CATALOG



SAVE UP TO
50% ON B-A
SELECTED
KITS

TOP VALUES
IN POWER
AND HAND
TOOLS

HI-FI AND
STEREO
SYSTEMS &
COMPONENTS

30 PAGES
OF BARGAINS
NOT IN ANY
OTHER CATALOG

100'S OF
NEW ITEMS
LISTED HERE
FOR 1ST TIME

A Complete Buying Guide for Everything in

RADIO TV ELECTRONICS

for DEALERS, SERVICE MEN, SHOPS, BROADCASTERS, INDUSTRIES, THEATRES, MANUFACTURERS, CHURCHES, HOTELS, PUBLIC UTILITIES, LABORATORIES, BUSINESS, EXPERIMENTERS, AMATEURS

- To locate products...
- To compare...
- To get...

UNDER PAGE 201-202, PHONE BATTERIES 1138

BURSTEIN-APPLEBEE CO. 1012-14 McGEE ST., KANSAS CITY 6, MO.

BURSTEIN-APPLEBEE CO. Dept. RE
1012-14 McGEE St., Kansas City 6, Mo.

Send Free 1961 B-A Catalog No. 611

NAME _____
ADDRESS _____
CITY _____ STATE _____

**RUSH COUPON
TODAY!**

SUPER MAGNET SUPER SAVING!!

Buy this Little Giant magnet, most powerful made, a sensational bargain! The low price of \$1.95 is less than 50% of what you'd pay for this magnet. Experimenters, hobbyists will find hundreds of uses for this powerful 4 oz. Alnico permanent magnet. LIFTS 5 lbs. EASILY. Limited quantity. Order several today. Measures 1 3/4 x 1 1/2".
Item No. 86 \$1.50
Special Bargain (Shp. Chgs. 10c)



250 POWER TELESCOPE LENS KIT

Make your own high powered 6 ft. telescope! Kit contains 2" diam., 75" focal length, ground and polished objective lens and necessary eye pieces. Magnifies 50x to 250x. Full instructions.

ITEM NO. 123
\$2.95
(Shp. Chgs. 10c)



AMAZING BLACK LIGHT

250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects.



Ship. wt. 2 lbs. \$2.95
ITEM NO. 87
(P. P. & Ndg. Chgs. 35c)

HUDSON SPECIALTIES CO., 160 W. 14th St. Dept. RE-1060, New York 7, N.Y.

I am enclosing full remittance for items circled below. (Be sure to include shipping charges.)

87 33 86 123
Name _____
Please Print Clearly
Address _____
City _____ Zone _____ State _____

WATTHOUR METER

Leading makes—reconditioned. Ideal for trailer parks. 100-110 volts, 60 cycles. 2-wire A.C. 5 amp. Heavy metal case 8 1/2" x 6 1/4" x 5". Easy to install. Ship. wt. 14 lbs.




ITEM NO. 33 \$4.50
NOW ONLY
(P.P. & Ndg. Chgs. \$1.25)

TV TUNERS OVERHAULED

ALL MAKES AND MODELS **\$9.95** NET — VHF OR UHF

UHF/VHF COMBINATION—\$19.90

90 DAYS WARRANTY

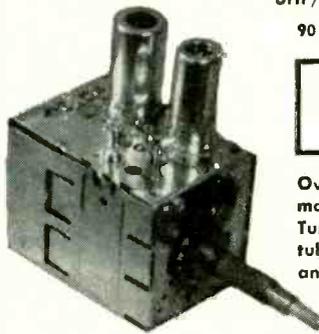

SAME DAY SERVICE

ON POPULAR TYPES—48 HOURS MOST OTHERS

Overhaul charge includes labor and minor parts; tubes and major parts are extra at net prices. Tuner to be overhauled should be shipped complete; include tubes, shield cover and any damaged parts. Quote model and state complaint. Pack well and insure.

WE WILL SHIP C.O.D.—F.O.B. CHICAGO OR TORONTO

Castle TV Tuner Service

5710 N. WESTERN
CHICAGO 45, ILL.

U.S.A.

136 MAIN ST.
TORONTO 13

CANADA

Suppliers of rebuilt TV Tuners to manufacturers, technicians & service dealers, coast to coast.

Original and Only Complete TV Tuner Service covering the North American Continent.

PHOTOGRAPHS RADIO-ELECTRONICS can use good photographs of service benches, service shops, high-fidelity audio layouts, and any other interesting and original radio-electronic devices. We will pay \$7.50 each for good professional photos or equivalent, suitable for reproduction. Full information on subject photographed will increase their acceptability.

The Editor, RADIO-ELECTRONICS

154 West 14th St.

New York 11, N. Y.

A "brass-tacks" guide to TIME-SAVING TEST PROCEDURES!



The manual that helps you cut testing time in half!

BASIC ELECTRONIC TEST PROCEDURES is a big new 316-page manual with the kind of "brass tacks" training that helps you locate TV, AM and FM troubles in a jiffy. Teaches you exactly what instruments to use and exactly when and how to use each type. Tells how to substitute one instrument for another and how to develop time-saving, money-making test methods.

Complete—Easy to Understand!

Here are some of the subjects it covers: Current Checks; making measurements of Power, Capacitance, Inductance, Resistance, AF, RF, Phase, Distortion & Modulation; checking Sensitivity, RF Gain, Fidelity, AVC Voltage, Operating Voltages, etc. Includes handy **VISUAL ALIGNMENT TECHNIQUES**. Even covers transmitter and industrial electronic test procedures. 190 how-to-do-it pictures and dozens of step-by-step troubleshooting procedures charts make things doubly easy. Price only \$8.00. Money-back guarantee.

PRACTICE 10 DAYS FREE!


Dept. RE-100, Technical Division
HOLT, RINEHART & WINSTON, INC.
383 Madison Ave., New York 17, N. Y.
Send **BASIC ELECTRONIC TEST PROCEDURES** Manual for 10-day free examination. If I like book, I will then send \$8.00 (plus postage) in full payment. Otherwise, I will return manual and owe you nothing. (SAVE! Send \$8.00 with order and we pay postage. Same 10-day return privilege with money refunded promptly.)
Name _____
Address _____
City, Zone, State _____
OUTSIDE U.S.A.—\$8.50 cash. 10-day money-back guarantee

TUNE ELECTRONIC ORGANS ACCURATELY—QUICKLY WITH A NEW

Schober AUTOTUNER

Every organ owner and service technician requires this valuable aid to precision organ tuning. This instrument enables anyone to quickly tune any electronic-oscillator organ (except Thomas) without previous knowledge or skill.

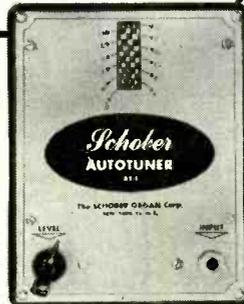An automatic stroboscopic indicator visually shows true pitch to an accuracy of 1/100 of a semitone (more accurate than human hearing), yet you pay about 1/3 the price of other tuning devices of similar precision.



Black plastic case with etched satin aluminum front panel. So lightweight it may be carried in your pocket. Size 6 3/4" x 5 1/4" x 2 1/4". Detailed instructions included.

\$6950

(completely assembled)

\$4950 (in assemble-it-yourself kit)

(N.Y.C. Residents add 3% Sales Tax)

MAIL ORDERS FILLED PROMPTLY • FULLY GUARANTEED


THE SCHOBBER ORGAN CORPORATION, Dpt. RE

43 West 61st Street, New York 23, N. Y.

Manufacturers of the World-Famous Schober Organ Kits.

offered to replace any original London-Scott 1000 stereo cartridges with the new ruggedized version. The company has also announced that it had received a Certificate of Merit for excellence of design and execution from the Art Directors Club of Boston for its booklet "How to Use Stereo High Fidelity Components in Your Decorating Plans."

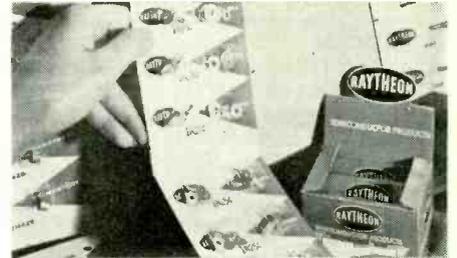Raytheon Co.'s Distributor Products Div.'s Unicenter in Westwood, Mass., has installed a new machine which



automatically bonds clear-plastic contour blisters to cardboard merchandiser panels so that 10 transistors can be shipped and displayed together.

Rek-O-Kut Co., New York, played host to 94 winners of its Tropical Holiday dealer-incentive promotion on a



week-long trip to Nassau in the Bahamas. Dealers and their wives are shown boarding the chartered plane for the return trip.

Vaco Products Co., Chicago, is offering purchasers of its Crimcut cutting and crimping tool a dollar book, "Shop Kinks," for 25c.



Kenneth B. Shaffer (left) was promoted to manager, distributor sales, of the RCA Electron Tube Div., Harrison, N. J., succeeding D. M. Branigan, who was recently appointed manager, electronic components marketing, of RCA's International Div. Shaffer had been distributor field sales manager. John R. Meagher (right) was appointed man-



ager of electronic instruments merchandising of the Distributor Products Dept. of the division. He has been a technical editor, field engineer and author and lecturer on test equipment for the company.

Francis J. Chamberlin was appointed vice president of sales of Clarostat Mfg. Co., Dover, N. H. He has been with the company since 1945, most recently as general sales manager.



The acquisition by Electro-Voice, Inc., Buchanan, Mich., of the Featheride Phono Pickup & Cartridge Div. of Webster Electric Co. of Racine was announced by Al Kahn, president of Electro-Voice. The newly acquired products will be marketed as Electro-Voice Featheride cartridges and tone arms and will be manufactured in the firm's new Eureka, Ill., plant.



Boyd B. Barrick, former central zone manager for Raytheon Co.'s Distributor Products Div., Westwood, Mass., was promoted to the position of general sales manager of the division.




Ralph H. G. Mathews joined Blonder-Tongue Labs., Newark, N. J., as director of marketing. He comes from Westinghouse Electric Corp., TV-Radio Div. He held the position of manager of national accounts and sales training at Westinghouse.



Alvin Grad has been named national sales manager for Mercury Electronics Corp., Mineola, N. Y. He is a veteran sales executive and was with such companies as Fada Radio, Admiral and Rytel.



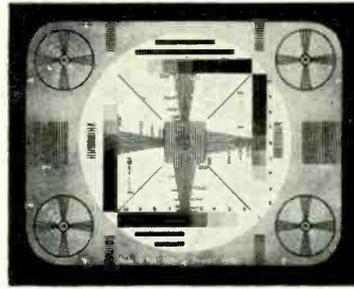Clyde J. Schultz was appointed sales promotion manager of Switchcraft, Inc., Chicago. He will be responsible for all phases of the advertising and sales promotion program of the Industrial and Distributor Sales Divisions. He comes to the company from Admiral Sales Corp. where he was sales promotion manager. **END**



TV TIPS FROM TRIAD

"It's this kind of job that makes me envy the box boy's career at a supermarket," said Joe, the Junior PTM, as he gloomily eyed the job on the bench.

"You should be an expert on them, since that's the second one in three days," said Bill.

"Same set, same trouble, but not same cure," said Joe. "The first set came in with a short between the yoke windings. I went down and picked up the replacement, compared terminal numbers, connected it, and it worked fine. This set came in, same type of short, so I bought the same yoke as before, compared numbers, connected it, and got a fine picture, but it was upside down and backwards. When I reversed the leads to make it read right I had the worst case of 'ring ripple' I have ever had."

"Did you, by any chance," asked Bill, "buy a replacement with all the parts wired in?"

"The counterman said it was an 'exact' replacement," answered Joe defensively. "But why was it perfect in one case, and like this in the second?"

"Hm," said Bill, as he looked, "did you notice where the leads came out of the first yoke when you had it mounted?"

"Out the bottom," said Joe promptly.

"Well, they come out the top the way this one is mounted," said Bill. "If I remember correctly they used different mountings in different runs. When you installed this yoke you had exactly the right anti-ring network on exactly the wrong terminals, because you had to reverse polarity to make the picture read 'right.' If you follow my system, use new parts to duplicate the wiring (and mounting) of the original, you would never know about this kind of trouble."

MORAL: It is probably impossible to "exactly" replace over four thousand yokes from a line of less than a hundred. If you use the correct basic unit (proper deflection and inductance) plus a Network Kit to duplicate the original installation, you will find that nearly all jobs can be done quickly and easily. Review your yoke fundamentals as outlined in PTM #3, a copy of which is available from your Triad Distributor or from Triad in Venice. **Triad Transformer Corporation**, 4055 Redwood Avenue, Venice, California.

ADD TO YOUR INCOME

Learn at Home to Fix APPLIANCES

FREE SAMPLE LESSON

Tester Furnished—No Extra Charge. National Radio Institute trains you at home. Every service customer is worth more when you can fix his electrical appliances. Mail coupon for Lesson and Catalog.

National Radio Inst., Dept. FKO, Washington 16, D.C.
Please send me Electrical Appliance Sample Lesson and Catalog FREE (No salesman will call).

Name.....Age.....
Address.....
City.....Zone.....State.....

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

NOW — Tune your crystal controlled citizens band transceiver on ALL channels. No need to buy additional receiver crystals—a **CROWN** citizens band tuner is all you need—simple to install—just plug this tuner into your receiver crystal socket and receive ANY citizens band channel.

CROWN ELECTRIC
"P. S. REG. 10"

CROWN ELECTRIC
P. S. REG. 10"

2x1x4 with 2" VERNIER DIAL

Complete Instructions Furnished
Specify Name and Model of Your Set When Ordering

Order Yours Today—Only \$12.95 Net
No C.O.D.—Send Check or Money Order

CROWN ELECTRIC PRODUCTS CO.
P.O. BOX 171 ORANGE, N. J.
DEALER INQUIRIES INVITED

ORDER YOUR ENCLOSURE KITS FROM HOMEWOOD

Bring out the best in your speakers... save dollars in assembly and finishing costs... get the fun of "doing-it-yourself"!



ONLY **\$11.95**

MODEL 6

Factory assembled, ready for finishing. Makes your 8" speaker sound like a million! Made of 1/2" hardwood ply, beautifully grained and smoothly sanded. 10" h. x 16" w. x 9" d. 9 lbs. Order two for matched stereo performance.



MODEL 1

4 1/2 cubic feet of baffle space assures you crisp, cleanest bass response from any 12" speaker system. Full-grained white birch ply, with pre-attached bracing cleats for easy assembly. Kit includes everything you need for assembly. 29" h. x 20" w. x 12 1/2" d. (5" legs). 25 lbs. \$18.95



MODEL 2

Clear-grained on four sides for bookshelf or floor use. Acoustically accurate for 12" systems, with adapter board for 8" speakers. Sturdy, 3/4" ply eliminates unwanted resonances, improves bass response. 14" h. x 21" w. x 11 3/4" d. 20 lbs. In Birch, \$14.50 In Walnut, \$19.95

MODEL 13. Finishing kit; includes generous quantities of everything you need to do a professional, long-lasting finishing job, plus brush, sandpaper and easy-to-follow instructions. Specify: Mahogany, Walnut, Blonde, Oak, Fruitwood, Maple, Cherry, Ebony, Natural. \$3.88

Ten-day money-back guarantee. All items shipped freight collect. Please send check or M.O. (No COD's)

HOMWOOD INDUSTRIES, Inc.

26A Court Street, Brooklyn 1, N.Y.

Please send me:

- () Model 6 () Model 1 () Model 2 (Birch) (Walnut)
 () Model 13
 () Homewood catalog

I enclose remittance in the amount of \$ _____

Name _____

Address _____

City _____ Zone _____ State _____

Almo
OFFERS BRAND NEW IMPORTED RADIO & TV RECEIVING TUBES!
FROM 65 to 75% OFF!
ONE YEAR GUARANTEE!

1B3GT LIST 2.90 YOUR COST .87
 6SN7GTB LIST 2.60 YOUR COST .78
 5U4GB LIST 2.10 YOUR COST .63
 12AU7 LIST 2.45 YOUR COST .74

TYPE	LIST	YOUR COST	TYPE	LIST	YOUR COST
1B3GT	2.90	.87	6C57	2.80	.98
1R5	2.55	.89	6DQ6A	4.10	1.44
1S5	2.55	.89	6J6	2.80	.98
1T4	2.40	.84	6K6GT	2.35	.82
1U4	2.35	.82	6L6G	4.20	1.47
1U5	2.05	.72	6SA7GT	3.25	1.14
1X2B	3.05	1.07	6S7GT	3.20	1.12
3AL5	1.85	.65	6SK7GT	3.05	1.07
3AU6	2.15	.75	6SL7GT	3.30	1.16
3AV6	1.15	.61	6SN7GTB	2.60	.78
3BN6	3.05	1.07	6SQ7GT	2.70	.95
3BZ6	2.25	.79	6TG	3.35	1.17
3CB6	2.25	.79	6U8	3.30	1.16
3DT6	2.20	.77	6V6GT	2.15	.75
3S4	2.45	.86	6W4GT	2.40	.84
3V4	2.35	.82	6W6GT	2.80	.98
4BQ7A	4.00	1.40	6X4	1.65	.58
5U4GB	2.10	.63	7AU7	2.60	.91
5U5	3.30	1.16	12AT6	1.65	.58
5Y3GT	1.75	.61	12AT7	3.05	1.07
6AC7GT	4.25	1.49	12AU6	2.15	.75
6AK5	4.25	1.47	12AU7	2.45	.74
6AL5	1.85	.65	12AV6	1.65	.58
6AQ5	2.15	.75	12AX4GTA	2.70	.95
6AT6	1.90	.67	12AX7	2.55	.89
6AU4GTA	3.35	1.17	12BA6	2.00	.70
6AU6	2.10	.74	12BE6	2.15	.75
6AV6	1.65	.58	12BH7A	3.05	1.07
6AW8	3.55	1.24	12BK5	3.80	1.33
6AX4GT	2.65	.93	12BQ6GTB	4.45	1.56
6BA6	2.00	.70	12BY7A	3.05	1.07
6BE6	2.20	.77	12DQ6A	4.20	1.47
6BG6G	6.50	2.28	12SA7GT	3.25	1.14
6BH6	2.70	.95	12S7GT	3.20	1.12
6BJ6	2.80	.98	12SK7GT	3.05	1.07
6BK5	3.50	1.23	12SL7GT	3.75	1.31
6BN6	3.05	1.07	12SN7GT	2.70	.95
6BN8	2.70	.95	12SQ7GT	2.65	.93
6BQ6GTB	4.35	1.52	35C5	2.15	.75
6BQ7A	3.95	1.38	35L6GT	2.40	.84
6BZ6	2.25	.79	35W4	1.40	.49
6C4	1.85	.65	35Z5GT	1.85	.65
6CB6	2.25	.79	50C5	2.15	.75
6CG7	2.45	.86	50L6GT	2.40	.84
6CL6	3.75	1.31			

new LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

NEEDLE CATALOG has illustrations of needles and how they are mounted in cartridges. Cross-references are given to several needle manufacturers as well as phonograph manufacturers. Tables list needle numbers, tip sizes, prices, cartridge numbers and old manufacturer's numbers. —Astatic Corp., Conneaut, Ohio.

PARTS AND ACCESSORIES are listed in a 375-page loose-leaf manual. Information and photographs are given on batteries, tubes, tuners, wrenches, knobs, antennas, etc. Available from manufacturer's distributors.—Zenith Sales Corp., 6001 W. Dickens Ave., Chicago 39, Ill. \$4.

GUIDE TO INDUSTRIAL PRODUCTS gives specifications on voltage regulators, special-purpose tubes, semiconductors; describes and illustrates knobs, and includes a cross-reference to competitors' tube types. Several sections in one folder.—Raytheon Co., Dist. Products Div., 411 Providence Turnpike, Westwood, Mass.

INDICATOR LAMPS and sockets are described in a 4-page folder. Bulbs are flat-topped with special construction for smaller size, longer life, stronger bases and higher light output. A colored nylon cap fits the bulb end. A matching line of sockets is available.—Sylvania Lighting Products, Div. Sylvania Electric Products, Inc., 60 Boston St., Salem, Mass.

MICROPHONE FACTS discusses operation principles of the parabolic-reflector microphone, the "machine-gun" microphone and the model 642, an extreme-directivity, wide-range, high-output instrument.—Electro-Voice, Inc., Buchanan, Mich.

CATALOG of stock panel meters lists more than 1068 models and sizes. 8-page *Bulletin No. 2061* has photographs and dimensional drawings.—Simpson Electric Co., 5200 W. Kinzie St., Chicago 44, Ill.

REPLACEMENT TV KNOBS are pictured

FREE Catalog of The WORLD'S FINEST GOV'T SURPLUS ELECTRONIC BARGAINS

UNIVERSITY 25 WATT DRIVER UNIT —

Delivers 25 Watt high volume low distortion output. Excellent reproduction for music and speech. Frequency range 90 to 9000 cycles. 15 ohm impedance matches all amplifiers. Standard 24 thread x 1 3/8" mounting nipple fits all transmitters and projectors. Size: 5 x 4 1/2". Wt.: 4 lbs. University No. SA-301—Gov't #MX-1054/U. Our Low Price—only **\$5.95**



Address Dept. RE • All Prices F.O.B. Lima, Ohio • 25% Deposit Required on C.O.D. Orders

FAIR RADIO SALES
 2133 ELIDA RD. • P.O. Box 1105 • LIMA, OHIO



SEND NOW FOR BIG FREE CATALOG!

NEW LITERATURE (Continued)

and listed for 12 makes of sets. This 8½ x 14½-inch chart has 12 pages.—GC Electronics Co., Div. Textron Electronics, 400 S. Wyman St., Rockford, Ill.

COMPRESSOR-LIMITER amplifier and control unit are described in a 4-page folder.—Westrex Corp., Recording Equipment Dept., 6601 Romaine St., Hollywood 38, Calif.

REPLACEMENT GUIDE lists ceramic-base printed circuits used in radios since January, 1950. *Manual K-352* lists manufacturers in alphabetical order. Schematics of entire line of 179 replacement printed circuits are shown along with capacitance and resistance ratings. Available from distributors or send 10c to manufacturer.—Sprague Products Co., 81 Marshall St., North Adams, Mass.

CATALOG of stereo and test equipment, radio and TV components, Citizens-band equipment, tools, books, public-address systems, cameras, etc. *Catalog 310* is largest (320 pages) and most comprehensive offered in firm's history.—Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

REFERENCE DATA for TV-antenna systems. *Booklet JP-1* lists cable data, frequency data for the different channels, information on manufacturer's tapoffs and a chart to simplify db calculations.—Jerrold Electronics Corp., 15 St. and Lehigh Ave., Philadelphia 32, Pa.



MICROPHONES are listed in *Catalog M10*. There are 12 pages of specifications, photographs, applications and prices. 8½ x 11 inches.—Astatic Corp., Conneaut, Ohio.

POWER SUPPLY HANDBOOK lists variable-frequency ac supplies, variable-voltage dc supplies (up to 600,000 volts) and voltage regulators. Seven pages of technical data cover such subjects as ripple, ac regulators and frequency changers.—Sorensen & Co., Inc., Richards Ave., S. Norwalk, Conn.

MULTICONDUCTOR cables in round and ribbon styles are listed in an 18-page catalog. Conductors and insulating materials (including Teflon) are discussed.—Times Wire & Cable Div., International Silver Co., Wallingford, Conn.

CLOSED CIRCUIT TV and its uses are covered in the 14-page booklet *How to Use Direct-Wire TV*. Some of the subjects discussed are medical uses, student training, pilferage protection and inter-departmental communication.—Argus A-V Systems Dept., Argus Cameras, Inc., 405 Fourth St., Ann Arbor, Mich.

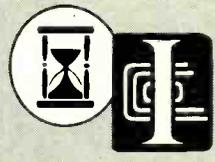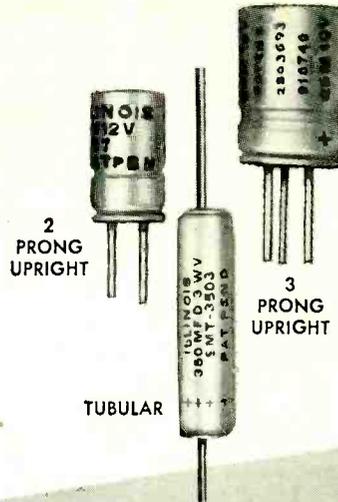TERMINAL BLOCKS and switches are described and illustrated in 32-page *catalog No. 16*. Blocks are barrier and pressure-contact (setscrew) types. Toggle switches meet military specifications.—Kulka Electric Corp., 633-643 S. Fulton Ave., Mount Vernon, N. Y. END



ILLINOIS
CONDENSER COMPANY
1616 North Throop
Chicago 22, Illinois
Phone EV 4-1300

NOW!
In stock at your distributor

SMT


SUB-MINIATURES

For all transistorized electronics

Unsurpassed where size is essential in countless replacement applications. Available in full range of capacities and voltages . . . SMT, SMTU (up-right), upright common positive, upright common negative and non-polarized.

Order from your distributor now. Our new SMT catalog is available upon request.

THE EVOLUTION OF A FAMOUS TAPE RECORDER

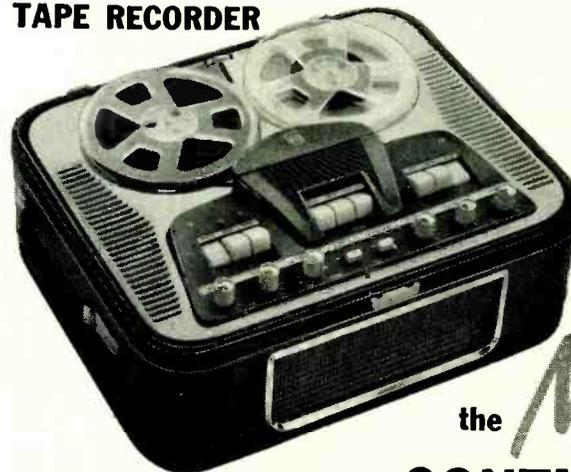

the *Norelco*[®]

CONTINENTAL "400" a new 4-track stereo-record/stereo-playback tape recorder guild-crafted for you by Philips of the Netherlands

(MODEL EL 3536) SPECIFICATIONS

- ◆ Four-track stereophonic or monophonic recording and playback
- ◆ Three tape speeds — 1½, 3¼ and 7½ ips
- ◆ Completely self-contained, including dual recording and playback preamplifiers, dual power amplifiers, two Norelco wide-range loudspeakers (second in lid) and stereo dynamic microphone (dual elements)
- ◆ Can also be used as a quality stereo hi-fi system with tuner or record player.

For additional descriptive literature write to: North American Philips Co., Inc. High Fidelity Products Division 230 Duffy Avenue Hicksville, L. I., N. Y.



BRAND NEW UNITED'S FIRST QUALITY TUBES

DISCOUNTS up to **80% OFF**
GUARANTEED ONE FULL YEAR! NOT USED! NO PULLS! **WHY PAY MORE?**

| Qty. Tube # Price |
|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|-------------------|
| ... 0Z4 .75 | ... 3CV5 .70 | ... 6AG7 .75 | ... 6BU8 .69 | ... 6J8 .77 | ... 12CU6/ .57 | ... 17L6 .57 |
| ... 1A5 .80 | ... 3DK6 .59 | ... 6AH4 .82 | ... 6BX7 1.02 | ... 6V6 .53 | ... GA 1.00 | ... 18A5 .90 |
| ... 1A7 .94 | ... 3DT6 .49 | ... 6BK4 .98 | ... 6BY6 .56 | ... 6WA .60 | ... 12CX7 .70 | ... 18AW6 .49 |
| ... 1AX2 .70 | ... 3Q4 .68 | ... 6AK5 3/1.00 | ... 6BZ6 .54 | ... 6W6 .68 | ... 12BV7 .80 | ... 18FX6 .52 |
| ... 1B3 .73 | ... 3Q5 .89 | ... 6AL5 .46 | ... 6BZ7 .96 | ... 6X4 .38 | ... 12BY7 .73 | ... 18Y6 .40 |
| ... 1C5 1.02 | ... 3S4 .50 | ... 6AL7 1.35 | ... 6BZ8 1.05 | ... 6X5 .51 | ... 12BZ7 .74 | ... 19AU4 .80 |
| ... 1C3 .73 | ... 3V4 .57 | ... 6AM8 .77 | ... 6C4 .42 | ... 6X8 .75 | ... 12C5 .55 | ... 19BG6 1.39 |
| ... 1G4 .70 | ... 4AU6 .54 | ... 6AN8 .84 | ... 6CB6 .53 | ... 7AD7 .80 | ... 12CU5 .55 | ... 19T8 .78 |
| ... 1H5 .75 | ... 4B6 .54 | ... 6AQ5 .82 | ... 6CD6G 1.20 | ... 7AT7 .70 | ... 12CN5 .55 | ... 21E6 1.40 |
| ... 1J3 .72 | ... 4BC5 .55 | ... 6AQ6 .60 | ... 6CD6GA 1.40 | ... 7AU7 .60 | ... 12CR6 .53 | ... 25A4 .71 |
| ... 1K3 .72 | ... 4BC8 .95 | ... 6AR5 .54 | ... 6CF6 .63 | ... 7E6 .75 | ... 12CT8 .90 | ... 25B6 1.00 |
| ... 1L4 .60 | ... 4BN6 .75 | ... 6AS5 .59 | ... 6C7 .59 | ... 8AU8 .82 | ... 12C6 .53 | ... 25C6 .42 |
| ... 1L4A .99 | ... 4BQ7 .95 | ... 6AS6 2.25 | ... 6C8 .76 | ... 8AW5 .92 | ... 12BB5 .68 | ... 25D6 1.20 |
| ... 1L4E .99 | ... 4BS8 .97 | ... 6AS8 .85 | ... 6CM7 .65 | ... 8BQ5 .59 | ... 12DE8 .74 | ... GB 1.49 |
| ... 1L4F .99 | ... 4BU8 .70 | ... 6AT6 .42 | ... 6CN7 .64 | ... 8C7 .61 | ... 12DL8 .84 | ... 25E6 .52 |
| ... 1L4G .99 | ... 4BZ6 .57 | ... 6AU4 .85 | ... 6CQ8 .83 | ... 8CM7 .67 | ... 12DQ6 1.00 | ... 25CD6/ .52 |
| ... 1LD5 .99 | ... 4BZ7 .95 | ... 6AUS 1.05 | ... 6CR6 .50 | ... 8CN7 .65 | ... 12DS7 .78 | ... CA 1.20 |
| ... 1LE3 .99 | ... 4CB6 .57 | ... 6AUG .49 | ... 6CS6 .56 | ... 8CX8 .90 | ... 12E6 .57 | ... GB 1.49 |
| ... 1LH3 .99 | ... 4CE6 .80 | ... 6AU7 .60 | ... 6CS7 .70 | ... 8EB8 .43 | ... 12E6 .57 | ... 25D6 1.35 |
| ... 1LH4 .99 | ... 4CY5 .70 | ... 6AUS .86 | ... 6CS7 .70 | ... 8E8 .43 | ... 12E6 .57 | ... 25E6 .52 |
| ... 1LN5 .99 | ... 4DE6 .61 | ... 6AV5 .97 | ... 6CX8 .90 | ... 10C8 .95 | ... 12E6 .57 | ... 25W4 .67 |
| ... 1N5 .99 | ... 4DE6 .61 | ... 6AV5 .97 | ... 6CX8 .90 | ... 10C8 .95 | ... 12E6 .57 | ... 25Z6 .65 |
| ... 1S4 .75 | ... 5A25 .51 | ... 6AX5 .75 | ... 6CY7 .70 | ... 11CY7 .74 | ... 12E6 .49 | ... 32E5 .52 |
| ... 1S5 .50 | ... 5AT8 .79 | ... 6BA6 .48 | ... 6DE6 .57 | ... 12AB5 .54 | ... 12E6 .52 | ... 32L7 .89 |
| ... 1T4 .57 | ... 5AV8 1.00 | ... 6BA7 .92 | ... 6DN7 .85 | ... 12AF3 .72 | ... 12AC6 .48 | ... 35B5 .65 |
| ... 1U4 .56 | ... 5B1 .95 | ... 6BA8 .91 | ... 6DQ6 1.00 | ... 12AF6 .48 | ... 12AC6 .48 | ... 35C5 .50 |
| ... 1U5 .49 | ... 5BK7 .82 | ... 6BC5 .54 | ... 6D5 .65 | ... 12AJ6 .45 | ... 12F8 .91 | ... 35L6 1.00 |
| ... 1V2 .99 | ... 5BQ7 .96 | ... 6BC7 .93 | ... 6DT6 .52 | ... 12AL5 .44 | ... 12F8 .91 | ... 35L6 1.00 |
| ... 1X2 .75 | ... 5BR8 .78 | ... 6BC8 .95 | ... 6E6 .55 | ... 12AL6 .44 | ... 12F8 .91 | ... 35L6 1.00 |
| ... 2AF2 .95 | ... 5CC8 .75 | ... 6BD6 .50 | ... 6EB8 .90 | ... 12A5 .51 | ... 12F8 .91 | ... 35L6 1.00 |
| ... 2B3 1.00 | ... 5EAB .79 | ... 6BE6 .54 | ... 6E8 .78 | ... 12AT6 .42 | ... 12S7 .75 | ... 36A3 .49 |
| ... 2BN4 .53 | ... 5EU8 .79 | ... 6BF5 .88 | ... 6EW5 .55 | ... 12AT7 .75 | ... 12S7 .75 | ... 40B2 1.50 |
| ... 2CY5 .70 | ... 5J1 .67 | ... 6BF6 .43 | ... 6F5 .85 | ... 12AU6 .49 | ... 12S7 .75 | ... 50B5 .59 |
| ... 3A3 .84 | ... 5T8 .80 | ... 6BG6 1.40 | ... 6H6 .55 | ... 12AU7 .59 | ... 12S7 .75 | ... 50C5 .52 |
| ... 3A4 .55 | ... 5U4 .59 | ... 6BGA 1.60 | ... 6J5G .36 | ... 12AV7 .74 | ... 12S7 .75 | ... 50E5 .54 |
| ... 3AF4 1.02 | ... 5UR8 .80 | ... 6BH6 .64 | ... 6J5GT .50 | ... 12AV7 .74 | ... 12S7 .75 | ... 50L6 .60 |
| ... 3AL5 .41 | ... 5V4 .82 | ... 6BH8 .86 | ... 6J6 .66 | ... 12AW6 .75 | ... 12S7 .75 | ... 70L6 .75 |
| ... 3AU6 .50 | ... 5V6 .55 | ... 6BJ6 .61 | ... 6J7 .85 | ... 12AX4 .66 | ... 12S7 .75 | ... 70L7 .85 |
| ... 3AV6 .40 | ... 5W4 .95 | ... 6BK5 .85 | ... 6K6 .58 | ... 12AX7 .62 | ... 12S7 .75 | ... 70L7 .85 |
| ... 3B2 1.50 | ... 5X4 .78 | ... 6BK7 .84 | ... 6L6 1.10 | ... 12AY7 1.44 | ... 12S7 .75 | ... 117Z6 1.05 |
| ... 3BA6 .50 | ... 5X8 .77 | ... 6BL7 .99 | ... 6SA .47 | ... 12AZ7 .62 | ... 12V6 .52 | ... 117Z6 1.05 |
| ... 3BC5 .53 | ... 5Y3 .45 | ... 6BN4 .56 | ... 6S4 .47 | ... 12B6 .62 | ... 12V6 .52 | ... 117Z6 1.05 |
| ... 3BE6 .51 | ... 5Y4 .77 | ... 6BN6 .73 | ... 6SC7 .75 | ... 12BA6 .49 | ... 14M7 .80 | ... 117Z6 1.05 |
| ... 3BN4 .63 | ... 6A7 1.10 | ... 6BQ5 .59 | ... 6SF5 .75 | ... 12BA7 .95 | ... 14N7 .80 | ... 117Z6 1.05 |
| ... 3BN6 .75 | ... 6A8 1.15 | ... 6BQ6 .75 | ... 6SH7 .75 | ... 12B8 .62 | ... 14N7 .80 | ... 117Z6 1.05 |
| ... 3B8 .70 | ... 6A8A .45 | ... 6BQ7 .94 | ... 6S7 .75 | ... 12B8 .62 | ... 14N7 .80 | ... 117Z6 1.05 |
| ... 3BY6 .54 | ... 6AC7 .85 | ... 6CUG/ .72 | ... 6SJ7 .75 | ... 12B8 .62 | ... 14N7 .80 | ... 117Z6 1.05 |
| ... 3BZ5 .54 | ... 6AF3 .92 | ... 6A 1.00 | ... 6SK7 3/1.00 | ... 12BF6 .43 | ... 17C6 .57 | ... 117Z6 1.05 |
| ... 3CB6 .53 | ... 6AF4 .96 | ... 6BQ7 .94 | ... 6SL7 .79 | ... 12BH7 .72 | ... 17C6 .57 | ... 117Z6 1.05 |
| ... 3CF6 .59 | ... 6AF4A .96 | ... 6BR8 .77 | ... 6SN7 .64 | ... 12BL6 .55 | ... 17D6 1.00 | ... 117Z6 1.05 |
| ... 3CS6 .51 | ... 6AG5 .64 | ... 6BS8 .53 | ... 6SQ7 .72 | ... 12BQ6 .55 | ... 17D6 1.00 | ... 117Z6 1.05 |
| ... 3CS6 .51 | ... 6AG5 .64 | ... 6BS8 .53 | ... 6T8 .84 | ... 12BQ6 .55 | ... 17D6 1.00 | ... 117Z6 1.05 |

SEND FOR COMPLETE PARTS CATALOG WITHOUT COST USE THIS AD AS ORDER BLANK

UNITED RADIO

CO.
BOX 1000 B
NEWARK, N. J.

TERMS: remit full price plus postage with order. No COD. Mail to Dept. RE. Excess postage will be refunded.

Subject to Prior Sale
\$5 MINIMUM ORDER

CARTOONS

RADIO-ELECTRONICS pays \$3.00 for good cartoon ideas and \$15 and up for finished work.

RADIO-ELECTRONICS

154 West 14th St.

New York 11, N. Y.

ELECTRONICS

Engineering-Technicians

Bachelor of Science Degree, 30 Months

Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Technician (12 Months)
- Industrial Electronics Technician (12 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans
DAY AND EVENING CLASSES

Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name _____
Address _____
City _____
State _____



Missile headed for outer space. Courtesy of Space Technology Laboratories, Inc.

U.S. Air Force Photo

HEALD'S ENGINEERING COLLEGE

Established 1863

Van Ness at Post, RE
San Francisco, Calif.

new BOOKS

FUNDAMENTALS OF NUCLEAR ENERGY AND POWER REACTORS, by Henry Jacobowitz. John F. Rider, Publisher, Inc., 116 W. 14 St., New York 11, N. Y. 6 x 9 in., 118 pp. \$2.95.

Written for technicians and students of physics, this begins with atomic theory, which is explained clearly with the aid of illustrations. The second chapter discusses fission and shows how energy is released. The last two chapters (most of the book) deal with types of reactors and power plants. Large sketches, cutaway drawings and photos show details of actual reactors. Specifications, control systems, cost and output are given.

TRANSISTORS. Saedi, Unlimited, 626 S. Federal St., Chicago, Ill. 8 1/2 x 11 in. 30 pp. \$1.25.

In a brief and elementary manner, this book explains transistor operation. It compares basic transistor circuits with those using tubes and discusses certain types of amplifiers and oscillators. A few pages give servicing hints.—IQ

2-WAY MOBILE RADIO HANDBOOK, by Jack Helmi. Howard W. Sams & Co., Indianapolis and Bobbs-Merrill Co., New York. 5 1/2 x 8 1/2 in. 250 pp. \$3.95.

More than a million vehicles are equipped for radio communication. This book discusses and explains the theory and practice of mobile transmitters and receivers, their alignment and repair. Topics include selective calling, a/c, squelch, antennas and power supplies. The book is directed to those who are already familiar with basic radio. The final chapter tells how to set up shop for servicing two-way radio sets and gives a rundown on the latest test equipment.—IQ

EXPLORATORY ELECTRICITY, by Joseph P. Arnold and Kenneth L. Schank. McKnight & McKnight Publishing Co., Bloomington, Ill. 8 1/2 x 10 in. 104 pp. \$1.25.

This book is written at the level of the junior high student. It begins with an interesting discussion of the work done by electricians, technicians and engineers, then proceeds to a study of electricity and its everyday uses. Experiments with batteries, motors, circuits and radio sets are described. A continuity tester and tube checker are among make-it-yourself items.

A 22-page manual, supplied free to teachers, discusses tools, shop layout, activity boards for experiments, and answers the questions given in the text.

MOON BASE, by T. C. Helvey. John F. Rider Publisher, Inc., 116 W. 14 St., New York 11, N. Y. 5 1/2 x 8 1/2 in. 72 pp. \$1.95

Before attempting anything as hazardous as a manned expedition to the moon, scientists must know conditions

SCHOOL DIRECTORY

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 28 mos. B.S. in electronic engineering obtainable. ECPD accredited, G.I. approved. Graduates in all branches of electronics with major companies. Start February, September, Dorms, campus. High School graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE

Dept. C Valparaiso, Indiana



ENGINEERING COURSES



E.E. Option Electronics or Power Mechanical, Civil & Physics Also in Liberal Arts presented through

HOME STUDY

Resident Classes Also Available If Desired
PACIFIC INTERNATIONAL COLLEGE OF ARTS & SCIENCES

Primarily a correspondence school

5719-M Santa Monica Blvd. Hollywood 38, Calif.

ELECTRONICS

PREPARE FOR A GOOD JOB!
BROADCAST ENGINEER
RADIO SERVICING AUTOMATION

TELEVISION SERVICING
BLACK & WHITE—COLOR

APPROVED FOR VETERANS AND SURVIVORS OF VETERANS
BUILDING AIR CONDITIONED
SEND FOR FREE LITERATURE

BALTIMORE TECHNICAL INSTITUTE
1425 EUTAW PLACE, BALTIMORE 17, MD.

TRANSISTORS



explained in 32 pages of terse copy and modern illustration. Invaluable to Service and Installation Technicians and Students. Available at \$1.25 a copy, 10 copies or more \$1.00 each. Special rates to schools and business firms.

saedi unlimited

626 SOUTH FEDERAL STREET
CHICAGO 5, ILLINOIS

AT LAST! A home study course covering all phases of electric and electronic organ servicing.
A NEW COURSE An extensive course covering every make of organ—repair, regulating, and troubleshooting.

Electronic ORGAN SERVICING

Your Opportunity To Get Into A New, Rapidly Expanding Field At The Start. Don't Miss It!!

WRITE NOW FOR FREE BOOKLET

NILES BRYANT SCHOOL
Dept. E., 3731 Stockton Blvd.
Sacramento 20, California

NHSC Approved * The Pioneer School
Established 1898

LEARN

LEARN
RADAR MICROWAVES
COMPUTERS—TRANSMITTERS
CODE • TV • RADIO
Phila. Wireless Technical Inst.
1533 Pine St., Philadelphia 2, Pa.
A Non-Profit Corp.
Founded in 1908
Write for free Catalog to Dept. RE-10
Classes now forming

engineering degree in 27 months

Grasp your chance for a better life. Rapid advancement. Better income. **BACHELOR OF SCIENCE DEGREE IN 27 MONTHS** in Elect. (Electronics or Power major), Mech., Civil, Aero., Chem., Engineering. **IN 36 MONTHS** in Business Administration (General Business, Acctg., Motor Transport Mgt. majors). Small classes. More professional class hours. Well-equipped labs. Campus. Dorms. Modest costs. Year-round operation. Founded 1884. Enter Jan., Mar., July, Sept., Write J. G. McCarthy, Director of Admissions, for Catalog and "Your Career in Engineering and Commerce" Book.

TRI-STATE COLLEGE 24100 College Ave.
Angola, Indiana

SCIENCE ENGINEERING

BACHELOR'S DEGREE IN 27 OR 36 MONTHS
Accelerated year-round program: Aero., Chem., Civil, Elec., Mech., Metal., Math., Chemistry, Physics. Modest rate. Earn board. New classes start Jan., Mar., June, Sept. Catalog. 15100 E. Washington Blvd., Fort Wayne 2, Ind.

INDIANA TECHNICAL COLLEGE

Learn Transistor Electronics At Home!

■ Prepare now for a profitable career in this growing field. Learn theory, construction and applications of all types of transistors with this proven home-study course from the Philco Technological Center.

FOR FREE INFORMATION
PLEASE WRITE TO:

PHILCO
TECHNOLOGICAL CENTER
"C" and Ontario Sts., Philadelphia 34, Pa.

FREE! ELECTRONICS CAREER KIT

If you're interested in breaking into a good-paying job in Radio-TV-Electronics, I.C.S. will send you absolutely free a famous Career Kit with 3 famous booklets that have helped thousands of others—just like yourself—on the road to real success. Includes:

- 1 "HOW TO SUCCEED" Career Guide — 36-page gold mine of career tips and information.
- 2 "JOB CATALOG" of opportunities in your field of interest.
- 3 "SAMPLE LESSON" (math) to demonstrate the famous I.C.S. method.

Send today for your free I.C.S. Career Kit with these 3 famous booklets. There's no obligation. This may be the big break you've been waiting for. Mark and mail the coupon today.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Dept. 37683J, Scranton 16, Penna.

Please send free Career Kit with 3 famous booklets


- General Electronics Radio-TV Serv'g Practical Electrician
 Industrial Electronics Sound Equip. Serv'g Profess'l Eng. (Elec.)
 Radio-TV Eng'r'g Electrical Eng'r'g Electrical Drafting
 Electronic Servicing Electrical Tech. Other _____

Name _____ Age _____

Address _____

City _____ State _____

FREE CAREER BOOKLET

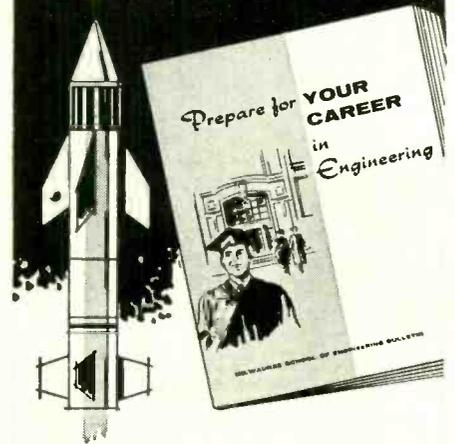

to guide you to a successful future in

ELECTRONICS RADIO-TV COMPUTERS ELECTRICAL ENGINEERING

This interesting pictorial booklet tells you how you can prepare for a dynamic career as an Electrical Engineer or Engineering Technician in many exciting, growing fields:

**MISSILES • RADAR • RESEARCH
ELECTRICAL POWER • ROCKETRY
AUTOMATION • AVIONICS
SALES • DEVELOPMENT**

Get all the facts about job opportunities, length of study, courses offered, degrees you can earn, scholarships, part-time work — as well as pictures of the Milwaukee School of Engineering's educational and recreational facilities. No obligation — it's yours free.

MILWAUKEE SCHOOL OF ENGINEERING

MAIL COUPON TODAY!

MILWAUKEE SCHOOL OF ENGINEERING
Dept. RE-1060, 1025 N. Milwaukee St.
Milwaukee, Wisconsin MS-113

Please send FREE "Your Career" booklet
I'm interested in Electronics Radio-TV
 Computers Electrical Engineering
 Mechanical Engineering
(PLEASE PRINT)

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I'm eligible for veterans education benefits.

Discharge date _____

"TAB" Tubes Tested, Inspected, Boxed
Six Months Guarantee! No Rejects!
NEW & Used Gov't & Mfrs. Surplus!

Orders \$10 or more, Receiving types only ppd. 48 states
 OA2 .80 88J6 .09 12AT7 .59 18S1 1.00
 OB2 .85 88K7 .09 12AT7 .84 117Z6 1.10
 OC3 .85 88L7 1.25 12B6G .04 117A 1.00
 OD3 .35 68N6 .08 12AU7 .09 2D21 2/S1
 OZ4 .50 68QZ 1.10 12AX7 .79 3D23 3.85
 1A7 .80 68Z7 1.25 12BA6 .65 117A 1.00
 1B3 .40 68C4 .70 12B6G .09 4J25 29.00
 1R5 .70 68C5 .09 12BD6 .50 4Z20 35.00
 1S4 .70 68C6 .80 12BE6 .09 4E27 7.00
 1T4 .70 68C6 .49 12BF6 .09 4PR60 20.50

Send \$5 for Catalog
 1U4 3/S1 6H6 3/S1 12BH7 .09 4X150G \$15
 1U5 .75 6J5 .52 12B7 .09 4X250 35.00
 1X2A .08 6J6 .48 12B7 .09 4X500 38.00
 3Q4 .08 6K6 .59 12C6 1.45 58P1 4.98
 3Q5 .08 6K7 .71 12SA7 .04 58P4 4.98
 3S4 .08 6L6 1.19 12S67 .09 3Z7 4.00
 3V4 .08 6S4 .59 12SH7 .09 100T 7.00
 5H4 .08 6S8 .09 12S7 .75 316A 5/81
 5U4 .08 6S7 .09 12S7 .04 316A 3/81
 5V4 .08 6S7 1.10 12S7 .84 416B 4.00

Wanted Surplus Electronics from schools & U
 5Y3 .59 6S7 .08 1986G 2.15 450T 42.00
 6A4 1.39 6S7 .79 19T6 1.10 60T 1.00
 6AC7 .70 6S7 .06 2580E 1.39 809 3.00
 6AG7 .08 6S7 .09 25L6 .09 811 4.40
 6AM6 .01 6S7 .70 25L6 .70 811 3.00
 6AK5 .09 6S7 .09 25Z5 .63 813 0.00
 6AL5 2/81 6S7 2/S1 25Z6 .75 814 3.45
 6AS 63 6S7 .09 25Z6 .39 854 1.10
 6AS7 3.00 6S7 .79 1E37 2.49 826 .59
 6AT6 .09 6T8 .08 32L6 .09 829B 8.00

Wanted 504 TL Tubes! Top \$1 Paid
 6AU4 1.10 6U8 .70 35A4 .09 866A 7.00
 6AU5 1.19 6V6GT .70 35Y4 .09 866A 2.75
 6AU6 .09 6W4 .79 35Z5 .03 1625 5/81
 6AX4 .79 6W6 .81 50A5 .09 6146 4.00
 6BA6 .09 6X4 2/81 50B9 .09 6146 4.00
 6B7 1.00 6X5 .49 50C5 .09 5881 9.70
 6BD6 .09 6Y6 .07 50L6 .09 6550 3.90
 6BE6 .39 7N7 .89 7E65 3.29 5874 1.10
 6BG6 1.50 12AL5 .59 75 .80 5894 12.00
 6BH6 .79 12AQ5 .75 80 .59 7193 10/81

TUBES WANTED! WE BUY! SELL & TRADE!

NEW SILICON 750MA* DIODES TOP HATS
GENERAL PURPOSE 400 PIV. AT 50 MA
SPECIAL 39c 25 FOR \$8

rms/piv 35/50 19c	rms/piv 70/100 29c	rms/piv 140/200 34c	rms/piv 210/300 43c
rms/piv 280/400 80c	rms/piv 350/500 82c	rms/piv 420/600 85c	rms/piv 490/700 85c
rms/piv 560/800 \$1.05	rms/piv 630/900 \$1.25	rms/piv 700/1000 \$1.70	rms/piv 770/1100 \$2.00

* CAPACITOR INPUT DERATE 20%
 \$5 or more this item we pay 1 P.P./U.S.

"NEW" "TEKSEL" SELENIUM RECTIFIERS
FULL WAVE BRIDGE RECTIFIERS. ONE YEAR GTD.
AMP. 18VAC 36VAC 72VAC 144VAC
CONT. 14VDC 28VDC 56VDC 112VDC

1AMP \$ 1.30	2AMP 2.15	3AMP 2.90	4AMP 4.15	10AMP 6.10
5.00	3.00	4.00	6.00	12.15
2.00	3.00	4.00	6.00	12.15
2.00	3.00	4.00	6.00	12.15
2.00	3.00	4.00	6.00	12.15

Write for Complete Rectifier Catalog

NEW Selenium Radio & TV Rectifiers! GTD.
65MA 45c @ 6 for \$2; 100MA 45c @ 12/\$5;
250MA 65c @ 10/\$6; 300MA 88c @ 10/\$8;
500MA \$1 @ 10/\$8
Orders this item \$10 or More, Postpaid 48 States!

NEW POWER CONVERTER
12VDC to 500VDC up to 200MA, 100 Watts; Tap at 250VDC Type C125JE
53% Ht efficiency, low ripple, low full current - Silicon rectifiers
Hi-RI Mag-metal tape wound transformer, fused & short circuit proof, anti in size! Quiet! Light weight! Conservatively built, ready to go. Conservatively Rated, Delco Transistors Heavy Copper Heat-sink. 12VDC to 250VDC up to 150MA Type C1225A \$39.

"SUNTAB" BATTERY-SELENIUM PHOTOCELL

SAP-Round 1 1/4" Dia.	\$1.00
10AP-ROUND 1 1/2" Dia.	\$1.75
15AP-ROUND 2" Dia.	\$3.00
2BP-RECT. 3/8 x 7/16	70c
5BP-RECT. 1-7/16 x 7/8	1.35
10BP-RECT. 1-11/16 x 7/8	2.00
KIT ALL SIX ONE EACH	7.00

ORDER QTY'S. TEN OR MORE DEDUCT 20%
 This Item Shipped Postpaid Orders \$5 Up

"TAB" KITS! "TAB" THE BEST KITS! "TAB"
All Kits Contain Most Popular Valves & Sizes

- | | |
|-------------------------------|----------------------------|
| Kit 2 Eng. Parallel Rules | Kit 5 Sub-Min Tubes |
| Kit 35 Precision Resistors | Kit 40 Standoff Insulators |
| Kit 10 Switches | Kit 35 Power Resistors |
| Kit 75 Resistors 1/2, 3/4, 1W | Kit 100 Ceramic Condensers |
| Kit 150 Carbon Resistors | Kit 5 Crystal Diodes |
| Kit 25 Panel Lamps | Kit 100 Fuses, Assorted |
| Kit 12 Electrolytic Cond's | Kit 100 Germanium Diodes |
| Kit 56 Tube Sockets | Kit 5 FT243 Xtal Holders |
| Kit 65 Tubular Cond's | Kit 8 Silicon Diodes |
| Kit 500 Lugs & Eyelets | Kit 5 Microswitches |
| Kit 10 Bathtub Oil Cond's | Kit 4 Ass'd Rectifiers |
| Kit 5 lbs. Surprise Pckg. | Kit 2 PNP Transistors |
| Kit 10 Xmtr Mica Cond's | Kit 4X50 Ft Hookup Wire |
| Kit 3 Phone/Patch Wires | Kit 2 Veeder Counters |
| Kit 3 Searchlights | Kit 2-Computer Tristodes |
| Kit Circular Slide Rule | Kit High Gain TWT Mike |
| Kit 12 Algrit Clip Ass't'd. | |

BUY 10 KITS - GET ONE FREE! EACH KIT 99c

- TRANSISTORS & ACCESSORIES**
 2N141 \$3, 2N442 \$4.50, 2N277 \$4, 2N278 \$5,
 2N135 \$1.39, 2N178 \$1.80, 2N177 \$1, 2N178 \$1.75,
 2N247 \$1.50, 2N255 \$1.20, 2N270 \$9.95,
 2N274 \$1.25, 2N408 \$1.80, 2N514 \$1.20, 2N741 \$1.80,
 2N579 \$2.20, 2N581 \$1.25, 2N582 \$2.10,
 2N174 \$8.50, 2N143 \$6.50.
 DIAMOND BASE MICA MOUNTING KIT. \$.30
 DELCO ROUND BASE MICA MOUNTING KIT. \$.30
 DELCO POWER HEAT SINK WITH FINS. \$.75

SNOOPERSCOPE TUBE 2" \$5 @ 2 for \$9
 B221 NEW ORIG. SIG CORPS RECALIB. RECONDI-
 TIONED OVERSEA PKCD NEW CALIBRATION \$1.10
 NEW BC1335 26.9 to 38.9 Mc's TRANSCIEVER WITH
 Q412V SUPPLY & SPARES OVERSEA PKCD. \$89
 AN-ARRR HOVLI GOOD COND. tubes. \$1.59
 SEND FOR NEW CATALOG 25c
 CO-AX CIRCUTS PL259A 45c @ 5 for \$2
 HVY DTY 115V/60CY SELSYNS TWO for \$9

"TAB"
 111-50 LIBERTY ST., N. Y. 6, N. Y.
 Send 25c PHONE: RECTOR 2-6245 For Catalog

NEW BOOKS (Continued)

in space and on the moon, and how humans will probably react to them. This authority presents a factual, frank discussion of the technical and psychological aspects. He makes recommendations as to food, air, equipment, medical care, etc. He concludes that the optimum crew would consist of two men and a woman.—IQ

RCA RECEIVING TUBE MANUAL. RCA, Electron Tube Div., Harrison, N. J. 5 1/2 x 8 1/4 in. 432 pp. \$1.

The useful data crammed into this latest edition make it a big dollar's worth. It describes uses, tests and installations of tubes and the design of circuits. About 60 pages at the beginning describe the use of tubes in basic circuits. About 20 more at the end are devoted to practical schematics of amplifiers, radios, power supplies, etc. Detailed characteristics are listed for recommended type tubes. Discontinued and renewal types are identified by being listed in smaller type.—IQ

INTRODUCTION TO ELECTRIC CIRCUITS, by Herbert W. Jackson. Prentice-Hall, Englewood, N.J. 6 x 9 in. 479 pp. \$8.75.

INTRODUCTION TO ELECTRIC ENGINEERING, (3rd ed.), by Robert P. Ward. Prentice-Hall, Englewood, N. J. 6 x 9 in. 372 pp. \$8.50.

Both volumes are highly recommended for their clarity and coverage. Both discuss fundamentals of magnetic circuits, dc and ac networks and measurements.

The first volume is written at the level of technical schools and is well suited for self-study. A chapter on vector analysis prepares the student for chapters on impedance and resonance. There are many numerical examples with answers.

The volume by Ward is more advanced and is directed to majors in electrical engineering. The author uses calculus. Topics include ferromagnetism, magnetic fields and transients. Problems and study questions are included. END

RADIO TV REPAIR

"All that hum needed was a little extra filtering."

OPPORTUNITY ADLETS
 Rates—50c per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for Dec. issue must reach us before October 10, 1960.
RADIO-ELECTRONICS, 154 West 14 St., New York 11, N. Y.

RADIOS. Top Quality. 6-Transistors \$14.95. AM 5-Tube \$8.95. AM-FM \$22.00. Add \$1.00 shipping. MYERS IMPORTS, 623 Gay Knoxville, Tenn.

HI-FI DOCTOR will solve your hi-fi problems on the spot. Acoustic, Audio, Radio Engineer. Stereo Designing. Professional visits, day evening. New York area. WILLIAM BOHN, Plaza 7-8569, weekdays.

PHOTO COPYING—RADIO—TELEVISION PRINTS—Other Services—Information—Calendar 10c. MASTER KIT COMPANY, Box 206, Belleville, Ont.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. HAZELTON INSTRUMENT CO., 128 Liberty Street, New York, N.Y.

AMPEX, Concertone, Crown, Magnecord, Presto, Norelco, Hogen, Tandberg, Sherwood, Itek-O-Kut, Scott, Shure, Dymakit, others... Trades, BOYNTON STUDIO, Dept. RE, 10 Pennsylvania Ave., Tuckahee, N.Y.

DON'T BUY HI-FI COMPONENTS. Kits, Tape, Tape Recorders until you get our low, low return mail quotes. "We Guarantee Not To Be Undersold." Wholesale Catalog Free. HI-FIDELITY CENTER, 1797RC First Avenue, New York 28, N.Y.

COMPONENTS, Recorders, Tapes. FREE Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N.Y.

DISCOUNTS UP TO 50% on Hi-Fi amplifiers, tuners, speakers, tape recorders, individual quotations only, no catalogs. CLASSIFIED HI-FI EXCHANGE, 2375 East 65th Street, Brooklyn 34, N.Y.

LEARN CODE. Quality for Amateur or Commercial License. Free Book, CANDLER SYSTEM, Dept. RE-10, Box 9226, Denver 20, Colo.

PROFESSIONAL ELECTRONIC PROJECTS—Organs, Timers, Computers, etc.—\$1 each. List Free. PARKS, Box 1665, Lake City Station, Seattle 55, Wash.

RADIO & TV TUBES at Manufacturers' Prices! 100% Guaranteed! Brand New! No re-brands or pulls! UNITED RADIO, Box 1000-It, Newark, N.J.

SONGPOEMS and LYRICS WANTED! Mail to: TIN PAN ALLEY, INC. 1650 Broadway, New York 19, N. Y.

LEARN WHILE ASLEEP. Hypnotize with your recorder, phonograph or amazing new Electronic Educator endless tape recorder. Catalog, details free. SLEEP-LEARNING ASSOCIATION, Box 24-RD, Olympia, Wash.

BEFORE YOU BUY RECEIVING TUBES OR ELECTRONIC COMPONENTS, send NOW for your Giant Free ZALYTRON Catalog No. 163—featuring nationally known Zalytron First Quality, TV-Radio Tubes, plus all types of Components, Kits, Amplifiers, Transmitters, etc. All priced to Save you Plenty—Why Pay More? ZALYTRON TUBE CORP., 220 W. 42nd St., N. Y. C.

RADIO & TELEVISION RECEIVING TUBES, brand new, first line name brands only. No rejects, no pulls. Discounts up to 66% off list. EDISON TUBE CO., Menlo Park, N.J.

CASH PAID! Sell your surplus electronic tubes. Want unusual, clean radio and tv receiving, transmitting, special-purpose, Magnetrons, Klystrons, broadcast types, etc. Want military & commercial lab/test and communications equipment such as G.R., I.P., AN/UPM prefix. Also want commercial receivers and transmitters. For a fair deal write BARRY, 512 Broadway, New York 12, N. Y. Walker 5-7000.

\$5-\$10 hour with your recorder. AUDIOGRAPHIC LABORATORIES, 2913 Santa Fe, Independence, Mo.

NEW RADIO-TV TUBES. Brand New. Automobile Radios Wholesale. SELCO PRODUCTS, Danvers 24, Mass.

DIAGRAMS FOR REPAIRING RADIOS \$1. Television \$2. Give make, Model, DIAGRAM SERVICE, Box 672 RE, Hartford 1, Conn.

NEW CONCEPT OF LEARNING SELF-HYPNOSIS! Now on tape or record! Free Literature. MCKINLEY-SMITH CO., Dept. T5, Box 3038, San Bernardino, Calif.

QUALITY PRINTING. Economically priced. Speedy service. Free samples on request. JOHN H. TAYLOR, R. D. 2, Box 215, West Middlesex, Pa.

MANUFACTURING AND PURCHASING ELECTRONIC PRODUCTS IN JAPAN. Every \$ spent overseas must return as export orders for some stateside product. Buying in Japan helps establish freedom, your profit, and me. Order thru or send inquiries to ALNOLD WOLFEVITON, of New Sakuragaoka Bldg., No. 2 Hanchi, Sakuragaoka, Shibuya, Tokyo, Japan. "Cable address TELLURUME TOKYO." (Also am looking for distribution contacts for new electronic products).



FREE!

Lafayette Radio's 324 PAGE 1961 Catalog

America's "Electronics & Hi-Fi Shopping Center"

40 years of service to Audiophiles, Experimenters, Hobbyists, Engineers, Technicians, Students, Servicemen and Dealers. **HERE IT IS** — the biggest, best and most comprehensive catalog you can ask for. Choose from thousands of items, all available for immediate delivery at the lowest, money-saving prices. And, as always, **SATISFACTION GUARANTEED OR MONEY REFUNDED.**

"The Best Buys In The Business"

- Stereophonic Hi-Fi Equipment
- Public Address Systems
- Tape Recorders
- Radio and TV Tubes and Parts
- Citizen Band Equipment
- Amateur Equipment
- Industrial Supplies

Exclusive at Lafayette. Lafayette Kits: Build a path to a new world of entertainment. Created, designed and engineered for top quality at top performance — there's more fun in doing it yourself, especially when it's so easy. An exclusive product of Lafayette Electronics — easily the best value for your money any day.

PLUS Hundreds of "specials" you'll find only at Lafayette.

Easy Pay Plan. The simplest, and quickest way to get what you want, when you want it. As little as \$2 down . . . up to 24 months to pay.


Mail the coupon today for your **FREE** copy of Lafayette Radio's 1961 catalog.



KT-650 FM Tuner Kit
54.50




TE-15 Tube Checker
19.95

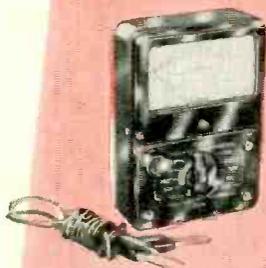

RW-60 20,000 Ohms Per Volt Multimeter
13.50



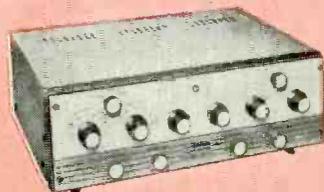RE-400 2-Speed Portable Tape Recorder
43.50



Stereo Control Center
KT-600, Kit 79.50
LA-600, Wired 134.50



Communications Receiver
KT-200, Kit HE-10, Wired
64.50 79.95



Lafayette Radio Electronics Corp.
Dept. JJ-6, P.O. Box 190
Jamaica 31, N. Y.

Send me the **FREE** Lafayette 324 page 1961 catalog 610

Name.....

Address.....

City..... Zone..... State.....


**Emergency
Industry
Farming
Pleasure**

NEW! LAFAYETTE HE-15A 2-WAY SUPERHET CITIZENS BAND TRANSCEIVER!



**Completely
Wired -
NOT A KIT!**

Made in U.S.A.

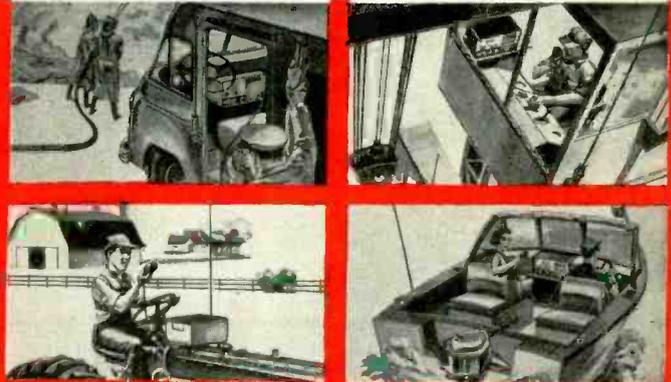

Not Superregenerative but SUPERHET!


COMPLETE 2-WAY COMMUNICATIONS FOR
BUSINESS, HOME, FARM, BOAT, AND SPORTS
NOW WITH ADDED FEATURES

- Effective Full-Wave Variable Noise Limiter • Five Prong Microphone Jack For Easy Relay Addition • RF Jack on Front Panel
- AND
- 5 Transmitting Positions • Tuneable Receiver Over Full 23 Channels • Planetary Vernier Tuning • Complete with Transmitting Crystal for Channel 9

CITIZENS BAND — The New Two-Way Personal Communications Method for Everyone — Fill out the FCC form enclosed with each Lafayette Transceiver. No examination or technical knowledge required — Any citizen 18 years or older is eligible for a license.

THE GREATEST VALUE in the CITIZENS BAND FIELD
Just think . . . now you can have economical, efficient 2-way radio communication from your home, office, store, auto, truck or boat . . . literally hundreds of uses. The Lafayette HE-15A Superheterodyne Transceiver is both a compact precision transmitter and receiver designed to operate on the new class D "Citizens Band." Two or more of these units furnish your own communications system covering up to a 20 mile or more radius depending on antenna height and terrain.
The Lafayette HE-15A meets all FCC requirements and operates in much the same manner as police and other short-wave communications systems. The Transceiver features 5 crystal controlled transmitting channels operating at a maximum legal power input of 5 watts fully modulated, RF stage in both transmitter and receiver. The 5 position crystal selector on the front panel selects any one of 5 transmitting frequencies. These 5 crystals are readily accessible by means of a removable front plate. The superheterodyne receiver is tuneable over the full 23 channel band with 3 watts audio output, AVC, and an amazingly effective Full-Wave Variable Noise Limiter. The noise limiter is continuously variable from the front panel for diminishing ignition and other unwanted noise pickup. A new 5 prong microphone jack makes

57⁵⁰
ONLY
5.00 Down

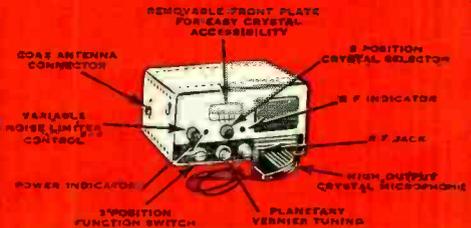

conversion to a push-to-talk relay a cinch. RF jack on the front panel may be used to monitor the current in the final tube using external meter.

Controls include a 3 position function switch (transmit, receive, and transmit with spring return), planetary vernier tuning plus variable noise limiter. Output impedance matches 52 and 72 ohm antenna with Amphenol type coax connector. Has large 4" PM speaker; input jack for crystal or ceramic microphone; power receptacle in rear for AC line and 6 or 12 volt external power supply. Supplied with single transmitting crystal for channel 9, high output crystal microphone, and brackets for easy mounting of units in auto, boat, etc. Operates on 115 volts AC. Addition of 6 or 12 volt power supply (separately supplied) adapts transceiver, for mobile operation. Size 10 1/4" W x 5 1/2" H x 6 3/8" D. Tube complement: 2-6U8A/6EA8, 1-6AL5, 16V6, 1-12AX7, 1-6AW8. Shpg. wt., 11 lbs.

- HE-15A 5.00 Down Net **57.50**
- POWER SUPPLY:** Adapts HE-15A for mobile operation. Complete with cable, 6 or 12 volt vibrator and mounting flanges. Completely enclosed. Size 4 1/4" D x 6" W x 4" H. Shpg. wt., 4 lbs.
- HE-16 For 12 Volts Net **10.95**
- HE-18 For 6 Volts Net **10.95**
- TRANSMITTING CRYSTALS:** For any of the 23 channels. Specify channel or frequency.
- HE-830 Net **1.95**



6.95

SENSATIONAL LAFAYETTE CITIZEN BAND MOBILE ANTENNA

THE SCOOP BUY FOR CITIZENS BAND MOBILES

- CHROME SWIVEL BASE
- PLUS
- STAINLESS STEEL SPRING
- PLUS
- 102 1/2" STAINLESS STEEL WHIP FOR OPTIMUM 11 METER PERFORMANCE

Chrome swivel ball mount base designed to be mounted on any surface. Stainless steel spring holds rod in properly adjusted position and prevents rod damage from shocks and blows. Stainless steel whip for maximum resiliency and strength. Shpg. wt., 4 lbs.

HE-800WX Net **6.95**

NEW! LAFAYETTE TELESCOPIC CITIZENS BAND WHIP ANTENNA

- Chrome Plated
- Telescopes From 16 1/2 to 40"
- Mounts Vertically or Right Angle

3.95

An outstanding antenna value. This high quality three section telescoping antenna is designed for attachment directly to your citizens band transceiver. Ideal for point to point service over short distances. Molded base loading coil has a threaded stud with a PL-259 plug—connector for vertical or right angle mounting. Shpg. wt.; 1 lb.

HE-19 Net **3.95**



NEW! 10,000 OHMS PER VOLT MULTITESTER

Outperforms Instruments Many Times Its Size

9.95

- Extra Large 3 1/2" Meter Face
- Completely Wired and Tested
- All Accessories Included

A convenient, pocket-sized instrument with an unusually sensitive 14,000 ohms-per-volt AC-DC meter, 1% resistors, single range selector switch. First capacity range requires 120V AC, second range requires 6V AC. Durable Bakelite case and panel; probes and flexible leads are plastic coated and color coded. Complete with battery. 4 1/2" x 3 1/2" x 1 1/8". Shpg. wt., 1 1/2 lbs.

TE-10 Net **9.95**
TE-14 Pigskin Carrying Case, shpg. wt., 8 oz. Net **1.95**

NEW! LAFAYETTE RADIO FIELD INDICATOR

- Provides a Continuous Indication of Transmitter Output
- Rugged 200 ua Meter Movement • Completely Portable
- Requires no Electricity, Batteries or Transmitter Connection.

With this rugged, new radio field indicator you can check performance of your marine, mobile or fixed transmitter . . . actually measures the RF field generated by any transmitter between 100KC and 250MC regardless of power. Features a 200 ua meter movement with a variable sensitivity control. Phone jack at rear of indicator accepts earphones thus providing an aural check of transmitter output. Antenna extends from 3/4 to 10 3/4". Powerful magnet on bottom plate allows easy mounting on car dashboard or metal surfaces. Use anywhere . . . requires no electricity or batteries. Dimensions: (less antenna) 3 1/4" W x 2 1/4" H x 2" D.

TM-14 Net **7.95**



PLEASE INCLUDE SHIPPING CHARGES WITH ORDER

**LAFAYETTE
RADIO**
165-08 LIBERTY AVENUE JAMAICA 33, NEW YORK

NEW YORK, N. Y.
100 6th Avenue

NEWARK, N. J.
24 Central Avenue

BRONX, N. Y.
542 E. Fordham Rd.


PARAMUS, N. J.
182 Route 17
(1 Mi. North Garden State Plaza)

BOSTON, MASS.
110 Federal Street

PLAINFIELD, N. J.
139 W. 2nd Street

LAFAYETTE
HI-FI KITS

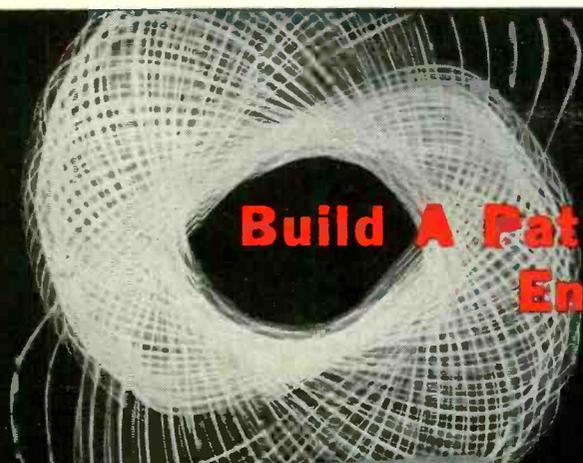Build A Path to A New World of Entertainment



KT-250A
50-WATT STEREO AMPLIFIER... 74.50



KT-500A
FM-AM STEREO TUNER... 74.50



KT-630A
STEREO PREAMPLIFIER... 79.50



KT-680 FM TUNER... 94.00



KT-236A
36-WATT STEREO AMPLIFIER... 59.50



KT-595 100-WATT
BASIC STEREO AMPLIFIER... 134.50

MONEY-BACK GUARANTEE
Lafayette Kits are exclusive products of Lafayette Electronics. Each Lafayette Kit must meet or exceed its published specifications, or your money is refunded in full.

ENGINEERING:

Created with the non-technical builder in mind. There's much more fun in assembling your own kit... and it's so easy.

DESIGN:

Each kit has the fine professional-looking touch. Styled to blend with every decor.

VALUE:

You can't get better units at these money-saving prices.

QUALITY:

Top performance due to high quality parts and engineering.




All Lafayette Kits are Available on the Easy Pay Plan.

Lafayette Radio Dept. JI-6
P.O. Box 190 Jamaica 31, N.Y.

Send me the **FREE 324-Page**
1961 Catalog No. 610

**CUT OUT
AND PASTE
ON POST
CARD**

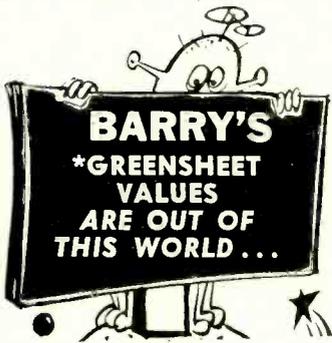Name _____
Address _____
City _____ Zone _____ State _____



* A complete catalog of specialized industrial Electronic TUBES and COMPONENTS... featuring Barry Electronics savings to Industry, Servicemen and Experimenters.

We have thousands of tube types in stock. First Quality at Sensible Prices. Buy with confidence.

Prove these values to yourself! Complete and mail the coupon below for your copy of the "Greensheet."

We'll also purchase your equipment and unused tubes. Send details: BARRY ELECTRONICS CORP. 512 Broadway, New York 12, N.Y. Dept. RE10.

Please send me a copy of the "Greensheet" and add my name to your mailing list.

(RE10)
 Name..... Title
 Company.....
 Address.....
 City..... State

A NOTE TO THE HI-FI BUYER
 AIR MAIL us your requirements for an IMMEDIATE LOWEST PRICE QUOTATION Components, Tapes and Records SHIPPED PROMPTLY AT LOWEST PRICES
WRITE TODAY FOR FREE CATALOG
AUDIO 714-R Lexington Ave.
UNLIMITED New York 22, N. Y.

FREE! CATALOG OF HI-FI, RADIO, TV PARTS & ACCESSORIES — yours for the asking!
Vidair ELECTRONICS MFG. CORP.
 44 CHURCH ST. • BALDWIN, N. Y.



... for their permanent mailing-list to receive advance information on all new electronic kit developments—

- TEST and MEASURING INSTRUMENTS
- HI-FI STEREO COMPONENTS
- HI-FI SPEAKER SYSTEMS
- MARINE INSTRUMENTS
- AUTOMOTIVE EQUIPMENT

When you want **PRECISION**-made electronic equipment (kits or wired), you want **PACO!** For your personal copy of the NEW 1961

PACO Catalog. WRITE:
PACO ELECTRONICS CO., INC.
 70-31 84th Street, Glendale 27, L. I., New York
 Kit Division of **PRECISION Apparatus Co., Inc.**
 a subsidiary of **Pacotronics, Inc.**

SERVICEMEN ←
T. V. and RADIO TUBES
 ALL TOP NAME BRANDS
 60-10-5% New—first quality—regular boxed—No Jobs, closeouts or pull-outs. SEND for catalog.
 (Representatives wanted for all states. High commission.)
RADIO TUBE SPECIALISTS
 397—7th Ave., Brooklyn 15, N.Y.

ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

Airex Radio Corp.	112
Allied Radio Corp.	13, 80, 81, 122
Almo Radio Company	128
Amphenol-Borg Electronics Corp.	10
Arkay International Inc.	96
Astaire Corp.	3rd Cover
Audio Empire	117
Audio Unlimited Inc.	136
Audion	96
B & K Mfg. Company	66, 67
Barry Electronics Corp.	136
Bell Telephone Labs.	22
Blonder-Tongue Labs.	30
Bonafide Radio	96
Brooks Radio & TV Corp.	121
Burstein-Appleebe Co.	125
Capitol Radio Engineering Inst.	102-105
Carlson Studios	122
Castle TV Tuner Service	126
Center Industrial, Inc.	124
Centralab Div. of Globe Union	78
Chemical Electronic Engineering	101
Chicago Standard Transformer Corp.	28
Cleveland Institute of Electronics	11
Commissioner Electronics Co.	66
Coyne Electrical School	89, 118
CREI-Atomics	106
Crown Electric Products Co.	127
DeVry Technical Institute	7
Dressner	97
Dynaco Inc.	116
Dyna-Empire	117
Electro Products Labs.	118
Electro-Voice, Inc.	99
Electronic Chemical Corp.	89
Electronic Instrument Co.	31, 32
Electronic Measurement Corp.	112
Electronic Publishing Co., Inc.	117
Fair Radio Sales	128
General Electric Co. (Electronics Components Div.)	94, 95
Granham School of Electronics	15
Haltcrafters	97
Harman-Kardon	24, 25
Head Engineering College	130
Health Company	62, 63, 64, 65
Holt, Rinehart & Winston Inc.	101, 124, 126
Homewood Industries	128
Hudson Specialties Co.	125
Illinois Condenser Co.	129
Indiana Technical College	67
Jerrold Electronics Co.	12
Key Electronics Co.	67
Lafayette Radio	133, 134, 135
Mercury Electronics	79, 108
Mid-American Relay Systems, Inc.	120
Mohawk Business Machines	118
Moss Electronic Inc.	90, 91
National Radio Institute	3, 19-20, 127
National Technical Schools	5
North American Phillips Co., Inc.	129
Ohmatsu Electric Co., Ltd.	96
Olson Radio Corp.	117
Opportunity Artists	132
Oxford Components, Inc.	72
PACO Electronics Co., Inc.	136
Peak Electronics Co.	119
Perma-Power Company	16
Picture Tube Outlet	113
Progressive "Edu-Kits" Inc.	110
RCA Electron Tube Div.	Back Cover
RCA Institutes	69-70, 120, 136
RCA Test Equipment Div.	100
Rad-Tel Tube Co.	123
Radio Shack Corp.	119
Radio Tube Specialties	134
Radio TV Training School	27
Reh-O-Kut Co., Inc.	87
Rinehart & Co., Inc.	101, 124, 126
Rohn Mfg., Co.	8
Sams (Howard W.) & Co., Inc.	29, 114, 115
Scholer Organ Co.	126
Scott, (H. H.) Inc.	21
Service Instruments Corp. (Sencore)	74, 75
Shure Brothers, Inc.	108
Sonotone Corp.	26
Sprague Products Co.	14
Stotts-Friedman Co.	122
Stromberg-Carlson	17
Superior Instruments Co.	112
Switchcraft, Inc.	113
Sylvania Electric Products Inc.	85
T. A. B.	132
Sarkis Tarzian, Inc.	109, 134
Thorens Co.	23
Trlad Transformer Corp.	127
Triplet Electrical Instrument Co.	2nd Cover
Tung-Sol Electric Co.	98
The Turner Microphone Company	111
United Radio Company	130
Vaco Products Company	124
D. Van Nostrand Co., Inc.	9, 122
Vidair	136
Vocaline Co. of America	18
Xcelite, Inc.	97






To Learn Some
 Vital Facts
 About Your Career
 In Electronics
 See Page 70

SCHOOL DIRECTORY PAGE 131

Baltimore Technical Institute
Niles Bryant School
Indiana Technical College
International Correspondence School
Milwaukee School of Engineering
Pacific International College of Arts & Sciences
Phila. Wireless Technical Institute
Philco Technological Center
Saedi Unlimited
Tri-State College
Valparaiso Technical Institute

ADVERTISING REPRESENTATIVES: Los Angeles:
 Harker-Husted-Coughlin, 400 South Alvarado St., Tel. DUNKirk 7-2328. **San Francisco:** Harker-Husted-Coughlin, 444 Market St., Tel. GRARfield 1-0151. **Chicago:** 8631 East Prairie Road, Skokie, Ill., Tel. ORchard 5-3740.

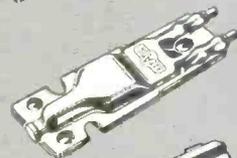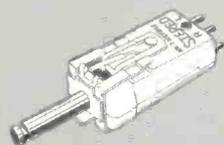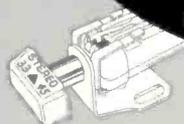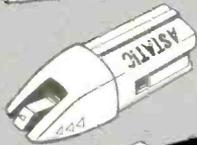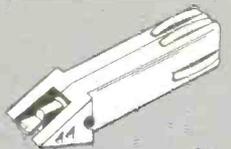FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4.



GO BY BRAND
GO BUY ASTATIC

YOU WOULDN'T GO
AFTER THE "BIG ONES"
WITH

"Bent Pin"

FISHING TACKLE



... and you can't go after big cartridge business without
ASTATIC

THE ONLY, REPEAT ONLY, COMPLETE PHONO CARTRIDGE LINE

Whether you sell, install or use phono cartridges, you're ahead with the one dominant name in the industry — ASTATIC. Only Astatic can give you, on every single replacement, the ORIGINAL or DIRECT REPLACEMENT cartridge that exactly matches the other components of the player.

AND VERY OFTEN THE PRICE IS BELOW THAT OF SUBSTITUTES. This is the one sure way to best results, to fullest quality and fidelity of sound reproduction. THIS IS THE ONE SOURCE OF MAXIMUM SALES AND PROFITS FOR YOU.

IT'S BETTER BUSINESS TO SELL ASTATIC
LEADER WITH ORIGINALS — FIRST WITH REPLACEMENTS

ASTATIC CERAMIC AND CRYSTAL PHONO CARTRIDGES: STEREO AND MONAURAL, PLUG-IN AND CONVENTIONAL, WITH DIAMOND OR SAPPHIRE STYLI



THE **Astatic** CORPORATION, CONNEAUT, OHIO

KNOWN THE WORLD OVER



IN CANADA: CANADIAN ASTATIC, LIMITED, TORONTO, ONTARIO
EXPORT SALES: ROBURN AGENCIES, INC., 431 GREENWICH ST.
N. Y. 13, N. Y., U. S. A.

FIRST NAME IN PHONO CARTRIDGES, NEEDLES, MICROPHONES

FACTS



to help you sell more
RCA Silverama Picture Tubes

... the All-New replacement picture tubes that command premium price and profits.

Here are the facts—proof that RCA Silverama is your customers' best picture tube buy.

1 FREE OF GLASS DEFECTS. Glass cord lines, scratches, chips, or buffed faceplates are common defects found in many brands of tubes made with used glass. Surest way to avoid these defects and also obtain the latest optical advances in faceplate engineering: an All-New RCA Silverama!

2 ALL-NEW. Of the three largest selling brands of replacement TV picture tubes, only RCA Silverama is guaranteed 100% all-new—new glass, new gun, new phosphor, new everything! You'll get written proof—right on the warranty card.

3 FINEST SCREEN QUALITY. Advanced screen coating and bonding processes combined with RCA's giant vibration-free screen settling machines assure the maximum in picture screen quality and uniformity.

4 RCA "KNOW-HOW" RCA's continuous product research and advanced design engineering have resulted in RCA Silverama picture tubes being steps ahead of all other brands.

5 WORLD'S FINEST. RCA Silverama is manufactured in the world's most modern manufacturing plant using all-new premium-quality materials. Result: RCA Silverama is the world's finest picture tube.

© Silverama

RCA Electron Tube Division, Harrison, New Jersey



The Most Trusted Name in Electronics
RADIO CORPORATION OF AMERICA