

# Radio-Electronics

MASTER

1964

SEPT. 50c

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACK, Editor-in-chief

GERNSBACK PUBLICATION

## Better Transistor Ignition Shooting Sweep and Sync Trouble How to Use the Q-Meter

MASTER

M/P

84

M  
A  
S  
T  
E  
R



M  
A  
S  
T  
E  
R

301.0575

REPLACES  
6DA6  
IF  
TUBE

### Superselective Adapter

PAGE 46

MASTER

www.americanradiohistory.com

CHARLES WATTS 10-64  
8595 WELLS ROAD  
CINCINNATI 42 OHIO



## How to replace top quality tubes with identical top quality tubes

Most of the quality TV sets you are presently servicing were designed around special Frame Grid tubes originated by Amperex. More and more tube types originated by Amperex are going into the sets you'll be handling in the future.

Amperex Frame Grid tubes provide 55% higher gain-bandwidth, simplify TV circuitry and speed up your servicing because their extraordinary uniformity virtually eliminates need for realignment when you replace tubes.

Amperex Frame Grid Tubes currently used by the major TV set makers include:

2ER5	2GK5	2HA5	3EH7	3GK5	3HA5	4EH7	4EJ7	4ES8	4GK5	4HA5	5GJ7
6EH7	6EJ7	6ER5	6ES8	6FY5	6GJ7	6GK5	6HA5	6HG8	7HG8	8GJ7	

If your distributor does not yet have all the Amperex types you need, please be patient—in some areas the demand keeps gaining on the supply.

Amperex Electronic Corporation, Hicksville, Long Island, New York 11802.



# RADIO SHACK® BREAKS THE PRICE OF FAMOUS-MAKE SOLID-STATE ( MADE in U.S.A. ) PUBLIC ADDRESS EQUIPMENT!

At All **36** RADIO SHACK STORES Coast to Coast

## CALIFORNIA

BAKERSFIELD — 1308 19th St.  
DOWNEY — Stonewood Shop. Ctr.  
LA MESA — Grossmont Shop. Ctr.  
LONG BEACH — 127 W. 7th St.  
SAN LEANDRO — Bay Fair Shop. Ctr.

## NEW YORK

NEW YORK — 1128 Ave. Americas  
SYRACUSE — 3057 Erie Blvd. East

## TEXAS

DALLAS — 1601 Main St.  
FORT WORTH — 1515 So. Univ. Dr.  
HOUSTON — 2315 Travis St.  
HOUSTON — 322 Northline Mall  
SAN ANTONIO — Wonderland Ctr.  
WACO — 1016 Austin Ave.

## ILLINOIS

CHICAGO — Evergreen Park, 95th St.

## OHIO

CINCINNATI — 852 Swifton Ctr.

## PENNSYLVANIA

PHILADELPHIA — 1128 Walnut St.

## MAINE

PORTLAND — Pine Tree Shop. Ctr.

## MINNESOTA

ST. PAUL — 16 E. 6th St.

## VIRGINIA

ARLINGTON — Washington-Lee Ctr.

## WASHINGTON

SEATTLE — 2024 3rd Ave.

## CONNECTICUT

NEW HAVEN — 92 York St.  
STAMFORD — 28 High Ridge Rd.  
WEST HARTFORD — 39 So. Main St.

## NEW HAMPSHIRE

MANCHESTER — 1247 Elm St.

## RHODE ISLAND

CRANSTON — 1301 Reservoir Ave.

## MASSACHUSETTS

BOSTON — 167 Washington St.  
BOSTON — 594 Washington St.  
BOSTON — 110 Federal St.  
BRAintree — South Shore Plaza  
BROOKLINE — 730 Commonwealth  
CAMBRIDGE — Fresh Pond Ctr.  
FRAMINGHAM — Shoppers' World  
LOWELL — Central Shop. Plaza  
SAUGUS — New England Shop. Ctr.  
SPRINGFIELD — 1182 Main St.  
WORCESTER — Lincoln Plaza



JUST IN TIME FOR ELECTIONS!



## SPECIAL PURCHASE SALE 15-30-60 WATT PUBLIC ADDRESS AMPLIFIERS

### ALL-TRANSISTOR 15 WATT

117V PLUS 12V  
AMPLIFIER

National Cat. Price:	Dealers' Net Price
<b>149<sup>95</sup></b>	<b>89<sup>97</sup></b>

In Lots of 3 or More	Bought Individually
<b>44<sup>95</sup></b>	<b>49<sup>95</sup></b>

MODEL 1500: 117 VAC, 50/60 cps plus 12 VDC; 40W; 500 ma idling current (battery). Includes AC/DC cables and cigar lighter attachment! 15W RMS, 30W IHFM, 4-8-16 ohms, and 70.7V. Controls: 3 gain, tone, scratch, power. Case included! 10 1/4 x 4 3/4 x 10 1/2"

### ALL-TRANSISTOR 30 WATT

PUBLIC ADDRESS  
AMPLIFIER

National Cat. Price	Dealers' Net Price
<b>277<sup>50</sup></b>	<b>163<sup>50</sup></b>

In Lots of 3 or More	Bought Individually
<b>69<sup>95</sup></b>	<b>79<sup>95</sup></b>

MODEL 3000: 30W RMS, 42W peak. Common features: 20-20,000 cps 2 db. under 2% total HD; outputs 4-8-16-50 ohms, 25-50-70.7 volts; 11 transistors, 4 diodes; 12 controls — gain, 3 mike gain, fader gain, 2 anti-feedback; bass; treble; rumble; scratch; power; 6 connectors; pilot light; fused 150W outlet; 117 VAC 50/60 cps (# 3000 — 1A, # 6000 — 2A). Case included! 13 1/2 x 5 3/4 x 11 1/2"

### ALL-TRANSISTOR 60 WATT

PUBLIC ADDRESS  
AMPLIFIER

National Cat. Price	Dealers' Net Price
<b>308<sup>00</sup></b>	<b>184<sup>00</sup></b>

In Lots of 3 or More	Bought Individually
<b>89<sup>95</sup></b>	<b>99<sup>95</sup></b>

MODEL 6000: 60W RMS, 84W peak. Common features: 20-20,000 cps 2 db. under 2% total HD; outputs 4-8-16-50 ohms, 25-50-70.7 volts; 11 transistors, 4 diodes; 12 controls — gain, 3 mike gain, fader gain, 2 anti-feedback; bass; treble; rumble; scratch; power; 6 connectors; pilot light; fused 150W outlet; 117 VAC 50/60 cps (# 3000 — 1A, # 6000 — 2A). Case included! 13 1/2 x 5 3/4 x 11 1/2"

## REALISTIC WEATHERPROOF PAGING and TALK-BACK SPEAKER



- 360° Locking Swivel!
- Built-in 70.7V Transformer!

**17<sup>95</sup>**

2 for 34<sup>95</sup>

Our own entirely new American-made Realistic 15 watt P.A. speaker! Lab tested superior at our price! Indestructible, non-resonant, weatherproof! 45 ohm tap. 40-1219E

## P. A. AMPLIFIER ACCESSORY SALE



(A) Remote Level Control for 1-3 mikes up to 1000' from amplifier, mikes or speakers. Includes 50' of cable. List: \$49.95 ..... #32-1032: 19.95  
(B) Rack Mounting Kit for installing amplifier in standard 19-inch relay rack. Finish matches amplifier. Model RR-29. List: \$19.25 ..... #32-1033: 9.95  
(C) Wall Mounting Kit: For extra convenience, adjusts to various angles; permits easy control access. All metal. Model WM-28. List: \$22.50 ..... #32-1034: 9.95  
(D) Microphone Input Transformer permits use of low-impedance mikes. Plugs into amplifier. Model AIT-37. List: \$37.95 ..... #32-1035: 14.95

### FREE RADIO SHACK 1965 CATALOG

Get yours at the Radio Shack store nearest you or write:  
Radio Shack, 730-A Commonwealth Ave., Boston 17, Mass.  
Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



# Radio-Electronics

SEPTEMBER 1964 VOL. XXXV No. 9

Over 55 Years of Electronic Publishing

## EDITORIAL

- 33 The Picturephone in Your Future .....Hugo Gernsback

## AUDIO-HIGH FIDELITY-STEREO

- 36 Super Communications Network for Your Home .....Arthur Schlang  
*Flexible intercom-paging-music system you can build*
- 56 Push-Pull Output from One Transistor .....Leonard E. Geisler  
*New meaning for "single-ended push-pull"!*
- 57 Dynamic Limiting with a Photoresistor
- 72 Equipment Report: Lafayette LA-200 and Knight KN999  
*Two all-transistor integrated stereo amplifiers*

## ELECTRONICS

- 34 Zenerless Transistor Ignition .....William C. King  
*Three transistors and a few other small parts in easy-to-build unit*
- 44 Psycho-Command and Psycho-Reaction .....J. F. Dusailly  
*Brain waves light a lamp at a distance*

## GENERAL

- 43 Potentiometer Features Build-in Vernier
- 50 Radio-Electronics Goes to the World's Fair  
*A picture tour of electronics at the Fair*
- 55 Terminal and Control Markings on Foreign Radios .....Peter E. Sutheim
- 59 What's your EQ?

## RADIO

- 45 Ac-De Radio Voltages Pretty Constant from Set to Set .....Philip Lacy
- COVER STORY 46 Add a Super-Selective Mechanical Filter .....R. E. Berge  
*Steep, flat-top i.f. curve can even separate upper and lower sidebands*
- 60 Money In Electronics Afloat .....Robert C. Beard  
*Marine radio needs You!*

## TELEVISION

- 53 Vertical Sweep and Sync Troubles .....Jack Darr  
*How the circuits work, what the symptoms mean*
- 57 Peewee Learns Sound Reasoning .....Mike Wayne  
*A vtm does some signal tracing to find an intermittent*
- 62 Service Clinic .....Jack Darr  
*Capacitors are cooperative*

## TEST INSTRUMENTS

- 40 Using the Q Meter .....Donald E. Bowen  
*How this lab essential works, and how to make it work for you*
- 49 Better Scope Transistor Checker .....Robert G. Warner
- 78 Equipment Report: Olson TE-179 and Hickok 235A  
*30,000-ohm-per-volt multimeter and a portable uhf/vhf field-strength meter*

## THE DEPARTMENTS

101 Corrections  
23 Correspondence  
110 New Books  
90 New Literature  
106 New Patents

84 New Products  
80 New Semiconductors & Tubes  
6 News Briefs  
100 Noteworthy Circuits

92 Technicians' News  
82 Technotes  
102 Try This One  
59 50 Years Ago



Member,  
Institute of High Fidelity  
Radio-Electronics  
is Indexed In  
Applied Science  
& Technology Index  
(Formerly  
Industrial Arts Index).

HUGO GERNSBACK, editor-in-chief and publisher. M. HARVEY GERNSBACK, editor. Fred Shunaman, managing editor. Robert F. Scott, W2PWG, technical editor. Peter E. Sutheim, associate editor. Jack Darr, service editor. I. Queen, editorial associate. John J. Lamson, eastern sales manager. Wm. Lyon McLaughlin, technical illustration director.

GERNSBACK PUBLICATIONS, INC., 154 W. 14 St., N.Y. 10011. AL 5-7755. Board Chairman Hugo Gernsback, President M. Harvey Gernsback, Secy. G. Atiquo, Treas. Charles A. Raibin

# Choose Your Tailor-Made Course in N.T.S. "PROJECT METHOD" ELECTRONICS!

Now! N.T.S. — one of America's oldest leading home-study and resident technical schools — offers you GREATER CAREER OPPORTUNITIES IN ELECTRONICS. N.T.S. "Project Method" home training lessons are shop-tested in the Resident School in Los Angeles. You work on practical job projects, learn to use shop manuals and schematics. Your N.T.S. training is individual. You proceed at your own pace. The Schools' practical methods, plus more than 60 years of experience, have helped thousands of students all over the world to successful careers. Prepare now for a secure future in one of 8 N.T.S. Electronics Courses designed to fit your own particular needs.



Work on the electronic "brains" of industry — computers, data processing and other automation equipment. Become a TV-Radio Technician, an electronics field engineer, or succeed in your own business.

## CHOOSE YOUR FIELD — INSURE YOUR FUTURE!

- 1 ELECTRONICS-TV-RADIO-SERVICING & COMMUNICATIONS** A basic course thoroughly covering fundamentals of electronics, radio, TV servicing and communications.
- 2 MASTER COURSE IN ELECTRONICS-TV-RADIO, PLUS ADVANCED TV & INDUSTRIAL ELECTRONICS** This course covers everything included in Course No. 1 plus Automation and every phase of the Electronics industry.
- 3 FCC LICENSE** Preparation for this government license essential for interesting jobs in radar, radio, television, communications, guided missiles, many others. Upon completion of this course, if you do not pass the FCC exam for a 1st Class Commercial Radiotelephone License your tuition will be refunded.
- 4 RADIO SERVICING (AM-FM-Transistors)** Train for radio sales and service with dealer or distributor.
- 5 TELEVISION SERVICING (Including Color)** Covers installation, adjustment, repair and servicing of black and white and color television . . . prepares you for your own sales and service business.
- 6 STEREO, HI-FI AND SOUND SYSTEMS** A growing field. Prepares you to build, install and service modern sound equipment for home or industry.
- 7 BASIC ELECTRONICS** Gives you the fundamentals you must know to build on for a future Electronics career. Also offers an excellent background for Salesmen, Purchasing Agents, and others in Electronics.
- 8 ELECTRONICS MATH** Simple, easy-to-follow instructions in the specialized math you need in many electronics jobs.



### CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training in our famous Resident School at Los Angeles in Sunny Southern California. N.T.S. is the oldest and largest school of its kind. Associate in Science Degree also offered in our Resident Program. Check Resident School box in coupon for full details.

### HIGH SCHOOL AT HOME

Learn easily. New modern method. National also offers accredited high school programs for men and women. Take only subjects you need. Study at your own pace. Latest approved textbooks—yours to keep—everything included at one low tuition. Check High School box in coupon for information.



### MAIL COUPON TODAY FOR FREE BOOK AND SAMPLE LESSON

In Field of Your Choice. You enroll by Mail — and Save Money. No Salesmen: This means lower tuition for you. Accredited Member N.H.S.C.



## NATIONAL TECHNICAL SCHOOLS

4000 S. Figueroa St., Los Angeles, California 90037

Please Rush FREE Electronics "Opportunity Book" and actual sample lesson on course checked below:

- Electronics-TV-Radio Servicing & Communications
- Master Course in Electronics-TV-RADIO Advanced TV & Industrial Electronics
- FCC License
- Radio Servicing (AM-FM-Transistors)
- Television Servicing (Including Color)
- Stereo, Hi-Fi and Sound Systems
- Basic Electronics  Electronics Math

Dept. RG-94

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

- Check here if interested ONLY in Classroom Training at L.A.
- Check here for High School Department Catalog only.



WORLD-WIDE TRAINING SINCE 1905  
4000 S. Figueroa St., Los Angeles, California 90037

# NEWS BRIEFS



Model of "public satellite No. 1" as it might appear to a viewer in space, looking past it towards its "service area."

## TRANSOCEANIC TV BY '65?

Trans-Atlantic telephone calls and live TV programs will be a reality in 1965, according to Dr. Allen E. Puckett, vice president of Hughes Aircraft Co. These will be possible with the help of "Public Satellite No. 1," now being built for Communications Satellite Corp.

The statement was made at a recent meeting of the American Institute of Aeronautics & Astronautics in Washington, at which a full-scale model of the satellite was displayed.

The new satellite, Early Bird, will be launched in synchronous orbit, hovering 22,300 miles above earth. It will take a position between North America and Europe, and it will be able to carry 240 two-way telephone calls simultaneously or an equivalent number of TV broadcasts or a combination of various forms of communication.

## LASER DRILLS NOW USEFUL

A practical application for the laser's well known ability to drill holes through hard metal (such as razor blades) has been announced by RCA's Aerospace Systems Div. in Burlington, Mass. The new laser drill has made holes as small as one ten-thousandth inch in diameter in tungsten wire. These holes are invisible to the naked eye.

Burton Clay, project engineer for the device, says this unique application can lead to extremely compact and fast micro-energy units for computers. Compactness and low electrical-energy re-

quirements in computer memories depends on drilling holes very close to each other in magnetic wire. The smaller the holes, the closer together they can be drilled.

Mechanical drills have been made as small as one-hundredth inch in diameter and electron-beam drills can make still smaller holes, but heating of the metal makes both methods impractical. The laser drill goes through "in a millionth of a second, so fast the surrounding material never gets a chance to heat up," Clay pointed out.

## VIDEO TAPE RECORDER TO HAVE 30 TRACKS


The new tape recorder being developed at the Illinois Institute of Technology will have 30 parallel longitudinal tracks on standard 1/4-inch audio tape, recording pioneer Marvin Camras told delegates to the IEEE Chicago Spring Conference on broadcast and TV receivers.

The 30 tracks are in three sets of 10 tracks each, Camras told his audience. Seven-inch reels of audio tape will be used for 60 minutes of recording or playback. Speed is 120 ips, and the picture bandwidth is expected to be about 2.5 mc. Cost will be not higher than \$500, Camras believes.
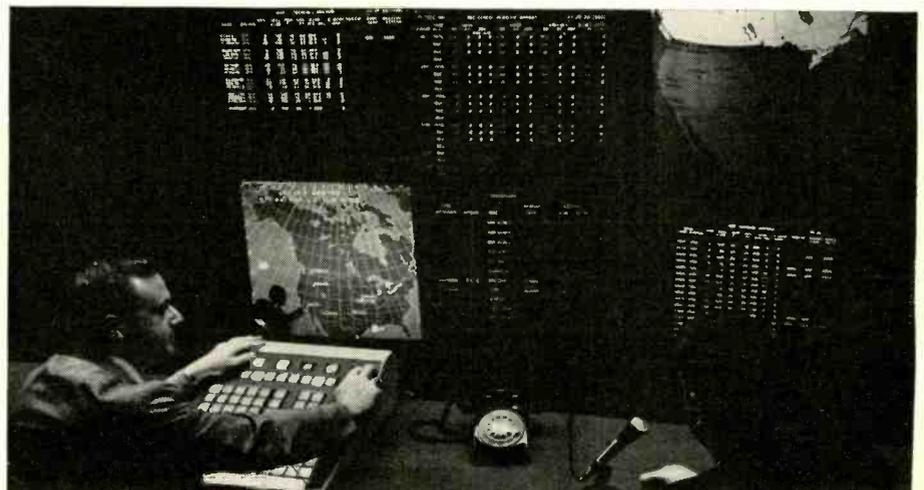
## STRATEGIC AIR COMMAND GETS NEW NERVE SYSTEM

The major elements of the Strategic

*A prototype display board at Paramus shows the variety of material that can be shown in seven colors.*




Air Command's new Command Control System (Project 465L) were displayed at a press conference at the ITT Data & Information Systems Div. in Paramus, N.J. The equipment is now being phased into SAC's underground control center at Offutt Air Force Base near Omaha.

The system is fed by numerous stations at Air Force bases around the country. Information on weather, bombers, missiles, tankers, personnel and other pertinent subjects is fed in by a message composer that converts standard messages into computer data. These are forwarded to the central computer at Offutt AFB, and processed.

The results are displayed on a special type of large wall display. Information is printed out on a 70-millimeter transparent film. Images of each message appear on the film, which is then projected by a projector with three sets of color lenses, so adjusted that the three images register on the screen. One lens is red, one blue, and one green. If all three images of the message are printed on the film, the three colored projected images register to make a white display. If only one image is printed, the areas before the other two lenses are made opaque, and only one color is projected on the screen.

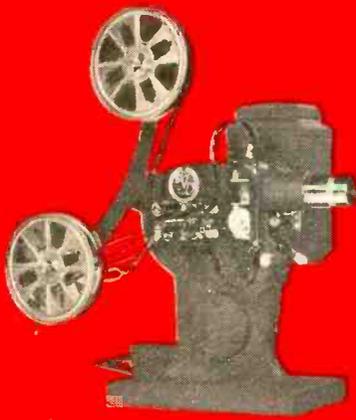By using one, two and three colors, seven distinct colors can be displayed, making it possible to present graphic charts, maps, etc. of much greater complexity than can be done in black and white. Printed data can also be emphasized and tabulated by the use of color.




"Learn-by-seeing"  
training MOVIES




Build & Keep a  
5" OSCILLOSCOPE

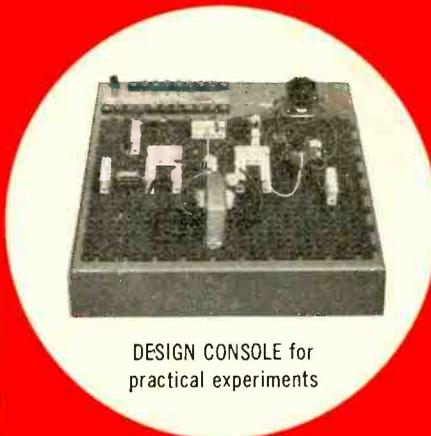Prepare  
AT HOME or  
in our CHICAGO  
or TORONTO  
Laboratories



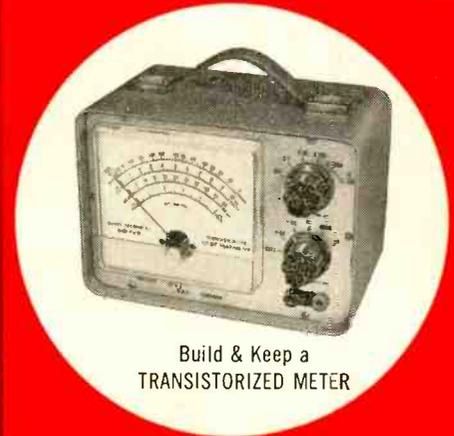DESIGN CONSOLE for  
practical experiments



Build & Keep a  
TRANSISTORIZED METER

DeVRY TECH SUPPLIES ALL THIS AND MORE TO PREPARE YOU TO

# Become an Electronics Technician

Would a career as an ELECTRONICS TECHNICIAN interest you? Perhaps you would like the Computer field . . . Instrumentation . . . Radio and Television . . . Automation or Control System work . . . a Space and Missile job. If so, READ ON.

Using DeVry's highly effective "programmed" texts - AND ALL OF THE PRACTICAL EQUIPMENT PICTURED ABOVE, many men, *probably much like you*, are now preparing at home in their spare time for wonderfully interesting, good-paying careers in every major branch of the vast, growing electronics industry. Others are

learning day or evening in our well-equipped Chicago or Toronto Laboratories.

You don't have to be a "super type" to get started toward a career in electronics! Far more important to success are ambition, average education and intelligence, interest in mechanical or electrical things.

SOUND INTERESTING? Then see for yourself how YOU may get ready to join the many DeVry graduates now enjoying good jobs, fine salaries and real progress in one of today's outstanding fields-ELECTRONICS. Mail the coupon today for no-obligation details.

## FREE!

Send for these two information-packed booklets NOW!

### EMPLOYMENT SERVICE

DeVry's highly effective Employment Service is available to all graduates at no additional cost.



## DeVry Technical Institute

Chicago • Toronto  
4141 Belmont Avenue  
Chicago, Illinois 60641



DeVRY TECHNICAL INSTITUTE  
4141 Belmont Ave., Chicago 41, Ill., Dept. RE-9-U

Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- |                                                      |                                                 |
|------------------------------------------------------|-------------------------------------------------|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications         |
| <input type="checkbox"/> Television and Radio        | <input type="checkbox"/> Computers              |
| <input type="checkbox"/> Microwaves                  | <input type="checkbox"/> Broadcasting           |
| <input type="checkbox"/> Radar                       | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics      | <input type="checkbox"/> Electronic Control     |

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Check here if you are under 16 years of age.

Canadian residents: Write DeVry Tech of Canada, Ltd.  
2094 970 Lawrence Avenue West, Toronto 19, Ontario



# SOLDERING all GUN

MODEL 450

**ONE  
LIGHTWEIGHT  
INSTRUMENT  
FOR PRINTED  
CIRCUITS**

(25-100 WATT RANGE)

**HOME WIRING**

(100-200 WATT RANGE)


**GUTTERS & PLUMBING**

(200-450 WATT RANGE)


**ONLY  
\$13.95  
INCLUDES  
HEAVY DUTY  
TIP**

The new Wen "All" Gun does any soldering job you can think of from delicate kit work and printed circuits to appliance repair to heavy jobs formerly requiring an industrial type soldering iron. Because of its perfect balance, the "All" Gun functions with minimum operator fatigue and with great precision. Three separate tips provide the ranges. A "pencil" tip (25-100 watt range) . . . a medium duty tip (100-200 watt range) . . . a heavy duty tip (200-450 watt range). You can change tips in seconds with just 2 set screws. No double triggers or tricky switches . . . a full range of heat-power is automatic with Wen's exclusive ATR. ATR (Automatic Thermal Regulation) is made possible through the use of a high temperature magnetic wire developed for the space age missile program.

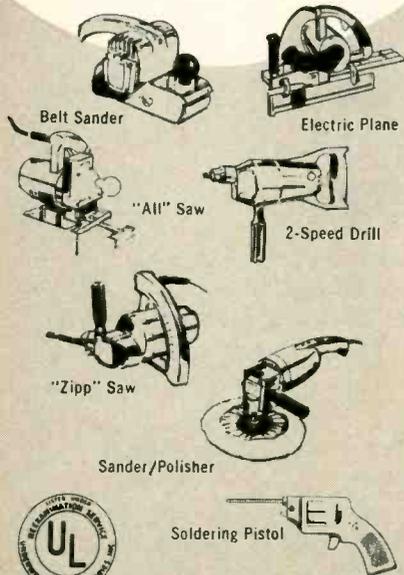Pencil tip, medium tip, flat iron attachment (to remove wood dents, seal plastic bags) and plastic cutter attachment (to cut plastic and tile) are sold separately.



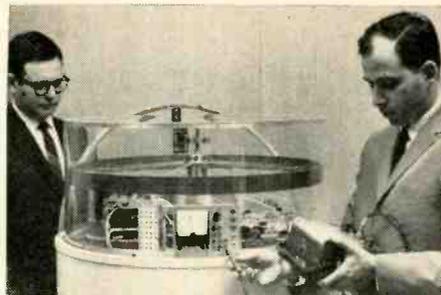**PRODUCTS, INC.**  
5810 Northwest Highway  
Chicago 31, Illinois



Project Director, Harold Perkel (left) and Dr. Robert Scher checking out a laboratory model of "Stabilite," the device that controls rocking, turning and twisting motions of an orbiting spacecraft.

### NEW STABILIZING SYSTEM KEEPS SATELLITES RIGHT

A new way of keeping satellites pointed in the desired direction has been announced by RCA's Astro-Electronics Div., Princeton, N.J. The new *Stabilite* has a coil through which current can be passed to form a magnetic field around the satellite, and a flywheel which controls the satellite's spin.

The magnetic field created around the satellite tends to line it up with that of the earth, while the flywheel controls rocking motion. Thus the *Stabilite* could keep the antenna of a communications satellite pointed continuously toward ground stations, or keep the telescope of an astronomical satellite pointed at a desired star or planet.

### TINYVISION—IN ALL SIZES

The tinyvision size race is galloping in both directions, reports *Television Digest*. Americans, thinking big, will have mammoth-size tinyvision with a 13-inch screen as well as the large 12-inch and the family 11-inch sizes. The Japanese, thinking small, are heading to-


ward the vanishing point with 4- and 3-inch sets. The new 13-inch tube size, developed by Lancaster Glass Co., will appear on one of the American sets this fall.

In the 11- and 12-inch sets we have Admiral, DuMont, Emerson, Magnavox, Curtis Mathes, Westinghouse, Zenith, Sears and Montgomery Ward. The mail-order houses and some of the standard brands are marketing Japanese-made sets. General Electric and Philco have announced 9-inch receivers. Mitsubishi expects to put a 6-inch color set on the market at some unannounced date. Sony has a 4-inch transistorized set, and Standard Radio a "Micro Miniaturized TV" with a 3-inch screen. The whole set is less than 3 inches high, 7 wide and 7 deep.
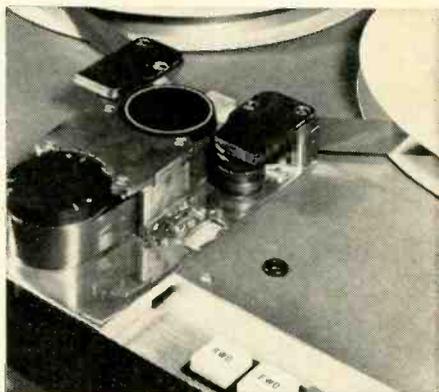
### NEW TAPE SYSTEM UPS FIDELITY

A new recorder that produces professional master tapes was described and demonstrated by 3M recently.

In a simplified description, 3M engineer John T. Mullin explained that the device was intended to give a better signal-to-noise ratio and loud but undistorted tones without introducing noise from the machine.



The tape transport mechanism of 3M's new professional mastering recorder.


This is done by recording on two tracks. One track of each channel records in the usual way; the other track is specially equalized to record signals of small volume. In playback, low-level signals are reproduced from the special track. As volume increases to the point where the low-level track produces distortion of 1% at any frequency, the tape switches over electronically onto the conventional track. The switching takes place in 1 millisecond, so that even steep transients of high amplitudes are reproduced without audible distortion.

The new system improves the dynamic range of sound recording up to 15 decibels, Mr. Mullin stated. Another feature of the system is the 350-kc bias frequency, which completely eliminates beats and "birdies."

#### Advertising Representatives:

- |                                                                                                                                                       |                                                                                                                  |
|-------------------------------------------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------------------------|
| <b>EAST</b><br>John J. Lamson<br>Eastern Sales Manager<br>Radio-Electronics<br>154 West 14th Street<br>New York, N.Y. 10011<br>(212) Algonquin 5-7755 | <b>MIDWEST</b><br>P. H. Dempers Co.<br>740 North Rush Street<br>Chicago, Illinois 60611<br>(312) Michigan 2-4245 |
| <b>SOUTHEAST</b><br>Neff Associates<br>15 Castle Harbor Isle<br>Fort Lauderdale, Fla.<br>(305) Logan 6-5656                                           | J. Sidney Crane, Assoc.<br>22 Eighth St., N.E.<br>Atlanta 9, Ga.<br>(404) TRinity 2-6720                         |
| <b>TEXAS/ARKANSAS</b><br>Media Sales Co. 2600 Douglas Avenue, Irving,<br>Texas 57060. (214) Blackburn 5-6573                                          |                                                                                                                  |
| <b>WEST COAST/OKLAHOMA</b><br>Husted-Coughlin, Inc. 1830 W. 8th Street<br>Los Angeles 57, Calif. (213) 389-3132                                       |                                                                                                                  |
| Huston-Coughlin, Inc. 444 Market Street<br>San Francisco 11, Calif. (415) GARfield 1-0151                                                             |                                                                                                                  |
| <b>UNITED KINGDOM</b><br>Publishing & Distributing Co., Ltd., Mitre House,<br>177 Regent St., London W.1, England                                     |                                                                                                                  |

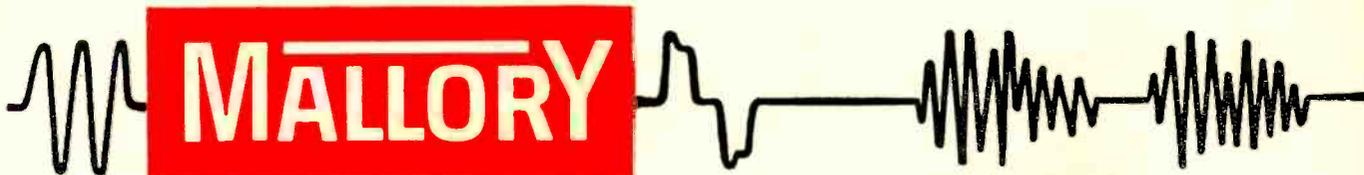Subscription Service: Address form 3579 and correspondence to Radio-Electronics, Subscriber Service, 154 West 14th Street, New York, N. Y. 10011. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address.




**MALLORY**

## Tips for Technicians

Mallory Distributor Products Company  
 P.O. Box 1558, Indianapolis, Ind. 46206  
 a division of P. R. Mallory & Co. Inc.
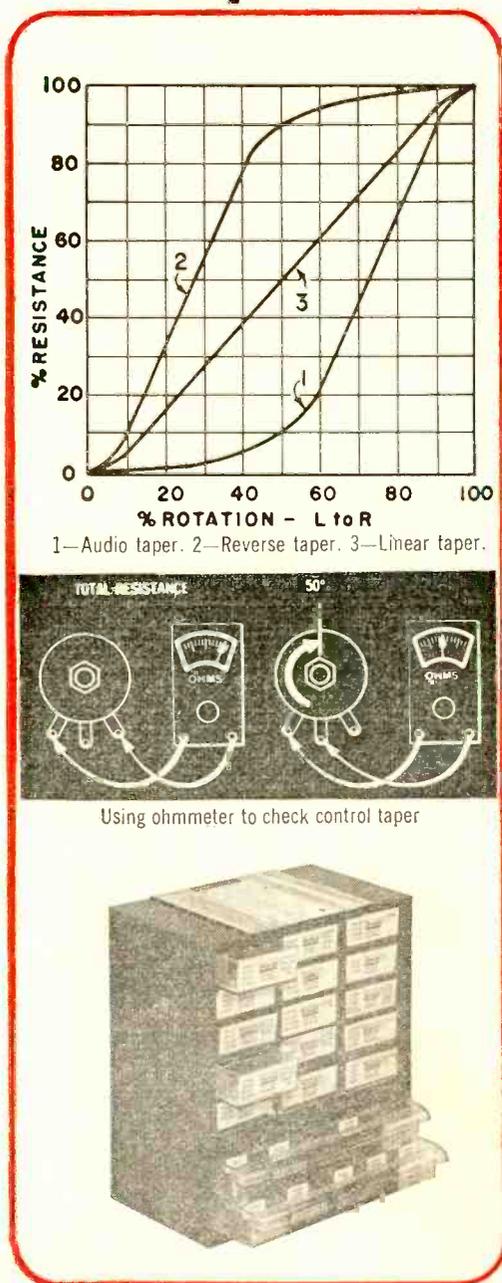
# How to choose and use replacement controls



There's more to replacing a volume control, "pot", or trimmer than simply selecting the proper value in ohms and watts. Naturally you *need* the proper value, but you also need the correct *taper* or the circuit won't perform properly.

What's taper? Briefly, it's the way resistance changes as you rotate the shaft. There are three basic tapers normally used which match the needs of different kinds of circuits. The chart shows how each of the three works.

**Audio taper** (often called left hand logarithmic by people who like big words) gives you a small increase in resistance at the beginning of shaft rotation and a faster increase toward the end (clockwise rotation). This matches the response of the human ear and is the reason audio tapers are generally used in volume controls and similar shunt circuits.

**Linear taper** is just that. Resistance change is exactly proportional to shaft rotation. All standard wire-wound controls have linear tapers. Carbon controls with linear tapers are commonly used in tone controls, sweep controls and other straight voltage-division uses.

**Reverse taper** (right hand logarithmic) is the opposite of an audio taper. You'll get a big change in resistance in the first half of shaft rotation and very little in the last half. This taper is used with cathode voltage controls such as TV contrast and many bias voltage controls.

In the Mallory STA-LOC® control system, it's easy to remember which taper is which. Linear controls end with "L", and audio with "A", and reverse with "R".

You can check which taper is used in an unknown control by connecting an ohmmeter as shown in the drawing.

First, measure total resistance. Then turn the shaft to 50% of rotation. If resistance is 50% of total, you have a linear taper. If it is 10% to 20% of total you have an audio taper. If it is around 80% of total you have a reverse taper.

To be sure you have the exact control when you need it, ask your Mallory distributor to show you one of the STA-LOC technician kits. With a STA-LOC kit you can make exact on-the-spot replacements of any of literally *thousands* of single, dual, push-pull, tandem, or clutch controls. Pieces snap together and *stay* together. STA-LOC kits are sensibly priced and are real money-makers and time-savers. See your Mallory distributor for everything you need in controls, capacitors, batteries, switches, resistors, and semiconductors.



#### WASHINGTON-NEW YORK-CHICAGO PICTUREPHONE SERVICE STARTS

Bell Telephone Co. inaugurated Picturephone service between New York, Washington and Chicago on June 24. Mrs. Lyndon B. Johnson was one of the first to use the service. She talked from Washington to Dr. Elizabeth Wood, a scientist with Bell Labs in New York.

Rates for the first 3 minutes are \$16 between New York and Washington, \$21 between Chicago and Washington and \$27 between Chicago and New York. Also taking part were two deaf teen-agers, who read each other's lips.

#### INITIATIVE IS OK, BUT . . .

Colice Radio Laboratory, Inc., a Brooklyn electronics firm listing branch offices in Chicago, Kansas City, Los

Angeles and San Francisco, turned out to be one youthful experimenter in a basement, according to a story released by the Better Business Bureau.

The "firm" had obtained samples and ordered equipment from several companies to complete work on projects such as "Satellite Tracking Station No. 9." Apparently no payments were forthcoming and the BBB received inquiries from several companies.

A request that the head of the company visit the BBB for an interview brought a nervous-looking man, who reported that he was the father of a 17-year-old boy with an abnormal interest in electronics. The boy had printed the Colice Labs letterhead and assembled, disassembled, and in general experimented in the family basement on the equipment received.

#### NO-MOVING-PARTS VALVE INVENTED BY WOMAN ENGINEER

Mrs. Barbara Lunde of NASA's Goddard Space Flight Center has invented a thermoelectric valve for controlling the jet spray of liquid propellants from satellite reaction jets. Such jets provide short bursts of power necessary to orient the satellite in space.

This thermoelectric valve freezes and thaws the liquid propellant right in the feed line from the fuel tank to the jet nozzle. Electric current applied in

one direction to the device draws heat from the line and cools it until the propellant is frozen. Then, by reversing the current, heat is applied to the line, which melts the propellant and lets it flow free. The action takes place in milliseconds.

#### IN-FLIGHT CLOSED CIRCUIT TV?

Two similar plans being offered to major airlines, one by Sony and the other by Ampex, would enable airline passengers to choose, from their seats, movies, stereo music, landing and take-off pictures, and en-route scenery.

The Sony scheme has 5-inch receivers behind each armrest. The Ampex unit, called Travelvision, will provide screens from 6 to 9 inches. Both systems use video tape recorders.

#### U.S.-FINLAND MOONBOUNCE ON 144-MC BAND

As a result of bouncing radio signals off the surface of the moon, an important first in amateur radio communications was achieved on April 12, 1964 when Bill Conkel, W6DNG, Long Beach, Calif., had a two-way conversation with Lenna Souminen, OH1NL in Nakkila, Finland, on 144 mc. This frequency is normally considered usable for no more than a few hundred miles. Mr. Conkel experimented for more than a dozen years and discarded 58 antenna designs before accomplishing this feat.

#### IMP I'S ELECTRONIC EQUIPMENT SURVIVES 8-HOUR SUBFREEZE

Explorer XVIII, known as IMP (Interplanetary Monitoring Platform), has survived 8 hours in the earth's shadow and temperatures of more than 400° below zero, and resumed normal operation after shutting off automatically in the instrument-freezing cold. IMP remained in the earth's shadow so long because its highly eccentric orbit carries it out 122,000 miles into space at apogee.

#### CALENDAR OF EVENTS

ARRL National Convention, Aug. 21-23; New York Hilton Hotel, New York, N.Y.

1964 Western Electronic Show and Convention (WESCON), Aug. 25-28; Los Angeles Sports Arena and Hollywood Park, Los Angeles, Calif.

Hi-Fi Show, Sept. 10-13; San Francisco Hilton Hotel, San Francisco, Calif.

International Convention on Military Electronics (MIL-E-CON 8), Sept. 14-16; Shoreham Hotel, Washington, D. C.

1964 Conference on Radio Meteorology, Sept. 14-18; National Bureau of Standards Boulder Laboratories, Boulder, Colo.

First National Conference on Automotive Electrical & Electronics Engineering, Sept. 22-23; McGregor Community Conference Center, Wayne State University, Detroit, Mich.

Third Electronic Trade Exhibition, Sept. 23-29; Apollohal, Amsterdam, Holland.

New York High-Fidelity Music Show, Oct. 1-4; New York Trade Show Building, New York, N.Y.

20th Annual National Electronics Conference, Oct. 19-21; McCormick Place, Chicago, Ill.

# AUTOTEXT AUTOTEXT AUTOTEXT


read about it on page 77

RCA's  
new  
easy way  
to learn  
ELECTRONICS  
at home

RCA INSTITUTES, INC.



The Most Trusted Name in Electronics

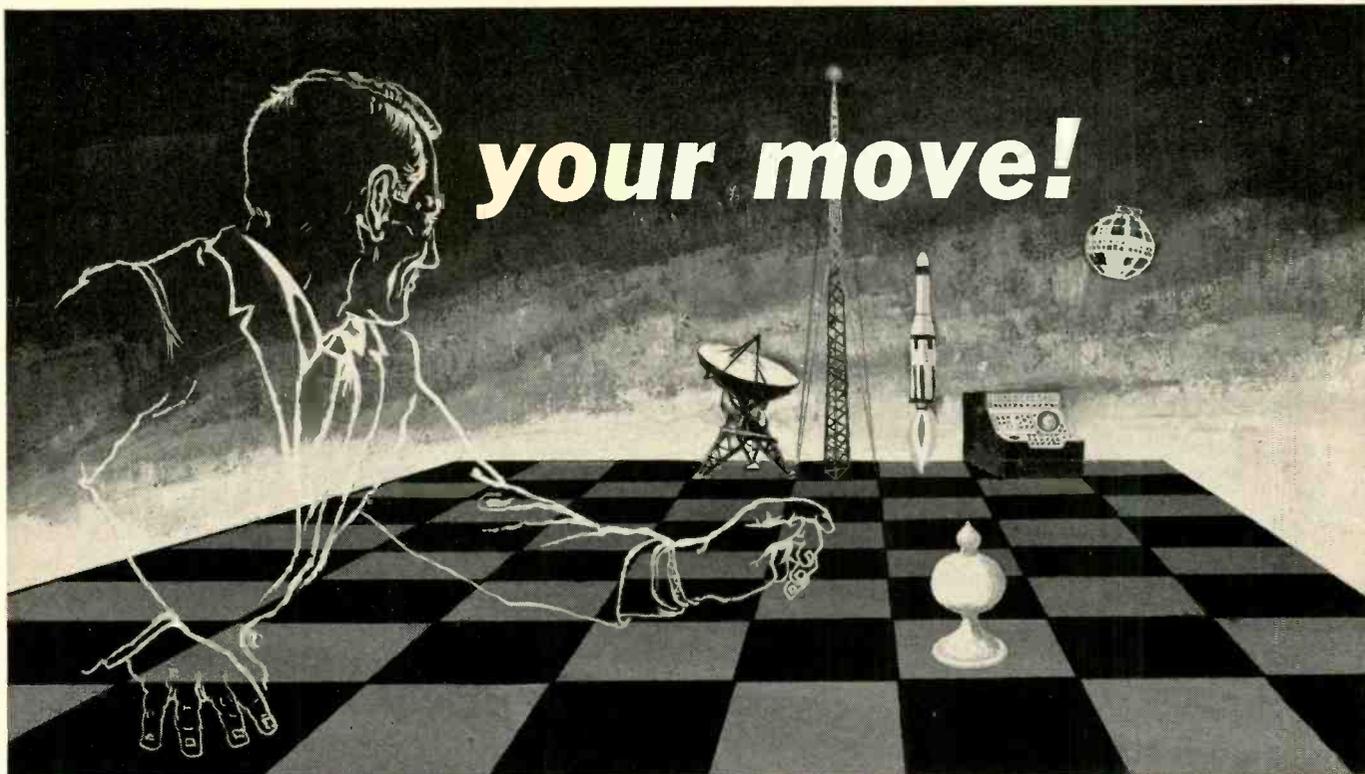

**The move into electronics is your decision. GRANTHAM SCHOOL OF ELECTRONICS makes your move easier . . .**

Beginning at the beginning, Grantham training progresses in a logical, step-by-step manner up through the complex theory of the Missile Age—and all of the math you will need is taught as an integral part of our lessons. Because we present these all-important basic principles with maximum penetration, *you will learn to think and reason electronics* rather than relying on half-understood concepts and rote-memory.

The Grantham program is made up of three consecutive steps, and each completed step increases your value as an electronics man. The following is a "thumb-nail sketch" of the Grantham 3-step program for electronics advancement:

- Course I leads to attainment of your First Class F.C.C. License and may be completed in the classroom or through home study.
- Course II gives you practical experience on a great variety of "live" electronic equipment in the Grantham Student Laboratory.
- Course III offers Advanced Electronics Training (including microwave and radar) and prepares you to advance to senior-technician status.

*Get complete details in our free 44-page booklet. Mail coupon, or telephone the school nearest you; phone numbers and addresses are listed below.*

Prepare for Employment and/or Advancement in Electronics  
by training with

**GRANTHAM SCHOOL OF ELECTRONICS**

**Los Angeles Division**  
1505 N. Western Ave., Los Angeles, Calif. 90027

Phone:  
**HO 7-7727**

**Seattle Division**  
408 Marion Street, Seattle, Wash. 98104

Phone:  
**MA 2-7227**

**Kansas City Division**  
3123 Gillham Road, Kansas City, Mo. 64109

Phone:  
**JE 1-6320**

**Washington Division**  
821 — 19th Street, N.W., Washington, D.C. 20006

Phone:  
**ST 3-3614**

(Mail in envelope or paste on postal card)


**National Headquarters Office 44-P**  
**Grantham School of Electronics**  
 1505 N. Western Ave., Hollywood 27, Calif.

Gentlemen:

Please send me your FREE 44-page booklet,  
"CAREERS IN ELECTRONICS."

Name \_\_\_\_\_ Age \_\_\_\_\_  
(PLEASE PRINT)

Address \_\_\_\_\_

City \_\_\_\_\_


State \_\_\_\_\_

I AM INTERESTED IN:  HOME STUDY  RESIDENT CLASSES


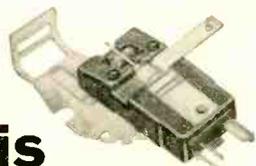
## This one is twice as safe.

When Sonotone designs a retractable cartridge, you can be sure it offers something extra. Like other retractable cartridges, the new Sonotone "21TR" withdraws into the safety of the arm to avoid bumps and bruises. Further, it has "bottoming" buttons which act as shock absorbers between the needle assembly and the record. Unlike other retractables, the "21TR" features the exclusive Sono-Flex<sup>®</sup> stylus, which can be dropped or mauled and still continue to provide superior performance. The high-output "21TR" is a direct replacement for the thousands of record players requiring a quality retractable cartridge.



## This one is twice as safe and twice as compliant.

The new Sonotone "23T" offers performance specifications never before available in a budget-priced ceramic cartridge—plus record protection. High compliance of 10; channel separation of 24 db; output voltage of 0.38; low tracking force of 2 to 4 grams make it the ideal replacement in quality stereo phonographs. Performance is only half the story of the "23T". This new cartridge features "bottoming" buttons and the flexible Sono-Flex<sup>®</sup> needle. Another Sonotone cartridge, the "22T," offers the high performance of the "23T" with a slightly higher output. Both feature the Sono-Flex plus a unique snap-in mounting bracket, for rapid replacement without tools.

## Both are direct replacements for popular makes

## ...and themselves.

**SONOTONE**  
audio products 

Sonotone Corp., Electronic Applications Div., Elmsford, New York  
Cartridges • Speakers • Microphones • Headphones • Hearing Aids • Batteries

### ASEE AWARD TO FREDERICK TERMAN

Acting President Frederick E. Terman of Stanford University received the Lamme Award of the American Society of Engineering Education at the Society's annual meeting. Previous recipients include Dr. Vannevar Bush, Dr. Terman's old teacher at MIT; Karl Compton and Theodore von Karman.



Dr. Terman is a member of the National Academy of Sciences, a consultant to President Johnson's Science Advisory Committee and a member of the Committee of Twenty-Five chosen to develop a plan for a National Academy of Engineering.

### LASER BEAMS MEASURE DEPTH OF MOON'S CRATERS

As reported by J. S. Courtney-Pratt of Bell Labs to the Society of Photographic Scientists & Engineers, the Armed Forces shot beams of laser light to the lip of a moon crater and then to the bottom. By timing the difference, engineers estimated that it is as much as 20,000 feet between the crater lip and the bottom. Comparable results have been obtained by measuring shadows in the craters.

Suggested uses for laser beams such as knocking branches off trees, cutting steel beams, death rays, or photographing large earth areas from the sky were dismissed as extravagant in Mr. Courtney-Pratt's report.


### ELECTRONICS STOPS SHOPLIFTERS

Television cameras, two-way radios, walkie-talkies are being adopted by an increasing number of stores, and are effective both as a deterrent and a weapon of apprehension. This was pointed out at a meeting of the San Fernando Valley shoplifting committee, an organization of local merchants and store security officers.

Even dummy cameras prove effective, it was reported.

# New, revolutionary way to choose a speaker system:

## listen

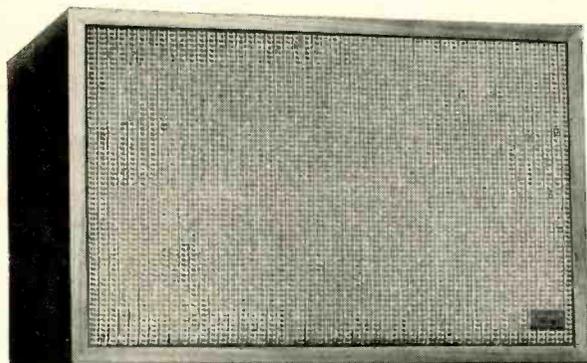

UNIVERSITY SENIOR II  
Ultra-Linear 12" woofer, 3½" mid-range, Sphericon Super-Tweeter; 25x15½x12½" D. \$99.50



UNIVERSITY COMPANION II  
Ultra-Linear 10" woofer, 3" mid-range, 3½" tweeter. 24x13½x11½" D. \$79.50



UNIVERSITY MINI-FLEX  
6½" woofer, 3" mid-range 3½" tweeter. 15x9¼x5¾" D. \$69.95



UNIVERSITY COMPANIONETTE  
Ultra-Linear 8" woofer, 3" mid-range, 3½" tweeter. 21¾x11½x8⅝" D. \$69.95


...and listen and listen. New? Revolutionary? Yes—when you consider how many people buy speakers based on the recommendation of others. Sound involves **subjective** criteria. The sound that pleases a friend, (a hi-fi editor or salesman, for that matter) will not necessarily please you. Therefore . . . hear and compare many systems. For the largest selection, **start with University**. Choose the superb University model that best meets your requirements, then compare it to all other brands of its type. For example—if it's a full-size bookshelf you want, ask your dealer to demonstrate the Senior II vs. the AR, KLH, and other bookshelf systems of similar size. You'll hear the difference. Especially in the mid-range. Especially in the Senior's complete absence of restraint, that tell-tale drawback of so many other bookshelf systems. Unlike other systems, the sound of the Senior, the Companion, or of **every** University system, large or small—is **free** and **open**. The bass is cleanly defined; the mid-range punches through for greater presence; the highs literally have wings. Want proof? (Of course you do) Visit your dealer . . . and **listen**. University sounds better. Free 1964 Guide to Component Stereo! Write: Dept. RE-9.



**LTV**  
**UNIVERSITY**

A DIVISION OF LING-TEMCO-VOUGHT, INC.  
9500 West Reno, Oklahoma City, Oklahoma
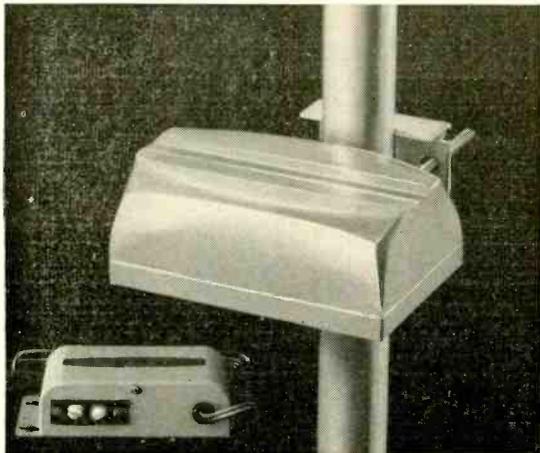
# "Costs a bit more than 1 transistor VHF amplifiers."



"It should—it has two transistors."

**"Fine, but is it worth the difference?"**

"You bet, when you measure the couple extra dollars against the many hours of superb TV reception you will enjoy."

**"Tell me more."**

"The new Blonder-Tongue Vamp-2 outperforms all home VHF amplifiers on the market, tube or transistor. Brings in sharp, clear pictures."

**"But, what's the real advantage of two transistors?"**

"More signal power, lower noise for snow-free reception."

**"But, I hear transistor units can overload from strong local TV stations?"**

"Not this one, that's where the extra transistor pays off."


**"I've got two sets."**

"The Vamp-2 delivers strong signals to two sets. It has a built-in splitter. Great for color TV. List \$38.95."

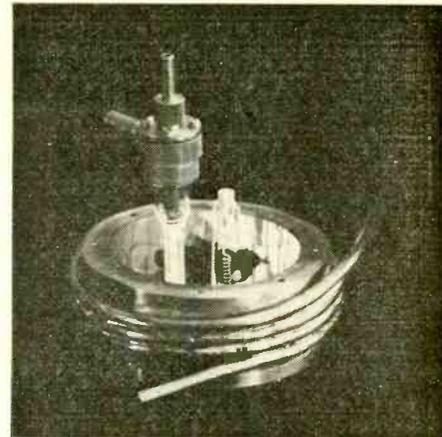**"Supposing I don't want to lay out the few extra dollars for the Vamp-2?"**

"Simple solution. The new Blonder-Tongue Vamp-1... the best one-transistor model on the market. Lists at \$25.50."

(This message was paid for out of the gross profits of BLONDER-TONGUE, 9 Alling St., Newark 2, N.J.)



*At left, projecting down into the housing, a 1-inch aluminum garnet crystal. To its right, the spiral-filament tungsten lamp that "pumps" the laser.*

## **NEW SOLID-STATE LASER WORKS AT ROOM TEMPERATURE**

A new rare earth aluminum garnet crystal optical maser (laser) is operating continuously at Bell Telephone Laboratories at room temperature—on light supplied by a tungsten lamp! Bell scientists, Dr. J. E. Geusic, H. M. Marcos and Dr. L. G. Van Uitert, produced the new crystal as a result of work on neodymium-doped yttrium aluminum, yttrium gallium and gadolinium gallium garnets.

Neodymium-doped yttrium aluminum garnet crystals operated in ordinary room temperature with light from a tungsten lamp with an input of 360 watts. Radiation was at 1.06 microns.

## **NO MINIATURIZATION FOR SOLID-STATE TV**

Because the glass picture tube governs the cabinet size of a TV set, there is no great chance of sets becoming smaller as they are transistorized.

However, according to Texas Instruments, Inc., who are selling transistor kits to TV set manufacturers, the



# NOW! get this **BIG BONUS** with your purchase of a **PHOTOFACT® Library!**

**FREE!** this deluxe new **Four-Drawer FILE CABINET** (with full-drawer suspension) worth **\$55.00**—available only with your purchase of a **PHOTOFACT LIBRARY** consisting of **200 SETS** plus valuable *Free extras!*


**boost your earning power—own and use the world's finest TV-radio service data**

Now, more than ever, it pays to own a PHOTOFACT Library—the time-saving troubleshooting partner guaranteed to help you earn more daily. Now, you can start or complete your PHOTOFACT Library the special Easy-Buy way, and get absolutely **FREE** with your purchase, the deluxe 4-drawer File Cabinet worth \$55.00, *plus* valuable extras described below!

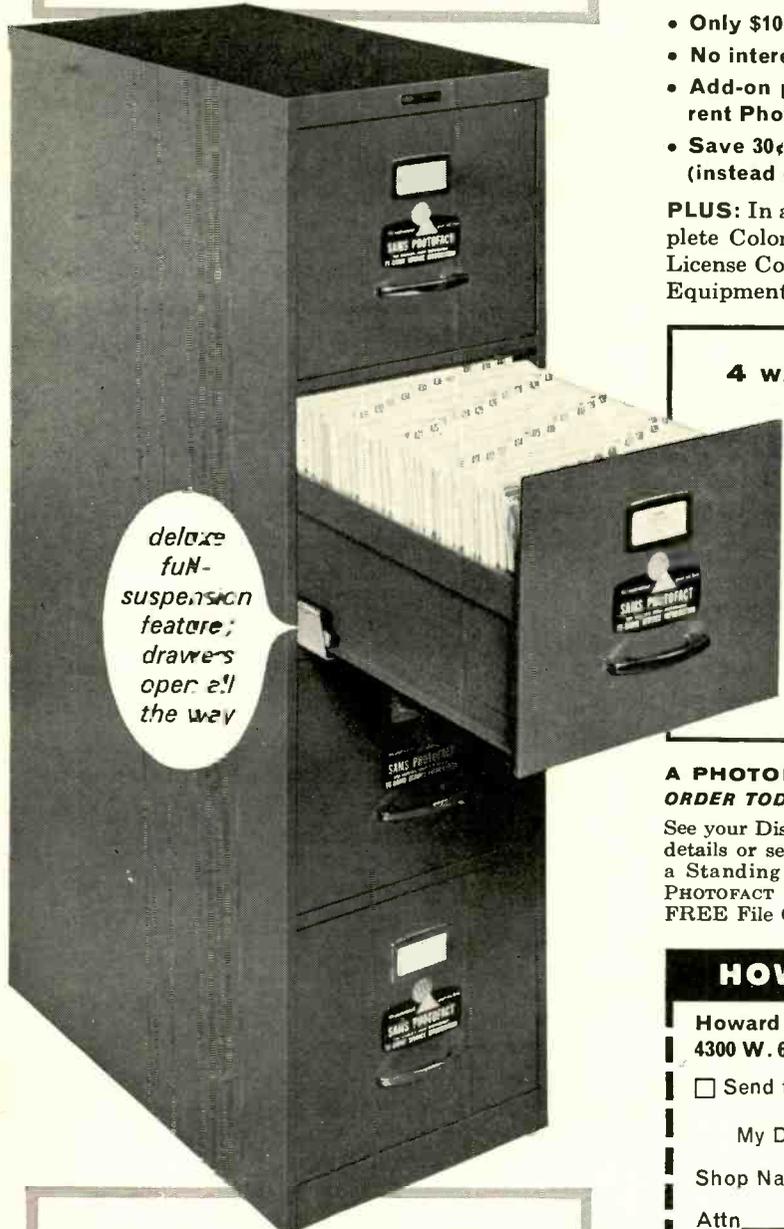**OWN A PHOTOFACT LIBRARY THE EASY-BUY WAY:**

- Only \$10 down • 30 months to pay
- No interest or carrying charges • Prepaid transportation
- Add-on privilege of a year's advance subscription to current Photofact data, on the same Easy-Buy contract
- Save 30¢ per Set—special \$1.95 price applies on Easy-Buy (instead of regular \$2.25 price)

**PLUS:** In addition to the deluxe File Cabinet, you get a complete Color TV Servicing Course, 2nd Class Radiotelephone License Course, Transistor Radio Servicing Course, and Test Equipment Guide!



**4 WAYS TO SELECT YOUR PHOTOFACT LIBRARY**

1. Complete your present PHOTOFACT Library
2. Order a PHOTOFACT "Starter" Library—200 Sets (Sets 401-600—coverage from 1958 to 1963—only \$12.66 per month).
3. Order by brand name and year—see the handy selection chart at your distributor.
4. Order a *complete* PHOTOFACT Library—get **FREE** File Cabinets to accommodate the *entire* library, the Courses listed above, *plus* an 8-volume Set of "101 Ways" Test Instrument books worth \$18.50.

**A PHOTOFACT LIBRARY PAYS ITS OWN WAY—ORDER TODAY AND GET THE FREE BONUS EXTRAS**

See your Distributor for PHOTOFACT Easy-Buy details or send coupon today! Ask also about a Standing Order Subscription to current PHOTOFACT and Specialized Service Series—**FREE** File Cabinet also available!

**GET THE DETAILS NOW**

**Offer for Limited Time Only—Act Now!**

**HOWARD W. SAMS & CO., INC.**

Howard W. Sams & Co., Inc. Dept. REF-9  
4300 W. 62nd St., Indianapolis, Ind. 46206

Send full information on Easy-Buy Plan



My Distributor is: \_\_\_\_\_

Shop Name \_\_\_\_\_


Attn \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

FASTATCH II CONTROL SYSTEM  
MORE CONVENIENT AND  
VERSATILE THAN EVER!

now  
*Centralab*  
gives you

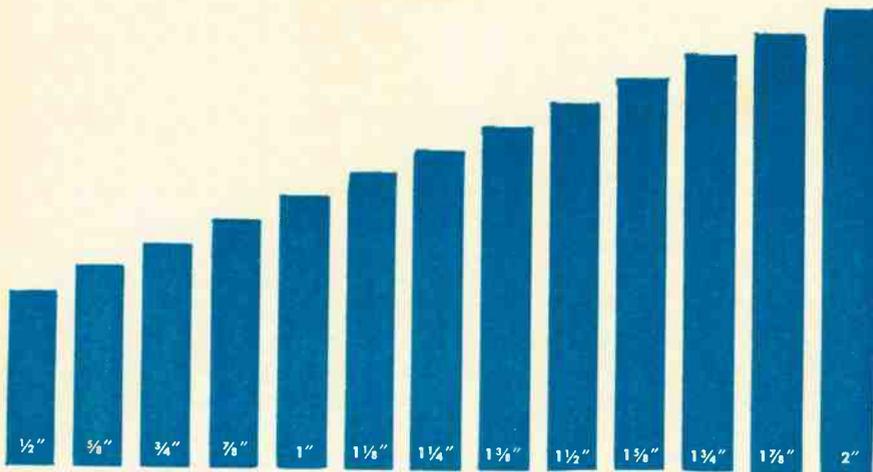

# SINGLE SHAFT CONTROLS

*with exact length shafts*



Need a control with a flat shaft—or  
split knurled—or screwdriver slot?

Maybe you need it with—or without  
—an attached line switch.

But two things are sure: You need a  
certain *exact* shaft length—and your  
Centralab distributor can supply it!

Centralab's new exact length solid  
shafts provide exact replacements for  
ALL your single control requirements,  
as well as twins for stereo, triples, and  
quads.

If you have the FRK-100 Fastatch  
II Kit, you can add these exact length  
shafts as you need them; they snap  
right into place on the Fastatch II  
front controls. Or, you can always get  
the exact control you need, instantly,  
from your Fastatch II distributor.

For a complete catalog on the  
Fastatch II Control System, write to  
Centralab or contact your distributor.


The Electronics Division of Globe-Union Inc.  
P. O. Box 591 Dept. 92-1, Milwaukee, Wisc. 53201  
In Canada: Centralab Canada Ltd., P. O. Box 400, Ajax, Ontario

B-6420

**Centralab**  
CORP.

EXCITING  
EXCITING

NEW LINE!  
NEW SOUND!

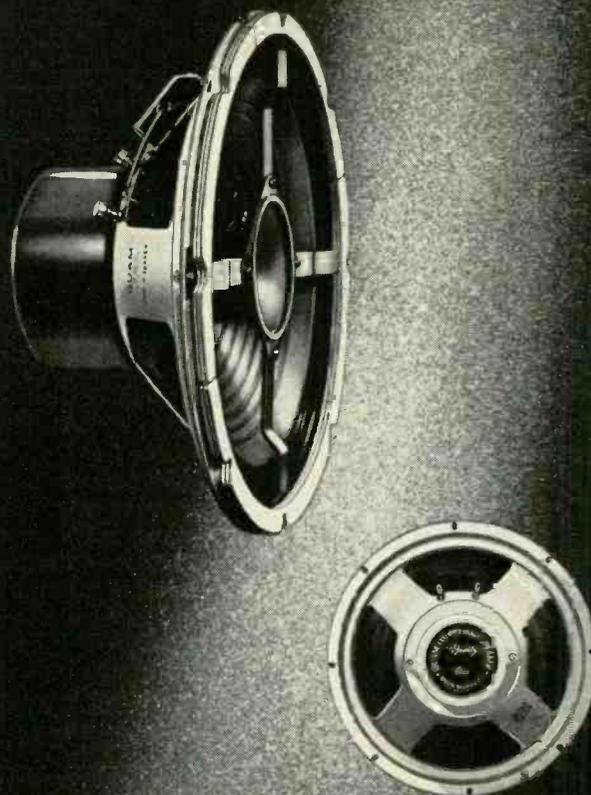

**QUAM**

## FULL FIDELITY HI-FI SPEAKERS

Slim-line styling! Ceramic magnets! Superb reproduction over the full audio spectrum! Complete choice: coaxials, extended range, tweeters, woofers! The new Quam hi-fi line is as modern as tomorrow—and it's designed to offer the *serviceman* a top-quality product at a *list* price that's lower than others' "audiophile net." (Quam never advertises net prices—to protect your mark-up!)

Use Quam Hi-Fi Speakers in new systems, as extension speakers in existing hi-fi systems, and as replacement improvements in stereo consoles. They'll open your way to exciting new sales!

Write for your free copy of the new Quam Hi-Fi Catalog HF-64.

**QUAM-NICHOLS COMPANY** • 234 East Marquette Road • Chicago, Illinois 60637

selling gimmick will be a 5-year warranty on the transistors.

The semiconductor manufacturer predicts that up to 100,000 transistorized TV sets will be sold this year.

#### RADAR SOUNDINGS FROM JUPITER

Last fall, independent groups of American and Soviet scientists experimented nightly for a month aiming signals at Jupiter. In a report in the magazine *Science*, Dr. Richard M. Goldstein of Caltech said that the return signals received offered strong evidence that they were indeed returning from Jupi-

ter, and indicated a high degree of smoothness for part of the planet's reflecting surface, a smoothness greater than that of Mars and far greater than Venus'. This smooth area is not in the planet's famous red spot.

#### UHF TUNERS TO "CLICK" THIS WINTER?

The second detent uhf tuner of the season has been announced by the F. W. Sickles Div. of General Instrument. An earlier one had already been announced by Oak Manufacturing Co. Motorola is using a pushbutton system on its better black-and-white sets.

#### BRIEF BRIEFS

Pilot Radio Corp., which dropped TV in 1952 (after making the first of the "tinyvisions") to make hi-fi equipment, is returning with a line of home-entertainment centers featuring color television, and a new line of sidetable stereo instruments, both equipped with solid-state electronics.

Raytheon reports peak-power outputs of 100 megawatts from a pulsed ruby laser, the highest peak power yet reported for a high-repetition laser. Pulse widths were 10 nanoseconds at repetitions greater than 1 pulse per second.

Small integrated transistor power supply regulator, made by Trio Labs of Plainview, N. Y., is packed in a power transistor case and sold as a superregulated Zener diode. The unit is intended to be inserted in a power supply like any other Zener diode, but with, however, vastly improved performance.

A New York hotel, the Rutledge, on Lexington Ave., is attempting to establish itself as "ham headquarters." Special discount rates are offered guests who produce an operator's license when registering, and an amateur station is available for the use of visiting hams.

NASA is testing an electronic shark repeller, a device that radiates a wide spectrum of frequencies from a 36-inch underwater dipole antenna. The frequency that repels the shark has not been identified, but it is believed that it affects the shark's sense of "smell".

RCA reports that color sets accounted for 3 out of every 10 set sales during the first part of 1964 END

**make it easy on yourself**  
See the direct answer—on only the range-scale you want—automatically

**B&K**

**Model 360**  
**V O Matic**



**Automatic Volt-Ohm-Milliammeter**

WITH  
BURN-OUT PROOF  
METER MOVEMENT

Sensitivity 20,000 ohms per volt DC; 5000 ohms per volt AC. Accuracy  $\pm 3\%$  DC;  $\pm 5\%$  AC; (full scale). DC Volts in 6 ranges 0-6000. AC Volts in 6 ranges 0-6000. AF (Output) in 4 ranges 0-300 volts. DC Current in 5 ranges 0-10 amps. Resistance in 4 ranges 0-100 megohms. Supplemental ranges also provided on external overlay meter scales. Meter movement protected against extreme overload and burn-out. Polarity reversing switch. Automatic ohms-adjust control. Fuse-protected shunts. Mirrored scale. Complete with  $1\frac{1}{2}$ -volt and 9-volt batteries, test leads, and easy-viewing stand. Batteries freshly packed separately.

**No Reading Errors!**  
**No Multiplying!**

Just set the range switch, and only the scale you want in the exact range you want appears *automatically*. Individual *full-size* wide-view scale for each range—and only one range-scale is visible at any one time. *Reading is clear, easy—and direct.* Net, \$5995

**DYNAMIC**  
**375 VTVM**




It's automatic! See only the full scale you want and read the exact answer—directly. No multiplying. Eliminates errors. Net, \$8995

See Your B&K  
Distributor  
or Write for  
Catalog  
AP21-R

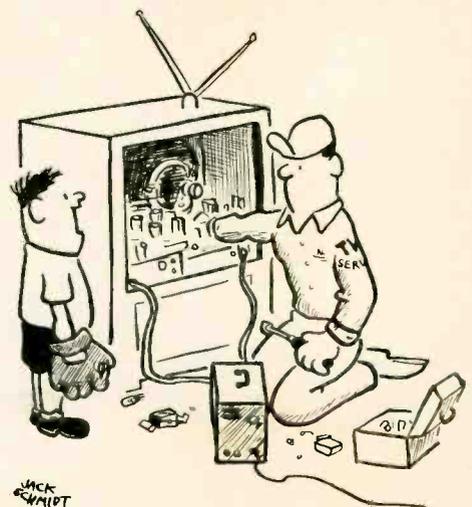**B&K**

**B&K MANUFACTURING CO.**  
DIVISION OF DYNASCAN CORPORATION  
1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.




"Are you the man that daddy says he's not going to pay?"

TO PROVE TO YOU...

# You really need 2 types of microphones



**BUY THIS FIXED-POSITION MICROPHONE**

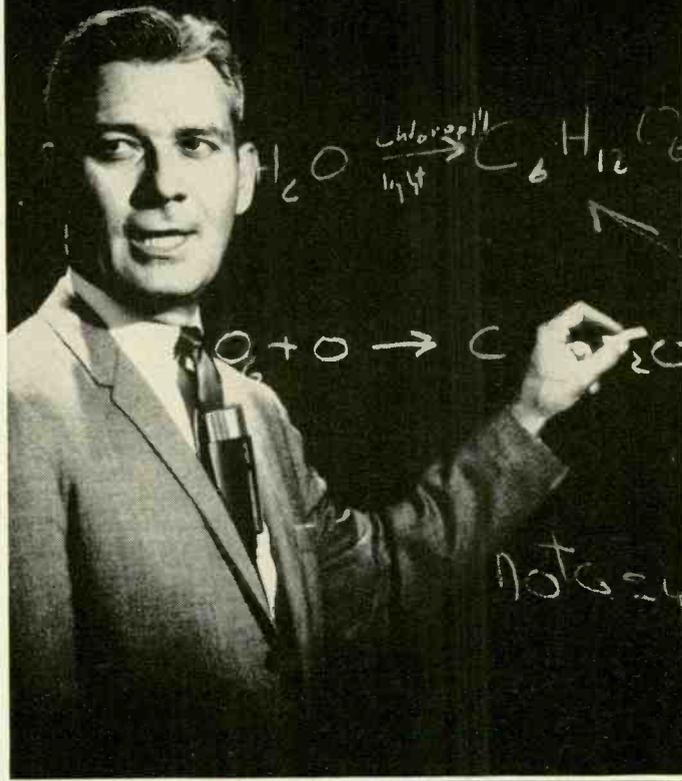


**...GET THIS LAVALIER FOR ONLY \$5.00**
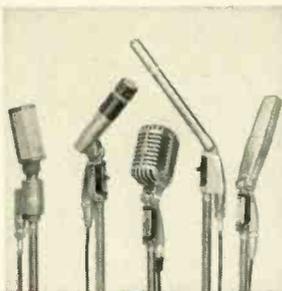
## SHURE MAKES THIS SPECIAL OFFER IN THE INTEREST OF IMPROVED SPEAKING TECHNIQUES

This special limited-time offer applies to the famous Unidyne II and III series and other fine Shure microphones listed below.\* Unidyne III is the only cardioid microphone with a completely uniform pickup about the axis at all frequencies—in all planes. Outstanding for voice or instruments.

\*Models 300, 315, 330, 333, 555W, 555, 545, 545S, 546, 556S, 576, 578, 578S. A Shure Lavalier for only \$5.00 with each, when you send in your guarantee registration card. Offer expires December 31, 1964.




For lecturers, teachers, ministers, managers, public speaking requires the freedom and flexibility of a second microphone. The ability to move around while talking frees the speaker for writing on a blackboard or handling visuals, makes any speaker more interesting, more effective. Prove it to yourself for only \$5.00 when you buy a Shure Microphone for fixed-location use.



Shure Brothers, Inc., 222 Hartrey Avenue, Evanston, Illinois

- Steps to obtain your Lavalier Microphone
- Purchase any of the microphones listed above thru your distributor or sound installer.
- Remove guarantee registration card from microphone package.
- Specify whether you wish high impedance or low impedance lavalier microphone in the comment section of guarantee registration card.
- Mail to Shure Brothers, Inc. with your check or money order for \$5.00. If sending cash please send by registered mail.
- That's all there is to do. Your microphone will be sent to you post paid. Sorry, no C.O.D.s.

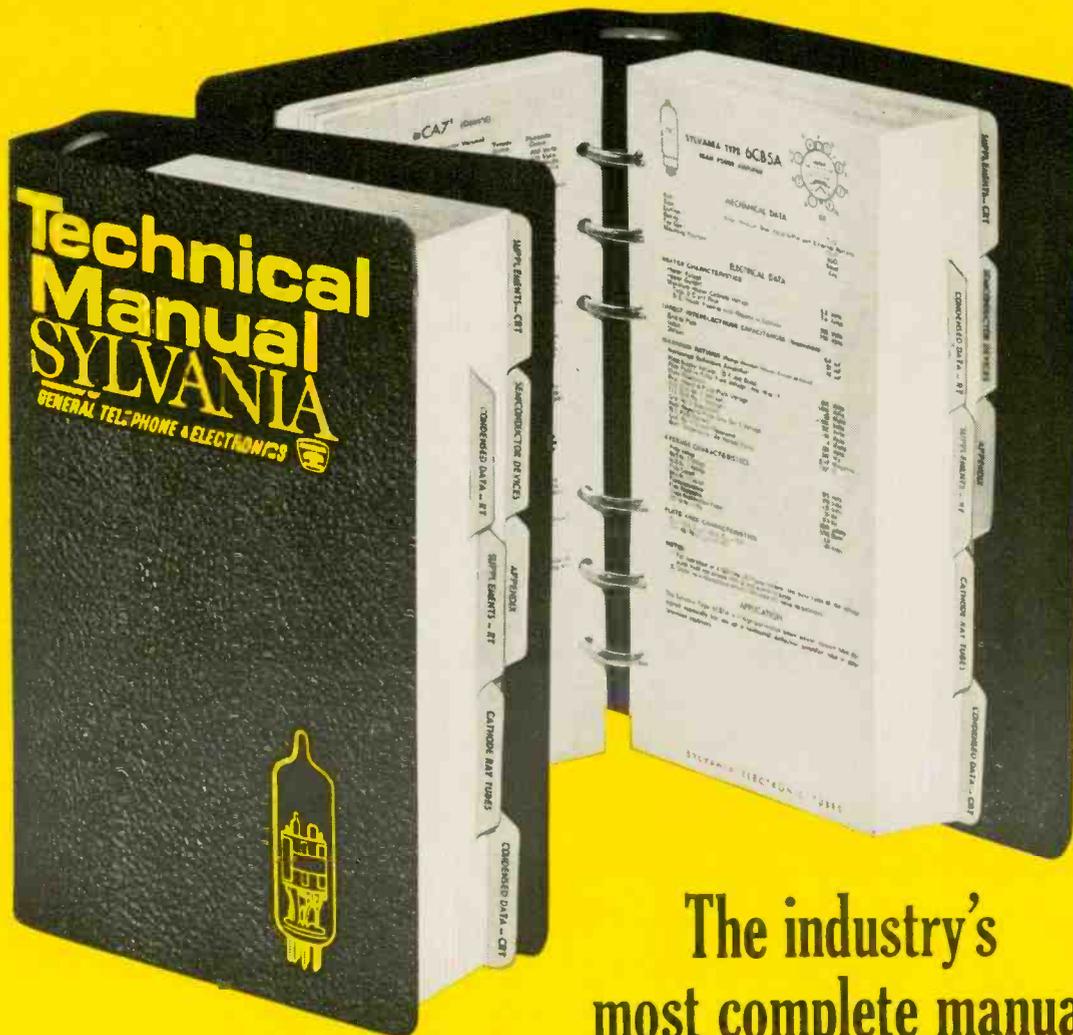you get **PRODUCT PLUS** from your Sylvania Distributor



## The industry's most complete manual

Even our non-customers say they can't do without it!

Sylvania's Technical Manual is still the most complete data source for up-to-date information on tubes... and has been since 1929. The current 12th Edition, for instance, will provide information on 2,225 tube types to more than 100,000 service men, technicians, dealers, distributors and other specifiers of tubes. (Incidentally, 2,225 is only the figure of the moment.) At periodic intervals, and at no extra charge, Sylvania mails supplementary data sheets to provide you with the latest information and insure that your Tech Manual is current.

Here are some of the other features you'll find in the manual's 700 pages:

- Data on Receiving Tubes, Cathode Ray Tubes, Semiconductor Diodes and Rectifiers, Special Purpose Tubes—all with complete characteristics.
- Picture Tube Interchangeability Guide
- European-American Receiving Tube Substitution Guide

- Semiconductor Diode Interchangeability Chart

• Master Index for quicker reference  
All in a sturdy 9½" x 6½" 6-ring binder with tabbed dividers.

The cost for the industry's most comprehensive manual is only \$3.00. See your Sylvania Distributor. And don't forget to mail in the prepaid post-card for the free supplement service.

**SYLVANIA**  
SUBSIDIARY OF  
**GENERAL TELEPHONE & ELECTRONICS GTE**

NEW CAPABILITIES IN: ELECTRONIC TUBES • SEMICONDUCTORS • MICROWAVE DEVICES • SPECIAL COMPONENTS • DISPLAY DEVICES

# C Correspondence

## OLD BACK ISSUES— REAL COLLECTORS' ITEMS

Dear Editor:

Do you know of anyone interested in acquiring the following magazines:

*Electrical Experimenter*

1917, 1918, 1919 (each a complete year) also 1920 (January–July)

*Science & Invention*

1920 (August–December)

1921, 1922 (each a complete year)

*Everyday Engineering*

1918, 1919, 1920 (each a complete year)

I would appreciate an offer, either for the lot or in part.

THOMAS H. CURTIS

99 Harrison Ave.

Fair Haven, N. J. 07702

## THE ERRONEOUS SPLITTER

Dear Editor:


Described in Try This One (June 1964, p. 84) was a device for matching multiple antennas to a single set or, equally well, one antenna to a number of sets. Unfortunately, the equation for determining R, the value of the shunt resistor to be used, is wrong. The equation for an N-port device with equal impedances at all ports is

$$R = \frac{NZ}{N-2}$$

The error in the original equation (where N-1 appeared in the denominator) is readily apparent by taking N = 2, a two-port pad—i.e., matching one set to one antenna. The value of R obtained,  $\frac{2Z}{2-1} = 2Z$ , would mean the impedance looking into the open port would be 2Z, 2Z and Z all in parallel, or Z/2. This is obviously a mismatch for a source of Z.

A little more thought along this line indicates that any finite resistance would mismatch the two-port system, since the second port impedance Z alone provides the correct match. In mathematical terms,  $R = \infty$ . The correct equation,  $(R = \frac{NZ}{N-2})$  shows this for two ports, since  $\frac{2Z}{2-2} = \infty$ .

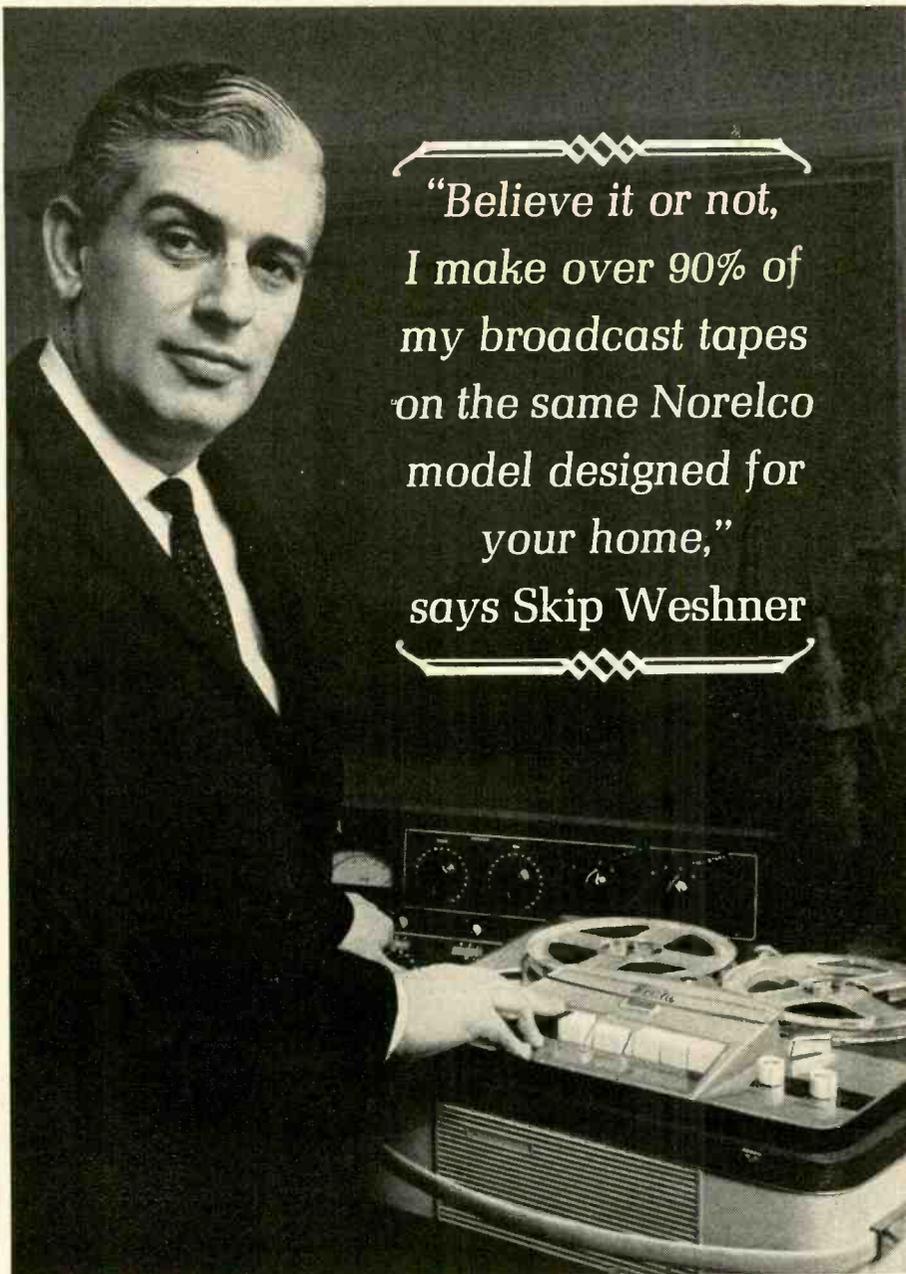In the laboratory, the most common application with the splitter is for



“Believe it or not,  
I make over 90% of  
my broadcast tapes  
on the same Norelco  
model designed for  
your home,”  
says Skip Weshner

“My tapes have to meet the broadcast standards of the leading FM stations around the country, whose other taped programs are normally recorded and played back on professional broadcast-studio consoles. My Norelco ‘401’ gives me tapes that not only meet or exceed these standards, but on playback on the ‘401’ I defy any listener to tell the difference between my live broadcasts and my taped ones!

“As to reliability, my Norelco has been on the firing line five nights a

week, month after month, year after year, and has required less maintenance than any other recorder I’ve ever used. It handles tape more gently, too: it doesn’t break tape, it doesn’t spill tape, it doesn’t stretch tape—not even the half-mil stuff I’m forced to use to get an hour’s broadcast on a 7” reel.

“Although the ‘401’ was designed for the operating convenience and for the pocketbook of the home user, in my book it has proved itself as a thoroughly professional instrument.”



The Norelco Continental ‘401’: 100% transistorized • 4-speed • 4-track stereo/mono, record/playback • completely self-contained with dual preamps, dual power amplifiers, two wide-range stereo-matched speakers and stereo dynamic microphone. (Two broadcast quality microphones can be used with simple adapter.)

At your hi-fi dealer’s—or write to Dept. S-9, North American Philips Company, Inc., High Fidelity Products Division, 100 East 42nd Street, New York, N. Y. 10017

**Norelco®**

# COMPUTER TECHNICIANS

*Immediate Stateside & Overseas Openings*

Must have a minimum of 2 years' experience in the maintenance of military or commercial computers or data processing systems.

Excellent benefits including stock savings plan.

Qualified candidates please send complete resume to Mr. Don Kirkland, Dept. 806.

## PHILCO TECHREP DIV.

A Subsidiary of Ford Motor Company

P. O. Box 4730

Philadelphia, Pa. 19134

An Equal Opportunity Employer


Everything you ever wanted in a CB transceiver!



**Newest! Most Versatile! Most Power Out!**

The 11 channel "Messenger III" will change every idea you ever had about what a Citizens Band unit should offer! Tiny, all transistor, it's really quiet, really hot! Interchangeable for base or mobile—use it as a full 5-watt battery powered portable pack set or a 3-watt PA system. The "Messenger III", with an aerospace transistor developed for the "Relay" communications satellite, delivers *more* power output with maximum legal input! Double conversion receiver with high 1st I.F. provides excellent spurious and image rejection. Set-and-forget "Volume" and "Squelch" controls make it possible for the first time to work "close-in" or at extended range with initial settings. Furnished with dynamic microphone—full line of accessories available for selective calling, portable field pack, or public address use!

Cat. No. 242-150.....\$189.95 Net

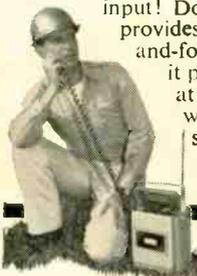

**WRITE TODAY**  
for details on the  
"Messenger" CB  
line—or see your  
distributor!



**E. F. JOHNSON COMPANY**

© 2510 Tenth Ave. S.W. • Waseca, Minnesota

Please send full details on the "Messenger" CB line.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

## Coming Next Month in Radio-Electronics

### BUILD A UNIVERSAL TAPE PREAMPLIFIER

A three-transistor, humless job, this preamp works with any recorder or player, regardless of input impedance. Small and simple to construct, it has no heat problems, is a low-noise device and has a longer life than the tube preamp it replaces.

### REPORT ON AMPLIFIED ANTENNAS

Are those antennas-with-transistors any good? If so, how much? Can they actually make reception worse? Is there a difference in performance between the ones that look like a box and those that resemble rabbit ears more closely? *Radio-Electronics* tested a number of these "amplified antennas." Next month, read what we found out!

### MOCKUP BENCH JIG SPEEDS COLOR SERVICE

Homer Davidson tells how an old color trade-in TV can be made into a time-and-money-saver for the TV shop starting to service color. Saves one man on color TV calls. Learn how he does it.


### MODERN STEREO CARTRIDGE REVIEW

A complete roundup of all the leading stereo cartridges—some of the differences between them, what they will do, and how they affect the listening audiophile. Not a colorless table of measurements—these cartridges were tested by playing records, and our reviewer reports on how they sound.

*You'll find these and many other articles, features and regular departments in next month's RADIO-ELECTRONICS.*

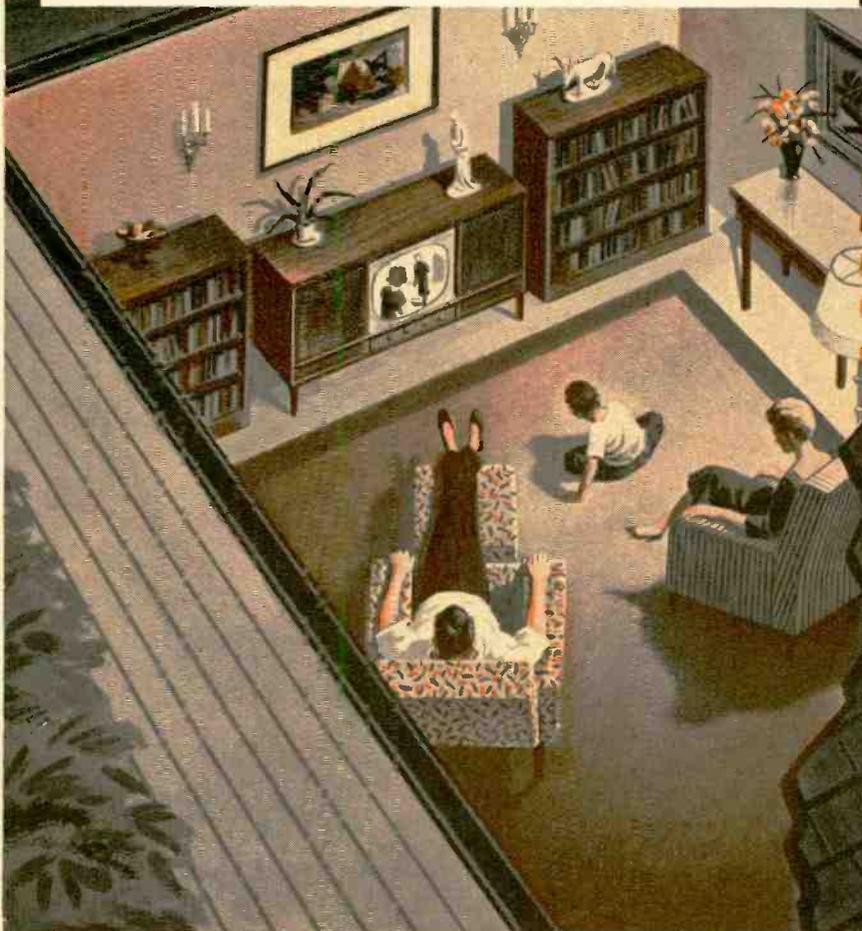**OCT. ISSUE (on sale Sept. 17)**

what PARALOG brought to VHF...  
**NEW**  
**PARACYL**  
**BRINGS TO UHF TV**



**...UHF all-channel antenna with fantastic vertical directivity**


**Good news!** The new Jerrold-Taco PARACYL antenna combines cylindrical-parabolic construction with an exclusive "Extended Resonance" driven dipole\* to deliver superior TV reception throughout the entire UHF band (channels 14 through 83).

Cylindrical-parabolic configuration assures the wide vertical interception area so necessary to capture elusive UHF signals, protect against "dead spots", and provide the greatest directivity. The "Extended Resonance" dipole driver actually changes its electrical length to present a half-wave appearance at the low and high ends of the UHF band, giving optimum gain and match all the way from 470 mc to 890 mc.

See your Jerrold-Taco distributor now, and learn how PARACYL antennas can open the door wide to big UHF sales for you.

\*Patent pending

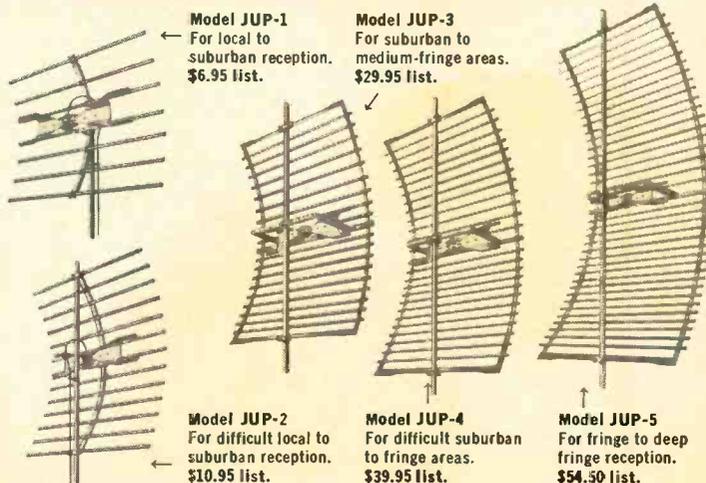Distributor Sales Division, Philadelphia, Pa. 19132



Model JUP-1  
For local to suburban reception.  
\$6.95 list.

Model JUP-3  
For suburban to medium-fringe areas.  
\$29.95 list.

Model JUP-2  
For difficult local to suburban reception.  
\$10.95 list.


Model JUP-4  
For difficult suburban to fringe areas.  
\$39.95 list.

Model JUP-5  
For fringe to deep fringe reception.  
\$54.50 list.

# TUNER REPAIRS

Includes ALL parts (except tubes)...  
ALL labor on ALL makes for complete overhaul.

# \$9.50

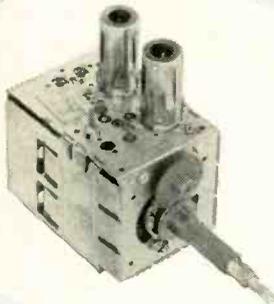

**FAST, 24-HOUR SERVICE**  
with **FULL YEAR WARRANTY**

Sarkes Tarzian, Inc., largest manufacturer of TV and FM tuners, maintains two completely-equipped Service Centers, offering fast, dependable tuner repair service. Tarzian-made tuners received one day will be repaired and shipped out the next. More time may be required on other makes. Every channel checked and realigned per manufacturer's specs. Tarzian offers full, 12-month guarantee against defective workmanship and parts failure due to normal usage. Cost, including all labor and parts (except tubes), is only \$9.50 and \$15 for UV combinations. No additional costs. No hidden charges. You pay shipping. Replacements at low cost are available on tuners beyond practical repair.

Always send TV make, chassis and Model number with faulty tuner. Check with your local distributor for Sarkes Tarzian replacement tuners, parts, or repair service. Or, use the address nearest you for fast factory repair service.



**SARKES TARZIAN, INC.**  
TUNER SERVICE DIVISION

Dept. 200  
537 South Walnut St.,  
Bloomington, Indiana  
Tel.: 332-6055

Dept. 200  
10654 Magnolia Blvd.,  
North Hollywood, Calif.  
Tel.: 769-2720

connecting multiple signal generators to one receiver (or active circuit), and I have often used the devices for that. However, I must object to the editor's use of the term *balanced*. A balanced circuit or network is defined as one in which the two sides are electrically alike or symmetrical to a common reference point, usually ground. The device shown is obviously not balanced when one considers any antenna as a source generator and the set as the receiver load; it is simply *ungrounded*.

LAWRENCE C. MIDDLEKAMP  
Laurel, Md.

## REDS SHOULD BE READ ✓

Dear Editor:

"Double Bridge Sensitivity" in the June 1964 issue is reminiscent of a circuit described in a book on meteorological tower instrumentation published last year in Russia. Does this mean that electronic hobbyists are missing some good bets if they fail to keep up with the Russian literature?

By the way, the miniature tape recorder mentioned by Steve P. Dow on p. 89 of the May issue can be used with a Knight-Kit 83Y261D tuner and a suitable speaker to make an inexpensive AM receiver for periods when the recorder would otherwise be loafing. The tuner output is plugged into the microphone jack, and the speaker into the earphone jack. With the recorder in the forward record mode, there is plenty of signal for the speaker. I use a retired 12-inch Jensen, but I have to admit it sounds better with 200  $\mu$ f across its terminals. Perhaps another reader could suggest some refinements for this hookup.

STU KELLOGG

Lexington, Mass.

## STICK IN A SURGE RESISTOR TO BE SURE ✓

Dear Editor:

In the August 1963 issue of RADIO-ELECTRONICS you had an article by Earl Hansen titled "Chopper Stabilized dc Amplifier." While most of the schematic is correct, Mr. Hansen omitted one very important component: the surge resistor preceding diode D5 in the power supply. Although a 1N2070 can handle up to a 6-amp peak for a small fraction of a second, a charging 80- $\mu$ f capacitor will quickly destroy the diode. A 68-ohm  $\frac{1}{2}$ -watt carbon resistor between the transformer and the diode limits the initial charging current and protects the diode.

GERALD FELDMAN

Los Angeles, Calif.

[Mr. Feldman's suggestion is a good one—putting in a surge-limiting resistor can hardly do any harm. But often, in low-current power supplies like the one in Mr. Hansen's amplifier, the dc resistance of the power transformer secondary is 100 ohms or more per half, limiting the maximum inrush current to an ampere or two.—Editor]

## TWO MORE USES FOR THE 6BN6 ✓

Dear Editor:

In the June 1964 issue of RADIO-ELECTRONICS, Leo Sands left out two valuable applications of the 6BN6:

1. As a gated-beam mixer good to at least 30 mc—described in Markus and Zeluff, *Electronics for Communications Engineers*, McGraw-Hill, 1952, p. 38.

2. As an excellent product detector for single-sideband reception—described in *Single Sideband for Amateur Radio*, American Radio Relay League (ARRL), 1962, p. 79.

I believe that this tube can also be used as a balanced modulator for generating SSB and DSB, but I cannot recall where I saw the circuit.

K. J. DESKUR

Endicott, N.Y.

## NATESA VS. FTC: PROBLEM STILL THERE

Dear Editor:

As a subscriber to RADIO-ELECTRONICS and several other publications, clubs and societies in electronics, I would appreciate a chance to comment on the Federal Trade Commission's decision barring NATESA from "blackballing" those distributors and wholesalers who trade with the general public and with part-time technicians.

Although I cannot agree with NATESA's view on the part-time technician, since I have known some who could challenge the best of the full-time professionals, I assume that the FTC and NATESA agree on how best to cure their patient.

But, a question: How is the FTC empowered to deal with those distributors and wholesalers that trade with the public on the same terms—and often better terms—than with dealers and service outfits? It is well known that, in Manhattan especially, this kind of trading hurts even the public, not to mention the scores of small businesses now and in the future.

Does the FTC have any answer to that problem?

J. S. BUITRAGO

Riverdale, N.Y.

END

# Color-TV servicing is profitable

GET THE MOST OUT OF IT WITH COLOR-TV TEST INSTRUMENTS FROM RCA—  
PIONEER OF COLOR TV



Making last-minute convergence adjustments on a color-TV receiver with an RCA WR-64A Color-Bar/Dot/Crosshatch Generator.

## (A) RCA WR-64A COLOR-BAR/DOT/CROSSHATCH GENERATOR

Low-cost, lightweight, portable instrument that provides all essential Color-TV test patterns:

- *Color-bar pattern*: ten bars of color for checking phase and matrixing, and for automatic frequency and phase alignment.
- *Crosshatch pattern*: thin sharp lines for adjusting vertical and horizontal linearity, static and dynamic convergence, raster size, and overscan.
- *Dot pattern*: small dots to facilitate accurate color convergence.

\$189.50\* with output cables

## (B) RCA WR-70A RF/VF/IF MARKER ADDER

For use with a marker generator and a sweep generator. Used for RF, IF, and VF sweep alignment in color and B&W TV receivers.

- Choice of four different marker shapes
- Provides very high-Q markers of high amplitude and narrow bandwidth

\$74.50\* complete with cables

## (C) RCA WO-91A 5-INCH OSCILLOSCOPE

A wideband scope for checking colorburst signals and general troubleshooting.

- Dual bandwidth: 4.5 Mc at 0.053 volt rms/in. sensitivity; 1.5 Mc at 0.018 volt rms/in. sensitivity.
- Continuously adjustable sweep frequency range: 10 cps to 100 Kc

\$249.50\* including direct/low capacitance probe and cable, ground cable, and insulated clip.

## (D) RCA WR-69A TELEVISION FM SWEEP GENERATOR

For visual alignment and troubleshooting of color and B&W TV receivers, and FM receivers.

- IF/Video output frequency continuously tunable from 50 Kc to 50 Mc.
- Sweep-frequency bandwidth continuously adjustable from 50 Kc to 20 Mc on IF/Video and FM; 12 Mc on TV channels

\$295.00\* including all necessary cables

## (E) RCA WR-99A CRYSTAL-CALIBRATED MARKER GENERATOR

Supplies a fundamental frequency RF carrier of crystal accuracy for aligning and troubleshooting color and B&W TV receivers, FM receivers.

- Most-used IF and RF frequencies indicated on the dial scale
- Sound and picture carrier markers available simultaneously

\$256.50\* complete with output cable and phone tip.

## (F) RCA WT-115A COLOR PICTURE TUBE TESTER

Designed specifically to test color-TV picture tubes, either in or out of the set. Tests each gun for emission quality, inter-electrode leakage and shorts.

- Large sensitive meter with separate 3-color scales
- Provision for accurate adjust-



New RCA Color Pict-O-Guide is now available through Authorized RCA Electron Tube Distributors.

ment of cut-off point for each gun  
\$89.50\* with cable, carrying case and socket assembly

See them all at your Authorized RCA Test Equipment Distributor.

\*Optional Distributor Resale Price  
All prices are subject to change without notice. Prices may be higher in Alaska, Hawaii and the West.

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N. J.




The Most Trusted Name in Electronics

fast, accurate, never lets you down . . .

New Burn-out,  
stick proof meter!

NEW  
SPEEDY  
SET-UP  
BOOKLET

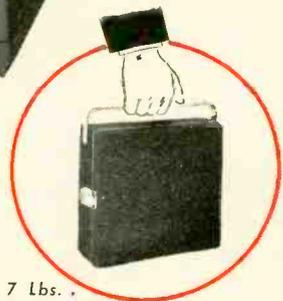

only

**\$7450**

**NEW TC 130**

Checks them all . . .  
including Novars, Compactrons,  
Nuvistors, 10 pin tubes — plus  
Picture Tubes!

Only 7 Lbs. . .  
Smaller Than A Portable Typewriter

Here's the famous MIGHTY MITE, America's fastest selling tube checker, with an all-new look and many new exclusive features. MIGHTY MITE III brings you even greater portability, versatility and operating simplicity beyond comparison. Controls are set as fast and simply as A-B-C right from the speedy set-up cards in the cover. The new functional cover can be quickly removed and placed in a spot with more light for faster reading of the set-up data or "cradled" in the specially designed handle as a space saver as shown above. New unique design also prevents cover from shutting on fingers or cutting of line cords as in older models.

In a nut shell . . . the MIGHTY MITE III is so very popular because it checks for control grid contamination and gas just like the earlier "eye tube" gas checkers (100 megohm sensitivity) and then with a flick of a switch, checks the tube for inter-element shorts and cathode emission at full operating levels. Sencore calls this "the stethoscope approach" . . . as each element is checked individually to be sure that the tube is operating like new. User after user has helped coin the phrase "this checker won't lie to me". Most claim that it will outperform large mutual conductance testers costing hundreds of dollars more and is a real winner in finding those "tough dogs" in critical circuits such as color TV and FM stereo.

**See Your Parts Distributor-- And See  
The Mighty Mite III For Yourself!**

**NEW**

**IMPROVED**

**MIGHTY  
MITE**

**NEW**

Lower voltage checks for  
Nuvistors and all new frame  
grid tubes, as demanded by  
tube manufacturers, but not  
found on other tube checkers.

**NEW**

Speedy indexed set-up cards  
to reduce "look-up" time.  
No more cumbersome booklets,  
or incomplete charts.

**NEW**

Simplified panel layout  
reduces set-up time — prevents  
set-up errors

**NEW**

Streamline styling  
with rounded corners  
and rubber feet, prevents  
marring Furniture — presents  
that "Professional look".

**SENCORE**

"Quality at its finest"

**426 SOUTH WESTGATE DRIVE  
ADDISON, ILLINOIS**


# The Picturephone In Your Future

ON APRIL 20, 1964, the American Telephone & Telegraph Co. unveiled its newest device, the *Picturephone*, at the New York World's Fair. (The *Picturephone* is shown on page 6 of the July 1964 RADIO-ELECTRONICS.) Viewers could see people across the country, as far away as Los Angeles, Calif., in a coast-to-coast press conference. Ever since, the long-awaited "See-as-you-talk" phone has been drawing huge crowds at the AT&T pavilion at the Fair. There, soundproof booths equipped with *Picturephones* allow visitors to talk with each other or with a nearby telephone operator. Visitors sit about 3 feet from the little instrument's screen, housed in a small desktop table set. Normal room illumination is sufficient for the little vidicon tube next to the set's screen to give a good picture. On June 24, the *Picturephone* went into commercial use in a circuit linking public booths in New York, Washington and Chicago.

Picture size is  $4\frac{3}{8}$  x  $5\frac{3}{4}$  inches. The control set uses no dial; it has pushbuttons which allow you to see yourself, another person or nothing at all at your choice.

The idea of the long-distance *Picturephone* is hoary with age. It probably was first used anywhere in word and picture in my novel, *Ralph 124C 41+* (A Romance of the Year 2660), originally published in installments beginning with the April 1911 issue of *Modern Electrics*, forerunner of RADIO-ELECTRONICS.

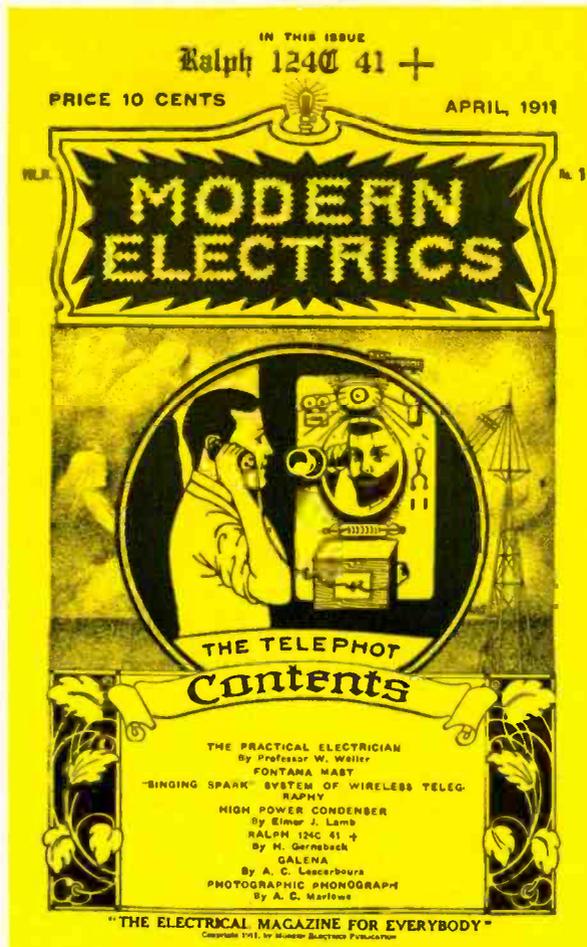For the record, 53 years ago the instrument was known as the *Telephot*. As the story opens, Ralph 124C 41+, one of the world's most renowned scientists and one of the ten celebrated *Plus men of the Planet*, is talking from New York long distance to a friend, over the telephot.



Front cover of the April 1911 issue of *MODERN ELECTRICS*, illustrating the use of the earliest known *Telephot*, now called the *Picturephone*.



This 1925 illustration of the *Telephot*, now known as the *Picturephone*, appeared in the first book reprint of the novel *RALPH 124C 41+*. Note microphone on top of loudspeaker, openings at left. The *Telephot* also foresaw the *Language Rectifier*, so far not realized.

# Radio-Electronics

Hugo Gernsback, Editor-in-Chief

... Immense Are the  
Coming Applications of  
This Great Device ...

Suddenly there is an interruption, just as we have today—and the screen of the telephot goes blank. Then:

"At this moment the voice ceased and Ralph's faceplate became clear. Somewhere in the Teleservice company's central office the connection had been broken. After several vain efforts to restore it Ralph was about to give up in disgust and leave the *Telephot* when the instrument began to glow again. But instead of the face of his friend there appeared that of a vivacious beautiful girl. She was in evening dress and behind her on a table stood a lighted lamp.

"Startled at the face of an utter stranger, an unconscious 'Oh!' escaped her lips, to which Ralph quickly replies:

"I beg your pardon, but 'Central' seems to have made another mistake. I shall certainly have to make a complaint about the service."

"Her reply indicated that the mistake of 'Central' was a little out of the ordinary, for he had been swung onto the Intercontinental Service as he at once understood when she said, 'Pardon, Monsieur, je ne comprends pas!'

"He immediately turned the small shining disc of the *Language Rectifier* on his instrument till the pointer rested on 'French.'"

This starts the great international and interplanetarian romance, with the heroine, Alice, in distant Switzerland. Ralph subsequently saves her, via electronics, from an immediately threatening avalanche.

While the *Picturephone* is now an assured fixture, what are its implications for the future?

At present, while it is new, it still is a luxury. AT&T made public its rates: \$16 for the first three minutes between New York and Washington, \$21 between Chi-

continued on page 81

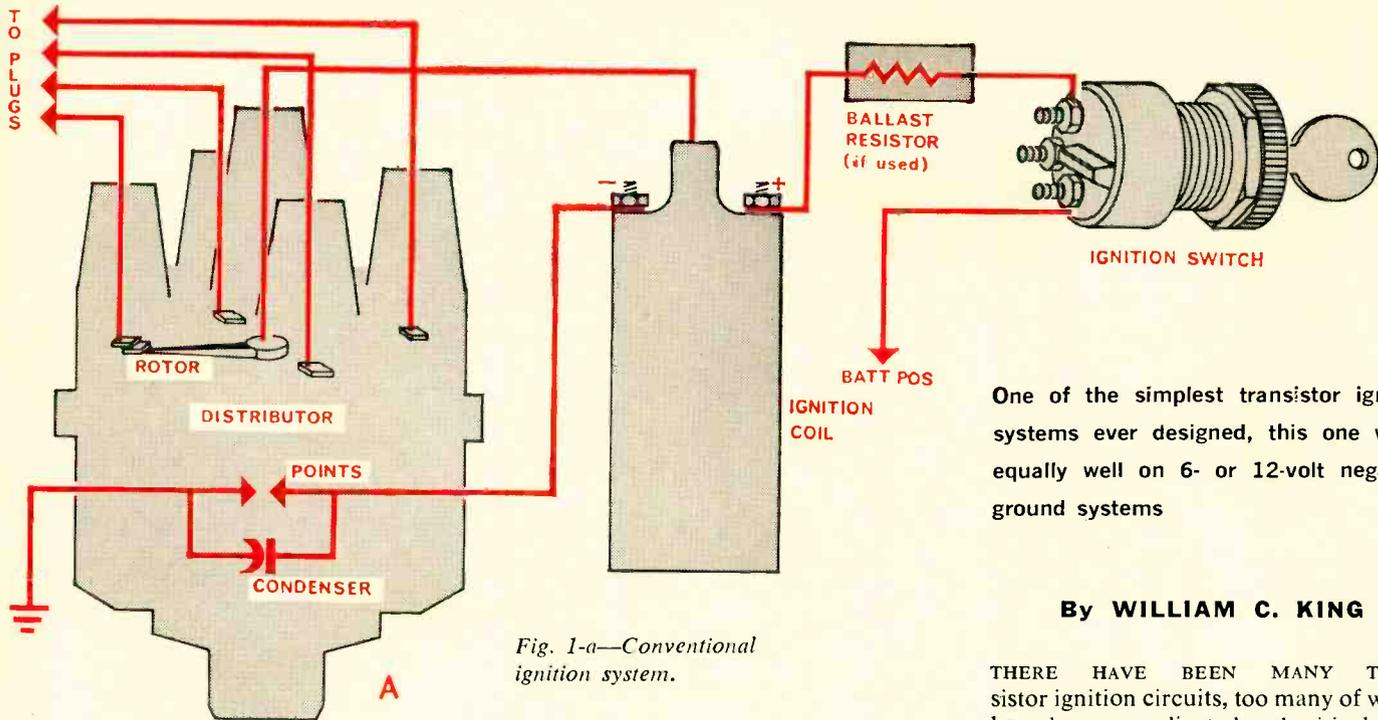


Fig. 1-a—Conventional ignition system.

One of the simplest transistor ignition systems ever designed, this one works equally well on 6- or 12-volt negative-ground systems

By WILLIAM C. KING

THERE HAVE BEEN MANY TRANSISTOR ignition circuits, too many of which have been complicated and critical. This circuit uses a basic series-connected transistor switch for simplicity. To eliminate the need for a special coil to lower the back voltage so that one or two transistors can take it, I've used three in series. The price of one or two more transistors is usually less than that of a special coil. The fact that no Zeners are used makes the system even more attractive.

Three 2N174's in series (see schematic) will withstand 240 volts, more than enough for a standard coil. They need not be matched, but the three in series require a network of base resistors to balance the voltage. R5, R6, R7 balance the "off" (high) voltage equally across the transistors. R1, R2 and R3 balance the transistors for an even voltage drop during conduction. The diodes provide base isolation, and R4 limits the total base current to around 0.75 amp. Theoretically the values for R5, R6 and R7 or for R1, R2 and R3 should be the same, but transistor characteristics vary. If you start with the values I have given, you should come close.

#### Construction and installation

I mounted the transistors on a 1/8 x 3 x 6-inch heat sink with the other parts on terminals between them.

After the system is built, you will need a 6-amp 12-volt power supply and a 2-ohm 100-watt resistor to adjust it.

# Zenerless Transistor Ignition

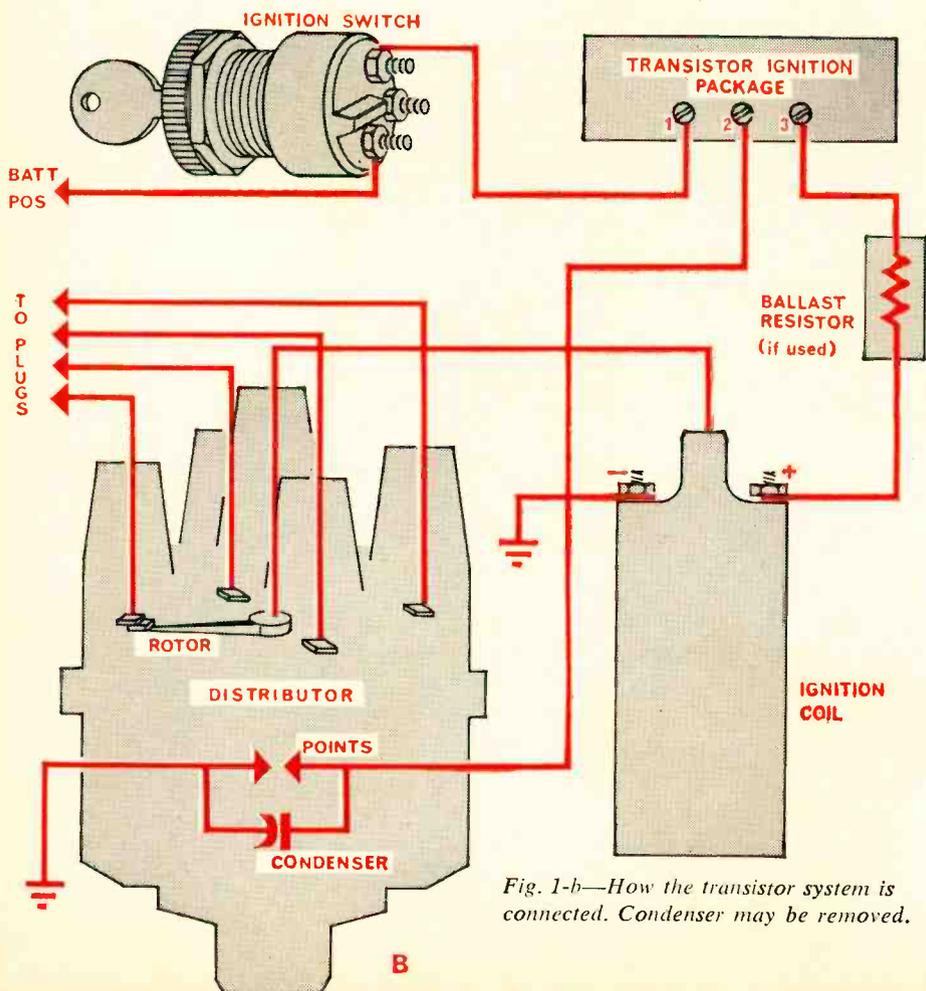


Fig. 1-b—How the transistor system is connected. Condenser may be removed.

An editor of Radio-Electronics, who used William King's ignition system for 4,000 miles of driving in a 1960 Ford Falcon, reported:


"The unit works and works well. It's downright easy to connect—one bolt bracket mounting and three leads.

"Points clean and not eroded at end of test period. Plugs also fairly clean, but not as good as points.

"Gas economy up by about 2 mpg (this only when engine tuned after system installed). Acceleration and smoothness of engine seemed improved, especially on long upgrades with engine lugging.

"If I had the time, I'd probably build one of these for myself."

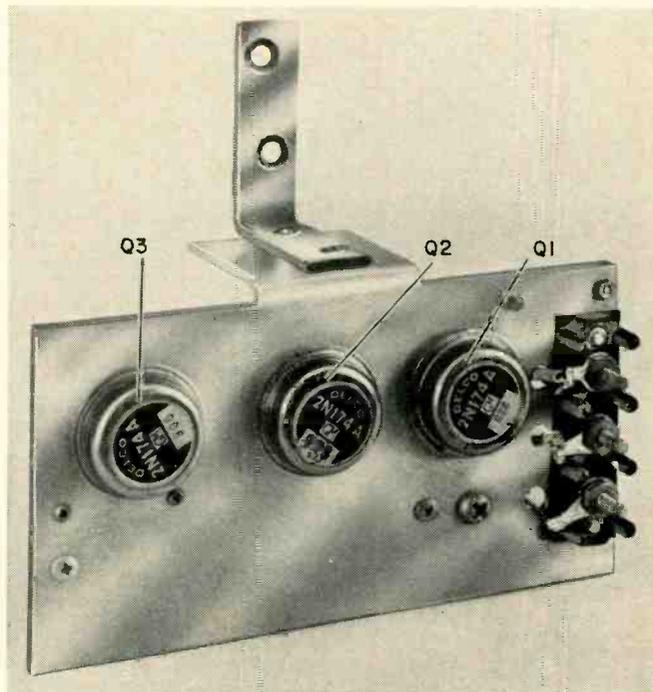Aluminum 1/8 inch thick doubles as heat sink and chassis. 2N174-A collectors are common to cases, and must be insulated from heat sink with mica washers.



1. Connect point 1 to B-plus, point 3 to R, which goes to B-minus. Don't connect 2 to anything yet. The transistors should be off. Now adjust R5 and R6 alternately for equal voltage drop across the transistors (from collector to emitter).

2. Ground point 2 now (this turns on the transistors) and check to see if the drops across the transistors are equal and about 0.3 volt or lower. If they are not equal, adjust R1, R2 and R3. If they are equal but too high, decrease R4. This completes adjustment.

Now install the system in the car (Fig. 1).

1. Select a cool location for the unit and mount it.

2. Refer to Figs 1-a and 1-b. Disconnect the lead from the negative side of the coil.

3. Trace the lead from the ballast resistor to the ignition switch. Disconnect the lead from the switch and connect it to point 3 on the transistor package terminal block.


4. Connect a lead from the switch terminal just freed to point 1 on the transistor package terminal block.

5. Ground the lead from the negative side of the coil.

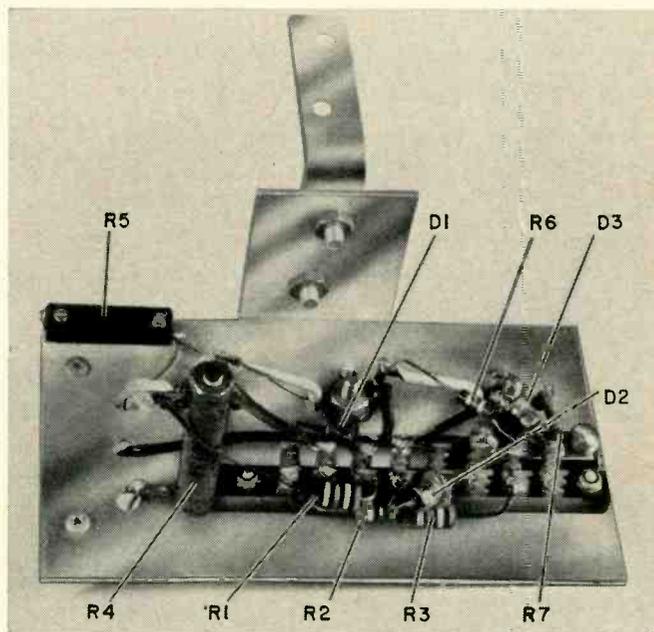
6. Connect the high side of the points to point 2 on the terminal block.

At this writing, the unit has been installed for approximately 1,000 miles each on a '59 Plymouth, a '58 Porsche, a '60 Chrysler 300 and a '61 Dodge. Driving conditions ranged from stop-and-go city driving through long high-speed trips including several desert crossings at temperatures above 100°. The waveforms are the same as they were when the equipment was installed and no parts have been replaced.

The Porsche has a 6-volt electrical system, and by reducing R4 to 5 ohms, the Zenerless ignition system worked just as well as on 12 volts. END



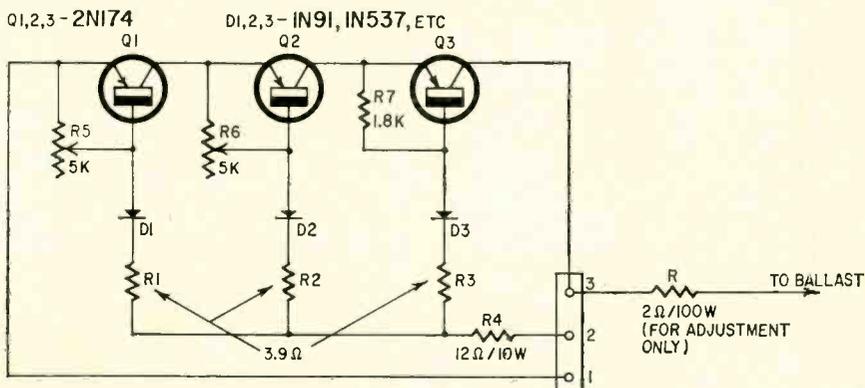
Circuit is easy and painless to wire. Watch diode polarities.



Circuit of Zenerless transistor ignition system.

- D1, D2, D3—100 piv min., 150 ma germanium or silicon diodes (minimum ratings) (1N91, 1N537, -538, -539, etc.)
- Q1, Q2, Q3—2N174 or 2N174-A (Delco, Motorola, RCA)
- R1, R2, R3—3.9 ohms, 1 watt
- R4—12 ohms, 10 watts

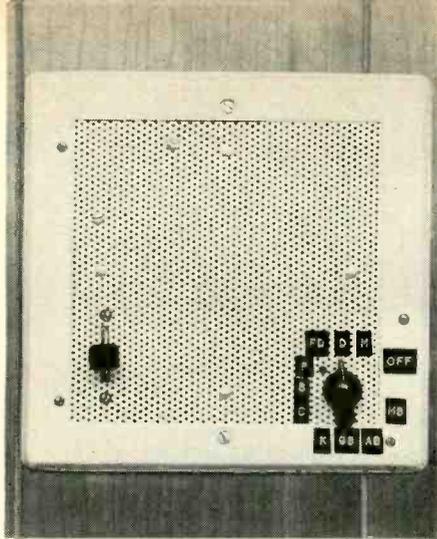- R5, R6—pots, 5,000 ohms (author used Bourns Trimpots, but ordinary carbon units are suitable)
- R7—1,800 ohms, 1/2 watt
- Aluminum sheet for heat sink and mounting bracket (see text)
- Solder lugs, miscellaneous hardware



One indoor station in author's system. Selector positions are Music, Den, Front Door, Patio, Basement, Conference, Kitchen, Guest Bedroom, Amy's Bedroom, Master Bedroom, and OFF.

4. To assure privacy, no station can be arbitrarily monitored by another station.

5. All internal stations can switch to a "music mode" where any audio from a centrally located phonograph, FM-AM tuner or tape deck can be listened to. If a station is addressed while in the music mode, it automatically switches to an intercom mode and only the caller is heard. After completion of the call, the station reverts to music mode.

6. For economy, only one transistor power amplifier is used for the entire system. This doesn't limit usefulness, since the chance is small that more than one call will be made at the same time. In the unlikely event two calls from different stations are made simultaneously, the conversations are mixed and heard as one by two listeners, but at reduced volume.

Stations in the music mode lose music audio during any intercom conversation regardless of whether or not they are being addressed. No intercom audio is heard either, unless these stations are being addressed. If you object to that, you can build two identical amplifiers, one for the music mode and the other for all intercom modes.

7. Front- and back-door stations cannot select individual stations, but always address in conference mode.

8. The transistor amplifier is left on at all times.

# Super Communications Network For Your Home

Designed originally for fun, this fabulous intercom turned out to be as vital as a telephone system!

By ARTHUR SCHLANG


Looking for an intercom system for my new home, I couldn't find anything at a reasonable cost that met all my needs. Most available systems consist of a master station and a number of remote stations. A remote may communicate with another remote only through the master station. For a completely flexible communication system, you'd need a full-time telephone operator at the master station! Furthermore, I wanted to use transistors. So I designed an intercom system with these features:

1. Any internal house station can address any other station individually without going through a centrally located master station.

2. Any station can address all other stations simultaneously ("conference mode").

3. Any internal house station can switch so that it cannot be called either individually or in conference mode.

Fig. 1—Complete circuit of indoor station. There are six others like it in author's system.

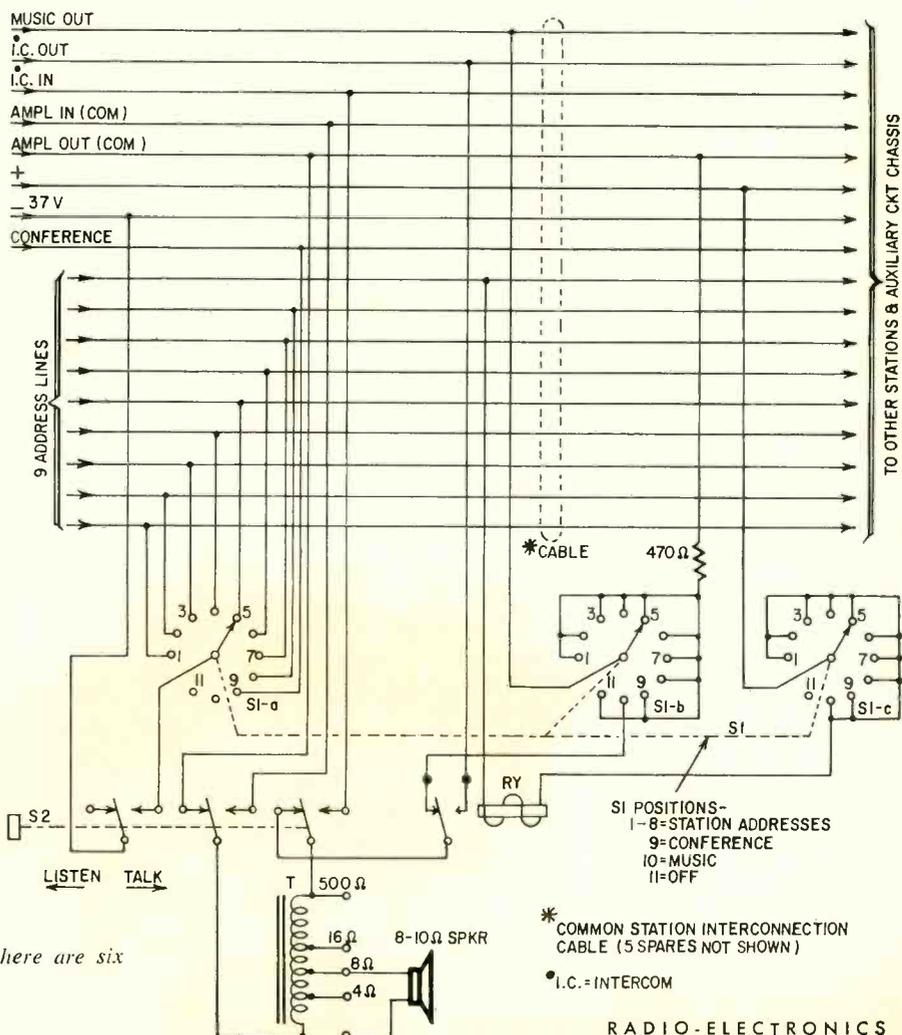


## What it does

Each internal house station has an 11-position rotary switch. Eight of these positions select eight other stations for address. (There are nine stations in all in my house.) The ninth switch position selects the conference mode, the tenth the music mode, and the eleventh position is off.

A station can be called by another regardless of its switch setting, except in the off position. A spring-return push-to-talk key switch is also provided at each station.

To address another station, select that station with the rotary switch, then press the key switch to talk. The key switch must be released to listen to the reply. For privacy, a station cannot be monitored unless its key switch is depressed. In my baby daughter's room, however, a latch is arranged so that the key can be held down for baby-sitting. You can do the same thing in a sick-room application. Sensitivity is enough to pick up normal conversation at any point in a room.

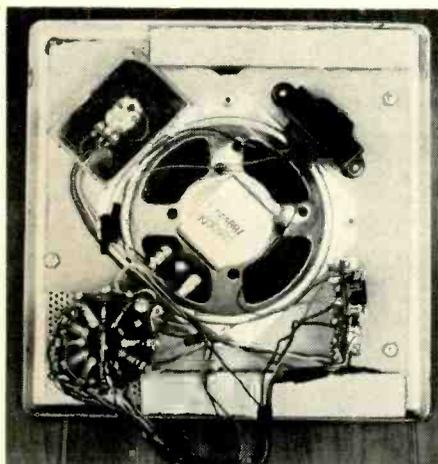To avoid confusion, always identify your station so that the addressee knows



Inside one of the indoor stations.

where to switch to answer. If you don't know a person's whereabouts, use the conference mode.

## Installing the system

Intercom wiring is best installed before wall and ceiling material is nailed

on the studding of a new house. Wiring through completed walls is possible but difficult. I used cable containing eleven twisted pairs of No. 22 wire in a plastic sheath (Birnbach catalog no. 4711) run between all stations. This provides five spare wires for future modifications.

Rather than do the metalwork for each station myself, I used commercially available remote stations. They consist of a metal wall box with a removable front bearing a speaker and switch.

(The speakers and housings I used were bought a long time ago—I don't remember who makes them. They are not at all critical. Utah makes suitable baffles; try an MS3 with baffle housing ME3 for outdoors, and an MS5 with ME45 baffle housing for indoors. A suitable indoor speaker is the Utah SP-4A1; outdoors, the SP35A1. Nutone also makes a series of speaker-and-baffle combinations. Lafayette stock no. SK-209 is a weatherproof outdoor speaker with louvered enclosure. And you can always drill and punch ordinary aluminum chassis yourself. Any of the large electronics supply house catalogs should give you many suggestions.)


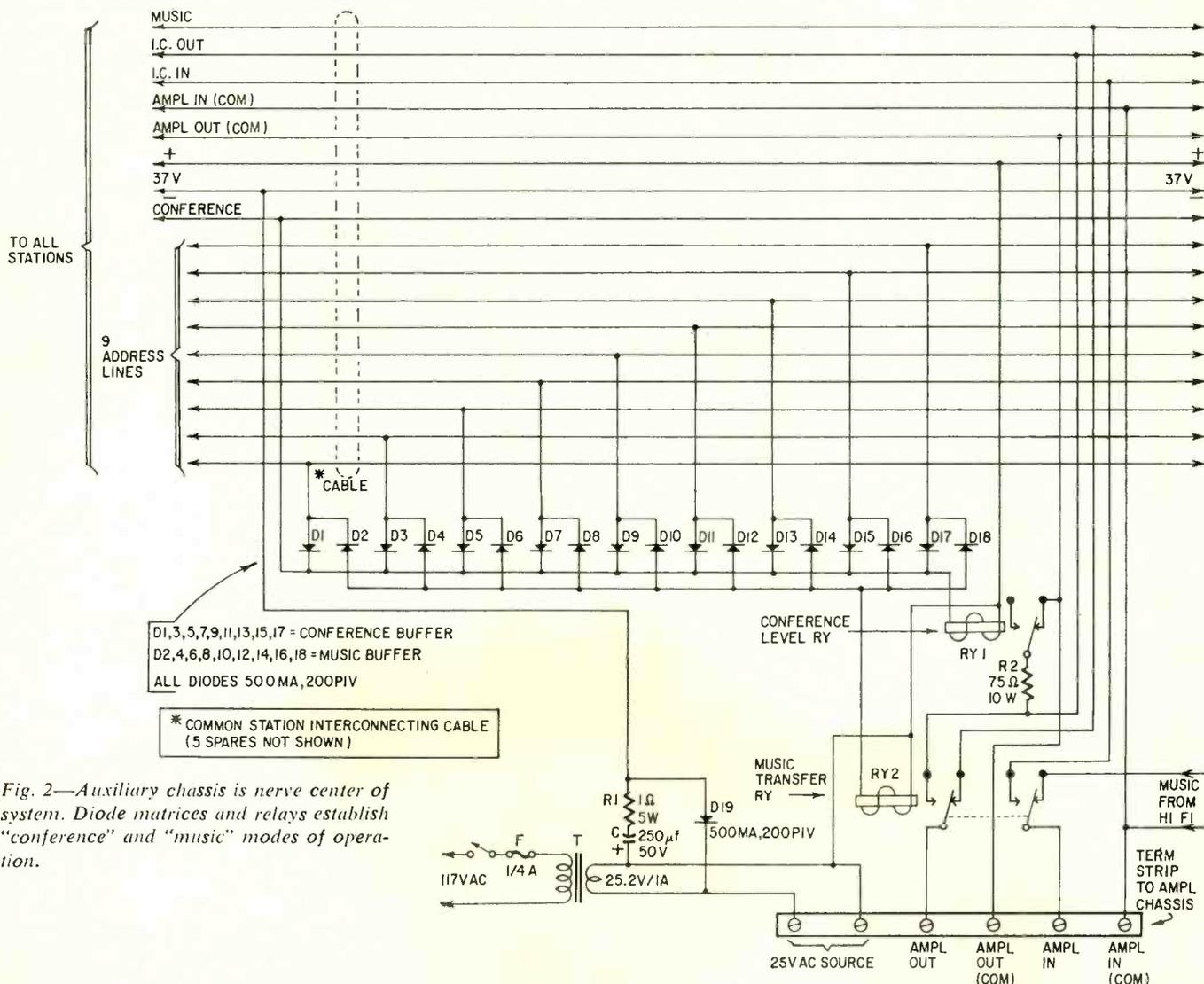


Fig. 2—Auxiliary chassis is nerve center of system. Diode matrices and relays establish "conference" and "music" modes of operation.

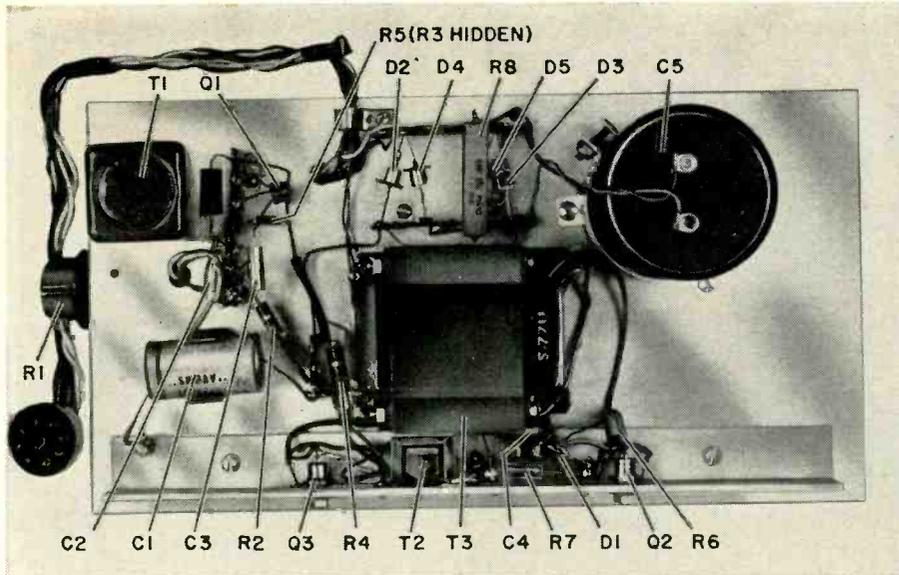



Two-stage, three-transistor amplifier is common to all modes of operation. Output transistors are double-ended stud-mounting type, heat-sunk on aluminum angle stock at forward edge of chassis. Other case types can be used, but must also be appropriately heat-sunk.

from the amplifier output. This maintains a constant audio level in switching from an individual to a conference address. You may have to trim this value to meet your needs. Music buffer diodes (D2-D18) in Fig. 2 energize the music transfer relay RY2 when any or all of the station lines are energized. These diodes also isolate individual address lines from each other.

Music relay RY2 then transfers the amplifier input from music input to the microphone lines. The amplifier output

is transferred from the music to the intercom output lines. When the music relay is energized, only those relays energized in each station (Fig. 1) can accept a call.

Deck S1-b in an individual station (Fig. 1) normally connects a 470-ohm resistor from the music line to the amplifier output common. When the switch is in the MUSIC (M) position, the 470-ohm resistor is removed from the circuit and the speaker with its transformer is connected instead. This puts con-

stant resistive load on the music line whether a station is listening to music or not, and keeps constant signal level for all switch settings.

Deck S1-c prevents a station relay from becoming energized in the OFF position. You can omit that deck if you don't mind being interrupted.

Dc power for all relay circuitry is developed by the small power supply in Fig. 2. Dc is used for control because the diode buffers must be correctly polarized, and to keep hum level down. The same transformer is used for amplifier power.

All the relays are inexpensive units distributed by Lafayette Radio, catalog No. F-260. Check that a small air gap is left between pole piece and armature when the relay is energized, or it may not drop out when power is removed. These relays have 5,000-ohm coils, so that even when all are energized simultaneously, power consumption is negligible. They come packaged in individual plastic cases. Leave the cases on when you mount the relays, for protection.

At front- and rear-door stations, there are no rotary switches, so all calls are in the conference mode (Fig. 4). Music is always on unless a spare music line is used for these two stations. This line can then be switched off at the amplifier.

### The amplifier

The transistor amplifier is straightforward. Be sure to mount the output transistors on heavy heat sinks. They are operated in class-B and can develop 15 watts.

The 2N539-A transistors used in the output stage (Q2, Q3) cost \$12.35 apiece from the manufacturer, Minneapolis-Honeywell. Two less expensive substitutes (in the diamond-shaped TO-3 package) are the 2N511-B, made by Bendix and Texas Instruments (\$6.35) and the 2N375 (Bendix and Motorola, \$4.10). These two alternate types are available from Newark Electronics Corp., 223 W. Madison St., Chicago 6.

Another way to beat the cost is to use a separate, lower-voltage power supply for the amplifier, making it possible to use output transistors with a lower breakdown rating (almost any of the old standards, like the 2N255, 2N-301, 2N301-A, 2N554, 2N1501, etc.). All that that requires is to use a separate power transformer (Stancor P-8130, 12.6 volts ct at 2 amps, for example) with the same rectifier and filter components shown in Fig. 3, to give a supply of about 18 volts. With that lower voltage, omit R4 in Fig. 3 (1,800 ohms) and change R6 to 470 ohms, 2 watts.

A universal audio output transformer included in the amplifier permits matching to various impedance lines.

END


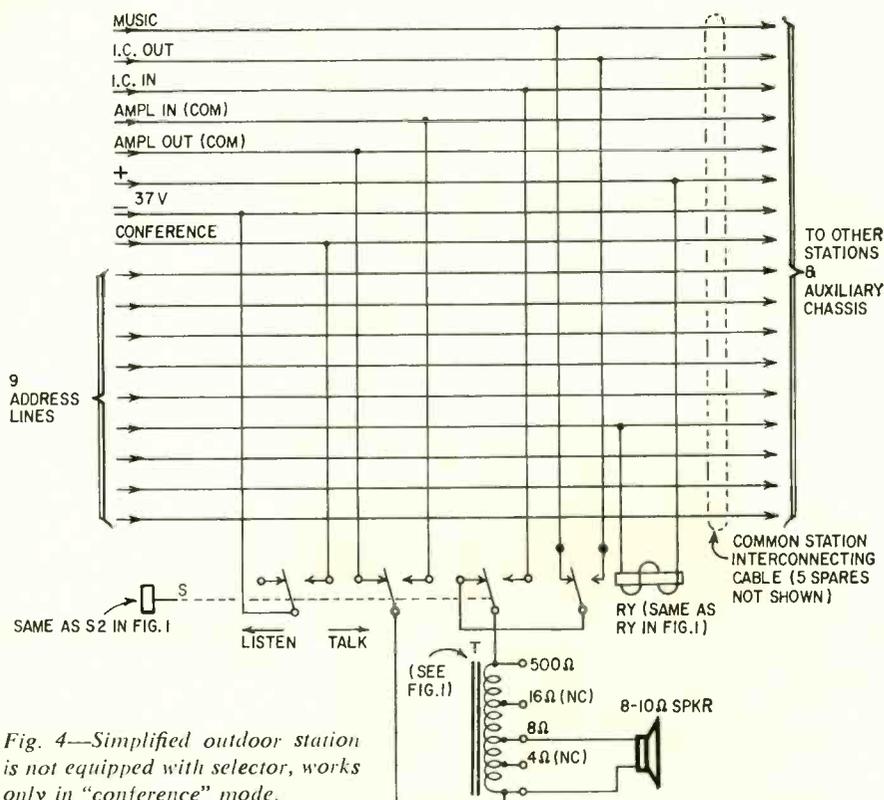


Fig. 4—Simplified outdoor station is not equipped with selector, works only in "conference" mode.

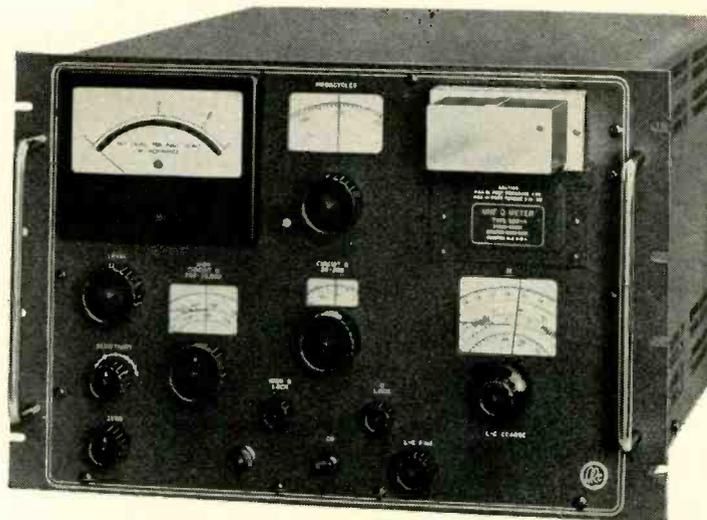

Boonton Q meter type 190-A



Boonton uhf Q meter, model 280-A

ONE OF THE MOST VERSATILE INSTRUMENTS YOU'LL EVER USE,  
THIS ONE BELONGS BY THE SIDE OF YOUR VTVM

# USING THE Q METER

By DONALD E. BOWEN

ALMOST EVERYONE KNOWS THAT THE Q, or figure of merit, of a tank circuit determines its selectivity. But that isn't the whole story. Many circuit parameters are determined by the tank-circuit Q: an oscillator's stability, the efficiency of a transmitter final, or the gain of an rf amplifier. And many circuit parameters determine the operating Q of a tank circuit: stray capacitance, connecting leads, amount of dc, and vacuum-tube plate resistance, to name only a few.

But the chore of determining the Q of a tank circuit accurately is just a little too much for the trusty grid dipper or the workbench signal generator. How, then, is Q measured?

Just as there are voltmeters to measure voltage and ohmmeters to measure resistance, there are Q meters to measure Q. And the very nature of the Q meter makes it one of the most versatile and useful rf test instruments in the workshop or lab. The meter is not restricted to rf, but works well into the audio range. You can use it to test audio chokes, transformers and video peaking coils. A Q meter can measure circuit Q, inductance and capacitance; or determine power factor, phase angle, losses in dielectric material, rf resistance, distributed capacitance, mutual conductance, and coefficient of coupling. The list goes on and on. Not only that, but it can

be used as a signal generator, an absorption wavemeter or a relative field-strength indicator.

## How it works

In understanding how the Q meter works, you may find Table 1 a help. You've probably seen these relationships before—they're generally known, and you'll find more complete explanations

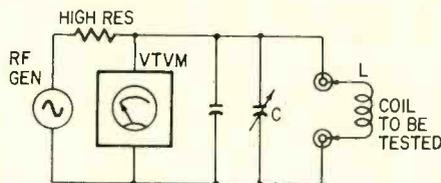


Fig. 1—"Susceptance-variation" method of measuring Q. Not the most accurate, it is seldom used commercially.

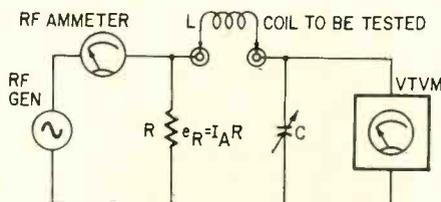



Fig. 2—"Circuit-magnification" Q-measuring technique. This is the foundation for most commercial systems.

in most electronics texts. Keeping them in mind it will be easier to see how the Q meter works.


The Q meter is made up of a calibrated oscillator, an injection circuit, a test mount for the circuit being tested and a high-impedance metering circuit. Two basic arrangements are commonly used for connecting the test circuit together. The less common of the two, shown in Fig. 1, is the *susceptance-variation* method. Fig. 2 shows the more common method: the *circuit-magnification* method.

The circuit of Fig. 1 depends on the *change in impedance* of a parallel-resonant circuit as it is tuned away from resonance. Test circuit LC is loosely coupled to the generator. Either the *delta-C* or *delta-F* method (delta, the Greek letter  $\Delta$ , is short for "change in . . .") of measuring Q can be used, depending on which is easier. Usually the delta-C method is used, the dial on capacitor C being set up so that the Q may be read direct.

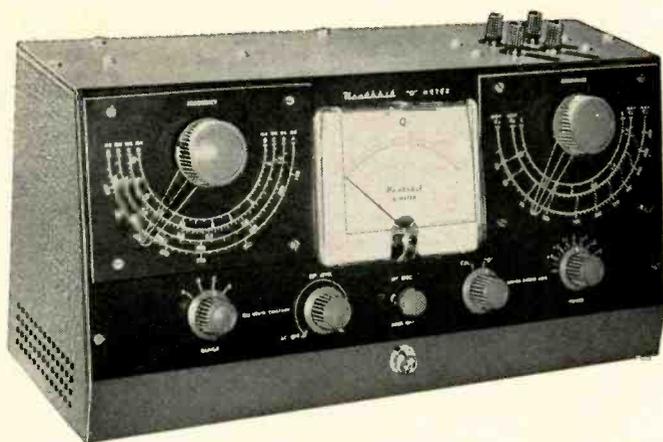In the circuit-magnification arrangement (Fig. 2), the rf oscillator applies a signal across the terminals of series-resonant circuit LC. The injection voltage is determined by measuring the rf current through resistor R. This resistor is small compared to the resistance of the circuit being tested (usually about



Heath model QM-1 Q meter

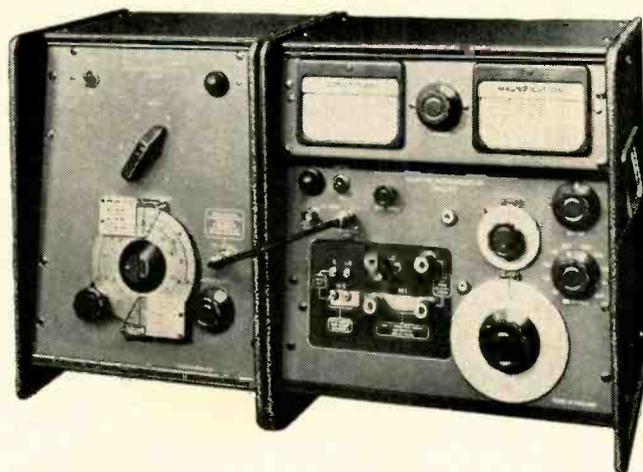

Marconi TF1245 Q meter connected to separate oscillator (left).

.05 ohm). The current is measured by the thermocouple ammeter. Variable capacitor C is located in the Q meter, and coil L is connected to jacks on the meter.

When the series circuit is tuned to resonance (or when the generator frequency is tuned to the resonant frequency of the LC circuit), the impedance between input and ground is low and a large current flows in the series-resonant circuit. Because of the high current, large out-of-phase voltages are generated in C and L. The voltage across C is measured by a high-impedance vtvm.

According to one of the basic Q relationships (Table 1),  $Q = \frac{E_x}{e_r}$ . Thus, the voltage across C (measured by the vtvm) divided by the voltage across R (a known value) is the circuit Q, which may be read directly from the vtvm (calibrated in Q units).

A variation of the basic circuit-magnification method is shown in Fig. 3. Notice that no ammeter is used. The signal generator looks like a constant-current source. The output voltage is

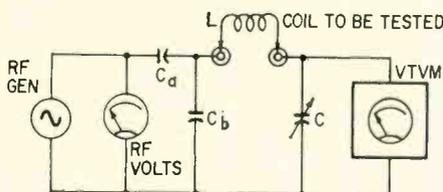


Fig. 3—A variation of the magnification method. This is the actual basic circuit of several Q meters on the market.

monitored and is held constant. It is applied to a small series capacitor ( $C_a$ ), connected to injection capacitor  $C_b$ . The value of  $C_b$  is very large compared to resonant-circuit capacitor C, so that the current is constant for practical cases.

Except for the use of the voltmeter-voltage-divider arrangement, this circuit is the same as that described in the previous paragraphs.

In vhf and uhf instruments, inductances are often used instead of capacitors  $C_a$  and  $C_b$ ,  $L_a$  being a large inductance and  $L_b$  being an extremely small one.

#### Commercial Q meters

Fig. 4 is a schematic of the Heathkit Q meter, model QM-1. The circuitry is typical. The 12AT7 is a variable-frequency rf oscillator with a cathode-follower output. The basic meter movement and the crystal diode monitor the output voltage. The rf signal is coupled to the test circuit (450-pf capacitor, 7-pf vernier and test jacks) by a 7-35-pf trimmer and a special .005- $\mu$ f injection capacitor. The vtvm uses a 12AU7, a 6AL5 and the basic meter movement. Power supply is included, so that the unit is self-contained.

In the photograph of the Heathkit unit, note that capacitance and inductance scales are included on the large dial on the right so that it is possible to read Q, capacitance and inductance values.

In addition to these common features, the Boonton instruments pictured can measure extremely low Q values, with meters designed to eliminate viewing parallax, thus allowing extremely accurate readings. One of the Boonton instruments, the 280-A, is designed especially for uhf. It has the additional feature of being able to measure components in-circuit and can measure the extremely high Q's of resonant cavities.

Additional flexibility has been incorporated in the Marconi TF-1245. Here, the Q meter contains no internal oscillator. Any oscillator capable of driving the unit may be used. The photograph shows the TF-1245 connected to a Marconi TF-1247 utility oscillator.

The Q meter (like any electronic instrument) can be only as good as its

TABLE 1. BASIC Q RELATIONSHIPS

$$Q = \frac{X_L}{R_s} = \frac{X_o}{R_s}$$

where  $R_s$  is the equivalent series resistance,  $X_L$  is the inductive reactance,  $X_o$  is the capacitive reactance.

$$Q = \frac{R_p}{X_L} = \frac{R_p}{X_o}$$

where  $R_p$  is the equivalent parallel resistance.

$$Q = \frac{f_o}{f_2 - f_1} = \frac{f_o}{\Delta f}$$

where  $f_o$  is the resonant frequency and  $f_1$  and  $f_2$  are the half-power points on the resonant curve.

$$Q = \frac{E_x}{e_r}$$

where  $e_r$  is the in-phase voltage and  $E_x$  is the reactive voltage across L or C.

$$Q = \tan \phi = \frac{1}{\cot \phi}$$

where  $\phi$  is the phase angle.

$$Q = \frac{2C_o}{C_2 - C_1} = \frac{2C_o}{\Delta C}$$

where  $\Delta C$  is the change in capacitance necessary to tune from the lower half-power point through resonance to the upper half-power point.

Note: Some of these relationships are approximate, but accurate within 1% for Q values above 7.

operator. It is a simple device, but you must be careful to make correct adjustments and to take accurate readings. Let's go over a few measurements that show how versatile a Q meter can be. Note that, although control names and markings vary with particular makes and models, general terms are used in the instructions below. And remember, there is no substitute for the instruction manual supplied with the equipment.

### Measurements on coils

**Measuring Q.** The fundamental and obvious use of the Q meter is to measure Q. The most common method is direct-reading, which works like this:

1. Connect the coil to the coil terminals.
  2. Adjust the Q-meter capacitance to the desired value (depending on the frequency at which you want to examine the Q).
  3. Set the Q-meter oscillator to the proper range.
  4. Set the "times Q" reading to some convenient whole-number value.
  5. Tune the Q-meter oscillator until you hit resonance—maximum reading on the Q vtm.
  6. Carefully readjust all settings, taking care to balance the vtm.
  7. Read Q by multiplying the "times Q" setting by the Q vtm reading.
- Check reading by measuring the change of capacitance necessary to bring

the Q vtm reading from 0.707 of maximum *below* resonance to 0.707 of maximum *above* resonance (these are the upper and lower half-power points of the resonance curve.) These values are substituted in the formula  $Q = \frac{2C_0}{\Delta C}$ . Values of C must be taken very carefully for this measurement.

**Inductance.** Although most Q meters contain a calibrated inductance scale, it's often useful to understand the method used to determine the inductance.

1. Resonate the coil at the desired frequency.
2. Read the frequency.
3. Read the value of capacitance that resonates the coil.
4. Substitute the values in the formula  $L = \frac{1}{\omega^2 C}$ , where  $\omega = 2\pi f$ .

If the distributed capacitance of the coil is important, the term C becomes the sum of the Q-meter capacitance reading and the distributed capacitance. You can determine the distributed capacitance this way:

1. With the coil connected to the Q meter, adjust the Q-meter capacitor to some low value. Call that value  $C_2$ .
2. Resonate the tuned circuit. Call this frequency  $f_2$ .
3. Tune the Q-meter generator to  $f_1 = \frac{1}{2}f_2$ .

4. Reresonate the tuned circuit, calling the new value of capacitance  $C_1$ .

5. Substitute those values in the formula  $C_D = \frac{C_1 - 4C_2}{3}$ .

**Mutual inductance and coupling coefficient.** These measurements are related and are conveniently made together. They should be made at or near the same frequency.

1. Measure the inductance of each of the coils separately, calling the two values  $L_1$  and  $L_2$ .
2. Measure the total inductance  $L_a$  with the coils in series aiding.
3. Measure the total inductance  $L_b$  with the coils series opposing.


4. Substitute in the formulas  $M = \frac{L_a - L_b}{4}$  for mutual inductance and  $K = \frac{L_a - L_b}{4\sqrt{L_1 L_2}} = \frac{M}{\sqrt{L_1 L_2}}$  for coefficient of coupling.

These inductance measurements represent a few of the coil tests you can make with a Q meter. There are many more. For example, the gain of coupled circuits can be measured and large inductors (even in the audio range) can be measured, to mention only two other applications.

### Capacitance measurements

Two types of capacitance measurements can be made on the Q meter: **series** and **parallel**. Series measurements are used to determine values of capaci-

Fig. 4—Circuit of the Heath QM-1, a relatively typical Q meter.

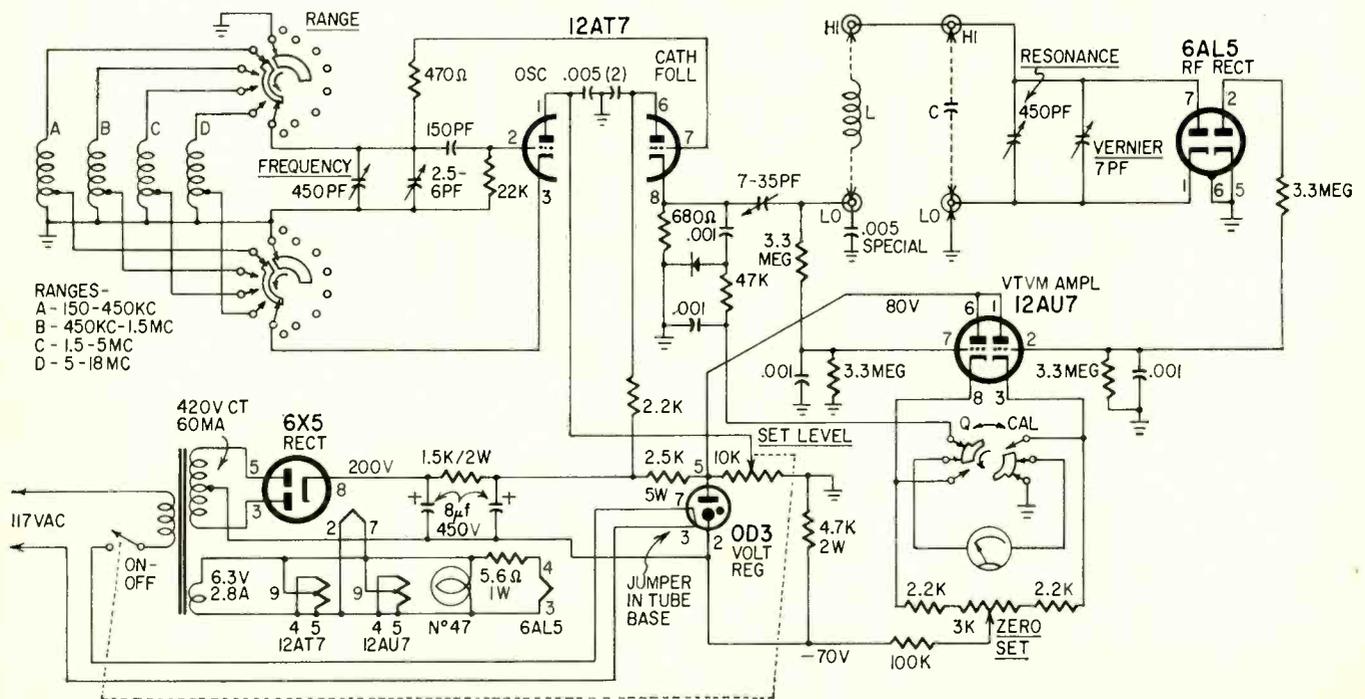

tance greater than the value of the Q meter's variable capacitor. Parallel measurements are used to measure small capacitors. This is the procedure for parallel measurements:

1. Connect a coil across the coil terminals on the Q meter.
2. Connect the unknown capacitor across the capacitor terminals of the Q meter.
3. Adjust the Q meter capacitor to some low value,  $C_1$ .
4. Tune the Q-meter generator to resonate the circuit. (Do this at the lowest possible frequency, to minimize the effect of lead inductance of the unknown capacitor.)
5. Remove the unknown capacitor.
6. Tune the Q-meter capacitor until the circuit is again resonant. The new value of capacitance is  $C_2$ .
7. Determine the value of the unknown capacitor:

$$C_x = C_2 - C_1.$$

#### Series capacitance measurements.

1. Connect the unknown capacitor between the low side of a coil and the low terminal of the Q meter.
2. Adjust the Q-meter capacitor to some high value  $C_2$ .
3. Tune the Q-meter generator to resonate the circuit (again at the lowest possible frequency to minimize the effect of lead inductance).
4. Short out the unknown capacitor with a short piece of heavy wire.
5. Reresonate the circuit by tuning the Q-meter capacitor to a new value,  $C_1$ .
6. Determine the value of the unknown capacitor by the formula

$$C_x = \frac{C_1 C_2}{C_2 - C_1}$$

Besides these fundamental capacitance measurements, it is possible, among other things, to determine phase shift of capacitors and to evaluate dielectric materials.

#### Other uses

The Q-measuring circuit of a Q meter contains an rf vtvm, a variable capacitor and terminals for connecting a coil to resonate with the variable capacitor. If an unshielded coil is connected to the terminals with the internal signal generator disabled, and the Q meter is placed near an active rf circuit,

its circuit may be tuned to the frequency radiated by the rf circuit. Resonance is indicated by a deflection of the Q-meter vtvm. You can then measure the frequency of the active rf circuit by disabling it and adjusting the Q-meter rf generator to the meter's tank-circuit resonance point. Read the resonant frequency off the generator frequency dial.

Q meters are being used to measure the parameters of semiconductor devices, characteristic impedance, velocity factor and loss in transmission lines.

Many Q-meter accessories are available from manufacturers; you can make others. Test coils and calibrating devices are among the most common accessories. Special test fixtures for measuring dielectric materials can extend the usefulness of the meter. Optical magnifiers, to permit more accurate scale readings, can be built or purchased.

#### A few precautions

The Q meter, in general, operates at rf. For that reason, components to be tested must be connected to the Q meter with short leads to insure maximum accuracy. Lead length becomes increasingly important at the higher frequencies.

Unshielded coils being measured on a Q meter are subject to stray rf fields, coupling to nearby resonant objects (even power cords or light bulbs!) and variations due to the proximity of your hands. If you can't eliminate these effects by locating the test circuits properly, use a large, grounded shield over the coil being tested.

All quality Q meters have internally regulated power supplies. In extreme cases it may be necessary to use line-voltage regulating transformers to keep the supply voltage within allowable limits. Extreme line-voltage variations may have a pronounced effect on the stability of the instrument.

Watch your grounds—make them to a common point. Keep contact resistance at the test-coil terminals as low as possible. Make your measurements in an area where stray rf signals are at a minimum, and where coils under test are not coupled to nearby objects. Keep your hands away from the coil under test. Check instrument setup (meter balance, etc.) periodically.


This fabulously versatile instrument can be bought as a kit or ready-made. Prices range from less than \$60 to several hundred. Occasionally, a good Q meter hits the surplus market—for instance, when a manufacturer goes out of business or updates his equipment. Then you can buy one for a small fraction of its original price. Any way you do it, it's an instrument worth having!

END

#### References

*The BRC Notebook*. Boonton Radio Corp., Boonton, N. J.: No. 1, Spring 1954; No. 4, Winter 1955; No. 8, Winter 1956; No. 13, Spring 1957; No. 16, Winter 1958; No. 27, Winter 1961; No. 28, Spring 1961.
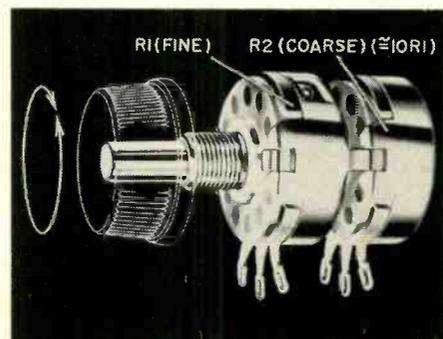
## Potentiometer Features Built-in Vernier




"Built-in backlash" is the term used to describe the working of this ingenious new variable resistor developed by the Allen-Bradley Co. Looking just like any ordinary ganged dual potentiometer, the Type JJV incorporates a deliberately "sloppy" coupling between front and rear sections to permit fine, high-resolution adjustments for zeroing meters, nulling bridges, or any other application where critical touch-ups of resistance are necessary.

The front section (R1) is normally made with the same taper as the rear section (R2), but with about  $\frac{1}{10}$  the resistance. As you begin to rotate the knob from its extreme counterclockwise stop, only R1 moves. About  $40^\circ$  from the stop, you "pick up" the R2, which until then has been idling in its notched coupling device. The shaft attached to R1 then drags the R2 wiper along, and you continue turning until you reach a meter reading (or scope indication, etc.) just beyond the value you want.

Overshooting the mark this way makes it necessary to turn the shaft back the opposite way to come down to the desired value. As you do so, the drive releases the coarser rear section, R2, and only the front section R1 is in the circuit. Because (in a rheostat-type connection) it is in series with R2 but only a small fraction of the value of R2, it can "trim down" the value very neatly. If you start from the clockwise stop, the coupling works the same way, but reversed. In other words, it works equally well in either direction.

If you continue turning after you reach the desired value, eventually you will again pick up the coarse section and ultimately return it to the end stop.

END

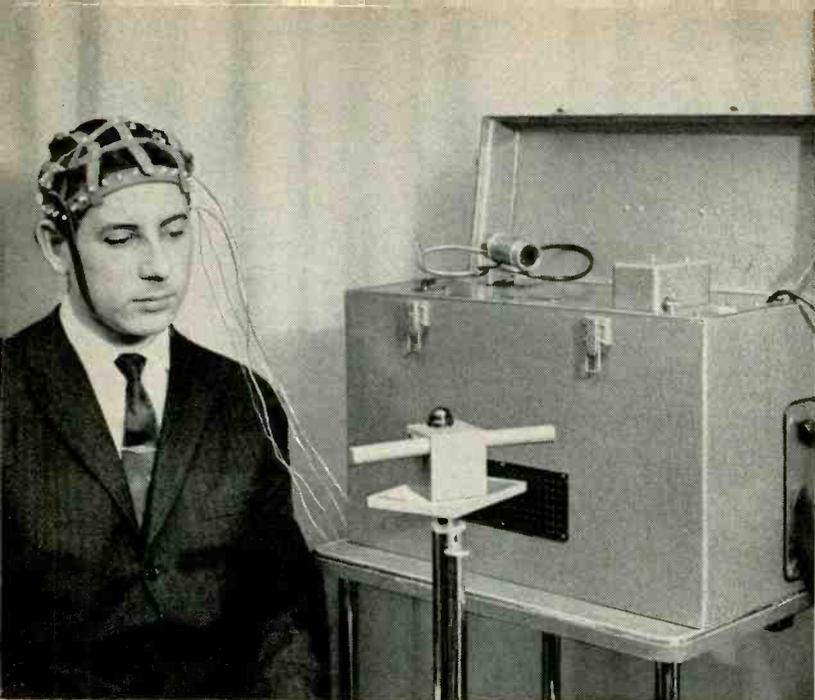

The experimental setup used by M. Dusailly.

# Psycho- Command and Psycho- Reaction

By J. F. DUSAILLY\*

IT IS POSSIBLE, BY CONCENTRATING  
THE WILL, TO ACTUATE  
A REMOTE MECHANISM

CEREBRAL ELECTRICITY WAS DISCOVERED by an English physiologist, Caton, in 1875: electrodes inserted into the brain of a trepanned ape recorded currents readable on a galvanometer. In 1929, after extensive research, Hans Berger demonstrated that the brain is a seat of electric oscillations and that mental activity modifies their amplitude and frequency.

The waves produced by the brain of a subject in physical and mental repose are called *alpha waves*. Their length is enormous (between 23,000 and 43,000 kilometers). Their frequencies vary from 7 to 13 cycles, and their amplitude from 5 to 50 microvolts (Fig. 1). Other waves (beta, delta, theta, gamma) have different amplitudes and frequencies.

The *electroencephalograph* supplies curves that represent the resultant of these brain waves. To analyze these curves and separate them into their components is an extremely delicate and to some extent subjective operation. Attempts have been made to produce results by mathematical (Fourier analysis) or physical (electric filter) methods. These are based on the hypothesis that the brain waves to be separated are originally perfectly sinusoidal. This, however, has not yet been demonstrated in practice.

The combination of a cerebral elec-

\*Chief, Information Center on Electronic Applications, Lampe Mazda, Compagnie des Lampes, Paris, France.

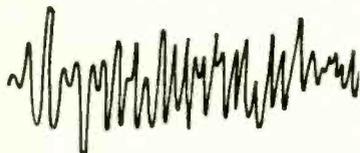


Fig. 1—Appearance of normal alpha-wave rhythm.

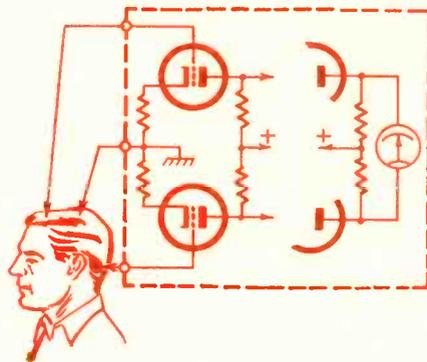


Fig. 2—How the electrodes are placed to amplify brain waves.

trocartograph with an electronic computer promises great progress in this domain. Such an instrument has been placed in service in the hospital of Salpêtrière. It is designed to furnish an automatic representation of the space-time distribution of the brain's electric activity.

### How are brain waves obtained?

The pickup devices for brain waves are silver electrodes applied to the scalp. It is not necessary to remove the hair. A pad, soaked with salt water and held in place with a rubber cap, makes a reasonably good contact. The placement of the electrodes and the excellence of the contact are important. The contact can be improved by using a conducting paste applied by massaging lightly into the skin in the area where the electrode is to be applied.

The voltages are weak, in the order of some dozens of microvolts. Unless a Faraday cage is used, it is necessary to shield the subject from surrounding fields—50 cycles created by the electric light lines [these experiments were made in France], atmospheric and industrial

electricity, high-frequency transmitters, etc.

The 50-cycle field is particularly annoying, because it can produce signals of the same order as those from the brain. To guard against the influence of everything that doesn't come from cerebral activity, a *differential amplifier* is used. It is sensitive to differences of potential between two neighboring points of the skull, but not sensitive to voltage variations common to the two points.

These voltages are taken between a neutral electrode, usually placed at the top of the skull, and two other electrodes, which may be variously situated (Fig. 2). The neutral electrode is connected to the ground (chassis) of the amplifier and to an excellent external ground. The amplifier must be excellently shielded.

In spite of all precautions, some stray signals do superimpose themselves on the alpha waves. These exist at various frequencies: the slowest due to movements of the head or eye, to unbalance in the connecting wires of the electrodes, and to some extent to voltages caused by cardiac activity. The highest frequencies can be produced by electromyograms (signals due to muscle movement.) [See "Electromyography" by Dr. Bernard Post, RADIO-ELECTRONICS, issue of November 1960.]

To eliminate the lowest-frequency

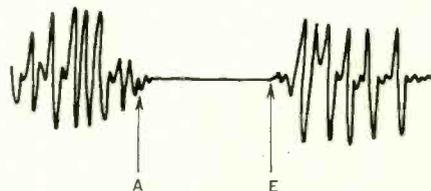


Fig. 3—Brain activity (between A and E) cuts down the size of the alpha waves.

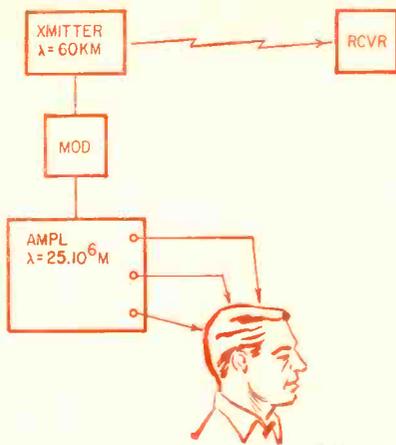


Fig. 4—Brain waves are amplified and used to modulate a transmitter which actuates a relay at the receiver.

undesirables, it is necessary to use circuits with a suitable time constant. The most practical is to utilize those employed in electroencephalography — 0.1, 0.3 and 0.7 second.

The amplitude of the alpha wave is maximum—in the order of 30 to 50  $\mu V$ —during physical and mental repose. If the subject concentrates, the amplitude of the alpha waves diminishes due to the action of the brain (Fig. 3). Our experiments in psycho-control use this variation of the brain waves.

#### Principles of psycho-control

Until now, waves emitted by the brain have produced no outside effect other than recordings on an electroencephalograph. We thought it might be possible to utilize these waves to control a mechanism (though the alpha waves are very weak—in the order of picowatts—and cannot produce any direct mechanical action at a distance).

To actuate a mechanism, the brain-wave voltages would have to be amplified considerably, then used to operate a sensitive relay to finally produce the desired reaction.

We arrive, therefore, at the general scheme of Fig. 4.

The waves are picked up by the electrodes on the head of the subject and amplified to the limit permitted by present techniques. The amplitude of these waves varies when the subject passes from mental repose to the cerebral activity required by the concentration of his will. These variations modulate very long electromagnetic waves.<sup>1</sup> These waves are under the control of the subject's will and produce the desired action. In our experiments, we were able to light or extinguish a small lamp at a distance, but of course it would be equally easy to control any other type of mechanism.

Let us make it completely clear that psycho-command is based on the *electromagnetic* transmission of cerebral activ-

<sup>1</sup>The long wavelength (60 km) was chosen to avoid all risk of interference from radio waves or electric fields.

ity and must not be confused with what one habitually refers to as transmission of thought (telepathy). Nevertheless, this experiment has created great interest among students of metaphysics. They feel that this is the first step in reducing the gap between pure science and metaphysical research.

#### Psychological reaction

Our experiments are especially delicate because they depend to some extent on the psychological state of the subject. One of the conditions for success is that he be a party to the experiment and be persuaded that it is likely to succeed. If he has any doubts, he will probably not be able to concentrate his will sufficiently.

A number of experiments over several months have already made it possible to come up with several interesting conclusions. Not only is there the possible action of the brain on a mechanism, but also a reaction of the mechanism on the brain—feedback.

As long as we are dealing with an "all or nothing" reaction (light the lamp or extinguish it), naturally the critical threshold of sensitivity depends to some extent on intangible conditions. This creates a certain anxiety in the subject—he fears he may not be able to light the lamp. If, on concentrating his will, he sees the lamp shine for only an instant, he is reassured by the success of the experiment and finds it very easy to keep the lamp lit. There we have a general psychological feedback reinforcing the input signal (the order given to the subject to light the lamp).

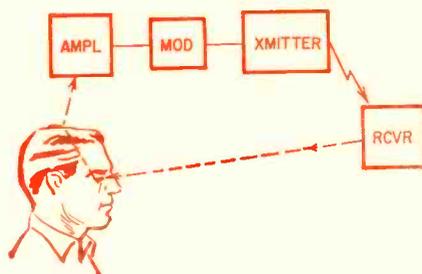


Fig. 5—The brain-amplifier-transmitter-receiver-brain cycle of the action and feedback.

If, for any reason, the subject is *not* able to light the lamp with his will, the psychological feedback may actually make it impossible for him to concentrate sufficiently. The lamp, then, cannot be lit. This reaction is strikingly similar to that of electronic amplifiers.

Fig. 5 shows the analogy between the man-mechanism complex and a purely mechanical servomechanism.

This discovery of psychological reaction (feedback) will almost certainly assist progress in psychological studies.

END

## AC-DC Radio Voltages: Pretty Constant From Set to Set

THERE ARE AT LEAST SEVERAL TRILLION AC-DC radios in this country (or so it seems!) and vast numbers of them need servicing. One encouraging observation is that these sets are pretty well standardized and their voltages, too, fall into general patterns. After considerable experimenting and study, I've found that voltage facts applicable to most AC-DC receivers can be summarized as:

With no signal, the rf grid of the converter tube, the grid of the i.f. amplifier tube, and the diode plates (when they are used as such; one is sometimes connected in another way) should show about -1 volt or less with respect to B-minus. A signal—at least, a strong one—should increase this voltage.

The oscillator grid of the converter tube usually reads between -6.5 and -12 volts.

The grid of the first audio tube should show about -1 volt.

These points operate at 0 volts: suppressor grids, the audio output tube grid, the cathode of the converter tube and the cathode of the first audio tube. In many sets, especially older ones, the cathode of the i.f. amplifier operates at 0 volts but it will show a slight positive voltage if there is a cathode resistor.

Positive voltages should always be found at these points: The plates and screen grids of the converter and i.f. amplifier tubes—usually between 80 and 100; the plate of the first audio tube—usually between 35 and 60; the audio output cathode—usually between 5 and 7; the screen grid of the audio output tube—usually between 80 and 100; the audio output—usually between 95 and 120; the rectifier cathode—usually between 110 and 125.

A person familiar with the layout of a radio can take all these measurements in a short time. With the voltmeter set for 150 volts, positive, check off the plates and screen grids and the rectifier cathode. That takes care of the rectifier. Switch to 50 (or 15) volts and catch the audio output tube grid and cathode. With the same setting, you can check the other cathodes and the suppressor grid or grids. Switch polarity and check the converter grids, (rf and oscillator) the i.f. amplifier grid, the diode plates and the grid of the first audio tube.

Use either a vtvm or a 20,000-ohms-per-volt tester. In either case, expect a variation of 10% from the accepted voltage standard.—Philip Lacy

# ADD A SUPER-SELECTIVE MECHANICAL FILTER

Like to pick up Rome on 845 kc, between US broadcasters on 840 and 850? If so, read on!

By R. E. BERGE

## COVER STORY



HAVE YOU EVER TUNED IN A WEAK DX station on your broadcast or short-wave receiver, only to have a powerful adjacent-channel station surge in and blot it out just as the announcer began to speak? Even reasonably good communications receivers have trouble on short-wave bands today. With so many new high-power stations the separation between broadcast stations is only 5 kc (sometimes even less) compared with the 10-kc separation on the medium-wave broadcast band.

Adding a Q-multiplier or a crystal filter will improve selectivity greatly, but these usually only narrow the peak of

the i.f. response curve, leaving the sides as they were (curves A and B in Fig. 1). They are most useful for CW reception.

A much greater improvement is possible by replacing the 455-kc input i.f. transformer with a *mechanical filter*. Unlike conventional couplings made up of L and C elements, these filters closely approximate the flat-topped, steep-skirted ideal bandpass response (curve C in Fig. 1).

You may be taken aback at the idea of modifying your receiver to the tune of \$30 to \$50. But if you can make an \$89 receiver as selective as one in the \$300 class, it's well worth while.

Mechanical filters are made of a series of small resonating nickel-alloy discs of extremely high Q—8,000 to 12,000. A complete filter consists of a magnetostrictive transducer (to convert electrical oscillations into mechanical oscillations and back), the mechanically resonant discs and disc coupling rods.

A signal sent through the transducer coil creates a magnetostrictive effect in its core. The core, attached to the resonant discs, alternately elongates and shortens, causing the discs to vibrate at their resonant frequency. Frequency of vibration is determined by the physical size of the discs and coupling rods. A second transducer at the far end of the assembly converts the mechanical movement back to electrical variations (Fig. 2-a). The effect is that of an elaborate multisection L-C filter (Fig. 2-b).

Wiring one of these filters into a typical receiver involves major surgery even though the filter itself is only about

the size of a K-Tran i.f. transformer. So I looked into the idea of an adapter that could be plugged into the first i.f. tube socket, without any wiring change in the receiver.

An experimental adapter was built using a battery-powered transistor to compensate for the 10-db loss of the mechanical filter. It worked so well with a Hammarlund HQ-100 that this article is the result.

Connecting the adapter is simple. Remove the first i.f. tube in the receiver and insert it in the socket atop the adapter. Then plug the adapter into the vacant tube socket in the receiver. This inserts the adapter between the first i.f. transformer and the first i.f. tube (at point X in Fig. 3).

### Circuit

The output of the mechanical filter is series-tuned and coupled to the base of the standard transistor i.f. amplifier. The only trick to the amplifier is the coupling of the grid to the i.f. tube. Here a vacuum-tube type i.f. transformer might be used with reasonably good results if space is available. The transistor amplifier in the model unit uses a cup-core coil (L) in the collector circuit.

The cup-core is a miniature Ferroxcube type 3C with a single-section bobbin. The winding consists of 100 turns of No. 36 enamel-coated magnet wire tapped at 40 turns from the bottom end. The parts list with Fig. 4 gives detailed parts information. A toroid coil of similar design would also be satisfactory. The inherent self-shielding characteristic of the ferrite cup-core and of the toroid

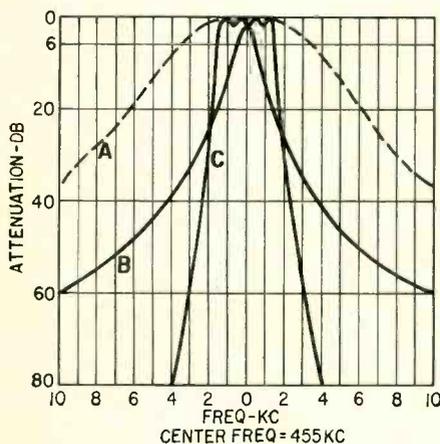


Fig. 1—Contrast between normal AM broadcast receiver i.f. curve (A), sharper, steeper communications receiver curve (B) which attenuates audio sidebands severely, and unique mechanical filter curve (C), with its flat top and extremely steep sides.

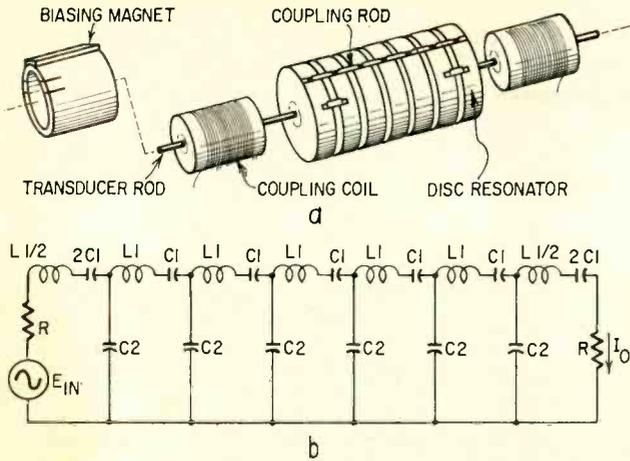


Fig. 2-a—Exploded view of Collins mechanical filter. Magnetostrictive drive from one coil is transmitted through discs via transducer and coupling rods. Coil at other end reconverts mechanical energy to electrical energy and sends it on to next amplifier stage. In (b), electrical analog of mechanical filter.

make them most satisfactory for this circuit.

The crux of the whole story is that the path of least resistance to the i.f. signal *must* be from the input pin on the adapter plug, through the mechanical filter, through the transistor amplifier, through the vacuum tube in the adapter socket, and back to the output pin on the adapter plug. Any stray coupling by other routes will reduce the filter's effectiveness. The mechanical layout may be similar to the one shown or you may arrange it according to your tastes, as long as you provide proper shielding to prevent leakage or feedback around the mechanical filter or transistor amplifier.

The secondary of the first i.f. transformer in your receiver is designed to have a high impedance so that it will match the high impedance of the following tube grid circuit. This makes it ideal

for coupling to a mechanical filter, which, when parallel-tuned, wants to "see" approximately 100,000 ohms. Normally a 130-pf capacitor will tune the filter, but peaking the tuning capacitance

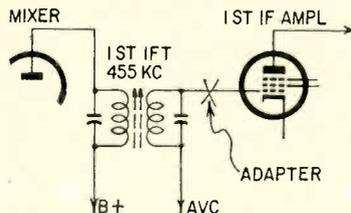


Fig. 3—Where the adapter goes, electrically.

for maximum signal at 455 kc will usually yield better performance.

The mechanical filter can be made to match a low-impedance load by series-tuning the output with about the same-value capacitor as that used for parallel

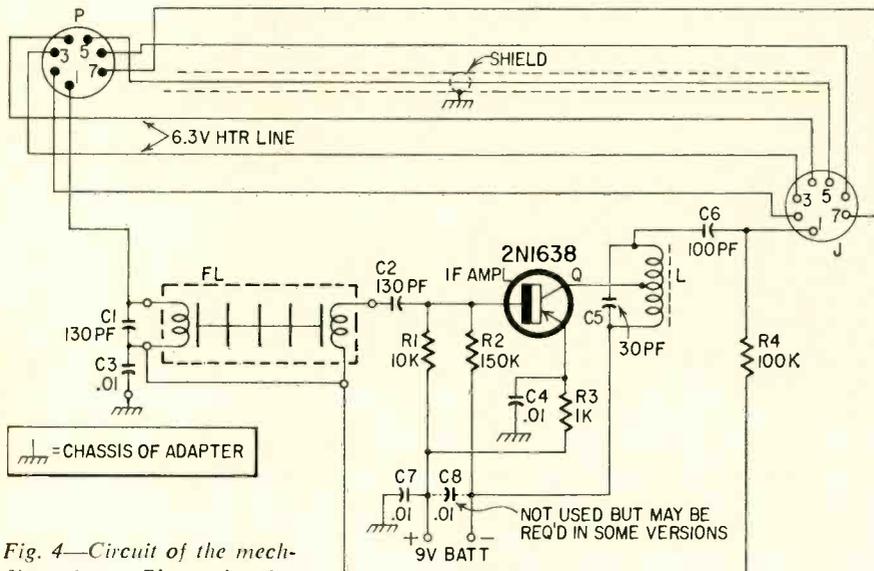


Fig. 4—Circuit of the mech-filter adapter. Plug and socket wiring shown is for 6BA6 and similar 7-in. miniature tubes.

- C1, C2—130 pf
- C3, C4, C7, C8—.01  $\mu$ f, 200 volts (Aerovox P83Z or equivalent)
- C5—30 pf mica or ceramic
- C6—100 pf
- FL—Collins mechanical filter (type F455Y-31 or F455FB-21—see text)
- J—tube socket to fit receiver's existing first i.f. tube
- L—cup-core coil: 100 turns No. 36 enameled, tapped 40 turns from low end. Core is Ferroxcube 332 P 133 B4-3C (2 pcs. required, 40¢ each). Bobbin, Ferroxcube 332 F 175 (1 required, 6¢ each). Order from

- Ferroxcube Corp. of America, Saugerties, N.Y.
- P—plug to fit existing first i.f. tube socket in receiver (Vector P7, P7A or equivalent)
- Q—2N1638 (RCA)
- R1—10,000 ohms
- R2—150,000 ohms
- R3—1,000 ohms
- R4—100,000 ohms
- All resistors 1/4 watt, 10% tolerance
- BATT—9-volt battery (RCA 216 or equivalent)
- Case—see text, Fig. 5 and photograph

The author sent us one of his adapters to try with several different kinds of receivers. First it was plugged into a National NC-88 all-wave receiver. It worked very well. Next we tried it on an old Fisher 50-R-2 FM-AM broadcast tuner, and had quite a surprise. We found signal-free spots between regular AM broadcast channels 10 kc apart. As we tuned, we found a station about midway between 1460 and 1470 kc. We knew it couldn't be a US or Canadian station, since our frequency allocations are at even 10-kc multiples.

When the music stopped, the announcer began speaking—in French. It turned out to be Radio Monte Carlo in Monaco! Our first European station on the AM broadcast band! Checking in the World Radio TV Handbook, we found that Monte Carlo is on 1466 kc, with 400 kw power.

Then we began hunting between US channels in earnest. A few evenings of listening in December (1963)—usually between 5 and 8 pm and occasionally from 11:30 pm to 1:30 am EST—brought positive identification of London on 1214, 1295 and 647 kc, Rome on 845 and Lisbon on 755 kc.

Others heard but not positively identified were BBC stations on 908, 1088 and 1457 kc, Voice of America in Munich on 1195, French stations at Lille on 1376, Bordeaux on 1205, Toulouse on 944 and Nancy on 836 kc. Note that all these are between normal North American channels. Without the adapter, the weak European stations were buried by the strong US and Canadian stations a few kilocycles away. The receiving location was suburban New Jersey, about 25 miles from Times Square.

The adapter's 3- or 4-kc selectivity proved its worth on the short-wave bands also, with the NC-88. The receiving location was only 7 miles from the powerful Voice of America transmitters at Bound Brook, N.J., which normally blanket 15 to 20 kc on either side of their frequency on ordinary receivers. With the adapter, it was possible to pick out weak stations only 10 kc away. With just normally-strong stations, it was no trick to pick out weak ones only 5 kc away. Background noise and heterodyne squeals were greatly reduced also, because of the narrow bandwidth.

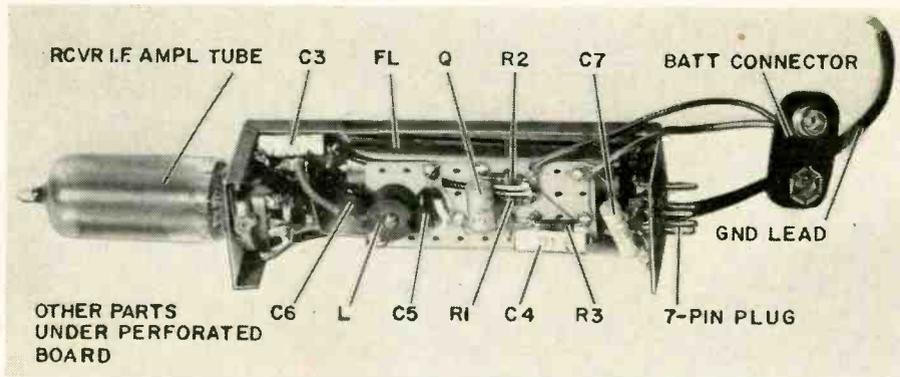


Fig. 5—Internal construction of adapter. Modifications are possible, but follow suggestions in text.

tuning. This capacitor also should be tuned for maximum signal at 455-kc. Series-tuned, the filter is a nearly ideal impedance match for the low-impedance transistor input.

Note that a dc path is provided in the adapter circuit to allow uninterrupted avc bias control on the grid of the i.f. tube. The lead used to connect the plate terminal of the socket to the same terminal on the plug should be shielded, with the shield tied to the adapter chassis. Use a twisted pair for the heater connections. All interconnecting leads between the plug and the socket are run in a shielded duct alongside the filter and amplifier sections of the adapter. An additional bypass capacitor may be necessary on the socket end of the screen interconnecting wire.

All bypass grounds are to the adapter chassis. The chassis, in turn, is grounded to the receiver chassis through a wire soldered to the adapter chassis. An alternate way is to connect the adapter chassis to the grounded heater lead. This won't work with a transformerless

(ac-dc) receiver, and, in any case, you'll always have to check to see which heater lead is grounded in case you use the adapter in other receivers.

A type F455Y-31 mechanical filter, available from the Components Div. of Collins Radio Co., Newport Beach, Calif., or from Collins distributors, for \$38 plus tax and postage, was used in the model adapter. The new plug-in type F455FB-21 (available only with 2.1-kc passband, and physically slightly larger) is also usable and can be bought direct from Collins or through distributors. Price postpaid from Newport Beach is \$26.50. All resistors are 1/4-watt size. Tuning capacitors are miniature Aerovox type P83Z.

#### Construction

The circuit of the adapter is shown in Fig. 4. Before building it, check your receiver to determine the tube in the first 455-kc i.f. stage. If it is a 6AU6, 6BA6 or 12BA6, a seven-pin plug and socket will be required in the adapter. (This is the type used on the unit shown.)

Two forms of the Collins magnetostrictive mechanical filter used in the adapter.



If it is a 6SK7, an octal plug and socket will be required. Measure the space available in your receiver to determine suitable outside dimensions for your plug-in unit.

Cut out and bend a piece of brass or copper sheet stock similar to the mounting bracket in Fig. 5. A socket and base plug similar to the type in your receiver's first i.f. stage are mounted in the bracket ends. The inner shield, also sheet copper or brass, is cut and mounted in such a position that it will isolate the mechanical filter and transistor amplifier circuit from the interconnecting wiring.

The unit shown in Fig. 5 and on the cover was designed to plug into the smallest practical space, such as the first i.f. stage of the HQ-100 receiver. The outside dimensions are 1 x 1 x 3 1/2 inches. In many cases, especially where the receiver uses octal tubes, more space is available. Small plug-in chassis with socket and plug attached, such as the ones manufactured by Vector Electronic Co., Glendale, Calif., are commercially available at most radio supply stores and may be a more convenient housing for the adapter. In all cases, the short lead from the grid pin of the plug to the parallel tuning capacitor on the mechanical filter input should be decoupled as much as possible from the other leads to the plug by a well located inner shield.

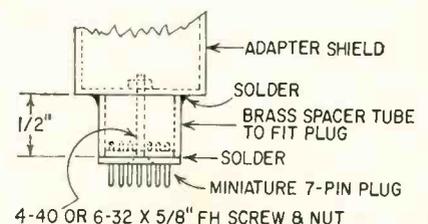


Fig. 6—Modification to bottom of adapter to make it fit tube sockets with integral shield bases. If tube was shielded, use shield-base socket for tube at top of adapter (J in Fig. 4)

Since the filter is 2 3/16 inches long plus terminals, the adapter is 3 1/2 inches long with maximum squeeze. If your receiver will not permit this additional height, the tube socket might be mounted at right angles to reduce effective height. Or build the unit with an extension cable between the adapter and the seven-pin (or octal) plug.

The extension will permit you to locate the adapter in a convenient spot in the receiver. The cable lengths should not exceed about 6 inches and the extension plate and grid leads must be shielded. Use low-capacitance cable, such as Belden 8421. Ground the shielding to the receiver and adapter chassis. Six inches of this cable has a capacitance of 8 to 10 pf. Since this is in parallel with C1 (130 pf) which tunes the input


of the mechanical filter, you may have to reduce C1's value by about 10 pf if you use the extension.

[If the i.f. amplifier tube in the set has a shield base, you may have to extend the adapter plug mounting as in Fig. 6. Also, you may have to shield the tube when you plug it into the filter adapter. However, shielding was not needed in any set in which we tested the adapter.—*Editor*]

Current drain of the amplifier is approximately 2 ma, so the life of a 9-volt transistor radio battery is very long. The battery should be mounted in a cool position, away from hot tubes or the power transformer. An on-off switch for the transistor amplifier may be mounted in a convenient spot, if desired.

After plugging the adapter into your receiver, be sure to peak up the tuning on the other i.f. stages to resonate exactly with the mechanical filter (its tuning is fixed at precisely 455 kc). If the i.f. in your receiver is more than 5 kc off, you may have to retrack the receiver's oscillator also, following the receiver service notes.

In an adapter of this type, it is not often possible to come up with perfect matching at all points in the circuit. This circuit is a practical happy medium with the transistor amplifier designed only to make up for the loss in the filter. You may be able to improve on it by winding a special transformer for coupling between the transistor output and grid output or in some other way. The price of a filter, about \$5 worth of other parts, and some of your own construction ingenuity will make that old receiver really sit up and talk. END

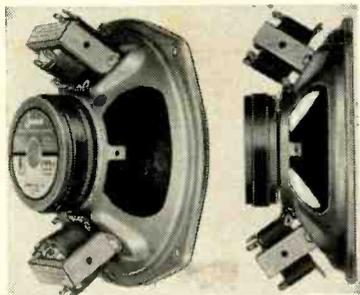

### "Dual Channel Access" Loudspeakers

Two output transformers on one speaker? Something new. Each works with a separate voice coil in the speaker. Thus one amplifier can be hooked up for regular program use, and another for special announcements, emergency signals, regular time signals (as in a school), or other special uses. For use by non-technical people, this type of speaker solves the switching problem beautifully—by eliminating it! The speakers are made by Jensen in two models, both with 8-ohm voice coils. They are available with transformers for 70- or 25-volt lines.

SEPTEMBER, 1964

# Better Scope Transistor Checker

By ROBERT G. WARNER

I BUILT AN INSTRUMENT LIKE THE ONE Daniel F. Smith described on page 32 of the May 1963 issue of RADIO-ELECTRONICS, and cataloged all my loose and occupied transistors.

But I found that adding an audio sine-wave generator to Mr. Smith's circuit makes it more useful.

With the generator, I can find out how the transistors behave at higher frequencies, and I have a way of measuring approximate transistor gain without using the slope of the trace on the scope screen.

Fig. 1 shows how I marked off the slope screen with slopes corresponding

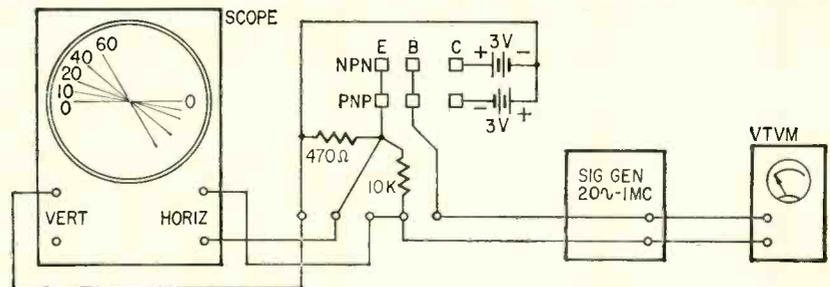


Fig. 1—Connections and scope markings.

to gains of 10 through 60. Setting the scope gain controls for a slope of 20 with the same signal applied to the vertical and horizontal inputs allows direct reading of gain. If I set the controls under those conditions for a slope of 10, I have to multiply my slope readings by 2, which lets me work with higher-gain transistors.

If the battery voltage is constant, I can get an approximation of the gain by measuring the voltage applied by the signal generator that is needed to produce only that part of the trace between "knee" and "instep", as shown in Fig. 2.

In other words, by adjusting the output of the generator we can find out how much signal is required to cover the complete amplifying range of the transistor. This signal, with constant battery voltage, should be about inversely proportional to gain. With a dc voltage of 3.1 and a signal frequency of 600 cycles, I found that 27 transistors with gains varying from 20 to 100 fitted fairly well to this formula:

$$\text{Gain} = 48/\text{ac volts}$$

At higher frequencies, using this method to determine gain becomes a necessity—on my scope, at least. Phase shift between vertical and horizontal amplifiers makes the straight line of Fig. 2 a very narrow ellipse at about 6,000 cycles. At 60 kc the trace is a distorted but definite ellipse, and at 600 kc, nearly a circle. Clearly, the slope of the trace can no longer be used to measure gain.

With the ac voltage method, gain checks are as easy at higher frequencies as at audio. Simply increase the voltage from the signal generator until the trace—whatever its shape—reaches a maximum height, beyond which it only broadens. That is the ac voltage required to "swing" the transistor along its operating range, shown in Fig. 2. Read the meter and substitute the reading for "ac volts" in the formula above.

This technique is especially useful for matching transistors to be used for medium-frequency work. Low-frequency gains give no hint of gain at higher frequencies. Two transistors from the same

radio both measured 67 at low frequency, but at 510 kc one read 120, the other 24. The high-gain transistor was in the rf, the other in the audio circuit.

I recently built a transistor frequency standard, and I found that I could improve performance noticeably by rearranging transistors according to the results from the gain check just described. Performance variations between transistors of the same type aren't restricted only to low-cost types. At 510 kc, gains for three \$3 transistors varied from 40 to 70. In instruments where transistor gain affects results, a little preliminary checking at the actual operating frequency can save time and trouble.

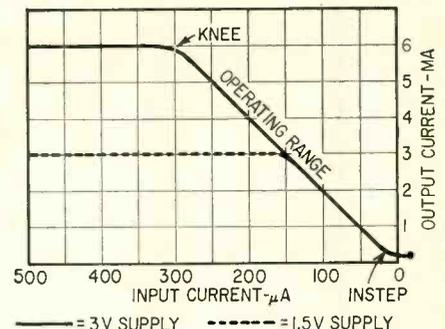


Fig. 2—Transistor operating range chart.

Though at high frequencies the scope traces don't give a direct indication of gain, the trace of a good, high-gain rf transistor is quite distinct from lower-gain, lower-frequency transistors.

My compliments to Mr. Smith for the simple way in which he presented his idea. END

# Radio-Electronics GOES TO THE WORLD'S FAIR




Color TV sets all over fairgrounds are programmed from this studio and control room at RCA pavilion (upper right). Public is invited to watch live shows telecast from four color cameras, four all-transistor videotape recorders and coaxial-cable rf distribution system. Pavilion also features see-yourself-on-color-TV, with a taped delay. You see yourself twice: once live and again 15 seconds later, exactly the same!





Whole family of Walt Disney "audioanimatronic" figures like "Granny" here are "cast" of 20-minute show at General Electric pavilion. Figures are driven by electropneumatic machinery, controlled by 32-track magnetic tape. Three closed-circuit TV monitors in background can be switched among 21 cameras around pavilion. In case of trouble, help can come fast. Charts and counters at right keep track of attendance.

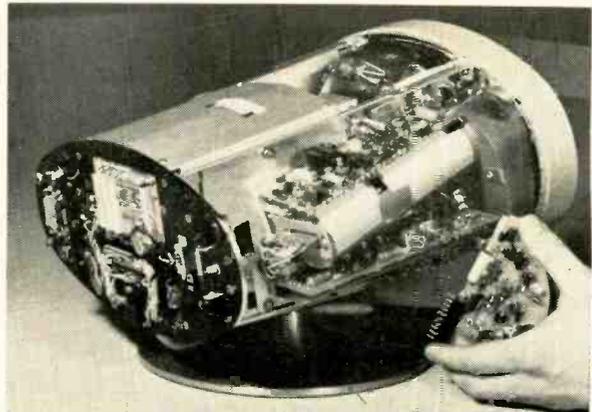Teleprinter has just divulged recipe for Swiss-cheese croquettes. Unit at National Cash Register pavilion is linked to computer (background). Other installations at NCR make magic squares based on visitors' favorite numbers, answer scientific questions, give information on vacation sites.



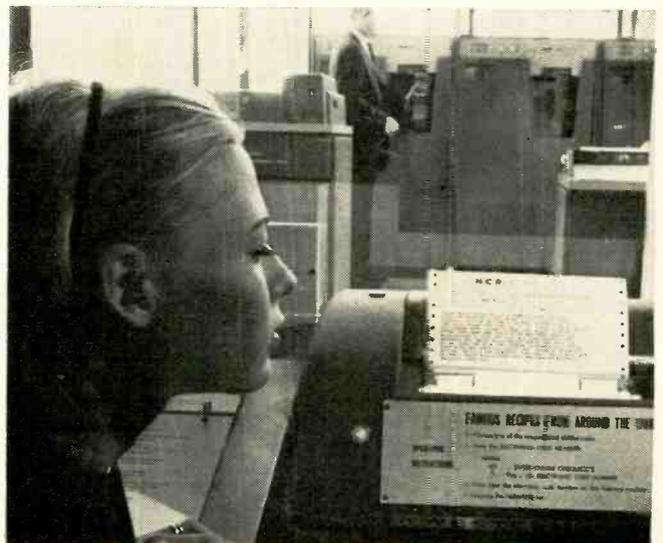What's inside Bell Telephone's Picturephone. Six booths at American Tel & Tel pavilion are equipped with Picturephones so visitors can talk to—and see—each other. (See July RADIO-ELECTRONICS, page 6.)



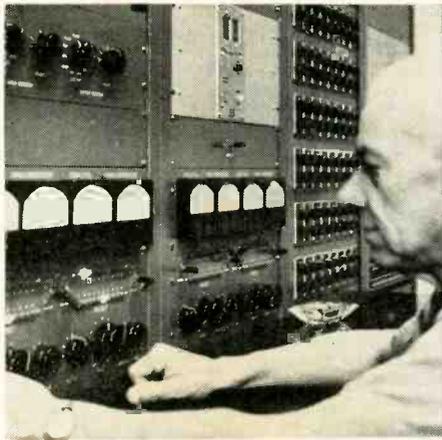

Elaborate sound system pipes "walking music", announcements and coded emergency signals to 470 RCA-designed speakers concealed in lamp posts all over grounds. System is controlled from panel which houses line amplifiers that drive 88 75-watt power amplifiers in 16 locations around fairgrounds. Level to each sector of fair is individually controlled, so each gets optimum sound. Music is pre-taped on 14-inch reels; cartridge tapes carry special announcements. Engineer Ed Mackey, above, is one of 12 who operate system.


## Sound System Sports Unusual Failure Monitor

The intricate sound system at the New York World's Fair would be a nightmare to operate and maintain if it weren't for an ingenious system of automatic checking and reporting designed to uncover failures and potential breakdowns immediately and pinpoint them exactly.

At each power amplifier location, which is remote from the main control room and may contain half a dozen amplifiers, there is a test chassis that includes an audio oscillator and timing mechanism. Once each hour, the program is cut off automatically at that bank of amplifiers only, and a short high-frequency audio pulse fed in. The input pulse is compared with the output pulse; if everything is shipshape, fine. If not, a relay flashes a lamp on a panel back at the master control room. The operator on duty, seeing the light, can tell instantly where the trouble is and send a man out to investigate.


The amplifier banks also incorporate thermostats that monitor the temperature of each unit. If an amplifier overheats (suggesting a short in a speaker line, a gassy tube, etc.) or goes cold (because of a burned-out tube or blown fuse), again a light flashes in the control room to pinpoint the trouble.

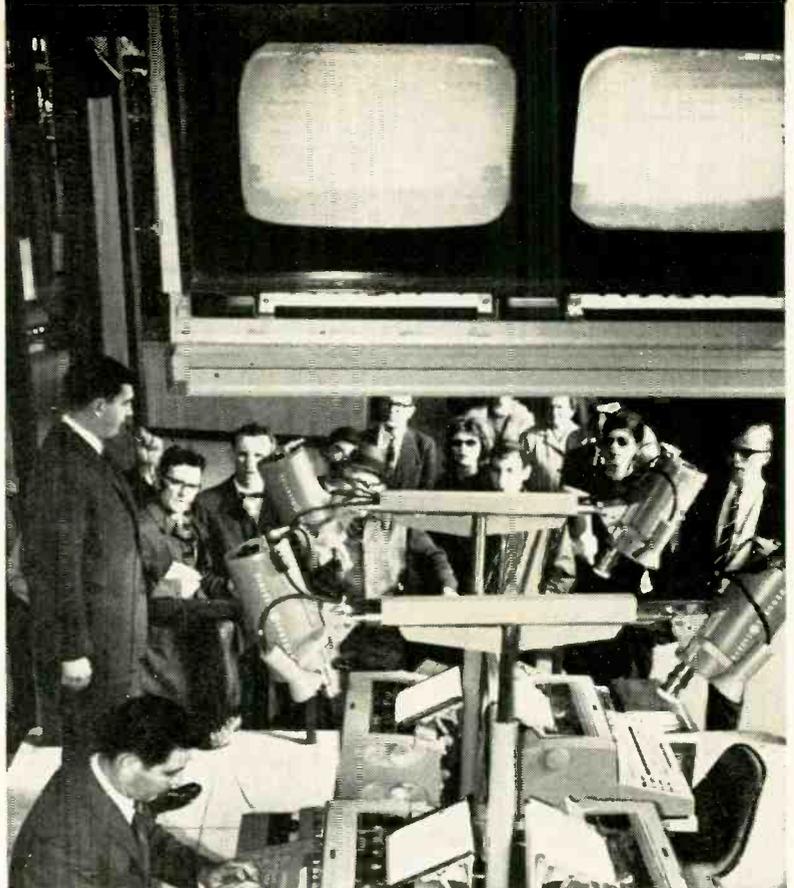
Jacks in patch panels at the control room make it quick and easy to substitute a defective unit without physically removing and replacing it, or to use some other-than-normal program routing, perhaps to bypass a dead amplifier. Flexibility and adaptability are key ideas behind the design of this amazing system.





Fairgoers watch typist copy Russian text into teleprinter which relays it 90 miles to IBM language-translating computer in Kingston, N.Y. English rendering, back in a second or two, is printed out on another machine. Overhead TV screens display Russian and English texts side by side.

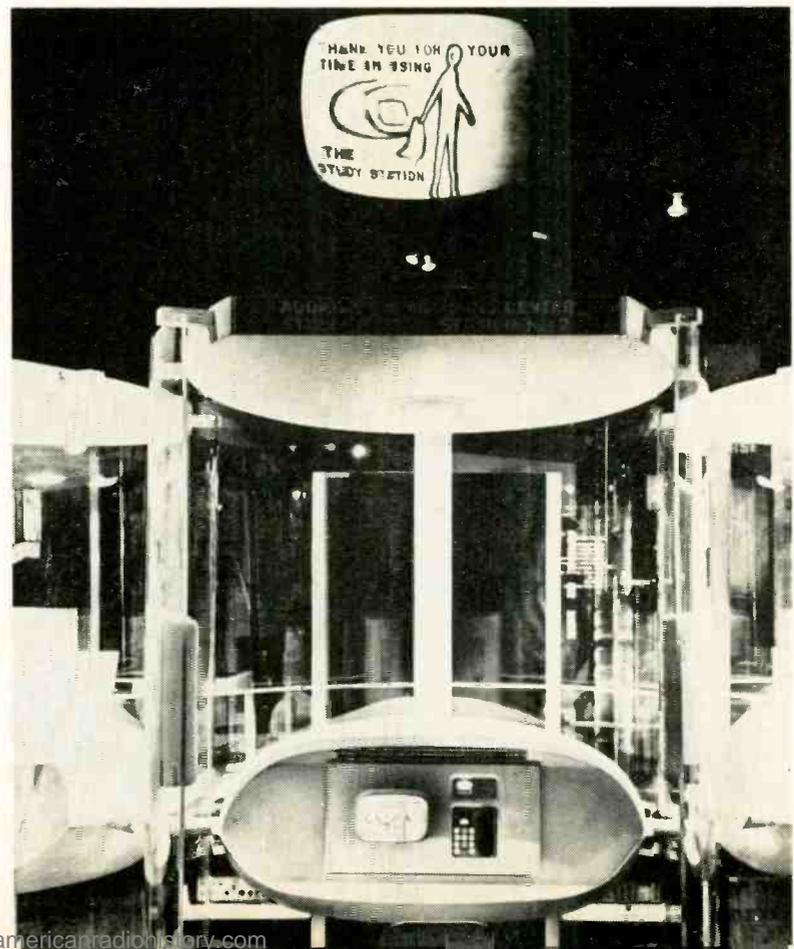Audiovisual Learning Center Station No. 2 in U. S. Pavilion is one of three designed to display potentialities of electronic teaching aids. Visitors can participate in learning programs. B&K 1076 Flying-Spot Scanner tele-vices fixed slides for display on screens like those in photo.



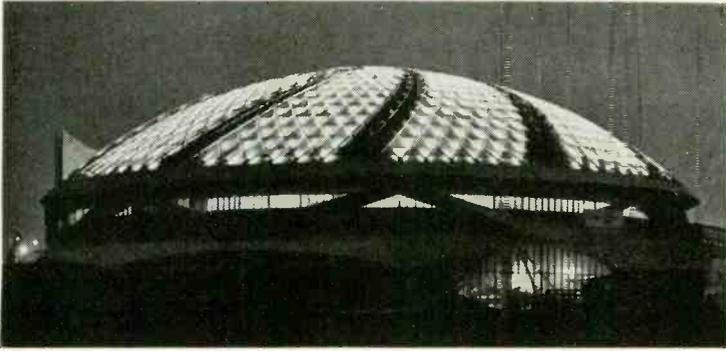

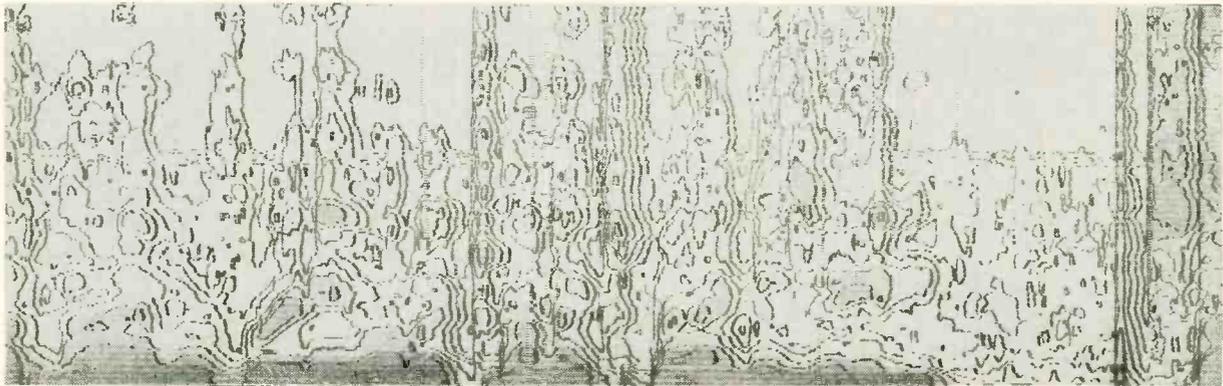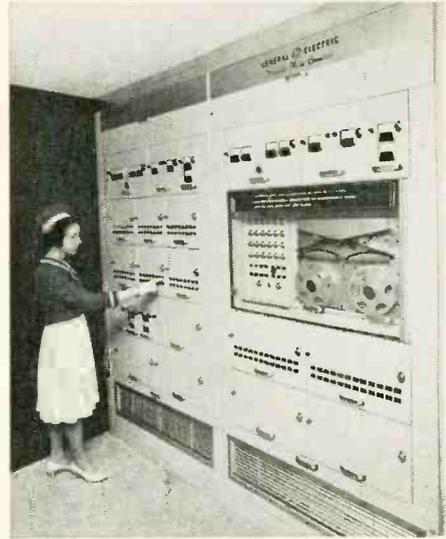G-E hostess points out control panel of "Directo-Matic" apparatus (right) used to control spectacular night-time dome lighting at G-E pavilion (above). Crisscross roof-supporting grid of steel tubes is flooded with 2,112 colored lights dimmed and turned on and off by silicon controlled rectifiers. Reels at right carry punched paper tape that controls lights.



Vocoder (in booth in back), valuable speech research tool, literally takes sounds apart and re-assembles them. It can alter pitch without affecting speed (unlike a tape recorder). Also at Bell (AT&T) pavilion was "speechprint" apparatus (counter in front). It makes distinctive patterns on paper of people's voices and helps researchers break speech sounds down into essential elements. Pattern reproduced above is R-E's associate editor's voice as he announces, "I'm from Radio-Electronics."

Another popular computer stunt at IBM pavilion is "character recognition." Visitor writes date of birth, all in figures, on card. Card is fed into machine, numbers are scanned optically and sent to computer, which extracts *New York Times* lead headline for that date. Headline is displayed on screen overhead, and visitor gets printed-out souvenir. System accepts many writing styles, though wild flourishes are rejected. Direct written-number recognition could speed data processing tremendously.



Squashed picture? Pointed heads? Screen look like somebody's changing slides? Find out why, and how to fix it

By JACK DARR  
SERVICE EDITOR

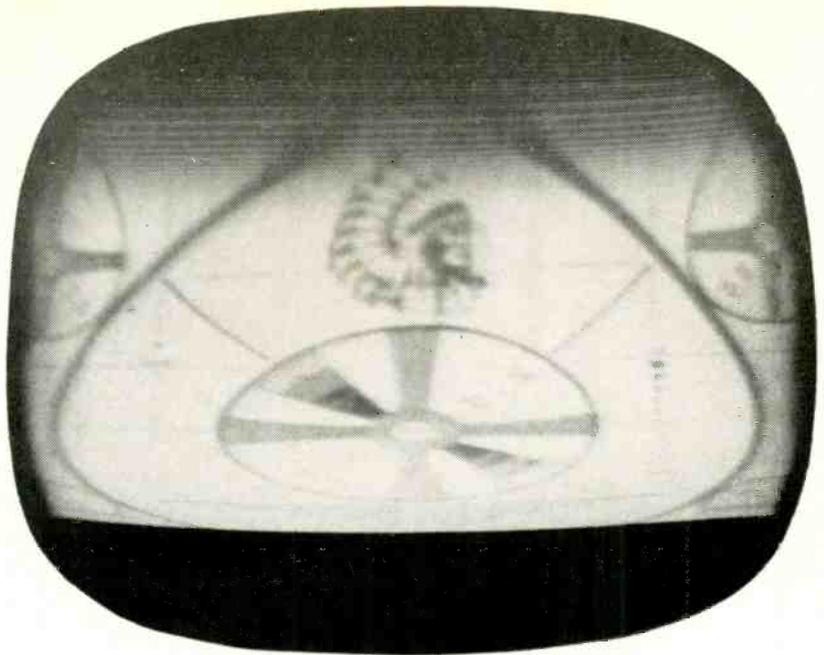


Fig. 2—Open vertical output cathode bypass compresses bottom of picture.

## Vertical Sweep and Sync Troubles

VERTICAL TROUBLES WILL ALWAYS CAUSE immediate complaints from customers. They're so obvious! Rolling, flipping, lack of height and poor vertical linearity show up so badly that even the most "unskilled" customer can see them. Poor vertical hold is very annoying, since the picture always rolls just at the most interesting part of the show. Let's look at some of the causes and cures for this.

A twist of the vertical hold control will tell you how the circuit is working. Normal: the picture should roll smoothly down, and the vertical blanking bar should stay the same width all the way (linearity good). Just before the bar gets to the bottom, it should suddenly snap out of sight. That means good sync. Turning the control the other way, the picture should hold until you reach the critical point, then roll upward (flip) very rapidly.

Rolling the bar halfway down the screen, then back up, the picture should show a very definite "snap" when it locks in. If it doesn't or if you can roll a picture *upward* slowly, there's trouble. The hold control should stop the picture somewhere near the center of its range. If it stops only when the control is all the way to one end, trouble again. Maybe not now, but soon. Fix it now and avoid a callback!

Now let's take a typical vertical oscillator-output stage apart and see what makes it tick. Fig. 1 shows a circuit used in a lot of sets lately. The tube is a twin-triode, in this case a 6CM7, but it could be any one of several like it. The triodes are different. The left, called the "oscillator" from now on, is a *voltage* amplifier, and the right ("output") is a *power* amplifier. This is a plate-coupled multivibrator circuit. Parts val-

ues shown here are taken from an actual circuit. You will find some other values in other sets, but the *function* of each will be the same.

This circuit works like all multivibrators. Think of it as a standard resistance-coupled amplifier circuit with the output fed back to the input, and it may be clearer; the plate of each tube is coupled to the grid of the other. One difference: because of the high signal level at the plate of the output half, the pulses are shaped and attenuated through the R-C network C4-R4-R5-C3 before being fed to the grid of the "oscillator". High resistance values are found, because most of these stages are fed from the boost.

Paper capacitors cause most of the trouble. Grid bias is critical, and most capacitors are connected between plate and grid in some way. Even a small leakage allows the plate voltage to leak through to the grid, and away goes your bias. Let's see what that can cause.

C1 couples the sync into the plate circuit of the oscillator. The sync here should be about 50-60 volts peak to peak, negative-going. This plate circuit is very high-impedance: look at the values of the resistors—7.5 megs, etc. So, if C1 leaks, it reduces the plate load resistance—note the 22,000-ohm resistor R1 to ground on the input side (part of the vertical integrator network). Symptom: poor sync action, no snap in the picture, and sometimes poor linearity.

C3 is part of the R-C network which feeds back pulses from the output

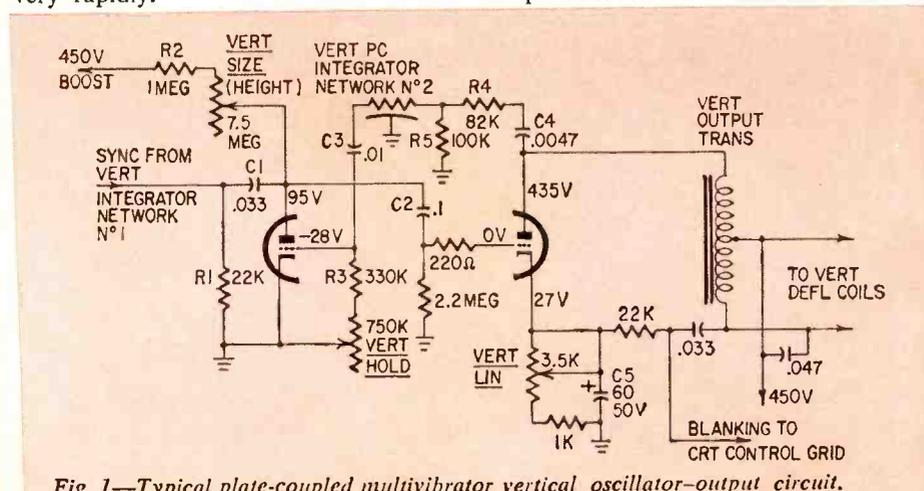


Fig. 1—Typical plate-coupled multivibrator vertical oscillator-output circuit.

plate to the input grid; this maintains the oscillator action. The pulses are reduced in amplitude, and shaped for the best linearity. Since this circuit feeds directly into the "frequency-determining" circuit, with the vertical hold control, you can see that any capacitor leakage here is going to foul up the hold action. The actual control of vertical frequency is done by the grid bias developed on the oscillator grid across the vertical hold control (up to 750,000 ohms) and its series resistor R3, 330,000 ohms. If we let any positive voltage leak into this circuit from the other plate, troubles!

Symptoms: very poor hold action

—control has to be jammed up against one end. If one of the capacitors (C3 or C4) is shorted, you'll probably not be able to get a picture to stand still at all. Most common symptom: "two pictures" on the screen, almost locked in. The oscillator is running at half normal speed.

C2 is the "main" coupling capacitor, between "oscillator" and "output" sections. If it leaks, it upsets the vertical linearity badly.

Last of the capacitors is the big electrolytic in the cathode circuit of the "output" stage, C5. If this opens or develops a high power factor, we get degeneration in the cathode and loss of

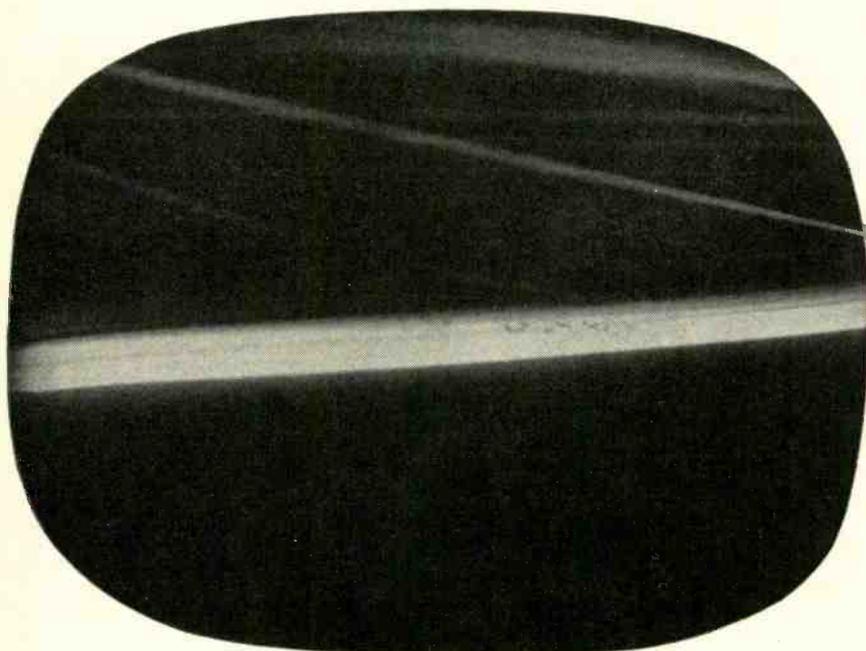


Fig. 4—Extreme mismatch in vertical output transformer!

Fig. 5—If this is all you can get after replacing an autotransformer with a two-winding type, reverse one of the windings.

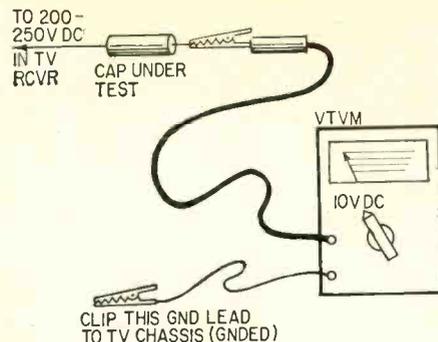
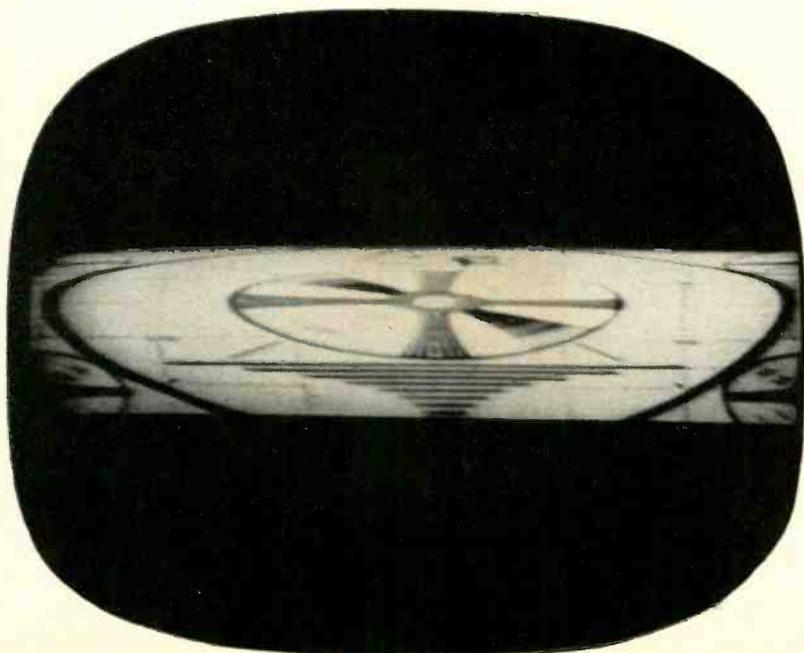


Fig. 3—Quick leakage test for paper capacitors.

gain. The picture will look like Fig. 2. Note the key symptom: compression at the *bottom* of the picture. Other defects—weak tubes, etc.—cause compression at the *top*. Simple test: just bridge a good electrolytic across C5, of any size from 50 to 100  $\mu$ f. If the picture comes back up to normal, C5 is bad; replace it. Incidentally, if you get "peculiar symptoms", especially as to the linearity, try disconnecting this capacitor if it's a part of a multiple electrolytic, and hooking in a separate unit. Some very unusual symptoms can come from leakage between elements of a multiple capacitor!

#### Testing paper capacitors for leakage

It takes only a *very* small leakage in any of the paper capacitors to upset things, so check carefully. If you have a tester that reads insulation resistance up to hundreds of megohms, use it and throw out any capacitor that won't give at least a  $\frac{3}{4}$ -scale reading. For replacements, use only 600-volt capacitors of the best quality you can get, and for goodness' sake *test them before you put them in!* Many a "dog" has been born by using new capacitors with more leakage than the ones you just took out!

Here's a quick check, just as accurate (Fig. 3). Set your vtvm on a low dc-volts scale; clip the ground to the TV chassis. Take the capacitor completely out of the circuit, and hook the dc volts probe to one end. Touch the other to a source of 250–300 volts dc in the TV set. If you get any reading at all, the capacitor is leaky.

In some sets, you can get the same check by pulling the tube, leaving the capacitor connected to the plate and taking the voltage reading at the grid end, unless the grid resistors are too small (less than 2 megohms total). By turning the set on, you apply positive voltage to the plate end of the capacitor. You can do this, even in series-string sets, because the semiconductor rectifier


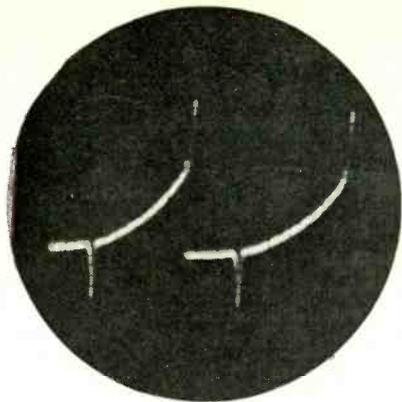


Fig. 6—Rolling picture halfway down puts sync pulses along trace at oscillator input.

Fig. 7—Same point as Fig. 6, but picture locked in.

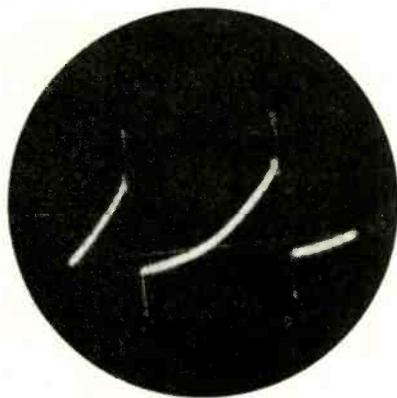

delivers B-plus voltage regardless of continuity in the heater circuit.

Resistors are also good possibilities for trouble. Measure each one carefully, according to its color code. Also, if the complaint is "slow drifting and loss of sync," heat each one with a soldering iron to see if it changes value. Most commonly found off are the resistor in series with the vertical hold control, and others that affect the frequency directly.

#### The vertical output transformer

A lot of these are replaced unnecessarily. They don't give too much trouble, really. Replace one only after checking out all capacitors and resistors. You can hang a new transformer in the circuit for a test without dismantling the old one. A couple of common troubles: wrong impedance—Fig. 4 shows a severe mismatch. Most vot's are auto-transformers now. They can be replaced by a separate-winding transformer of the correct impedance, by connecting the end of the primary to the end of the secondary. Watch your phasing! If you make a replacement and find something like Fig. 5, reverse one of the windings.

#### Sync

There's only one thing you can check sync with, and that's a scope with a low-capacitance probe. Connect it to the sync input, plate or grid, and turn

the vertical hold control until the blanking bar rolls about halfway down the screen. You should see a pattern somewhat like Fig. 6. That, by the way, was taken from a different oscillator circuit and shows positive-going sync. In the multivibrator type, the sync is negative-going, but what we're after is "Is it there, and if so, is it high enough?" In most cases, the value will be given on the schematic.

Grid sync is usually around 7-10 volts p-p, while plate sync will run from 40 to 60 volts p-p.

A "locked" picture looks like Fig. 7. This is at an oscillator grid, and the apparent nonlinearity is normal; it's corrected in the output stage. These waveforms, too, will be shown on the diagram. However, the picture itself is by far the easiest thing to trace nonlinearity with, because of conditions in the set, and possible differences between your scope and the one they took the waveform pictures with. Use a test pattern, or some round figure in a commercial, like the CBS "eye". That's a very good linearity checker.

In a very few sets, you can improve vertical sync by changing values in the vertical integrator. A classic example of this is the old G-E "M" series portable. If you reduce the 100,000-ohm series resistor to about 56,000 ohms, and increase the series capacitor to about .02  $\mu$ f, this brings up the vertical sync amplitude and helps out amazingly. However, do that sort of thing only as a last resort. If you do it, be sure to check not only for sync amplitude but for possible bad effects on linearity, etc.

Open vertical height and linearity controls can often be "repaired" by simply moving a lead to the other end of the resistance element. These controls are usually connected as rheostats, with only the slider and one end used. If the element opens up at one end, move the wire to the other, and you won't have to replace the control. Makes it work backward, of course, but nobody's supposed to be fooling with it anyhow but us! Intermittent vertical sweep trouble in lots of cases comes from a "dirty spot" on either the linearity or the height control. This is caused by the control slider sitting in the same place for some time. You can usually get around this either by cleaning the control or by moving the slider to another place, compensating by resetting the other control very slightly. Sometimes, if the burnt spot is too big, you'll have to move the lead to the other end of the control to get a fresh spot for the slider to sit on. END

## Terminal and Control Markings on Foreign Radios

With the ever-increasing number of foreign-made radios and phonographs being imported into the USA, the chance that a technician will run into one goes up.

### RADIO-PHONO

	PHONO INPUT		TREBLE
	MIKE INPUT		BASS
	TAPE INPUT		POWER ON-OFF
	EARPHONE OUTPUT (ΩHMS)		INCREASE (VOLUME, ETC.)
	SPEAKER OUTPUT (ΩHMS)		AC ONLY, VOLTS
	SINGLE-WIRE ANTENNA		AC-DC, VOLTS
	DIPOLE ANTENNA		HIGH VOLTAGE!
	GROUND		LEFT RIGHT FOR STEREO SPEAKER CONNECTIONS ETC.


### TELEVISION

	BRIGHTNESS		UHF STATIONS (CHANNELS)
	CONTRAST		50-60 CYCLE (POWER)
	HORIZONTAL HOLD		REMOTE CONTROL SOCKET
	VERTICAL HOLD		VHF DIPOLE
	HI-FI SWITCH		UHF DIPOLE
	VHF SWITCH		VERTICAL LINEARITY
	UHF SWITCH		HORIZONTAL LINEARITY
	VHF STATIONS (CHANNELS)		HEIGHT
			WIDTH

The sets are "internationalized" to some extent by their use of symbols rather than words to mark the various controls and functions. The symbols have been pretty well standardized throughout Europe by the efforts of the IEC and the Philips Co., and most of them are easily recognizable. Some, however, are a little more obscure; so, as a guide to the man who encounters a Grundig or Geloso or Tandberg or Telefunken, here are the symbols and their meanings.—Peter E. Sutheim
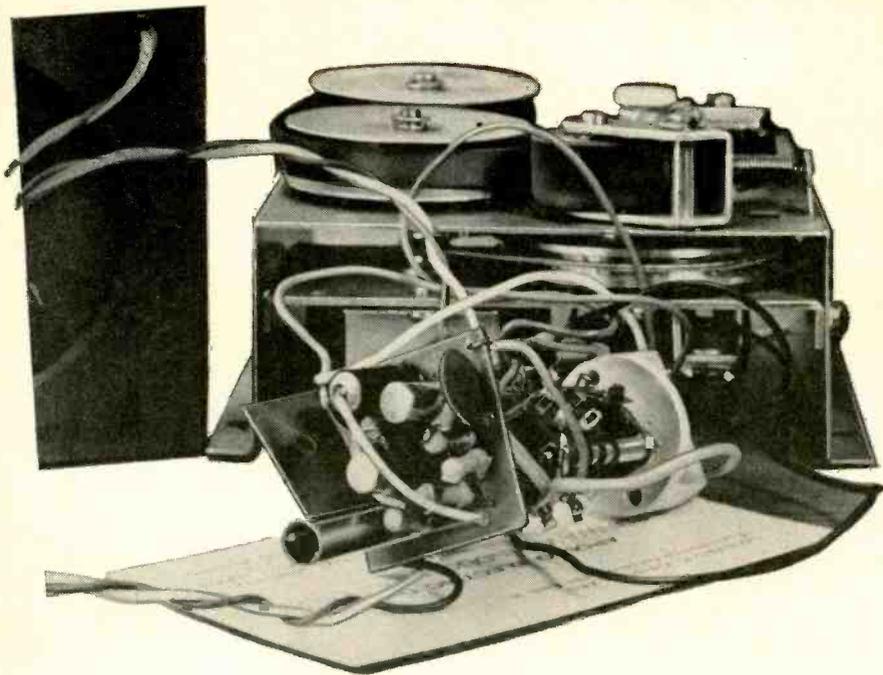
### Rotator Repair, Part II Unavoidable Postponement

The first installment of "Rotator Repair," by Homer L. Davidson, appeared in last month's issue. Because of additional information on some of the material in the second portion, we are re-editing it, and it has become inexpedient to include it in this issue. It will appear in October.



*Tiny amplifier, after circuit in Fig. 1, is smaller than switch it's mounted on. It was designed for tape recorder to be used in talking doll.*

# Push-Pull Output From One Transistor

Single output transistor drives two speakers in push-pull in these direct-coupled amplifiers

THIS ARTICLE MIGHT HAVE BEEN TITLED "How to Get Something for Nothing—Almost." Here is a deliciously simple amplifier with a push-pull output taken from a single transistor, connected much like the familiar split-load phase inverter. Fig. 1 shows a two-transistor circuit designed around the principle. Direct coupling saves many parts and assures excellent low-frequency response. With the details given here, you can apply the same techniques to other transistors, for other applications.

In Fig. 1, Q1 is both an ac driver and part of the dc bias system, since the amplifier is direct-coupled. Try to

By **LEONARD E. GEISLER**

get as nearly as possible the voltages shown on the schematic. Other transistors may need some value juggling. In any case, try to get equal dc drops across the output transistor's two loads (emitter and collector). Q2, the output transistor, should be biased (by varying R2) so that it works near the center of its class-A load-line, for minimum distortion.

C2 in Fig. 1 allows you to tailor the amplifier's response to fit a particular application. The larger C2, the higher the gain of the whole amplifier. With C2 omitted altogether, there is heavy negative feedback around the amplifier and its response is pretty flat


from dc (if C1 is jumped) to over 30 kc. But the gain is only 35 db. The value of C2 shown in Fig. 1 gives fairly flat response above 1 kc, puts 500 cycles about 2 db down and rolls off rapidly below that. At 100 cycles there is very little gain at all. This was done deliberately in the original to compensate for an unwanted resonance in the little speakers it was to be used with.

Power output, using 2N215's as shown, is a conservative 35 mw. On a scope, clipping was visible at 50 mw, though not really audible. At 60 mw it was audible, but could be eliminated by disconnecting C2. Then, naturally, the amplifier needed a higher driving voltage.

### More muscle


If you want high power, try transistors in TO-3 (diamond-shaped) cases,

- R1, R3—4,700 ohms
- R2—6,800 ohms
- C1—0.1  $\mu$ f
- C2—.05  $\mu$ f (see text)
- Q1, Q2—2N215
- 2 8-ohm speakers (see text)

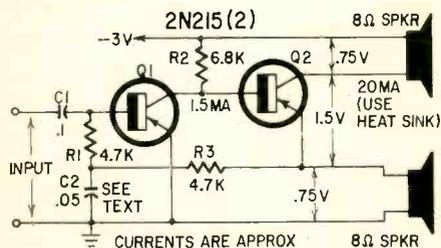


*Fig. 1—Low-power version. You can use a single speaker with a double voice coil.*

- R1—68,000 ohms
- R2—8,200 ohms (see text)
- R3—see text
- C—0.5  $\mu$ f
- Q1, Q2—2N215
- Q3—2N554
- 2 4-ohm speakers (see text)

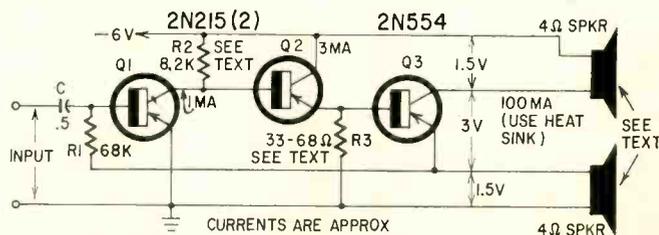

*Fig. 2—Higher-powered circuit. Feedback through R1 gives excellent performance.*

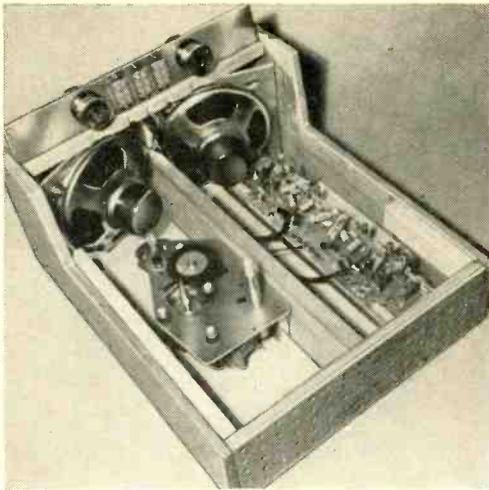

Two views of a miniature stereo phonograph using two amplifiers like ones described.



with heat sinks. Fig. 2 shows the circuit adapted for a 2N554 to yield about 1 watt output. R3 should be kept between 33 and 68 ohms. Again, vary R2 as necessary to give Q3 the correct static dc bias (adjust for  $I_c$  of about 100 ma).

Both circuits are stable between  $-10^\circ\text{C}$  and  $55^\circ\text{C}$ . Beyond these limits, R1 in both circuits should be reduced 20 to 40%.

Input impedance is several thousand ohms in both circuits, so they can be driven easily by other transistor circuits or by high-impedance devices through step-down transformers.

The output load can be two separate speakers or transformer windings,

or combined into a single speaker with a bifilar-wound double voice coil. With proper attention to phasing and dc polarity, you can prevent mechanical biasing on the speaker (off-centering due to dc component of current through voice coil). If the two windings are in phase, the output stage will oscillate in the grounded-base mode.

If you're interested in fuller (mathematical) analysis of this idea, turn to "Splitting the Load," by O. Greiter, *Wireless World*, February 1962, page 71. (The article came to my attention only after the lab work on this amplifier was done.)

### Applications


The photographs above show a tiny stereo phonograph using amplifiers like the ones described here. The head shows an early version in the lab. It's lying on an ordinary  $2 \times 3\frac{1}{2}$ -inch calling card. Above it is a miniature "disposable" tape recorder deck intended for a talking doll. That's standard  $\frac{1}{4}$ -inch tape, which should show you how small this amplifier can be! Actually, it was developed as a "gutless wonder" suitable for use in a disposable tape recorder. Think a little, and you'll surely be able to dream up uses for this simple, reliable circuit. END

## dynamic limiting with a photoresistor

ONE OF THE MOST MADDENING THINGS a PA technician has to contend with is the vast and rapid change in volume as the speaker, previously talking in a normal voice at about 2 feet from the microphone, leans into the mike and raises his voice to emphasize a point. The technician must rush to turn down the volume—and, shortly after, to turn it up again.

Dynamic limiting is the answer and one interesting method, introduced in some recent Philips amplifiers, is shown here. The principle follows the diagram (Fig. 1). A photoresistor is used as the control. It forms one part of a voltage divider. The other parts consist of isolating resistors R3 and R4.


A portion of the output signal is taken from winding L on the output transformer, fed through R6 and R7 to a small lamp focused on the photoresistor. When the lamp lights brightly with a strong output signal, the photoresistor's resistance drops, reducing the signal input to the amplifier. Because of the delay in the lamp filament lighting, sudden or short-duration voltage pulses have no effect. To limit these pulses, a

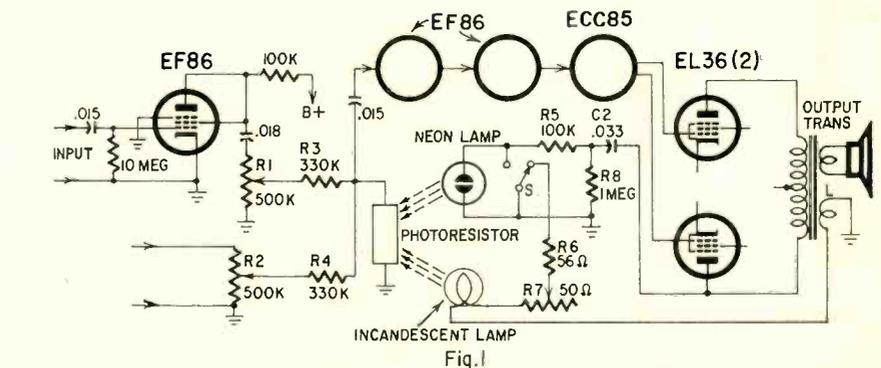

(An expander-compressor using neon lamps and a photoresistive cell, the Fairchild Componder, is made in this country (*RADIO-ELECTRONICS*, Jan. 1962, p. 39).

neon lamp is also included. It reacts more rapidly, but requires a greater voltage before it lights.

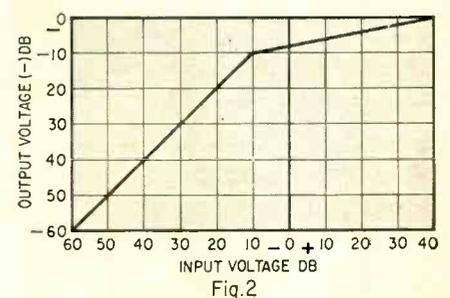The curve (Fig. 2) shows the effect of the circuit. You can see that with this type of regulation, up to about 35-db greater variation in the input signal is possible before running into the severe distortion that accompanies an overloaded amplifier. Possibility of acoustic feedback is also reduced.—*Radio og Fjernsyn*, March, 1962



Peewee was muttering to himself.

"What's the matter?" I asked.

"It's the dern sound on this RCA."

"What's the matter with it?"

"If I knew that, I'd have it fixed," he retorted.

"OK," I said, "I'll rephrase the question. How does it act?"

"Acts terrible," he replied, now being deliberately obnoxious but, after a pause for effect, he continued. "It plays OK for 30 minutes or so, then the audio drops to nothing."

"What have you checked?" I asked.

"Just about everything."

"Then you should have it narrowed down pretty close—just check the few things you haven't checked and you got it made."

"Aw-w, you know what I mean," grumbled Peewee. "How can you check an intermittent? Every time I start to put a test probe onto something it starts playing again."


"Have you narrowed down the trouble at all?" I wanted to know.

"Well," said Peewee, "at least I know it's somewhere before the volume control. I put our audio signal tracer there and left it. When the sound went off, it went off on the signal tracer, too."

"Good, at least we know the trouble isn't in the audio amplifier or output stage, so it must be somewhere between the video detector and the volume control—that is, if the picture isn't going off too."

"Picture stays OK," he assured me. Then he asked, "Do you know some easy way of localizing that part of the circuit?"

"Oh, there are probably lotsa ways of

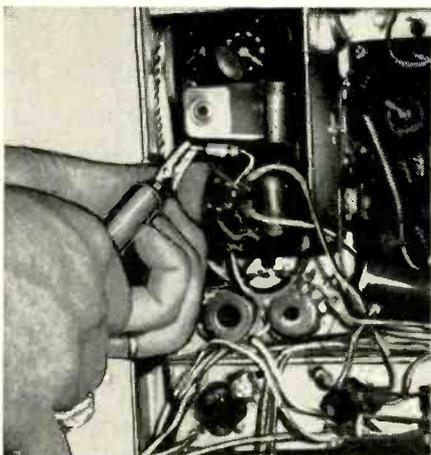

Clipping the vtvm onto the limiter grid resistor.

doing it but since you want an easy way, why not use the vtvm?"

"Look here at the schematic," I instructed. "See the 47,000-ohm resistor in the grid circuit of the 5U8?"

# Peewee Learns Sound Reasoning

YOU WON'T NECESSARILY CURE A BAD CONNECTION BY RESOLDERING EVERYTHING IN SIGHT

By MIKE WAYNE

"You mean R101?"

"I mean R101. That's the limiter grid resistor."

"Even I know that, but so what?"

"So what happens when a signal is coming into this stage?"

"You get a negative voltage across the resistor, I guess."

"Right," I agreed. "And that voltage is proportional to what?"

"To the signal strength, I suppose."

"Bravo," I said. "Does that suggest a way to use the vtvm?"

Peewee thought a moment and then started radiating effervescence like an Alka-Seltzer dropped in water. "If the signal is dropping out between the video amplifier and the 5U8 grid," he reasoned, "it'll show up as a drop in voltage across the limiter grid resistor."

"Congratulations! Now put the vtvm on there and wait. When the sound goes down again, you'll know which way to look for the trouble. Right?"

"Right."

About 15 minutes later the sound dropped down again but the voltage reading didn't waver.

It's OK up to the limiter

"What does that tell you?" I asked.

"Means everything's hunkydory up to the limiter," he replied. "And that just leaves the limiter tube and the detector transformer that could be bad."

"Whoa up a minute," I cautioned.

"Not so fast. It also leaves the wiring, a half-dozen resistors and capacitors,

not to mention the detector tube and its circuits."

"Y' think it might be the printed-circuit board?" he asked.

"Could be, and it looks like someone before us had the same idea, judging by all the soldering that's been done."

"I guess you could say that was a pretty popular board," said Peewee.

"How's that?"

"Looks like it was in its second printing."

"I see your point. But let's get on with the problem and see if we can't localize it to either the limiter or detector stage."

"Why not put the vtvm across the ratio detector capacitor, C108?" he wondered.

"Now you're thinkin'. But this circuit is a little unusual. One side of the capacitor isn't grounded. Let's just measure from one side of it to ground."

"Will that work OK?"


"Sure, it'll be simply measuring the voltage drop across half the detector load resistance."

"Why doesn't this circuit have a grounded capacitor?" he wanted to know.

"Makes it simpler to adjust," I answered. "All you have to do is connect a vtvm between the junction of the 39,000-ohm resistor and the .0082- $\mu$ f capacitor and ground, and then adjust the detector transformer slug for zero voltage."

"On a station signal?" he asked.

"That's the best way. But let's get

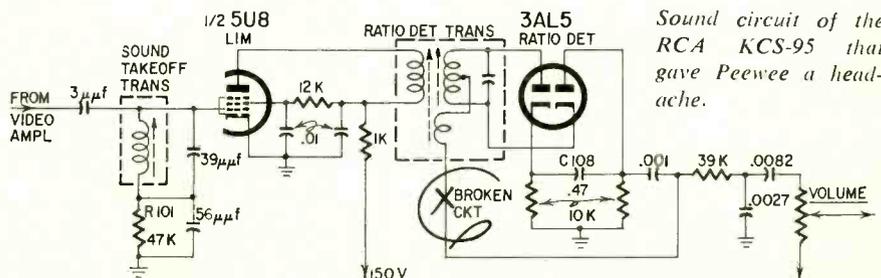

Sound circuit of the RCA KCS-95 that gave Peewee a headache.

back to the trouble. Connect the vtvm through this hole in the shield to one side of the 0.47- $\mu$ f capacitor (C108)."

Peewee did as he was told but, as soon as he moved the probe, the sound returned full volume. "Wouldn't you know it?" he said disgustedly.

"Don't worry about it. We have to have a reference anyhow."

He clipped on the test lead and we noted the reading. This time, as if finally giving up its capricious habits, the sound dropped out in a couple of minutes.

"Well, I'll be derved," said Peewee. "Come here."

I walked over and glanced at the meter at which he stared in disbelief.

"Didn't budge, did it?" I smiled knowingly, but I was almost as surprised as he.


We both looked at the circuit again.

"You sure the sound goes down when you hook the tracer to the top of the volume control?"

"Dern sure," he asserted.

"Then that doesn't leave much, does it?"

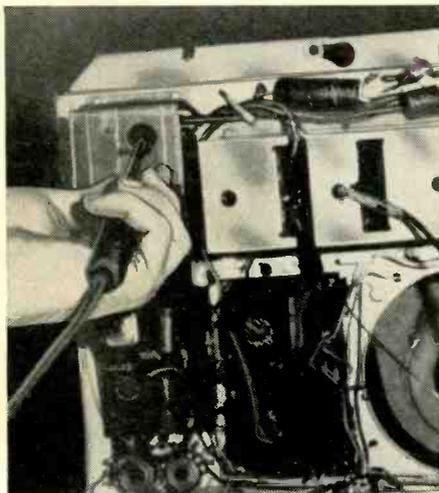"Just a capacitor or three and a resistor. I've already checked on the other side of the .0082 capacitor and there was no sound there either. Then I moved back to the other side of the 39,-



Connecting the vtvm to one side of ratio-detector capacitor C108, through the hole provided in the shield.

000-ohm resistor and it wasn't there either."

"Then that just leaves a broken printed circuit or an open in the tertiary winding inside the detector transformer. Watch the terminals while I wiggle the transformer."

I moved the transformer gently from side to side. The sound came back on

once or twice in random fashion. Then Peewee yelled, "I see it! I see it! The terminal on the transformer is loose from the board."


Peewee resoldered the connection while I philosophized, "Try as you will to resolder every connection on a printed board, you'll just about always miss the one bad place—at least that's been my experience. Whoever worked on this set before had the same trouble. All his soldering probably just quieted things down 'til he got the set back to the customer's home. When it started to act up again the same way, the customer was disgusted and brought the set to us. Our friend, whoever he was, lost a customer because he didn't have a way to localize the trouble."

"My turn to take to the soap box," said Peewee. "Ever notice how if connections get close together when they're not supposed to, they'll short sure as shootin'—but when they're close together and supposed to be together, they'll open every time—ever think about that?"

"How's that again?"

"Oh, never mind," he said, "who listens to me anyhow?"

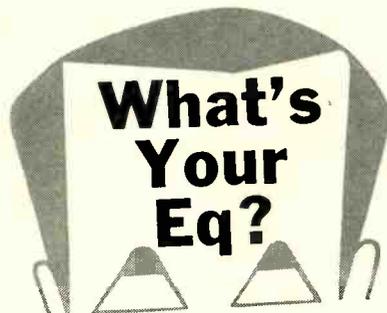
I thought he seemed just a little peeved that I had apparently missed this bit of world-shaking wisdom. END



Conducted by  
E. D. CLARK
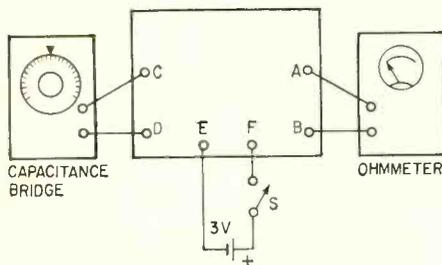
### What's in the Box?

I have presented this problem to many technicians and, though the answer is simple, they have failed to find it. This, I think, is due to the fact that they tend to complicate a simple problem.



Before the switch is closed, the capacitance bridge reads 5 pf, and the ohmmeter reads 1 ohm. After the switch

Two puzzlers for the students, theoretician and practical man. Simple? Double-check your answers before you say you've solved them. If you have an interesting or unusual puzzle (with an answer) send it to us. We will pay \$10 for each one accepted. We're especially interested in service stinkers or engineering stumblers on actual electronic equipment. We get so many letters we can't answer individual ones, but we'll print the more interesting solutions—ones the original authors never thought of.


Write EQ Editor, Radio-Electronics, 154 West 14th Street, New York, N. Y. 10011.

Answers to this month's puzzles are on page 105.

is closed, the bridge reads 50 pf, and the ohmmeter 5 ohms. Reverse battery polarity, and readings revert to original. Voltage check at terminals A-B shows no voltage present. What's in the black box?—E.J. Cunningham
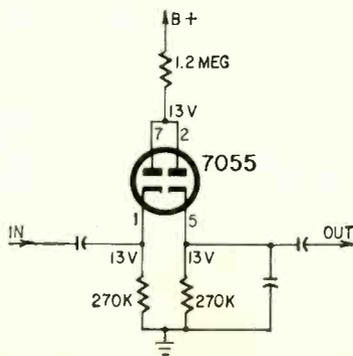
### Reverse Polarity

In trouble-shooting a 40-mc, 100-watt mobile transmitter, all electrode voltages as measured with a standard



20,000 ohms per volt vom agree with the manufacturer's schematic—except that the voltage at the plates of the 7055 (12AL5) audio limiter is a negative 13 volts! A new-tested tube results in the same reading. What is wrong? Hint: An 11-meg vtvm reads a positive 13 volts, but when both meters are connected to the plates, both read -13 volts.—Basil Barbee

### 50 Years Ago

In Gernsback Publications  
In September, 1914  
Electrical Experimenter

How to Use the "Electro" Loose Coupler.

Experimental Electricity Course (Lesson 13), by S. Gernsback & H. Winfield Secor.

Another Improved Buzzer Transmitter, by Frank H. Broome.

Danger Signs for Radio Stations.

A Simple Electroscope.

Aerial Mast Construction, by Charles Fitzgerald.

The Sayville Wireless Station.

A Good Mineral Detector, by Ralph Humphrey.

Automatic Ticker Receiver, by John Hays Hammond.

New Pickard Detector Stand.

THE ELECTRONICS TECHNICIAN LOCATED near water is a natural in the highly profitable, sometimes exciting, service work aboard boats. Their ever-increasing electronic gear requires competent service and, with few exceptions, the circuits are refreshingly simple compared to even the simplest TV.

In many locations, a scarcity of marine electronics specialists means that, with relatively easy preparation and a little ambition, you can easily earn many times your initial marine service investment during your first season on the boats.

To service ship-to-shore radios, you need a Second-Class radiotelephone operator's license. With a ship radar endorsement for it, you can capitalize on the rapidly expanding radar service field, where rates run as high as \$10 an hour. A few weeks of boning up on Elements I, II, III and VIII in a good license manual will cinch the FCC examination.

No license is required to service numerous other marine electronic gadgets: depth sounders, hailers, intercoms, radio direction finders, electronic sirens, power converters and battery charging systems, and automatic pilots. Service data are packed with most new equipment and usually kept handy by the boat owner. Service manuals can be obtained from manufacturers for small fees. Bendix\* publishes a perpetual service manual covering all marine electronic

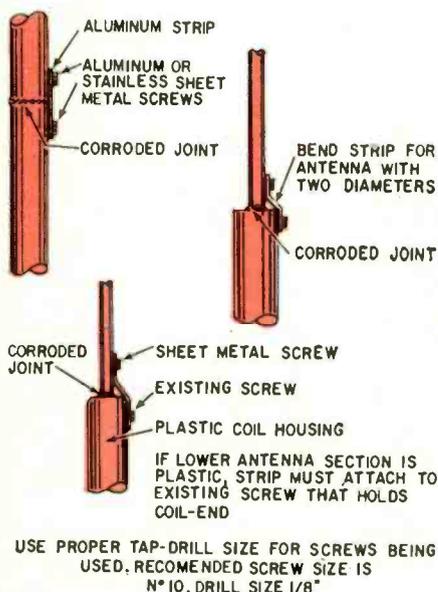


Fig. 1—Corroded antenna section joints that can't be separated for cleaning can be bypassed electrically with strip of metal. Be sure aluminum strip touches only other aluminum parts (except for stainless steel screws); otherwise—corrosion!

\*Bendix Corp., Marine Dept., 8211 Lankershim Blvd., No. Hollywood, Calif.

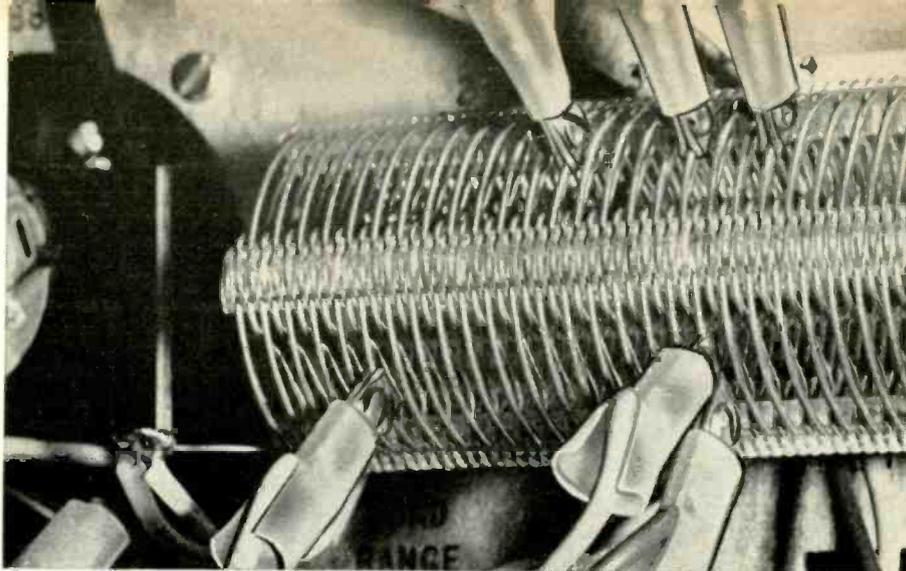


Fig. 2—Typical coil-tapping method used in most marine radiotelephones for tuning antenna, tank and loading coils. This is antenna coil of Bendix SK-242.

## Money In Electronics Afloat

What you need to get started in marine electronics service. Tuning and troubleshooting transmitters

By ROBERT C. BEARD

PART I

items ever made by them. It is kept current by frequent supplements, though the initial and only cost is under \$20. Most circuits are simple and basic, however, and you will quickly ignore manuals except for rare dog jobs.

My purpose here is to acquaint you with the most common—though not obvious to the novice—troubles in marine service, so you can go right to work on the boats with confidence. Most other problems will be basic circuit analysis.

Making money on the boats means working fast and accurately. This dictates a careful choice of tools and equipment for doing all possible work on the job—without ac power. A transistor power converter (Heath MP-10, or equal) with 8 feet of wire and large battery clips will operate a soldering iron or tube tester from boat batteries.

Your regular service kit should also include open-end and socket wrenches up to 1/2 inch and a contact burnisher. Carry a spray can of CRC\*\* corrosion proofing (available at most marinas). For space and weight saving, your multimeter should be small and light (Triplet 310 or equivalent). Cover the bottom of your kit with rubber or leather to prevent marring deck surfaces.

A separate "marine service kit" can consist of a batteryless field-strength meter (Heath PM-2 or equivalent), power converter, transistor frequency and modulation meter, supply of marine crystals and pad of transmitter certification slips. These carry well in a canvas

beach valise or similar container. A tube tester need not be carried routinely because tube failures are infrequent.

For this reason, you won't need to enlarge tube stock immediately. As you encounter failures, buy an extra of the type required. Common TV and radio tubes are used generally except in transmitters where output stages use 12-CU6, 12DQ6, 807, 6883 and similar types. A few of these in stock might prevent a return trip. A small stock of transistors is necessary, and Tung Sol types ET-1 through ET-7 (or equivalent) will serve most purposes. A few extra types such as 2N234A, 2N677B and 2N1136B, will handle modulator and driver failures in most transistor units.

Your stock of marine crystals may be of .01% tolerance since marine tolerances are .02%. The most used frequencies are 2182, 2638 and 2738 kc, plus marine radiotelephone operator frequencies for your area and Coast Guard channels. A list of these is available from the Coast Guard or equipment manufacturers. The above are transmitter frequencies; in most cases, receiver crystals will be those frequencies plus 455 kc (the i.f.), except marine telephones, which send and receive on different frequencies. Receiver crystals for them will be the assigned telephone transmitting frequency plus 455 kc. Petersent makes reliable, low-priced marine stock crystals. Their type Z-9 holder is the small size with 1/2-inch pin spacing. Since some radiotelephones use large

\*\*CRC, 116 Chestnut St., Philadelphia, Pa.

†Petersen Radio Co., Inc., 2800 W. Broadway, Council Bluffs, Iowa.

holders (3/4-inch spacing), stock adapters from small to large to eliminate duplicate stock of crystals in large holders. Crystal correlation capacitances vary considerably, but initial stock should be 20–25 pf, which will put most rigs within tolerance. Frequency checks on various transmitters will soon indicate whether you need stock different-capacitance holders for certain units.

Vibrators are needed for radiotelephones and depth sounders. Some Bendix sounders use special ones available only from Bendix; however, following types will handle most requirements: 1016248 (Bendix), G1501 (12 v), 1601 (6 v), G1601 (12 v), 292-3904G2 (Raytheon, 60 cycles) and 115 cycles, 4-prong synchronous from Sonar.‡

Neon bulbs in depth sounders need frequent replacement. NE-51H's will repair White Echo Sounders, and stock of replacement bulbs (NE-2 type) from Sonar will do for most other makes. Special bulbs are used in some Bendix and Raytheon models. These must be obtained from their manufacturers; however, they do not need replacement often.

#### Radiotelephone service

The most common radiotelephone complaint: "They can't hear me!" If modulation is present with low rf output, check the antenna system first. Corrosion where lead-in wire attaches to

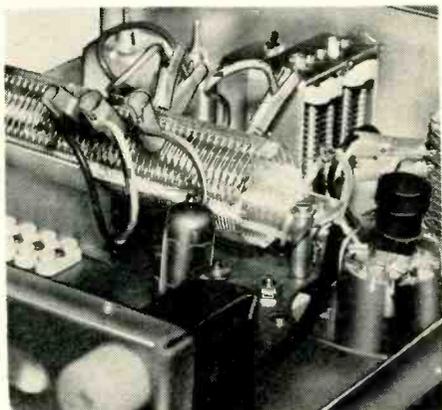


Fig. 3—Variable capacitors (at far end of chassis) are used in this model to tune two highest-frequency channels.

antenna can make a bad connection despite a tight mechanical joint. Cleaning wire end, bolt and antenna surface thoroughly corrects this problem. Spray CRC over finished job to prevent future corrosion.

Corrosion also breaks continuity between antenna sections, especially on aluminum antennas. Loading coil connections suffer likewise. Check for resistance by connecting your ohmmeter (on R × 1 scale) to bare metal on each side of suspected joint. Any resistance

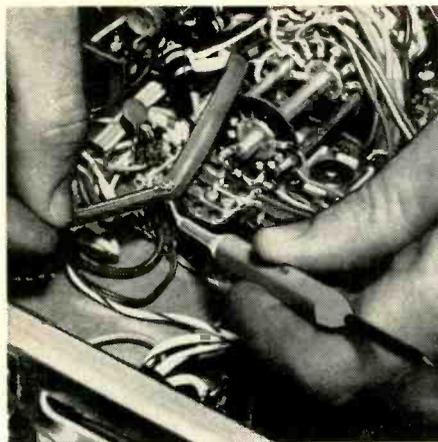


Fig. 4—Use folded strip of crocus cloth (abrasive side out) to clean both halves of relay contact simultaneously.

reading indicates need for repair (Fig. 1).

Repeat transmitter and antenna tuning after cleaning or otherwise altering antenna circuit. Most marine rigs tune both plate tank and antenna coil with movable coil taps (Fig. 2). Better outfits have variable capacitors to supplement taps in plate circuits (Fig. 3). Some use third tapped coil for antenna loading adjustments, but most have trimmers. If the transmitter lacks a milliammeter, it will have chassis jack (sometimes well hidden) for connecting your portable meter.

Always tune highest channel first, working downward in frequency, to minimize detuning of previously tuned channels, regardless of channel number sequence used. Standard color-coding of channel tap wires is shown in table.

Remove antenna and set all load adjustments to mid-position. Remove tank coil taps. Grasp highest-frequency tap by plastic insulator and, while keying transmitter with your other hand, move tap carefully from turn to turn on coil, starting at plate end, until you read minimum plate current. Tighten tap at that point and, if there is a variable capacitor, tune for final dip. Repeat for all channels in order of descending frequency. Be careful to keep hands off output tube plate cap and other nearby high-voltage components. High-powered rigs have a "low-power" switch for tuning.

Attach antenna lead and again key transmitter on highest channel. If plate current exceeds rating, reduce coupling by adjusting load tap or trimmer until current is below normal. Keep transmitter "on" periods brief. Then remove antenna coil tap for same channel and move it up or down antenna coil for maximum field strength. Finally readjust load trimmer (or tap) for rated plate current. If normal current cannot be obtained, plate tank Q is wrong.

Moving plate coil tap one or two turns up or down and retuning will correct Q, after which antenna loading will produce proper input. Repeat procedure for each channel in order of descending frequency.

A few transmitters (especially some Hartman models) have considerable interaction of antenna tuning and plate tank resonance. You will have to make several "redippings" of plate current as proper antenna loading is reached.

Old radiophones sometimes become intermittently weak because of corrosion between coil and taps. Tuning an old rig by tap selection is often impossible without thoroughly sanding tap clip and all coil turns.

Check fuses if rig is dead. In addition to fuses on chassis, fuses are often installed in the battery line in engine compartment. Often main power is handled by relay, controlled by transmitter on-off switch. Burnt and dirty relay contacts are frequent troublemakers. Fig. 4 shows one method of cleaning contacts. Fold an 8-inch strip of crocus cloth to form a 4-inch strip with abrasive on both outside faces. Using suitable tool to push contacts gently together, draw strip between them, cleaning both

#### STANDARD CHANNEL-NUMBER COLOR-CODES

Channel	Color	Channel	Color
1	brown	5	green
2	red	6	blue
3	orange	7	violet
4	yellow	8	gray or white

Coding follows standard resistor-capacitor code except for omission of 0 and 9.

points simultaneously. Repeat several times on each set of points to insure good contact.

Transmitter oscillators are untuned and rarely give trouble. If grid drive seems weak on one channel, try new crystal. (New crystal must be frequency-checked.)

Modulation loss is common. Sometimes modulator or driver tubes or transistors fail. More often, cause is damaged mike cartridge or broken wires in microphone cable or fittings.

Radiotelephone circuits are simple and reliable. "Tough dog" service problems are almost unknown. If one occurs, it is usually in the receiver section. Beware of units that have been hit directly or indirectly by lightning. Never under any circumstances estimate repair on such a job. There are too many good but weakened parts you'll be held responsible for when they fail soon after repairs.

The next article in this group will cover the installation and troubleshooting of depth sounders.

‡Sonar Radio Corp., 73 Wortman Ave., Brooklyn 7, N.Y.

by Jack Darr  
Service Editor



This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 154 West 14th Street, New York 10011.

WHILE WE'RE TRYING TO DIAGNOSE trouble, we're thinking about inductance, resistance and capacitance. Which one is "bad"? Well, you don't have to worry about *one* thing: capacitance. Not capacitors—capacitance. Why? Resistors can change in value; inductors can short and change inductance; but capacitors change capacitance? Nay, nay—never! (With the inevitable exception that proves the rule, of course.)

Capacitors are prone to numerous troubles: they leak, they short, they open, but they don't change capacitance—at least not enough to throw the circuit out of operation. To change the value of a capacitor, you'd have to open it, add or take off some of the "plates" or foil, and reseal it! The only thing it is likely to do along these lines is open completely. This, of course, can be checked very easily by bridging a duplicate unit across the suspected one. Would that all other tests were as simple!

So, while you're doing your diagnostic thinking about a circuit, leave this one thing out of your mind. It'll leave it just that little bit less cluttered and, goodness knows, we can always use that. There are plenty of things to confuse us as it is.

By all means suspect *every* capacitor in a circuit of being leaky, shorted or open. These are things that *can* happen, and do. So, aim your thinking at these possibilities; think of the possible effects of a few volts leakage through a capacitor into a very high-impedance grid circuit; the effect on grid bias of a dead short in a capacitor, or what would happen if a vital bypass were to open, and so on.

The one exception? The electrolytics. As the fluid or paste in them dries out, they *can* and do change capacitance. This plays hob with the filtering efficiency. So, *always* suspect electrolytics of changing capacitance, and always of going *lower*. Here again, we have a quick check: bridge a good one across the suspect and see if you get rid of some of the troubles you're working

on. If it's a multiple unit, disconnect the one you suspect and bridge the circuit with a good one. This eliminates the chance that there was leakage between units.

See if this doesn't help just a little.

### TV remote control trouble

*A customer brought in an Admiral TV with remote control. Channel-change bar wouldn't work, but volume-control bar worked fine. I checked everything in the set, but no results. He left town with the set before I could find the trouble! What do you think it was?—W. S., Saco, Me.*

This would almost have to be one of two things: either a mistuned "bar" in the transmitter or something in the double relay in the remote unit. Since one function is OK, one side of the relay must be working. I'd then suspect a dirty relay contact on the other side.

Also, the transmitter bar, which is basically a *bell*, could be out of tune. This would give you *sound*, but at the wrong frequency! So this particular function wouldn't work. I remember a very similar instance on a Zenith super-sonic remote control, with four bars. One didn't work. Finally, I took the unit apart and found a bit of *chewing gum* on the side of this bar! Threw it out of resonance far enough so that it would not close the relay! A crack or chip out of a bar or misadjustment of the holder will do the same thing. Even though you can hear the bar ringing, check to be sure that it's ringing at the right frequency!

### Hum bar

*I have replaced the picture tube on an Admiral 20Y4BF. Now the picture has a very black bar across the bottom and very bright retrace lines at the top. Only about two-thirds of the picture is visible. I can't find a vertical-size control on this set either.—J. F. S., Cleveland, Ohio*

This could be double trouble, but your worst trouble right now is in that

hum bar. The picture is being blacked out at the bottom and brightened at the top by 60-cycle hum in the video. This is verified by the fact that there is only a single bar. Power-supply trouble would cause 120-cycle hum, making two dark bars.

The first step is to replace the tubes that could cause this (by developing heater-cathode leakage), the 6S4 vertical output, 6BH8 vertical oscillator, the 6AW8 video amplifier and the tubes in the tuner and video i.f.

If this doesn't help, check the electrolytic capacitors which could allow hum to feed into the video. These would be the 10- $\mu$ f from the 6S4 cathode to B-plus boost; the 5- $\mu$ f capacitor on the video amplifier screen grid; the 20- $\mu$ f capacitor from the 6S4 cathode to ground, and the power-supply filter capacitors.

A scope is a great help in locating this kind of trouble. Simply check all of your B-plus supply lines and voltage taps, looking for unusually high hum levels. Anything above about 0.5 volt should be viewed with suspicion!

There *is* a vertical height control on this Admiral chassis, by the way. It is a 2.5-meg pot in the plate circuit of the 6BH8 vertical oscillator and is located right underneath the 6CU6 horizontal-output tube, looking from the back of the chassis.

The 21ALP4 tube is electrostatically focused. Be sure to set the ion trap for maximum brightness, then move it slightly around the neck of the tube, watching the scanning lines, for best focus.

### Modern record player for old Philco

*I have a Philco 42-1013 radio-phonograph combination for repair. The set is all in good shape now, and I want to add a modern record changer. It works, but the tone quality is awful. What am I going to have to do to get better tone?—L. D., Erlanger, Ky.*

This was the model that used the Beam-O-Lite pickup. It had a tiny pho-

toelectric cell in the pickup head with an exciter lamp. A mirror on the stylus varied the amount of light falling on the cell (Fig. 1). Of course, the output of this was pretty low. So a matching transformer and a pretty high-gain preamp were used.

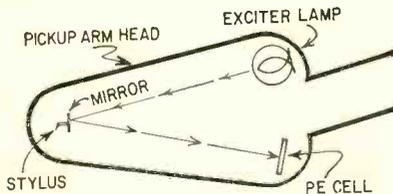


Fig. 1—Philco Beam-o-Lite cartridge used exciter lamp powered by ultrasonic oscillator on amplifier chassis.

This is the 7C6 tube at the left front corner of the chassis. The transformer is a separate unit in a heavy iron case, and is usually mounted on the cabinet, with a shielded lead to the chassis. Fig. 2 shows the original circuit.

Your basic trouble is simply too much input from the modern cartridge.

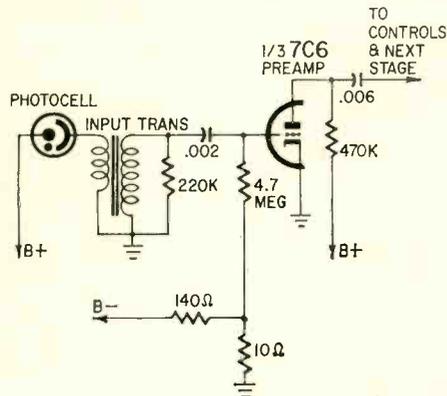


Fig. 2—Original Beam-O-Lite circuit.

The preamp is overloading. (I had the same trouble in several of these sets.) So, just cut the gain down.

If you have a high-output cartridge, skip the preamp entirely and go into the XXFM audio tube (pin 3's the grid). If not, reduce the plate load on the 7C6 preamp. This is 470,000 ohms

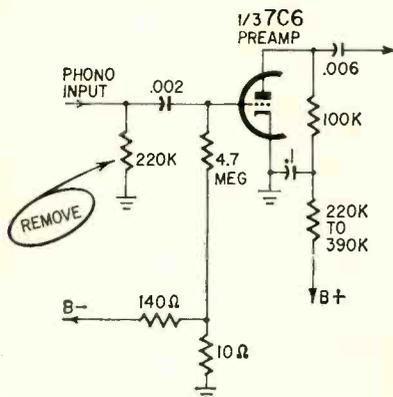


Fig. 3—Changes to original preamp to make is usable with ceramic cartridge.

now. Break this up into two resistors, as shown in Fig. 3, and bypass the junction. This reduces the gain by lowering the plate load resistor.

Watch out for the bias on the 7C6. Its grid returns to a negative point on the voltage divider in the B- circuit, a 140- and a 10-ohm resistor network from center tap of the power transformer secondary to chassis.

The 7C5 tube nearest the oscillator trimmers in the center of the chassis is a supersonic oscillator used to feed the exciter lamp; take it out.

#### Flyback arcing in KCS-68

The anode of the 6CD6 arcs over in an RCA KCS-68C. It won't blow the fuse, but it'll eat up the flyback if I leave it on! I've got -20 volts on the grid of the 6CD6, and all other voltages seem to be OK.—R. C., Philadelphia, Pa.

This could be insulation breakdown in the flyback, since this set runs rather high peak voltages. I'd recommend spraying with an acrylic plastic, using at least three coats, well dried between applications. Or try the High-Voltage Putty insulation made by Colman.

The drive voltage sounds just a little low to me. I'd check the horizontal oscillator, and the settings of the drive and horizontal linearity controls. Adjust

for minimum cathode current on the 6CD6, with a 0-500 dc milliammeter in series with the cathode. Arcing over like this is often due to slight overheating of the flyback, which softens the wax and makes the arcing "easier" for the high voltage.

You might also try one of the "beefed-up" flybacks made by Triad and others. A D-53 fits this set, I think.

#### Intermittent focus and raster

I have an RCA color TV, model 21CD-7999. Everything is fine for a few minutes after it's turned on. Then the screen brightens, gets very reddish and goes out of focus. Now and then it goes completely dark. I can sometimes turn the brightness up and get the picture back.—G. M., Orlando, Fla.

From experience with similar cases, I'd suspect an intermittent damper tube. Also, the reduction of boost voltage, with the decrease in load on the flyback, apparently changes the focus by changing the voltage applied to the focus rectifier. I'm not quite sure about the exact cause of the "red shift," but it probably has something to do with the loss of boost voltage.

Also, you could have a defective red amplifier or green amplifier. Here, the reddish tint would be due to a loss of green, not an increase of red. END

new! easy!  
**AUTOTEXT**  
**IS THE FASTEST**  
**WAY TO LEARN**  
**electronics at home**

SEE RCA INSTITUTE'S AD ON PAGE 77



The Most Trusted Name in Electronics

**No matter what job you have today  
CIE can help you move ahead  
...fast!**



It's a fact. The men holding down high-paying, challenging jobs in electronics have one thing in common . . . they *know* practical electronic theory. And now . . . thanks to Cleveland Institute of Electronics . . . you can join this select group of successful men. First, find "you" in the picture. Second, read about the CIE Program that matches your present occupation. Third, fill out the postage-paid reply card and drop it in the nearest mail box. You'll soon see why modern, effective CIE Home Study has helped thousands move ahead in electronics . . . can do the same for you. But act now. The demand will never be greater for ambitious men who *prepare* themselves for the top jobs in electronics.

**1 Radio-TV Servicemen:** Boost your business fast. Get your Commercial FCC License and service mobile radios used by police and fire departments, taxi and truck fleets . . . also maintain marine electronics, broadcast station equipment, CB, etc. CIE's First Class FCC License program is the quick risk-free way to prepare for the tough FCC exam. Switching to a job in industry? With our comprehensive Electronics Technology program under your belt . . . you're a cinch to get just the one you want.

**2 "Ham" Operators:** Turn that hobby into a profitable profession. Prepare for a rewarding job at one of the country's 5,000 Commercial Radio and TV stations. CIE's Broadcast Engineering program will teach you how to select, use, maintain all types of Radio and TV station broadcasting equipment; also prepares you for the First Class FCC License.

**3 Communications Specialists:** Want a top job with a telephone company, a railroad, a pipeline company or any firm with a big stake in communications? CIE's Electronic Communications program will change that wish to reality. Covers mobile radio, microwave; carrier telephony, too, if you want it. Gets you a Second Class FCC Ticket.

**4 Military Electronic Specialists:** Staying in . . . or getting out, CIE's Electronics Technology program will help nail down your next promotion . . . or land that first high-paying job in civilian life. You'll learn new electronic principles . . . know how to apply them for troubleshooting all types of electronic equipment.

**5 Electricians:** Electronics is here to stay! CIE's Industrial Electronics and Automation program takes the mystery out of "exotic" new industrial control systems, electronic heating and welding, servomechanisms, solid state devices, ultrasonics, X-ray . . . has everything you need to understand your new electronic equipment.

**6 Ambitious Men . . . anywhere:** Electronics is the world's fastest-growing industry . . . a 17 billion dollar business that's grown 400% in the last 10 years. Right now there are thousands of good steady jobs just waiting for trained men. CIE's Electronics Technology program provides

complete understanding of electronics theory and fundamentals . . . prepares you for the First Class Commercial FCC License. Whether you're in Electronics now . . . or just thinking about changing to this exciting career field; whether you work in industry, business, government, or the military . . . this is the program for you.

---

### CLEVELAND INSTITUTE HOME STUDY IS FAST, ECONOMICAL, EFFECTIVE. HERE'S WHY:

**Modern up-to-date material . . . including three exciting new subjects.** Every day . . . the Electronics Industry sees new developments in equipment, design methods, application techniques. CIE lesson material keeps pace. For example . . . our new Troubleshooting lessons give you a fast, systematic method of locating faults on *any* electronic equipment. New lesson material on Transistors covers this vital subject clearly, concisely . . . shows how they work, where and how you use them. And a new Micro-miniaturization lesson describes all types of micro components . . . explains such critical subjects as integrated circuits and microwatt electronics. It's the kind of knowledge you want—the kind of knowledge you'll use!

**An FCC license . . . or your money back.** All CIE Programs (except Industrial Electronics and Advanced Engineering) are backed by our famous Commercial FCC License Warranty: "If you fail the FCC exam for the License specified after completing your program . . . all tuition will be refunded." Compare this to any other FCC License offer. You'll see it's about as close to a sure thing as you'll ever find!

**"Check-point" programmed learning . . . plus FCC Progress Reviews.** CIE Home Study works! You learn at *your* best learning speed. All material comes in small, easy-to-understand segments . . . is "locked-in" by examples, diagrams, explanations. You learn thoroughly . . . and remember what you learn! And FCC Licensing Programs include special Progress Reviews covering hundreds of questions and answers just like those on the FCC License Exam.

**Free nationwide job placement service . . . for life, for every CIE graduate.** Every 60 days . . . while you're a student and after graduation CIE will send you an up-to-date list of many high-paying job opportunities with top companies across the country. We'll also provide you with 200 professionally-prepared resumes to help you land the job you want!

**Thirty years of experience . . . highly qualified instructors . . . accredited.** Since 1934, Electronics home study has been Cleveland Institute's *only* business. Our instructors are experts in electronics and are currently training some 15,500 students. We are accredited by the Accrediting Commission of the National Home Study Council. This Commission has been approved by the U. S. Office of Education as a "nationally recognized accrediting agency" under the terms of Public Laws 82-550 and 85-864.

---

Now is the time  
to make your move in Electronics

Mail Reply Card Today



# Cleveland Institute of Electronics

Dept. RE-95 1776 East 17th Street Cleveland, Ohio 44114

# 26 Heathkit® Values...There Are

**Why Do More People Choose Heathkit Electronics Over Any Other Kit Manufacturer?**


- 1. 8 Great Product Lines To Choose From!** Over 250 kits . . . the world's largest selection! Stereo hi-fi, amateur radio, test & service, marine, laboratory, educational, automotive, home & hobby kits . . . something in every line to fit every need and budget.
- 2. Quality You Can Count On!** Name brand components combined with experienced design to insure up-to-date performance and dependability. The world's most experienced kit engineers, using the latest techniques, develop, produce & test every kit for ease of assembly and highest quality.
- 3. Factory To You Savings!** *No* distributor markups, *no* dealer profits . . . just prompt, to-your-door delivery! You put your money in the product, not its distribution. Add the savings of

"do-it-yourself," and you'll see why Heath is your best buy.


- 4. Fast & Simple To Build!** Every kit is designed with the kit builder in mind. No special skills or knowledge needed. And the famous Heathkit manuals leave nothing to question . . . just clear, non-technical language supported by carefully detailed illustrations. You're assured of professional results!
- 5. Extra Service!** An expert staff of technical correspondents to answer any question about selection, construction and use of your kit . . . factory repair service with original parts should you ever need it . . . time payment convenience with liberal terms and easy monthly payments. Get the complete Heath story including descriptions of all 250 Heathkit products . . . use the handy order form, and send for your Free Catalog now!



## Stereo/Hi-Fi Kits

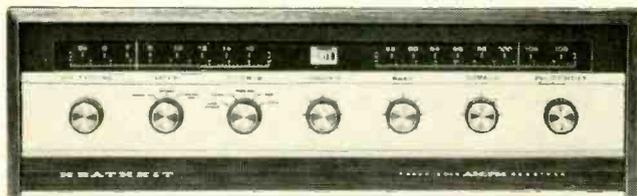


**All-Transistor, AM/FM/FM Stereo Receiver AR-13 . . . \$195.00**—43 transistor, 18 diode circuitry for cool, instant, hum-free operation, plus the quick, uncompromising beauty of "transistor sound." Compact, yet houses two 20-watt power amplifiers (33 watts each, IHF music power), two preamplifiers, and a wide-band AM/FM/FM Stereo tuner. Attractive new "low-silhouette" walnut cabinet. Just add 2 speakers for a complete stereo system. 34 lbs.

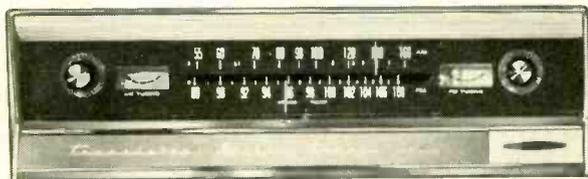

**Deluxe All-Transistor, AM/FM/FM Stereo Tuner AJ-43 . . . \$119.95**—Up to the minute AM, beautifully quiet FM, thrilling natural FM Stereo . . . all reproduced in the exciting new dimension of "transistor sound." Features 25-transistor, 9-diode circuitry, automatic switching to stereo, AFC, stereo phase control, filtered outputs for direct, beat-free stereo recording, and handsome tan vinyl-clad steel cabinet. 19 lbs.




**Matching Deluxe All-Transistor 70-Watt Stereo Amplifier AA-21 . . . \$139.95**—Enjoy the quick, unmodified response of every instrument, each with its characteristic sound realistically reproduced. No compromising! Enjoy 100 watts of IHF music power at  $\pm 1$  db from 13 to 25,000 cps. Enjoy cool, instant, hum-free operation from its 26-transistor, 10-diode circuitry. Simple to assemble. 29 lbs.

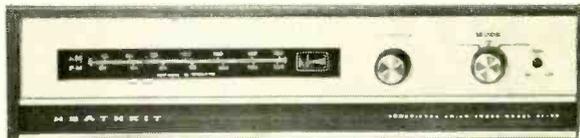


**Low-Cost All-Transistor AM/FM/FM Stereo Tuner AJ-33 . . . \$99.95**—Features 20-transistor, 10-diode circuitry for cool, "hum-free" operation and longer life, built-in stereo demodulator, AFC for drift-free reception, stereo broadcast indicator light, filtered outputs for direct, beat-free stereo recording, concealed secondary controls to prevent accidental system changes, and "low-silhouette" walnut cabinet. 17 lbs.



**Matching All-Transistor 40-Watt Stereo Amplifier AA-22 . . . \$99.95**—Produces a full 66 watts IHF music power at  $\pm 1$  db from 15 to 30,000 cps. Quick, clean, unmodified "transistor sound." 20-transistor, 10-diode circuitry for cool, instant, trouble-free operation and long life. 5 stereo inputs for versatile performance. Concealed secondary controls. Handsome "low-silhouette" walnut cabinet. 23 lbs.

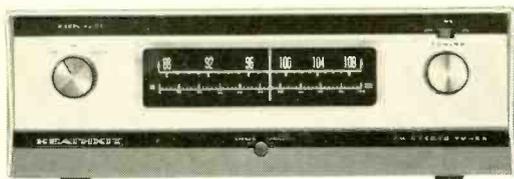

**New FM/FM Stereo "Tube-Type" Tuner AJ-13 . . . Only \$49.95!** Easy to own! Only 3 simple controls to operate. Features built-in FM stereo circuitry, stereo indicator light, automatic frequency control for drift-free reception, flywheel tuning, lighted slide-rule dial, external antenna terminals, preassembled, prealigned "front end," and new mocha brown, beige & black color styling. Matches the AA-32 Amplifier. 16 lbs.

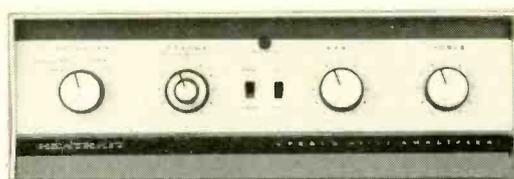

**New 16-Watt "Tube-Type" Stereo Amplifier AA-32 . . . \$39.95!** An inexpensive way to start a modern stereo system in your home. Operates with magnetic as well as ceramic phono cartridges; delivers full power (20 watts IHF) within  $\pm 1$  db from 30 to 30,000 cps; has full-range controls, 4 stereo inputs, 2 four-stage preamplifiers, 2 push-pull power output stages; plus new mocha brown, beige & black color styling. Matches the AJ-13 tuner. 15 lbs.

# 244 More To Choose From!



## Home Entertainment Kits

### Deluxe All-Channel High Fidelity 21" Color TV Set GR-53A . . . \$399.00

—Compares in features & performance to sets costing \$800! Tunes all UHF & VHF channels, 2 thru 83, to bring you sharp, true-to-life color and black & white pictures, plus hi-fi sound. Exclusive built-in self-servicing center . . . allows you to adjust and maintain set yourself. Features high definition 21" color tube with anti-glare bonded safety glass; 24,000 volt regulated picture power; Deluxe Standard-Kollsman VHF tuner with push-to-tune fine tuning & new transistor UHF tuner; 26-tube, 8-diode circuit. All critical assemblies prebuilt & tested! Goes from parts to picture in just 25 hours! Can be wall mounted or installed in Heathkit walnut-finished hardboard cabinet. 1 year warranty on picture tube, 90 days on all other parts. You can't buy a better Color TV set yet this is priced with the lowest! GR-53A, chassis, tubes, mask, UHF & VHF tuners, mounting kit, speaker, 127 lbs. . . . \$399.00 GRA-53-6, cabinet, 52 lbs. . . . \$49.00.


GR-53A  
**\$399<sup>00</sup>**  
(less cabinet)


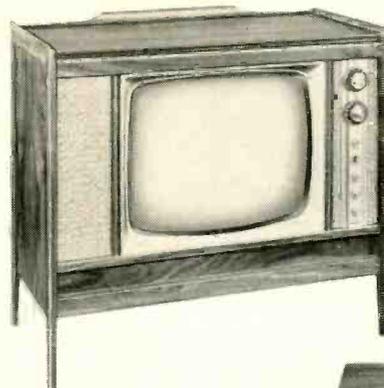
### Deluxe All-Channel Hi-Fidelity 23" Black & White TV Set GR-22A . . . \$199.00

—Features UHF & VHF in one unit for all-channel reception. Exclusive Heathkit advanced TV circuitry for both hi-fi picture & sound. Incorporates the finest set of parts & tubes ever designed into a TV set. Simple to build with all critical circuits factory built & tested . . . assembles in just 12 hours. Can be custom mounted or installed in handsome walnut cabinet (optional). GR-22A, chassis & tubes, UHF, (no mask), 84 lbs. . . . \$199.00. GRA-22-1, walnut cabinet, 66 lbs. . . . \$89.95. GRA-22-2, TV wall mask, 13 lbs. . . . \$25.95.

GR-22A  
**\$199<sup>00</sup>**  
(less cabinet & mask)



1964 Heathkit/Thomas Organ GD-232A . . . \$349.95—Provides the whole family with countless hours of fun, relaxation, entertainment, education, and immeasurable satisfaction. Compares in features to organs costing \$700! Can be built & played by beginners—no special skills or knowledge required! Features 10 true organ voices; new variable repeat percussion that produces additional banjo, marimba, mandolin, balalaika effects; two 37-note keyboards, each ranging C thru C; 13-note heel & toe bass pedals; expression pedal; keyboard balance control; 20-watt peak power amplifier & speaker; transistorized plug-in tone generators; hand-crafted walnut cabinet. GD-232A, 156 lbs. GDA-232-1, walnut bench, 19 lbs. . . . \$24.95.

GD-232A  
**\$349<sup>95</sup>**  
(less bench)



### New! Heathkit Garage Door Opener System GD-20A . . . \$124.90

Automatically opens garage door & turns on light. Easy one-man installation. Operates overhead track, most jamb & pivot doors up to 8' high. Foolproof. Requires no license. Includes pocket-size VHF transmitter with superhet receiver (both factory assembled) plus simple-to-build mechanism. Units also available separately. 69 lbs.

GD-20A  
**\$124<sup>90</sup>**



### New! NELI Transistor Ignition System Kit . . . Only \$34.95—Save \$35!

Features 4-transistor, zener-diode protected circuitry; built-in conversion plug for switching to conventional ignition. Operates on 6 or 12 V. DC pos. or neg. ground system—installs easily on all cars, foreign & domestic. Completely sealed against moisture, corrosion, etc. Simple to assemble . . . everything included. 7 lbs.

GDP-134  
**\$34<sup>95</sup>**



New! Motor Speed Control GD-973 . . . \$17.50—Reduces power tool speed without loss of operating efficiency. Ideal for use with drills, saws, mixers . . . any power tool with a universal AC-DC motor with a rating of 10 amperes or less. Prolongs life of drill bits, blades and other attachments. Has Silicon Controlled Rectifier with feedback circuit that slows motor, yet maintains high torque power! Adjustable speed control lets you dial desired motor speed. 3 lbs.

GD-973  
**\$17<sup>50</sup>**





## Test Instrument Kits

IM-11  
\$24<sup>95</sup>




**World's Largest Selling Vacuum Tube Voltmeter IM-11 . . . \$24.95**—A versatile performer anywhere in electronics! Features a new single AC/Ohms/DC probe; 7 AC, 7 DC, & 7 Ohms ranges; easy-to-read 4½" 200 UA meter; 1% precision resistor for high accuracy; and an extended low frequency response of ± 1 db from 25 cps to 1 mc. Functions include AC volts (RMS), AC volts (peak-to-peak), DC volts, resistance and db measurements. Easy circuit board assembly. 5 lbs. Assembled IMW-11 . . . \$39.95.



IM-13  
\$32<sup>95</sup>

**Deluxe "Service Bench" Vacuum Tube Voltmeter IM-13 . . . \$32.95**—Measures AC volts (RMS), DC volts, resistance & db. Separate 1.5 & 5 volt AC scales for high accuracy; "gimbal" mounting bracket for easy bench, shelf or wall mounting; meter tilts to any angle for best viewing; smooth vernier action zero & ohms adjust controls; large, easy-to-read 6" 200 UA meter; and single AC/Ohms/DC test probe. 7 lbs. Assembled IMW-13 . . . \$49.95.

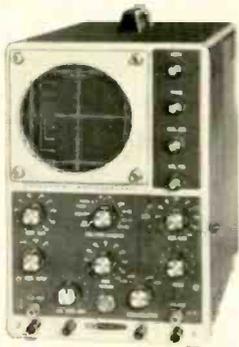

IO-12  
\$76<sup>95</sup>

**Extra Duty Wide-Band 5" Oscilloscope IO-12 . . . \$76.95**—Boasts professional styling & features at low cost! Has 5 mc bandwidth for color TV servicing, famous Heath patented sweep circuit—(10 cps to 500 kc), push-pull vertical & horizontal amplifiers, and two circuit boards & wiring harness for quick, easy assembly. Other features include positive trace position controls, peak-to-peak calibration reference, automatic sync circuit, Z-axis input, 5U1 CR tube, and a husky power supply. Excellent linearity with lock-in characteristics allow stable waveform presentations at upper frequency limits. 24 lbs. Assembled IOW-12 . . . \$126.95.

IG-82  
\$51<sup>95</sup>



**Professional Sine-Square Wave Generator IG-82 . . . \$51.95**—Ideal for any application in service and general laboratory work. Less than .25% sine wave distortion. Less than .15 microsecond square wave rise time. Sine & square wave output available simultaneously. Covers 20 cps to 1 mc in 5 bands. Features exact frequency calibrating system for proper dial tracking. 13 lbs.



IT-21  
\$44<sup>95</sup>

**Quality Heathkit Tube Checker IT-21 . . . \$44.95**—Simplifies servicing . . . eliminates guesswork! Tests all tube types, including new Compactron, Nuistor, Novar and 10-pin miniatures. Features multi-colored "Bad?-Good" meter scale; and constant tension, free-rolling roll chart mechanism. Individual tube element switches protect against obsolescence. Has color-coded wiring harness for fast, easy assembly. Compact size with handy carrying handle make it ideal for field use. 12 lbs.

IG-112  
\$99<sup>00</sup>



**New! Heathkit FM Stereo Generator IG-112 . . . \$99.00**—Produces all signals required for trouble-shooting & alignment of multiplex adapters, FM tuners and receivers. Generates mono FM or composite stereo FM signals. Switch selection of 400 cps, 1000 cps, 5000 cps, 19 kc, 38 kc, plus 65 kc or 67 kc SCA test signals for complete alignment capability. Simple to assemble and operate. 10 lbs.



IG-72  
\$41<sup>95</sup>

**Heathkit Audio Generator Kit IG-72 . . . \$41.95**—Produces near-perfect sine wave audio signals. Less than .1 of 1% distortion between 20 and 20,000 cps. Output level and frequency accurate to within ± 5%. Switch selected output frequencies, 10 cps to 100 kc. Large 4½" 200 UA meter calibrated in volts and decibels. Output attenuator operates in steps of 10 db, and is calibrated in 8 full scale meter ranges. 8 lbs.

## Citizen's Band Kits



GW-42  
\$119<sup>95</sup>



MW-34  
\$89<sup>95</sup>



GW-22A  
\$59<sup>95</sup>



GW-52  
\$74<sup>95</sup>



GW-31  
\$19<sup>95</sup>



HO-13  
\$79<sup>00</sup>

**Deluxe "Master Station" Transceiver GW-42 . . . \$119.95**—Operates "mobile" or "fixed" with built-in 3-way power supply. Other deluxe features include 5 crystal-controlled transmit & receive channels, built-in 4-tone selective call circuitry, all-channel receiver tuning, tuning meter, adjustable squelch, switchable automatic noise limiter. Complete with AC & DC power cables, PTT microphone, and crystals for 1 channel (specify). 23 lbs.

**New Versatility! 2-Way Citizen's Band Radio MW-34 . . . \$89.95**—Provides 5 watts of input power for reliable communications from boat to boat, car to boat, car and home. Features 5 crystal-controlled transmit-receive channels (one transmit crystal on front panel); variable receiving tuning with spotting switch; 3-way power supply (6 or 12 V. DC or 117 V. AC); RF stage for superb reception; and attractive black, white, & blue Heathkit marine styled cabinet. 19 lbs.

**5-Channel Citizen's Band Transceiver GW-22A . . . \$59.95**—Low cost! Ideal for business or personal communications. 5 crystal-controlled transmit & receive channels; superheterodyne receiver with RF stage; built-in squelch & automatic noise limiter; PTT crystal microphone; and crystals for one channel (specify). GW-22A (117 v. AC, less selective call). GW-22D (6 or 12 v. DC, less selective call) . . . \$64.95. 14 lbs. GW-32A (117 v. AC, with selective call) . . . \$84.95. GW-32D (6 or 12 v. DC, with selective call) . . . \$89.95. 15 lbs.

**Powerful 1-Watt "Walkie-Talkie" GW-52 . . . \$74.95 each**—10-transistor, 2-diode circuit; 3-mile inter-unit operation; crystal-controlled transmit & receive; rechargeable \$20 battery; built-in 117 VAC battery charger; FCC license pack; crystals for 1 channel (specify). 4 lbs.

**Deluxe 9-Transistor "Walkie-Talkie" GW-21 . . . \$44.95 each**—1 to 3 mile operation range; portable—battery powered; crystal-controlled transmit/receive; superhet receiver; built-in squelch & automatic noise limiter; crystals for 1 channel (specify). 3 lbs.

**Low Cost 4-Transistor "Walkie-Talkie" GW-31 . . . \$19.95 each**—1-mile operation; crystal-controlled transmitter; super-regenerative receiver; 75 hour operation. Only \$35.00 a pair! No license, forms, tests or age limit. Less battery. Crystals for 1 channel (specify). 2 lbs.

**New! Heathkit "Ham-Scan" Spectrum Monitor HO-13 . . . \$79.00**—Adds "sight" to sounds of amateur radio and CB operations. Operates with virtually all receivers in use today. Monitors up to 100 kc of band spectrum—50 kc on either side of the signal to which you are tuned. Ideal for spotting band openings, checking carrier & sideband suppression, or identifying AM, CW, or SSB received signals. 12 lbs.

Buy Now—Use this Order Blank



### FREE CATALOG

See these and over 250 other exciting Heathkits available in easy-to-build kit form. Save 50% or more by doing the easy assembly yourself! Send for your free catalog today!

Note: All prices and specifications subject to change without notice.

Enclosed find  check  money order.

Please ship C.O.D.

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery.

On Parcel Post orders include postage for weight shown.

All prices are net F.O.B. Benton Harbor, Michigan and apply to Continental U. S. and Possessions only. 20% deposit is required on all C.O.D. orders.

**HEATH COMPANY, Dept. 20-9-1**  
Benton Harbor, Michigan 49023

Please send free Heathkit Catalog.

**ORDER  
BLANK**

Quantity	Model	Description	Wt.	Price Ea.	Total

SHIP VIA:  Parcel Post  Express  Freight  Best Way

Postage

Total

NAME \_\_\_\_\_

(Please Print)

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP NO. \_\_\_\_\_

CL-7/B

# AUDIO EQUIPMENT REPORTS

## Lafayette LA-200 Transistor Stereo Amplifier



THIS IS A HONEY OF AN AMPLIFIER. Small, light, clean-sounding—and absolutely ice-cold. It measures only 13 inches wide by 4¼ high by 9 deep, and weighs less than 14 pounds. There is no apparent rise in cabinet temperature after hours of operation in a warm room.

The LA-200 delivers, at moderate levels, the kind of sound that has come to be associated with good transistor amplifiers (and with many tube amplifiers, too): crisp transients, sharp reproduction of plucked string bass and clear quality of extremely complex sounds, like a full orchestra or a pipe organ playing *fortissimo*. At high levels, the sound muddies up a bit.


Which brings me to my chief criticism: the specifications do not tell all. For one thing, the specified power of 22 watts per channel is IHF music power. Continuous sine-wave power is only about 15 watts at mid-range, tapering off to 10 or less at extremes. Further, the specified power is delivered only into a 4-ohm load, which includes only a few quality speakers. An 8-ohm load cuts the

power approximately in half, and a 16-ohm load about in half again. But I used the amplifier only with 8-ohm speakers on each channel, and the sound, subjectively, was very satisfying.

The probable reason for the big difference between music power and sine-wave power is the absence of a regulated power supply. But that, on the other hand, accounts for the small size and low cost of the amplifier. You can't have it all ways!

One of the most attractive points of the LA-200 is its foolproof output circuit. Go ahead, short the speaker terminals—all day, if you like. The sound "turns funny"—comes and goes intermittently, and the pilot light dims accordingly, but this will go on indefinitely until the short is removed. Egged on by the confidence of the instruction manual, I tried everything I could think of to make the amplifier cry "Uncle!" but it wouldn't.

All controls and switches have an uncommonly smooth feel, as though they are all viscous-damped. The tone controls are "split," as you can see from the photograph (the two leftmost knobs), so that you can adjust bass and treble individually for each channel, to compensate for speaker differences. The switches along the bottom row are all rocker-action types, which is fun. All you have to do is squint and aim a stiff finger at the switch and position you want, and *phfft!*—the volume control is loudness-compensated, or the rumble filter is in, etc.

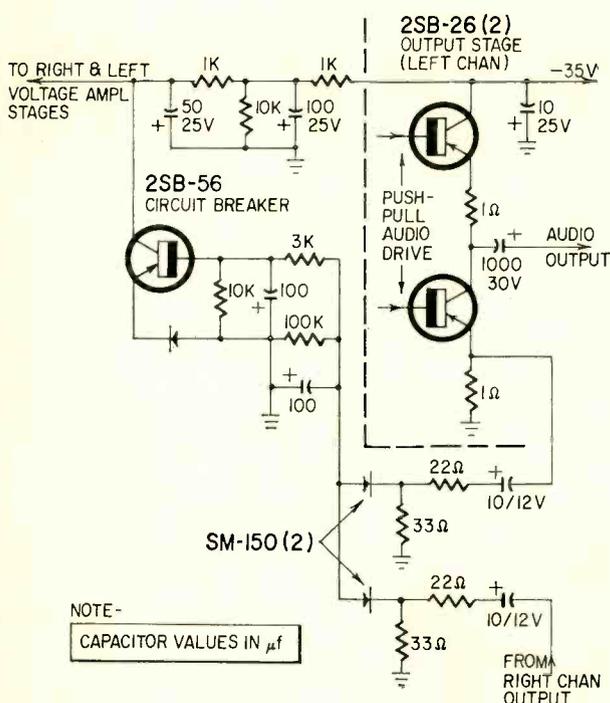

### SPECIFICATIONS

(The manufacturer's)

**IHF Music Power:** 22 watts per channel  
**Frequency response:**  $\pm 1$  db, 20-20,000 cycles  
**Harmonic distortion:** 1%  
**Hum & noise:** Tuner input, -74 db; mag. phono input, -54 db  
**Tone controls:**  $\pm 10$  db  
**Inputs** for tape head, magnetic phono, ceramic phono, tuner and auxiliary high-level source.  
**Outputs** for speaker and tape recorder.  
**Price:** \$109.50

The 2SB-56 electronic circuit breaker in the LA-200 protects output transistor against shorts in the speaker circuit by removing collector voltage from the voltage amplifiers in the first stage of both power amplifiers.

A few things might have been done differently, for my taste (but this is almost carping): The action of the controls, though velvety, is fairly tight, and the knob surfaces are so smooth that my fingers kept slipping a little. Fluted knobs, or ones with a knurled band around them, would probably be just as handsome and a lot easier to grab.

I missed a "mono" position: one in which the channels are tied together for monophonic listening from both channels of a stereo cartridge. That kills a lot of surface noise. Instead, LEFT, RIGHT and REVERSE positions are provided besides the usual STEREO.

The rumble and scratch filters are effective, but a little drastic. There is a very prominent loss of bass and treble, respectively, when they are switched in.

I appreciated the headphone jack on the front panel, with a speaker on-off switch. The speaker phasing switch in back is handy to have, too.

### Technicalia

The output stage of each channel is fairly conventional—a "single-ended push-pull" connection of two p-n-p power transistors. The speaker is connected to the junction of the upper transistor's emitter and the lower's collector through a 1,000- $\mu\text{f}$  capacitor to keep the speaker and the dc operating voltages out of each other's hair. (That 1,000  $\mu\text{f}$  is a bit small for a 4-ohm load, which no doubt accounts for a little falling off of power below 100 cycles.)

The protective circuit is ingenious. It is basically an electronic circuit breaker in the collector supply to the input stage of the left and right power amplifiers. A sampling of each channel's audio is taken from across a 1-ohm stabilizing resistor (see diagram) in the emitter of the lower transistor of each push-pull output pair. This is rectified to a negative dc voltage with respect to ground, and applied to the base of a p-n-p transistor. The emitter of that transistor is grounded through a silicon diode, and its collector is connected to the power supply point for the first "main amplifier" stages.

When the biasing (from the rectified audio signal) exceeds the small forward threshold voltage of the diode and transistor, the transistor conducts, shorting to ground the supply at the point where the collector is connected, and cutting off the sound. This happens only when the audio signal current through the stabilizing resistors (and the voltage across them) is greater than in normal operation at maximum power. It would be if the output terminals are shorted while the amplifier is being driven.

Because of the long time-constant of the protection circuit, the audio comes and goes at regular intervals of about a second until the short is cleared. Works like a charm.—Peter E. Sutheim

# why **two** JFD UHF log-periodic TV antennas?

Because our engineers realize that no single antenna design is the answer to all UHF reception conditions.


UHF frequencies are more adversely affected by surroundings. Degradation due to receiver noise is greater on UHF. Also, UHF signal losses are greater than VHF.

Consequently, our R & D Laboratories in Champaign, Illinois, have developed two new UHF antenna concepts based on the acclaimed patented Log-Periodic formula of the Antenna Research Laboratories of the University of Illinois:

## JFD LPV-U LOG-PERIODIC UHF ANTENNAS

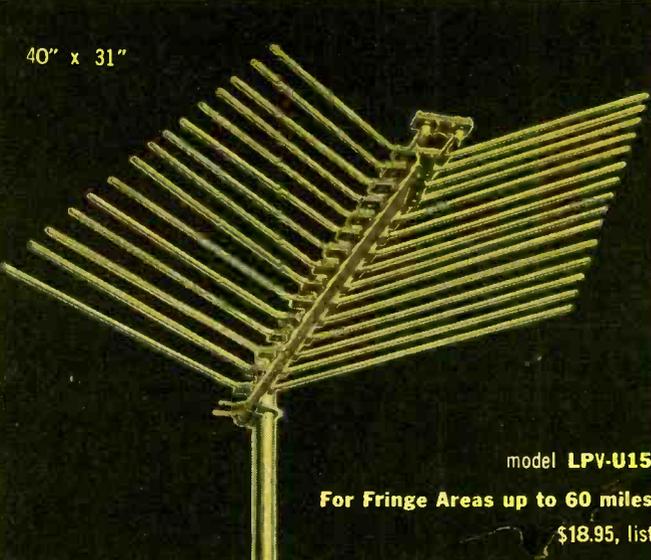**1**

for reception of UHF Channels 14 to 83 and VHF 7 to 13 in cluttered city or hilly areas where high gain and sharp directivity is needed for crisp ghost-free UHF reception in B/W or COLOR!



40" x 31"

model **LPV-U15**  
For Fringe Areas up to 60 miles  
\$18.95, list

26° to 29° narrow "E" plane (horizontal) beamwidths eliminate ghosts resulting from horizontal reflections—and combine with "H" plane (vertical) beamwidth, as low as 40°, to give over-all high gain.

- Exclusive new UHF Log-Periodic frequency independent design provides flat, high gain across the band—excellent 300 ohm match gives below  $\geq 1$  VSWR.
- 30% to 50% more effective gain and directivity than corner reflectors and stacked bowtie-screens on UHF channels 14 to 83—plus a bonus VHF gain of up to 6 db on channels 7-13.
- Inline solid aluminum rod construction for least wind and ice loading area.
- Beautifully gold alodized for lasting eye-appeal.
- 100% pre-assembled—nothing to swing out or tighten—no movable joints.
- Stainless steel take-off terminals.

**2**

## JFD UHF ZIG-A-LOG LOG-PERIODIC UHF ANTENNAS

where the "ultimate" in UHF color, and black and white reception is required.



model **LPV-ZU10** 1-Bay Zig-A-Log \$17.95, list

31" H. x 6" W. x 43" D.

Provides rotator-less reception of stations as far as 48° apart—up to 60 miles distant. (If the LPV-ZU10 receives 707 micro-volts or more signal voltage when pointed directly at each of the stations, then it will receive all stations clearly when pointed toward the center of the group of stations desired. The angle between stations on extreme left and right, however, should not exceed 48°.)

- Gain: 13.5 to 14 db. VSWR; under 1.8:1. 300 ohm impedance.
- Outperforms 8-Bay bowtie-screen reflector antenna
- Ultimate in corrosion-protection: Gold alodized aluminum elements . . . Rohm & Haas Implex & square crossarm . . . stainless steel take-off terminals.



31" H. x 29" W. x 43" D.

model **LPV-ZU20** "E" plane stacked Zig-A-Log array  
\$37.50, list

**TAME**  
KEEP TV FREE

Narrow 25° "E" (horizontal) and 30° "H" (vertical) plane patterns minimize ghosts caused by horizontal and vertical reflections in flat fringe terrain up to 90 miles from transmitters.


- Gain: 16-17 db, VSWR: under 2:1. 300 ohm impedance.
- Today's most powerful UHF array—matches effective gain of large parabolics—with much less wind, snow and ice-loading area.
- Locks on transmitter signal—no need to re-orient.
- Ultimate in corrosion-protection: Gold alodized aluminum elements . . . Rohm & Haas Implex & square crossarm . . . stainless steel take-off terminals.

Whether the location calls for VHF . . . or UHF . . . or FM . . . or VHF/UHF/FM—there is a JFD Log Periodic antenna to suit your installation needs—perfectly.

WRITE FOR BROCHURES 624 & 711 FOR FULL DATA.

BETTER YET, GET THEM FROM YOUR DISTRIBUTOR TODAY!

**JFD JFD ELECTRONICS CORPORATION**  
15th Avenue at 62nd Street, Brooklyn, N. Y. 11219  
JFD Electronics-Southern Inc., Oxford, North Carolina  
JFD International, 64-14 Woodside Ave., Woodside 77, N. Y.  
JFD Canada, Ltd., 51 McCormack Street, Toronto, Ontario,

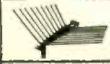FOUR JFD LPV-U LOG-PERIODICS TO CHOOSE FROM:			
Model	Range	Outperforms	List
 LPV-U21	up to 80 miles	12-bay bowtie-screen	\$27.95
 LPV-U15	up to 60 miles	8-bay bowtie screen	18.95
 LPV-U9	up to 40 miles	4-bay bowtie-screen	12.50
 LPV-U5	up to 25 miles	corner reflector	6.95

LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,958,081; 2,985,879; 3,011,168; 3,108,280 AND ADDITIONAL PATENTS PENDING IN U. S. A. AND CANADA. PRODUCED BY JFD ELECTRONICS CORPORATION UNDER EXCLUSIVE LICENSE FROM THE UNIVERSITY OF ILLINOIS FOUNDATION.

# NEW SAMS BOOKS

## Two-Way Mobile Radio Handbook

Newly Revised and Enlarged Edition

by Jack Helmi. Describes and analyzes the latest developments in 2-way communications equipment. The most comprehensive coverage of mobile radio for new buyers, present users, and those interested in servicing this type of equipment. Covers operational theory of basic systems; types of receivers available; transmitters, control systems; power; servicing and maintenance (includes pointers on setting up a mobile-radio service shop). Invaluable for practical understanding of 2-way radio circuitry and equipment. 256 pages; 5 1/2 x 8 1/2". **\$395**  
Order MRS-2, only.

## TV Receiver Tube Usage Guide

by the Howard W. Sams Engineering Staff. Available for the first time—a complete guidebook for TV technicians, listing the tubes, fuses, and semiconductor diodes required to repair individual TV models. Receivers are listed by manufacturer, chassis and model numbers—data provided tells you exactly what to take along to repair a specific set. Covers over 25 different manufacturers of hundreds of TV models (including color receivers). Tubes and functions are listed for each model, along with fuses and diodes used. This real time-saver belongs in every tube caddy and on the workbench. 96 pages; 5 1/2 x 8 1/2". Order TUR-1, only. **\$195**

**ONLY COURSE OF ITS KIND**  
5-Volume HOWARD W. SAMS

**Basic Electricity/Electronics**

New, unique positive training worth hundreds of dollars. First completely new course to be published in the last 10 years...using the latest programmed method for quick, effective learning.

Vol. 1. Basic Principles & Applications  
Vol. 2. How AC & DC Circuits Work  
Vol. 3. Understanding Tube & Transistor Circuits  
Vol. 4. Understanding & Using Test Instruments  
Vol. 5. Motors & Generators—How They Work

(Complete Set contains over 1300 pages; 1250 illustrations; 51 chapters; in sturdy slipcase)  
Order EGY-50, only. **\$1995**

## Technical Writer's and Editor's Stylebook

by Rufus P. Turner. The first practical and complete guide for technical writers and editors. Describes the fundamentals of technical writing for magazine articles, books, reports, etc. Explains in text and examples the basics of good writing techniques; use of tech symbols, mathematics, technical phraseology, punctuation, capitalization, prefixes and suffixes, devices for emphasis, etc. Tells how to prepare an outline, how to ready a manuscript for publication. Has appendices showing symbols from various technical fields. An invaluable reference for writers in any technical field. 192 pages; 5 1/2 x 8 1/2". **\$395**  
Order TWS-1 (softbound), only.

Order TWH-1, (hardbound), only. **\$4.95**

## Handbook of Algebraic & Trigonometric Functions

by Allan Lytel. A complete selection of basic formulas and tables of mathematics at the high school and beginning college level. The first part of the book includes formulas for geometry, algebra, trigonometry, and calculus; the second part is devoted to 24 sections of mathematical tables and conversions. An extremely practical reference for students, technicians, and engineers. 160 pages; 5 1/2 x 8 1/2". Order ALG-1, only. **\$295**

## Replacement Guide for TV & Auto Radio Controls

Vol. 6. Bigger and better than ever—covers over 38,000 TV and 1500 auto radio models. Lists recommended replacement controls made by Centralab, Clarostat, CTS-IRC, and Mallory. 192 pages; 8 1/2 x 11". Order RGC-6, still only. **\$100**

## HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. RE-9, 4300 W. 62nd Street, Indianapolis, Ind. 46206

Send me the following books:

- MRS-2  EGY-50  TWH-1  RGC-6  
 TUR-1  ALG-1  TWS-1

\$ \_\_\_\_\_ enclosed.  Send FREE Booklist

Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

My Distributor is \_\_\_\_\_

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7
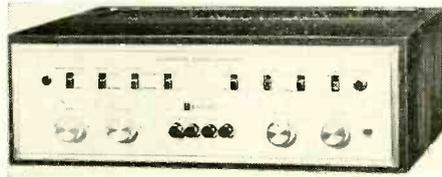
## Knight KN999 All-Transistor Integrated Stereo Amplifier

THE "INTEGRATED" COMBINATION OF preamp and amplifier in a single package dominates the hi-fi market so completely that most manufacturers no longer offer independent amplifiers and preamps.



### SPECIFICATIONS

(All specifications are the manufacturer's)

Power output: 100 watts IHF. Each channel 50 watts; 35 watts per channel continuous sine wave.

Frequency response:  $\pm 1/2$  db, 20-25,000 cps.

Harmonic distortion: 1%.

Hum & noise: -80 db, tuner and aux.; -65 db, phono and tape inputs.

Sensitivity: 0.1 v, tuner and aux.; 2.5 mv tape; 2 mv phono inputs, for full rated output power.

Outputs: 4, 8, 16 ohms per channel to speakers; hi-z center channel; hi-z to stereo recorder; lo-z to stereo headphones.

Dimensions: 4 1/2 x 13 7/8 x 12 3/4 inches

Weight: 20 lb

Price: \$179.95 less case

With rare exceptions, integrated units have failed by several notches to meet the standards of fidelity the state of the art permits, and which are often met by even moderately priced combinations of independent units. Power output has been low, and often only half the rated power has been available at high and low ends of the audio range. Distortion has been high, especially at the bottom end, and transient response poor. Even the best never crossed the line that separates the merely good from the superb.

It is in upgrading this type of equipment that the transistor can make its greatest contribution, as the Knight KN999 amplifier admirably shows.

Capable of delivering 35 watts sine-wave power per channel, the KN999 is one of the two or three most powerful integrated units on the market. It delivers nearly full output over the full audio range—down less than 1/2 db at 20 and at 20,000 cycles. Harmonic distortion at maximum output averages 1% over the whole range; IM distortion is just over 2%. In terms of measured characteristics, the amplifier misses the top rung in only one respect: distortion is almost as high at low levels as at maximum output.

But that seems to be true of almost all transistor amplifiers, and seems to be the price we have to pay, at present, for the benefits transistors bring. The low-level distortion is not too much higher than in comparable tube type integrated units, and the benefits more than compensate.

This is the first integrated amplifier I have used which gives a "big amplifier" sound. Transient response is superb, the reproduction of the bass instruments awe-inspiring, and the definition of detail notably superior.

The control facilities are elaborate. I commend especially the use of push-buttons for selecting input sources—not only simpler and more convenient than a rotary switch, but less likely to produce transistor-destroying and ear-annoying transients. There are only four knobs on the panel: BASS, TREBLE, BALANCE and LOUDNESS. The bass and treble controls for both channels are ganged. Eight slide switches control power, choice of mono or stereo, channel reverse, phase reverse, high- and low-cut filters, loudness compensation and tape monitoring. The two high-level inputs (tuner and auxiliary) have ganged input level controls. There is a high-impedance center-channel output jack to feed another amplifier for center-channel fill, or to provide monophonic sound (via an additional amplifier) for remote speakers. A jack on the front panel accommodates low-impedance stereo headphones. There are phono jacks in back for tape output.

The circuitry is simple, compared to many other transistor amplifiers. Two transistors in a feedback pair, with equalization in the feedback loop, constitute the low-level preamp section of each channel. Loudness compensation, high-cut and low-cut filters are simple passive R-C networks. An emitter follower feeds the bass and treble tone-control networks, similar to the tube type Baxandall circuit (also included in a feedback loop).

A driver feeds the "single-ended push-pull" output stage through a transformer to provide balanced input. Four transistors are used in each output stage. They are protected against excessive drive by shunt diodes at the input. The feedback loop goes from the output to the emitter of the driver stage. The voltage to the low-level stages is regulated by a series transistor regulator.

The power transformer has a tapped primary with 117- and 127-volt inputs. It arrives with the line connected to the 127-volt tap. This provides considerable protection against high line-voltage surges. In locations where the line voltage is below 120, the amplifier will not deliver its full rated output power as it comes. The input can, however, be shifted to the 117-volt tap.

A thermal circuit breaker breaks the power circuit if the ambient temperature rises to the danger point.

Two ac outlets controlled by the power switch are available at the rear so a tuner, tape recorder or whatever can be turned on and off along with the amplifier.—Joseph Marshall

Exclusive with **RCA** ...

# AUTOTEXT

## new, faster, easier way toward a career in electronics

**EXCLUSIVE WITH RCA.** "AUTOTEXT", developed by RCA and introduced by RCA Institutes, Inc. is a system of programmed instruction, a method of learning proved with thousands of students. This beginning course in electronics is accurately planned so that as you read a series of statements, questions, and answers, you learn almost without realizing it. It's fast! It's easy! It's fun!

**BEGIN NOW WITH RCA "AUTOTEXT".** Now you can start your home training the amazing new RCA "AUTOTEXT" way. And, you get a complete set of theory lessons, service practice lessons, experiment lessons, and all the kits you need. Because "AUTOTEXT" has been designed to help you master the fundamentals of electronics more quickly, more easily—almost automatically—you'll be ready to go on to advanced training in electronics sooner than you ever thought possible.

**STUDENT PROVED.** Prove it to yourself as others throughout the country are now doing. An interest or inclination in electronics is all you need. RCA "AUTOTEXT" helps you to do the rest. The future is unlimited. The jobs are available! The important thing is to get started now.

### CLASSROOM TRAINING ALSO AVAILABLE

RCA Institutes Resident School in New York City and RCA Technical Institute in Cherry Hill (near Camden), New Jersey offer training that will prepare you to work in rewarding positions in fields such as automation, communications, television, computers, and other industrial and advanced electronic applications. You are eligible even if you haven't completed high school. Check Classroom training and information will be rushed to you.

### Complete Selection of Home Training Courses.

- Electronics Fundamentals (also available in Spanish)
- TV Servicing
- Color TV
- Transistors
- Communications Electronics
- FCC License Preparation
- Mobile Communications
- Drafting
- Computer Programming
- Automation Electronics
- Industrial Electronics
  - Automatic Controls
  - Industrial Applications
  - Nuclear Instrumentation
  - Digital Techniques

All RCA Institutes Home Training Courses are complete step by step easy-to-understand units. You get prime quality equipment in the kits furnished to you to keep and use on the job. In addition, RCA's liberal tuition plan affords you the most economical possible method of home study training. You pay for lessons only as you order them. If you should wish to interrupt your training for any reason, you do not owe one cent. Licensed by the N.Y. State Department of Education. Approved for Veterans.

**Send postcard for free illustrated book today!**  
**Specify home training or classroom training!**


**RCA INSTITUTES, INC., Dept. RE-94**  
350 West 4th St., New York 14, N. Y.



**THE MOST TRUSTED NAME IN ELECTRONICS**

# CASTLE

NEW  
EASTERN  
LOCATION

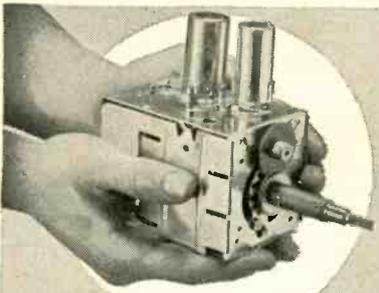

ALL MAKES  
ALL LABOR  
AND PARTS  
(EXCEPT TUBES)\*  
**9.95**  
ONE PRICE  
ONE LOW PRICE INCLUDES ALL UHF  
VHF AND UV COMBINATION\* TUNERS

**Fast Service . . .** Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint.

**90 Day Warranty**  
Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

**CASTLE TV TUNER SERVICE, INC.**  
5715 N. Western Avenue, Chicago 45, Ill.  
New Eastern Location  
41-96 Vernon Blvd., Long Island City 1, N.Y.  
In Canada: 136 Main St., Toronto 13, Ont.  
\*Major Parts are additional in Canada

**QUANTITY TUBE BUYERS  
GET RAD-TEL'S QUALITY  
BRAND NEW TUBES**

YOUR  
CHOICE  
**1B3-1G3  
1K3-1J3  
FREE!**

UP TO  
**75%  
OFF** \*  
\*Mfrs.  
sug.  
list  
price

WITH THE  
PURCHASE  
OF EVERY  
10 TUBES!

**Money Back Guarantee**  
Tubes branded and  
boxed Rad-Tel


Type Price	Type Price	Type Price
024 .79	6AV6 .41	6W4 .61
1B3 .79	6AX4 .66	6X8 .80
1R5 .77	6BE6 .55	7AU7 .65
1X2 .82	6BG6 1.70	12AD6 .57
2BN4 .64	6BN4 .62	12AT7 .76
3BZ6 .56	6BN8 .76	12AU7 .61
3CB6 .56	6BO6 1.12	12AV6 .41
3V4 .63	6BT7 1.00	12AX4 .67
4BQ7 1.01	6CS9 .95	12AK7 .63
5AT8 .83	6CB6 .55	12AZ7 .86
5CG8 .81	6CC7 .61	12BA6 .50
5CL8 .76	6CL6 .94	12BE6 .53
5U4 .60	6CY5 .70	12BH7 .77
5U8 .84	6D06 1.10	12BL6 .56
5Y3 .46	6EA8 .79	12BY7 .77
6AF4 1.01	6I6 .71	12SK7 .95
6AH6 1.10	6K6 .63	12SQ7 .91
6AK5 .95	6L6 1.06	25BQ6 1.17
6AL5 .47	6S4 .52	25L6 .57
6AN8 .78	6SL7 .84	35C5 .51
6AN8 .93	6SN7 .65	35W4 .42
6A05 .53	6SQ7 .94	35Z5 .60
6A55 .60	6T8 .85	50C5 .53
6AU4 .85	6U8 .83	50L6 .61
6AU6 .52	6V6 .54	

TERMS: 25% deposit on all orders  
balance COD. Orders under \$5 add  
\$1 handling charge plus postage.  
Orders over \$5 plus postage.


**RAD-TEL TUBE COMPANY**

Dept. RE, 55 Chambers Street, Newark, N. J. 07105

## test equipment reports

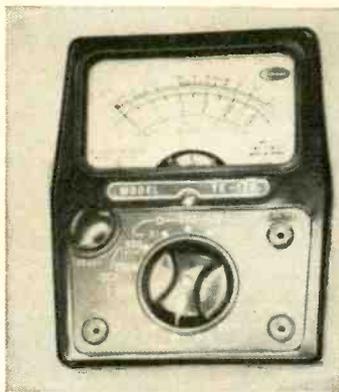

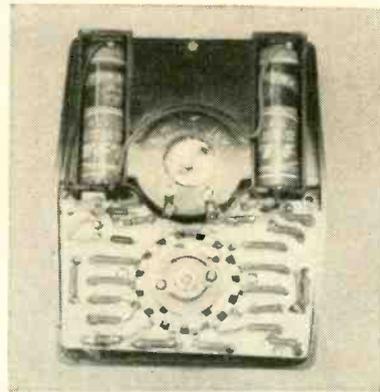Olson TE-179 multimeter is flat and compact.



Every inch of space inside case has been used intelligently.

### Olson TE-179 30,000-ohm-per-volt Multimeter

A TRULY VERSATILE POCKET-SIZED VOM is always good news. With the Olson TE-179, which has ranges from 0.25 to 1,000 volts dc, you can measure low base-to-emitter potentials or high plate voltages—at 30,000 ohms per volt,  $\pm 3\%$  of full scale.

Ac ranges are from 10 to 500 volts, in four ranges, at 12,000 ohms per volt,  $\pm 4\%$  of full scale.

Twenty-five years ago, 1,000 ohms per volt was the common meter resistance. Advances in electronics have demanded higher and higher meter sensitivities. Most of this is due to the smaller tolerances allowed—20% resistors were good enough for radio receivers. Now 5% resistors are used in some TV circuits and 1% components are found in many nonentertainment electronics devices.

The additional current drain caused by putting test prods across a resistor can make a circuit inoperative during the test and indicate trouble where there is none. It can cause completely erroneous meter readings.

High-sensitivity meters reduce the loading on a circuit. For example, any 20,000-ohm-per-volt meter will draw 50  $\mu$ a for a full-scale reading on any range of 1 volt dc or higher. At 30,000 ohms per volt the current drawn by the meter drops to 33  $\mu$ a.

The pocket-sized Olson TE-179 is not much larger than most transistor radios. At  $4\frac{1}{8}$  inches high,  $3\frac{1}{2}$  inches wide and  $1\frac{1}{16}$  inches thick it is smaller than many.


The 18 basic ranges can be increased to 22 by using the furnished tables and charts. These add three db ranges and one for capacitance measurement from .001 to 0.2  $\mu$ f.

Capacitance is measured by using a 10-volt source and the 10-volt ac range on the meter. For most accurate readings the 10-volt ac source should be adjustable—it is set for a full-scale reading with the circuit completed. Just like zeroing an ohmmeter.

The circuit is then opened and the capacitor connected into it. Read the meter and look up the reading on the chart.

Keeping semiconductor testing in mind, the manufacturer even gives a basic schematic showing the polarity of the voltage at the test prods in the ohmmeter ranges. This is also important when checking circuits containing electrolytic capacitors—particularly those with low working voltages. The ohmmeter circuit is powered by two 1.5-volt penlight cells.

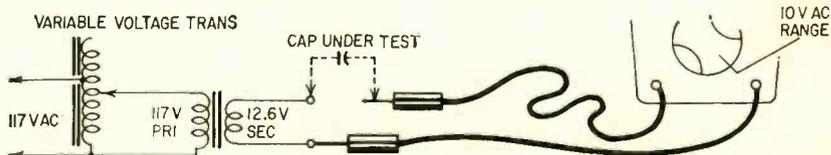The instruction manual contains many other items on how to get the most use from this high-sensitivity handul. It costs \$13.92.—Elmer C. Carlson



The Olson TE-179 measures capacitors by reading ac voltage passed by capacitor in series with external ac source. Meter reading is converted to capacitance with help of chart supplied.

*Hickok 235A Vhf/Uhf  
Field Strength Meter*



Hickok's new 235A field-strength meter is a compact, battery-operated instrument, using a 3A5 twin-triode tube. Like the new TV sets, it's "all-channel", covering vhf and uhf. It's a superheterodyne, with a crystal mixer; half the 3A5 is used as an oscillator; the other half is a superregenerative i.f. amplifier at 40 mc.

The i.f. amplifier works in the logarithmic mode; its plate current varies in proportion to the *logarithm* of the signal voltage on its grid. This gives a logarithmic scale on the meter, which is a 200- $\mu$ a unit connected in a bridge circuit in the plate of the i.f. tube.

The amplitude of the superregenerative oscillation is adjusted to zero the meter. Two variable inductances are used: a coarse adjustment, inside the case, and the fine adjustment on the panel, marked ZERO ADJUST. Hickok claims  $\pm 3$ -db accuracy on the vhf bands and +6, -2 db on uhf. Most of the error will be at the ends of the scale; accuracy is very good in the most-used center part.

Power comes from a 90-volt B-battery and two 1.5-volt A batteries. Since the plate current is in microamps, battery life should be good. An NE-51 neon lamp on the panel is used as a pilot light and battery-condition indicator. It's also the voltage regulator! Connected in the meter circuit, the firing voltage of the lamp regulates the plate voltage of the i.f. tube and the bridge. (Neon lamps have firing voltages between 60 and 70 volts, due to manufacturing tolerances. The maker will supply replacement lamps with the correct voltage on request. This is stamped inside the case near the NE-51 socket.)

The meter has three scales: low vhf, high vhf and uhf. Center-scale on the low band is 1,000  $\mu$ v, on the high vhf band 100  $\mu$ v, and on uhf, about 800  $\mu$ v. The first calibration mark (at the left) is 10 on vhf and 30 on uhf. This puts the most-used parts of the scale in the most accurate place, near the center. In strong-signal areas, and in community-antenna work, where signal

strengths in thousands of microvolts must be measured, simple resistive pads will bring the readings back to center. A 20-db pad will multiply all readings by 10, and a 40-db pad by 100. Resistor values for making these pads are given in the instruction book.

The 235A has 75-ohm input, through an auto-radio type coaxial jack on the panel. A CM-1 "Calimatch" balun transformer is mounted inside the lid, for 300-ohm inputs. It connects to the 75-ohm input through a short coax link furnished with the instrument. A calibration chart printed inside the lid gives correction factors. On vhf these are very small, but they should be used on uhf for maximum accuracy.


A highly selective input filter gives maximum image rejection on vhf. On uhf, this filter is designed to give the best impedance matching, with a slightly lower image-rejection ratio. Some spurious responses may be found, but they can usually be identified as coming from strong vhf signals. Calibration is extremely close and the tuning is sharp, even on strong signals. An earphone jack on the panel can be used with crystal phones to identify sound and picture carriers, or noise.

The only unfavorable reaction I got on this instrument was from the thumb-screw terminals on the Calimatch balun transformer; they're hard to get at. However, a short piece of 300-ohm ribbon with a two-terminal block on the end, permanently attached, would solve that.

A very clearly written instruction book is furnished. Read it carefully before you use the instrument. That applies to all of 'em, though!

A field-strength meter was a very valuable instrument back in the 'good old days', and if uhf gets going, it will be again. We'll be back on the roofs running up and down hunting for signals, and the fastest way of finding a uhf signal, with its many peculiarities, is a probe antenna and a good uhf field-strength meter.

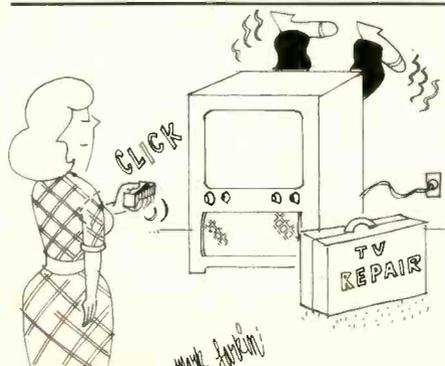The meter (price \$229.50) is housed in a durable metal case with a handle, and should be easy to work on a roof. Construction (I peeked!) is excellent—well shielded and sturdy.—  
*Jack Darr*



**Add to Your Profits in  
Radio-TV Repairs with**

**PROFESSIONAL  
APPLIANCE SERVICING**

**Learn easily, quickly with  
NRI's new course**

Appliance Servicing is a natural, profitable side-line for Radio-TV Repairmen. The boom in electric appliances means greater profits for you. There are probably hundreds of broken appliances right in your neighborhood.

Free book tells you about profitable opportunities for you to increase your income *fast*.

NRI, the world-famous home study school, now offers a *new, low-cost course* to prepare you quickly for extra profits. Training includes appliance test equipment and covers—

- Small and Large Home Appliances
- Farm and Commercial Equipment
- Small Gasoline Engines

—there is even a special course arrangement to learn air conditioning and refrigeration.

*If you are in business for yourself, course costs can be tax deductible.*

Send for FREE book describing opportunities and details of course—plus a sample lesson. There's no obligation and no salesman will call. Send coupon below or write:

Appliance Division, Dept. 503-094  
National Radio Institute  
Washington, D.C. 20016



Send for  
**FREE  
BOOKS**

Appliance Division, Dept. 503-094  
National Radio Institute  
Washington, D.C. 20016

Please send Free Book on Professional Appliance Servicing and Sample Lesson.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_

State \_\_\_\_\_

Accredited Member National Home Study Council



## The Photophone In Your Future

continued from page 33



From TAME Magazine—a parody of TIME—published Christmas, 1944. A more up-to-date version of the Picturephone, then called Teleview, as illustrated here. Note the microphone and speaker. Meraki permits dialing from a distance of 10–25 feet. Another Meraki [Menos (mind)—radio—kinetics] is worn on the head of the person using the instrument. His brain waves operate the Meraki transmitter, signals from which dial the telephone. The girl's bald head is a proposed hygienic development, supposedly to come by 2044.

cago and Washington, and \$27 between Chicago and New York.

These rates, in the foreseeable future, will naturally come down and will, in all probability, with electronic advances, approach the prevailing long-distance phone charges.

What about other foreseeable necessary technical advances of the future? Ralph in the story spoke of a *Language Rectifier*. A great deal of work on this internationally necessary invention has already been accomplished by scores of laboratories all over the world. We would be surprised if the problem were not solved by 1975, at the present rate of progress of the electronic computer.

Probably the next requirement is 3D or three-dimensional TV. We have mentioned this at length and frequently on this page. Anyone who has ever watched a baseball game or other sports has been struck by the inadequacy of the two-dimensional, flat TV picture of our present-day sets. Technicians and inventors know that 3D will be achieved without question in the future. Our own guess: The solution most likely may lie in a *multiple transparent screen* that will show the picture in depth, perhaps with a plurality of split cathode rays.

Finally, the perfected Picturephone, to be universally acceptable, must of necessity be *in full color*.

We can see a vast and unbelievable expansion of the future Picturephone as a shopping instrumentality alone. Here is why:

Shopping today is a major chore—and it will be worse in the future—because of our totally inadequate streets, over-

crowded stores, impossible traffic, time loss and general frustration in shopping from store to store.

In the future you will be shopping by Picturephone while you stay either home or at your office. If you are a man, let us say, and you wish to buy a number of ties, you can do it in minutes, thanks to the color Picturephone. You will see everything you buy in full natural colors. If your wife wants to buy a dress or a pair of slacks—she sees them in the real colors. Or she may want to buy a rug, a pair of shoes or what not. *Now she sees what she buys*, without any guesswork. Most of the frustration is now eliminated.

All this, however, is only a single application of the Picturephone.

There are literally thousands of other uses: “Whenever it is too difficult; too dangerous; too expensive; too inconvenient; too inaccessible; too far; too hot; too cold; too high; too low; too dark; too small to observe directly—use television,” says an excellent book, *Television in Science and Industry*, written in 1958 by V. K. Zworykin, famed inventor of the iconoscope and the kinescope. And, we might add, *don't overlook the hundreds of new uses of the finally improved future Picturephone.\**

Finally and parenthetically, may we delicately but firmly point out one fact to the wildly perturbed lady columnists who, lately *en masse* have denounced the perfectly innocent Picturephone as a nasty electronic ogre and a horrible example of a new infraction of woman's privacy.

The simple technological fact is this: No one, least of all the Picturephone, could possibly intrude on your privacy, unless you want it to. There is a button or a switch you must press first to become visible to a caller.

No press, no see! See!

—H.G.

\*See also the long list of industrial and other uses in *Atypical Television, Radio-Electronics*, October, 1958.

# EIGHT

## INSTRUMENTS IN ONE



- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker

**Transistor Analyzer Model 212**  
 Factory Wired & Tested — \$18.50  
 Easy-to-Assemble Kit — \$13.50

**YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS!** All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

**Features:**  
 Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.  
 Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me **FREE** catalog of the complete value-packed EMC line, and name of local distributor.

NAME \_\_\_\_\_ RE-9


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

## EMC

**ELECTRONIC MEASUREMENTS CORP.**  
 625 Broadway, New York 12, New York  
 Export: Pan-Mar Corp., 1270 B'way, N.Y. 1

# SOLDERING TIPS FOR HI-FI KIT BUILDERS

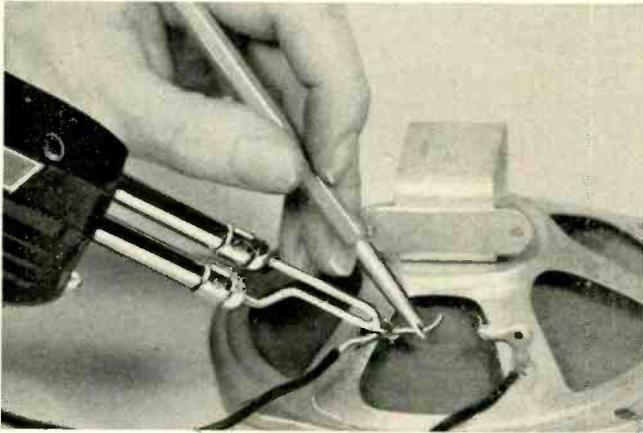

## POSITION AND HOLD WIRE

Joint must remain perfectly still until solder sets. An easy way to accomplish this is to hold the wire with a soldering aid. Blowing on solder will speed setting.



## USE PROFESSIONAL EQUIPMENT


Virtually all radio and TV servicemen use Weller Dual Heat Soldering Guns. A Weller Expert Soldering Gun Kit includes everything you need for strong, noise-free connections.

A Weller Dual Heat Gun is indispensable in electronic soldering. Heat and spotlight come on instantly when trigger is pulled. 2 trigger positions let you switch instantly to low 100-watt or high 140-watt heat. Low heat prevents damage to components and prolongs tip life. High heat is ready when you need it.

Kit includes gun in plastic utility case, 3 tips, tip wrench, flux brush, soldering aid and solder. Model 8200PK \$8.95. Weller Electric Corp., Easton, Pa.

**Weller**


WORLD LEADER IN SOLDERING TECHNOLOGY

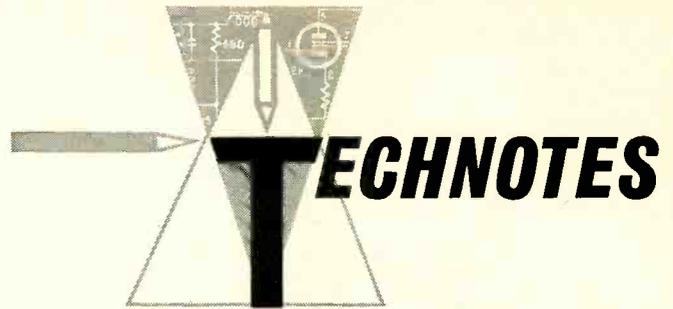
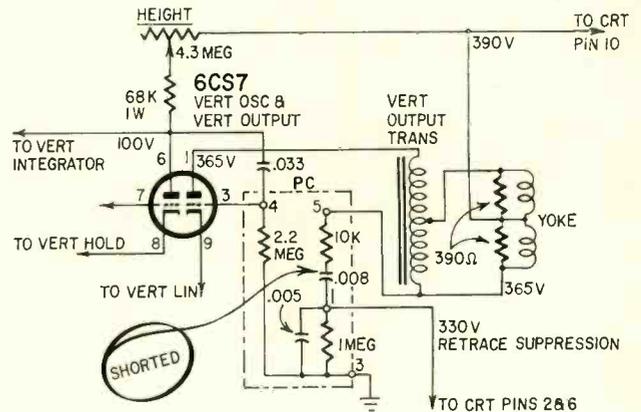
## PHILCO 9L41U—UNCONTROLLABLE BRIGHTNESS

In this set brightness was always maximum; the control had no effect. CRT checked OK. Retrace lines were visible.

Voltage measurements showed nothing unusual until I came to pin 1 of the printed-circuit R-C network: 330 volts. This was being applied directly to the CRT control grid, causing the brightness trouble. The cause (see schematic) was a shorted .008- $\mu$ f capacitor in the R-C network. In the




Philco 8L41, -42, -43 and "U-suffix" versions, as well as in the 8P51A-U, this capacitor is .005  $\mu$ f.

You don't have to order a new circuit plate to restore normal operation. Cut away terminal 5 completely. Solder a .008- $\mu$ f 600-volt (or higher) capacitor to No. 1, and substitute one end of a 10,000-ohm  $\frac{1}{2}$ -watt resistor for pin 5. Connect the free ends of these two parts together, running one around each side of the circuit plate.—*Roberto Abrego*
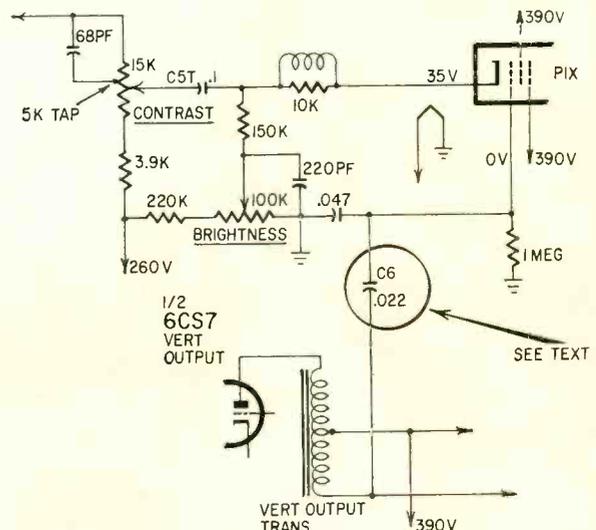
## PHILCO 7L40

*Complaint:* Brightness control has no effect.

Video output was normal. C5T and brightness control



resistance were all right. But the CRT cathode measured 390 volts instead of 35, and the No. 1 grid showed 390


instead of zero.

The trouble was caused by a shorted C6 (circled on schematic below). Replacing it (with a 600-volt unit) cleared the trouble.—Tom Horiuchi

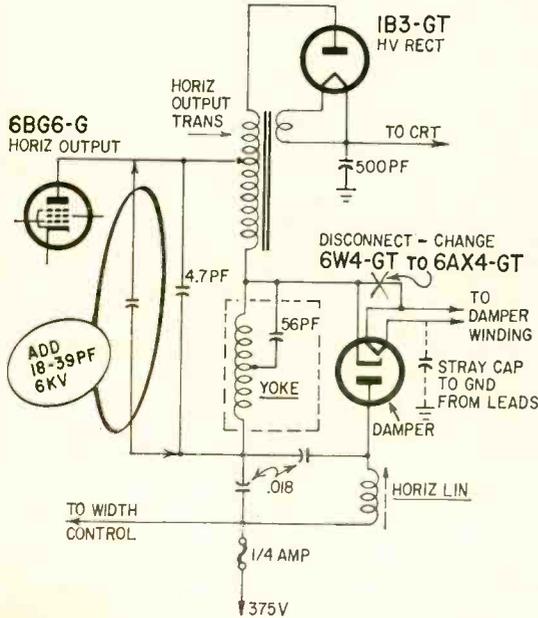**RCA KCS-49A: INSUFFICIENT WIDTH**

The picture was narrow by about 3 inches on each side, and the trouble was due to stray capacitance from the damper-tube heater lead to ground, as well as in the transformer. This bypassed to ground some of the energy that should have gone to the yoke. The overall efficiency of the sweep system had deteriorated.

Here's what we did. We disconnected the wire from heater to cathode of the 6W4-GT, thus isolating the stray capacitance. The 6W4-GT was changed to a 6AX4-GT to forestall heater-to-cathode arcing.




Adding about 39 pf (at 6 kv) across the flyback and yoke windings as shown in the diagram decreased high voltage somewhat and increased the width. Use the smallest possible capacitor for this job.

Also see page 38 of the June 1959 issue of RADIO-ELECTRONICS for more on this subject.—Warren Dere

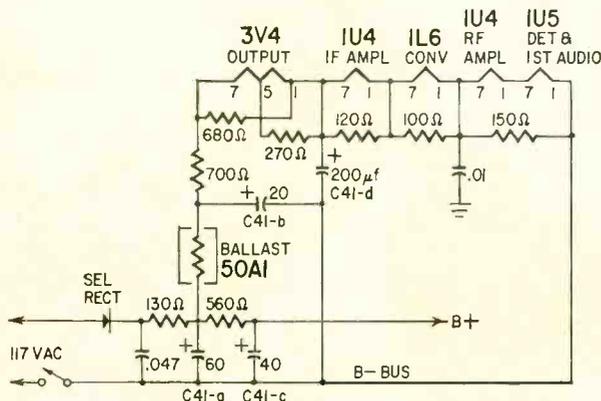**ZENITH T600 PORTABLE RADIO**

In this set, the 1L6 converter tube failed too often. It lit up like a Christmas tree every time the set was turned on.



Strangely, removing all the rest of the tubes did not change the situation—even though this is a series filament string.

Turned out finally that poor filter capacitors let high ac ripple pass through the string. A new four-section capacitor (C41) solved the problem.—Tom Horiuchi

END

**BECOME A RADIO TECHNICIAN**

for only \$26.95

**BUILD 20 RADIO**

**CIRCUITS AT HOME**

with the New Progressive **RADIO "EDU-KIT"®**

Reg. U.S. Pat. Off.

**All Guaranteed to Work!**

**PRACTICAL HOME RADIO COURSE** only **\$26.95**



**NOW INCLUDES**

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ AMPLIFIER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

TRAINING ELECTRONICS TECHNICIANS SINCE 1946

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

**FREE EXTRAS**

- SET OF TOOLS
- RADIO & ELECTRONICS TESTER
- ELECTRIC SOLDERING IRON
- TESTER INSTRUCTION MANUAL
- MEMBERSHIP IN RADIO-TV CLUB
- CONSULTATION SERVICE
- HI-FI GUIDE
- QUIZZES
- TV BOOK
- FCC AMATEUR LICENSE TRAINING
- RADIO BOOK
- PRINTED CIRCUITRY
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- CERTIFICATE OF MERIT
- VALUABLE DISCOUNT CARD

**WHAT THE "EDU-KIT" OFFERS YOU**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. This kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements. You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and lay out radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay, only \$26.95 complete.

**THE KIT FOR EVERYONE**

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

**PROGRESSIVE TEACHING METHOD**

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques gradually, and a progressive manner and at your own rate. You will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are 20 Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector, Square Wave Generator and Amplifier circuits. These are not unprofessional "bread board" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory; troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

**THE "EDU-KIT" IS COMPLETE**

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manual, hookup wire, solder, selenium rectifiers, volume controls, switches, knobs, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to the F.C.C. type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

J. Statistis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

**UNCONDITIONAL MONEY-BACK GUARANTEE**

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand the Progressive Radio "Edu-Kit" is now available in Spanish as well as English. It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc., for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional guarantee upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

**ORDER FROM AD - RECEIVE FREE BONUS RADIO & TV PARTS JACKPOT WORTH \$15.**

- Send "Edu-Kit" Postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.D. I will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."


Name .....  
Address .....

**Progressive "EDU-KITS" Inc.**

1186 Broadway, Dept. 227G  
Hewlett, N. Y.


(ATT: S. GOODMAN, M.S. IN ED., PRES.)

# new Products

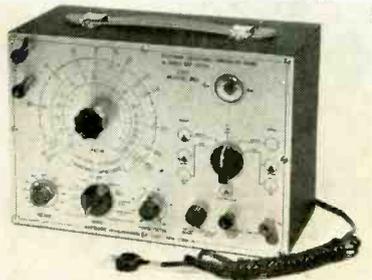
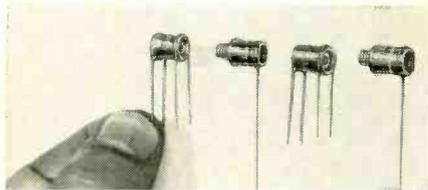
## R-C BRIDGE AND IN-CIRCUIT CAPACITOR CHECKER

*Model 801*, combines functions of two instruments in checking capacitors. Comparator bridge measures resistance from 0.5 ohm to 500 megohms and capacitance from 10 pf to 5,000  $\mu$ f in 4 ranges. In-circuit tests: detection of open capacitors for any value above 50 pf, with shunt resistance as low as 30 ohms for 350 pf; short detection on all nonelectrolytic capacitors with shunt resistance as low as 100 ohms; and indication of intermittents. R, L and C ratio measurements from .05 to 20, or 400 to 1. 1629 tube provides sensitive indication on all tests. Kit or wired and tested.—**Electronic Measurements Corp.**, 625 Broadway, New York 12, N. Y.



## CAPACITORS

*Series VC900*. A group of 4 subminiature glass piston trimmer capacitors with wide capacitance ranges of 1.2 to 16.0 pf and 1.0 to 10.0 pf. *Series VC900* contains telescopic adjustment mechanism with 500-cycle adjustment life, over 600% greater than requirements of Mil-C-14409B. Shown: *VC960* with standard glass dielectric for printed circuits; *VC950* with standard glass for panel mounting; *VC961* with JFD green glass for printed circuits; *VC951* with green glass for panel mounting.—**Components Div., JFD Electronics Corp.**, 1462 62 St., Brooklyn, N.Y. 11219

## STEREO RECORDER

*Sony model 464-SL* is a stereo and mono record and playback tape recorder designed as a deluxe teaching instrument,

featuring stereo record amplifiers, built-in mono power amp and speaker, student/teacher comparison switch and stereo line outputs for connection to external playback amplifiers. Power: 65 watts, 110-117 vac, 60 cycle; tape speeds: 7½ and 3¾ ips; frequency response: 40-15,000 at 7½ ips; signal to noise ratio: 45 db; flutter and wow: less than 0.19% at 7½ ips; inputs: 2 microphone and 2 high-level



line; outputs: 2 high-level line. Comes with two-tone molded carrying case and one Sony *F-96* dynamic microphone.—**Superscope, Inc.**, 8150 Vineland Ave., Sun Valley, Calif.


## SPEAKERS

*OP-6* and *OP-8*. Integral close-coupled inner horn and diaphragm eliminate conventional phasing plugs, insure impedance



match to outer bell. Outer bell has true exponential flair to reduce distortion. Magnetic structure has heavy Alnico V center-pole magnets and heat sink to protect the units' high power-handling capacity. ¾-inch wall sections of *Implex A*, a high-impact material impervious to weather, eliminate sympathetic vibrations. Standard stock units with built-in 70- or 25-

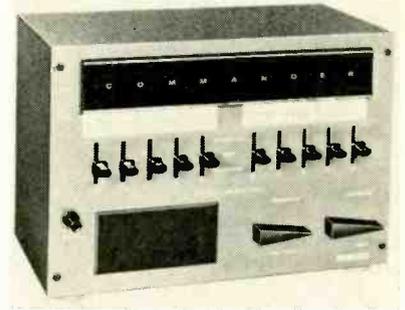volt constant voltage transformers with 45-ohm tap.—**Oxford Transducer Corp.**, 2331 N. Washtenaw Ave., Chicago 47, Ill.




## PACKAGED SOUND INSTALLATION

*Powrcom series* master switching and control console adds talk-back and intercom facilities to paging and background music systems; permits independent music and paging in selected areas simultaneously. Also for selective monitoring and surveillance as in factories, garages, shopping centers, etc. *MPC-10* 10-station master console (illustrated): optional switch bank expands it to 20 stations; *RPS-1* remote station for low-level paging, talk-back and call origination; *SWB-1* switchbox originates calls for any loudspeaker in system; *Trim Panel G* for mounting *MPC-10* into standard 19-inch rack; *JB-14* junction box for interconnection between console and speaker lines.—**Commercial Sound Div., Harman-Kardon**, 55 Ames Court, Plainview, N. Y.
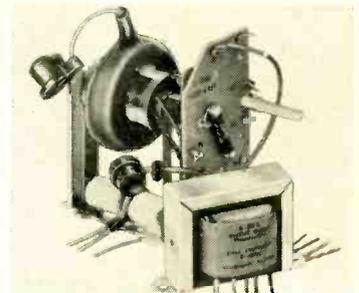
## MICROPHONE

*Model 8000* is shock-mounted cardioid dynamic microphone specifically designed for home recordist (or for churches, nightclubs, schools and location AM, FM and TV broadcasting). Low-priced, the mike is guaranteed against defects for 5 years. Frequency response is 70-15,000 cycles, and the diaphragm will, it is claimed, retain its original level of performance for the life of the microphone.—**Special Prods. Div., LTV University**, 9500 W. Reno, Oklahoma City, Okla.



## FLYBACKS AND VERTICAL OUTPUT TRANSFORMERS


These color TV sweep components (flybacks *D-300* through *D-304* and vertical

outputs A-300X through A-305X) were designed for 10 RCA parts numbers, but due to widespread use of basic RCA design can be used as replacements for 17 other brands.—Triad Distributor Div. of Litton Industries, 305 N. Bryant St., Huntington, Ind.


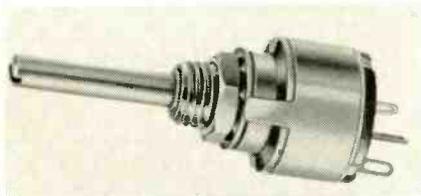
#### UNDERWATER SPEAKER

Model MM-2PPS, with hermetically sealed components and Polypropylene plastic housing, is designed to make flush mounting installation in existing light niches a snap. With a frequency response of 100 to 10,000 cycles and power capacity of 30 watts, one MM-2PPS will distribute sound through a pool up to 30 x 30 feet.—LTV University, 9500 W. Reno, Oklahoma City, Okla.



#### POTENTIOMETER

Series 63M, is of the hot-molded carbon type, is rated at 0.5 watts and measures 1/2 in. in diameter. Its fused and polymerized base incorporates the carbon resistance element, terminals and base structure as well as the carrier contact in a high-dielectric-strength assembly. The carrier is fitted into a plastic disc; the rotational stop is all metal. Meets all applicable military specifications.—Clarostat Mfg. Co., Inc., Dover, N. H.




#### CB RADIO

Mark Nine is a 27-megacycle unit designed low and slim (3 1/2 x 1 1/4 x 3 in.) so that it can be installed under the dash. A combination meter indicates the strength of transmitted and incoming signals. A spotting switch allows precise manual tuning of the receiver without the use of


receiver crystals, and permits the user to spot the proper crystal-controlled transmit frequency to respond to an incoming call. Operates on 115-volt ac power supply. Accessory 6- and 12-volt dc supply for mobile operations is optional. Weight including mike is 9 lb.—RCA Electronic Components & Devices, Harrison, N. J.
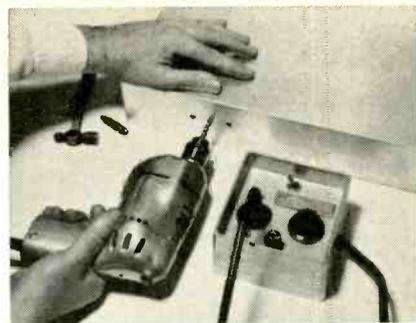
#### PLUG-IN MOTOR SPEED CONTROL

A new series being marketed through electronic parts distributors, Speedial controls are designed for universal (ac-dc) and series dc motors, are also suitable for use on electrical clutches and brakes requiring 0-90 volts dc. Available with ratings of 5 amps, 120 volts ac input to 15 amps, 240 volts ac input, in aluminum housings



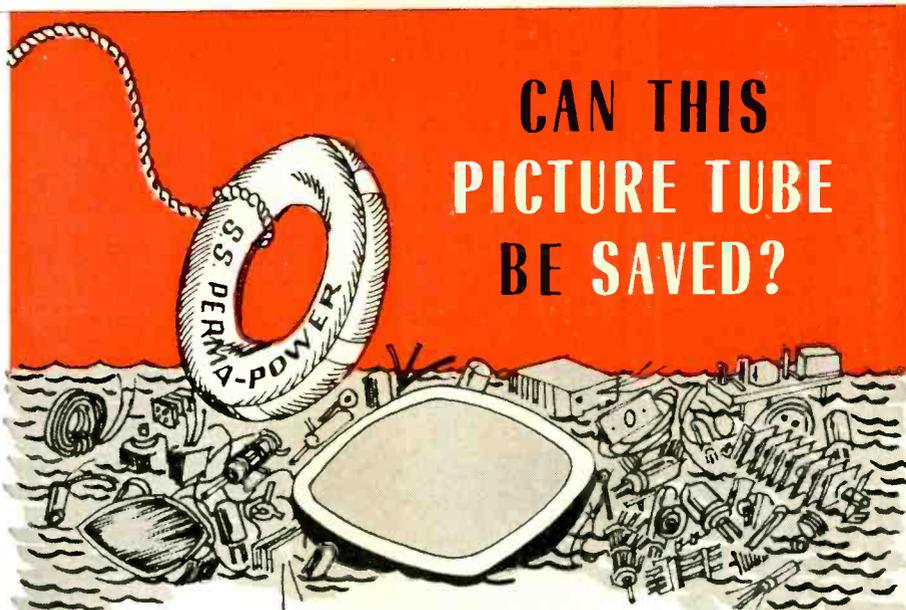of 4 1/2 x 4 1/2 x 2 1/2 in. A 3-position switch permits selection of variable control, full voltage (direct connection to the line voltage) and off positions.—International Resistance Co., 414 N. 13 St., Philadelphia, Pa. 19108



# CAN THIS PICTURE TUBE BE SAVED?

Fading dull picture tubes bounce back pronto with **Perma-Power Briteners**

Give new life, new brightness to aging picture tubes—and watch your customer's confidence in you bounce back, too, when you sell a \$4.00 britener instead of a \$70.00 tube. (Then you're a cinch for the tube sale later.)

It's easy with Perma-Power's Tu-Brite. Handsomely packaged for instant acceptance, color-coded by base type for instant selection. The right voltage is assured. With Tu-Brite, if the base is right, the boost is right. Make sure you have all three models in stock.

**Model C-202** for duodecal base CRT's.

**Model C-212** for 110° button base CRT's.

**Model C-222** for 110° shell base CRT's. Net \$2.25 each.

Write for free Britener Selector Chart, your guide to the base type of every picture tube now in the field.

**YES!** Perma-Power Brightens Color Sets, Too. Color-Brite Model C-501, Net \$5.85 each.



# Perma-Power COMPANY


5740 North Tripp Avenue • Chicago, Illinois 60646

Phone: 539-7171 (Area Code 312)

← X 85 + 86 All 1-6

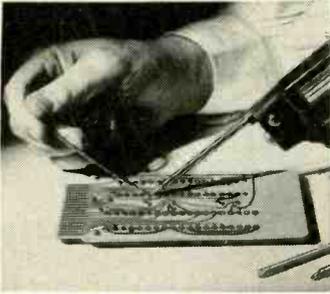**BOOSTER-ROTATOR COMBINATION**

The *Gemini* combines an automatic rotator with a transistorized booster and 2-set coupler so that only one transmission line is required; 80 feet of low-loss 4-conductor line is included. There are 2 versions of the *Gemini*: model 9518 for TV and FM; model 9527 for TV only. 90-day instant-replacement guarantee.—Channel Master Corp., Ellenville, N. Y.




**FINE-POINT SOLDERING TIP**

Wen model 75 soldering pistol. Tip temperature of 100–130 watt device from peak surge rating of 50 watts and normal draw of 30 watts. 3-inch tip assembly steps down for 3/16- to 1/8-in. diameter, tapering to fine point.—Wen Products, Inc., 5810 Northwest Highway, Chicago, Ill. 60631

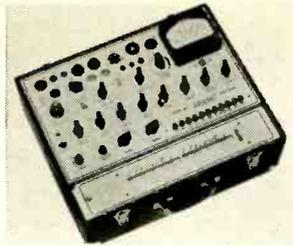**TUBE TESTER**

Model 580 permits setting test conditions directly from a tube handbook without




reference to the roll chart; has transistorized gas test circuit for measurement of gas down to .05  $\mu$ a. Four conductance ranges to 60,000  $\mu$ mhos. Leakage can be read directly on the meter, sensitive to 50 megohms. There is a pushbutton test of dual tubes; plate, grid and cathode jacks for access to these elements under test conditions; illuminated meter and roll chart.—Hickok Electrical Instrument Co., 10514 Dupont Ave., Cleveland 8, Ohio



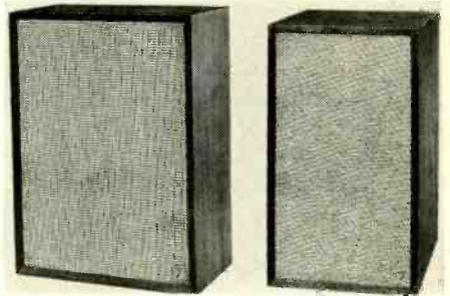**CLIPPER/COMPRESSOR/SPEECH AMPLIFIER**

The "Hi-Gainer" is designed to give an extra audio punch to CB, ham and commercial radio telephone transmitters, and

is completely self-powered by a 9-volt battery. It allows 100% modulation with normal speech, and may be used mobile or base.—Control Products, 123 Ave. U, Brooklyn 23, N. Y.



**TWO SPEAKER SYSTEMS**

The *Beverly Hills* (model SE-880) and the *Scarsdale* (model SE-80), the first an enclosure with two 8-inch speakers and the second with single 8-inch speaker, are constructed of 3/4-in. nonresonant panels finished in hand-rubbed oiled walnut veneer, each joint being lock-mitered. Both enclosures are vented. Model SE-880: response 45–20,000 cycles; power 40 watts; average programming 80 watts peak; impedance 8 to 16 ohms. Model SE-80: response 45 to 20,000 cycles; power rating 20 watts; average programming 40 watts peak; impedance 8 ohms.—Sonotone Corp., Elmsford, N. Y.



**PORTABLE TV INVERTER**

The 12TV12, powers portable TV sets from a 12-volt battery in automotive and marine equipment, house trailers, campers, etc. It has a special switch tap for radio receivers, dictating machines, phonographs, shavers or other transformer-operated equipment with a 75% to 100% power factor not requiring more than 120 volts.—Cornell-Dubilier Electronics Div., 50 Paris St., Newark 1, N. J.

**PORTABLE LOUDSPEAKER**



*Sonocaster*, 8 lbs., plastic housing. 8-in. coaxial driver unit for outdoor/indoor hi-fi use. Ceramic magnet assembly, double-

wound voice coil. Response, 70–13,000 cycles; nominal dispersion, 120°; power capacity, 30 watts peak; impedance, 8 ohms; crossover, 3,500 cycles. 16 1/4 x 17 x 5 1/2 in.—Electro-Voice, Inc., Buchanan, Mich.

**STEREO CERAMIC CARTRIDGE**

*Featheride 149DF* and *150DF* in 10-pack merchandising carton with point-of-sale



## Your new copy is waiting

**FREE!** For fun and pride in assembly, for long years of pleasure and performance, for new adventures in creative electronics mail the coupon below and get Conar's brand new catalog of quality do-it-yourself and assembled kits and equipment. Read about items from TV set kits to transistor radios . . . from VTVM's to scopes . . . from tube testers to tools. And every item in the Conar catalog is backed by a no-nonsense, no-loopholes, money-back guarantee! See for yourself why Conar, a division of National Radio Institute, is just about the fastest growing entry in the quality kit and equipment business.

# CONAR

**MAIL THIS COUPON NOW**


CONAR 3939 Wisconsin Ave., Washington 16, D.C. JC4C

Please send me your new catalog.

Name \_\_\_\_\_


Address \_\_\_\_\_

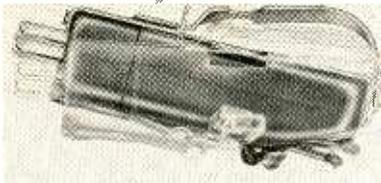City \_\_\_\_\_ State \_\_\_\_\_ Z-Code \_\_\_\_\_



literature. Spring-suspension permits cartridge to pivot when sudden force is applied, brings stylus off record surface and places soft "sole" on surface. Mounts in any arm with standard  $\frac{1}{2}$  or  $\frac{3}{16}$ -in. mounting centers. 149DF tracks at 2-4 grams; 150DF at 4-6 grams.—Electro-Voice, Inc., Buchanan, Mich.

#### HI-FI LOUDSPEAKERS

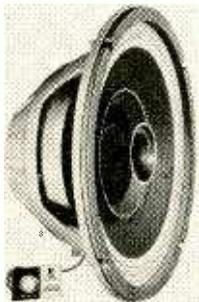


*Delta series. Model DL-220:* 3-element, 12-in. coaxial unit. *DL-120:* dual-cone, 12-in. speaker. *DL-80:* dual-cone, 8-in. speaker. Each has Syntox magnetic systems; Flexair suspensions; binding-post terminals;

die-cast housings; stable spider suspensions for positive voice-coil centering; power capacity 20 watts.—Jensen Manufacturing Co., 6601 S. Laramie Ave., Chicago, Ill. 60638
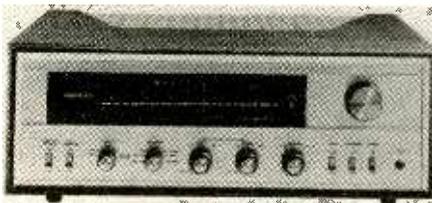
#### FM STEREO TUNER/AMPLIFIER

*Model 345.* 3 new circuits: low-impedance symmetrical output drive; series-gate time-switching multiplex for good stereo separation and presence; pulse-suppression limiting for minimum interference. 64



watts of audio. Front-panel earphone jack. Stereo indicator shows when stereo is being received. Preamp tubes have dc on heaters.—H. H. Scott, Inc., Dept. P, 111 Powdermill Rd., Maynard, Mass.

#### MAGNIFYING GLASS




Premium with purchase of 12 *Vu-Brites*, either *C-401* parallel or *C-402* series brighteners. 2-in. diameter glass folds in leatherette case.—Perma-Power Co., 5740 N. Tripp Ave., Chicago, Ill. 60646
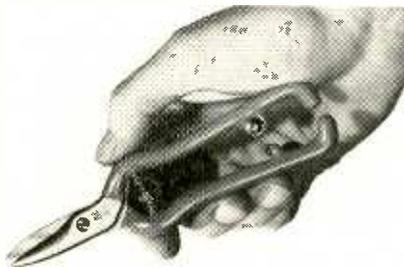
#### ELECTRONIC SNIPS

No. 86 fine wire and filament cutters. High-carbon drop-forged tool steel. For removing insulating coverings and cutting

sheet metals up to .025 in. thick. Thumb-operated latch keeps snips closed, coil spring returns blades to open position.



Chrome-plated blades, plastic-coated handles.  $6\frac{1}{2}$  in. long, length of cut  $1\frac{1}{4}$  in.—Xcelite Inc., Orchard Park, N. Y.

#### CAPACITOR CHECKER

*Model TO-6 Tel-Ohmike.* Low ac bridge voltage for checking low-voltage electro-



lytics and ceramics in transistorized circuits. Measures 0 to 2,000  $\mu\text{f}$  in 5 overlapping ranges, insulation resistance to 50,000 megohms, power factor to 50%, leakage current in 4 ranges from 0 to 60 ma. Burnout-proof meter, safety discharge switch, 3-wire line cord. Charcoal-gray panel.—Sprague Electric Co., North Adams, Mass.

#### TRANSISTORIZED BATTERY CHARGER

*Model BC2.* Charges 6-12-volt batteries at up to 6 amps. Current drops as battery reaches full charge; automatic-reset circuit



breaker prevents damage to charger or battery. Aluminum case,  $3\frac{1}{2} \times 4\frac{1}{2} \times 5$  in.  $6\frac{1}{2}$ -ft. lead wires, 6-ft. ac cord, ammeter.—Workman Electronic Products, Inc., Box 5397, Sarasota, Fla.;

END


All specifications from manufacturers' data.

# BEST BUY SCOPES

Eico's uncompromising attention to engineering excellence plus efficient Eico manufacturing and marketing techniques, give you laboratory standard performance at dramatic savings. Whether you buy kit or factory-wired, you can always count on getting the most for your test equipment dollar from Eico.
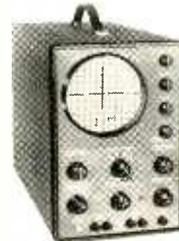
## 5-INCH

**EICO 427 ADVANCED GENERAL PURPOSE 5" SCOPE** High sensitivity scope has all the facilities and quality demanded for servicing audio, communications and industrial equipment. Vert. amp. flat from DC to 500 kc, —6 db at 1 mc; 3.5 mv rms/cm sensitivity. Horiz. amp. flat from 2 cps to 450 kc; 0.18 v rms/cm sensitivity. Automatic sync. Sweeps from 10 cps to 100 kc. Kit **\$69.95**; Wired **\$109.95**.




**EICO 460 WIDEBAND 5" SCOPE** For color & black-and-white TV servicing. Easily reproduces 3.58 mc color TV synchronizing burst. Vert. amp. flat from DC to 4.5 mc, usable to 10 mc; 25 mv rms/inch sensitivity. Horiz. amp. flat from 1 cps to 400 kc; 0.6 v rms/inch sensitivity. Automatic sync. Sweeps from below 10 cps to 100 kc. Kit **\$89.95**; Wired **\$129.50**.


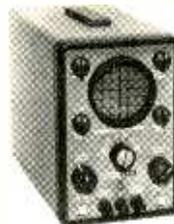
## 3-INCH

**EICO 430 PORTABLE GENERAL PURPOSE 3" SCOPE** Remarkably fine compact scope. Excellent for servicing audio, communications, and industrial equipment. Ideal as a ham shack monitor. Flat-face 3" CRT with mu metal shield eliminates affects of external fields. Vert. amp. flat from 2 cps to 500 kc, —6 db at 1 mc; 25 mv rms/cm sensitivity. Horiz. amp. from 2 cps to 350 kc, 0.25 v rms/cm sensitivity. Sweeps from 10 cps to 100 kc. Kit **\$69.95**; Wired **\$99.95**.



**PLUS—the new 435 wide band 3-inch scope.** All the features of the 460 in a 3-inch compact portable. Ideal for color TV and industrial servicing, and testing. Weighs only 15 lbs. Kit **\$99.95**; Wired **\$149.95**.



**EICO**

EICO Electronic Instrument Co., Inc.  
131-01 39th Avenue, Flushing, N.Y. 11352

Please send 1964 Catalog RE-9

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



# NEW! Winegard BOOSTER COUPLER

A Dramatic Improvement  
on an Old Favorite



MODEL  
BC-208  
Runs 1-4 TV or FM Sets  
Replaces Model WBC4-X

ONLY  
**\$29.95**  
LIST

Winegard engineers have used two of the new 6HA5 ampliframe shielded triode tubes and new circuitry to create the all new Winegard Booster coupler that dramatically increases signal power & cuts noise to a minimum. This increased power means 8 DB gain to each of 4 outputs, reducing snow, picture smear and interaction between sets.

FM gets a boost in this new circuit as well, because it covers the entire FM Band 88-108MC. The new BC-208 Booster Coupler is another forward-looking product from Winegard . . . providing better color, black and white and FM reception. Ask your distributor or write today for spec. sheets.

**Winegard Co.** ANTENNA SYSTEMS

3013-I Kirkwood • Burlington, Iowa

## booklets New Literature catalogs charts

**CAPSULE THERMISTOR COURSE No. 7**, single loose-leaf page, "Thermistors—How They Compare with Thermocouples, Resistance Thermometers." Resistance-temperature graph collates resistance change of thermistors with platinum. Table shows output voltage change with temperature for thermistors, platinum resistance bulbs, and thermocouples.—**Fenwal Electronics, Inc.**, Sales Engineering Dept., 63 Fountain St., Framingham, Mass.

**MODULES CATALOG, SP-173**, 40 pages, 4 colors, lists 90 germanium digital modules with specs, logic and circuit diagrams, other details on 200-ke, 1-mc and 5-mc circuits.—**Packard Bell Electronics**, Computer Div., 2700 S. Fairview St., Santa Ana, Calif.

**POWER SUPPLY DATA FILE**, 10 application bulletins: 6401—Protecting the Power Supply and its Load from Each Other. Part I. 6402—How Far—The Custom/Power Range of Sizes and Types Defined—At Last! 6403—The Primary Bridge and Primary Clipper Regulators—Two New Approaches. 6404—How to Check Your Power Supply Specification for Validity. 6405—Programming Power Supplies—Analog and Digital Techniques. 6406—Solid-State Power Supplies: Types and Techniques. 6407—Low Dissipation Regulators and Protective Circuits. 6408—DC Reference Supplies—Current and Voltage. 6409—How Big? How Heavy? How Efficient? How Hot? How Much? 6410—Case Histories—All of Them with Happy Endings. Available free to qualified engineers and designers. Will be supplemented periodically.—**Trio Labs Inc.**, Custom/Power Div., Dupont Dr., Plainview, N.Y.

**CB CATALOG SHEETS**, announcing two new transceiver models, *Escort* and *Companion II*. 2 pages on each detailing general, transmitter and receiver features.—**Pearce-Simpson, Inc.**, 2295 N.W. 14 St., Miami 35, Fla.

**WHOLESALE DISTRIBUTORS CATALOG**, 280 pages. Illustrated, with descriptions of complete line of distributor's stock, at OEM (original equipment manufacturer) prices, including semi-conductors, tubes, capacitors, resistors, transformers, switches, relays, fuses, terminals, connectors, CB equipment, cabinets, etc.—**Klaus Radio & Electric Co.**, 403 E. Lake St., Peoria, Ill. 61614

**STEREO TAPE RECORDER, model TX10**. 4-page, 2-color brochure with photos and specs on portable/studio model, e.g. 55 db signal-to-noise ratio, 1% total harmonic distortion, 3 heads (erase, record, playback), hysteresis synchronous motor, horizontal or vertical operation, 3- to 10½-inch reels, 2 high-level inputs and 2 mike inputs, 3 output jacks. Also information on accessories, portable amplifiers.—**Newcomb Audio Products Co.**, 6824 Lexington Ave., Hollywood 38, Calif.

**ZENER DIODES CATALOG, Bulletin 122-264**, 20 pages, lists and describes nearly 500 Zener diode types and variations from micro diodes through ½-watt and 1-watt to 10-watt types. Characteristics of MIL-E-1900 types, ultra-stable temperature-compensated reference elements, temperature-compensated glass Zeners and low-voltage forward regulators. Curves and dimensions, loose-leaf punched.—**TRW Semiconductors Inc.**, 14520 Aviation Blvd., Lawndale, Calif.

**COPPER OXIDE INSTRUMENT RECTIFIERS**, Series 80 (with photo) and Series 160-U (with diagram). Full specifications given on one loose page each.—**Conant Laboratories**, 6500 "O" St., Lincoln, Neb. 68505

**PUBLICATIONS BULLETIN, 1964**, describes in 4 pages two new radio and TV manuals, plus earlier manuals, and includes 1 page of hints on how to use radio-TV data.—**Supreme Publications**, 1760 Balsam Rd., Highland Park, Ill.

**KIT CATALOG, May 1964**. 48 pages, 2 colors, photos of kits after assembly. Color TV, organs, CB, ham and short-wave radios, intercoms, garage-door opener, computer system, marine accessories (antennas, deck speakers, vapor detector, depth sounder, rudder indicator, ground system, tachometer), test instruments, hobby tools, amplifiers, cartridges, headphones, record changers, speakers, tape recorders, tuners and receivers.—**Heath Co.**, Benton Harbor, Mich.

**WINDOW POSTER, series RP-33**, 17 x 22 in., with black-and-white cartoon, headlined "Is 'Do-It-Yourself' TV Service As Dangerous As They Say?", two columns of text and credited at the bottom to "Your Independent TV-Radio Service Dealer."—**Sprague Products Co.**, North Adams, Mass.

**WIRE AND CABLE CATALOG, No. W-4**. 52 pages detail more than 7,000 items from stock including coaxial cable to military specs, control and instrumentation cable, flat ribbon cable, unshielded control cable and UL-approved hookup wire. 2 colors, illustrated.—**Alpha Wire Corp.**, 180 Varick St., New York, N.Y. 10014

**PUSHBUTTON SWITCH CATALOGS, L-169A, L-172, L-173, L-176**. 14 pages in all, dealing with momentary-contact type subminiature push-button switches and matching indicator lights with characteristics, catalog numbers, dimensions, circuitry, mounting instructions.—**Dialight Corp.**, 60 Stewart Ave., Brooklyn, N.Y. 11237

**RELAYS, Engineering Bulletin 101-64**, 6-page folder in 3 colors with specs, illustrations and mounting data on new line of dry-reed and mercury-wetted contact relays. 40 stock part numbers including printed-circuit and octal plug-in units.—**Magnecraft Electric Co.**, 5581B N. Lynch Ave., Chicago, Ill. 60630

**CATALOG ADDITION** to Trimpot catalog, *Bulletin MC/C/O*, 4 pages on discrete microcomponents meeting military specs; resistors, capacitors, inductors, transformers, with specs, curves, characteristics.—**Bourns, Inc.**, Trimpot Div., 1200 Columbia Ave., Riverside, Calif.

**GENERAL CATALOG AND REPLACEMENT GUIDE No. 164**, 136 pages, photos, price

# DID YOU READ ABOUT RCA's new easy way to learn electronics at home?

see RCA Institutes  
ad on page 77



The Most Trusted Name in Electronics

list for radio-TV replacement and industrial coils, MIL-spec rf chokes, line filter chokes, diathermy chokes, i.f. transformers, i.f. trimmers. Looseleaf punched.—**J. W. Miller Co.**, 5917 S. Main St., Los Angeles, Calif.

**GLASS CAPACITORS.** *Booklet 93-160*, 4 pages, looseleaf punched. Describes CYW type capacitors. Graphs of operating-range capacitance, insulation resistance, dissipation factor, Q. Cross-indexed for Mil specs.—**Westinghouse Electronic Capacitor Dept.**, Irwin, Pa.

**TIN OXIDE RESISTORS BULLETINS.** 4 single looseleaf sheets. *CE-2.10* describes LPI-2 (2-watt) and LPI-10 (10-watt) low-power units; *CE-2.21* is on NA-style precision resistors; *CE-2.31* describes HNR-style resistors which show failure rate of .00057% per 1,000 hr.; *CE-2.32*, HRL-style, failure rate .015% per 1,000 hr. Photos, curves, specs. applications—**Corning Glass Works**, Electronic Prods. Div., Raleigh, N.C.

**REPLACEMENT AND INTERCHANGEABILITY GUIDE** for transistors and diodes, 3½ x 5 in., 20 pages, pocket edition of manufacturer's **Transistor & Diode Replacement Interchangeability Chart** (wall). Lists 3,000 transistor and diodes and 40 Semitron units that replace them.—**Semitronics Corp.**, 265 Canal St., New York, N.Y. 10013

**STEREO TAPES CATALOG.** May 1964, 28 pages, 3½ x 8½ in. Monthly service; contains all new releases from United Stereo Tapes.—**Ampex Corp.**, Consumer & Educational Products Div., 2201 Landmeier Rd., Elk Grove Village, Ill.

**FOUR-LAYER DIODE BULLETIN, C-101**, looseleaf-punched single sheet; photos, curves and specs of silicon diodes 1N3831 and 1N3846.—**National Transistor**, subsidiary of ITT, 500 Broadway, Lawrence, Mass.

**ANTENNA REFERENCE INDEX**, 18 antenna types described in 16-page, 2-color booklet. Lists patterns, radiation impedances, gain, other performance characteristics of 18 basic types including phased arrays.—**Sylvania Electric Products Inc.**, Dept. M-P, 100 1st Ave., Waltham 54, Mass.

**PRECISION FILM RESISTORS CATALOG**, 6 pages, looseleaf, foldout, 2 colors; complete specs on 8 types of metal film resistors and 16 deposited carbon types.—**Campbell Industries**, Div. of Clarostat Mfg. Co., Inc., Dover, N.H.

**FILTER CATALOG, No. C-100**, 2 colors, 32 pages; photos, drawings, curves, specs covering line of low-pass, bandpass, tunable bandpass filters, SWR-measuring devices, tunable frequency multipliers, power dividers, impedance transformers. Special model numbering system in each product group.—**Telonic Engineering Co.**, Marketing Dept., 480 Mermaid St., Laguna Beach, Calif.

**1964 MASTER INDEX** lists every television and radio set included in "Most-Often-Needed Servicing" manuals (18 TV manuals, 24 radio volumes). To find volume and page of material, look up under name of set. 42 pages. Usually 25¢; 10¢ to RADIO-ELECTRONICS readers.—**Supreme Publications**, 1760 Balsam Rd., Highland Park, Ill.

**CERAMIC FIXED CAPACITORS, Bulletin UNM 64-1**, 12 pages, looseleaf; photos, curves, specs on Uniceram High-Q and High-K types, plus description of sampling kit USK-63.—**JFD Electronics Corp.**, 15th Ave. at 62 St., Brooklyn, N.Y. 11219

**KIT CATALOG, 1964 "Edu-Kit"**, 50-page booklet includes wired as well as kit instruments, components, transistors, hi-fi, ham, photo kits. Also books and courses.—**Progressive "Edu-Kits" Inc.**, Dept. R-E, 1186 Broadway, Hewlett, N.Y.

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears.

UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

Give your mobile installation this **PROFESSIONAL "SPRING" TUNE-UP!**

Brand new from the Antenna Specialists—the professional touch to dress up and power up your mobile rig! Famous high-performance, low-noise A/S base-load design . . . "17-7" stainless steel whip (bend it in a full circle, snaps back to perfect vertical!) . . . fine-tuning adapter built-in. Now—available with a beautiful, functional stainless steel shock spring! Complete with cable and connectors, wide choice of base mounts. Tool over to your CB dealer today!

**M-124 "SUPER MAGGIE MOBILE" CB ANTENNAS**


(Newest "Hot Rod" to match perfectly the great M-117 "Super Magnum" base antenna)

**"SPRING" TUNE-UP FOR YOUR PRESENT ANTENNA! M-126 CONVERSION KIT**

Spring, adapter, wrench, all hardware for adding Shock Spring to M-67, M-73, M-74.

almost forgotten...

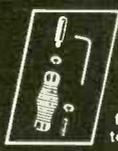Send for details on our **ZEUS AC ELECTRIC GENERATORS** Noise-free portable power . . . 2 models.




**22 TRAM**

ENGINEERED FOR TOP PERFORMANCE  
MANUFACTURED FOR QUALITY  
GUARANTEED FOR RELIABILITY

BEFORE YOU BUY—CHECK THE SPECS... WRITE TO:

**Citizen's Band TRANSCEIVERS**  
**Mobile & Base**

**TRAM ELECTRONICS INCORPORATED**  
P. O. BOX 187, WINNISQUAM, N. H.

# technicians' News

## FTC-DELAWARE VALLEY CASE AROUSES INTEREST

The Federal Trade Commission's charges against the TV Service Association of Delaware Valley (reported in August RADIO-ELECTRONICS, page 82) have stirred ripples in the industry. The *Audio Times*, a New York trade paper, disagrees firmly with TSADV's harsh boycotting of "dual-distributing" wholesalers, yet "believes that the action taken by the FTC against the *TSA News* [TSADV's monthly publication] is a blow against a free press. . . . If the FTC can make its charges stick against the publication . . . the result will be to intimidate other trade editors—to prevent them from speaking out on issues of importance . . ."

The editorial went on to say that at last the FTC would have to face squarely the issue of dual distribution.

That issue arises whenever a wholesale supplier of appliances or parts or accessories begins to advertise and sell to the general public as well as to his trade clients, thus putting himself into competition with the small dealers who depend on him. Because he can sell to the public at a lower price than a dealer, he has an unfair competitive price advantage over the dealers who buy from him and have to make their profit also.

Some actions that the FTC cites in the charges against the TSADV date back 5 years. Specifically, the FTC charges, the TSADV:

Communicated to [offending] wholesale distributors threats of concerted withdrawal of patronage.

Combined to boycott these wholesale distributors to coerce them to discontinue selling equipment or parts at retail in competition with individuals or organizations engaged in servicing and repair.

Dictated or attempted to dictate practices to be followed by wholesalers in the conduct of their business involving such matters as hours, display windows and advertising.

Published "white lists" of dealers who cooperated in refusing to sell at retail.

Used paid shoppers to check on distributors.

Generally, the FTC held, those

practices impeded competition and deprived the public of the choice of vendors to which they are entitled.

## TRI-STATE COUNCIL TECHNICAL PROGRAM VOTED IN AT "TELERAMA"; OFFICERS ELECTED

"Telarama '64", organized by the Tri-State Council of TV Service Associations, a group comprising Delaware, Pennsylvania and New Jersey service associations, was pronounced a great success by Tony De Franco, editor of the group's publication *The Vanguard* and newly elected president of the organization.

Held in Atlantic City, N. J., June 19-22, the annual convention gave member technicians an opportunity to meet, discuss the industry and investigate new equipment. Tops on the business agenda was discussion and approval of what is described as "one of the most ambitious technical and business training programs ever conceived for the benefit of the television service technician."

As part of that program, Tri-State Council will have available for its affiliated associations four (different-make) 1965 color TV sets, one for each association, and a collection of the most modern test, service and alignment equipment (color bar generators, sweep and marker generators, circuit analyzers and

# "MOVING OUT SALE" N.Y.C. TAKING OVER, 13-BLOCKS FOR TRADE CENTER & WE'RE IN IT

We must unload 3 BULGING WAREHOUSES . . . at the GREATEST PRICE SLASH in Electronic History!

FREE \$1 BUY WITH EVERY 10 YOU ORDER Only applies to "\$1" Buys FREE GIFT WITH EVERY ORDER

## IT'S NOT CHRISTMAS . . . but

- CHRISTMAS TREE LIGHTS (25) \$2  
wired socket units, asst colors . . .  
Price above last Christmas . . . now \$1
- 25" TALL — TALKING DOLL \$8  
sophisticated — blonde, brunette or redhead, 11 cue recitations  
Price above last Christmas . . . now 4
- \$50 STARLITE AM-FM RADIO \$28  
12 Transistors, Deluxe quality, sold on a money refund basis—complete
- PLAYBOY HI-FI 6 TRANSISTOR RADIO \$6  
Style, Quality, Performance money-refund basis—Complete . . .
- STARLITE TAPE RECORDER \$10  
Brand new, Complete, worth double
- \$27 MERCURY RECTIFIER TESTER \$7  
tests all types, brochure on request
- UNIVERSAL 5" PM SPEAKER \$1  
Ainco 5 magnet, quality tone . . .
- UNIVERSAL 4" PM SPEAKER \$1  
Ainco 5 magnet, quality tone . . .
- ELECTROSTATIC 3" TWEETER SPEAKER \$1  
for FM, HI-FI, etc. . . .
- 2 — UNIVERSAL 2 1/4" PM SPEAKERS \$1  
for Radios, Intercom, as multiple Speakers, etc. . . .
- 4 — AUDIO OUTPUT TRANSFORMERS \$1  
501.6 type . . . . .
- 3 — AUDIO OUTPUT TRANSFORMERS \$1  
6K6, 6V6 . . . . .
- 3 — AUDIO OUTPUT TRANSFORMERS \$1  
3V4, 3Q4, 3S4 . . . . .

- 100'—STANDARD ZIP CORD \$1  
2 conductor #18 white or brown
- 100'—MINIATURE ZIP CORD \$1  
2 conductor, serves 101 uses . . . . .
- 100—ASST. RADIO KNOBS \$1  
all selected popular types . . . . .
- 100—RADIO & TV SOCKETS \$1  
all type 7 pin, 8 pin, 9 pin, etc.
- 100—ASST. TERMINAL STRIPS \$1  
all types, 1-lug to 6-lug . . . . .
- 100—ASST. CERAMIC CONDENSERS \$1  
some in 5% . . . . .
- 100—CERAMIC CONDENSERS \$1  
Erie 50mmf-50v, 5% . . . . .
- 100 — ASSORTED 1/2 WATT RESISTORS \$1  
some in 5% . . . . .
- 100 — ASST 1/4 WATT RESISTORS \$1  
choice ohmages, some 5% . . . . .
- 70 — ASSORTED 1 WATT RESISTORS \$1  
some in 5% . . . . .
- 35 — ASSORTED 2 WATT RESISTORS \$1  
some in 5% . . . . .
- 50—PRECISION RESISTORS \$1  
asst. list price \$50 less 98% . . . . .
- 20 — ASST'D WIREWOUND RESISTORS \$1  
5, 10, 20 watt . . . . .
- 6 — ASST. SELENIUM RECTIFIERS \$1  
65ma, 100ma, 300ma, etc.
- 25 — SYLVANIA HEAT SINKS \$1  
for Transistors, etc. . . . .
- 2—EMERGENCY AUTO LAMPS \$1  
Red dome blinker, incl Battery saves lives on highway stops . . . . .

## TV BARGAIN COLUMN

- RCA COLOR TV CHASSIS #CTC-11 \$86  
less Tubes, details on request . . . . .
- STANDARD TV TUNER 41 mc \$5  
Complete with Tubes & Schematic . . . . .
- STANDARD TV TUNER 21mc \$5  
Complete with Tubes & Schematic . . . . .
- G.E. TV POWER TRANSFORMER \$4  
250ma, 360/360v, 6.3-9A, 5v-3A . . . . .
- \$15.00 TELEVISION PARTS \$1  
"JACKPOT" best buy ever . . . . .
- 4 — TV ALIGNMENT TOOLS \$1  
most useful assortment . . . . .
- \$12 TV FLYBACK TRANS 90° \$1  
for all type TV's incl schematic
- 90° TV DEFLECTION YOKE \$1  
wired network, schematic diag. . . . .
- 70° FLYBACK TRANSFORMER \$1  
universal incl schematic diagram
- 70° TV DEFLECTION YOKE \$1  
wired network, incl schematic . . . . .
- 3—TV VERT OUTPUT TRANS \$1  
universal 10:1 ratio for all TV's . . . . .
- 4—DUMONT VERT OSC TRANS \$1  
incl schematic for many TV uses
- 20—ASSORTED TV COILS \$1  
I.F. video, sound, ratio, etc. . . . .
- 40—ASSORTED TV KNOBS \$1  
all standard types, \$40 value . . . . .
- 4 — TV ELECTROLYTIC CONDENSERS \$1  
Sprague 80-250v . . . . .

## MARKET SCOOP COLUMN

- 6—IBM COMPUTER SECTIONS \$1  
loaded with Transistors, Condensers, Diodes, Resistors, Etc—sold big at 2 for \$1 & reordered—terrific buy now at . . . . . 6 for \$1
- TOP BRAND RADIO & TV TUBES \$1  
60/10/10%—Brochure on Request
- 20—ITT SELENIUM RECTIFIERS \$1  
65ma for Radios, Meters, Chargers, Transistors, Experiments, etc. 40000 in stock . . . all orders filled
- \$200 SONOTONE HEARING AID \$5  
less Earpiece & Batteries . . . . .
- STEREO PHONO AMPLIFIER \$2  
wired—each channel 3 watt . . . . .
- 2—25BK5 TUBES & 2-OUTPUT TRANS \$2  
completes above Amp . . . . .
- MAGNAVOX PIECE OF EQUIPMENT \$1  
loaded with deluxe parts . . . . .
- MAGNAVOX SET OF TUBES \$1  
12AU7 and 2—12AX7, for above
- 50—ASSORTED MILAR CONDENSERS \$1  
.001 to .47 . . . . .
- CRYSTAL LAPEL MICROPHONE \$1  
High impedance, 200-6000 cps . . . . .
- \$17.50 WEBSTER DIAMOND \$1  
CARTRIDGE Stereo . . . . .
- RONNETTE DUAL SAPPHIRE \$1  
CARTRIDGE flipover type . . . . .
- BONANZA "JACKPOT" not gold, not oil, but a wealth of Electronic Items—Money-Back-guarantee . . . . . \$5

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y. TELEPHONE (Orl)land 7-2359

CRT testers. All this is to be supplied in rotation to the member groups.

Technical meetings will be scheduled to demonstrate the equipment and explain how to use it. Each association will rotate the equipment among its members and, at the end of 3 months, another make of color set will be made available, until every member has had experience with each of the four sets and all of the equipment.

Similar programs are planned for transistor TV sets, hi-fi-stereo equipment, tape recorders and other home-entertainment devices the technician is called on to service.

Lectures and demonstrations on business management have also been scheduled.

The Tri-State Council elected officers during the Telerama convention. Tony De Franco became president; Peter Rapagnani was re-elected vice president. The new secretary is Joseph Papovich, and Ray Dellinger continues as treasurer.

**EIA BEGINS "ADDITIONAL SERVICE" PROGRAM**

The Electronic Industries Association's Distributor Products Div. will launch a regional test of a proposed national program to stimulate sales of electronic replacement parts through service dealers by encouraging them to

ask customers, "What else needs fixing?"

Norman A. Triplett, executive vice president in charge of marketing for Triplett Electrical Instrument Co. and chairman of the EIA program, said materials will be developed to educate dealers in the "additional service" approach. Many homes contain second radios, TV's or phonographs not in working order which could be repaired if the customer were reminded of them.

Triplett said the program will be patterned after a successful one conducted by the petroleum industry, under which service-station dealers pushed sales of gas, oil and parts by asking, "Fill 'er up?" or "Check your oil?"

At this writing, the region for the test program has not been selected.

**PHILCO GETS NATESA AWARD**

For the second consecutive year, Philco Corp has been presented the "Friends of Service" award by the National Alliance of Television & Radio Service Associations. Philco was cited for its continuing cooperation with the independent dealer and technician.

Alex Tagnon, field service manager at Philco, accepted the award plaque on behalf of Philco's Parts and Service Operation from William Childs, NATESA's West Central vice president, at the association's Spring Directors Conference in Memphis, Tenn. END

**BUILD this new portable MOOG Hi-Fi Amplifier Speaker**



- **NEW MOLDED ENCLOSURE!**  
Enhances any decor. Rugged enough to meet critical field requirements. Lightweight... only 20 lbs.
- **NEW OPTIONAL RE-CHARGEABLE BATTERY!**  
Long-life 10-volt re-chargeable battery mounted inside for economical, portable operation. A.C. supply and connectors for external 12-volt battery provided as standard equipment.
- **NEW TRANSISTOR CIRCUITRY!**  
15-watt solid state amplifier with two independent low noise inputs for true "transistor sound".
- **JAMES B. LANSING SPEAKER!**

Kit Model PMS-15 \$129.95 less battery  
Kit Model PMS-15B \$174.95 with battery

**R. A. MOOG CO.**  
Dept. 1011, Trumansburg, N.Y.

Send further information

Send \_\_\_\_\_ Kit(s) without battery @ \$129.95

Send \_\_\_\_\_ Kit(s) with battery @ \$174.95

Enclosed is  check  money order. No C.O.D.s please. Prices F.O.B. Trumansburg, N.Y.

NAME \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

**IMMEDIATE DELIVERY... SCIENTIFIC LIGHT PACKING** for safe delivery at minimum cost. **HANDY WAY TO ORDER**—Pencil mark items & enclose with check or money order, add extra for shipping, excess refunded with advantage to customer. Tearsheet will be returned with order, as your packing slip.

- |                                                                                     |                                                                                            |                                                                                          |
|-------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------|
| <input type="checkbox"/> 1-LB SPOOL ROSIN-CORE SOLDER 40/60 top quality \$1         | <input type="checkbox"/> 10-6' ELECTRIC LINE CORDS with plug standard brands \$1           | <input type="checkbox"/> 5-\$15.00 RADIO PARTS "JACK-POT" handy assortment \$1           |
| <input type="checkbox"/> 250-ASST. SOLDERING LUGS best types and sizes \$1          | <input type="checkbox"/> 4 - 50' SPOOLS HOOK-UP WIRE 4 different colors \$1                | <input type="checkbox"/> 50-RCA LUCITE RADIO KNOBS popular type w. indicator pointer \$1 |
| <input type="checkbox"/> 250-ASST. WOOD SCREWS finest popular selection \$1         | <input type="checkbox"/> 100' - INSULATED SHIELDED WIRE #20 braided metal jacket \$1       | <input type="checkbox"/> 5-ASST. SIZES RADIO CHASSIS PANS drilled & plated \$1           |
| <input type="checkbox"/> 250 - ASST. SELF TAPPING SCREWS #6, #8, etc. \$1           | <input type="checkbox"/> 32'-TEST PROD WIRE deluxe quality, red or black \$1               | <input type="checkbox"/> 5-VARIABLE CONDENSERS asst. popular super-het types \$1         |
| <input type="checkbox"/> 150-ASST. 6/32 SCREWS and 150 6/32 HEX NUTS \$1            | <input type="checkbox"/> 100'-HI-VOLTAGE WIRE for TV, special circuits, etc. \$1           | <input type="checkbox"/> 50-ASSORTED PRINTED CIRCUIT SOCKETS best types \$1              |
| <input type="checkbox"/> 150-ASST. 8/32 SCREWS and 150-8/32 HEX NUTS \$1            | <input type="checkbox"/> 200'-BUSS WIRE #20 tinned for hookups, special circuits, etc. \$1 | <input type="checkbox"/> 35 - INSTRUMENT POINTER KNOBS selected popular types \$1        |
| <input type="checkbox"/> 150-6/32 HEX NUTS and 150-8/32 HEX NUTS \$1                | <input type="checkbox"/> 100' - TWIN TV LEAD-IN WIRE 300 ohm, heavy duty \$1               | <input type="checkbox"/> 100' - FINEST NYLON DIAL CORD best size. 028 gauge \$1          |
| <input type="checkbox"/> 100 - ASST. RUBBER & FELT FEET FOR CABINETS best sizes \$1 | <input type="checkbox"/> 5-TV CHEATER CORDS with both plugs \$1                            | <input type="checkbox"/> 20-ASST. PILOT LIGHTS #44, 48, 47, 51, etc. \$1                 |
| <input type="checkbox"/> 10-ASSORTED SLIDE SWITCHES SPST, DPDT, etc. \$1            | <input type="checkbox"/> 20 - ASSORTED GRID CAPS for 1B3, 1X2, 6BG6, 6BQ6, etc. \$1        | <input type="checkbox"/> 10-ASST. DIODE CRYSTALS 5-1N60 and 5-1N64 \$1                   |
| <input type="checkbox"/> 4-TOGGLE SWITCHES SPST, SPDT, DPST, DPDT \$1               | <input type="checkbox"/> 50-ASSORTED TV PEAKING COILS all popular types \$1                | <input type="checkbox"/> 3 - ELECTROLYTIC CONDENSERS 50/30-150v \$1                      |
| <input type="checkbox"/> 15-ASST. ROTARY SWITCHES all popular types \$20 value \$1  | <input type="checkbox"/> 3-1/2 MEG VOLUME CONTROLS with switch, 3" shaft \$1               | <input type="checkbox"/> 4 - ELECTROLYTIC CONDENSERS 40/40mf-400 volts \$1               |
| <input type="checkbox"/> 50-ASSORTED #3AG FUSES Popular assorted ampere ratings \$1 | <input type="checkbox"/> 5 - ASST. 4 WATT WIRE-WOUND CONTROLS \$1                          | <input type="checkbox"/> 10 - ASST. RADIO ELECTROLYTIC CONDENSERS \$1                    |
| <input type="checkbox"/> 20-STANDARD FUSE HOLDERS for 3AG fuses, easy mount \$1     | <input type="checkbox"/> 10-ASSORTED VOLUME CONTROLS less switch \$1                       | <input type="checkbox"/> 7 - ASST. TV ELECTROLYTIC CONDENSERS \$1                        |
| <input type="checkbox"/> 50 - STRIPS ASSORTED SPAGHETTI handy sizes \$1             | <input type="checkbox"/> 5-ASSORTED VOLUME CONTROLS with switch \$1                        | <input type="checkbox"/> 50 - ASST. TUBULAR CONDENSERS .001 to .47 to 600v \$1           |
| <input type="checkbox"/> 100-ASSORTED RUBBER GROMMETS best sizes \$1                | <input type="checkbox"/> 10 SETS - DELUXE PLUGS & JACKS asst. for many purposes \$1        | <input type="checkbox"/> 20-GOODALL TUBULAR CONDENSERS .047-600v \$1                     |
| <input type="checkbox"/> 10 - SURE-GRIP ALLIGATOR CLIPS 2" plated \$1               | <input type="checkbox"/> 15-RADIO OSCILLATOR COILS standard 456kc \$1                      | <input type="checkbox"/> 20-BENDIX CONDENSERS .007-2000v \$15 value \$1                  |
| <input type="checkbox"/> 10 - SETS PHONO PLUGS & PIN JACKS RCA type \$1             | <input type="checkbox"/> 3-I.F. COIL TRANSFORMERS 456kc. most popular type \$1             | <input type="checkbox"/> 100-FAHNSTOCK CLIPS \$1                                         |
|                                                                                     |                                                                                            | <input type="checkbox"/> 15 - TOGGLE SWITCHES SPST deluxe U.L. approved, 101 uses \$1    |

- MARKET SCOOP COLUMN**
- 10-ASSORTED TUBES Radio, Television and Industrial \$1
  - 10-SYLVANIA 1U4 TUBES brand new Jan., individual cartons also serves as 1T4 \$1
  - ALL AMERICAN TUBE KIT Top Standard Brand 12BA6, 12BE6, 12AV6, 50C5, 35W4 \$2
  - 3 - TOP BRAND 35W4 TUBES \$1
  - 1 - SQ. YARD GRILLE CLOTH most popular brown & gold design \$1
  - 1000' SPOOL HOOK-UP WIRE #22, solid, black, \$8.50 value \$1
  - 5-I.F. COIL TRANSFORMERS sub-min for Transistor Radios \$1
  - 5 - AUDIO OUTPUT TRANSFORM sub-min for Trans Radios \$1
  - 5-PNP TRANSISTORS general purpose, TO-5 case \$1
  - 5-NPN TRANSISTORS general purpose, TO-5 case \$1
  - 5-ASSORTED TRANSFORMERS Radio, TV and Industrial \$1
  - 1000-ASST. HARDWARE KIT screws, nuts, washers, rivets, etc. \$1
  - 1000-ASSORTED RIVETS most useful selected sizes \$1
  - 1000-ASSORTED WASHERS most useful selected sizes \$1
  - 2 - STANDARD ELECTROLYTIC CONDENSERS 40/40-450v \$1
  - 100-MIXED DEAL "JACKPOT" Condensers, Resistors, Surprises \$1

**BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y.** TELEPHONE Corlanti 7-2359

# NEW! LAFAYETTE 70-WATT COMPLETE AM-FM STEREO RECEIVER

Model LR-800

Just Add Speakers and Enjoy FM,  
FM Stereo and High-  
Quality AM Reception



**199<sup>50</sup>**

with case

99-0005WX

- A powerful 70-Watt Amplifier plus Complete Preamplifier Control Facilities plus a Standard AM Tuner plus a Sensitive FM Tuner plus an FM Stereo Tuner—all on One Compact chassis
- Amazing FM "Stereo Search" Circuit Signals Presence of Stereo Broadcasts
- Tuned Nuvistor "Front End" Provides Greater Sensitivity, Lower Noise, Less Heat
- Bar-Type Tuning Indicator for AM and FM
- Variable AFC Control • Imported

# NEW! LAFAYETTE Criterion® 1000- PROFESSIONAL 4-TRACK SELF-CONTAINED STEREO TAPE RECORDER

featuring **MAGNIFICENT TEAK CABINETS**



99-1501WX

**199<sup>50</sup>**

- Plays 2- and 4-Track Stereo and 4-Track Monaural
- Records 4-Track Stereo and Monaural
- 3-Speeds: 1 $\frac{7}{8}$ , 3 $\frac{3}{4}$  and 7 $\frac{1}{2}$  ips
- 6 Pushbutton Tape Motion Controls
- Records Sound with Sound
- Automatic Shut-off Electrically and Mechanically Returns Recorder to Stop Position
- Transistorized Stereo Preamplifiers
- Complete with 2 Dynamic Microphones, Cables, 7" Take-up Reel • Imported

# LAFAYETTE RADIO ELECTRONICS


## 1965 Catalog No. 650

Over 500 Pages—Featuring  
Everything in Electronics for  
**HOME • INDUSTRY • LABORATORY**

from the  
"World's Hi-Fi & Electronics Center"

- Stereo Hi-Fi—all famous brands plus Lafayette's own top-rated components
- Citizens Band—transceivers, Walkie-Talkies and accessories
- Tape Recorders • Ham Gear
- Test Equipment
- Radios, TV's, and Accessories
- P.A. Equipment; Intercoms
- Cameras; Optical Goods
- Marine Equipment; Auto Accessories
- Musical Instruments; Tools; Books and MUCH MORE

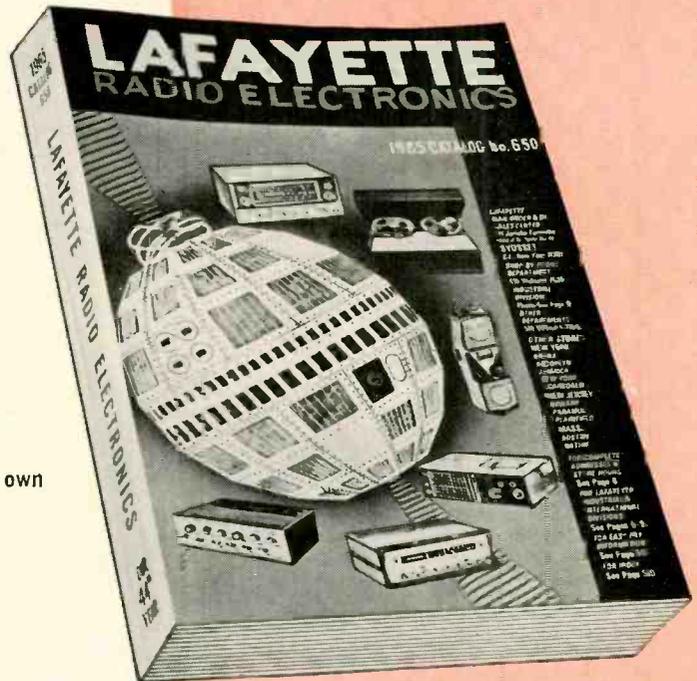**BUY ON TIME**—Use Lafayette's famous Easy-Pay Credit plan  
... up to 24 Months to Pay



See the Largest Selection in  
Our 44-Year History


MAIL THE ATTACHED CARD OR THE COUPON BELOW FOR YOUR FREE 1965 CATALOG

LAFAYETTE 12-TRANSISTOR  
C.B. WALKIE-TALKIE Model HE-100

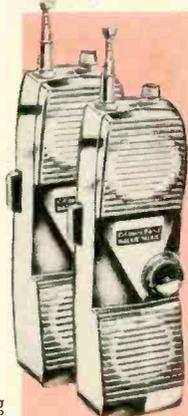**39<sup>95</sup>**

2-for- 78.88

- Variable Squelch Reduces Background Noise
- Separate Microphone and Speaker for Better Modulation and Increased Range
- Optional Plug-in 117 Volt AC Power Pack
- With Leather Case, Earphone, Telescoping Antenna, Batteries, Crystals for Channel 10 • Imported



99-3022

NEW! LAFAYETTE ALL-TRANSISTOR  
C.B. "WALKIE-TALKIE" Model HA-70

**10<sup>95</sup>**

2-for- 21.00

- Great Fun for Kids too! At a Price Everyone Can Afford
- Ideal for Picknicking, Fishing, Hunting, Camping, etc.
- Complete with Telescoping Antenna, Transmit Crystal, Battery, Plastic Carrying Case • Imported



99-3011

NEW! LAFAYETTE 6-TRANSISTOR  
C.B. WALKIE-TALKIE Model HA-85

**21<sup>95</sup>**

2-for-42.75

- Transmits and Receives up to 1 Mile
- Crystal-Controlled Transmit and Receive
- 6 Transistors plus 2 Diodes
- Complete with Leather Carrying Case, Earphone, Telescoping Antenna, Batteries, Pair of Crystals • Imported



99-3013

### LAFAYETTE RADIO ELECTRONICS

Mail Order and L.I. Sales Center

111 Jericho Turnpike Syosset, L.I., New York

New York, N.Y.  
100 Sixth Ave.

Jamaica, N.Y.  
165-08 Liberty Ave.

Brooklyn, N.Y.  
2265 Bedford Ave.

Bronx, N.Y.  
542 E. Fordham Rd.

Scarsdale, N.Y.  
691 Central  
(Park) Ave.

Newark, N.J.  
24 Central Ave.

Paramus, N.J.  
182 Route 17

Plainfield, N.J.  
139 W. 2 St.

Boston, Mass.  
584 Commonwealth  
Ave.

Natick, Mass.  
1400 Worcester St.

NEW!  
NEW YORK CITY  
STORE!  
WATCH FOR  
OPENING SOON!

### LAFAYETTE RADIO ELECTRONICS

Dept. J14-1, P.O. Box 10  
Syosset, L. I., N. Y. 11791

- Send me the FREE 1965 Lafayette Catalog 650
- \$..... enclosed; send me .....
- (Prices do not include shipping charges).

Name .....

Address .....

City .....

State .....

Zip .....

# NEW! LAFAYETTE 23-CHANNEL CRYSTAL-CONTROLLED DUAL CONVERSION 5-WATT CB TRANSCEIVER

Efficient, dependable 2-way communications in any fixed or mobile application is assured with this rugged, new 5-watt CB transceiver. A military-type frequency synthesizing circuit makes it possible to transmit and receive over the full range of 23 channels with crystal-controlled accuracy—no extra crystals to buy and install! Advanced Range-Boost circuit can be used to increase sideband power during transmission—lets you get through when noisy conditions make reception of your signal difficult!

Highly efficient circuit design uses 13 tubes (including two nuvistors) and 8 diodes to provide top performance under a wide range of operating conditions. Dual-conversion receiver offers high  $.3 \mu\text{v}$  sensitivity and low noise, plus excellent adjacent channel rejection. Includes every needed feature for optimum reception—crystal-controlled “fine tuning” capability on all channels of  $\pm 2.5 \text{ Kc}$  (Delta Tuning), high-efficiency variable noise limiter, variable squelch, and Automatic Volume Control. Also included is an illuminated meter which indicates relative RF power output or received signal strength in “S” units, and plug-in facilities for the Lafayette PRIVA-COM selector call unit.

Operates in a fixed or mobile location with equal ease . . . has built-in power supply for either 117V AC or 12V DC. Specially designed “Vari-Tilt” mounting bracket simplifies mobile installation—permits fast removal of the transceiver too! And, there’s nothing else to buy—you get all crystals and a built-in vibrator for 12V DC, plus 2 power cables. Measures a compact 12”Wx5”Hx10”D (including controls and plugs at rear). Imported.

Model HB-400.

99-3001WX

**169<sup>50</sup>**

## WITH ADVANCED “RANGE-BOOST” CIRCUIT

### Model HB-400



*Double Side Band Full Carrier*

- ✓ Meets All FCC Requirements
- ✓ Precision-Engineered and Ruggedly Built For Reliable 2-Way Radio Communications

- Frequency Synthesized Circuit Provides 23 Crystal-Controlled Transmit & Receive Channels—No Extra Crystals to Buy!
- Continuous One-Control Channel Tuning
- Full 5-Watt Input
- Push-To-Talk Microphone & Electronic Switching
- Dual Conversion Receiver With  $3/10 \mu\text{v}$  Sensitivity
- Delta Tuning Offers “Fine Tuning” of  $\pm 2.5 \text{ Kc}$  on Receive
- Variable Squelch, Variable Noise Limiter, AGC
- Built-in 117V AC & 12V DC Power Supply
- “Vari-Tilt” Mounting Bracket for Easy Mobile Installation
- Plug-in Facilities For Lafayette Selective Call Unit


## ADVANCED “RANGE-BOOST” CIRCUIT

*Increases Your Effective Range—Lets You Get Through When Others Fail!*

Want to effectively increase your range? You can—with Range-Boost! A simple turn of a switch on the HB-400 increases the average percentage of modulation and lets your voice cut through QRM and noise to reach further . . . gives you more “talk-power” when you need it—without overmodulating!


CONVENTIONAL

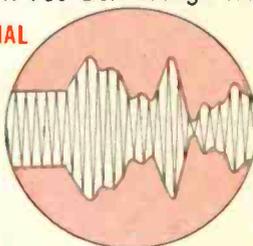Average Percentage of Modulation is Lower



WITH RANGE-BOOST

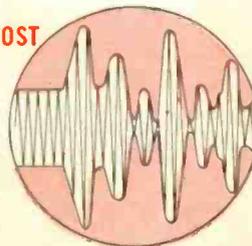Average Percentage of Modulation is Higher—Sideband Power is Increased



# NEW! LAFAYETTE ALL-TRANSISTOR DUAL CONVERSION 5 WATT CB TRANSCEIVER

**FEATURING  
AUTHENTIC MECHANICAL  
FILTER**

**Model HB-500**



Small, Compact . . . Measures Only 11 $\frac{1}{8}$ "Wx6 $\frac{1}{8}$ "Dx3"H.  
Low Current Drain . . . 350 ma on Receive, 850 ma on Transmit.

■ 12 Crystal Transmit Positions plus 12 Crystal Receive Positions ■ 23 Channel Tunable Receiver with Precise Vernier Tuning ■ Dual Conversion Super-heterodyne Receiver ■ 15 Transistors, 3 Diodes, 1 Zener Diode plus 1 Thermistor ■ Zener Diode Voltage Regulated Receive Oscillator for Superior Frequency Stability ■ Dependable Sealed Relay Switching ■ Automatic Noise Limiter ■ Variable Squelch ■ For 12 Volt DC Mobile Operation (Negative or Positive Ground) or for 117V AC Operation when used with Matching Solid State AC Power Supply (Optional) ■ Meets All FCC Regulations Part 95

If you're looking for a high-performance CB transceiver in a small, compact size, you'll want the HB-500! Using advanced solid-state circuitry, this transceiver offers full 5-watt performance, yet is small enough to fit conveniently into the most compact car. And, battery drain is so low as to be negligible—the transceiver draws no more than .35 amps on receive, .85 amps on transmit. As a result, you need neither heavy-duty battery nor

generator—an important advantage in mobile applications! The transmitter features full crystal control on any 12 of the 23 CB channels. Dual conversion receiver with better than .5  $\mu$ v sensitivity offers 12 crystal-controlled channels, plus full 23 channel tuning capability. A 455 Kc mechanical filter provides ultra-sharp receiver selectivity—virtually eliminates adjacent channel interference! Other features include an efficient Automatic Noise Limiter, variable Squelch for silencing the receiver on standby, spotting switch for exact frequency location on tunable receiver, "S" meter and illuminated channel dials. This rugged transceiver offers instantaneous, cool-running operation and features printed


circuit, all-transistor design. Equipped with mobile mounting bracket, push-to-talk dynamic microphone, crystals for operation on channel 12. Operates on 12V DC (neg. or pos. ground) or on 117V AC with optional solid-state power supply. Imported.

Model HB-500.

**139<sup>50</sup>**

99-3027WX

## HIGHLY SELECTIVE MECHANICAL FILTER

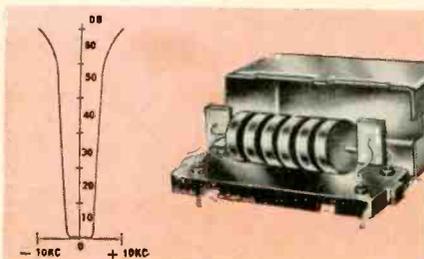

With CB channels only 10 Kc apart, selectivity is important! In the HB-500, ultra-sharp selectivity is achieved by means of a true mechanical bandpass filter in the 455 Kc IF section. At 10 Kc on either side of the center frequency, the filter provides 60 db of attenuation — an extremely high rejection ratio that assures complete adjacent channel rejection!


## Model HB-501 Solid State AC Power Supply

Matching solid state AC power supply for HB-500 for fixed station operation (at home, business office). Transceiver rests on power supply to form attractive integrated unit. Size 11 $\frac{1}{8}$ "x6 $\frac{1}{8}$ "x3 $\frac{1}{2}$ ". Imported.

99-3028 ..... Net 16.95

# ANNOUNCING A NEW GERNSBACK BOOK CONTAINING THE MOST USED, MOST NEEDED

FORMULAS AND DATA IN ELECTRONICS

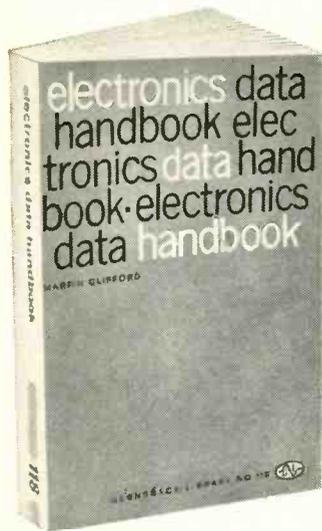

## ELECTRONICS DATA HANDBOOK

By MARTIN CLIFFORD

160 PAGES \$2.95 PAPERBACK  
G/L No. 118 \$4.60 Clothbound

- For technicians, engineers, students, hobbyists, hams, experimenters
- Arranged in logical, orderly fashion for quick easy reference
- A basic book for your library

If you had only one book in your professional library, this would have to be it. This single volume answers such everyday questions as these: What formula do I need for this problem? Is there an easier formula? Where can I find the data I need? What substitutions can I make in formulas? What sequence of formulas must I use if I need to work with several of them? This one book gives you all the answers, grouped under appropriate headings. You'll wonder how you ever got along without it. Send for your copy today.

### PARTIAL LIST OF CONTENTS

**D. C. Resistors** in series. Resistors in parallel. Resistors in series-parallel. Conversion of units. Resistance of a copper line. Length of a desired resistance. Calculating wire gauge. Resistance vs. temperature. Forms of Ohm's law. Power. Voltage drops. Bleeders. Bias resistors. Batteries in series. Batteries in parallel. Batteries in series-parallel. Kirchhoff's laws. The voltage law. The current law.

**A. C. Wave length.** Period. Frequency. Instantaneous current. Instantaneous voltage. Pulsating direct current. Alternating and direct currents combined. Capacitors in series. Capacitors in parallel. Capacitors in series-parallel. Amount of electricity stored in a capacitor. Capacitive reactance. Voltage distribution across capacitors in networks. Inductors. Inductors in series. Inductors in parallel. Mutual inductance. Coupled inductance. Inductors in series, aiding. Inductors in series, opposing. Inductors in parallel, aiding. Inductors in parallel, opposing. Q factor. Coefficient of coupling. Inductive reactance. Impedance. Phase angle. Ohm's law for alternating current. Power factor. True power. Apparent power. Resonance. Numerical magnitude of impedance . . . single resistor, resistors in series, single inductor, inductors in series, single capacitor, capacitors in series, resistance and inductance in series, resistance and capacitance in series, inductance and capacitance in series, resistance, inductance and capacitance in series, resistors in parallel, inductors in parallel, capacitors in parallel, inductance and resistance in parallel, capacitance and resistance in parallel, inductance and capacitance in parallel, inductance, resistance and capacitance in parallel, inductance and series resistance in parallel with capacitance, and capacitance and series resistance in parallel with inductance and series resistance.

**VACUUM TUBES** Thermionic emission. Amplification factor. Dynamic plate resistance. Mutual conductance (transconductance). Gain of an amplifier stage. Voltage output. Determining tube constants. Triode power output. Pentode power output. Maximum power output. Maximum undistorted power output. Plate efficiency. Approximate load resistance. Triode and pentode power sensitivity. Detector efficiency. Negative feedback. Miller effect. Rectifier ripple. Filter formulas. Regulation.

**TRANSISTORS** Emitter resistance. Base resistance. Collector resistance. Current gain. Voltage gain. Power gain. Collector capacitance. Cutoff frequency. Input impedance. Output impedance. Alpha. Beta. Negative resistance. Power dissipation. Power output.

**ANTENNAS and TRANSMISSION LINES:** Length of a Hertz antenna. Physical length vs. electrical length. Formula for "end" effect. Resonant frequency. Physical height in wavelengths. Antenna current. Antenna power. Characteristic impedance. Transmission line current. Transmission line peak voltage. Transmission line losses. Attenuation. Frequency. Field strength. Capacitance of a vertical antenna.

**MEASUREMENTS:** D. C. resistance of a milliammeter. Ohms-volt rating of a voltmeter. Ammeter shunts. Multi-range shunts. Voltage multipliers. Wheatstone bridge. Slide-wire bridge. Kelvin bridge. Series and shunt ohmmeters. Measuring resistance with a voltmeter. Measuring inductance with voltmeter and ammeter. Measuring capacitance. Capacitance-resistance bridge. Wien bridge.

**TABLES and MISCELLANEOUS DATA** Copper wire table. Specific resistance and temperature coefficients. Table of common logarithms. Natural sines and cosines. Natural tangents and cotangents. Table of vector conversions. Conversion factors. Constants. Mathematical symbols. Resistor color code. Capacitor color codes. Dielectric constants. Transformer color codes. I.F. transformer color codes.


- Buy now from your electronics parts distributor or mail in coupon
- Money-back guarantee within 10 days if not completely satisfied
- Books purchased for professional purposes are tax deductible

### GERNSBACK LIBRARY, Inc.

154 West 14th Street, New York, N. Y. 10011


Enclosed is \$\_\_\_\_\_ Please send  
 \_\_\_\_\_ copy(ies) of Electronics Data Handbook @ \$2.95 (paperback)  
 \_\_\_\_\_ copy(ies) of Electronics Data Handbook @ \$4.60 (clothbound)  
 Name \_\_\_\_\_  
 Street \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

## noteworthy

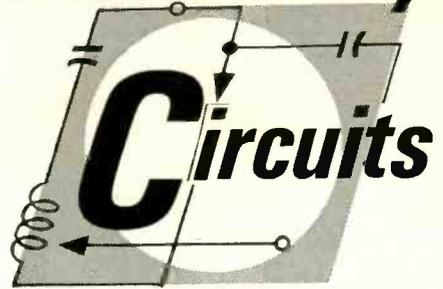
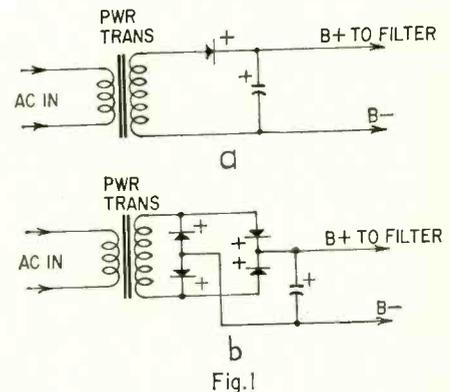
### IMPROVING THE HALF-WAVE SUPPLY

Many electronic devices use a half-wave power supply (Fig. 1-a) consisting of a power transformer and a silicon diode. If hum is an inherent problem, con-




sider converting the circuit to a full-wave bridge type (Fig. 1-b) by adding three more silicon diodes. The ripple voltage is lower and its fundamental frequency is doubled, thus making the filter more effective. Also, the output voltage is slightly higher.—Charles Erwin Cohn
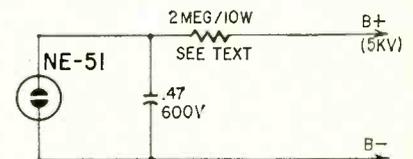
### HIGH-VOLTAGE INDICATOR LIGHT

While building a 5-kv transmitter power supply we needed a pilot lamp to indicate whether the filter capacitors were charged. This was necessary for safety as the bleeder resistor took 20 seconds to discharge the filters.

First thought was a neon lamp with a high-value series resistor. This worked fine at high voltages, but below 500 volts the lamp was just barely visible.




At 300 volts, it went out.

Finally the circuit shown evolved. At voltages from 5,000 to 500, the 2-megohm resistor acts as a dropping resistor for the neon lamp.; Below 500 volts, the circuit becomes a relaxation oscillator, and the lamp blinks brightly. The circuit gives a good indication of voltage from 5,000 to about 65. When this voltage is reached, further discharge of the filter capacitors is very quick. The 2-megohm 10-watt resistor is a special high-voltage type manufactured by In-

ternational Resistance Co. and called the MVP-17. This resistor is made on special order for around \$2.80 to \$5, depending on tolerance. IRC has a \$10 minimum-order policy. You can substitute a number of smaller 10-watt resistors in series to get the equivalent resistance.—*Irwin Math*

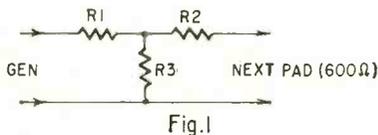
### PADS FOR THE LAB-QUALITY AUDIO GENERATOR

For anyone who has found it impossible to get certain precision resistors used in the attenuator network of the




db atten	R1	R2	R3
	(Values in ohms; K = 1,000)		
1	46.4	21.5	5,110
2	51.1	90.9	2,610
4	110	178	1,330
6	261	75	681
10	383	82.5	316
20	511	316 & 3,840	100
		in parallel	
40	316	27.8K & 820K*	287
		in parallel	

\*10% tolerance sufficient

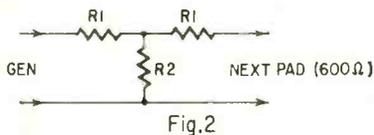

db atten	R1 (ohms)	R2 (ohms)
	(K = 1,000)	
1	34.8 & 3.9K* in parallel	5,110 & 90.9 in series
2	68.1	2,610 & 220K* in parallel
4	121 & 14.7 in series	1,000 & 261 in series
6	100 & 100 in series	825 & 33K* in parallel
10	316 & 20K* in parallel	422
20	464 & 26.1 in series	121
40	562 & 26.1 in series	12.1

\*10% tolerance sufficient

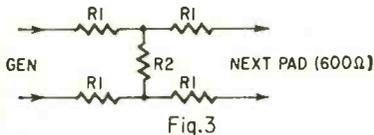

db atten	R1 (ohms; K = 1,000)
1	17.8 & 560* in parallel
2	34.8 & 2.7K* in parallel
4	68.1
6	100
10	162 & 3.3K* in parallel
20	261 & 3.9K* in parallel
40	316 in parallel with 3.9K* & 330* in series

\*10% tolerance sufficient. Values for R2 are the same as those in Fig. 2.


# GREAT NEW SCOTT KITS! AT A NEW LOW PRICE!

Have fun... save money... build the world's best stereo... with great new stereo kits from Scott. Scott's full-color instruction book and matching Part-Charts make these kits a breeze to put together... and, they'll give you and your family years of trouble-free enjoyment. The LT-110B FM stereo tuner incorporates famous Scott Sonic

Monitor and factory-wired, pre-aligned silver-plated front end and Time-Switching multiplex sections for top reception and stereo quality even in fringe areas. The LK-48B stereo amplifier includes switched front headphone output, powered center channel output for driving extension speakers, and many other unique Scott features.



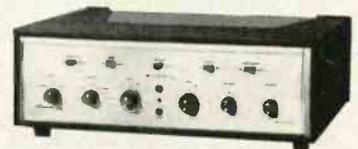LT-110B FM Stereo Multiplex Tuner \$139.95



LK-48B 80-Watt Stereo Amplifier Kit \$129.95

### FREE 24 PAGE BOOKLET

H. H. SCOTT, INC., 111 Powdermill Road, Maynard, Mass.

570-09

Rush me Scott's free 24-page Custom Stereo Guide:

Name \_\_\_\_\_ Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



Export: Scott International, 111 Powdermill Road, Maynard, Mass.  
Canada: Atlas Radio Corp., 50 Wingold Avenue, Toronto

"Lab-Quality Audio Generator" (RADIO-ELECTRONICS, May 1964), here are three types of pads, with the same attenuation, using standard 1% resistors. Each type is designed to work into 600

ohms, as in Fig. 4. The other pads use dpdt switches as shown in the article. All networks are accurate to within 1% of 600 ohms and the necessary attenuation.—*Robert Russell*

[Resistors of the values specified in the original article are made by Aero-vox.—*Editor*] END

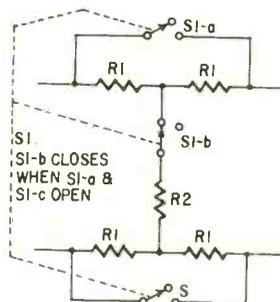


Fig. 4

ohms, and also to give the generator a load of 600 ohms.

The one shown in Fig. 1 does not give 600 ohms looking back from the load. Both the unbalanced type (Fig. 2) and the balanced (Fig. 3) do provide 600 ohms at either end. If the balanced pad is used, a 3pdt switch is required for


### CORRECTIONS

There is a misprint in the calculation in the "Case of the Lost Energy" in the "What's Your EQ?" on page 47 on the August issue. The answer to the first part of the problem is 5,000  $\mu$ Joules or .005 Joule.

Professor Hughes has called our attention to two errors in his co-authored article "Hi-Fi Pickup Arm—Theory and Practice" in the May 1964 issue. The mounting plate (part A) should be 1 1/8 inch wide—not 2 1/8 in. as indicated in Fig. 6. It was fabricated from 1/16-in. stock. The 1/8-in. notation is an error. However, this thickness is not at all critical and any convenient sheet stock may be used.
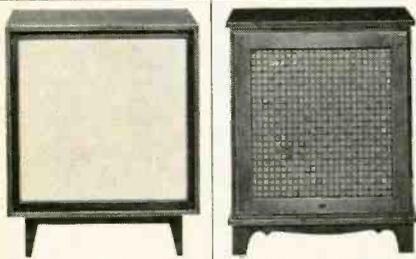
# build your own bozak

URBAN OR EARLY AMERICAN  
INFINITE-BAFFLE SPEAKER CABINETS



For the Bozak 2-way B-300  
and 3-way B-302A Speaker  
Systems. Complete Kits for  
easy assembly and finishing.

*Bozak*

See your Franchised Bozak Dealer DARIEN / CONNECTICUT

## Why Do You Read So Slowly?

A noted publisher in Chicago reports there is a simple technique of rapid reading which should enable you to double your reading speed and yet retain much more. Most people do not realize how much they could increase their pleasure, success and income by reading faster and more accurately.


According to this publisher, anyone, regardless of his present reading skill, can use this simple technique to improve his reading ability to a remarkable degree. Whether reading stories, books, technical matter, it becomes possible to read sentences at a glance and entire pages in seconds with this method.

To acquaint the readers of this newspaper with the easy-to-follow rules for developing rapid reading skill, the company has printed full details of its interesting self-training method in a new book, "Adventures in Reading Improvement" mailed free to anyone who requests it. No obligation. Simply send your request to: Reading, 835 Diversey Parkway, Dept. 448C Chicago, Illinois 60614. A postcard will do.


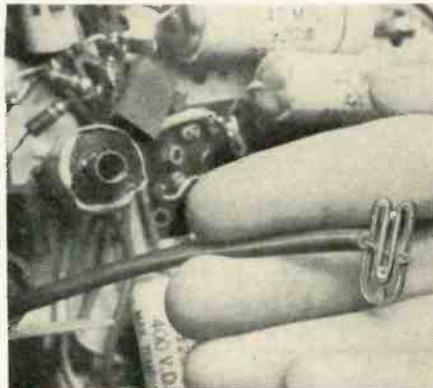
### COLOR-CODING WITH CLIPS


Those plastic paper clips of assorted colors available at stationery stores may be used for marking wires and terminals when replacing defective parts in electronic gear. Clip a colored



clip to each wire and terminal to enable you to solder in the new part properly. Even if you accidentally drop one of the clips into circuit wiring, there's no danger of a short circuit.—*John Comstock*
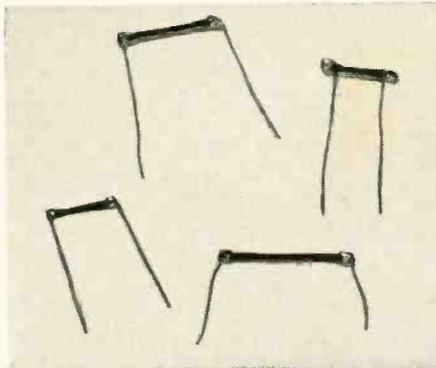
### DRAFTING LEAD MAKES TEMPORARY RESISTORS

The photo shows several home-brew resistors of assorted values. They were made by wrapping several turns of No. 20 wire about both ends of a piece of draftsman's lead. I normally use "Eagle Turquoise" brand, but any good grade of automatic-pencil drafting lead should



work equally well. After wrapping the wire, solder on the wrapped area.

The length of the resistor depends upon the resistance desired. The 3H lead


of the brand mentioned measures about 1 ohm per inch. Generally speaking, the softer the grade of lead, the less resistance for given length. The finished product by no means represents the equivalent of a commercial resistor, but these substitutes may be used until you can buy a proper commercial unit.

Use draftsman's lead for its uniform consistency. Common pencil lead is not recommended, since it is likely to have "hot spots" — uneven concentration of graphite in the filler material. Such spots cause the current to follow a low-resistance path within the lead, rather than giving the equal distribution desired.

The power rating of these units is approximately  $\frac{1}{3}$  watt.—*Roy R. Niehaus, Jr.*
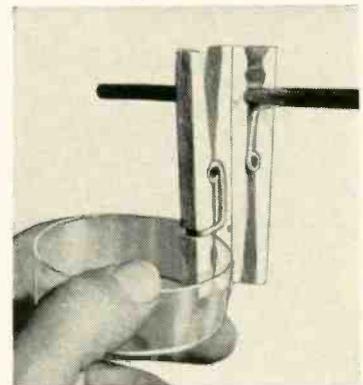
### DOUBLE-JAW CLAMP FROM CLOTHESPIN

A double-jaw clamp from two spring type clothespins that will be like a third hand can be rigged quickly by gluing two clothespins together, end to end and side by side as shown in the




photograph. Use white glue and the two pieces will be cemented permanently. In an emergency, you can fasten the clothespins together by taping or with a rubber band. The clamp is great for holding small articles for soldering, letting paint or glue dry, etc.—*Glen F. Stillwell*

### SCOPE INPUT GIMMICK

As you experiment with electronic circuits, you will sometimes find one that refuses to work right unless your scope or vtvm is connected to it, or *not* connected to it. The reason is that the critical circuit is strongly affected by the input impedance of the instrument. Since you

can't leave the scope in the circuit full-time, make a substitute for experimenting on the circuit even when the scope is needed elsewhere.

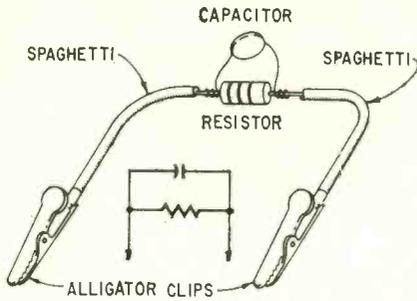Prepare a gimmick like the one shown here, from a resistor and a ce-



ramic capacitor and two alligator clips. Choose a resistor equal to the resistive part of the instrument's input impedance (usually specified), and a capacitor slightly larger than the capacitive part, to substitute for the absent test leads.

—Tom Jaski

### BLOWN FUSE COIL FORM

Blown fuses of the popular 3AG cartridge type make excellent low-loss forms for miniature rf coils, especially rf chokes. The fuse diameter is 1/4 inch, and the end caps are easily soldered to. The desired number of turns should be wound between the two end caps. The result will be a neat rf coil that can be mounted in fuse clips or, if pigtail fuses are used, soldered directly into a circuit.

The required number of turns for a particular inductance can be readily calculated from the simple single-layer inductor formula in the *Radio Amateur's Handbook*, or almost any radio handbook.—Irwin Math

### GROMMET GIMMICK

To install rubber grommets, bumpers, etc. held in place by forcing the rubber through a hole in a chassis, loop a wire around the narrow part of the grommet, push both ends of the wire through the hole where the grommet is to go, then give the wire a strong tug.

Remove the wire by pulling on one end.—Harry J. Miller


### CEILING MOUNTS ROLL-DOWN CHARTS

Here is a novel suggestion that will impress the customer and aid the service technician. At a desired spot in the shop, locate the ceiling rafters. Nail a wide and fairly thick board between two ceiling rafters. On this board, mount hardware for the desired number of extra-long window shades. On these shades cement price lists, charts, and other items you or a customer might want to see.

Label each shade string, so you can find the proper chart or price list at once.—A. von Zook
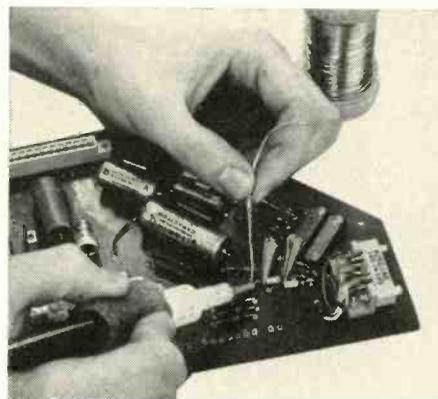
### CLIP-ON HEAT SINKS PROTECT DELICATE PARTS

The photo shows miniature alligator clips with felt cemented into their jaws, clipped to the leads of heat-sensitive components on a printed-circuit board. The felt is wetted just before use, and the water absorbs heat. Clips like



the Mueller 30 or 30C are tiny enough not to get in the way of even very tight soldering jobs.—Boeing Airplane Co.

END

**COYNE**  
TRAINS YOU  
IN SPARE TIME  
AT HOME

COYNE  
QUALITY  
TRAINING  
AT LOWEST  
COST

# TELEVISION

## COLOR TV- RADIO-ELECTRONICS

Coyne—and only Coyne—can give you this modern TV Home Training. Easy to follow 2150 photos and diagrams covering Radios-TV, Color, UHF, Transistors. We also show you how to start making money while learning, right at home. Get your basic training at home, then make a flash finish with 2 weeks of actual shop work in Chicago under direction of same instructors who guide our resident students.

**LOW COST—Easy to Pay**  
You don't pay for costly "put together" kits. Small monthly payments and low, low cost make it easy for everyone to train. Free employment service for graduates—or we show you how to start your own service business on a "shoestring." Send name today for complete facts and valuable book on Television. No salesman will call. Everything mailed free, postpaid.

**Coyne**  
**Electronics Institute**  
Not for Profit  
1501 W. Congress Parkway  
Dept. 64-H5, CHICAGO 7, ILL.

**FREE**  
of Extra Charge  
to Graduates  
**TWO WEEKS**  
Shop Training in Chicago

No increase in home training cost, but the day you graduate you will be entitled to two full weeks of personal instruction on actual projects in the great Shop-Labs of Coyne in Chicago—without one cent of extra tuition whatsoever.

**FREE Just Send Name**

No charge. No obligation. No salesman will bother you. Just send name for free copy of big 24 page book on quickest, lowest cost way to train for top pay job or business of your own. Mail coupon today.



**COYNE ELECTRONICS INSTITUTE, Dept. 64-H5**  
1501 W. Congress Parkway, Chicago 7, Ill.  
Please mail free book and offer of two weeks personal training in Chicago without extra tuition for home study graduates. Explain low monthly payments.

NAME \_\_\_\_\_ AGE \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY & STATE \_\_\_\_\_

## "Use it



## with any 12 volt CB transceiver"

### New Cadre Selective Call encoder-decoder

Put an end to meaningless chatter at the home base and in the mobile units. Contact only the stations you want to talk to. 3-tone, fool-proof selective call system provides up to 24 different tone codes. Code can be changed in field easily with no special relay needed. Easy connection to any of the famous Cadre 5-watt CB transceivers—works with all 12 volt transceivers, regardless of make. Get the Cadre 524 today. Only \$69.95.

**CADRE INDUSTRIES CORP.**  
Commercial Products Div., Endicott, N.Y.

### SOLDERING MINIATURE TUBE SOCKETS

After spending many hours wiring a receiver, I found that the tubes would not fit into the sockets, because solder had flowed into the pins of the tube socket itself. Trying to heat the pins and remove the solder proved fruitless.

The only alternative I had was to replace each and every socket, this time taking more care. So that I won't have the same problem again, I now insert an old tube into the socket before soldering.

This will not prevent solder from flowing into the pins of the socket. However, since the solder will not stick to miniature tube pins, any solder flowing into the tube socket pins will just surround the pins. The tube can still be removed without any trouble. What's more, I can put my good tubes back in!—Loren M. Mitchell

# SPECIAL INTRODUCTORY OFFER!



Join the Gernsback Electronics Book Club today, and get this outstanding practical two-volume set

# only 99c

(Regularly \$9.90 . . . Originally a \$25 Training Course!)

with membership in  
the Gernsback Electronics Book Club

**New Shortcuts to TV Servicing** by Leonard C. Lane was originally prepared as a complete course in TV servicing. This two-volume set will show you how to repair television receivers quickly and easily. There's no theory or math. Instead, you learn to repair television receivers in a minimum amount of time by recognizing certain symptoms. Profusely illustrated with hundreds of photographs, illustrations and schematics

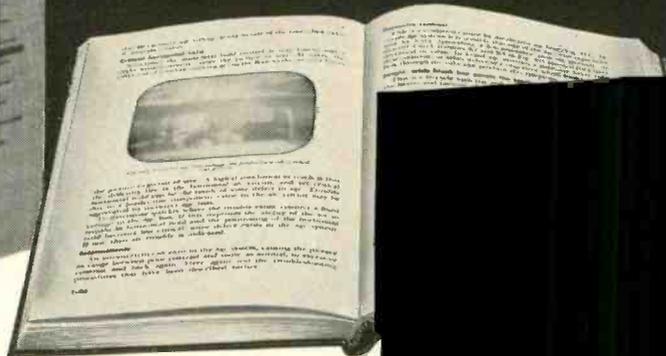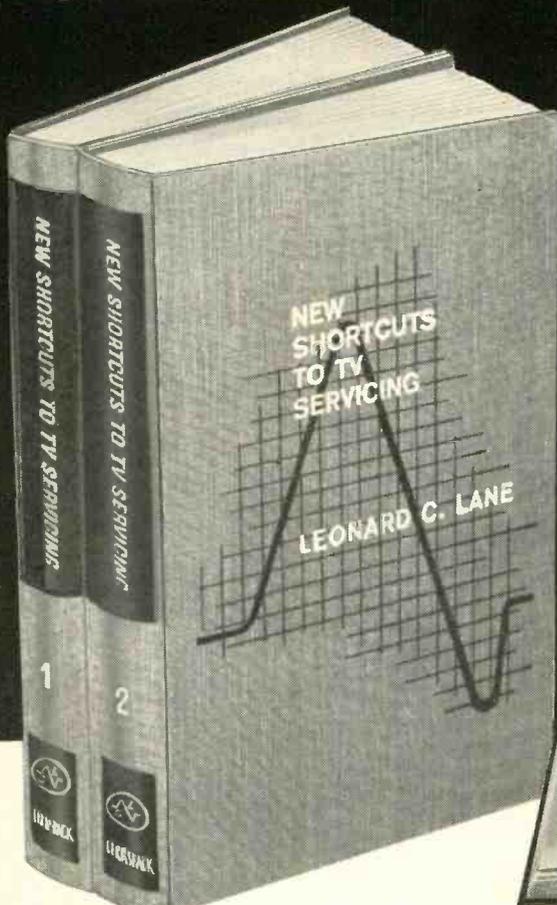

Here is a fabulous offer to introduce you to Gernsback Library's famous Electronics Book Club, specifically designed to help you increase your knowledge and earning power.

### WHY SHOULD YOU JOIN!

Whatever your interest in electronics - radio and TV servicing, audio and hi-fi, industrial or defense electronics, electronics as a hobby - you'll find that the Electronics Book Club will help you get the job you want, keep it, improve it, or make your leisure hours more enjoyable. By broadening your knowledge and skills, you'll build your earning power and electronics enjoyment as well.

### WHAT KIND OF BOOKS ARE OFFERED?

From Gernsback Library and other leading publishers come the country's most respected books in the field of electronics. All are deluxe, hard-covered, attractive looking books of permanent value - books you'll want to own and keep in your personal, professional library.

### HOW THE CLUB WORKS

The Electronics Book Club will send you, regularly, a newsy bul-

letin describing in detail select one or more books. You agree to accept delivery in the next 12 months.

Simply fill out and return the two-volume set of "New Shortcuts to TV Servicing" which regularly sells for \$9.90. If you are not satisfied within 10 days and membership is canceled, you'll be able to return the books at member's price.

### TYPICAL

- Electronics Data Handbook  
Reg. \$4.60—Club price \$3.75  
(You save 90c)
- Basic TV Course  
Reg. 5.75—Club price \$4.85  
(You save 90c)
- Basic Transistor Course  
Reg. \$5.75—Club price \$4.50  
(You save \$1.25)
- How to Build Tiny Electronic Circuits  
Reg. \$5.85—Club price \$4.95  
(You save 90c)
- Radio Servicing Made Easy (2 Vols.)  
Reg. \$9.95—Club price \$7.75  
(You save \$2.20)
- The Oscilloscope  
Reg. \$5.20—Club price \$3.95  
(You save \$1.25)
- How to Make Money Operating Your Own Radio and TV Service Business  
Reg. \$5.00—Club price \$3.75  
(You save \$1.25)
- Elements of Electron Physics  
Reg. \$5.65—Club price \$4.45  
(You save \$1.20)
- Electronic Design Charts  
Reg. \$5.95—Club price \$4.95  
(You save \$1.00)
- Horizontal Sweep Servicing Handbook  
Reg. \$5.75—Club price \$4.50  
(You save \$1.25)
- Basic Radio Course  
Reg. \$5.75—Club price \$4.85  
(You save 90c)
- Evening Home Receiver Course  
Reg. \$5.00—Club price \$3.75  
(You save \$1.25)
- Basic Math Course for Electronics  
Reg. \$6.45—Club price \$5.15  
(You save \$1.30)
- The V.T.V.M.  
Reg. \$4.60—Club price \$3.35  
(You save \$1.25)
- Transistor Reference Book  
Reg. \$6.00—Club price \$4.50  
(You save \$1.50)
- Industrial Electronics Made Easy  
Reg. \$5.95—Club price \$4.35  
(You save \$1.60)
- Fundamentals of Semiconductors  
Reg. \$4.60—Club price \$3.25  
(You save \$1.35)
- Tubes and Circuits  
Reg. \$4.95—Club price \$3.75  
(You save \$1.20)
- Hi-Fi Made Easy  
Reg. \$5.00—Club price \$3.75  
(You save \$1.25)
- Basic Industrial Electronics Course  
Reg. \$5.95—Club price \$4.70  
(You save \$1.25)
- The Story of Stereo  
Reg. \$5.00—Club price \$3.60  
(You save \$1.40)
- How to Fix Transistor Radios & Printed Circuits (2 vols.)  
Reg. \$9.95—Club price \$6.50  
(You save \$3.45)

## GERNSBACK LIBRARY, INC.

154 West 14th Street, New York, N. Y. 10011 94A


Enroll me as a member of the G/L Electronics Book Club. Start my membership with the two-volume set NEW SHORTCUTS TO TV SERVICING for only 99c (plus a few cents postage). Thereafter, send me the club bulletin describing the current selection which I may purchase at a special discount price if I wish. I understand that my only obligation is to purchase just 4 additional books within the next 12 months, and that I may cancel anytime thereafter. I also understand that I may cancel immediately, simply by returning the two-volume set within 10 days.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_ Code \_\_\_\_\_

We pay postage if you send your remittance with this coupon. You have the same return privilege.  Remittance enclosed.



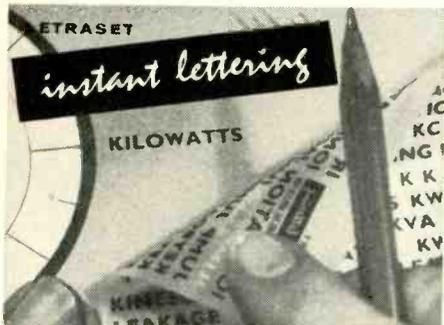Because you've got to SEE it to BELIEVE it... we will send you a FREE sample!



## A REVOLUTIONARY NEW METHOD FOR MARKING ELECTRONIC EQUIPMENT

Try this sample and you'll agree. "Instant Lettering" is the easiest, quickest way to get professional lettering you've ever seen. Self-adhesive letters printed on a special plastic sheet are just pressed down into position on any equipment, drawing, schematic, etc. Transfers to practically any surface. Looks like printing.

AVAILABLE IN THE FOLLOWING SETS AT \$4.95 EACH

- TITLES FOR ELECTRONIC EQUIPMENT
- TERMINAL & CHASSIS MARKING KIT
- METER & DIAL MARKING KIT

With these three kits you can completely mark prototype electronic equipment from component parts to finished control panel and meters — and make them look like finished production equipment.

In stock at leading electronics distributors or direct.

SEND FOR FREE SAMPLE AND FOLDER

**THE DATA CORPORATION**

63 71st STREET • DEPT. 613-3 • GUTTENBERG, NEW JERSEY

## NEW PRICES from QUIETROLE



the oldest, most widely proved and sold radio and TV lubricant

2 oz. bottle with dropper	LIST \$1.49
4 oz. bottle	LIST 2.54
4 oz. bottle (brush-n-cap)	LIST 2.64
8 oz. bottle	LIST 5.07
6 oz. spray can — with extender	LIST 2.79
3 oz. spray can — with extender	LIST 1.79


Quietrole is your guarantee of the most effective, quick silencer of noisy radio and TV controls — the quality product that is a top value. Get Quietrole at quality jobbers.

Some territories still available for experienced representation.



manufactured by **QUIETROLE Company**  
Spartanburg, South Carolina

# new Patents

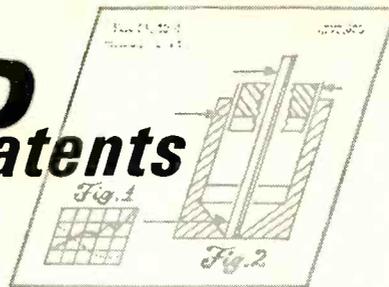


## PAY-TV DECODER

PATENT No. 3,116,363

Helias Doundoulakis, Brooklyn, N.Y. (Assigned to Teleglobe Pay-TV System, Inc., New York, N.Y.)

In this system, the transmitter sends normal video and audio signals, with the exception of the horizontal sync pulses, which are replaced by


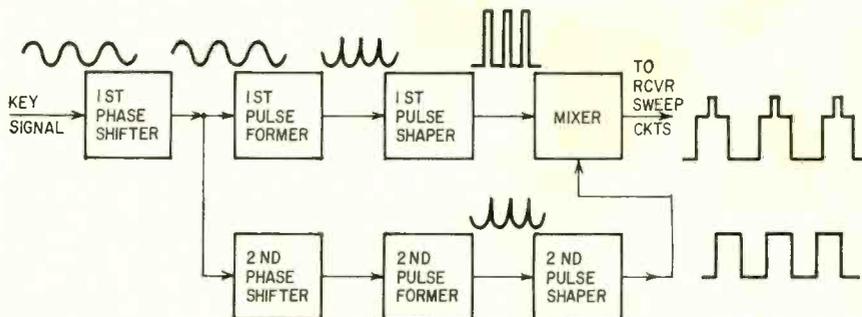
operative when a coin is inserted or when predetermined signals are received over the telephone line.



sine waves of controlled frequency. A decoder box, placed between the TV antenna and receiver, converts these key sine waves into sync pulses and permits normal reception. The decoder becomes

The diagram shows how the received key signal is shifted and shaped to build the sync and blanking signal properly. The mixer output is a conventional horizontal sync pulse.

TV RCVR'S IN VARIOUS HOMES

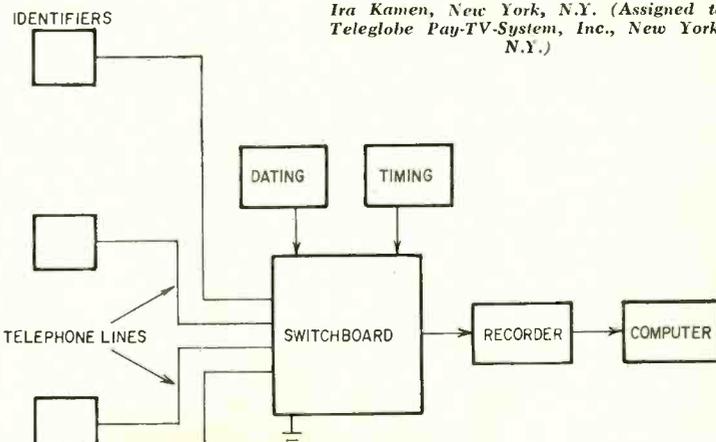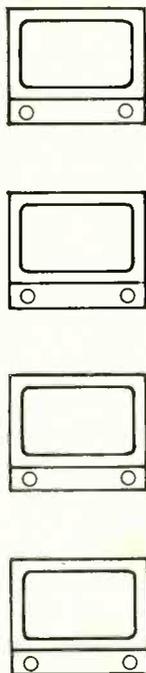

## TV AUDIENCE SURVEY

PATENT No. 3,126,513

Ira Kamen, New York, N.Y. (Assigned to Teleglobe Pay-TV System, Inc., New York, N.Y.)

This system interrogates TV receivers to determine which channel they are tuned to. Each identifier contains tuned circuits and intercepts emission from the TV set's local oscillator, whose frequency, of course, indicates the channel tuned in. The information is sent by land wire to a switchboard where date, time and channel data are filled in. If desired, a computer is used to evaluate the results.

The inventor also describes an arrangement (not shown) whereby the viewer states his reaction to a given program by pressing suitable buttons on his TV.

## FM STEREO

PATENT No. 3,122,610

Antal Csicsatka, Utica, N.Y. (Assigned to General Electric Co.)

This is one of the patents on which modern FM stereo is based. It packs all signals on a single FM carrier, and is compatible with mono. Separate microphones (left and right) deliver sound to a matrix which supplies L + R and L - R. The

first component is combined with a 19-kc pilot frequency. Both are frequency-modulated on a carrier (around 100 kc) which, after multiplication, becomes the transmitted FM carrier.

The L - R component is amplitude-modulated

on a 38-kc subcarrier, which is suppressed, leaving only the sidebands. Various time delays are inserted to assure that the components will reach the main FM modulator at the proper instant.

A source feeds in commercials and background music if desired.

At the receiver the circuits are conventional until after the discriminator. The pilot frequency is recovered and doubled to supply the missing subcarrier for demodulating L - R. The sidebands are transmitted through a bandpass filter to the detector.

L + R and L - R both enter the matrix circuit, and separate L and R components emerge to feed corresponding amplifiers and speakers. In a mono receiver, only the L + R is utilized. Since it represents the output of both left and right microphones, it is a complete, natural pickup.


The description of the system is illustrated by eight schematic and block diagrams.

### NUCLEAR ANEMOMETER

PATENT No. 3,109,098

Abraham E. Cohen, Wyanamassa, N. J. (may be manufactured or used by US Government without royalty payment)

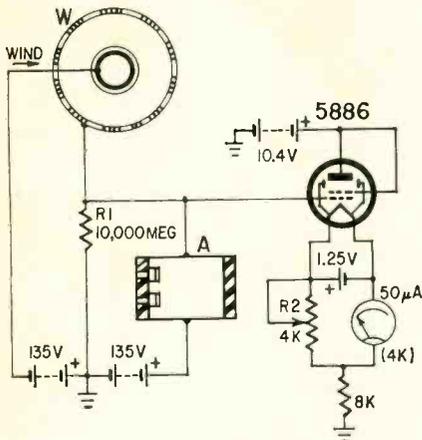This device measures wind speed. Wind chamber W is two concentric spheres, with the outer one perforated to let air pass. The inner sphere is coated with radium 266 or other isotope to ionize the air. Auxiliary chamber A is equipped



with baffles to minimize passage of air through it, but it, too, ionizes the air within it.

The polarized electrodes of each chamber attract ions which flow (in opposite directions) through R1. If wind blows through W, it removes some of the ions and changes the voltage across R1 proportionately.

V is an electrometer which detects the weak voltage across R1. With zero voltage, R2 is set to balance out the meter deflection.


Temperature or altitude changes affect air pressure, so they introduce errors. Since they affect W and A equally, however, they are balanced out. The wind affects W alone.

### AUTOMATIC LEVEL CONTROL

PATENT No. 3,117,287

Lawrence N. Damico, E. Boston, Mass. (Assigned to Raytheon Co., Lexington, Mass.)

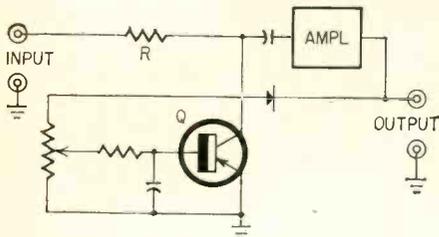Q and R form a voltage divider across the amplifier input. Rectified output from the amplifier controls Q's resistance, in the shunt leg of the di-



vider. Greater output means lower resistance, and less signal delivered to the amplifier. Therefore, Q tends to maintain an average output from the amplifier.

The gain of the amplifier itself remains constant. This reduces the possibility of introducing noise or distortion in the amplifier. END

# SCHOOL DIRECTORY

## SCIENCE/ ENGINEERING

Educationally-strong college courses in the fastest growing professional fields of Physics, Mathematics, Engineering (Nuclear, Electronic, Electrical); including Engineering Technology (Nuclear, Electronic). Optional four-quarter, all-year schedule permits completion of regular 4-year B.S. degree courses in three years; and, A.S. degree courses in two years. Electronic Engineering includes computer and space communication systems; and, laser/infrared engineering. Fall Quarter enrollments limited. Write now to Director of Admissions, for Catalog E-10.

**NORTHRIDGE COLLEGE OF  
SCIENCE & ENGINEERING**  
NORTHRIDGE, CALIFORNIA 91325


### Learn Electronics for your SPACE-AGE EDUCATION at the center of America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech, in sunny Southern California.

**COLLEGE OF ENGINEERING.** Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

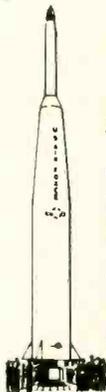**A & P SCHOOL.** Practical experience on real aircraft. One-year course prepares you for F. A. A. A & P certificate. **WRITE TODAY FOR CATALOG.**

**NORTHROP INSTITUTE OF TECHNOLOGY**  
1199 W. Arbor Vitae, Inglewood, Calif.



## B. S. Degree in 36 months

Small professionally-oriented college. Four-quarter year permits completion of B.S. Degree in three years. Summer attendance optional. **Engineering:** Electrical (electronics or power option), Mechanical, Civil, Chemical, Aeronautical. **Business Administration:** General Business, Accounting, Motor Transportation Administration. One-year Drafting-Design Certificate program. Outstanding placement of graduates. Founded 1884. Rich heritage. Excellent faculty. Small classes. 200-acre campus. Well equipped labs. New library. Residence halls. *Modest costs.* Enter Jan., March, June, Sept. *For catalog and View Book, write J. G. McCarthy, Director of Admissions.*



## TRI-STATE COLLEGE

2494 College Avenue • Angola, Indiana

## EARN Electronics Engineering DEGREE

You can earn an A.S.E.E. degree at home. College level HOME STUDY courses taught so you can understand them. Continue your education, earn more in the highly paid electronics industry. Missiles, computers, transistors, automation, complete electronics. Over 27,000 graduates now employed. Resident school available at our Chicago campus—Founded 1934. Send for free catalog.

**American Institute of Engineering & Technology**  
1139 West Fullerton Parkway, Chicago 14, Ill.

## MATHEMATICS ELECTRONICS

These courses are the result of many years of study and thought by the President of IHSI, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics and electrical and electronic engineering.

You will have to see the lessons to appreciate them!  
**YOU SIGN NO CONTRACTS**—you pay ONLY for the Lessons you order.

Write today for your outline of courses. You have nothing to lose, and everything to gain!  
**The INDIANA Home Study Institute**  
Eastern Division  
64 Hemenway Road  
Framingham, Mass.

**ETI** Engineering Technician  
A.S. Degree—2 Years  
Electronics Engineer  
B.S. Degree  
Evening Courses Available  
**ELECTRONIC TECHNICAL INSTITUTE**  
970 W. Manchester Ave., Inglewood, Calif.  
4863 El Cajon Blvd., San Diego, Calif.

**FOR AN ELECTRONICS CAREER**  
Write For Free Catalog RE  
WEEKLY TUITION

MICROWAVE TECHNIQUES—TV  
INDUSTRIAL ELECTRONICS  
COMPUTERS—RADIO TRANS-  
MITTERS—RADAR—TRANSISTORS

**PHILADELPHIA WIRELESS  
TECHNICAL INSTITUTE**  
1533 Pine Street Philadelphia 2, Pa.  
Founded in 1908 • A Non-Profit Corp.

## GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology and Electronic Technology curricula both available. Assoc. degree in 20 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Sept., Feb. Dorms, campus. High school graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL  
INSTITUTE**  
Department C, Valparaiso, Indiana



when it's time to think of college you should read this

**FREE CAREER BOOKLET**  
about electronics at

**MISOE**



**MILWAUKEE MS-220  
SCHOOL OF ENGINEERING**

Dept. RE-964, 1025 N. Milwaukee Street  
Milwaukee, Wisconsin 53201

Tell me about an engineering career through residence study in:

Electrical fields  Mechanical fields

Name..... Age.....

Address.....

City, State.....



## "TABTRON" AC & DC POWER SUPPLIES!

Model T201A Lab Supply \$50  
0 to 20VDC at 10 Amps  
Filtered

STEPPLES 320 VARI-  
ABLE "VARIAC"  
RATED 330 WATTS  
PINPOINT VOLTAGE CON-  
TROL • DW RECTIFIER  
XFMR for F.W.B. 4  
SILICON 18A DIODES in  
F.W.B. • TWO/LARGE  
METERS V&A SWAY  
BINDING POSTS COM-  
PUTER ELECTROLYTIC  
• FILTERED RIPPLE 0.1% at 2AMPS • 3% at  
10amps • COMPACT SHROUD • CIRCUIT/BKR. OUT-  
PUT PROTECTED • INPUT FUSED 115VAC 50 to  
500CVS • TIGTOR BATTY CHGR: PLATER S42 5A/ME  
SPECS. NON-FILTERED 0 to 15VDC at 10amps  
IDEAL "NICAD" BATTERY CHARGER • Q225L  
CONVERTER DC to AC 12VDC INPUT to 115VAC  
225 WATT SQ WAVE/60CYCLES. Q225L \$40



See Distributor or Write Dept. RE9  
**TECHNICAL APPARATUS BUILDERS**  
SIX CHURCH ST., NEW YORK 6, N. Y. U.S.A.

## "TAB", SILICON 750MA\* DIODES

NEWEST TYPE! LOW LEAKAGE			
Piv/Rms 50/35	Piv/Rms 100/70	Piv/Rms 200/140	Piv/Rms 300/210
.05 ea.	.12 ea.	.24 ea.	.36 ea.
Piv/Rms 400/280	Piv/Rms 500/350	Piv/Rms 600/420	Piv/Rms 700/490
.20 ea.	.24 ea.	.32 ea.	.40 ea.
Piv/Rms 800/560	Piv/Rms 900/630	Piv/Rms 1000/700	Piv/Rms 1100/770
.48 ea.	.55 ea.	.70 ea.	.75 ea.

Sil. Presst 18A up to 100 Piv . . . 4 for \$1  
Micro or MuSwitch CSD 35 Amp/AC-DC . . . 3 for \$1

## "TAB" \* SCR'S \* TRANSISTORS \* DIODES!!

Full Leads Factory Tested & Gtd. U.S.A. Mfg.  
PNP 50Watt/15amp NiPower T036 Pckg:  
2N441, 442, 277, 278, D5501 up to  
50 volts/VCO \$1.25 @ 80V, 2 for \$5  
2N278, 443, 174 up to 80V, 2 for \$5  
PNP/10Watt/3A-2N155, 156, 235, 242, 254,  
255, 256, 257, 301, 351, c35 @ 4 for \$1  
PNP/Signal up to one watt . . . 5 for \$1  
PNP/Signal IF, RF, OSC, TOS, OVS, c25 @ 6 for \$1  
PNP 2N670/300MW c35 @ 4 for \$1  
PNP 2N671, 1Watt c35 @ 3 for \$1  
Silicon PNP T05 & T018, Pckg c25 @ 5 for \$1  
T036, T03, Pckg Mica Mtg Kit 5 for \$1  
Power Heat Sink Fine 180 \$1.25 @ 5 for \$5  
3 Amp/T03/Pwr Transistors Untested! 10 for \$1  
Pwr Transistors T03/3A Untested . . . 10 for \$1  
Silicon Diodes up to one watt . . . 5 for \$1  
Silicon Diodes 35 Amp Studs Untested . . . 3 for \$1  
Silicon Diodes epoxy/750Ma Untested . . . 25 for \$1

2N1038 4/\$1, 1039 3/\$1, 1040 2/\$1, 1041 \$1  
2N538, 549, 540/3 Amp . . . 2 for \$1  
Zener 50/100V Auto Ignition . . . 3 for \$1  
100V Auto Ignition Transistor . . . \$3  
Kit Zeners 400 Mv to 10W Asstd . . . 3 for \$1

TERMS: Money Back Guarantee!  
Our 18th year, \$2 Min. order  
F.O.B. N.Y.C. Add ship charges  
or for C.O.D. 25% Dep. Prices  
shown subject to change.  
111-GS Liberty St., N. Y. 6, N. Y.  
Send 25¢ Phone: REcor 2-6245 for Catalog

## SILICON RECTIFIER SALE

IMMEDIATE DELIVERY  
FULLY GTD NEWEST TYPE  
AMERICAN MADE NEWEST TYPE  
FULLY TESTED

750 MA-SILICON "TOPHAT" DIODES			
LOW LEAKAGE FULL LEAD LENGTH			
Piv/RMS 50/35	Piv/RMS 100/70	Piv/RMS 200/140	Piv/RMS 300/210
.05 ea.	.09 ea.	.12 ea.	.16 ea.
Piv/RMS 400/280	Piv/RMS 500/350	Piv/RMS 600/420	Piv/RMS 700/490
.20 ea.	.24 ea.	.32 ea.	.40 ea.
Piv/RMS 800/560	Piv/RMS 900/630	Piv/RMS 1000/700	Piv/RMS 1100/770
.48 ea.	.55 ea.	.70 ea.	.75 ea.

## ALL TESTS AC & DC & FWD & LOAD

SILICON POWER DIODE STUDS				
D.C. AMPS	50 PIV 35 RMS	100 PIV 70 RMS	150 PIV 105 RMS	200 PIV 140 RMS
3	.12 ea.	.18 ea.	.22 ea.	.30 ea.
12	.45	1.15	1.50	1.70
35	.90	2.30	2.30	2.80
50	1.90	2.15	2.55	3.15
100	1.75	4.60	5.65	8.00

D.C. AMPS	300 PIV 210 RMS	400 PIV 280 RMS	500 PIV 350 RMS	600 PIV 450 RMS
3	.40 ea.	.45 ea.	.55 ea.	.65 ea.
12	1.10	1.35	1.50	1.70
35	2.35	2.55	3.00	3.50
50	3.50	4.00	3.00	3.40
100	3.75	4.60	5.65	8.00

## "SCR" SILICON CONTROLLED RECTIFIERS "SCR"

PRV	7 AMP	16 AMP	25 AMP	PRV	7 AMP	16 AMP	25 AMP
25	.50	.85	1.20	250	2.30	2.65	3.10
50	.85	1.20	1.40	300	2.60	3.00	3.40
100	1.35	1.80	2.20	400	3.00	3.40	4.15
150	1.60	2.10	2.65	500	3.75	4.25	4.75
200	1.75	2.40	2.90	600	4.00	5.00	5.25

Money Back guarantee. \$2.00 min. order. Orders  
F.D.B. NYC. Include check or money order. Shpg.  
charges plus. C.O.D. orders 25% down.

Warren Electronic Components  
663-65 Broadway, N. Y., N. Y. 10012 • OR 3-2620

## FREE Catalog

OF THE WORLD'S FINEST  
ELECTRONIC GOV'T  
SURPLUS BARGAINS

HUNDREDS OF TOP QUALITY  
ITEMS — Receivers, Transmitters,  
Microphones, Inverters, Power Supplies,  
Meters, Phones, Antennas, Indicators,  
Filters, Transformers, Amplifiers,  
Leadsets, Converters, Control Boxes,  
Dynamotors, Test Equipment, Motors,  
Blowers, Cable, Keyers, Chokes, Hand-  
sets, Switches, etc., etc. Send for Free  
Catalog—Dept. RE.

**FAIR RADIO SALES**  
2133 ELIDA RD. • Box 1105 • LIMA, OHIO

Convert any television to sensitive  
**BIG-SCREEN OSCILLOSCOPE**  
with minor, inexpensive  
changes. Ingenious circuit. No  
electronic experience needed to  
follow our clearly illustrated  
plans. TECHNICIANS, HAMS,  
EXPERIMENTERS, BROAD-  
CASTERS. Use in shop, school,  
lab. Any set—any size screen.

FULL PLANS \$2  
RELCO, Dept. RE-9, Box 10563, Houston 18, Tex.

**TV TUNERS REBUILT**  
and Exchanged \$9.50 plus  
All Makes-Models ONLY\* ship-  
charges.

- Includes All Parts Except Tubes
- Aligned to Factory Specifications
- 90 Day Full Warranty
- Practical repairs

Ship tuner complete with tubes, broken parts, tuner cover,  
Give model # and state complaint.  
VALLEY TV TUNER SERVICE • PO 9-4730  
5641-A Cahuenga Blvd., North Hollywood, Calif.

**NEW\*\*\*SEMI-CONDUCTORS**  
PNP—2N63, 2N64, 2N362, 2N381, 2N382, 2N383,  
2N404, 2M1681, 2N1706, 2N1008, 2N1966, 807, 901V,  
987A, Patch transformer, 4 watts . . . \$1.00  
PNP—2N77, 2N2076, 2N274, 2N284, 2N356A, 2N398A,  
2N526, 2N626, 2N600, Dynaquads T/1595, 25B171b,  
25A101a  
NPN—2N147, 2N214, 2N367A, 2N377A, 2N385A, 2N388,  
2N558, 2N679, 2N439, 2N1000, 2N1302, 2N1304,  
2N1473, 2N1605  
PNP—Power, 2N173, 2N441, 2N442, 2N443, 2N540,  
2N1011, 2N2048, 2N705, 874123, 11L1E, \$1.25  
PNP—Power, 2N176, 2N358, 2N255, 2N307A, 2N1283,  
2N1227  
PNP—2N456 T/I, 2N533 Delco . . . \$2.50  
Deluxe Transistor Ignition System 6-12 volt negative  
grd., Complete Tungsol unit, factory packed, with in-  
structions R.C.A., Sylvania, T/I, Tungsol, G.I., Cleve-  
land, Philco, Delco, Motorola, etc.

**DIODES**  
Germanium: 1N34a, 1N54, 1N80, 1N90, 1N126, TS4b,  
CTP-563 . . . 12/\$1.00  
Silicon: 1N91, 1N181, 1N217, 1N537, PS770, SG2101,  
1N411 . . . 30¢  
1N483b, 1N484, 1N628, GP150, 18 Amp, Motorola 60c  
Zeners: SV3372, 114 V, 1N429—6.2 V, H92—18V, 30c  
12 volt—1 watt, SCR 3 amp, 100PIV . . . \$1.00  
1N2840b, 1N2843b, Motorola, To 3 case . . . \$5.00

**ELECTROLYTICS & TANTALYTICS**  
8 assorted; all popular values, sub-min. U.S.A. 8/\$1.00  
10 ass'd; Tantalitics, Famous Brands . . . 10/\$2.00

**TRANSFORMERS**  
Driver, Interstage, & Output, C.T., Sub-min . . . 3/\$1.00  
Filament, 24 volt, sec., Pri 115 VAC, 60 cy . . . \$1.25  
C.B. Patch transformer, 4 watts . . . \$1.50  
455 Kc. Osc. I.F. center tapped 1/2 $\times$ 3 $\times$ g, all stages 4/\$1.00  
Volume Controls with switch, sub-min., 2000, 2,500,  
5K, 10K . . . 3/\$1.00  
Speakers; sub-min; 8 ohms output, 100 ohms output \$1.00  
Speakers; Tweeters 3/2 inch . . . \$1.50  
Variable capacitors, 3 $\times$ 3 $\times$ 4" superhet, plastic . . . 75c  
Circuit breakers, push-button . . . 25c  
Tiny switches; SPST, miniature . . . 25c  
Pin jacks, pin plugs, "H.H. Smith" red, black, green 10c  
Adapters; RCA plug to PL 68, PL 55 . . . 50c  
P.C. Boards, loaded with transistors, components, etc.  
T/I . . . \$1.00  
20K Precision wire-wound "Helipot" 5% tol. min. \$1.50  
Transistor push-button terminal posts, gold-plated \$1.00  
"Turner" Model 80 microphone . . . \$6.95

Write for Free Catalog  
Minimum order \$3.00 prepaid  
Postage free in U.S.A.  
**TRANSISTORS UNLIMITED COMPANY**  
Post Office Box 442, Great Neck, L. I., N. Y.  
Warehouse & Office  
462 Jericho Turnpike, Mineola, N. Y.  
516-PI 7-7221

## Solve Electronics Problems Fast With Special New Slide Rule

Professional, high quality instru-  
ment . . . specifically designed for  
electronic engineers and techni-  
cians . . . made to our rigid  
specs by Pickett & Eckel. Has  
special scales for solving react-  
ance and resonance frequency  
problems. Accurately and quickly  
locates decimal points. Carries  
widely used formulas and con-  
version factors not found on any other  
slide rule. Comes complete with  
top-grain leather carrying case, il-  
lustrated instruction manual, 90  
day consultation service — all  
for just \$14.95. Carries lifetime  
guarantee against defects in mater-  
ial and workmanship.



## SEND COUPON TODAY

TO: CLEVELAND INSTITUTE  
OF ELECTRONICS

1776 E. 17th St., Dept. RE-102 Cleveland, Ohio 44114

Please send me your electronics slide rule.  
I am enclosing \$14.95. (If not fully satisfied  
after 10 day trial, CIE will refund payment.)  
 Please send additional descriptive literature.

Name \_\_\_\_\_  
(Please Print)  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## FREE CATALOG!

148 PAGES • NEARLY 4,000 BARGAINS  
OPTICS • SCIENCE • MATH

Completely new, enlarged edition, new  
items, categories, illustrations, 148 new,  
easy-to-read pages packed with nearly  
4000 items. Dozens of electrical and elec-  
tromagnetic parts, accessories. Enormous  
selection of Astronomical Telescopes,  
Microscopes, Binoculars, Magnifiers, Mag-  
nets, Lenses, Prisms. Many war surplus  
items . . . for hobbyists, experimenters,  
workers. (Factory direct prices.)

## CLIP AND MAIL COUPON TODAY

EDMUND SCIENTIFIC CO., Barrington, N. J.  
PLEASE SEND ME FREE CATALOG "EH"  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

## LOW-COST BUSINESS AIDS FOR RADIO-TV SERVICE

Order books, invoice forms, job ticket  
books, service call books, cash books and  
statement books for use with your rub-  
ber stamp. Customer file systems, book-  
keeping systems, many others. Write for  
FREE 32 PAGE CATALOG now.  
OELRICH PUBLICATIONS  
6556 Higgins Rd., Chicago, Ill. 60656

## BRAND NEW BYPA TV TEST TUBE

"A must for every serviceman" (Radio Elec-  
tronics, Jan. 1964 issue, page 32)—Only  
\$17.95. Send check or money order for  
immediate delivery to:  
**SAMSON KINESCOPE INC.**  
250 N. Goodman St.  
Rochester N.Y. 14607

# ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors which may appear in the index below.

Allied Radio Corp.	85-86
Amperex Electronic Corp.	Second Cover
Antenna Specialists Co., The	91
B & K Manufacturing Co.	18
Blonder-Tongue	14
Bozak	102
Brooks Radio & TV Corp.	92-93
Cadre Industries Corp.	103
Capitol Radio Engineering Institute, The	29-32
Castle TV Tuner Service, Inc.	78
Centralab (Electronics Div. of Globe-Union, Inc.)	16
<b>CLASSIFIED</b>	<b>111</b>
Cleveland Institute of Electronics	64-67, 109
Conar (Div. of National Radio Institute)	88
Coyne Electronics Institute	103
Data Corp., The	106
DeVry Technical Institute	7
EICO Electronic Instrument Co., Inc.	89
Electronic Measurements Corp. (EMC)	81
Gernsback Library, Inc.	100, 104
Grantham School of Electronics	11
Heald's Engineering College	108
Heath Co.	68-71
International Crystal Manufacturing Co., Inc.	112
Jensen Manufacturing Co. (Div. of the Muter Co.)	Third Cover
Jerrold Electronics	25
JFD Electronics Corp.	73
Johnson Co., E. F.	24
Lafayette Radio Electronics	94-99
Mallory & Co., Inc., P. R.	9
<b>MARKET CENTER</b>	<b>109</b>
Moog Co., R. A.	93
National Radio Institute	19-20, 79
National Technical Schools	5
North American Philips Co., Inc. (NORELCO)	23
Perma-Power Co.	87
Philco-Teclrep Division (Subsidiary of Ford Motor Co.)	24
Polypaks	109
Progressive "Edu-Kits", Inc.	83
Quam-Nichols Co.	17
Quietrole Co.	106
Rad-Tel Tube Co.	78

Radio Shack	3
RCA Electronic Components & Devices	Fourth Cover
RCA Institutes Inc.	10, 63, 75-77, 90
RCA Test Equipment	27
Reading Improvement Program	102
Sams & Co., Inc. Howard W.	15, 74
Sarkes Tarzian, Inc. (Tuner Service Div.)	26
<b>SCHOOL DIRECTORY</b>	<b>107</b>
Scott, Inc., H. H.	101
Sencore	28
Shure Brothers, Inc.	21
Sonotone Corp.	12
Sylvania (Subsidiary of General Telephone & Electronics)	22
Tarzian, Inc. Sarkes (Tuner Service Div.)	26
Tram Electronics, Inc.	91
United Radio Co.	105
University, LTV (Div. of Ling-Temco-Vought, Inc.)	13
Weller Electric Corp.	82
Wen Products, Inc.	10
Winegard Co.	90

<b>MARKET CENTER</b>	<b>108-109</b>
Cleveland Institute of Electronics	Editors and Engineers, Ltd.
Edmund Scientific Co.	Fair Radio Sales
Oelrich Publications	Relco
Samson Kinescope, Inc.	Stereo-Parti
Tab	Transistors Unlimited Co.
Valley TV Tuner Service	Warren Electronic Components
<b>SCHOOL DIRECTORY</b>	<b>107</b>
American Institute of Engineering & Technology	Electronic Technical Institute
Indiana Home Study Institute, The (Eastern Div.)	Milwaukee School of Engineering
Northridge College of Science & Engineering	Northrop Institute of Technology
Philadelphia Wireless Technical Institute	Tri-State College
Valparaiso Technical Institute	

**WORLD'S EQUIVALENT TUBES**  
(Bran's Equivalent Tubes Vade Mecum)

Over 43,900 comparisons and replacements. Covers standard tubes to advanced comparisons.

Book #493... **\$8.00** (Foreign \$8.50)  
From your electronic parts distributor or  
**EDITORS and ENGINEERS, Ltd.**  
Summerland 5, California 93067

**RENT**

FREE BROCHURE

**STEREO TAPES**

Postpaid 2 to 5 day delivery (48 States)

**eo stereo-parti**

1616-D TERRACE WAY, SANTA ROSA, CALIF.

**TREASURE FINDERS**

Supersensitive new transistor models detect buried gold, silver, coins, firearms. Locate Indian burial grounds, explore beaches, shacks, ghost towns. \$19.95 up. FREE CATALOG.

RELCO Dept. RE-9; BOX 10563, Houston, Texas 77018

**WANT BACK ISSUES?**


Back numbers of most issues of RADIO-ELECTRONICS are available upon request. This year's issues 50¢; Last year's issues 55¢; Previous year 60¢, etc., up to a maximum of \$1 per copy. **RADIO-ELECTRONICS**, 154 West 14th St., New York N. Y. 10011.

**1-AMP-700V SYLVANIA EPOXY RECTIFIERS**

SILVER AXIAL LEADS

**5 for 1.00**

COMPARE UP TO 10.00

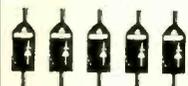


**ELECTROSTATIC TWEETER \$1.49**

MADE BY LORENZ FOR GRUNDIG-4" sq.

Illustration resembles tweeters in stock

EACH 2 for 2.50

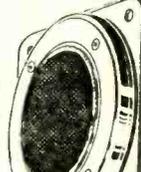

**TESTED 10 WATT ZENERS \$1.49 EA.**

WRITE FOR OTHER VOLTAGES

<input type="checkbox"/> 5V	<input type="checkbox"/> 42V
<input type="checkbox"/> 6V	<input type="checkbox"/> 45V
<input type="checkbox"/> 12V	<input type="checkbox"/> 60V
<input type="checkbox"/> 20V	<input type="checkbox"/> 70V
<input type="checkbox"/> 24V	<input type="checkbox"/> 80V
	<input type="checkbox"/> 90V
	<input type="checkbox"/> 100V
	<input type="checkbox"/> 110V
	<input type="checkbox"/> 124V



**DOUBLE BONUS \$25**

25¢ for handling PLUS FREE

**CHOOSE ANY \$1 ITEM FREE**

GET BOTH GIFTS FREE WITH EVERY \$10 ORDER

FREE WORTH OF:

- Transistors
- Rectifiers
- Condensers
- Diodes
- Knobs
- Coils, etc.

**1.95 3-TRANSISTOR AMPLIFIER**

Only 3"x2"x3/4" • Wired, subminiature

Printed Circuit • W/Transistors

**6-AMP-1000V SILICON STUD RECTIFIERS \$1.49**

2 FOR

**30 SPRAGUE "EPOXY" MOLDED CONDENSERS, yellow case, to 1mf, asstd voltages \$1**

**WORLD'S MOST POPULAR \$1 PARTS PAKS**

30 MOLDED COND., black beauty, mylar, vit-Q \$1

10 PHONO PLUG-n-JACK SETS, tuners-amps... \$1

10 TANTALUM ELECTROLYTICS, worth \$15... \$1

60 HI-Q RESISTORS, 1/2, 1, 2W to 1 meg, 5% too \$1

100 ASST. HALF WATT RESISTORS, 5% too \$1

35 ALLEN BRADLEY & IRC TWO WATERS \$1

50 COILS & CHOKES, rf-if, osc-peaking, etc \$1

\$25 RADIO-n-TV SURPRISE, wide variety \$1

10 TRANSISTOR ELECTROLYTICS, 10 to 100mf \$1

50 RADIO & TV KNOBS, asstd. colors, styles \$1

10 VOLUME CONTROLS to 1 meg, switch too \$1

50 MICA CAPACITORS, to .01mf, silvers too \$1

**FACTORY TESTED SEMI-KON-DUCTORS**

1-SILICON NPN "PLANAR" 2N718, TO18 case... \$1

6 TOP HAT RECTIFIERS, 750 mil, 400 volts... \$1

2-500 MC PNP MESA TRANSISTORS, TO18 case \$1

20 WATT NPN SILICON MESA 2N1648 tr'stistors \$1

1-2N705 MESA 300 mc, 300 mw, pnp, TO18... \$1

2-25-AMP SILICON STUD RECTIFIERS... \$1

6 TRANSISTOR RADIO SET, osc-lfs-driver, p-p \$1

2 'MESA' 4-WATT TRANSSTR., n-pn, silicon, TO5... \$1

15 UPRIGHT SILICON DIODES, worth \$40... \$1

4 GENERAL ELECTRIC 2N170 RF NPN transistors \$1

HOFFMAN SATELITE SILICON SUN CELL, 3/8x1" \$1

5 GENERAL ELECTRIC 2N107 PNP transistors \$1

25 SEMI-KON-DUCTORS: transistors, diodes, rect. \$1

3 2N255 PWR TRANSISTORS, or equal, TO3 case \$1

5 SUN BATTERIES TO 1 1/2" sizes, lite sensitive \$1

1 3N35 TETRODE 150me transistor, silicon... \$1

3 CB5 20-WATT TRANSSTR., pnp, stud, 2N1320 \$1

2-2N341 NPN SILICON TRANSISTORS, 1 watt \$1

15 NPN TRANSISTORS, asst types and cases... \$1

15 PNP TRANSISTORS, asst types and cases... \$1

10 FAMOUS CK722 TRANSISTORS, pnp... \$1

3 CB5 35W PWR TRANSSTR., 2N1434, pnp, stud... \$1

10 NPN SWITCHING transistors, 2N440 equals \$1

**50-WATT TRANSISTORS 3 for \$1**

gold plated • TO36 case • untested

4 CK721 TRANSSTR in new aluminum case, pnp... \$1

4 SUBMINIATURE 2N131 TRANSSTR, rf-if, pnp... \$1

SILICON PLANARS: 2N497, 2N498, each... \$1

2 TRANSISTOR 1N429 ZENER REFERENCES... \$1

1 85W SILICON PWR TRANSSTR, n-pn, like 2N1212... \$1

3 2N243 750 MW NPN SILICON transistors, TO22... \$1

6 ZENER DIODES, upright styles, assorted... \$1

TEXAS 20-WATT, TO5, heat sink stud, 2N1042 \$1

1 2N964 EPITAXIAL MESA, 500 MC, PNP, TO-18... \$1

10 NPN SWITCHING TRANSISTORS, TO 5 case... \$1

3 2N1264 UHF TRANSISTORS, TO5 case... \$1

4 G.E. 2N43 OUTPUT TRANSISTORS, TO5 case... \$1

3 TEXAS 20W TRANS'RS, 2N1035, heat-sink, TO5 \$1

1 2N706 500MW, 300MC NPN PLANAR, TO18 \$1

6 2N112 TYPE IF, OSC TRANSSTR., TO22 Untested... \$1

4 SYLVANIA 2N35 NPN, transistors, TO22... \$1

3 1-WATT ZENER DIODES, axial leads, 6V... \$1

**SALE! SALE! SALE!**

**25 \$1 per pak**

25 TRANSISTORS: audio switching, rf untested

25 TOP HAT RECTIFIERS 750 mil untested

25 EPOXY RECTIFIERS axial lead, 750 mil untested

25 GERMANIUM DIODES 1N34, 1N48 untested

**SILICON POWER DIODE STUDS**

Amps	Volts	Sale	Amps	Volts	Sale	Amps	Volts	Sale
6	300	37¢	25	200	1.60	50	200	3.75
6	400	59¢	25	300	1.75	100	25	1.50
6	600	69¢	25	400	1.95	100	50	1.80
6	800	89¢	25	600	2.50	100	100	2.2
6	1000	95¢	25	50	1.05	100	150	2.75
12	50	49¢	25	400	1.29	240	25	4.50
12	100	69¢	25	150	1.50	240	50	4.95
12	200	88¢	25	200	1.75	240	100	5.90
12	300	1.19	25	300	1.95	240	150	6.75
12	400	1.37	25	300	2.5*	240	200	8.25
12	50	.99	50	25	1.50	240	300	12.50
25	100	1.29	50	50	1.50	240	400	19.95
			50	100	2.95			

**10¢ FOR OUR "FALL" BARGAIN CATALOG ON:**

Semiconductors Poly Paks Parts

**POLY PAKS**

TERMS: send check, money order, include postage-avg. wt. per pak 1 lb. Rated, net 30 days. CODs 25%

P.O. BOX 942R  
SO. LYNNFIELD, MASS.  
"PAK-KING" OF THE WORLD

## CLASSIFIED ADVERTISING ORDER FORM

Please refer to heading at top of classified section for complete data concerning terms, frequency discounts, closing dates, word count, etc.

No. of Words { @ .30 Non-Commercial Rate } = \$  
 { @ .55 Commercial Rate }

Total Enclosed \$

Insert \_\_\_\_\_ time(s)

Starting with \_\_\_\_\_ issue

Payment must accompany order unless placed through accredited advertising agency. 94

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 154 WEST 14TH ST., NEW YORK, N.Y. 10011

# new Books

**TRANSISTORIZED MINIATURE AMPLIFIER AND TUNER APPLICATIONS**, by Rufus P. Turner. Lafayette Radio Electronics Corp., Syosset, N. Y. 11791. 5½ x 8½ in., 95 pp. Paper, \$1.50

Practical uses for Lafayette's ready-built tuner and series of audio amplifiers now available. Ham radio, control and test equipment are represented.

**AUDELS PROGRAMMED BASIC ELECTRICITY COURSE**, by Milton Rosenberg. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5 x 6¾ in., 138 pp. Cloth, \$4.

A comprehensive course from basic electron theory through dc and ac circuit theory to measurement techniques. Presented in "programmed instruction" style. Reader begins at top of right-hand page numbered 12 with question 1, answers it,

checks his answer by turning to next right-hand page (13). There he also finds question 2, and so on through to page 137, for a total of 125 questions. Then he turns the book upside down and begins from the back, doing questions 126-250. A total of 8 such cycles completes the course (1,000 questions).

**"EVEREADY" BATTERY APPLICATIONS AND ENGINEERING DATA**. Battery Engineering Dept., Union Carbide Corp., Consumer Products Div., 270 Park Ave., New York, N.Y. 10017. 5½ x 8½ in., 515 pp. Paper. Free on request on company letterheads.

Possibly the most complete reference guide to dry batteries ever assembled. Covers carbon-zinc, alkaline, nickel-cadmium, mercury and silver batteries with practically all the information the reader could imagine asking for.

**PASSIVE AUDIO NETWORK DESIGN**, by Howard M. Tremaine. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5½ x 8½ in., 288 pp. Paper, \$4.95

Attenuators, equalizers and filters with applications to amplifiers, recorders, cross-overs, etc. Many charts and tables simplify the computations.

**COLOR TELEVISION FUNDAMENTALS**, by Milton S. Kiver. Second Edition. McGraw-Hill Book Co., 330 W. 42 St., New York, N.Y. 10036. 6 x 9 in., 335 pp. Cloth, \$10.95.

For TV technicians who wish to keep up to date on the latest circuits. One chapter is devoted to detailed alignment procedures for typical receivers.

**ESSENTIALS OF DIELECTROMAGNETIC ENGINEERING**, by H. M. Schlicke. John Wiley & Sons, Inc., 605 Third Ave., New York 16, N.Y. 5¼ x 9 in., 242 pp. Cloth, \$9.50

An advanced text on two important materials: ferrites and high-permittivity dielectrics, covering theory and applications.

**PRACTICAL TRANSISTOR THEORY**, by E. Patrick Wiesner. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5½ x 8½ in., 128 pp. Paper, \$2.50

An elementary coverage of semiconductors, their characteristics and applications to electronics.

**COMMUNICATION FOR ENGINEERS**, by Charles A. Ranous. Allyn & Bacon, Inc., 150 Tremont St., Boston 11, Mass. 5¼ x 9 in., 183 pp. Cloth, \$5.95

How to prepare technical speeches, instructions and reports, with actual examples and procedures taken from practice.

**DISCOVERING THE UNIVERSE**, by Bernard and Joyce Lovell. Harper & Row, 49 E. 33 St., New York 16, N.Y. 7½ x 10 in., 136 pp. Cloth, \$3.95.

The distinguished British radio astronomer and his wife have turned out a very attractive work, both in text and illustration. Starting with early astronomy and early radio astronomy, they take us on through the present day (with, of course, plenty of mention of the Jodrell Bank telescope), through space probes and rockets, and on to the extreme reaches of the universe.

**RUTHERFORD AND THE NATURE OF THE ATOM**, by E. N. da C. Andrade. Doubleday & Co., Inc., 575 Madison Ave., New York 22, N.Y. 4¼ x 7 in., 218 pp. Paper, \$1.25.

A highly readable, carefully worked-out life of the founder of atomic physics. By one of his earlier students.

**TELEVISION TAPE FUNDAMENTALS**, by Harold E. Ennes. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. spiral bound. 5½ x 8½ in., 256 pp. Paper, \$5.95

Operation and maintenance of TV tape equipment and systems. Detailed analysis of circuits, techniques and waveforms for engineers and students. END

# ELECTRONICS



## Engineering-Technicians

**Bachelor of Science Degree, 30 Months**  
 Save Two Years' Time

The Nation's increased demand for Engineers,

Electronic Technicians, Radio TV Technicians is at an all time high. Heald Graduates are in demand for Preferred High Paying Salaries. Train now for a lucrative satisfying lifetime career.

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
  - Electrical Engineering (B.S. Degree)
  - Mechanical Engineering (B.S. Degree)
  - Civil Engineering (B.S. Degree)
  - Architecture (B.S. Degree) (36 Months)

**Approved for Veterans**  
**DAY AND EVENING CLASSES**

Write for Catalog and Registration Application.  
 New Term Starting Soon.

Your Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_

# HEALD'S

**ENGINEERING COLLEGE**  
 Est. 1863—101 Years  
 Van Ness at Post, RE  
 San Francisco, Calif.

# Classified Ads

**COMMERCIAL RATE** (for firms or individuals offering commercial products or services): 55¢ per word . . . minimum 10 words.

**NON-COMMERCIAL RATE** (for individuals who want to buy or sell personal items): 30¢ per word . . . no minimum.

Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for November issue must reach us before September 14th.

**WORD COUNT:** Include name and address. Name of city (Des Moines) or of state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8x10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

## EDUCATION/ INSTRUCTION

HIGHLY-effective home study review for FCC commercial phone exams. Free literature! **COOK'S SCHOOL OF ELECTRONICS**, Craigmont, Idaho 83523.

FCC LICENSE in 6 weeks. First Class Radio Telephone. Results Guaranteed. **ELKINS RADIO SCHOOL**, 2603E Inwood, Dallas, Tex.

PHOTOGRAPHY FOR PLEASURE or profit. Learn at home. Practical basic training. Long established school. Free book. **AMERICAN SCHOOL OF PHOTOGRAPHY**, 835 Diversey Parkway, Dept. 1876, Chicago, Ill. 60614.

SLEEP LEARNING. Hypnotism! Tapes, records, books, equipment. Details, strange catalog FREE. **RESEARCH ASSOCIATION**, Box 24-RD, Olympia, Wash.

## BUSINESS AIDS

1,000 Business Cards, "Raised Letters" \$3.95 postpaid. Samples. **ROUTH RE9**, 2633 Randleman, Greensboro, N.C. 27406.

JUST STARTING IN TV SERVICE? Write for FREE 32 PAGE CATALOG of Service Order books, invoices, job tickets, phone message books, statements and file systems. **OELRICH PUBLICATIONS**, 6556 W. Higgins, Chicago, Ill. 60656.

## Electronics

BEFORE You Buy Receiving Tubes, Test Equipment, Hi-Fi Components, Kits, Parts, etc. . . . send for your Giant Free Zalytron Current Catalog, featuring all STANDARD BRAND TUBES all Brand New Premium Individually Boxed, One Year Guarantee—all at BIGGEST DISCOUNTS in America! We serve professional servicemen, hobbyists, experimenters, engineers, technicians. WHY PAY MORE? **ZALYTRON TUBE CORP.**, 469R Jericho Turnpike, Mineola, N. Y.

TRANSISTORIZED Treasure Detectors Find buried gold, silver, coins. \$19.95 up. Kits available. Free catalog. **RELCO-A25**, Box 10563, Houston 18, Texas.

PRINTED CIRCUIT BOARDS. Hams, Experimenters. Catalog 10¢. **P/M ELECTRONICS**, Box 6288, Seattle, Wash. 98188.

TRANSISTOR TELEVISION TRANSLATORS. Re-broadcast 25 miles, meets F.C.C. specifications, Battery powered. **KEITH ANDERSON COMPANY**, Piedmont, So. Dak.

7" TV TEST TUBE—\$6.99. Tubes 6146—\$2.95; 6211 (12AU7 equiv.) 39¢, 3 for \$1. Germanium diodes, tested, equiv. 1N34, 1N60 etc., 30 for \$1. Tophat silicon rectifiers, 750MA—1000 PIV 75¢. Transistors, tubes, resistors, condensers, etc., bargain priced. Free catalog. **ARCTURUS ELECTRONICS**, Dept. RE, 502-22nd St., Union City, N. J. 07087.

DIAGRAMS FOR REPAIRING RADIOS \$1.00. Television \$2.50. Give make, model. **DIAGRAM SERVICE**, Box 1151 RE, Manchester, Conn.

IGNITION! Transistor, Coil, Ballast \$7.50. Free Parts List. **TRANSFIRE**, Carlisle 20, Mass.

CONVERT any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2. **RELCO**, Box 10563, Houston 18, Tex.

TRANSISTORS, SCR's, diodes, nickel-cadmium batteries, meters, crystals, components. Quality guaranteed. Send 10¢ for catalog. **ELECTRONIC COMPONENTS CO.** P.O. Box 2902B, Baton Rouge, La. 70821.

TV CAMERAS, transmitters, converters, etc. Lowest Factory prices. Catalog 10¢. **VANGUARD**, 190-48-99th Ave., Hollis, N.Y. 11423.

GOVERNMENT SURPLUS JEEPS—\$62.50, Voltmeters—\$1.05, Transmitters—\$6.18, Oscilloscopes, Walkie-Talkies, Multimeters. Typical Surplus Prices. Exciting Details Free. Write: **ENTERPRISES**, Box 402-F19, Jamaica 30, N.Y.

JAPANESE MERCHANDISE from Radio to Camera. Any inquiries answered. Catalog, information and pricelist \$1.00. **TOMIO UENO**, No. 538 Shibamatacho Katushikaku, Tokyo, Japan.

PROFESSIONAL ELECTRONICS PROJECTS—Organs, Timers, Computers, etc.—\$1 up. Catalog free. **PARKS**, Box 1665, Seattle, Wash. 98125.

FREE ELECTRONICS CATALOG. Tremendous bargains. **ELECTROLABS**, Department C-228G, Hewlett, N.Y. 11557.

\$100.00 Weekly spare time selling Banshee TS-30 electronic transistor ignitions systems and coils. First major ignition improvement in over 50 years. Big demand. Details, write. **SLEEP ELECTRONICS**, Drawer 178RE, Ellenton, Fla. 33532.

DIAGRAMS for 1919 to 1955 radios \$1.00. Condensed television diagrams \$1.00. Give model. **A. ADAMS**, 866 Memorial Ave., Williamsport, Pa. 17702.

TRANSISTOR IGNITION. Three transistor \$14.95. Also complete system, 400:1 coil \$15.00. Catalogue, write. **ELECTRO-MART**, 1616 South 81st Milwaukee, Wis. 53214.

RESISTORS metal-oxide film. Low noise level. Long life operation. 1/8 watt 12¢. 1/4 watt 10¢. precision. 1/2 watt 7¢. 1 watt 9¢. 2% 5%. List on request. **O. M. FARNSWORTH**, 88 Berkeley St., Rochester 7, N.Y.

DON'T BUY any special purpose or industrial transmitting tubes until you receive our special quotations. Lowest prices in USA. Cash paid for brand new tubes of all descriptions irrespective of age or quantity. **UNITED RADIO CO.**, Newark, N.J.

SALVAGE CIRCUIT BOARDS packed with dozens of transistors, diodes, miniature transformers, capacitors etc. Assortment "A" \$5.00, "B" \$4.00, "C" \$3.00, all different, postpaid. **ENGINEERING ASSOCIATES**, 434 Patterson Road, Dayton, Ohio 45419.

15 DISTANCE One-tube plans-25¢; One-tube Handbook-50¢. Includes Transistor experiments, catalog. **LABORATORIES**, 1131-B Valota, Redwood City, Calif.

RADIO & TV TUBES 33¢. Free List. **CORNELL**, 4217-E University, San Diego, Calif. 92105.

CAPACITORS disc ceramic, 50 assorted \$1.00 HI-Q, NPO, N-750. **O. M. FARNSWORTH**, 88 Berkeley St., Rochester 7, N.Y.

## General

LEARN MORSE International Code Alphabet in half hour. Mail \$2.00 check or money order for laminated, pocket-size, fifty word mnemonic to: **MNEMONICS ASSOCIATES**, 56 Grand Street, White Plains, N.Y. 10601.

TV SERVICE ORDER BOOKS for use with your rubber stamp. Duplicate or triplicate. Low cost. Write for FREE 32 PAGE CATALOG and Special Rubber Stamp Offer. **OELRICH PUBLICATIONS**, 6556 W. Higgins, Chicago, Ill. 60656.

## Canadians

GIANT SURPLUS BARGAIN PACKED CATALOGS. Electronics, Hi-Fi, Shotwave, Amateur, Citizens Radio, Rush \$1.00 (Refunded). **ETCO**, Box 741, Dept. R. Montreal, Canada.

## WANTED

PHOTOGRAPHS and TRANSPARENCIES wanted — to \$500.00 each. Valuable information — Free. Write **PICTURE**, Box 74607, Hollywood, 90004.

G-R, H-P, L&N, etc. Special tubes, manuals, military electronics. **ENGINEERING ASSOCIATES**, 434 Patterson Road, Davton 19 Ohio.

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! **BARRY**, 512 Broadway, New York, N. Y. 10012, 212 WALKER 5-7000.

## SERVICES

SPEAKER RECONING. Satisfaction Guaranteed. **C & M RECONE CO.**, 18 E. Trenton Ave., Morrisville, Pa.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. **HAZELTON INSTRUMENT CO.**, 128 Liberty St., New York, N.Y.

TV TUNERS Rebuilt and Aligned per manufacturers specification. Only \$9.50. Any Make UHF or VHF. We ship COD Ninety day written guarantee. Ship complete with tubes or write for free mailing kit and dealer brochure. **JW ELECTRONICS**, Box 51 D, Bloomington, Ind.

METERS—MULTIMETERS REPAIRED and calibrated. **BIGELOW ELECTRONICS**, Box 71-B, Bluffton, Ohio.

RCA TEST EQUIPMENT. Authorized Repair & Calibration Center, Nationwide. **EDWIN BOHR/ELECTRONICS P.O.** Box 4457 Chattanooga, Tenn. 37415.

COMPLETE ELECTRONIC INSTRUMENT repairs and calibrations, fast, cost saving service. **GENERAL ELECTRONICS Sales & Service Co.**, Box 52362, New Orleans, La. 70150.

TRANSISTORIZED products dealers catalog, \$1. **INTERMARKET**, CPO 1717, Tokyo, Japan.

BORROW \$1,233 AIRMAIL! Repay \$54 for twenty-nine months. State licensed. **POSTAL FINANCE**, Dept. 16-R, Kansas City 1, Kan.

## Money Making Opportunities

EARN TOP \$\$ in INDUSTRIAL WRITING part or full time-free lance or for industry! Learn professional secrets at home in spare time. No tech. know-how necessary. Prepare manuals, brochures, ads, reports little as six months. Get free book, **ATWS** Dept. 1, 5504 Hollywood Blvd., Hollywood 28, Calif.

HIGH WEEKLY EARNINGS! Address-mail letters featuring real merchandise. Get \$10 with every order-keep \$8 profit. Supplies furnished. Free particulars. **MODERN MERCHANDISING**, Box 357, Oceanside, N.Y.

## Audio—Hi-fi

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. **CARSTON**, 125-R East 88, N.Y.C. 10028.

RENT STEREO TAPES—over 2,500 different—all major labels—free brochure. **STEREO-PARTI**, 1616 Terrace Way, Santa Rosa, Calif.

HI FI, Ham Equipment, Discount Catalog. **MENDOTA CAMERA SHOP**, Mendota, Minn.

TAPE recorders, Hi-Fi components, Sleep-learning equipment, Tapes, Unusual values. Free catalog. **DRESSNER**, 1523 Jericho Turnpike, New Hyde Park 5, N.Y.


WINDSOR TAPE CLUB members HEAR BEFORE THEY BUY. Free "samplers" of new releases. Save on tape purchases—all major labels. Free Brochure—**WINDSOR TAPE CLUB**, Dept. A, Windsor, Calif.

HI-FI COMPONENTS. Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. **HI FIDELITY CENTER**, 1797 (R) 1st Ave., New York, N. Y. 10028.

SARKES Tarzian's Galaxie tensilized Mylar: 1800'/1.69, 2400'/2.79, 3600'/3.89. Postpaid. Free all-components, tape catalog. **POFE**, 1716-RE Northfield, Muncie, Ind.

DISCOUNT RECORDS—All labels. Write **CLIFF HOUSE** Box 42-R9, Utica, N.Y.

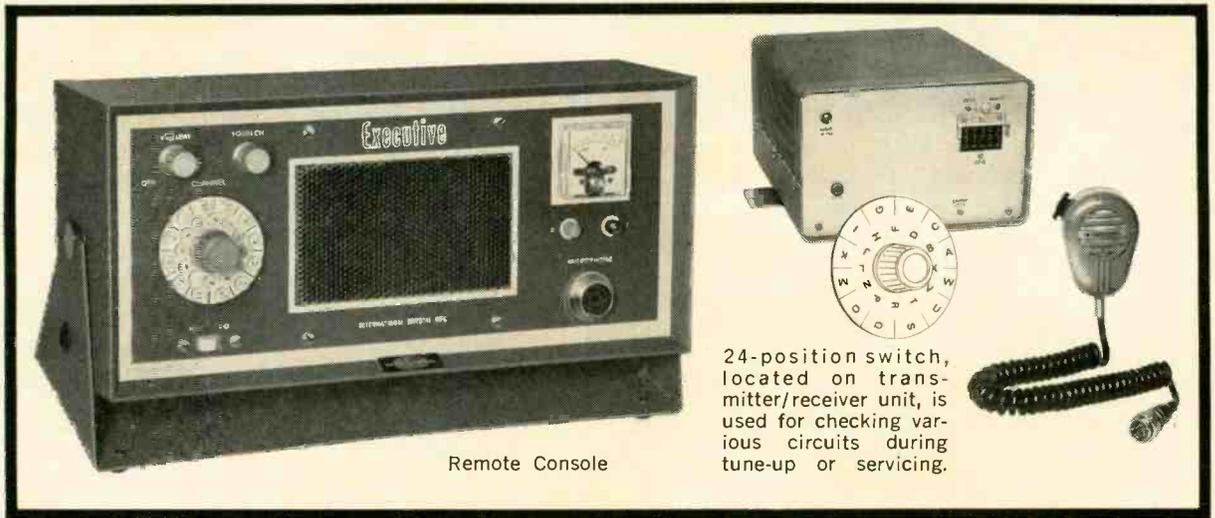SAVE 30-60%. Stereo music on tape, FREE! 50 page discount catalog. Blank tape, recorders, Norelco speakers, **SAXITONE**, 1776 Columbia Road, Washington, D.C. 20009.



Remote Console

24-position switch, located on transmitter/receiver unit, is used for checking various circuits during tune-up or servicing.

**INTERNATIONAL  
EXECUTIVE  
750-HB2**

**introducing**  
(with Built-in Test Circuits)

**INTERNATIONAL  
EXECUTIVE  
750-HM2**


It's totally new . . . a Citizens Band transceiver with built-in test circuits. Now at the "turn" of a switch, located on the transmitter/receiver unit, you can instantly check the operating performance of various circuits within the set. Makes tune-up and servicing easy. Checks filament, plate and input voltages, transmitter forward and reflected power, modulation, etc.

This "years ahead" built-in test feature has been incorporated into International's two new transceivers. The 750-HB2 with its functionally designed remote console\* for desk-top installation, and the 750-HM2 for mobile communication. Both transceivers have 23 crystal controlled channels, and operate on 115 vac, 12 vdc, and 6 vdc.

**NEW** Built-in test circuits. **NEW** Delayed/Expanded AVC. **NEW** Simplified cabling. **NEW** Built-in S/Meter and Transmit/Meter as standard equipment. **NEW** Microphone with improved characteristics for better "close talk" quality. **NEW** Speech Clipper/Filter Amplifier.

\*Base station remote console available separately. Ask for RMO-24 HB2

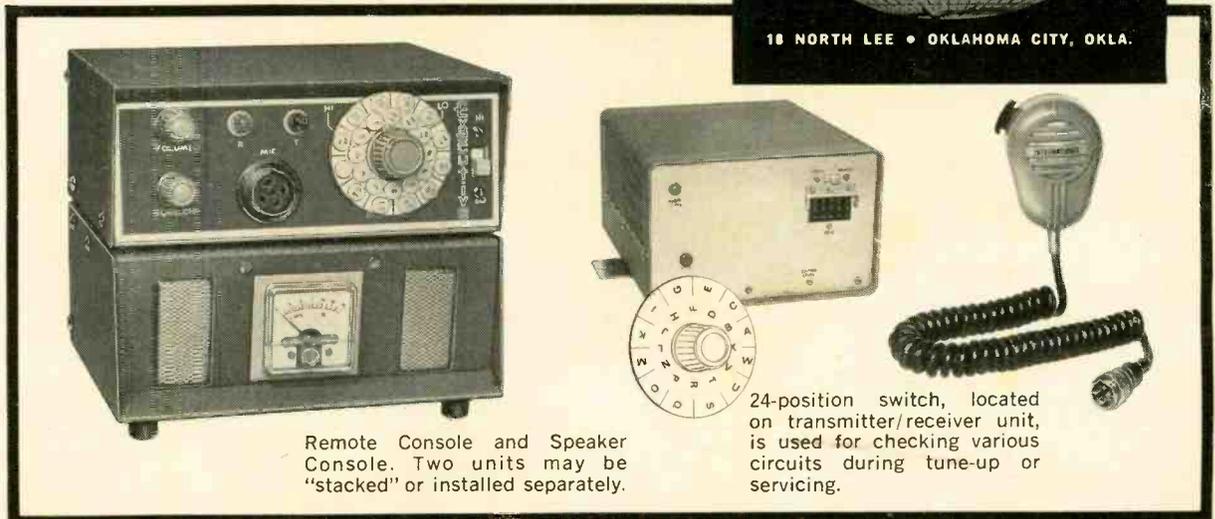See the 750-HB2 and 750-HM2 at your International dealer today! Ask him about his trade-in/trade-up plan.



Remote Console and Speaker Console. Two units may be "stacked" or installed separately.

24-position switch, located on transmitter/receiver unit, is used for checking various circuits during tune-up or servicing.

**ONLY JENSEN'S  
NEW DL-220  
GIVES YOU  
ALL THESE  
EXTRA  
VALUE  
FEATURES!**

1. Exclusive low-distortion FLEXAIR® suspension.
2. Super-low 25-cycle resonance for rock-bottom bass.
3. Circular horn wide-angle compression tweeter.
4. Fully adjustable HF-balance control on 30" cable.
5. Precision SYNTOX-6® magnetic system.
6. Die-cast metal housing for permanent alignment.
7. Binding post terminals for quick, easy connections.
8. Stable spider suspension for positive voice-coil centering.



**Model DL-220**  
3-ELEMENT 12" FLEXAIR® COAXIAL  
Outstanding performance at phenomenally low cost! Genuine compression HF unit and heavy-duty 12-inch woofer with mid-range radiator add up to smooth, full response. Power capacity, 20 watts. Frequency range, 25-16,000 cps. Resonance, 25 cps. HF balance control on 30" extension cable.  
DL-220 Net.....\$34.75

**NEW FROM JENSEN**

**DELTA** T.M.  
**S E R I E S**

**YOUR BEST SPEAKER VALUE**

**Model DL-120**  
Dual-Cone 12" FLEXAIR®  
12-inch, high-performance two-way loudspeaker similar to DL-220 but without coaxial HF unit. Frequency Range, 40-15,000 cycles; 20 watts.  
DL-120 Net.....\$21.50



**Model DL-80**  
Dual-Cone 8" FLEXAIR®  
A quality 8-inch high-fidelity unit for cost minded enthusiasts who demand Jensen quality. 50-15,000 cps; 20 watts.  
DL-80 Net.....\$15.25




Write for free brochure MY

RCA Calibration Center's Resistance Standard — accuracy 0.0002%.

RCA Frequency Standard being used to calibrate an oscillator


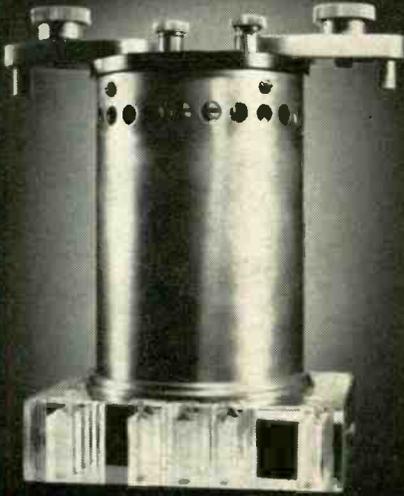
Recertifying Calibration Tubes on the RCA Static Characteristic Standard



Calibrating portable Standard Cell on the RCA Primary Voltage Standard.



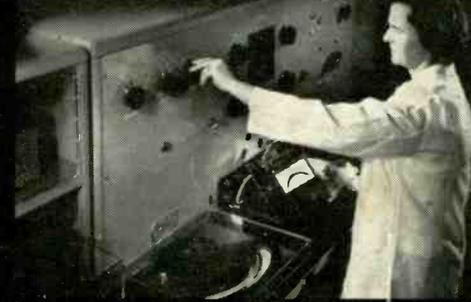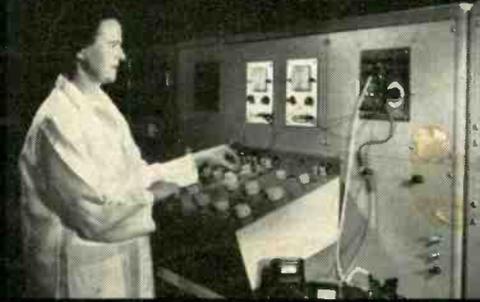Voltmeter being calibrated on the RCA AC Voltage and Current Standard.



# RCA ELECTRON TUBE RELIABILITY BEGINS HERE

## DEPENDABLE PERFORMANCE



## IS THE END RESULT

No reliability program for receiving tubes can be better than the test instruments and equipments it employs.

That's why RCA maintains the extensive Calibration Center in its Harrison, N. J., tube manufacturing plant (see photos above). The Center's responsibility: to assure that all measuring instruments and equipments, used in tube development from initial design through volume production, are accurate within rigidly specified limits. Here is how this is accomplished:

**1** The Calibration Center's own equipments are calibrated by standards (voltage, resistance, capacitance, frequency) whose values are regularly checked against standards of the National Bureau of Standards.

**2** Measuring instruments used in all research, design, development and application laboratories are calibrated directly from the Center's equipments.

**3** Sets of Calibration Tubes, selected to cover every type and family of tubes, are measured in the Calibration Center and used by the Center's personnel to periodically verify the accuracy of all factory tube-testing equipments.

**4** Sets of Control Tubes, evaluated under the supervision of the Calibration Center, constantly monitor the repeatability of factory tube-testing equipments.

Our Harrison Calibration Center is another example of the effort we make to assure the specified and dependable performance of every receiving tube that bears the emblem of RCA... performance that benefits you through customer satisfaction.

**SEE YOUR  
AUTHORIZED RCA DISTRIBUTOR  
FOR TOP-QUALITY  
RCA RECEIVING TUBES**

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N.J.



The Most Trusted Name in Electronics