


# Radio-Electronics

TELEVISION • SERVICE • HIGH FIDELITY  
HUGO GERNSBACK, Editor-in-chief

**SPECIAL SECTION**  
**CB**  
and  
**COMMUNICATIONS**

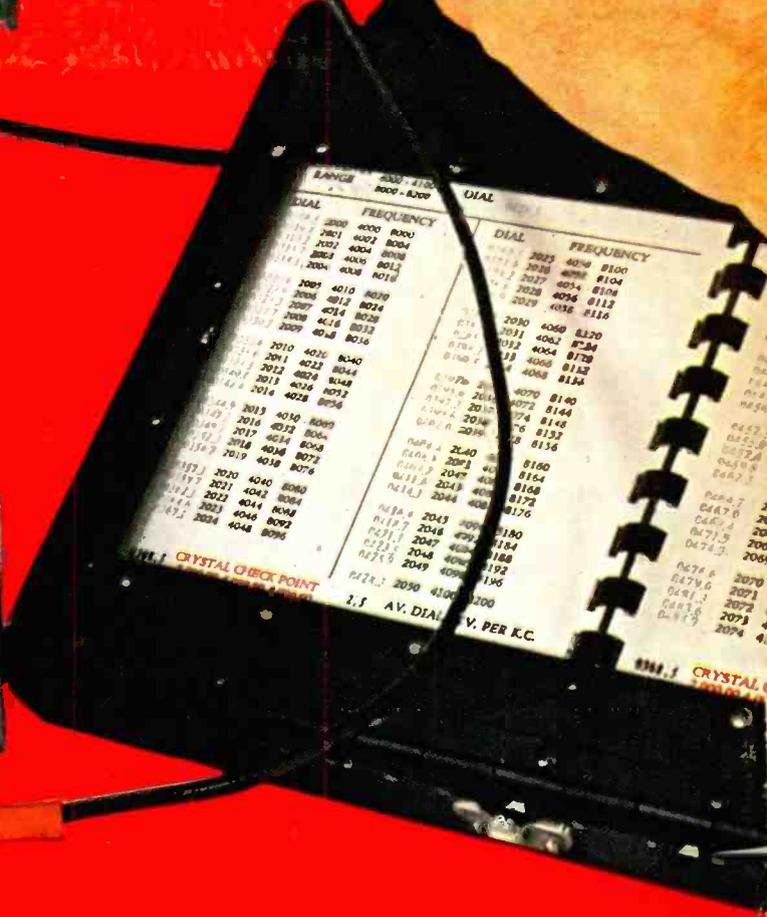**Lead-in: Weakest Link**

**FM Stereo:**  
**Station Directory**  
**Receiver Project**



**CB**  
**Troubleshooter's**  
**Casebook**



**Checking CB Frequency**

# ONE MILLION OHMS PER VOLT



## V-O-M

**Model 630-M**  
**VOLT-OHM-MICROAMMETER**

**\$210.00**

Suggested U.S.A. user net



Triplet Model 630-M features the input impedance of a VTVM with the convenience of a V-O-M. The 630-M's sensitivity is derived from the singular achievement of its basic 0-1 D.C. microampere movement. The 630-M incorporates no amplifiers, no warm-up, and no power requirements. Model 630-M is a true V-O-M whose engineering excellence is based on 60 years of instrument manufacturing, and contains the top quality associated only with Triplet.

- 1** 1,000,000 ohms per volt D.C. for greater accuracy on high resistance circuits. 20,000 ohms per volt A.C.
- 2** 1 ua Suspension Meter Movement. No pivots, bearings, or rolling friction. Extremely rugged. Greater sensitivity and repeatability.
- 3** 61 ranges, usable with frequencies through 100KC. Temperature compensated. 1½% D.C. accuracy, 3% A.C. in horizontal position.

**TRIPLET ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO**



MANUFACTURERS OF PANEL AND PORTABLE INSTRUMENTS; ELECTRICAL AND ELECTRONIC TEST EQUIPMENT

# RADIO SHACK® POLICE RADIOS!

ORIGINATED BY RADIO SHACK! NOW AVAILABLE: HIGH BAND OR LOW BAND!



*tune in crisis* with the original, official Realistic PATROLMAN™ — now available in both *high* and *low band* models — just 24.95 each. Each radio features

VHF plus the regular broadcast band for news and sports . . . continuous no-drift tuning . . . batteries and AC adapter. Proven performance — 1,000's already in use. Originated and sold only by Radio Shack, PATROLMAN™ is the most compact and reliable solid state VHF/MW radio in the world. *Quantity discounts available. Order today by mail, phone or in person. Immediate delivery.*

**POLICE**  
Civil Defense  
and Emergency  
**FIRE**  
Mobile Telephone  
and Industrial  
**TAXIS**  
Railroads  
and Trucks  
**PLANES**

## REALISTIC™ PATROLMAN™

Size 6x3 1/2". Net wt. 1 lb. Ship wt. 3 lbs.  
Built-in AM and VHF antennas.

<b>HIGH BAND</b> VHF: 147-174 MC AM: 535-1605 KC <b>24<sup>95</sup></b> Order #12-627	<b>LOW BAND</b> VHF: 30-50 MC AM: 535-1605 KC <b>24<sup>95</sup></b> Order #12-628
---	--

<b>JETSTREAM AIR BAND</b> VHF: 108-135 MC AM: 535-1605 KC <b>21<sup>95</sup></b> Order #12-626	<b>117V AC ADAPTOR</b> Eliminates (and recharges) batteries for these radios. <b>4<sup>95</sup></b> Order #12-702
--	--



FREE 1968 RADIO SHACK CATALOG  
Check coupon below.



### ORDER NOW FROM THE RADIO SHACK® STORE NEAREST YOU!

- ARIZONA — Phoenix
- ARKANSAS — Little Rock
- CALIFORNIA — Anaheim, Bakersfield, Covina, Downey, Gardena, Glendale, Inglewood, La Habra, Long Beach, Los Angeles, Mission Hills, Mountain View, Oakland, Pasadena, Pomona, Reseda, Sacramento, San Bruno, San Diego, San Francisco, Santa Ana, Santa Monica, Torrance, West Covina
- COLORADO — Denver
- CONNECTICUT — Hamden, Manchester, New Britain, New Haven, New London, Orange, Stamford, West Hartford
- FLORIDA — Jacksonville, Orlando
- GEORGIA — Atlanta
- ILLINOIS — Belleville, Chicago, Harvey
- KANSAS — Wichita
- LOUISIANA — Gretna, New Orleans
- MAINE — Portland
- MARYLAND — Langley Park
- MASSACHUSETTS — Boston, Braintree, Brockton, Brookline, Cambridge, Dedham, Framingham, Lowell, Medford, Natick, Quincy, Saugus, Springfield, Waltham, West Springfield, Worcester
- MICHIGAN — Detroit
- MINNESOTA — Minneapolis, St. Paul
- MISSOURI — Kansas City, St. Joseph, St. Louis
- NEBRASKA — Omaha
- NEW HAMPSHIRE — Manchester
- NEW JERSEY — Pennsauken
- NEW MEXICO — Albuquerque
- NEW YORK — Albany, Binghamton, Buffalo, New York, Schenectady, Syracuse
- NORTH CAROLINA — Charlotte
- OHIO — Cincinnati, Cleveland, Lima
- OKLAHOMA — Oklahoma City, Tulsa
- OREGON — Portland
- PENNSYLVANIA — Greensburg, Philadelphia, Pittsburgh
- RHODE ISLAND — Providence, East Providence
- TENNESSEE — Memphis, Nashville
- TEXAS — Abilene, Arlington, Austin, Brownsville, Corpus Christi, Dallas, El Paso, Fort Worth, Houston, Lubbock, Midland, San Antonio, Sherman, Waco
- UTAH — Salt Lake City
- VIRGINIA — Arlington, Virginia Beach
- WASHINGTON — Seattle

RADIO SHACK } East : 730 Commonwealth Ave., Boston, Mass. 02215  
West : 1515 So. University Dr., Ft. Worth, Tex. 76107

"Patrolman" High Band/AM Radio .....\$24.95\*

"Patrolman" Low Band/AM Radio .....\$24.95\*

"Jetstream" Air Band/AM Radio .....\$21.95\*

Plug-in AC Adapter for Radios .....\$ 4.95\*

FREE 1968 Radio Shack Catalog. Dept. 5Y

\*Add 50c per item for postage and handling.

NAME \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Circle 8 on reader's service card

← Circle 7 on reader's service card

## FCC, CB and the Public

Recently, the Federal Communications Commission proposed basic changes in the Citizens band. It appears to me that these proposals (which were reported in our News Briefs column in the June and July 1967 issues) make sense. They seem a continuation of the Commission's efforts to clean up the CB mess.

Unfortunately, the FCC apparently doesn't have the resources to police CB effectively. Anyone who listens to the 27-MHz channels for even a short time can hear the attitude of many CB licensees; there is little fear of being caught violating FCC rules, so there are many violations.

Until a few years ago, it was difficult for the Commission to keep broadcast stations within the rules. Why? All the FCC could do to a radio or TV station was revoke its license. It was like having only one penalty for speeding—a life sentence. How often would such a penalty be used?

Congress recently gave the FCC a system of fines which could be levied against broadcasters. For a minor technical violation, the penalty might be \$50. For a prolonged and serious breach, it might be \$5,000. What's important is that the Commission was given the tools with which to work.

Now the time has come for Congress to give

the FCC the money to hire more personnel. If the rules are to be enforced, this can be done only by additional inspectors, monitors, and field engineers. With the present FCC budget, rule enforcement is spotty and CB licensees know it. They know the Commission must police *all* radio services—from broadcasting to taxicab radio, from satellites to ship-to-shore.

Ideally, we are all good citizens who obey the law—and the FCC rules. Realistically, there are always those few inconsiderate individuals who blindly or deliberately violate the law—and FCC rules. The more they are allowed to get away with it, the more tempted we all are to cheat just a little. Eventually the whole thing gets out of hand, and you have a mess—like CB today. Laxity in rule enforcement doesn't do anyone any good.

When Congress enacted the Communications Act and created the FCC, public service was the keynote. To allow the greatest public service on the Citizens band, the FCC must be able to enforce the rules adequately. The FCC needs more people; it needs more money to hire those people. Only Congress can appropriate that money. I think it should.

—Thomas R. Haskett

# Radio-Electronics

August 1967 VOL. XXXVIII No. 8  
Over 55 Years of Electronics Publishing

## EDITORIAL

- 2 FCC, CB and the Public.....Thomas R. Haskett

## CB & COMMUNICATIONS

- 22 In the Shop... With Jack.....Jack Darr  
*Service Clinic*
- 38 Two Interference Nullers.....Jack Althouse and  
*A pair of heterodyne killers for your receiver* Otis Van Houten
- 47 Electronic Antenna Rotation.....Ray D. Thrower  
*The elements stay put—only electrons are moved*
- 50 Check CB Frequencies with BC-221 and a Converter..Ron Gunn  
*Here's an adapter you can make to increase the accuracy of that surplus frequency meter*
- 57 Build Your Own Shortwave Receiver.....I. Queen  
*A fascinating yet low-cost project*
- 60 Remote-Reading Field Meter.....James B. White  
*Useful for monitoring transmitter output on CB, amateur, or commercial two-way*
- 82 More About Hydrionics
- 83 CB Troubleshooter's Casebook.....Andrew J. Mueller  
*New service tips on class-D transceivers*

## AUDIO / HI-FI / STEREO

- 32 A Modern FM Stereo Adapter.....Kenneth F. Buegel  
*Up-to-date components and simple design make magnificent multiplex*
- 34 Stereo FM Stations  
*A new directory*
- 54 Build An All-Transistor Mixer-Amplifier.....Harvey Inman  
*Got two mikes and only one input? Try this portable mixer*
- 71 Equipment Report: Shure V-15 Type II Cartridge

## SERVICING

- 42 In's and Out's of Lead-Ins.....Edward A. Lacy  
*How to route cable and twinlead — all around the house*
- 67 Luck is a Lady.....Frank Salerno  
*Training, experience and equipment aren't everything!*

## GENERAL ELECTRONICS


- 45 Canada's First Satellite Station.....James W. Essex  
*Space communication comes to the north country*
- 89 R-E Puzzler
- 95 R-E Puzzler Answer.....Edmund A. Braun

## THE DEPARTMENTS


- |  |                          |
|--|--------------------------|
| 14 Correspondence                            | 4 News Briefs            |
| 95 New Books                                 | 94 Noteworthy Circuits   |
| 80 New Literature                            | 86 Technotes             |
| 75 New Products                              | 95 Try This One          |
| 90 New Semiconductors, Microcircuits & Tubes | 66 What's Your EQ?       |
|  | 93 50 Years Ago          |
|  | 72 Reader's Service Page |



p 38—SIGNAL SLICER

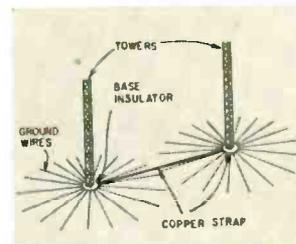


p 47—NO-TURN ANTENNA

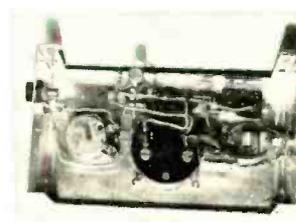

p 60—MEASURE RF



p 54 MIX YOUR MIKES

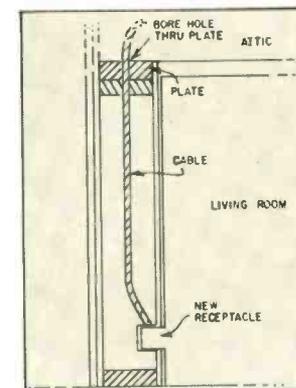

p 42—CABLE THE HOUSE

p 67—TECHNICIAN'S LUCK



RADIO - ELECTRONICS, AUGUST 1967, Volume XXXVIII, No. 8. Published monthly by Gernsback Publications, Inc., at Ferry St., Concord, N. H. 03302. Editorial, Advertising, and Executive offices: 154 West 14th Street, New York 10011. Circulation Office, Boulder, Colo. 80302.


Second-class postage paid at Concord, N. H. Printed in U.S.A. One-year subscription rate: U. S. and possessions, Canada, \$5. Pan-American countries, \$6. Other countries, \$6.50. Single copies: 60c. © 1967, by Gernsback Publications, Inc. All rights reserved. POSTMASTERS: Notices of undelivered copies (Form 3579) to Boulder, Colo. 80302.

## COVER FEATURE



p 50—CB transmitters must be frequency-checked from time to time. This construction project lets you use a surplus BC-221 with increased accuracy for 27-MHz transmitter testing.

## ADD STEREO

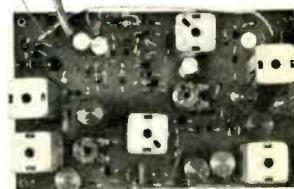

p 32—Got a mono FM tuner? Want wall-to-wall sound? Make this adapter and relax in two-channel bliss.



Member,  
Institute of High Fidelity.  
Radio-Electronics is Indexed in  
*Applied Science & Technology Index* (formerly *Industrial Arts Index*)

# NEWS BRIEFS

## MONO DISC TO FADE

For several years—since the introduction of the stereo LP—most music has been available in both mono and stereo recordings. A nuisance to manufacturers, the dual-release practice may be on the verge of extinction.

EMI, the giant British-based producer of electronics and records, announced this summer that they were discontinuing the production of mono classical LP's (in favor of stereo only). Three American firms—Columbia, Mercury and RCA—are in the process of eliminating the price differential between stereo and mono versions of their recordings.

If and when mono records are eliminated, it would seem wise to produce all phonographs with stereo cartridges. Thus stereo discs could be played by everyone, even though in some cases both channels might be paralleled through a single amplifier.

## NONINDUCTIVE TUNING

Integrated circuits have made possible microminiaturization of electronics circuits. But LC tuning networks are still physically bulky. One new method of achieving resonance was discovered recently by Westinghouse Molecular Electronics Div. It's a tiny transistor that can be voltage-tuned to resonance.

The solid-state device is made with a cantilever gate electrode over an MOS transistor. The lever is fine-tuned by a polarizing voltage. Input signals must be of the proper frequency to get through the device, which is essentially a tiny bandpass filter. It is currently being made in the 3- to 100-kHz range.

## LASERS AND MEDICINE

A blind person may soon be able to use the purest kind of light to help him find his way. Scientists at RCA Laboratories in Princeton, N.J., have constructed a cane with two semiconductor lasers which locate obstacles in the user's path. The laser beams are reflected from points ahead of the sightless person, as shown in the photo. Upon bounceback, the beams activate photoelectric cells which trigger into vibration two pins in the cane handle.



An intervening object interrupts the laser beams, stopping the vibrations. The blind person can literally "feel" his way.

Cane developer William J. Hannan says that the infrared injection laser beams are produced by gallium arsenide diodes. Each diode is pulsed 20 times a second, 80 nsec at a time. The cane is still developmental and has limited usefulness at present.

Meanwhile, a number of authorities are calling for stricter safety around lasers. It has been known for some time that even split-second exposure to a laser beam can cause blinding and permanent burns of the retina. Recent laboratory experiments have proved that lasers can produce fatal


hemorrhages in the brains of mice. Currently several states, the Defense Department and the US Public Health Service are investigating hazards that may threaten workers using lasers.

## TV DEVELOPMENTS

During May and June new developments in TV popped up all over the place.

**Solid-state color:** Modular semiconductor color receiver is now on the market. The set—produced by Motorola—has a 23-inch (viewable diagonal) CRT, IC's, and only two vacuum tubes—the kinescope and the HV rectifier. Circuit consists of 10 plug-in modules, each carrying one-year warranty. Out of warranty, modules will be replaceable for \$15 each. Meanwhile Sony Corp. has demonstrated a prototype model of a personal color receiver with a 7-inch (viewable diagonal) screen. CRT is a three-gun Chromatron and is the only vacuum tube in the chassis. The 18-lb set is expected on the market in 1968. (Speaking of the Chromatron, a single-gun version has been successfully adapted by engineers in France for use with that country's SECAM color-TV system.)

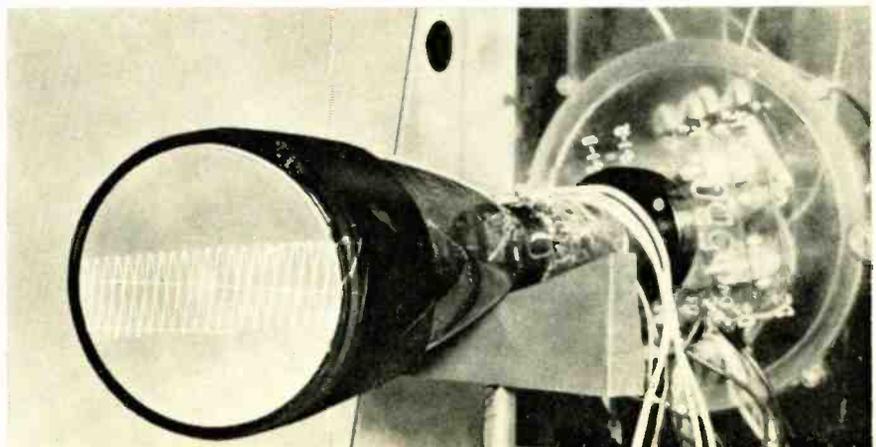**The \$50 TV:** Will we have a video version of the standard ac-dc table radio? Maybe—now that General Electric has developed a receiving tube kit and basic circuit for a 12-inch (viewable diagonal) receiver. Kit consists of 4 Compactrons and 1 miniature tube which perform all functions except





A SUBSIDIARY OF  **BELL-HOWELL**

# SEE WHY so many DeVry-trained Men Step Into Electronics Jobs the Day after Graduation!

## **EVERY GRADUATE CAN ALSO RECEIVE EMPLOYMENT HELP THROUGH HIS ENTIRE CAREER, AT NO ADDED COST**

DeVry's greatest claim to fame is the progress of its graduates. Our aim is to prepare a man so thoroughly that we can recommend him to employers . . . ready to step into a job the day after graduation. If we expect to continue to help employers, our graduates have to be good! That is why we provide top quality instruction—followed by career-long employment service at no added cost.

DeVry's educational programs are designed to prepare men 17-45 in their spare time at home or in any of our three well-equipped, modern resident schools in Chicago, Phoenix or Canada. Why not fill in and mail coupon for free facts today?

**Approved for Veterans.**

### **For FREE Information**

Lack of technical experience is no barrier to the man who wants to prepare for a career in ELECTRONICS. Send coupon for two FREE booklets and find out why.



Accredited Member of National Home Study Council

**DEVRY INSTITUTE OF TECHNOLOGY**

4141 BELMONT AVENUE, CHICAGO, ILLINOIS 60641

### **DeVRY INSTITUTE of TECHNOLOGY**

**4141 Belmont Avenue, Chicago, Ill. 60641, Dept. RE-8-X**

Please give me your two free booklets, "Pockets Guide to Real Earnings," and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- |  |   |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications         |
| <input type="checkbox"/> Television and Radio        | <input type="checkbox"/> Computers              |
| <input type="checkbox"/> Microwaves                  | <input type="checkbox"/> Broadcasting           |
| <input type="checkbox"/> Radar                       | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics      | <input type="checkbox"/> Electronic Control     |

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ State or Province \_\_\_\_\_ Zone or Zip Code \_\_\_\_\_

Check here if you are under 16 years of age.

2106 **HOME STUDY AND RESIDENT SCHOOL PROGRAMS  
AVAILABLE IN CANADA. SEND FOR DETAILS.**

Circle 9 on reader's service card

**NEWS BRIEFS continued**

those of the tuner. Circuitry has been reduced to the bare minimum, using single-tube oscillators and a high-gain, single video i.f. amplifier.

**One gun, two colors:** A new CRT is made with two phosphor layers on the screen, separated by a barrier layer. By switching the final anode voltage, the beam can excite either phosphor, displaying either or both of two colors. Sylvania engineers devised the new tube for commercial, industrial and military applications—anywhere simultaneous display of two different data is desired.

**Small-screen US color:** It's not in receivers yet, but RCA has begun production of a new rectangular, rare-earth phosphor picture tube measuring 14 inches (viewable diagonal). Such a medium-sized CRT makes possible easily portable color receivers.

**Tiny black-and-white:** By using a 1-inch CRT and an integrated circuit, Sony has developed a prototype 2-lb personal TV. Set is not yet available.

**One-man TV station:** The man in the photo is taking a video picture, transmitting it to a nearby mobile truck via the transmitter on his back, and receiving instructions through another rf



channel. He can leave the camera and it may be operated by rf remote control from the truck. Portable camera/transmitter (which weighs 54 lbs) was produced by CBS Laboratories.

**X-ray TV callbacks:** The high-voltage supply in a television receiver can produce X-rays; unless certain precautions are taken by the manufacturer, such X-rays may cause harm to viewers. These precautions are designed into the chassis in almost every case. In May, however, G-E's quality control section found that some of their large-screen receivers were emitting soft X-rays slightly above the acceptable limit. The company then began a callback program (at their expense) to re-

place the HV regulator and readjust the power supply. G-E emphasized that radiation level, while above the acceptable limit, was *not* high enough to harm viewers. Furthermore, the rays were emitted towards the floor, not towards the viewers. Receivers were also checked by Consumers Union (the independent research and testing organization which publishes *Consumer Reports*). Their findings confirmed G-E's, that radiation was not at a harmful level.

**\$500 home color recorder:** It may be feasible within a couple of years, and is made possible by the development of a different type of tape transport. Newell Associates has worked out a different system of tape handling which removes tension and makes high speed possible without danger of breakage. This means fixed heads, high tape speeds, video bandwidth, and ultimately a less complicated machine.

**Microwave/video pictures for pilots:** No, they don't watch old movies while flying the airliner. System—called Microvision—uses microwaves to scan a runway and deliver a picture to a TV screen in the cockpit. Thus pilots can land even in thick fogs. New all-weather landing system was developed by Bendix and is now undergoing flight tests.

**Image enhancer:** Space-relayed TV pictures are often fuzzy, so CBS Laboratories devised a way to sharpen images. Ultrasonic delay lines in the equipment retain video information long enough for each point to be compared with surrounding points. Contrast is then emphasized and noise information eliminated. Using this technique, networks and stations can now clean up noisy pictures.

**Multiplex TV with printed copy:** An experimental system is currently under test by RCA which would transmit fixed-image information during the vertical blanking period. As in the facsimile method, RCA's system would scan print or pictorial matter at the transmitting station. At the home re-



# Radio-Electronics

154 WEST 14TH STREET  
NEW YORK 10011

HUGO GERNSBACK, *editor-in-chief*  
M. HARVEY GERNSBACK, *publisher*  
FOREST H. BELT, *editor*  
Bruce Ward, *production manager*  
Robert F. Scott, *W2PWG, senior editor*  
Thomas R. Haskett, *managing editor*  
Jack Darr, *service editor*  
I. Queen, *editorial associate*  
Allen B. Smith, *science editor*  
Peter E. Sulheim, *audio editor*  
Wm. Lyon McLaughlin,  
*technical illustration director*  
Maxine Schware, *assistant to editor*  
Adelaide Cassity, *production assistant*  
G. Aliquo, *circulation manager*

Cover by Harry Schlack

RADIO-ELECTRONICS is published by Gernsback Publications, Inc.

Chairman of the Board: Hugo Gernsback  
President: M. Harvey Gernsback  
Vice President-Secretary: G. Aliquo

## ADVERTISING REPRESENTATIVES

### EAST

John J. Lamson,  
RADIO-ELECTRONICS, 154 West 14th Street,  
New York 10011, 212-255-7755

MIDWEST/N.&S. Car., Ga., Tenn.  
Robert Pattis, the Bill Pattis Co., 4761 West  
Touhy Ave., Lincolnwood, Ill. 60646,  
312-679-1100

W. COAST/Texas/Arkansas/Oklahoma  
J. E. Publishers Representative Co., 8380  
Melrose Ave., Los Angeles, Calif. 90069,  
213-653 5841; 420 Market St., San Francisco,  
Calif. 94111, 415-981-4527

### UNITED KINGDOM

Publishing & Distributing Co., Ltd., Mitre  
House, 177 Regent St., London W.1, England

**SUBSCRIPTION SERVICE:** Send all subscription correspondence and orders to RADIO-ELECTRONICS, Subscription Department, Boulder, Colo. 80302. For change of address, allow six weeks, furnishing both the old and new addresses and if possible enclosing label from a recent issue.

**MOVING?** Or writing about subscription? Be sure to fill out form below.

For FASTEST service on address change, missing copies, etc., attach old mailing label in first space below. Otherwise please print clearly your address as we now have it.

OLD ADDRESS (Attach old label if available)

Name .....  
Address .....  
City ..... State .....  
Zip Code .....

### NEW ADDRESS

Name .....  
Address .....  
City ..... State .....  
Zip Code .....

Mail to: RADIO-ELECTRONICS  
Subscription Dept. Boulder, Colo. 80302

RADIO-ELECTRONICS

# This Revolving Tool Caddy

## FREE

When you buy  
RCA SK-Series  
Transistors and Rectifiers—  
The Industry's Leading  
Replacement Line



Tools and Parts not included with caddy

Here's just the tool caddy you've always needed to keep handy around the shop or home work benches. It's Rubbermaid's portable caddy that keeps tools and small parts organized and always at hand. Made of high-impact styrene and designed to revolve on eight ball bearings as a "lazy susan," the caddy is yours free—with the purchase of RCA SK-Series replacement devices from your participating RCA Distributor.

Drop by your RCA Distributor today. He has all details. Act now. Pick up your supply of the RCA SK-Series replacements and take home this brand new tool caddy as well—free—from your participating RCA Distributor.

AVAILABLE THROUGH YOUR PARTICIPATING RCA DISTRIBUTOR

RCA Electronic Components and Devices, Harrison, N. J. 07029




The Most Trusted Name in Electronics

A photograph showing three boxes of RCA SK-Series replacement components. The boxes are black with red and white text. One box is labeled "SK-3012" and "TOP-OF-THE-LINE REPLACEMENT TRANSISTOR". Another box is labeled "SK-3010" and "TOP-OF-THE-LINE REPLACEMENT TRANSISTOR". A third box is labeled "SK-3011" and "TOP-OF-THE-LINE REPLACEMENT TRANSISTOR". The boxes are arranged in a cluster, with one in the foreground and two behind it.

**RCA's carton-packed  
SK-Series "Top-of-the-Line" replacements**

include 19 transistors, 2 rectifiers and 2 integrated circuits that can replace more than 9,000 solid-state devices. Cross-referenced in the RCA Solid-State Replacement Guide against both domestic and foreign types, these 23 top performing RCA types can help solve most solid-state replacement problems for experimenters, hobbyists, hams and technicians. Check your RCA Distributor for the SK-Series Replacement line and the replacement guide.

# NRI GIVES YOU THE RIGHT BALANCE...

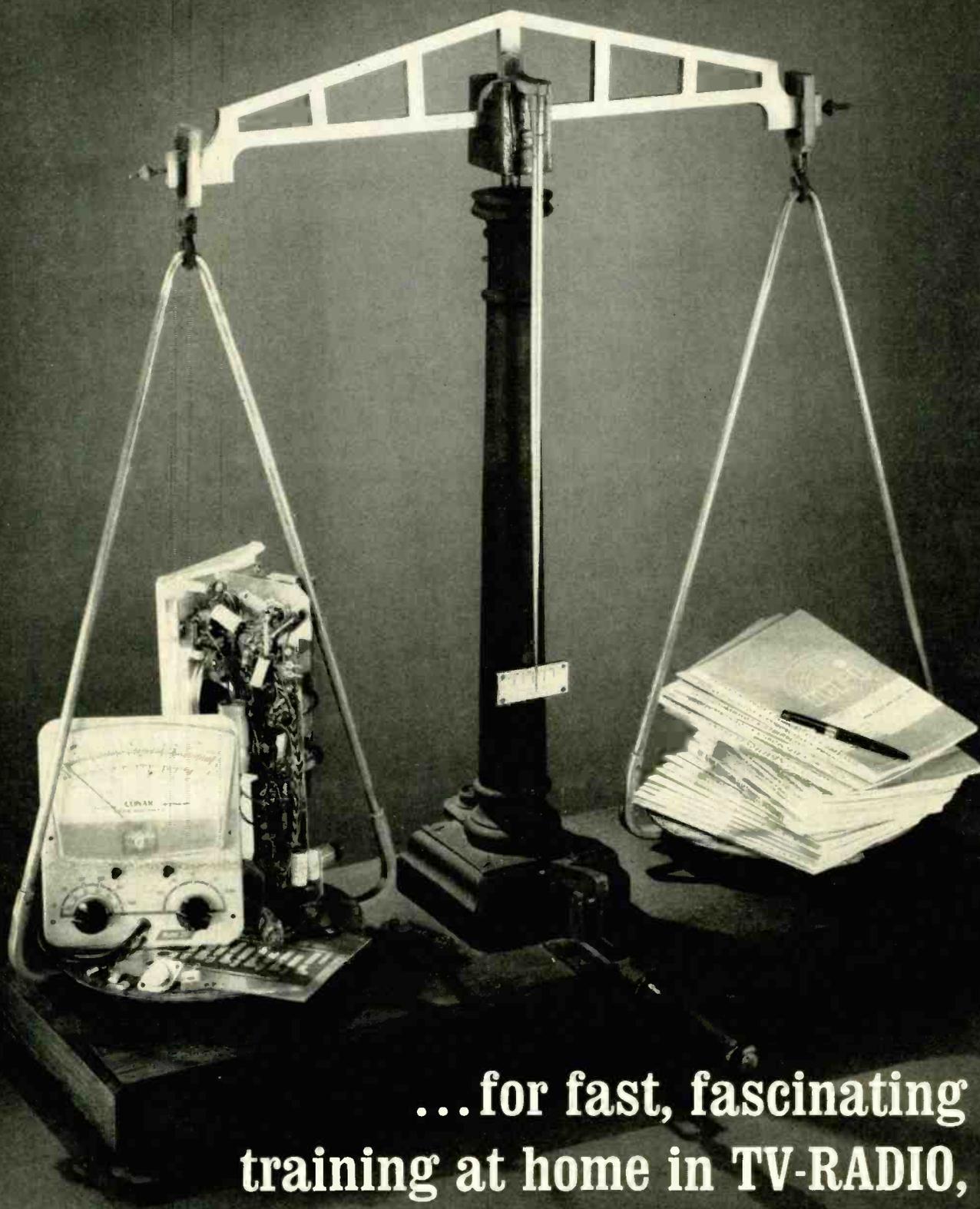

...for fast, fascinating  
training at home in TV-RADIO,  
COMMUNICATIONS, ELECTRONICS

# Experience is still your best teacher

## Here's how you get it with NRI job-simulated training

Ask any teacher, job counselor, engineer, technician or prospective employer about the need for practical application of theory in Electronics. He'll tell you Electronics is as much a "hands on" profession as dentistry or chemistry. That's the way you learn at home with NRI. You put to work the theory you read in "bite-size" texts, using designed-for-learning lab equipment you build with professional components. You introduce defects into circuits, do experiments, until the "why" of circuitry and equipment operation comes clear through demonstration. You gain experience with transistors and solid-state designs as well as conventional tube circuits.

NRI lab equipment is designed and engineered from chassis up for education through practical experience — not for entertainment. The fact that the end results of your projects are usable, quality products is a personal bonus for you. Everything about NRI training has but one ultimate goal — to make you **employable** in your chosen field of Electronics by preparing you to prove your practical understanding of actual equipment; by giving you the equivalent of months, even years, of on-the-job training. There is no end of oppor-

tunity for the trained man in Electronics. You can earn extra money in your spare time, have your own full-time business, or qualify quickly for career positions in business, industry, government. Discover for yourself the ease and excitement of NRI training. Mail the postage-free card today for the new NRI Color Catalog. No obligation. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Div., Washington, D. C. 20016.

## NRI has trained thousands



L. V. Lynch, Louisville, Ky., was a factory worker with American Tobacco Co., now he's an Electronics Technician with the same firm.

He says, "I don't see how the NRI way of teaching could be improved."



G. L. Roberts, Champaign, Ill., is Senior Technician at the U. of Illinois Coordinated Science Laboratory. In two years he received five pay raises. Says Roberts, "I attribute my present position to NRI training."

raises. Says Roberts, "I attribute my present position to NRI training."



Ronald L. Ritter of Eatontown, N.J., received a promotion before even finishing the NRI Communications course, after scoring one of the highest grades in Army proficiency tests. He works with the U. S. Army Electronics Lab, Ft. Monmouth, N.J. "Through NRI, I know I can handle a job of responsibility."

highest grades in Army proficiency tests. He works with the U. S. Army Electronics Lab, Ft. Monmouth, N.J. "Through NRI, I know I can handle a job of responsibility."



Don House, Lubbock, Tex., went into his own Servicing business six months after completing NRI training. This former clothes salesman just bought a new house and reports, "I look forward to making twice as much money as I would have in my former work."

bought a new house and reports, "I look forward to making twice as much money as I would have in my former work."

**APPROVED UNDER NEW GI BILL. If you served since January 31, 1955, or are in service, check GI line on postage-free card.**


Accredited by the Accrediting Commission of the National Home Study Council

Over 50 Years of Leadership



in Electronics Training

## YOU GET MORE FOR YOUR MONEY FROM NRI

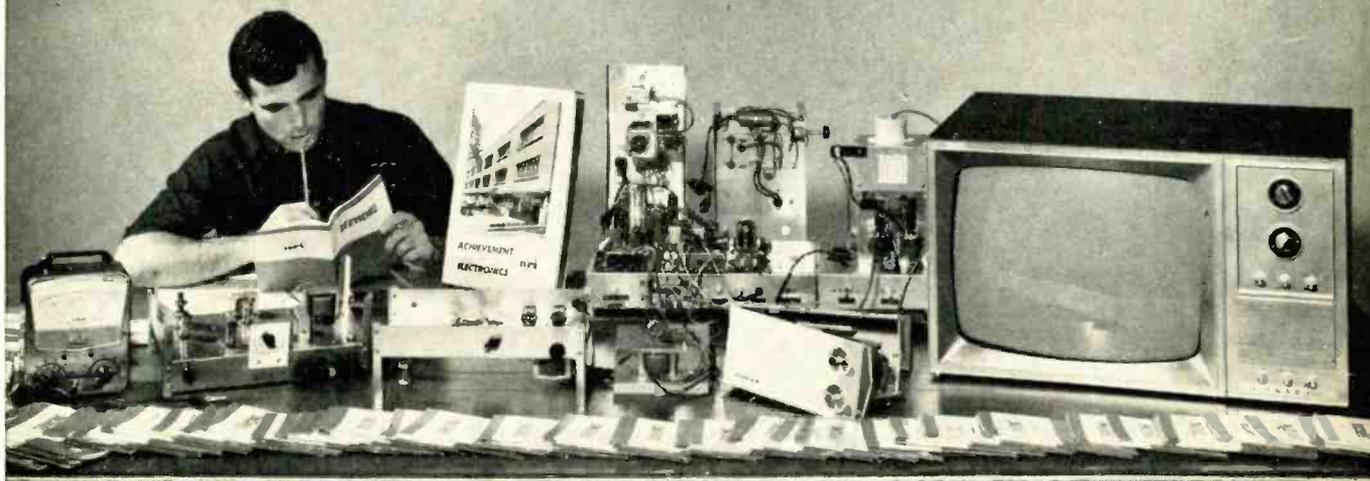

Everything you see here is included in one typical NRI home study course. Other courses are equally complete. Your training starts with the NRI Achievement Kit, sent the day you enroll. It contains the first of your "bite-size" texts which are programmed with

designed-for-learning professional lab equipment. Step-by-step, you learn with your hands as well as your head. You discover the "why" of circuitry as you acquire the professional's most valuable tool — practical experience in Electronics.

**NEWS BRIEFS continued**


ceiver, an adapter would produce a printed copy (see photo) utilizing an electrostatic printing process currently used by office copying machines. RCA has applied to the FCC for permission to conduct an on-the-air test in New York City.

**GERNSBACK SCHOLARSHIP AWARDED**

The 1967-68 Hugo Gernsback Scholarship awarded annually to a New York University student was won

this year by William Conis. The \$1,000 grant is presented to a student chosen by NYU's College of Engineering faculty.

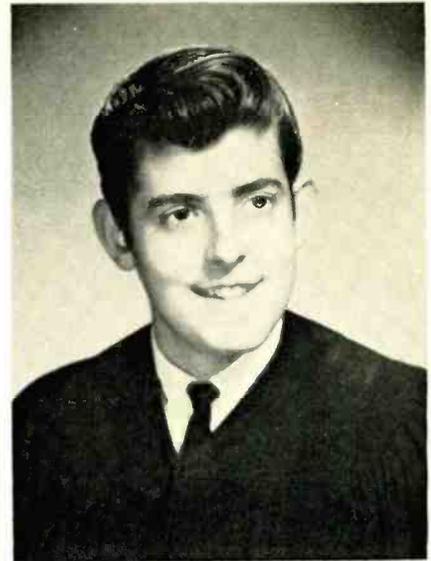Conis is a Manhattan native who says he "... spoke only Greek till the age of six since no one at home could speak English." He completed high school in three years and was named valedictorian of his senior class. At NYU he chose to major in electrical engineering and was tapped for Eta Kappa Nu (the electrical engineering honor society). Currently vice president



of the campus chapter of IEEE, Conis has been on the Dean's Honor List since he enrolled at NYU. Upon graduation in 1968, he hopes to specialize in solid-state or communications work.



Powerful, rugged, sleek Northrop F5-A "Freedom Fighter" is helping to keep the peace for the U. S. and 14 allied nations.

**Powerful.  
Rugged.  
Sleek.  
Lightweight.  
Goes anywhere.**

**New CB-21 "REACTOR II"  
eight-channel solid state CB transceiver**



**only \$139<sup>95</sup>**

Tallyho! Here's the hot new CB-21, the one that packs more punch into less space than any rig airborne! Using advanced techniques of space-age electronics, Hallicrafters has built in more talk power than ever before—cleaner, more readable signal with far less extraneous noise and a **minimum of 3.5 watts output**. Compare the features—then take off for your Hallicrafters dealer!

- Eight channel convenience • 17 transistors, six diodes • Built-in noise limiting circuits • Dual conversion receiver with ceramic filters for superb rejection and selectivity • Illuminated channel selector • PA-hailer circuitry built in



the new ideas in communications  
are born at ... **hallicrafters**

A Subsidiary of Northrop Corporation  
5th & Kostner Aves., Chicago, Ill. 60624

Export: International Div., Canada, Gould Sales Co.


Circle 12 on reader's service card

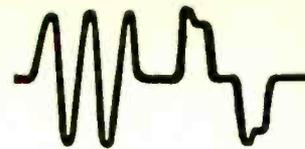**20-YEAR BATTERY**

The massive power blackout of November 1965, which paralyzed New York City and many nearby areas, taught one lesson: Everyone should keep flashlights and battery-operated radios on hand for such emergencies. Because batteries eventually deteriorate—even when unused, you may not be quite sure those standby cells have any life left in them.




The 1.5-volt alkaline cell shown in the photo has been designed to last 20 years if not used. Developed by Mallory and designated a "reserve" battery, the cell will be furnished to the user in a standby condition. When you need to use it, you turn the top cap, releasing liquid electrolyte and activating the cell. Not yet on the market, the battery will initially be made in D-size, and will be priced slightly higher than regular alkaline cells. **END**



## Using silicon rectifiers in horizontal AFC circuits

FIG. 1. 6AL5 AFC CIRCUITS

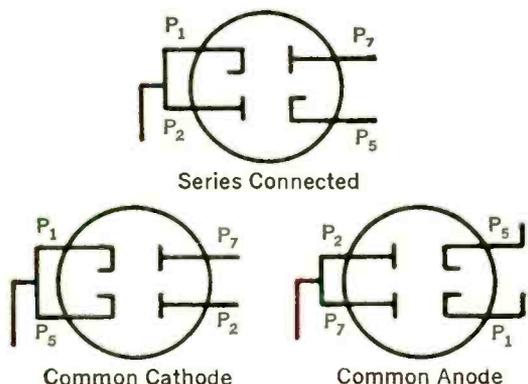


Many of the older TV sets you'll run into have a 6AL5 dual rectifier tube in the horizontal automatic frequency control circuit. Its function is to insure a stable horizontal frequency, by comparing the input signal from the sync separator with a feedback signal from the horizontal output. Three different circuits were used for this job, as shown in Figure 1.

In some later sets, selenium rectifiers took over the 6AL5 job for AFC. These were connected as shown in Figure 2.

When you run into one of these AFC circuits that needs fixing, you can do your customer a favor by switching to Mallory silicon rectifiers. You'll give him a repair job that will shape up this part of the set for all time, at no extra cost. You won't have to chase around finding a selenium stack with exactly the rating you need. And you're sure you won't ever have a call-back on the job.

FIG. 2. SELENIUM RECTIFIER AFC CIRCUITS

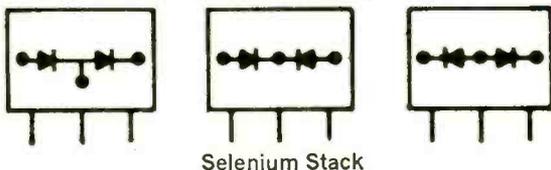


Selenium Stack

You can go either of two ways with Mallory silicon replacements. Simplest is to use a Mallory packaged rectifier circuit—a pair of factory-connected rectifiers in a single compact plastic case. Cost is slightly less than two separate rectifiers, and installed reliability is better because you have fewer solder connections to make. The VB doubler is ideal for the series-connected AFC circuit; just get a Mallory VB100 and hook it to the tube socket. For the common cathode AFC circuit, use a Mallory CTP100 (full wave, center tap positive). And for the common anode circuit, use a Mallory CTN100 (full wave center tap negative).


Or if you prefer to work with separate rectifiers, get yourself a pair of Mallory Type A's. The A100 will work fine. Either way, just make your connections as shown in Figure 3.

For this service, 100 volt ratings are ample to give you full protection against transient "spikes" and assure long life. For other applications in TV sets, stereo, radios and industrial equipment, take a look at the complete line of Mallory power rectifiers, zener diodes and other semiconductors stocked by your Mallory Distributor. He's a good guy to know for everything you need for service, prototype building or experimental work. Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Indiana 46206.

FIG. 3. MALLORY SILICON RECTIFIER REPLACEMENTS

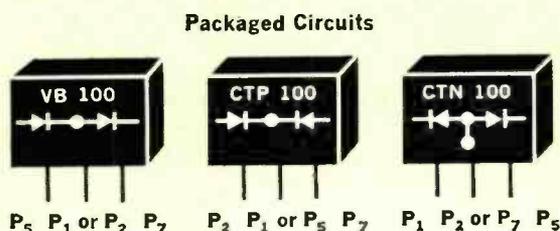

Type A Rectifiers

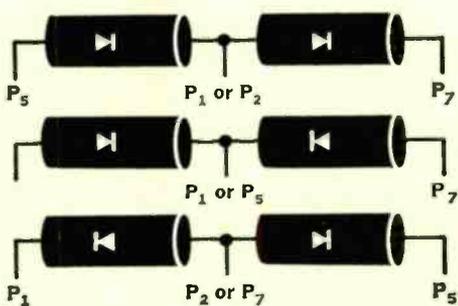

DON'T FORGET TO ASK 'EM—*What else needs fixing?*

Circle 13 on reader's service card



has  
everything  
in

# chemicals

From service cements to aerosol cleaners, from solvents to lubricants, only GC satisfies the critical chemical needs of the electronics field.

All GC chemicals are formulated to meet rigid requirements; packaged for convenience; and "proven in use" to make electronic jobs easier, faster, more profitable.

Remember too, with GC aerosols you get double value . . . highest product quality plus valuable GC "BONUS COUPONS".

Get more for your money . . . always insist on GC!

Write for your Giant **FREE GC Catalog** today . . . over 12,000 items including TV Hardware, Phono Drives, Chemicals, Alignment Tools, Audio, Hi-Fi, Stereo & Tape Recorder Accessories, Nuts & Bolts, Plugs & Jacks, Service Aids, and Resistive Devices.

*only GC gives you  
everything in electronics.  
..... for almost 40 years!*



## GC ELECTRONICS COMPANY

400 South Wyman Street  
Rockford, Illinois 61101  
A DIVISION OF HYDROMETALS, INC.

Circle 14 on reader's service card



Radio-Television  
Service Cement  
Cat. No. 30-2



SPRA-KLEEN  
Contact-Control Cleaner  
Cat. No. 8666



SPRA-LUBE  
Cleaner-Lubricant  
Cat. No. 8888




Jif  
CLEANS  
CONTACTS  
GC "JIF"  
Contact and Control  
Cleaner  
Cat. No. 8670



"Super Grip"  
Epoxy Glue  
Cat. No. 347



Super Freeze Mist  
Cat. No. 8668

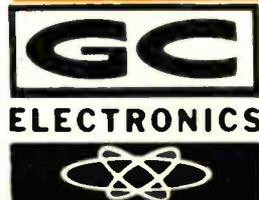

## EDITORIALS DRAW COMMENTS

Dear Editor:

Your April editorial "The Hands That Feed ETV" deserves complimentary comment.

Two points especially: Concerning sets which do not function without the skilled hands and knowledge of the electronic technician, dead electronic equipment can be embalmed for all time.

The second concerns the so-called "exposes." If those who guide the programs of ETV would look into other fields of business—not overlooking the professions—they could find dishonesty that would make the TV man a pygmy by comparison.

Your closing thought about the "bitten hand" is apt; what is more to the point, yet, is the mutilated spirit and morale of those dedicated men whose characters are blackened, and which requires a long time to heal. I have winced more than once when a customer makes a crack about the repairman, and I wonder how bright his own halo might be.

HOWARD WOLFSON  
*Secretary, ARTS, Illinois, Inc.*

Dear Editor:

I read your editorial in the April 1967 issue, where you mentioned a shortage of TV technicians. I would like to know where you and a few others get your information.

I am a journeyman TV technician. I have asthma and decided in January to find something where the climate was more agreeable. I was in five western states and found the same conditions in all. Right now I am thinking strongly of leaving the TV service field after 10 years experience because of what I have found every place I looked.

My first stop was in the San Francisco area. Union scale was \$4.25 an hour but all I could find was outside service openings—not a single bench job in the area.

I found openings in almost every smaller town, but each required a 6-day week with wages ranging from \$85 to \$125. How can a man raise his family decently on that? Only a few places

The microphone  
with backbone...

MODEL 674

now has a  
staunch new  
companion!

MODEL 676

**E-V** In just a few short months the Electro-Voice Model 676 has gained quite a reputation as a problem solver—no matter what the odds. Now the 676 has a teammate. The Model 674 has the same unique backbone that rejects unwanted sound...an exclusive with Continuously Variable-D (CV-D)<sup>TM</sup> microphones from Electro-Voice. And the improvement in performance is dramatic.

Troubled with feedback or interfering noise pickup? Most cardioid microphones cancel best at only one frequency—but CV-D\* insures a useful cardioid pattern over the entire response range. And its small size means the pickup is symmetrical on any axis.

Bothered by rumble, reverberation, or loss of presence? A recessed switch lets you attenuate bass (by 5 or 10 db at 100 Hz) to stop problems at their source. And there's no unwanted bass

boost when performers work ultra-close. CV-D eliminates this "proximity effect" so common to other cardioids.

Wind and shock noise are almost completely shut out by the CV-D design. Efficient screening protects against damaging dust and magnetic particles, and guards against annoying "pops".

As for overall sound quality, only expensive professional models compare with the 676 and 674. The exclusive Acoustalloy<sup>®</sup> diaphragm gets the credit. It's indestructible—yet low in mass to give you smooth, peak-free, wide-range response with high output.

The Model 676 slips easily into its 1" stand clamp for quick, positive mounting. The fine balance and shorter length of the 676, and absence of an on-off switch makes it ideal for hand-held or suspended applications.

The Model 674 offers identical performance but is provided with a stand-

ard mounting stud and on-off switch. Either high- or balanced low-impedance output can be selected at the cable of both microphones.

Choose the 676 or 674 in satin chrome or non-reflecting gray finish for just \$100.00. Gold finish can be ordered for \$10.00 more (list prices less normal trade discounts). There is no better way to stand up to your toughest sound pickup problems. Proof is waiting at your nearby E-V sound specialist's. Or write for free catalog of Electro-Voice microphones today.

An important footnote: There is no time limit to our warranty! If an E-V microphone should fail, just send it to us. If there's even a hint that our workmanship or materials weren't up to par, the repair is no charge—even decades from now! Fair enough?

\*Patent No. 3,115,207

ELECTRO-VOICE, INC., Dept. 872E; 613 Cecil Street, Buchanan, Michigan 49107

Circle 15 on reader's service card

www.americanradiohistory.com

**Electro-Voice**<sup>®</sup>  
SETTING NEW STANDARDS IN SOUND

Why settle for less? Buy the Best!  
THE FABULOUS

# MARK TEN CAPACITIVE DISCHARGE IGNITION SYSTEM



Available in easy-to-build kit form at only

**\$29.95** ppd.!

Only **\$44.95** ppd.!

Dramatically improve the performance of your car—or any vehicle. Racers and Pacers from Sebring to Suburbia by the thousands attest to the peerless performance of the Mark Ten. Delta's remarkable electronic achievement, proven for four years, is often copied, never excelled.

**Ready for these?**

- ▲ Dramatic increase in acceleration
- ▲ Longer point and plug life
- ▲ Improved gasoline mileage
- ▲ Complete combustion
- ▲ Smoother performance

Ready? Order today!

## BE YOUR OWN MECHANIC



Tune-up

**DWELL METER \$12.95** ppd.

A universal precision instrument for use in tuning all vehicles, regardless of the number of cylinders or battery polarity. Gives correct point dwell readings on vehicles equipped with capacitive discharge, transistor or conventional ignition. Precision accuracy at low cost.

- ▲ Portable, high-impact case for rugged work
- ▲ Large, easy-to-read 3½ inch precision jeweled meter
- ▲ Wide scale — reads dwell angles in degrees
- ▲ All solid state



Tune-up

**TACHOMETER \$14.95** ppd.

A universal precision instrument for making carburetor adjustments on all vehicles, regardless of the number of cylinders or battery polarity. Gives precise RPM readings on vehicles equipped with capacitive discharge, transistor or conventional ignition. Gives you better gas mileage, fuel savings and peak engine operation.

- ▲ Large, easy-to-read 3½ inch precision jeweled meter
- ▲ Portable, high-impact case for rugged work
- ▲ Range: 0 to 1200 RPM
- ▲ All solid state

## DELTA PRODUCTS, INC.

P.O. BOX 1147 RE • GRAND JUNCTION, COLORADO 81501

Enclosed is \$\_\_\_\_\_ Ship prepaid.  Ship C.O.D.

Please send:  Dwell Meters @ \$12.95  Mark Tens (Assembled) @ \$44.95  
 Tach Meters @ \$14.95  Mark Tens (Delta Kit) @ \$29.95

(12 volt positive or negative ground only)  
 Specify —  Positive Ground  Negative Ground  6 or  12 volt

Car Year \_\_\_\_\_ Make \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

City/State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 16 on reader's service card

www.americanradiohistory.com

**CORRESPONDENCE continued**

did I find a union and then with few members.

If there was a real shortage of technicians, conditions would be a lot better. As things stand now, I may let my First-Class Phone License expire and go into construction work.


S. GENE BENEFIELD

Tacoma, Wash.

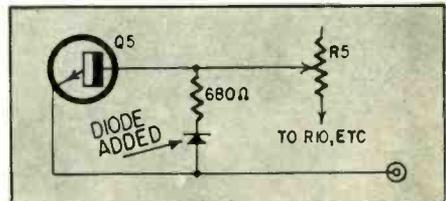**REGULATED SUPPLY**

Dear Editor:

I recently constructed the "All-Silicon Regulated Power Supply" from the June 1966 issue. To my chagrin, the initial "smoke test" ended with a burned-out 2N3053 (Q5). Careful checking of the wiring disclosed no error so I inserted another 2N3053. This time the supply performed well on "hi" range, but after a few minutes on "lo," Zap! went the 2N3053 again.



Some measurements and cerebral exercise showed that when the output control (R5) is adjusted for full output, the base-emitter of Q5 is reverse biased by an amount equal to the Zener voltage (D7) minus the IR drop across resistor R10. In the "lo" range position (with full output setting of R5), the drop across R10 is approximately 5 volts which places the base-emitter junction at 7 volts (reverse bias). The RCA data for the 2N3053 gives a maximum rating of 5 volts for reverse bias.

A simple remedy is to connect a silicon diode (similar to D6) and a 680 ohm, ½ watt resistor to the base-emitter of Q5 as shown.

ARTHUR G. BURNS

Tarrytown, N. Y.

**SIMPLE SHUTTLE**

Dear Editor:


I'm writing in regard to the article "Simple Winding Aid for Toroids" (March 1967, page 81). Rather than go to all the trouble of making one, it is much easier to use a double-end open-end wrench. They come in all sizes and most hobbyists and professionals have them in their tool kits.

H. MORRILL



Phoenix, Ariz.

END

#129 (retail price \$4.95)

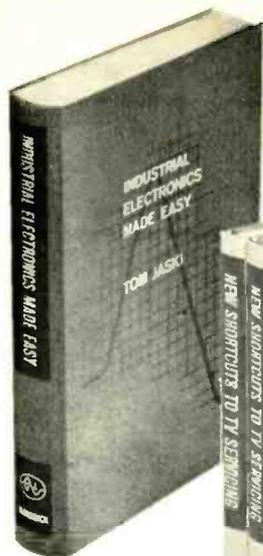


#54 (retail price \$4.60)

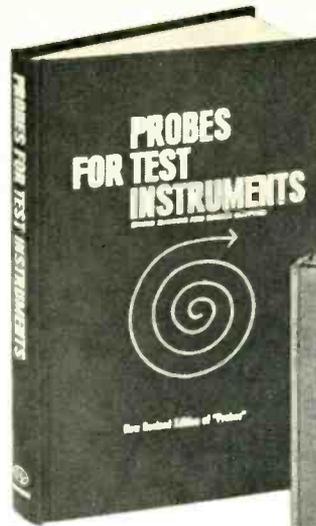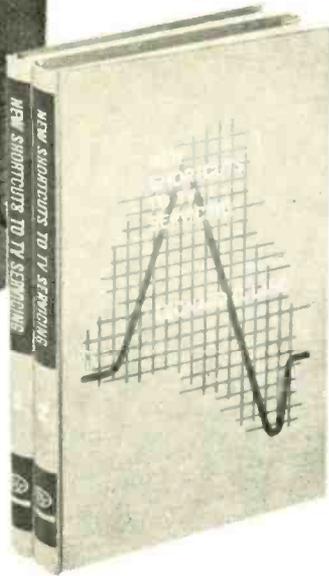

#99 (retail price \$5.95)
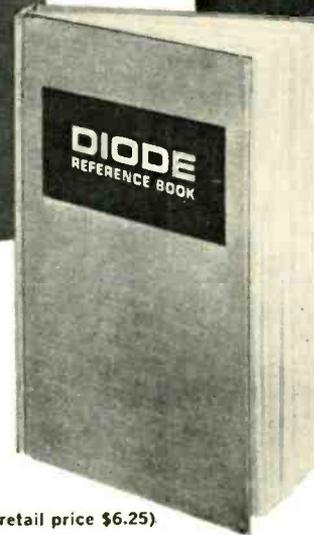
#95 (retail price \$9.90 counts as 1 volume)



#127 (retail price \$6.25)

# Start your electronics library with any 3 for only \$2.00!

## Retail value up to \$22.10 . . . yours with trial membership in the famous Gernsback Electronics Book Club.

An extraordinary offer to introduce you to Gernsback Library's famous Electronics Book Club, especially designed to help you increase your know-how, earning power and enjoyment of electronics.

Whatever your interest in electronics—radio and TV servicing, audio and hi-fi, industrial electronics, communications, electronics as a hobby—you will find that the Electronics Book Club will help you get the job you want, keep it, improve it or make your leisure hours more enjoyable. With the club providing you with top quality books, you may broaden your knowledge and skills to build your income and increase enjoyment of electronics, too

**What books are offered?** From Gernsback Library and other leading technical publishers come the country's most respected books in the field of electronics. Each one is written by a professional, acknowledged expert in his field and designed with you in mind. All are deluxe, hardbound books to be used as a basic tool and offered at considerable cash savings to members—up to 50% off list price—regardless of higher retail prices.

**How the club works.** The Electronics Book Club will send you every other month the news bulletin describing a new book in a vital area of electronics. As a member, you alone decide whether you want a particular book or not. You get 3 books worth up to \$22.10 now for \$2.00 and need take only 4 more within the year, from a wide selection to be offered. Every year the club offers about 25 high quality, hardbound books on electronics. The club saves you money on the books you take, regardless of higher retail prices.

**How to join.** Mail the coupon below today. You will be sent your 3 books immediately. We will bill you \$2.00 (plus a few cents postage). If you are not pleased, send the books back within 10 days and membership will be cancelled. Otherwise you will enjoy all these benefits:

1. Free 10 day examination privilege.
2. Continuous cash savings.
3. Free charts given with many books.
4. You alone decide which books you want.
5. Club books are practical working tools written by experts.

**Gernsback Electronics Book Club, Dep't. RE 87  
154 West 14 Street, New York, N.Y. 10011**

Please enroll me in the Electronics Book Club and send me the 3 books I have circled below. Bill me only \$2.00 plus shipping. If not pleased I may return the books within 10 days and this membership will be cancelled.

As a member, I need accept as few as 4 additional books a year and may resign any time after purchasing them. All books will be described to me in advance in the club bulletin and a convenient form will always be provided for my use if I don't wish to receive a forthcoming book.

Offer good in U.S.A. and Canada only.

Canadian members please add currency exchange.


Circle 3 book numbers    99    95    54    127    129

Name .....

Address .....


City ..... State ..... Zip .....
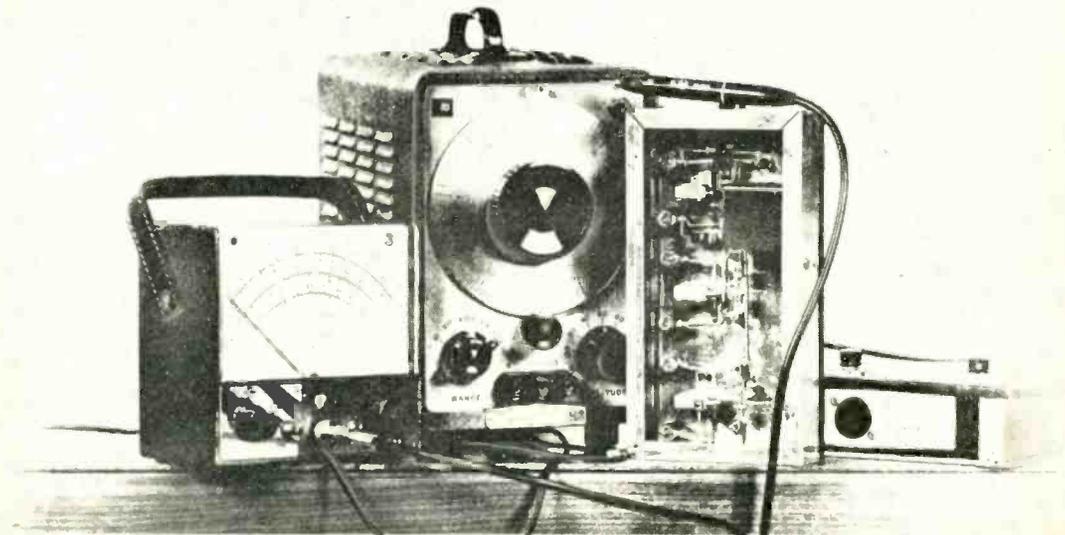
# SOMEONE SHOULD DEVELOP AN EASY WAY TO LEARN ELECTRONICS AT HOME


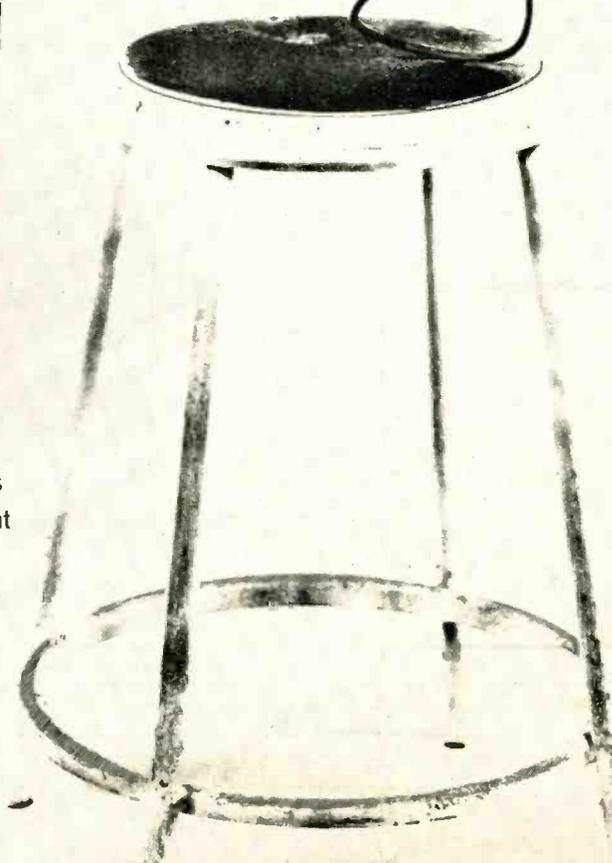
## RCA INSTITUTES DID!

Here is a whole new approach to learning electronics at home! RCA Institutes, one of the nations' largest schools devoted to electronics, has developed a faster, easier way for you to gain the skills and the knowledge you need for the career of your choice. Here for the first time, is a student-proved, scientifically designed way to learn. If you have had any doubts in the past about home training in electronics —if you have hesitated because you thought you might not be able to keep up—or that electronics was too complicated to learn—here is your answer! Read how RCA Institutes has revolutionized its entire home training ideas!



## NEW CAREER PROGRAMS BEGIN WITH "AUTOTEXT" INSTRUCTION METHOD!

Start to learn the field of your choice immediately!

No previous training or experience in electronics needed!

With this new revolutionized method of home training you pick the career of your choice—and RCA Institutes trains you for it. RCA's Career Programs assure you that everything you learn will help you go directly to the field that you have chosen! No wasted time learning things you'll never use on the job! The Career Program you choose is especially designed to get you into that career in the fastest, easiest possible way!

And each Career Program starts with the amazing "AUTOTEXT" Programmed Instruction Method—the new, faster way to learn that's almost automatic! "AUTOTEXT" helps even those who have had trouble with conventional home training methods in the past. This is the "Space Age" way to learn everything you need to know with the least amount of time and effort.

### CHOOSE A CAREER PROGRAM NOW

Your next stop may be the job of your choice. Each one of these RCA Institutes Career Programs is a complete unit. It contains the know-how you need to step into a profitable career. Here are the names of the programs and the kinds of jobs they train you for. Which one is for you?

**Television Servicing.** Prepares you for a career as a TV Technician/Service man; Master Antenna Systems Technician; TV Laboratory Technician; Educational TV Technician.

**FCC License Preparation.** For those who want to become TV Station Engineers, Communications Laboratory Technicians, or Field Engineers.

**Automation Electronics.** Gets you ready to be an Automation Electronics Technician; Manufacturer's Representative; Industrial Electronics Technician.

**Automatic Controls.** Prepares you to be an Automatic Controls Electronics Technician; Industrial Laboratory Technician; Maintenance Technician; Field Engineer.

**Digital Techniques.** For a career as a Digital Techniques Electronics Technician; Industrial Electronics Technician; Industrial Laboratory Technician.

**Telecommunications.** For a job as TV Station Engineer, Mobile Communications Technician, Marine Radio Technician.

**Industrial Electronics.** For jobs as Industrial Electronics Technicians; Field Engineers; Maintenance Technicians; Industrial Laboratory Technicians.

**Nuclear Instrumentation.** For those who want careers as Nuclear Instrumentation Electronics Technicians; Industrial Laboratory Technicians; Industrial Electronics Technicians.

**Solid State Electronics.** Become a specialist in the Semiconductor Field.

**Electronics Drafting.** Junior Draftsman, Junior Technical Illustrator; Parts Inspector; Design Draftsman Trainee Chartist.

### SEPARATE COURSES

In addition, in order to meet specific needs, RCA Institutes offers a wide variety of separate courses which may be taken independently of the Career Programs, on all subjects from Electronics Fundamentals to Computer Programming. Complete information will be sent with your other materials.

### LIBERAL TUITION PLAN

RCA offers you a unique Liberal Tuition Plan—your most economical way to learn. You pay for lessons only as you order them. No long term contracts. If you wish to stop your training for any reason, you may do so and not owe one cent until you resume the course.

### VALUABLE EQUIPMENT

You receive valuable equipment to keep and use on the job—and you never have to take apart one piece to build another. New—Programmed Electronics Breadboard. You now will receive a scientifically programmed electronic bread-

board with your study material. This breadboard provides limitless experimentation with basic electrical and electronic circuits involving vacuum tubes and transistors and includes the construction of a working signal generator and superheterodyne AM Receiver.

**Bonus From RCA—Multimeter and Oscilloscope Kits.** At no additional cost, you will receive with every RCA Institutes Career Program the instruments and kit material you need to build a multimeter and oscilloscope. The inclusion of both these kits is an RCA extra.

### CLASSROOM TRAINING ALSO AVAILABLE

RCA Institutes maintains one of the largest schools of its kind in New York City where classroom and laboratory training is available in day or evening sessions. You may be admitted without any previous technical training; preparatory courses are available if you haven't completed high school. Coeducational classes start four times a year.

### FREE PLACEMENT SERVICE

In recent years, 9 out of 10 Resident School students who used the Free Placement Service had their jobs waiting for them when they graduated. And many of these jobs were with top companies in the field—such as IBM, Bell Telephone Labs, General Electric, RCA, and radio and TV stations and other communications systems throughout the world.

**SEND ATTACHED POSTAGE PAID CARD FOR COMPLETE INFORMATION, NO OBLIGATION. NO SALESMAN WILL CALL.**

**ALL RCA INSTITUTES COURSES  
AVAILABLE UNDER NEW GI BILL.**


**RCA INSTITUTES, Inc.** Dept. RE-87

A Service of Radio Corporation of America  
350 West 4th St., New York, N.Y. 10014



**The Most Trusted Name in Electronics**
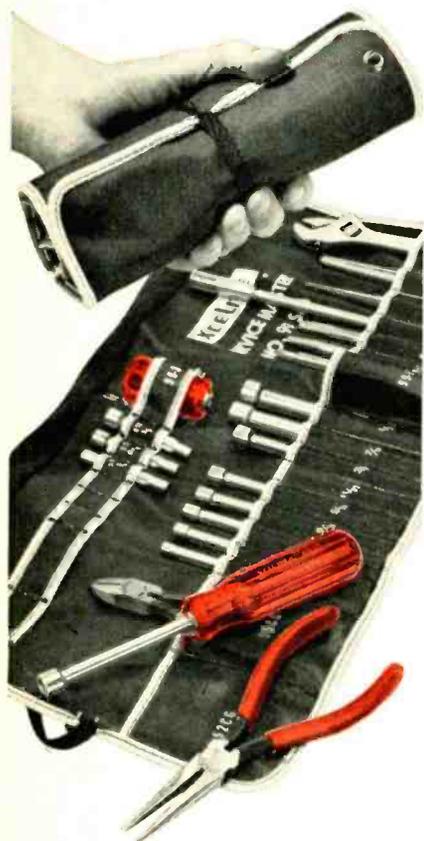
# SERVICE MASTER HANDIEST HANDFUL of service tools



23 essential tools at your fingertips in this lightweight (only 2¾ lbs.), compact, easy-to-carry, roll-up kit. Contains long nose plier, diagonal plier, adjustable wrench, regular and stubby plastic handles with these interchangeable blades: 9 regular and 3 stubby nutdriver, 2 slotted and 1 Phillips screwdriver, 2 reamer, 1 extension. Eyelets in plastic-coated canvas case permit wall hanging. New elastic loop secures roll, eliminates need for tying.

## many optional accessories:

Junior and Tee handles... Additional nutdriver, Phillips & slotted screwdriver, and extension blade sizes... Allen hex type, Bristol multiple spline, Frearson, Scrufox, and clutch head blades... Awl/Scraper... Chuck adaptors to use blades in spiral ratchet drivers.

WRITE FOR CATALOG 166

# XCELITE

XCELITE, INC., 10 Bank St., Orchard Park, N. Y. 14127

In Canada contact Charles W. Pointon, Ltd.

Circle 18 on reader's service card

Formerly SERVICE CLINIC

## In the Shop . . . With Jack

By JACK DARR

Judging from letters in my mailbox, some people have trouble getting normal range out of their CB transmitters. With a 5-watt rig, range isn't much, and proper setup and adjustment are very important.

A common problem is downward modulation. Normally, the rf amplitude should *increase* with modulation; if it goes down, you've got troubles—also far less transmitting range.

### How to tell whether it goes up or down?

Here's a simple but effective way to measure the amplitude of the transmitted rf signal (Fig. 1). All you need is a pickup rod a few feet long, a general-purpose diode, and a meter. You can use a vom or vtvm, or even a 0-1-mA meter. The pickup rod must be 8 or 10 feet from the CB antenna, and don't let anybody stand between the two. This system will give you good coupling, and when you turn on the transmitter without saying anything, you'll read the value of rf being radiated.

Now, when you modulate this rf energy, you *add power*. In an AM transmitter, about half the output power is in the modulation. Fig. 2 shows how this works with signal voltages as you'd see it if you put a scope on the antenna. The 50-volt audio signal adds to the 50-volt rf, for a total of 100 volts peak. This is voltage; because  $P = E^2/R$ , the power increase is 22% with 100% modulation.

In the CB transmitter the audio circuit consists of the mike, voltage amplifier and modulator stage. It is usually capable of supplying 5 watts of audio power to the final, which is what's needed for full modulation.

What is there in the rf circuit? An oscillator feeds rf to the power output or final stage. This is followed (Fig. 3) by a tuned pi network for tuning and loading and a pi-network filter to keep the harmonics out of Uncle John's old TV set next door (we hope!). With 5 watts dc plate input and an efficiency of 70% at best, there is a *potential* 3.5-watt rf output. Can you actually get 3.5 watts of rf?

That depends on how well the final stage is tuned, on how well the antenna

continued on page 26

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 154 West 14th Street, New York 10011.

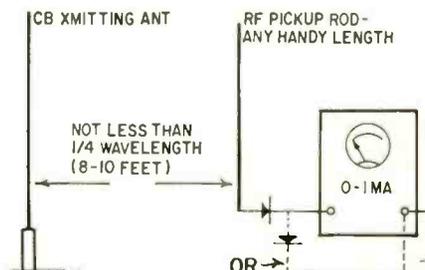


Fig. 1—How to measure the rf signal.


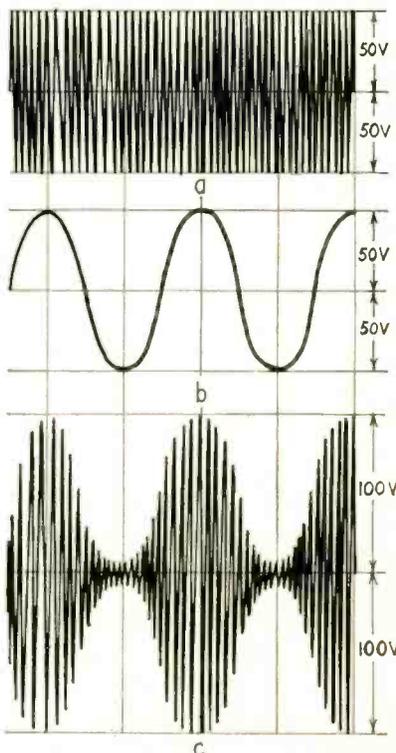


Fig. 2—Unmodulated rf (a) adds with audio (b) to produce modulated rf (c).

# New Solid-State High Impedance V-O-M

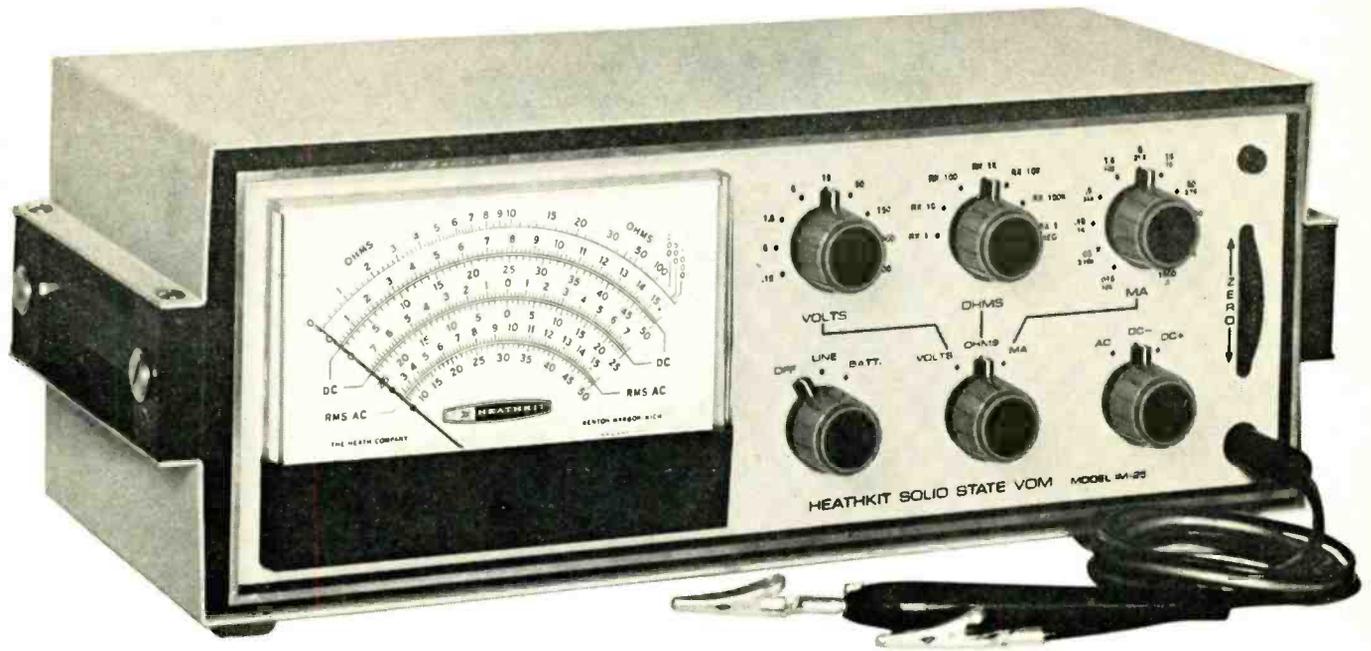

## The Unique New Heathkit® IM-25

**Kit \$80      Wired \$115**

Never Before Has An Instrument With These Features  
and Performance Been Available At Less Than \$200

• 13 Silicon Transistors Plus 2 Field Effect Transistors • 11 Megohm Input Impedance on DC • 10 Megohm Input Impedance on AC • 9 DC Voltage Ranges From 150 Millivolts Full Scale to 1500 Volts Full Scale . . . Accuracy = 3% Full Scale • 9 AC Voltage Ranges From 150 Millivolts Full Scale to 1500 Volts Full Scale . . . Accuracy = 5% Full Scale • 7 Resistance Ranges, 10 Ohms Center Scale x1, x10, x100, x1k, x10k, x100k, x1 Meg . . . Measures From One Ohm to 1000 Megohms • 11 Current Ranges From 15 Microamps Full Scale to 1.5 Amps Full Scale . . . Accuracy = 4% DC, = 5% AC • AC Response to 100 kHz • 6", 200 ua Meter With Zero Center Scales For Positive and Negative Voltage Measurements Without Switching • 1% Precision Resistors • Separate Switch For Each Function Eliminates Constant Changing • Ten-Turn Thumb-wheel Zero Adjustment For Precision Settings • Built-In 120/240 VAC, 50-60 Hz Power Supply Plus In-Cabinet Holders For Battery Supply During Portable Operation • Easy Circuit Board Assembly • New Heath Instrument Styling With "Unitized" Construction and Low Profile Appearance • Color Styled in Handsome Beige and Black

**IM-25 SPECIFICATIONS — DC SECTION:** Voltmeter: Ranges: 0 - 0.15, 0.5, 1.5, 15, 50, 150, 500, 1500 volts full scale. Input Resistance: 11 megohms on all ranges. Accuracy: ±3% of full scale. Milliammeter: Ranges: 0 - 0.15, .05, 0.15, 0.5, 1.5, 5, 15, 50, 150, 500, 1500 ma full scale. Input Resistance: 0.1 ohm (1500 ma) to 10 K ohm (0.015 ma). Accuracy: ±4% of full scale. **AC SECTION:** Voltmeter: Ranges: 0 - 0.15, 0.5, 1.5, 15, 50, 150, 500, 1500 volts full scale. Input Resistance: 10 megohm shunted by 150 uuf. Accuracy: ±5% of full scale. Frequency Response: ±2 db 10 Hz - 100 kHz. Milliammeter: Ranges: 0 - 0.015, 0.05, 0.15, 0.5, 1.5, 5, 15, 50, 150, 500, 1500 ma, full scale. Input Resistance: 0.1 ohm (1500 ma) to 10 k ohm (0.015 ma). Accuracy: ±5% of full scale. **Ohm Meter:** Ranges: 10 ohm center scale x1, x10, x100, x1k, x10k, x100k, x1 meg. Probe: Combined AC - OHMS - DC switching probe, single jack input for Probe and Ground connections, Circuit ground isolated from cabinet. **Dividers:** 1% Precision Type. **Meter:** 6", 200 ua, 100° movement. **Transistors, Diodes:** 2 - 2N4304 FET transistor; 13 - 2N3393 silicon junction transistor; 1 - 9.1 V zener diode; 1-13 V zener diode; 4-1N191 germanium diode; 1 silicon Power Supply diode. **POWER SUPPLIES:** Ohms Circuit: 3 volts. (C - cells) Ohms Circuit Bias: 1.35 volt (E1N Mercury Cell). Amplifier Circuit: 18 volts. **Battery Operation:** C cells. **Line Operation:** Transformer operated 1/2 wave circuit, operable on either 120 or 240 V AC 50-60 Hz.

The first of an exciting new line of Heathkit test instruments, the IM-25 Solid-State V-O-M does all the measurement jobs normally required in tube or transistor circuits with the no-loading high impedance of a VTVM, the convenience and versatility of a VOM, and the accuracy and sensitivity of separate lab instruments.

Accuracy of the impressive specifications of the IM-25 are assured by careful attention to design details. For example, the input of the IM-25 "floats," isolating the input circuit from the cabinet. (The cabinet is grounded by a three-wire line cord.) Double Zener-diode regulation minimizes zero shift when changing from line to battery operation. Ohms scale calibration is a set-and-forget adjustment. DC voltage measurements require only a shorted input check of meter zero. Applied voltage during resistance measurements is less than 100 millivolts from a constant-current source to avoid the possibility of erroneous readings or circuitry damage.

Those who choose the kit model IM-25 rather than the factory assembled and tested version will find it far easier to build than any other kit meter we've ever offered. All components mount on just one circuit board . . . even the switches. No more tedious divider circuit wiring. And a special wiring harness is provided.

A die-cast panel bezel ties both front and rear panels together with the circuit board supported between to permit removal of the cabinet shells without impairing operation. Convenient carrying handles are recessed in each of the cabinet shell mounting strips.

Whether you choose the factory assembled model or the kit version, we believe you will find the IM-25 a significant step forward in design and value . . . capable of creditable service in any application.

Kit IM-25, 10 lbs. . . . . \$80.00  
Assembled IMW-25, 10 lbs. . . . . \$115.00



### FREE CATALOG

Describes these and over 250 kits for stereo/hi-fi, color TV, amateur radio, shortwave, test, CB, marine, educational, home and hobby. Save up to 50% by doing the easy assembly yourself. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022

HEATH COMPANY, Dept. 20-8  
Benton Harbor, Michigan 49022

Enclosed is \$ \_\_\_\_\_, plus shipping.

Please send model (s) \_\_\_\_\_

Please send FREE Heathkit Catalog.

Name \_\_\_\_\_ (Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Prices & specifications subject to change without notice.

TE-158



# Are you eligible for the Bright Guy Awards?

It's easy to get them—and to get all the business they'll bring you. New customers. More sales. More money.

The Bright Guy Awards is the big program Sylvania's running this year to boost your sales.

Your Sylvania distributor can put your name and address in TV Guide ads in your area. The ads call you "the brightest serviceman in town"—and tell people in your town why they should call you.


You'll get into the Yellow Pages, too, under the heading "TV Service and Repairs."

Once again this year you'll be eligible for over one hundred valuable, interesting



—and tell people in your town why they should call you.

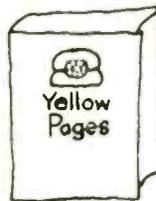
You'll get into the Yellow Pages, too, under the heading



SMB-Bright Guy gifts, just for buying the Sylvania TV replacement parts you normally buy anyway.

And you'll get window displays proclaiming you "the brightest"—the TV serviceman everyone's reading about.

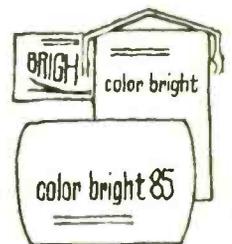You're eligible for the Bright Guy Awards just by buying Sylvania's famous *color bright 85*<sup>®</sup> picture tube. And our other picture tubes, and our receiving tubes. So see your Sylvania distributor.



Sylvania Electronic Tube Division, Electronic Components Group, Seneca Falls, New York 13148.

**SYLVANIA**  
SUBSIDIARY OF  
GENERAL TELEPHONE & ELECTRONICS **GTE**

Circle 20 on reader's service card

and transmission line are matched to the rf output, and on how well the antenna was installed!

The output power of any amplifier stage depends on how well it is matched to the load. Check the antenna (load) and coax to make sure they are 50 ohms and properly coupled.

If everything is working normally, when you push the transmit button and whistle into the mike, you'll see the meter reading *increase* by about 25%. It makes no difference what the actual me-

ter readings are, only what percentage of increase there is.

Suppose the reading drops—say from 1 to about 0.75. Trouble! This is downward modulation, and it means that you are *losing* power instead of gaining it with modulation. A scope would show how power is being lost (Fig. 4).

What's happening? Audio is simply overpowering the weak rf output, and trying to drive it into negative output (which isn't too likely!). So, for certain parts of the cycle, there is no rf power output at all. This produces audio


distortion in the received signal; the tone gets very squawky.

Downward modulation has to occur in the rf final stage. That's the *only* place the output can change. Output goes down if the antenna is mistuned or an incorrect load (antenna) is used. Since the audio modulation level can be considered as fixed, the only cure for downward modulation is get the rf level up to where it ought to be.

For most efficient power transfer (highest rf output) the antenna must be tuned and loaded correctly. You start by tuning the plate tank circuit to resonance (the TUNE adjustment in Fig. 3). You can use a field-strength meter and tune for maximum rf output; or you can hook a dc milliammeter into the plate current. The peak on the FS meter and the dip in plate current should be *at the same* setting of TUNE. That's the first step.

Now, with maximum rf current circulating in the plate tank coil, you need to get it to the antenna with the
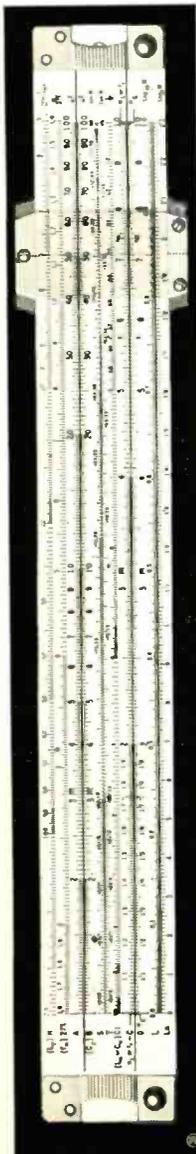
## Now, for men in electronics —“a whole new era of quick calculation”



**T**HERE MUST BE THOUSANDS OF PEOPLE in electronics who have never had the marvelous adventure of calculating problems with a single slide rule; other thousands have had to content themselves with a slide rule not specifically designed for electronics. For both groups, the new slide rule designed and marketed by Cleveland Institute of Electronics and built for them by Pickett will open a whole new era of quick calculations.

“Even if you have never had a slide rule in your hands before, the four-lesson instruction course that is included takes you by the hand and leads you from simple calculations right through resonance and reactance problems with hardly a hitch. If you already use a slide rule, you'll find the lessons a first-rate refresher course. And it explains in detail the shortcuts built into this new rule.”

From an article in  
**Radio Electronics Magazine**

Want complete details about this time-saving new Electronics Slide Rule? Just mail coupon below . . . or write Cleveland Institute of Electronics, Dept. RE-143, 1776 East 17th St., Cleveland, Ohio 44114.

How to Solve Electronics Problems in Seconds



Mail this coupon for  
**FREE BOOKLET**

**CIE** Cleveland Institute of Electronics  
1776 E. 17th St., Cleveland, Ohio 44114

Please send me without charge or obligation your booklet describing the CIE Electronics Slide Rule and Instruction Course. Also FREE if I act at once: a handy pocket-size Electronics Data Guide.

Name \_\_\_\_\_ (please print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Accredited Member National Home Study Council  
A Leader in Electronics Training . . . Since 1934 RE-143

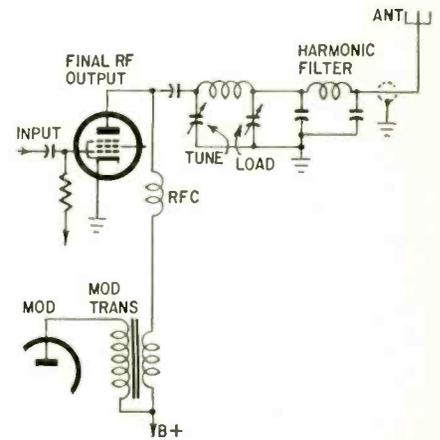


Fig. 3—You'll almost always find the cause of downward modulation in this circuit.

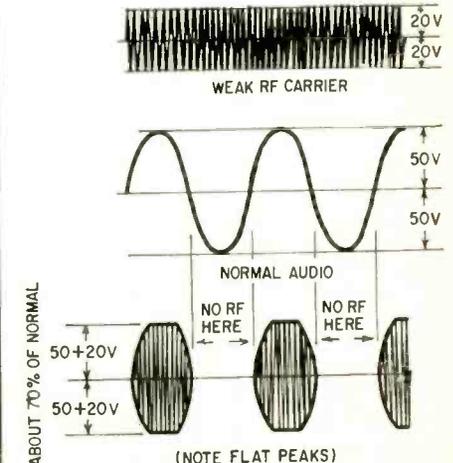


Fig. 4—A weak rf carrier swamped by audio produces downward modulation.

least loss; this is what the LOAD adjustment is for. (Since the antenna inductance and capacitance are fixed, you have to adjust the transmitter circuits to match the antenna.) Once again, adjust for maximum reading on the field-strength meter, indicating increasing rf power output.

As you adjust LOAD, you'll see the plate-current reading rise from its "dipped" value. You're taking power out of the circuit, so you have to raise the current; power means current times voltage. As you increase loading, the plate dip will become shallower until at full output it may be barely visible. It must still be there, however, when the plate-tank tuning is varied.

If the plate tank is *not* at resonance, you'll have an out-of-phase condition, and lose rf power. The plate circuit will not deliver maximum rf power to the antenna, and you'll have improper modulation.

If you want to see these patterns, or use a scope for tuning-up adjustments or modulation tests, be sure to feed rf directly to the vertical plates of the scope CRT. Don't try to go through the vertical amplifiers of the scope. Even a "wideband" scope won't carry the 27-MHz rf signal very far! Since you won't be able to use the scope vertical gain control, you'll have to adjust image height by altering the length or spacing of the rf pickup.

If you follow this method of tuning up, and make darn sure the antenna is correctly installed, you'll get the maximum "talk-power" out of any CB transmitter. Not only does this insure maximum range, but it makes the signal far more readable by eliminating over-modulation distortion.

If you still have downward modulation, this indicates one or more of the following troubles:


1. Insufficient grid drive to the final amplifier. This can be caused by a detuned oscillator or buffer stage or a weak oscillator or buffer tube.
2. Insufficient grid bias on modulated stage. Check grid and cathode resistors for correct value.
3. High-impedance power supply. Check output filter capacitor. Replace with a larger value if necessary to eliminate the trouble.

#### Burned-up socket

*The HV rectifier socket in this Zenith color chassis burned up, but I can't see why! I replaced it, and the set*

*works fine. What happened?—P.M., Detroit, Mich.*

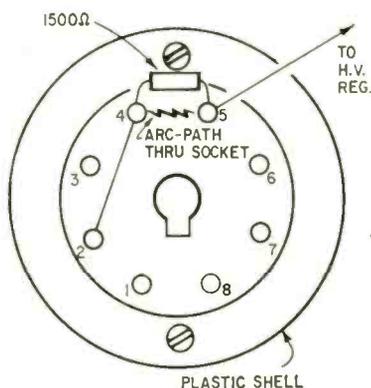The 1,500-ohm resistor in series with the HV lead opened. This resistor is tied across plus 4 and 5 on the socket;



so, the HV simply jumped this gap and kept on! In a little while, the heat caused by the arc burned the socket up. The diagram shows how it works.

#### Remote volume control in car

*I've mounted my transistor car radio in the trunk; I have a remote-control gadget for tuning, but I'm having trouble working out a suitable remote volume control.—D. G., Montreal, Canada*

Having a transistor output stage, you can't fool around with simple pot-type controls, for you'll get into trouble with output transistors. The best kind of remote control is an L-pad, of the same impedance as your speaker, whatever it happens to be.

In your set, it's a 3.2-ohm voice coil, which is unusual in transistor radios, but handy. You can get several kinds of L-pads in 4-ohm sizes. They are used with hi-fi systems, where they control the volume while maintaining a constant impedance across the audio line at all times. END

#### KNOW YOUR L's AND T's

is good advice to anyone concerned with audio, hi-fi, stereo, PA, or tape recording. Want a pair of remote speakers in your back yard? Probably you'll use L or T pads for volume control. Here's a nuts-and-bolts rundown of what's available, how they work, and how to use them. Read it in

September RADIO-ELECTRONICS.

**It will actually take you longer to read this advertisement than to install this new "Quick Grip" mobile antenna mount. No holes to drill. Cable is completely hidden. Makes the world's finest antennas the world's most practical.**




Practically every A/S mobile CB antenna made may be ordered with a "Quick-Grip" mount, including all versions of the mighty Maggie Mobiles.


Model M-176, illustrated above. M-175, same coil and whip less spring. M-177 is "Quick-Grip" version of our great 18" Mighty-Mite. Mount only also available.

**the antenna specialists CO.** division of Anzac Industries, Inc.

12435 Euclid Ave., Cleveland, Ohio 44106  
Export: 64-14 Woodside Ave., "Stripes of Quality"  
Woodside, N.Y. 11377

**“Get more  
education  
or  
get out of  
electronics  
...that’s my advice.”**

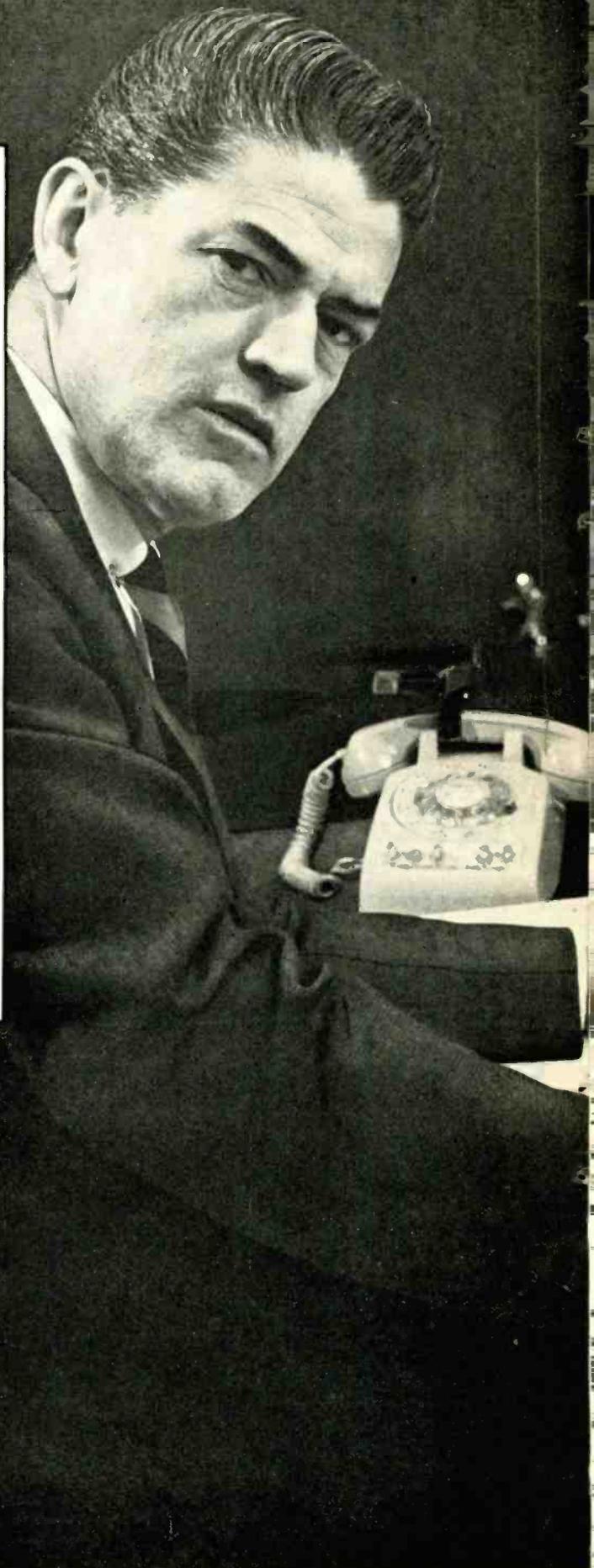

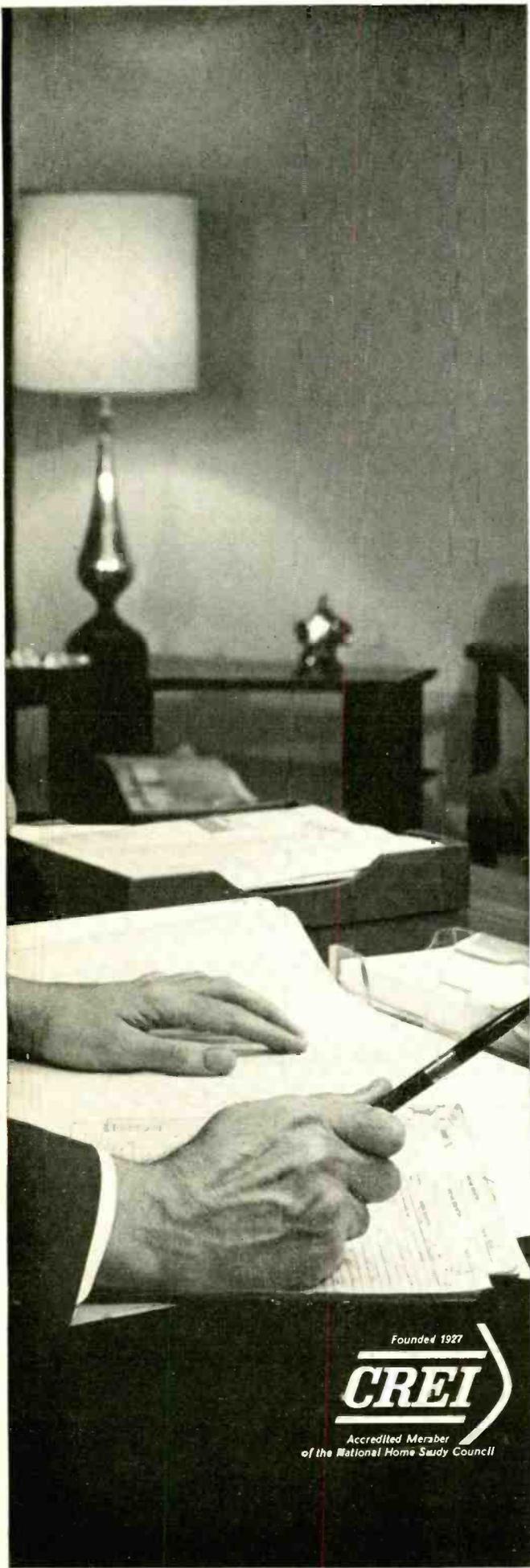

Founded 1927  
**CREI**  
 Accredited Member  
 of the National Home Study Council

**Ask any man who really knows the electronics industry.**

Opportunities are few for men without advanced technical education. If you stay on that level, you'll never make much money. And you'll be among the first to go in a layoff.

But, if you supplement your experience with more education in electronics, you can become a specialist. You'll enjoy good income and excellent security. You won't have to worry about automation or advances in technology putting you out of a job.

How can you get the additional education you must have to protect your future—and the future of those who depend on you? Going back to school isn't easy for a man with a job and family obligations.

CREI Home Study Programs offer you a practical way to get more education without going back to school. You study at home, at your own pace, on your own schedule. And you study with the assurance that what you learn can be applied on the job immediately to make you worth more money to your employer.

You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. Air-mail postpaid card for your copy. If card is detached, use coupon below or write: CREI, Dept. 1408-E, 3224 Sixteenth Street, N.W., Washington, D.C. 20010.



**The Capitol Radio Engineering Institute**  
 A Division of McGraw-Hill, Inc.  
 Dept. 1408-E, 3224 Sixteenth Street, N.W.  
 Washington, D.C. 20010

Please send me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP CODE \_\_\_\_\_

EMPLOYED BY \_\_\_\_\_


TYPE OF PRESENT WORK \_\_\_\_\_  G.I. BILL

I am interested in  Electronic Engineering Technology  
 Space Electronics  Nuclear Engineering Technology  
 Industrial Electronics for Automation  
 Computer Systems Technology

**APPROVED FOR TRAINING UNDER NEW G.I. BILL**

# A Modern FM Stereo Adapter

By **KENNETH F. BUEGEL**

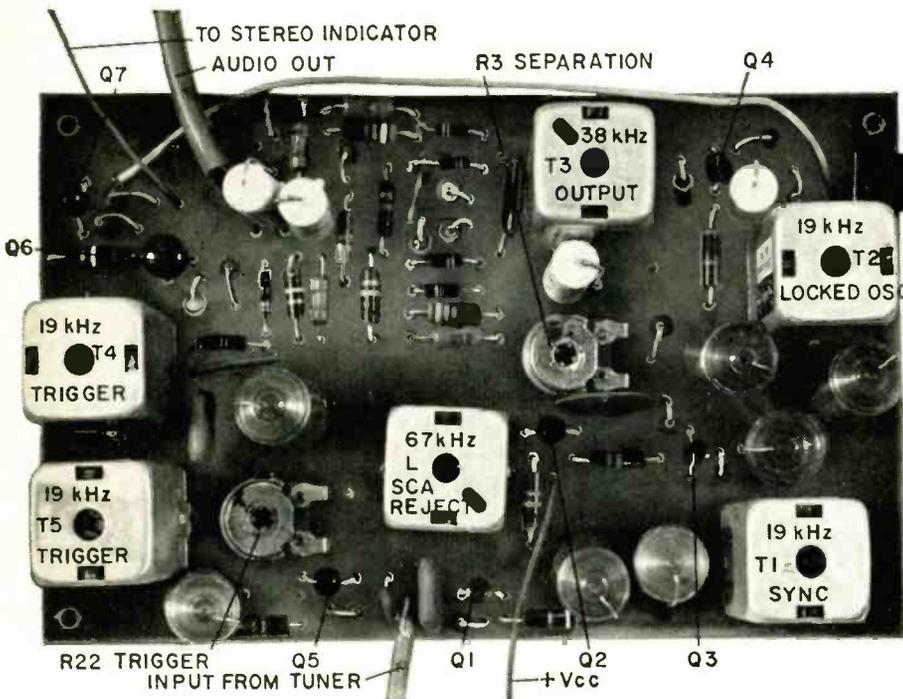

THIS STEREO FM DEMODULATOR IS DESIGNED AROUND RECENT SILICON PLANAR TRANSISTORS AND USES HIGH-STABILITY POLYSTYRENE CAPACITORS. IT IS COMPATIBLE WITH ANY DETECTOR OUTPUT LEVEL BETWEEN 0.3 AND 5 VOLTS PEAK TO PEAK. SEPARATION ON A PROPERLY CONSTRUCTED UNIT WILL EXCEED 30 DB FROM 50 Hz TO 14 KHz, AND 40 DB FROM 100 Hz TO 10 KHz.

Many stereo listeners are puzzled when a good stereo adapter added to a previously satisfactory tuner fails to produce adequate separation. Often the trouble lies in unexpected areas. When you've been intelligent and careful in connecting the adapter to the tuner, and the antenna installation isn't faulty, what else could be wrong?

In almost every instance I have investigated, the problem was caused by restricted tuner bandwidth, which causes a distorted response in the 23-53-kHz subcarrier range. Many otherwise fine

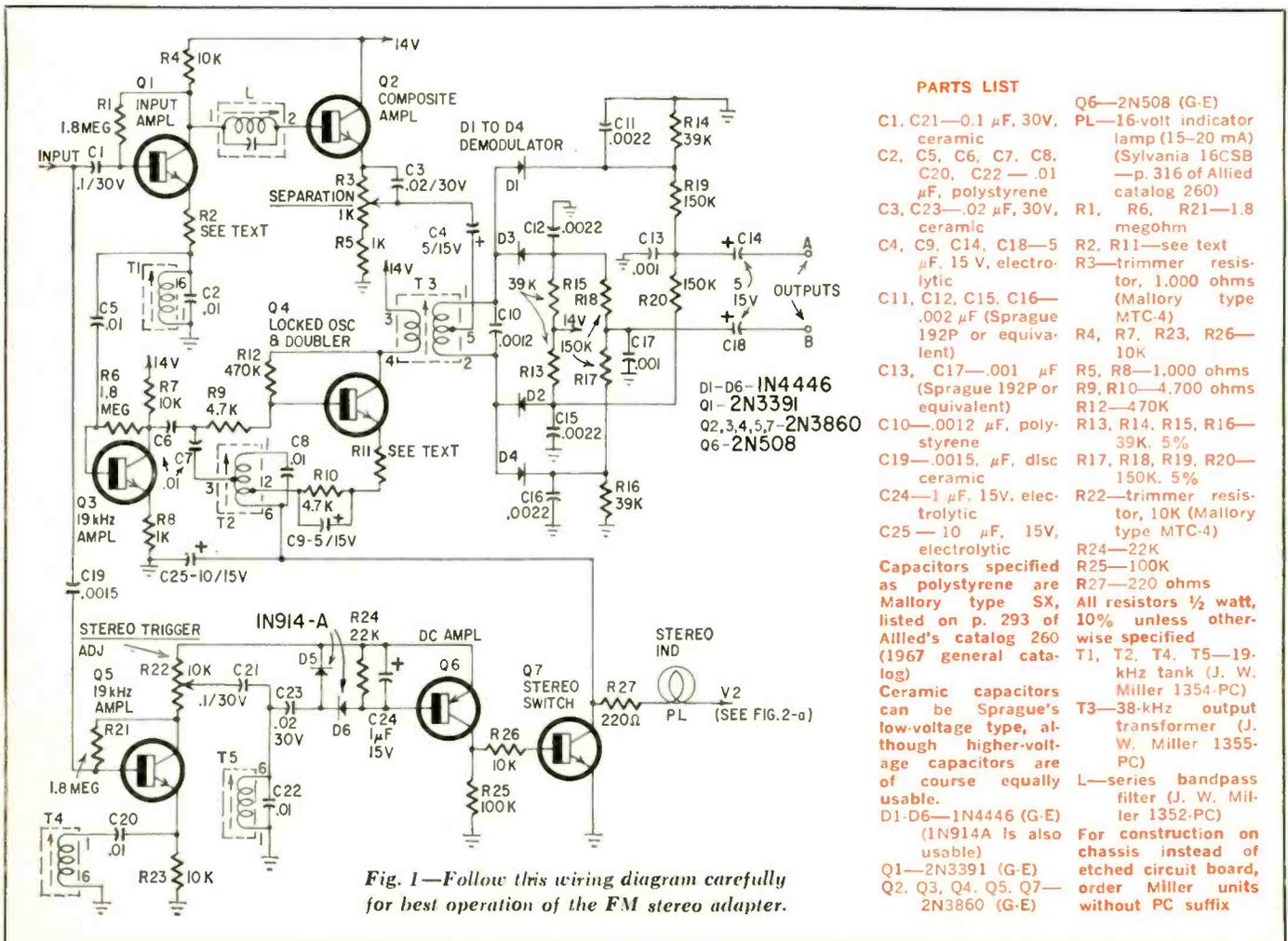


Fig. 1—Follow this wiring diagram carefully for best operation of the FM stereo adapter.

## PARTS LIST

- C1, C21—0.1  $\mu$ F, 30V, ceramic
  - C2, C5, C6, C7, C8, C20, C22—0.1  $\mu$ F, polystyrene
  - C3, C23—0.02  $\mu$ F, 30V, ceramic
  - C4, C9, C14, C18—5  $\mu$ F, 15 V, electrolytic
  - C11, C12, C15, C16—0.002  $\mu$ F (Sprague 192P or equivalent)
  - C13, C17—0.01  $\mu$ F (Sprague 192P or equivalent)
  - C10—0.0012  $\mu$ F, polystyrene
  - C19—0.0015  $\mu$ F, disc ceramic
  - C24—1  $\mu$ F, 15V, electrolytic
  - C25—10  $\mu$ F, 15V, electrolytic
  - Capacitors specified as polystyrene are Mallory type SX, listed on p. 293 of Allied's catalog 260 (1967 general catalog)
  - Ceramic capacitors can be Sprague's low-voltage type, although higher-voltage capacitors are of course equally usable.
  - D1-D6—1N4446 (G-E) (1N914A is also usable)
  - Q1—2N3391 (G-E)
  - Q2, Q3, Q4, Q5, Q7—2N3860 (G-E)
  - Q6—2N508 (G-E)
  - PL—16-volt indicator lamp (15-20 mA) (Sylvania 16CSB—p. 316 of Allied catalog 260)
  - R1, R6, R21—1.8 megohm
  - R2, R11—see text
  - R3—trimmer resistor, 1,000 ohms (Mallory type MTC-4)
  - R4, R7, R23, R26—10K
  - R5, R8—1,000 ohms
  - R9, R10—4,700 ohms
  - R12—470K
  - R13, R14, R15, R16—39K, 5%
  - R17, R18, R19, R20—150K, 5%
  - R22—trimmer resistor, 10K (Mallory type MTC-4)
  - R24—22K
  - R25—100K
  - R27—220 ohms
  - T1, T2, T4, T5—19-kHz tank (J. W. Miller 1354-PC)
  - T3—38-kHz output transformer (J. W. Miller 1355-PC)
  - L—series bandpass filter (J. W. Miller 1352-PC)
- For construction on chassis instead of etched circuit board, order Miller units without PC suffix

tuners may have this defect. It is possible to compensate for it.

This decoder incorporates just that kind of compensation. The schematic is in Fig. 1. Input stage Q1 has adjustable gain to match different tuner output levels. Because of heavy feedback the input impedance is high enough to allow direct connection to a vacuum-tube tuner without heavy loading. The value of R2 is selected during alignment.

L is the SCA (Subsidiary Communications Authorization) rejection filter, which, with the well-balanced output detectors, keeps SCA program matter inaudible. Emitter follower Q2 sends composite audio at low impedance to the center tap of T3, a 38-kHz doubler in the collector of Q4. The pilot signal developed across T1 is amplified by Q3 and synchronizes the 19-kHz locked oscillator, Q4.


Q5 selects and amplifies the 19-kHz pilot signal. R22 is the trigger adjustment, which sets the level of pilot signal required to switch the adapter to stereo reception. D5 and D6 charge C24 with rectified pilot signal until Q6, a dc amplifier, is forward-biased.

Q6 drives Q7 into saturation, which lights lamp PL and brings the lower end of T2 to ground potential. Under these conditions Q4 oscillates and T3 provides the switching signals to the output detectors. Diode pairs D1-D3 and D2-D4 will conduct alternately at the 38-kHz switching rate and channel left and right components of the signal applied to T3 centertap to correct outputs.

During monaural reception, when no pilot signal is present, Q7 will be cut off and its collector at supply potential. A slight reverse bias will prevent oscillation in Q4. There is now a path through D1, D2, R13, and R14; thus the monaural signal applied to the center tap of T3 appears at output A. A similar path exists for the same signal to appear at output B. The de-emphasis networks precede output jacks.

The decoder circuits draw about 8 mA from a 14-volt supply. PL's current is 20 mA from a slightly higher potential. If it is not convenient to draw this much current from an available source, the regulated supply shown in Fig. 2 will power the decoder.

When constructed on an etched circuit board, the complete decoder, including required bottom clearance, fits in a space 3 3/4 x 6 x 2 inches. Since the unit is extremely stable and won't need constant adjustment, it can be tucked away in an unused cabinet corner. If you decide on chassis construction, a recommended size is 7 by 9 inches. This provides room for the power supply, terminal strips, transistor sockets, etc. If you plan to build on a chassis instead of on a circuit board, be certain to order

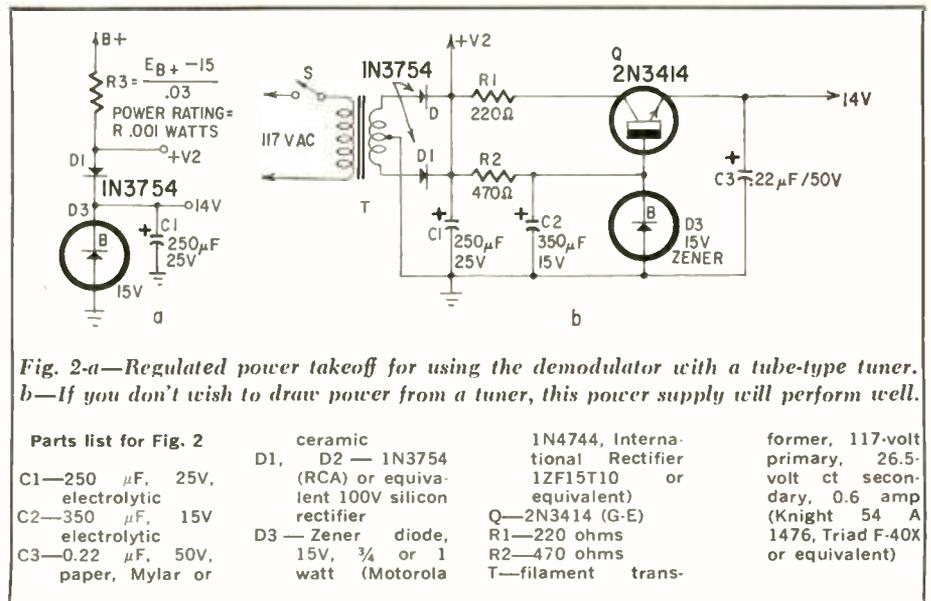

the transformers without the PC (printed circuit) suffix.

In mounting parts to the wiring board, first install the transformers, then R3, R22, all other resistors and capacitors (except R2 and R11), and finally the transistors and polystyrene capacitors.

The first step in alignment is to measure the multiplex output level of the tuner with an oscilloscope. Use the highest peak-to-peak reading as a reference. Use an input level, from an audio generator to the decoder, of 25% higher than this reference level. (Use any convenient frequency in the audio range.) Choose a value for R2 between 3.9K and 12K (larger input, larger value) which allows undistorted reproduction of the input signal as seen on a scope at the emitter of Q2.

Next insert a 67-kHz signal (this should be accurate) and tune L for *minimum* signal at Q2's emitter. Insert a 19-kHz signal at one-fourth reference level and tune T1 for *maximum* voltage across its winding. Reduce the input signal and tune T4 and T5, with R22 at maximum, for maximum voltage across R24. During tuning reduce the input level until the voltage across R24 starts to decrease; at this point the tuning effect is most pronounced.

Tack in a 470-ohm resistor for R11 and temporarily ground the collector of

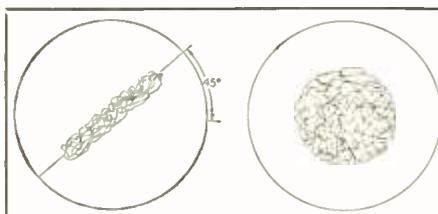


Fig. 3-a—Poor stereo separation; b—good separation; scope at adapter output.

Q7. Tune T3 for maximum amplitude of the 38-kHz waveform at Q4's collector. Then tune T2 until any jitter in the waveform disappears, indicating synchronization with the input signal. Continue to retune T1, T2, and T3, while reducing the input level, until the oscillator is synchronized with a 19-kHz input signal at least 26 dB (one-twentieth) below reference.

Select a value for R11 between 200 and 1,000 ohms that provides maximum undistorted 38-kHz output. Too low a value will give lower-amplitude switching voltages and reduced separation. Adjacent cycles of the switching waveform will not have identical height (this is normal) but should be within 20%.

If you have access to a stereo multiplex generator, remove the ground at Q7's collector and inject a composite signal at reference level. Set R22 to place Q7 in saturation and adjust R3 for maximum separation.

If such a generator is not available, you can run through the procedure just described with the decoder connected to a tuner receiving a stereo transmission. Connect a potentiometer (about 100K) to the tuner output to allow the input to the decoder to be reduced during alignment.

After preliminary adjustment remove the potentiometer from the circuit. Connect outputs A and B to the vertical and horizontal inputs of a scope. Tune to a station known to be transmitting a stereophonic broadcast. Adjust R22 until PL lights. The scope pattern will probably resemble Fig. 3-a. Adjust R3 until the scope display looks like Fig. 3-b. A slight touchup of T1 and resetting of R3 will result in best separation. If the separation seems poor, try another stereo station or broadcast.

END

# Stereo FM Stations

In the US and Canada the number of FM stations broadcasting in stereo continues to grow. More than 700 currently air two-channel programs at various times of the day. This list includes all known stations. Some may be heard in towns other than those shown.

## ALABAMA

Albertville	WQSB-FM	105.1
Andalusia	WNBX	98.1
Birmingham	WCRT-FM	96.5
	WSFM	93.7
Dothan	WDOF-FM	99.7
Florence	WDOI-FM	107.3
Huntsville	WAHR	99.1
	WNDA	95.1
Mobile	WKRQ-FM	99.9
	WLPR-FM	96.1
Monroeville	WMFC-FM	99.3
Montgomery	WAJM	103.3
	WFMI-FM	98.9
Muscle Shoals	WLAY-FM	105.5
Selma	WHBB-FM	100.1
Tuscaloosa	WACT-FM	105.5
	WTBC-FM	95.7

## ALASKA

Anchorage	KAMU	102.1
	KNIK-FM	105.5

## ARIZONA

Phoenix	KHEP-FM	101.5
	KMEO	96.9
	KNIX	102.5
	KOOL-FM	94.5
	KRFM	95.5
Tucson	KSOM	92.9

## ARKANSAS

El Dorado	KELD-FM	103.1
	KRIL	99.3
Fayetteville	KNWA-FM	103.9
Fort Smith	KMAG	99.1
Hot Springs	KGUS-FM	97.5
Jonesboro	KBTM-FM	101.9
Little Rock	KARK-FM	103.7

## CALIFORNIA

Alameda	KJAZ	92.7
Bakersfield	KGEE-FM	101.5
	KIFM	96.5
Berkeley	KPAT-FM	102.9
Carlsbad	KARL-FM	95.9
Coachella	KCHV-FM	93.7
Escondido	KOWN-FM	92.1
Fresno	KCIB	94.5
	KFRE-FM	93.7
	KXQR	102.7
Garden Grove	KTBT	94.3
Lodi	KCVR-FM	97.7
Long Beach	KNOB	97.9
Los Angeles	KBBi	107.5
	KBIG-FM	104.3
	KCBH	98.7
	KFAC-FM	92.3
	KFMU	97.1
	KFOX-FM	100.3
	KMET	94.7
	KPOL-FM	93.9

	KRHM	102.7
	KXLU	89.1
Los Banos	KLBS-FM	95.9
Los Gatos	KLGS	95.3
Marysville	KRFD	99.9
Monterey	KMBY-FM	96.9
Newport Beach	KOCM	103.1
Oceanside	KUDE-FM	102.1
Palm Springs	KDES-FM	104.7
Patterson	KOSO	93.1
Redondo Beach	KKOP	93.5
Riverside	KDUO	97.5
Sacramento	KCRA-FM	96.1
	KFBK-FM	92.5
	KHIQ	105.1
	KSFM	96.9
Salinas	KSBW-FM	102.5
San Diego	KBBW	102.9
	KFMX	96.5
	KGB-FM	101.5
	KLRO	94.9
	KPRI	106.5
San Fernando	KVFM	94.3
San Francisco	KABL-FM	98.1
	KBRG	105.3
	KFOG	104.5
	KGO-FM	103.7
	KKHI-FM	95.7
	KMPX	106.9
	KPEN	101.3
	KSFR	94.9
San Jose	KEEN-FM	100.3
	KSJO-FM	92.3
San Luis Obispo	KSBY-FM	93.3
San Rafael	KTIM-FM	100.9
Santa Ana	KWIZ-FM	96.7
Santa Barbara	KGUD-FM	99.9
	KMUZ	103.3
Santa Clara	KREP	105.7
Santa Maria	KXFM	99.1
Stockton	KUOP	91.3
Tracy	KSRT	100.9
Tulare	KDFR-FM	106.7
	KGEN-FM	94.9
Turlock	KOSO	93.1
Ventura	KUDU-FM	95.1
Visalia	KONG-FM	92.9
Walnut Creek	KDFM	92.1
Woodland	KATT	102.5

## COLORADO

Boulder	KRNW	97.3
Colorado Springs	KPIK-FM	94.3
Denver	KFML-FM	98.5
	KLIR-FM	100.3
	KOSI-FM	101.1
	KTGM	105.1
Fort Collins	KFMF	93.3
Loveland	KLOV-FM	102.3
Manitou Springs	KCMS-FM	102.7

## CONNECTICUT

Bridgeport	WJZZ	99.9
Brookfield	WGHF	95.1

Fairfield	WSHU	91.1
Hartford	WHCN	105.9
	WTIC-FM	96.5
Meriden	WBMI	95.7
New Haven	WNHC-FM	99.1
	WYBC-FM	94.3

## DELAWARE

Wilmington	WDEL-FM	93.7
	WJBR	99.5

## DISTRICT OF COLUMBIA

(Washington)	WASH	97.1
	WGAY	99.5
	WGMS-FM	103.5
	WMAL-FM	107.3

## FLORIDA

Belle Glade	WSWN-FM	93.5
Boca Raton	WWOG	99.9
Bradenton	WBRD-FM	103.3
Clearwater	WTAN-FM	95.7
Cocoa	WEZY-FM	99.3
Cocoa Beach	WRKT-FM	104.1
	WXBR	101.1
Coral Gables	WVCG-FM	105.1
Crestview	WAAZ-FM	104.9
Daytona Beach	WNDB-FM	94.5
Fort Lauderdale	WFLM	105.9
	WMJR	100.7
Fort Myers	WINK-FM	96.9
Fort Walton Beach	WFTW-FM	99.3
Gainesville	WRUF-FM	103.7
Jacksonville	WIVY-FM	102.9
	WJAX-FM	95.1
	WKTZ-FM	96.1
	WQIK	99.1
Marianna	WTOT-FM	100.9
Miami	WGBS-FM	96.3
	WIOD-FM	97.3
	WWPB	101.5
Miami Beach	WAEZ	94.9
Milton	WXBM-FM	102.3
Orlando	WHOO-FM	96.5
Palm Beach	WWOS	97.9
Panama City	WMAI-FM	107.9
Pensacola	WPEX-FM	94.1
St. Augustine	WFOY-FM	97.7
St. Petersburg	WTCX	99.5
Sarasota	WSAF-FM	102.5
Stuart	WMCF	92.7
Tallahassee	WBGm	98.9
	WFSU-FM	91.5
Tampa	WFLA-FM	93.3
West Palm Beach	WPBF	107.9
Winter Haven	WXKL-FM	97.5

## GEORGIA

Albany	WGPC-FM	104.5
	WJIZ	96.3
Americus	WOEC-FM	94.3
Athens	WGAU-FM	95.5
Atlanta	WKLS	96.1
	WLTA-FM	99.7
	WSB-FM	98.5
Carrollton	WBTR-FM	92.1
Columbus	WRBL-FM	102.9
Cornelia	WCON-FM	99.3
Gainesville	WDUN-FM	106.7
Griffin	WKEU-FM	97.7

La Grange WLAG-FM 104.1  
 Milledgeville WMVG-FM 102.3  
 Moultrie WMTM-FM 93.9  
 Rome WRGA-FM 102.3  
 Savannah WROM-FM 97.7  
 Valdosta WTOC-FM 94.1  
 WGOV-FM 92.9

**HAWAII**

Honolulu KAIM-FM 95.5  
 KPOI-FM 97.5

**IDAHO**

Boise KBOI-FM 97.9  
 Idaho Falls KID-FM 96.1  
 Lewiston KOZE-FM 96.7

**ILLINOIS**

Aurora WMRO-FM 107.9  
 Bloomington WJBC-FM 101.5  
 Champaign WLRW 94.5  
 Charleston WEIC-FM 92.1  
 Chicago WEFM 99.5  
 WFMT 98.7  
 WKFM 103.5  
 WLS-FM 94.7  
 WMAQ-FM 101.1  
 WSDM 97.9  
 WXRT 93.1  
 WTAS 102.3  
 Crete WSOY-FM 102.9  
 Decatur WMRY-FM 101.1  
 East St. Louis WXFH 105.9  
 Elmwood Park WJOL-FM 96.7  
 Joliet WLUV-FM 96.7  
 Loves Park WLBH-FM 96.9  
 Mattoon WMBD-FM 92.5  
 Peoria WBBA-FM 97.7  
 Pittsfield WGEM-FM 105.1  
 Quincy WTAD-FM 99.5  
 Rockford WROK-FM 97.5  
 Rock Island WHBF-FM 98.9  
 Springfield WFMB 104.5  
 WTAX-FM 103.7

**INDIANA**

Columbus WCSI-FM 101.5  
 Evansville WIKY-FM 104.1  
 Fort Wayne WKJG-FM 97.3  
 WPTH 95.1  
 Greenfield WSMJ 99.5  
 Hartford City WWHC 104.9  
 Indianapolis WFMS 95.5  
 WIFE-FM 107.9  
 Kendallville WAWK-FM 93.3  
 Kokomo WKMO 93.5  
 Lafayette WASK-FM 105.3  
 Marion WMRI-FM 106.9  
 Peru WARU-FM 98.3  
 Plainfield WJMK 98.3  
 Richmond WKBV-FM 101.3  
 South Bend WNDU-FM 92.9  
 WSBT-FM 101.5  
 Terre Haute WTHI-FM 99.9  
 WVTS 100.7  
 Vincennes WAOV-FM 96.7

**IOWA**

Ames WOI-FM 90.1  
 Cedar Rapids KHAK-FM 98.1  
 WMT-FM 104.5  
 Des Moines KDMI 97.3

Dubuque KWDM 93.3  
 Fort Dodge KDTH-FM 105.3  
 Fort Dodge KWMT-FM 94.5  
 Iowa City KXIC-FM 100.7  
 Sioux City KDVR 97.9  
 Waterloo KXEL-FM 105.7

**KANSAS**

Dodge City KGNO-FM 95.5  
 Emporia KVOE-FM 104.9  
 Kansas City KCJC 98.1  
 Lawrence KANU 91.5  
 KLWN-FM 105.9  
 Leavenworth KCLO-FM 98.9  
 Newton KJRG-FM 92.3  
 Scott City KFLA-FM 94.3  
 Wichita KCMB-FM 107.3  
 KQTY 101.3

**KENTUCKY**

Ashland WCMI-FM 93.7  
 Lexington WVLK-FM 92.9  
 Louisville WHAS-FM 97.5  
 Owensboro WSTO 96.1

**LOUISIANA**

Alexandria KALB-FM 96.9  
 Baton Rouge WJBO-FM 102.5  
 Oe Ridder KDLA-FM 101.7  
 Hammond WTGI 107.1  
 Houma KCIL-FM 107.1  
 Lafayette KPFL-FM 99.9  
 Lake Charles KPLC-FM 99.5  
 La Place WCKW 92.3  
 Monroe KMLB-FM 104.1  
 KNOE-FM 101.9  
 New Orleans WDSU-FM 93.3  
 WNNR-FM 97.1  
 WWMT 95.7  
 WWOM-FM 98.5  
 Opelousas KSLO-FM 107.1  
 Ruston KRUS-FM 107.1  
 Shreveport KBCL-FM 96.5  
 KWKH-FM 94.5  
 Thibodaux KTIB-FM 106.3

**MAINE**

Brunswick WCME-FM 98.9  
 Caribou WFST-FM 97.7

**MARYLAND**

Baltimore WAQE-FM 101.9  
 WBAL-FM 97.9  
 WFMM-FM 93.1  
 WITH-FM 104.3  
 Bethesda WHFS 102.3  
 WJMD 94.7  
 Cumberland WCUM-FM 102.9  
 Halfway WHAG-FM 96.7  
 Salisbury WBOC-FM 94.3  
 Takoma Park WGTS-FM 91.9

**MASSACHUSETTS**

Boston WBCN 104.1  
 WGBH-FM 89.7  
 WHDH-FM 94.5  
 Framingham WKOX-FM 105.7  
 Lynn WLYN-FM 101.7  
 North Adams WMNB-FM 100.1  
 Waltham WCRB-FM 102.5  
 Worcester WSRS 96.1

**MICHIGAN**

Bay City WBCN-FM 96.1  
 WNEM-FM 102.5  
 Detroit WABX 99.5  
 WBFG 98.7  
 WDET-FM 101.9  
 WDTM 106.7  
 WGPR 107.5  
 WJBK-FM 93.1  
 WLDM 95.5  
 WOMC 104.3  
 WXYZ-FM 101.1  
 East Lansing WSWM 99.1  
 WVIC-FM 94.9  
 Flint WGMZ 107.9  
 Grand Rapids WFUR-FM 102.9  
 WJFM 93.7  
 WOOD-FM 105.7  
 Holland WHTC-FM 96.1  
 Interlochen WIAA 88.3  
 Kalamazoo WSEO-FM 106.5  
 WMUK 102.1  
 Marquette WDMJ-FM 95.7  
 Midland WQDC 99.7  
 Mount Pleasant WCEN-FM 94.5  
 Saginaw WSAM-FM 98.1  
 Saline WOIA 102.9  
 Traverse City WLDR-FM 101.9  
 WTCM-FM 103.5

**MINNESOTA**

Anoka KTWN 107.9  
 Golden Valley KQRS-FM 92.5  
 Minneapolis-St. Paul KSTP-FM 94.5  
 KWFH 97.1  
 WAYL 93.7  
 WLOL-FM 99.5  
 WPBC-FM 101.3  
 Rochester KNXR 97.5  
 KROC-FM 106.9  
 St. Louis Park KRSI-FM 104.1  
 Willmar KWLM-FM 102.5

**MISSISSIPPI**

Biloxi WVMI-FM 106.3  
 Corinth WKCU-FM 94.3  
 Forest WQST 92.5  
 Greenwood WSWG 99.1  
 Gulfport WROA-FM 107.1  
 Hattiesburg WFOR-FM 103.7  
 Houston WCPC-FM 93.3  
 Jackson WWHO 94.7  
 Kosciusko WKOZ-FM 105.1  
 Laurel WNSL-FM 100.3  
 Natchez WNAT-FM 95.1  
 New Albany WNAU-FM 103.5  
 Pascagoula WPMP-FM 99.1

**MISSOURI**

Cape Girardeau KZYM-FM 102.9  
 Crestwood KSHE 94.7  
 Dexter KDEX-FM 107.3  
 Joplin KSYN 92.5  
 Kansas City KCMO-FM 94.9  
 KMBC-FM 99.7  
 St. Louis KCFM 93.7  
 Sedalia KSIS-FM 92.1  
 Springfield KTXR 101.5

**MONTANA**

Billings KURL-FM 97.1  
 Great Falls KOPR-FM 106.3

**NEBRASKA**

Columbus KJSK-FM 101.1  
 Lincoln KWHG 106.3  
 Omaha KOIL-FM 96.1  
 KOWH-FM 94.1

**NEVADA**

Las Vegas KORK-FM 97.1  
 KRGN 101.9  
 KVEG-FM 92.3  
 Reno KNEV 95.5  
 KSRN 104.5

**NEW HAMPSHIRE**

Mount Washington WMTW-FM 94.9  
 Nashua WOTW-FM 106.3

**NEW JERSEY**

Atlantic City WFPG-FM 96.9  
 Dover WDHA-FM 105.5  
 Long Branch WRLB 107.1  
 Paterson WPAT-FM 93.1  
 Princeton WPRB 103.3  
 Trenton WBUD-FM 101.5  
 WTOA 97.5

**NEW MEXICO**

Albuquerque KHFM 96.3  
 KRST 92.3  
 Hobbs KHOB-FM 95.7  
 Los Alamos KRSN-FM 98.5  
 Roswell KBIM-FM 94.9  
 Santa Fe KSNM 95.5  
 University Park KRWG 91.7

**NEW YORK**

Albany WHRL-FM 103.1  
 Babylon WGSM-FM 94.3  
 Binghamton WBNF-FM 98.1  
 Buffalo WADV 106.5  
 WDCX 99.5  
 De Pew WBLK-FM 93.7  
 Elmira WENY-FM 92.7  
 Garden City WLIR 92.7  
 Ithaca WVBR-FM 93.5  
 Jamestown WKSJ-FM 101.7  
 Lake Success WTFM 103.5  
 Middletown WALL-FM 92.7  
 Mount Kisco WRNW 107.1  
 New York WABC-FM 95.5  
 WCBS-FM 101.1  
 WKCR 89.9  
 WNBC-FM 97.1  
 WNEW-FM 102.7  
 WNYC-FM 93.9  
 WOR-FM 98.7  
 WPIX-FM 101.9  
 WQXR-FM 96.3  
 WRFM 105.1  
 Patchogue WPAC-FM 106.1  
 Plattsburgh WEAV-FM 99.9  
 Riverhead WHRF 103.9  
 Rochester WBBF-FM 92.5  
 WCMF 96.5

Schenectady WGFM 99.5  
 Syracuse WONO 107.9  
 WSYR-FM 94.5  
 Troy WFLY-FM 92.3  
 Utica WRUN-FM 104.3  
 WUFM 107.3

**NORTH****CAROLINA**

Black Mountain WMIT 106.9  
 Burlington WBBB-FM 101.1  
 Charlotte WBT-FM 107.9  
 WSOC-FM 103.7  
 Fayetteville WFNC-FM 98.1  
 Greensboro WMDE 98.7  
 WQMG 97.1  
 Greenville WNCT-FM 107.7  
 Hickory WHKY-FM 102.9  
 WIRC-FM 95.7  
 Jacksonville WXQR-FM 105.5  
 Leaksville WLOE-FM 94.5  
 Raleigh WPTF-FM 94.7  
 Reidsville WWMO 102.1  
 Statesville WFMX 105.7  
 Washington WITN-FM 93.3  
 Williamston WIAM-FM 103.7

**NORTH DAKOTA**

Fargo WDAY-FM 93.7  
 Grand Forks KVBC-FM 94.7

**OHIO**

Ashtabula WREO-FM 97.1  
 Cambridge WILE-FM 96.7  
 Canton WCNO 106.9  
 WHBC-FM 94.1  
 Cincinnati WAEF-FM 98.5  
 WCXL 105.1  
 WKRC-FM 101.9  
 Cleveland WCLV 95.5  
 WDOK 102.1  
 WHK-FM 100.7  
 WNOB 107.9  
 WZAK 93.1  
 Columbus WBNS-FM 97.1  
 Elyria WBEA 107.3  
 Fairfield WCNW-FM 94.9  
 Findlay WFIN-FM 100.5  
 Kettering WVUD-FM 99.9  
 Mansfield WVNO-FM 106.1  
 Medina WDBN 94.9  
 Middletown WPFB-FM 105.9  
 Port Clinton WRWR-FM 94.5  
 Portsmouth WNXT-FM 99.3  
 WPAY-FM 104.1  
 Salem WSOM-FM 105.1  
 Springfield WBLY-FM 102.9  
 Toledo WCWA-FM 104.7  
 WSPD-FM 101.5  
 Urbana WCOM-FM 101.7  
 Wooster WWST-FM 104.5  
 Youngstown WBBW-FM 93.3

**OKLAHOMA**

Lawton KLAJ 101.5  
 Midwest City KXLS-FM 92.5  
 Oklahoma City KFNB 101.9  
 KOCY-FM 96.1  
 KOFM 104.1  
 KYFM 98.9

Stillwater KOSU-FM 91.7  
 KSPI-FM 93.9  
 Tahlequah KTLQ-FM 101.7  
 Tulsa KOCW 97.5  
 KRAV 96.5

**OREGON**

Eugene KFMJ 97.9  
 KWFS-FM 96.1  
 Portland KOIN-FM 101.1  
 KPFM 97.1  
 KXL-FM 95.5

**PENNSYLVANIA**

Allentown WFMZ 100.7  
 Altoona WFBG-FM 98.1  
 Boyertown WBYO-FM 107.5  
 Braddock WLOA-FM 96.9  
 Chambersburg WCHA-FM 95.1  
 Ebensburg WEND-FM 99.1  
 Ephrata WCSA-FM 105.1  
 Erie WWYN-FM 99.9  
 Hanover WYCR 98.5  
 Harrisburg WTPA-FM 104.1  
 Johnstown WJAC-FM 95.5  
 Lancaster WGAL-FM 101.3  
 Lock Haven WBPZ-FM 92.1  
 Oil City WDJR 98.5  
 Philadelphia WDVR 101.1  
 WFIL-FM 102.1  
 WFLN-FM 95.7  
 WHAT-FM 96.5  
 WMMR-FM 93.3  
 WPBS 98.9  
 WPEN-FM 102.9  
 WQAL 106.1  
 KQV-FM 102.5  
 WKJF 93.7  
 WYDD-FM 104.7  
 Reading WRFY-FM 102.5  
 Red Lion WCCB-FM 96.1  
 Ridgway WKBI-FM 94.3  
 Scranton WWDL-FM 104.9  
 State College WMAJ-FM 103.1  
 WRSC-FM 96.7  
 Tyrone WGMR-FM 101.1  
 Warren WRRN 92.3  
 Wilkes-Barre WYZZ 92.9

**PUERTO RICO**

Aguadilla WABA-FM 100.3  
 Arecibo WNIK-FM 106.3  
 Mayaguez WKJB-FM 99.1  
 Ponce WLEO-FM 101.9  
 WPAB-FM 93.3  
 WFID 95.7  
 Rio Piedras WJAC-FM 102.5  
 San Juan

**RHODE ISLAND**

Providence WBRU 95.5  
 WCRQ 101.5  
 WHIM-FM 94.1

**SOUTH CAROLINA**

Beaufort WBEU-FM 98.7  
 Columbia WCOS-FM 97.9  
 Conway WLAT-FM 104.1

Florence WJMX-FM 103.1  
 Greenville WMUU-FM 94.5  
 North Charleston WKTM 102.5  
 Seneca WBFM 98.1  
 Spartanburg WSPA-FM 98.9

**SOUTH DAKOTA**

Sioux Falls KELO-FM 92.5

**TENNESSEE**

Brownsville WBHT-FM 95.3  
 Chattanooga WDEF-FM 92.3  
 WDDO-FM 96.5  
 Clinton WYSH-FM 104.9  
 Greeneville WOFM-FM 94.9  
 Humboldt WIRJ-FM 102.3  
 Kingsport WKPT-FM 98.5  
 Knoxville WEZK 97.5  
 Manchester WMSR-FM 99.7  
 McKenzie WKTA 106.9  
 Memphis KLYX 101.1  
 WMC-FM 99.7  
 Morristown WMTN-FM 95.9  
 Nashville WLAC-FM 105.9  
 WNFO-FM 103.3  
 WSIX-FM 97.9  
 Sevierville WSEV-FM 102.1  
 Tullahoma WJIG-FM 93.3

**TEXAS**

Abilene KWKC-FM 105.1  
 Amarillo KVII-FM 94.1  
 Austin KHFI-FM 98.3  
 KTBC-FM 93.7  
 Beaumont KTRM-FM 95.1  
 KLVI-FM 94.1  
 Big Spring KFNE 95.3  
 Brownwood KFRN-FM 99.3  
 Bryan KORA-FM 98.3  
 Clear Lake City KMSC 102.1  
 Dallas KBOX-FM 100.3  
 KIXL-FM 104.5  
 KRLO-FM 92.3  
 WRR-FM 101.1  
 El Paso KTSM-FM 99.9  
 Fort Worth KCUL-FM 93.9  
 KFJZ-FM 97.1  
 KXOL-FM 99.5  
 WBAP-FM 96.3  
 Gainesville KGAF-FM 94.5  
 Highland Park KVIL-FM 103.7  
 Houston KBNO 93.7  
 KFMK 97.9  
 KLEF 94.5  
 KODA-FM 99.1  
 KQUE 102.9  
 KRBE 104.1  
 KXYZ-FM 96.5  
 Longview KLUE-FM 105.7  
 Lubbock KBFM 96.3  
 KLBK-FM 94.5  
 KSEL-FM 93.7  
 McAllen KQXX-FM 98.5  
 Odessa KWMO 99.1  
 Port Arthur KFMP 93.3  
 San Angelo KWLW 93.9  
 San Antonio KEEZ 97.3  
 KITE-FM 104.5  
 KITY 92.9  
 KMFM 96.1  
 Sinton KTOO-FM 101.3  
 Texarkana KOSY-FM 102.5

Victoria KTXN-FM 92.1  
 Waco KEFC 95.5  
 Wichita Falls KNTO 95.1

**UTAH**

Ogden KBOC 101.9  
 Salt Lake City KLUB-FM 97.1  
 KSL-FM 100.3  
 KSOP-FM 104.3  
 KWHO-FM 93.3

**VIRGINIA**

Harrisonburg WSWA-FM 100.7  
 Lynchburg WWOOD-FM 100.1  
 Martinsville WMVA-FM 96.3  
 Newport News WGH-FM 97.3  
 Norfolk WTAR-FM 95.7  
 WYFI-FM 99.7  
 WSSV-FM 99.3  
 Petersburg WFMV 103.7  
 Roanoke WSLS-FM 99.1  
 South Hill WJWS-FM 105.5  
 Suffolk WXYW 92.9  
 Winchester WHPL-FM 102.5

**WASHINGTON**

Aberdeen KDUX-FM 104.7  
 Bellingham KERI 104.3  
 Bremerton KBRO-FM 106.9  
 Edmonds KGFN 105.3  
 Richland KCYS 95.1  
 Seattle KBBX 98.9  
 KETO-FM 101.5  
 KIRO-FM 100.7  
 KISW 99.9  
 KIXI-FM 95.7  
 KLSN 96.5  
 Spokane KDNC-FM 93.7  
 KHQ-FM 98.1  
 KTWD 105.7  
 Tacoma KLAY-FM 106.1

**WEST VIRGINIA**

Beckley WBKW 99.5  
 Bluefield WHIS-FM 104.5  
 Charleston WKNA 98.5  
 WVAF 99.9  
 Martinsburg WEPN-FM 97.5  
 Morgantown WAJR-FM 101.9  
 St. Albans WKLC-FM 105.1  
 Wheeling WTRF-FM 107.5

**WISCONSIN**

Delafield WHAD 90.7  
 Eau Claire WIAL-FM 94.1  
 Green Bay WBAY-FM 101.1  
 Janesville WCLO-FM 99.9  
 La Crosse WWLA-FM 93.3  
 Kenosha WAXO 96.9  
 WLIP-FM 95.1  
 Madison WHA-FM 88.7  
 WISM-FM 98.1  
 WMFM 104.1  
 WRVB-FM 102.5  
 Manitowoc WKUB-FM 92.1  
 Marshfield WDLB-FM 106.5  
 Milwaukee WAWA 102.1  
 WFMR 96.5  
 WISN-FM 97.3  
 WTMJ-FM 94.5

Oshkosh WOSH-FM 103.9  
 Platteville WSWW-FM 99.3  
 Sauk City WVLR 96.7  
 Tomah WTMB-FM 98.9  
 Two Rivers WTRW-FM 102.3  
 Waupaca WDX-FM 92.7  
 Wausau WSAU-FM 95.5  
 West Bend WBKV-FM 92.5

**WYOMING**

Cheyenne KVWO-FM 106.3

**CANADA**

**ALBERTA**

Calgary CHFM-FM 95.9  
 Edmonton CFRN-FM 100.3  
 Red Deer CKRD-FM 98.9

**BRITISH COLUMBIA**

Kamloops CFFM-FM 98.3  
 Penticton CKOK-FM 97.1  
 Vancouver CHQM-FM 103.5  
 CKLG-FM 99.3  
 CFMS-FM 98.5  
 Victoria

**MANITOBA**

Brandon CKX-FM 96.1  
 Winnipeg CJOB-FM 97.5  
 CKY-FM 92.1

**NEW BRUNSWICK**

St. John CFBC-FM 98.9

**ONTARIO**

Cobourg-Port Hope CHWC 103.1  
 Hamilton CHML-FM 95.3  
 Kingston CKWS-FM 96.3  
 London CFPL-FM 95.9  
 Ottawa CFMO 93.9  
 Port Arthur CKPR-FM 94.3  
 Sault Ste. Marie CJIC-FM 100.5  
 CKCY-FM 104.3  
 Sudbury CKSO-FM 92.7  
 Toronto CHFI-FM 98.1  
 CHUM-FM 104.5  
 CJRT-FM 91.1  
 CKFM 99.9  
 Windsor CKLW-FM 93.9


**QUEBEC**

Montreal CFCF-FM 92.5  
 CJFM-FM 95.9  
 CJMS-FM 94.3  
 CKGM-FM 97.7  
 Quebec CHRC-FM 98.1  
 Rimouski CJBR-FM 101.5  
 Ste. Anne de la Pocatiere CHGB-FM 102.9  
 Sherbrooke CHLT-FM 102.7  
 Verdun CKVL-FM 96.9

**SASKATCHEWAN**

Saskatoon CFMC-FM 103.9  
 CJUS-FM 89.7  
 END

# TWO INTERFERENCE NULLERS

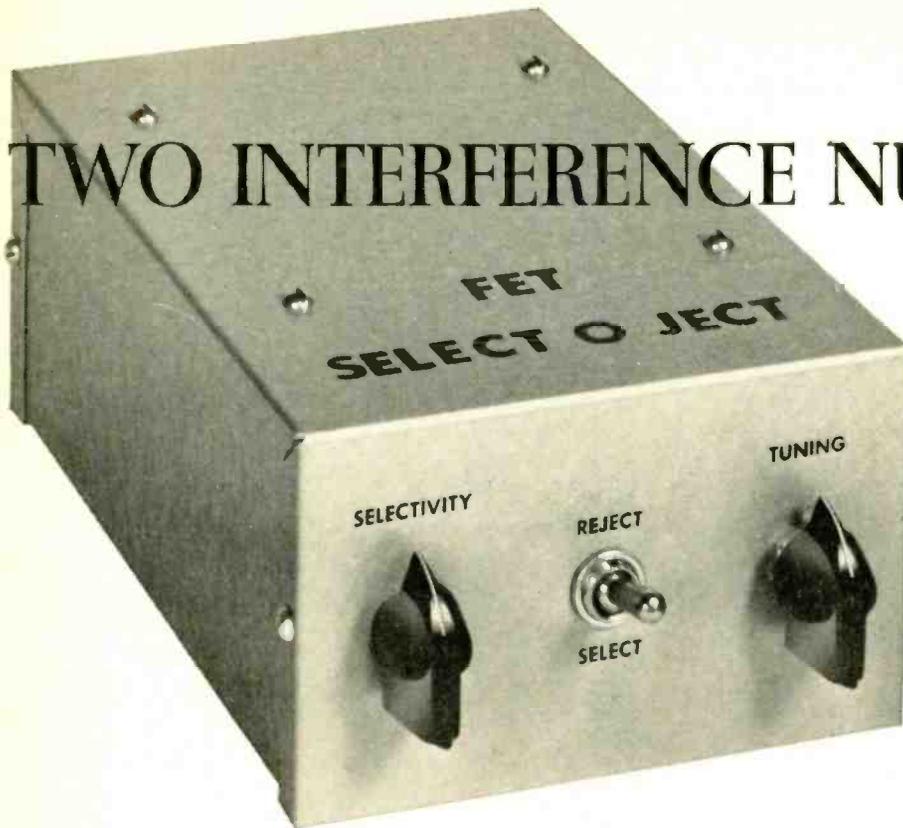

By JACK ALTHOUSE  
and OTIS VAN HOUTEN

IN COMMUNICATION RECEIVERS (CB, commercial two-way, SWL or amateur) heterodyne interference from undesired signals is a constant problem. Here is a pair of construction projects, both solid-state, and each with its own solution to the problem.

## Selectoject

Devised some years ago, this circuit was named for what it does: select, oscillate, or reject. It works in the audio section of the receiver, where it can (a) select a narrow band for amplification, rejecting all others, or (b) reject only a narrow slice of frequencies.

In the *select* mode, shown in Fig. 1, a selected frequency is boosted. The first phase shifter operates only at the desired frequency, while the third shifter (or inverter) works at all frequencies. Because of the feedback loop, the selected frequency is shifted  $360^\circ$  ( $180^\circ$  by each inverter) and added to the input. The combined signal at that frequency has a greater amplitude (adjusted by the *SELECTIVITY* control) than the original. Since all other frequencies are only shifted  $180^\circ$ , they tend to partially cancel out.

In the *reject* mode (shown in Fig. 2) the selected frequency is split into two channels. The second and third shifters give all frequencies a  $180^\circ$  shift, but the first inverter gives the selected frequency an additional  $180^\circ$ . When the two channels are combined, the selected frequency cancels out.

To make the circuit oscillate, it's only necessary to place it in the *select* mode and increase feedback until it equals the input. At this point the unit becomes a perfectly good audio oscillator for testing.

This Selectoject uses FET's, which are ideally suited for phase inverters. Not only are they made in both p- and n-channel types, they are high-impedance devices which will match most existing receiver circuits.

Fig. 3 is the schematic of the Selectoject. To maintain symmetry, you should use matched pairs for R1-R2 and R5-

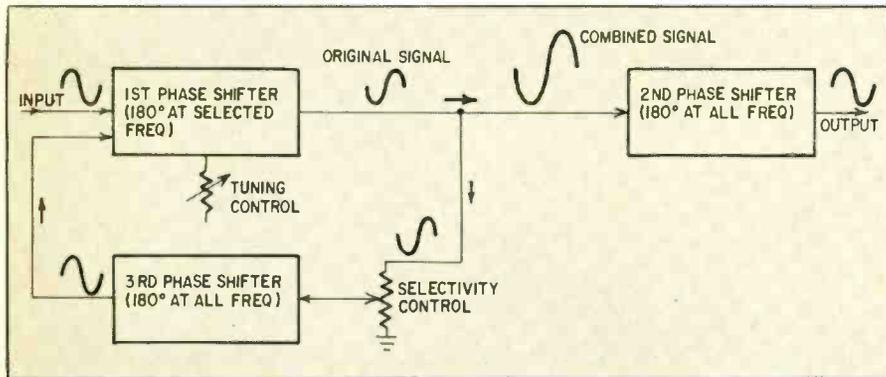


Fig. 1—When operating in the "select" mode, the Selectoject uses positive feedback to increase the amplitude of the desired narrow band of frequencies fed to the output.


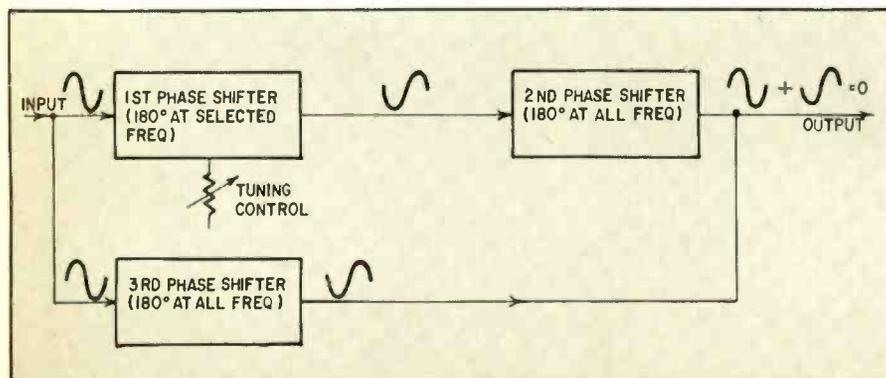


Fig. 2—The Selectoject can also reject a narrow frequency range. This is accomplished by inverting part of the signal so it cancels itself. Other frequencies are unaffected.

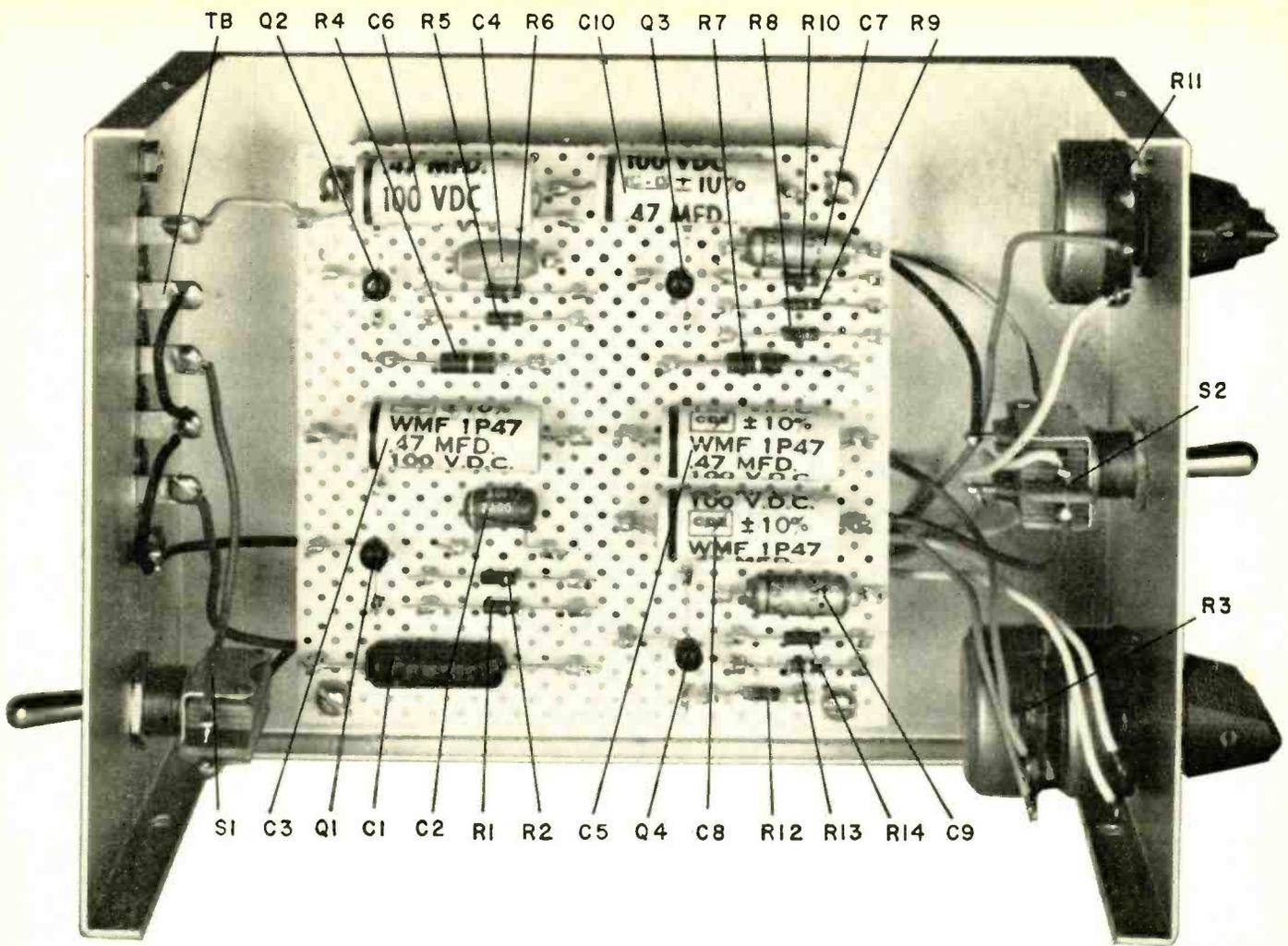

### Selectoject Parts List

- C1—.01  $\mu$ F, 200 volts
- C2, C4—.0022  $\mu$ F, 100 volts
- C3, C5, C6, C8, C10—0.47  $\mu$ F, 100 volts
- C7, C9—10  $\mu$ F, 10 volts, electrolytic
- Q1, Q2, Q3, Q4—2N4360 FET, Fairchild  
(send post card to Marketing Services, Fairchild Semiconductors, 313 Fairchild Drive, Mountain View, Calif., and request name and address of your nearest Fairchild stocking distributor)
- R1, R2—2,200 ohms (matched pair)
- R3—dual pot, 500K audio taper
- R4, R7—2.2 meg
- R5, R6—2,200 ohms (matched pair)
- R8—1,000 ohms
- R9, R13—220 ohms
- R10, R14—2,200 ohms
- R11—pot. 1 meg, audio taper
- R12—4,700 ohms
- All fixed resistors  $\frac{1}{4}$  watt
- S1—spst toggle switch
- S2—dpdt toggle switch
- Miscellaneous—5-terminal strip,  $4\frac{1}{2}$  x  $4\frac{1}{2}$ -in. perforated board, 7 x 5 x 3-in. metal box, terminals and spacers for board.

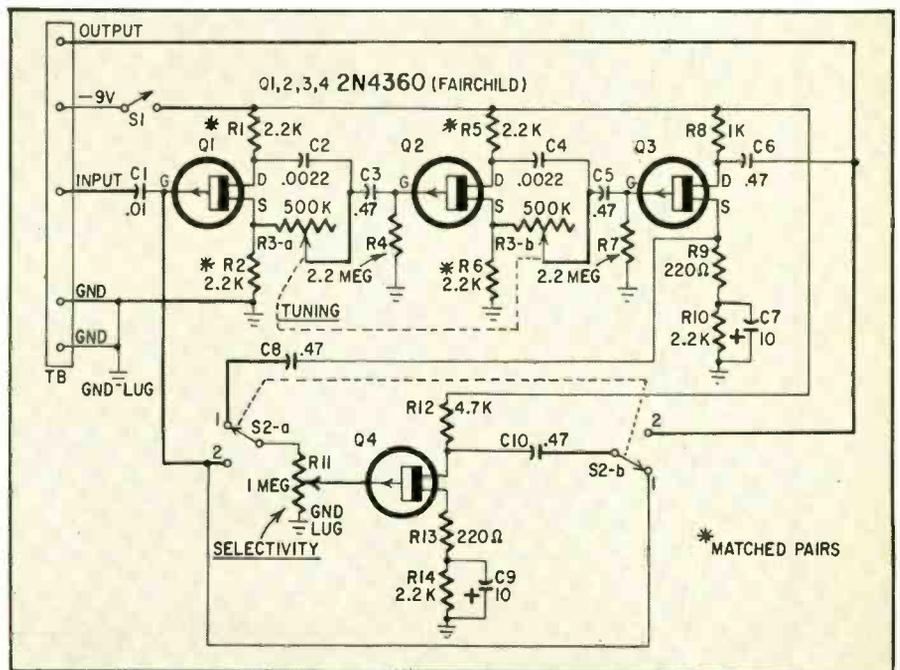


Fig. 3—FET Selectoject circuit is obviously much like the old vacuum-tube version. Heavy lines are those wires which join the perforated board to the case components.

R6. You can buy 1% resistors, or use an ohmmeter to select close pairs from a number of 2,200-ohm units.

The easiest way to build the Selectoject is to mount and wire the components on the  $4\frac{1}{2}$  x  $4\frac{1}{2}$ -inch perforated


board as shown in the photo above. But drill mounting holes both in the board and in the 7 x 5 x 3-inch box first. Wires from the board to the panel components are drawn in heavier lines in Fig. 3.

FET lead arrangement is shown in

Fig. 4-a, while 4-b shows how to bend the leads for board mounting.

The battery isn't shown in the schematic, for you may want to power your unit from an external source. There is room in the box, however, to mount a

## TWO INTERFERENCE NULLERS

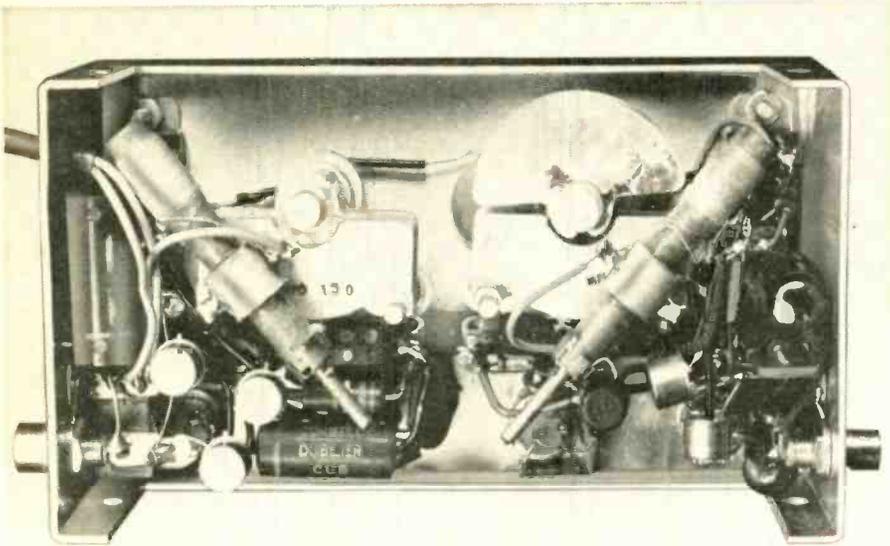

One author built two Q multipliers in a single case, to have double nulling capability.



Front view of the completed twin Q multiplier (Peak or Nuller) receiver accessory.

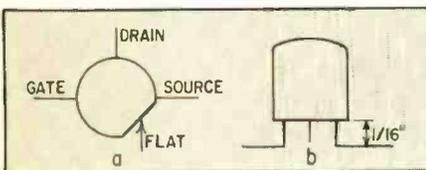


Fig. 4-a—You'll find the FET lead coding easy to make out, but there's one thing you won't believe. It makes no difference if drain and source leads are interchanged! b—To facilitate mounting on the perforated board, bend FET leads like this.

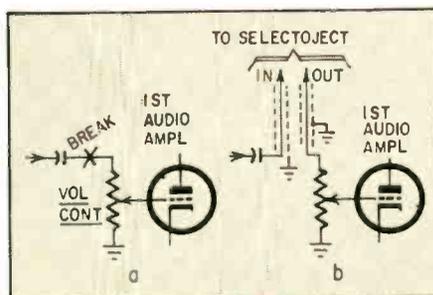


Fig. 5—Follow these steps to connect Selectoject to audio section of receiver.

9-volt transistor battery. As the Selectoject draws only about 4 mA, a zinc-carbon type (NEDA 1604) should last about 48 hours. A mercury battery (NEDA 1604M) will be good for two or three times that.

This device is made to work into a high-impedance receiver audio section, and should be connected as shown in Fig. 5.

In practice, you'll find it easiest to reject a single heterodyne with the TUNING control. SELECTIVITY controls the amount of null or boost. If an interfering signal produces a fundamental and harmonics, you'll probably get best results in the *select* mode, tuning for best signal-to-noise ratio.

### Q multiplier

Another way of getting rid of heterodyne interference in a receiver is by varying the Q of the i.f. circuit. For instance, the Colpitts oscillator of Fig. 6, when connected in a receiver i.f. stage, will vary the selectivity depending on the position of R3.

With R3 set for zero resistance, maximum positive feedback occurs and the circuit oscillates at a frequency determined by L, C1, C2 and C5. Under this condition, the Q of the LC tank is almost infinite, producing high gain around the selected frequency. The effect in the receiver is the same as rejecting all other frequencies. By adding a third transistor, the circuit can null out a narrow frequency range.

The frequency of the *peak* or *null* can be varied over a 25-kHz range centered on 455 kHz. *Peak* bandwidth is adjustable from 1 to 20 kHz, while *null* bandwidth can be widened to eliminate most typical voice signals. The entire circuit can, depending on control settings, provide voltage gains from 5 to 10.

Refer to Fig. 7 for circuit function. The input is isolated from the receiver by R1, and the output is similarly isolated by its connection to the feedback-stage (Q2) emitter. This makes cable connections to the receiver uncritical.

In the *peak* mode, the i.f. input signal is applied to a voltage divider consisting of R1 in series with the parallel combination of R2, the input impedance of Q1, and the resonant impedance of the tank. At the tank's resonant frequency ( $f_r$ ) the input impedance of Q1 is high due to the bootstrap feedback connection through R3. But at frequencies other than  $f_r$ , circuit impedance is much less, as is developed voltage.

Emitter follower Q2 isolates the input and output stages, and the output is taken from the collector circuit of Q3.

In the *null* mode, the signal from output amplifier Q3 is fed back to the input tank. This negative feedback

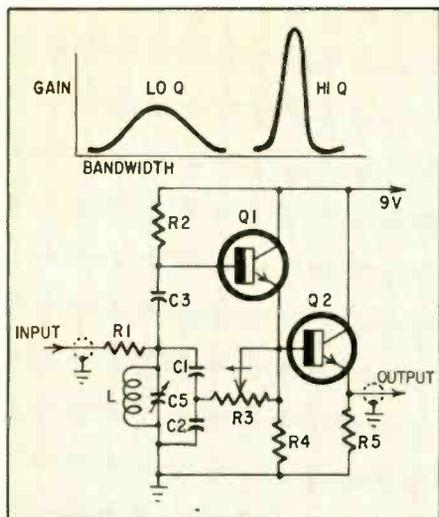


Fig. 6—A Colpitts oscillator can be used as a Q multiplier in a receiver i.f. stage.

causes gain to be very low at  $f_r$ , producing a notch (or null) in the i.f. response curve.

Construction requirements aren't critical, with two exceptions: R2 and R8, nominally 270 K, should be chosen to drop half the supply voltage to the respective bases of Q1 and Q3. The transistors may be npn's like the 2N388, 2N365A or 2N1304. Specifications should be at least the following:  $f_{th}$  5+ MHz,  $E_{ce}$  20+ volts,  $P_c$  100+ mW,  $h_{fe}$  100+.

As shown in the photo, you can build the Q multiplier with point-to-point wiring in a small box. (The model shown is actually two separate Q multipliers in series, which permits more effective deheterodyning.) Or you may prefer a perforated board. Be sure the tank circuit components are rigidly mounted in a box with tight corners, for proper shielding.

Signal connections are shown in Fig. 8. Remove the agc connection to the i.f. transformer, and ground the bottom of the winding. Then add a 470K resistor from the last i.f. grid to the agc line just disconnected. Use shielded cable to connect the Q multiplier to the *in* and *out* points shown in Fig. 8.

If you wish, you may use a 9-volt battery to power the system (as mentioned above). To avoid the nuisance of changing batteries, you can alternatively steal the approximately 20 mA needed (for the twin version) from the receiver audio output stage, as illustrated in Fig. 9. Dc cathode voltage should be in the range of 8-13. The effective power-circuit resistance of the twin Q multiplier is about 450 ohms, so you can substitute the circuit for an existing output-stage cathode resistor in the range of 400-500 ohms. If your receiver uses

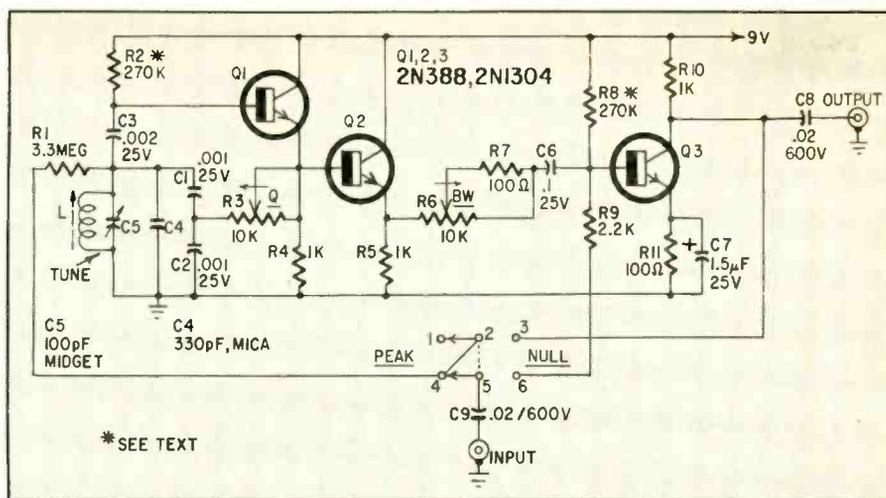


Fig. 7—Complete schematic of the solid-state Q multiplier. For greater flexibility in interference rejection, you may want to build two and put them in series. You'll then be able to cut through much hash by nulling out two signals, and copy cleaner signals.

#### Q Multiplier Parts List

- C1, C2—.001  $\mu$ F, 25 volts
- C3—.002  $\mu$ F, 25 volts
- C4—330 pF, mica
- C5—100 pF, midget variable
- C6—0.1  $\mu$ F, 25 volts
- C7—1.5  $\mu$ F, 25 volts, electrolytic
- C8, C9—.02  $\mu$ F, 600 volts
- L—40 to 300  $\mu$ H variable (J. W. Miller 2002, or equivalent)

Q1, Q2, Q3—2N1304 (see text) or equivalent

- R1—3.3 meg
- R2, R8—270K (see text)
- R3, R6—pot. 10K linear taper
- R4, R5, R10—1,000 ohms
- R7, R11—100 ohms
- R9—2.200 ohms

All fixed resistors  $\frac{1}{2}$  watt

Miscellaneous—input and output phono jacks, aluminum case, tie strips, shielded cable.

another value, you'll have to shunt it with an added resistor to equalize the load. Be sure to use a cathode bypass electrolytic of about 50 to 100  $\mu$ F at 25 volts—add one if not already present.

To align the circuit, apply a 455-kHz signal to the input jack. With C5 (the TUNE control) in the middle of its range and the switch set to PEAK, adjust L for maximum output. Be sure the Q and BW controls are at midrotation, with Q set just below oscillation point.

In operation, the TUNE control adjusts the position or frequency of the peak or null. The bandwidth control sharpens or broadens, and the Q control adjusts the height or depth of the peak or null. For initial adjustment, tune in a signal on the receiver with the switch in the NULL position and the TUNE control detuned. Turn the bandwidth control to maximum clockwise position and rotate the Q control until you hear a squeal in the speaker—indicating oscillation. Now turn the Q control counterclockwise until oscillation just stops. The Q control is now properly adjusted.

So there you are—take your choice, get out that soldering tool, and start your way toward slicing out interference!

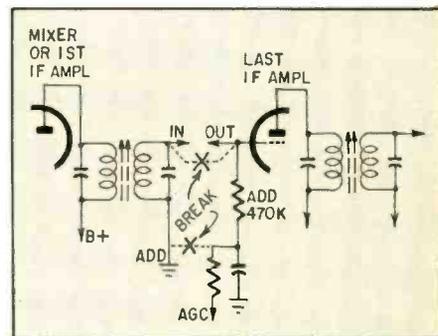


Fig. 8—Q multiplier connection to receiver.

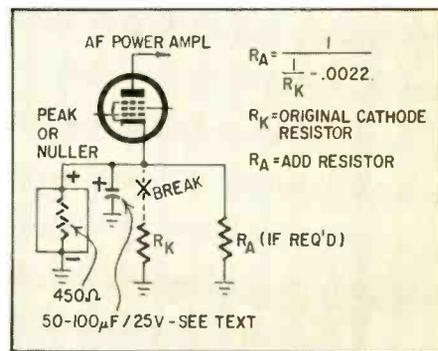


Fig. 9—How to steal power for the Q mult.

# IN'S AND OUT'S OF LEAD-INS

They're only pieces of wire, but they carry that all-important signal

By EDWARD A. LACY

AN ANTENNA FARM ON THE OUTSIDE of your vine-covered cottage may result in a jungle of lead-in wires inside its walls. For whether you have TV, ham, SWL, Citizens-band or FM antennas (some poor souls have all of these!) the antenna lead-in presents a problem: How do you get the thing into the house neatly, efficiently and safely?

Some would say, "Just drill a hole in the wall and pull it through." Many installations plainly follow this direct approach.


Unfortunately, this simple method usually looks atrocious (especially if you are living in rented quarters). It's inconvenient to disconnect or service, and it may be unsafe according to the National Electrical Code.

There are simple, straightforward procedures to fit most lead-in problems, however, plus new hardware to make the job easier. By following a few simple fundamentals, you can please your wife, get the best possible signal in and out of the house, and not electrocute your children and pets in the process.


Let's follow your lead-in from the antenna to your equipment. We'll assume that you have made good mechanical and electrical connections at the antenna, there is no mechanical strain on the connections, and all connections have been made as weatherproof as possible. Weatherproof coax connectors by covering with silicone grease and all other connections by wrapping well with plastic tape or covering with a weatherboot.

If you have mast-mounted equipment—preamplifiers or matching transformers, for example—make sure you leave a drip loop (a U-shaped piece of the lead-in) to keep rain from running into your equipment. If you have an antenna rotator, leave enough slack in the lead-in to permit rotation. Extra slack also may be useful should you want to bring the antenna down to your level when disconnecting the lead-in. Don't forget to ground the mast and fit an efficient lightning arrester to the lead.

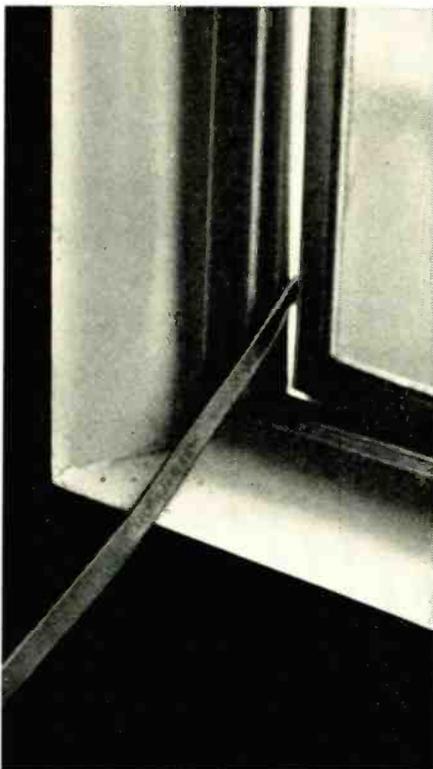We won't get into the controversy of coax vs twin-lead for TV here, ex-



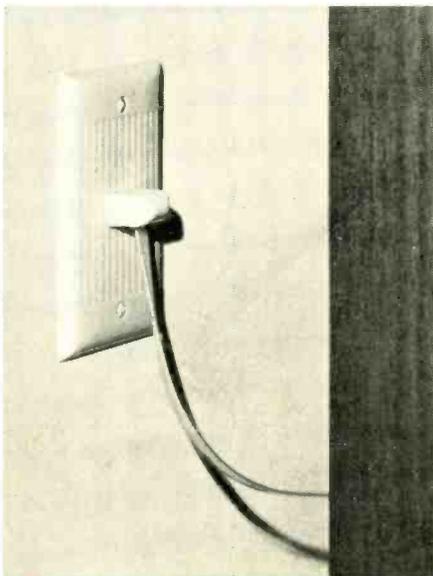*How not to route lead-in; the insulator wears through and the screen won't fit.*



*To move the TV and clean the rug, you simply unplug the lead-in at the wall box.*

cept to say that coax is not nearly so critical to install, especially for color TV. If you *do* use coax for TV, get all-channel cable so you will be set up for uhf, regardless of whether you now have high-channel stations on the air in your area.

No matter what type of lead-in you use, *do not* run it above or below power lines. Mount and restrict the lead-in so it can swing no closer than 10 feet to wires carrying more than 250 volts; no closer than 2 feet to wires carrying less than 250 volts. If no more than 150 volts are involved, you can run the lead-in within 4 inches of the power line, provided all lines are mounted securely to preserve the minimum permanent separation.

With coax or shielded twin-lead, you can tape it to the mast about every 6 feet with plastic tape. This will keep it from blowing in the breeze and eventually breaking because of vibration. With oval or all-weather twin-lead (no more flat twin-lead, please!), use plastic clips or all-polyethylene-head standoff insulators every 6 feet down the mast and across the roof of your quarters. Note that suitable types of twin-lead are too rigid to be twisted as was required for flat line.

For transmitting antennas, if coax is not used, mount the lead-in at least 3 inches away from the outer wall of the building, using nonabsorptive insulated supports.

When bringing the lead-in into the house, you can run it directly through or alongside metal pipes *if you use coax or shielded twin-lead*. Unshielded twin-lead, of course, must avoid such pipes if possible.

The only precautions necessary with coax: Don't crush it; don't pierce the insulation with staples, etc. Use hand-driven staples instead of a staple gun to avoid indenting the shield. Shielded twin-lead requires similar care.

Now, where should you bring the lead-in into the house? New hardware allows you to bring it in practically any place—the roof, eaves, window or window board, basement or foundation wall, even directly through the outer

wall to the point where the lead-in will be used. Which method is best?

If one or more of your antenna outlets is to be mounted directly on an outside wall of your house, then it will probably be easier to bring the antenna directly through the wall using either a coax or twin-lead wall-through connector. You can, however, come up through the basement or crawl space and drill up through the floor for outside-wall outlets.

For all inside-wall outlets, come through the attic (by way of the eaves, ventilator or roof), through the basement (by way of a basement window or wall), or through the crawl space under the house (by way of a ventilator or the foundation wall) and then up (or down) the wall as needed. Don't plan on snaking a lead-in *down* an outside wall; insulation and braces make it too difficult a task.

Of these methods, the basement route is certainly the most convenient (unless you have a finished ceiling in the basement). You won't have to snake the lead-in down from the ceiling. For homes without a basement, the crawl space has the same advantage, too, if you care to brush aside the spiders and other denizens of the dusty, dark hole.

If none of these methods works, you can, as a last resort, bring the lead-in through a window pane or window board near your gear. This technique, however, is unsightly and it hampers or prevents normal opening and closing of that window. For transmitting antennas: If your lead-in consists of bare wire, you should bring it into the house at a point where a human cannot touch it. Rf burns are *dangerous and painful*.

Once you have determined the point of entry for your lead-in, bring it close to that point and form a drip loop. If you're using TV twin-lead, *do not* leave a full coil at this point (or any other point); it's murder for color!

Strap the lead-in securely to the outside of the house so there will be no mechanical strain on the feedthrough connector.

Mount the lightning arrester close by, attach the antenna to it, and connect the appropriate ground wire. Arresters are not required for coax, if the outer shield is permanently and effectively grounded with an efficient grounding clamp. Note, however, that coax lightning arresters *are* made for Citizens-band and ham antennas. To protect shielded twin-lead from lightning, connect as shown in Fig. 1.

At this point, it's necessary to decide where to place the multi-set coupler if you have or anticipate having more than one TV. If one of your outlets is mounted on an outside wall, mount the coupler in a weatherproof box on the outside of the house. If the outlets are to be mounted on inside walls, or if you come up to an outside-wall outlet through the basement or crawl space, then you can place the coupler conveniently inside the house.

When installing coax, it is not necessary to use a bushing or feedthrough insulator to go through the wall, window or ventilation opening. If you wish, you can use a standard coax wall-through insulator (Fig. 2) which has a

coax receptacle on the inside end. Twin-lead should be brought in through a feedthrough bushing or insulator (GC Electronics 1551 or Mosley 625 or equivalent, available with receptacle socket).

If you're not using coax for your transmitter, bring the lead-in through a drilled window pane or a rigid non-absorptive noncombustible insulating tube.

Once you have picked the feedthrough insulator, you can determine the size of hole you will need to drill.

To drill through masonry foundations, use extra-length carbide-tip drills. For wood foundations, use standard 18-inch electrician's drills. Both types are large enough to drill holes for coax, but the masonry bit is not large enough for bushings or feedthrough insulators.

To make masonry holes for bushings, start the hole with a carbide-tip bit, using a slow-speed drill if possible, and finish it with a regular star drill bit—a steel rod with a star-shaped point. Hold the star bit in one hand and strike a sharp blow with a hammer or mallet. Rotate the bit slightly after each blow. Since this is a hard, time-consuming job, try to go through a mortar joint, brick or cinder block instead of concrete, which is extremely difficult to drill through.

If possible, drill the hole so it slants down slightly toward the outside so rain won't run through the bushing into the house.

Instead of a star drill, you may use a large electric drill. Make certain the drill is grounded with a three-conductor wire and plug, since you'll probably be outdoors when using it.

After inserting the feedthrough (Fig. 2) or coax, make the hole water- and weather-proof by putting it with a material such as General Electric's bathroom seal or ordinary caulking compound.

#### CAUTION

**Do not drill into a wall or roof if you suspect there is an electric power line somewhere underneath. Several electricians, who should have known better, have been electrocuted this way.**

**Use protective goggles and work gloves when drilling or chipping masonry.**

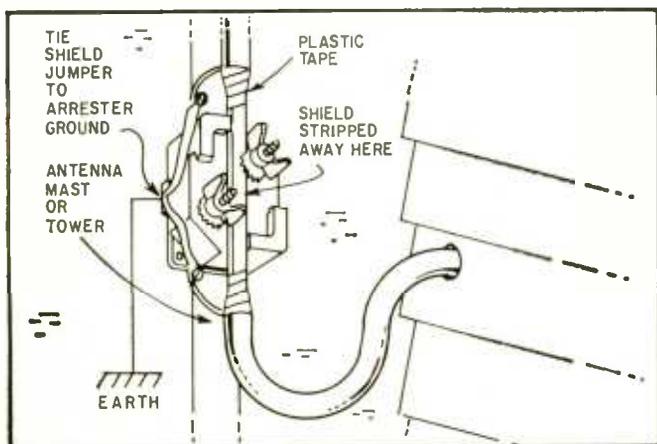


Fig. 1—Before routing cable or twin-lead inside a building, be sure to use some form of lightning arrester. Ground it well.

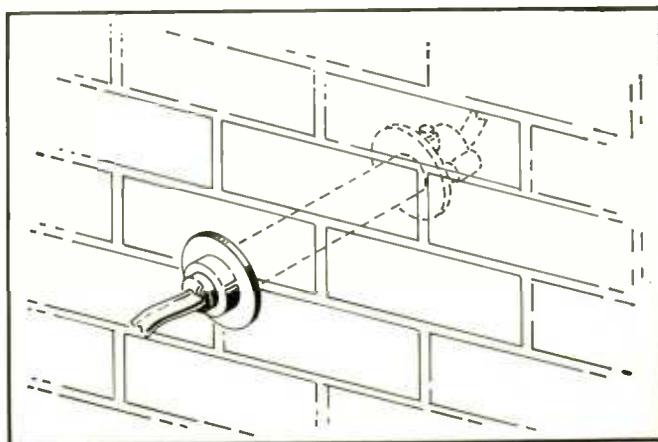


Fig. 2—You'll find that a wall feedthrough insulator is needed with twin-lead to protect and secure the body of the lead-in.

## IN'S AND OUT'S OF LEAD-INS

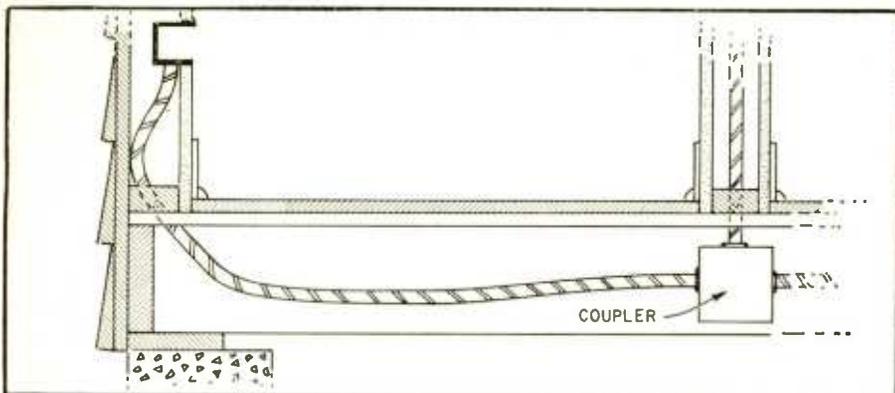


Fig. 3—Often you can make a neat job by routing cable between basement rafters (in other words, just below ground-floor level). Outlet boxes for the cable go in walls.

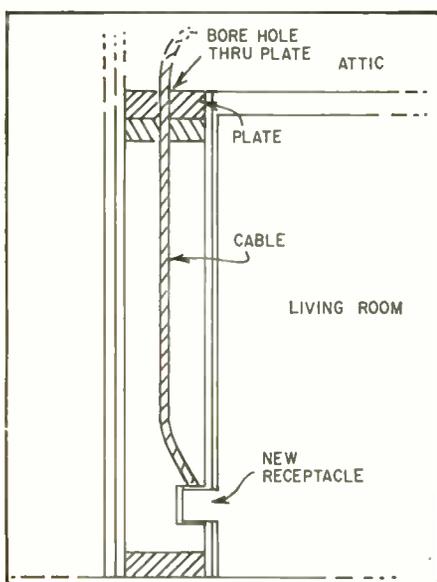


Fig. 4—Another way of running lead-in to a wall box is down through the attic.

To insert the lead-in through a feedthrough or a hole, *do not* strip the end of the lead-in until you have pushed it through.

Inside the house, mount any traps, filters, mixers, splitters, couplers, etc. you may have for TV or FM in a place convenient for adjustment and servicing, but not exposed to an undue amount of dust and moisture.

In running the lead-in to the outlets, remember: Do not run lead-in nearer than 2 inches to power conductors, unless the power conductors are in cable armor or unless they are permanently separated by a continuous and firmly fixed nonconductor such as flexible tubing or porcelain tubes.

Staple coax and shielded twin-lead on the inside of the house, using the same precautions as you did on the outside of the house. Standoff insulators are not necessary indoors; twin-lead can be held in place with plastic clips. Try to

avoid long runs of unshielded twin-lead, and keep it away from plumbing pipes and metal-backed lath.

When using shielded twin-lead, maintain shield continuity by splicing a jumper across the cable shields when you encounter boosters, couplers, outlets, etc. It's easier to make these connections when you install the cable than to go back later to do it.

If you are running the lead-in underneath the floor, run it directly beneath the new outlet opening (Fig. 3) and drill a hole up through the subfloor and through the 2 by 4 plate on top of it. CAUTION: Be careful not to drill into a power line.

If you are running lead-in through the attic, carrying it directly to the point over the wall in which the outlet is to be mounted, then drill down through the ceiling plate (Fig. 4). If your outlet is next to a closet, it may be simpler to come down through the closet ceiling in a corner of the closet where the lead-in will not be obtrusive.

Now, come back up to the main floor and cut a hole in the wall large enough to mount plaster straps or mounting brackets. Mount the brackets. Attach the lead-in to the outlet plate, then attach the plate to the brackets.

As indicated in Fig. 5, there are several manufacturers who are now making 300-ohm and coax outlets as well as coax or twin-lead in combination with rotor outlets. *Avoid those outlets that combine ac power outlets with antenna outlets.* Most, if not all of these, do not conform to the National Electrical Code.

What should you do when you need outlets on two floors? You *can* bring a lead-in all the way from the attic through an inside wall down to the bottom floor, but it's a tricky business: You must remove the baseboard on the second floor and drill from the second floor toward the wall of the floor beneath. It's easier to run the second lead-in down the outside (or up the outside, depending on where your coupler is located) of the house.

Note that there are two types of antenna outlets: surface mounted and flush mounted. The flush-mounted type allows you to hide your wiring; of course, the surface-mounted type is easier to install.

If you are using coax for TV reception, you can use either a coax outlet or an outlet which has a 75- to 300-ohm matching transformer built in. If you are in a very strong signal area, unwanted TV signals can be received by the short length of lead-in that runs from the TV to the wall outlet. In such cases, use the coax outlet and mount the matching transformer on the back of the set.

END

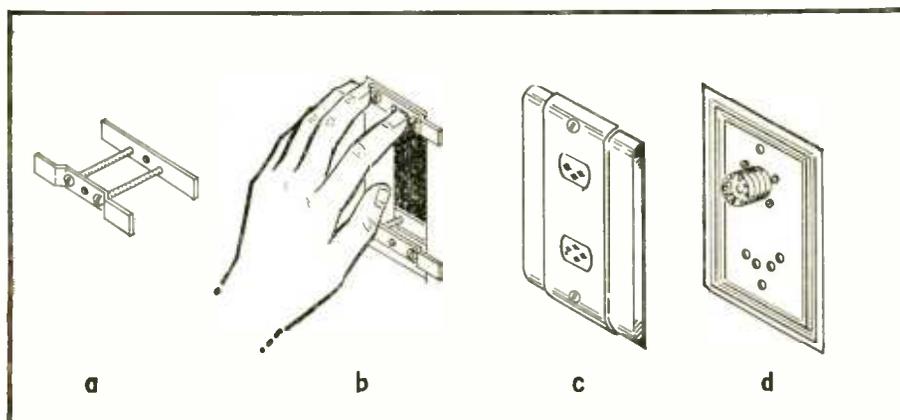


Fig. 5—How to install cable and twin-lead receptacles. Cut hole in wall, then use plaster straps (a) at top and bottom of hole (b). Receptacle panels attach to straps and are available in either twinlead (c) or coax (d) types. Some have antenna-rotator jacks.

# Canada's First Satellite Station

By JAMES W. ESSEX

WITH THE DECISION OF CANADA'S Department of Transport (equivalent to the US's FCC) to build a satellite receiving station, the northland country is assured participation in the fast-growing chain of international communication satellites. A signatory to the International Agreement covering ownership and use of the system, Intelsat Canada has a 3½% ownership in the corporation which owns and operates satellites Early Bird, Lani Bird and Canary Bird. This percentage may be small, but it is significant as it places Canada fifth on the list of participating nations.

It's also worth noting that this northern neighbor of the US boasts one of three commercial satellite-receiving stations in North America, complementing the US stations at Andover, Me., and Brewster Flat, Wash.

The site selected for the station is on Canada's thinly populated eastern coast, not far from Halifax, Nova Scotia. Rising high above rocky terrain, the huge Dacron balloon which covers the antenna looms like a giant "puffball." Over 100 feet high, it's an impressive sight. Air pressure from five compressors maintains the form of the dome. The interior is completely unobstructed.

The town (Mill Village), near which the station was placed, is located about 85 miles southwest of the port city of Halifax. The site was chosen to provide a near-ideal proximity to Europe and Early Bird. The location also

is remote from large built-up areas to minimize electrical interference. Adequate housing is available in the immediate vicinity, as are suitable power-line facilities.

In spite of the fact that signals from a synchronous satellite like Early Bird are virtually line-of-sight, the high frequency (4,000 to 6,000 MHz) and low power (3 watts) require an antenna having truly impressive gain and directional characteristics. The cost of this installation (\$9 million Canadian) attests to the financial and physical difficulties involved in providing such an antenna. Maneuverability—needed to accommodate the network of satellites that one day will circle the earth—also adds to the cost. Canada plans to be part of this world-wide network of orbiting satellites.

The Canadian parabolic dish can be constantly checked for precision by focusing it on a "man-made ground satellite." This signal source is actually a miniature version of the real one and is mounted on a steel tower 7 miles from the dish. When triggered by the giant antenna, signals are emitted in much the same manner as from the real satellite. With the exact range and bearing of the ground satellite known, the use of a boresight telescope allows operators to align the antenna visually by peering through an opening in the Dacron balloon covering.

High-gain parametric amplifiers having extremely high signal-to-noise ratios amplify the incoming signals. These sensitive circuits operate in a


closed-cycle liquid-helium environment within 4.5° of absolute zero, a practice which minimizes random electron noise within the amplifiers. The low-level (-100 dB) signals are then converted to a 70-MHz intermediate frequency using a superheterodyne mixer. The 70-MHz signals are fed to the control room where they are further amplified.

The antenna is used both for transmitting and receiving. A duplexer system is used for switching. Two modes of transmission are possible—SSB and FM—using two 10-kW transmitters operating in the range of 5,925–6,425 MHz. Other equipment associated with the antenna, including the transmitters, is housed within the dome.

A combination administration/control building is located 1,000 feet distant. Interconnecting electrical cables are housed in an above-ground tunnel that runs out to the antenna. After processing, signals from the site are fed into a microwave network with terminals in Montreal and Andover, Me. Remote control of the antenna also is possible from this building.


Operation of the station is the responsibility of the Canadian Overseas Telecommunications Corp. (COTC). About 40 persons, staff and scientists, are required to maintain its role in the international network. From the beginning, the station has been "commercial." Its future applications depend, not only on the proper assessment of present uses, but what is yet to be learned from satellite communication practices.


END

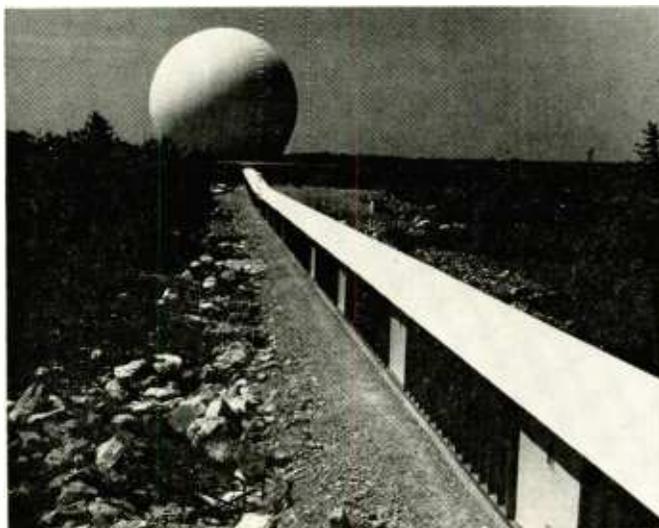



The satellite tracking antenna is housed inside the distant radome made of Dacron. The "bubble" is over 100 feet high.

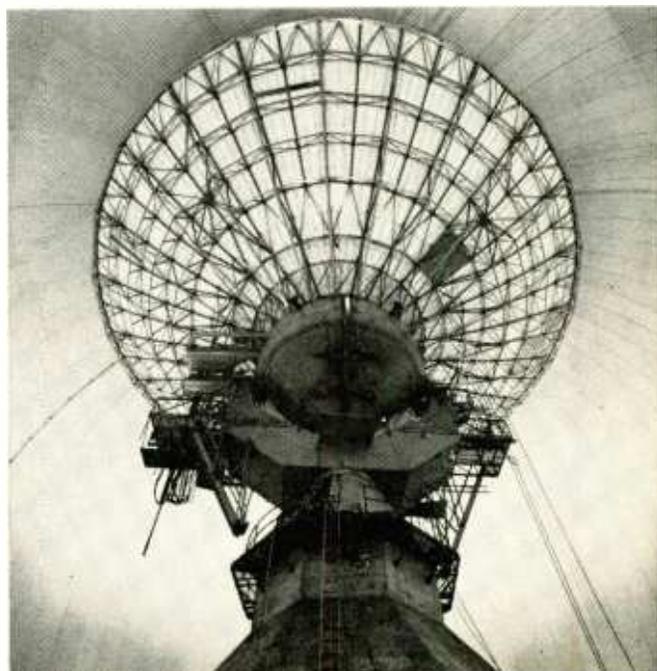Inside the radome stands the giant parabolic antenna. Note the size of the access ladder near the base of the antenna.



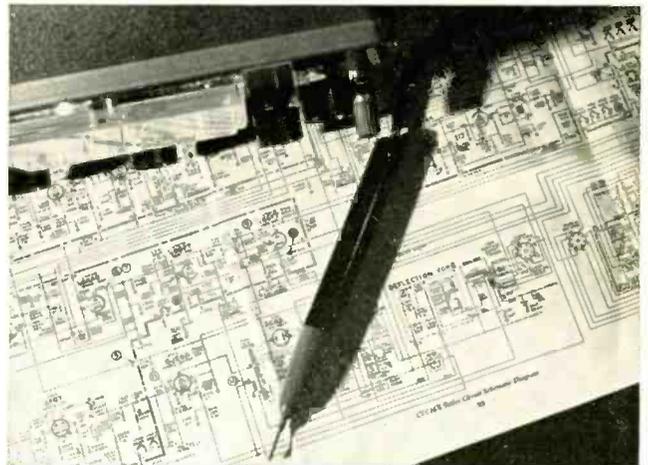

**Whatever your electronics interest,**

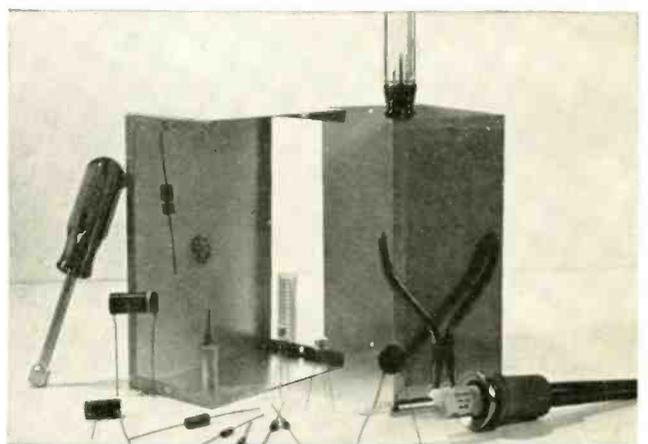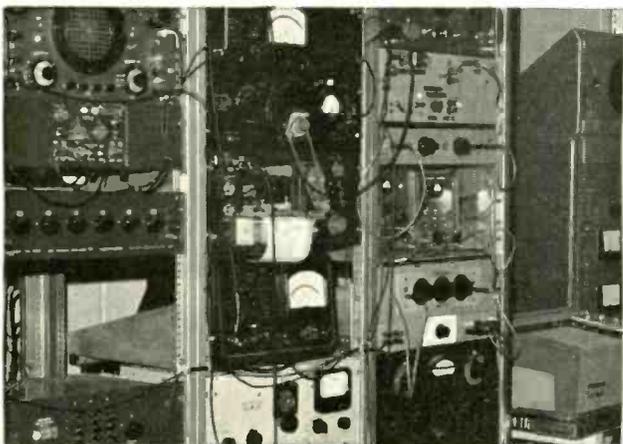

**here are 12 powerful reasons why you should subscribe to RADIO-ELECTRONICS.**

(besides the \$9.60 you can save over newsstand prices)

In 1966 more than 160,000 readers interested in every area of electronics learned from and profited by: January's Annual Color TV issue  ..... February, which highlighted practical construction projects  ..... March, a Hi-Fi/Stereo/Tape issue  ..... April, a career series feature  ..... May, which contained a line-up of home video recorders and their workings.  ..... June, an annual issue on microcircuits and transistors  ..... July's special section on Stereo FM  ..... August's Test Equipment issue, which delved into do-it-yourself instrumentation  ..... September, with CB and communications content for "two-wayers"  ..... October, full of the news in industrial electronics  ..... November, which turned out to be a music issue featuring guitar amps, etc.  ..... December, which featured electronic auto servicing  ..... and its pros and cons. **You get all this ...** plus monthly features like Jack Darr's Service Clinic ... reports on test equipment and audio components ... new products ... technotes ... new literature and books and more.

# Radio-Electronics



# Electronic Antenna Rotation

By RAY D. THROWER, WA6PZR

IN HAM-BAND, CB AND TWO-WAY COMMUNICATION, a fixed antenna has one disadvantage—it can't be turned. This means it's nondirectional and unless most of your communication is in one direction you pick up undesired signals along with the desired ones. The answer to this problem, of course, is a beam, so you can null out interfering stations and get more gain in the desired direction (or directions).

Unfortunately, most low-frequency beams (80 or 160 meters) are large, expensive, and often objectionable to neighbors. Even at higher frequencies, beams are subject to mechanical problems, being exposed to the weather as they are.

Rather than physically turning the antenna, why not do the same thing electrically? Broadcast and commercial two-way stations have been doing this for years. Recently even some TV receiving and CB antennas have appeared using the same principle. The system is called a *directional array*, and consists of two or more vertical radiators or elements. Spacing and phasing of the two radiators are adjusted so that the rf fields add in some compass headings (thus producing greater signal) and cancel in others (thus producing lesser signal).

## Basic DA operation

Fig. 1 shows three directional patterns you can obtain using two vertical radiators, a couple of hundred feet of transmission line, and some switches. Suppose you put up a tower or pole insulated from ground and used it as an antenna. The dashed-line circles in Fig. 1 show the pattern you'd get—a perfect nondirectional circle. Now suppose you put up another tower (you could actually use a flagpole or a telephone pole, and hang an insulated long wire off the side, just as long as the radiator is vertical). Space the second radiator 90 electrical degrees, or a quarter wavelength, away from the first.

First tie the transmitter to the first tower (let's call it X). Now tie the second (Y) in parallel, *but* insert enough additional line to delay the rf by 90 electrical degrees. The pattern you get is shown in Fig. 1-a, a cardioid with a sharp null in one direction and a large lobe in the opposite. Reverse the phasing and you will reverse the pattern, as in Fig. 1-b.

Add another 90° phase delay in the line to Y, or a total delay of 180°, and

you'll have the pattern of Fig. 1-c, a bidirectional figure 8, with two sharp nulls at right angles to the lobes.

These are the three basic patterns that will be most useful in nulling out undesired stations and copying desired ones.

## Antennas and ground system


There are steel or aluminum towers used for fringe-area TV reception which are reasonably priced and will do nicely as vertical radiators for low frequencies. For base insulators, you can buy ceramic cup types that electric power companies use on high-voltage line towers. You'll have to guy the towers, and break the guys with porcelain strain or egg insulators.

Alternatively, you can put up telephone poles or flagpoles and hang an insulated wire off the side as a radiator.

The two radiators should be equal in height. How high they are depends on

how much money and guy space is available. Fig. 2 shows vertical-radiation patterns for four vertical radiators of four different heights, separately. At (a) a 270° tower has a great deal of high-angle radiation and only moderate ground-wave propagation. The 225° or  $\frac{5}{8}$ -wave antenna at (b) has the theoretical maximum groundwave efficiency (good chiefly for local work, or long-hop DX), with only small lobes at skywave angles. The half-wave antenna of (c) has very little high-angle radiation and still a great deal of low-angle. Finally, the 90° or quarter-wave radiator of (d) is a fair compromise between high- and low-angle propagation.

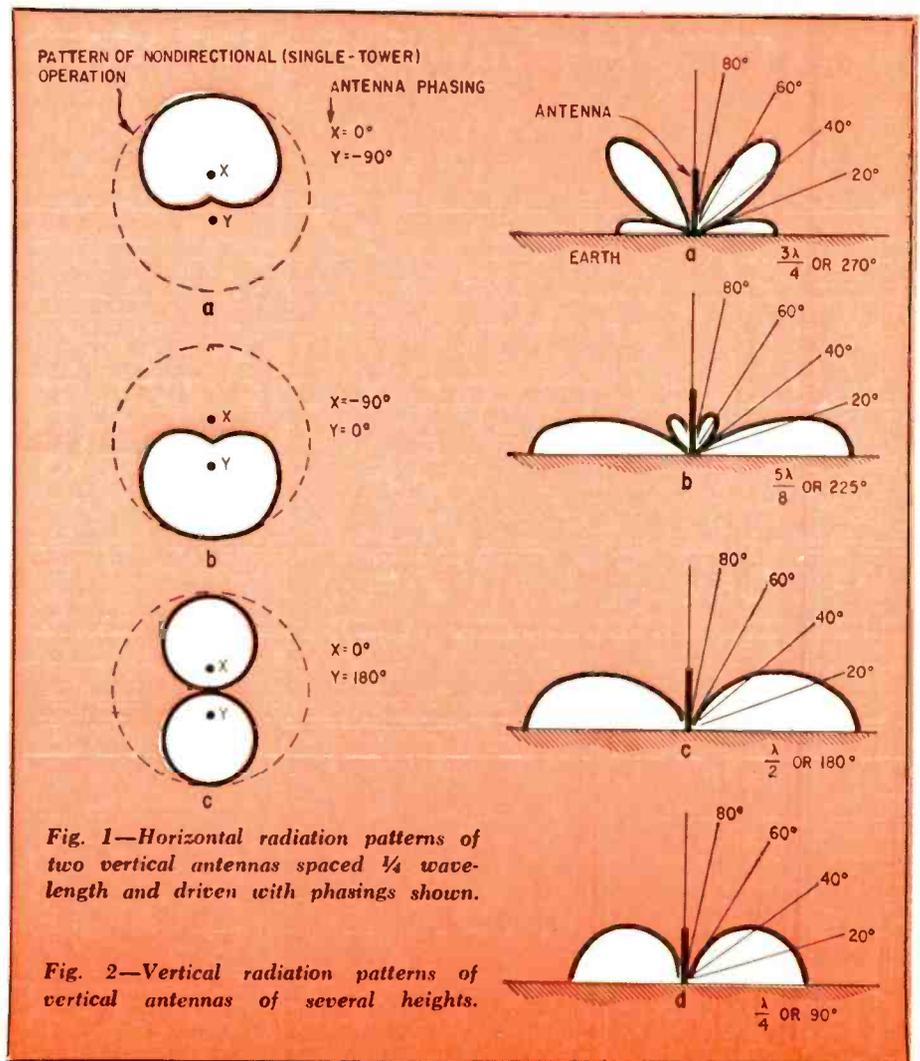Since the shorter towers cost less, the quarter-wave is probably the best bet, and you may decide to make do with even less. Don't try anything less than a 45° or eighth-wave height, however; it will be so inefficient your time and money will be wasted. Such short



# Electronic Antenna Rotation

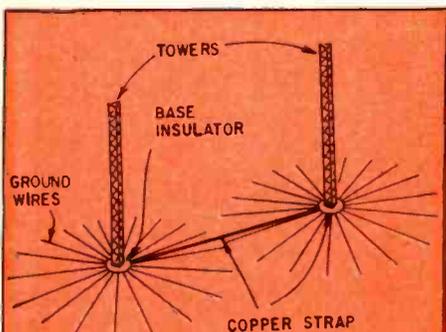


Fig. 3—A fairly good ground system.

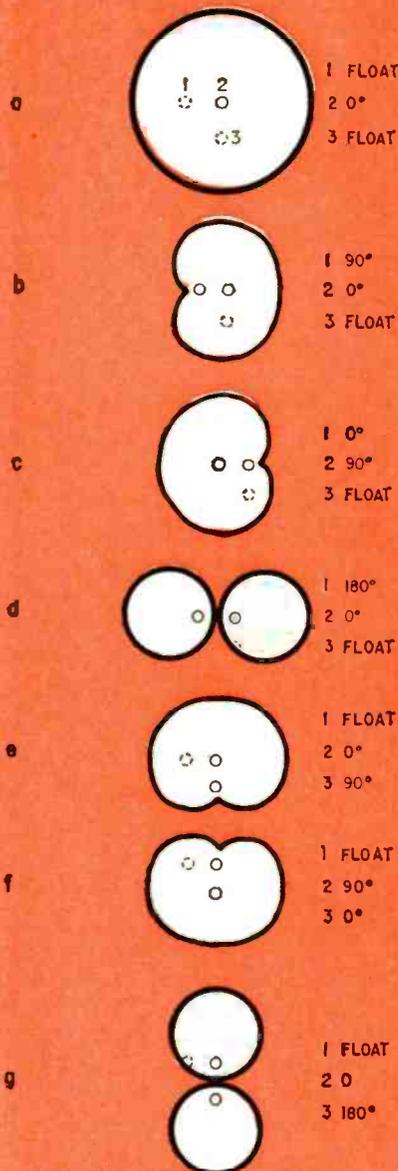


Fig. 4—By using 3 towers in an L-shaped array, you get these 7 patterns.

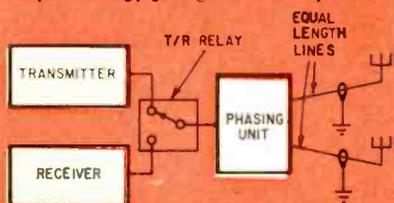


Fig. 5—How to connect phasing unit.

antennas have low radiation resistances and ground-system losses take most of the rf power. They also have lots of reactance and are difficult to match to transmitters.

The towers should be spaced 90 electrical degrees apart (a quarter wavelength). This is the best compromise between two undesirable extremes. Greater than 90° spacing produces a pattern with an increasing number of lobes and nulls. Closer than 90° spacing produces high mutual impedance between towers, which lowers radiation resistance and requires more rf driving current. Up go the losses and down goes the system efficiency.

If you don't plan to put a good ground system in, then don't bother to put up the radiators at all. As I said before, you'll be wasting time and money. The radiation resistance of an antenna is what the rf works into. But in a vertical radiator the ground system is the electrical return—the other half of the circuit—so the ground-system resistance is in series with the radiation resistance of the antenna.

A vertical radiator 54° (0.15 wavelength) in height has a radiation resistance of about 10 ohms. In Fig. 3 radial wires are laid in the ground extending outward from the base of each tower. Considering just one tower for a moment, if there are 120 radials each a quarter wavelength long, ground resistance will be about 1 ohm. Total system resistance is 11 ohms. If a 100-watt transmitter is connected, the ground system will take about 9 watts, leaving 91 watts for the antenna to radiate into space.

Suppose the ground system consists of merely a piece of pipe driven into the ground at the base of the antenna. Ground resistance would be about 50 ohms, for a total of 60 ohms. Assuming the same 100-watt transmitter, the ground-system loss would be 83 watts, leaving only 17 watts for the antenna.

If you can't afford to put a lot of copper into the ground, it's better to put shorter rather than fewer radials. Try for at least 15 or 20 equally spaced radials. Since you have few, they don't have to be so long—only about an eighth wave. Making them longer will have almost no effect.

As Fig. 3 illustrates, bond the radials to a ring of copper strap around the base of each tower. Connect the shield of the transmission line to the ring. Use a section of strap between the towers to tie the wire ends where they overlap. Use another strap to connect the two base rings together. Radial wires may be buried a few inches in soil (not deeper, though) or left on the surface if there's no pedestrian traffic.

Your operating frequency will determine the height of the antennas. For 160-meter (1.9-kHz) use, you'll probably want to use eighth-wave towers, about 65 feet high, since a quarter wavelength is 130 feet, and that kind of steel runs into money. Here are quarter wavelengths for other bands:

Band in meters	Freq. in MHz	Approx. $\frac{\lambda}{4}$ in ft
80	3.9	63
40	7.1	35
20	14.1	17
CB	27.0	9
10	29.0	8
6	50.0	5

Specify the center of the frequencies you operate on and use the following formula to determine *exact* antenna height and spacing:

$$\frac{\lambda}{4} \text{ (ft)} = \frac{246}{f \text{ (MHz)}}$$

At the higher frequencies—say from 27 MHz on up—it becomes quite simple to erect poles or tubular masts. Also, you can even use ground-plane antennas on a roof, but their operation will vary from those described here. This article concerns *only* vertical radiators with bases on the earth itself.

## Choosing patterns


Decide how many and what patterns you want, for this will determine how many towers you must erect. With two radiators, you'll be able to get four useful patterns (more are available, but hardly worth the trouble). Three are shown in Fig. 1. The fourth (not shown) is nondirectional, obtained by driving only a single tower.

If you erect two radiators in a north-south line, signal lobes will be also north-south. How to get east-west lobes? Simple—put up a third radiator, making an L-shaped array, again using 90° spacing. By driving only two towers at a time you can shift patterns. Fig. 4 shows how.
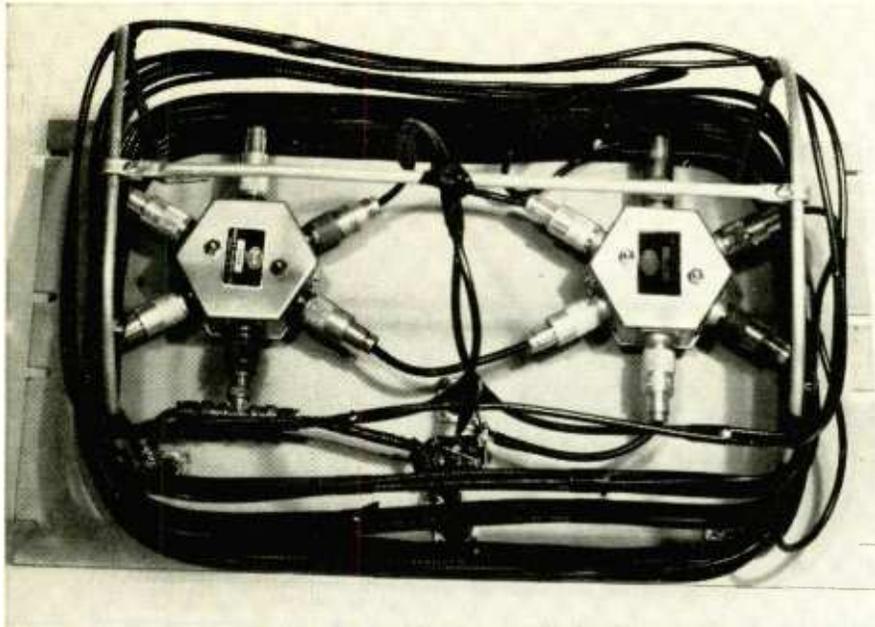
## The phasing unit

As Fig. 5 shows, the system for introducing phase delay is placed between the transmit-receive relay and the towers. The transmission lines from the phasing unit to the towers must be exactly equal in length, so no unwanted phase shift is introduced.

Circuit connections are shown in Fig. 6. All switches are coaxial. S1 and S2 must be switched separately by hand and must always be in equal positions. As shown, S2 allows tower 2 to float, while S3 connects tower 1 to the direct line from the transmitter, for nondirec-



While this isn't the unit described in the text, it shows switch and cable placement.

tional operation.

When S1-S2 are in position B, the first 90° delay line is put in series with the transmitter output and tower 2. This produces pattern C of Fig. 4. With S1-S2 in position C, both 90° sections of line are put in series with tower 2, producing pattern D of Fig. 4. S3 is used to reverse the cardioid pattern C to B.

S4 is optional but necessary if a third tower is used. Tower 2 becomes the

center radiator, while towers 1 and 3 are alternately floated by S4, thus changing pattern orientation from east-west to north-south.

Components specified in the parts list will operate up to 1 kW and 100 MHz. Below about 150 watts and 5 MHz, you can save money by using RG-58/U and noncoaxial switches.

After you've decided the operating frequency, compute the 90° length, with

the wavelength mentioned earlier. As an example, for 3.9 MHz, 90° is 63 feet. Multiply this figure by the propagation constant of the coax you're using. This constant is found in many engineering handbooks and also in cable manufacturers' catalogs. For RG-8/U and RG-58/U the constant is 0.66. Thus  $63 \times 0.66$  is 41.6, or about 41½ feet.

The photo shows a slightly different system, but illustrates parts placement on the back of the cabinet front panel. Bolt a frame of tubing to the panel as a cable support. After you've cut the lines and attached connectors, form the cable into loops around the support frame and tape or lace them in position. Be sure to leave enough slack at the ends to reach switches and connectors. Don't force the coax into sharp bends or you'll change impedance and create a hot spot for arcover, as well as increase standing-wave ratio.

It's a good idea to place S1, S2 and S3 as close together as possible, so the coax between them can be very short. This prevents adding undesirable phase shift between radiators.

### Tuning the system

Simply float tower 2, and load tower 1 to match your transmitter output as you normally would. Then reverse the procedure. One big advantage to using quarter-wave radiators is that reactance is practically zero. Radiation resistance of such a tower will be about 35 ohms. This is not a bad match to 50-ohm cable, since the ground resistance will be in series, and will probably be 5 to 25 ohms. When both towers are being driven in parallel the total resistance will be half that of each. This means when switching from non-D (nondirectional) to DA (directional array) operation you'll have to retune the transmitter output. Of course, if you never use non-D the resistance will remain constant. Even in the three-tower array no more than two towers are used at a time. You can, of course, add compensation—a dummy load resistor to be switched in place of the floated tower. This cuts radiated power in half, though.

Don't forget to use a lightning arrester at the base of each tower. Commercial models are available at parts houses. They are inserted into the feedline at the antenna base.

It's not a good idea to switch patterns while the transmitter's on the air, for you can cause voltage surges across switches that may damage them or the coax. Kill the high voltage when switching. In the receive mode you'll do no damage by switching. In fact, the system patterns are just as valid for receiving, and that's where you'll find the real value of this array. When you reverse a null, away goes an interfering signal! Have fun with your directional system. END


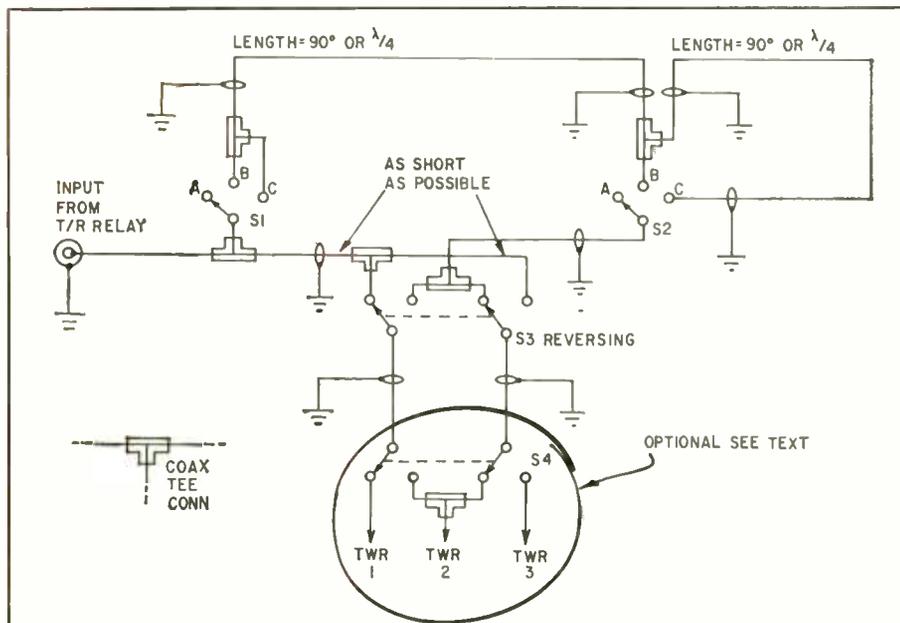


Fig. 6—Interconnections inside phasing unit. All wiring must be coaxial cable.

- |  |   |  |
|--|---|--|
| <b>Parts List</b>  | (Dow-Key DK78-T, or equivalent)                                   | 3—coax receptacles, uhf type, SO-239 (Amphenol 83-1R, or equivalent) |
| S1, S2—coaxial switch, sp3t, with uhf-type connections (Dow-Key DK78-3, or equivalent) | 6—tee connectors, uhf type, M-358 (Amphenol 83-1T, or equivalent) | RG-8/U coaxial cable, as needed                                      |
| S3 (and S4, if used)—coaxial switch, dpdt, with uhf-type connections                   | 27—coax plugs, uhf type, PL-259 (Amphenol 83-1SP, or equivalent)  | Panel and cabinet to fit cable lengths                               |

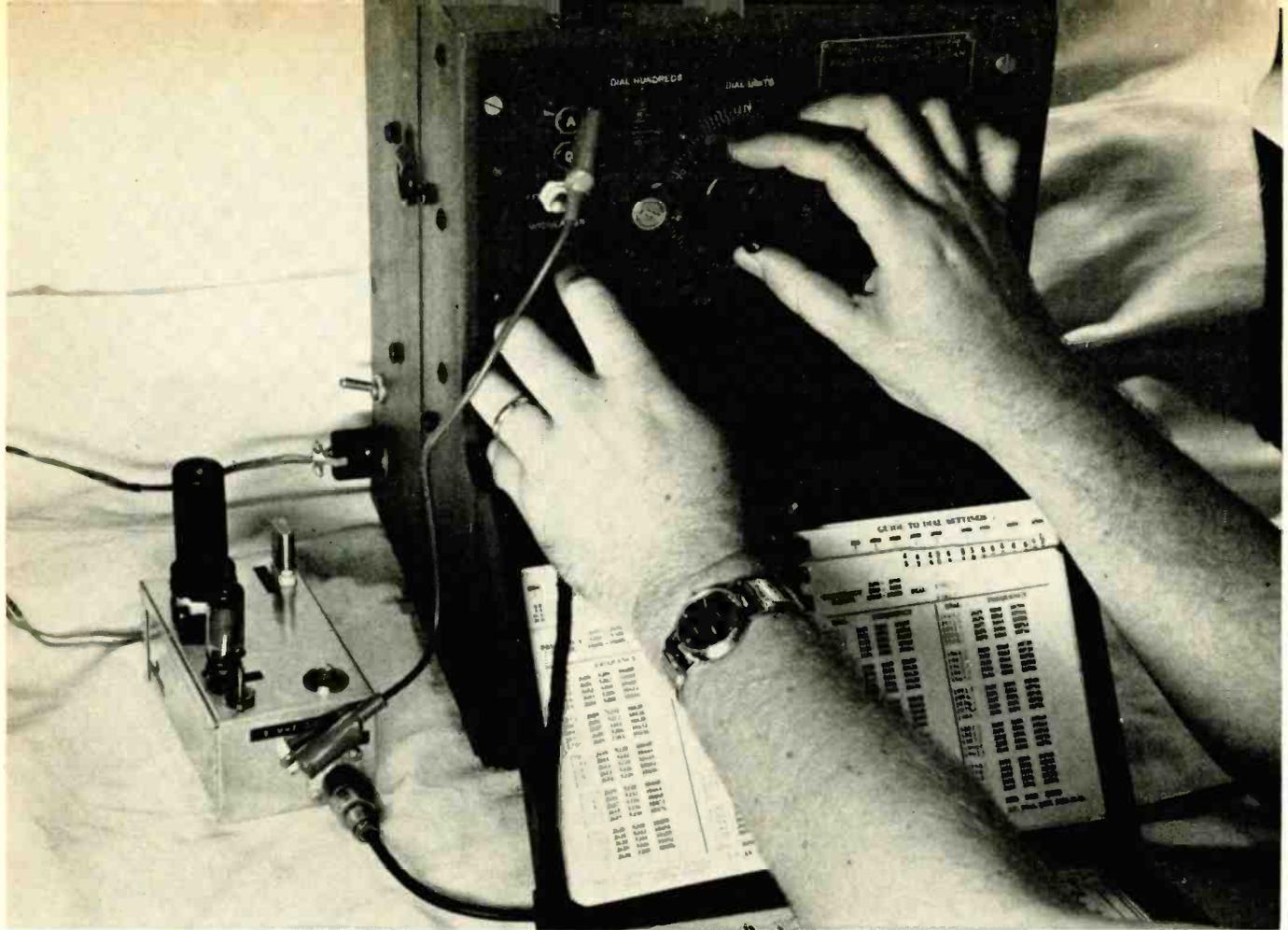

# Check CB Frequencies With BC-221 and a Converter

By RON GUNN

WITH THE CONVERTER AND THE INFORMATION in this article, you can measure Class-D Citizens-band frequencies on a surplus BC221 or LM frequency meter to an accuracy of .0015% or better, a maximum of 400 Hz. Other hf and vhf frequencies can be read off at the same 400-Hz accuracy with this technique. A little experimentation will demonstrate the actual limits over which you can have confidence in the readings. The trick is an easily built and inexpensive crystal-controlled converter, a principle used in the best receivers and frequency-measuring equipment. We'll also talk about the modification and use of the meter for maximum accuracy.

Nothing is more discouraging than having to turn down a job because you don't have the necessary equipment. Many technicians own a BC221 or LM, but dependable measurement of Class-D frequencies is not possible on the bare BC221. Its accuracy of .02% is four times the allowable 1,350-Hz limit on the band. That .02% is only 400 Hz at 2

MHz, though. The frequency converter you can build from this article accurately heterodynes the 27-MHz output of the Class-D transmitter to about 2 MHz so that you can get 400-Hz accuracy.

## The converter

The converter consists of two parts (Fig. 1): a crystal-controlled oscillator and a pentagrid mixer. The fundamental frequency of the crystal oscillator is 5 MHz. This fundamental or its harmonics are beat against WWV at 5, 10, 15 or 20 MHz for calibration. A small trimmer is wired across the crystal so you can zero-beat the oscillator.

The plate circuit of the electron-coupled oscillator is set to the fifth harmonic of the basic frequency, or 25 MHz. The extreme stability of this oscillator under use is due to the very loose coupling to the mixer (5 pF), the fact that the plate circuit is tuned to a high harmonic, and the added isolation obtained by using an electron-coupled circuit.

A pentagrid mixer gives additional isolation between the transmitter signal to be measured and the standard oscillator. Any pulling of the oscillator would affect the frequency reading and must be avoided. In this circuit, keying the transmitter on and off does not change the oscillator-WWV beat by even 1 Hz.

A dummy load is included to take the transmitter output. A lamp is used to observe transmitter output during the frequency check. A sample of the signal is taken off through a 5-pF capacitor and goes to the pentagrid mixer.

The difference between the 25-MHz standard input and the 27-MHz transmitter signal is developed across the 2-MHz broadband tuned circuit in the mixer plate and is coupled through a high-voltage capacitor to the output feedthrough. A high-voltage capacitor is used to reduce the possibility of the mixer B+ getting to the user's hand! A clip lead goes to the BC221 input.

Using a 6AG7 for the oscillator seems somewhat like using a steam roller to squash a bug, but it is a dependable and sensitive oscillator. Very loose coupling can be used because only a small percentage of its power is required. Its high gain reduces crystal current, so

drift in the oscillator frequency is minimized. Reasonable substitutes would be the 5763 or 12BY7.

### Converter construction

The converter in the photos was built in a 5¼ x 3 x 2½-inch Minibox. There was plenty of room. Construction took a couple of hours and alignment, after a half-hour warmup, took but a few minutes.

Layout is not particularly critical, but don't mount the crystal too close to the 6AG7. Locate the crystal padder so it can be adjusted easily. The output circuit at 25 MHz must also be tunable while the converter is operating, though it will have to be set only once. Leads from connector J to the dummy load should be short to minimize radiation.

### Frequency meter


A well-calibrated BC221 or equivalent is the heart of this frequency-measuring setup. Be sure yours is in good shape before depending on it. A reasonable guideline is to allow less than one corrector division between check points. Even then, auxiliary checkpoints will have to be used, as explained further on.

Make sure that the coupling capacitor to the audio-amplifier grid is 0.22 µF or larger, as in Fig. 2-a. Many of them aren't. Parallel a 0.22-µF 200-volt paper capacitor with the existing one anyhow; it won't hurt and you do want to hear those low beat notes. Next, rewire the cathode of the audio amplifier as Fig. 2-a or 2-b. Now you will hear low beat notes.

Put in a three-conductor Jones plug as a power takeoff from the power supply to the converter. Include an spst switch in the B+ lead.
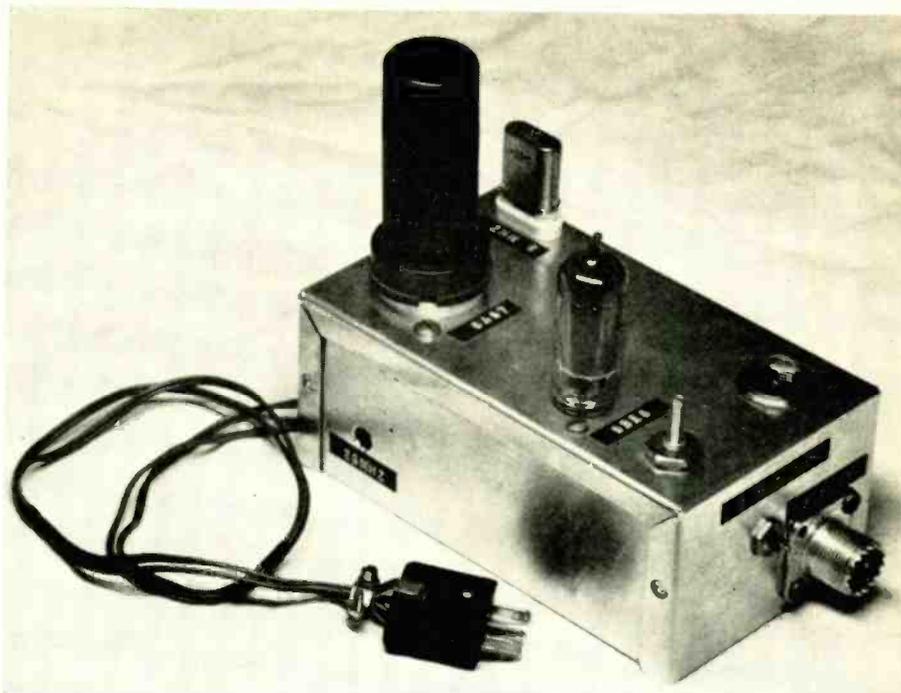
### Converter setup and adjustment

Warm up the meter and the converter for ½ hour or more. Set a nearby receiver on WWV. Zero the crystal oscil-



Converter you can build from this article is essential for upping accuracy of BC-221.

#### Converter Parts List

- C1—ceramic trimmer, 1.5 to 7 pF, NPO (Centralab 822EZ or equivalent)
- C2—10 pF, silvered mica
- C3—150 pF, silvered mica
- C4, C5, C8, C10—.005 µF, disc ceramic
- C6—ceramic trimmer, 3 to 12 pF, NPO (Centralab 822FZ or equivalent)
- C7, C13—5 pF, disc ceramic
- C9—.001 µF, disc ceramic
- C11—6.8 pF, disc ceramic, NPO
- C12—100 pF, disc ceramic, 2 kV
- J—type SO-239 coaxial female connector
- L1—5 µH (can be 14 turns Air Dux 832 or B&W 3016 coil stock)
- L2—800 µH (J. W. Miller 4412 adjustable rf coil)
- R1—100K
- R2—56K
- R3—1 meg
- R4—7,500 ohms
- R5—220K
- R6—470K
- R7—20 ohms, 2 watts
- R8—100 ohms, 1 watt

- All resistors ½ watt 10% carbon except as noted.
- RFC—300 µH, rf choke (J. W. Miller 9350-20 or 70F334A1—listed in Allied Industrial Catalog)
- V1—6AG7
- V2—6BE6
- XTAL—5-MHz crystal for 32-pF load, 25°C, with socket
- No. 47 pilot lamp and socket
- Two-piece aluminum case, 5¼ x 3 x 2½ in.

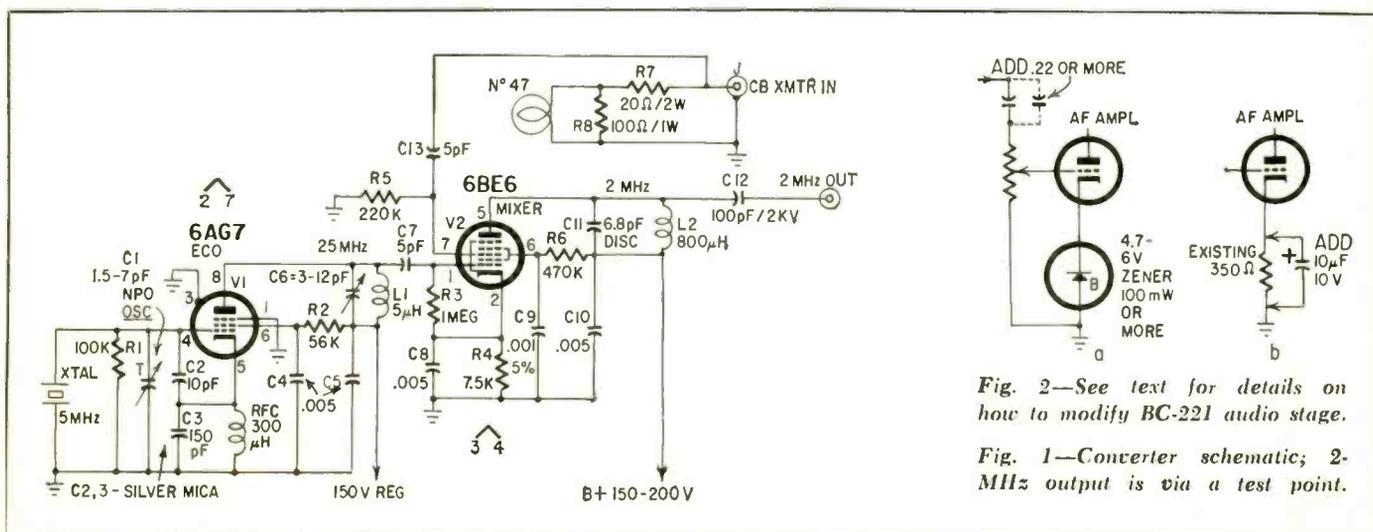


Fig. 2—See text for details on how to modify BC-221 audio stage.

Fig. 1—Converter schematic; 2-MHz output is via a test point.

lator and the frequency-meter 1,000-kHz oscillator to it. The switch in the converter B+ allows the converter to be turned off conveniently for zeroing the meter. Leave the WWV receiver on. It will serve to monitor the converter oscillator frequency.

Now run a clip lead from the converter output to the frequency-meter input and run the CB transceiver into the

5-watt input connector. Put the transceiver on some intermediate channel, such as 11, and jot down the frequency (channel 11 = 27.085 MHz). Now subtract 25 MHz from this figure and, after calibrating with the corrector, set the frequency meter on this difference frequency (27.085 - 25.000 = 2.085 MHz).

The transceiver will hear a signal if

everything is working properly. If there is no S-meter, connect a vvm to the avc bus. Set the 25-MHz adjustment in the plate of the converter oscillator for maximum reading on the S-meter or vvm. Then adjust the slug-tuned coil in the plate of the mixer for maximum signal. The converter is ready to use.

All 27-MHz frequencies will now come out accurately at 2 MHz. The table gives the channels and the frequencies they should read out at on the meter. Accurate channel-center signals of moderate strength are available for receiver calibration.

Channels 1, 2 and 3 are measured by taking the difference from 30 MHz. This inverts the readings. On these three channels a low reading on the frequency meter means the transmitter is high in frequency and vice versa.

Harmonics of the crystal oscillator can be tuned in at exact 5-MHz intervals to beyond 100 MHz. By adding another vhf tuned circuit in series with the 25-MHz plate circuit shown, the operating range could easily go past 150 MHz.


#### Meter operation

The BC221 frequency meter is originally calibrated with the corrector at one point. The readings in the book are not related to any one check point. You get best accuracy when you use the nearest one. The original checkpoints are too widely separated, even if the meter is acceptable as described earlier, for a 100-200-Hz tolerance in calibration to be maintained. Auxiliary checkpoints are required to reduce this span. The first two on the meter, for instance, are at 2,000 and 2,166.666 kHz, a span of more than 160 kHz. This is the range where we want 200-Hz or better accuracy of readings.


To improve accuracy in this range by a wide margin (the frequency may be off by 1 kHz or more if you use only the original check points), use the very good check point at 2,100 kHz and the very weak one at 2,050. For 2,035 to 2,065 (channels 7, 8 and 9) check the meter at 2,000 kHz, then tune to 2,050 to see if the beat note there is audible. If it is, zero it to reduce the calibration error at that point. For 2,075 thru 2,135 use the 2,100 check point, then shift to 2,166.666 to calibrate for 2,155 through 2,175.

Always use the closest check points and auxiliary ones as you go up. On my meter 2,000, 2,050, 2,100, 2,166.666, 2,200 and 2,250 are usable. On a reasonably good meter, the error will be less than 200 Hz. Mine held to less than 100 Hz on most channels when calibrated this way and checked on a digital counter (to the cycle!).

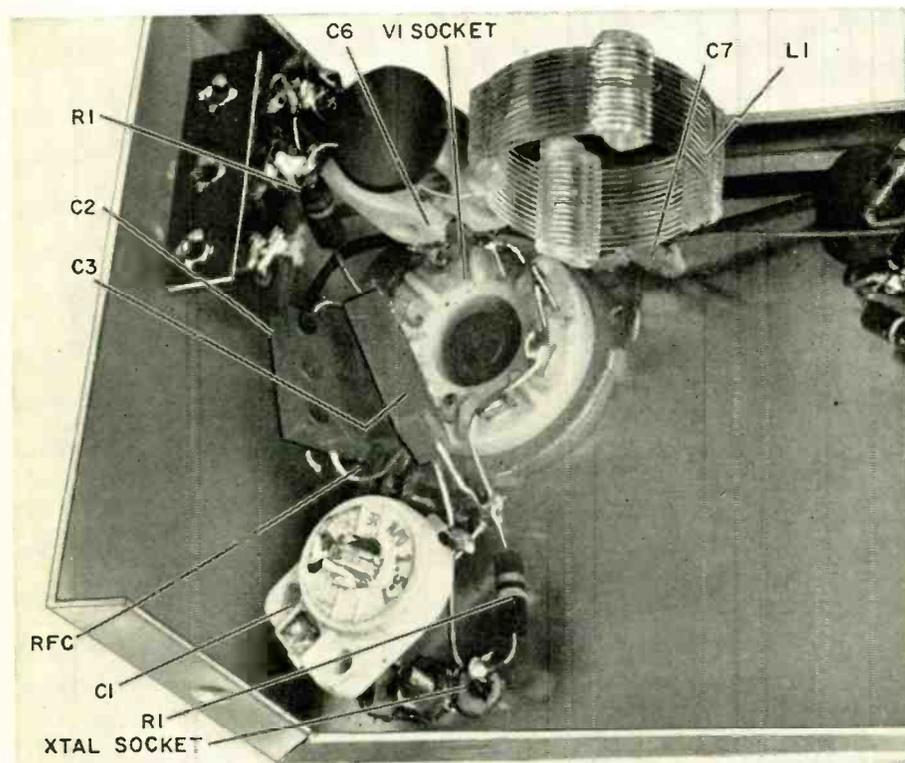When you get the converter and frequency meter going, practice a while



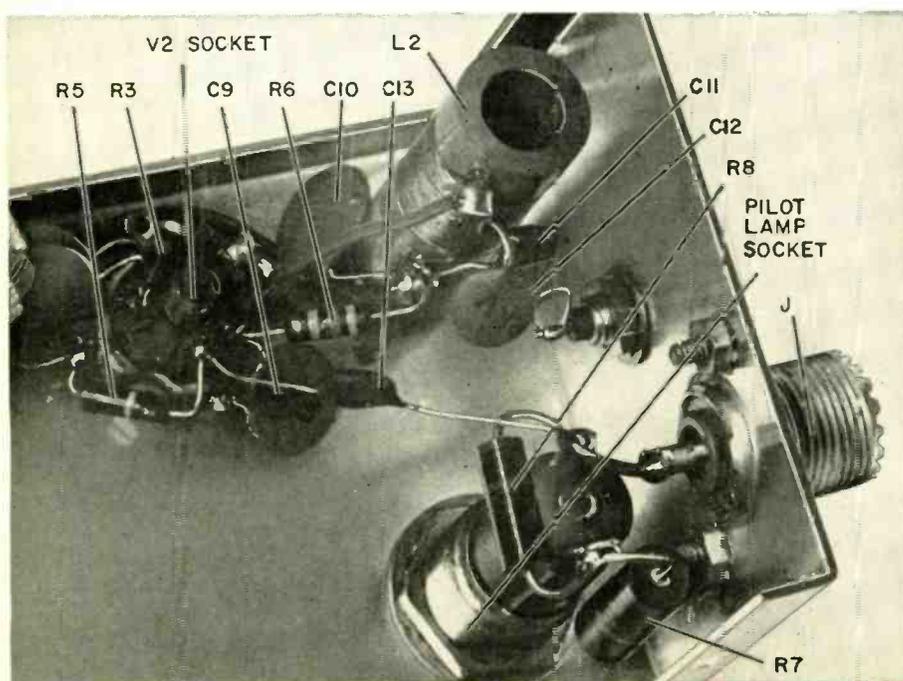Closeup of 6AG7 electron-coupled oscillator stage with visible parts keyed to Fig. 1.



The 6BE6 mixer stage is located near the input for signal from the CB transmitter.

by reading signals off the air. If signals appear consistently high or low on a particular channel, especially when far from a check point, that part of the dial must be checked. Zero the corrector on the check point above the channel in question, then find out how many dial divisions of error there are at the check point below. If the error is too great, that part of the dial will require closer check points. These points are shown in the table.

Always go to the regular check point, then to the auxiliary check points shown. The reason is that many beats may appear in the range of the corrector. By using the regular check points first, the correct auxiliaries are within audible range and need be zeroed with the corrector only for accurate dial calibration.

Using the auxiliaries will always increase accuracy, but if your meter is reasonably good to begin with, your accuracy will be more than adequate. Read the auxiliaries as though they were

signals, to see how close your meter is. If it is within a couple of hundred Hz, the auxiliaries need not be used unless a channel shows up very close to the edge. Now we have accuracy to burn!

#### Accuracy

Once you compensate for calibration error as described above, the greatest factor tending to throw off readings is under control. What else could go wrong? The BC221 manual mentions a few things that can be eliminated easily. If a 150-volt regulated ac supply is used, for instance, the 325-Hz allowance for low batteries is eliminated.

The manual also allows 250-Hz error for the 1,000-kHz standard being off. Checking against WWV at monthly intervals will reduce this error considerably. Checking the 1,000-kHz oscillator when the converter oscillator is checked (before each job) will eliminate it entirely.

Other maximum sources of error as listed in the manual are these:

- |   |        |
|---|--------|
| 1. Small shocks   | 100 Hz |
| 2. Locking the dial   | 30 Hz  |
| 3. Warming up   | 100 Hz |
| 4. Changing load on antenna post                                | 50 Hz  |
| 5. 10% drop in battery voltage or 5° ambient temperature change | 325 Hz |

Items 1, 2 and 4 are things to think about when operating the meter. Items 3 and 5 are error-producing only as the frequency of the 1,000-kHz standard is affected, and apply primarily to field work. We are then left with the calibration error, which is slight near the check points.

There is a built-in limit to the calibration accuracy because the calibration book is good only to the nearest tenth of a division. The approximate separation between tenths is 50 Hz, so any point in the book may split this difference and be off by up to 25 Hz in either direction.

Given an accurate setting of the converter oscillator and the 1,000-kHz meter standard, the overall error of this setup is very small. You can make readings consistently to 100 Hz or less. This accuracy will decrease as you get away from the check points, depending on the meter. Know yours: with a poor one you might have to use all of the auxiliaries shown in the table to get acceptable accuracy.

#### Other applications

The principle of operation we've talked about applies to any other band as long as the 5-MHz oscillator harmonics are strong enough. Higher harmonics can be strengthened by adding another tuned circuit or by substituting a different one if you don't need the range around 25 MHz.

If more strength is necessary in the harmonic output, a varactor would undoubtedly help a lot, particularly at vhf. Zeroing the 5-MHz oscillator to WWV becomes critical at higher frequencies. A 50-Hz error at 10 MHz becomes 600 Hz at 120 MHz. Also, it is best to stick with the 2- to 4-MHz basic high range of the instrument, even though subtraction must be used on some readings. There are few birdies and misleading signals to cause confusion.

This setup is a real pleasure to use. It isn't tricky or temperamental. It can be reset to a previous setting within 50 Hz, and the absolute accuracy is not much worse than that near the check points.

*Frequency certification and any transmitter adjustment that might affect the frequency can be done only by holders of an FCC First- or Second-Class Radiotelephone License.*

END

CB CHANNELS AND FREQUENCIES AS READ ON BC221

Chan	Freq (MHz)	Read at kHz	Check	Aux Check	Note
1	26.965	3,035			1
2	26.975	3,025			1
3	26.985	3,015			1
4	27.005	2,005	2,000		
5	27.015	2,015	2,000		
6	27.025	2,025	2,000	2,040	
7	27.035	2,035	2,050	2,040	2
8	27.055	2,055	2,050		
9	27.065	2,065	2,050	2,067	3
10	27.075	2,075	2,100	2,067	3
11	27.085	2,085	2,100		
12	27.105	2,105	2,100		
13	27.115	2,115	2,100	2,125	
14	27.125	2,125	2,100	2,125	
15	27.135	2,135	2,100	2,133	3
16	27.155	2,155	2,166	2,150	
17	27.165	2,165	2,166		
18	27.175	2,175	2,166		
19	27.185	2,185	2,200		
20	27.205	2,205	2,200		
21	27.215	2,215	2,200		
22	27.225	2,225	2,200	2,233	3
23	27.255	2,255	2,250		

#### Notes

1. Reading obtained by subtraction from 30 MHz. High meter reading means transmitter is low in frequency.

2. Calibrate with corrector at 2,000 kHz before moving to 2,050.

3. Auxiliary check point reading shown must be interpolated from calibration book.

Use the spaces under the frequencies given in the Read at kHz, Check, and Aux Check columns for writing in your own meter calibration points. This table then becomes a permanent reference for your own frequency meter.

There's not an audio man alive who won't find a use for one of these in the next few months! Try one yourself—and find out



# Build An All-Transistor Mixer-Amplifier

By HARVEY INMAN

ALTHOUGH THIS MIXER-AMPLIFIER WAS designed for low-cost remote broadcast pickups, it has dozens of other uses in recording, broadcasting and public address. Even if you don't need a balanced 600-ohm line output monitored by a VU meter (which it has), you'll appreciate this amplifier's low output impedance. With it you can run long lines to the input of a recorder or amplifier with very little noise pickup or loss of high frequencies.

The mixer-amplifier can be built for less than \$50 including meter and cabinet—much less if you can scrounge some of the parts or eliminate the meter circuit.

The amplifier's distortion is less than 1%. Its frequency response is within 1 dB from 50 Hz to 15 kHz. Noise is at least 50 dB below the output level corresponding to an input of -60 dBm. With good components and reasonable care in construction, you should be able to easily equal those specifications yourself.

Only two types of transistors were used in the completed design. Q1 through Q6 are pnp general-purpose replacement transistors (RCA SK3004). Q7 is npn (RCA SK3010). Similar general-purpose transistors are made by other major manufacturers and probably would give good results.

There are two input channels using high-level mixing. A master gain control was not considered necessary for a two-channel mixer and was omit-

ted for simplicity and economy. For the same reasons, no input transformers are used. While input transformers allow the use of balanced microphone lines, good transformers are expensive and add nothing to the performance of a transistor input in most cases. If you want to add one, you can.

A low-impedance microphone will operate satisfactorily, and with low noise, directly into the transistors. The input impedance to the transistors is high enough to permit a microphone to work into an essentially unloaded input, as is recommended for most low-impedance microphones.

The input stages (Q1 and Q2) represent a compromise between low-noise operation and high-signal-handling capability. Besides lowering the gain, the unbypassed 100-ohm resistors in the emitter circuits raise input impedance, lower distortion, and let the transistors handle a larger input signal without overload.

The mixing circuit is very simple and effective. The mixing loss at maximum gain settings is very small with this type of circuit, and interaction between the two controls is only about 3 dB when a control is turned all the way open. This is apparent only when feeding in a steady tone and is not noticeable with normal program material. At normal settings of the controls, no interaction at all is apparent.

This type of gain control should be used only when feeding out of a circuit of relatively high impedance to prevent, among other troubles, a change in frequency response as the control is

varied. The output impedance in this case is approximately the resistance of the 10,000-ohm collector resistors (R4, R10). The coupling capacitors (C3, C6) are in series with this impedance and the impedance looking into the pots. Their reactances are small enough to be negligible at the lowest frequency of interest.

Q3 and Q4 are conventional voltage-amplification stages. Emitter resistor R20 is bypassed at the higher frequencies to compensate for the declining high-frequency response of the output transformer. The low-end response was considered adequate without compensation. A higher-quality transformer would have made the high-frequency correction unnecessary, but the trouble of compensating the response was cheap compared to the price of a first-quality transformer. Again, if you wish, you may use one.

Q5 is a direct-coupled driver for Q6 and Q7. This stage must pass somewhat more collector current than the preceding stages to drive the output transistors with low distortion.

The output stage operates class-B single-ended push-pull. This type of circuit has several advantages over a transformer-coupled output stage for a high-quality amplifier. The output transformer for a conventional class-B stage must have very tight coupling between the two halves of the primary winding to prevent ringing when the current is abruptly switched from one winding to the other each half-cycle. In the single-ended push-pull stage, no such demand is made on the output transformer. The


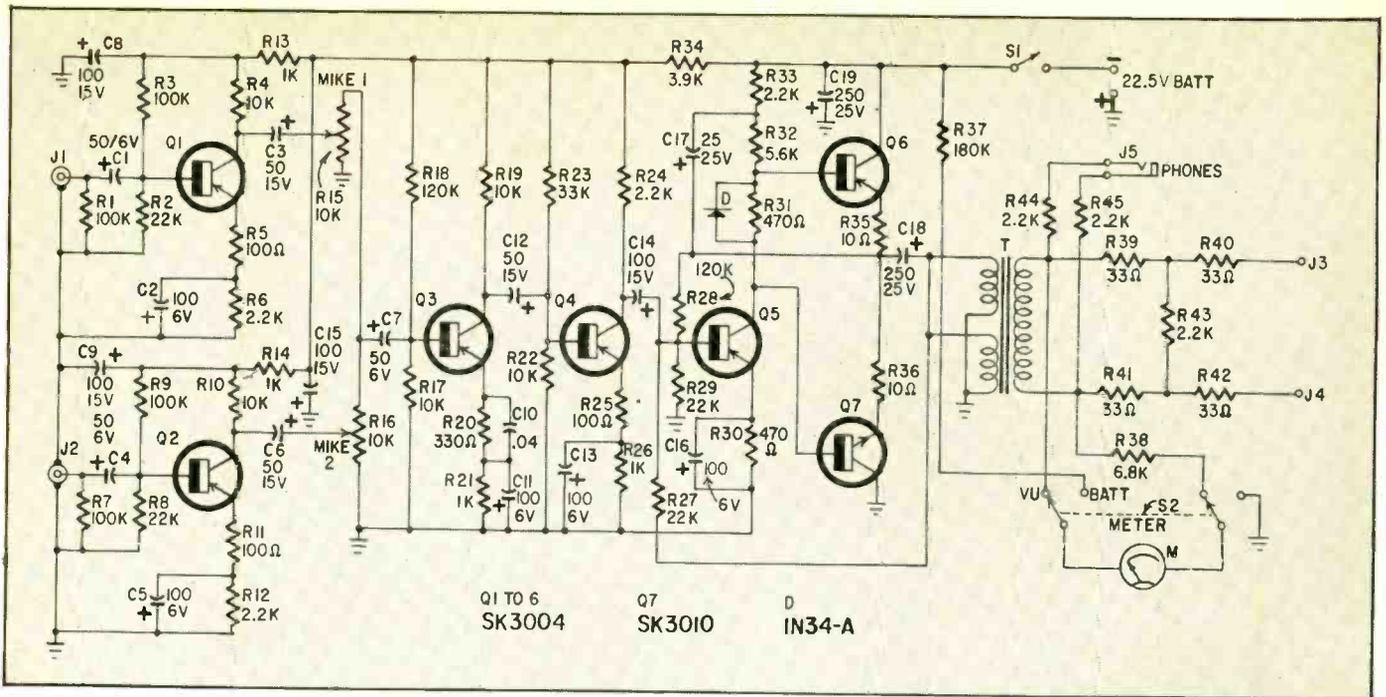


Fig. 1—Schematic of the battery-powered all-transistor mixer-amplifier. Use it for PA, recording, or general sound work.

- |  |  |   |   |
|--|--|---|---|
| C1, C4, C7—50 $\mu$ F, 6 V, electrolytic             | J1, J2—microphone connectors (to match mike plugs) | R4, R10, R17, R19, R22—10K                  | R35, R36—10 ohms  |
| C2, C5, C11, C13, C16—100 $\mu$ F, 6 V, electrolytic | J3, J4—binding-post terminals (2 required)         | R5, R11, R25—100 ohms                       | R37—180K  |
| C3, C6, C12—50 $\mu$ F, 15 V, electrolytic           | J5—headphone jack (single-circuit)                 | R6, R12, R24, R33, R43, R44, R45—2,200 ohms | R38—6,800 ohms  |
| C8, C9, C14, C15—100 $\mu$ F, 15 V, electrolytic     | M—VU meter (Lafayette 99 C 5043)                   | R13, R14, R21, R26—1,000 ohms               | R39, R40, R41, R42—33 ohms  |
| C10—.04 $\mu$ F, paper or ceramic                    | Q1, Q2, Q3, Q4, Q5, Q6—SK3004 (RCA)                | R15, R16—10K audio-taper pots               | All resistors 10% tolerance, 1/2 watt                               |
| C17—25 $\mu$ F, 25 V, electrolytic                   | Q7—SK3010 (RCA)                                    | R18, R28—120K                               | BATT—22 1/2-volt battery (Eveready 763 or equivalent)               |
| C18, C19—250 $\mu$ F, 25 V, electrolytic             | R1, R3, R7, R9—100K                                | R20—330 ohms                                | S1—spst slide switch  |
| D—IN34A diode  | R2, R8, R27, R29—22K                               | R23—33K                                     | S2—dpdt slide switch  |
|  |  | R30, R31—470 ohms                           | T—150-ohm to 600-ohm line-to-line transformer (SNC 1P161) see text. |
|  |  | R32—5,600 ohms                              |   |
|  |  | R34—3,900 ohms                              |   |

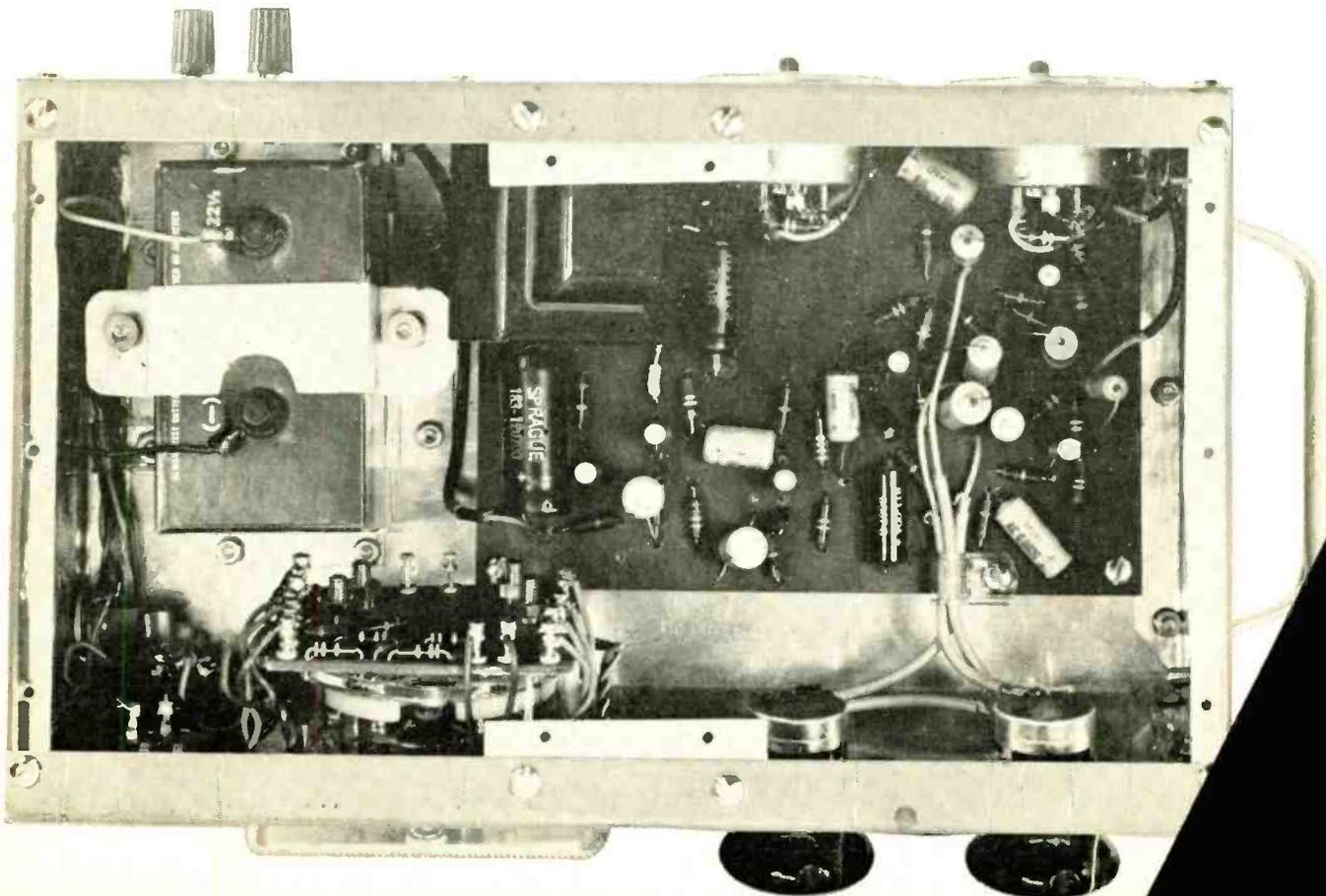

## Build An All-Transistor Mixer-Amplifier

two halves of each cycle are combined in the output stage itself, and a transformer is needed only for impedance matching or for feeding a balanced line. This will depend on your usage.

The stage operates as an emitter follower, with the advantages of low output impedance, low distortion, and better high-frequency response. Because of the built-in negative feedback, the output transistors do not have to be critically matched. This should make your job easier.

Any class-B stage must conduct a certain minimum resting current to prevent crossover distortion (a "jog" in the waveform where the signal is switched from one transistor to the other). This kind of distortion is especially objectionable. It is decreased here to a very small value by forward-biasing Q6 and Q7 for about 1.5 mA collector current. The bias is set by diode D, shunted by R31. The voltage drop across D does a good job of stabilizing the current of Q6 and Q7 with declining battery voltage and varying temperatures. This makes performance fairly constant in the field.

T is a multi-impedance transformer. A Stancor A-4350 may be substituted. Connect the primary for 125 ohms and the secondary for 500. Change C10 to .015  $\mu$ F.

The negative-feedback networks are designed to allow the amplifier to be unconditionally stable. Feedback from the output stage is returned to the base of Q5 by two paths. Feedback through R28 tends to stabilize the voltage division between Q6 and Q7, as well as reduce distortion and lower output impedance. R27 supplies additional feedback and helps prevent a dropoff in low-frequency response caused by the increasing reactance of C18 at low frequencies. Positive feedback through C17 furnishes Q5 with a higher effective collector voltage under signal conditions. This greatly aids Q5 in supplying the voltage swing necessary at full amplifier

the proper damping and frequency response, it should be fed from a source resistance of 3,900 ohms. For levels higher than +4 VU the meter multiplier usually takes the form of a T-pad. For this inexpensive meter, a single series resistor was chosen to make the meter read zero when +4 dBm appears at the output terminals loaded with a 600-ohm resistor. Once again, a compromise has worked out fine in practice, but it is not recommended if you go to the expense of a standard VU meter.

The meter is also used to check the battery condition. When METER switch S2 is placed in the BAT position, the meter is connected to the battery through R37, which is selected to make the meter read zero with a new battery. Thus you have a quick check "on location."

After constructing the amplifier, make a few measurements to verify correct operation. The voltage at the junction of R35 and R36 should be half the battery voltage. A difference of a few tenths of a volt is nothing to worry about, but if the voltage is off by more than about 0.5 volt, change R28 to the next higher or lower standard value that you can obtain.

A radically different voltage at this point indicates a defective component somewhere in the output or driver stage. The measurements should be made with a new battery, since it is not possible to hold this optimum voltage division with a weak battery.

Measure the current drawn by the complete amplifier. Normal current is between 7 and 8 mA. The output stage should draw about 1.5 mA. Check roughly by first measuring the current drawn by the amplifier, then placing a temporary short across D and observing the decrease in current when the forward bias of Q6 and Q7 is thus removed. R31 should be decreased if the change in current is more than 1.5 mA. If the change is less than 1.5 mA, remove R31 entirely.

The signal-to-noise ratio was 57 dB with -60 dBm input from a 600-ohm source and the gain adjusted for +4 dBm output. When the gain was increased for +14 dBm output, with the input at

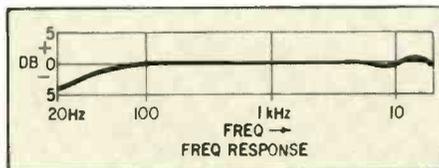


Fig. 2—Frequency response of amplifier meets broadcast standards. The 0-DB reference level is actually +4 dBm (+4 VU) measured at amplifier output.

the same level, the noise was 60 dB down. This indicates that a significant amount of the residual noise is generated in the stages after the mixers.

Maximum gain through each channel is about 80 dB, more than adequate for all normal use. The input stages are designed to handle microphone levels. If inputs other than microphones are used, it might be necessary to attenuate the signal before putting it into the amplifier.

Battery life with the specified battery should be well over 100 hours. The amplifier will still operate properly when the voltage has dropped to 15. At this point the distortion is still below 1%, and the gain drops only slightly.

The main portion of the amplifier was built on a 4- by 6-inch etched circuit board, and this method is highly recommended if possible. Copper-clad board and etchant solution are available from electronics mail-order houses; and the work is not difficult. The circuit pattern can be painted on the copper side of the board with a small brush and quick-drying lacquer. After etching, the paint is easily removed with lacquer thinner or speaker-cement solvent. You can also do a good job with perforated phenolic board.


The output pad, R37, R38, R44 and R45 were mounted on a second small board, which was drilled to mount on the meter terminals. The meter terminal nuts hold the board in place. The output transformer was mounted to the back of the cabinet.

No instability appeared, but as with any high-gain amplifier the input circuits should be well separated from the output.

I had a cabinet made of sheet aluminum. A small commercially made utility cabinet will serve just as well. A removable bottom plate allows access to the inside. The circuit board is mounted to the inside top of the cabinet on metal spacers. After cutting all holes in the cabinet, I spray-painted it and labeled the controls, switches and jacks with decals.

If you use the amplifier to feed a high-impedance (unterminated) load, connect a 620-ohm 1/2-watt resistor across the output terminals. The amplifier will work without it, but the VU meter readings will be different and the frequency response may be altered. Substantial runs of line (perhaps 100 feet or more) are usually possible with unshielded twisted-pair. If hum or radio-frequency interference is a problem, you will have to turn to shielded, two-conductor cable.

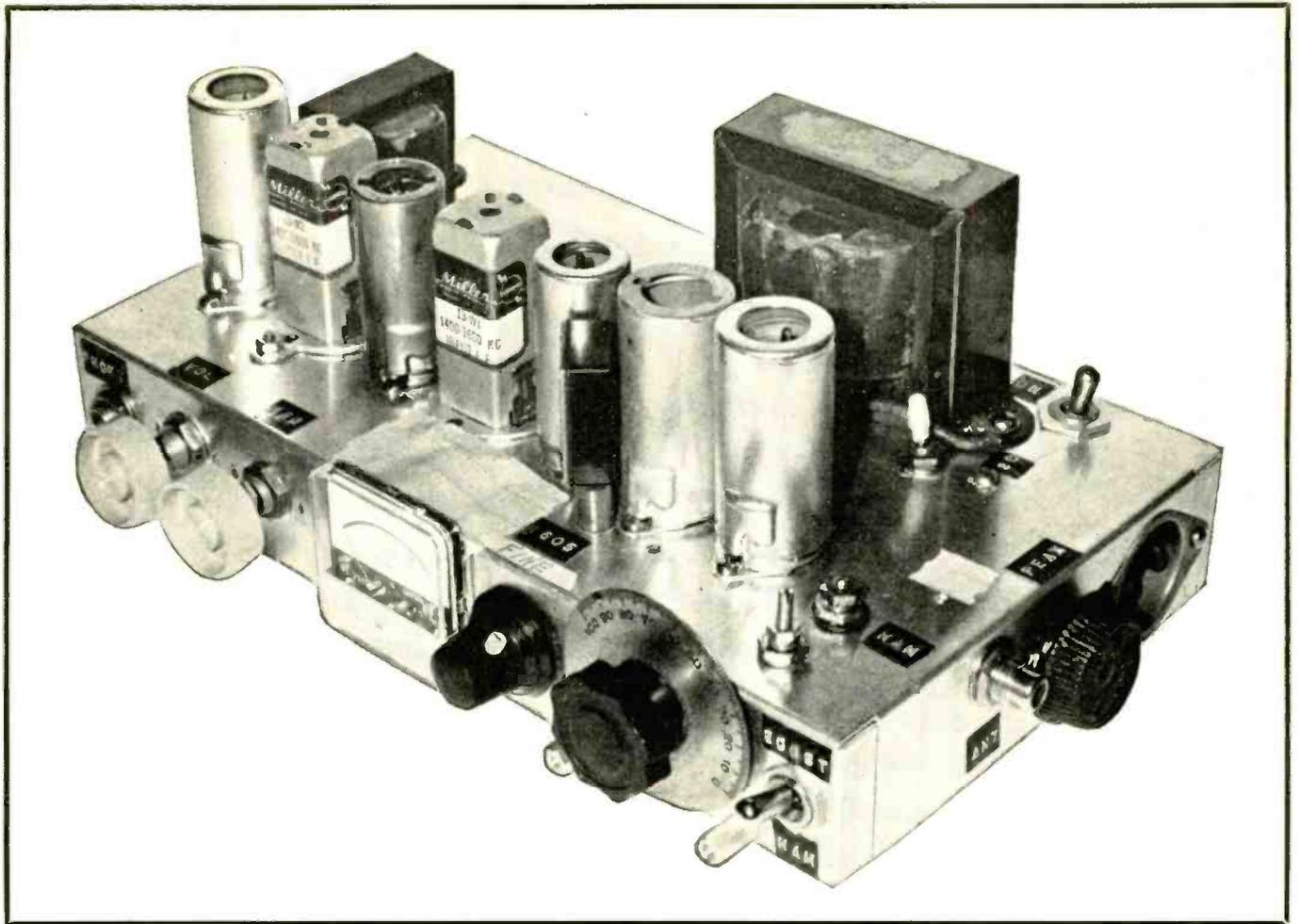Carefully built and adjusted, this amplifier should give years of service with only occasional battery replacement. END



# Build Your Own Shortwave Receiver

Here's a good way to gain valuable construction experience in radio

By I. QUEEN

SHORT-WAVE LISTENING IS AN EXCITING and rewarding pastime. Because of the remarkably distant reception (DX) possible at the higher frequencies, stations from all over the world often are picked up even with simple receivers.

For short-wave listeners (SWL's) two major signal categories are of specific interest: international broadcasting and amateur transmissions. Broadcasting offers frequent news reports, interesting sidelights on far-away places, speeches made by heads of foreign governments, and symphonic concerts. Amateurs transmit their semi-personal messages to each other, some by code, some by voice. Something is nearly always doing on these bands. But, one thing that is not easy to find is product advertising!

Some time ago, I looked through several radio catalogs searching for a

receiver for general short-wave listening. Since I already own a modern commercial set capable of picking up signals from almost anywhere in the world, the new set was to be used away from home for casual listening. Some receivers were for hams only, others for broadcasting only. Some had poor selectivity, others no provision for code listening. Some were simply too big or too expensive for a set to be used only occasionally.

Finding no unit that fulfilled my requirements, I resolved to build my own. After several preliminary models, the one described here evolved. Its cost is well under \$50, and it offers four short-wave bands: 3.4-4.1, 5.8-6.8, 6.7-7.4 and 9-10 (all in MHz). The first and third are ham bands, 80 and 40 meters, respectively. The other two are popular international-broadcast bands.

Actually, since the 40-meter amateur band is shared by broadcasters, there are three BC bands.

Selectivity is high, thanks to the double-crystal filter and two high-gain i.f. stages. Sensitivity is so great that a 4-foot wire antenna is sufficient to bring in signals from around the world.

Note that each band is limited in coverage; in fact, to 1 MHz or less. This is a distinct advantage. Relatively few of the short-wave frequencies are occupied by signals useful to SWL's. About 90% of the spectrum is filled with strange sounds—the buzzes and whistles of high-power telegraphy, teletype and experimental signals which cannot be deciphered by the average listener. The most interesting voice and code (CW) signals appear in compact bands like the ones mentioned.

An unusual feature of this receiver

## Build Your Own Shortwave Receiver

is that it utilizes a method that doubles the number of bands without changing the oscillator circuit. In a normal superhet, the incoming rf signal is consistently below (or above) the local oscillator frequency. In this receiver, it may be either above or below, depending on how the antenna is tuned. The i.f. is about 1.6 MHz. If the signal-input antenna circuit is tuned 1.6 MHz higher than the local oscillator, we may tune one band of frequencies. If the input is tuned 1.6 MHz lower than the oscillator, we may tune another band.

Using this approach, only two oscillator ranges are required. One range, 5.0–5.7 MHz, is used to tune 3.4–4.1 MHz and 6.7–7.4 MHz, depending on whether the input circuit is tuned above or below the oscillator frequency. The second oscillator range, 7.4–8.4 MHz, tunes 5.8–6.8 and 9–10 MHz, depending on how the antenna circuit is tuned.

All that need be done is to peak up the antenna capacitor. This may be done either by listening to the noise background or, having heard a signal, by tuning the input circuit to maximum.

The relatively high i.f. (1.6 MHz) was chosen to minimize images. Transformers at this frequency are readily available.

### Basic circuit operation

A short antenna (as noted previously, a 4-foot wire will bring in stations from all over the world) picks up the SW signals. L1–C2 resonates to peak them up and delivers them to the converter grid, where they are mixed with the signal from local oscillator V1-b.

Switch S2 selects the amateur- or broadcast-band coils as desired. The HAM position covers 3.4–4.1 MHz, or 6.7–7.4, depending on the setting of antenna-input capacitor C2. In BDCST position, we may hear either 5.8–6.8 or 9–10 MHz.

When S1 is closed, part of L1 is shorted, and the circuit tunes from 5–10 MHz. For 80-meter coverage, the full 45-turn coil is required. A slightly larger antenna is recommended for this band.

The desired signal frequency is fed from the converter through the crystal filter at the input of the i.f. strip. One crystal is cut for a slightly different frequency from the other. The response of the filter gives sufficient selectivity for tuning code signals in a crowded band, yet it's broad enough to assure clear speech reception on AM and SSB.

The two i.f. stages are designed for high gain. Each is controlled by age voltage. A tuning meter with a 0–1-mA movement is used in the plate lead of V3. The value of R13 is chosen so that M reads near full scale with no signal. About 2,000 ohms will be suitable in most cases. Use a 10K pot and adjust for full-scale meter deflection.

When a signal is tuned in, the age voltage becomes more negative, reducing the plate current. The meter then indicates the lesser current. Moderately strong signals drop the needle to about midscale; very strong ones reduce the deflection nearly to zero. Besides being useful in tuning signals, the meter is a valuable aid to alignment.

Diode detector D1 rectifies the rf signal after it passes through the i.f. sec-

tion. The detected signal is then fed directly to phone jack J2 or to the two-stage audio amplifier. There is sufficient gain here to bring nearly all signals to full loudspeaker volume.

CW signals are received by using regeneration in the second i.f. stage. Note that the suppressor of V3 is not grounded directly. Instead, a 2,000-ohm rheostat is included. As the resistance of R11 is increased, the stage regenerates. This is not as satisfactory an arrangement as having a separate bfo, but it works well enough to satisfy most SWL's.

Although we had not intended this receiver to receive SSB (single-sideband) signals, it can be done. Bring the i.f. stage to oscillation, then carefully adjust C10-b. This tiny variable capacitor works in conjunction with main-tuning capacitor C10-a. The fine-tuning capacitor is made from a 15-pF variable by cutting out all but two or three plates. The capacitance becomes so small that it can be used to fine-tune SSB stations. To get undistorted SSB signals, you must be able to vary the frequency over a very small range. With the aid of C10-b and a little care, you'll be able to tune sideband signals quite handily.

The power supply is conventional and supplies about 120 volts at 15 mA to the receiver. Hum is very low and will hardly be noticeable, even at full volume.

### Construction


The receiver is built on an aluminum chassis, 9½ x 5 x 1½ inches. It is shallow enough so you can get your fingers and a soldering iron into it. All controls are on the front apron, except the ON-OFF switch, peaking (antenna) control and S1.

An important construction detail is the spacing between tube sockets and i.f. transformers, which are in a straight line across the chassis. The center of this line is 1⅝ inches from the front.


Looking down on the top of the chassis and measuring from the left-hand side of the chassis, we find the following dimensions to the center of each component:

V4 9-pin socket	¾ inch
T2 i.f. transformer	1⅞ inches
V3 7-pin socket	3 inches
T1 i.f. transformer	4⅞ inches
V2 7-pin socket	5¼ inches
L4 9-pin socket	6⅜ inches
V1 9-pin socket	7½ inches

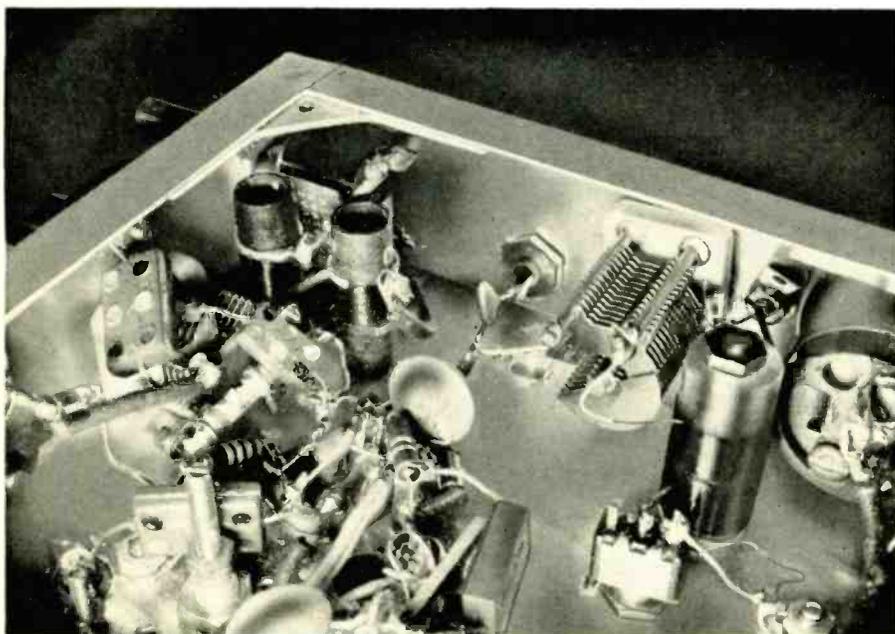L4 is a ⅜-inch diameter slug-tuned coil mounted with slug-screw down (un-



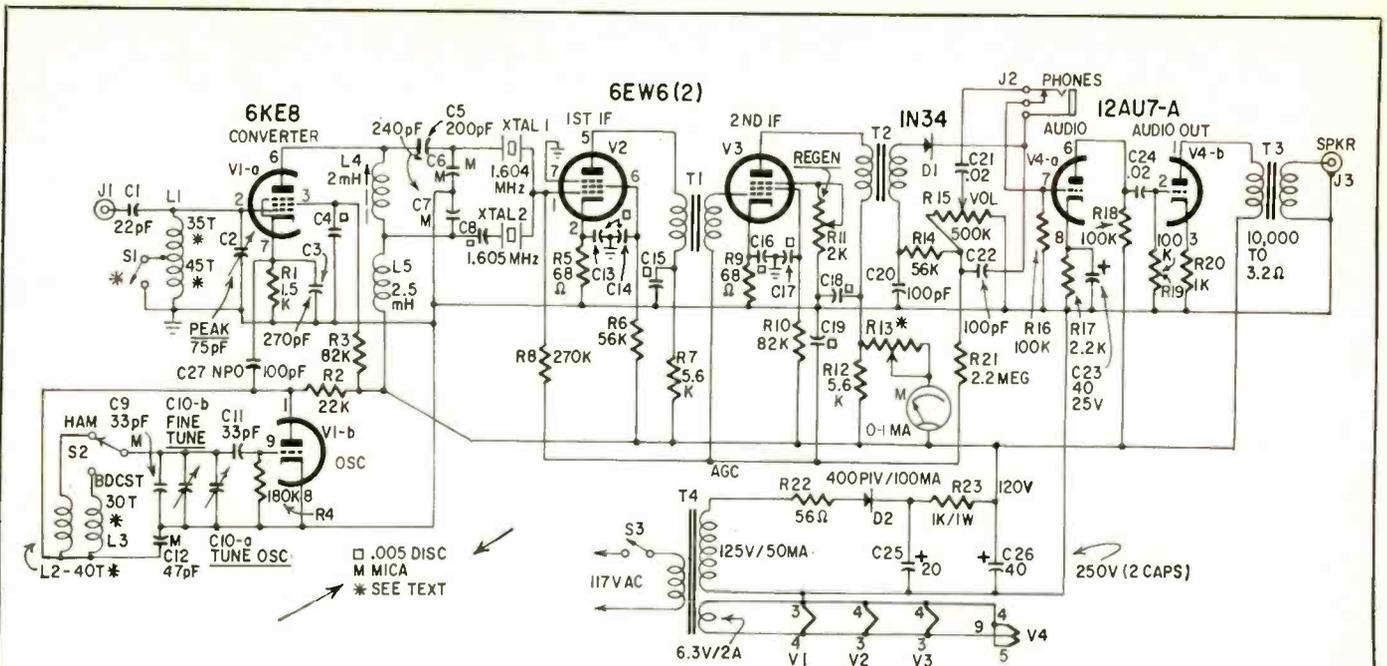Front-end components are tightly, but carefully, placed to minimize stray pickup.



The receiver constitutes a fairly straightforward circuit. It's simple—only 4 tubes and 2 diodes.

#### PARTS LIST

R1—1,500 ohms  
 R2—22K  
 R3, R10—82K  
 R4—180K  
 R5, R9—68 ohms  
 R6, R14—56K  
 R5, R12—5,600 ohms  
 R8—270K  
 R11—2,000 ohm pot, linear taper  
 R13—10K pot, linear taper (see text)  
 R15—500K pot, audio taper  
 R16, R18, R19—100K  
 R17—2,200 ohms  
 R20—1,000 ohms  
 R21—2.2 megohms  
 R22—56 ohms  
 R23—1,000 ohms, 1 watt

Otherwise unmarked resistors are 1/2 watt  
 C1—22 pF, disc  
 C2—75 pF, air variable  
 C3—270 pF, disc  
 C4, C13, C14, C15, C16, C17, C18, C19—.005 μF, disc  
 C5—200 pF, mica  
 C6, C7—240 pF, mica  
 C9—33 pF, mica  
 C10a—main tuning, 50 pF, air variable  
 C10b—vernier tuning, see text  
 C11—33 pF, disc  
 C12—47 pF, mica  
 C20, C22—100 pF, disc  
 C21—.02 μF, disc  
 C23—40 μF, 25 V, electrolytic  
 C24—.02 μF, paper  
 C25—20 μF, 250 V, electrolytic  
 C26—40 μF, 250 V, electrolytic  
 C27—100 pF, NPO

T1—input i.f. transformer, 1.6 MHz (Miller 13 W1)  
 T2—output i.f. transformer, 1.6 MHz (Miller 13 W2)  
 T3—audio-output transformer, 10K to 3.2 ohms  
 T4—power transformer (Merit P 3045 or equivalent)  
 L1—coil, 1/2-in. diam, No. 30 enameled wire wound on polystyrene form, 80 turns, tapped at 35/45 point  
 L2—slug-tuned coil, 3/8-in. diam, No. 34 enameled wire, 40 turns  
 L3—slug-tuned coil, 3/8-in. diam, No. 30 enameled wire, 30 turns  
 L4—slug-tuned coil, approx 2 mH (Miller 4414)  
 L5—2.5 mH, choke  
 All coils are close-wound

XTAL1—1.604-MHz crystal (Texas Crystals)  
 XTAL2—1.605-MHz crystal (Texas Crystals)  
 Sockets for above crystals  
 V1—6KE8  
 V2, V3—6EW6  
 V4—12AU7-A  
 7-pin tube sockets and shields (2)  
 9-pin tube sockets and shields (3)  
 Power-line male socket  
 S1—spst  
 S2—spdt toggle  
 D1—1N34A  
 D2—400-piv diode, 100 mA  
 M—tuning meter, 0–1 mA (Lafayette 99R2513)  
 J1, J3—phono-type jacks  
 J2—headphone jack  
 Chassis, 9 1/2 x 5 x 1 1/2 inches  
 Hardware, knobs, terminal strips, lugs, etc.

der the chassis). It is housed inside a nine-pin tube shield which offers both shielding and mechanical protection. Discard the socket itself after separating it from the metal mounting. Using two screws, mount this base on the chassis, using as the center point a distance 6 3/8 inches from the left-hand side of the chassis. The coil itself will be above chassis.

The tuning meter is 1 1/2 inches in diameter, too large to fit on the front panel. Cut a square hole 1 x 1 inch on the top of the chassis, near the front. This allows the top of the meter to protrude above the chassis. Now, with a 1 1/2-inch hole cutter, cut out the front apron. The meter will then fit on the front apron with only the top of it showing through the square hole.

Antenna (peaking) capacitor C2 is

mounted on the right-hand side of the chassis near coil L1.

Keep rf and i.f. leads short, as usual; parts placement is not critical otherwise. The power supply is placed toward the rear of the chassis.

The crystal filter uses mica capacitors at C5, C6, C7. Use mica capacitors also for C9 and C12 in the oscillator section. A signal generator or grid dip meter will be helpful for aligning oscillator coils L2 and L3.

After you have listened for a while, you may wish to calibrate the main tuning dial. The 80-meter band will cover most of the dial. The 6-MHz band will be near the low end of the capacitor, and the 10-MHz band will come in near the high end. The 40-meter band will be received near the upper end of the dial.

When properly tuned, there should

be no instability on any band. Tune up the regeneration for maximum gain, but not too near the point of oscillation. If you are seeking CW signals, of course, you should go past the critical point.

Remember that the antenna circuit will tune either *above* or *below* the local oscillator frequency. If both are tuned near the same frequency, you may notice some instability, and the converter stage may oscillate. This improper tuning of the set should be avoided.


You will find you get remarkable results from this receiver on the bands for which it is designed. It is compact and light enough to carry with you on vacation or when visiting. And, when properly tuned, it will bring in stations from the far ends of the earth to provide many hours of interesting SW listening.

END

# Remote-Reading Field Meter

You say you can't see rf? Build this monitor and you'll be able to watch your transmitter output

By JAMES B. WHITE

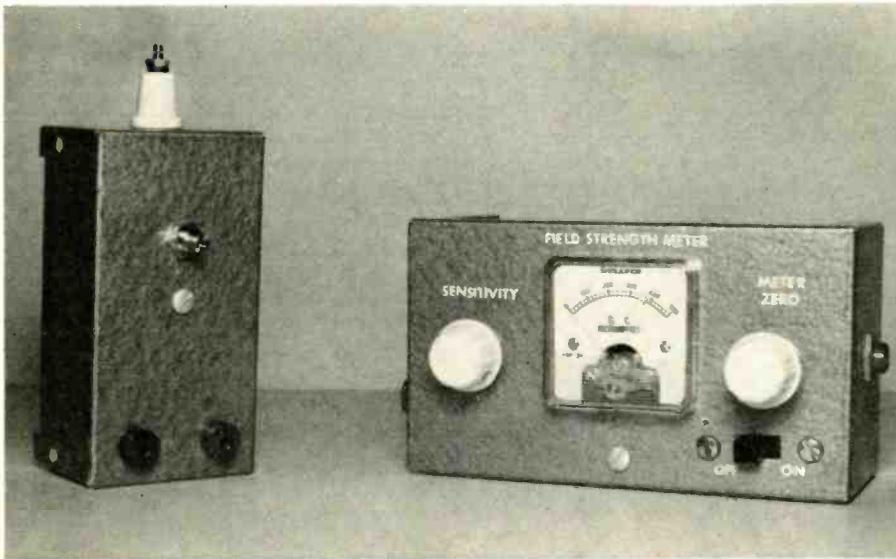

EVERY GOOD TRANSMITTER OPERATOR IS interested in his radiated signal. Nothing is more evident as one listens to CB, ham or commercial two-way channels. Very often comparison checks are asked for, modulation reports are solicited and signal-strength measurements are noted. If you are going to operate any transmitter, you need a means of monitoring your signal every moment you are on the air.

This field-strength meter can be set up permanently to provide a visual report every time the transmitter is used. Mobile units can be checked in just a moment by having the operator key the mike. This meter is invaluable in the construction of beam antennas. Because of the remote-reading feature, you can put the detector out in the field while you watch the indicator by the antenna. This lets you check forward gain and front-to-back ratio.

## The circuit

The field meter consists of two units, a detector and an indicator. The detector is the utmost in simplicity, containing only about a dozen parts. It's nothing more than a tuned circuit, which resonates at the transmitter frequency, and a detector diode. Rf is picked up by a whip antenna on a feed-through insulator mounted on the case.

The indicator unit is only slightly more complicated; it is a transistorized voltmeter with two controls—SENSITIVITY (R1) and ZERO (R4). There's also a phone jack, to monitor detected audio. The power supply is simply two pen-light cells (AA size).

## Construction

Both units are housed in small aluminum boxes. Components are wired point-to-point and are self-supporting.

Locate and drill the mounting holes first. Be sure the jack holes are large enough to allow the insulating shoulder washers to fit. The black jack doesn't have to be insulated from the box, but the red one must be. The hole in the top of the detector box must be large enough to pass the feedthrough insulator. Be careful mounting the in-



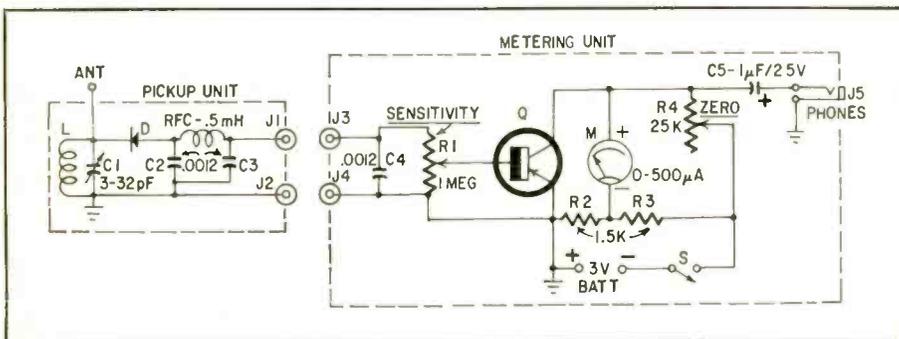


Fig. 1—Each section of the field meter should be constructed in its own metal box.

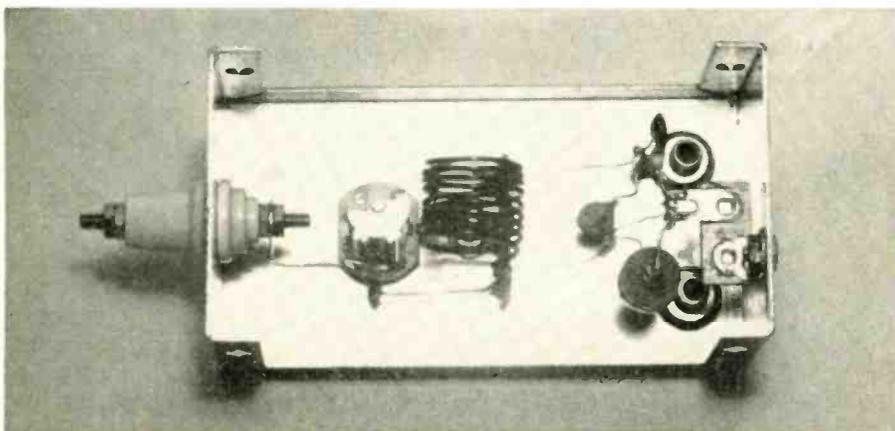

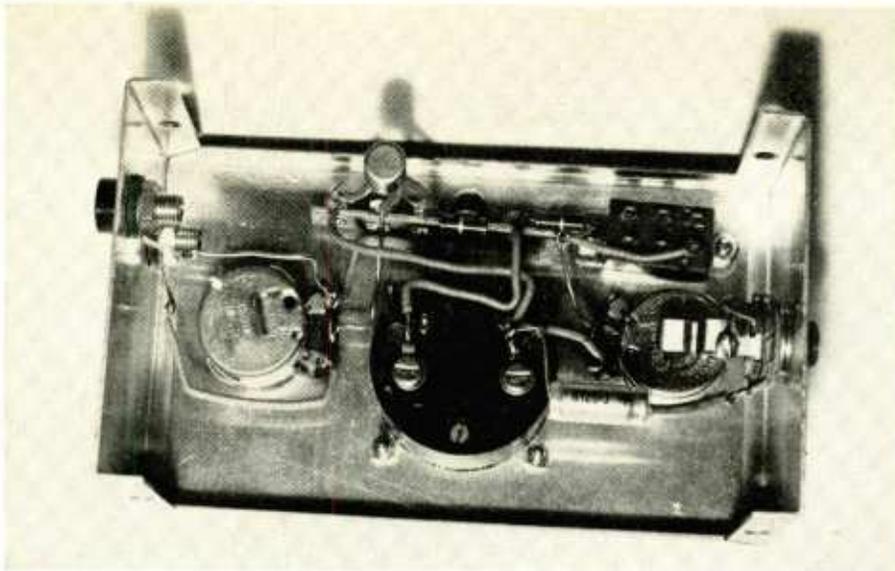There's more than enough room inside the detector box for mounting all components.



For best (and easiest) results, use simple, point-to-point wiring inside indicator unit.

sulator: if you tighten it too much, you'll crack it.

The meter hole in the indicator unit will probably be a problem unless you have a socket punch the right size.

Try this: Scribe a circle 1½ inches in diameter and drill a series of ⅛-inch holes about just inside the circle. Keep them as close together as you can.

Knock out the metal between the holes, leaving a ragged hole just under 1½ inches in diameter. This hole can be dressed off with a small round file. You can use the same technique to mount the power switch.

Next, mount and wire the components. Note carefully the meter polarity and wire it accordingly. Be careful with

the diode and transistor. When you have completed all the wiring except the semiconductors, check your work carefully. Then wire in the diode and the transistor. Cut leads to a length that will allow ample working room. Slip a small piece of spaghetti over each lead. As you solder, be wary of too much heat. Use long-nosed pliers, with a rubber band around the handles, as a heatsink. Or try locking pliers.

With the two penlight cells connected you can check out the indicator unit. Turn the power switch on. The meter may go off scale to the left, or it may read to the right. Rotating R4 should zero the pointer. If it does, set the metering unit aside till later. If not, check your wiring.

The photographs show a CB channel coil soldered in place. This coil will also tune the 10-meter ham band. The other coil specifications are listed. The four low-frequency coils are regular TV peaking coils and rf chokes. The higher-frequency coil is hand-wound.

### Using the meter

Connect the detector to the indicator, red jack to red jack, and black to black. Turn on the power and zero the meter with the ZERO control. Set SENSITIVITY so the arm of the pot is at chassis potential (should be maximum counterclockwise). Turn on the transmitter and advance SENSITIVITY until you get a reading. Tune C1 for maximum meter indication. Depending on transmitter rf power, you may or may not need a piece of wire connected to the feedthrough insulator. If the meter doesn't work properly, recheck wiring. If it does, you are ready to use the instrument.

Mount the detector as far as you can from the antenna to be checked. If you plan to use the meter for keeping a constant check on a base station, put the detector as far as possible from both antenna and transmitter. The location will be determined largely by the amount of wire you have and how big your lot is. The two units can be separated by several hundred feet.

A short pickup antenna must be connected to the antenna feedthrough insulator. Its length is determined by power and antenna-to-antenna spacing. Cut several pieces, try them, and use the one which causes the meter to read up scale, but not consistently off scale.

You'll find this field meter useful in observing day-to-day transmitter and antenna operation. If anything deteriorates—low line voltage, a weak output stage, or a shorted or open antenna element—you'll know it the next time you put the rig on the air. The meter is also handy in servicing transmitters because it lets you "see" rf.

(continued on page 66)

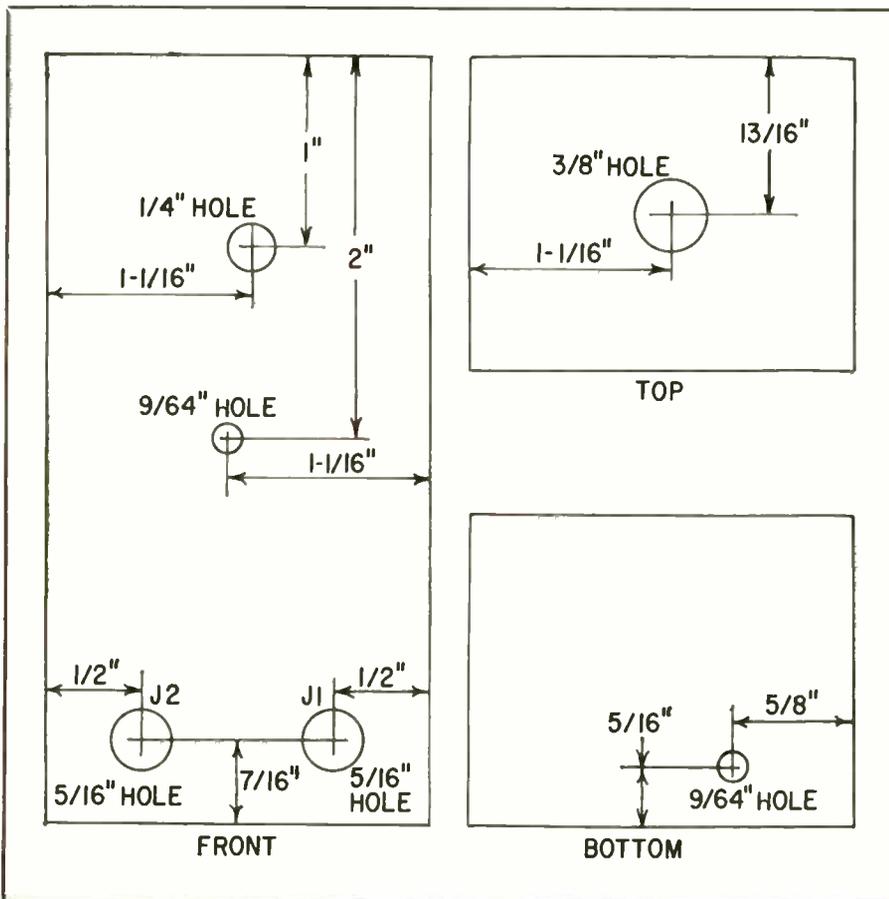


Fig. 2—Locate and drill holes as shown in the detector box. Ream edges smooth.

# How to get into One of the hottest money-making fields in electronics today— servicing two-way radios!



**HE'S FLYING HIGH.** Before he got his CIE training and FCC License, Ed Dulaney's only professional skill was as a commercial pilot engaged in crop dusting. Today he has his own two-way radio company, with seven full-time employees. "I am much better off financially, and really enjoy my work," he says. Read here how you can break into this profitable field.

**More than 5 million two-way transmitters have skyrocketed the demand for service men and field, system, and R&D engineers. Topnotch licensed experts can earn \$12,000 a year or more. You can be your own boss, build your own company. And you don't need a college education to break in.**

**H**OW WOULD YOU LIKE to start collecting your share of the big money being made in electronics today? To start earning \$5 to \$7 an hour... \$200 to \$300 a week... \$10,000 to \$15,000 a year?

Your best bet today, especially if you

don't have a college education, is probably in the field of two-way radio.

Two-way radio is booming. Today there are more than *five million* two-way transmitters for police cars, fire department vehicles, taxis, trucks, boats, planes, etc. and Citizen's Band uses—

*Circle 24 on reader's service card*

and the number is still growing at the rate of 80,000 new transmitters per month.

This wildfire boom presents a solid gold opportunity for trained two-way radio service experts. Many of them are earning \$5,000 to \$10,000 a year *more* than the average radio-TV repair man.

### Why You'll Earn Top Pay

One reason is that the United States Government doesn't permit anyone to service two-way radio systems unless he is *licensed* by the Federal Communications Commission. And there simply aren't enough licensed electronics experts to go around.

Another reason two-way radio men earn so much more than radio-TV service men is that they are needed more often and more desperately. A home radio or television set may need repair only once every year or two, and there's no real emergency when it does. But a two-way radio user must keep those transmitters operating at all times, and *must* have their frequency modulation and plate power input checked at regular intervals by licensed personnel to meet FCC requirements.

This means that the available licensed experts can "write their own ticket" when it comes to earnings. Some work by the hour and usually charge at least \$5.00 per hour, \$7.50 on evenings and Sundays, plus travel expenses. A more common arrangement is to be paid a monthly retainer fee by each customer. Although rates vary widely, this fixed charge might be \$20 a month for the base station and \$7.50 for each mobile station. A survey showed that one man can easily maintain at least 100 stations, averaging 15 base stations and 85 mobiles. This would add up to at least \$12,000 a year.

#### Be Your Own Boss

There are other advantages too. You can become your own boss—work entirely by yourself or gradually build your own fully staffed service company. Instead of being chained to a workbench, machine, or desk all day, you'll move around, see lots of action, rub shoulders with important police and fire officials and business executives who depend on two-way radio for their daily operations. You may even be tapped for a big job working for one of the two-way radio manufacturers in field service, factory quality control, or laboratory research and development.

#### How To Get Started

How do you break into the ranks of the big-money earners in two-way radio? This is probably the best way:

1. Without quitting your present job, learn enough about electronics fundamentals to pass the Government FCC Exam and get your Commercial FCC License.
2. Then get a job in a two-way radio service shop and "learn the ropes" of the business.
3. As soon as you've earned a reputation as an expert, there are several ways you can go. You can move *out* and start signing up and servicing your own customers. You might become a franchised service representative of a big manufacturer and then start getting into two-way radio sales, where one sales contract might net you \$5,000. Or you may even be invited to move *up* into a high-prestige

FCC Form 708-A

**The United States of America**  
**FEDERAL COMMUNICATIONS COMMISSION**  
**RADIO TELEPHONE OPERATOR LICENSE**  
**FIRST CLASS**  
 (General Radiotelephone Certificate)

*This certifies that* TUMMY WILLIS JUFFY **EN**  
 IS A LICENSED RADIO OPERATOR AUTHORIZED SUBJECT TO ANY SPECIAL ENDORSEMENT # 1 TO OPERATE THE CLASSES OF LICENSED RADIO STATIONS FOR WHICH THIS CLASS OF LICENSE IS VALID UNDER THE ORDINANCES, RULES AND REGULATIONS OF THE FEDERAL COMMUNICATIONS COMMISSION, ANY STATUTE OF THE UNITED STATES AND ANY TREATY TO WHICH THE UNITED STATES IS A PARTY. THIS LICENSE IS GRANTED UNDER THE AUTHORITY OF THE COMMUNICATION ACT OF 1934, AMENDMENTS AND THE TERMS AND CONDITIONS THEREOF AND OF ALL LEGISLATIVE ACTS, EXECUTIVE ORDERS AND DECREES TO WHICH THE UNITED STATES IS A PARTY AND ALL ORDERS, RULES AND REGULATIONS OF THE FEDERAL COMMUNICATIONS COMMISSION WHICH ARE BINDING UPON RADIO OPERATORS ARE MADE A PART HEREOF AS THOUGH SPECIFICALLY SET OUT IN FULL HEREIN. NEITHER THIS LICENSE NOR THE RIGHTS CERTIFIED TO BEHEREIN SHALL BE REPRODUCED OR OTHERWISE TRANSFERRED TO ANY OTHER PERSON.

PLACE AND DATE OF ISSUANCE: BUFFALO, NEW YORK SEPTEMBER 11, 1963  
 DATE AND TIME OF EXPIRATION: SEPTEMBER 11, 1974 AT THREE O'CLOCK P.M. EASTERN STANDARD TIME  
 SPECIAL ENDORSEMENT: OPERATOR ENDORSEMENT - SEPTEMBER 11, 1963 - BUFFALO, NEW YORK

*Tummy Willis Juffy*  
 Licensee

*John P. Waples*  
 Chief, Radio Division  
 Federal Communications Commission

NOT VALID UNTIL SIGNED

**THIS COULD BE YOUR "TICKET" TO A GOOD LIVING.** You must have a Commercial FCC License to service two-way radios. Two out of three men who take the FCC exam flunk it... but nine out of ten CIE graduates pass it the first time they try!

salaried job with one of the major manufacturers either in the plant or out in the field.

The first step—mastering the fundamentals of Electronics in your spare time and getting your FCC License—can be easier than you think.

Cleveland Institute of Electronics has been successfully teaching electronics by mail for over thirty years. Right at home, in your spare time, you learn electronics step by step. Our AUTO-PROGRAMMED™ lessons and coaching by expert instructors make everything clear and easy, even for men who thought they were "poor learners." You'll learn not only the fundamentals that apply to all electronics design and servicing, but also the specific procedures for installing, troubleshooting, and maintaining two-way mobile equipment.

#### Get Your FCC License... or Your Money Back!

By the time you've finished your CIE course, you'll be able to pass the FCC License Exam with ease. Better than nine out of ten CIE-trained men pass the FCC Exam the first time they try, even though two out of three non-CIE men fail. This startling record of achievement makes possible the famous CIE

warranty: you'll pass the FCC Exam upon completion of your course or your tuition will be refunded in full.

Ed Dulaney is an outstanding example of the success possible through CIE training. Before he studied with CIE, Dulaney was a crop duster. Today he owns the Dulaney Communications Service, with seven people working for him repairing and manufacturing two-way equipment. Says Dulaney: "I found the CIE training thorough and the lessons easy to understand. No question about it—the CIE course was the best investment I ever made."

Find out more about how to get ahead in all fields of electronics, including two-way radio. Mail the bound-in postpaid reply card for two FREE books, "How To Get A Commercial FCC License" and "How To Succeed In Electronics." If card has been removed, just send us your name and address on a postcard.

#### ENROLL UNDER NEW G.I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, OR are in service now, check box on reply card for G.I. Bill information.

**CIE** Cleveland Institute of Electronics  
 1776 E. 17th St., Dept. RE-38, Cleveland, Ohio 44114

A Leader in Electronics Training... Since 1934 • Accredited Member National Home Study Council




# Remote-Reading Field Meter

## PARTS LIST

- C1—air trimmer, 3–32 pF (E. F. Johnson 160-130 or equivalent)
- C2, C3, C4—.0012  $\mu$ F, disc ceramic
- C5—1  $\mu$ F, 25 volts, electrolytic
- R1—pot, 1 meg, linear taper
- R2, R3—1,500 ohms, 1/2 watt
- R4—pot, 25K, linear taper
- J1, J2, J3, J4—insulated banana jacks, 2 red, 2 black (H. H. Smith 205 or equivalent)
- J5—phone jack
- Q—pnp general-purpose audio transistor (RCA SK3009 or equivalent)
- M—meter, 0–500  $\mu$ A (Monarch PMC-5S)
- S—dpdt slide switch
- RFC—rf choke, 0.5 mH (National R50)
- D—1N34A general-purpose diode
- BATT—2 penlight cells, 1 1/2 volts, AA size
- Detector box—metal, 1 5/8 x 2 1/8 x 4 inches (Bud CU2101A)
- Indicator box—metal, 2 1/8 x 5 1/4 x 3 inches (Bud CU2106A)
- Miscellaneous—4 banana plugs to match jacks, phone jack, knobs, wire and screws, and 1 feedthrough insulator (E. F. Johnson 135-50 or equivalent)
- Coil data (L):
  - 3.0 to 5.0 MHz—73- $\mu$ H peaking coil (J. W. Miller 6172 or equivalent)
  - 4.2 to 7.5 MHz—36- $\mu$ H peaking coil (J. W. Miller 6176)
  - 7 to 14 MHz—10- $\mu$ H rf choke (J. W. Miller 4612 or equivalent)
  - 13 to 26 MHz—3.9- $\mu$ H rf choke (J. W. Miller 4608 or equivalent)
  - 25 to 55 MHz—10 turns No. 18 enamel wire, 3/4-in. diameter, self-supporting

Fig. 3—Indicator box holes must be cut carefully, especially the large meter hole.

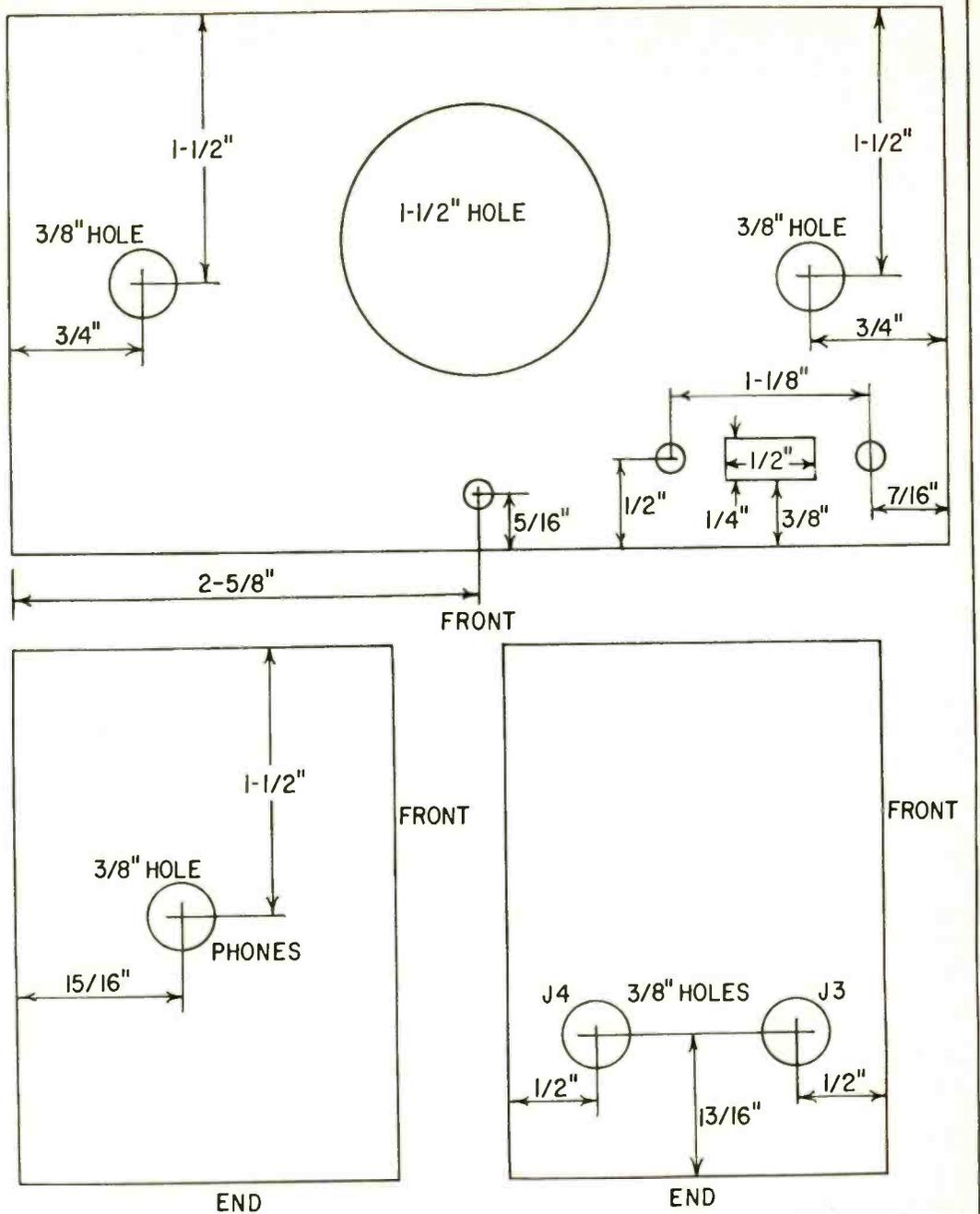


# WHAT'S YOUR EQ?

Conducted by E. D. Clark
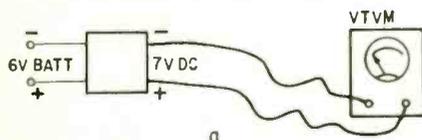
## Voltage Booster

The black box contains a single, common electronic component. It is not



a battery, has no moving parts, and does not oscillate. What is it?

—Richard P. Speck


Two puzzlers for the student, theoretician and practical man. Simple? Double-check your answers before you say you've solved them. If you have an interesting or unusual puzzle (with an answer) send it to us. We will pay \$10 for each one accepted. We're especially interested in service stinkers or engineering stumpers on actual electronic equipment. We get so many letters we can't answer individual ones, but we'll print the more interesting solutions—ones the original authors never thought of.

Write EQ Editor, Radio-Electronics, 154 West 14th Street, New York, N. Y. 10011.

Answers to this month's puzzles are on page 93.

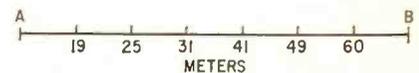
## Shifted Tuning

The dial of a shortwave receiver is shown. A is the high-frequency end; B is the low-frequency end. When tuning from A to B, stations are received at



indicated frequencies. Yet when tuning from B to A, stations are shifted to the left. There is no slip or backlash. What causes the shift?

—C. S. S. Sheno

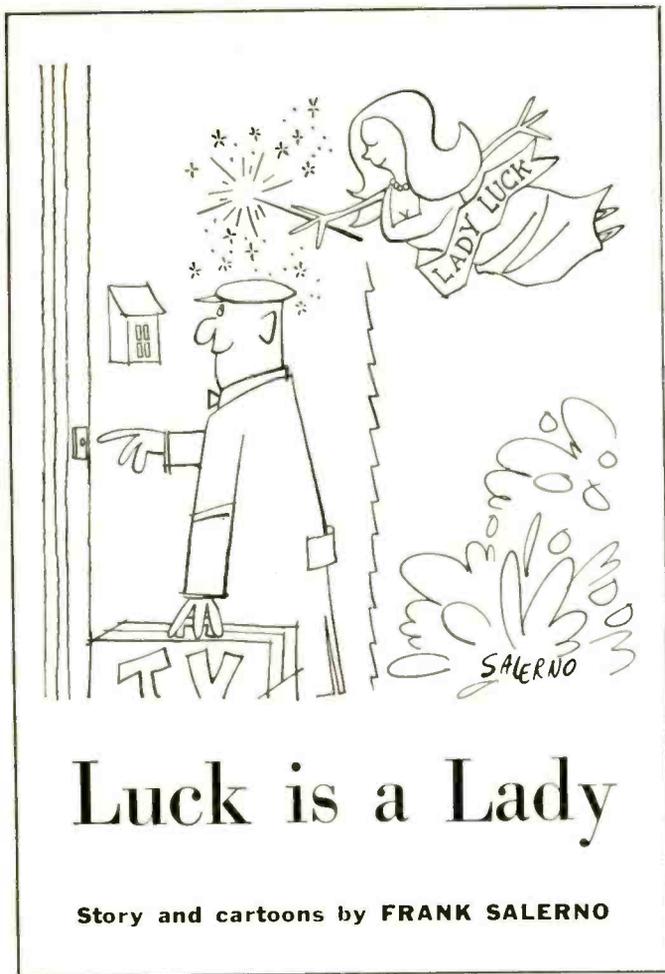

# Luck is a Lady


Story and cartoons by **FRANK SALERNO**

A LITTLE LUCK GOES A LONG WAY IN TV SERVICING. THERE come those trying times when all skill fails and we must pray for the deliverance of luck. And in our business we find ourselves praying more and more each day.

Take, for instance, the RCA KCS68C that I serviced recently. No picture. It didn't take long to see that the fly-back transformer looked like a lump of coal. The customer told me that three flybacks had been replaced in this set in as many years and he begged me to find the cause of these costly breakdowns. I promised to do my best.

When I installed the new part in the shop, I gave the horizontal sweep section a complete voltage and current check. Everything looked fine. All voltages throughout the system checked good and 6CD6 cathode current was a respectable 120 mA. I set up all the sweep adjustments according to the manufacturer's recommendations, including horizontal width for slight overscan and linearity for minimum circuit current. So far as I could see, the receiver was in perfect shape and ready for delivery. But I wasn't pressed to return it, so I decided to cook it for a couple of days just to be sure.

Next morning I was lucky enough to catch a test pattern on the air, which gave me a chance to make a few finer adjustments. Lucky for me because I noticed something that was not perceptible when I checked the set against a regular TV program the day before. I adjusted the circles to a 1/4-inch overscan on each side, turned away to some other work. When I looked back 5 minutes later the pattern had stretched away out. This seemed odd. I cooled the set down and tried again. Sure enough, the same thing happened

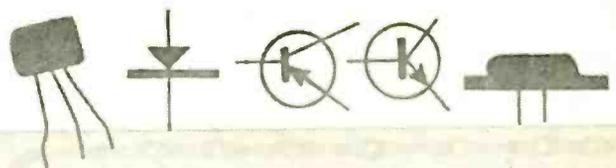

## TEST TRANSISTORS IN SECONDS in-circuit

TR139  
**89<sup>50</sup>**



Also check all  
transistors, diodes,  
and rectifiers out  
of circuit for true AC beta  
and Icbo leakage.

**Your best answer for solid state servicing, production line testing, quality control and design.**

Sencore has developed a new, dynamic in-circuit transistor tester that really works—the TR139—that lets you check any transistor or diode in-circuit without disconnecting a single lead. Nothing could be simpler, quicker or more accurate. Also checks all transistors, diodes and rectifiers out of circuit.

**BETA MEASUREMENTS**—Beta is the all-important gain factor of a transistor; compares to the gm of a tube. The Sencore TR139 actually measures the ratio of signal on the base to that on the collector. This ratio of signal in to signal out is true AC beta.

**ICBO MEASUREMENTS**—The TR139 also gives you the leakage current (Icbo) of any transistor in microamps directly on the meter.

**DIODE TESTS**—Checks both rectifiers and diodes either in or out of the circuit. Measures the actual front to back conduction in micro-amps.

**COMPLETE PROTECTION**—A special circuit protects even the most delicate transistors and diodes, even if the leads are accidentally hooked up to the wrong terminals.

**NO SET-UP BOOK**—Just hook up any unknown transistor to the TR139 and it will read true AC beta and Icbo leakage. Determines PNP or NPN types at the flick of a switch.

Compare to laboratory testers costing much more. . . . \$89.50

See America's Most Complete Line of Professional Test Instruments — At Your Distributor Now.



NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

**SENCORE**

426 SOUTH WESTGATE DRIVE, ADDISON, ILLINOIS 60101

Circle 25 on reader's service card

# NEW! LAFAYETTE HB-525B Solid State 2-Way Radio

WITH "S/PRF" Meter



99-3144WX\*

- Size: 2<sup>3</sup>/<sub>8</sub>" by 6<sup>1</sup>/<sub>4</sub>"

**149<sup>95</sup>**

## 23 CB Crystal Controlled Channels All Crystals Supplied

- 19 Transistors, 9 Diodes, Thermistor
- Dual Conversion Receiver for Extra Selectivity and Sensitivity
- Full 5-Watt Input
- Range Boost™ Circuitry for Added Power
- 3-Position Delta Tune—Provides Accurate Fine Tuning
- Mechanical 455KC Filter for Superior Selectivity
- Push-to-Talk Dynamic Microphone
- Variable Squelch plus Series Gate Automatic Noise Limiting
- Public Address System (with external speaker)
- 12-Volt DC Operation (pos. or neg. ground) 6-Volt DC (with optional DC Power Supply)
- Accepts Priva-Com® Plug-in Tone Caller

\*Imported



**FREE**

JUST OFF PRESS!

1968

**CATALOG 680**

Over 500  
Pages

Featuring Everything in Electronics for

• HOME • INDUSTRY • LABORATORY

from the "World's Hi-Fi & Electronics Center"

LAFAYETTE Radio ELECTRONICS  
Dept. JH-7 P.O. Box 10  
Syosset, L. I., N. Y. 11791

Send me the FREE 1968 Lafayette Catalog 680

JH-7

Name .....

Address .....

City ..... State ..... Zip .....

Circle 26 on reader's service card

## LUCK IS A LADY

a second time. The picture came on normally and, within 5 minutes, began to expand. There was no blooming or loss of brightness—just a 2-inch stretch on each side.


I now had to reconsider a fact that had seemed peculiar to me when I had first noticed it, but since everything else had fallen so neatly into place I had mistakenly ignored it. While screwing the width-coil slug in from end to end on the day before, I found it gave me a large peak, a sudden dip and then another peak. We're all familiar with adjustable coils having two peaks. Although I had never known a width coil to have more than one, I passed this off as a first-time-for-everything kind of thing.

Now, in view of the new problem, I looked closer at the width coil. When the picture stretched out, it was easy to restore it to normal size by readjusting the width, but then the predictable happened. When the receiver was turned on from a cold start, the test pattern was 2 inches short on each side of the screen.

My first step, of course, was to try a new coil, but that didn't help. I checked all the capacitors in the width and yoke circuits but results were still negative. After hours of time-consuming tests I couldn't find any reason for the picture to behave that way. Actually, I could easily have got by with the condition had I delivered the receiver, because it was not noticeable on a regular TV program. But I was convinced that whatever was causing this unusual behavior was related to the high failure rate of the flybacks. I kept on looking.

It was at this point that Lady Luck stepped in and tapped me with a wonderful stroke—in disguise. As I tuned and retuned the width coil I found a new problem. I began to get flashover under one of the two 6W4-GT sockets. The way the chassis was lying, I couldn't see exactly where the arcing came from, but as I tuned the coil in and out, looking for that one reliable setting, the flashover would break out intermittently. For one brief moment the arcing sustained



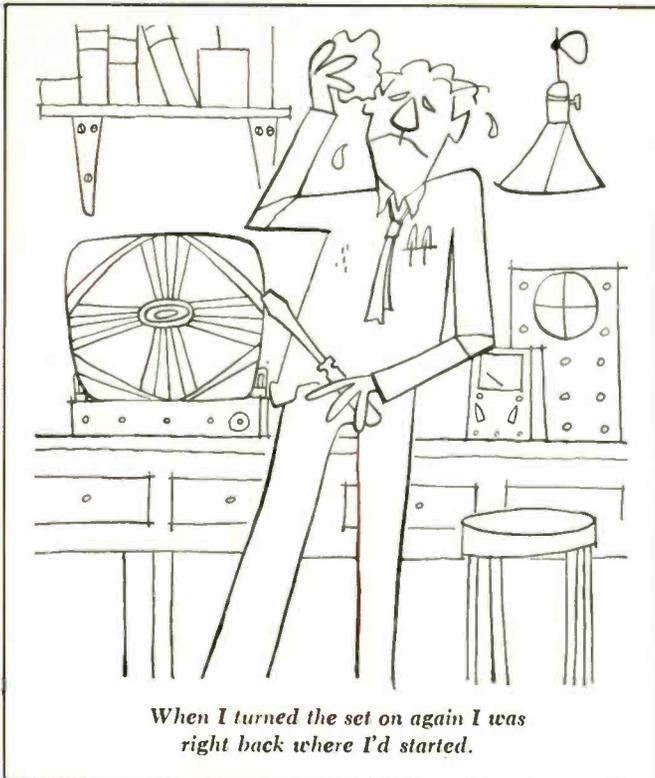


When I turned the set on again I was right back where I'd started.

itself long enough for me to discover that I suddenly lost the double width peaks. I went from maximum to minimum inductance with the coil slug and got the normal minimum to maximum to size—without the dip!


It was time to find out just what was going on under that 6W4 socket. I opened up the high-voltage cage for a better look. There, between pins 2 and 3 of the socket, was a beautiful carbon path. Pin 2 seemed to be used only as a tie point for a capacitor and a wire, so I simply clipped the pin off the socket and taped it. When I turned the set on again, I was right back where I had started. The width coil got back its two peaks and its associated stretch problem.

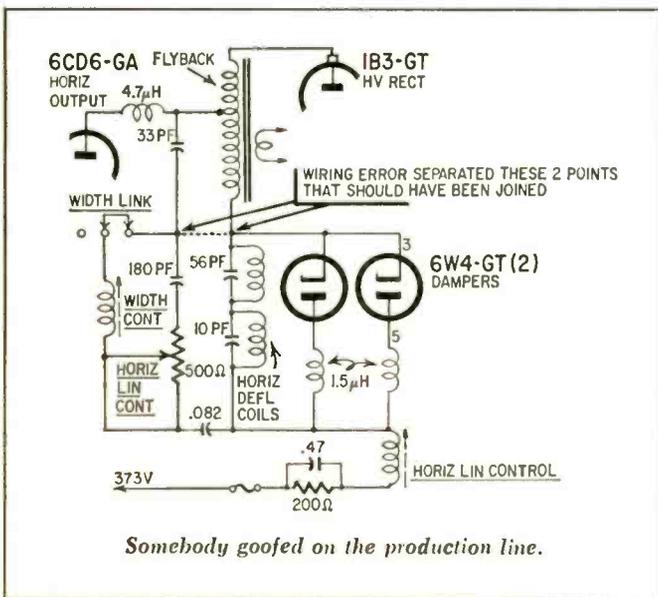But Lady Luck had flirted with me and I chased her. What had happened in that brief moment when the arcing



Somebody goofed on the production line.

# GAS WELDING TORCH

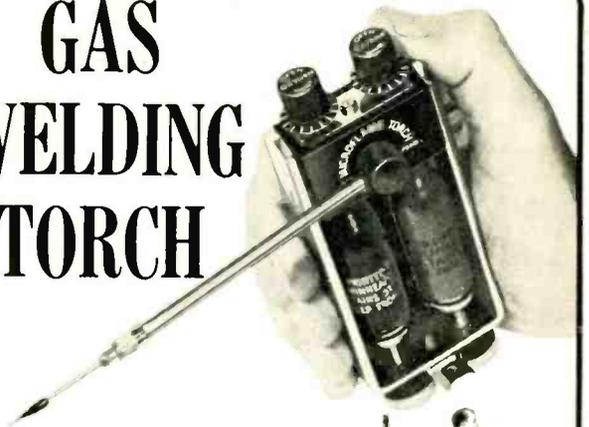

Uses **OXYGEN** and **LP GAS**

- Completely self-contained.
- Produces 5000° pin-point flame.
- Welds, brazes, solders.
- Hundreds of lightweight uses.
- Suggested list — \$19.95.

GET COMPLETE DETAILS AT MOST INDUSTRIAL DISTRIBUTORS, OR WRITE TO MICROFLAME, INC.



HOME WORKSHOP



TECHNICIANS



REPAIR AND SERVICE SHOPS

**MICROFLAME, INC.**

7800 COMPUTER AVENUE  
MINNEAPOLIS, MINNESOTA 55424

Circle 27 on reader's service card

Designed and manufactured in U.S.A.

## NEVER A BURNOUT

IN 6 EMC **DIODE-PROTECTED** VOMS



NOBODY ELSE BUT EMC DESIGNS IN SO MUCH VALUE!  
• Professional quality and versatility • Lifetime protection against electrical abuse • No meter burn-out, needle damage, or fuse replacement

### VOLOMETER

Model 109A Factory Wired & Tested \$28.95  
Model 109AK Easy-to-Assemble Kit \$21.15

20,000 Ω/v DC sens. 10,000 Ω/v AC sens. 4 1/2", 40µa meter. High impact bakelite case. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 3 DC current ranges: 0-30-300ma; 0-3A. 3 resistance ranges: 0-20K, -200K, -20 megs. 5 db ranges: -4 to +67db. With carrying strap. 5 1/4" W x 6 3/4" H x 2 7/8" D.

### VOLOMETER

Model 103A Factory Wired & Tested \$20.75  
Model 103AK Easy-to-Assemble Kit \$16.80

4 1/2", 2% accurate, 800µa D'Arsonval type meter. One zero adjustment for both resistance ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 db ranges: -4 to +64db. 5 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-120ma; 0-1.2A. 2 resistance ranges: 0-1K, 0-1 meg. 5 1/4" W x 6 3/4" H x 2 7/8" D.

### POCKET SIZE VOLOMETER

Model 102A Factory Wired & Tested \$16.95  
Model 102AK Easy-to-Assemble Kit \$14.40

3 1/2", 2% accurate 800µa D'Arsonval type meter. One zero adj. for both res. ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 3 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-130ma; 0-1.2A. Resistance: 0-1K, 0-1 meg. 3 3/4" W x 6 1/4" H x 2" D.

EMC, 625 Broadway, New York 12, N.Y.

Send me **FREE** catalog of the complete value-packed EMC line, and name of local distributor.

NAME \_\_\_\_\_ RE-8


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

# EMC

ELECTRONIC MEASUREMENTS CORP.  
625 Broadway, New York 12, New York  
Export: Pan-Mar Corp., 1270 B'way, N.Y. 1

## LUCK IS A LADY

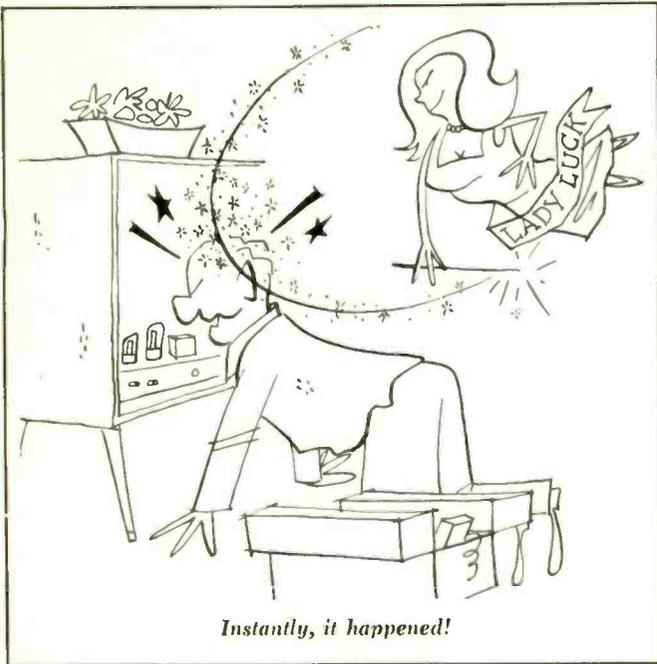

sustained itself and the whole system snapped to normal? I read the schematic and I looked at the wiring. I looked at the wiring and I read the schematic. Very gradually the webs parted and the fog lifted. It all suddenly became clear. The wire and capacitor that had been soldered to pin 2 of the 6W4 socket and that had so obligingly arced over for me were

supposed to be connected to pin 3, the damper cathodes. It was a wiring error right from the factory and had gone unnoticed all these years. The partial schematic shows how easily it defied discovery. Neither voltage nor resistance measurements could unearth it—only an amazing stroke of luck like a compassionate little flashover. When the wiring was corrected, the problem vanished.

Of course, Miss Luck has many varied ways of presenting her lovely self, and, Lord knows, she's always welcome.

An old customer of mine owns an F4632 Philco. He'd been having sound trouble with it for the better part of a year. The complaint had always been the same—volume would drop for a while, rise again, drop and rise. This might happen for a week straight and then not happen for a month. Every time I made a service call the set worked fine but, despite a whole new set of audio tubes, I continued to receive complaints. I finally took the chassis to the shop.

As you'd expect, the sound worked perfectly for 3 days. Out of sheer desperation, I replaced both the sound takeoff and sound detector transformers, checked the set out for another couple of days and delivered the chassis.


I was hoping for the best, to be sure, but I was worried. These repair jobs where nothing concrete is established hardly ever work out well. Nevertheless, I finished screwing down the back cover while listening to a program, still trying to find that one missing clue before leaving.

Instantly, it happened! The sound shot down and at last I knew why. It was while tightening the last screw that my hand brushed the rear-mounted TV-phono switch and the volume went down to a whisper. I merely touched the switch again with my forefinger and the volume shot up to normal. I sprayed some contact cleaner into the switch and the trouble was gone.

Once more, that ageless beauty, Lady Luck, saved the day and my sanity. END

For all your field servicing requirements . . .
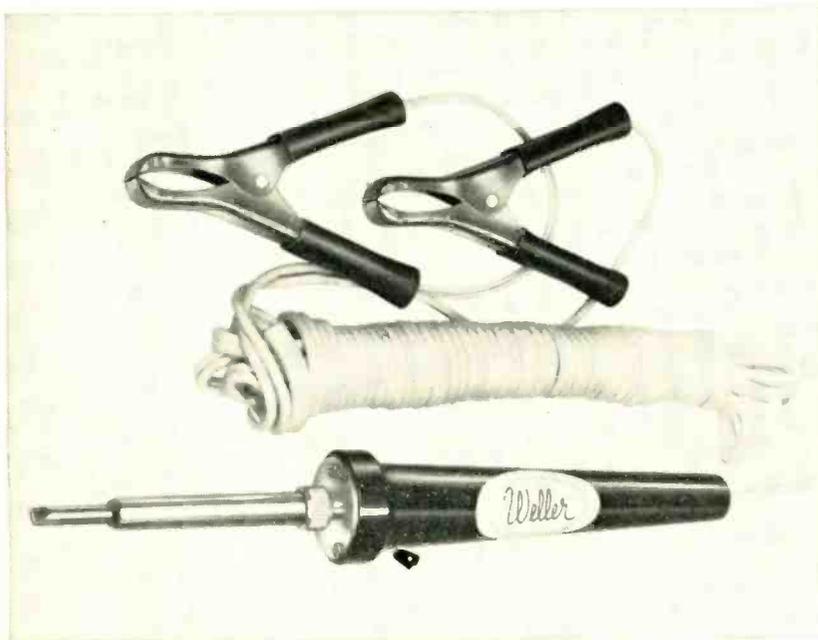
## New *Weller*® battery operated soldering iron with tip temperature control



Here's a new Weller light-weight soldering iron that operates from any 12-volt battery or 12-14 volt AC/DC power supply. Meets all your needs in mobile communications soldering—in automotive, marine, aircraft and many other applications. Features Weller's patented "Temperature Sensing" system. Tip temperature is controlled at 700° F. Iron offers minimal power drain, long life, rapid recovery. 12-ft. power cord includes battery **\$14.60**<sub>list</sub> clips. Model TCP-12.

Also available for 24-48 volt operation. Model TCP-24.

AT YOUR ELECTRONICS PARTS DISTRIBUTOR  
**WELLER ELECTRIC CORP., Easton, Pa. WORLD LEADER IN SOLDERING TECHNOLOGY**

Circle 29 on reader's service card

## EQUIPMENT REPORT

### A Cartridge and a Record to Test It Shure V-15 Type II

Circle 23 on reader's service card

THE WORLD OF HIGH FIDELITY HAS ALWAYS been one of JND's, as the psychologist would say: just-noticeable differences. They add up, of course; recorded music does sound a lot better now than it did 15 or 20 years ago, when hi-fi began being an industry.

Still, within any given year's worth of new products, it is usually impossible to point honestly to a particular component and say, "There! That one is worlds better than the others." This makes things difficult for the audio reviewer. The outcome is too often a nit-picking review that either discourages lengthily on altogether irrelevant matters like the finish of the tone-arm shell, or a review in which the lack of any discernible difference is painted over with a coat of adjectives.

Now Shure Bros. has brought out a new cartridge that once more represents a small improvement overall—but the improvement is definite and specific. This new pickup is a revised version of the respected plain V-15.

The design process for the V-15 Type II seems to have been about as scientific as cartridge design can be. Shure amassed a collection of records that had been found hard to trace—records that at some point caused the stylus to lose contact with the groove wall and produce very audible distortion. They found that these records had peak groove velocities beyond the ability of then-available pickups to follow. There was nothing actually *wrong* with the recordings; they just demanded too much. The maximum velocities on such records were determined and used as a design criterion.

Shure's engineers decided to build a cartridge that would trace grooves with such abnormally high peak velocities, instead of simply lowering tip mass and increasing compliance on the assumption that those are always Good Things to do.

It turned out that the interlocking of variables was so complex that calculating them was beyond practical limits of time and manpower. Shure used an analog computer to generate an electrical model (analog) of a proposed design. It thus became practical to vary parameters like tip mass, stylus velocity, compliance of the moving assembly, and so forth, without building an endless number of real cartridges. (There are

easily a dozen interdependent variables, depending on what you count in and what you ignore.)

The result was the V-15 Type II, and it really works. To prove it, Shure produced a recording, called "An Audio Obstacle Course" (\$3.95 postpaid from Shure Bros. Inc., 222 Hartrey Ave., Evanston, Ill. 60204). The record immediately aroused people's suspicions: how could they be sure it wasn't doctored to favor the new cartridge? Well, I have demonstrated to my own satisfaction that it's an honest job. I have played the Obstacle Course with the new Shure pickup and with others. I have also played "problem" recordings of music with the new pickup and with others, including Shure's older V-15.

The new cartridge definitely does trace high-velocity grooves better than anything else I've used. The improvement is most noticeable on recordings with much high-frequency percussive material: harpsichord, guitar and banjo, cymbal clashes and such; but it is clearly apparent also in music for brass instruments.

You can buy the record and try it for yourself. I won't dwell on what to listen for, since the printed matter with the record explains that very well. Most of the material on the record is brief musical passages played by various "difficult" instruments. The passages are repeated four times, each run 4 dB higher than the preceding one.

The highest-level passage cannot be traced by most cartridges without increasing the stylus force well above the specified figure. The sound becomes harsh and gritty, or there comes a knocking or chattering noise on top of the music, depending on the type of recorded material and on the degree to which the stylus fails to follow the groove. (Shure warns that the Obstacle Course should not be played more than 10 times with "ordinary" cartridges, else the high frequencies will be erased permanently. Lots of pickups shouldn't be used on this record at all.)

The sound of the V-15 II is clear and colorless overall, as good as any I've heard. That far, it isn't substantially different from a lot of other good pickups. Where it shines is on recordings that have much of the high-velocity material we've been talking about. Whether the new V-15 is worth the money (\$67.50) to you depends on how fussy you are and how much you value your records. If you do own records that have stung you with harsh breakup noises at high levels, the Shure V-15 Type II may solve your problem.—Peter E. Sutherland END

## new Sams books


### Audio Amplifier Design

by *Farl J. Waters*. Written for the audio enthusiast interested in designing his own amplifiers, either single-stage or for a complete multistage stereo system. Explains the theory of each stage; then illustrates design methods through an example showing how component values may be determined; finally, an actual design problem is undertaken and solved. Those readers who have an aversion to mathematics will welcome the generous use of nomographs throughout the book. Through their use, problems can be solved easily by simply placing a straightedge across appropriate values. 160 pages; 5½ x 8½". Order 20560, only. \$425


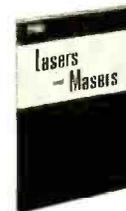
### Lasers and Masers

by *Charles A. Pike* (under the direction of *Training and Retraining, Inc.*). This programmed text describes the basic operating principles of the laser and maser, and details the characteristics of representative types. As new types make their appearance, the same basic principles will continue to apply. Physics is introduced only to the extent required to understand the subject. Includes the early history and development of the atomic structure upon which laser and maser devices are based. Questions and answers for study and review purposes are included at the close of each topic. 176 pages; 5½ x 8½". Order 20559, only. \$495



### Hi-Fi Stereo Handbook, Revised

by *William F. Boyce*. You'll find all the information you want on hi-fi and stereo in this completely updated third edition of the classic book on high-fidelity. Includes new material on stereo needles, headphones, adapter circuits, tape-cartridge players, and multiplex operation. Covers a number of new transistor circuits, including preamps, amplifiers, and stereo control circuits; includes new information on recording techniques, compact hi-fi systems, and multipath-checking equipment. The ideal reference guide for everyone interested in high-fidelity sound. 288 pages; 5½ x 8½". Order 20565, only. \$495



### 101 Ways to Use Your Ham Test Equipment, 2nd Ed.

by *Robert G. Middleton*. This practical handbook encourages the ham to explore the total possibilities of his test equipment. Describes how to save time using basic ham test instruments and how to avoid trial-and-error experimentation. Covers the use of dip meters, antenna impedance meters, vom's and vtvm's, scopes, reflected-power and swr meters, and bridges. Describes proper test setups, procedures, and how to evaluate test results. Fully illustrated. 160 pages; 5½ x 8½". Order 20566, only. \$295

### Handbook of the Elements

by *Samuel Ruben*. An invaluable reference about the chemical elements for students and engineers. The 25 physical and chemical constants referred to most frequently are given for each element. Nine of these are summarized at the top of the page devoted to each element. The atomic structures of the 104 elements are sufficiently detailed to serve as a reference for advanced research. Equivalent names are given in Spanish, French, German, Russian, Hebrew, Japanese, and Chinese. 128 pages; 5½ x 8½". \$325 comb-bound. Order 20563, only.

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor . . .

HOWARD W. SAMS & CO., INC.  
4300 WEST 82nd ST. • INDIANAPOLIS, INDIANA  
Circle 30 on reader's service card

## RADIO-ELECTRONICS READER'S SERVICE

Here's how you can get manufacturers' literature fast:

1. Tear out the post card on the facing page. Clearly print or type your name and address.

**Include zip code! Manufacturers will not guarantee to fill your requests unless your zip code is on the reader service card!**

2. Circle the number on the card that corresponds to the number appearing at the bottom of the **New Products, New Literature or Equipment Report** in which you are interested.

For literature on products advertised in this issue, circle the number on the card that corresponds to the number appearing at the bottom of the advertisement in which you are interested. Use the convenient index below to locate quickly a particular advertisement.

3. Mail the card to us (no postage required in U.S.A.)

**Advertisements in this issue offering free literature (see the advertisements for products being advertised):**

ANTENNA SPECIALISTS CO. (DIV. OF DYNASCAN INDUSTRIES, INC.) (Pg. 27)	Circle 22
BROOKS RADIO & TV CORP. (Pg. 90-91)	Circle 120
BURSTEIN-APPLEBEE (Pg. 85)	Circle 118
CASTLE TV TUNER SERVICE, INC. (Pg. 75)	Circle 106
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 26)	Circle 21
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 62-65)	Circle 24
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 91)	Circle 121
CORNELL-DUBILIER (Third Cover)	Circle 149
CORNELL ELECTRONICS CO. (Pg. 98)	Circle 146
DELTA PRODUCTS, INC. (Pg. 16)	Circle 16
DEVRY INSTITUTE OF TECHNOLOGY (Pg. 5)	Circle 9
EDMUND SCIENTIFIC CORP. (Pg. 97)	Circle 144
ELECTRO-VOICE, INC. (Pg. 15)	Circle 15
FINNEY CO. (Pg. 81)	Circle 113
GC ELECTRONICS CO. (Pg. 14)	Circle 14
HALLICRAFTERS (Pg. 12)	Circle 12
HEALD ENGINEERING COLLEGE (Pg. 93)	Circle 124
HEATH CO. (Pg. 23)	Circle 19
INTERNATIONAL CRYSTAL MFG. CO., INC. (Pg. 100)	Circle 148
JUDSON RESEARCH AND MFG. CO. (Pg. 76)	Circle 108
LAFAYETTE RADIO ELECTRONICS (Pg. 68)	Circle 26
MALLORY DISTRIBUTOR PRODUCTS CO. (DIV. OF P. R. MALLORY & CO., INC.) (Pg. 13)	Circle 13

### HELP US COMPLETE THE PROFILE OF OUR READERS!

At the bottom of the Reader's Service Card, you'll find numbers from 1 through 6. Circle the numbers on the Reader's Service Card to indicate which of the following types of Magazines Read

- 1 Electronic Technician or PF Reporter
- 2 Electronic Design or Electronics
- 3 Popular Electronics or Electronics Illustrated
- 4 Hi-Fi Stereo Review or High Fidelity
- 5 Popular Photography or Modern Photography
- 6 Popular Science or Popular Mechanics

MEMORY STUDIES (Pg. 75)	Circle 107
MICROFLAME, INC. (Pg. 69)	Circle 27
MOSLEY ELECTRONICS, INC. (Pg. 83)	Circle 114
MULTICORE SALES CORP. (Pg. 90)	Circle 119
MUSIC ASSOCIATED (Pg. 93)	Circle 122
NOVA-TECH, INC. (Pg. 80)	Circle 112
OLSON ELECTRONICS, INC. (Pg. 76)	Circle 109
PACE COMMUNICATIONS CORP. (Pg. 84)	Circle 115
POLYPAKS (Pg. 99)	Circle 147
RADIO SHACK (Pg. 1)	Circle 8
SAMS & CO., INC., HOWARD W. (Pg. 71)	Circle 30
SENCORE (Pg. 67)	Circle 25
SENCORE (Pg. 89)	Circle 116
SOLID STATE SALES (Pg. 96)	Circle 143
SONOTONE CORP. (ELECTRONIC APPLICATIONS DIV.) (Pg. 93)	Circle 123
SPRAGUE PRODUCTS CO. (Pg. 77)	Circle 110
SURPLUS CENTER (Pg. 80)	Circle 111
SYLVANIA (SUBSIDIARY OF GENERAL TELEPHONE & ELECTRONICS) (Pg. 24-25)	Circle 20
TRIPLETT ELECTRICAL INSTRUMENT CO. (Second Cover)	Circle 7
WARREN ELECTRONIC COMPONENTS (Pg. 97)	Circle 145
WELLER ELECTRIC CO. (Pg. 70)	Circle 29
XCELITE, INC. (Pg. 22)	Circle 18

# NEW PRODUCTS

More information on new products is available free from the manufacturers of items identified by a Reader's Service number. Turn to the Reader's Service Card facing page 72 and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.




**12-CHANNEL CB RADIO, Auto-Mate.** Solid-state. 5 W. Transmitter/converter uses conventional auto radio and antenna for reception. Transmits up to 10 miles. Includes built-in antenna matching network. Channel-9 crystal installed. \$69.95—Pace Communications Corp.

Circle 46 on reader's service card



**TUBE TESTER, TC142 Mighty Mite V.** Tests over 3,000 tube types. Horizontal in-line switch arrangement. Sensitivity, 100 megohms. Includes setup booklet. \$74.50—Sencore

Circle 47 on reader's service card

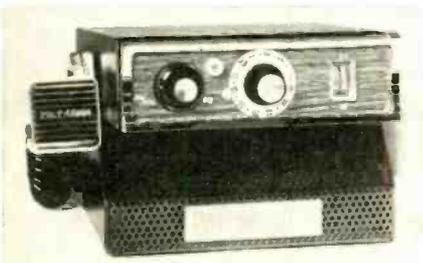

**23-CHANNEL TRANSCEIVER, Poly-Comm 23C.** Solid-state. Sensitivity, .05  $\mu$ V at 2:1 s/n, .12  $\mu$ V at 10:1 s/n.

Audio response, 6 dB from 350 to 3,000 Hz. Output, 3 W. Floating, series-gate type noise limiter. *Poly-Call Tone Alert* can be attached. \$199.50—Polytronics


Circle 48 on reader's service card

**BURGLAR-ALARM KIT.** For autos, trucks. High-pitched siren sounds when trunk, hood or doors are opened. Includes No. 10 siren, relay, pick-proof key-lock



switch, lock cover, in-line fuse, 6 door switches, 2 switch brackets, wire, terminals, screws, instructions.—Jubilee Mfg. Co.

Circle 49 on reader's service card

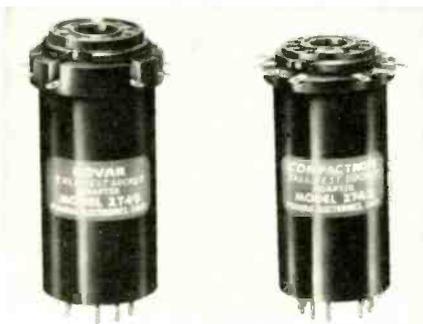

**TEST SOCKET ADAPTERS, 9-Pin Novar, model 2749; 12-Pin Compactron, model 2742.** For test measurements from tube sockets equipped with captive or telescoping tube shields. Adapters tall enough to rise above top of tube shields. Model 2749, \$3.25, model 2742, \$3.55.—Pomona Electronics

Circle 50 on reader's service card

**AMATEUR-BAND COMMUNICATIONS RECEIVER, Heathkit SB-301.** Covers 80- through 10-meter amateur bands for AM, CW, SSB and RTTY plus 15- to 15.5-MHz coverage for WWV reception. Automatic noise limiter. Front-panel switching. Crystal-controlled front

**COMPLETE TUNER OVERHAUL**

**9<sup>95</sup>**

**ALL LABOR AND PARTS (EXCEPT TUBES & TRANSISTORS)\***



  
VHF

  
UHF

  
COLOR

  
UV

  
TRANSISTOR

**COLOR TUNERS**      GUARANTEED COLOR ALIGNMENT — NO ADDITIONAL CHARGE

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days. UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only. Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.) And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

**CASTLE**  
TV TUNER SERVICE, INC.

5715 N. Western Ave., Chicago 45, Illinois  
41-96 Vernon Blvd., Long Island City 1, N. Y.

For service in Canada write to Chicago or use reader service card in this magazine.  
\*Major parts are charged extra in Canada.

Circle 106 on reader's service card

## Why Can't You Control Your Memory?

A noted publisher in Chicago reports there is a simple technique for acquiring a powerful memory which can pay you real dividends in both business and social advancement and works like magic to give you added poise, necessary self-confidence and greater popularity.

According to this publisher, many people do not realize how much they could influence others simply by remembering accurately everything they see, hear, or read. Whether in business, at social functions or even in casual conversations with new acquaintances, there are ways in which you can dominate each situation by your ability to remember.

To acquaint the readers of this publication with the easy-to-follow rules for developing skill in remembering anything you choose to remember, the publishers have printed full details of their self-training method in a new book, "Adventures in Memory," which will be mailed free to anyone who requests it. No obligation. Send your name, address, and zip code to: Memory Studies, 835 Diversey Parkway, Dept. 684-018, Chicago, Ill. 60614. A postcard will do.

Circle 107 on reader's service card

WE DON'T CLAIM  
OUR ELECTRONIC  
IGNITION SYSTEM  
IS BEST . . .



OUR  
CUSTOMERS DO!

WRITE TODAY FOR FREE LITERATURE

**JUDSON**

RESEARCH AND MFG. CO.  
CONSHOHOCKEN, PA., U.S.A.



Circle 108 on reader's service card

**Olson**



**FREE**

Fill in coupon for a FREE One Year Subscription to OLSON ELECTRONICS' Fantastic Value Packed Catalog—Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_  
GIVE ZIP CODE \_\_\_\_\_

If you have a friend interested in electronics send his name and address for a FREE subscription also.

**OLSON ELECTRONICS, INC.**

593 S. Forge Street Akron, Ohio 44308


Circle 109 on reader's service card

NEW PRODUCTS continued




end. Linear master oscillator. Sensitivity,  $\pm 0.3$  mV for 10 dB signal-plus-noise to noise ratio. SSB selectivity, 2.1 kHz. Optional filters for AM and CW. 23 lb. \$260—Heath Co.

Circle 51 on reader's service card

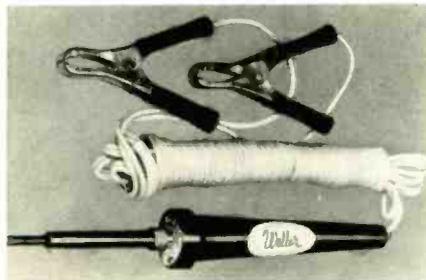

12-VOLT SOLDERING IRON, model TCP-12. Includes 12-ft power cord with battery clips, 700°F 3/16-in. screw-driver tip. Temperature control system minimizes battery drain.—Weller Electric

Circle 52 on reader's service card

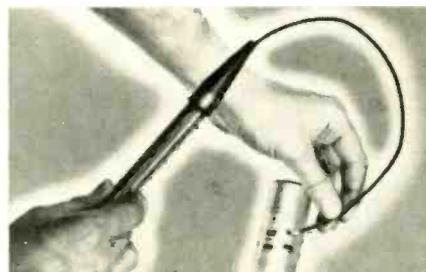

FLEXIBLE LIGHT, *Flexilight*, No. 60,648. Maximum bending radius of  $\frac{3}{4}$  in. Plastic fiber light guide couples to a rotary-switch penlight. \$2.75—Edmund Scientific Co.

Circle 53 on reader's service card



RECEIVER-TURNTABLE, model SC 6. Features AM, FM, FM/stereo with automatic switching circuit between FM and FM/stereo. Includes stereo head-


phone receptacle on front panel, tuning meter. Provision for tape recorder. Optional Lucite dust cover. \$239.50—Harman-Kardon, Inc.

Circle 54 on reader's service card



NEW COMPACT RECORDER, AG-500 series. Solid-state. Signal-to-noise ratio, 50-60 dB. Flutter, 0.25% rms at 3% ips max. Available in 1 channel, 2-channel stereo, 2-channel  $\frac{1}{4}$ -track stereo. \$1,200-1,524.—Ampex

Circle 55 on reader's service card

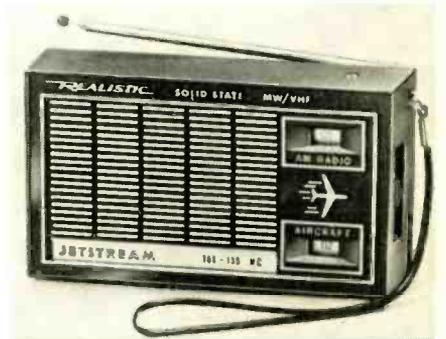

AM/VHF-AIR BAND POCKET PORTABLE, the *Jetstream*. AM broadcasts plus 108-135 MHz for aircraft, tower and weather transmissions. 6 x 3 $\frac{1}{2}$  x 1 $\frac{1}{2}$  in. 1 lb. Ac adapter available. \$21.95—Radio Shack


Circle 56 on reader's service card



BARRIER STRIP CONNECTOR, *Scotchflex* No. 515. For use with No. 500 flat cable in music, sound and low-voltage control systems. Foam adhesive backing. 4 openings. 10 per carton, 5 cartons per case.—Dept. EL 7-13, 3M Co.


Circle 57 on reader's service card

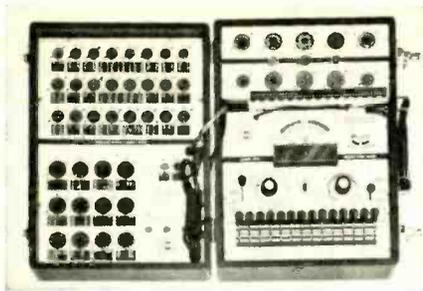PORTABLE TUBE TESTER, model 107-C. Features 6AF6G "eye" tube in shorts and grid-circuit tests. Constant-



voltage transformer. Features grid-circuit, dynamic-mutual-conductance and cathode-emission tests. 13 x 9 x 7 in. 115 Vac. \$198.50—Seco

Circle 58 on reader's service card

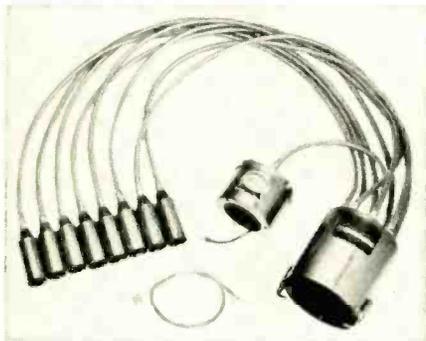

**INTERFERENCE KIT**, model HH-8. High-tension coil-to-distributor filter lead replaces existing lead. 8 filters snap in place between sparkplugs and leads. Moisture-proof, flashover-proof. \$12.95.—Hallett

Circle 59 on reader's service card



**COMBO ORGAN**, the *Rheem Mark VII*. Portable stereo. Features psychedelic sounds, bass fuzz. Provision for 192 electronic sound combinations. 16-ft solo stop, bass keyboard coupler to 7 full octaves, multitone booster, full-range variable vibrato, walking bass, bass boost. \$660—Rheem Musical Instruments

Circle 60 on reader's service card

**PORTABLE RADIO-CASSETTE PLAYER COMBINATION**, Model L573. AM-FM/AFC. Removable front panel, interchangeable mono and stereo cassettes,

# WHY risk your reputation with "just-as-good" capacitors?

When you pay little or no attention to quality in tubular replacement capacitors, you leave yourself wide open for criticism of your work . . . you risk your reputation . . . you stand to lose customers. It just doesn't pay to take a chance on capacitors with unknown or debatable performance records when it's so easy to get guaranteed dependable tubulars from your Sprague distributor!

## There's no "maybe" with these 2 great **SPRAGUE DIFILM® TUBULARS!**

The ultimate in tubular capacitor construction. Dual dielectric . . . polyester film and special capacitor tissue . . . combines the best features of both. Impregnated with HCX®, an exclusive Sprague synthetic hydrocarbon material which fills every void in the paper, every pinhole in the plastic film *before it solidifies*, resulting in a rock-hard capacitor section . . . there's no oil to leak, no wax to drip. Designed for 105°C (220°F) operation without voltage derating.

### DIFILM® ORANGE DROP® Dipped Tubular Capacitors



A "must" for applications where only radial-lead capacitors will fit . . . the perfect replacement for dipped capacitors now used in many leading TV sets. Double-dipped in rugged epoxy resin for positive protection against extreme heat and humidity. No other dipped tubular capacitor can match Sprague Orange Drops!



### DIFILM® BLACK BEAUTY® Molded Tubular Capacitors


The world's most humidity-resistant molded capacitors. Tough, protective outer case of non-flammable molded phenolic . . . cannot be damaged in handling or installation. Black Beauty Capacitors will withstand the hottest temperatures to be found in any TV or radio set, even in the most humid climates.

For complete listings, get your copy of Catalog C-617 from your Sprague distributor, or write to Sprague Products Company, 81 Marshall Street, North Adams, Massachusetts.

WORLD'S LARGEST MANUFACTURER OF CAPACITORS  
65-6110 R1



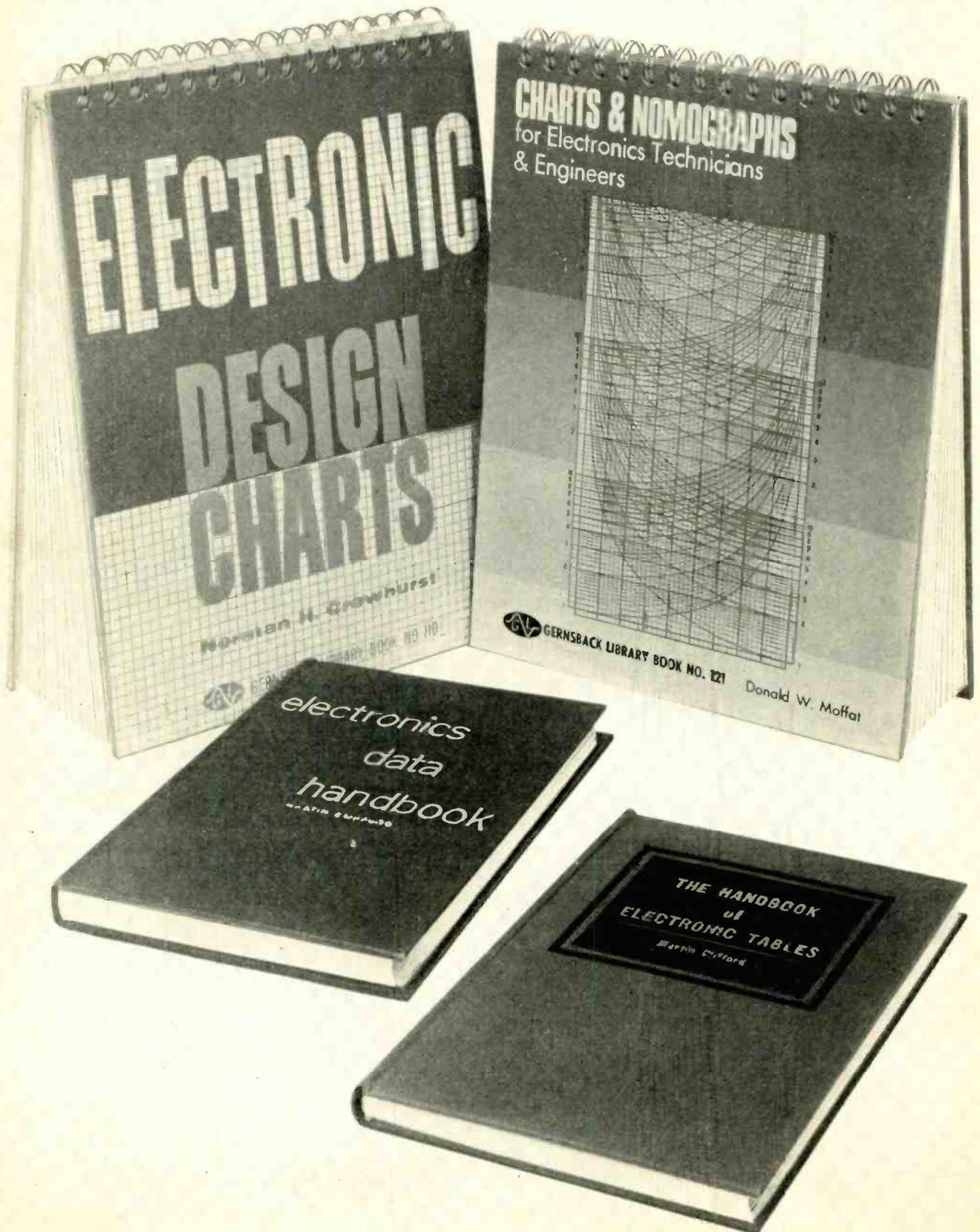**A free 10-day trial to prove you can solve any electronics problem with these 4 databooks and save \$5.00 in the process.**



These four comprehensive databooks will put immediate answers at your fingertips to speed you through your projects faster and more efficiently. Now you will have instant answers—charts, nomographs, tables, formulas, key data—all engineered by specialists to meet your specific needs.


Here is the first place to look for authoritative answers to your toughest electronics problems—whether you are working with theoretical applications or practical projects. You focus quickly on the answers you want, reducing hours of figuring to seconds.

The great value of these databooks is in their organization. Every conceivable type of problem is covered. These books will never be out-of-date. You'll keep them at your elbow continually . . . to save time, effort and trouble.

Return the coupon and we will send you ALL 4 databooks for you to use for 10 days. There is no obligation. If you don't agree that these books are indispensable tools that you'll use for years to come . . . just send them back. What's more—if you take all 4 volumes—you may have them at the special money-saving combination price of only \$16.80—instead of the \$21.80 they cost if purchased individually. You save \$5.00. Cost is tax deductible for business.


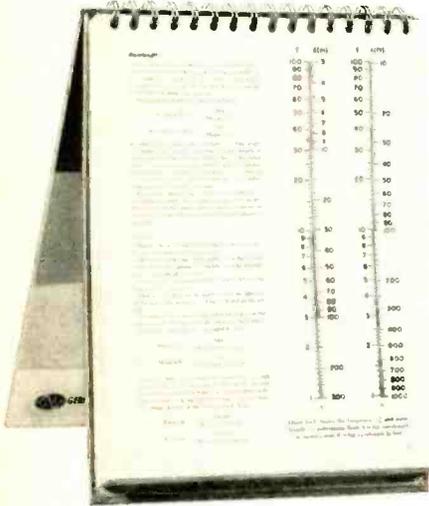
**Save an extra \$1.00.**

Send your check or money order with your order for the complete set of 4 databooks. You save us billing costs, which we'll pass on to you. We pay postage and you deduct an extra \$1.00 off the combination price of \$16.80. (Same return privileges apply.)




◀ **CHARTS AND NOMOGRAPHS** by Donald W. Moffat. 96 pages of instant solutions to hundreds of electronics problems. Avoid tedious calculations that delay your work. Simply turn to the appropriate page, put your ruler in place and read off the correct answers for a whole family of solutions simultaneously. Large, stand-up, 8-1/2 x 11" format specifically designed for ease of use. Cloth bound. \$5.95 if ordered separately.

**ELECTRONIC DESIGN CHARTS** by Norman H. Crowhurst. 128 pages—50 different charts give you more information in less time. Save hours of design . . . simplify design procedure . . . solve electronics problems quickly, and easily. Permanent spiral binding keeps large, 8-1/2 x 11" pages standing flat for ready reference. A valuable working tool for engineers and technicians. Cloth bound. \$5.95 if ordered separately.

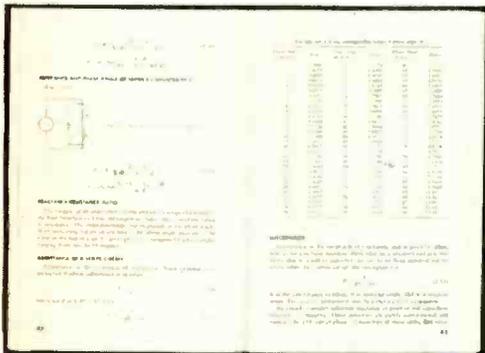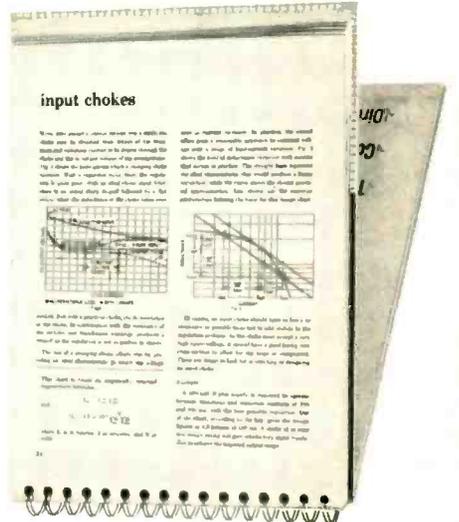

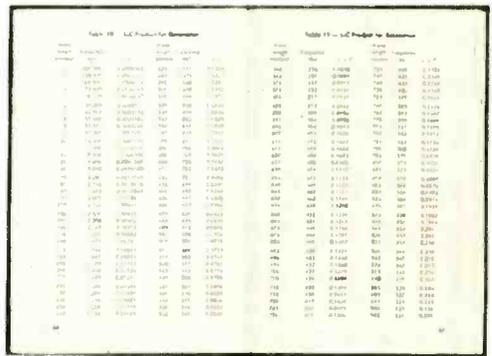**THE HANDBOOK OF ELECTRONICS TABLES** by Martin Clifford. A valuable new approach for accurate solutions to a wide range of electronics problems. This 160-page reference eliminates the need for mathematical computations, formulas, slide rules. All answers have been worked out for you in easy-to-use, accurate, electronic tables. Cloth bound. \$4.95 if ordered separately.



▲ **ELECTRONICS DATA HANDBOOK** by Martin Clifford. 160 pages of the most needed electronics formulas and data gathered, arranged and coordinated for easy reference. An indispensable reference. Cloth bound. \$4.95 if ordered separately.

**Save an extra \$1.00. Send payment in with order for all 4 Databooks. Deduct \$1.00 from \$16.80 price.**

GERNSBACK LIBRARY, INC. Dept. RE 87  
154 West 14th Street, New York, N. Y. 10011

Send me the following Databooks for free 10-day trial

- ELECTRONIC DESIGN CHARTS . . . . . \$5.95
- ELECTRONICS DATA HANDBOOK . . . . . 4.95
- CHARTS AND NOMOGRAPHS . . . . . 5.95
- HANDBOOK OF ELECTRONIC TABLES . . . . . 4.95
- ALL 4 BOOKS AT THE MONEY-SAVING PRICE OF \$16.80

New York residents please add sales tax.  
Canadian residents please add currency exchange.

Enclosed \$ \_\_\_\_\_ Bill me

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**THIS OFFER GOOD ONLY IN THE U.S. AND CANADA.**

## U.S. GOV'T ELECTRONIC SURPLUS

• Nationally Known-World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

ORDER DIRECT FROM AD or WRITE FOR CATALOGS

### STANDARD DIAL TELEPHONE

• (ITEM #715) - Standard, Commercial telephone same as used throughout U.S.A. Attractive polished black, like new condition. Use as extension phone to private systems or connect several phones together for local intercom system. Full instructions are furnished. Wt. 9 lbs. Original Cost \$24.50. F.O.B. **\$5.95**



### STEP-BY-STEP AUTOMATIC SWITCH

• (ITEM #738) - Amazing "up-and-around" electro-magnetic telephone switch. Dial any bank call from 1 to 100. Make your own telephone system. Can also be used to remotely control up to 100 circuits over a single pair of wires.

• One of our FOUR STAR bargains. Comes complete with data, one dial and one line bank. Size: 5" x 7" x 13", Wt. 16 lbs. Cost Gov't Over \$75.00. Complete: Switch, Cover, dial, line bank, instructions. F.O.B. **\$9.95**



### TYPICAL BUYS FROM OUR 1967 CATALOGS

\$ 350.00 - Geared 2-hp Battery Golf Car Motor ..... **\$24.95**  
 \$ 15.00 - Westinghouse DC Ammeter, 0 to 300 ..... **\$ 7.11**  
 \$ 40.00 - Vacuum/Pressure Pump, 12-VDC ..... **\$11.95**  
 \* \* \* - 80-MW Walkie-Talkies, Per Pair ..... **\$19.60**  
 \* \* \* - Deluxe, Multi-Range, AC/DC Tester ..... **\$ 8.98**  
 \$4000.00 - Carrier Telephone Amplifier System ..... **\$13.91**

### SPECIAL SALE Correspondence Course In ELECTRICAL ENGINEERING



Sells For \$10.79 Postpaid  
Outside U.S.A. **\$8.79** In U.S.A.

• (ITEM #A181) - Wonderful chance to obtain technical training at Amazing Low Cost! Lincoln Engineering School has suspended its Correspondence Course because of increased operating costs. We offer a limited number of the school's complete Electrical Engineering Course but without the examination paper grading service. The course contains all 14 lesson unit books. Each book has the regular exam, and in a separate section, "Standard Answers" to each exam question.

• Course is well written, easy to understand, profusely illustrated. Reader's Digest size, easy to carry and study in spare time. Many Lincoln Engineering School students holding excellent jobs as a result of E.E.S. training. Course contains latest information on transistors, silicon diodes, etc. Additional book on how to build and operate a "Home Laboratory and Experimental Bench" furnished with each course.

SEND 25¢ COIN OR STAMPS FOR 3 MAIN CATALOGS

All Items FOB Lincoln Money Back Guarantee

### SURPLUS CENTER

DEPT. RE-087 LINCOLN, NEBR. 68501

Circle 111 on reader's service card



## New 5 Band POLICE PORTABLE

Hear all police communications: patrol cars, base stations, motorcycles, helicopters. Also tunes Fire Departments, State Highway Patrols, Sheriff's Departments, auto telephones, taxis, all radio equipped vehicles. *Fascinating and exciting listening 24 hours a day!* Marine/Shortwave Band brings in all marine communications. Special Weather Band gives accurate forecasts and reports around the clock. Regular AM Broadcast Band brings in stations ordinary radios never get. *Also plugs into regular house current.*


5 BANDS: 150-175 MC, 30-50 MC, 1.5-4.5 MC  
 200-400 KC, 550-1600 KC

Complete with leather case, batteries, antennas, house current adapter. \$129.95. Unconditional 10 day money back return privilege. Write for Free Booklet.

Nova-Tech, Inc., 630 Meyer Lane, Dept. RE, Redondo Beach, Calif. 90278

Circle 112 on reader's service card

## NEW PRODUCTS continued

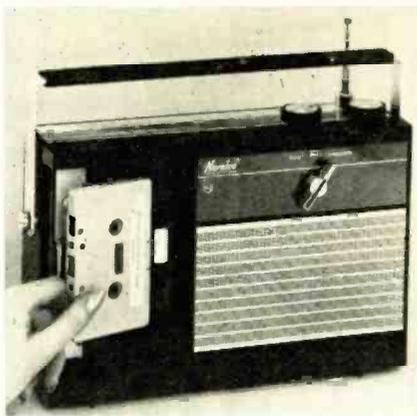


automatic pushbutton cassette ejector. 5 D batteries, adaptable to ac. 4-in. speaker, ferrite antenna for AM, telescopic aerial with 360° swivel action for FM. Includes outlets for earphone listening. 6 1/2 x 10 1/2 x 3 in., 6 lb. \$119.95—Norelco

Circle 61 on reader's service card



10-CHANNEL CB RADIO, the Companion IV. Solid-state. Includes optional handset. 2 1/4 x 8 1/2 x 6 1/2 in. 3 1/2 lb. Front and bottom speakers. Touch-tap tuning. Includes PA system jack, electronic switching, receive and transmit indicator light, class-B push-pull audio amplifier, LC filter, 2 rf stages in receiver. \$139.90—Pearce-Simpson, Inc.

Circle 62 on reader's service card

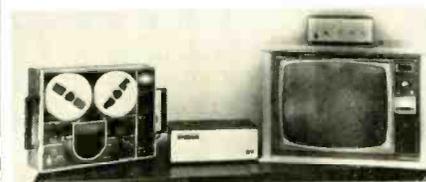

COLOR VTR ADAPTER, model EV-200. Allows industrial video tape recorders to record and reproduce color.—Sony Corp. END

Circle 63 on reader's service card

MOSFET's AND IGFET's sound like Martian political parties or underwater monsters. But they're actually two new semiconductor devices. Everytime somebody invents a new transistor or diode, it seems harder to understand the name than to learn how the device works. Find out what MOSFET and other solid-state abbreviations mean in September RADIO-ELECTRONICS.

# NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here are free for the asking with a Reader's Service number. Turn to the Reader's Service Card facing page 72 and circle the numbers of the items you want. Then detach and mail the card. No postage required!

AUTOTRANSFORMER PRODUCT GUIDE. Illustrated. Describes standard and deluxe variable and isolated variable transformers.—Staco, Inc.

Circle 64 on reader's service card

REPLACEMENTS PARTS CATALOG, No. 33GL. 24 pages. Illustrated. 5 sections and index. Specs, dimensions, application data of 2,000 components.—Centralab Electronics Div., Globe-Union, Inc.

Circle 65 on reader's service card

1967 CATALOG. 52 pages. Lists 14,000 components. Includes batteries, flashlights, capacitors, controls, jacks, plugs, semiconductors, switches, circuit breakers, timers, vibrators. Section with performance charts, product diagrams, packaging and literature details.—Mallory

Circle 66 on reader's service card

BULLETIN ON 14-PIECE NUT- AND SCREWDRIVER KIT. No. N367 describes No. 99PR kit. Illustrated. Kit has breakproof, shock-proof Series 99 Service Master (UL) plastic handle, 9 interchangeable nutdriver blades, 2 Phillips single-end screwdriver blades, 2 single-end blades for slotted screws.—Xcelite, Inc.

Circle 67 on reader's service card

AUDIO CATALOG. 116 pages. Includes professional audio and audio-visual equipment, video tape recorders, closed-circuit TV, stereo equipment, accessories. For industrial, educational, professional uses.—Sonocraft Corp.

Circle 68 on reader's service card

SPECS ON AMPLI-VOX SOUND COLUMN LECTERN, Model S-500, Bulletin LASS-500. Printed as file folder. Specs on amplifier, microphone, speaker, self-contained system. Includes frequency-response curves, speaker directivity patterns, information on 117V ac power adapter, other accessories.—Perna-Power Co.

Circle 69 on reader's service card

CONDENSED CATALOG OF VECO THERMISTORS, VARISTORS, No. MGP681. Data include resistance-temperature characteristics, dissipation and time constants, electrical properties, dimensions.—VECO END

Circle 70 on reader's service card

**EXTRA POWER**  
with  
**FINCO**  
**AMPLIFIERS**  
*For perfect color TV and  
FM Stereo Reception*

**FINCO MODEL #65-4**  
Antenna Amplifier  
\$47.95 list VHF-TV  
Two-transistor Antenna  
Amplifier for 75 OHM  
Downlead, and power  
supply with built-in  
single or dual 300 ohm  
outputs. Provides 12  
dB gain in the low band  
and 14 dB gain in the  
high band.



**FINCO MODEL #65-1**  
Distribution Amplifier  
\$29.95 list 2-tube 4-  
output VHF-TV or FM  
Distribution Amplifier  
for 300 OHM Opera-  
tion, providing 8 dB  
gain at each 300 ohm  
output to feed home or  
commercial systems.

**FINCO MODEL #65-5**  
Distribution Amplifier  
\$44.95 list VHF-TV 75  
OHM Single Outlet Dis-  
tribution Amplified for  
deluxe home or com-  
mercial use to feed  
multiple sets through  
line tap offs or split-  
ters. Delivers 17 dB  
Low Band and 14 dB  
High Band.



**FINCO MODEL #65-2**  
Distribution Amplifier  
\$39.95 list 2-tube 4-  
output VHF-TV or FM  
Distribution Amplifier  
for 75 OHM CO-AX  
Operation, providing 6  
dB gain at each 75 ohm  
output to feed deluxe  
home or commercial  
systems.

**FINCO MODEL #65-6**  
Amplifiers \$79.95 list.  
VHF-TV Antenna Mount-  
ed two-transistor pre-  
amplifier with 75 OHM  
two-tube Single Output  
Distribution Post-am-  
plifier up to 30 dB gain  
for improved reception.  
Used in home or com-  
mercial installations to  
feed multiple sets.



**FINCO MODEL #65-3**  
Antenna Amplifier  
\$44.95 list New VHF-  
TV Antenna Amplifier  
and Power Supply with  
built in single or dual  
outputs to improve re-  
ception of weak signals  
in fringe areas. Pro-  
vides 12 dB gain in the  
low band and 14 dB  
gain in the high band.

**FINCO MODEL #65-7**  
FM Signal Amplifier  
\$24.95 list. One-tran-  
sistor Indoor Behind-  
the-set FM amplifier  
with a passive filter in-  
put circuit to reject sig-  
nals outside the FM  
band which cause in-  
terference. Delivers 20  
dB Gain.



**Sets "COME ALIVE" with  
Brilliant Sound and Color**

A Finco high-gain, low-noise amplifier  
will bring in the sharpest **COLOR** or  
B & W TV picture and the finest sound!

**All FINCO Products are Engineered  
For Color!**



Write for Color Brochure #20-411.

**THE FINNEY COMPANY**

34 W. Interstate Street • Dept. • Bedford, Ohio 44146

# MORE ABOUT HYDRONICS

The May 1967 issue of RADIO-ELECTRONICS carried an article by Jack Althouse entitled "Build Hydronic-Radiation Transmitter." Little is known about *hydronics*; Wallace Minto—who coined the term, claims it's a new form of communication different from radio. Jack Althouse then built a hydronic transmitting system which apparently works. How it works is still a controversial subject.

R-E reader Peter Lefferts wrote us, suggesting further hydronics experiments. He believes there may be another explanation for hydronic radiation (besides the "up-over-down" theory mentioned by Althouse). He has used "ground-conduction antennas" consisting of ground rods spaced up to 600 feet apart. Working from 5 to 76 kHz with a simple rf oscillator, he claims to have heard signals transmitted entirely through the earth. He also believes he heard a radio station over 1,000 miles away using this method.

Since Lefferts experimented with conventional transmitters, he concludes that conventional radiation was involved. He suggests the antenna created a magnetic loop effectively larger than itself. When the hydronic antenna is near water surface, the greatest effect is observed. Lefferts's theory: The water provides a *spreading conducting* path located in a vertical plane. The water then radiates like a large single-turn loop antenna. Water conductivity acts like a ground plane, and useful radiation occurs just above the surface.

Further, the spreading radio waves continue magnetically to induce circulating currents just under the water surface, and thus provide coupling back to the antenna. Lefferts thinks this explains how conventional radio waves are picked up by his conductive ground antenna. [Underground antennas have been known for years to pick up signals from the broadcast band to at least the 80-meter ham band.—Editor] He suggests the following experiments:

**Loop antennas:** Place the plane of the loop perpendicular with the water surface and parallel with the plane of the hydronic transmitter antenna plates. Connect the loop to a receiver and tune in the transmitted frequency, monitoring avc voltage with a voltmeter. If the magnetic-field and circulating-current theory is correct, you should observe an increase in received signal when the hydronic antenna is

first dipped in the water.

**Fluid effects:** Some have suggested that hydronics is related to magnetohydrodynamics (or the current-induced motions of a conducting liquid). Two experiments could prove or disprove this theory:

1. Measure the velocity of propagation in water. You could do this by measuring the phase delay of a received signal by comparing it (on a scope) with the same signal as transmitted. If the propagation rate is found about the same as that for radio waves in air, this would seem to rule out water movement.

2. The hydronic antenna should be tried in salt-water-soaked earth. If transmission ranges are similar to those in water, as Lefferts suspects, then this suggests no fluid rf action.

**Antennas:** 1. Set up a hydronic transmitter and receiver with antennas in a single body of water and measure received signal strength. Then place the two antennas in separate, electrically isolated bodies of water the same distance apart (for instance, two tubs of water) and remeasure avc. If the magnetic-loop theory is correct,

results should be similar.

2. Instead of running twisted wires to the antenna plates (as Althouse did), use separate wires run parallel and apart. This should increase loop size and transfer more signal. As the antenna plates are dropped deeper, the conductive-loop area should be greater and signal strength should increase, rather than decrease, (as Althouse found).

**Shielding:** 1. Will insulating the hydronic antenna reduce reception? If not, *why not*—since water presumably conducts the signal.

2. Will a conducting shield around the antenna reduce reception? For an antenna near the surface, must the shield be under the surface, above the surface, or completely surrounding the antenna?

3. If a conducting shield or plate reduces signal level, will a plate with holes in it (to allow water movement) also produce shielding?


We hope some of you will try to answer the above questions. Let RADIO-ELECTRONICS know what you find out. Perhaps the hydronics mystery can be solved.

## ANOTHER SUGGESTION

Dear Editor:

The hydronic radiation system described in your May issue sounds like it has a great deal in common with earth-conduction communication (see illustration), which to the best of my knowledge has little if anything to do with "electromagnetic and magnetohydrodynamic forces, characteristi-

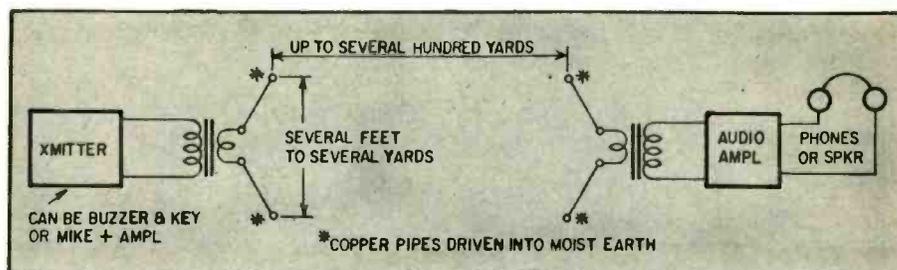erable plain old electrical conduction between the plates. There is also doubtless some capacitive transfer between transmitting and receiving antennas. I wonder whether the system would work equally well in distilled water, which ionizes only very weakly, and so is a relatively poor conductor, or in water with some nonionizing substance dissolved in it—like sugar, for



cally propagated through a water medium. . . ." As usually attempted, earth conduction "radio" uses audio frequencies, although it would probably work with low- or medium-frequency rf.

It seems to me that when the propagation medium is some kind of electrochemically ionizable solution (such as water with some quantity of dissolved salts), there must be consid-

erance? The question of how large a role electrical conduction and capacitance play in the transmission is not taken up in the article.

I think it is time to devise a series of experiments to separate, if possible, the effects of conduction, induction, capacitance and electromagnetic radiation in the hydronics scheme.

GEORGE MARTINSON

New York City


END

# CB Troubleshooter's Casebook

Compiled by  
Andrew J. Mueller

**Case 1:** Loud 60-Hz hum on receive with the volume control turned up. The hum disappears with the volume control turned down.

**Common to:** Olson Spotter 2

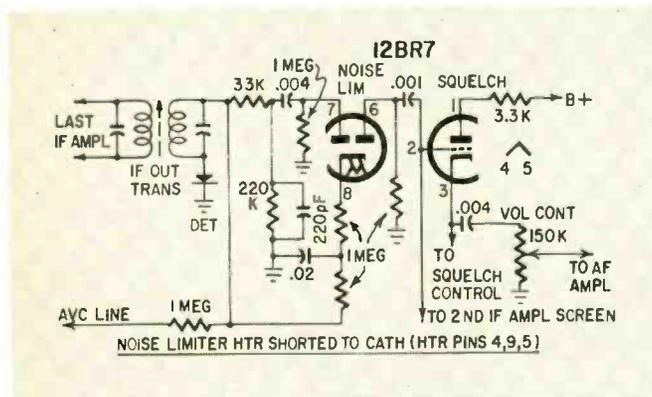


**Remedy:** Replace 12BR7 tube in the receiver.

**Reasoning:** This tube shorts from the heater to cathode in the diode sections. This feeds ac into the audio system when the volume control is turned up.

**Case 2:** When the unit is operated on 12 volts, it doesn't transmit but receives okay. This unit works perfectly on 117 volts ac.

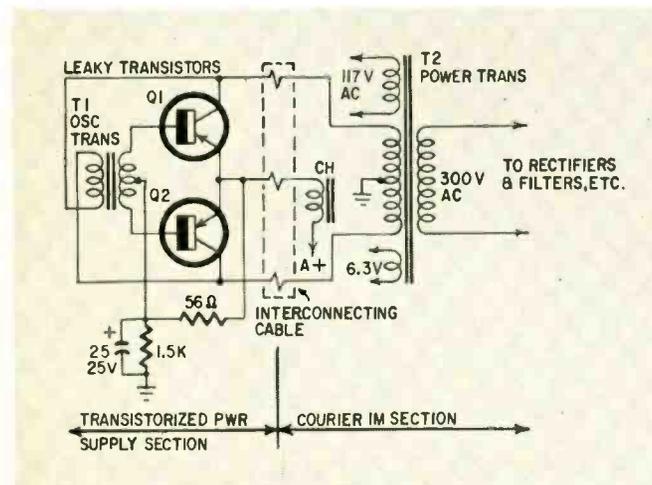**Common to:** ECI Courier 1M with TPS (Transistorized Power Supply).



**Remedy:** Replace both transistors in the TPS.

**Reasoning:** The transistors are leaky. On receive, the set doesn't need as much B+ so everything operates normally. When the unit is switched to transmit, a heavier load is put on the power supply. This causes the transistors to stop oscillating; hence the unit goes dead on transmit but not on receive.

# For CB Antennas Specify MOSLEY

## ① DEMON

A short mobile antenna measuring 17"; long on performance. Center loaded. Stainless steel whip. SWR 1.5/1 or better. Screw on and off. Antenna complete with coax, chrome plated spring and hdw. Weight 1.5 lbs.  
MODEL DA-27

## ② DEPUTY

Similar to DA-27, but base loaded and longer. Measures 43 3/4".  
MODEL DP-27

## ③ CADET TWINS


About the most versatile CB antenna on the market today. Suction cup mount for temporary use on cars, trailers, boats etc. Use on all smooth surfaces - wood and fiberglass included. No ground. Length 3'. Center loaded. No hole drilling. Installs in seconds. Wt. 1 lb.  
MODEL SUC-1

## ④ PER-1

A permanent version of the SUC-1.  
MODEL PER-1

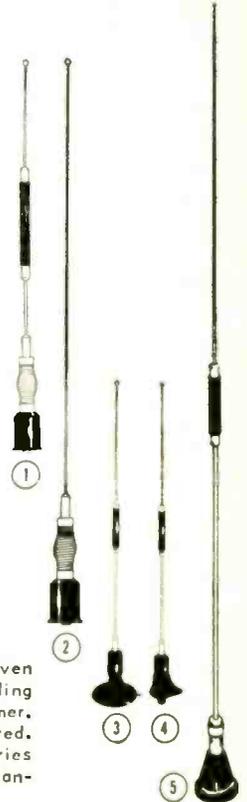
## ⑤ SILVER DOLPHIN

Performance proven marine antenna, dependable even in out-of-the-way coves! Height 8' 5". Loading through salt-resistant, weather-proof transformer. SWR 1.5/1 over 23 channels. No ground required. Fold over base hinge. Weight 3.4 lbs. Accessories available for angle mounting and for clamping antenna to window ledge.  
MODEL D-27



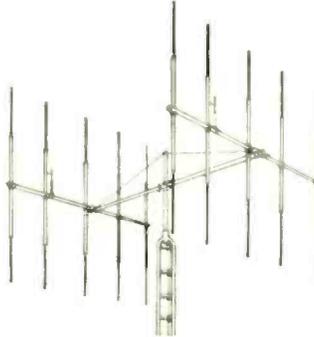
## STACK'IT

To nearly double the effective power of the transmitter, stacking beams is recommended. Results in extra reliable point-to-point communications. Mosley Stack'it beam kits include everything needed for the stacking job. From two well-known Mosley performance proven beams, coax yoke, hardware, guy rope, boom, to concise assembly instructions. Feed with 52 ohm coax (not included). 80 MPH wind survival. Average assembled weight 42 pounds. Three models available:  
MODEL SKT-3  
MODEL SKT-4  
MODEL SKT-5


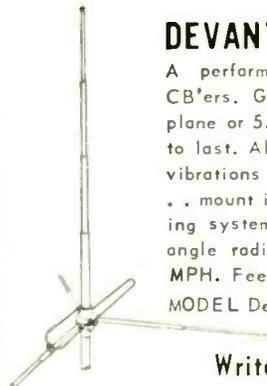
## DEVANT '1'

A performance proven vertical antenna popular with CB'ers. Gain 3.4 db. compared to quarter wave ground plane or 5.9 db. over isotropic source. Rugged and built to last. Aluminum ends tapered to reduce wind load and vibrations causing metal fatigue. So lightweight . . . mount it yourself! Exclusive 'Induct-O-Match' matching system. Height 19' 7 1/2". SWR 1.5/1 or better. Low angle radiation. Lightning protected. Wind survival 80 MPH. Feed with 52 ohm coax. Assembled wt. 7.5 lbs.  
MODEL Devant 1.



Write for FREE Catalog . . . Dept. 139

**Mosley Electronics Inc.** 4610 N. Lindbergh Blvd.,  
Bridgeton Missouri 63042

Circle 114 on reader's service card

# INCOMPARABLE PACE 2300



## 23 CHANNEL MOBILE CB RADIOTELEPHONE

Here is the ultimate in efficient, ultra-reliable solid state two-way Citizens Band radio communication, with more exclusive features than any other all-silicon transceiver.

Transmitter—equipped with heavy silicon diamond output transistor, rated at full authorized power (5 watts) • delivers 4 watts (typical) with 100% modulation • double conversion superheterodyne receiver with narrow band, shaped audio response • custom styled to match interior auto decor—handsome walnut grain metal case and chrome bezel • all 23 channels installed and factory tuned • full size "S" meter installed and calibrated • local/distance receiver sensitivity control • exclusive noise limiting • Public Address and loud hailer facility with front panel control and separate speaker jacks • equipped for "Private Caller" selective call accessory • quick-snap power cord and bracket for easy transfer to other vehicle • new locking latch rack • full year guarantee on all parts, plus lifetime guarantee on glass fiber circuit board.

**\$219.95**

Write for complete information:  
**((P)) PACE COMMUNICATIONS CORP.**


24049 Frampton Ave., Harbor City, Calif. 90710 / Telephone: (213) 325-8444  
Export Div: 64-14 Woodside Ave., Woodside, N. Y. / Also available in Canada.

Circle 115 on reader's service card
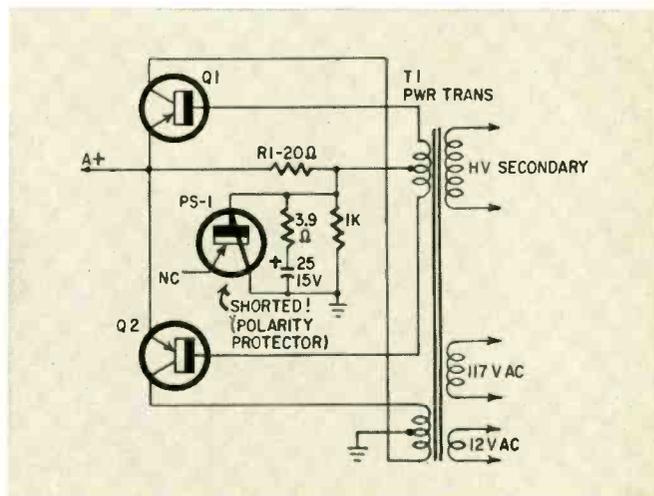
### CB TROUBLESHOOTER'S CASEBOOK

**Case 3:** Transceiver blows fuses on 12-volt operation, but works normally on 117 volts ac.

**Common to:** Pearce-Simpson Companion I




**Remedy:** Replace shorted polarity protector, PS-1.

**Reasoning:** When the unit is placed on 12 volts, the A+ line is shorted through R1 and PS-1 to ground. This is almost a dead short, which will blow a fuse. The unit will operate normally on 117 Vac because this part of the circuit is not used on 117-volt operation.

**Case 4:** Intermittent receive and transmit. The neon lamp goes off when the unit quits.

**Common to:** Heathkit GW-10

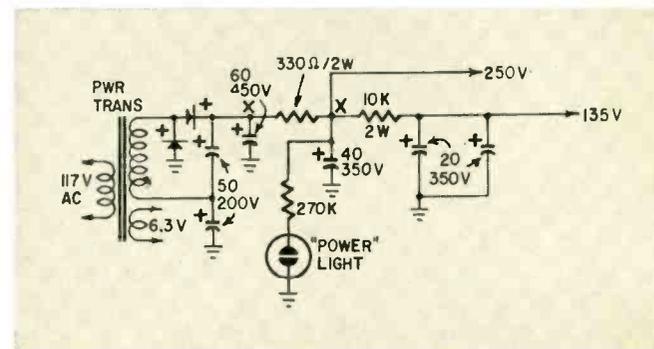


**Remedy:** Solder the loose connections at the points indicated by an "X" on the schematic.

**Reasoning:** Poor solder connections between the electrolytic capacitors and the 2-watt resistors cause this trouble. This is especially true with home-built kits. Due to the large wire size of the resistors and the many wires being soldered at these points, this spot is often not soldered, or very poorly so.

**Case 5:** Transceiver intermittently blows fuses on 12-volt operation. Okay on 117 Vac.

**Common to:** General VS-6

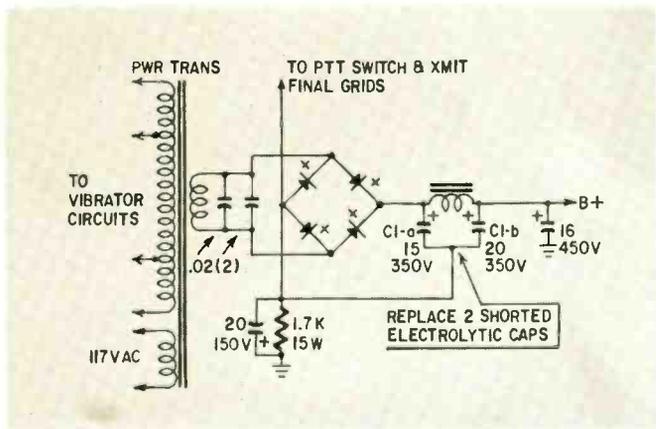


**Remedy:** Replace shorted filter capacitor C1-a, b and check the voltage regulator of the automobile. Reduce regulator output to 13.6 volts if you find the output too high.

**Reasoning:** High input voltages to the receiver from the auto will cause B+ voltage to become higher than the ratings of filter capacitor C1. Thus C1 breaks down and shorts. If this happens, check the generator output voltage before reinstalling the transceiver in the car.

**Case 6:** Weak receive but transmit okay.

**Common to:** Hallicrafter CB-7

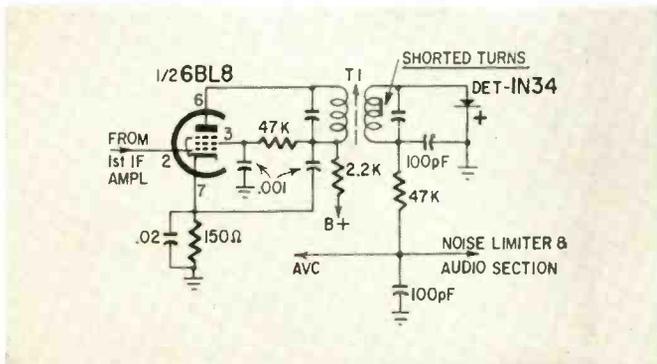

**Remedy:** Replace last i.f. transformer, T1.

**Reasoning:** Shorted turns in T1 cause this problem. This action reduces circuit Q, killing almost all the signal. Trouble can be a tough dog to find. While the coil peaks normally, the output of this stage is very low. Hence you can be led to believe the trouble lies elsewhere. END

## COMING NEXT MONTH

**COLOR TV** is an important part of electronics and is (a mystery) (not very clear) to me. I should (study color) (pick it up on the job). I don't like dull textbooks, so I will (forget about color) (read the easy-to-understand programmed primer on color coming in September RADIO-ELECTRONICS).

**CREATIVE SERVICING** means you don't just start replacing components at random when troubleshooting electronics gear. Hit-or-miss is mostly miss—you waste time, do a poor job, and make less money. Why not take a few minutes to find out a logical and practical troubleshooting method? No matter how much electronics experience you have, you'll be interested in this article on logical servicing, in September RADIO-ELECTRONICS.

**BIGGER... BETTER THAN EVER!**

**FREE!**

**SEND TODAY FOR YOUR NEW 40th ANNIVERSARY 1967 CATALOG**



**YOUR BUYING GUIDE FOR**

- Stereo & Hi-Fi Systems & Components.
- Tape Recorders.
- Electronic Parts, Tubes, Tools.
- Phonos & Records.
- Cameras and Film.
- Public Address.
- Citizens Band.
- Ham Gear.
- Transistor & FM-AM Radios.

**252 GIANT VALUE PACKED PAGES!**

**BURSTEIN-APPLEBEE CO.**

Dept. RE, 1012 McGee, Kansas City, Mo. 64106

Rush me the FREE 1967 B-A Catalog.

Name.....

Address.....

City.....

State..... Zip Code.....

Circle 118 on reader's service card





**WORLD'S FINEST**  
**5-CORE SOLDER**



**ERSIN MULTICORE**  
**NEW EASY DISPENSER PAK**  
**ONLY 69¢**

BUY IT AT RADIO-TV PARTS STORES  
MULTICORE SALES CORP. WESTBURY, N.Y. 11590  
Circle 119 on reader's service card

# NEW SEMICONDUCTORS, MICROCIRCUITS & TUBES

## DO-IT-YOURSELF IC


Research laboratories and small companies can now carry out R & D projects involving IC's without having complete microcircuit manufacturing facilities at their disposal. This is made possible by Westinghouse's new Insta-Circuit monolithic silicon breadboard. All the customer has to do is to link the active areas of the tiny unit in various circuit combinations to suit his specific needs. The only equipment required is a wire bonding machine equipped with a microscope to facilitate connecting hair-thin gold bonds between various areas of the tiny silicon chip.

The Insta-Circuit breadboard contains 8 transistors, 44 resistors and 5 diodes—all within a chip no larger than the pupil of the human eye. It sells for \$29.
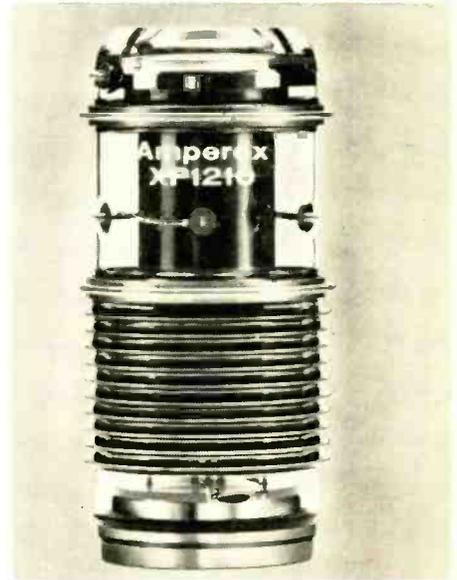
## PHOTOMULTIPLIER AND X-RAY TUBES

The XP1210 is a new tetrode focused photomultiplier tube capable of unusually fast response and high efficiency. Featuring a 2-inch cathode, the tube has the following typical param-


eters (voltage-dependent): electron transit time 18 nsec, rise time 0.6 nsec, collection efficiency 90% or better at 5,300 A, luminous sensitivity (average) 60  $\mu$ A/lumen, nominal gain  $10^8$  and nominal dark current  $14 \times 10^{-17}$  A/



## \$1000 REWARD

TO ANYONE—Who can show us an Established Competitor who could sell & deliver all the items on this list at the prices & in the quantities that we do! HOW DO WE DO IT?

Our TREMENDOUS BUYING POWER & PURCHASING EXPERIENCE make it possible. We invest Thousands of Dollars (in just a single item) to create a good DOLLAR BUY, resulting in the AMAZING & EXCITING OFFERS that follow:

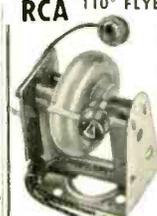- |   |   |   |  |
|---|---|---|--|
| <input type="checkbox"/> ERSIN MULTICORE SOLDER 69¢   | <input type="checkbox"/> 4 - TV ALIGNMENT TOOLS \$1<br>most useful assortment .....                                       | <input type="checkbox"/> RCA 110° FLYBACK TRANSFORMER   | <input type="checkbox"/> UNIVERSAL 4" PM SPEAKER 49¢<br>Alnico 5 magnet, quality tone ...                              |
| <input type="checkbox"/> 1 - LB SPOOL ROSIN-CORE SOLDER \$1.39<br>40/60 top quality .....       | <input type="checkbox"/> 7 - ASST. TV ELECTROLYTIC CONDENSERS \$1<br>popular selection .....                              |  We scooped the Market Latest type — standard for all 110° TV's RCA's design of large Coil produces 18kV—assuring adequate width Incl Schematic Diagram application for any TV List price \$13.90 Your price .. \$3 10% off in lots of 3 | <input type="checkbox"/> 100 - ASST. RADIO KNOBS \$1<br>all selected popular types .....                               |
| <input type="checkbox"/> 2 - G.E. PIECES OF EQUIPMENT \$1<br>stacked with over 200 useful parts | <input type="checkbox"/> \$15.00 TELEVISION PARTS "JACKPOT" best buy ever .....   | <input type="checkbox"/> 110° TV DEFLECTION YOKE for all type TV's Incl schematic same as Thordarson Y502 list \$20 \$3   | <input type="checkbox"/> 40 - ASSORTED TV KNOBS \$1<br>all standard types. \$20 value .....                            |
| <input type="checkbox"/> 3 - 50' SPOOLS HOOK-UP WIRE \$1<br>assorted colors .....               | <input type="checkbox"/> BONANZA "JACKPOT" not gold, not oil, but a wealth of Electronic Items—Money-Back-guarantee ..... | <input type="checkbox"/> "COMBINATION SPECIAL" RCA 110° FLYBACK plus 110° DEFLECTION YOKE .. \$5  | <input type="checkbox"/> 10 - ASSORTED DIODE CRYSTALS \$1<br>1N34, 1N48, 1N60, 1N64, 1N82                              |
| <input type="checkbox"/> 50 - ASSORTED MYLAR CONDENSERS popular selected types .. \$1           | <input type="checkbox"/> 10 SETS - DELUXE PLUGS & JACKS asst. for many purposes .. \$1                                    | <input type="checkbox"/> 90° FLYBACK TRANSFORMER for all type TV's Incl schematic \$2   | <input type="checkbox"/> 10 - STANDARD TRANSISTORS \$1<br>NPN & PNP 2N404, 2N414, etc.                                 |
| <input type="checkbox"/> 100 - MIXED DEAL "JACKPOT" Condensers, Resistors, Surprises .. \$1     | <input type="checkbox"/> 10 - SETS PHONO PLUGS & PIN JACKS RCA type .....   | <input type="checkbox"/> 90° TV DEFLECTION YOKE for all type TV's Incl schematic .. \$2   | <input type="checkbox"/> 5 - TOP HAT SILICON RECTI. \$1<br>FIERS 500ma-600v top quality ...                            |
| <input type="checkbox"/> 10 - ASSORTED SLIDE SWITCHES SPST, SPDT, DPDT, etc. .... \$1           | <input type="checkbox"/> 10 - SURE-GRIP ALLIGATOR CLIPS 2" plated .....   | <input type="checkbox"/> 70° FLYBACK TRANSFORMER for all type TV's Incl schematic \$1   | <input type="checkbox"/> BSR #UA-25 STEREO RECORD CHANGER complete w/ cartridge latest deluxe nothing better made \$16 |
| <input type="checkbox"/> 20 - EXPERIMENTER'S COIL "JACKPOT" assorted for 101 uses \$1           | <input type="checkbox"/> 50 - RADIO & TV SOCKETS all type 7 pin, 8 pin, 9 pin, etc. \$1                                   | <input type="checkbox"/> 70° TV DEFLECTION YOKE for all type TV's Incl schematic \$1  | <input type="checkbox"/> BSR MONAURAL CARTRIDGE \$1.49<br>Universal dual flipover sapphire                             |
| <input type="checkbox"/> 20 - ASST. PILOT LIGHTS #44, 46, 47, 51, etc. .... \$1                 | <input type="checkbox"/> 50 - ASSORTED #3AG FUSES popular ampere ratings .....  | <input type="checkbox"/> 20 - ASSORTED TV COILS i.F. video, sound, ratio, etc. .... \$1   | <input type="checkbox"/> BSR STEREO CARTRIDGE \$2.49<br>Universal dual flipover sapphire                               |
| <input type="checkbox"/> 50 - ASST. DISC CERAMIC CONDENSERS popular numbers .. \$1              | <input type="checkbox"/> 100 - STRIPS ASSORTED SPAGHETTI handy sizes .....  |   | <input type="checkbox"/> ASTATIC #13T STEREO CAR. \$2.78<br>TRIDGE plug-in, power point ...                            |
| <input type="checkbox"/> 10 - ASST. RADIO ELECTROLYTIC CONDENSERS \$1                           | <input type="checkbox"/> 100 - ASSORTED RUBBER GROMMETS best sizes .....  |   | <input type="checkbox"/> 3 - SAPPHIRE STYLUS NEEDLES \$1<br>Ronette type for most cartridges ..                        |
| <input type="checkbox"/> 20 - STANDARD TUBULAR CONDENSERS .047-600v .....                       | <input type="checkbox"/> 50 - ASSORTED PRINTED CIRCUIT SOCKETS best types .....   |   | <input type="checkbox"/> 3 - STANDARD SAPPHIRE NEEDLES for all thumbscrew cartridges \$1                               |
| <input type="checkbox"/> 3 - 1/2 MEG VOLUME CONTROLS with switch, 3" shaft .....                | <input type="checkbox"/> 10 - ASSORTED VOLUME CONTROLS less switch .....  |   | <input type="checkbox"/> 10 - G.E. SAPPHIRE NEEDLES \$1<br>4G, VR-11, etc. (\$25.00 value) ..                          |
| <input type="checkbox"/> 7 - ASSORTED VOLUME CONTROLS with switch .....                         | <input type="checkbox"/> 7 - ASSORTED VOLUME CONTROLS with switch .....   |   |  |

FREE \$1 BUY WITH EVERY 10 YOU ORDER

Only applies to "\$1" Buys

FREE GIFT WITH EVERY ORDER

IMMEDIATE DELIVERY ... Scientific light packing for safe delivery at minimum cost. HANDY WAY TO ORDER: Pencil mark or write amounts wanted in each box, place letter F in box for Free \$1 BUY. Enclose with check or money order, add extra for shipping. Tearsheets will be returned as packing slips in your order, plus lists of new offers.

Name .....

Address .....

Cost of goods .....

Shipping estimated .....

TOTAL .....

Please specify refund on shipping overpayment desired:  CHECK  POSTAGE STAMPS  MERCHANDISE (our choice) with advantage to customer

**BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N. Y. 10024**

TELEPHONE 212-874 5600


Circle 120 on reader's service card



tubes can be obtained from Amperex Electronics Corp., Hicksville, N. Y. 11802.
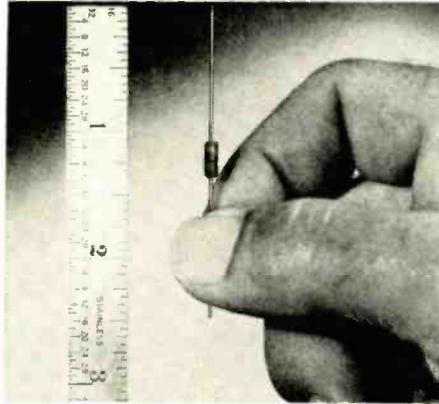
### 1-WATT ZENER VOLTAGE REGULATORS

The G3 through G12 make up a new series of 1-watt glass Zener diodes designed for regulator and other industrial and commercial applications requiring stable long-term operation. The small size (DO-7) makes this series especially suited for high-density packaging applications.



Available in a nominal Zener voltage range from 3 to 12 V and tolerances of 20%, 10% and 5%. The series is described in Bulletin C103 from International Rectifier, Dept. 781-C2, 233 Kansas St., El Segundo, Calif. 90245.



## FREE Electronics Data Guide

Want help in working out those tricky electronics calculations? Send for our FREE Electronics Data Guide. This heavy-duty plastic guide fits right in your shirt pocket—gives you instant reference to over 40 indispensable electronics formulas...plus conversion factors, color codes and decibel table as well. Saves you time and the trouble of memorizing or "looking it up." A "must" for every man interested in electronics—provided as a service by CIE. Why not get your FREE Data Guide today? Just fill in your name and address below, then cut out this ad and mail it to:

**Cleveland Institute of Electronics**  
1776 E. 17th St., Cleveland, Ohio 44114

Name \_\_\_\_\_  
(Please Print)  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

Accredited Member National Home Study Council. 906

Circle 121 on reader's service card

cm<sup>2</sup>. When operating at potentials up to 8 kV, the tube does not show tendency toward ionization or corona.

The FX-30 and FX-30M are the smallest flash X-ray tubes commercially available. The FX-30 envelope is 1½ in. in diameter and 2½ in. long. Overall length is 3¾ in. The miniature version (FX-30M) is in a ½ × 1½-in. envelope and is 2 in. long overall.


Both tubes have a pulse duration of 100 μsec with a duty cycle of 1 pulse per 5 sec. Maximum plate voltage in air is 30 kV. Plate current is 1 A. Used in diagnostic studies of destructive weapons testing, stress-analysis equipment and similar applications.

Further information on these three

**CANADIANS: Ordering is easy . . . we do the paperwork . . . try a small order**
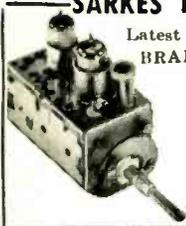
### SARKES TARZIAN TV TUNER 41mc

Latest Compact Model—good for all 41 mc TV's.  
BRAND NEW—MONEY BACK GUARANTEE



Best TUNER "SARKES TARZIAN" ever made—last word for stability, definition & smoothness of operation. An opportunity—to improve and bring your TV Receiver up-to-date.

COMPLETE with Tubes & Schematic . . . \$7.95

### HIGHWAVE AM-FM PORTABLE RADIO



Elegance in Ebony & Chrome  
14 Transistors - A Powerhouse of Quality Reception with AFC Operates on 4 "C" Cells  
22" Telescoping FM Antenna & Personal Listening attachment  
Money refund - if not better than any Known Brand selling for even twice the price  
8" x 5¼" x 2¼" - 4 lbs

COMPLETE . . . \$19.50


### IBM COMPUTER SECTIONS

8 assorted Units we sell for \$1 are loaded with over 150 valuable parts.  
Incl. — Transistors, Condensers, Resistors, Heat Sinks, Diodes, Etc.  
**8 for \$1**  
**100 for \$10**

- |   |  |   |   |
|---|--|---|---|
| <input type="checkbox"/> 1000—ASST. HARDWARE KIT \$1<br>screws, nuts, washers, rivets, etc. | <input type="checkbox"/> UNIV. 3" x 5" PM SPEAKER 59¢<br>Best type for Radios, TV, Etc.                            | <input type="checkbox"/> 100—ASST ¼ WATT RESISTORS \$1<br>stand. choice ohmages, some in 5%   | <input type="checkbox"/> 10—7" TV TAPE REELS \$1<br>all you want, 8000 in stock   |
| <input type="checkbox"/> 300 — ASSORTED HEX NUTS \$1<br>2/56, 4/40, 5/40, 6/32, 8/32        | <input type="checkbox"/> 3—ELECTROLYTIC CONDENSERS \$1<br>most popular number 50/30—150v                           | <input type="checkbox"/> 100 — ASST ½ WATT RESISTORS \$1<br>stand. choice ohmages, some in 5% | <input type="checkbox"/> TAPE RECORDER — assorted types \$4<br>good, bad, broken, as-is, postluck                         |
| <input type="checkbox"/> 250—ASST. SOLDERING LUGS \$1<br>best types and sizes               | <input type="checkbox"/> 15 — G.E. #NE-2 TUBES \$1<br>Neon Glow Lamp for 101 uses                                  | <input type="checkbox"/> 70 — ASST 1 WATT RESISTORS \$1<br>stand. choice ohmages, some in 5%  | <input type="checkbox"/> TRANSISTOR RADIO <i>best type</i> \$1.50<br>good, bad, broken, as-is, postluck                   |
| <input type="checkbox"/> 250—ASST. WOOD SCREWS \$1<br>finest popular selection              | <input type="checkbox"/> CLEAN UP THE KITCHEN "JACK-POT" \$1<br>Big Deal<br>only one to a customer                 | <input type="checkbox"/> 35 — ASST 2 WATT RESISTORS \$1<br>stand. choice ohmages, some in 5%  | <input type="checkbox"/> 10 — TRANSISTOR RADIO EAR-PIECES \$1<br>wired complete with plug                                 |
| <input type="checkbox"/> 250 — ASST. SELF TAPPING SCREWS \$1<br>#6, #8, etc.                | <input type="checkbox"/> HEARING AID AMPLIFIER \$2<br>incl. 3 Tubes, Mike, etc. (as is)                            | <input type="checkbox"/> 50 — PRECISION RESISTORS \$1<br>asst. list-price \$50 less 98%       | <input type="checkbox"/> 100 — ASST. TUBULAR CONDENSERS \$1<br>.001 to .47 to 600v  |
| <input type="checkbox"/> 150—ASST. 6/32 SCREWS and 150 6/32 HEX NUTS \$1                    | <input type="checkbox"/> CHAPT ZU DI MITZIA "JACK-POT" \$1<br>"double your money back if not completely satisfied" | <input type="checkbox"/> 20 — ASST'ED WIREWOUND RESISTORS \$1<br>5, 10, 20 watt               | <input type="checkbox"/> 50 — TUBE CARTONS (colored) \$1<br>assorted sizes for Popular Tubes or—50 of any size you select |
| <input type="checkbox"/> 150—ASST. 8/32 SCREWS and 150—8/32 HEX NUTS \$1                    | <input type="checkbox"/> 50 — ASST. TERMINAL STRIPS \$1<br>all types, 1-lug to 6-lug                               | <input type="checkbox"/> 100 — ASST. MICA CONDENSERS \$1<br>some in 5%                        | <input type="checkbox"/> 10 — ASSORTED TUBES \$1<br>Radio, Television and Industrial                                      |
| <input type="checkbox"/> 150—ASST. 2/56 SCREWS and 150—2/56 HEX NUTS \$1                    | <input type="checkbox"/> 25 — INSTRUMENT POINTER KNOBS \$1<br>selected popular types                               | <input type="checkbox"/> TELEPHONE RECORDING DEVICE \$1<br>Instant suction cup fit            | <input type="checkbox"/> 10—TUNGSOIL 12FK6 TUBES \$1<br>brand new individually cartoned                                   |
| <input type="checkbox"/> 150—ASST. 4/40 SCREWS and 150—4/40 HEX NUTS \$1                    | <input type="checkbox"/> 5 — I.F. COIL TRANSFORMERS \$1<br>sub-min for Transistor Radios                           | <input type="checkbox"/> CRYSTAL LAPEL MICROPHONE \$1<br>high impedance, 200-8000 cps         | <input type="checkbox"/> ALL AMERICAN TUBE KIT \$2<br>Top Standard Brand — 12BA6, 12BE6, 12AV6, 50C5, 35W4                |
| <input type="checkbox"/> 150—ASST. 5/40 SCREWS and 150—5/40 HEX NUTS \$1                    | <input type="checkbox"/> 5 — AUDIO OUTPUT TRANSFORM \$1<br>Sub-min for Trans Radios                                | <input type="checkbox"/> \$15.00 RADIO PARTS "JACK-POT" \$1<br>handy assortment               | <input type="checkbox"/> 5—ASSORTED TRANSFORMERS \$1<br>Radio, TV and Industrial  |
| <input type="checkbox"/> 500—ASSORTED RIVETS \$1<br>most useful selected sizes              | <input type="checkbox"/> 4 — TOGGLE SWITCHES \$1<br>SPST, SPDT, DPST, DPDT   | <input type="checkbox"/> 5 — PNP TRANSISTORS \$1<br>general purpose, TO-5 case                | <input type="checkbox"/> 250 — WIRE-FEED-THRU GROMMETS \$1<br>3/16" L, 3/16" OD, 1/16" hole                               |
| <input type="checkbox"/> 500—ASSORTED WASHERS \$1<br>most useful selected sizes             | <input type="checkbox"/> 32—TEST PROD WIRE \$1<br>deluxe quality, red or black                                     | <input type="checkbox"/> 5 — NPN TRANSISTORS \$1<br>general purpose, TO-5 case                | <input type="checkbox"/> 250—TACK RUBBER BUMPERS \$1<br>3/8"—good for piece of wood cabinets                              |
| <input type="checkbox"/> 100 — ASST. RUBBER & FELT FEET FOR CABINETS \$1<br>best sizes      |  | <input type="checkbox"/> 15 — ASST. ROTARY SWITCHES \$1<br>all popular types \$20 value       | <input type="checkbox"/> FATHOM DEPTH PIECE OF EQUIPMENT \$1<br>loaded with good parts                                    |


MERCHANDISE WANTED in any quantity — TUBES (all types) — RADIO & TV PARTS — EQUIPMENT finished or unfinished — immediate cash.  
Please send samples, quotes & amounts — only new merchandise bought.
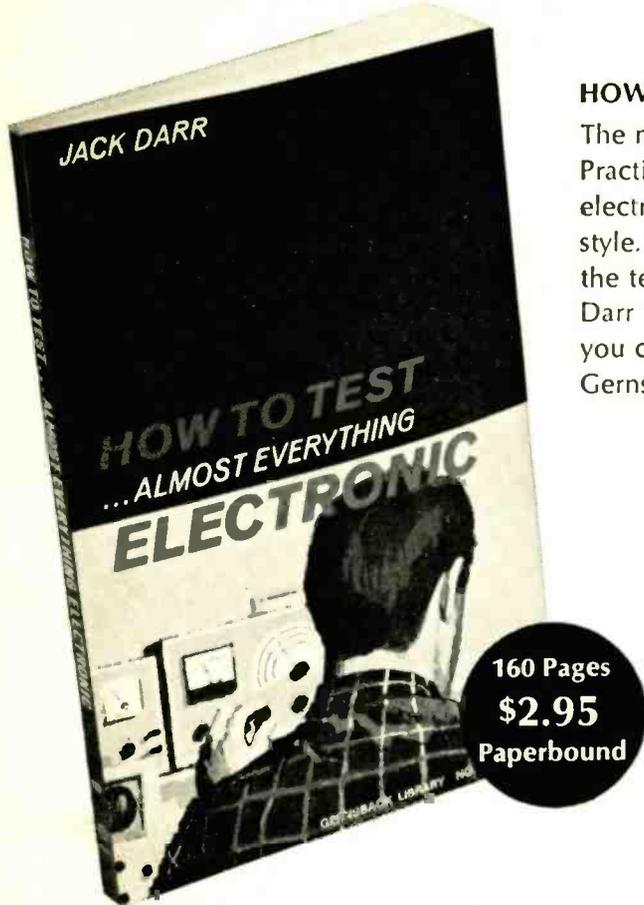
# Now...learn how to test and service electronics— read the new Darr Twins.


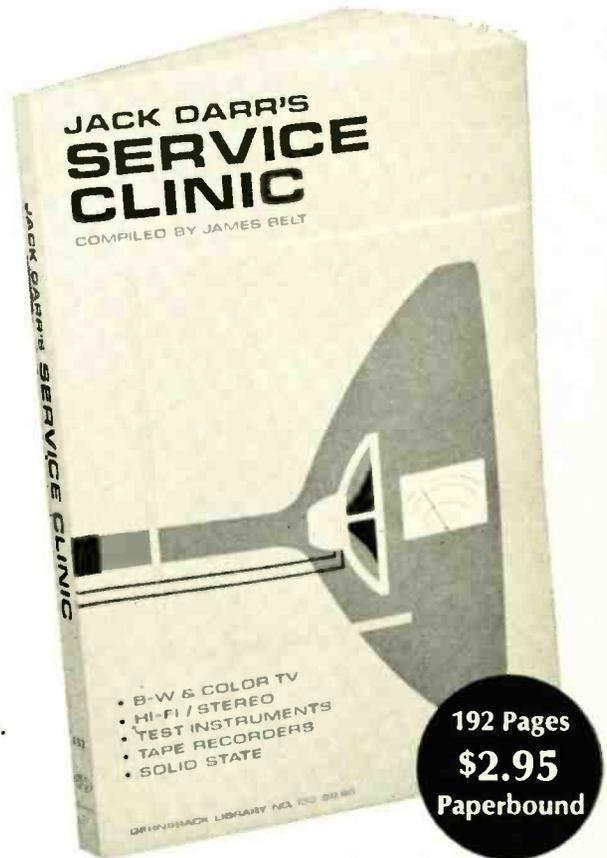
## HOW TO TEST ... ALMOST EVERYTHING ELECTRONIC

The most accurate title ever put on the cover of a book. Practically every testing technique for almost every kind of electronic equipment laid out for you in easy, highly readable style. Hundreds of illustrations make text crystal clear. With the test equipment you now own, and a few simple devices Darr shows you how to make easily and inexpensively, you can test faster and more accurately than ever. Gernsback Library #132.



## JACK DARR'S SERVICE CLINIC

Compiled by James Belt. The most helpful material from RADIO-ELECTRONICS Service Editor Jack Darr's monthly "Service Clinic." Every chapter contains distillations of concise and witty instruction about testing and troubleshooting, followed by actual reader questions and answers. Hundreds of questions selected for lasting usefulness and grouped under convenient categories for easy reference. Gernsback Library #133.

Available at your local Allied Radio, Federated Purchaser, Lafayette Radio, Newark Electronics, Radio Shack and dealer stores listed below, and other parts dealers.

CALIFORNIA  
Carousel Electronic Supply  
271 - 9th St.  
San Francisco

Elmar Electronics  
228 Charleston Rd.  
Mountain View

Henry Radio  
11240 W. Olympic Blvd.  
Los Angeles

Quement Industrial  
Electronics  
1000 Bascom Ave.  
San Jose

Zack Radio Supply Co.  
1444 Market St.  
San Francisco

HAWAII  
Radio TV Corp. Ltd.  
432 Keawe St.  
Honolulu, Oahu

NEW MEXICO  
Mannies Electronic Supply  
802 So. Soland Dr.  
Las Cruces

NEW YORK  
Arrow Electronics, Inc.  
900 Broad Hollow Rd.  
Farmingdale

Yonkers Electric Supply,  
Inc.

541 Nepperhan Ave.

Yonkers

OHIO

Custom Electronics, Inc.

1918 So. Brown St.

Dayton

Euclid Radio Co.

16379 Euclid Ave.

East Cleveland

Winteradio, Inc.

1468 W. 25th St.

Cleveland

PENNSYLVANIA

Cameradio Co.

1121 Penn. Ave.  
Pittsburgh

Olson Electronics  
3405 Saw Mill Run Rd.  
Pittsburgh

Radio Electric Service  
701 Arch St.  
Philadelphia

WASHINGTON  
Pearl Radio & Electronics  
1300 First Ave.  
Seattle

Radio Supply Co.  
6213 - 13th Ave. So.  
Seattle


# WHAT'S YOUR EQ?

These are the answers.

Puzzles are on page 66.
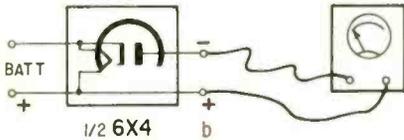
## Voltage Booster

The box contains an ordinary vacuum tube. Electrons leave the hot cathode with enough energy to reach the plate even though it is slightly more



negative. In a triode, the grid, rather than the plate, should be used. Using a vtvm, cathode-to-plate voltages up to 2.5 may be obtained. This voltage drops rapidly with load, but short-circuit currents over 100  $\mu$ A are normal.

## Shifted Tuning

The gang capacitor has been lubricated with machine oil. Starting from A (unmeshed blades), the rotor blades are free and the capacitor functions normally. At B (meshed), the blades are in contact with the reservoir of oil. Due to surface tension, oil evenly spreads between rotor and stator plates, acting as a dielectric, increasing the capacitance. Hence station frequencies are shifted. When the gang is tuned back to A, the blades are again free and the oil seeps out, restoring normal capacitance.

END

## 50 Years Ago

In Gernsback Publications  
From August, 1917  
Electrical Experimenter

Thunder-Storms and Lightning  
Rods

Women Radio Operators To Aid  
Uncle Sam

Unique Electrical Apparatus Reads  
the Mind

Details of a 20,000 Meter Un-  
damped Radio Receiver

Enjoy the "music-only" programs now available on the FM broadcast band from coast to coast.

- NO COMMERCIALS •
- NO INTERRUPTIONS •

It's easy! Just plug Music Associated's Sub Carrier Detector into multiplex jack of your FM tuner or easily wire into discriminator. Tune through your FM dial and hear programs of continuous commercial-free music you are now missing. The Detector, self-powered and with electronic mute for quieting between selections, permits reception of popular background music programs no longer sent by wire but transmitted as hidden programs on the FM broadcast band from coast to coast. Use with any FM tuner. Size: 5 1/2" x 9". Shipping weight approx. 7 lbs.

**KIT \$49.50**  
(with pre-tuned coils, no alignment necessary)

**WIRED \$75.00** (Covers extra \$4.95 ea.)

Current list of FM Broadcast stations with SCA authorization \$1.00

**MUSIC ASSOCIATED**  
65 Glenwood Road, Upper Montclair, N. J.  
Phone: (201)-744-3387 07043

Circle 122 on reader's service card

# Our policies are your best insurance:



Sonotone has been the reliable, quality name in replacement phono cartridges since 1947. We've made and sold 20 million of them. When you service with Sonotone cartridges, you can be assured you are servicing with the best. *We'll stake our name on that.*

**REPLACE WITH SONOTONE CARTRIDGES.** There's a complete line for immediate replacement of virtually every cartridge in use today. Prove it to yourself — fill out and mail coupon TODAY for your free copy of Sonotone's 1967 "computer-programmed" cartridge replacement manual.

Send today for complete information:

Sonotone Corporation, Dept. 107  
Elmsford, New York 10523


Just fill out and mail this coupon for your free copy of Sonotone's 1967 "computer-programmed" cartridge replacement manual.

YOUR NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_  
STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Circle 123 on reader's service card

COLOR TV is an important part of electronics and is (a mystery) (not very clear) to me. I should (study color) (pick it up on the job). I don't like dull textbooks, so I will (forget about color) (read the easy-to-understand programed primer on color coming in September RADIO-ELECTRONICS).

# ELECTRONICS

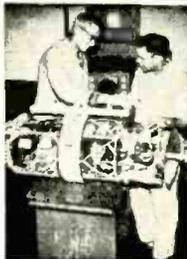

## Engineering-Technicians

**Bachelor of Science Degree, 30 Months**  
Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
  - Electrical Engineering (B.S. Degree)
  - Mechanical Engineering (B.S. Degree)
  - Civil Engineering (B.S. Degree)
  - Architecture (B.S. Degree)

Electronic Technicians, Radio TV Technicians is at an all time high. Heald Graduates are in demand for Preferred High Paying Salaries. Train now for a lucrative satisfying lifetime career.

**Approved for Veterans**


**DAY AND EVENING CLASSES**

Write for Catalog and Registration Application.  
New Term Starting Soon.

Your Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_

**HEALD COLLEGES**  
SINCE 1863  
1215 Van Ness Avenue  
San Francisco, California

Circle 124 on reader's service card

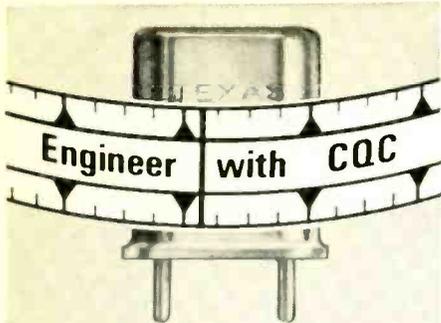

### MORE CONTROL

Control of quality throughout precision manufacturing gives you crystals that assure exact frequency control.

### MORE RELIABILITY

You'll stay on frequency better with CQC. And, you can rely on your CQC dealer to fill your needs promptly.

See your dealer for prices and data on CQC



## TEXAS CRYSTALS

Div. of Whitehall Electronics

1000 Crystal Drive  
Fort Myers, Fla. 33901

Plants in Fort Myers and Los Angeles

KNOW YOUR L's AND T's is good advice to anyone concerned with audio, hi-fi, stereo, PA, or tape recording. Want a pair of remote speakers in your backyard? Probably you'll use L or T pads for volume control. Here's a nuts-and-bolts rundown of what's available, how they work, and how to use them. Read it in September **RADIO-ELECTRONICS**.

## LIFE INSURANCE

ISSUED BY MAIL • KEEP IT FOR LIFE  
**MAIL THIS AD** NO OBLIGATION  
APPLICATION MAILED TO YOU

\$5000 ENTRY AGES 21 to 70 • \$2000 ENTRY AGES 21 to 80  
Whole Life Policy pays world-wide for death from any cause, any time, except during first policy year for either suicide or death from undisclosed pre-existing health conditions. Mail your name, address, zip code, year of birth and ad to Great Lakes Insurance Co., Elkin, Ill. 60120, Dept. HD125J6

## BIG CATALOG

World's "BEST BUYS" in GOV'T. SURPLUS Electronic Equipment

**BC-603 RECEIVER**—F.M. 20—27.9 MC. Continuous tuning and 10 preset push button channel selector. With sensitivity squelch & volume controls, 2 watt output to self contained speaker, one microvolt sensitivity, 2.65 KC I.F. 10 Tubes: 3/6AC7, 1/6J5, 2/12SG7, 2/6SL7, 1/6HG, & 1/6V6GT. Voltage required 12/24 volts for filaments, 220 VDC @ 80 MA for high volt. Size: 11½ x 6¼ x 12½". Wt.: **\$32.95**  
35 lbs. Used: \$44.95  
**BC-603 RECEIVER, CONVERTED to 30-45 MC. U: \$44.95**  
**AC POWER SUPPLY f/BC-603: Wired \$14.95 • Kit \$10.00**  
**DM-34 Dynamotor for 12 VDC operation . . . New: \$ 4.95**  
Prices F.O.B. Lima, O.—25% Deposit on COD's—BIG CATALOG—Send 25¢, Receive 50¢ credit on your order!

**FAIR RADIO SALES**  
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

# NOTEWORTHY CIRCUITS

## TRANSISTOR SLIDE CHANGER

A pause between taped commentary can be used to control your solenoid-actuated slide projector. You will recall this method was used in my "Silentac" electronic slide changer in the June 1964 issue. Here is a transistor version of the control circuit.

The circuit consists of two common-emitter amplifiers operated without bias. The control relay is in Q2's collector circuit. A signal from the recorder's speaker terminals is fed to the base of Q1. When there is no signal from the recorder, capacitor C1 is charged to full supply voltage and Q1 and Q2 are cut off as a result.

RY1 is not energized. Contact 1-2 of RY1 is closed, energizing RY2 and closing contact 5-6 on RY2; contact 3-4 of RY1 remains open. The control loop between terminals X and Y is normally held open by RY1 contact 3-4. The slide actuator is tripped by momentarily closing the loop.

When the recorded commentary



starts, Q1 saturates on negative half-cycles, drawing current through R1. This lowers the voltage on Q1's collector and permits C1 to discharge through diode D. The amplified signal drives Q2 to conduction, energizing RY1 to close contact 3-4 and open 1-2.

Although contact 1-2 is now open, RY2 remains energized for the period required for C2 to discharge through its coil. This delay is long enough to actuate the changer solenoid and project the first slide.

RY1 is energized and RY2 is not, as long as commentary continues. When there is a pause in commentary, C1 starts charging through Q2, keeping RY1 energized during the charging interval. When the pause exceeds a predetermined limit, Q2 cuts off and RY1 releases (drops out). Contact 1-2 closes, resulting in the sequence already described. When commentary resumes, a new cycle starts and the next slide is projected.

—W. G. Landrieu

END

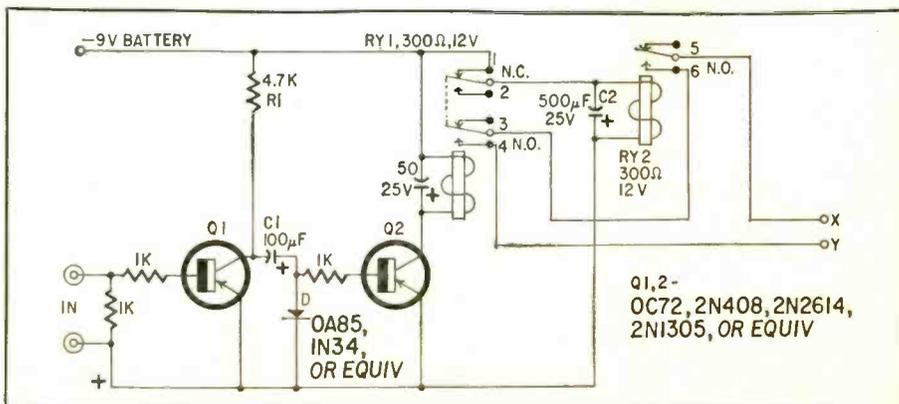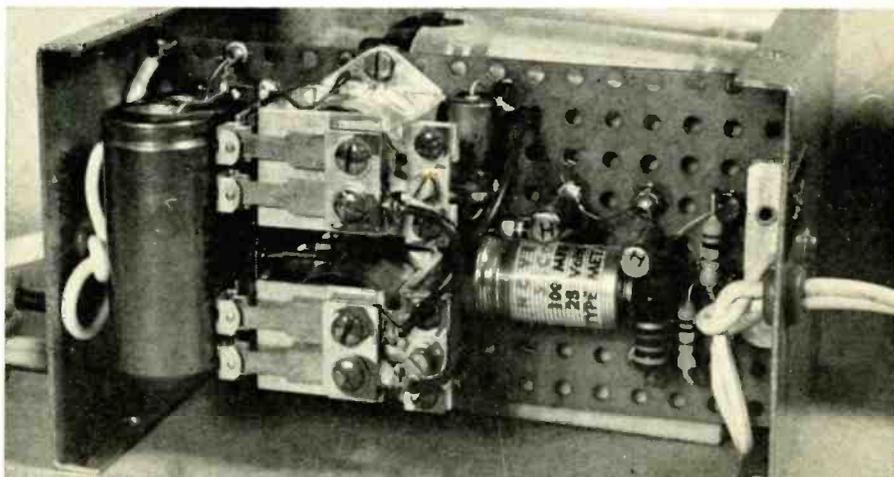

Solution to  
R-E Puzzler for  
July 1967

- |                   |                   |
|-------------------|-------------------|
| 1 autotransformer | 13 dosimeter      |
| 2 photoconductive | 14 thermionic     |
| 3 electroacoustic | 15 barretter      |
| 4 dopant          | 16 chromaticity   |
| 5 trinitistor     | 17 toroidal       |
| 6 additron        | 18 unidirectional |
| 7 demodulation    | 19 instability    |
| 8 transmitter     | 20 concentric     |
| 9 tertiary        | 21 substrate      |
| 10 padder         | 22 actinium       |
| 11 alligator      | 23 oscillation    |
| 12 epitaxy        | 24 photovaristor  |
- 25 Intermodulation

Subtract 4 points for any part you didn't answer correctly. Perfect score is 100.  
Your rating:

- |                         |                 |
|-------------------------|-----------------|
| 60-64 Fair              | 76-84 Middlin'. |
| 68-72 Fair to middlin'. | 88-96 Good.     |
- 100 Perfect! Tell your wife to bake a cake and celebrate!

By Edmund A. Braun

# NEW BOOKS

**ELECTRONICS DRAFTING WORKBOOK**, by Cyrus Kirshner and Kurt M. Stone. McGraw-Hill Book Co., 330 W. 42 St., New York, N. Y. 8½ x 11 in., 96 pp. Paper, \$4.50

Just what the name implies—a workbook. Page by page, the reader does his drawing right in the workbook. Can be used for self-study, although we feel its best use would come in connection with a suitable drafting textbook or with an instructor who can explain the assignments in a little more detail.

**PRINCIPLES OF AERIAL DESIGN**, by H. Page. D. Van Nostrand Co., Inc. 120 Alexander St., Princeton, N. J. 5½ x 8½ in., 172 pp. Leatherette, \$1.75

Published originally in London by Iliffe Books Ltd., this is a book for post-graduate engineers. The majority of the book is deeply mathematical, but the last chapter on practical forms of antennas is exactly that—practical. Almost any high-school graduate can learn about aeriels (antennas) from that section.

**MICROWAVE VALVES**, by I. C. H. Dix and W. H. Aldous. Iliffe Books Ltd., Dorset House, Stamford Street, London, S. E. 1, England. 5½ x 8½ in., 280 pp. Leatherette, \$7.70


On microwave tubes. Includes helix-type traveling-wave tubes of both low and high power. Also covers linear crossed-field tubes, cylindrical crossed-field tubes, amplifiers and magnetrons. Has supporting math, but depends heavily on cross-sectional sketches and diagrams to get the principles across. Smoothly written, well indexed.

END


# TRY THIS ONE
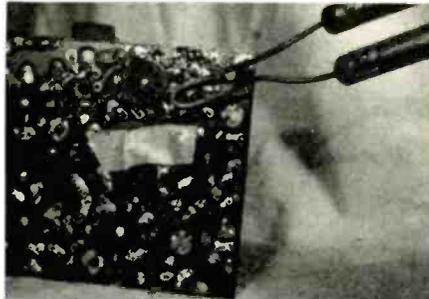
## MASKING TAPE AS SOLDERING AID

Recently, while making a connection on a vertical printed-circuit chassis, molten solder flowed down and shorted several circuits. I've since found masking tape a simple solution to the prob-



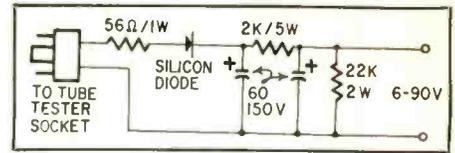lem. Just stick it tightly over the foil areas directly under the area being repaired. This prevents molten solder from falling on and shorting other surfaces.  
—Peter Legon



## BATTERY ELIMINATOR FROM TUBE TESTER

This kink is a real time saver when servicing tube-type battery portables. I use the filament-voltage output of my tube tester along with an outboard rectifier and filter as a B-battery eliminator. This saves time when the right battery is not available.

The diagram shows the circuit of the adapter. It supplies B+ voltages from 6 to 90. I adjust the output voltage with the filament-voltage selector. An octal tube base connects the adapter to the tube tester. You can connect the battery eliminator to the set through insulated clips or matching battery connectors.—Oscar Blair

END

# SCHOOL DIRECTORY



## Learn Electronics for your SPACE-AGE EDUCATION at the center of

America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech. in sunny Southern California.

**COLLEGE OF ENGINEERING.** Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

**A & P SCHOOL.** Practical experience on real aircraft. One-year course prepares you for F.A.A. A & P certificate. **WRITE TODAY FOR CATALOG.**

**NORTHROP INSTITUTE OF TECHNOLOGY**  
1199 W. Arbor Vitae, Inglewood, Calif.

## for a professional career

Tri-State graduates hold important engineering and business administration posts throughout the U. S. This professionally-oriented small college has outstanding placement record. Four-quarter year permits degree in three years. Excellent faculty. Well-equipped labs. Beautiful 300-acre campus. Accredited. Small classes. Modest costs. One-year Drafting-Design Certificate program. Enter Sept., Jan., March, June. For Catalog, write Director Admissions indicating career interest.

**TRI-STATE COLLEGE**  
2487 College Avenue, Angola, Indiana 46703



## Get Your First Class Commercial F. C. C. LICENSE

thru spare-time study by correspondence. Our money-back warranty protects your investment. (Approved for Veterans) Write for Brochure 67. It's free.

**Grantham School of Electronics**  
1505 N. Western Av., Hollywood, Cal. 90027

## GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology and Electronic Technology curricula both available. Assoc. degree in 20 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Sept., Feb. Terms. campus. High school graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Department C, Valparaiso, Indiana



Let **COYNE** Train You **AT HOME** for Big Pay in **TELEVISION** **RADIO** **COLOR TV**

## MAIL COUPON FOR FREE BOOK

Coyne Electronics Institute Dept. C7-C5  
1501 W. Congress Pkwy., Chicago, Ill. 60607  
Send FREE Book showing how I can get Coyne Quality Home Training in TV-Radio at Low Cost on Easy Terms.

Name.....  
Address.....  
City..... State..... Zip.....  
Phone..... Age.....

Put X here if interested in Resident School for Associate Degree in Electronics Engineering and Technology, or shorter courses in Electricity, Radio-TV, Electronics. Approved GI Bill. Spare time employment and tuition payment plans available.

# MARKET CENTER

## GENERAL

CONVERT ANY TELEVISION to sensitive Big-Screen Oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. RELCO-A25, Box 10563, Houston 18, Texas

TV SERVICE ORDER BOOKS for use with your rubber stamp. Duplicate or triplicate. Low cost. Write for FREE 32 PAGE CATALOG and Special Rubber Stamp Offer. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656

FREE ELECTRONICS (new and surplus) Parts catalog. We repair multimeters. BIGELOW ELECTRONICS, Bluffton, Ohio 45817



**TUNAVERTERS**  
POLICE, FIRE, AIR-CRAFT, MARINE AND AMATEUR CALLS ON YOUR BROADCAST RADIO! Tunable RF converters. 6-1 reduction tuning.

See complete listing in June RE, page 76  
HERBERT SALCH & CO., WOODSBORO REB, TEX. 78393



**CUT DOWN ON MOBIL IGNITION NOISE.**  
DON'T BE FOOLED BY IMITATIONS!  
Get the ORIGINAL

### SYDMUR SOLID STATE "CD" IGNITION SYSTEM!

High Quality Components used throughout. Fiberglass Printed Circuit Board. Unitized Construction. Simplified Kit Assembly.

Construction Article in Nov. 1966 Popular Electronics Thousands of satisfied customers.

Write for Free Literature TODAY.

COMPAC Assembled . . . \$34.75

COMPAC KIT . . . \$24.95

\*Add 75¢ for mailing and handling

N.Y. State Residents add Sales Tax

SYDMUR ELECTRONICS SPECIALTIES

1268 E. 12th St. Brooklyn, N.Y. 11230

PRINTING PRESSES, Type, Supplies. Lists 5¢.  
TURNBAUGH SERVICE, Mechanicsburg, Pa.

TREASURE HUNTERS! PROSPECTORS! Relco's new instruments detect buried gold, silver, coins. Kits, assembled models. Transistorized. Weighs 3 pounds. \$19.95 up. Free catalog. RELCO-A25, Box 10839, Houston, Texas 77018

## WANTED

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! BARRY, 512 Broadway, New York, N. Y. 10012, 212 WALKER 5-7000

WANTED: Radar Equipment AN/TPS-10D, APT-9, SCR-584, AN/GPG-1, M-33 etc., P. J. PLISHNER, 550 Fifth Avenue, N. Y. Tele: 212 JU 6-4691

**"TAB" • SILICON ONE-AMP DIODES**  
Full Leads Factory Tested & Gtd! U.S.A. Mfg

Piv/Rms	Piv/Rms	Piv/Rms	Piv/Rms
50/35	100/70	200/140	300/210
05	07	10	12
400/280	600/420	800/560	900/7630
14	21	30	40
1000/700	1100/770	1700/1000	2400/1680
50	70	120	200

TERMS: Money Back Guarantee Our 22nd Year. 52 Min. Add Shipping Charges  
111 GD LIBERTY ST., N. Y. 6, N. Y.  
Send 25¢ Phone: REctor 2-6245 for Catalog

## SALE ON ELECTRONICS BOOKS!

5 FOR \$3.98—  
\$16.50 VALUE

Guaranteed \$16.50 Value. Grab bag of 5 Gernsback electronics books on testing, test equipment, TV, radio, hi-fi, stereo, etc. Clearance of books which sell for as high as \$4.50. Guaranteed retail value of \$16.50. Retail prices clearly printed on covers. Send check or money order to: GRAB BAG DEPT. D87, Gernsback Library, Inc., 154 West 14th Street, New York, N.Y. 10011.

# ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

Allied Radio Corp. . . . .	87-88
Antenna Specialists Co., The (A Div. of Dynascan Industries, Inc.) . . . . .	27
Brooks Radio & TV Corp. . . . .	90-91
Burstein-Applebee Co. . . . .	85
Capitol Radio Engineering Institute, The . . . . .	28-31
Castle TV Tuner Service, Inc. . . . .	75
<b>CLASSIFIED</b> . . . . .	96-99
Cleveland Institute of Electronics . . . . .	26, 62-65, 91
Cornell-Dubilier . . . . .	Third Cover
Cornell Electronics Co. . . . .	98
Delta Products, Inc. . . . .	16
DeVry Institute of Technology . . . . .	5
Electro-Voice, Inc. . . . .	15
Electronic Measurement Corp. (EMC) . . . . .	69
Fair Radio Sales . . . . .	94
Finney Co. . . . .	81
GC Electronics Co. . . . .	14
Gernsback Library . . . . .	17, 78-79, 92, 97
Great Lakes Insurance Co. . . . .	94
Hallcrafters . . . . .	12
Heald Engineering College . . . . .	93
Health Company . . . . .	23
International Crystal Mfg. Co., Inc. . . . .	100
Judson Research and Mfg. Co. . . . .	76
Lafayette Radio Electronics . . . . .	68
Mallory Distributor Products Company (Div. of P. R. Mallory & Co., Inc.) . . . . .	13
Memory Studies . . . . .	75
Microflame, Inc. . . . .	69
Mosley Electronics, Inc. . . . .	83
Multicoore Sales Corp. . . . .	90
Music Associated . . . . .	93
National Radio Institute . . . . .	8-11
Nova-Tech, Inc. . . . .	80
Olson Electronics, Inc. . . . .	76
Pace Communications Corp. . . . .	84
Poly Paks . . . . .	99
Radio Shack . . . . .	1
RCA Electronic Components & Devices Semiconductors . . . . .	7
Tubes . . . . .	Fourth Cover
RCA Institutes, Inc. . . . .	18-21
Sams & Co., Inc., Howard W. . . . .	71
Sencore . . . . .	67, 89
Solid State Sales . . . . .	96
Sonotone Corp. (Electronic Applications Div.) . . . . .	93
Sprague Products Company . . . . .	77
Surplus Center . . . . .	80
Sylvania (Subsidiary of General Telephone & Electronics) . . . . .	24-25
Texas Crystals (Div. of Whitehall Electronics Corp.) . . . . .	94
Triplett Electrical Instrument Company . . . . .	Second Cover
Warren Electronic Components . . . . .	97
Weller Electric Co. . . . .	70
Xcelite, Inc. . . . .	22
<b>MARKET CENTER</b> . . . . .	96-99
Edmund Scientific Corp. . . . .	
Salch & Co., Herbert (Marketing Division of Tompkins Radio Products) . . . . .	
Sydmur Electronics Specialties . . . . .	
TAB . . . . .	
<b>SCHOOL DIRECTORY</b> . . . . .	95
Coyne Electronics Institute . . . . .	
Grantham School of Electronics . . . . .	
Northrop College of Science & Engineering . . . . .	
Tri-State College . . . . .	
Valparaiso Technical Institute . . . . .	

## INTEGRATED CIRCUITS



JK FLIP FLOPS . . . . . \$1.15  
DUAL NAND NOR GATES . . . \$1.00  
SR CLOCKED FLIP FLOPS . . . \$1.15  
SRT FLIP FLOPS . . . . . \$1.15  
EXPANDABLE OR GATES . . . \$1.00

TO-85 flat pack. Guaranteed to work. They come complete with schematic, elect. characteristic sheet and some typical applications.



POST OFFICE BOX 74 D  
SOMERVILLE, MASS. 02143

Send For Our Latest Catalog Featuring Transistors, Rectifiers And Components

1.25 Amp (Glass Amps)  
A controlled avalanche rectifier in which the PRV may be exceeded without destroying the rectifier.

PRV	AMP
100	.12
200	.15
400	.20
600	.25
800	.35
1000	.50

Top Hat & Epoxy

PRV	AMP
100	.07
200	.09
400	.12
600	.20
800	.25
1000	.50
1200	.65
1400	.85
1600	1.00
1800	1.20





Silicon Control Rectifiers  
TO-66 pack Studs

PRV	3A	7A	20A
50	.35	.50	.80
100	.50	.70	1.35
200	.75	1.05	1.90
300	1.25	1.60	2.45
400	1.50	2.10	2.85
500	1.75	2.80	3.50
600	2.00	3.00	
700	2.25	3.50	
1000		5.00	

Terms: FOB Cambridge, Mass. Send check or Money Order. Include Postage, Average Wt. per package 1/2 lb. Allow for C.O.D. Minimum Order \$3.00

Circle 143 on reader's service card
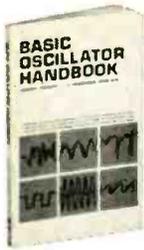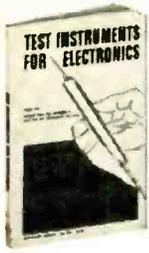
## Two new "know-how" books you'll want to read.



### Basic Oscillator Handbook

by Norman H. Crowhurst. A complete book on oscillators. When you need information on oscillators, you can stop hopping from book to book. This single volume makes you an oscillator expert. Basic Oscillator Handbook presents a fresh, clear-cut approach that you can understand and use immediately. Gives all the how's and why's of oscillators. 160 pages.

Order #130 .....\$2.95

### Test Instruments for Electronics

Edited by Martin Clifford in cooperation with the editors of Radio-Electronics. 24 experts tell you how to increase the efficiency and capabilities of your vom, vvm and scope. Teaches you how to build new, low-cost test instruments to supplement present equipment to extend their usefulness to perform tests you cannot do now. Test instruments for Electronics could be the most profitable \$2.95 buy you'll ever make just in terms of the time you'll save in one day's work.

Order #131 .....\$2.95

Order from your electronic parts distributor today, or mail to:

Gernsback Library, Inc., Dept. RE87  
154 West 14th Street, New York, N. Y. 10011

Send the following books:

- #130 (\$2.95)  
 #131 (\$2.95)

I enclose \$..... (prices 10% higher in Canada)

Name .....

Address .....

City ..... State ..... Zip .....

My distributor is .....

## AUDIO - HI-FI

RENT STEREO TAPES—over 2,500 different—all major labels—free brochure. STEREO-PARTI, 1616-R Terrace Way, Santa Rosa, Calif. 95404

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. HI-FIDELITY CENTER, 239R East 149th St., N.Y., N.Y. 10451

TAPE RECORDER SALE. Brand new, latest models, \$10.00 above cost. ARKAY SALES, 1028-E Commonwealth Ave., Boston, Mass. 02215

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. CARSTON, 1686-R Second Ave. N.Y.C. 10028

STEREO TAPES. Save up to 60% (no membership fees, postpaid anywhere USA). Free 60-page catalog. We discount batteries, recorders, tape accessories. Beware of slogans "not undersold." as the discount information you supply our competitor is usually reported to the factory. SAKITONE, 1776 Columbia Road, Washington, D. C. 20009

TAPEMATES makes available to you ALL 4-TRACK STEREO TAPES—ALL LABELS—postpaid to your door—at tremendous savings. For free brochure write TAPEMATES CLUB. 5727 W. Jefferson Blvd., Los Angeles, Calif. 90016

HI-FIDELITY COMPONENTS, Ham Marine and Communication equipment at considerable savings. If you want to save money write us for our low prices on all your needs. AIREX RADIO CORP., 132 (RE) Nassau St., New York, N.Y. 10038

HAMMOND Stereo Reverberation mechanisms—\$7. CAL'S, Box 234, Dearborn, Michigan 48121

LIKE MUSIC WITHOUT COMMERCIALS? Completely wired 67 KHz SCA (background music) adapter Model SCA-2 for \$34.95. Five tuned circuits, two silicon transistor amplifier and ratio detector. Four connections to your FM receiver. Instructions included—No adjustments. Operates on 6 to 12 Volts DC. Size: 2 1/2 x 3 x 3/4 inches. Dealer inquiries invited. Available installed in a nationally advertised six tube AM-FM radio for \$59.95. Also available installed in a nationally advertised ten transistor AM-FM portable for \$79.95. Texas residents add 2% sales tax. KENZAC CO., P.O. Box 66251, Houston, Texas 77006

## INVENTIONS & PATENTS

INVENTIONS-IDEAS developed: Cash/Royalty sales. Member: UNITED STATES CHAMBER COMMERCE, Raymond Lee, 130-U W. 42nd, New York City 10036

## BUSINESS AIDS

JUST STARTING IN TV SERVICE? Write for FREE 32 PAGE CATALOG of Service Order books, invoices, job tickets, phone message books, statements and file systems. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656.

1,000 Business Cards, "Raised Letters" \$3.95 postpaid. Samples. ROUTH, 5717 Friendswood, Greensboro, N. C. 27409

## ELECTRONICS

BARGAINS in Canadian Electronic equipment and surplus. Send \$1.00 for giant catalogs. ETCO, Box 741, Dept. R, Montreal, Canada

PROFESSIONAL ELECTRONICS PROJECTS—\$1 up. Catalog 25¢. PARKS, Box 25565A, Seattle, Wash. 98125

TUBES, "Oldies", latest. Lists free. STEINMETZ, 7519 Maplewood, Hammond, Indiana 46324

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, California 92105

TRANSISTORS-DIODES—Components. Large selection. Write for FREE catalogue. ELECTRONIC COMPONENTS CO. Box 2902B, Baton Rouge, La. 70821

## UNUSUAL BARGAINS

... MANY U. S. GOV'T SURPLUS

### GIANT WEATHER BALLOONS



"Balls of fun" for kids, traffic stoppers for stores, terrific for amateur meteorologists. Create a neighborhood great backyard fun. Exciting beach attraction. Made of heavy duty neoprene. Inflate with vacuum cleaner or auto air hose, or locally available helium for high rise.  
Book No. 60,56EH  
(8' diam.) \$2.00 Ppd.  
Stock No. 60,632EH  
(16' diam.) \$7.00 Ppd.

### NEW SURPLUS NI-Cd BATTERIES

Save more than 50%! Long life—accept 300 charge and discharge cycles. 1.25 volts per cell—750 milliamper hours capacity. Excel. charge retention. Hermetically sealed. Indefinite storage life. Multiple cells welded in series—easily cut. Combine to form btry. 7/8" dia. x 1-5/8" high. Spec. Price for 100 up. Low-cost charger separate.

Order #	Cells	DC Volt.	Price Ppd.
40,086EH	1	1.25	\$ 1.50
40,087EH	2	2.50	2.75
60,632EH	3	3.75	5.00
60,634EH	4	5.00	4.80
70,812EH	Trickle Charger (1-10 cells)		10.95

### DUPONT PLASTIC LIGHT GUIDE KIT



Experiment with amazing new plastic fiber optic light guides. 1001 uses for mfrs., experimenters, hobbyists. Use for exciting new projects and products. Guides transmit light same as wire conduct electricity. Use to illuminate remote areas, multiple locations from single source, confine light to small areas, conduct sensing and control systems. Inc. two 2' guides, source, lens, diode, connectors. Stock No. 70, 855EH \$10.00 Ppd.

Order by Stock No. Check or M. O.—Money-Back Guarantee. EDMUND SCIENTIFIC CO., Barrington, N. J. 08007

### CLIP AND MAIL COUPON TODAY

#### SEND FOR FREE CATALOG "EH"

Completely new 1967 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many war surplus items; for hobbyists, experimenters, workshop, factory. Mail coupon for catalog "EH".



NAME .....

ADDRESS .....

CITY ..... STATE ..... ZIP .....

Circle 144 on reader's service card

## SILICON RECTIFIER SALE

IMMEDIATE DELIVERY

FULLY GTD NEWEST TYPE  
AMERICAN MADE FULLY TESTED

1 AMP SILICON "TOPHAT" & EPOXY DIODES

LOW LEAKAGE FULL LEAD LENGTH

PIV/RMS	PIV/RMS	PIV/RMS	PIV/RMS
50/35	100/70	200/140	300/210
.05 ea.	.07 ea.	.10 ea.	.12 ea.
400/280	500/350	600/420	700/490
.14 ea.	.19 ea.	.25 ea.	.25 ea.
800/560	900/630	1000/700	1100/770
.30 ea.	.40 ea.	.50 ea.	.70 ea.

ALL TESTS AC & DC & FWD & LOAD

SILICON POWER DIODE STUDS

D.C. AMPS	50 PIV	100 PIV	150 PIV	200 PIV
	35 RMS	70 RMS	105 RMS	140 RMS
3	.08 ea.	.12 ea.	.16 ea.	.22 ea.
12	.25	.50	.65	1.75
35	.65	1.25	1.25	1.40
100	1.00	1.20	1.50	1.75
160	2.50	3.00		3.75

D.C. AMPS	300 PIV	400 PIV	500 PIV	600 PIV
	210 RMS	280 RMS	350 RMS	450 RMS
3	.27 ea.	.30 ea.	.37 ea.	.45 ea.
12	.90	1.30	1.60	1.95
35	2.00	2.35	2.60	3.00
100	2.50	3.50	4.00	5.00
160	4.25	4.75		6.10

"SCR" SILICON CONTROLLED RECTIFIERS "SCR"		"SCR"	
PRV AMP	AMP AMP	PRV AMP	AMP AMP
7	25	16	25
25	.50	75	1.00
50	.60	90	1.25
100	.80	1.25	1.50
150	.90	1.60	2.00
200	1.25	1.80	2.25
		250	1.75
		300	2.00
		400	2.40
		500	2.75
		600	3.00
		800	3.40
		1000	4.00
		1500	4.50

SPECIALS! SPECIALS!

Westinghouse 160 AMP, 500 PIV SILICON HI-POWER STUO RECTIFIER IN1666.

Limited quantity. \$5.10 ea. 10 for \$45.00

100 Different Precision Resistors

1/2—1—2 Watt 1/2%—1% TOL \$1.25

Asst transistor Kit. P.N.P.—N.P.N.

All popular types. Unchecked

100 for \$2.95 500 for \$9.95

Computer Grade Condenser 15,500 MFD

12 VDC American Mfg. .75 ea.

Type IN34 DIODE GLASS .07 ea 100 for \$5

Money Back guarantee. \$2.00 min. order. Include additional \$ for postage. Send check or money order. C.O.D. orders 25% down.

Warren Electronic Components

230 Mercer St., N. Y., N. Y. 10012 • 212 OR 3-2620

Circle 145 on reader's service card

# MARKET CENTER

RECEIVING & INDUSTRIAL TUBES, TRANSISTORS, All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request FREE Giant Catalog and SAVE! ZALYTRON, 469 Jericho Turnpike, Mineola, N.Y. 11501

FREE Catalog. Electronic parts, tubes. Wholesale. Thousands of items. Unbeatable prices. ARCTURUS ELECTRONICS RE, 502-22 St., Union City, N. J. 07087

Discharge IGNITION, PHOTOFLASH. Free catalog parts, kits. TRANSPARK, Carlisle, Mass. 01741

"CRYSTAL EXPERIMENTER'S" Handbook—50¢. Catalog LABORATORIES, 12041-B Sheridan, Garden Grove, Calif. 92640

ELECTRONIC PARTS! Components, transistors, diodes, kits, relays, and many special items. Guaranteed. Send 25¢ for 100 page catalog. GENERAL SALES CO., P.O. Box 2031C, Freeport, Texas 77541

MESHNA'S TRANSISTORIZED CONVERTER KIT Converts car radio to receive police & fire. 35-50Mc or 100-200Mc. (one Mc tuning) with simple step instructions \$5.00. MESHNA, No. Reading, Mass. 01864

SURPLUS SEMICONDUCTORS and miniature electronic parts. Send 25¢ for catalog. ECD COMPANY, P.O. Box 1432, Plainfield, N. J. 07061

TV CAMERAS: Assembled and kits. Also plans, vidicons, lenses, scan coils, etc. NEW catalog 10¢. ATV RESEARCH, Box 453, Dakota City, Nebr. 68731

GIANT JAPANESE ELECTRONICS CATALOG. \$1. DEE, 10639A Riverside, North Hollywood, Calif. 91602

CATHODIC Protection instructions \$1.00. F. F. KNAPP, P.O. Box 854, Scottsdale, Arizona 85252

## WHEN YOU ORDER MERCHANDISE BY MAIL . . .

- Be sure to include your name and address. Include your zip code number.
- Type or print if you can—if not, write clearly.
- Don't send cash! Remit by check or money order.
- Include allowances for postage charges if you know the weight of what you're ordering.
- Mention you saw it in

## RADIO-ELECTRONICS

CB POWER BOOSTER—THE POWSEFORMER. Increase radiated output, modulation, and receiver sensitivity. Connects between wall plug and rig. Great for all AC rigs. Send \$8.95 ppd. DYNAMIC DEVELOPMENT, Dept. 103, P.O. Box 2084-D, Pasadena, Calif. 91105

SAVE ON DIODES. If you use germanium or silicon diodes in quantities of 5000 to a million, get our low, low prices. Send specs or request samples. RUTLAND MANUFACTURING CO., Watertown, Mass. 617-924-8000

### 8 PIECE TOOL KIT

69¢  
-10 Shipping  
contains  
4 Bristle  
Wrenches  
1 Hex Blade  
2 Alignment  
(tuning) Tools

in original mfr's bags and boxes

# CORNELL

## TUBES

### 1 YR. GUARANTEED

Mutual Conductance Lab-tested, Individually Boxed, Branded and Code Dated, Tubes are new, or used and so marked.

# 33¢

PER TUBE

100 TUBES OR MORE:  
**30¢ PER TUBE**

**Special!**  
With every \$10 Order

# 25¢

per tube

(No Limit) from this list  
6AG5 6SN7  
6AQ5 6CB6 6S4  
6AU6 6J6 6W4

NEW! EASY TO USE!  
**COLOR TV DEGAUSSER** \$3.95  
plus 40¢ shipping

**INTERFERENCE TV TRAPPER**  
SUPPRESS PICTURE INTERFERENCE CAUSED BY:  
• AUTO IGNITION  
• AIRPLANES  
• APPLIANCES  
• NEON SIGNS  
• OIL BURNERS  
• AMATEUR RADIO TRANSMITTERS

**TV LIFESAVER!**  
STOP TUBE BURNOUTS!

PROTECTS TV TUBES FROM BURNOUT!  
SAVES COSTLY SERVICE CALLS!  
SAVES YOU MONEY!  
SAVES YOUR SERVICE!  
SAVES YOUR TV!  
SAVES YOUR TIME!  
SAVES YOUR NEIGHBORS!  
SAVES YOUR EYES!  
SAVES YOUR HEARING!

**\$1.79**  
+ 20¢ shipping.

**SILICON RECTIFIERS**

all purpose **ELECTRONIC CLEANER** 89¢  
plus 20¢ shipping

**TUBE CARTONS**  
HIGH GLASS CLAY COATED PER FORBUSH WITH BUILT IN DIAGONAL PARTITIONS

SIZE	FOR TUBE SIZE	PRICE PER 10 CARTONS	PRICE PER 100 CARTONS
NO. 1	6A5	.29	2.59
NO. 2	6A6	.39	3.49
NO. 3	6A7	.59	5.29
NO. 4	6A8	.89	7.99

**TUBE SUBSTITUTES** \$1.25

Other tubes at low prices—send for free list

OZ4	6A55	6CD6	6K6	6X4	12BF6
1B3	6AT6	6CF6	6K7	6X8	12BH7
1J3/1K3	6AT8	6CG7	6Q7	7A7	12BL6
1H5	6AU4	6CG8	6S4	7A8	12BY7
1L4	6AU5	6CM7	6SA7	7B6	12C5
1T4	6AU6				12CA5
1U4	6AV6				12SN7
1X2	6AW8				12SQ7
3BZ6	6AX4				25L6
3DG4	6BA6				25Z6
5U4	6BC5				35W4
5UR	6BD6	6CZ5	6SH7	7C5	35Z3
5V4	6BG6	6D6	6S17	7N7	50L6
5Y3	6BJ6	6DA4	6SK7	7Y4	24
6A6	6BL7	6DE6	6SL7	12AD6	27
6AB	6BN4	6D06	6SN7	12AE6	77
6AB4	6BN6	6EA7	6SQ7	12AF6	78
6AC7	6B06	6EM5	6SR7	12AT7	84/6Z4
6AG5	6BQ7	6F6	6U7	12AU7	36B7
6AK5	6RZ6	6GH8	6U8	12AX7	6350
6AL5	6C4	6H6	6V6	12BA6	6463
6AN8	6C6	6J5	6W4	12BD6	7044
6AQ5	6CB6	6J6	6W6	12BE6	

**RADIO-TV TUBE TESTER** 2.89  
plus 10¢ shipping

TEST and REPAIR TV & RADIO SETS APPLIANCES

**BARGAIN CORNER**

Solder Iron 1.49  
Elect Tape .89  
Epoxy (pr.) .79  
Diode Kit .39  
Noise Filter .89  
Neon Tester .59  
Solder .39  
Antenna Coupler 1.89  
Battery Charger 4.95

**Prestige & Success are yours as an ELECTRONIC EXPERT**

FOR CORNELL CUSTOMERS ONLY by special arrangement with the publisher, these amazing bargains are available.

COMPLETE RADIO SERVICING AND BASIC ELECTRONICS COURSE ONLY \$3.00 (\$2.50 + 50¢ postage charge)

NEW PRACTICAL TV TRAINING COURSE ONLY \$3.50 (\$3.00 + 50¢ postage charge)

Both above courses \$6.00

## CORNELL ELECTRONICS CO.

Dept RE 8 4217 University Ave., San Diego, Calif. 92105

TERMS: Add 3¢ per tube shipping. Orders under \$5.00 add 3¢ per tube shipping plus 50¢ handling. Canadian orders add approximate postage. Send 25¢ deposit on C.O.D. orders. No C.O.D. orders under \$5.00 or to Canada. No 24 hr. free offer on personal check orders. 5-DAY MONEY BACK OFFER.

Circle 146 on reader's service card

SEND FOR FREE CATALOG

DIAGRAMS Television-Radio, all different, 10 lbs. carton, \$5.99, postpaid. BEITMAN, 1760 Balsom, Highland Park, Illinois 60035

BRAND NEW TUBES. World's lowest prices on Radio, TV-Industrial-special purpose tubes. Write for free parts catalog. UNITED RADIO CO., Newark, N.J. 07101

## GOVERNMENT SURPLUS

72 page illustrated Government Surplus Radio, Gadgets Catalog 25¢. MESHNA, Nahant, Mass. 01908

## EDUCATION/ INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING. New home study course covering all makes electronic organ including transistors. Experimental kits—schematics—trouble-shooting. Accredited NHSC-GI Approved. Write for free booklet. NILES BRYANT SCHOOL, 3631 Stockton Blvd., Dept. F. Sacramento 20, Calif.

CORRESPONDENCE COURSES—B.Sc., Engineering, Electronics, Catalog \$1. CANADIAN INSTITUTE OF SCIENCE & TECHNOLOGY, 263E Adelaide St. W., Toronto

WANTED! TV-RADIOMEN to learn aircraft electronics servicing. Numerous job openings everywhere. Write: ACADEMY AVIONICS, Reno/Stead Airport, Reno, Nevada

SLEEP LEARNING. Hypnotism! Tapes, records, books, equipment. Details, strange catalog FREE. RESEARCH ASSOCIATION, Box 24-RD, Olympia, Wash.

HIGHLY EFFECTIVE HOME STUDY COURSE in Electronics Engineering Mathematics with circuit applications. Earn your Associate in Science degree. Free literature. COOK'S INSTITUTE OF ELECTRONICS ENGINEERING, P.O. Box 36185, Houston, Texas 77036 (Established 1945.)

HIGHLY EFFECTIVE HOME STUDY REVIEW for FCC commercial phone exams. Free literature. COOK'S SCHOOL OF ELECTRONICS, P.O. Box 36185, Houston, Texas 77036

ASSOCIATE DEGREE IN ELECTRONICS earned, first half by correspondence and second half in residence. Free catalog. GRANTHAM INSTITUTE, 1505 N. Western Ave., Hollywood, Calif. 90027

FCC First Class License in six weeks—nation's highest success rate—approved for Veterans Training. Write ELKINS INSTITUTE, 2603E Inwood Road, Dallas, Texas 75235

## SERVICES

Transistorized products dealers catalog. \$1. INTERMARKET, CPO 1717, Tokyo, Japan.

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services): 60¢ per word . . . minimum 10 words.

NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items): 30¢ per word . . . no minimum.

Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for September issue must reach us before July 10th.

WORD COUNT: Include name and address. Name of city (Des Moines) or state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8-10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

## CLASSIFIED ADVERTISING ORDER FORM

For complete data concerning classified advertising please refer to box elsewhere in Market Center section.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

{ @ .30 Non-Commercial Rate }  
No. of Words { @ .60 Commercial Rate } = \$

Total Enclosed \$ \_\_\_\_\_  
Insert \_\_\_\_\_ time(s)  
Starting with \_\_\_\_\_ Issue  
Payment must accompany order unless placed through accredited advertising agency 87

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 154 WEST 14TH ST., NEW YORK, N.Y. 10011

# MOVIN'SALE

3 BULGING WAREHOUSES

We will have 2 Places to serve you soon

**DOUBLE BONUS** PLUS CHOOSE ANY \$100 ITEM FREE

**\$25** WORTH OF TRANSISTORS, RECTIFIERS, RESISTORS, CONDENSERS, DIODES & ETC.

Add 25¢ for handling

BOTH FREE WITH ANY \$10 ORDER

1 AMP  800 PIV TOP HAT RECTIFIERS **5 for \$1**

400 mc NPN SILICON **5 for \$1** 2N706

Watts | V<sub>cb</sub> | I<sub>cr</sub> | I<sub>ma</sub>  
1.5 | 30 | 20 | 300 | 150

## FACTORY TESTED \$1 SEMI-KON-DUCTORS

- 2-85 WATT 2N424 PLANAR, silicon, TO-53 npn
- DUAL TRANSISTORS  PNP (2N2807)  NPN 2N2060
- 3-40W NPN SILICON MESA 2N1618 transistor . \$1
- 4 2N170 TRANSISTORS, by GE, npn for gen'l rf . \$1
- 10 3Amp RECT's, studs, silicon, to 800 V no test \$1
- 4-2N255 POWER TRANSISTOR EQUALS . \$1
- 10 PNP SWITCHING TRANSISTORS, 2N104, no test \$1
- 2N3088 "N" Channel FET'S Very High Input Z \$1
- 5 2N107 TRANS'RS, by GE, npn, pop, audio jnk . \$1
- 3-2N1613 3W NPN SIL, 120 mc, by "theem" . \$1
- 3-45AMP POWER RECTIFIERS, stud, silicon . . . \$1
- 10 PNP SWITCHING TRANSISTORS, no test .TO5 \$1
- 4 2N43 OUTPUT TRANSISTORS, by GE, npn, TO5 \$1
- 1-IGNITION SWITCHING TRANSISTORS, 10-AMP \$1
- 25 GERMANIUM & SILICON DIODES, no test . . \$1
- 25 TOP HAT RECTIFIERS, silicon, 750ma, no test \$1
- 2-1000 MC-TRANSISTOR 2N918 NPN SILICON \$1
- 4 2N333 NPN SILICON transistors, Transistron \$1
- 4 BIDIRECTIONAL TRANSISTORS, 2N1641 . . . . . \$1
- 10 NPN SWITCHING TRANSISTORS, 2N338 no test \$1
- 15 PNP TRANSISTORS, CK722, 2N35, 107, no test \$1
- 15 NPN TRANSISTORS, 2N35, 170, 440, no test . . \$1
- 30 TRANSISTORS, rf, lf, audio osc-ifs, TO5 no test \$1
- 10 FAMOUS CK722 TRANSISTORS, npn no test . . . \$1

1-Amp TOP HAT AND EPOXIES					
PIV	Sale	PIV	Sale	PIV	Sale
50	5¢	600	19¢	1400	69¢
100	7¢	800	25¢	1600	89¢
200	9¢	1000	45¢	1800	99¢
400	11¢	1200	59¢	2000	1.50

## WORLD'S MOST POPULAR \$1 PARTS PAKS

- 30 "YELLOW" MYLAR CONDENSERS, asstd val \$1
- 60 CERAMIC CONDENSERS, discs, npn's, to .05 \$1
- 60 TUBULAR CONDENSERS, to .5mf, to 1Kv, asst \$1
- 40 DISC CONDENSERS, 27mmf to .05mf to 1KV \$1
- 60 TUBE SOCKETS, receptacles, plugs, audio, etc. \$1
- 30 POWER RESISTORS, 5 to 50W, to 24 Kohms. \$1
- 65 HALF WATTERS, asst incl: A.B., 5% too! . . \$1
- 60 HI-O RESISTORS, 1/2, 1, 2W, 1% & 5% values \$1
- 10 VOLUME CONTROLS, to 1 meg, switch too! . \$1
- 10 ELECTROLYTICS, to 500mf, asst FP & tubulars \$1
- 50 RADIO & TV KNOBS, asstd, colors & styles . \$1
- 4 TRANSISTOR TRANSFORMERS, asst, worth \$25 \$1
- 40 PRECISION RESISTORS, 1/2, 1, 2W, 1% values \$1
- 40 CORNING "LOW NOISE" resistors, asst. . . \$1
- 10 PHONO PLUG & JACK SETS, tuners, amps . \$1
- 50 TERMINALSTRIPS, 1 to 8 solder lug types . \$1

**'GLASS AMP' ★** Handles PIV Sale  
2 Amps 50 7¢  
100 9¢  
**ONE AMP** A controlled avalanche rectifier 200 11¢  
**SILICON** the rated 400 13¢  
**RECTIFIERS** PRV may be exceeded without the rectifier breaking down. 600 19¢  
800 29¢  
1000 45¢

→ MONEY BACK GUARANTEE ←

10¢ FOR OUR "FALL" BARGAIN CATALOG ON:  
 Semiconductors  Poly Paks  Parts

**POLY PAKS**

TERMS: send check, money order, include postage—avg. wt. per pak 1 lb. Rated, net 30 days. CODs 2-5¢

P.O. BOX 942R  
50, LYNNFIELD, MASS. 01940  
"PAK-KING" of the World

Circle 147 on reader's service card

# Meet The Dividers!


## ICD SERIES INTEGRATED CIRCUIT DIVIDERS

They are new from International. Use them for crystal controlled time bases, scope calibrators, and clock sources.

International ICD units are totally integrated circuit frequency dividers. They are smaller than a pack of cigarettes (1" x 2¼" x 2¾"). All have two separate outputs. They are packaged in nine types providing divide ratios 2 thru 10. No tuning or adjustment is required. The output pulse has the same stability as the driving pulse. Voltage required, 3.6 vdc  $\pm$  10%.

### FREQUENCY RANGE

ICD-10 to 10 MHz	\$19.95 ea.
ICD-2 thru ICD-9 to 2 MHz	\$19.95 ea.
ICD Buffer (for feeding more than one circuit)	\$ 9.95 ea.

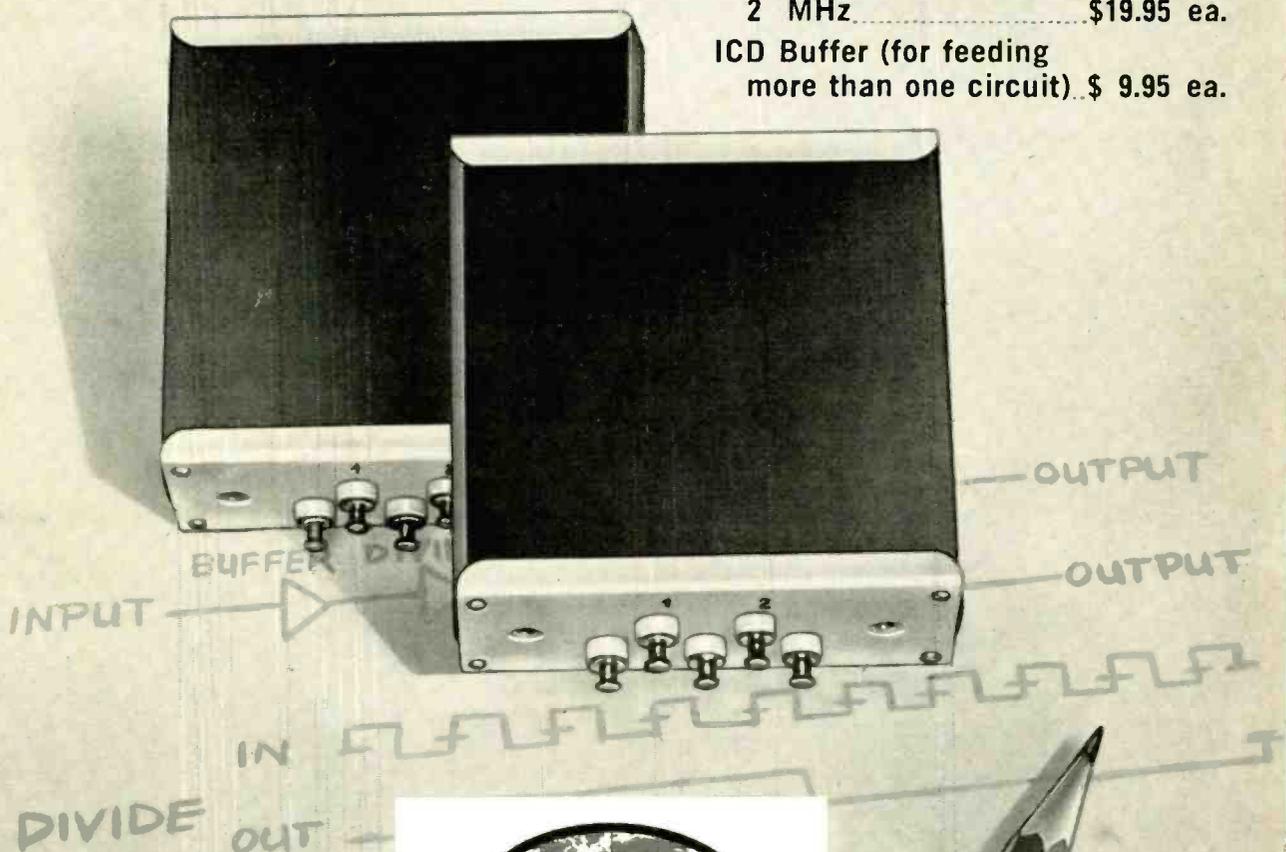

WRITE FOR COMPLETE CATALOG.

**INTERNATIONAL**  
CRYSTAL MFG. CO., INC.  
10 NO. LEE • OKLA. CITY, OKLA. 73102

# NO REWARD THE EXACT KID



Be on the lookout for the Wide Ranger. He represents CDE's wide-range electrolytic program in the TV serviceman's never ending fight for easier, faster, more profitable service calls.

It doesn't pay you to go looking for the Exact Kid—any Exact Kid.

The Wide Ranger's 200-plus replacement electrolytics do the job of the Exact Kid's thousands. So your distributor always has the wide range electrolytic you need, in stock.

That's why everybody calls the CDE **WIDE RANGER\*** a Good Guy.

**CDE** CORNELL-DUBILIER



Service your Color TV customers with confidence...  
with RCA HI-LITE picture tubes!

Customer satisfaction... and consequently your service reputation... can very often depend on the quality of the replacement parts you use. When it comes to replacement picture tubes, you can depend on an RCA HI-LITE for picture brightness and color fidelity at its finest. Install them and you literally "up-date" your customer's set with the same quality... the same tubes... that go into today's original equipment sets.

Enjoy the confidence of offering the best. Rely on RCA picture tubes to protect your service reputation. They are designed to protect the biggest reputation in the Color TV industry.

RCA Electronic Components and Devices, Harrison, N. J.



The Most Trusted Name in Electronics

