

60c ■ SEPT. 1967


Radio-^{IND}Electronics

TELEVISION · SERVICING · HIGH FIDELITY

HUGO GERNSBACK, Editor-in-chief

A
GERNSBACK
PUBLICATION


ABC's of Color TV

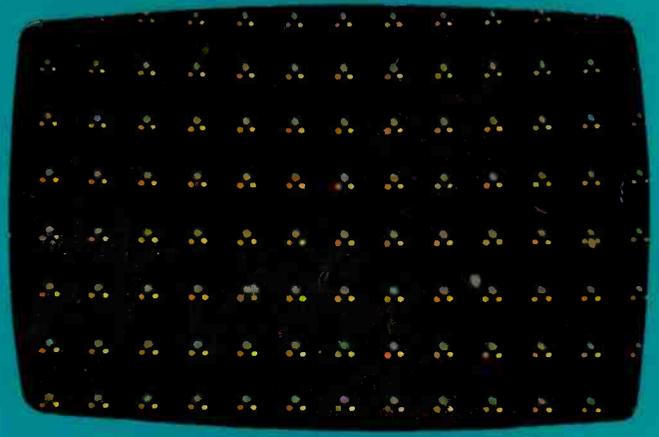


Creative Servicing



Transistor Servicing

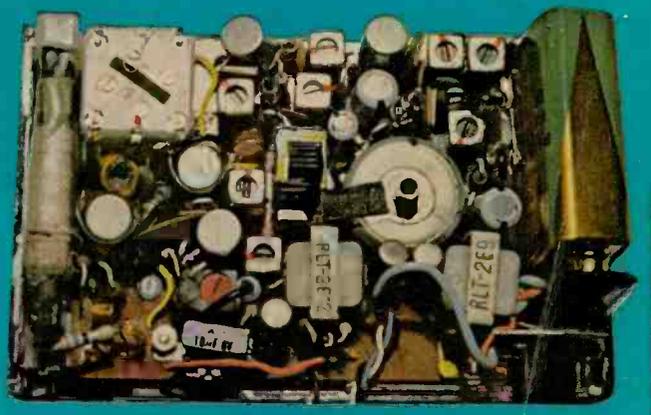

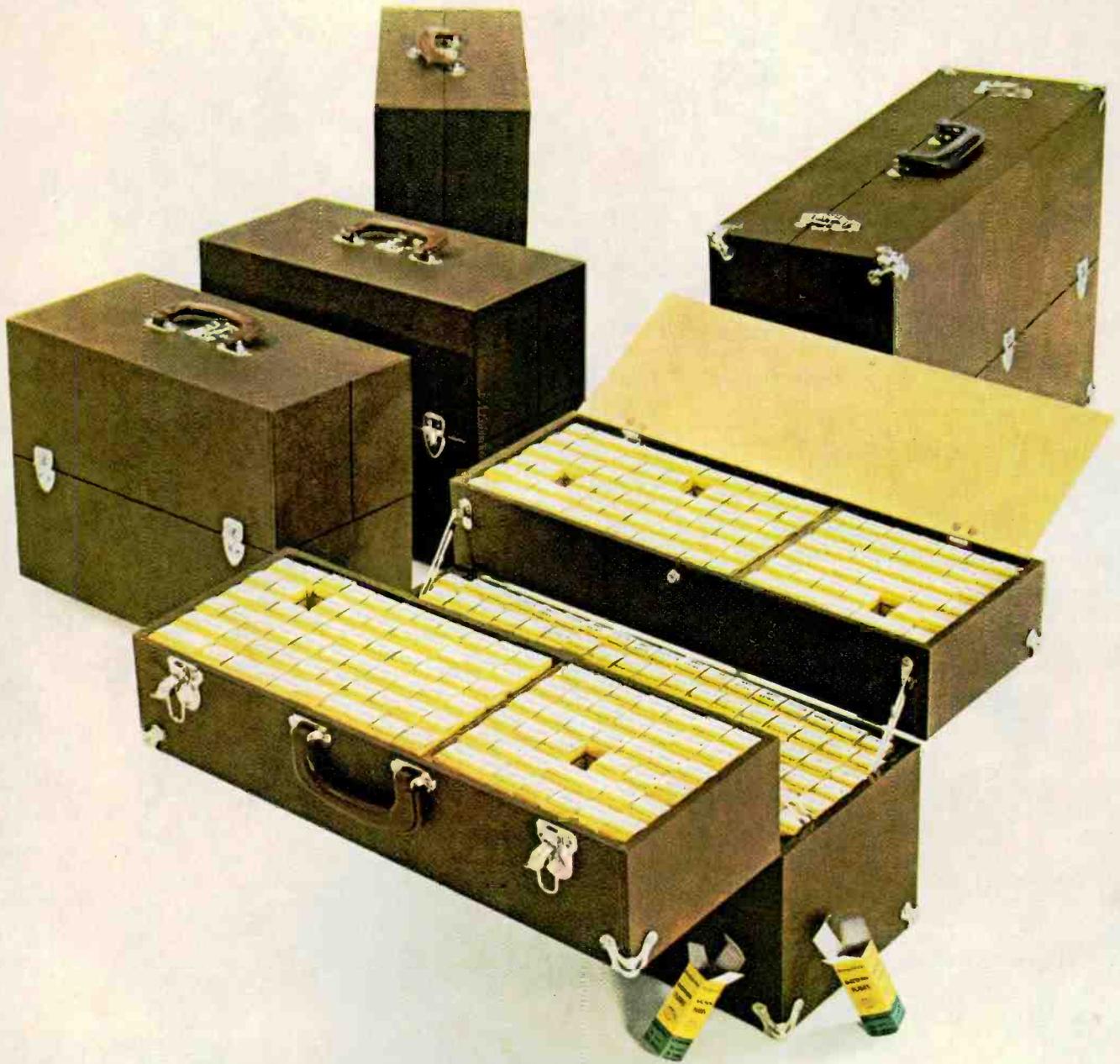


One out of every five
professional servicemen
has switched to Amperex
TV replacement tubes

It takes a lot of quality to change the buying habits of 20% of the most knowledgeable technicians in the business. These servicemen are following the pattern set by the leading TV manufacturers, who are designing more and more of their quality lines around tubes originated by Amperex. The Amperex line of popular types is expanding all the time. Look for the green and yellow cartons at your distributor's or write: Amperex Electronic Corp., Hicksville, L. I., N. Y. 11802.



Amperex

TOMORROW'S THINKING IN TODAY'S PRODUCTS

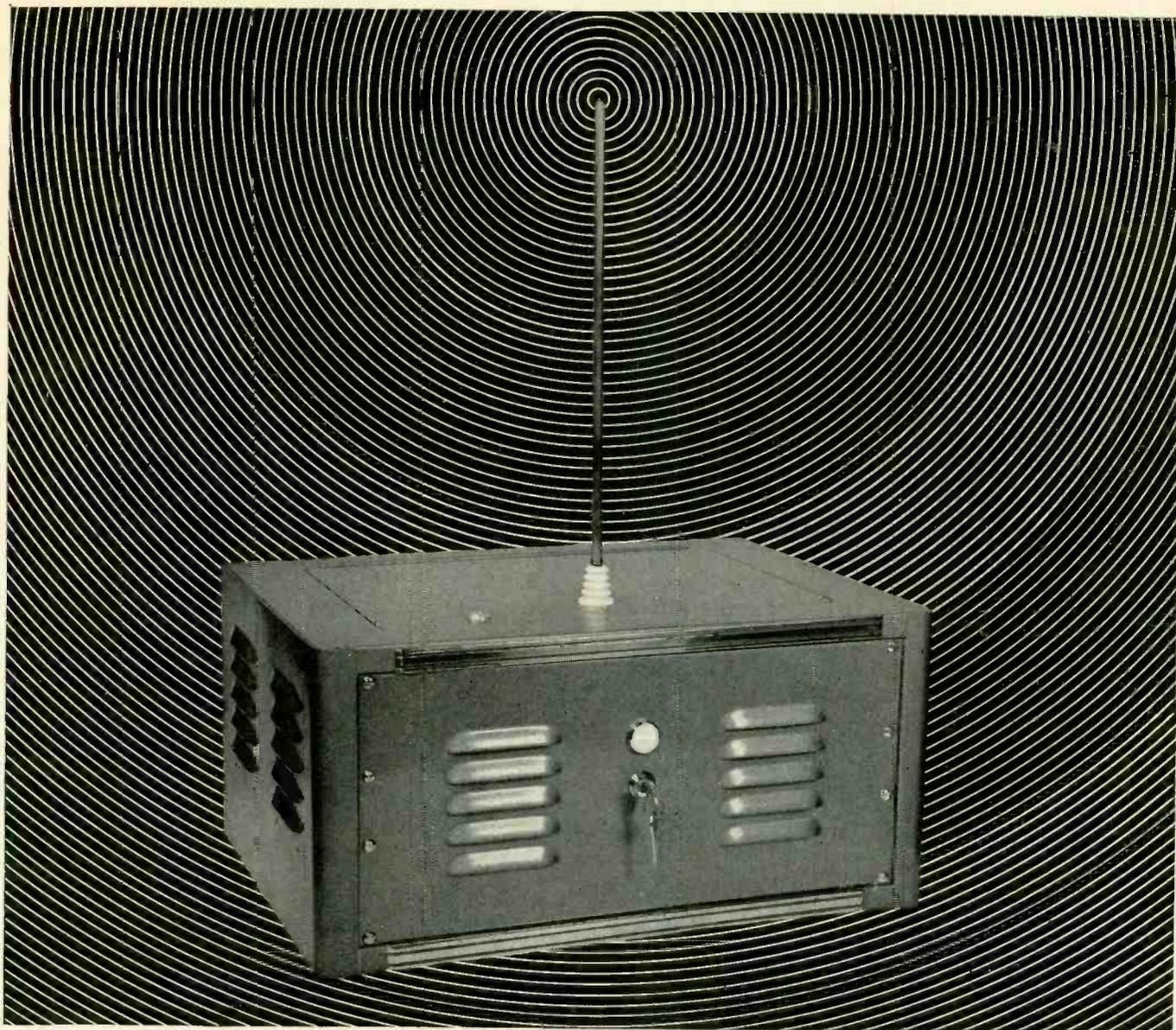

You are now in Radar Sentry Alarm's r.f. microwave field. Don't move a muscle!

This security system is so sensitive, it can be adjusted to detect the motion of your arm turning this page.

And if this Portable Model Unit were within 35 feet of you and you moved... people up to a half-mile away could hear the siren. Plus with optional equipment, it can detect fire... turn on lights... even notify police.

What does a burglar alarm have to do with you?

Just this: Radar Sentry is no ordinary alarm. It is the most modern and effective security system available. And it's also electronic.

That's why we need you. We need Dealers with technical knowledge. For the most successful Dealers for Radar Sentry Alarm are men who know electronics. This is a product that sells itself when demonstrated properly.

It's been proven time after time. In fact, many of the more than one thousand readers of electronics magazines who became Dealers in the past year — sold a system on their *first* demonstration.

And that's why we need men with technical knowledge and experience.

Men like you.

How about it?

Do you want to start a business of your own... or expand your present business with a product that in 8 years has become the world-wide leader in its field?

Do you want to earn up to \$5,000 a year in your spare time?

Do you want to earn \$20,000 and more full time?

We'll show you how.

O.K., now you can move.

Fill out the coupon and get complete Dealer/Distributor information... free.

Mail to: RADAR DEVICES MANUFACTURING CORP.
22003 Harper Ave., St. Clair Shores, Michigan 48080

RE-9



Please tell me how I can have a business of my own distributing Radar Sentry Alarm Systems. I understand there is no obligation.

Name _____

Address _____

City _____ State & Code _____

← Circle 7 on reader's service card

Circle 8 on reader's service card

Brainwaves and Electronics

Combining two branches of science is hardly new, and the results are often startling. Yet, despite the knowledge we have of body science and electronic science, there is one combination of the two whose development seems unduly slow.

A close friend of mine is quadriplegic. A double case of polio—bulbar and spinal—a few years ago—left both arms mostly and both legs totally paralyzed. The polio bug “eats up” random sections of the motor nerves running from the brain to muscles. When the bug severs nerves like this, the muscles at the ends of those nerves no longer receive the brainwaves that tell them to function. Paralysis results.

The impulses or brainwaves that make muscles work are electrical. The waves are strong enough to be seen on an oscilloscope, heard on a set of headphones, or carried by wires and made to operate servomotors. These characteristics are put to work in some recently developed artificial arms.

For example, the stump of an arm-amputee still contains the ends of certain nerves that originate at the brain. These are the nerves that formerly reached all the way to the forearm, wrist, and fingers. Impulses traveling down these nerves formerly caused the forearm, wrist and fingers to work. Neurologists can find these nerves in the stump and attach electrical sensors to them.

The nerve impulses from the sensors are fed to a tiny servo computer. The amputee can, with the motor section of his brain, go through the brain-motions of, let's say, making a fist, which takes impulses in several nerves. These brain waves travel down the several nerves to the stump as electrical impulses and are picked up by the sensors. The impulses are gathered into the tiny computer and fed to appropriate motors in the artificial limb. This electromechanical arm makes a fist, driven by the wearer's will to make a fist.

This can't help my friend, though. His nerves are severed somewhere in his spinal column. Consequently, there are no nerve ends to tap onto.

Anyway, he is not an amputee, nor would he want to become one, so prosthetic limbs are out. However, he could use his own limbs. Tests with an electromyograph—a machine that measures the ability of a muscle to function—show that though there has been considerable atrophy of muscle tissue, my friend still has muscle capability in his legs.

He is in the predicament of thousands who are crippled by polio and other nerve-damaging diseases or birth defects. His brain still functions excellently. His muscles could still work. What keeps him from walking or using his arms is the “open wiring” in his spinal cord. The electrical brainwaves for his motor actions can't reach the muscles where they can do some good. Because of the atrophy from disuse, and because a certain amount of muscular damage was done during the acute stages of his polio, my friend's muscles probably need stronger brainwave impulses than yours or mine do, so amplification might be needed.

Medical and electronic science, working together, should develop an answer for this. My friend's motor brainwaves could be tapped off at the top of his spinal column or directly at his brain, amplified as much as necessary, processed by computer if need be, and fed to appropriate muscles in his arms and legs.

What about cases where brain damage has occurred and motor impulses from the brain are missing? Motor brainwaves from a normal person could be recorded on tape and then “played back” into the muscles of the handicapped person. Any number of central means could be devised, including balance sensors, speed regulators, and so on.

No one today has the whole answer, and it will be a while in coming. But, I'll not be surprised, one day a few years from now, to see my friend come walking in like anyone else.

Forest A. Belt

Radio-Electronics

September 1967 VOL. XXXVIII No. 9
Over 55 Years of Electronics Publishing

EDITORIAL

- 2 Brainwaves and Electronics Forest H. Belt

TELEVISION AND RADIO

- 22 In the Shop . . . With Jack Jack Darr
Service Clinic
- 32 Learn Color the Programed Way Glenn M. Rawlings
Get the facts the easy way—one at a time
- 39 Creative Electronic Servicing
Evaluate symptoms and isolate troubles to reduce bench time
- 50 Antenna Report
- 51 Be Brave! Take on Transistor Radios! Homer L. Davidson
A procedure that makes servicing them about as routine as shaving
- 58 It Can't Be All Bad Phil Prindle
House calls and tough dogs can ruin a technician's day

AUDIO / HI-FI / STEREO

- 36 Know Your L- and T-Pads James A. Fred
How they operate and where to use them
- 43 What Kind of Noise Annoys a Tape? Glen F. Stillwell
Even a little is too much. Hints on how to get rid of squeaks in tape decks
- 72 A Class-D Hi-Fi Amplifier
Practical circuit using pulse-width modulation

TEST INSTRUMENTS

- 44 Build This Transistor Characteristic Plotter John H. Fasal
Useful in identifying those nondescript "bargains"
- 67 The Ohm Splitter J. T. McCormick
A direct-reading ohmmeter for low, low resistance

GENERAL ELECTRONICS

- 48 MAT • MOST • MOSFET • UFET • FET:
Understanding Solid-State Talk Rufus P. Turner
Puzzled by transistor names? This is the real dope on semiconductors
- 61 Updating the Self-Holding Relay Ronald L. Ives
Relay in solid-state circuit performs in new ways
- 62 Servicing Ultrasonic Cleaners R. C. Roetger
Easy as a walk to the bank
- 99 R-E Puzzler Answer Edmund A. Braun

THE DEPARTMENTS


- | | |
|--|--------------------------|
| 6 Correspondence | 4 News Briefs |
| 16 New Books | 98 Noteworthy Circuits |
| 82 New Literature | 92 Technotes |
| 77 New Products | 99 Try This One |
| 90 New Semiconductors, Microcircuits & Tubes | 93 50 Years Ago |
| | 74 Reader's Service Page |




p 51—DEBUG TRANSISTORS



p 58—COULD BE WORSE

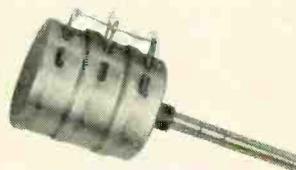


p 36—IMPEDANCE VS VOLUME

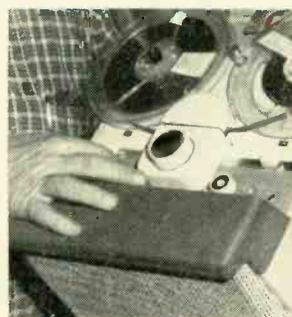

p 43—KILL THAT SQUEAK

p 61—HYBRID RELAYS

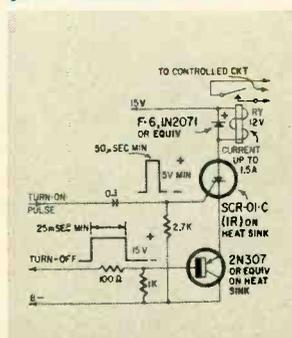

RADIO - ELECTRONICS, SEPTEMBER 1967, Volume XXXVIII, No. 9. Published monthly by Gernsback Publications, Inc., at Ferry St., Concord, N. H. 03302


Editorial, Advertising, and Executive offices: 154 West 14th Street, New York 10011.

Circulation Office, Boulder, Colo. 80302.

Second-class postage paid at Concord, N. H. Printed in U. S. A. One-year subscription rate: U. S. and possessions, Canada, \$5. Pan-American countries, \$6. Other countries, \$6.50. Single copies: 60c. © 1967, by Gernsback Publications, Inc. All rights reserved.

POSTMASTERS: Notices of undelivered copies (Form 3579) to Boulder, Colo. 80302.

COVER FEATURE

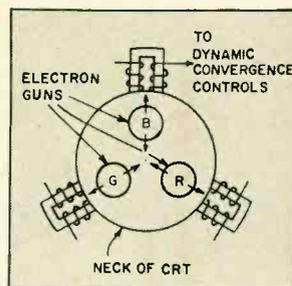

p 32—New self-teaching technique lets you learn color TV at your own rate of speed and is error-proof.

HIGH-FREQUENCY WASH




p 62—Ultrasonic cleaners are easier to fix than a TV set. Here's how they work and what can go wrong with them.



Member,
Institute of High Fidelity.
Radio-Electronics is indexed in
Applied Science & Technology Index
(formerly *Industrial Arts Index*)

Pocketable TV

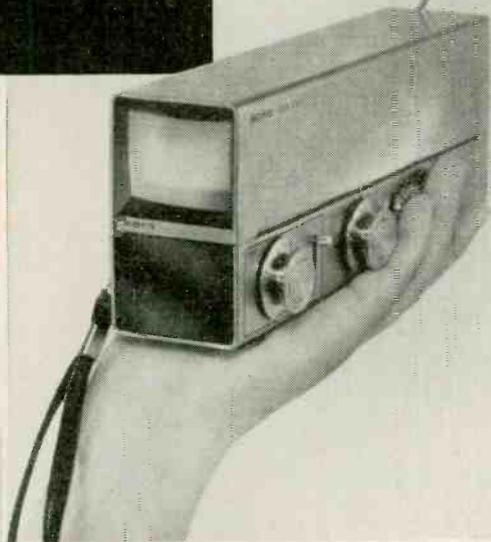
Future TV sets, judging by this Sony model, will be about half the size of a carton of cigarettes, weigh only 2 pounds, use integrated circuits and a 1 inch CRT, receive all vhf and uhf channels, and operate on ac line or batteries.



World's Smallest Detector

Germanium-immersed infrared detector (tiny black area in center of white circle) is dwarfed by the bee's eye. Detector is .04-inch in diameter. Produced by Barnes Engineering Co., Stamford, Conn., for spacecraft instruments to study Earth.

NEWS BRIEFS

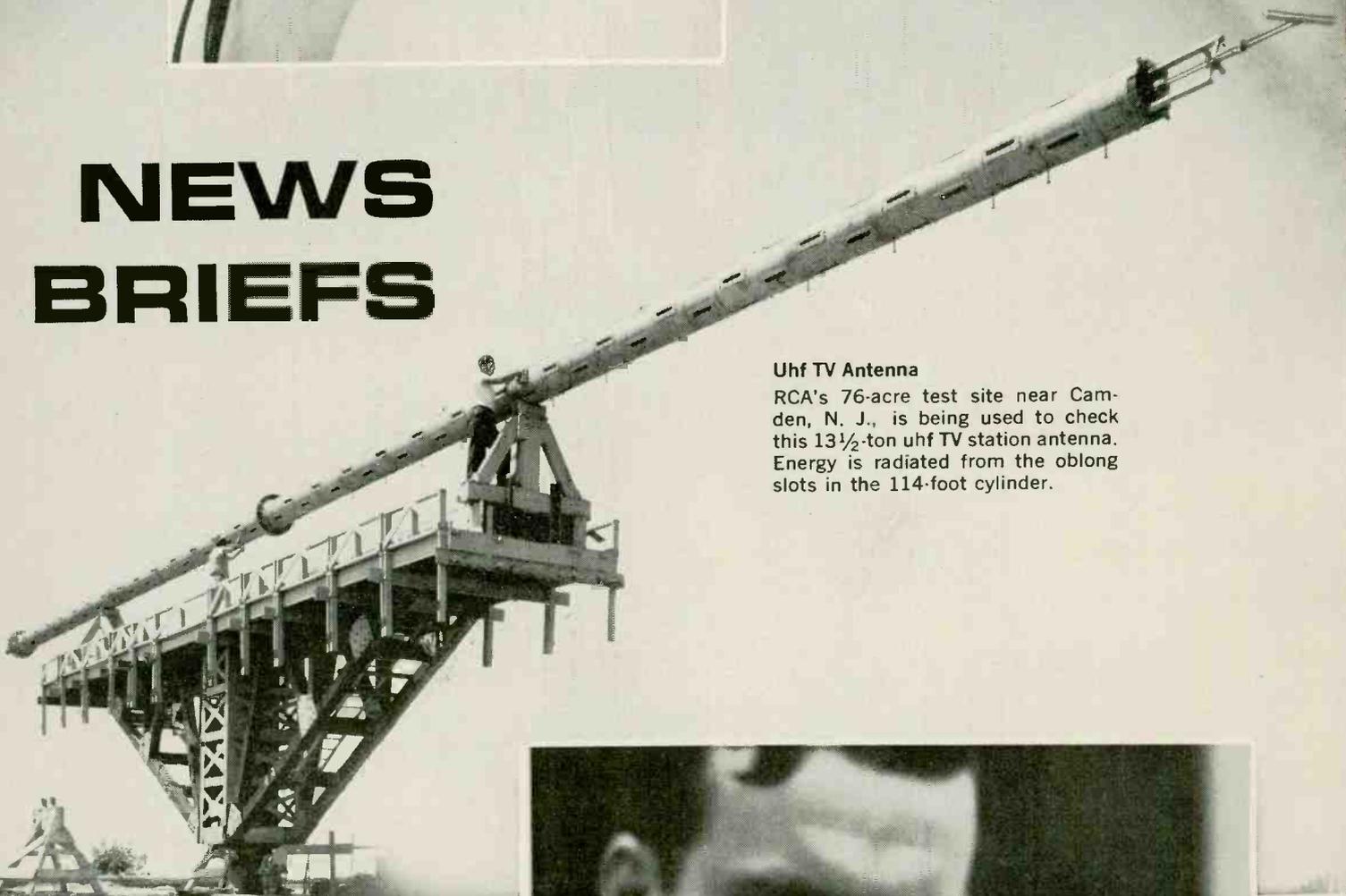

Uhf TV Antenna


RCA's 76-acre test site near Camden, N. J., is being used to check this 13½-ton uhf TV station antenna. Energy is radiated from the oblong slots in the 114-foot cylinder.

Lineless Telephone

Bell Telephone Laboratories' experimental telephone—shown with case removed—contains a transmitter, receiver, ringer elements, antenna system, signaling circuit board and rechargeable batteries. Provides simultaneous 2-way conversation (not push-to-talk) as well as dialing and ringing. Range is 100 to 1,500 feet from a fixed station.



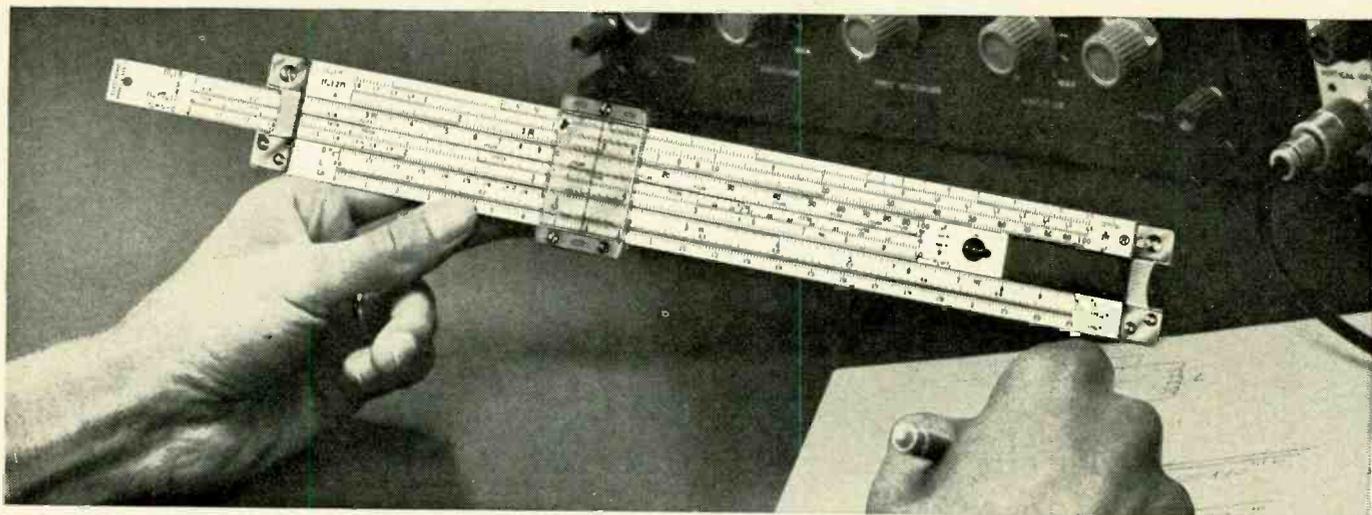Even if you've never had a slide rule in your hands before



...you can now start solving electronics problems fast with this new electronics slide rule and course

HAVE YOU EVER ENVIED the way some fellows whip out a "slip stick" and whiz through a problem in multiplication, division, square root, logs, etc., instead of struggling through it with pad and pencil?

Now you can "outshine" them—even if you've never used a slide rule before. (If you're already using a conventional slide rule, you'll learn new tricks with this one.)

You can do, in just a few seconds, not only common mathematical calculations but also special electronics problems in resonance and reactance that even a conventional slide rule can't directly answer.

The secret is in this new Electronics Slide Rule and a complete how-to-do-it Course developed especially for men in electronics by the Cleveland Institute of Electronics.

This is a professional slide rule in every detail, made exclusively for us by Pickett, Inc. It can do everything a regular slide rule can—and more. It has two special scales for solving resonant frequency problems and inductive or capacitive reactance problems or any problem involving the factor 2π . On the other side... a unique decimal point locator plus useful electronics formulas and conversion factors. Also included is a handsome leather carrying case with a heavy-duty plastic liner, removable belt-loop, and flip-open cover.

The Course gives you not just printed instruction but *personal tutoring* in the use of this lightning-quick calculator. You get four full-length AUTO-PROGRAMMED™ lessons which "start from scratch" and teach you with actual examples everything you need to know. These lessons have been carefully designed to meet the same high educational standards as the electronics career courses for which our school is famous. Each lesson you do may be sent in to CIE, where it will be personally graded by one of our expert instructors the same day he receives it and returned to you with his comments.

To make friends with career-minded electronics men around the country, we have deliberately underpriced the CIE Slide Rule and Course. The low cost will really surprise you.

Find out more about this remarkable new Slide Rule and Course and what they can do for you. We have prepared a Free Booklet explaining them in detail. Send for it today. No obligation, of course—just an opportunity to get in on the best offer ever made to people in electronics. Mail coupon, or write Cleveland Institute of Electronics, Dept. RE-144, 1776 East 17th St., Cleveland, Ohio 44114.

CIE Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114


Acclaimed by Electronics Experts

"It opens a whole new era of quick calculations. Even if you never had a slide rule in your hands before, the four-lesson instruction course that is included takes you by the hand and leads you from simple calculations right through resonance and reactance problems with hardly a hitch. If you already use a slide rule, you'll find the lessons a first rate refresher course. And they explain in detail the shortcuts built into this new rule."
—WAYNE LEMONS, *Radio-Electronics*

"Why didn't someone think of this before?...the slide rule saved me time the very first day. The 'refresher' course is a marvel of clarity. I couldn't help being amazed at how many standard formula functions I was performing the hard way."
—OLIVER P. FERRELL, Editor, *Popular Electronics*

"I was very intrigued by the 'quickie' electronics problem solutions. It is an ingenious technique. The special scales should be of decided value to any technician or engineer. Your slide rule is a natural."
—JOSEPH J. DeFRANCE, Head of Electrical Technology Dept., New York City Community College.

Mail this coupon for
FREE
BOOKLET

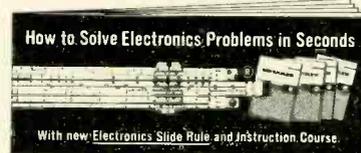

Cleveland Institute of Electronics
1776 East 17th Street, Cleveland, Ohio 44114

Please send me without charge or obligation your booklet describing the CIE Electronics Slide Rule and Instruction Course. **ALSO FREE** if I act at once: a handy pocket-size Electronics Data Guide.

Name _____ (please print)

Address _____

City _____ State _____ Zip _____

Accredited Member National Home Study Council
A Leader in Electronics Training... Since 1934.

RE-144

Listen!



Hang it fast
and easy
then forget it!

The new Jensen VH-100 Series horn speakers were designed for fast installation and a lower installed cost. Their new and exclusive features let you install three VH-100's for the labor penalty previously charged for two.

KWIKON® connectors, an easily detached base, universal angle adjustment, accessible power control and an optional pre-integrated transformer are but a few of the many advantages of these rugged new weatherproof 32 watt speakers.


Our new brochure tells all.

Write Jensen Manufacturing Division, The Muter Company, 6601 South Laramie Avenue, Chicago, Illinois. 60638.

jensen

Circle 10 on reader's service card


Correspondence

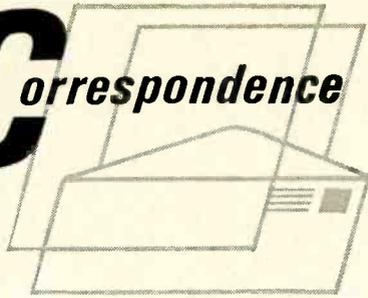

TWIN SLAVE

Dear Editor:

I have just read the article "Twin 200 Watt-Second Solid-State Strobe Slaves" by E. F. Rice in March RADIO-ELECTRONICS. I would like to make one suggestion for improved safety. The 3pdt switch to discharge capacitors when power is turned off will leave the capacitors charged if the fuse blows or if the power cord is unplugged with the switch left on. If S1 were replaced with an spst switch and a relay, the capacitors will always be discharged except while power is actually applied to the unit. The relay can have dpdt (or dpst normally closed) contacts, with a 6.3-volt ac or 117-volt ac coil.

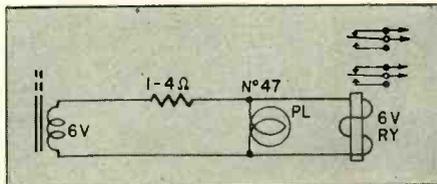

The spst switch is connected in place of S1-a. The normally closed contacts of the relay are connected in place of S1-b and S1-c (see sketch). The relay coil is connected, depending on its voltage rating, to the 6-volt transformer winding or across the primary of the power transformer.

W. J. STILES

Wentzville, Mo.

APRIL FOOL

Dear Editor:

I have a DUD service department, ready to service any and all DUDS (Digital Unit Diagnosis System). All have had five or more years of digital computer service as prerequisite for employment in my service shop.

Please forward all information available, so we can start our service by the promised April 1.

JAMES T. DINSMORE

Fort Worth, Texas

[Four large manufacturers wrote for more information on our April Fool story, and two, like you Mr. Dinsmore,

Radio-Electronics

154 WEST 14TH STREET
NEW YORK 10011

HUGO GERNSBACK, *editor-in-chief*

M. HARVEY GERNSBACK, *publisher*

FOREST H. BELT, *editor*

Robert F. Scott, *W2PWG, senior editor*

Thomas R. Haskett, *managing editor*

Jack Darr, *service editor*

I. Queen, *editorial associate*

Peter E. Sutheim, *audio editor*

Maxine Schwere, *assistant to editor*

Wm. Lyon McLaughlin,
technical illustration director

Bruce Ward, *production manager*

Adelaide Cassity, *production assistant*

G. Aliquo, *circulation manager*

Cover by Harry Schlack

RADIO-ELECTRONICS is published by Gernsback Publications, Inc.

Chairman of the Board: Hugo Gernsback

President: M. Harvey Gernsback

Vice President-Secretary: G. Aliquo

ADVERTISING REPRESENTATIVES

EAST

John J. Lamson,

RADIO-ELECTRONICS, 154 West 14th Street,
New York 10011, 212-255-7755

MIDWEST/N.&S. Car., Ga., Tenn.

Robert Pattis, the Bill Pattis Co., 4761 West
Touhy Ave., Lincolnwood, Ill. 60646,
312-679-1100

W. COAST/Texas/Arkansas/Oklahoma

J. E. Publishers Representative Co., 8380
Melrose Ave., Los Angeles, Calif. 90069,
213-653-5841; 420 Market St., San Francisco,
Calif. 94111, 415-981-4527

UNITED KINGDOM

Publishing & Distributing Co., Ltd., Mitre
House, 177 Regent St., London W.1, England

SUBSCRIPTION SERVICE: Send all subscription correspondence and orders to RADIO-ELECTRONICS, Subscription Department, Boulder, Colo. 80302. For change of address, allow six weeks, furnishing both the old and new addresses and if possible enclosing label from a recent issue.

MOVING? Or writing about subscription? Be sure to fill out form below.

For FASTEST service on address change, missing copies, etc., attach old mailing label in first space below. Otherwise please print clearly your address as we now have it.

OLD ADDRESS (Attach old label if available)

Name

Address

City State

Zip Code

NEW ADDRESS


Name

Address

City State

Zip Code

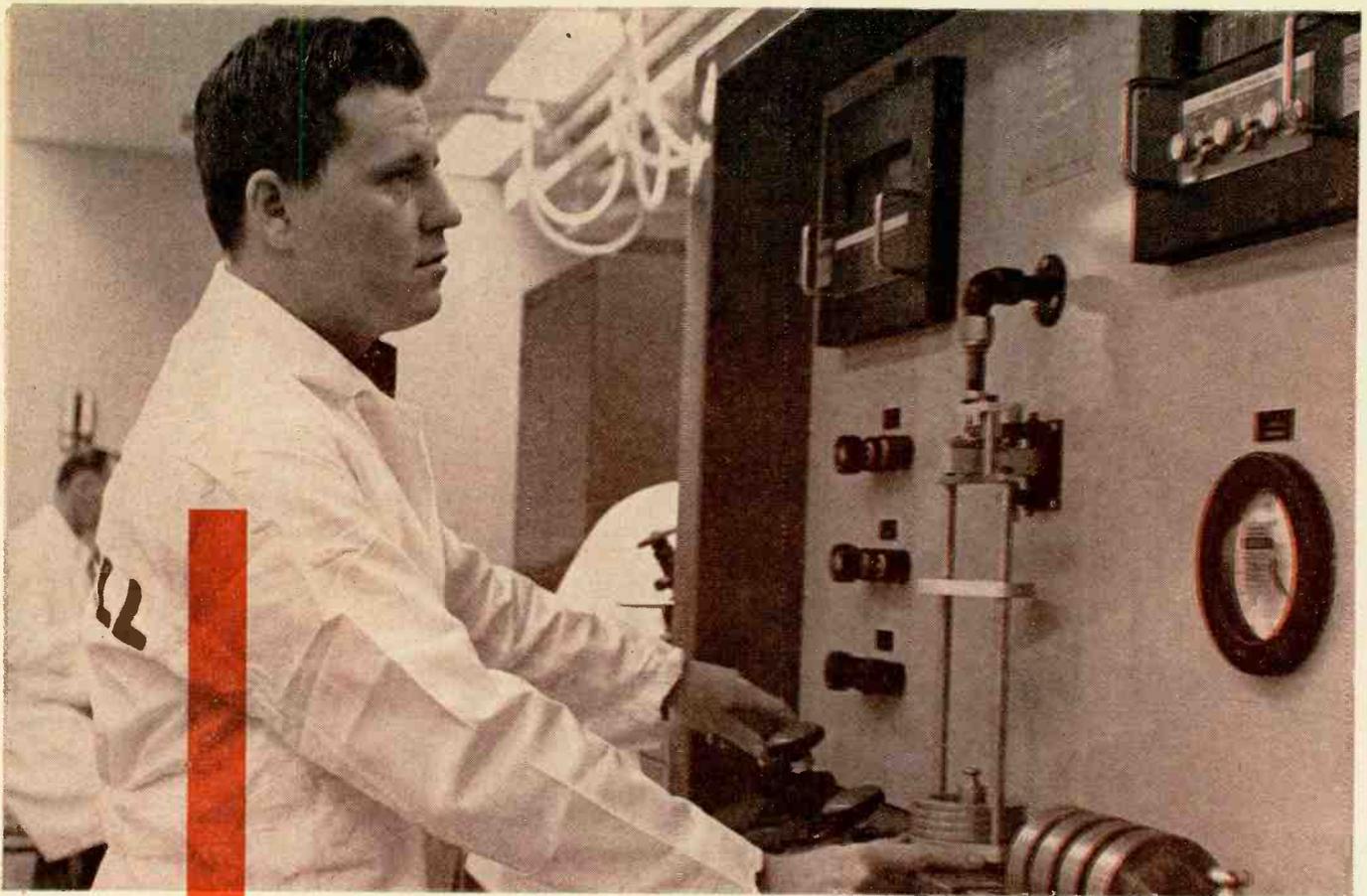Mail to: RADIO-ELECTRONICS
Subscription Dept. Boulder, Colo. 80302



DeVry Not Only Trained Me... But Helped Me Get a Good Job in Electronics

"One of the luckiest days of my life was when I sent for DeVry Tech's informative booklets on Electronics. It was my start toward a wonderful future," says William L. Hudson, originally from Pennsylvania.

"I attended DeVry's Resident School. Upon graduation, without added cost, their Employment Service helped me get a job. Like other graduates of their Resident School and Home Study programs, I am entitled to career-long placement service whenever I need it. That's a wonderful feeling!" concluded Hudson, who is shown above at his job as a laboratory electronics technician for a prominent manufacturer in the space program.

If you are between 17 and 45 years of age, send the coupon now for free details. See how DeVry

may prepare you at home in your spare time — or in day or evening classes at one of its three resident schools in Chicago, Phoenix or Canada. If you enroll in resident school, we help you find a part-time job to defray some of your expenses, if you wish.

Start to make the big switch now toward a bright, profitable future. The first step is to fill in and mail the coupon below.

Approved for Veterans

A SUBSIDIARY OF  **BELL & HOWELL**

DeVRY INSTITUTE of TECHNOLOGY 4141 Belmont Avenue, Chicago, Ill. 60641, Dept. RE-9-X

Please give me your two free booklets, "Pocket Guide to Real Earnings," and "Electronics in Space Travel"; also include details on how to prepare for a career in Electronics. I am interested in the following opportunity fields (check one or more):

- | | |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications |
| <input type="checkbox"/> Television and Radio | <input type="checkbox"/> Computers |
| <input type="checkbox"/> Microwaves | <input type="checkbox"/> Broadcasting |
| <input type="checkbox"/> Radar | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics | <input type="checkbox"/> Electronic Control |

Name _____ Age _____

Address _____ Apt. _____

City _____ State or Province _____ Zone or Zip Code _____

Check here if you are under 16 years of age.

**HOME STUDY AND RESIDENT SCHOOL PROGRAMS
AVAILABLE IN CANADA. SEND FOR DETAILS.**

2107

Send for Full Facts!

Get two FREE booklets with facts on how a DeVry educational program may prepare you to enter the big field of electronics.




ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL

DeVRY INSTITUTE OF TECHNOLOGY

4141 BELMONT AVENUE, CHICAGO, ILLINOIS 60641

EXPERIENCE IS STILL YOUR BEST TEACHER

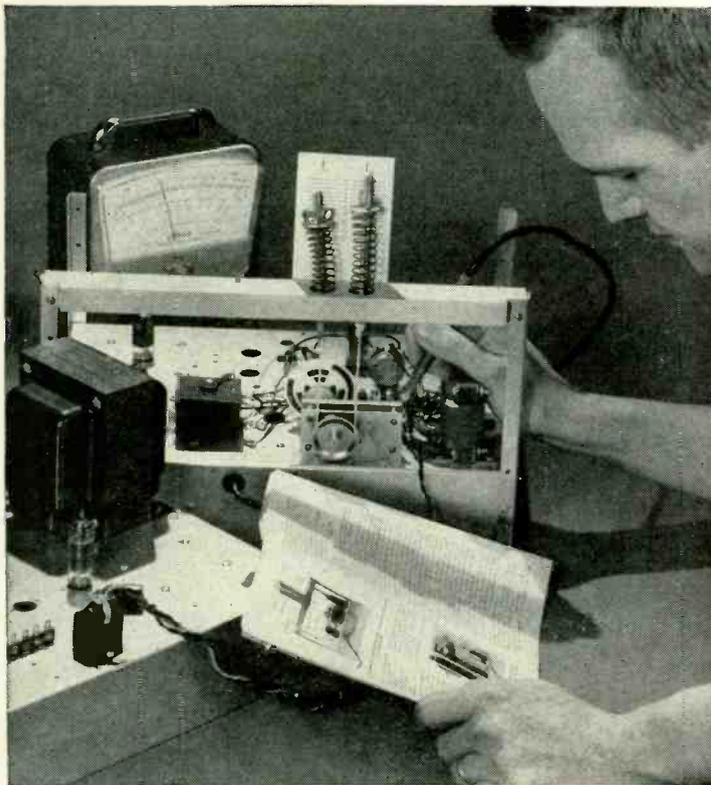

That is why NRI has invested more in Professional Lab Equipment than all other home-study schools combined. It makes training at home in Electronics fast and fascinating. Your hands are trained as well as your head.



**OLDEST AND LARGEST
SCHOOL OF ITS KIND**

Accredited by the Accrediting Commission of the National Home Study Council

You get more for your money from NRI

—more value, more solid experience so essential to careers in Electronics. NRI's pioneering "discovery" method is the result of more than half a century of simplifying, organizing, dramatizing subject matter. In each of NRI's major courses you learn by doing. You demonstrate theory you read in "bite-size" texts programmed with NRI designed-for-learning professional lab equipment. Electronics comes alive in a unique, fascinating way. You'll take pleasure in evidence you can feel and touch of increasing skills in Electronics, as you introduce defects into circuits you build, perform experiments, discover the "why" of circuitry and equipment operation.

Almost without realizing it, the NRI discovery method gives you the professional's most valuable tool—practical experience. You learn maintenance, installation, construction and trouble-shooting of Electronic circuits of any description. Whether your chosen field is Industrial Electronics, Communications or TV-Radio Servicing, NRI prepares you quickly to be employable in this booming field or to earn extra money in your spare time or have your own full-time business. And you start out with training equivalent to months—even years—of on-the-job training.

NRI Has Trained More Men for Electronics Than Any Other School

—By actual count, the number of individuals who have enrolled for Electronics with NRI could easily populate a city the size of New Orleans or Indianapolis. Over three-quarters of a million have enrolled with NRI since 1914. How well NRI training has proved its value is evident from the thousands of letters we receive from graduates. Letters like those excerpted below. Take the first step to a rewarding new career today. Mail the postage-free card. No obligation. No salesman will call. NATIONAL RADIO INSTITUTE, Electronics Division, Washington, D.C. 20016.



L. V. Lynch, Louisville, Ky., was a factory worker with American Tobacco Co., now he's an Electronics Technician with the same firm. "I don't see how the NRI way of teaching could be improved."



G. L. Roberts, Champaign, Ill., is Senior Technician at the U. of Illinois Coordinated Science Laboratory. In two years he received five pay raises. Says Roberts, "I attribute my present position to NRI training."




Don House, Lubbock, Tex., went into his own Servicing business six months after completing NRI training. This former clothes salesman just bought a new house and reports, "I look forward to making twice as much money as I would have in my former work."




Ronald L. Ritter of Eatontown, N.J., received a promotion before finishing the NRI Communication course, scoring one of the highest grades in Army proficiency tests. He works with the U.S. Army Electronics Lab, Ft. Monmouth, N.J. "Through NRI, I know I can handle a job of responsibility."

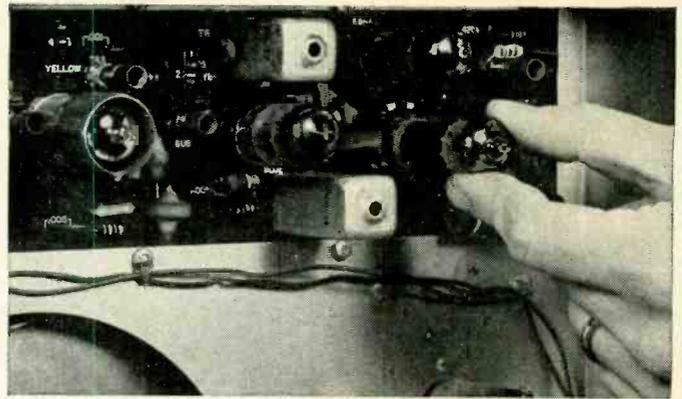APPROVED UNDER NEW GI BILL. If you served since January 31, 1955, or are in service, check GI line on postage-free card.




COLOR TV CIRCUITRY COMES ALIVE

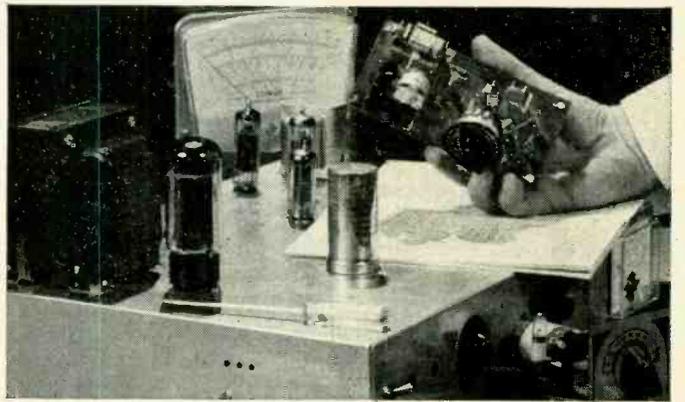as you build, stage-by-stage, the only custom Color-TV engineered for training. You grasp a professional understanding of all color circuits through logical demonstrations never before presented. The TV-Radio Servicing course includes your choice of black and white or color training equipment.



COMMUNICATIONS EXPERIENCE

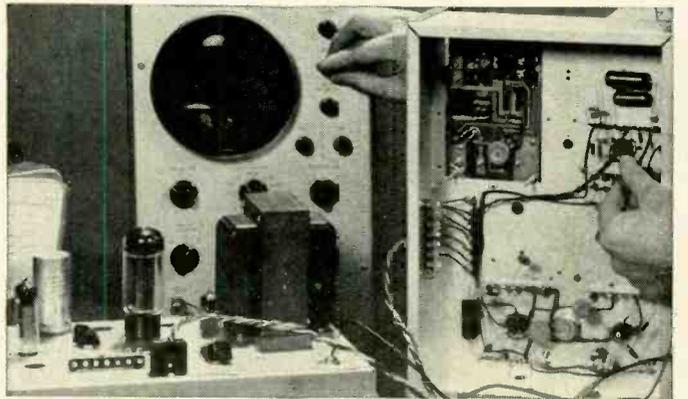comparable to many months on the job is yours as you build and use a VTVM with solid-state power supply, perform experiments on transmission line and antenna systems and build and work with an operating, phone-cw, 30-watt transmitter suitable for use on the 80-meter amateur band. Again, no other home-study school offers this equipment. You pass your FCC exams—or get your money back.



COMPETENT TECHNICAL ABILITY

can be instantly demonstrated by you on completing the NRI course in Industrial Electronics. As you learn, you actually build and use your own motor control circuits, telemetering devices and even digital computer circuits which you program to solve simple problems. All major NRI courses include use of transistors, solid-state devices, printed circuits.

WHY bother with makeshift twist-prong capacitor replacements?

When you substitute capacitor sizes and ratings, you leave yourself wide open for criticism of your work . . . you risk your reputation . . . you stand to lose customers. It just doesn't pay to use makeshifts when it's so easy to get the exact replacement from your Sprague distributor!

Get the right SIZE,
right RATING every time
with improved



SPRAGUE TWIST-LOK® CAPACITORS!

2,365 different capacitors to choose from!

The industry's most complete selection of twist-prong capacitors, bar none. Greater reliability, too. Exclusive Sprague cover design provides a leak-proof seal which permits capacitors to withstand higher ripple currents.

GET YOUR COPY of Sprague's comprehensive Electrolytic Capacitor Replacement Manual K-109 from your Sprague Distributor, or write Sprague Products Co., 81 Marshall Street, North Adams, Mass.



WORLD'S LARGEST MANUFACTURER OF CAPACITORS

68-126-63R2

Circle 12 on reader's service card

CORRESPONDENCE continued

offered maintenance. Very good. The last laugh may be on all of us. One company is close to computerized troubleshooting, and another has an infrared device that analyzes operation by the heat patterns in a chassis.—Editor]

MIDYEAR REPORT

Dear Editor:

The article "Midyear Report on Electronics" by Larry Allen in your June 1967 issue is most interesting and informative. However, I take issue with the statement "Citizens band is slowing down, but commercial two-way radio is making up for it."

LEO G. SANDS

New York City

MORE ON BAFFLES

Dear Editor:

James F. Novak, in "Baffle: Speaker-Air Interface" in the June issue, correctly points out that the range of low-frequency response in an infinite baffle or closed-box speaker system is determined exclusively by the bass resonant frequency, and that the level of bass response is determined by the Q. He then concludes with the familiar saw: "A large box allows *more* and *cleaner* bass than a small box."

The bass resonant frequency of an acoustic suspension speaker can be made as low as the designer wants it to be. The Q can also be adjusted to whatever value the designer thinks proper. There is nothing in the small size of the box which imposes special limitations (outside of efficiency).

In short, the range and level of bass response in a properly designed acoustic suspension system is exactly the same as in a properly designed infinite baffle system using the same size woofer. Further, the substitution of air springiness for mechanical suspension stiffness reduces bass harmonic distortion radically, usually by 75% to 90%.

ROY F. ALLISON

END

*Acoustic Research, Inc.
Cambridge, Mass.*

CORRECTION

There are two errors in "Build Your Own Shortwave Receiver," in our August 1967 issue. On the schematic, one side of C22, the cathode of D1, and the sleeve of J2 are shown connected together. This common connection should also be tied to the ground bus. On page 58, middle column, second paragraph, the second sentence should read: "For 80-meter coverage, the full 80-turn coil is required." END

**New low cost.
 New ease of operation.
 No waiting. No warm-up.
 No adjustments.
 Brightest patterns in the industry.**



The **B&K** 1242 Color Generator is all bu\$ine\$\$!

There's nothing else like it. The all-new B&K 1242 represents the highest state of the art today. Go ahead and compare it; it's unique.

Ultrastable solid-state circuits make antiquated heating elements unnecessary. The 1242 works instantly in all service

environments — no waiting, no warm-up, no adjustments. Other units have up to 3 times as many front panel controls. For ease of operation, the 1242 has just two: color level and selector switch. It provides dots, crosshatch, horizontal or vertical lines, and color bars. And these are the sharpest, brightest patterns in the industry.

The 1242 handles easily, too. It's the smallest, lightest-weight color generator! Rugged, too; it's all steel, with storage


space for leads. It's transformer powered and complete with leads. Calls take less time and you make more money, because you can go from a cold or hot truck into a home and get right to work.

On every count, the new B&K 1242 is amazing. In time saved, it will pay for itself in just a few weeks — especially at this low price: \$99.95

B&K Division of Dynascan Corporation
 1801 W. Belle Plaine • Chicago, Illinois 60613



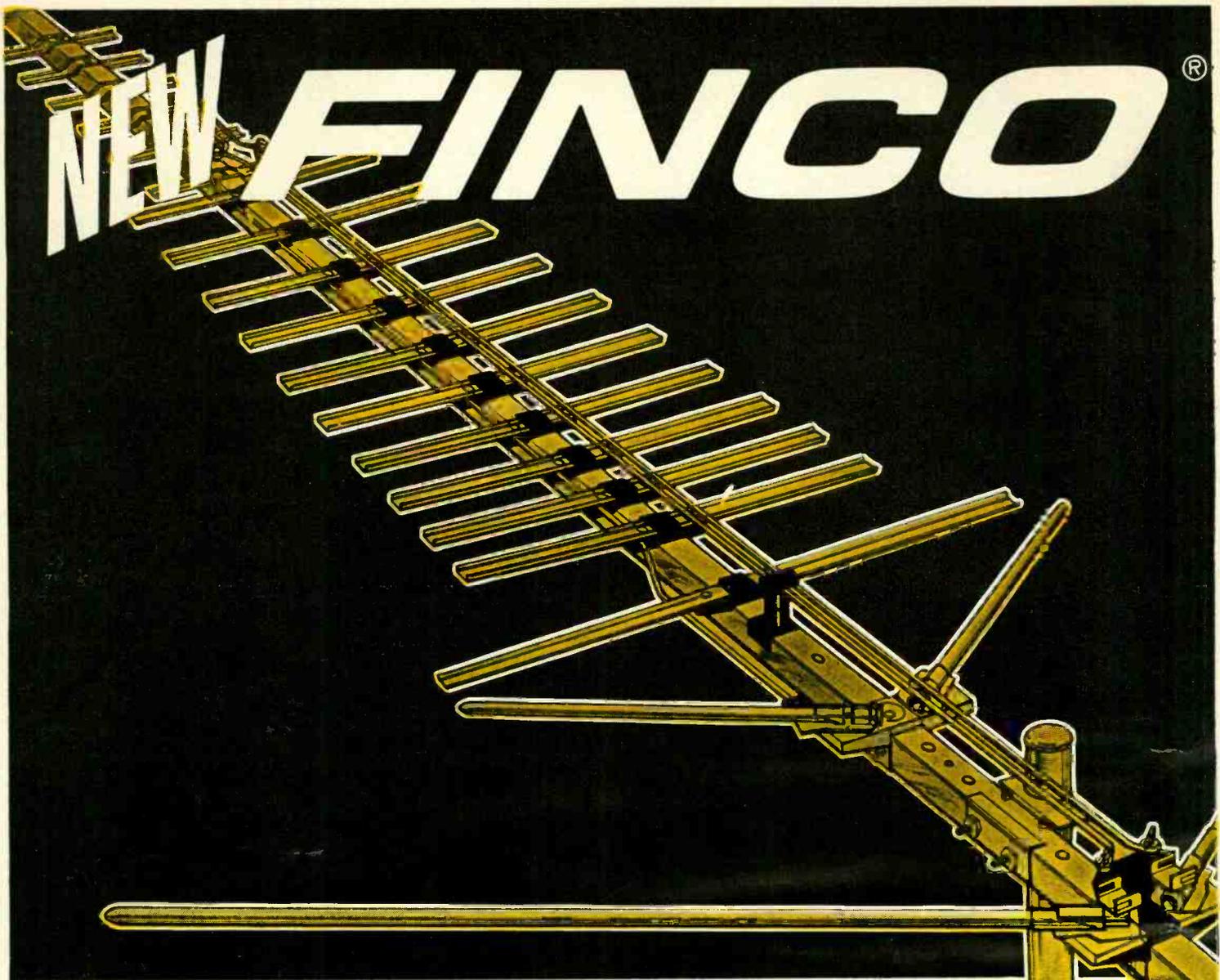Where Electronic Innovation Is A Way Of Life



“the ANTENNA that captures the RAINBOW”

No two reception areas are alike in the number of stations, UHF and VHF, station channel frequencies, and signal strengths.

FINCO has developed the Color Spectrum Series of antennas – “Signal Customized” – to exactly fit the requirements of any given area. There is a model scientifically designed and engineered for every area, even the most troublesome, and for all combinations of signal conditions.

Engineering studies show that a receiving antenna should have more gain as channel frequency is increased – that is, channel 6 more than channel 2, channel 13 more than channel 7, and UHF from channel 14 on up...

- 1 – to compensate for signal strength loss
- 2 – to compensate for down-lead loss
- 3 – to meet receiver requirements for more signal to operate properly

FINCO Color Spectrum Antennas obtain this frequency dependent characteristic through a newly developed principle of spacing between elements. Gain increases as frequency increases. This new FINCO engineering break-through, combined with superior flat response patterns and unusually high front-to-back ratios, assure the finest COLOR and B & W reception possible... everywhere.



Write for full information on “Signal Customized” Antennas:

THE FINNEY COMPANY

34 West Interstate Street • Dept. RE • Bedford, Ohio 44146

Circle 14 on reader's service card

RADIO-ELECTRONICS











COLOR SPECTRUM

T.M.

ANTENNAS

are "signal customized" for better reception.

Check this chart for the FINCO "SIGNAL CUSTOMIZED" Antenna best suited for your area

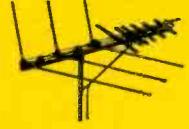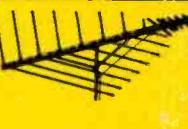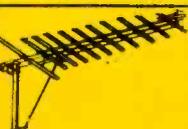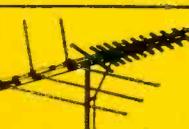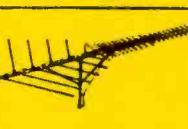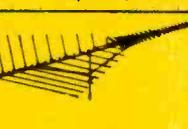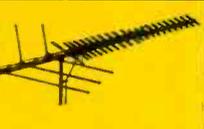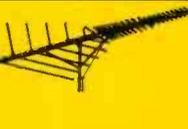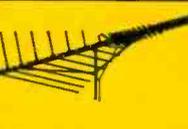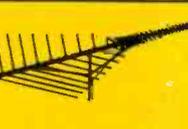STRENGTH OF UHF SIGNAL AT RECEIVING ANTENNA LOCATION	Strength of VHF Signal at Receiving Antenna Location				
	NO VHF	VHF SIGNAL STRONG	VHF SIGNAL MODERATE	VHF SIGNAL WEAK	VHF SIGNAL VERY WEAK
NO UHF →		 CS-V3 \$10.95	 CS-V5 \$17.50 CS-V7 \$24.95	 CS-V10 \$35.95	 CS-V15 \$48.50 CS-V18 \$56.50
UHF SIGNAL STRONG →	 CS-U1 \$9.95	 CS-A1 \$18.95	 CS-B1 \$29.95	 CS-C1 \$43.95	 CS-C1 \$43.95
UHF SIGNAL WEAK →	 CS-U2 \$14.95	 CS-A2 \$22.95	 CS-B3 \$49.95	 CS-C3 \$59.95	 CS-D3 \$69.95
UHF SIGNAL VERY WEAK →	 CS-U3 \$21.95	 CS-A3 \$30.95	 CS-B3 \$49.95	 CS-C3 \$59.95	 CS-D3 \$69.95

NOTE: In addition to the regular 300 ohm models (above), each model is available in a 75 ohm coaxial cable downlead where this type of installation is preferable. These models, designated "XCS", each come complete with a compact behind-the-set 75 ohm to 300 ohm balun-splitter to match the antenna system to the proper set terminals.

Why settle for less? Buy the Best!

THE FABULOUS

MARK TEN

CAPACITIVE DISCHARGE
IGNITION SYSTEM



Available in
easy-to-build
kit form
at only

\$29.95
ppd.!

Only
\$44.95
ppd.!


Dramatically improve the performance of your car—or any vehicle. Racers and Pacers from Sebring to Suburbia by the thousands attest to the peerless performance of the Mark Ten. Delta's remarkable electronic achievement, proven for four years, is often copied, never excelled.

Ready for these?

- ▲ Dramatic increase in acceleration
- ▲ Longer point and plug life
- ▲ Improved gasoline mileage
- ▲ Complete combustion
- ▲ Smoother performance

Ready? Order today!

BE YOUR OWN MECHANIC

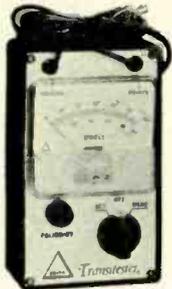

Tune-up

DWELL METER \$12.95 ppd.

A universal precision instrument for use in tuning all vehicles, regardless of the number of cylinders or battery polarity. Gives correct point dwell readings on vehicles equipped with capacitive discharge, transistor or conventional ignition. Precision accuracy at low cost.

- ▲ Portable, high-impact case for rugged work
- ▲ Large, easy-to-read 3½ inch precision jeweled meter
- ▲ Wide scale — reads dwell angles in degrees
- ▲ All solid state



Tune-up

TACHOMETER \$14.95 ppd.

A universal precision instrument for making carburetor adjustments on all vehicles, regardless of the number of cylinders or battery polarity. Gives precise RPM readings on vehicles equipped with capacitive discharge, transistor or conventional ignition. Gives you better gas mileage, fuel savings and peak engine operation.

- ▲ Large, easy-to-read 3½ inch precision jeweled meter
- ▲ Portable, high-impact case for rugged work
- ▲ Range: 0 to 1200 RPM
- ▲ All solid state



DELTA PRODUCTS, INC.

P.O. BOX 1147 RE • GRAND JUNCTION, COLORADO 81501

Enclosed is \$_____

Ship prepaid. Ship C.O.D.

Please send: Dwell Meters @ \$12.95

Mark Tens (Assembled) @ \$44.95

Tach Meters @ \$14.95

Mark Tens (Delta Kit) @ \$29.95

(12 volt positive or negative ground only)

Specify — Positive Ground Negative Ground 6 or 12 volt

Car Year _____ Make _____

Name _____

Address _____

City/State _____ Zip _____

Circle 15 on reader's service card

NEW BOOKS

AUDIO SYSTEMS, by Julian L. Bernstein. John Wiley & Sons, Inc., 605 Third Ave., New York, N. Y. 10016. 5½ x 8½ in., 110 pp. Paper, \$4.50

A thorough study of audio systems, written somewhat in textbook form. Includes examples with solutions as a part of each chapter; then provides a number of problems but doesn't give answers for them. Takes up the nature of audio signals and noise, measurement units, attenuators, mixing systems, amplifiers, recording, and equalizers. Also studies the electromechanical devices used in audio systems. Enough mathematics to explain the principles. but nothing beyond ordinary algebra. The reading isn't light, but shouldn't be difficult for a high-school graduate.

DESIGNING TRANSISTOR I.F. AMPLIFIERS and TRANSISTOR BANDPASS AMPLIFIERS, by W. T. Heterscheid. Springer-Verlag, New York, Inc., 175 Fifth Ave., New York, N. Y. 10010. 6¼ x 9¼ in., 358 pp. and 314 pp. Cloth, \$12.00 and \$11.40

This pair of books is part of the "Philips Technical Library" series by this publisher. Both are designed as engineering texts, as the title of the first implies. They go well into the calculus of design, but, as is sometimes the case with well-written books, the nonengineer can learn a lot between formulas and charts. Two good books for advanced study.

THE TREASURE HUNTER'S MANUAL, by Carl von Mueller. The Gold Bug, Box 588, Alamo, Calif. 94507. 5½ x 8½ in., 336 pp. Paper, \$6.00

Not technical, but a lot of our readers express interest in treasure-hunting devices, and this book deals with practically every facet of treasure-hunting. It discusses tools and instruments for treasure-hunting, but doesn't give any technical data on them. Even if you aren't a treasure-hunter, you might enjoy the tales of treasure-and-how-it-got-there that pepper the book.

TRANSISTOR CIRCUIT ANALYSIS AND DESIGN, by Franklin C. Fitchen. D. Van Nostrand Co., 120 Alexander St., Princeton, N. J. 08540. 6½ x 9½ in., 426 pp. Cloth, \$8.50


Second edition of a book published first in 1960. Covers most of the latest types of transistors, beginning with semiconductor physics and devices, and continuing through advanced pulse and switching circuits. Covers applications of transistors and consumer devices as well as communications and computer units. Although well loaded with mathematics, the text doesn't depend entirely on them for understanding. Each chapter is accompanied by a group of related problems for the reader to work out; answers are provided for only a few of them.

END

CONTROL
WIND NOISE,
"POP"
& FEEDBACK

...PLUS:

VIBRATION PROBLEMS

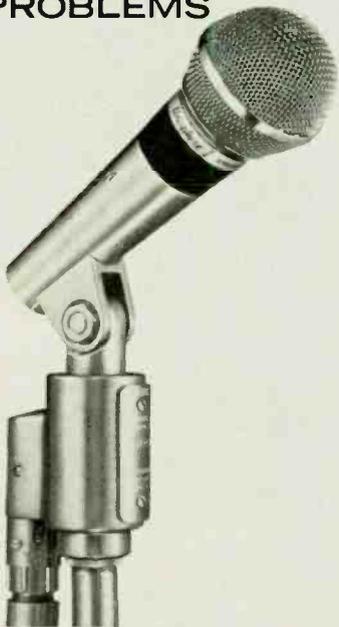

SHOCK-MOUNTED UNISPHERE™ I

Model 566. All the superb feedback and pop-control characteristics of the famed Shure Unisphere I, plus built-in vibration-isolation shock-mount which prevents pickup of mechanical vibrations and handling noise. \$140.00 List.

QUICK CUT-OFF PROBLEMS



SWITCH-MOUNTED UNISPHERE™ I

Model 565S. Now, a built-in on-off switch and permanent swivel mounting are added to the premium-quality Unisphere I—already famous for its uniform pick-up pattern at all frequencies, in all planes, and built-in wind-noise and explosive breath "pop" protection. \$100.00 List.

OVERLOAD PROBLEMS



ADJUSTABLE VOLUME UNISPHERE™ A

Model 585SAV. One of the most ingenious microphones ever! Volume control right on the Unisphere enables the user to reduce output if audio break-up due to overload occurs. Also, enables a speaker or singer to control his own volume for dramatic effects. \$72.50 List.

Model 565SC. \$102.00 List.*

3 NEW CARDIoids FROM

SHURE


Write for Complete Data Sheets / Shure Brothers, Inc., 222 Hartrey Ave., Evanston, Illinois 60204

*Same as 565S, but with "C" series (3-in-1) connector attached.

© 1967 Shure Brothers, Inc.

Circle 16 on reader's service card

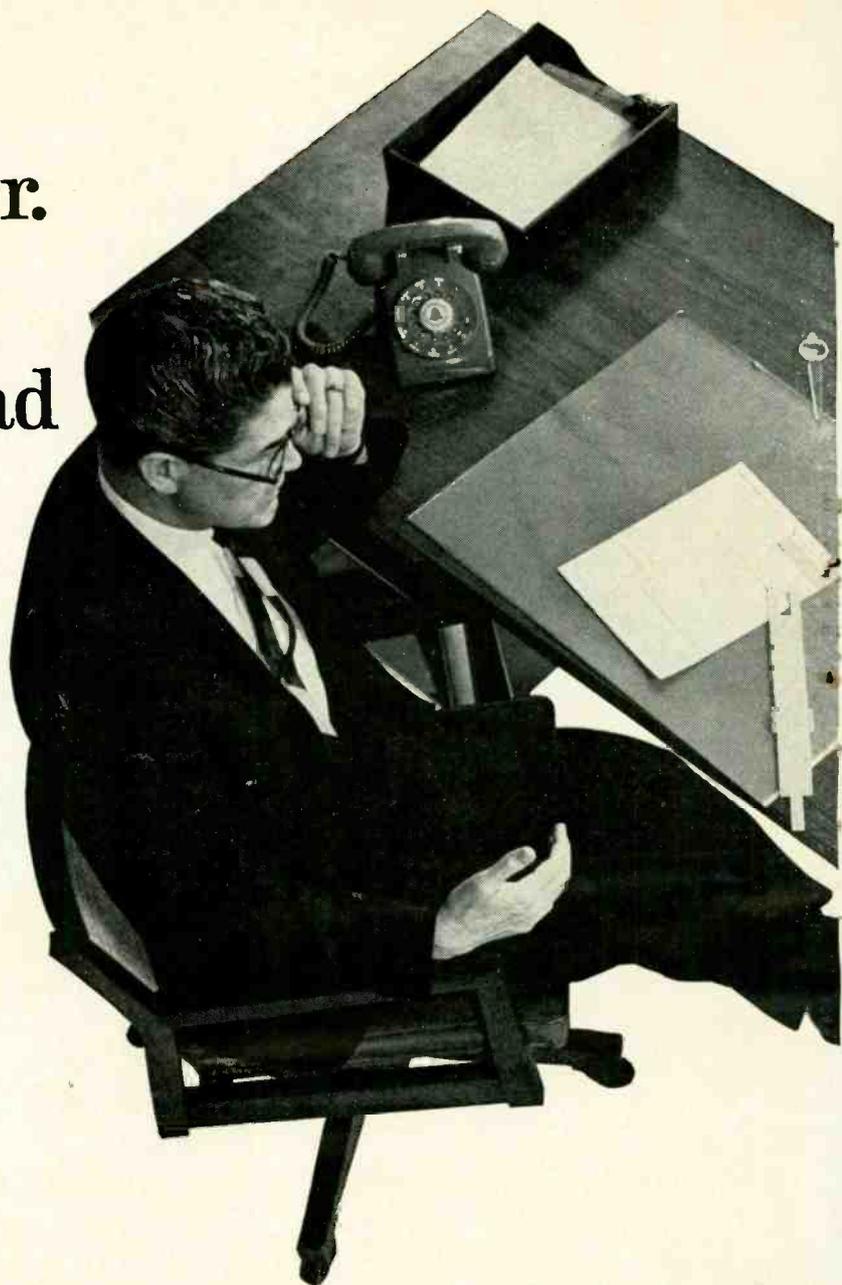**“He’s a good worker.
I’d promote him
right now if he had
more education
in electronics.”**



Could they be talking about you?


You'll miss a lot of opportunities if you try to get along in the electronics industry without an advanced education. Many doors will be closed to you, and no amount of hard work will open them.

But you can build a rewarding career if you supplement your experience with specialized knowledge of one of the key areas of electronics. As a specialist, you will enjoy security, excellent pay, and the kind of future you want for yourself and your family.

Going back to school isn't easy for a man with a

full-time job and family obligations. But CREI Home Study Programs make it possible for you to get the additional education you need without attending classes. You study at home, at your own pace, on your own schedule. You study with the assurance that what you learn can be applied to the job immediately.

CREI Programs cover all important areas of electronics including communications, radar and sonar, even missile and spacecraft guidance. You're sure to find a program that fits your career objectives.

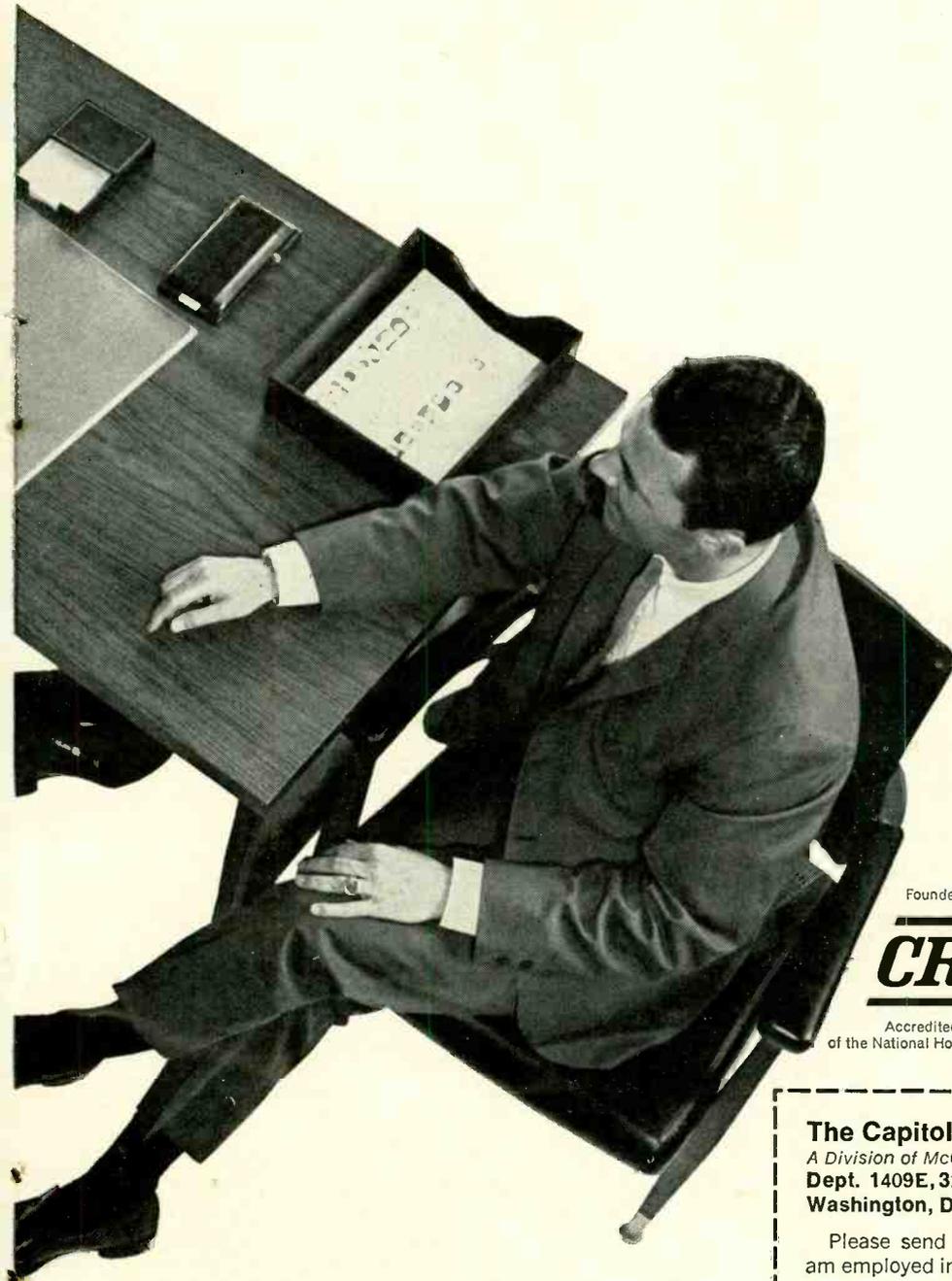

Founded 1927

CREI

Accredited Member
of the National Home Study Council

You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. Airmail post-paid card for your copy. If card is detached, use coupon at right or write:

CREI, Dept. 1409E
3224 16th St., N.W.,
Washington, D.C. 20010.



The Capitol Radio Engineering Institute

A Division of McGraw-Hill, Inc.

**Dept. 1409E, 3224 Sixteenth Street, N.W.
Washington, D.C. 20010**

Please send me FREE book describing CREI Programs. I am employed in electronics and have a high school education.

NAME _____ AGE _____

ADDRESS _____

CITY _____ STATE _____ ZIP CODE _____

EMPLOYED BY _____

TYPE OF PRESENT WORK _____ G.I. BILL

- I am interested in Electronic Engineering Technology
 Space Electronics Nuclear Engineering Technology
 Industrial Electronics for Automation
 Computer Systems Technology

APPROVED FOR TRAINING UNDER NEW G.I. BILL

In the Shop . . . With Jack

By JACK DARR

"I'VE CHECKED EVERY PART in that circuit and it still doesn't work!" Does that sound familiar? It certainly does to me, for it's about the most common complaint in my Clinic mail.

One, if you have checked every part in this circuit and it won't work, what about the possibility that the trouble isn't in *this* circuit at all? Two, the statement may be false! It should be: "I've checked every part in the circuit *that I can think of*, and it still won't work." Consider this; if you *have* checked "every part" and replaced the bad ones, it *would* work! This is simple logic, something that we forget to use at too-frequent intervals.

Let us look at a typical case, using the regular guinea pig (my wife's husband).

He examines a fairly new Zenith color TV, and finds only a thin white line across the tube. First diagnosis is easy; no vertical sweep. Well, everyone knows that this defect is caused by a bad capacitor somewhere in the vertical oscillator, if new tubes won't cure it. (Or is it? Let's see.)

Checking tubes, voltages, etc., plus moving the height and linearity controls (in case one of them had developed a dirty spot under the slider) do no good at all. Quick check of yoke and output transformer shows okay. Low-voltage supply okay. Bench job.

Humming a gay tune, he sets the chassis on the bench, without even connecting the extension cables, and starts checking capacitors very nonchalantly. Snap job. Ho-hum. But 15 minutes later, he has checked all seven capacitors and found them perfect,

checked all "associated resistors," plus the controls. Not an easy job, now.

He's got one symptom, now, though. The plate voltage on the triode section of the 6BA11 "oscillator" half comes up to normal when first turned on, but drops very rapidly to about 6-8 volts as the tube warms up. Well, he knows what causes this—a leaky coupling capacitor. Hmm. Coupling capacitor perfect, grid voltage zero. Since he had jumpered the heater voltage to the control grid of the 6HE5 output tube, and produced a 6- to 8-inch raster, the trouble *was* in the oscillator (input) section, but where?



All the parts in the feedback loop were checked. All capacitors good, no leakage at all. He'd even unhooked the little PC integrator unit and checked it for capacitor leakage to ground; fine. (The diagram shows the complete circuit, or all we need of it.)

Rechecking the grid voltage of the 6BA11 triode, he now notices that there is a very small negative voltage


continued on page 26

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

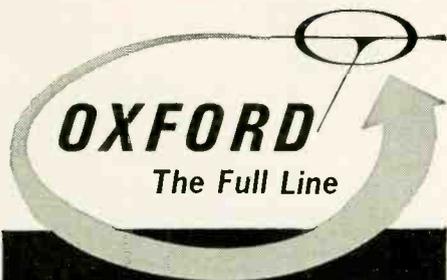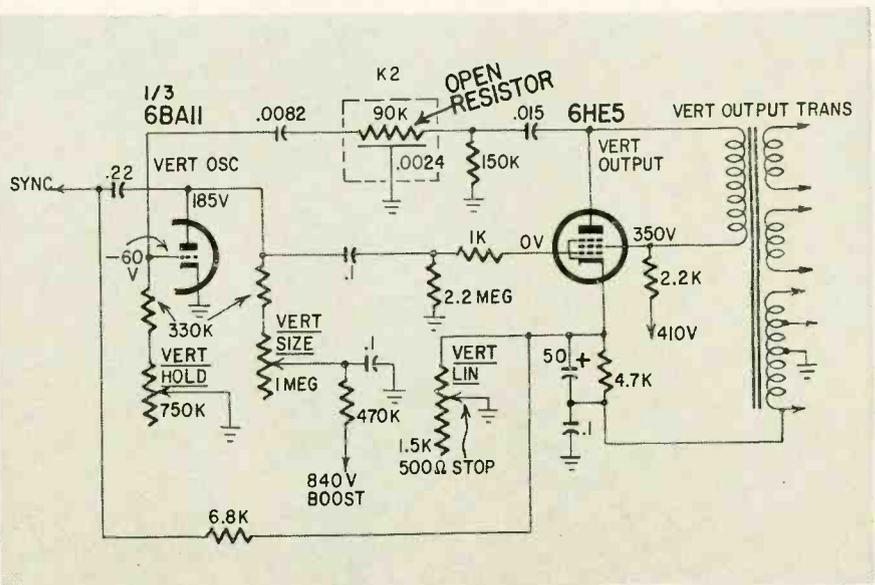
If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 154 West 14th Street, New York 10011.



**Commercial Sound
Speaker Source...**

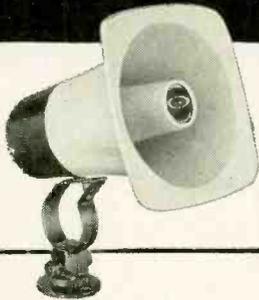

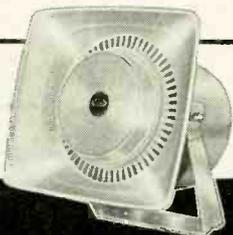You never compromise with fidelity or quality when you specify Oxford on all your speaker needs.



That's because Oxford electronic and sound engineers know that specialized applications require specialized developments. Oxford doesn't produce just horn or cone types. Oxford studies the application and the problem develops specific units for specific needs. You're never stuck with trying to pour a bushel basket into a pint measure. Paging and talk-back horns, outdoor hi-fi systems, P.A. systems and other commercial sound installations all find the perfect speaker for the system at Oxford.



Match your skills with the Oxford line of speakers that bring out the best in every sound installation. Write for the Oxford catalog of "speakers for every purpose" today!

**OXFORD TRANSDUCER
COMPANY** A Division of
Oxford Electric Corporation

3911 S. Michigan Ave.
Chicago, Ill. 60653

Circle 18 on reader's service card

Getting a hernia and not getting paid for it?

Let Arcolytic® capacitors lift the load off your mind. Or anywhere else it happens to be.

These aluminum electrolytics are built to last: wound with computer-grade 99.99% pure aluminum foil so they'll keep operating in your customers' sets even at continuous temperatures of 85°C.

You'll find they take the worry right out of premature failure, lost customer confidence and costly call-backs.

There's no premium cost, either. Arcolytics are priced along with other home entertainment capacitors.

Ask your Authorized Arco Distributor for Arcolytic electrolytic capacitors in single-section tubular, multiple-section tubular, or twist-mount designs. It may be the best break you get this year.

Arco Electronics


A DIVISION OF LORAL CORPORATION
Community Drive, Great Neck, N. Y. /
Arlington, Texas / Elk Grove Village,
Illinois / Pasadena, Menlo Park,
California. Write for our free catalog.



Circle 19 on reader's service card

Look What's NEW In The

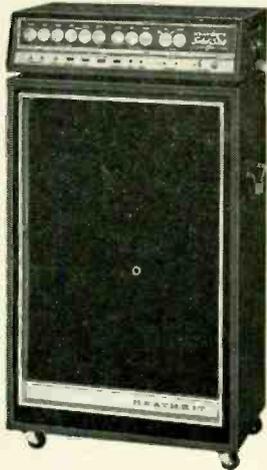NEW! Deluxe Solid-State Combo Amplifier & Speaker System!



Special Combo Offer!

Kit TAS-17-2 Amplifier &
2 Speaker Systems
Save \$20.00

\$395⁰⁰

240 lbs.

All the "big sound" features every combo wants . . . tremolo, built-in "fuzz", brightness, reverb plus a shattering 120 watts of EIA music power. Has 3 independent input channels each with 2 input jacks. Handles lead or bass guitars, combo organ, singer's mike, even a record changer. Speaker system features two special 12" woofers, special horn driver and matching black vinyl-covered wood cabinet.

NEW LOW PRICE On Heathkit "180" Deluxe Color TV



Kit GR-180
Was \$379.95

Now Only

\$349⁹⁵

(less cab.)

Now Save \$30 on this superb set. Features 180 sq. in. rectangular viewing area, plus exclusive built-in servicing facilities so you can converge and maintain the best color pictures at all times. Also has 24,000 volt picture power, automatic degaussing, rare earth phosphors for livelier colors, 3-stage IF, plus many more advanced features. Choice of installation . . . in a wall, your custom cabinet or an old black & white set cabinet, Heath assembled contemporary (Illust. \$49.95) or Early American (\$75.00) floor cabinets, or new Heath table model (\$24.95) cabinet. Build in 25 hours. 102 lbs.

Kit TA-17
Amplifier

\$175⁰⁰

Kit TA-17-1
Speaker System

\$120⁰⁰

NEW! Low Cost Single-Channel Solid-State Guitar Amplifier



Kit TA-27
\$89⁹⁵

Boasts 20 watts EIA music power, 40 watts peak power; variable tremolo & reverb; two inputs that handle lead guitars; singer's mike; special heavy-duty 12" speaker; line bypass reversing switch that reduces hum; transformer-operated power supply; and handsome leather-textured, black vinyl covered wood cabinet with extruded aluminum front panel and chrome knobs. 35 lbs.

NOW Available Fully Assembled . . . Heathkit "Starmaker" Dual-Channel Guitar Amplifier



Assembled
TAW-16
\$199⁹⁵

(Kit TA-16
\$134.95)

Features all solid-state circuit; 25 watts EIA, 60 watts peak power; two channels, one for accompaniment, accordion or mike, the other for variable tremolo & reverb; two inputs each channel; two 12" heavy-duty speakers; line bypass reversing switch for hum reduction; leather-textured black vinyl covered wood cabinet with extruded aluminum front panel & chrome knobs. For extra savings, build the kit version in just 15 hours. 52 lbs.

NEW! Heathkit Soldering Iron



Kit GH-17
\$14⁹⁵

Ideal for kit-building or other electronic soldering jobs. Safe 6 volt, 25 watt GE midget iron with non-corroding tip. 3 heat ranges. Excellent heat recovery time. Quick warm-up . . . iron ready in 2 minutes. Protective metal cage. Build in an hour. 5 lbs.

NOW Available Fully Assembled . . . World's Most Advanced Stereo Receiver!



Assembled
ARW-15
\$499⁹⁵

(less cab.)

Kit AR-15,
\$329.95

Acclaimed by owners & audio experts for its advanced features like integrated circuits and crystal filters in the IF amplifier section; ultra-sensitive FET FM tuner; 150 watts dynamic music power; complete AM, FM and FM stereo listening; positive circuit protection; all-silicon transistors; "black magic" panel lighting; stereo only switch; adjustable phase control for best stereo and many more. 34 lbs. Optional wrap-around walnut cabinet \$19.95

NEW! Professional 10-Band Shortwave Listener's Receiver



Kit SB-310
\$249⁰⁰

Covers 6 shortwave bands (49, 41, 31, 25, 19 & 16 meters) . . . 80, 40 & 20 meter ham bands . . . 11 meter CB. Includes 5 kHz crystal filter for AM, SSB and CW listening. Features selectivity that slices stations down to last kHz . . . no more guessing station identities; 11-tube circuit; crystal-controlled front-end for same rate tuning on all bands; prebuilt & aligned LMO; tuning dial to knob ratio 4 to 1; and many more deluxe SWL features. 2-tone green metal cabinet included. Optional crystal filters for optimum CW & SSB available. 20 lbs.

'68 HEATHKIT® Catalog!

Introducing The Exciting New Look Of Heathkit Solid-State Instruments!

Now from Heath... the most exciting innovation in electronic instrumentation... new ultra-functional cabinet styling. These new Heathkit instruments feature a cabinet frame consisting of front and rear panels with side rails that completely support the component chassis independent of the top and bottom cabinet shells... allows complete freedom for assembly, checkout and calibration. You'll like the

clean bold panel & meter markings for easier reading... the easier-to-grasp knobs... the compact size... and the retractable carrying handles that are concealed in the side rails. The die-cast front panel bezel styled in chrome and black, the black side rails, and the special two-tone beige front panels and cabinet shells give these new instruments an appearance as up-to-date as their performance.

NEW! Deluxe Solid-State Volt-Ohm Meter... Battery Plus Built-In AC Power

Features 8 DC and 8 AC voltage ranges from 0.5v to 1500 v. full scale; 7 ohmmeter ranges x1 (10 ohms center scale), x10, x100, x1k, x10k, x100k and x1 megohm; 11 megohm input resistance on DC ranges; 1 megohm on AC ranges; internal battery or 120/240 v., 50/60 Hz AC power for portable or "in-shop" operation; large, easy-to-read 6" 100 uA meter; separate switches for individual functions; single test probe with finger-tip flip switch for all measurements; simple circuit board construction.

Solid-State High Impedance Volt-Ohm-Milliammeter

All silicon transistors plus FET's. Features 9 AC and 9 DC voltage full scale ranges down to 150 mv; 11 current ranges from 15 uA to 1.5A full scale; 7 resistance ranges (10 ohms center scale) measure one ohm to 1000 megohms; AC plus battery power for portability; 6" 200 uA meter with zero center scale for + & - voltage measurements without switching; accuracy of ± 3% full scale on DC volts, ± 5% on AC volts; separate range switches for each function; 1% precision resistors; 10-turn thumbwheel zero adjustment; fast circuit board construction. 10 lbs.

New FM Stereo Generator For RF, IF and FM Stereo Alignment


Produces virtually all signals for trouble-shooting & aligning multiplex adapters, FM tuners and receivers. Generates mono FM or composite stereo FM signals. Crystal-controlled 19 kHz (± 2 Hz) pilot signal, adjustable from 0 to 10% for checking tuner lock-in range. Switch-selection of 400 Hz, 1000 Hz, 5000 Hz, 19 kHz, and 65 kHz or 67 kHz SCA signals for complete alignment capability. 100 MHz sweep signal (adjustable ± 2 MHz) for overall RF and IF alignment. Built-in crystal controlled marker oscillator for IF and dial tracking checks. Phase test capability. No balance adjustment needed for equal right and left channel modulation levels.

New Variable Regulated High Voltage Power Supply


Features 6v. and 12 v. AC filament voltages; also furnishes B+ from 0 to 400 volts DC, bias from 0 to -100 volts DC; separate panel meters monitor B+ output voltage & current; voltmeter switched to read C- volts; output terminals isolated for safety; high voltage and bias may be switched "off" with filaments still "on" for maximum testing efficiency and safety.

New Solid-State Regulated Low Voltage Power Supply


New Zener reference-voltage power supply. New up-dated circuit that is virtually immune to overload from exotic transients. Relay-protected against short circuit & overload. Provides 0.5 to 50 volts DC with better than ± 15 millivolts regulation. 4 current ranges: 50 mA, 150 mA, 500 mA & 1.5 A. Adjustable current limiter: 30 to 100% on all ranges. Panel meter shows output voltage or current. Choice of kit or assembled versions.

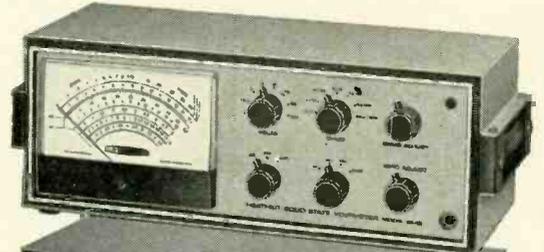

Kit IM-16
\$44⁹⁵

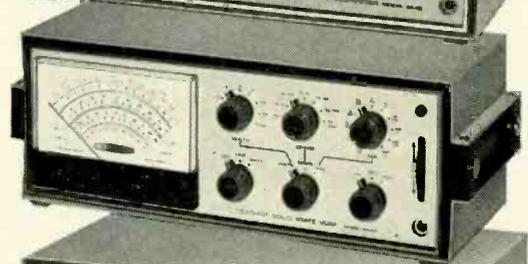


Kit IM-25
\$80⁰⁰
Wired IMW-25
\$115.00

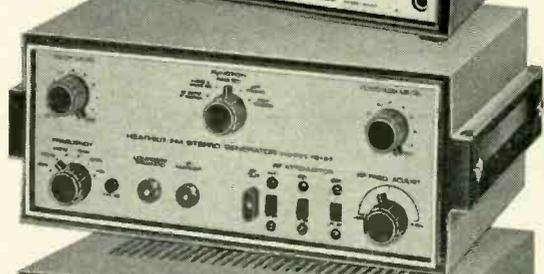

Kit IG-37
\$79⁹⁵



Kit IP-17
\$59⁹⁵

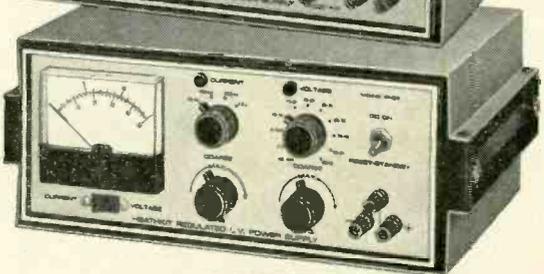

Kit IP-27
\$76⁹⁵
Wired IPW-27
\$119.95



NEW
FREE 1968
CATALOG!

Now with more kits, more color. Fully describes these along with over 300 kits for stereo/hi-fi, color TV, electronic organs, electric guitar & amplifier, amateur radio, marine, educational, CB, home & hobby. Mail coupon or write Heath Company, Benton Harbor, Michigan 49022.

HEATH COMPANY, Dept. 20-9
Benton Harbor, Michigan 49022
In Canada, Daystrom Ltd.

Enclosed is \$ _____, including shipping.

Please send model (s) _____

Please send FREE Heathkit Catalog.

Name _____

Address _____

City _____

State _____

Zip _____


Prices & specifications subject to change without notice.

CL-301

A plug for...



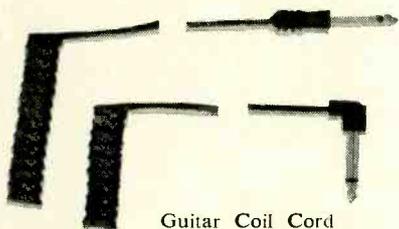Stereo Headset
Extension Coil Cord
"Molded-On" Stereo head
set extension coil cord.
Three conductor phone plug one end
of 15' (extended) coil cable. The other
end, a 3 conductor phone jack. Retracted
length 3'.



Guitar Coil Cord
Molded-On guitar coil cord. Engineered to connect guitar to amplifier. Molded-On right angle, completely shielded phone plug, one end of 20' (extended) black jacket, shielded coil cable. The other end a straight Molded-On phone plug. Retracted length is 3'. Part No. 20' RSP-RE.

BARKER

MOLDED-ON® PLUGS AND CONNECTORS

The World's Largest Manufacturer
of Molded-On Cables and Connectors

The greatest name in "Molded-On" plugs and connectors is Barker—manufacturers of connecting cables for every audio, hi-fi and stereo need.

Barker plugs are solid plastic units, molded directly onto the wire ends to provide unfailing performance and unexcelled appearance. Barker has the most manufacturing experience . . . the most engineering experience.

If you are a manufacturer of—amplifiers, tuners, record changers, microphones, speaker accessories, stereo head sets or musical instruments—let Barker be your source of supply. Let us quote you! Distributors and dealers: write for our latest catalog. All our products made on our U.S.A. premises. Circle Reader's Service # for our latest catalog. For speedier service, write us direct.

BARKER PRODUCTS CO.

344 Central St., Saugus, Mass. 01906

Subsidiary of
Component Manufacturing Service, Inc.

Circle 21 on reader's service card

In the Shop . . . With Jack continued

on it. He hasn't used the scope up to now, for the circuit obviously was not oscillating, and there were no waveforms to look at! So now, up with the LO-CAP probe and see what's going on. After all, this is a multivibrator, and about the only way you can keep an MVB circuit from oscillating is take a hammer to one of the tubes.

Oh, ho! A very tiny "ripple" on the grid. Turning up the scope gain, he finds an odd pattern; instead of the 60-Hz sawteeth, a "sinewave-looking" sort of waveform, but fast; about 600 Hz at least! (By turning the height control wide open, he gets a small raster.

Now, he takes the obvious next step in the process; he goes and gets a cup of coffee. Returning, he sits and stares at the set. It's trying very hard to tell him something. Finally, it dawns on him—if the oscillator is running fast, there must be an open part in the frequency-determining circuit!

All the capacitors in the feedback loop had been checked for capacitance as well as leakage, so that wasn't it. What was left. Oh, ho. He sees one. Unhooking the little PC integrator in the feedback loop, he checks it for continuity; previous check had been only for capacitor leakage. Wheel! It's open! This one is supposed to have 90K of series resistance with .0024 μ F of capacitance! The C is pretty close, but there's no R at all; it's almost completely open! Replacing the integrator cures the trouble!

Now, let us use perfect 20-20 hindsight to see what stuck our guinea pig for so long. One, he'd frozen on the idea that this had to be capacitor trouble, because it is in a very large percentage of similar cases. Two, he wasn't thinking clearly about possible causes of this kind of trouble if the capacitors were okay, as they were. With the feedback loop open, the oscillator couldn't work at its normal frequency, but it was trying as hard as it could. With one of the components out, it had to work at a much higher frequency, with, of course, a much reduced amplitude.

The first thought, after the capacitor test failed, was a "tube trouble." Incorrect bias (positive) caused the tube to draw so much current through the very-high-value plate resistors that the plate voltage fell to almost zero. Well, in itself, this was true; however, it was not due to a shorted coupling capacitor, but simply to the fact that the grid had gone to zero bias, and, in this tube and circuit, that was enough to kill the plate voltage!

The conclusions to be drawn from

this are: One, suspect everything in the circuit, no matter how unusual you think it might be for this particular part to fail. Two, if "checking every part in the circuit" doesn't produce a cure, look somewhere else! It is entirely possible that this circuit is not the cause of the trouble you see. Three, don't sit there and fight it: go get a cuppa coffee!

Selective color loss

I get good color on channel 4, but not on channel 5, 8, or 11, all in the same town. I've tried substituting tubes in the color circuits, burst amplifier, phase detector, and so on, but no luck. I use coax lead-in with a balun at the set. To get all channels I had to add a small trimmer capacitor across the antenna terminals. What's wrong?—A.P., Dallas, Tex.

I believe you're working in the wrong section. If you do get color on even one station, your color section must be okay, since it is common to all channels! This type of trouble can only be caused by something which is changed for different channels. The tuner, for example. Check your oscillator settings to make sure that you're on the right side of the color carrier, etc.


I would also, very definitely, check your antenna and lead-in system. Try taking it off entirely and substituting rabbit ears for a test. See if you can get color with this kind of setup, even if it is terribly snowy. If so, then your present antenna system has a "suckout" or trap effect in it somewhere that is attenuating the color signal on all channels except 4.

Car radio overload

I have a 1962 Chevrolet auto radio for repair, and the complaint is blurring and distortion when the customer gets too near to the radio station. Is there anything that can be done about this?—L.P.G., Secaucus, N. J.

The first step, which you may have already taken, is to make sure that his antenna trimmer is adjusted properly, for maximum volume at about 1,400 kHz. If this doesn't cure it, then you may have to modify the front end of the radio slightly.

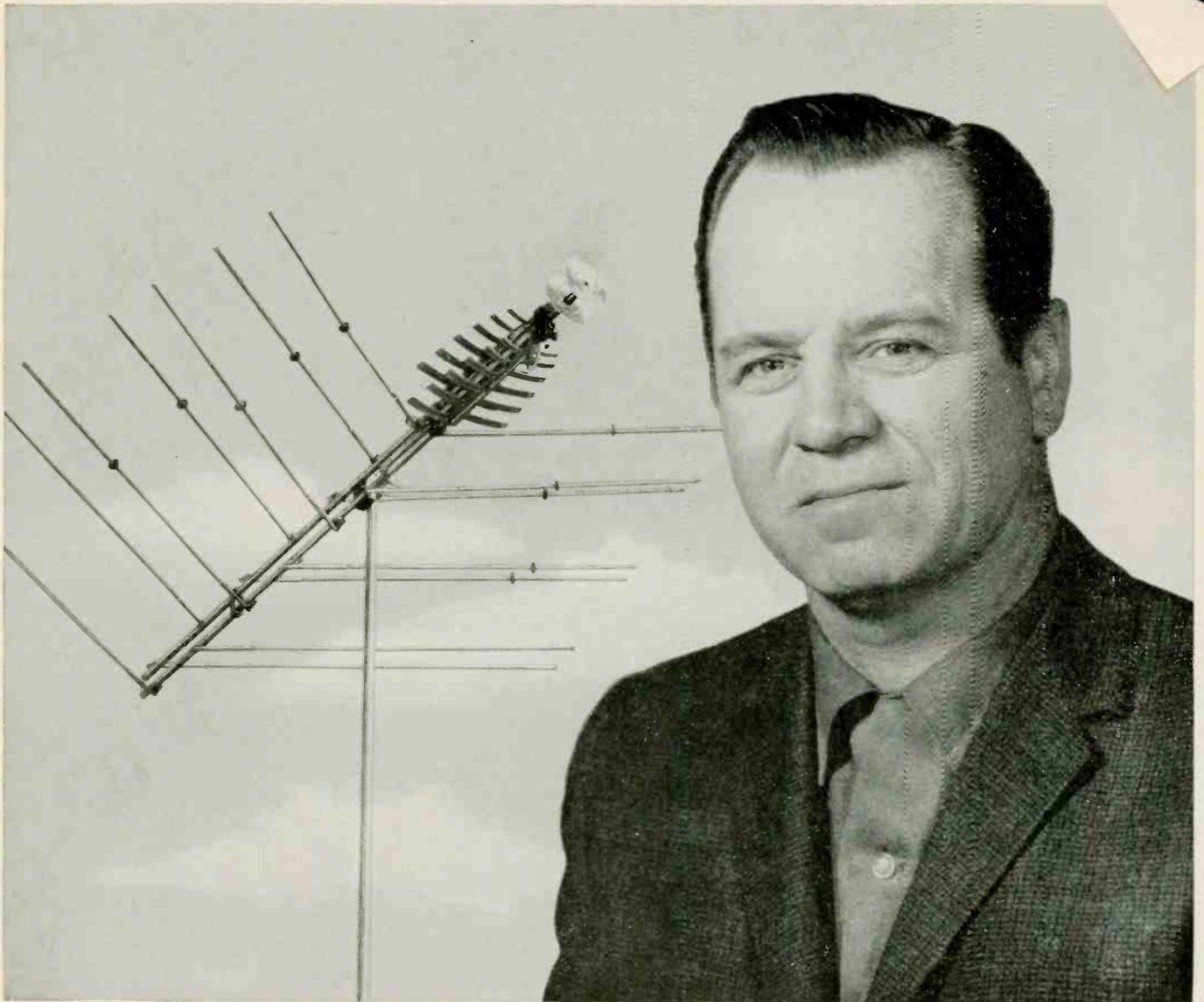The basic trouble is overloading of the rf transistor by the strong signal. Take the antenna coil out of the set, and, very carefully, unwind two turns from the secondary. This will cut down on the level of rf signal, and should reduce the distortion. END



“Out here in the fringes, your reputation depends on the pictures you deliver...”

That’s why we stick to JFD Color Laser antennas,” affirms HARRY MELANDER, of Melander’s Appliance Center, Alta, Iowa.

“The nearest TV stations to us are channels 4 and 9 from Sioux City, over 60 miles away and channel 21 from Fort Dodge, some 70 miles away in the opposite direction. And on their way here the signals have to get through some heavily wooded hills. This makes it real easy for snow and ghosts to creep into the pictures—especially in color.

“We rely on JFD LPV antennas exclusively because they always come through with reception that’s ghost-

free and color-true—despite this distance and terrain.”

Harry Melander depends on both LPV-TV Log Periodics and Color Lasers—like other professionals—to deliver the performance his customers expect from a professional.

Here’s why:

W-I-D-E BAND LPV LOG PERIODIC DESIGN delivers *more gain, higher signal-to-noise ratios, pinpoint directivity* that kills ghosts—VHF and UHF.

SHOWROOM QUALITY COLOR—flat response across each channel. No “suck-outs” or “roll-off.” *Out-performs* any other antenna in color or black/white—keeps customers sold.

CAPACITOR-COUPLED ELEMENTS work on *both* fundamental and harmonic modes. *Entire* antenna (not just part of it as in other antennas) responds to *every* channel.

RUGGED NEW “FLIP-LOK” ASSEMBLY snaps out elements—keeps them *tight* and right on target.

Switch to the JFD LPV—the professional’s antenna • Your JFD LPV distributor can prove it to you!

JFD®

JFD ELECTRONICS CO.

15 Avenue at 62 Street, Brooklyn, N.Y. 11219

JFD International, 64-14 Woodside Ave., Woodside, N.Y. 11377 JFD Canada, Ltd., Ontario, Canada

JFD de Venezuela, S.A., Avenida Los Haticos 125-97, Maracaibo, Venezuela

LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,958,081; 2,945,879; 3,011,164; 3,108,280; 3,150,376; 3,210,767; RE. 25,740 AND ADDITIONAL PATENTS PENDING IN U.S.A. AND CANADA. PRODUCED BY JFD ELECTRONICS CO. UNDER EXCLUSIVE LICENSE FROM THE UNIVERSITY OF ILLINOIS FOUNDATION. LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,955,287 AND 3,015,821 AND ADDITIONAL PATENTS PENDING.

Circle 22 on reader’s service card

Gene Frost was “stuck” in low-pay TV repair work. Then two co-workers suggested he take a CIE home study course in electronics. Today he’s living in a new house, owns two good cars and a color TV set, and holds an important technical job at North American Aviation. If you’d like to get ahead the way he did, read his inspiring story here.

IF YOU LIKE ELECTRONICS—and are trapped in a dull, low-paying job—the story of Eugene Frost’s success can open your eyes to a good way to get ahead.

Back in 1957, Gene Frost was stalled in a low-pay TV repair job. Before that, he’d driven a cab, repaired washers, rebuilt electric motors, and been a furnace salesman. He’d turned to TV service work in hopes of a better future—but soon found he was stymied there too.

“I’d had lots of TV training,” Frost recalls today, “including numerous factory schools and a semester of ad-

vanced TV at a college in Dayton. But even so, I was stuck at \$1.50 an hour.”

Gene Frost’s wife recalls those days all too well. “We were living in a rented double,” she says, “at \$25 a month. And there were no modern conveniences.”

“We were driving a six-year-old car,” adds Mr. Frost, “but we had no choice. No matter what I did, there seemed to be no way to get ahead.”

Learns of CIE

Then one day at the shop, Frost got to talking with two fellow workers who were taking CIE courses... pre-

paring for better jobs by studying electronics at home in their spare time. “They were so well satisfied,” Mr. Frost relates, “that I decided to try the course myself.”

He was not disappointed. “The lessons,” he declares, “were wonderful—well presented and easy to understand. And I liked the relationship with my instructor. He made notes on the work I sent in, giving me a clear explanation of the areas where I had problems. It was even better than taking a course in person because I had plenty of time to read over his comments.”

Studies at Night

“While taking the course from CIE,” Mr. Frost continues, “I kept right on with my regular job and studied at night. After graduating, I went on with my TV repair work while looking for an opening where I could put my new training to use.”

His opportunity wasn’t long in coming. With his CIE training, he qualified for his 2nd Class FCC License, and soon afterward passed the entrance examination at North American Aviation. “You can imagine how I felt,” says Mr. Frost. “My new job paid \$228 a month more!”


“CIE training helped pay for my new house,”

says Eugene Frost
of Columbus, Ohio



Circle 23 on reader's service card

Currently, Mr. Frost reports, he's an inspector of major electronic systems, checking the work of as many as 18 men. "I don't lift anything heavier than a pencil," he says. "It's pleasant work and work that I feel is important."

Changes Standard of Living

Gene Frost's wife shares his enthusiasm. "CIE training has changed our standard of living completely," she says.

"Our new house is just one example," chimes in Mr. Frost. "We also have a color TV and two good cars instead of one old one. Now we can get out and enjoy life. Last summer we took a 5,000 mile trip through the West in our new air-conditioned Pontiac."

"No doubt about it," Gene Frost concludes. "My CIE electronics course has really paid off. Every minute and every dollar I spent on it was worth it."

Why Training is Important

Gene Frost has discovered what many others never learn until it is too late: that to get ahead in electronics today, you need to know more than soldering connections, testing circuits, and

replacing components. You need to really know the fundamentals.

Without such knowledge, you're limited to "thinking with your hands" ... learning by taking things apart and putting them back together. You can never hope to be anything more than a serviceman. And in this kind of work, your pay will stay low because you're competing with every home handyman and part-time basement tinkerer.

But for men with training in the fundamentals of electronics, there are no such limitations. They think with their heads, not their hands. They're qualified for assignments that are far beyond the capacity of the "screw-driver and pliers" repairman.

The future for trained technicians is bright indeed. Thousands of men are desperately needed in virtually every field of electronics, from 2-way mobile radio to computer testing and troubleshooting. And with demands

like this, salaries have . . . Many technicians earn \$8,000, \$12,000 or more a year.

How can you get the training you need to cash in on this booming demand? Gene Frost found the answer in CIE. And so can you.

Send for Free Book

Thousands who are advancing their electronics careers started by reading our famous book, "How To Succeed In Electronics." It tells of the many electronics careers open to men with the proper training. And it tells which courses of study best prepare you for the work you want.

If you'd like to get ahead the way Gene Frost did, let us send you this 40-page book free. With it we'll include our other helpful book, "How To Get A Commercial FCC License." Just fill out and mail the attached card. Or, if the card is missing, write to CIE at the address below.



CIE

**Cleveland Institute
of Electronics**

1776 E. 17th St., Dept. RE-39
Cleveland, Ohio 44114

Accredited Member National Home Study Council

ENROLL UNDER G.I. BILL

All CIE courses are available under the new G.I. Bill. If you served on active duty since January 31, 1955, or are in service now, check box on reply card for G.I. Bill information.



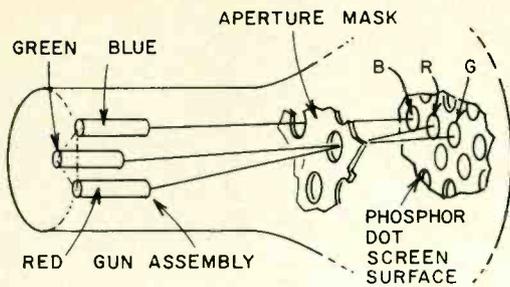


Fig. 1—The aperture mask guides the beams.

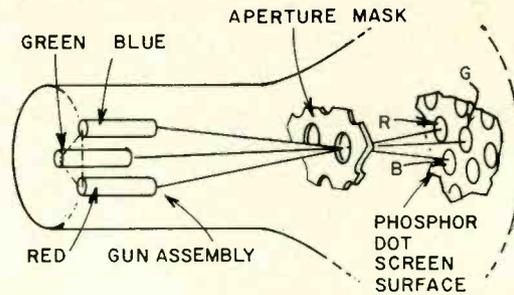


Fig. 2—If one beam doesn't track with the others, it can pass through the wrong hole in the mask.

Learn Color the Programed Way

You'll find this an easy system for picking up the fundamentals painlessly By GLENN M. RAWLINGS

Do you hate to study? Do you have trouble remembering what you've read? Maybe you'll find this question-and-answer technique easier to follow. Just begin by reading BLOCK 1.

As you can see in Fig. 1, the neck of a color picture tube contains three electron guns. They are focused through an aperture mask so the electron beam from each gun strikes only a particular group of phosphor dots on the screen surface. Unlike black-and-white TV, where only one type of phosphor material is used, three types are required for color. Each phosphor emits either red, blue or green light when struck by an electron beam. The phosphor dots are arranged in a triangular pattern. Normally, the beam from one of the guns strikes only the red dots, another the green, and the third strikes only the blue dots. If any two of the guns are turned off, the screen should then be a solid-color display of either red, blue or green; obviously this depends on which gun is on. This proper gun-dot relationship is called *purity*.

In practice you can't obtain an *absolutely* pure screen. By careful adjustment, though, you'll get nearly perfect purity. In general, there are two purity adjustments: Whole-screen purity is adjusted by moving a double ring-magnet assembly around the neck of the tube. Purity near the outer edges of the screen is accomplished by moving the deflection yoke forward or backward on the neck of the picture tube. Both these adjustments magnetically affect the electron beams of all three guns; each beam then strikes only its own color phosphor dots on the screen surface. Important point: *purity adjustments affect all three beams simultaneously. So will a stray magnetic field near the CRT.*

Question: Which of the following would have the most effect on the screen purity of a color receiver?

- Adjustment of the i.f. strip. Go to **Block 20.**
- Received signal strength. Go to **Block 8.**
- A stray magnetic field near the area of the picture tube. Go to **Block 7.**

2 Not correct. Return to **BLOCK 12** and restudy.

3 Wrong. Go back to **BLOCK 7**, restudy and select another answer.

4 Would you believe . . . *false!* Go back to **BLOCK 11** for the correct answer.

Through the process of elimination, you have chosen the correct answer. This same procedure should be used for all servicing.

The color picture tube can reproduce black-and-white images only under certain conditions. When no signal is being received, the screen (or raster) will seem white (assuming the color circuits are operating properly). This is so because all three guns are turned on. Your eye mixes the colored light into white.

The light values between black and white are called gray-scale values.

As shown in Figs. 1 and 2, there are three different color phosphor dots on the screen surface. To produce a correct gray scale, the amount of light emitted from each phosphor dot must be equal to the others. Since there is a considerable difference in the efficiency of the phosphors, a different beam intensity is required for equal light emission. For example, to produce a white screen, the green gun may contribute only about 25%; the red and blue guns contribute the remaining 75%.

In order for the various light levels in a monochrome picture to appear as proper values of gray, a definite relationship of the three beam currents must be maintained. The primary adjustments for setting this relationship are the screen and background controls.

Question: In a color tube producing a white raster, the beam currents from each gun are different. Why?

- To compensate for losses in beam energy due to their striking the aperture mask. Go to **Block 14**.
- To compensate for the difference in emission efficiency of the red, blue and green phosphor materials. Go to **Block 21**.
- Because of improper adjustments to the screen controls. Go to **Block 16**.

6 No. Return to **BLOCK 15** and try again.

Your answer is right. A stray magnetic field would put a steady deflection force on the beams, causing them to strike improper phosphor dots. The symptom of this unwanted field usually is a colored patch on some area of the screen. Degaussing the picture tube will eliminate the problem.

As previously mentioned, the purity adjustments affect all three guns simultaneously. The next adjustments to be mentioned control beam deflection of each gun separately.

Even though you get correct purity, it is possible for one, two or all three of the beams to be passing through the wrong holes in the aperture mask. Notice in Fig. 2 that the blue beam is actually passing through a different hole in the mask than the other two. Although it is striking the proper color, the blue beam isn't positioned properly with respect to the other beams.

For proper color pictures, the beams must be converged, or aligned, so that all three pass through the same hole at the same time. This is called *convergence*. If the beams do not converge properly, a color fringe will appear around the edge of objects on a b-w picture.

To make convergence adjustments, you *must* use a dot or crosshatch pattern to see what effect you're having on the beams. The convergence controls interact; if you adjust one, you'll have to adjust the others.

During *static* convergence adjustments, the beams are first made to overlay each other in the center of the screen. When the beams are deflected toward screen edges, they travel farther and pass through the mask at a different angle than before. Because of this, *dynamic* convergence voltages are applied to coils around the

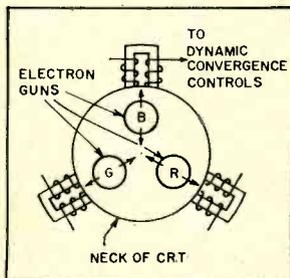


Fig. 3—If you could look into the neck of the tricolor CRT from behind the screen, this is what you'd see. Electron beams from the three guns are deflected dynamically by magnetic fields produced by the coils.

neck of the tube (Fig. 3). These coils create fields which deflect the electron beams slightly. Thus proper convergence is maintained during the entire scanning process.

Question: Which of the following best describes a convergence problem?

- The raster is not a pure, solid color. Go to **Block 3**.
- When viewing a black-and-white picture, you see a fringe of green on the edge of objects in the scene. Go to **Block 12**.
- In a black-and-white picture, areas of low brightness seem to be more purple than black. Go to **Block 18**.

8 Your answer is *wrong!* Return to **BLOCK 1**.

9 Wrong. While it is true that some technicians have a permanent "crosshatch" burned on their eyeballs from long convergence sessions, this is not the answer. Return to **BLOCK 17**.


10 Wrong. Return to **BLOCK 17** and reread.

Your answer is correct. When proper, the delay causes black-and-white (luminance) and color (chrominance) signals to overlap each other at the picture tube. Troubles in the delay line can cause symptoms such as ghosts or a complete loss of picture.

As previously mentioned, the 3.58-MHz local oscillator is synchronized to the transmitted color burst signal. This *phase-locked* signal is then "mixed" in the color demodulator tubes and compared with the transmitted color sideband information. The instantaneous color-demodulator-tube plate voltage represents picture-tube beam intensity for a given color at a specific time. In practice, only red and blue sidebands are mixed in the demodulator tubes. Green is produced by comparing the blue and red demodulated signals against the reference luminance signal. Luminance (or Y) contains all three colors—red, green and blue. This re-establishes a definite relationship which existed at the transmission of these signals. A process called *matrixing* produces the proper amounts of red, blue and green by algebraic summation of the various signals.

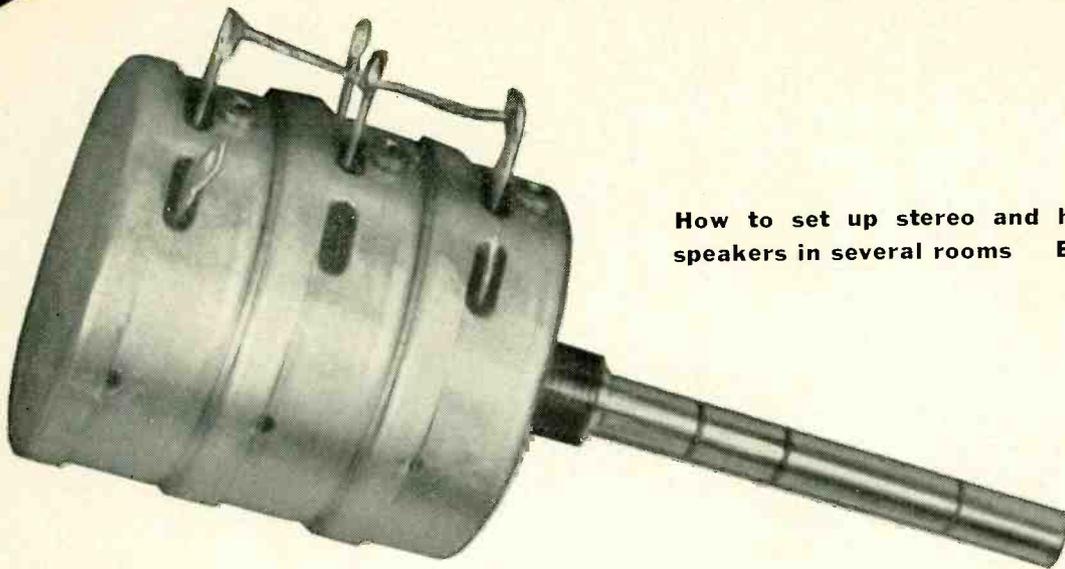Question: The 3.58-MHz crystal controlled (local) oscillator is synchronized to the color sideband signal.

- True. Go to **Block 4**.
- False. Go to **Block 17**.



How to set up stereo and hi-fi systems with speakers in several rooms By JAMES A. FRED

KNOW YOUR L- AND T-PADS

FREQUENTLY, IT IS NECESSARY TO VARY the volume of a loudspeaker independently of the amplifier, as in the case of a remote speaker in a bedroom. To achieve attenuation and to avoid the introduction of distortion, a "pad" can be used. A pad is an attenuator that does not change the circuit impedance as attenuation is varied.

The L-pad

The L-pad is less expensive to build than the T-pad, since only two resistance sections are ganged together. The resistance element in the front section is called the series leg; the back element is called the shunt leg. The L-pad (Fig. 1), consisting of two sections, maintains the circuit impedance independent of attenuation at only one pair of terminals.

To analyze the operation of an L-pad, refer to Table I, "Rotational Measurements for a 16-Ohm L-Pad." As an example, let us use a 16-ohm speaker connected to a 16-ohm L-pad and an amplifier. (The data in this table are actual measurements made on production L-pads.) Notice that the resistance of the series leg is the same as the characteristic impedance of the L-pad,

while the resistance of the shunt is eight times as much. At the counterclockwise end, or 0° of rotation, series resistance is 16.29 ohms, shunt resistance 0.2 ohm, impedance 16 ohms, and attenuation 38.2 dB. At 50% or 150° of rotation, series resistance is 7.76 ohms, shunt resistance 18.5 ohms, impedance 16.35

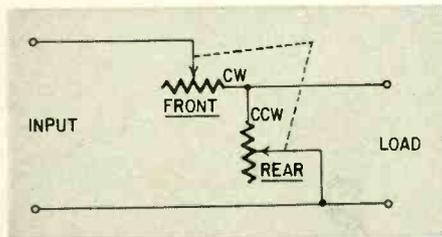


Fig. 1—Diagram of a variable L-pad.

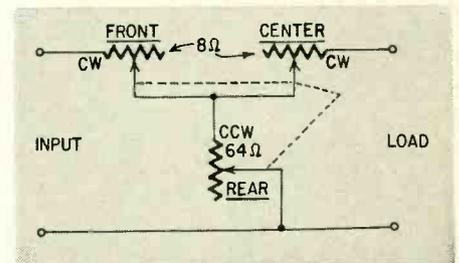


Fig. 3—A typical 8-ohm variable T-pad.

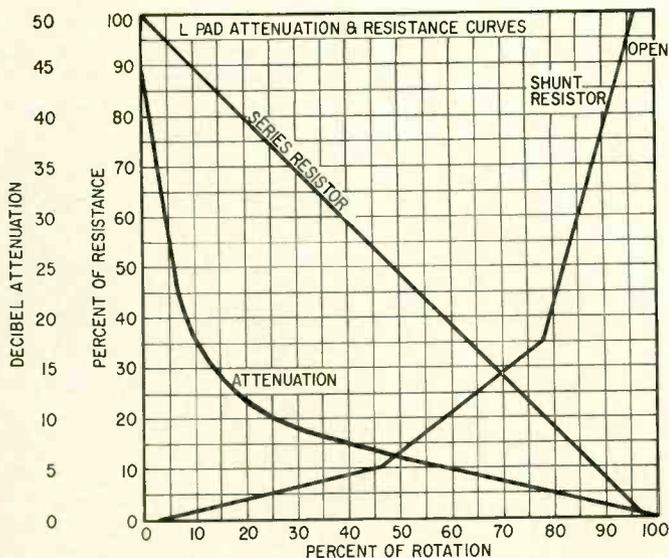


Fig. 2—How attenuation of L-pad changes as shaft is rotated.

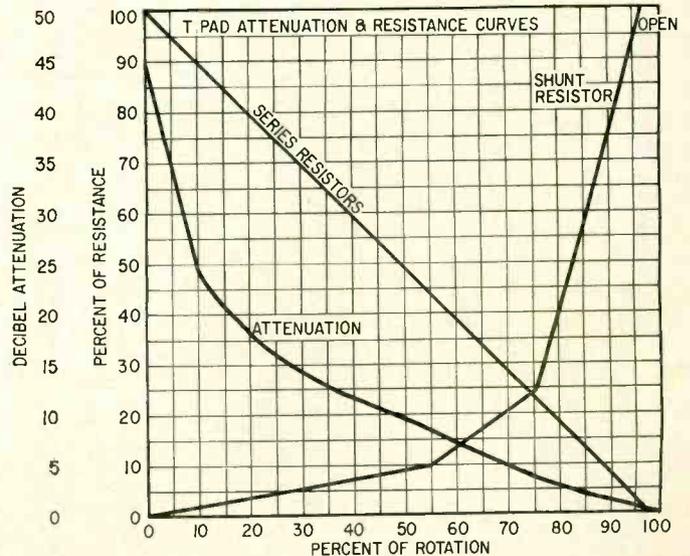


Fig. 4—Typical attenuation curves for a variable T-pad.

ohms, and attenuation 5.4 dB. At 100% or 293° of rotation, series resistance is 0.19 ohm, shunt resistance is infinite, impedance is 16.19 ohms, and attenuation is practically zero. As the L-pad is rotated from one end to the other, the impedance stays essentially the same.

The graph of Fig. 2, "L-Pad Attenuation and Resistance Curves," can be used to approximate the necessary resistance values for the resistance legs. Notice that the series leg is linear, while the shunt resistor is a tapered winding in three linear sections. This tapered winding gives the L-pad a more nearly linear attenuation. Total resistance of the shunt leg will be eight times that of the series leg. The series resistance will be the same as the rated impedance of the L-pad. Total attenuation is 45 dB. Since the threshold of audibility usually is assumed to be -60 dB, you will still be able to hear a signal even with the L-pad turned to the counterclockwise end of rotation. If it becomes necessary to cut the sound out completely, a switch must be used to open up the line. If so, it would be best to have the switch substitute a fixed resistor of the same value as the L-pad, to maintain proper loading in the circuit.

L-pads can be used as described to control the volume of loudspeakers, but T-pads are generally preferred for this purpose, as explained in the following section.

The T-pad

Where it is important that an attenuator and the amount of attenuation have no effect on circuit impedance, a T-pad is used. The T-pad (see photo and Fig. 3) consists of three control sections ganged together and operated by a single shaft. The front and middle elements have resistance values equal to the impedances they are to be matched to, and are referred to as the legs. The resistance of the rear element, or shunt leg, is usually eight times the value of either of the series legs.

Table II, "Rotational Measurements For an 8-Ohm T-Pad," shows how the T pad operates. When the control is at the ccw end of rotation, the input series resistance is 8.26 ohms, output series resistance 8.09 ohms, impedance 8.26 ohms, and attenuation 53.5 dB. At 50% or 150° rotation, the input series resistance is 3.93 ohms, output series resistance 3.92 ohms, impedance 7.87 ohms, and attenuation 9.65 dB. At full clockwise rotation, the input series resistance is .036 ohm, output series resistance .029 ohm, impedance 8.06 ohms, and attenuation practically zero. From one end of rotation to the other, the T-pad impedance stayed at essentially 8 ohms.

The graph of Fig. 4, "T-Pad At-

tenuation and Resistance Curves," can be used to approximate the resistance necessary for the resistance legs. For example, let us say that we need a 16-ohm T-pad. From the curves, we find that the series leg will be a 16-ohm linear-wound element, and that two will be needed.

The shunt element will be eight times this value, or 128 ohms, made in three linear sections. The first section of the shunt element should be 10% of the overall resistance, or about 13 ohms in the first 55% of rotation. The second section should be 15% of the overall resistance, or 20 ohms in the next 21%

of rotation. The third section of the shunt winding should be 75% of the overall resistance, or 95 ohms in the next 21% of rotation. The shunt coil is open for the last 3% of its rotation.

Those who are content to accept the preceding explanation on faith alone can stop here, and will probably be satisfied to buy and use L- and T-pads as always in the past. For those who are mathematically minded, we will proceed a little deeper into the subject.

The attenuation of a resistance pad is expressed as a number of decibels (dB), where the dB expresses the ratio between two different amounts of power

TABLE I.
Rotational Measurements For a 16-Ohm L Pad.

Degrees of Rotation	Series Resis.	Shunt Resis.	Impedance	Decibels Atten.
0	16.29	0.20	16.00	38.2
10	15.74	0.26	16.00	35.9
20	15.18	1.45	16.51	21.6
30	14.49	2.41	16.58	17.7
40	13.94	3.52	16.83	14.9
50	13.39	4.62	16.98	13.0
60	12.84	5.73	17.06	11.6
70	12.30	6.67	17.00	10.3
80	11.74	7.72	16.94	9.7
90	11.06	8.62	16.66	9.1
100	10.51	9.72	16.56	8.4
110	9.86	10.83	16.42	7.9
120	9.41	11.71	16.17	7.5
130	8.87	12.82	15.99	7.0
140	8.31	14.73	15.99	6.4
150	7.76	18.50	16.35	5.4
160	7.10	22.17	16.40	4.7
170	6.54	25.94	16.44	4.2
180	5.98	29.75	16.60	3.8
190	5.44	33.56	16.25	3.4
200	4.90	37.39	16.11	3.1
210	4.38	41.20	15.90	2.9
220	3.80	44.47	15.56	2.7
230	3.27	52.34	15.52	2.3
240	2.80	65.50	15.66	1.9
250	2.32	83.10	15.62	1.5
260	1.61	99.30	15.37	1.3
270	1.01	115.5	15.06	1.2
280 (hop-off)	0.41	125.3	14.56	1.0
290	0.16	inf.	16.16	0.09
293	0.19	inf.	16.19	0.09

KNOW YOUR L- AND T-PADS

at two points—input and output, in this case.

$$\text{decibels} = 10 \text{ Log } \frac{P_1}{P_2}$$

$$= 20 \text{ Log } \frac{V_1}{V_2} = 20 \text{ Log } \frac{R_1}{R_2}$$

Strictly speaking, dB's can be used to express voltage or current ratios only when the two points in question have the same impedance value. However, when matching stereo controls in actual practice, input and output impedances are ignored. It is mainly in speaker

matching, in the telephone industry, and in the broadcast industry that impedances are so critically matched.

Let us go back to the impedance of the T-pad and draw an equivalent-circuit diagram (Fig. 5), but with a load. As you can see, the first series leg (8.26 ohms) is in series with the shunt leg (.034 ohms), which is in parallel with the second series coil (8.09 ohms), which is in series with the 8-ohm load impedance. Working it out in simple arithmetic, we have 16.09 ohms in parallel with .034 ohm, which gives us .03 ohm. The 8.26 ohms and .03 ohm added

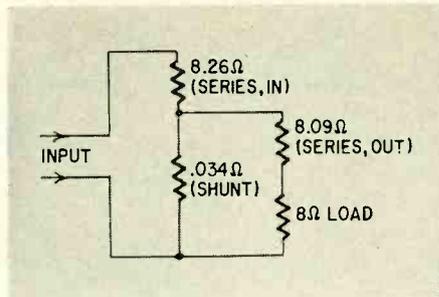


Fig. 5—Equivalent circuit of a T-pad and its load set up for the maximum loss.

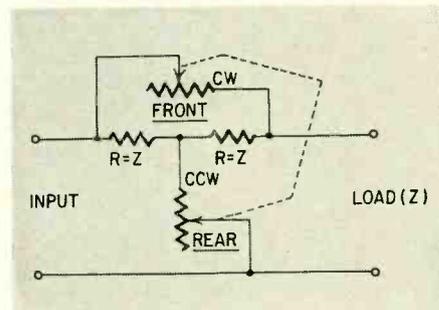


Fig. 6—A variable bridge-T attenuator has only two elements which change value. ("Front" and "rear" labels are reversed.)

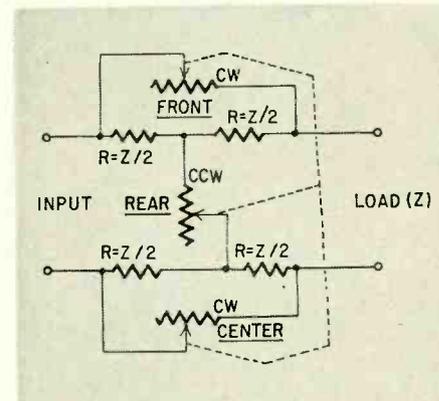


Fig. 7—Variable bridge-H attenuator has three variable and four fixed resistors.

together give us approximately 8 ohms, the nominal impedance of this T-pad.

An equivalent-circuit diagram of the L-pad can be drawn and analyzed the same way.

This article is limited to L- and T-pads, because these are the ones most readily available to technicians and experimenters. There are other types.

Instead of T-pads, some companies supply variable bridged-T pads; these require only two variable sections plus two fixed resistors. This is less expensive and, in many cases, a bridged-T pad (Fig. 6) will work adequately in place of a straight 3-section T-pad.

Another type usually available on request is the bridged-H pad (Fig. 7). This pad consists of a conventional T-pad with four fixed resistors connected as shown. The resistors help to give a more linear attenuation curve. END

TABLE II.
Rotational Measurements For an 8-Ohm T Pad.

Degrees of Rotation	Series in Resis.	Shunt Resis.	Series out Resis.	Impedance	Decibels Atten.
0	8.26	.034	8.09	8.26	53.5
10	7.98	.0826	7.98	8.08	45.8
20	7.68	.480	7.68	8.14	30.6
30	7.40	.910	7.38	8.26	25.1
40	7.09	1.35	7.04	8.33	21.7
50	6.80	1.78	6.78	8.39	19.4
60	6.53	2.22	6.53	8.46	17.6
70	6.23	2.66	6.22	8.47	16.05
80	5.92	3.02	5.91	8.40	15.00
90	5.63	3.47	5.61	8.40	13.85
100	5.33	3.90	5.38	8.35	12.9
110	5.03	4.27	5.02	8.25	12.15
120	4.79	4.72	4.78	8.23	11.4
130	4.49	5.10	4.50	8.16	10.8
140	4.24	5.51	4.22	8.04	10.2
150	3.93	5.87	3.92	7.87	9.65
160	3.69	6.30	3.63	7.78	9.10
170	3.37	6.87	3.32	7.65	8.45
180	3.09	8.53	3.10	7.90	7.25
190	2.80	10.20	2.80	8.05	6.30
200	2.50	11.95	2.50	8.08	5.20
210	2.20	13.63	2.20	8.03	4.90
220	1.95	15.00	1.90	7.91	4.45
230	1.65	18.09	1.65	7.94	3.70
240	1.40	27.08	1.35	8.35	2.80
250	1.10	36.10	1.11	8.39	1.95
260	.806	45.18	.858	8.20	1.60
270	.507	54.2	.57	7.91	1.30
280	.231	63.1	.28	7.57	1.05
285 (hop-off)	.083	63.3	.107	7.27	1.05
290	.0307	inf.	.0286	8.05	.065
293	.036	inf.	.029	8.06	.065

Creative Electronic Servicing

Think logically before you troubleshoot and you'll solve the problem faster

By LARRY ALLEN

CAUSE-TO-EFFECT REASONING. TUBE changing. Parts substitution. Hit-and-miss. Cut-and-try. Localizing. Signal tracing. Parts checking. Sectionalizing. Signal injection. Half-section analysis. Divide and test.

All these terms are familiar. Each represents an approach to the problem of finding the cause of trouble in a faulty piece of electronics gear. There are two more terms I'd like to add: psychology and creativity.

You may already have a pretty good idea how psychology applies to troubleshooting. My dictionary calls *psychology* the science of the mind—why people think and act as they do. Your most powerful troubleshooting tool is your mind; it sorts and classifies whatever trouble clues you track down and figures out what is causing them.

If your mind tracks down and processes the clues logically, you are a good troubleshooter. If you jump around from clue to clue, in no logical order, chances are you run into tough dogs more often than you should.

So . . . what about creativity? *Creativity*, according to the dictionary, has to do with inventiveness. In just those terms, then, we can say that creative troubleshooting is finding (inventing) new ways to locate faults in electronic equipment.

What thoughts run through your mind when you first walk up to a repair job on your bench—say, a television receiver? If you have a paper handy right now, jot down what your first step is.

You will use at least three of your senses: *sight*, to see if the raster or picture comes on or if the tubes light, and to watch for smoke or other visual signs of trouble; *hearing*, to verify if the sound section works or has too much hum, or if the horizontal oscillator is working, or if the telltale crackling is there when the high voltage first comes on; and *smell*, to decide if anything is overheating, or sniff ozone caused by corona.

In all these cases, sensory stimuli (as psychology manuals call them) are being sent to your brain in hopes it can

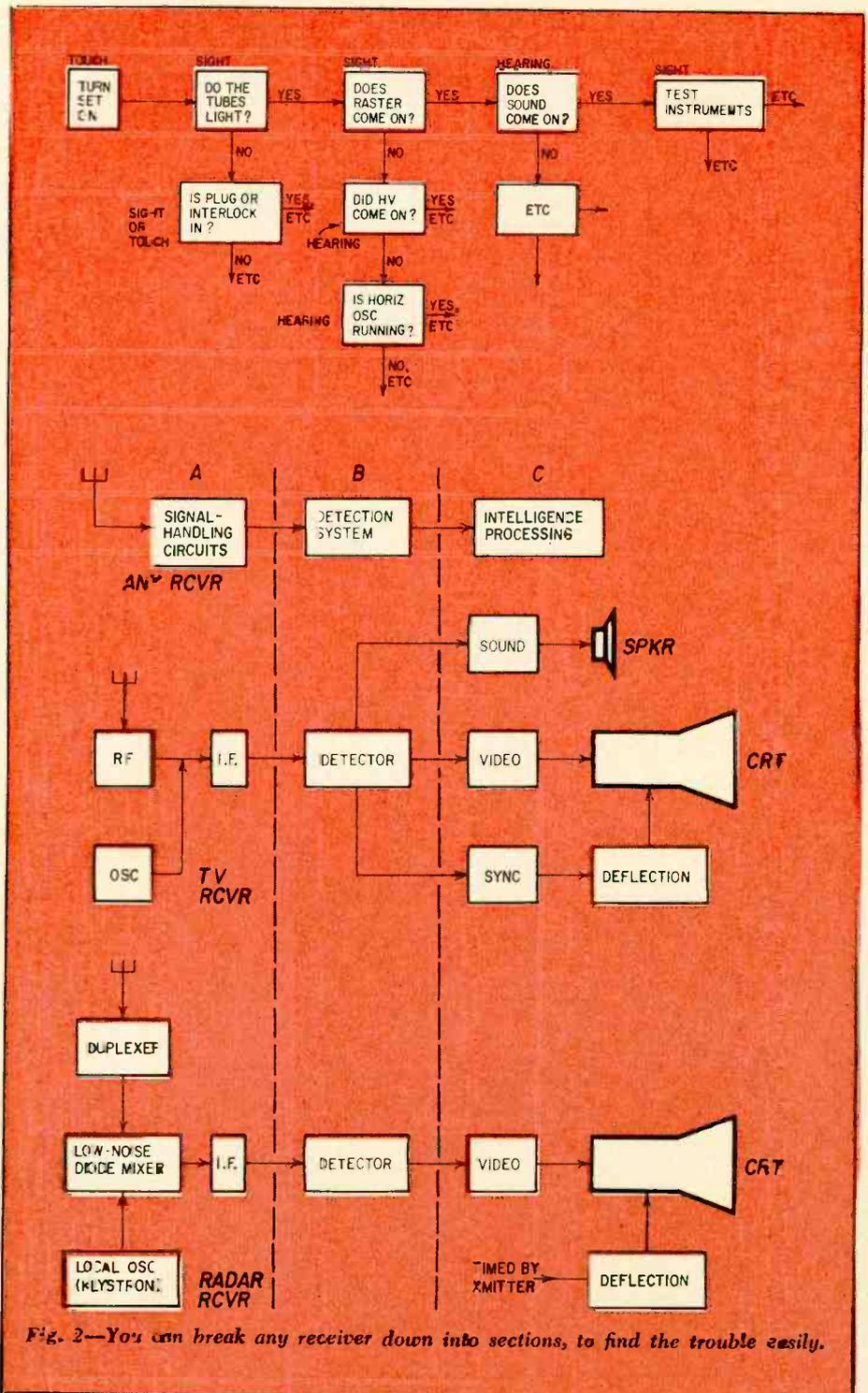


Fig. 2—You can break any receiver down into sections, to find the trouble easily.

Creative Electronic Servicing

decipher their meanings. All the information from the four senses funnels into the computer you think of as your brain; the output is some conclusion about the information.

Now, about the psychology of that conclusion. Here is how a conclusion is synthesized (another psych-book term) in one example. You *sniff*: no smell of burning, so on to the next sense. You *listen*: no station sound, but you can hear the horizontal oscillator start and the high voltage charge up the aquadag on the CRT, so your brain registers that something is blocking station sound. You *feel*: the volume-control knob is all the way down and turning it up brings on station sound. Your brain registers that the set's stimuli to smell and hearing are normal.

Finally you *look*: the screen is black. Brain says, aha! Here is a major clue. Conclusion, then: The trouble in this set is something that prevents a raster in spite of the high voltage you already know is present (you heard it crackle into existence).

Then you go on to other stimuli or combinations of them. You probe with your senses for other clues. When your senses have reached their limits, you employ extensions of them. Meters, scopes, probes, and other instruments give your brain—via your senses, even with the instruments—a clue to where the real trouble lies.

For most effective troubleshooting, the thought process or psychology of your actions should follow a logical pattern. This pattern can be broken down a little further. It can be thought of as *yes* and *no* responses to questions your brain is asking through your senses. Take a look at the brief example in Fig. 1. When you reach the point where your senses can't tell you any more (and this point is reached quickly, for the brain sorts clues rapidly), then test instruments provide the next clues for your brain to process.

From this you can see that troubleshooting can be broken down psychologically into fairly simple steps or decisions. Many of them take only split

fractions of a second. To the experienced technician these decisions seem second-nature and are made almost without conscious thought. The many conclusions are drawn so automatically, quickly and unnoticeably that the uninitiated, watching an old-timer work, is almost always totally unaware so many decisions are even being made. An apprentice often doesn't even learn about this logical—psychological reasoning that is so important a part of competent troubleshooting. He gets the idea that the old-timer's speed is all the result of experience.

Now let me get back to creativity, and how it applies to troubleshooting. An interesting thing about the creative approach to servicing is that it is useful to newcomer and old-timer alike. Learned thoroughly and used properly, creative methods do not depend on experience. You do not have to memorize hundreds of case histories. You can troubleshoot a set using the creative approach without ever having serviced that particular complaint or set before.

One warning! No system of servicing—creative or otherwise—is a substitute for knowing the operation of the system or equipment you are servicing. You *must* learn the operation of basic circuits and their interrelationships, and then you can apply creative techniques to servicing any possible combination of these circuits. That is why no electronic equipment will be beyond your ability.

Creativity equals inventiveness. That doesn't mean you have to redesign or reinvent the circuit to service it properly. It means you should practice inventiveness in your approach to servicing the circuit.

Creativity begins when you decide what question to ask of the set, section or circuit. Take the yes-no approach, for example. In the troubleshooting situation cited earlier, you smelled, listened, looked, and felt. Each time, you made an answer. If you looked to see if a tube was lit, you decided either yes it was or no it wasn't. If you smelled to see if the power transformer was smoking, you decided it was or wasn't. If you felt to see if it was too hot, either it was or it wasn't. You have to analyze the circuit to ask the right question.

If the yes-no system will work when you ask questions with your senses, it will also work when you ask them with test instruments. If you're checking with a voltmeter at the plate of a tube, you're asking: Is voltage there? Answer, yes or no. If yes, is it low? Yes or no. If no, then is it high? Yes or no. You ask and answer this series of questions in the time it takes to touch the probe to the tube pin. The instrument lets you see

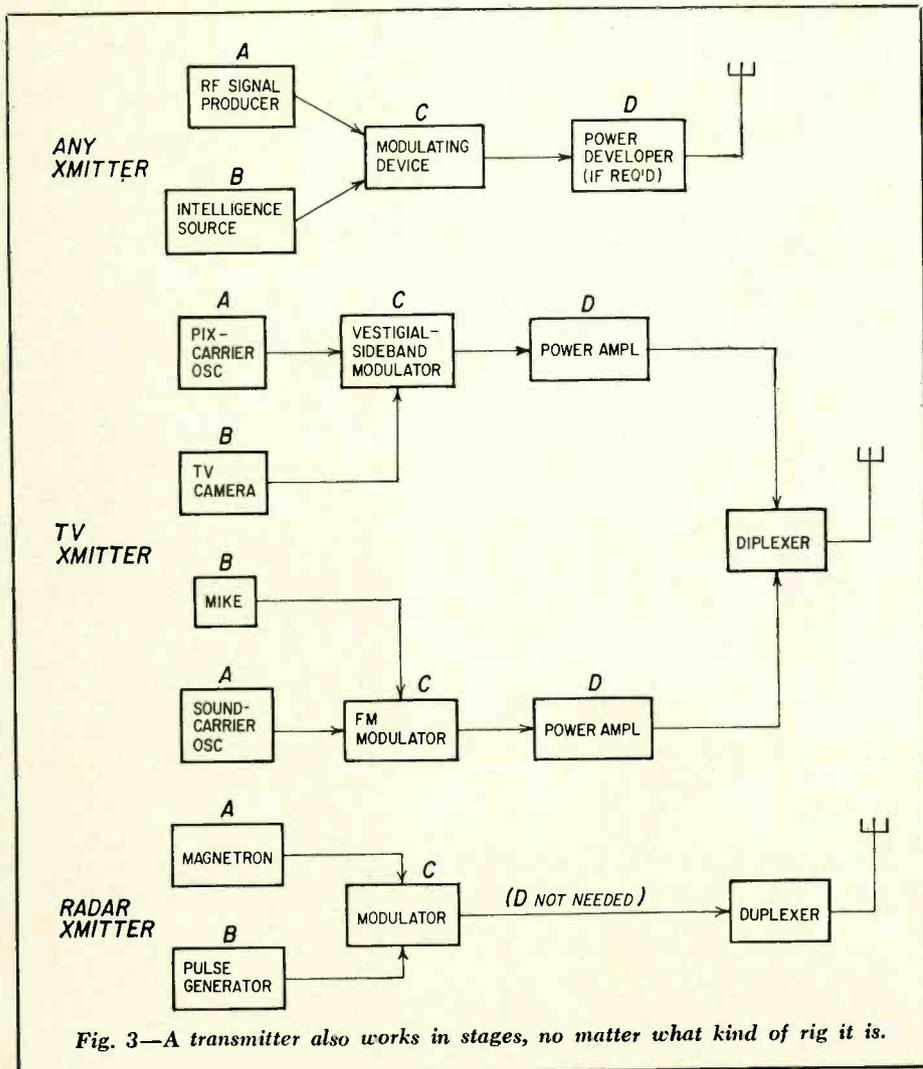


Fig. 3—A transmitter also works in stages, no matter what kind of rig it is.

something you couldn't observe with your unaided senses.

Suppose you're signal-tracing an audio section by the injection method. You touch the generator output probe to the audio amplifier plate and listen. Is there sound at the speaker? Yes or no. If no, go on to the next point nearer the speaker. If yes, move back toward the detector or audio input point. You're using instruments to supplement your senses. And you're employing creativity to select the questions you ask of the circuit. In any overall servicing process, you can put creativity to work on section stage, circuit, part.

If you still don't understand how creativity fits in, here are some long sentences that may clarify it for you: *Creativity* is involved when you decide just what troubleshooting technique you will use in a particular set or with a particular complaint. *Creativity* is being used when you adapt a single principle of troubleshooting to fit the many servicing situations or the various equipments you encounter. *Creativity* means putting clues together to draw a conclusion: Which system is at fault, which section is at fault, which stage is at fault, which circuit is at fault, and finally which part is at fault. *Creativity* is in the picture when you are deciding what to do about the fault: Do you align, repair or replace? Do you order an exact replacement or can you substitute? And so on.

Now let's move back to psychology—the thought processes of creative servicing. The best place to start servicing any equipment is by visualizing it as a whole system, made up of main sections. Fig. 2 shows how a receiver is sectionalized and how this division applies to a TV receiver and to a radar receiver. The identical main sections exist in a CB receiver, a satellite receiver, a microwave relay receiver, transistor radio, and in any other kind of receiver that you can imagine.

Fig. 3 shows the same principle of breaking into sections as it is applied to transmitters. You can easily see how it applies to TV and radar transmitters. The same principles apply to other transmitters, no matter what their primary purpose.

Understanding the basic premise, you can move on to the next step in creative troubleshooting: breaking the section down into stages. Fig. 4 shows the fundamentals. We're taking the A section of both receivers in Fig. 2 and breaking down only that section. You can see how nearly alike these sections are in a radar receiver and a television receiver. If you apply creative thinking to your troubleshooting, you'll find you can service the one just as easily as the other.

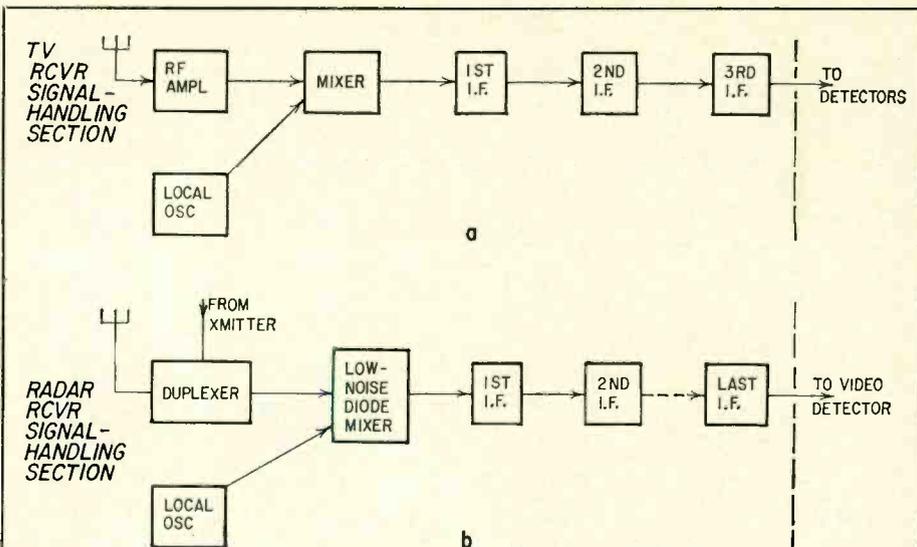


Fig. 4—Though you may know only TV, chances are you could service radar.

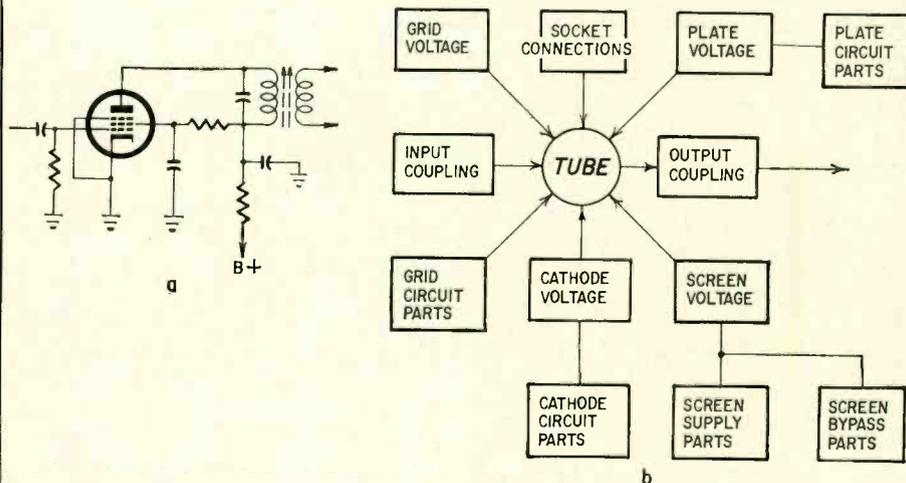


Fig. 5—Once you've found the defective stage, break it down into components.

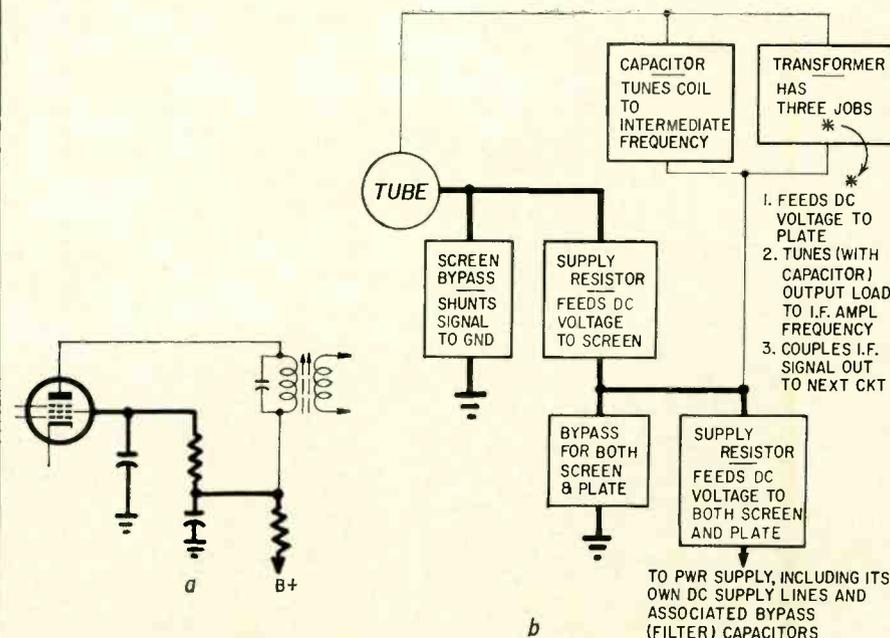



Fig. 6—Keep in mind the functions that each device is supposed to perform.

Creative Electronic Servicing

Creative troubleshooting now has brought you to the logical breakdown of sections into stages. What do you do with the stages? Ask them questions just as you did the sections. Is the signal getting through the mixer? Yes or no. Is the signal reaching the third i.f.? Yes or no.

On each answer you base your next logical step. Good psychology (thinking).

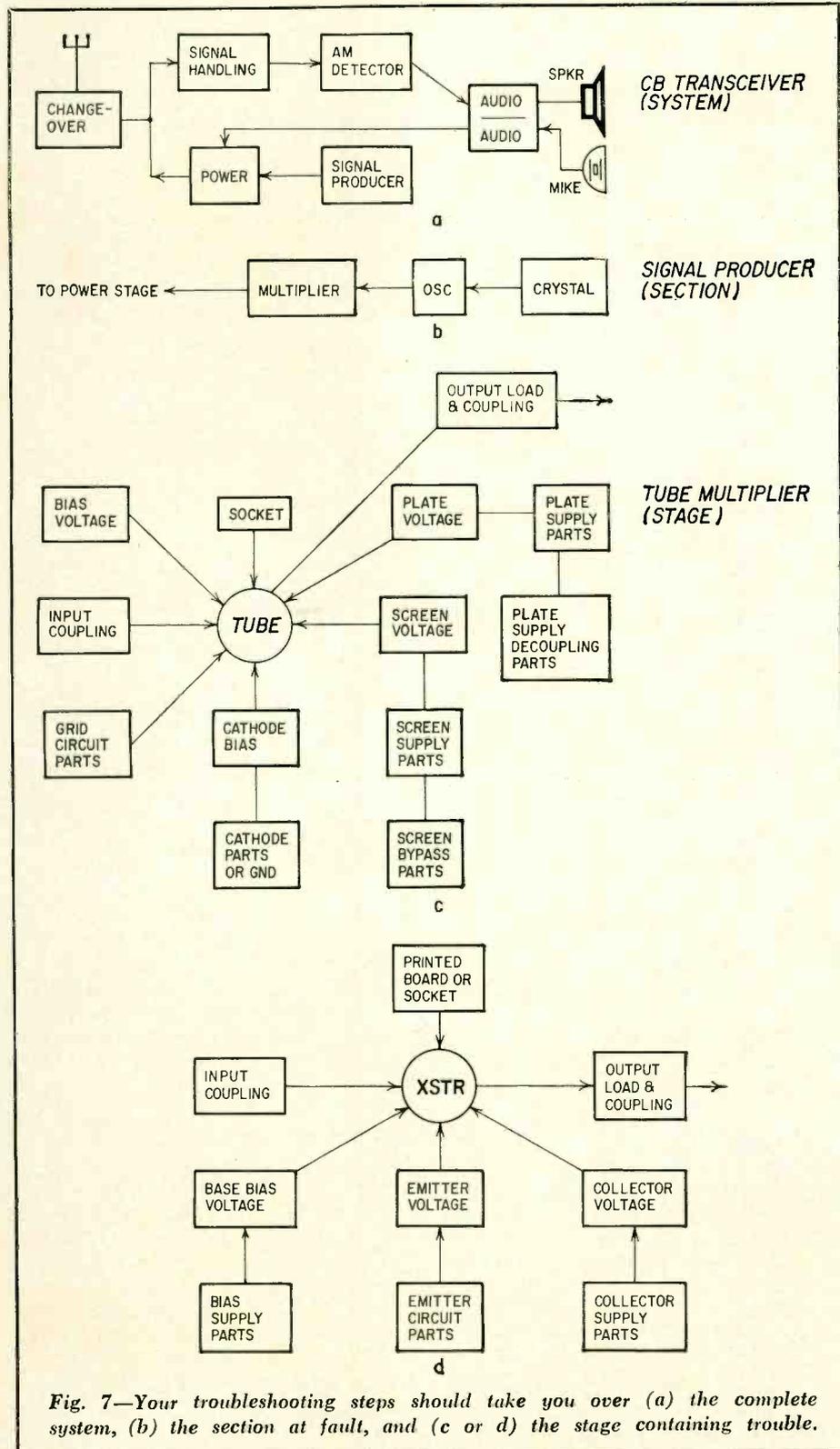Suppose the signal is being blocked at the fifth i.f. stage in the radar receiver. Fig. 5 shows, in blocks that are equivalent to the schematic, how you can break down the i.f. stage in your



next psychologically correct step of troubleshooting. The blocks represent the factors you must examine. You can apply your creative practice of asking the yes-no question about each factor.

Next in your line of psychologically correct troubleshooting procedures is a breakdown of the stage into circuits. You noticed Fig. 5-b was already broken down into circuit segments: grid, cathode, screen, plate, and socket. Fig. 6-a shows schematically both the screen and plate circuits in this stage, with the screen circuit in heavy lines. The circuits and the components have several functions; Fig. 6-b labels them.

Will the creative servicing method we've been using apply here? Most emphatically, yes. Each component has a function, sometimes more than one. Consider the transformer as a good example. You must ask: Is it feeding dc voltage to the plate of the tube? Is its tuning to the correct frequency? Is its tuning too broad? Is it coupling the i.f. signal to the next stage? Each question has a yes or no answer, and can then be followed with: why?


With that *why?*, the next step in our creative troubleshooting procedure has been reached. You either replace the faulty part or you test it further.

Let's run through this logical procedure once more—this time with a CB transceiver. Fig. 7 shows the several steps in breaking it down into psychologically manageable sections, stages, circuits, parts. It's easy. Try breaking down something you've been asked to troubleshoot. You'll find you can reduce the most complicated electronic gear to easily understood proportions.

When I began defining creativity for you, I pointed out that it means inventiveness. You can be as inventive about your servicing techniques as you like. Most useful will be a method that applies to almost every situation and kind of equipment. If you find yourself changing methods to fit various types of equipment, you haven't yet found the one most versatile.

One final point about being the top-notch troubleshooter that creative methods of servicing qualify you to be. Neither creative servicing nor psychological reasoning can fix a set for you. Mechanical and muscular movements are still needed. You have to take sections apart, sometimes, to reach the parts that are causing trouble. It often takes digging. Once you have mastered a psychologically sound approach to servicing, one that is creative enough to be applied to any kind of electronic equipment you're asked to service, the difference between you and the true expert will be in how well and how confidently you dig in.

END

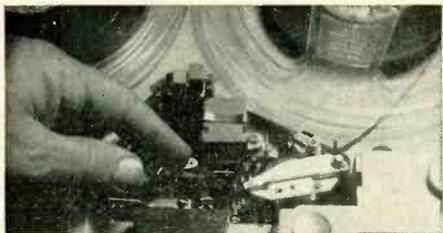


WHAT KIND OF NOISE ANNOYS A TAPE?

Squeaks, rattles and bangs make difficult listening, no matter where they are in a tape deck


By **GLEN F. STILLWELL**

WHAT A BOTHER, WHEN YOU FLIP THE play switch of your tape machine and get set to hear some good music, to hear instead a lot of sound—hum, squeals, rattles, squeaks, clicks, sighs, moans, and what-have-you—you didn't bargain for. It's enough to drive a tape listener to distraction.

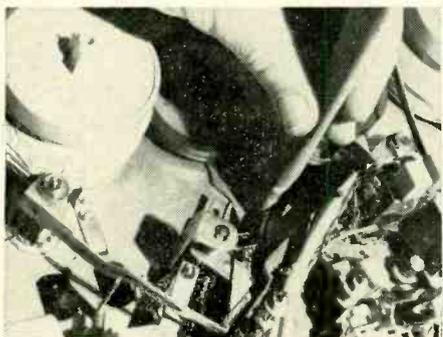Mostly these are mechanical noises that develop in tape machines, and about which there is very little in the books. You can sometimes hear them being picked up by the microphone, so that they are part of that tape no matter what



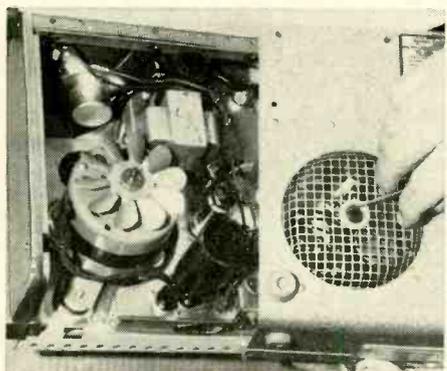You can use a sheet of sandpaper to smooth out any high spots that may develop on the flywheel of a tape deck.



Fan and fan-cage screen can be a source of rattle. Bent fan blade can scrape, or the fan shaft may extend and rub screen.

machine it might be played on and no matter how good that machine might be.

The electronic technician and the recording buff should both know what to do about these annoying defects. In more than a decade of using, testing, repairing, and experimenting with tape recorders, I've run into some real noisemakers. So I'll pass some of them along to you.

I'll skip experiences with earlier machines that are not around anymore and deal with present-day models. As a matter-of-fact, the latter, with their complicated controls and accessories, are the big offenders in the unusual-noise department. One of the first troublemakers I ever encountered was a recorder that developed a strange squeak that was finally traced to a faulty counter.


To locate the source of noise in a recorder, you must first decide in what part of the machine the noise is originating. A noise in the speaker is often difficult to locate because it may be being picked up far back and amplified. Poor shielding, faulty connections and a microphonic tube are a few of the things that can cause this kind of noise. Best start out your troubleshooting by checking all tubes. An intermittent howl I once heard in an extremely compact recorder originated in one of the tubes—easy to correct, hard to find.

Tape or deck trouble?

When the noise shows up in the speaker, you also have to suspect the playback head and the tape. If the tape is suspected of "printing through" (thin tape), the solution is obvious—new tape. However, if there is a bleeding from one track to another, realignment of the magnetic head may be the answer to the problem.

On the other hand, faulty linkages and noisy mechanical action are so often the cause of noise that little more need be said about electronic faults. At the outset, in troubleshooting mechanical-movement noises, check for vibrations by applying finger pressure to various areas of the recorder case and deck. You can determine this way whether the recorder is properly put together and all screws tightened.

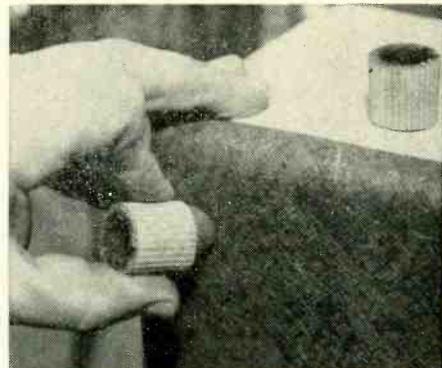Intermittent clicking or squeaking noises often develop in older recorders as a result of hardened rubber-faced



Sections of garden hose can be pushed over hardened rubber feet to absorb noise.




Tilting the machine to different positions is one way to check for unusual noises.

driving wheels. Spotty wear of this kind can be caused by the user's too-rapid tape-speed shifting. The wheel may look satisfactory, but an undetected flat spot, even though very slight, can be an awful noisemaker.

When you have to replace defective rubber-faced wheels, it is generally advisable also to renew drive pinions and belts to make sure that the noise is completely eliminated. In a Telefunken recorder that had this trouble, the pinion had been redesigned to improve quietness of operation.

An initial step in troubleshooting is to remove all protective covers and then replace the control knobs so that mechanical linkages and their movements can be observed in actual operation. A model 400 Norelco recorder developed a high-level, continuous scuffing sound that could not be found until the case was opened up and the mechanism ob-

continued on page 93

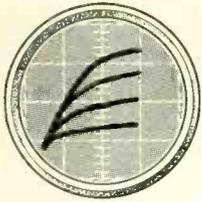

Build This Transistor Characteristic Plotter

A construction project to display curve families on your scope screen By JOHN H. FASAL*

A CURVE OF COLLECTOR CURRENT VS collector voltage with constant base current is useful when you are designing transistor circuits. Applying manufacturer's data to characteristic curves assures proper use of a transistor. You can determine the limits of thermal dissipation and transient operation as well as correct values for current transfer and saturation. In addition the rapid display of a set of curves is an excellent way to match transistor pairs.

Devices for plotting transistor characteristics are commercially available. However, they're expensive. An electro-mechanical version costs less but does most of the work of a design-engineer's model.

Operating principles

The basic schematic of an electro-mechanical plotter is shown in Fig. 1. A fluctuating dc voltage from a full-wave rectifier is applied between collector and emitter of transistor Q. This voltage is fed to the horizontal input of a scope. The voltage drop across resistor R_E in the emitter circuit is proportional to emitter current. This drop drives the vertical amplifier of the scope. The horizontal beam deflection is proportional to the instantaneous emitter-collector voltage while vertical deflection is proportional to the emitter current. This value is practically equal to the collector current. The base is biased by i_b obtained from a constant-current

source consisting of a 6-volt NiCad battery, adjustable voltage divider R_D and series resistor R_S .

This circuit causes the scope beam to trace the $V_{EC}-I_C$ characteristic of the transistor. Circuit nonlinearities may introduce some errors; these must be avoided.

Series resistor R_E is across the scope vertical input. The voltage drop across R_E —which is what the scope displays—is caused by a current which reduces emitter-collector voltage. This V_{EC} reduction has no relation to the driving voltage. So, to minimize this nonlinearity between driving voltage and emitter-collector voltage, the drop across R_E must be small compared with the driving voltage. This means the vertical scope amplifier has to be running at higher gain than the horizontal amplifier.

Bias current should be applied between base and emitter rather than base and ground, to avoid negative feedback across emitter resistance R_E . This feedback may become disturbing if current amplification in the transistor is high. This necessity of using a floating bias source makes the use of a line-powered constant-current source impractical. Since there's no common ground, efficient filtering is almost impossible; 120-Hz ripple would get into the sensitive base circuit and distort the scope traces.

For the same reason, the NiCad battery can't be trickle-charged during plotter operation. The charging device has to be disconnected at this time from both battery terminals. An OPERATE-CHARGE switch disconnects the battery from the load circuit so that battery discharge is avoided even if the line is disconnected.

A third precaution must be taken to assure constant-current base bias. Base current is determined, not only by applied dc voltage and series resistor R_S , but also by base resistance r_b . This value is determined by collector current and transistor Beta. R_S has to be high compared to r_b to stabilize base current.

It's desirable to display several curves simultaneously on the CRT, each

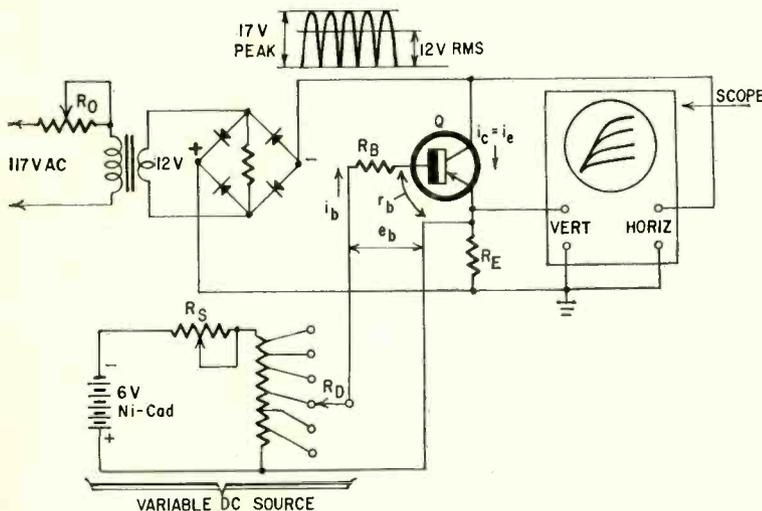


Fig. 1—Here is the basic schematic of the characteristic plotter.

Parts List	
R1—pot, 5,000 ohms, 5 watts	diode, at least 150 mA, 100 piv
R2—see text	T1—117V pri to 12V sec, at least 150 mA
R3—68K, 1/2 watt	T2—117V pri to 12V sec, at least 2 amps
R4—200 ohms, 1/2 watt, 5%	S1, S2—spst toggle switch
R5—pot, 10K, 1/2 watt	S3—spdt slide switch
R6, R7, R8, R9, R10, R11—pot, 250 ohms, 2 watts, WW, (CTS series 115, type 117 or equivalent; Federated Purchaser, Inc., 155 U.S. Highway 22, Springfield, N.J. 07081. Stock No. 117R-251A. \$1.25 each.)	S4—spdt toggle switch
R12—see text	S5—rotary switch, 4 poles, 3 circuits, nonshorting
D1, D2, D3, D4, D5—silicon	S6—pushbutton, NC
	S7-a, S7-b, S7-c, S7-d, S7-e, S7-f—reed switch (Gordos MR600 or MR606 or equivalent. MR600—Newark 60F3407, \$1.00; MR-
	606—Newark 60F3408, \$1.05.)
	J1, J2, J3, J4, J5, J6—pin jacks
	Magnets—Alnico V, 1/8 x 1/8 x 3/4 inch, (Permag S5B-559 or equivalent) and 1/4 x 1/4 x 1 1/8 inches, (Permag S5B560 or equivalent) Available from Permag Corp., 88-06 Van Wyck Expressway, Jamaica, N. Y. 11418; \$2.50 for both.
	Motor—600-rpm synchronous-clock type (Haydon or equivalent)
	Transistor sockets (3), TO-5

*Assistant chief engineer, Alarms Engineering, Walter Kidde Co., Belleville, N. J.

determined by a different bias value. Due to CRT persistence, bias voltages can be changed rapidly so that five or six curves can be traced and will appear almost at the same time. It works out that a set of curves must be traced in about $\frac{1}{60}$ sec. The time available for horizontal sweep is about $\frac{1}{600}$ sec. With rectified 60-Hz ac, a square wave is produced that can be used to sweep four times (two times up and two times down). This produces four superimposed traces. These four traces for each curve are more than sufficient to create the impression of persistence.

The sweep system


Commercial plotting instruments often use a complicated sweep generator and an electronic switching device to vary bias current. This version is simpler, using a rectified sine wave as sweep. Bias is switched by a simple rotating magnet that activates a set of reed switches.

Fig. 2 is the plotter schematic. R1 varies the amplitude of the voltage through T1, to adjust sweep length of the curve. R2, in parallel with this secondary, corrects sine-wave distortion caused by R1. The value of R2 must be determined by experiment with a scope connected to T1 secondary and a resistor in parallel with both.

The output of the rectifier bridge D1-D4 is connected to polarity-reversal switch S5, which permits changing two things at once. One is the polarity of the sweep applied between emitter and collector of the transistor; the other is the polarity of the dc biasing voltage from the 6-volt NiCad battery.

This change in polarity is necessary to switch from pnp to npn mode. The scope horizontal deflection plates are controlled by the sweep voltage, and the vertical deflection follows the voltage drop across resistor R_E (R4 in Fig. 2). This resistor is a shunt for emitter-current measurement.

Transformer T2 with independent switch S2 and fuse F2, serves two purposes: It provides energy to charge the NiCad cells if switch S3 is in the CHARGE position. If S3 is on OPERATE, T2 powers the motor driving the rotating magnet. This magnet activates the six reed switches which change the bias currents. A third set of contacts on S3 disconnects the voltage divider from the battery circuit if the plotter is not in operation. The voltage divider itself consists of an adjustable series resistor R5 (10,000 ohms) and potentiometers R6-R11 (250 ohms each). Each resistor center point is connected with the base of the transistor through the closed reed switch (S7-a-S7-f), spdt switch S4, normally closed pushbutton switch S6 and series resistor R3. Bias current can be meas-

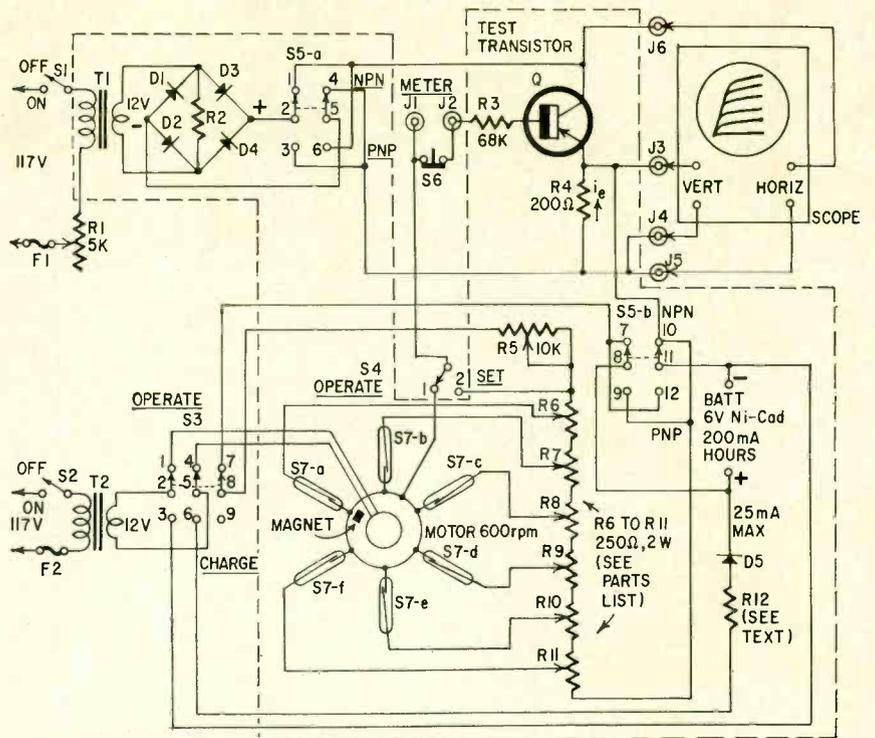

ALL PARTS WITHIN THE DASHED LINE ON THE PRINTED BOARD

Fig. 2—Complete schematic diagram for wiring the curve tracer.


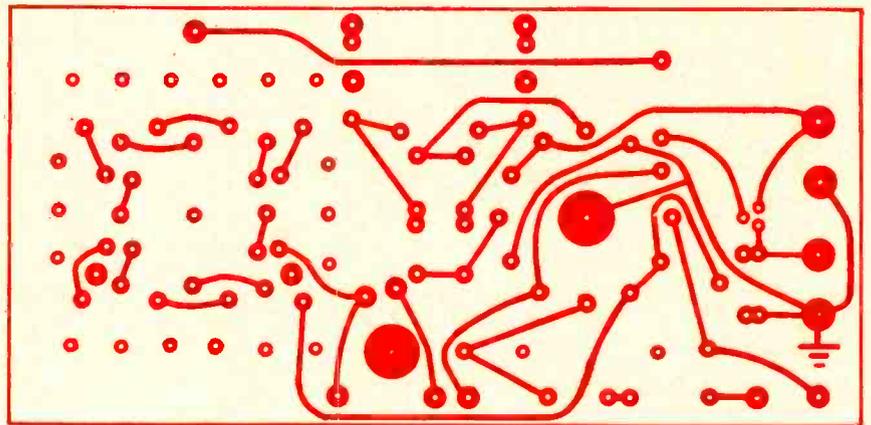


Fig. 3-a—Make a photocopy exactly twice this size and you have the pattern for laying out the PC board. b—(below)—Here's where the parts are mounted on the PC board.

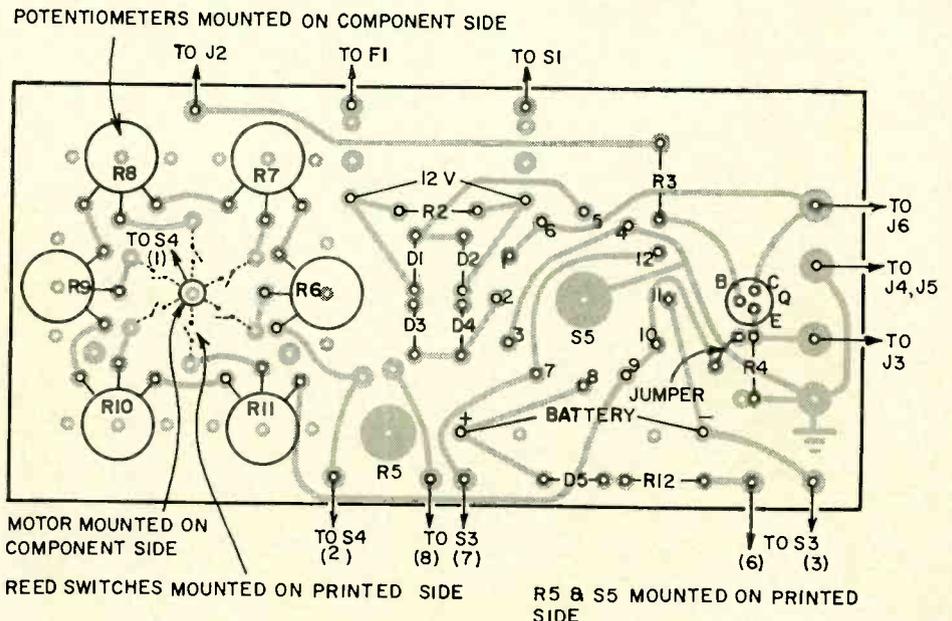

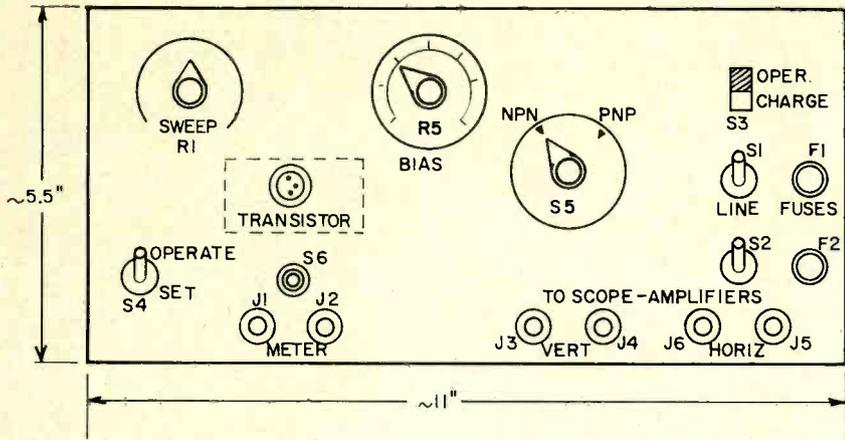


Fig. 4—Suggested front-panel layout. Note second transistor socket on panel, wired in parallel with one on board. Use plug (made from third transistor socket) and cable between sockets on panel and the printed circuit board.


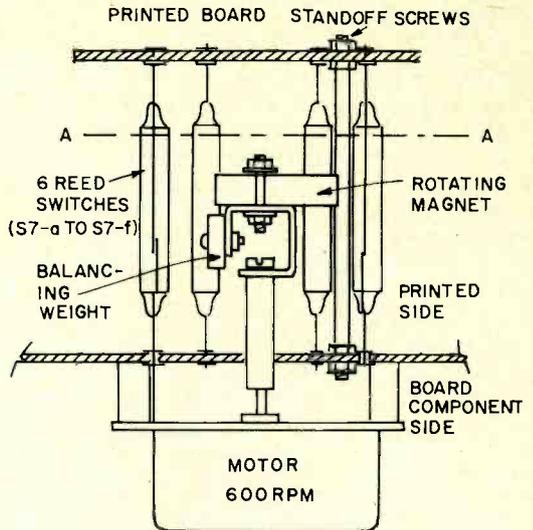


Fig. 5—(at right)—Small printed board is mounted on standoffs behind the main board. Reed switches go between boards. Motor is mounted on front of main board. T1 and T2 are on front and rear of the main board, respectively.

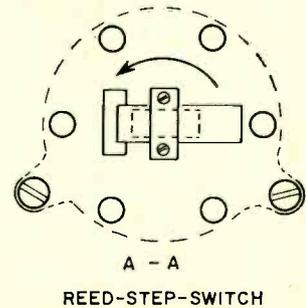

OPERATION OF STEPSWITCH S7

Fig. 6—As the motor turns, the magnet rotates, closing the reed switches one by one.

is chosen so that charging current does not exceed 25 mA (to be applied for 14 hours for full charge).
A printed circuit (Fig. 3) contains all components shown in Fig. 2 within the dotted line. The printed board is attached to the front panel with standoffs. Rotary switch S5 and pot R5 are mounted on the printed board; their

shafts are passed through the front panel, where the knobs are mounted. Front-panel layout is shown in Fig. 4, and the following parts are mounted on it: switches S1, S2, S3, S4 and S6; fuses F1 and F2; terminals J1-J6; line rheostat R1, and a transistor socket. This panel-mounted socket is connected with short leads and a plug to an identical socket on the printed board.

It's convenient to connect front-

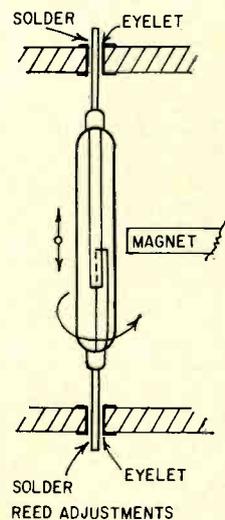


Fig. 7—Position for proper operation.

panel components with the printed-board terminals by a wiring harness.

To sweep through the reed switches in $\frac{1}{10}$ sec, the motor speed must be 600 rpm. Synchronous clock motors of this speed are readily available. The torque necessary to rotate the magnet is not high if the rotating magnet is well balanced. Of course, the torque has to be high enough to overcome the interaction between magnet and reeds. A torque of at least 100–150 inch-ounces—referring to 1 rpm—is advisable.

The motor is mounted on $\frac{1}{2}$ -inch standoffs on the component side of the board. The hole in the printed board for the motor shaft should be at least $\frac{1}{2}$ inch in diameter. The magnet is $\frac{1}{4} \times \frac{1}{4} \times \frac{1}{2}$ inch. Fig. 5 shows how to mount the magnet on a bracket attached to the motor shaft. It's necessary to attach a piece of nonmagnetic material to the lighter end of the bracket as a counterbalance to the magnet.

One end of each of the six reed switches is soldered to an eyelet on the printed board, so the switches form a circle around the motor-shaft hole. A second, smaller printed board is used for soldering the other ends of the reed switches. This smaller board is mounted on two standoffs. A $\frac{1}{4}$ -inch hole in the center of the small board allows motor-shaft adjustments. Each reed switch is about $1\frac{1}{2}$ inches long and should have a sensitivity of at least 50 ampere-turns.

It is very important that the rotating permanent magnet be adjusted to activate only one switch at a time. This means that the magnet should always release one switch before closing the next. Fig. 6 illustrates reed switch layout and magnet triggering.

Switch alignment

You'll have to position each reed switch carefully before soldering, rotating the magnet while you do so. Magnetic force must attract the longer reed and close the switch. Be sure the axis of the rotating magnet is well centered within the reed-switch circle. Fig. 7 shows how to adjust each reed switch for best triggering.

Reed-switch make-and-break intervals can be controlled another way—slip an open magnetic ring over the glass tube of the switch. After adjustment, glue the ring to the tube with a drop of cement. You should adjust the reeds as follows: Use a screwdriver to turn the motor shaft and thereby rotate the magnet. Turn each reed switch until it is triggered by the magnet each time around. Make sure all switches are activated consecutively. Finally, adjust the counterbalance for minimum vibration of the magnet during rotation.

Make preliminary adjustments before you install the printed board in the

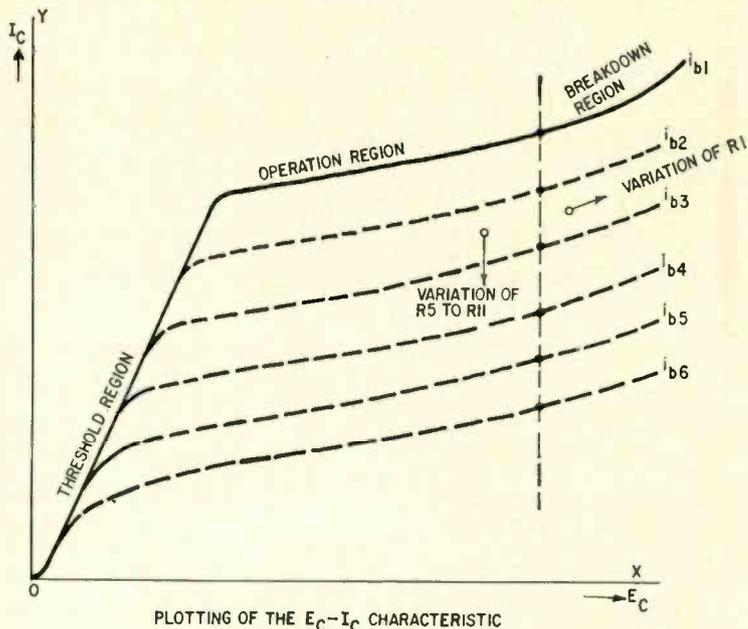


Fig. 8—Plotting of the E_c-I_c characteristic on the CRT screen.

cabinet. First, the batteries must be charged and the value of resistor R12 determined for the correct charging rate. Connect a decade resistor box in series with a milliammeter on the 100-mA range. This combination should be substituted for R12 in the circuit. Set S3 in CHARGE position and adjust the decade box for a 15–25-mA meter reading. Install for R12 a 1-watt resistor of the value found by the box test. A discharged battery will take about 14 hours to charge fully. At the end of this time its open-circuit terminal voltage should be 7 volts.

(A) Display of a single curve representing the highest bias setting:

1. Disconnect T2 by throwing S2 OFF. (The motor has to be stopped to display a single curve only.)
2. Throw S3 to OPERATE. This disconnects the charging circuit from the battery and connects the battery to the pot.
3. Turn bias pots R6 to R11 and R5 to midrange.
4. Set polarity switch S5 to the PNP or NPN position corresponding to the transistor type to be tested.
5. Insert the transistor into the socket.
6. Connect the horizontal and vertical outputs of the plotter to the scope.
7. Put switch S4 in the SET position. (This produces a fixed base bias adjustable by R5.)
8. Set the scope sweep selector to EXTERNAL position and the scope vertical and horizontal sensitivities for 1 volt/inch and 0.5 volt/inch, respectively.

9. Energize transformer T1 by throwing S1 to the ON position.
10. Slowly increase the sweep voltage by decreasing resistor R1 and correct, if necessary, the horizontal and vertical sensitivities until one characteristic curve appears sharp and well centered on the screen.

A typical pnp curve is shown in Fig. 8. If the curve appears rotated by 180° the transistor is an npn. Fig. 9 shows how the curve display changes with various scope gain settings.

If the curve doesn't appear as in Figs. 8 and 9, several things may be wrong. If the curve is a straight line only, the vertical sweep voltage may be too small. Try decreasing R1 and adjusting scope vertical gain. If the flat part of the curve is too short, try increasing horizontal gain.

If you find double-tracing or loops in the curve, there's probably noise in the bias circuit. The cure is to shorten connections and keep ac line connections away from sensitive parts of the circuit. You may have to shield some portions. Check resistor R2 for a sine waveform of the sweep.

If the steep part of the curve is too short, the vertical scope amplification may be too low, or there may be insufficient bias voltage. Try increasing vertical gain or reducing resistor R5 (or both).

If the slopes of the steep and flat parts of the curve are too large, and the breakdown region is too extended, the horizontal gain is too low or the sweep voltage is too high. Try readjusting horizontal amplifier gain and rheostat R1.

(B) Display of a family of six
continued on page 88

MAT · MOST · MOSFET · UFET · FET: UNDERSTANDING SOLID-STATE TALK

Names and abbreviations for the semiconductor family

By RUFUS P. TURNER

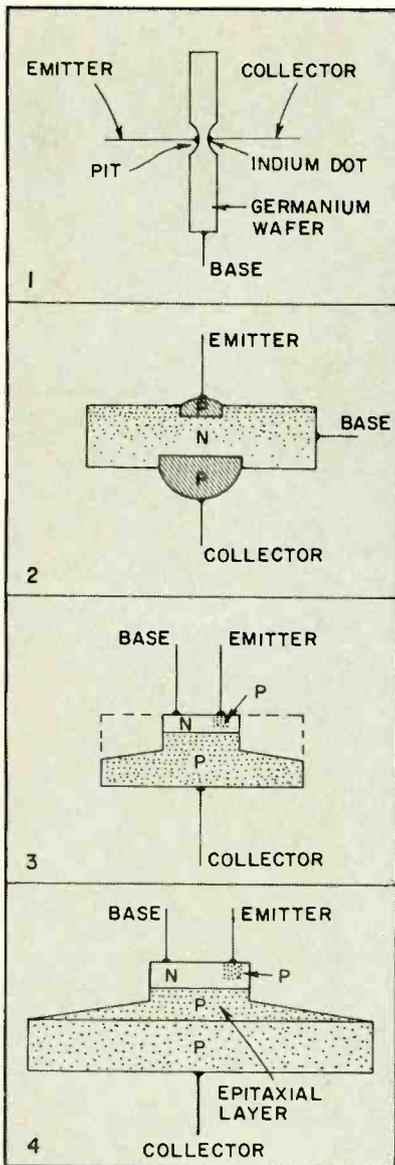


Fig. 1—First improved junction transistor was the surface-barrier type.

Fig. 2—With the drift transistor came an increase in upper-frequency limit.

Fig. 3—To overcome low voltage limit, the mesa transistor was developed.

Fig. 4—Still higher voltage-handling was built into the epitaxial mesa.

A QUICK GLANCE THROUGH TODAY'S technical literature leaves the impression that the electronics field has as many abbreviations and acronyms as Washington does. And indeed there are quite a few—some bewildering. Consider, for example, MAT, MOST, MOSFET, FET, UFET, and IGFET!

A great many of these creations are in the family of transistors and related devices. But it was not always so. In the beginning, in the midst of a vacuum-tube population explosion, there was only a transistor—a point-contact thing that resembled a germanium diode with two whiskers instead of one. If the transistor had remained as it was, manufacturers might have varied its characteristics all over the lot but just assigned type numbers like those of tubes—or perhaps even simpler ones.

But along came another kind of transistor, more rugged and stable and easier to make. This *junction* transistor was dubbed NPN and PNP according to the order in which the negative and positive layers were placed in the semiconductor sandwich. This not only introduced two three-letter symbols, but required that the first transistor also have its own distinguishing initials (PC for point-contact). The letters game was under way.

How early terms grew

Two limitations of early transistors were low input impedance and low operating frequency. The junction transistor didn't improve matters much when it first appeared. Overcoming these shortcomings has spawned many types of transistors, eventually requiring the descriptive acronyms which name them.

First, the *surface barrier transistor* raised the top frequency capability to 50 MHz and beyond. This new device had a thin base layer and smooth subminiature electrodes, formed through a revolutionary process: Tiny pits were etched in the germanium substrate by electrolysis. Fine jets of metallic (indium) salt solution, carrying direct current, were sprayed against opposite faces of the semiconductor wafer. When the wall between the pit floors was thin enough, the dc polarity was reversed, causing a tiny

dot of the metal (Fig. 1) to be plated at the bottom of each pit, forming emitter and collector. The term *surface barrier transistor* is a good mouthful; so, with typical American zest for abbreviating, we quickly cut that down to SBT. With that step, the family of acronyms grew to PC, NPN, PNP and SBT.

MAT and MADT (SBDT)

Later work showed that operation of the SBT could be improved further by alloying the tiny electrodes to some extent into the semiconductor base. That was done by heating the structure after the indium dots had been deposited deep in the SBT pits. The result was the *microalloy transistor* (MAT).

Still further work in this SBT family showed that reliability could be increased and parameters controlled more closely by diffusing a base-doping impurity into the semiconductor wafer of the MAT before depositing the electrode dots. The result: the *microalloy diffused transistor* (MADT). This type has also been called *surface barrier diffused transistor* (SBDT).

Progressively, the SBT, MAT and MADT (SBDT) offered higher top-frequency operation (important in vhf radio and high-speed computers) than that available with either the PC, NPN or PNP. However, voltage ratings were still low.

The next device to raise the high-frequency limit was the drift transistor. In this alloy-junction unit (Fig. 2), the concentration of impurity in the wafer (base) is graduated, being highest in the region of the emitter. The internal drift field created by this distribution speeds up the transistor's internal currents. Faster action inside the device increases the maximum frequency at which it will operate efficiently.

Hills and plains

To achieve higher voltage-handling ability to go with improved high-frequency operation, designers evolved a somewhat hill-shaped device which then became immensely popular. The odd appearance results from restricting the junction region to a small swelling atop a much larger semiconductor wafer. The

wafer also acts as collector. The *post-alloy-diffused transistor* (PADT) is one result of this odd conformation.

The starting point of the PADT is the collector—a wafer of P-type semiconductor large enough to handle the desired voltage. First, a thin N layer is diffused into the top of the wafer and becomes the base. Next, a small P region is diffused or alloyed into the thin base and becomes the emitter, and a small pellet of N material is alloyed into the base for contact. Finally, the unneeded part of the wafer is etched away, leaving the emitter and base in the swelling, and the collector occupying most of the remaining wafer.

The SBT, MAT, MADT and PADT all used a thin base region in a comparatively thick wafer, thus avoiding the fragility of the extremely thin wafer a PNP or NPN would require for high frequencies. But still other higher-frequency units came forth. Fig. 3, for example, shows the cross-section of another transistor in which an extremely thin base layer is deposited in a thick, therefore mechanically rugged, substrate. The starting point is a wafer of P-type semiconductor of the thickness indicated by dashed lines. First, a very thin N layer is diffused into the top of the wafer to form the base. Next, a small P region is alloyed into the N-type base to make the emitter. Finally, most of the wafer structure is etched away, leaving the base and emitter in a little plateau. The Spanish word for hill or table—*mesa*—names this transistor.

The mesa transistor may be improved (Fig. 4) by forming a thin, high-resistivity layer in the original P material before the N-type base is diffused in. This resistive layer divides the collector into two parts. Because its atoms integrate neatly into the crystalline structure of the collector, the resistive layer is termed *epitaxial*. This layer permits higher-voltage operation of the *epitaxial mesa* transistor. What it does is allow heavy doping in the main part of the collector, for low saturation voltage, without reducing the voltage-handling ability of the entire collector.

We drop from the hills to the plains when we move from the mesa transistor to one which is processed completely in a flat wafer, hence called *planar*. The starting point is a wafer of N-type silicon, the bulk of which will become the collector. First, a coat of silicon oxide is formed on the top face. Next, a circular trough is etched out of the oxide; through this "hole," a large P-type base region is diffused and spreads into the wafer (Fig. 5). Then, a concentric disk-shaped area of the oxide is etched away, and an N-type emitter region diffused into the wafer through that bared space. Finally, ring- and disk-shaped contacts

are deposited, as shown. The emitter-base and collector-base junctions would be exposed on the top face of the wafer and subject to contamination and short circuit if they were not protected by the oxide layer. The latter is said to *passivate* the planar transistor.

The advantages of the epitaxial layer in the mesa transistor are available also for the planar. Fig. 6 shows this layer added to the planar structure previously described. The result is the *planar epitaxial passivated* (PEP) transistor. (Incidentally, we also have PEP diodes.)

The field-effect family

The devices just described—SBT, MAT, MADT, PADT, mesa, epitaxial mesa, planar, PEP—improved high-frequency operation of the transistor, and the latter ones in the group also raised operating voltages. None, however, accomplished anything in the direction of increasing input impedance; low input impedance had been a limiting factor in many applications. The first device with high input impedance was the *field-effect transistor* (FET).

Fig. 7 shows the basic FET. An N-type silicon bar (the *channel*) has contacts (*source* and *drain*) attached to opposite ends, and P regions (*gate* electrodes) diffused a shallow depth into opposite faces. The source acts like the cathode of a tube, the drain like the plate, and the gate like the control grid.

A depletion region inside the channel surrounds the gate electrodes, as shown in Fig. 7-a. If negative bias voltage applied to the gate is increased, the depletion regions expand toward each other, narrowing the channel and reducing current flow from drain to source. At some high value of bias, the regions meet (Fig. 7-b), closing the channel completely and cutting off the current. Thus, the gate acts like the negative-biased grid of a triode tube. The gate, as a reverse-biased PN junction, is responsible for the FET high input impedance.

The channel may be N-type and the gates negative-biased P-type (as shown in Fig. 7). Conversely, the channel may be P-type material and the gates N-type, in which case positive bias is necessary. Separate acronyms are sometimes used to show which is which: NFET or PFET. The term *unipolar field-effect transistor* (UFET or UNIFET) also is sometimes used, to denote that the current carriers passing through the channel are of one type—holes or electrons, depending on the type of channel material used. (Conversely, conventional transistors are called *bipolar*, to indicate that their operation depends upon emission into the semiconductor of carriers of the opposite type. There is no such

continued on page 83

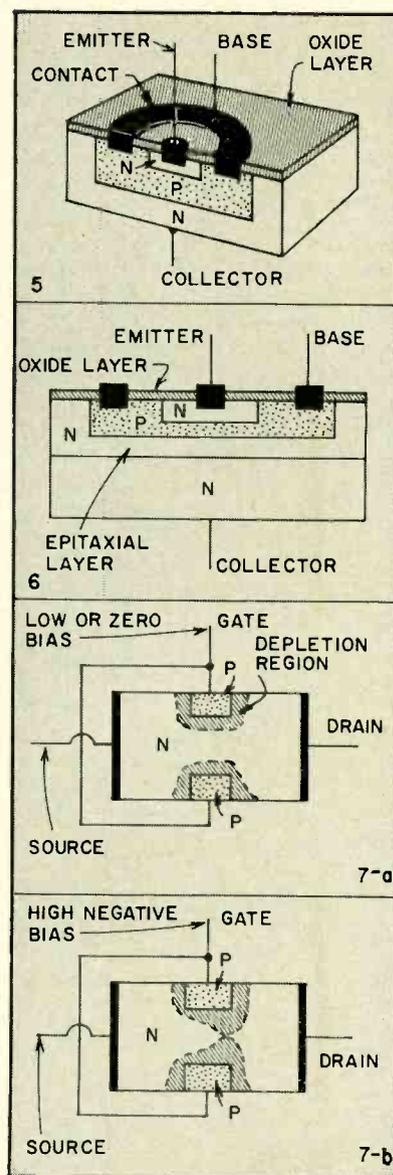


Fig. 5—Planar transistor is so-called because it's shaped like a plain.

Fig. 6—Planar epitaxial passivated transistor, a further improvement.

Fig. 7-a—Basic field-effect transistor uses gate field as control. b—With high gate field, current flow from source to drain is small.


ANTENNA REPORT

LAST FALL AN unusual antenna—the *Americus SkyProbe*—was introduced in Lewisburg, Ohio, by its developers, UniScience Laboratories. As reported in R-E's July 1967 News Briefs, the SkyProbe was demonstrated by being dropped 139 feet into a metal-cased water well and connected to a TV receiver with 300-ohm lead-in. A Dayton, Ohio, newspaper reported that the antenna produced good pictures on the TV from stations 20 to 50 miles distant.

We wrote Dr. John Eagle, head of UniScience, who replied that his antenna is "not a dipole [sic] but can receive both color and uhf beneath the earth's surface." He further claimed that classic theories of TV and radar reception are "incorrect or incomplete," and that neither antenna size nor height is a "controlling factor" in reception.

On May 7, 1967, *The New York Times* carried an advertisement by a New York City department store, offering the SkyProbe antenna for \$12.99. The ad stated: "SkyProbe revolutionary outdoor TV antenna gives clear, sharp reception from every direction. . . . It's a brand new concept that utilizes basic radar techniques to give you clear, sharp reception from any angle." Perhaps the most interesting line in the ad read: "This *solid-state* outdoor antenna is only 18" . . ." (emphasis supplied). We found these same claims in an ad in the *Cincinnati Post & Times Star* during October 1966, and in literature sent to us by UniScience.

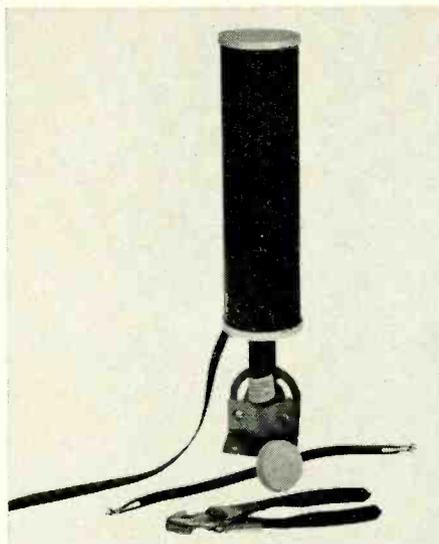A RADIO-ELECTRONICS staffer purchased a SkyProbe from the store, paying the advertised price. The name of the magazine was not mentioned. Several of us then compared the performance of the SkyProbe with existing antennas at four locations. The experiments were performed using the signals



The SkyProbe (top) R-E purchased had two lead-ins (one for TV, one for FM). "Impelator" (see text) is next to pliers.

received from New York City TV stations on channels 2, 4, 5, 7, 9, 11 and 13.

An R-E staffer took the SkyProbe to his home in Plainfield, N.J.—about 25 miles from the TV transmitters atop the Empire State Building in Manhattan. At this location, an outdoor antenna is essential for good TV reception. The SkyProbe produced only marginal results when compared with the existing outdoor antenna—a stacked dipole-reflector-director combination which had been installed some years before.

Our next test was in the Rockaway Beach section of Queens, at a site with a clear shot at the TV transmitter site 14 air miles distant. Normally the portable TV with built-in antenna used at that location picks up a good picture with a few ghosts now and then on all vhf channels. When the SkyProbe was

substituted for the built-in telescoping antenna, there was a barely noticeable improvement in picture quality on channel 5, and a slight impairment of quality on channels 7 and 11. Otherwise reception was the same.

Next the SkyProbe was placed on the window sill facing toward the transmitter site—a practice suggested in the ad. There was no noticeable change in signal quality except on channels 5 and 13, which got worse.

Similar experiments were carried out on the 16th floor of an apartment building in Lower Manhattan. Although this site is only 1.6 miles (line-of-sight) from the TV transmitters, nearby buildings cause severe ghosting when indoor antennas are used. The SkyProbe was compared with rabbit ears. There was no noticeable difference in performance between the two, whether the SkyProbe was placed atop the TV set or on the window sill—which faced away from the TV transmitter site.


Finally, we brought a portable TV to the R-E editorial offices on 14th Street, just one air mile from the Empire State Building. Again, we tried the SkyProbe and compared it with rabbit ears. Ghosts from the nearby buildings caused poor pictures on nearly all channels, and this condition was not noticeably improved by the SkyProbe—whether located inside the office or on the window sill facing toward the transmitter location.

Antenna prices


We found rabbit-ear TV antennas at discount houses, parts distributors and department stores, at prices ranging from \$1.50 to \$4.50. These were simple rabbit ears—with nothing to switch or change in the circuit. We used the same type of antenna in our experiments.

Finally, we took the SkyProbe apart to find out what was inside it. The photos show what we found. Once we had removed the plastic outer sheath, we found a spiral of aluminum wire—about No. 8—wound on a cardboard tube. Foam-type plastic filled all empty space within the sheath. Inside the cardboard tube we found another black plastic tube, and inside this we found No. 12 aluminum wire, bunched together. The spiral was connected to one side of the 300-ohm lead, while the bunched wire was connected to the other. A second piece of 300-ohm lead, marked "radio" (for FM) was found to terminate (one side of the line only) in a piece of wire mesh measuring 1 by 3 inches. This mesh seemed capacitively coupled to the spiral.

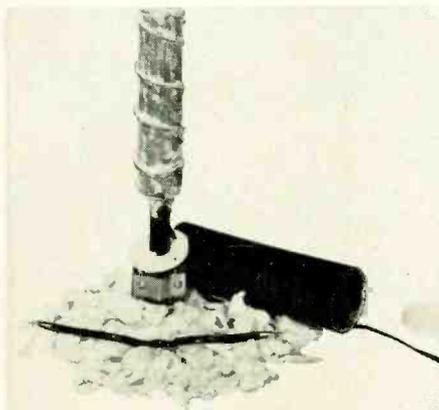Along with the SkyProbe, our purchase included what was called an "im-




Under the plastic sheath, a wire helix.

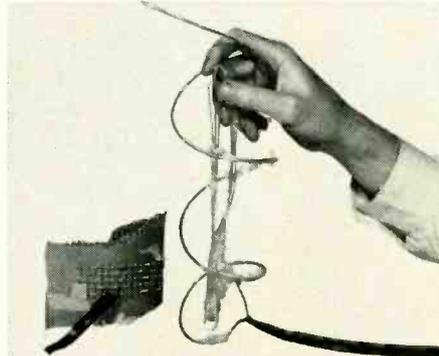

TV lead (right) connected to the helix and to bunched-up wire within. FM lead and mesh capacitive coupler are at left.

continued on page 84

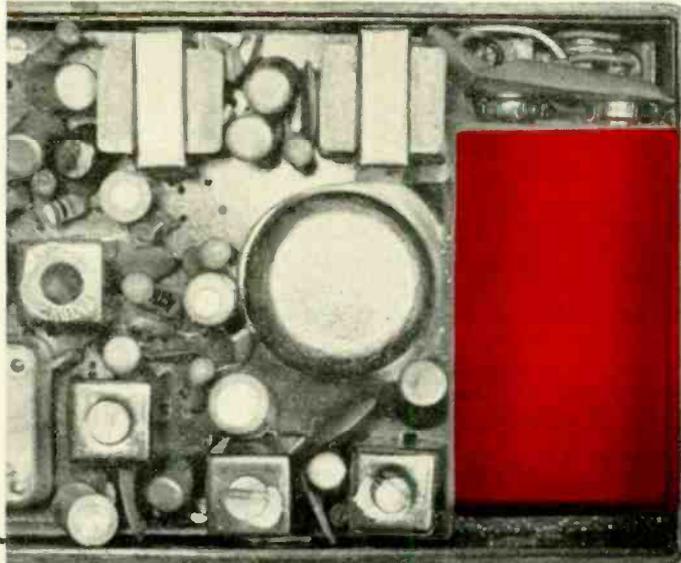

Be Brave! Take On Transistor Radios!

If you're turning away people with little squawkboxes, you're losing your share of a booming business By HOMER L. DAVIDSON

DON'T LOOK AT THAT SMALL POCKET transistor set and say, "We don't fix them." Why let *Joe's Radio Repair* down the street have the job?

Time is the important factor in repairing transistor radios. If the repair runs over half the cost of the radio, most customers will not have them fixed. I don't blame them. Do you?

Most of the trouble with that small transistor radio is the owner himself. He has left the batteries in too long, dropped the radio, or tried to fix it himself. Yes, wear and tear does enter into the picture, but only about 20% of the time.

Break transistor radio repair jobs down into sections and components and, with a little experience, you're in business and making money.

Test equipment? It isn't elaborate or costly: a harmonic generator for audio, i.f. and rf signal injection; a voltmeter to check voltage and resist-

ance; and a low-voltage supply with a milliammeter, to supply voltage to the radio and measure current drain. Basic equipment with knowledge beats elaborate equipment and no knowledge.


Before we begin, let's look at the trouble listed on the repair ticket. When you take the set, write down *everything* the customer says is wrong with the radio. Be complete. Some customers resent too many questions, but you are trying to save time to make money.

On the repair ticket it states that the radio is dead, intermittent, was dropped by the owner, had a new battery only last week, or will just pick up the local stations. You will rarely read that the owner tried to repair it himself. Yet, it happens. Remember, most of the trouble is what the owner has done.

He has let the batteries run down, or put them in backwards. Or, since the earphone was plugged in, the speaker

doesn't work. He, or his son or daughter, dropped the radio—which was supposed to have an unbreakable case. The owner tried to fix the radio himself after it was dropped and the printed circuit board was partly broken. He decided on soldering the joints (with acid-core solder) and what a mess! He thought he could improve the reception by turning those small screws, which happen to be i.f. adjustments. Of course, he didn't have a small screwdriver, so the i.f. can is torn and has to be replaced.

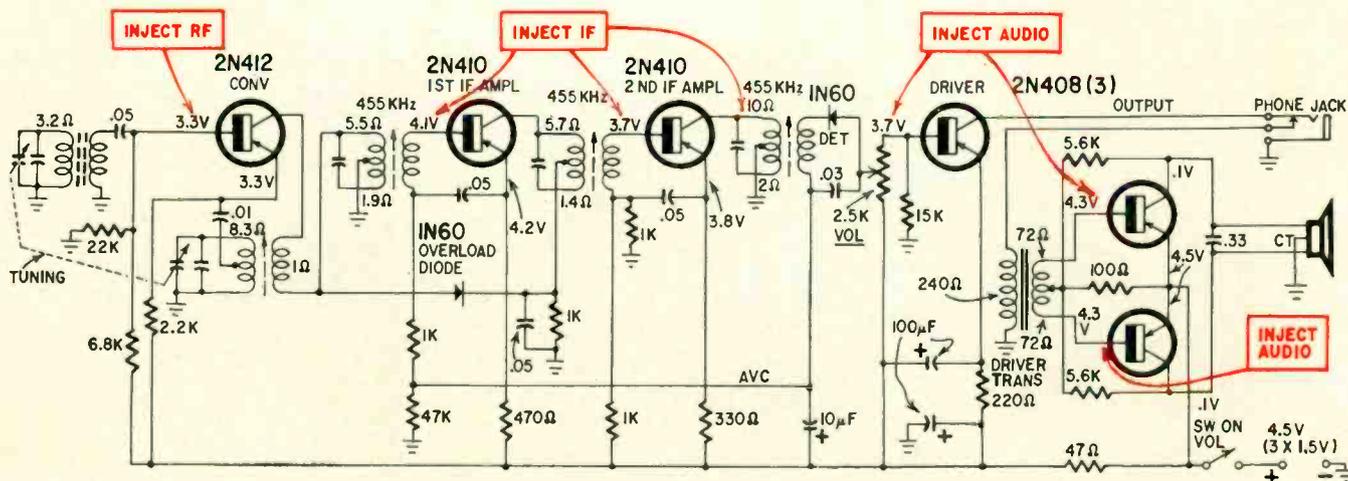Enough about the customer. Let's start finding the trouble in a dead transistor radio. The radio has a new battery in it—that was the first thing the customer thought of. A weak battery will cause low volume, no sound, squealing, or motorboating. Check for correct battery polarity. You can check batteries with a battery checker or with a voltmeter. The radio's switch should be



Circuit of a fairly typical six-transistor radio. Note center-tapped speaker and lack of output transformer. Diagram also shows where to inject what kind of signal as an aid to troubleshooting. All the necessary signals can come from a single generator.

Be Brave! Take On Transistor Radios!

Service pocket sets

on. If a 1½-volt battery drops to 1 volt, discard it.

Generally, you'll hear hiss in the speaker if the audio and some of the i.f. section is working. Run the volume control up and down. A scratchy or rushing sound indicates that at least part of the amplifying section is working. But *this* radio is dead. Clip the dc power supply in place of the batteries. Set the correct battery voltage and then switch the meter to current. If the current reads above, let's say 30 mA, you have a shorted transistor, or leaky filter capacitor. The average current drain of different sizes of radios is shown below:

5-transistor radio	5 to 11 mA
6 " "	5 to 20 mA
7 " "	10 to 25 mA
8 " "	10 to 25 mA

Testing by signal injection

If you still have no sound and the current drain is fairly normal, inject an audio signal from the harmonic generator to the center terminal of the volume control. You can also place a screwdriver there or touch it with your finger and listen for a click or hum in the speaker. Another simple method is to

hold a soldering gun near the first audio transistor. The 60-Hz field from the soldering gun will make a hum in the speaker. *By starting at the volume control, you have divided the transistor circuit in two and can go either way to find the trouble.*

Proceed to the base of each audio transistor with the audio signal and through to the speaker until you can hear the tone. Many times the earphone jack gets jammed and opens the connection to the speaker. An open speaker is unlikely, but it does happen occasionally when the voice coil is center-tapped. In this case there is low volume and distorted sound. A bad transistor or defective bias will also cause distortion, so check voltages. Speaker trouble is generally caused by rattling and dented cones.


Let's assume you have audio at the speaker when the signal is injected at the volume control. Proceed by inserting an i.f. signal at the base of each i.f. transistor, working back toward the mixer, until you hear the tone. A defective i.f. transformer will generally show up as a loss of gain, or no signal at all, or very broad tuning during alignment.

If the i.f.'s seem okay, inject an rf signal at the base of the converter transistor, then at the antenna. The small antennas give a lot of trouble. They are usually mounted on a separate fiber board and then soldered to the circuit board. The connections often break, making reception erratic.

The alignment of most transistor radios can be touched up with the harmonic generator. Inject an i.f. signal into the base of the converter stage and adjust each i.f. transformer for loudest tone. Set the harmonic generator for as low a reading as possible, with the tuning capacitor plates full open. Tune in a station around 1,000 kHz and adjust the oscillator section trimmer while you rock the variable capacitor shaft backward and forward through the 1,000 kHz station. Inject an rf harmonic signal into the antenna, set the tuning capacitor to 1,600 kHz on the dial and peak the rf trimmer. Check stations around the high and low ends of the band. Readjust the oscillator and rf trimmers as needed to get correct dial readings and good sensitivity. (I know of a technician who uses his fluorescent bench light to align radios. He simply



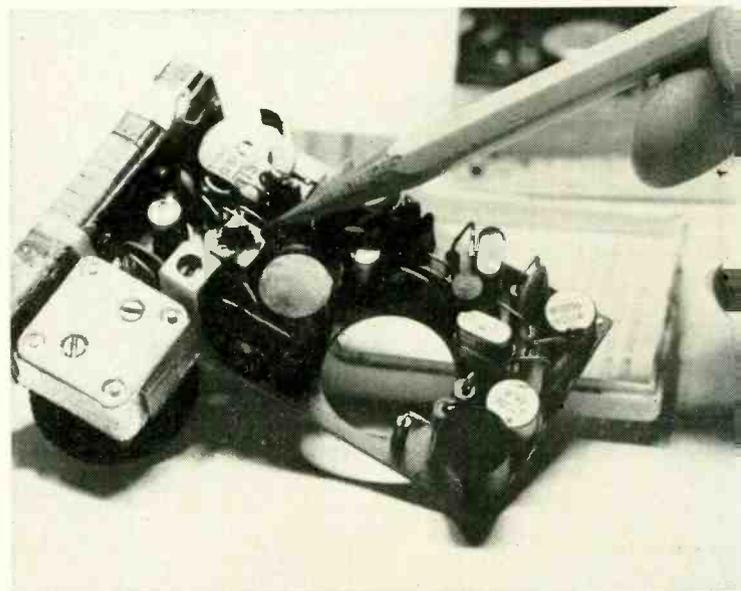Instruments for transistor-radio fixing: A broadband signal generator, a volt-ohm-milliammeter and a battery eliminator.



The customer admitted trying to improve reception by tightening those little screws. But he didn't use the right tool!

at a profit with a few well-known troubleshooting techniques.

holds the radio close to the light and uses it as a noise generator.)

Intermittents

When the repair ticket says the radio is intermittent, you can safely bet that the board is broken or parts have come loose. One customer said, "I just press on the case and my radio quits." Dropping the radio is one of the greatest hazards and, generally, something gives. A broken board is quite easy to see. The best thing to do is to order a new board and replace all the components, but what customer is going to wait a month for the board when he wants the radio fixed today? Excuse me—I should have said *right now!*

A PC board isn't too hard to fix. On direct lines, run a heavy piece of bare copper wire across the break and solder it in place. Do this in a couple of places to make the board rigid. I still use hookup wire to solder around the other breaks. The solder supports often break off where they fasten to the plastic case. Solder eyelets or larger washers in place to make a solid mount.

Larger components, such as output and interstage transformers, the tuning

capacitor and the volume control, can become loosened when the set is dropped. Pressing on the board shows the set is intermittent. This is especially true of the variable capacitor, where connections stick through the board and are soldered to the printed circuit. Hit these joints with a good hot iron, because the contact may be had above the soldered connection, where you cannot see it.


A customer brought in a small radio that used up a battery in 4 to 5 days. For 2 weeks it would play perfectly. Then the same thing would happen. Upon checking the radio, I found that when the radio was turned off, I could still hear a small sound from the speaker on local stations. A small wire from the switch was being pressed against a sharp junction on the board, shorting across the on-off switch. When the contact was made, the radio was on all the time, but the volume was down.

When you replace a transistor or i.f. transformer, heat the connection and pull the solder downward. This will leave only a small portion soldered, or none. Keep working the component back and forth when doing this. You can clean


the holes with a toothpick or sharp pencil. (Pick up a couple extra toothpicks during your coffee break.) I always like to let the radio play when I solder any connections. That way I know that I've made a good joint. Also, if I get careless and solder runs onto the next lug, I know it at once. Have the milliammeter in series with the battery when you do any soldering with the radio on. A short will show as heavy current drain.

Many technicians stay away from printed circuits of any kind. Become one who doesn't, for they are here to stay. Learn all you can about printed circuits and get experience in repairing them. You can make money at it. Trouble is my bread and butter. In the radio and TV business, every minute of the day you are taking care of your customer's electronic troubles.

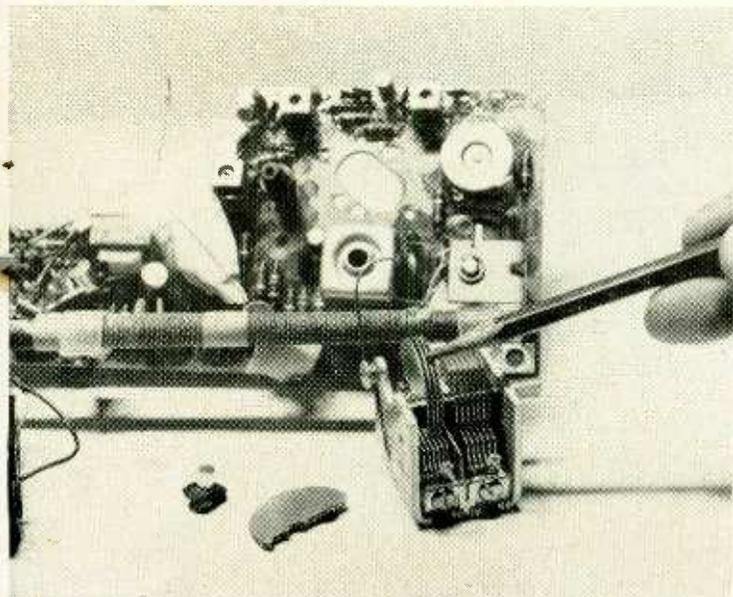Why learn transistor radio servicing? One of our customers—Mr. Jones—has eight of them in his household. We repair them and make money doing it. Oh, yes . . . I almost forgot: Mr. Jones also has two automobiles with a radio in each, two TV sets, one small table radio, and I just sold him a big stereo set last Christmas. END




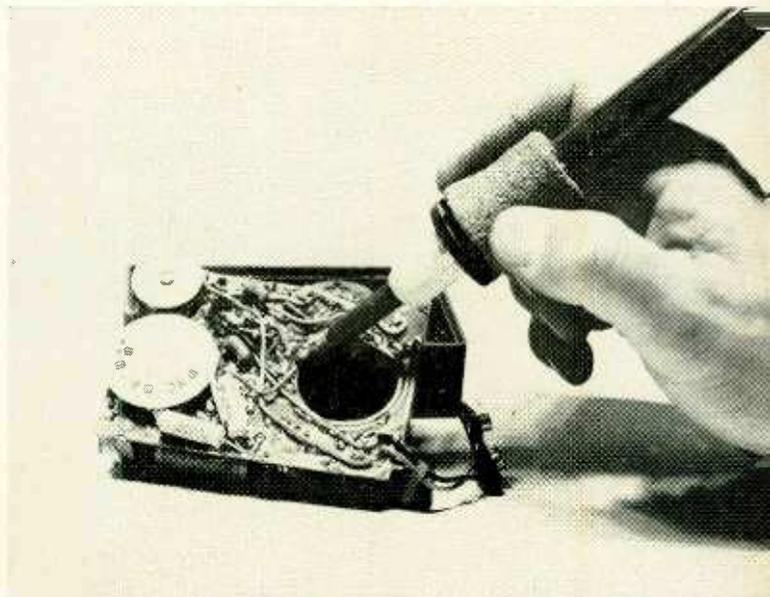This receiver was dropped, and batteries fell against the tuning capacitor, amputating three plates. Cure—a new capacitor.



Another case of a drop breaking the circuit board; opens were bridged with insulated wire to correct the trouble.

There's more than one road to success.

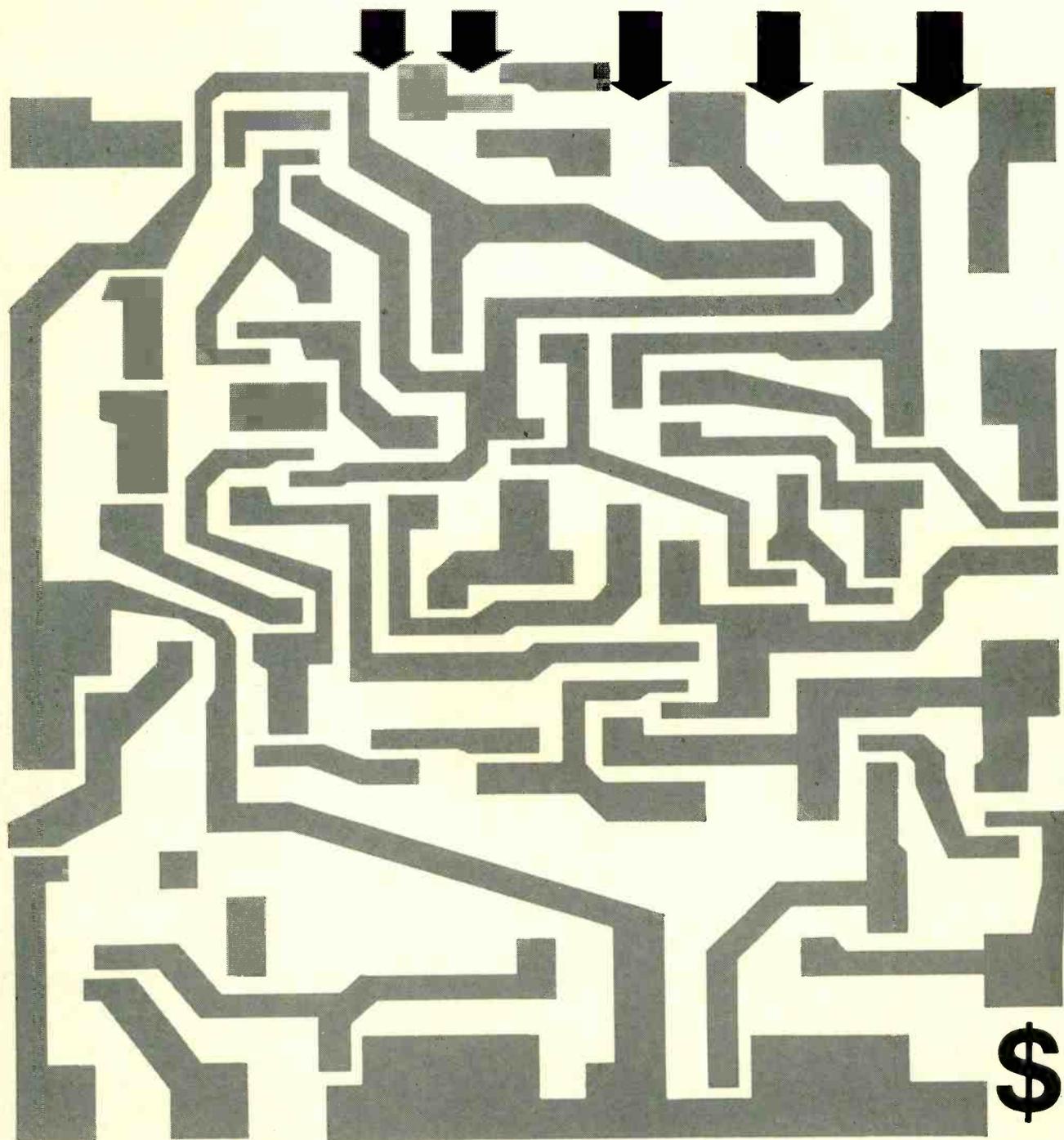

An integrated circuit enlarged several thousand times

RCA Institutes can help find the one best for you!

Are you trying to find your way through a maze of career possibilities? Find out how RCA Institutes can start you on your way toward a well paying job in electronics. Send the attached card today!

Learn electronics at home faster, easier, almost automatically— with RCA AUTOTEXT

Are you just a beginner with an interest in the exciting field of electronics? Or, are you already earning a living in electronics and want to brush-up or expand your knowledge in a more rewarding field of electronics? In either case, AUTOTEXT, RCA Institutes' own method of Home Training will help you learn electronics more quickly and with less effort, even if you've had trouble with conventional learning methods in the past.

THOUSANDS OF WELL PAID JOBS ARE OPEN NOW TO MEN SKILLED IN ELECTRONICS!

Thousands of well paid jobs in electronics go unfilled every year because not enough men have taken the opportunity to train themselves for these openings. RCA Institutes has done something positive to help men with an aptitude and interest in electronics to qualify for these jobs.

HOME STUDY CAN TRAIN YOU FOR REWARDING CAREER OPPORTUNITIES

To help fill the "manpower gap" in the electronics field, RCA Institutes has developed a broad scope of Home Training courses, all designed to lead to a well paying career in electronics in the least possible time. You also have the opportunity to enroll in an RCA "Career Program" exclusively created to train you quickly for the job you want! Each "Career Program" starts with the amazing AUTOTEXT Programmed Instruction Method. And, all along the way, your program is supervised by RCA Institutes experts who become personally involved in your training and help you over any "rough spots" that may develop.

VARIETY OF KITS ARE YOURS TO KEEP

To give practical application to your studies, a variety of valuable RCA Institutes engineered kits are included in your program. Each kit is complete in itself, and yours to keep at no extra cost. You get the new Programmed Electronics Breadboard for limitless experiments, including building a work-

ing signal generator, multimeter, and a fully transistorized superheterodyne AM receiver.

ONLY FROM RCA INSTITUTES— TRANSISTORIZED TV KIT— VALUABLE OSCILLOSCOPE

All students receive a valuable oscilloscope. Those enrolled in the Television program receive the all-new transistorized TV Kit. Both at no extra cost and only from RCA Institutes.

CHOOSE THE "CAREER PROGRAM" THAT APPEALS MOST TO YOU

Start today on the electronics career of your choice. Pick the one that suits you best and mark it off on the attached card.

- Television Servicing
- Telecommunications
- FCC License Preparation
- Automation Electronics
- Automatic Controls
- Digital Techniques
- Industrial Electronics
- Nuclear Instrumentation
- Solid State Electronics
- Electronics Drafting

ADVANCED TRAINING

For those already working in electronics, RCA Institutes offers advanced courses. You can start on a higher level without wasting time on work you already know.

UNIQUE TUITION PLAN

With RCA Institutes Training, you progress at your own pace. You only pay for lessons as you order them. You don't sign a long-term contract. There's

no large down-payment to lose if you decide not to continue. You're never badgered for monthly payments. Even if you decide to interrupt your training at any time, you don't pay a single cent more.

CLASSROOM TRAINING ALSO AVAILABLE

If you prefer, you can attend classes at RCA Institutes Resident School, one of the largest of its kind in New York City. Coeducational classroom and laboratory training, day and evening sessions, start four times a year. Simply check "Classroom Training" on the attached card for full information.

FREE PLACEMENT SERVICE, TOO

In recent years, 9 out of 10 Resident School students who used the Free Placement Service have been placed before or shortly after graduation. This Service is available to Home Study students.

**SEND ATTACHED POSTAGE PAID
CARD TODAY. FREE DESCRIPTIVE
BOOK YOURS WITHOUT OBLIGATION.
NO SALESMAN WILL CALL.**

All RCA Institutes courses and programs are approved for veterans under the New G.I. Bill.

RCA INSTITUTES, INC. Dept. ZRE.97
350 West 4th Street
New York, N.Y. 10014



The Most Trusted Name In Electronics



IT CAN'T BE ALL BAD

By PHIL PRINDLE

AS SOON AS I UNLOCKED THE DOOR OF MY SHOP I knew it was going to be one of those days. The phone was ringing already!

"Good morning, Ernie's TV Repair," I greeted the caller as cheerfully as possible. Early morning isn't my best time of day and I hadn't had my second cup of coffee. It was Mrs. Stumpp. She lives about five miles out of town, has six kids that are really terrors and never pays her previous bill until her set breaks down again.

Glumly I assured her that I'd be out as soon as Charlie showed up to watch the shop. Charlie's my part-time helper, a crackerjack technician but decidedly not the punctual type.

While waiting for Charlie to make his appearance I checked my answering service to see what other house calls were in store.

Mrs. Whitaker was one. I'd told her six months ago the picture tube was going. No doubt by this time it was gone for good. Better take one along just in case.

One call was from the school. They wanted me there before noon because six teachers were planning to have their classes watch Mr. Dan the Mathemagics Man at 1:30. I hoped I'd be magician enough to have the set fixed by then!

And finally a call from a Miss Marnar. Hmmmm, might be interesting. Bachelor that I

am, I'm always willing to check out new material providing it's over twenty-one and under forty! I decided to leave that call for last—just in case it was a complicated job.

Drat that Charlie—where the heck was he this morning?

I had just decided to get some bench work done while I waited for Charlie to come in, when a customer walked in with a portable phonograph. "Can you fix this?" she asked. "The turntable goes around but there's no sound!"

"We'll try," I smiled, "We'll try." Then my smile faded. "Where did you get this?"

"Oh, I bought it down at the discount store a couple of years ago. They had a big sale."

"Ummmm," I said as I searched for a brand name. Just as I thought. One of those import jobs where it's impossible to find a circuit diagram and if you're lucky enough to find the trouble it's almost certain you can't get a replacement part.

"We'll look it over," I told the customer after explaining the possible difficulties. "We'll call you and let you know what we find."

I'll leave that one for Charlie, I decided, if he ever gets here.

I turned back to the workbench to recheck a color set that had been giving us trouble for a couple of days. It had trouble in the color-sync stage. We'd checked the sync-phase detector and the reference oscillator, and had tried to find the trouble

with a scope, but so far no luck. Just as I was really getting somewhere a client came in with a bunch of tubes to check—one of these do-it-yourselfers who would no doubt end up by bringing the set in anyway. Especially since all the tubes checked out okay.

Fortunately, Charlie finally showed up. He'd had a flat on the way. I told him to keep working on the color set and to check out the phonograph.

Storm clouds were gathering as I hopped into my truck. Looks like rain, I thought, reminding myself I had better get a new windshield wiper blade—no sense driving the truck into a ditch to go with the other troubles I'd had today.

I bee-lined for the school, which seemed to be the most urgent call. Mrs. Stumpp and her six kids would just have to go without TV for another hour.

At the school, a secretary led me to the set where I spent forty-five minutes checking it and finding nothing wrong. Then the principal appeared.

"We had some vandalism here over the weekend," he said. "Now that I think of it, the antenna looks bent."

Fifteen minutes later we had located the custodian, who provided a ladder. Sure enough, some mischievous student with a grudge against the school had not only bent the antenna but had disconnected the lead-in. I had service restored in five minutes—in time, I hoped, for the kids to see Mr. Mathemagician.

Grabbing a quick sandwich at the lunch counter on the edge of town, I drove out to Mrs. Stumpp's house. Sure enough there sat four of her six children staring at the dark screen. Unfortunately, one of her school-age boys was home with a cold. He opened the door and greeted me with, "What took ya so long? I missed all the cartoons!"

I ignored his comment and attacked the dilapidated set. The back hung loosely by one screw. It was necessary to remove a toy airplane, a handful of marbles and several wads of stale bubblegum before I could get at the tubes. All the while, the younger children were pummeling each other and shrieking loudly. School-age boy was fingering something that looked suspiciously like a bean shooter. As I leaned over the set, "Ping!" He had zeroed in right on the back of my neck. I was muttering under my breath as I completed my investigation. The two speaker wires dangled loosely. No doubt one of the kids had pulled them loose while reaching in for the toys he had hidden there.

"That will do it, Mrs. Stumpp," I said when the wires had been secured. "Umm, about that last bill I sent. . . ."

"Guess I do owe you sumthin'," she muttered, producing two grimy one-dollar bills from her apron pocket. "Just send me another bill for today's job will ya?"

It suddenly struck me that at this rate I wasn't going to make any money today.


"But Mrs. Stumpp," I protested, "the last bill was for ten dollars and this house call will be seven-fifty."

"Two's all I got. And look how long it took ya to get here. I oughta get a reduced price!"

"Yeah, I missed all my cartoons!" interrupted Junior.

I had to bite my tongue to keep from telling her it was worth double time to drive out to her place and put up with her offspring. I forced a smile. "Well, thank you, Mrs. Stumpp. Just have your children keep their toys somewhere else and maybe the set will keep working for a while."

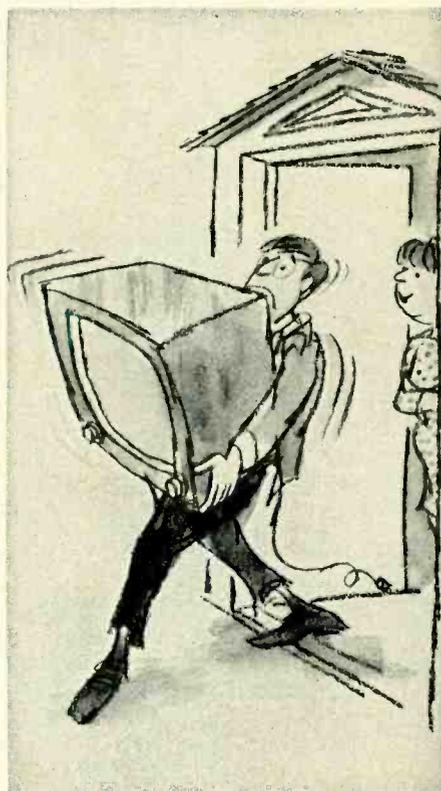Breathing a sigh of relief to be finished with that call, I dashed back to town to check on Mrs. Whitaker's set. The picture tube, as I had suspected, was quite, quite dead.



I had to haul off her old TV for nothing.

"I can have this fixed up good as new in no time," I told her happily. No problems here, I thought.

"How much is it going to cost?" she demanded. I quoted the price of the tube and installation charge.

"Will that be one of those modern up-to-date picture tubes?"

"Yes." I was a little puzzled.

"Then that'll fix it so I can get color on it!"

I explained as patiently as possible that changing the picture tube would not make a black-and-white set receive color. Mrs. Whitaker seemed to be giving the matter great thought.

"Well, in that case," she said finally, "if you'll haul off this old set for me, I'll just go downtown and get me a new color TV!"

Oh, no, I grumbled inwardly, now she wants



When I came to, I saw a lovely face near mine. "Oh you poor man," she squealed. "You're bleeding!"

me to play junk man. "Why don't you call the Goodwill or something?" I protested feebly.

"Why bother? You're right here. And I'll be sure to call you when I need someone to fix the color set."

What doesn't a guy have to do these days to keep a satisfied customer?!

Reluctantly I lugged the set out to the truck. By this time, the sky was really dark and a few large drops of rain were splattering my windshield, so I stopped at a service station for a new wiper blade. I spotted a phone and called Charlie to see if any more calls had come in. There weren't any, but he reported no progress on the color set. Instead, he'd discovered trouble in the scope and was busy trying to fix that! I told him to close up at six if I wasn't back, and headed for my last call. What a day this had been so far!

I had some difficulty finding the address Miss Marner had given. I finally located it—a cute rose-covered cottage in back of a larger house. Noting there was no antenna on the smaller house I knocked on the door.

"M-Miss Marner," I stammered as a vision of loveliness opened the door.

"Yes, come in," she invited in a soft, husky voice.

"I—I'm the TV man," I quavered, for Miss Marner was truly a dream after the nightmarish day I'd had. 36-24-36 if my eyes didn't deceive me.

"Yes, I know," she smiled. "It says 'Ernie's TV' on your shirt. Now," she said, pointing to a large box on the floor, "I'd like you to put up my antenna. I just moved here from an apartment and

I can't get any reception with rabbit ears."

Suppressing a shudder at the thought of the nasty weather building up outside, I replied, "Yes, Miss" and proceeded to unwrap the antenna.

"I'll make some coffee," she suggested. "You'll be cold when you come down."

A real doll, I thought. No one else had offered me anything all day.

Since there was no ladder in sight I climbed cautiously up the rose trellis. The rain was still just a sprinkle, but the rolling of thunder made me work as quickly as possible. I was just tightening the last guy wire when *Crrrack!* a flash of lightning hit the antenna.

I regained consciousness with Miss Marner's lovely face just inches above mine. I was lying on the wet grass but she was thoughtfully holding an umbrella over us.

"You poor, poor man," she cooed as she prodded me gently to see if I had any broken bones. I let her poke while I gingerly wriggled my arms and legs and decided I was okay.

"Ooh, you're bleeding!" she squealed. I reached up to my forehead and felt a small gash.

"It's nothing," I said bravely. "But it is cold out here." Miss Marner was shivering and so was I.

"You just come right in and I'll get you some nice, hot coffee and a Band-Aid for your head."

For service like this I was happy to install antennas in the rain and even to shed a few drops of blood! It's been a heck of a day, I thought as Miss Marner assisted me into her cozy cottage. It's a good thing I called Charlie. I had a feeling I wouldn't get back to the shop by six! END

Updating the Self-Holding Relay

Semiconductors are used in the modern version of an old, old circuit

By RONALD L. IVES

A few years before World War I, a number of experimenters, mostly in the telephone industry, discovered how to make a relay hold itself on. Connected as in Fig. 1, if it were turned on by a short pulse, it would remain on indefinitely. Closing the pushbutton momentarily energizes the relay coil. The armature then pulls down, connecting the main supply to the coil; ergo, the relay remains closed indefinitely. You can open the contacts only by opening the supply, by a switch, relay or any other means.

The turn-on pulse can be obtained from a capacitor discharge or even from the flyback of an inductance. In a few sophisticated devices, shutoff is obtained by means of a second winding on the core. This winding is so polarized that, when energized, the magnetic field of the first coil is cancelled.

The classic circuit of Fig. 1 works on either ac or dc; more sophisticated circuits work on dc only.

Transistorized shutoff

Shortly after World War II, transistors became available, and the shutoff function of the self-holding relay could be greatly simplified. The basic circuit for transistorized shutoff is shown in Fig. 2, with constants for a specific example. Turn-off function here is performed by the transistor. Under normal conditions, its base is tied to system negative, and it is conducting. When an adequate positive bias is applied to the base, the transistor cuts off, opening the circuit through the relay coil. Note that, so long as there is a common negative, the turn-on, supply and turn-off voltages (all positive) need not come from the same source.

Turn-on and turn-off voltages can be pulses supplied through capacitors. This is usually inconvenient, however, as the pulses must have an amplitude

about equal to the relay voltage. Furthermore, pulse duration must be at least as long as the response time of the relay (about 1/25 second in most instances).

Operating limits are quite flexible with the circuit of Fig. 2. Relay voltage can be anything from 5 to 25, and relay current anything up to 1.5 amps. Ranges can be extended by the use of higher-voltage or higher-current transistors.

Although the 2N307 audio transistor is quite rugged, resisting thermal and other abuse, you won't get dependable operation for long unless the transistor is equipped with an adequate heat sink. With negative-ground systems, this requirement can be met by bolting the transistor to a metal chassis. When the transistor is not at chassis potential, a heat sink consisting of a sheet of copper, 3 x 3 x 1/16 inch, is usually adequate. Allow plenty of room around it for convectional cooling.

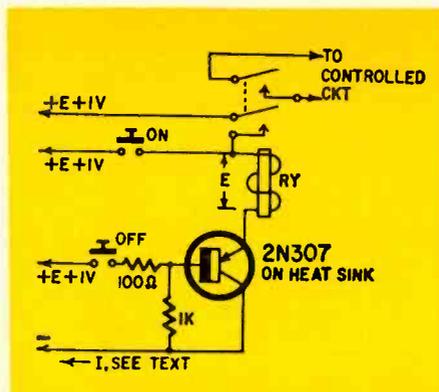


Fig. 2—Transistor substitutes for a normally closed switch. A positive pulse applied to the base opens it.

SCR turn-on

Within the last year or so, the silicon controlled rectifier, which is practically a solid-state thyatron, has become available at reasonable prices. The SCR is a rectifier that doesn't conduct until triggered; once triggered, it conducts until it's shut off. The circuit of a relay arranged for SCR turn-on and transistor shutoff is shown in Fig. 3. It operates as follows: When the power supply is turned on, the SCR, which has not been triggered, does not conduct, and the relay is not actuated. The transistor, whose base is tied to system minus, is capable of conducting whenever energized.

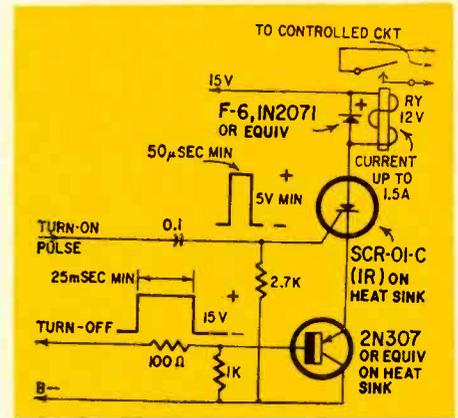


Fig. 3—Newest version uses SCR turn-on.

When the SCR is triggered, by a pulse of approximately +5 volts lasting about 50 μsec, the entire circuit conducts and the relay operates. As the SCR, once triggered, remains conducting until it is turned off by a supply interruption, the relay is held on.

The controlled circuit is turned off by putting a positive bias on the base of the transistor. This cuts off the transistor, interrupting the supply, so that the SCR stops conducting and the relay releases. The shutoff pulse must have sufficient amplitude to cut off the transistor completely. In the circuit of Fig. 3, 15 volts is required. If a lesser value is used, the relay will release momentarily (the SCR is still conducting), and then be actuated again at the end of the pulse.

Turn-on and turn-off potential can be obtained from the main supply, or from any other convenient source, so long as all sources have a common negative.

Performance and service life

The circuits outlined here are excellent performers, needing a minimum of maintenance. As far as can be determined, the service life of the circuit depends chiefly on the life of the relay, provided the solid-state devices are not overvolted and have adequate heat sinks.

The oldest direct-relay device I know of (Fig. 1) recently quit after 23 years of service. (The relay wore out.) One of the first relay-transistor circuits I built (Fig. 2) is still working perfectly after 5½ years of commercial service. It's reasonable to assume that a silicon controlled rectifier, if operated within its ratings and not mistreated, should last indefinitely.

END


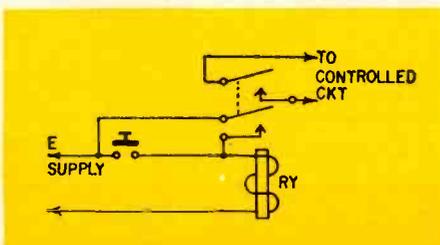


Fig. 1—The classical self-holding relay.

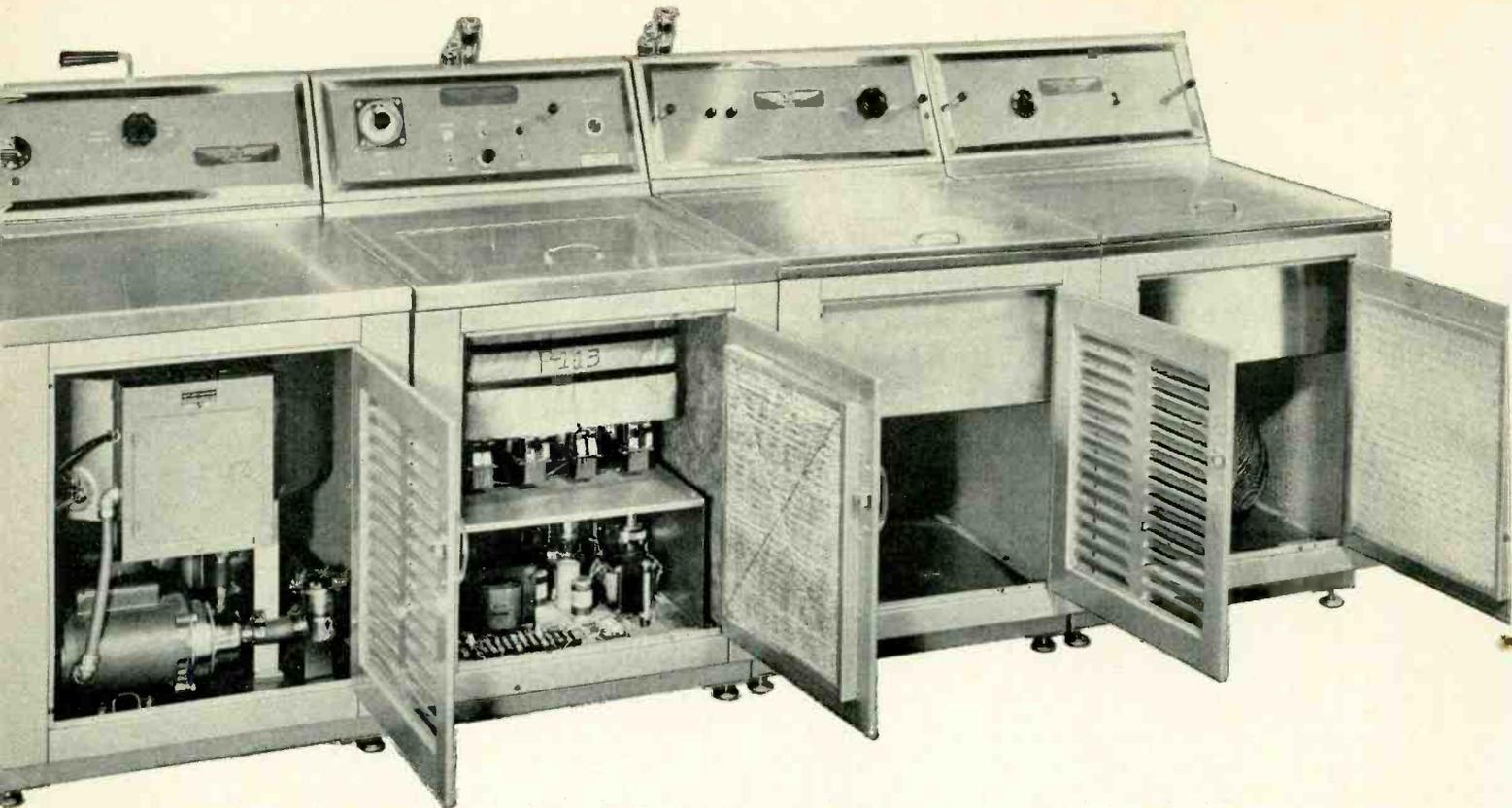

Servicing Ultrasonic Cleaners

A useful sideline for electronics technicians By R. C. ROETGER

THE ELECTRONIC SERVICE TECHNICIAN who wishes to expand his activities will find servicing ultrasonic cleaners a profitable field which does not require vast learning of new techniques. Because many plants do not have sufficient electronic equipment to warrant a full-time electronics expert, they are frequently faced with the necessity of calling on a "factory man." This involves, not only the high charge for such service, but also often costly production delays. These factors make a strong case for having a technician available locally.

If a service technician understands audio-oscillator principles and is well versed in audio-amplifier maintenance, he has 90% of the required know-how already. True, the frequencies involved in ultrasonics are above the audible range but basic audio principles still apply. It only remains for the technician to become acquainted with the general configuration of commercial cleaners so that he will have some idea of where to look for what. Such information is important mostly when no service manual is available. The troubleshooting hints at the end of this article are based on practical experience and should help you if you are a newcomer, until you develop your own methods.

The first time a technician opens a

cleaner he may be somewhat disconcerted by the conglomeration of pipes, valves, heaters and so forth. There is no need to worry, however, for these are plumbing components, and have nothing to do with generating ultrasonic power.

All ultrasonic cleaners include a minimum of three sections:

1. The generator produces the ultrasonic energy—at a frequency of 20 to 50 kHz.
2. The transducer converts the electrical energy to mechanical movement and agitates the cleaning liquid. The transducer is mounted on or made integral with the bottom of the ultrasonic cleaning tank.
3. The control equipment starts and stops the cleaner. In more elaborate equipment, it also controls liquid temperature, cleaning time and filtering.

Other items may include electric heaters and thermostats to maintain the cleaning liquid at a desired temperature, timers which automatically determine the length of the cleaning period, spray rinses that wash off dirt loosened by ultrasonic action, and a system for filtering the cleaning liquid.

Most of the work to be done by the

electronic technician will be on the generator and transducer. On the other hand, there are some accessory items which he may handle profitably, depending upon his ability and facilities.

Ultrasonic generators

Ultrasonic generators are either high-power oscillators with the output taken off directly or low-power ones coupled to an amplifier which drives the transducer.

With a knowledge of tube types, the technician looking into his first cleaner can spot the oscillator and amplifier. But he may have trouble finding a dc plate supply. Why? There is none. This type of generator can use ac on the tube plates. Ultrasonic power is generated only during the half-cycle when the plates are positive. The stage may be either single-ended or push-pull, equivalent in efficiency to a half- or full-wave rectifier.

The major differences among manufacturers are the methods of producing ultrasonic oscillations. The most common systems use either a tapped oscillator coil or a feedback transformer. Sometimes there is a power amplifier driven by a tertiary winding on the oscillator transformer. Fig. 1 shows some typical commercial units with tubes. At

least one manufacturer produces a solid-state generator, with 32 transistors in push-pull parallel and a full-wave silicon rectifier.

Transducers

Transducers used in commercial cleaners are of the magnetostrictive or piezoelectric type. If the cleaning tank is small, say a quart or so, the transducer will be of the single-element type. Larger tanks holding many gallons are driven by a number of transducer elements in parallel or series-parallel. The specific makeup of elements vary with the particular manufacturer. In magnetostrictive types, an element usually consists of a core and a winding. Crystal transducer elements are generally blocks about 3 x 3 x 5 inches or slightly larger. Magnetostriction transducers are polarized by either permanent magnets or dc from a small solid-state rectifier.

Controls

A pair of toggle switches is usually all that is required to control small, simple cleaners. One of them controls filament power; the other, through a relay, controls plate power. Large elaborate units will require controls for various accessories. Fig. 2 illustrates a typical control circuit for a high-power cleaner. It is shown not so much to indicate a particular setup as to acquaint the technician with a typical sequence diagram. Points to remember about these diagrams are:

- Relay contacts are seldom shown near the actuating coil.
- Transformer secondaries are not always shown near the primary.
- Electronic components are not identified on the equipment but can be located by the wire or terminal-strip number.
- Control equipment is usually operated on 117 volts ac, even though the main equipment uses a higher voltage.

Troubleshooting

Once trouble is encountered and the technician has made the usual voltage and resistance checks, replaced tubes with available spares, or improvised bench-test setups to check high-power output tubes, it then becomes necessary to have some specific troubleshooting hints to ease the job.

Other than complete failure, or failure of auxiliary equipment, the most common complaint is the loss of cleaning efficiency. Although this can be caused by cleaning-liquid faults (dirty, too cold, etc.), a plant or operator problem, other causes may be defective transducers or low generator output.

When it is suspected that the transducer or generator is the source of trouble, here's what to do:

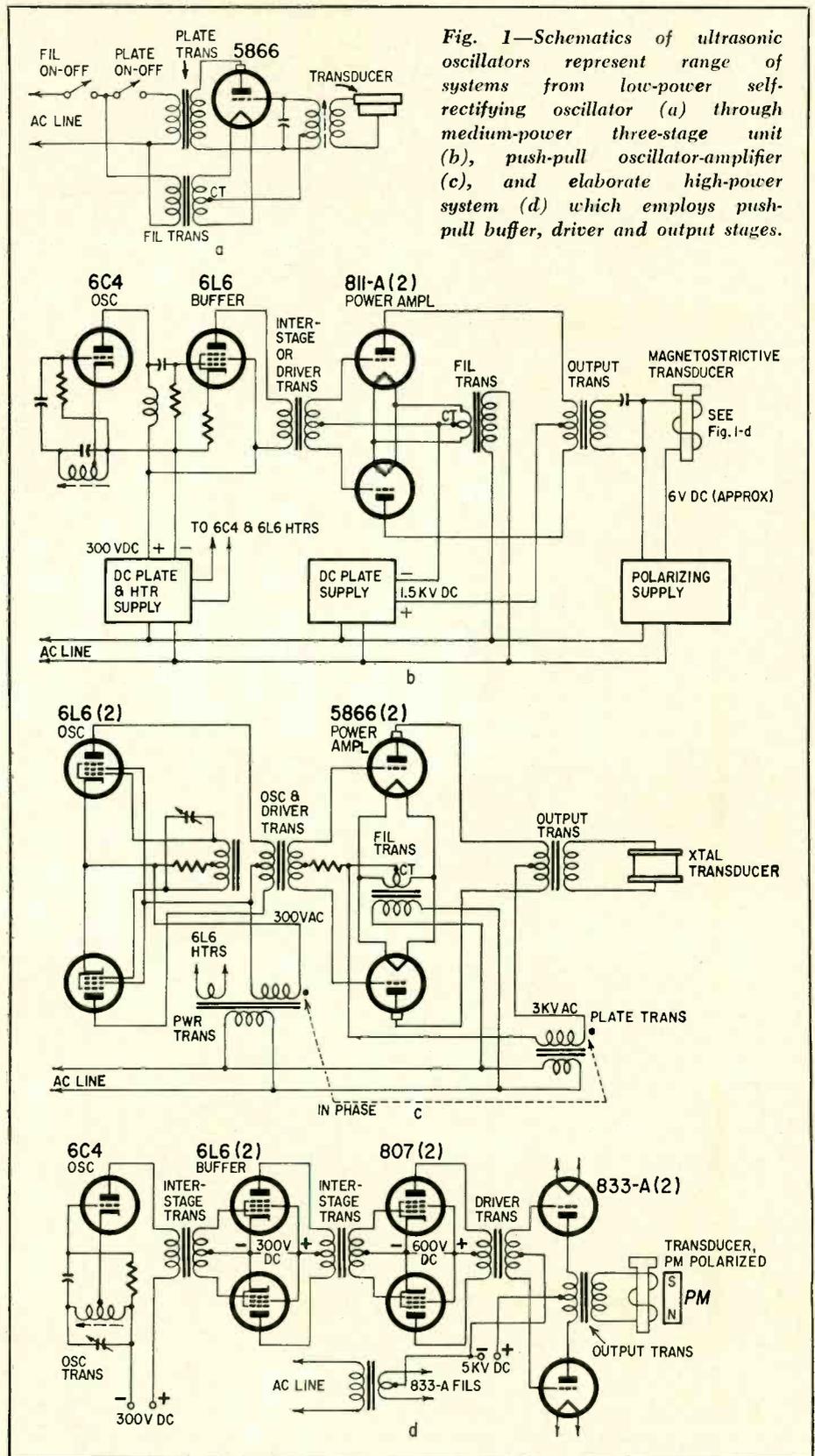


Fig. 1—Schematics of ultrasonic oscillators represent range of systems from low-power self-rectifying oscillator (a) through medium-power three-stage unit (b), push-pull oscillator-amplifier (c), and elaborate high-power system (d) which employs push-pull buffer, driver and output stages.

Nickel, iron, chromium, cobalt and other ferromagnetic materials change dimensions when in a magnetic field. This effect—called magnetostriction—varies with material and strength of the field. In ultrasonic transducers, the most-often-used magnetostrictive effect is the change in length along the axis of the external field. In an oscillating field, the material expands and contracts at the frequency of oscillation. A magnetostrictive transducer is generally made of tin tubes, rods or laminations formed into a core as the driving coil. Piezoelectric transducers are quartz or ceramic crystals which vibrate at the exciting frequency. The amplitude of the vibrations is greatest at the resonant frequency of the crystal.

Servicing Ultrasonic Cleaners

1. Rotate the oscillator tuning control to determine if it is set for maximum agitation in the tank. If the cleaner has a tuning meter, compare the reading with the manufacturer's specifications. A normal meter reading with poor agitation suggests transducer trouble; a low or very high reading is indicative of generator trouble.

2. Isolate the transducer elements and check. In many transducers a damaged element will not knock out the entire unit. In wound types, look for opens, shorts or a short to the core (grounding). Compare winding resistance of all elements to detect shorted turns. If available, a bridge should be used for this measurement. A check for opens, shorts, or grounds should also be made in crystal transducers. An open will be indicated by the absence of a capacitive kick with the vom on the $R \times 100K$ range.

3. Check for loss of polarizing voltage (when used) on magnetostriction transducers. Rotating the polarizing control (if any) should cause a change in the output plate current.

4. Using the ac scale of the vom

and a .05- μF 600-volt capacitor in series with the probe, measure the signal on the grid(s) of the output stage and compare it with the manufacturer's data or handbook values. If it is too low, work back toward the oscillator until the loss of gain is located.

5. In push-pull-parallel solid-state generators look for defective transistors. These can often be detected by their burned emitter resistors.

6. Make certain the cleaning liquid is at the correct temperature; a faulty thermostat might be cutting off the heat.

Complete equipment failure usually makes it easier for the technician. The following "cookbook" approach has been found to be practical in such cases:

1. Check all fuses.
2. Check door and cover safety interlocks.
3. Check the time-delay relay if filaments are on but plate voltage is not.
4. Check coax cable between generator and transducer for a short or open.

5. Check the transducer when loss of efficiency is the symptom.

6. See that the oscillator is not detuned. Tinkering with the oscillator or a defective component could cause the frequency to be outside the response range of the transducer, or may even cause complete failure to oscillate.

7. If a thermostat is used to hold the generator off until the cleaning liquid reaches a certain temperature, check it.

8. Check any air-flow interlock switches used in connection with the oscillator. If a multichassis, self-rectifying unit has been dismantled for any reason, make sure the polarity phase of the interconnecting ac lines has not been reversed.

Normally the electronics man will not be asked to work on the accessory equipment. Nevertheless, some knowledge of the related problems may prove useful. Some common troubles:

Liquid not heating or heating insufficiently:

Cause—Defective thermostat or defective heating elements.

Remedy—Isolate heating elements and check for opens. Defective elements must be replaced. Some thermostats may be repaired if the trouble is confined to the contacts.

No circulation:

Cause—Clogged filter, stuck valve, or faulty pump.

Remedy—If pump motor is not running, check for applied voltage and a tripped protective device. (If pump motor is running, a plumbing problem is suggested.) A faulty motor may be repairable economically.

Inoperative solenoid valve:

Cause—Mechanical binding or open coil.

Remedy—Replace coil.

Power-tube cooling fan inoperative:

Cause—Defective motor winding or bad bearing.

Remedy—Replace fan.

Precautions

The high voltages employed in the output stage of modern generators are dangerous. Be especially careful when measuring or working around them.

Respect the ultrasonic-frequency output voltage even on transistorized generators operating with less than 50 volts bias.

Avoid physical contact with the cleaning liquid unless you are sure it will not harm the skin.

Avoid breathing vapors from the liquid. If possible, work with plain water in the tank.

END


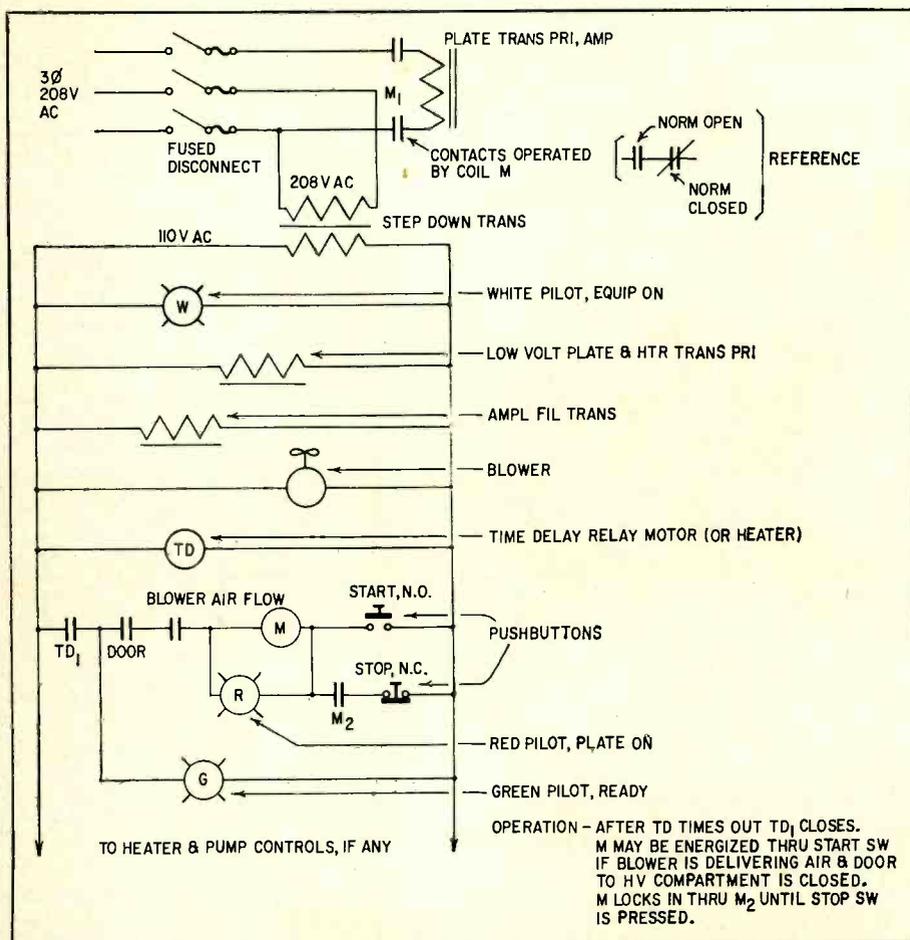


Fig. 2—Sequence diagram shows order in which power is applied to ultrasonic cleaner.

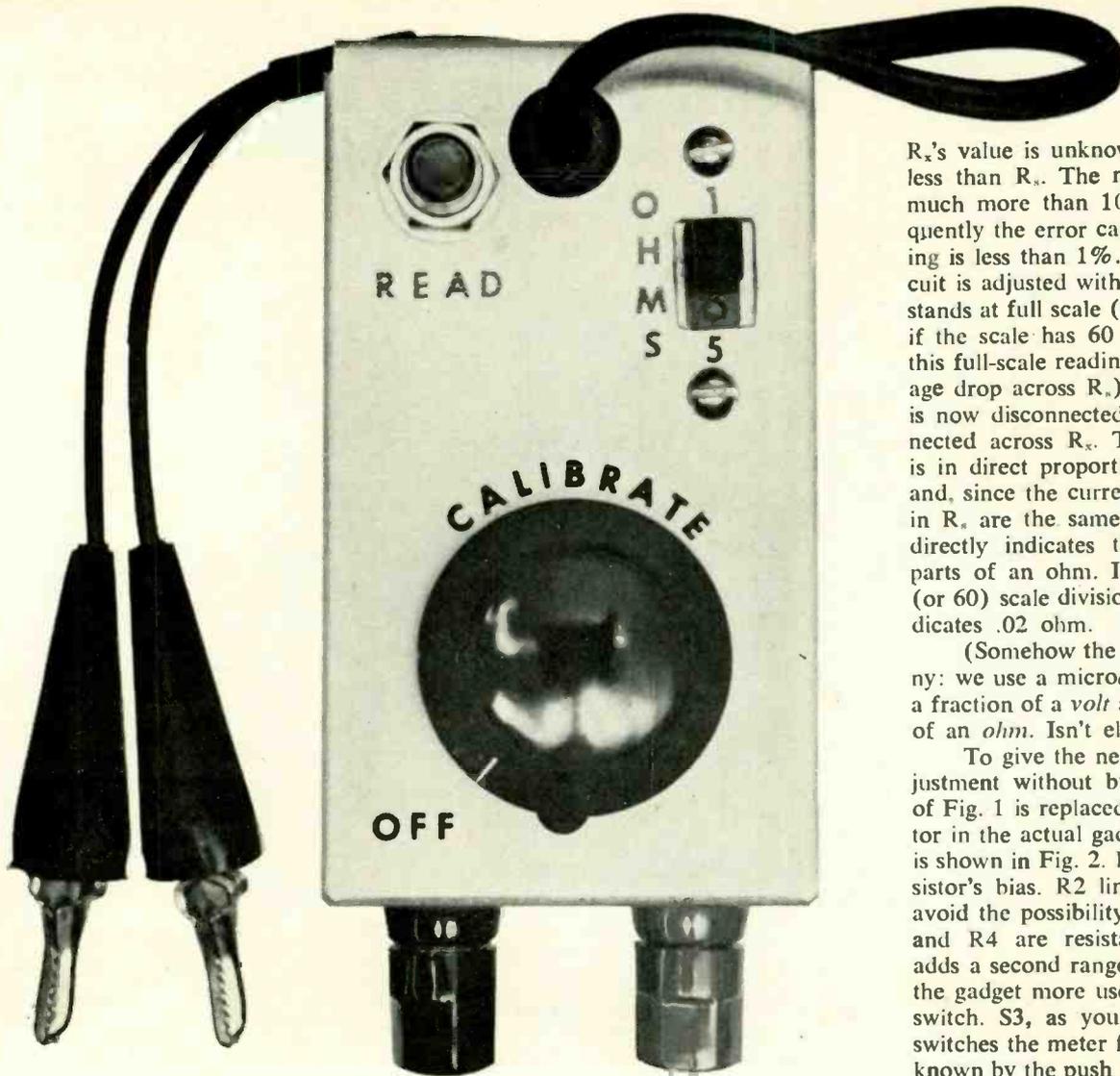

THE OHM SPLITTER

Use almost any vom to measure fractions of an ohm accurately with this adapter

By J. T. McCORMICK

IN THESE DAYS OF TRANSISTOR IGNITION systems and powerful amplifiers working at low voltage, it is sometimes necessary to get the lowdown on a resistor whose value is less than 1 ohm. This inexpensive ohm-splitting gadget will let you spread 1 ohm clear across the face of your multimeter.

Unlike the $R \times 1$ range of the usual ohmmeter, the gadget's accuracy is independent of battery condition. Moreover, you read fractions of an ohm directly on the dc scale—just as you do volts and amperes.

The Ohm Splitter can be used with any vom or multimeter that has a 50-, 60- or 100- μ A current range. It can have its own meter if frequent use justifies the expense. The percent accuracy of the meter has no bearing on the accuracy of resistance measurement, but

linearity does. The meter should have good linearity.

The gadget uses the principle that any part of a series-connected dc circuit carries exactly the same current as any other part. Fig. 1 shows the idea. R_s is a 1-ohm resistor used as a standard.

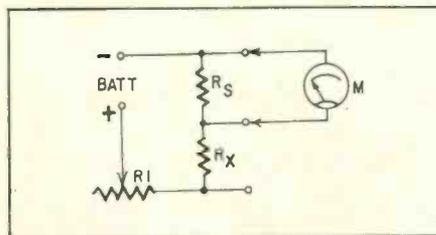


Fig. 1—Principle of Ohm Splitter is to adjust current through standard and unknown for known voltage drop across standard, then transfer meter to unknown.

R_x 's value is unknown, but presumably less than R_s . The meter's resistance is much more than 100 times R_s , consequently the error caused by meter loading is less than 1%. Current in the circuit is adjusted with R1 until the meter stands at full scale (or at the "50" mark if the scale has 60 divisions). We call this full-scale reading (actually the voltage drop across R_s) 1 ohm. The meter is now disconnected from R_s and connected across R_x . The drop across R_x is in direct proportion to its resistance and, since the current values in R_x and in R_s are the same, the meter reading directly indicates the value of R_x in parts of an ohm. If the meter has 50 (or 60) scale divisions, each division indicates .02 ohm.

(Somehow the situation seems funny: we use a microammeter to measure a fraction of a volt and call it a fraction of an ohm. Isn't electronics grand?)

To give the necessary range of adjustment without burning, the rheostat of Fig. 1 is replaced by a cheap transistor in the actual gadget. The full circuit is shown in Fig. 2. R1 controls the transistor's bias. R2 limits base current to avoid the possibility of burning R1. R3 and R4 are resistance standards. R4 adds a second range (5 ohms) to make the gadget more useful. S2 is the range switch. S3, as you can see, painlessly switches the meter from standard to unknown by the push of a button. D limits meter voltage to less than 1 volt in case the button is pushed with no R_x connected.


That's really the whole story. The Ohm Splitter can be built to suit your taste, but some remarks about the components may be helpful.

Q can be almost any "bargain" germanium power transistor, even a rather leaky one. It dissipates only a fraction of a watt and needs no heat sink. D, too, can be of the "bargain" variety, but don't use a miniature diode. Current can be quite heavy, depending on the setting of R1.

Ordinary lamp cord can be used for test leads. Attach these leads permanently; the uncertain resistance of plugs and jacks cannot be tolerated. Any means of connecting the meter is acceptable. Five-way binding posts will take any meter.

I know of at least one multimeter which has a resistance of 6,000 ohms on its 60- μ A range. This means a 300-mA load on the Ohm Splitter's battery when using the 1-ohm range. Use C-size cells or alkaline cells if you are likely to use such a meter.

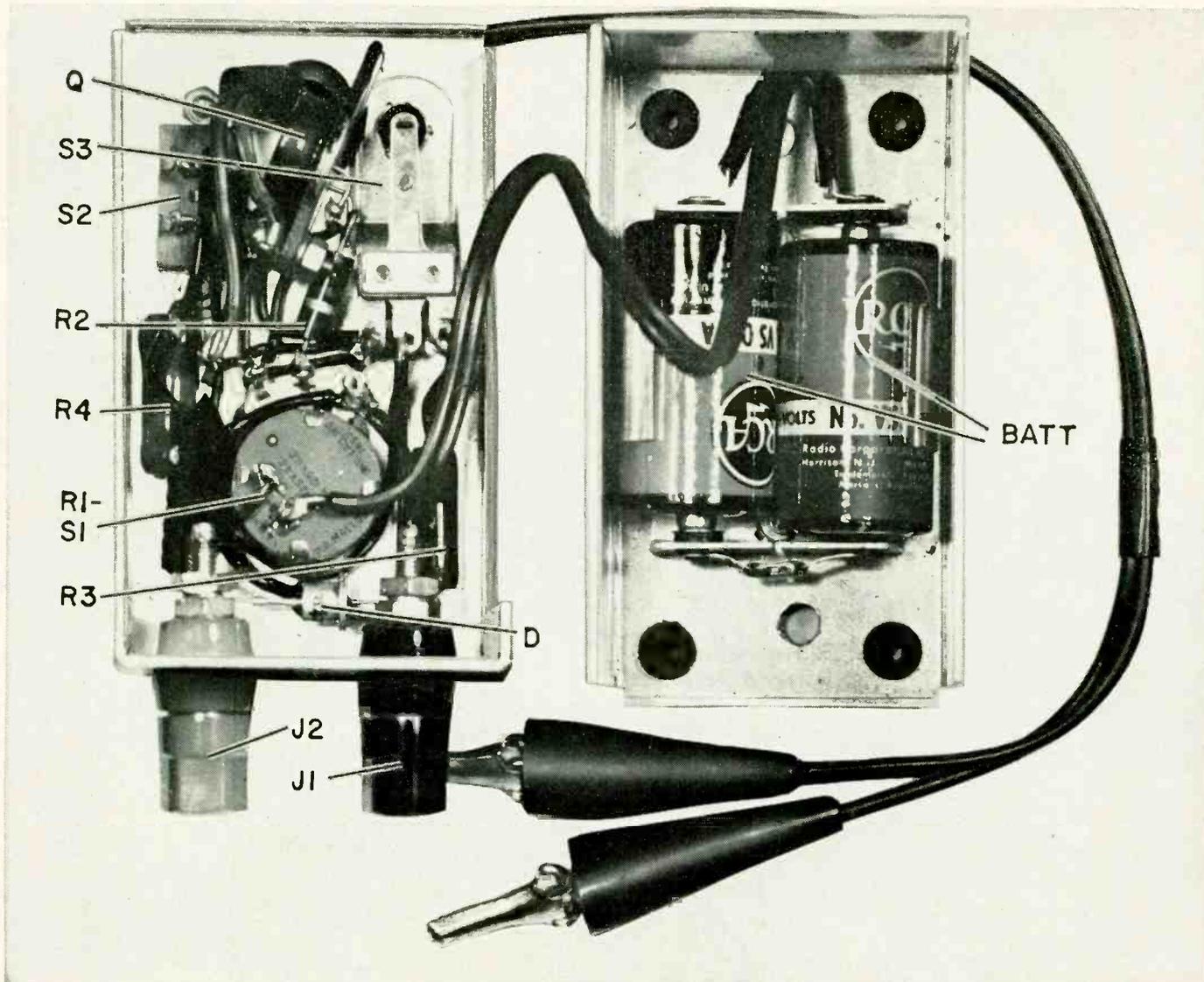Wirewound resistors are specified because they are readily obtainable. Incidentally, I used a 10% wirewound for



Solder connections must be good, especially in series circuit including S1, Q, the battery, R3 and R4, and the clips.

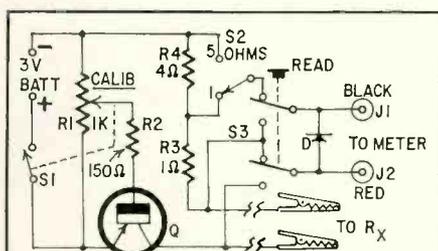


Fig. 2—Circuit of the entire Ohm Splitter. Transistor and diode can be almost any kind. See the parts list for data.

PARTS LIST

BATT—3-volt battery (2 C-cells)
 D—500-mA silicon diode, any voltage
 J1—black 5-way binding post
 J2—red 5-way binding post
 Q—germanium power transistor (1-watt dissipation or higher)
 R1—pot, 1,000 ohms, with spst switch
 R2—150 ohms, ½ W, 10%
 R3—1 ohm, low-wattage wirewound, 5%
 R4—4 ohms, low-wattage wirewound, 5%
 S1—spst switch on R1
 S2—spdt slide switch
 S3—dpdt pushbutton switch
 Case (author used 2¼ x 2¼ x 4-inch aluminum box), 2 crocodile clips, 2-cell battery holder, knob, etc.

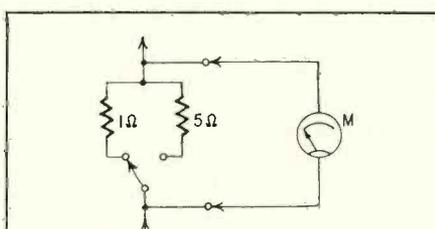


Fig. 3—DON'T try this circuit arrangement: It puts the unpredictable contact resistance of the switch into the circuit.

Since the indicating meter acts as a millivoltmeter, a higher range but lower resistance will often work better. For example: a 1-mA, 100-mV movement (meter resistance 100 ohms) reads full scale at 100 mA with the unknown terminals shorted, and, of course, less than that for any readable value of unknown. What is required for this instrument is a low-resistance meter, rather than a small-current type.

R4, and had to pad it with a foot of No. 32 wire rolled up in a piece of tape to bring it more nearly into line. If you want to use 1% resistors, ½-watt rating will do. Burstein-Applebee lists them in the 1-ohm value—but not the 4-ohm. Solder four 1-ohmers in series for R4; don't be tempted to use the idea of Fig. 3. The resistance of the switch would be included in your standard—and you would have no standard. The resistance of a switch cannot be assumed to be zero, nor expected to remain at a particular value.

The resistance of the test leads is the first thing to measure with the Ohm Splitter. Clip the ends together, calibrate, and push the button. This resistance must be subtracted from all future measurements. I shortened my leads to .02 ohm, so that it is necessary to subtract only one scale division. When using the 5-ohm range (where each scale division equals 0.1 ohm), lead resistance can usually be ignored. END

Join the PHOTOFACT[®]-OF-THE-MONTH Club

and receive each and every month

THE WORLD'S FINEST TV-RADIO SERVICE DATA

Complete up-to-the-minute coverage • Save over \$60 per year!

Howard W. Sams now offers this great new monthly package exclusively for P.O.M. members!

You get your 6 new PHOTOFACT Sets every month in sturdy new file folders sealed in factory carton to insure perfect condition and completeness—easier-than-ever to file and use. Now—only \$10 per month and you get 20% MORE COVERAGE!

NOW! more current model coverage each month to keep you ahead earning more—
AND YOU SAVE OVER \$60 PER YEAR!

As a PHOTOFACT-OF-THE-MONTH CLUB member, you get 6 new PHOTOFACT Sets every month—the world's finest TV-radio service data—with all the time-saving, profit-boosting help you want!



**AT LEAST
6 COLOR TV
FOLDERS MONTHLY**

**NOW! ONLY
\$10 PER MONTH
brings you
20% MORE
PHOTOFACT[®]
coverage!**

*complete current coverage of
at least 50 chassis each and
every month for less than*

20¢ per chassis model!

To stay ahead, to save money (individually purchased sets now sell for \$2.50 each)—join the PHOTOFACT-OF-THE-MONTH CLUB now!

see how PHOTOFACT boosts your earning power!

**SUBSCRIBE TODAY THROUGH
YOUR SAMS DISTRIBUTOR OR
USE THIS HANDY ORDER FORM**



TRY A THREE-MONTH P.O.M. SUBSCRIPTION

HOWARD W. SAMS & CO., INC. Dept. REF-9
4300 W. 62nd St., Indianapolis, Ind. 46268

Enroll me for a 3-month membership in the Photofact-of-the-Month Club. I agree to pay \$10 per month, and understand I will receive 6 current Photofact Sets monthly for 3 months to be delivered by my Sams Distributor (named below).

Name _____

Shop Name _____

Address _____

City _____ State _____ Zip _____

My Sams Distributor is: _____

Signed: _____

Circle 26 on reader's service card

CIRCLIT ANALYZERS



PS 127—Wide Band 5" Oscilloscope with direct reading P to P volts. **\$199.50**



SM 112B — Combination VTVM-VOM with automatic scale indication. **\$89.95**



SS 137—Sweep Circuit Analyzer for both black & white and color TV **\$94.50**



FS 134—Field Strength Meter covers all VHF and UHF channels plus FM. **\$199.50**

PICTURE TUBE TESTERS & REJ.



CR 143—CRT Champion Deluxe CRT checker and rejuvenator. A must for accurate color CRT testing. **\$99.50**



CR 13 — CRT Cadet: CRT checker and rejuvenator. Easy to set-up; fast to use. **\$79.95**


COLOR GENERATORS



CG 10 — Lo Boy Standard Color Bar Generator — battery operated. **\$89.95**



CG 12 — Lo Boy Standard Color Bar Generator — AC operated and 4.5 mc tuning crystal. **\$109.95**

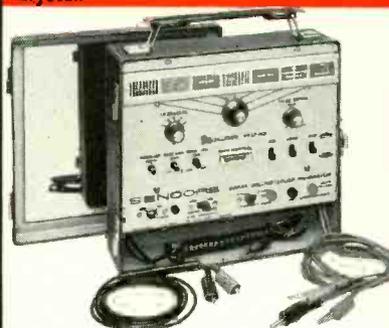

CG 141—Color King Standard Color Bar Generator with exclusive TEMP CONTROL for absolute stability. **\$149.95**



CA 122B—Deluxe Color Circuit Analyzer for black & white and color. **\$187.50**

NEW for 1967

*the most complete
line of quality
time-saving test
instruments by*

SENCORE

NO. 1 MANUFACTURER OF ELECTRONIC MAINTENANCE EQUIPMENT

Here's the big SENCORE line-up for '67. All new, all improved. Each instrument is the finest in the field, designed, engineered and built to save time, make you money. Every instrument is

triple tested for guaranteed accuracy. Compact, portable, rugged. All steel encased. Priced right — check and compare. SENCORE... your best buy, always.

TRANSISTOR TESTING




TR 139—In-Circuit, Out of Circuit Transistor Tester that works every time **\$89.50**



TR 115—Out of Circuit Transistor Tester. Easy to use. **\$24.95**



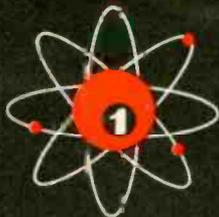BE 124—Battery Eliminator for fast repair of transistor radios. **\$24.95**



MULTIPLEX



MX 129—Deluxe Multiplex Generator for fast repair of FM Stereo receivers. **\$169.50**



MX 11—Channelizer FM Stereo Multiplex Generator simplifies stereo servicing. **\$99.50**

SUBSTITUTION

RC 144—Handy 36 Resistor - Capacitor substitution unit—lower than the cost of the parts! **\$14.95**




RC 145—Handy 53 Resistor, Capacitor and Electrolytic substitution with full protection. **\$34.95**



RC 146—Handy 75 Resistors, Capacitors, Electrolytics, Power Resistors, and Universal Silicon and Selenium Rectifiers at your fingertips. **\$44.95**



TUBE TESTERS

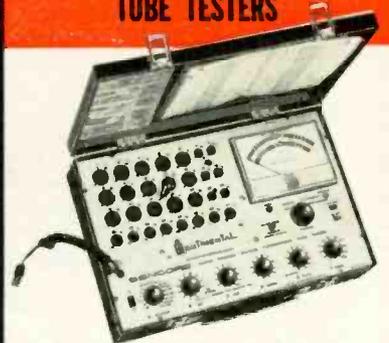

MU 140 Continental Mutual Conductance Tube Tester—also speedy Mighty Mite tester with first three controls. **\$179.50**



TC 13T—Semi-Automatic Tube Tester for you or your customer. Easy to operate—sensitive. **\$99.50**



TC 142—New Mighty Mite V speed and sensitive in home or shop tube tester. **\$74.50**

FC 147—Filament Checker. A must for series string filament testing. **\$4.95**



BE 113—Dual TV Bias Supply. Two 0 to 20 volts DC supplies for alignment or AGC trouble shooting. **\$12.75**



FREE
SEND
FOR NEW 1967
SENCORE
CATALOG


SENCORE, INC. 426 S. Westgate Dr., Addison, Ill. 60101

Please rush me your FREE 1967 catalog, showing all your new instruments.

NAME _____ (Please print)

ADDRESS _____

CITY _____ STATE _____ ZIP _____

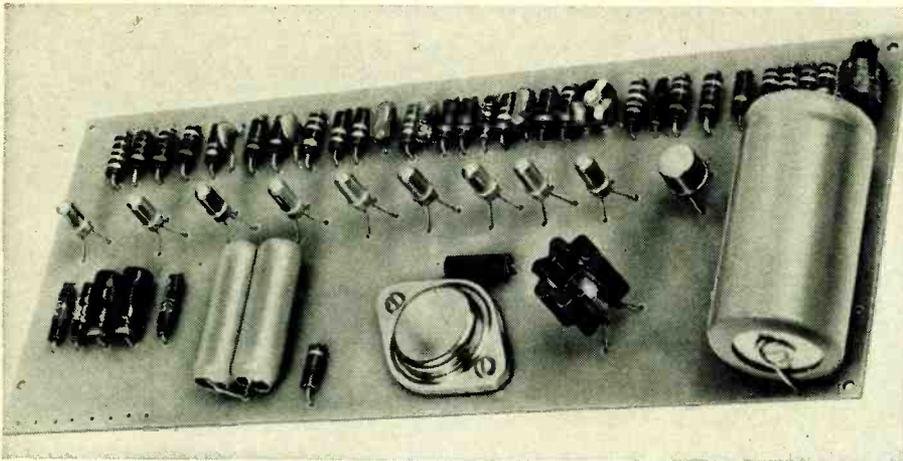

A CLASS-D HI-FI AMPLIFIER

A practical circuit using pulse-width modulation

By I. QUEEN

SWITCHING AMPLIFIERS HAVE BEEN DESCRIBED several times in recent publications. A build-it-yourself amplifier of this kind was covered in a series of articles by Norman Crowhurst which began in RADIO-ELECTRONICS for July 1965. The response of the amplifier was quite limited and I wondered what could be done to broaden it for hi-fi use. I found my answer during a trip to England. I came across the Sinclair X-20 switching-type hi-fi amplifier. This mode of operation is also called class D and pulse-width modulation. This is a description of that unit.

The X-20 uses 12 transistors, is mounted on a printed-board measuring 8¼ x 3¼ x 1 inches, and weighs less than 4½ oz. It has less than 0.1% total harmonic distortion at 10 watts. Though it is capable of 40 watts peak music power, Sinclair specifies it at 20 watts of average music power.

The X-20 was available without power supply or volume and tone con-

trols. We mounted the X-20 in an aluminum chassis (10 x 5 x 3 inches) and added the tone and volume controls and power supply. Fig. 1 shows the simple

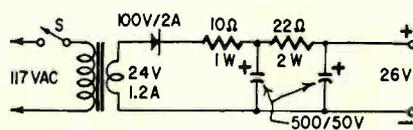


Fig. 1—Power supply for the amplifier.

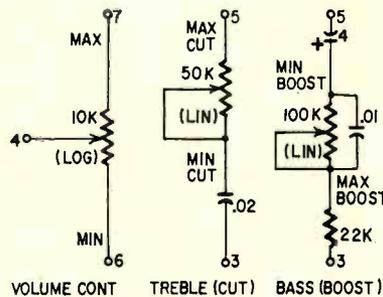


Fig. 2—Amplifier controls. Either or both tone controls can be used.

supply we used, and Fig. 2 the controls.

The schematic of the X-20 is shown in Fig. 3. The operation is as follows:

Q1 is a preamplifier stage which can handle as little as 1 mV (into 5,000 ohms). The preamp stage is followed by high-gain stages Q2 and Q3, after the external volume control. Q4 and Q5 form a free-running multivibrator at about 75 kHz. The output of Q5 is a square wave. It is fed into Q6, a feedback integrator—note the capacitor between collector and base. After integration, the waveform becomes triangular, and is fed into Q8 and Q9. Q7 (a transistor with collector left open so it acts as a diode) conducts only when the applied signal exceeds the negative bias at its emitter—that is, its anode in this hookup.

C7 and Q8 differentiate the square waves, converting them to pulses. Negative peaks drive Q8 to conduction, blocking Q9. Positive peaks will block Q8, thus permitting Q9 to conduct. Due to the large amplification of Q8 and Q9, the transistors are overloaded by these pulses, and their tops are flattened. The output becomes a symmetrical square wave, assuming there is no audio signal being fed into the amplifier.

When audio is applied, signals from Q3 are fed through R8 and C12. Q7, acting as a diode, mixes them with the pulses from Q6. When the speech signal is positive-going, it adds to the positive pulse, increasing and widening it. At the same time, the positive-going speech signal will reduce and narrow the negative pulse, when it is present. Of course, when the audio wave goes negative, the opposite will happen (see Fig. 4). During a complete audio cycle, the output waveform from Q9 will look like Fig. 4-a, then like 4-b, back to 4-a, then to 4-c, then finally back to 4-a. The pulses, varying in width according to the audio-rate signal being fed to the amplifier, are reduced in amplitude by R20 and R21, then fed to the base of Q10.

Transistor Q10 acts as a control de-

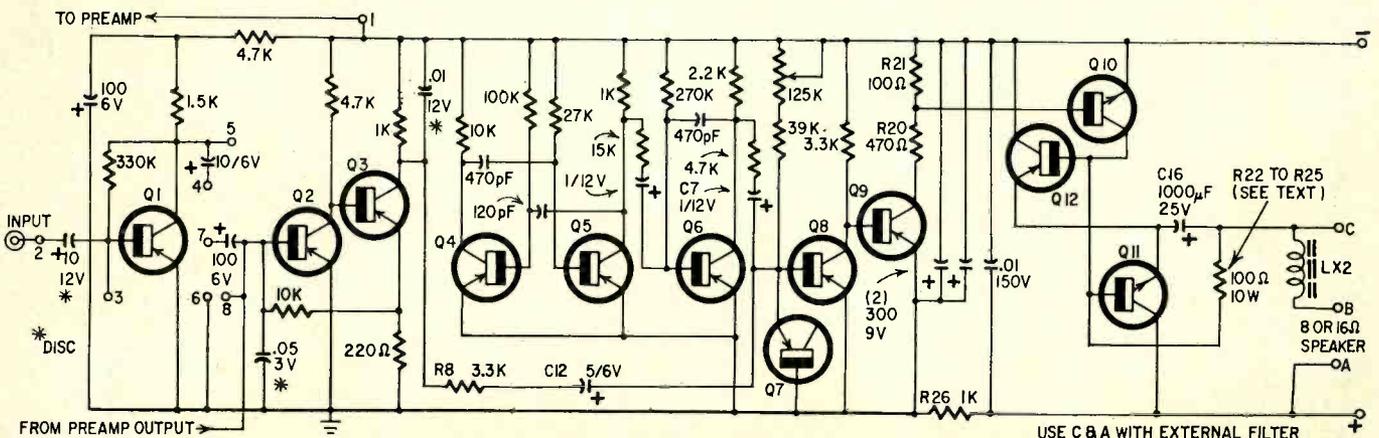


Fig. 3—Schematic of the Sinclair X-20 pulse-width modulated amplifier.

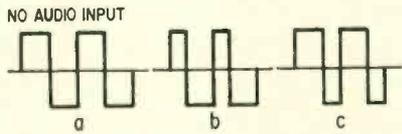


Fig. 4—Amplifier output waveforms. Pulse width—above and below baseline—varies with instantaneous polarity and frequency of the audio signal. a—No audio input, b—the negative audio half-cycle, c—the positive half-cycle.

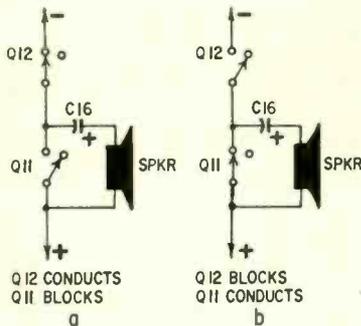


Fig. 5—Basic output circuit with Q11 and Q12 represented by switches.

vice, whose resistance varies with its base bias. When the base goes more positive (than its emitter) Q10 conducts. The transistor blocks when the base goes more negative, of course.

The two-transistor output stage, Q11 and Q12, is in series across the power supply. When the control transistor conducts, the bases of both output transistors are in effect connected to negative. Therefore, Q12 conducts, while Q11 blocks. On the other hand, when the control transistor is blocked, the bases of the output transistors return to positive, through resistors R22, R23, R24, R25 (shown as a 100-ohm, 10-watt unit) and the speaker. Q11 conducts, and Q12 is cut off.

What effect does this have on the speaker? Fig. 5 shows. For the moment, assume there is no audio to the amplifier. Q10 will have equal on-off intervals at the high switching frequency of 75 kHz. Q11 and Q12 are represented by switches. In Fig. 5-a, C16 will charge through the speaker. In 5-b, it discharges and current goes through the speaker in the opposite direction.

When audio is applied to the input of the amplifier, conditions change. The negative and positive pulse widths are no longer equal. One output transistor will conduct for a longer period than the other. During the next half-cycle, the second transistor will conduct longer. And so on. This pulse width varies at the audio rate of the input signal, which becomes audible in the speaker. END



has
everything
in

TV hardware

GC-Telco, the world's largest basic manufacturer of TV antenna hardware, is your most complete single source for all TV antenna installation needs, indoor and outdoor antennas, and antenna accessories.

Choose from the largest selection of chimney, roof, wall or vent-type mounts, all available in attractively carded kits, antenna masts, lead-in and rotor wire, stand-offs, lightning arrestors, ground and guy wire needs . . . everything needed to make any installation easier, faster, more efficient.

For quality, versatility, and dependability, go with the leader . . . make GC-Telco your No. 1 source today.

Write for your Giant FREE GC Catalog today . . . over 12,000 items including TV Hardware, Phono Drives, Chemicals, Alignment Tools, Audio, Hi-Fi, Stereo & Tape Recorder Accessories, Nuts & Bolts, Plugs & Jacks, Service Aids, and Resistive Devices.



*only GC gives you
everything in electronics.
..... for almost 40 years!*

GC ELECTRONICS COMPANY

400 South Wyman Street
Rockford, Illinois 61101

A DIVISION OF HYDROMETALS, INC.


Circle 28 on reader's service card



Telco Snap-In
Chimney Mount
Cat. No. 8610



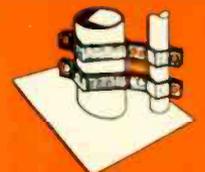Telco Ratchet Type
Chimney Mount
Cat. No. 8006



Telco Vent Mount
Cat. No. 8002



Telco E-Z Stand-Off
Cat. No. E-Z 8027
Wood Screw Stand-Off
Cat. No. 8028



Telco 3-Way Antenna Klip
Cat. No. 9015



RADIO-ELECTRONICS READER'S SERVICE

Here's how you can get manufacturers' literature fast:

1. Tear out the post card on the facing page. Clearly print or type your name and address.

Include zip code! Manufacturers will not guarantee to fill your requests unless your zip code is on the reader service card!

2. Circle the number on the card that corresponds to the number appearing at the bottom of the **New Products, New Literature or Equipment Report** in which you are interested.

For literature on products advertised in this issue, circle the number on the card that corresponds to the number appearing at the bottom of the advertisement in which you are interested. Use the convenient index below to locate quickly a particular advertisement.

3. Mail the card to us (no postage required in U.S.A.)


Advertisements in this issue offering free literature (see the advertisements for products being advertised):

AMPEREX ELECTRONICS CORP. (Second Cover)	Circle 7
AMPLIFIER CORP. OF AMERICA (Pg. 90)	Circle 132
ARCO ELECTRONICS (A Division of Loral Corp.) (Pg. 23)	Circle 19
B & K (Division of Dynascan Corp.) (Pg. 13)	Circle 13
BARKER PRODUCTS CO. (Audio Division of Component Manufacturing Services, Inc.) (Pg. 26)	Circle 21
BROOKS RADIO & TV CORP. (Pg. 90-91)	Circle 133
BURSTEIN-APPLEBEE CO. (Pg. 88)	Circle 129
CASTLE TV TUNER SERVICE, INC. (Pg. 83)	Circle 123
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 5)	Circle 9
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 28-31)	Circle 23
CORNELL-DUBILIER (Third Cover)	Circle 149
CORNELL ELECTRONICS CO. (Pg. 102)	Circle 146
DELTA PRODUCTS, INC. (Pg. 16)	Circle 15
DEVRY INSTITUTE OF TECHNOLOGY (A Subsidiary of Bell & Howell) (Pg. 7)	Circle 11
EDMUND SCIENTIFIC CORP. (Pg. 101)	Circle 144
FINNEY CO. (Pg. 14-15)	Circle 14
GBC AMERICA CORP. (Pg. 77)	Circle 114
GC ELECTRONICS CO. (Pg. 73)	Circle 28
HEALD ENGINEERING COLLEGE (Pg. 93)	Circle 138
HEATH CO. (Pg. 24-25)	Circle 20

INTERNATIONAL CRYSTAL MFG. CO., INC. (Pg. 104)	Circle 148
JFD ELECTRONICS CO. (Pg. 27)	Circle 22
JENSEN MANUFACTURING DIVISION (The Muter Co.) (Pg. 6)	Circle 10
LAFAYETTE RADIO ELECTRONICS (Pg. 85-86)	Circle 127
MALLORY, P. R. & CO. (Pg. 81)	Circle 118
MICROFLAME, INC. (Pg. 89)	Circle 131
MIKE QUINN ELECTRONICS (Pg. 84)	Circle 125
MUSIC ASSOCIATED (Pg. 82)	Circle 121
OLSON ELECTRONICS, INC. (Pg. 83)	Circle 124
OXFORD TRANSDUCER CO. (A Division of Electric Corp.) (Pg. 22)	Circle 18
PERMOFLUX CORP. (Pg. 98)	Circle 140
POLY PAKS (Pg. 103)	Circle 147
QUAM-NICHOLS CO. (Pg. 80)	Circle 117
QUIETROLE CO. (Pg. 82)	Circle 122
RADAR DEVICES (Pg. 1)	Circle 8
RADIO SHACK (Pg. 94-97)	Circle 139
READING IMPROVEMENT PROGRAM (Pg. 91)	Circle 134
RYE INDUSTRIES, INC. (Pg. 88)	Circle 128
RYE INDUSTRIES, INC. (Pg. 89)	Circle 130
S & A ELECTRONICS INC. (Pg. 92)	Circle 135
SALCH & CO., HERBERT (Marketing Division of Tompkins Radio Products) (Pg. 84)	Circle 126
SAMS & CO., INC., HOWARD W. (Pg. 69)	Circle 26
SAMS & CO., INC., HOWARD W. (Pg. 82)	Circle 120
SENCORE (Pg. 70-71)	Circle 29
SHURE BROS. (Pg. 17)	Circle 16
SOLID STATE SALES (Pg. 100)	Circle 142
SONY CORP. OF AMERICA (Pg. 81)	Circle 119
SPRAGUE PRODUCTS COMPANY (Pg. 12)	Circle 12
SURPLUS CENTER (Pg. 98)	Circle 141
TURNER MICROPHONE CO. (Pg. 87)	Circle 110
UNITED RADIO CO. (Pg. 101)	Circle 143
WARREN ELECTRONIC COMPONENTS (Pg. 102)	Circle 145

NEW PRODUCTS

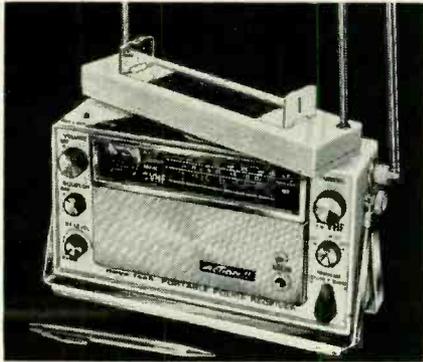More information on new products is available free from the manufacturers of items identified by a Reader's Service number. Turn to the Reader's Service Card facing page 74 and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.



5-BAND PORTABLE POLICE RECEIVER AND RADIO DIRECTION FINDER, Action!! 14 transistors. Solid-state. Covers 30-50 and 150-175-MHz Business bands, low-frequency beacon and weather band, marine/shortwave band and standard AM broadcast band. 4-way power supply. Rotating antenna. Includes squelch control, Morse-code plate, calibrated optical sights, removable mounting bracket, 2 headphone jacks, dial light, 3 extendable ship antennas. Also includes leather carrying case, batteries, miniature earphone, house-current adapter. 3 x 9 x 6 in. 2½ lb. \$129.95—Nova-Tech, Inc.

Circle 46 on reader's service card



AMPLIFIED SPLITTER, the Homer, model HVB-3P for TV and FM. Features the inductive-coupled emitter feedback circuit. The new I.C.E.F. circuit combines the low distortion and strong-signal-handling properties of the common-base circuit with the low-noise high-gain properties of the common-emitter circuit. Intersect isolation, 14 dB. 75-ohm coax. Includes 5 BTF-591 solderless male coax connectors for RG-59/U type cable. 4½ x 1¾ x 1¾ in. \$27.50.—Blonder-Tongue Laboratories, Inc.

Circle 47 on reader's service card

14-PIECE NUTDRIVER/SCREWDRIVER ROLL KIT, model no. 99PR. Includes a regular Series 99 Service Master handle, 9 interchangeable nutdriver blades with hex openings from 3/16 in to ½ in., Nos. 1 and 2 Phillips single-end screwdriver blades, 2 single-end blades




for slotted screws with tip widths of 3/16 and ½ in. Shockproof, breakproof plastic handle holds all blades from Series 99.—Xcelite, Inc.

Circle 48 on reader's service card



AUTOMATIC VOLTAGE REGULATOR, model D-210. For appliances rated up to 400W. Automatically boosts line voltage 10V when the line drops below 110V.—Perma-Power Co.

Circle 49 on reader's service card

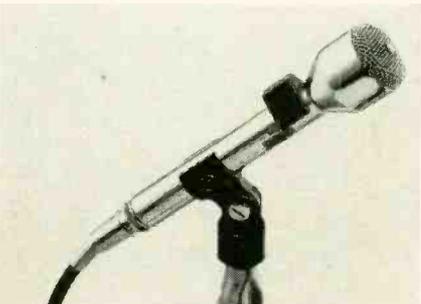

HAND-AND-STAND MIKE, model 631. Features a magnetically operated

This Unique **FREE BOOK** can put you into the **TOP PROFIT CCTV BUSINESS**



The encyclopedia of the CCTV industry covers everything from cameras to wall mounts, all of them exclusive—available only thru GBC.

SHOWS YOU HOW YOU CAN CASH IN BIG in the market the experts describe as "fantastically big"... "scratched only on the surface" and "ready to break wide open."

EVERY ITEM YOU NEED to pick up the business that's waiting for you, all around you. Everything to help you make any type of CCTV installation a simple one. It's all here in this permanent hard-bound, loose leaf book, and it's all yours FREE.

The only one complete source supplier in CCTV.

GBC America Corp.

89 FRANKLIN ST., NEW YORK, N.Y. 10013 • Phone: WOrth 6-5412

GBC AMERICA CORP.

89 Franklin St., New York, N.Y. 10013

Gentlemen:

Please send me the GBC Book with no obligation on my part. (Attach coupon to your letterhead, please.)

Name _____

Business Name _____

Address _____

City, State _____ Zip Code _____

Circle 114 on reader's service card

One of a series of brief discussions
by Electro-Voice engineers



THE SEARCH FOR REACH

JOHN R. GILLIOM
Loudspeaker Project Engineer

Horn-and-driver loudspeakers are generally used in applications where extended reach and high efficiency are needed, such as at stadiums, athletic fields, etc. Where maximum reach is needed, large horns are often used to concentrate all of the available energy in a narrow beam. This technique is effective at low and mid frequencies.

At high frequencies, however, the large horn mouth is several wavelengths in diameter, so that the radiated power is concentrated into an increasingly narrow beam that does not fully cover the desired sound field. Secondly, the reentrant folds in the horn path have dimensions on the order of a wavelength at high frequencies. Acoustic losses are inevitable when the air path dimension at the bend is greater than about one quarter wavelength. Even with the use of wide-range drivers, severe losses in intelligibility are encountered with large reentrant horns.

A third problem is the production of harmonic and intermodulation distortion at high frequencies. The narrow throat section typical of most large reentrant horns gives rise to non-linear compression of air. For example, a large horn with 150 cycle cutoff and $\frac{7}{8}$ " diameter throat produces about 17% second harmonic distortion at 3kc with just one acoustic watt output from the driver.¹ This type of distortion rises with increasing frequency because it is proportional to the number of wavelengths through which sound passes at high pressure.

A unique solution to the problem of high-level propagation of high frequencies is the Electro-Voice Model AC100 Compound Concentrating Projector. The driver is horn-loaded on both sides of the diaphragm, with energy below 1kc being radiated from the rear into a large low-frequency horn. Output above 1kc radiates from the front of the diaphragm into a small, short horn with only two 90° bends, mounted coaxially with the low frequency horn. Both horns have similar dispersion patterns for uniform coverage.

Harmonic distortion is significantly reduced in the compound horn, due to the very short horn length at high frequencies. Intermodulation distortion is also lessened since lows and highs are separated. The resultant lower distortion and extended frequency response increases intelligibility in the listening area. A larger useful listening area also results from the uniform distribution of energy at all frequencies.

The AC100 horn and its matching drivers offer an economical and efficient answer to problems of extended reach. Its compact dimensions belie its ability to extend sound coverage where low distortion and high sound levels are required.

¹ L. Beranek. *Acoustics*, p. 276.


For technical data on any E-V product, write:
ELECTRO-VOICE, INC., Dept. 973E
613 Cecil St., Buchanan, Michigan 49107

Electro-Voice
SETTING NEW STANDARDS IN SOUND

NEW PRODUCTS continued


reed relay switch, the *Uniseal*. 4-stage filter traps dirt and provides blast protection. Mechanical nesting construction. Frequency response, 100-13,000 Hz. Output, -55 dB. Includes the 310 stand clamp. Available in satin chrome or matte satin nickel finish. \$60—Electro-Voice, Inc.

Circle 50 on reader's service card

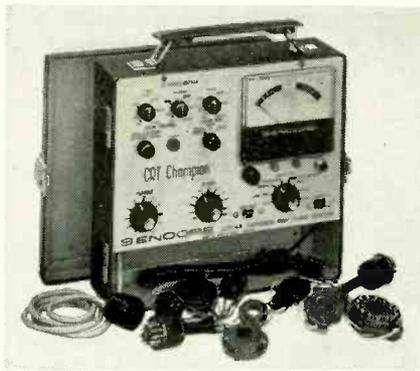

CRT TESTER, model CR143. Fully automatic. Separate G2 screen grid controls. Makes all standard color and b-w CRT tests. Rejuvenation and shorts removal made with *Automatic Rejuvenation Circuit*. Includes plug-in sockets. 10 x 9 x 3½ in. 11 lb. \$99.50—Sencore


Circle 51 on reader's service card

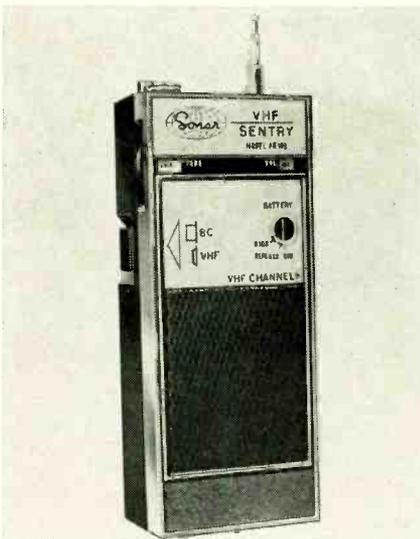

PORTABLE VHF MONITOR RECEIVERS, models FR-103, FR-106, AR-107 for 150-175, 20-50 and 108-136 MHz, respectively. Solid-state. Operate on 2 crystal-controlled vhf channels plus broadcast band. Built-in battery-condition meter, adjustable antenna. Include earphone and carrying strap. 5½ x 2½ x 1½ in. 11 oz. \$39.95—Sonar Radio Corp.

Circle 52 on reader's service card

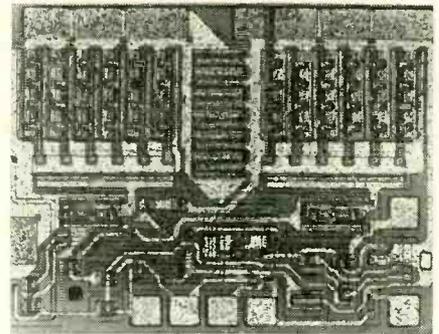AUDIO AMPLIFIER, model MC-1554G. Fully monolithic. Output, 1W. Total harmonic distortion, less than 0.4%




from 20-20,000 Hz. Housed in a 10-pin low-profile metal can. Input impedance, 10 ohms; output impedance, 0.2 ohms. Voltage gain adjustable to 9, 18 or 36. Output voltage sensitivity to power-supply variations, 40 mV/V. Drain current, 11 mA dc with a 16-V power supply at zero signal input.—Motorola Semiconductor

Circle 53 on reader's service card



STEREO COMPACT, model 230. 4-track stereo record and playback system. Built-in solid-state stereo control center. Input and switching facilities for the connection of external hi-fi components. 3 tape speeds, retractomatic pinch roller, automatic end-of-reel shutoff, digital tape counter. Includes 2 VU meters; stereo headset jack; left, right, and stereo speaker modes; 2 Sony F-45 cardioid dynamic mikes.—Sony Superscope

Circle 54 on reader's service card

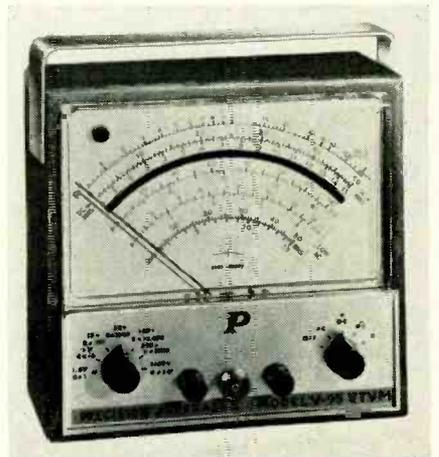

PROFESSIONAL VTVM, model V-95. Has solid-state power supply which replaces the batteries normally required in ohmmeter section. Includes mirrored

New RCA Parts Catalogs make it easier for you to locate the right number — fast.

You'll find these new easy-to-use catalogs save you time and money . . . reduce parts hunting time; to increase profitable bench time.

A complete complement of RCA replacement parts catalogs offers a new, easy arrangement for locating genuine RCA replacement parts, for popular home instruments.

Original Equipment Manufacturers' Part numbers are also listed—with suggested RCA replacement part numbers. Items are listed by part name, manufacturer and part number—from Audio Output to Yoke; from Diode 14m7 to ZD100B; from brand "A" Phono Cartridge to "X" Transformer.

For every RCA Victor Color TV from 1963 through 1966, there is a complete parts list by model name and number. Each model is illustrated. Sub-assemblies, such as Tuner and Record Changer, are pictured with an exploded view, showing correct line-up of parts.

To obtain your copies, of the catalogs listed below, contact your RCA Parts Distributor.



THE MOST TRUSTED NAME IN ELECTRONICS

RCA PARTS AND ACCESSORIES, Deptford, N.J.



The following RCA Catalogs are available now:

MLP-155—RCA VICTOR COLOR TV. 1963 Models. Parts Lists by Model
MLP-156—RCA VICTOR COLOR TV. 1964 Models. Parts Lists by Model
MLP-157—RCA VICTOR COLOR TV. 1965 Models. Parts Lists by Model
MLP-158—RCA VICTOR COLOR TV. 1966 Models. Parts Lists by Model
MCP-198—DIODE REPLACEMENT GUIDE
MCP-199—TRANSISTOR REPLACEMENT GUIDE

MCP-104—RCA TV TUNER TO REPLACEMENT STOCK NUMBER CROSS REFERENCE
MCP-105—RCA COLOR TV COMPONENT REPLACEMENT GUIDE
MCP-106—RCA PHONOGRAPH CARTRIDGE AND NEEDLE REPLACEMENT GUIDE
MCP-107—RCA COLOR AND BLACK-AND-WHITE TV COMPONENT REPLACEMENT GUIDE
MCP-168—RCA ELECTROLYTIC CAPACITOR REPLACEMENT GUIDE

Impedance mismatch problems?

When most voice coil impedances were either 3.2 ohms or 8 ohms, speaker replacement was relatively simple. Then came transistor sets, and equipment without output transformers, and now voice coil impedances range all over the map.


It's important to remember that a mismatched impedance in a speaker replacement will almost surely create problems... from a loss of volume to a blown transistor.

Quam... and only Quam... helps you avoid these problems these three ways:

1. WIDE CHOICE—As Photofacts/Counterfacts participants, we know in advance what voice coil impedance the new equipment will require, so we generally have the right speaker in our comprehensive line *when you need it*.

2. VERSATILE SPEAKERS—Quam *multi-tap speakers* offer a choice of impedances in a single unit. Available in all the sizes you need for automotive replacement, Quam multi-taps handle 10, 20, or 40 ohm applications.

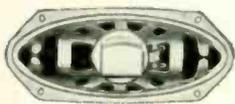3. SPECIAL SERVICE—Just in case you run across an oddball, we offer this convenient exclusive: *any Quam speaker can be supplied with any voice coil impedance, only \$1.00 extra, list price.*



QUAM

THE QUALITY LINE
FOR EVERY SPEAKER NEED

QUAM-NICHOLS COMPANY

234 East Marquette Road • Chicago, Illinois 60637

Circle 117 on reader's service card

NEW PRODUCTS continued


scales to eliminate parallax, specially calibrated scales for reading low-voltage measurements during transistor analysis in the 0.5-, 1-, 1.5- and 5-V ranges, and simplified peak-to-peak and dB scales. Accessory high-voltage and rf probes available at \$12.95 and \$7.95, respectively. \$79.95—Precision Apparatus

Circle 55 on reader's service card



CAPACITOR-DISCHARGE TRANSISTORIZED IGNITION SYSTEM, the *Fyreball*. For racing cars and boats, 12 or 24V. Positive and negative ground systems. Fiberglass printed-circuit board. Can be dry-cell-operated. Uses stock ignition coil and distributor. 4 x 6 x 6 in. Under 2 lb. \$84.75—Sydmur Electronic Specialties


Circle 56 on reader's service card

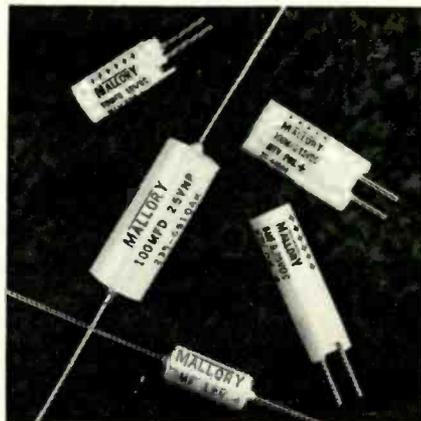

MOLDED-CASE ELECTROLYTIC CAPACITORS. MTA and MTV capacitors. 12 case sizes, axial and vertical lead types. Fully molded in plastic. Voltage, 3-50V dc. Capacitance to 1,000 μ F. \$0.09-0.15 ea. in quantity.—P. R. Mallory & Co., Inc.


Circle 57 on reader's service card

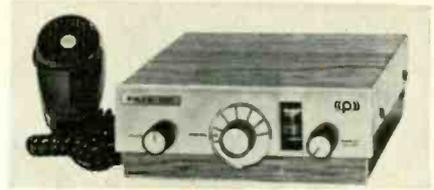6-CHANNEL CB RECEIVER, the *PACE 100*. Solid-state. Built-in S-meter. Double-conversion receiver. Designed for mobile use. 5-W transmitter boosted by automatic speech compression. Communications up to 20 miles. Also features lifetime-guaranteed glass-fiber circuit board, 1-year warranty on all parts, all-silicon transistor design, adjustable squelch con-




trol, automatic deep noise clipping, provision for *Pace Selective Call* system. \$129.95—Pace Communications Corp.

Circle 58 on reader's service card

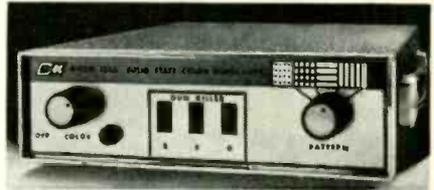

COLOR GENERATOR, model 1242. Solid-state. Features complete stability in all service extremes. Only 2 front-panel controls: amplitude and pattern-selector switch. Also features over 5,000 mV rf output on channels 3 and 4, built-in gun killer with *Miniclips* for easy connection, Zener-diode-regulated transformer power supply. 6 $\frac{1}{2}$ x 9 $\frac{1}{2}$ x 2 in. 2 lb. \$99.95—B & K

Circle 59 on reader's service card

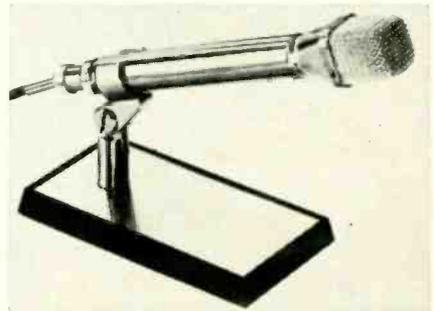

CARDIOID DYNAMIC MIKE, model M0264. For recording, PA. Includes desk stand, 20-ft cable. Response, 100-14,000 Hz. Impedance, 50K. 7 $\frac{1}{2}$ in. long x 1 $\frac{1}{2}$ in. diam.—Olson

Circle 60 on reader's service card



AMPLIFIED STEREO HEADPHONE, the *Amplitwin*. Features a speaker, miniaturized 4-stage solid-state amplifier, battery, on-off switch, volume control, high- and low-level inputs in each ear cup. Operates as a standard headphone when the amplifiers are

switched off. Acoustic response, 16-15,000 Hz. Includes connecting cords, padded storage/carrying case. \$79.50—Telex Corp.


Circle 61 on reader's service card



TAPE CARTRIDGE CLEANER KIT, the Musi-Kleen. Includes cleaning solution and 5 replaceable Kleen-Tape belts. Plastic container. \$5.95.—Audiotex

Circle 62 on reader's service card

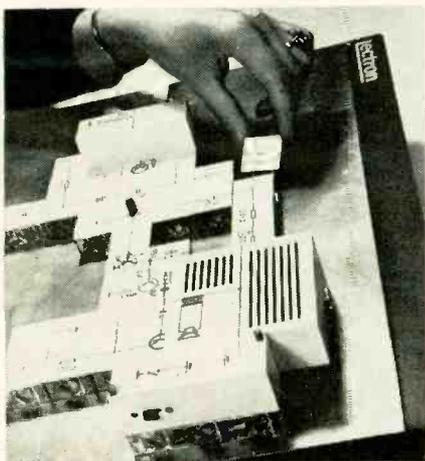Write direct to the manufacturer for information on the item listed below:




ELECTRONIC DOMINOES, a learning aid for electronic theory. More than 90 experiments possible with a single set, including AM radio receivers, electronic thermometer, fire alarm, directional signals, light measurement, tone generation, dusk switch, battery checker, voltage divider, rectifier, amplifier, sound-level meter, flash circuit. Individual units held together by built-in magnets. Each domino contains a circuit element inside a plastic container, with the element symbol imprinted on the top of the element. Instruction book of experiments included.—Macalaster Scientific Corp., Div. of Raytheon, Lexington, Mass. 02173 END

Low-drain Solid-state tone signal needs no amplifier

The Sonalert® Signal makes it a cinch to rig all sorts of alarm circuits for the home, shop, auto or boat. Works with just about any triggering device, operates on 6-28 VDC, draws only 3-14 ma. 110-volt AC model draws only as much current as a neon pilot lamp.

It's completely solid-state. No arcing contacts, no RF noise. Highest reliability. Tone output is either 2800 or 4500 Hz, at 68 to 80 db.

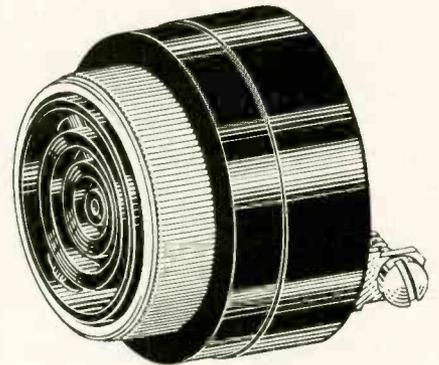Ask your Mallory Distributor for booklet of ideas, circuits, projects. Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Ind. 46206.



MALLORY


Circle 118 on reader's service card

A TIME MACHINE YOU CAN BUILD—It does great tricks with your home-movie camera. Film a flower's growth during a whole day, then watch it leap from seed to blossom in minutes on the screen. This electronic time-compression machine triggers your camera at precise intervals. Read about it in the October RADIO-ELECTRONICS

The new Sony FM Stereo Tuner is highly sensitive. It pulls in the weakest stations sharply and clearly. For all its sensitivity, it is unusually insensitive. An ingenious new cadmium-sulfide CdS bandpass RF attenuator protects weak stations from being blanketed by strong signals. There's so much to recommend the ST-5000W. Double-tuning IF transformers, at all 8 stages of the IF section, reject spurious signals and noise. A 5-gang, high precision, silver-plated tuning capacitor contributes to excellent sensitivity. A

tuning meter pinpoints the center of any channel visually. Another meter helps adjust the antenna for maximum signal pick-up. A stereo switch automatically selects the correct mode—stereo or mono. An indicator light spots stereo programs. An adjustable muting switch suppresses interstation noise. Tune in the ST-5000W at your hi-fi dealer. Suggested list \$399.50. Sony Corp. of America, Dept. H., 47-47 Van Dam St., Long Island City, **SONY**® New York 11101

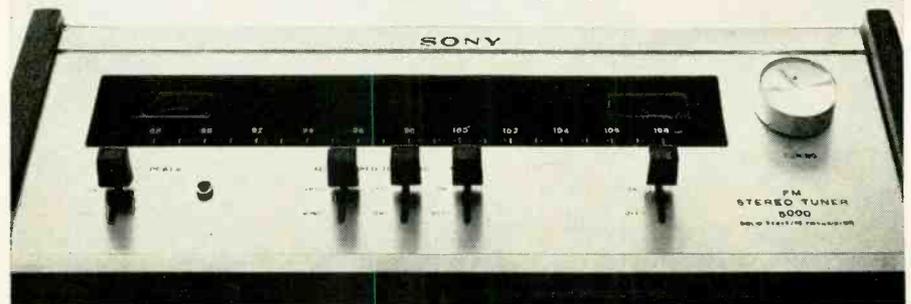Can a sensitive FM Stereo Tuner also be insensitive? Tune in and find out.



Circle 119 on reader's service card

How to Read Schematic Diagrams (2nd Ed.)



by Donald E. Herrington. Enlarged, updated and more valuable than ever. Explains all types of schematics; shows symbols for all circuit components, and explains their functions. Describes how components are connected into circuits and gives symbols for these connections. With this background of understanding, a signal is traced through a typical superhet receiver. Explains in detail variations likely to be encountered in both symbols and designations. Includes review questions at end of each chapter. An invaluable reference for everyone in electronics. 160 pages; 5½ x 8½".

Order 20568, only. \$295

Walkie-Talkie Handbook

by Leo G. Sands. Describes basic types of walkie-talkies (licensed and unlicensed) now on the market. An indispensable guide to the proper selection of a walkie-talkie for prospective buyers. Describes types of applications and circuitry used in various units; covers accessories, specifications, maintenance, and licensing requirements (Part 95 of FCC rules covering the citizens band in which most walkie-talkies operate is included). An extremely practical and helpful book. 176 pages; 5½ x 8½".

Order 20572, only. \$395



new Sams books



Transistorized Amateur Radio Projects

by Charles Caringella, W6NJV. Presents a broad range of transistorized ham radio construction projects for the beginner as well as the advanced amateur. Projects include: electronic c-w keyer, code-practice oscillator, VOX transmitter control, transistor tester, field-strength meter, regulated power supplies, 80- and 40-meter novice c-w transmitter, 2- and 6-meter voice transmitters, and low-noise converters. Provides full information and parts lists for each project; all projects have been designed, built, and carefully tested to insure trouble-free construction and operation. Several projects utilize printed-board construction; negatives are included for etching required boards. 138 pages; 5½ x 8½".

Order 20570, only. \$325

CB Radio Antennas (2nd Ed.)

by David E. Hicks. This updated edition is the most complete book on the subject; explains how to set up a CB antenna system to get maximum "reach" with CB units. A practical guide for those planning to get into CB operation, or for present operators who want to improve the performance of their present setup. Requires no prior knowledge of antenna design and installation. Explains radio wave characteristics as they affect antenna design, communicating ranges to be expected, base- and mobile-antenna installations, how to improve existing antenna systems, and antenna maintenance. 144 pages; 5½ x 8½".

Order 20567, only. \$325

Bridges and Other Null Devices

by Rufus P. Turner. Fills the "information gap" on bridge-type instruments—covering every present significant bridge design. Begins with an explanation of the null principle and basic theory of bridge circuits, then shows how design is applied to specific instruments for widely varying applications. Provides practical "know-how" in the proper use of bridge instruments and helps in the selection and purchase of the right bridge instruments to meet the reader's requirements. 144 pages;

Order 20564, only. \$325

These and over 300 other SAMS Books are available from your local Electronics Parts Distributor . . .

HOWARD W. SAMS & CO., INC.
4300 WEST 62nd ST. • INDIANAPOLIS, INDIANA 46286

Circle 120 on reader's service card

NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here are free for the asking with a Reader's Service number. Turn to the Reader's Service Card facing page 74 and circle the numbers of the items you want. Then detach and mail the card. No postage required!

TEST INSTRUMENT CATALOG, No. 360.

12 pp. Includes Sencore's two new picture-tube checkers, the *CRT Cadet*, model CR13, and the *CRT Champion*, model CR143.—Sencore

Circle 63 on reader's service card

CB ANTENNA AND ACCESSORIES BROCHURES. Illustrations and specs of *CLR* antennas, *Duo-Beams*, roof mounts, fender and cowl mounts, and toppers.—Hy-Gain Electronics Corp.

Circle 64 on reader's service card

COMPONENTS CATALOG. 5 pp. Specs of ceramic disc and tubular capacitors, precision trimmers, film capacitors, and semiconductors.—Erie Technological Products, Inc.

Circle 65 on reader's service card

COMPLETE CATALOG FOR OPTICS, SCIENCE AND MATH. No. 674. 147 illustrated pages. Describes more than 3,800 items.—Edmund Scientific Co.

Circle 66 on reader's service card

TEST EQUIPMENT CATALOG, No. 67D.

8 pp. Describes color-bar generators, CRT testers, oscilloscopes, probes, radio analyzers, signal generators, sweep generators, transistor testers, tube testers, video scanners, vom's, vtvm's.—Hickok Electrical Instrument Co.

Circle 67 on reader's service card

CATALOG OF GOLD LINE UHF CONNECTORS, ADAPTERS, AND SPECIAL ACCESSORIES FOR HAMS AND CB'ERS. Illustrated, 6 pp. Accessories featured include the *Signal Hunter* direction-finding antenna, coaxial switches, automobile alternator and generator filters, a lightning arrester and a *CB Matcher* antenna matching network that insures a VSWR of 1.1:1 for full power.—Gold Line Connector, Inc.

Circle 68 on reader's service card

MICROPHONE CATALOG, SAH-115, A Microphone For Every Purpose. 12 pp. Lists Sonotone's complete line of dynamic and ceramic mikes. Includes microphone parts and accessories.—Sonotone Corp.

Circle 69 on reader's service card

1967 CATALOG. 31 pp. Illustrated. Specs, graphs and descriptions of *MIL-T-27B* military transformers and commercial-industrial transformers.—Microtran Co., Inc.


Circle 70 on reader's service card

NICKEL-CADMIUM BATTERY DATA CATALOG, No. BA-189. 8 pages. Includes commercial nickel-cadmium sealed cells, commercial and military aircraft batteries, special-purpose batteries and nickel-cadmium space battery. Section on *PCA-131* nickel-cadmium battery charger/analyzer. Specs.—Sonotone

Circle 71 on reader's service card

Enjoy the "music-only" programs now available on the FM broadcast band from coast to coast.

- NO COMMERCIALS •
- NO INTERRUPTIONS •

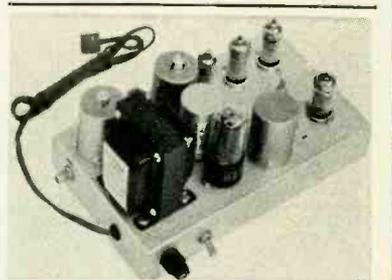

It's easy! Just plug Music Associated's Sub Carrier Detector into multiplex jack of your FM tuner or easily wire into discriminator. Tune through your FM dial and hear programs of continuous commercial-free music you are now missing. The Detector, self-powered and with electronic mute for quieting between selections, permits reception of popular background music programs no longer sent by wire but transmitted as hidden programs on the FM broadcast band from coast to coast. Use with any FM tuner. Size: 5½" x 9". Shipping weight approx. 7 lbs.

KIT \$4950
(with pre-tuned coils, no alignment necessary)

WIRED \$7500 (Covers extra \$4.95 ea.)

Current list of FM broadcast stations with SCA authorization \$1.00

MUSIC ASSOCIATED
65 Glenwood Road, Upper Montclair, N. J.
Phone: (201)-744-3387 07043

Circle 121 on reader's service card

FOR BIGGER PROFITS make

QUIETROLE

your silent partner!



QUIETROLE is the quality lubricant-cleanser that silences noisy radio, TV, (black and white, color too) and instrument controls. Works as silent partner to save time, build added income for you.

Harmless to plastics or metals . . . is non-conductive, non-corrosive, non-flammable. Zero effect on capacity and resistance. Leader for over 20 years.

Get QUIETROLE

- Mark II for tuners
- Spray Pack for controls and switches
- Silitron for general use



manufactured by

QUIETROLE COMPANY
Spartanburg, South Carolina

Circle 122 on reader's service card

UNDERSTANDING SOLID-STATE TALK

continued from page 49

emitter action in unipolar FET's, since the gates are reverse-biased and serve only to set up a transverse electric field in the channel.) And the term JFET (*junction field-effect transistor*) may be found in some data.

Higher input impedance than that afforded by the conventional FET is pro-

HI-FI 1968: What's available to audio lovers tomorrow? There's a real assortment to choose from, and innovations abound. Read about what you can do with systems and components, speakers and cartridges, in the October issue of **RADIO-ELECTRONICS**

LIFE INSURANCE ISSUED BY MAIL • KEEP IT FOR LIFE MAIL THIS AD NO OBLIGATION APPLICATION MAILED TO YOU

\$5000 ENTRY AGES 21 to 70 • \$2000 ENTRY AGES 21 to 80
Whole Life Policy pays world-wide for death from any cause, any time, except during first policy year for either suicide or death from undisclosed pre-existing health conditions. Mail your name, address, zip code, year of birth and ad to Great Lakes Insurance Co., Elgin, Ill. 60120 Dept. JD125J6



HOW TO
TEST...
ALMOST
EVERYTHING
ELECTRONIC

By
JACK
DARR

The title tells the story. Increase and improve your testing ability with your own test equipment plus a few easily and inexpensively made devices. Darr covers almost every technique for nearly every piece of electronic equipment in an easy, breezy fashion. A very readable, clearly illustrated text. 160 pages. G/L #132. Softbound \$2.95.

At your
Gernsback Library dealer

vided by the device shown in Fig. 8. Separate N regions are diffused (for source and drain electrodes) into a P-type substrate. An oxide layer is formed on the top face of the substrate, and a metallic gate electrode is deposited on top of the oxide. From its configuration, this type of field-effect device is termed *metal-oxide semiconductor* (MOS), *metal-oxide-semiconductor transistor* (MOST), or *metal-oxide-semiconductor field-effect transistor* (MOSFET). It is also sometimes called an *insulated-gate field-effect transistor* (IGFET) from the fact that the oxide layer insulates the gate electrode from the substrate.

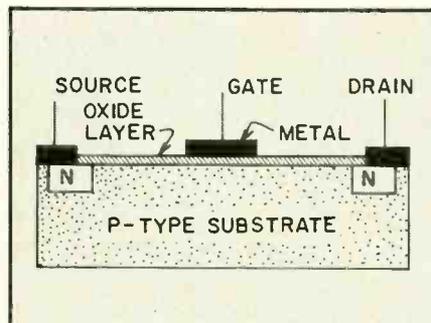


Fig. 8—The basic insulated-gate FET.

The extremely high input impedance of the MOST results from its almost zero leakage current from the gate, because of the oxide insulation. The dc stability of the MOST is less than that of the FET, possibly also because of the oxide layer, but the MOST is a good rf device.

Other acronyms

One of the newest solid-state acronyms is RGT—for *Resonant Gate Transistor*. The heart of each RGT is a tiny solid-gold tuning fork, which makes it possible to tune IC's without bulky coils. A silicon wafer the size of a quarter holds 500 RGT's.

In addition to acronyms and abbreviations which describe the transistors themselves, another one seen on transistor and diode data sheets is JEDEC. This one stands for *Joint Electronic Device Engineering Council*, and its presence means that the component has been registered by that group and given an identifying number.

Outside of the transistor-diode corner of the electronics world, there are of course many other acronyms—MASER, LASER, RADAR, SONAR, SOFAR, and many more—but that is another story. . . .

END

COMPLETE TUNER OVERHAUL

9⁹⁵

ALL LABOR AND PARTS
(EXCEPT TUBES & TRANSISTORS)*

VHF

UHF

COLOR

U-V

TRANSISTOR

COLOR TUNERS **GUARANTEED COLOR ALIGNMENT — NO ADDITIONAL CHARGE**

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.
UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.
Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)
And remember—for over a decade Castle has been the leader in this specialized field . . . your assurance of the best in TV tuner overhauling.

CASTLE

TV TUNER SERVICE, INC.

5715 N. Western Ave., Chicago 45, Illinois
41-96 Vernon Blvd., Long Island City 1, N. Y.

For service in Canada write to Chicago or use reader service card in this magazine.
*Major parts are charged extra in Canada.

Circle 123 on reader's service card

Olson®

FREE

Fill in coupon for a FREE One Year Subscription to OLSON ELECTRONICS' Fantastic Value Packed Catalog—Unheard of LOW, LOW PRICES on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.

NAME _____
ADDRESS _____
CITY _____ STATE _____
GIVE ZIP CODE _____

If you have a friend interested in electronics send his name and address for a FREE subscription also.

OLSON ELECTRONICS, INC.

702 S. Forge Street Akron, Ohio 44308

Circle 124 on reader's service card

INTEGRATED CIRCUIT AND MICRO-DEVICE SALE

IC's TO-5 or all TO-46 Case, Gates, Flipflops, etc. with 8 hole test socket, 100 asstd. \$10.95
 IC's Flat Packs, as above, 100 asstd. \$12.50
 All IC's sample test over 50% good. Schematics, identification & test info. included.
 Hi-Gain (Darlington) Amplifier, TO-18, 4 lead Similar 2N998, Tested 6 for \$2.95
 Field Effect Trans. (FET) P channel Similar 2N3277, TO-5, 4 lead, tested 3 for \$2.95
 Chopper, NPN Hi-Speed, dual emitter TO-18 Similar 3N87, tested 6 for \$2.95
 Dual Trans. 6 lead, choice TO-18, NPN or TO-5 PNP or NPN, Diff. Amplif. Choppers. dual switches Similar 2N2980, 3726, 2060. Tested .. 6 for \$2.95
 Microclareed Relay $\frac{3}{8}$ " sq. x $1\frac{1}{4}$ " Ax. leads. Norm. open 3000 ohm. Pick on 6V 3ma. 4 for \$2.95
 Memory Plane 5" x 8" with 4000 wired toroid bits. \$9.75. Complete 8 plane unit \$75.00
 Ultra-Tiny "Steeltab" Transistors, .060" sq. HF Amplif. & Osc. or Univ. Amplif. & Switch. Elect. similar 2N913, 915, 916. choice ... 6 for \$2.95
 Same Steeltab Diodes similar FD100 12 for \$2.95
 Above steeltabs Bubblepak indiv. cards.
GRAND MIX Over 1000 3, 4, 6, 8, 10 lead TO-5, TO-18, TO-46, mostly Transistors, but include Darl. IC's, FETs and diodes. sample Test 50% to 90% good \$19.50

Free Goody Bag with \$10 order,
 Canadian order \$10 minimum.
 Calif. orders 4% sales tax.

Postage please for Amazing Free Catalog.

MIKE QUINN ELECTRONICS


Bldg. 727 Langley Street
 Oakland Airport, Calif. 94614

Circle 125 on reader's service card

TUNAVERTER

POLICE-FIRE-AIRCRAFT CALLS

—TUNABILITY — USABILITY — QUALITY —

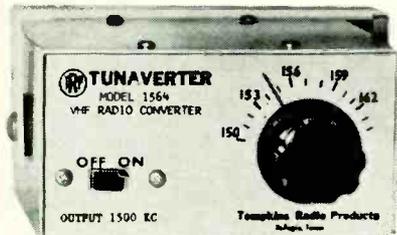

TUNABLE, CALIBRATED solid state converters to change your auto and home radios into excellent, sensitive, selective, calibrated and VHF receivers!

"Your little converters are absolutely tremendous! I would recommend them to anyone."

Paul English, Canada

- 6-1 reduction tuning!
- HF—2 gang tuning!
- VHF—3 gang tuning!
- FREE 24" conn. coax!
- Plug into auto radio!
- American Made!
- 9 volt btry powered!
- Size 2 1/4 x 3 1/2 x 4 1/2"

• 2 WEEK MONEY BACK GUARANTEE!

Models for AM & FM		BAND	MODEL	COVERS	OUTPUT	PRICE
Marine	Marine	2.3-3.0 mc	550 kc	\$19.95 ppd		
SW & WWV	SWL	9.3-10 mc	550 kc	\$19.95 ppd		
CB & 10 M	273	26.9-30 mc	1500 kc	\$29.95 ppd		
6 meters	504	50-54 mc	1500 kc	\$29.95 ppd		
2 meters	1450	144-150 mc	1500 kc	\$29.95 ppd		
Police, fire, & Marine	}	308	30-38 mc	1500 kc	\$29.95 ppd	
		375	37-50 mc	1500 kc	\$29.95 ppd	
		1564	150-164 mc	1500 kc	\$29.95 ppd	
Aircraft	1828	118-128 mc	1500 kc	\$29.95 ppd		
Radiation loop for use with home radios					\$1.25 ppd	
Fast AIR MAIL add \$.85 ea.						

Order from:

HERBERT SALCH & CO. Marketing Division of Tompkins Radio Products
 Woodsboro RE9, Texas 78393

Dealers invited

Circle 126 on reader's service card

ANTENNA REPORT

continued from page 50


pelator for set attachment between vhf and uhf lugs" (quoted from slip of paper found with the device). As shown in the photo, the "impelator" appeared to be a plaster disc with two short pieces of 300-ohm lead coming from each side of it. When we broke the plaster, we discovered that the 300-ohm line was a single intact piece, with no components of any kind attached. There was no apparent purpose for the plaster, and the line apparently served merely as a jumper.

To summarize: Despite advertising claims, the SkyProbe antenna is *not* solid-state; it contains no transistors or diodes. Inside the plastic sheath we found nothing but wire, plastic foam and cardboard. The SkyProbe seems to work about as well as ordinary rabbit ears—except that it is not essentially directional, and thus cannot null out ghosts. (We oriented our reference rabbit-ears for best pictures.) Furthermore, the SkyProbe does not appear to perform as well as an outdoor directional antenna.

The SkyProbe sold in New York City for \$12.99. In Cincinnati the price was \$8.57. Each figure is several times the price of rabbit ears, which we found comparable in performance.

—Thomas R. Haskett.

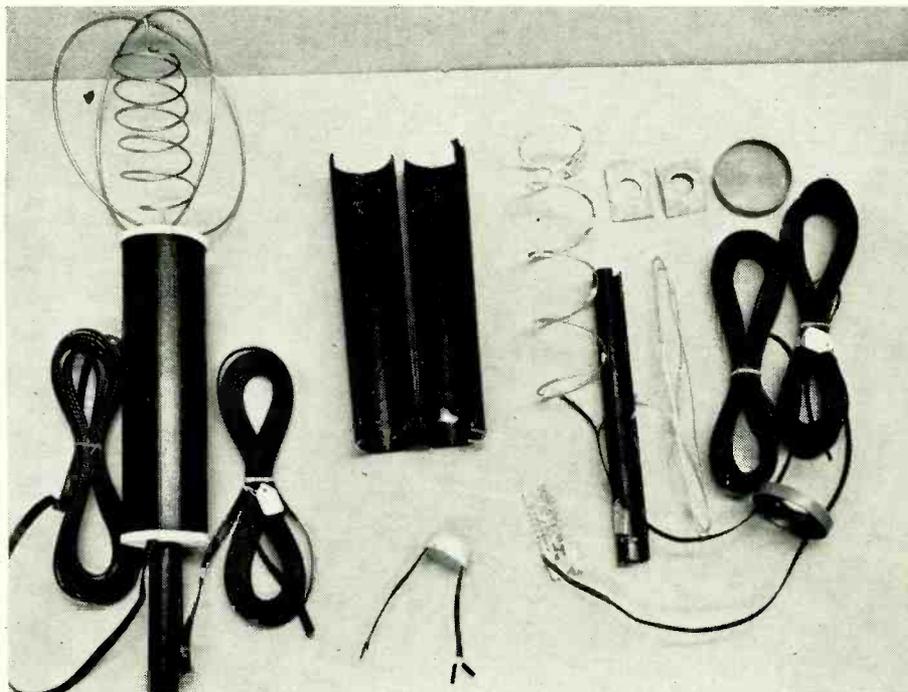[As we were preparing the above report, we received the following letter and photos.—Editor]



Reader Sellars bought D-19A SkyProbe (assembled left) and D-19 (disassembled right).

Dear Editor:

In your July 1967 News Briefs you told of a demonstration of a new antenna, the *Americus SkyProbe*, developed by John M. Eagle of UniScience Laboratories, Inc.

Being very much interested in new antenna developments, especially the new Air Force Subminiature Integrated Antenna (SIA, which was also mentioned in the July News Briefs), in our broadcast and CATV activities, we ordered an *Americus SkyProbe* antenna from UniScience Laboratories. We received three antennas: *SkyProbe* model D-19, *SkyProbe* model D-19A, and a *MiniProbe* (advertised for local reception only). The accompanying photo shows, on the left, the assembled D-19A with the fancy hardware on one end. Our costs for these antennas (presumably net prices) were \$5.99, \$7.47 and \$3.50, respectively.

A cursory test of these antennas was all it took to convince us that the most elaborate of the three was almost as effective as a set of rabbit-ears. Most, if not all, reception came from the lead-in wire rather than the antenna.

An Abraham & Straus advertisement in *The New York Times* of Sunday, May 7, 1967, intrigued us. It described the *SkyProbe* model D-19, priced at \$12.99, and said: "This solid-state outdoor antenna is only 18", yet gives amazing black and white, color and AM/FM reception. It's a brand new concept that utilizes basic radar techniques to give you clear, sharp reception." (Emphasis added.) We decided to dis-

FREE LAFAYETTE 1968 CATALOG



Mail
This Card
Today

Over
500
Pages

Featuring Everything
in Electronics for
• HOME
• INDUSTRY
• LABORATORY
from the "World's Hi-Fi
& Electronics Center"

Use
LAFAYETTE'S
Easy-Pay
Budget Plan
NO MONEY DOWN...
Up to
24 Months to Pay

Satisfaction
guaranteed
or Money Refunded

DO A
FRIEND
A FAVOR—
give him this
card to send
for his
FREE
LAFAYETTE
CATALOG

STORE LOCATIONS

NEW YORK	NEW JERSEY	MASSACHUSETTS	PENNSYLVANIA	CONNECTICUT
Bronx Brooklyn Jamaica	Manhattan Scarsdale Syosset	Newark Paramus Plainfield	Saugus Boston Natick	King of Prussia Philadelphia Pittsburg
Hamden W. Hartford		WASHINGTON, D.C. Area: Falls Church, Va. Mt. Rainier, Md.		

LAFAYETTE Radio ELECTRONICS
Dept. JI-7 P.O. Box 10
Syosset, L.I., N.Y. 11791

Send me the Free 1968 Lafayette Catalog 680

Name _____

Address _____

City _____ State _____ Zip _____

(Please Give Your Zip Code No.)



Mail This
Card Today
For Your
FREE!

1968 Lafayette Catalog 680

Name _____

Address _____

City _____

State _____

Zip _____

(Please Give Your Zip Code No.)

Dept. JI-7

PLACE
STAMP
HERE

LAFAYETTE
RADIO ELECTRONICS

P.O. BOX 10
SYOSSET, L.I., N.Y. 11791

Mail
the Coupon
Today for Your
FREE 1968
Lafayette
Catalog 680

Mail The Card Today for Your

FREE!

LAFAYETTE 1968 Catalog 680



Over
500
Pages



Shop At the
"World's Hi-Fi &
Electronics Center"
For Widest Selection,
Low Prices

Stereo Hi-Fi • Citizens Band •
Ham Gear • Tape Recorders •
Test Equipment • TV and Radio
• Phonographs, Accessories •
Intercoms and PA • Closed Circuit
TV • Tubes and Parts • Cameras
• Auto Accessories • Musical
Instruments • Tools • Books

Featuring

Everything in Electronics for
• HOME • INDUSTRY • LABORATORY

LAFAYETTE

RADIO ELECTRONICS

P.O. BOX 10

SYOSSET, L.I., N.Y. 11791

PLACE
STAMP
HERE

Dept. JI-7

Name

Address

City

State

Zip

FREE!



Mail This Card Today For Your

FREE!

1968 Lafayette Catalog 680

NOW - REVOLUTIONARY NEW



New! Solid State "IC"
Stereo Receivers



Electronic Miracle
of the Space Age



New! Solid State "IC"
2-Way Radios



New! Solid State Stereo Tape
Recorders



New! Criterion Speaker Systems



New! Dyna Com Series
Super Walkie-Talkies



New! Musical Instruments and
Accessories

Do A Friend A Favor...

Have a friend interested in hi-fi or electronics? Send us his name and address and we will send him his own personal copy of the 1968 Lafayette Catalog 680.


FREE

Mail The Card Today

assemble the D-19 to see what was inside. The photo shows the results.

There was no evidence of any transistors, diodes or anything else which could be called "solid-state" devices. We found nothing resembling any "basic radar techniques" except for the wire itself which, I guess, is basic to any radar unit.

The crowning blow of all, however, was the small, round device with two short lead-in wires in the lower center of the photograph. It was described as the "fantastic new Americus Impelator to replace all other jumper systems." It is to be used to connect the uhf to the vhf antenna terminals on the receiver so that one antenna could serve both terminals. Normally such a device would be a matching transformer. After the photograph was made we broke the device open. The last photograph shows the results. It proved to be a solid piece of epoxy material with *one piece* of lead-in wire running into it and directly back out—nothing else! Indeed, it was "fantastic"!

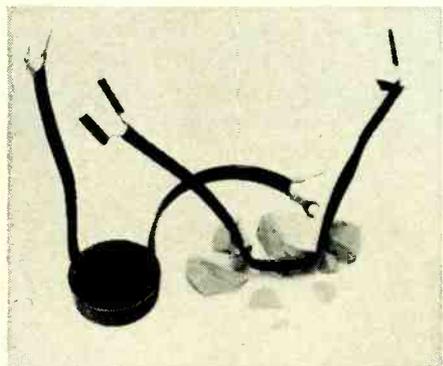

The "Impelator" purchased by reader Sellars turned out to be an antenna-terminal jumper—just as R-E's did.

My reason for writing this letter is not to take you or your fine magazine to task. I felt that you would want to have the results of our investigation and to know that this antenna is in no way related to the SIA. It is merely a hunk of junk worth perhaps \$1.00 at the most. In my opinion UniScience is perpetrating a hoax and cheating the unsuspecting public.


By means of copies of this letter and photographs I am also informing the National and two local Better Business Bureaus as well as the Federal Trade Commission, and two consumer magazines so they may take whatever action they deem appropriate.

LACY S. SELLARS

Jefferson Standard Broadcasting Co.
Charlotte, N. C.

END

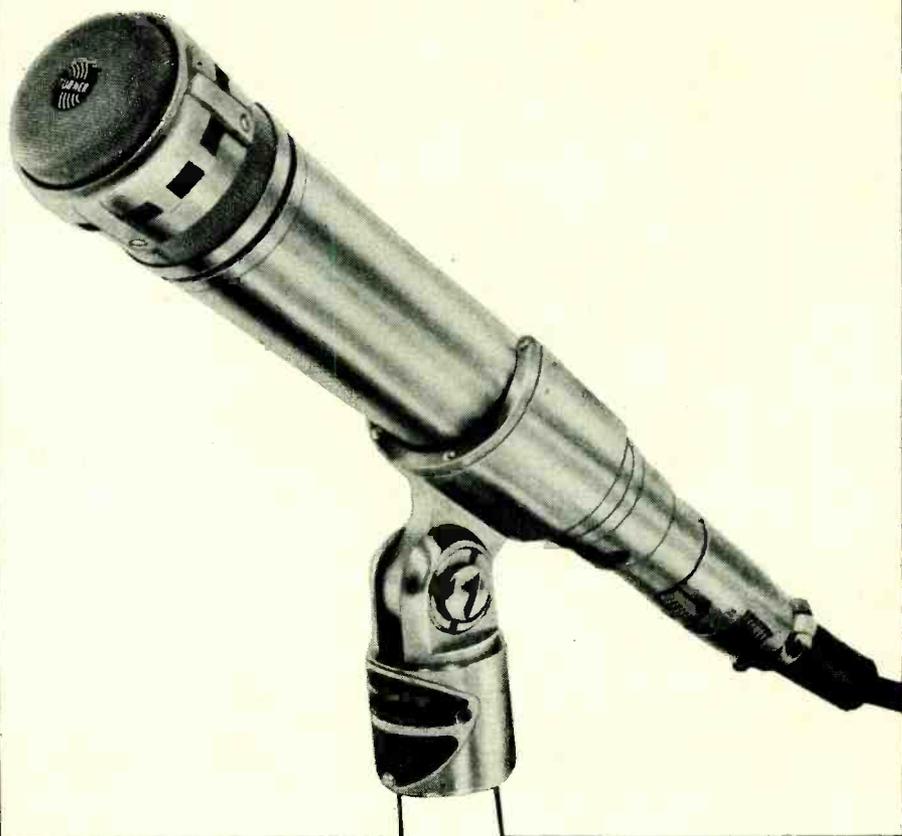
**For home recording,
stereo taping,
public address work...**



**Eliminate
background
noise, feedback,
with the
TURNER 500
Cardioid.** Model 500 List Price \$84.00

The Turner Microphone Company—Cedar Rapids, Iowa

Circle 110 on reader's service card

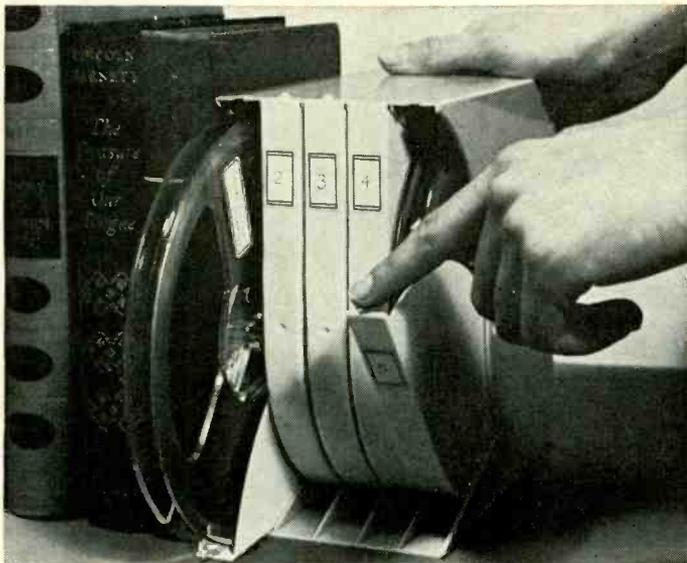

A clever tape file

Stores 5 reels in one sturdy plastic case with swing-out compartments. Protects these valuable tapes, keeps them handy, indexed and orderly. Stacks horizontally or vertically, comes in three sizes (for 3-, 5-, 7-inch reels). Handsome two-tone beige. (A neat 8-mm film file too!)

3"	\$2.99
5"	\$4.45
7"	\$4.95
(all prices less reels)	



Available through your local distributor, or write to:

RYE INDUSTRIES INC.

123 Spencer Place, Mamaroneck, N.Y. 10543

Circle 128 on reader's service card

FREE!

**BIGGER... BETTER
THAN EVER!**



**40th ANNIVERSARY
1967 CATALOG**



**YOUR BUYING GUIDE
FOR:**

- Stereo & Hi-Fi Systems & Components.
- Tape Recorders.
- Electronics Parts, Tubes, Tools.
- Phonos & Records.
- Ham Gear.
- Test Instruments & Kits.
- Cameras & Film.
- P.A. • Citizens Band.
- Radio & TV Sets.
- Musical Instruments.

**SEND FOR
YOURS TODAY!**

BURSTEIN-APPLEBEE CO.

Dept. RE1, 1012 McGee, Kansas City, Mo. 64106
 Rush me the FREE 1967 B-A Catalog.

Name.....

Address.....

City.....State.....Zip Code.....

Circle 129 on reader's service card

Build This Transistor Characteristic Plotter

continued from page 47

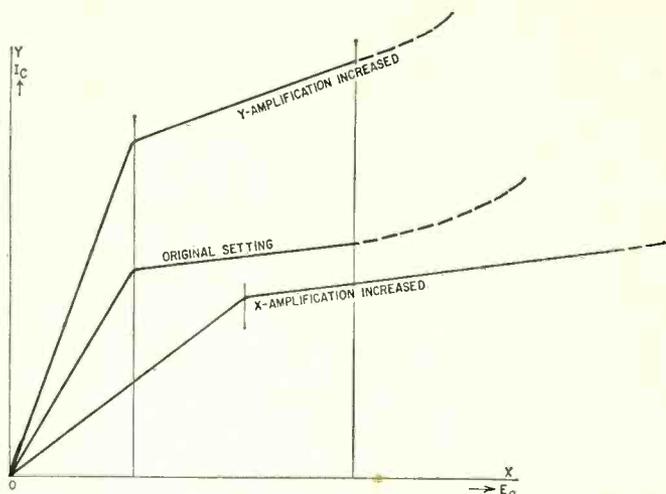


Fig. 9—The scope amplification affects the slope of the curves.

curves from six different bias values.

Put S4 in OPERATE position. Adjust pots R6 through R11 for 6 different bias values. Turn the rotating magnet with a screwdriver and observe the scope. Each time the magnet closes a reed switch, the bias will change and another curve will appear on the screen (compare with Fig. 8). If all switches are correctly operating and the bias values are set correspondingly higher, six different characteristics will appear on the screen at almost equal distances from each other.

Throw S3 to OPERATE and close S2. The motor will start to rotate, and the set of six curves should appear simultaneously on the screen.

Again you may find a few malfunctions. A single missing curve is probably the result of reed-switch failure or improper operation. Readjust the failing switch.

If a curve jumps on the screen, one switch is probably closing before the preceding switch has opened. Readjust the incorrect switches by observing action while slowly turning the magnet by hand.

If the curves have different values of intensity or brightness, the closing times of the reed switches are unequal. Try centering the axis of the rotating magnet with respect to the reed switches. Check reed switch adjustments.

If only five characteristics are visible, the sixth is probably lost in the bottom of the trace. This indicates that bias on R11 is lower than threshold voltage. Increase bias by readjusting R11 and R5 or both. Readjust the vertical amplifier of the scope if necessary.

Excessive flicking of the display indicates that transfer time is too long or the motor speed is too slow. The remedy is to reduce transfer time by decreasing the gap between the rotating magnet and the reed switches and by readjusting the reed switches. Be sure the motor speed is not less than 600 rpm.

Calibration

Displaying a family of characteristic curves is an excellent way to match and compare transistors. However, the advantage of plotting characteristics can best be realized by calibrating the scope screen in terms of transistor parameters. What you need is a grid which will fit over the CRT face, so you can read values of voltage and current through the transistor.

Here's a simple method of calibration: Obtain a sheet of clear plastic as large as the CRT face. Draw on the sheet 25

to 50 horizontal and vertical parallel lines at equal distances from each other. Display a set of transistor characteristics on the screen. Adjust centering so the curve origin starts at a lower-left grid intersection (if pnp transistor—put the origin in the upper right-hand corner for npn).

Don't touch the scope gain controls, but disconnect horizontal and vertical inputs from the plotter and center the trace. Inject an undistorted ac signal into the horizontal and then into the vertical amplifier in turn. (In each case the unused input must be grounded.) Adjust the input-signal amplitude (not scope gain) until the trace fills about three-quarters of the screen both horizontally and vertically.

Measure the rms values of the two injected voltages. Multiply these rms voltages by 2.28 to find the peak-to-peak values. The beam deflections are proportional. For easier grid reading, change the input voltages so the distances between the parallel grid lines correspond to convenient voltage values (for instance, 0.1 volt, 50 mV, etc.)

Record these voltages for later reference.

Since the vertical deflections have to be calibrated in current, not voltage, each voltage value must be divided by 200 (the value of R4) to obtain the corresponding value of current. (Assume that 10 vertical divisions correspond to 1 volt p-p. That's equal to 0.355 volt rms. Each vertical division is then 0.1 volt divided by 200, or 0.5 mA of current.)

Display the set of curves again, with origin at the same intersection as before. Readjust, if necessary, the sweep voltage with R1, to fit the family of curves well into the screen area.

Connect a microammeter (250–500 μ A full scale) to jacks J1 and J2. Stop the motor by throwing switch S2 to OFF. Turn the rotating magnet by hand until it faces reed switch S7-a. Push S6 and read bias current. Adjust pot R6 for a convenient bias-current reading. The curve should be near the original position on the screen.

Repeat this bias setting for each curve in turn. Place the magnet in positions facing reed switches S7-b to S7-f, and adjust the pots R7 to R11 for equal increases in bias currents (for instance 480, 400, 320, 240, 160 and 80 steps of 80 μ A each). Record these settings for later reference.

The preceding calibration method is useful for many transistors, if you adapt the array to the characteristics of each transistor. Do this by adjusting the sweep voltage only (R1). Under these conditions, as long as the vertical and horizontal gain and bias settings are not changed, the calibration remains valid.



Any change in gain or bias current requires new calibration.

After you've finished calibrating the instrument, mount the front panel and PC board in the cabinet. Pot R5 is the only front-panel control affecting calibration. Because of this, it's advisable to provide a dial with exact graduation. This permits precise recalibration (Fig. 4). The positions of all other switches and controls should be well designated.

Don't forget to make notes of scope gain-control settings, since they affect the calibration. In any case you can check for correct calibration by taking voltmeter readings at the scope inputs and microammeter readings on jacks J1 and J2 (after pressing the pushbutton). END

PRACTICAL HINTS FOR CB SERVICE are yours in an article on CB talk troubles. Without proper modulation, a CB transceiver is useless. Keep your customers happy with correctly adjusted talk power, and keep your cash register full.

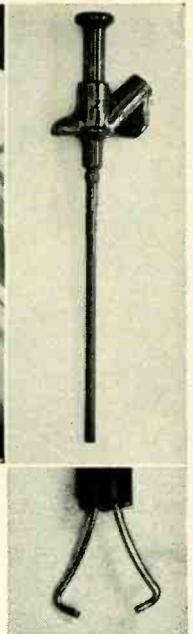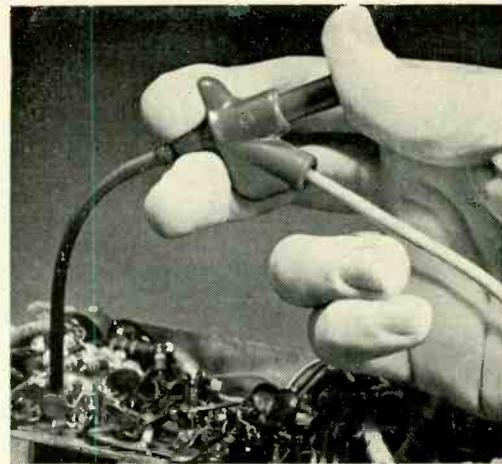TOUGH DOGS—the benchman's nemesis—can be solved if you're willing to take them on fearlessly. Find out about some peculiar radio and TV receiver troubles, and how they were corrected. Read both these up-to-the-minute servicing articles in the October issue.



Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this  Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?



Available through your local distributor, or write to:

RYE INDUSTRIES INC.

123 Spencer Place, Mamaroneck, N.Y. 10543

Circle 130 on reader's service card

\$147

GAS WELDING TORCH



Uses **OXYGEN** and **LP GAS**

- Completely self-contained.
- Produces 5000° pin-point flame.
- Welds, brazes, solders.
- Hundreds of lightweight uses.
- Suggested list — \$19.95.

GET COMPLETE DETAILS AT MOST INDUSTRIAL DISTRIBUTORS, OR WRITE TO MICROFLAME, INC.



MICROFLAME, INC.

7800 COMPUTER AVENUE
MINNEAPOLIS, MINNESOTA 55424

Circle 131 on reader's service card

Assure 100% COMPLETE ERASURE of Recorded Tape ON THE REEL



Use the **Magneraser**[®]

— the Original and still the best!

Quickly erases a reel of magnetic tape or sound film of any size or type. Erasure is 100% complete even on severely overloaded tape. Lowers background noise level of unused tape 3 to 6 db. Also demagnetizes record-playback and erase heads. Only \$24.00. Two-Year Guarantee. Available at your dealer's or write us.

New ULTRA-SENSITIVE FLUTTER METER



With built-in Three-Range Filter, 3 kc Test Oscillator, High Gain Pre-amplifier and Limiter. Filter Ranges: 0.5 to 6 cps; 0.5 to 250 cps; 5 to 250 cps.

Designed for rapid visual indication of flutter and wow. Meets standards set by the IEEE . . . Condensed Specs.: Input Voltage, 0.001 to 300 Volts; Ranges, 0.01 to 3%; Limiter Range, 20 db.; Oscillator (built-in), 3000 cycles; Net Price, \$495.00 Write for complete specifications and free 12-page booklet on Flutter.

AMPLIFIER CORP. of AMERICA
75 Frost St., Westbury, N. Y. 11590 • (516) 333-9100

Circle 132 on reader's service card


NEW SEMICONDUCTORS, MICROCIRCUITS & TUBES

TWO NEW TUBES FOR 2-WAY RADIO

The Amperex 8603 is a beam power tetrode specifically designed to have the lowest possible IM distortion when used as a linear rf power amplifier in SSB transceivers and mobile marine and aircraft equipment operating up to 75 MHz. It can deliver 43 watts PEP with third-order IM distortion better than 40 dB down under CCS operation. Under ICAS, 56 watts output may be obtained with slightly higher distortion.

The 8647 is designed for use as an rf power amplifier, oscillator and frequency multiplier up to 250 MHz and is recommended for class-C FM service. At 175 MHz typical CCS, ICAS and PTTS (1 minute on, 4 minutes off) ratings are 33, 40 and 49 watts, respectively. These outputs can be obtained with about 2.5 watts of rf drive power.

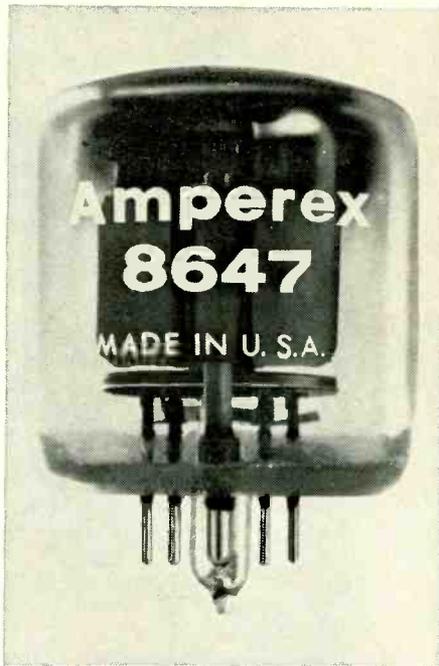Designed for use in transistorized mobile equipment, both these Amperex



\$1000 REWARD

TO ANYONE—Who can show us an Established Competitor who could sell & deliver all the items on this list at the prices & in the quantities that we do! HOW DO WE DO IT?

Our TREMENDOUS BUYING POWER & PURCHASING EXPERIENCE make it possible. We invest Thousands of Dollars (in just a single item) to create a good DOLLAR BUY, resulting in the AMAZING & EXCITING OFFERS that follow:

- | | | | |
|---|---|---|---|
| <input type="checkbox"/> \$35 POWER SUPPLY input 110v output 12v, 1 amp (filtered D.C.) for Trans. TV, Radio or Amplifier | <input type="checkbox"/> 4 — TV ALIGNMENT TOOLS most useful assortment | <input type="checkbox"/> RCA 110° FLYBACK TRANSFORMER | <input type="checkbox"/> UNIVERSAL 4" PM SPEAKER Alnico 5 magnet, quality tone |
| <input type="checkbox"/> 1 — LB SPOOL ROSIN-CORE SOLDER 40/60 top quality | <input type="checkbox"/> 7 — ASST. TV ELECTROLYTIC CONDENSERS popular selection | <input type="checkbox"/> We scooped the Market Latest type — standard for all 110° TV's RCA's design of large Coil produces 18KV— assuring adequate width Incl Schematic Diagram application for any TV List price \$13.90 Your price .. \$3 10% off in lots of 3 | <input type="checkbox"/> 100 — ASST. RADIO KNOBS all selected popular types |
| <input type="checkbox"/> 2—G.E. PIECES OF EQUIPMENT stacked with over 200 useful parts | <input type="checkbox"/> \$15.00 TELEVISION PARTS "JACKPOT" best buy ever | <input type="checkbox"/> 110° TV DEFLECTION YOKE for all type TV's incl schematic same as Thordarson Y502 list \$20 | <input type="checkbox"/> 40 — ASSORTED TV KNOBS all standard types, \$20 value |
| <input type="checkbox"/> 3—50' SPOOLS HOOK-UP WIRE assorted colors | <input type="checkbox"/> BONANZA "JACKPOT" not gold, not oil, but a wealth of Electronic Items—Money-Back-guarantee | <input type="checkbox"/> "COMBINATION SPECIAL" RCA 110° FLYBACK plus 110° DEFLECTION YOKE | <input type="checkbox"/> 10—ASSORTED DIODE CRYSTALS 1N34, 1N48, 1N60, 1N64, 1N82 |
| <input type="checkbox"/> 50 — ASSORTED MYLAR CONDENSERS popular selected types | <input type="checkbox"/> 10 SETS — DELUXE PLUGS & JACKS asst. for many purposes | <input type="checkbox"/> 90° FLYBACK TRANSFORMER for all type TV's incl schematic | <input type="checkbox"/> 10—STANDARD TRANSISTORS NPN & PNP 2N404, 2N414, etc. |
| <input type="checkbox"/> 100 — MIXED DEAL "JACKPOT" Condensers, Resistors, Surprises | <input type="checkbox"/> 10 — SETS PHONO PLUGS & PIN JACKS RCA type | <input type="checkbox"/> 70° FLYBACK TRANSFORMER for all type TV's incl schematic | <input type="checkbox"/> 5 — TOP HAT SILICON RECTIFIERS 500ma-400v — big value |
| <input type="checkbox"/> 10—ASSORTED SLIDE SWITCHES SPST, SPDT, DPDT, etc. | <input type="checkbox"/> 10 — SURE-GRIP ALLIGATOR CLIPS 2" plated | <input type="checkbox"/> 70° TV DEFLECTION YOKE for all type TV's incl schematic | <input type="checkbox"/> BSR #UA-25 STEREO RECORD CHANGER complete w/ cartridge latest deluxe nothing better made |
| <input type="checkbox"/> 20 — EXPERIMENTER'S COIL "JACKPOT" assorted for 101 uses | <input type="checkbox"/> 50 — RADIO & TV SOCKETS all type 7 pin, 8 pin, 9 pin, etc. | <input type="checkbox"/> 20—ASSORTED TV COILS I.F. video, sound, ratio, etc. | <input type="checkbox"/> BSR MONAURAL CARTRIDGE Universal dual flipover sapphire |
| <input type="checkbox"/> 20—ASST. PILOT LIGHTS #44, 46, 47, 51, etc. | <input type="checkbox"/> 50 — ASSORTED #3AG FUSES popular ampere ratings | | <input type="checkbox"/> BSR STEREO CARTRIDGE Universal dual flipover sapphire |
| <input type="checkbox"/> 50 — ASST. DISC CERAMIC CONDENSERS popular numbers | <input type="checkbox"/> 100 — STRIPS ASSORTED SPAGHETTI handy sizes | | <input type="checkbox"/> ASTATIC #13T STEREO CARTRIDGE plug-in, power point |
| <input type="checkbox"/> 10 — ASST. RADIO ELECTROLYTIC CONDENSERS | <input type="checkbox"/> 100—ASSORTED RUBBER GROMMETS best sizes | | <input type="checkbox"/> 3—SAPPHIRE STYLUS NEEDLES Ronette type for most cartridges |
| <input type="checkbox"/> 20 — STANDARD TUBULAR CONDENSERS .047-600v | <input type="checkbox"/> 50—ASSORTED PRINTED CIRCUIT SOCKETS best types | | <input type="checkbox"/> 3—STANDARD SAPPHIRE NEEDLES for all thumbscrew cartridges |
| <input type="checkbox"/> 3—½ MEG VOLUME CONTROLS with switch, 3" shaft | <input type="checkbox"/> 10—ASSORTED VOLUME CONTROLS less switch | | <input type="checkbox"/> 10 — G.E. SAPPHIRE NEEDLES 4G, VR-11, etc. (\$25.00 value) |
| | <input type="checkbox"/> 7—ASSORTED VOLUME CONTROLS with switch | | |

FREE \$1 BUY WITH EVERY 10 YOU ORDER

Only applies to "\$1" Buys

FREE GIFT WITH EVERY ORDER

IMMEDIATE DELIVERY . . . Scientific light packing for safe delivery at minimum cost. HANDY WAY TO ORDER: Pencil mark or write amounts wanted in each box, place letter F in box for Free \$1 BUY. Enclose with check or money order, add extra for shipping. Tearsheets will be returned as packing slips in your order, plus lists of new offers.

Name

Address

Cost of goods

Shipping

estimated

TOTAL

Please specify refund on shipping overpayment desired: CHECK POSTAGE STAMPS MERCHANDISE (our choice) with advantage to customer

BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N. Y. 10024

TELEPHONE 212-374 5600

tubes feature zirconium-coated molybdenum anodes and instant-heating cathodes. The tubes have a special base in which the anode pin is brought out separately from the normal pin circle to simplify under-chassis input and output circuit shielding.

LOW-COST PLASTIC FET'S

The MPF103, -104 and -105 make up a series of three new Motorola n-channel junction field-effect transis-

tors for general-purpose audio and switching applications. The low price—50 cents each in 1,000 up quantities—is expected to lead to their wide acceptance in operational amplifiers and in the input stages of audio amplifiers and other consumer and industrial products where high input impedance is desirable.

Major characteristics:

Characteristics	MPF 103	MPF 104	MPF 105
Forward transfer admittance (μ mhos)	3,000	4,000	4,500
Max gate-source cutoff volts (dc)	-6	-7	-8
Zero-gate-voltage drain current (mA)	1-5	2-9	4-16
Min gate-source breakdown volts	-25	-25	-25
Max input cap (pF)	7	7	7
Max output admittance (μ mhos)	50	50	50
Max reverse transfer cap (pF)	3	3	3

END



Why Do You Read So Slowly?

A noted publisher in Chicago reports there is a simple technique of rapid reading which should enable you to double your reading speed and yet retain much more. Most people do not realize how much they could increase their pleasure, success and income by reading faster and more accurately.


According to the publisher, anyone, regardless of his present reading skill, can use this simple technique to improve his reading ability to a remarkable degree. Whether reading stories, books, technical matter, it becomes possible to read sentences at a glance and entire pages in seconds with this method.

To acquaint the readers of this publication with the easy-to-follow rules for developing rapid reading skill, the company has printed full details of its interesting self-training methods in a new booklet, "How to Read Faster and Retain More" mailed free to anyone who requests it. No obligation. Send your name, address, and zip code to: Reading, 835 Diversey Parkway, Dept. 684-019, Chicago, Ill. 60614. A postcard will do.

Circle 134 on reader's service card

CANADIANS: Ordering is easy . . . we do the paperwork . . . try a small order

SARKES TARZIAN TV TUNER 41mc

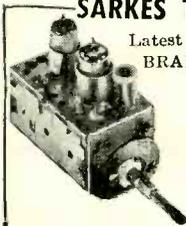


Latest Compact Model—good for all 41 mc TV's
BRAND NEW—MONEY BACK GUARANTEE

Best TUNER "SARKES TARZIAN" ever made—last word for stability, definition & smoothness of operation. An opportunity—to improve and bring your TV Receiver up-to-date.


COMPLETE with Tubes & Schematic . . . \$7.95

HIGHWAVE AM-FM PORTABLE RADIO

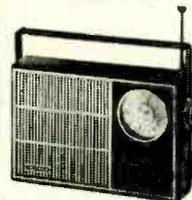

Elegance in Ebony & Chrome
14 Transistors - A Powerhouse of Quality Reception with AFC Operates on 4 "C" Cells
22" Telescoping FM Antenna & Personal Listening attachment
Money refund - If not better than any Known Brand selling for even twice the price
8"x5 1/4"x2 1/4" - 4 lbs
FREE - extra set of batteries

COMPLETE . . . \$19.50

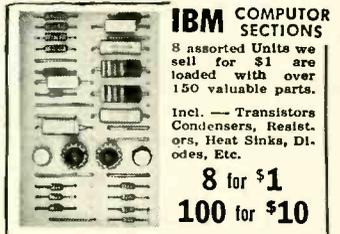


IBM COMPUTER SECTIONS

8 assorted Units we sell for \$1 are loaded with over 150 valuable parts.
Incl. — Transistors
Condensers, Resistors, Heat Sinks, Diodes, Etc.

8 for \$1
100 for \$10

- 1000—ASST. HARDWARE KIT \$1
screws, nuts, washers, rivets, etc.
- 300 — ASSORTED HEX NUTS \$1
2/56, 4/40, 5/40, 6/32, 8/32 ..
- 250—ASST. SOLDERING LUGS \$1
best types and sizes
- 250—ASST. WOOD SCREWS \$1
finest popular selection
- 250 — ASST. SELF TAPPING SCREWS #6, #8, etc. \$1
- 150—ASST. 6/32 SCREWS and 150-2/56 HEX NUTS \$1
- 150—ASST. 8/32 SCREWS and 150-8/32 HEX NUTS \$1
- 150—ASST. 2/56 SCREWS and 150-2/56 HEX NUTS \$1
- 150—ASST. 4/40 SCREWS and 150-4/40 HEX NUTS \$1
- 150—ASST. 5/40 SCREWS and 150-5/40 HEX NUTS \$1
- 500—ASSORTED RIVETS most useful selected sizes
- 500—ASSORTED WASHERS most useful selected sizes
- 100 — ASST. RUBBER & FELT FEET FOR CABINETS best sizes
- UNIV. 3" x 5" PM SPEAKER \$9.95
Best type for Radios, TV, Etc. . .
- 3—ELECTROLYTIC CONDENSERS most popular number 50/30—150v \$1
- 3—TOP BRAND SILICON RECTIFIERS 1 amp, 1000 PIV
- 15 — G.E. #NE-2 TUBES Neon Glow Lamp for 101 uses .. \$1
- CLEAN UP THE KITCHEN "JACK-POT" Big Deal only one to a customer
- HEARING AID AMPLIFIER Incl. 3 Tubes, Mike, etc. (as is) \$2
- CHAPT ZU DI MIZIA "JACK-POT" double your money back if not completely satisfied
- 50 — ASST. TERMINAL STRIPS all types, 1-lug to 6-lug
- 25 — INSTRUMENT POINTER KNOBS selected popular types .. \$1
- 5 — I.F. COIL TRANSFORMERS sub-min for Transistor Radios \$1
- 5 — AUDIO OUTPUT TRANSFORM Sub-min for Trans Radios \$1
- 4 — TOGGLE SWITCHES SPST, SPDT, DPST, DPDT
- 32'—TEST PROD WIRE deluxe quality, red or black
- 100—ASST 1/4 WATT RESISTORS stand. choice ohmages, some in 5% \$1
- 100 — ASST 1/2 WATT RESISTORS stand. choice ohmages, some in 5% \$1
- 70 — ASST 1 WATT RESISTORS stand. choice ohmages, some in 5% \$1
- 35 — ASST 2 WATT RESISTORS stand. choice ohmages, some in 5% \$1
- 50 — PRECISION RESISTORS asst. list-price \$50 less 98% .. \$1
- 20 — ASS'TED WIREWOUND RESISTORS, 5, 10, 20 watt \$1
- 100 — ASST. MICA CONDENSERS some in 5%
- TELEPHONE RECORDING DEVICE instant suction cup fit
- CRYSTAL LAPEL MICROPHONE high impedance, 200-6000 cps .. \$1
- 25' — MICROPHONE CABLE deluxe, 2 conductor, shielded .. \$1
- \$15.00 RADIO PARTS "JACK-POT" handy assortment
- 5 — PNP TRANSISTORS general purpose, TO-5 case
- 5 — NPN TRANSISTORS general purpose, TO-5 case
- 15 — ASST. ROTARY SWITCHES all popular types \$20 value
- 10 — 7" TV TAPE REELS all you want, 8000 in stock
- TAPE RECORDER — assorted types good, bad, broken, as-is, potluck \$4
- TRANSISTOR RADIO asst type good, bad, broken, as-is, potluck \$1.50
- 10 — TRANSISTOR RADIO EARPIECES wired complete with plug \$1
- 100 — ASST. TUBULAR CONDENSERS .001 to .47 to 600v .. \$1
- 50 — TUBE CARTONS (colored) assorted sizes for Popular Tubes or—50 of any size you select .. \$1
- 10 — ASSORTED TUBES Radio, Television and Industrial .. \$1
- 10—TUNGSO 12FK6 TUBES brand new individually cartoned .. \$1
- ALL AMERICAN TUBE KIT Top Standard Brand — 12BA6, 12BE6, 12AV6, 50C5, 35W4 ... \$2
- 2 — TV VERTICAL OUTPUT TRANSFORMERS 10:1 ratio
- 5—ASSORTED TRANSFORMERS Radio, TV and Industrial
- 4 — AUDIO OUTPUT TRANSFORMERS asst. 6L6, 50L6, 6K6, 3Q4
- 20 — ELECTROLYTIC CONDENSERS 25mfd-6v, top quality

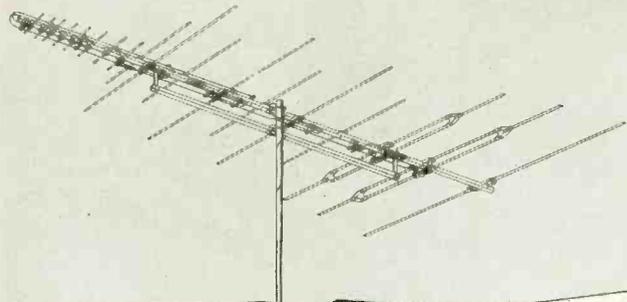MERCHANDISE WANTED in any quantity — TUBES (all types) — RADIO & TV PARTS — EQUIPMENT finished or unfinished — immediate cash. Please send samples, quotes & amounts — only new merchandise bought.



**3-Way Combination
FREE SPACE STANDING WAVE
MAGNETIC ANTENNA**

**ZEROS IN
YOUR SIGNAL—**

**Discriminates Between
Desired Signal and
Unwanted Noise!**

Here is an antenna with the unique ability to discriminate between the desired signal and unwanted noise! A complete absence of minor lobes and an extremely high front to back ratio are characteristics of these antennas. This is made possible by the development of the Free Space Standing Wave Magnetic Drive Antenna system (F.S.M.). The outstanding electrical qualities, combined with the simplified mechanical construction of this system yields a total performance package unparalleled in today's market. 4 models, 60-inch to 180-inch boom, all modestly priced.

UNEXCELLED!

UHF — VHF — FM — COLOR

INVESTIGATE NOW!

S&A Electronics Inc.

Manufacturers of the TARGET ANTENNA


210 West Florence Street
Toledo, Ohio 43605

Circle 135 on reader's service card

TECHNOTES

ROTATOR MOTOR REPAIR

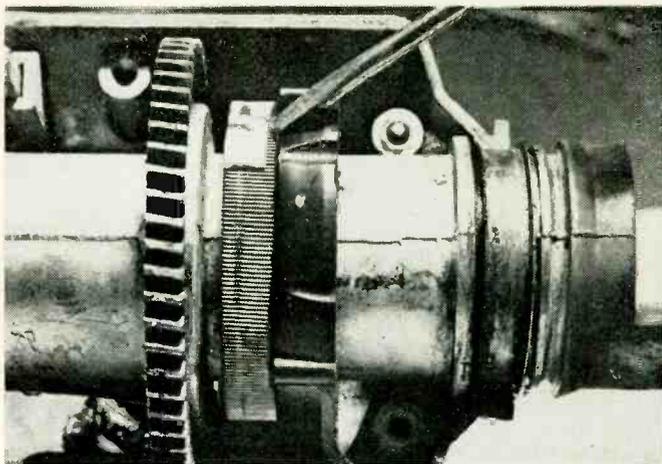
The antenna rotator had quit—and of course stopped in the wrong direction for good TV reception. I took the rotator down and disassembled the motor. The small direc-



tion-indicator rheostat had opened where the wiper blade slides on it. This was Sunday, the rotator had to be repaired, and naturally I didn't have an extra rheostat on hand. I laid a small copper strip inside the rheostat and soldered it to the copper turns. This completed the circuit, and the rotator has been working ever since.—*Homer L. Davidson*

1965 DELCO/CHEVROLET RADIOS

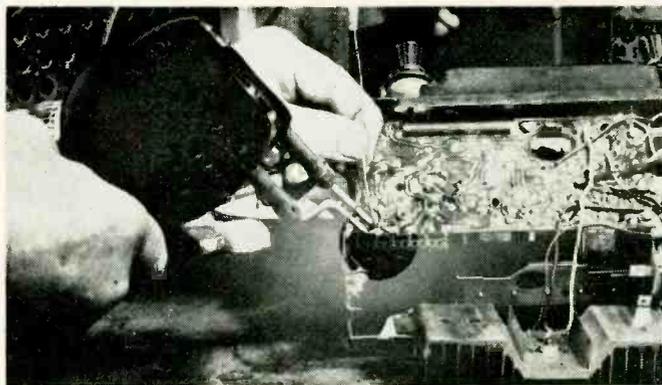An intermittent oscillator trimmer capacitor in early 1965 Chevrolet auto radios can cause intermittent reception, frequency drift and cutting-out at the low end of the dial. This can be checked by using a pencil or blunt tool to push gently on the oscillator adjustment screw—usually sealed with red paint.



It is quite a job to change this capacitor because it is mounted under the circuit board. First, loosen the board from the chassis. Unsolder the tuning unit and pry the soldered terminals away from the soldered connections. Apply heat to the trimmer capacitor terminals and suck the molten solder off the board. Clean out all trimmer terminal holes before inserting the replacement unit. Solder all terminals, button up the chassis and then realign the front end.—*David Mark*

END

WHAT KIND OF NOISE ANNOYS A TAPE?

(continued from page 43)

inner surface of a drive belt was hitting one of the tube shields.

In a similar category is the loose motor fan with blades that strike a projection on the housing. The early 1500 series Wollensak had a fan-shaft projection that caused no end of noise when the recorder was not properly positioned. Fortunately the trouble was easily spotted. In the case of most such noises, the sound is telegraphed to other areas and you may spend hours trying to locate the source.

Such was the case when the takeup reel on a Sony was rubbing against a high spot on the cover. Similarly a high spot on the brake of a Uher recorder had me scratching my head for more than an hour. These puzzlers are at their worst when the offending noise comes and goes. Invariably it is on hand at demonstration time or when you are using the microphone and want recording-studio quietness.

Linkage vibration at odd times is another hard-to-locate source of noise. For this reason, when the recorder is an old one, time in locating a noise can actually be saved by getting the machine into operation and simply watching it for a while. Look for broken tiny tension springs and for missing or displaced pads or cushions.

Portable recorders that develop what sounds like excessive hum may need an additional end-play washer on the motor shaft. Test for this by tilting the instrument this way and that while it is in operation. The rubber feet on some recorders may harden and won't absorb normal motor vibration. This can be corrected easily by pushing sections of garden hose over the worn feet. Also, in extreme cases, a felt pad under the instrument will silence the noise. **END**

50 Years Ago


In Gernsback Publications
From September, 1917
Electrical Experimenter

U.S. Blows Up Tesla Radio Tower
Spy Aerials

The Marvels of Radio-Activity

The Franklin Experimental Club

The Present Status of the Audion

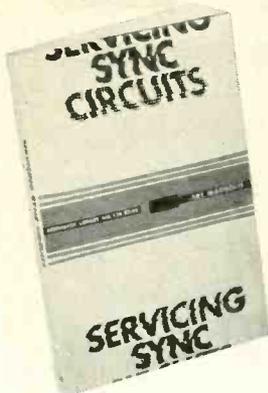

SERVICING SYNC CIRCUITS

By
ART
MARGOLIS

A comprehensive guide to sync circuitry, its uses and varieties in TV receivers. It tells how and with what to troubleshoot problems. Completely illustrated with actual case histories based on specific makes and models, "Servicing Sync Circuits" contains a "photo index" of sync troubles photographed right off the TV screen. Includes new transistor sync circuits, too. 141 pages. G/L #134. Softbound \$2.95.

At your
Gernsback Library dealer

Audio-Color

Lets you see your music



ASSEMBLED \$54.95
KIT FORM \$44.95
\$5 DOWN — \$5 MONTH

Walnut finished cabinet included
Shipped REA Collect

Easy to build, easy to install. All transistor AUDIO-COLOR adds a visual dimension to musical enjoyment. A brilliantly moving panorama of color casts dancing images on a soft frosted screen, reflecting rising and falling volume with each beat of the music. Here's a truly unique and exciting new musical experience. Make check or money order to CONAR.

SEND FOR FREE CONAR CATALOG

CONAR Division of National Radio Institute
Dept. JC7C, 3939 Wisc. Ave., Washington, D.C. 20016

IS WIDE BANDWIDTH ESSENTIAL FOR HIGH FIDELITY? Everyone has his own theory, so why not try an ear test, using a roomful of listeners? That's what our audio editor did, to find out how important bandwidth is to hi-fi. Read what he learned in the October RADIO-ELECTRONICS.

ELECTRONICS

Engineering-Technicians


Bachelor of Science Degree, 30 Months
Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
 - Electrical Engineering (B.S. Degree)
 - Mechanical Engineering (B.S. Degree)
 - Civil Engineering (B.S. Degree)
 - Architecture (B.S. Degree) (36 Months)

Approved for Veterans
DAY AND EVENING CLASSES

Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name
Address
City
State

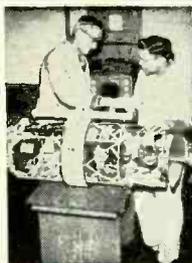

The Nation's increased demand for Engineers,

Electronic Technicians, Radio TV Technicians is at an all time high. Heald Graduates are in demand for Preferred High Paying Salaries. Train now for a lucrative satisfying lifetime career.




1215 Van Ness Avenue
San Francisco, California

Circle 138 on reader's service card

RADIO SHACK *Wharfedale* SPEAKER RIOT!

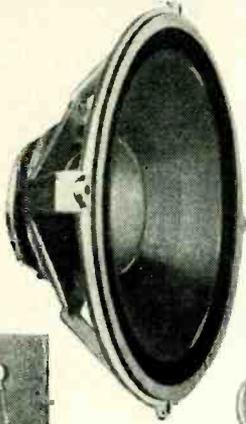Giant Special Purchase! The Audio Buy of the Year!



Another Radio Shack exclusive — the speaker kit riot of the century! We're offering the "guts" of a WHARFEDALE speaker system in kit form, including woofer, tweeter, all network parts, and detailed instructions for installation in your existing cabinet or for building an enclosure. This same speaker was nationally advertised by the manufacturer at \$122.50 in a cabinet.

YOU
PAY
ONLY **49⁹⁵**

Wharfedale features: heavy-duty 12 $\frac{1}{2}$ " long-throw die-cast-chassis woofer with massive 5 $\frac{1}{2}$ -lb. Sheffield steel magnet; high-excursion cone suspension with cone resonance of 24 cps! 4" tweeter has huge 1 $\frac{1}{4}$ -lb. magnet and die-cast basket! Wool cloth suspension! The professional 2-section LCR crossover network includes an aluminum-clad series capacitor for tweeter, variable potentiometer to let you custom-compensate system for room acoustics. SPECIFICATIONS: Response: 35-18,500 cps. Power (IHF per Channel): 8 watts (Min.), 30 Watts (Max.). Impedance: 8 ohms. Acoustic Control: treble, continuously variable. Crossover Point: 1000 cps. #40-922



COMPANION SPECIAL PURCHASE FROM *EMI*

High Compliance 4" Speaker Value!

3⁹⁹
EACH

4 to 12:	3.77
13 to 24:	3.69

British acoustic suspension speaker for custom hi-fi replacement in compact enclosures, or as an extension. Cone is suspended by cloth surround that provides cone excursion never before possible in a speaker this size. Massive ceramic magnet develops over 13,000 Gauss! 15 watt music power; 50-15,000 cps response; 8 ohms. #40-1908.

3 BLAZING WATTS OF TRANSCEIVER POWER!

NEW!



- 4-Crystal 2-Channel Operation!
- Call Alert! Range Gain!
- Center-Loaded Antenna!
- Separate Mike and Speaker!

79⁹⁵
NO
MONEY
DOWN

NEW FOR '68 — the fabulous Realistic TRC-99. Has 19 solid state devices on military quality PC boards; RF stage; center loaded 57" telescopic whip for the ultimate in performance. Plus call alert; separate ceramic mike and speaker; exclusive lock-to-talk switch; battery condition meter; and a die cast case that can really take it! AGC and ANL; squelch; dual channel operation WITH ALL 4 CRYSTALS for channel 5 and 11 — plug-in, of course, so it's really a 23-channel transceiver! 6 side facilities for external speaker, beep tone, channel, external mike, external antenna and 12 VDC power supply. Optional 12V battery pack available. #21-107.

TRC-66/ALSO NEW FOR '68!

A step down in power and cost, the dual-channel TRC-66 is similar to the '99' but is rated at 1 $\frac{1}{2}$ watts and includes 4 crystals for Ch. 11 only. #21-105

59⁹⁵


NEW! *EMICRONTA* 6 $\frac{1}{2}$ " VTVM

39⁹⁵

Factory Wired & Tested!

- Easy-to-Read 2-Color Scale!
- Response: 30 cps to 10 MC!

Features zero-center scale for alignment of FM/TV detector circuits; high-input impedance; precision resistors for accurate readings. AC Volts: RMS: 0.1 to 1500 V. (7 ranges); DC Volts: 0.1 to 1500 V. (7 ranges). Peak-to-peak 4-4000 V. (7 ranges); Output -20 db — +65 db (7 ranges). Resistance: 0.2 Ω to 1000 meg-ohms (7 ranges). 117 VAC, 50/60 cy. With leads and instruction manual. Size: 7 $\frac{1}{2}$ x 6 $\frac{1}{4}$ x 8 $\frac{1}{8}$ ". #22-025

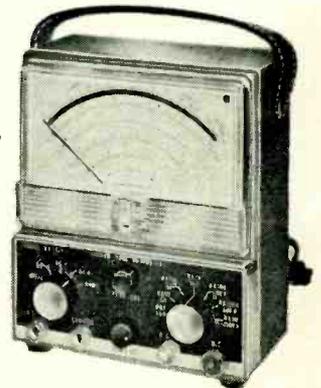


50,000 OHMS/VOLT 26-RANGE MULTITESTER

27⁹⁵

- 4" Meter w/ Mirrored Scale!
- 1% Precision Resistors!
- Meter Protection Circuit!

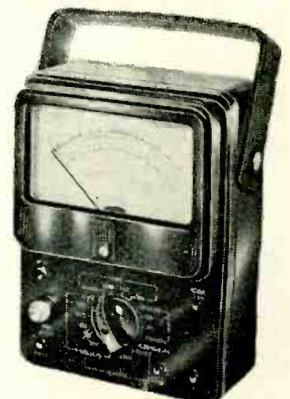DC Volts: 0-0.5-2.5-10-50-250-1000V at 50,000 Ω /volts. AC: 0.25-10-50-250-100V at 12,500 Ω /volts. DC current 2 μ a-2.5-250ma — 1.0 amps. DC resistance: Rx 1/10/100/1000. Center reading scale 90/900/9000/90,000 Ω . DB: -20 to +64 in 5 ranges. Batteries, leads, instructions included. 7 x 5 $\frac{1}{2}$ x 2 $\frac{3}{8}$ ". #22-150



Circle 139 on reader's service card


TRY THIS ONE

SHORTING STICK FOR TV HIGH VOLTAGE

If you are tired of being belted by high-voltage discharge—especially in color sets—when you change the voltage-regulator tube or high-voltage rectifier, you'll find this gadget a valuable addition to your tool kit. It is very inexpensive and goes together in minutes.

Start with a flat (or round) piece of insulated material (I used a 12-inch piece of a broken yardstick). Next, get a small piece of brass shim stock from your auto supply house. Cut a "V" in the shim stock and then bolt or rivet it to the stick so about 2 inches protrudes from the end. Solder an 18-inch piece of test lead to the brass and add an alligator clip as in the drawing.

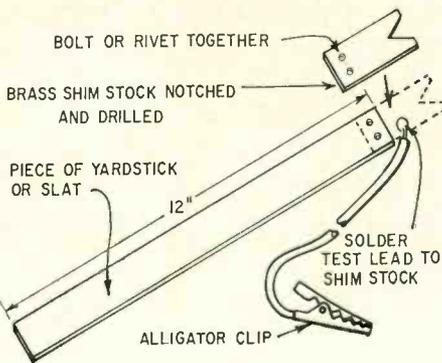To use, clip the test lead to the chassis and, using the stick as a handle, slide the strip under the rubber insulator on the CRT high-voltage anode lead. The brass strip touches the anode con-



ductor and the residual charge drains off to ground. You can then put your hand in the cage and remove the tubes without getting smacked.

—John H. Larry

END

Solution to R-E Puzzler for August 1967

- | | |
|-------------------|--------------------|
| 1 superheterodyne | 13 arrester |
| 2 lithium | 14 electrode |
| 3 antinodes | 15 detent |
| 4 etchant | 16 germanium |
| 5 spaghetti | 17 analyzer |
| 6 conduit | 18 duodiode |
| 7 connection | 19 ceramic |
| 8 kilovoltmeter | 20 dielectric |
| 9 doublet | 21 getter |
| 10 raster | 22 soldering |
| 11 element | 23 prototype |
| 12 friction | 24 joint |
| | 25 radiogoniometer |

Deduct 4 points for each part you missed.

Your rating:

- | | |
|---------------|---------------|
| 60-64 Walk. | 76-84 Double. |
| 68-72 Single. | 88-96 Triple. |
- 100 OHM RUN! Congratulations!

By Edmund A. Braun



JACK DARR'S SERVICE CLINIC

Packed with the most helpful material from RADIO-ELECTRONICS' Service Editor Jack Darr's monthly "Service Clinic." A must for testing and troubleshooting. Every chapter crammed with precise, concrete instruction based on actual reader questions and answers. Hundreds of questions chosen for lasting practicality and listed under convenient categories for handy reference. 192 pages. G/L #133. Softbound \$2.95.

At your Gernsback Library dealer

SEPTEMBER 1967

99

SCHOOL DIRECTORY

ENGINEERING MATHEMATICS

NOW! A NEW WAY TO LEARN—I. H. S. I. WAY. A complete home study course in engineering math to help you get the position you want—**MORE MONEY—MORE RESPECT.**

COURSE PREPARED BY COLLEGE PROFESSORS who have lectured to thousands of men on math and engineering. You learn at home quickly, easily—**AS FAST** as you want.

YOU SIGN NO CONTRACTS Pay only if satisfied—you owe it to yourself to examine the **INDIANA HOME STUDY INSTITUTE COURSE IN ENGINEERING MATH.**

FREE BONUS—if you join now, a refresher course in basic arithmetic.

Write for Brochure—No Obligation.

THE INDIANA HOME STUDY INSTITUTE
Dept. RE-9, P.O. Box 1189
Panama City, Fla. 32401

Get Your First Class Commercial

F. C. C. LICENSE

thru spare-time study by correspondence. Our money-back warranty protects your investment. (Approved for Veterans) Write for Brochure 67. It's free.

Grantham School of Electronics
1505 N. Western Av., Hollywood, Cal. 90027

Learn Electronics for your SPACE-AGE EDUCATION


at the center of America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech, in sunny Southern California.

COLLEGE OF ENGINEERING. Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

A & P SCHOOL. Practical experience on real aircraft. One-year course prepares you for F. A. A. A & P certificate. **WRITE TODAY FOR CATALOG.**

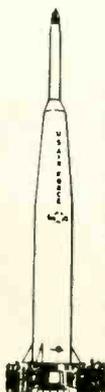NORTHROP INSTITUTE OF TECHNOLOGY
1199 W. Arbor Vitae, Inglewood, Calif.



for a professional career

Tri-State graduates hold important engineering and business administration posts throughout the U. S. This professionally-oriented small college has outstanding placement record. Four-quarter year permits degree in three years. Excellent faculty. Well-equipped labs. Beautiful 300-acre campus. Accredited. Small classes. Modest costs. One-year Drafting-Design Certificate program. Enter Jan., March, June, Sept. For Catalog, write Director Admissions indicating career interest.



TRI-STATE COLLEGE
2497 College Avenue, Angola, Indiana 46703

GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology and Electronic Technology curricula both available. Assoc. degree in 29 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Sept., Feb. Dorms, campus. High school graduate or equivalent. Catalog.

VALPARAISO TECHNICAL INSTITUTE
Department C, Valparaiso, Indiana



TELEVISION RADIO COLOR TV

MAIL COUPON FOR FREE BOOK

Coyne Electronics Institute Dept. 67-C5
1501 W. Congress Pkwy., Chicago, Ill. 60607

Send information as checked below

- HOME TRAINING in TV • Radio • Color TV • Electronics
- RESIDENT SCHOOL COURSES in Electronics, Electricity, Engineering, Radio-TV, Color TV, Refrigeration, and FCC

Name.....
Address.....
City.....State.....Zip.....
Phone.....Age.....

VA Approved—GI Bill

MARKET CENTER

NAVY MARINE BAND WALKIE TALKIE

TRANS. & RECEIVER—This equipment is crystal controlled and can be operated on any one channel in freq. range 2.3 to 4.5 MC. Voice (A3) communication only; output of Trans. is 0.2 watts & satisfactory communication between units over average terrain should be maintained approx. up to one (1) mile. With tubes: 1/1B5, 1/1R5, 2/1T4, 3/3B4. Voltages required: 67.5 VDC 3 MA; 135 VDC 4 MA; 1.5 VDC 225 MA for REC.—67.5 VDC 1.5 MA; 135 VDC 19 MA; 1.5 VDC 225 MA; & —6 VDC 30 MA for TRANS. Unit comes in a waterproof plastic case with space for batt. or power supply. Telescoping antenna 8 ft. has special loading coil. Complete w/tubes, antenna, 2 crystals FT-243 (no choice of freq.) headphones, carbon mic., canvas cover, & manual. Size: **\$9.95**

8" x 8" x 2 3/4". Wt.: 8 lbs.

"DAV" MODEL—Same as above, but with directional finding loop circuit for homing; & lip mic. Comes in plywood case w/carrying straps. Size: 14 x 10 x 3". Wt.: 11 lbs. **\$12.95**

Prices F.O.B. Lima, O.—25% Deposit on COD's—BIG CATALOG—Send 25¢, Receive 50¢ credit on your order!

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

GENERAL

CONVERT ANY TELEVISION to sensitive Big-Screen Oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. RELCO-A25, Box 10563, Houston 18, Texas

TV SERVICE ORDER BOOKS for use with your rubber stamp. Duplicate or triplicate. Low cost. Write for FREE 32 PAGE CATALOG and Special Rubber Stamp Offer. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656

FREE ELECTRONICS (new and surplus) Parts catalog. We repair multimeters. BIGELOW ELECTRONICS, Bluffton, Ohio 45817

TREASURE HUNTERS! PROSPECTORS! Relco's new instruments detect buried gold, silver, coins. Kits, assembled models. Transistorized. Weighs 3 pounds. \$19.95 up. Free catalog. RELCO A25, Box 10839, Houston, Texas 77018

BACK-ISSUES, Electronic, Scientific Magazine. SEMCO, Box 130, Roxboro, Quebec, Canada

WANTED

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! BARRY, 512 Broadway, New York, N. Y. 10012, 212 WALKER 5-7000

AUDIO — HI-FI

RENT STEREO TAPES—over 2,500 different—all major labels—free brochure. STEREO-PARTI, 1616-R Terrace Way, Santa Rosa, Calif. 95404

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15 day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. HI-FIDELITY CENTER, 239R East 149th St., N.Y., N.Y. 10451

TAPE RECORDER SALE. Brand new, latest models, \$10.00 above cost. ARKAY SALES, 1028 E Commonwealth Ave., Boston, Mass. 02215

"TAB" • SILICON ONE-AMP DIODES
Full Leads Factory Tested & Grd! U.S.A. Mfg

Piv/Rms 50/35 .05	Piv/Rms 100/70 .07	Piv/Rms 200/140 .10	Piv/Rms 300/210 .12
400/280 .14	600/420 .21	800/560 .30	900/630 .40
1000/700 .50	1100/770 .70	1700/1000 1.20	2400/1680 2.00

"TAB" TERMS: Money Back Guarantee Our 22nd Year. \$2 Min. Add Shipping Charges

111 GD LIBERTY ST., N. Y. 6, N. Y.
Send 25¢ Phone: RECTOR 2-6245 for Catalog

AC POWER FROM YOUR CAR OR BOAT BATTERY

Standard home electricity (60 cycle, 117 volts) for small appliances, record players, tape recorders, tools, etc.


Inverters from 25 to 600 watts, priced as low as \$15.95.

See your Electronics Parts Dealer, or write



terado CORPORATION
1053 Raymond Ave., St. Paul, Minn. 55108

INTEGRATED CIRCUITS

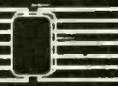

1.25 Amp (Glass Amps)
A controlled avalanche rectifier in which the PRV may be exceeded without destroying the rectifier.

PRV	AMP
100	.07
200	.09
400	.12
600	.20
800	.25
1000	.50
1200	.65
1400	.85
1600	1.00
1800	1.20

PRV	AMP
100	.12
200	.15
400	.20
600	.25
800	.35
1000	.50

JK FLIP FLOPS . . . \$1.15
DUAL NAND NOR GATES . . . \$1.00
SR CLOCKED FLIP FLOPS . . . \$1.15
SRT FLIP FLOPS . . . \$1.15
EXPANDABLE OR GATES . . . \$1.00

TO-85 flat pack. Guaranteed to work. They come complete with schematic, elect. characteristic sheet and some typical applications.

**POST OFFICE BOX 74 D
SOMERVILLE, MASS. 02143**

Send For Our Latest Catalog Featuring Transistors, Rectifiers And Components




Silicon Control Rectifiers TO-66 pack Studs

PRV	3A	7A	20A
50	.35	.50	.80
100	.50	.70	1.35
200	.75	1.05	1.90
300	1.25	1.60	2.45
400	1.50	2.10	2.85
500	1.75	2.80	3.50
600	2.00	3.00	
700	2.25	3.50	
1000		5.00	

Terms: FOB Cambridge, Mass. Send check or Money Order. Include Postage, Average Wt. per package 1/2 lb. Allow for C.O.D. Minimum Order \$3.00

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

Allied Radio Corp.	65-66
Amperex Electronic Corp.	Second Cover
Amplifier Corp. of America	90
Arco Electronics (A Division of Loral Corporation)	23
B & K (Division of Dynascan Corporation)	13
Barker Products Co. (Audio Division of Component Manufacturing Service, Inc.)	26
Brooks Radio & TV Corp.	90-91
Burstein-Applebee Co.	88
Capitol Radio Engineering Institute, The	18-21
Castle TV Tuner Service, Inc.	83
CLASSIFIED	100-103
Cleveland Institute of Electronics	5, 28-31
Conar (Div. of National Radio Institute)	93
Cornell-Dubilier	Third Cover
Cornell Electronics Co.	102
Delta Products, Inc.	16
DeVry Institute of Technology (A Subsidiary of Bell & Howell)	7
Electro-Voice, Inc.	78
Finney Co.	14-15
GBC American Corp.	77
GC Electronics Co.	73
Gernsback Library Inc.	83, 93, 99
Great Lakes Insurance Co.	83
Heald Engineering College	93
Heath Company	24-25
International Crystal Mfg. Co., Inc.	104
Jensen Manufacturing Division (The Muter Company)	6
JFD Electronics Corp.	27
Lafayette Radio Electronics	85-86
Mallory Distributor Products Company (Div. of P. R. Mallory & Co., Inc.)	81
Microflame, Inc.	89
Mike Quinn Electronics	84
Music Associated	82
National Radio Institute	8-11
Olson Electronics, Inc.	83
Oxford Transducer Company (A Division of Oxford Electric Corporation)	22
Permosflux Corp.	98
Poly Paks	103
Quam-Nichols Co.	80
Quietrole Co.	82
Radar Devices	1
Radio Shack	94-97
RCA Electronic Components and Devices Tubes	Fourth Cover
RCA Institutes, Inc.	54-57
RCA Parts and Accessories	79
Reading Improvement Program	91
Rye Industries, Inc.	88-89
S & A Electronics Inc.	92
Salch & Co., Herbert (Marketing Division of Tompkins Radio Products)	84
Sams & Co., Inc., Howard W.	69, 82
Sencore	70-71
Shure Bros.	17
Solid-State Sales	100
Sony Corp. of America	81
Sprague Products Company	12
Surplus Center	98
Turner Microphone Company, The	87
United Radio Co.	101
Warren Electronic Components	102
MARKET CENTER	100-103
Arcturus Electronics Co.	
Edmund Scientific Corp.	
Fair Radio Sales	
Leeds Radio	
TAB	
Terado Corporation	
Treasureprobe	
SCHOOL DIRECTORY	99
Coyne Electronics Institute	
Grantham School of Electronics	
Indiana Home Study Institute, The	
Northrop College of Science & Engineering	
Tri-State College	
Valparaiso Technical Institute	

Circle 142 on reader's service card

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. CARSTON, 1686-R Second Ave. N.Y.C. 10028

STEREO TAPES. Save up to 60% (no membership fees, postpaid anywhere USA). Free 60-page catalog. We discount batteries, recorders, tape accessories. Beware of slogans "not undersold," as the discount information you supply our competitor is usually reported to the factory. SAXITONE, 1776 Columbia Road, Washington, D. C. 20009

TAPEMATES makes available to you ALL 4-TRACK STEREO TAPES—ALL LABELS—postpaid to your door—at tremendous savings. For free brochure, write TAPEMATES CLUB, 5727 W. Jefferson Blvd., Los Angeles, Calif. 90016

HI-FIDELITY COMPONENTS, Ham Marine and Communication equipment at considerable savings. If you want to save money write us for our low prices on all your needs. AIREX RADIO CORP., 132 (RE) Nassau St., New York, N.Y. 10038

LIKE MUSIC WITHOUT COMMERCIALS? Completely wired 67 KHz SCA (background music) adapter Model SCA-2 for \$34.95. Five tuned circuits, two silicon transistor amplifier and ratio detector. Four connections to your FM receiver. Instructions included—No adjustments. Operates on 6 to 12 Volts DC. Size: 2 1/2 x 3 x 3/4 inches. Dealer inquiries invited. Available installed in a nationally advertised six tube AM-FM radio for \$59.95. Also available installed in a nationally advertised ten transistor AM-FM portable for \$79.95. Texas residents add 2% sales tax. KENZAC CO., P.O. Box 66251, Houston, Texas 77006

NEW HAMMOND REVERBERATION Mechanisms —\$4. CAL'S, Box 234, Dearborn, Michigan 48121

INVENTIONS & PATENTS

INVENTIONS-IDEAS developed: Cash/Royalty sales. Member: UNITED STATES CHAMBER COMMERCE, Raymond Lee, 130-U W. 42nd, New York City 10036

BUSINESS AIDS

JUST STARTING IN TV SERVICE? Write for FREE 32 PAGE CATALOG of Service Order books, invoices, job tickets, phone message books, statements and file systems. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656.

1,000 Business Cards, "Raised Letters" \$3.95 postpaid. Samples. ROUTH, 5717 Friendswood, Greensboro, N. C. 27409

BUSINESS OPPORTUNITIES

Business for sale—TELEVISION RADIO APPLIANCE SERVICE SHOP. Connected, well equipped in thriving small town with good payroll. Good location. Building under lease with 4140 sq. ft. floor. P.O. Box 5, Pittsboro, North Carolina 27312

ELECTRONICS

BARGAINS in Canadian Electronic equipment and surplus. Send \$1.00 for giant catalogs. ETCO, Box 741, Dept. R, Montreal, Canada

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services): 60¢ per word . . . minimum 10 words.

NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items): 30¢ per word . . . no minimum.

Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for October issue must reach us before August 10th.

WORD COUNT: Include name and address. Name of city (Des Moines) or state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8-10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

CLASSIFIED ADVERTISING ORDER FORM

For complete data concerning classified advertising please refer to box elsewhere in Market Center section.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

{ @ .30 Non-Commercial Rate }
No. of Words { @ .60 Commercial Rate } = \$

Total Enclosed \$

Insert _____ time(s)

Starting with _____ issue

Payment must accompany all ads placed through accredited advertising agency 97

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

SIGNATURE _____

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 154 WEST 14TH ST., NEW YORK, N.Y. 10011

\$1.00 SALE \$1.00 SALE

THE PACKS LISTED BELOW ARE YOURS FOR \$1 EACH
Compare Our Prices

- 4—50' SPOOLS HOOKUP WIRE
- 125—MIXED DEAL "JACK-POT" Cond. Resist. Surprises
- 25—EXPERIMENT. COIL Assort. for 101 uses.
- 24—ASST. PILOT LIGHTS
- 75—ASST. DISC. CERAMIC COND.
- 12—ASST. RADIO ELECTROLYTIC CONDENSERS
- 60—ASST. TUB. CONDENSERS .001 to .47 to 600 v.
- 6—ASST. SELENIUM RECTIFIERS 65, 100, 300 ma. etc.
- 8—ASST. TV ELECTROLYTIC CONDENSERS
- 6—ASST. TRANSFORMERS/6—AUDIO OUTPUT. TRANSF.
- 15—ASST. DIODE CRYSTALS/12—STAND. TRANSISTORS
- 6—TOP HAT SILICON RECT./4—ELEC. COND. 50-60-150 V
- 6—I.F. COIL TRANSFORMERS sub. min. for Transist.
- 12—TOGGLE SWITCHES-SPST Removed from new equip.
- 75—ASST. 1 W. RESISTORS Stand. choice ohm.
- 40—ASST. 2 W. RESISTORS Stand. choice ohm.
- 60—PRECISION RESISTORS ASST.
- 24—ASST. WIREWOUND RESISTORS 5, 10, 20 watt
- 110—ASST. MICA CONDENSERS
- 6—PNP TRANSISTORS General purp. TO-5 case
- 6—NPN TRANSISTORS General purp. TO-5 case
- 17 ASST. ROTARY SWITCHES All pop. types

No C.O.D. Orders—\$5.00 Min.

PLEASE INCLUDE POSTAGE

WRITE FOR OUR PARTS & TUBE CATALOG, LOWEST WORLD PRICE ON BRAND NEW TUBES, ESTABLISHED 1926

LARGEST STOCK OF XMITTING & SPECIAL PURPOSE TUBES IN THE U.S.A.

UNITED RADIO CO.

56 FERRY ST., NEWARK, N.J. 07105

Circle 143 on reader's service card

UNUSUAL BARGAINS

... MANY U. S. GOV'T SURPLUS

GIANT WEATHER BALLOONS



"Balls of fun" for kids, traffic stoppers for stores, terrific for amateur meteorologists. Create a neighborhood sensation. Great backyard fun. Exciting beach attraction. Made of heavy duty neoprene. Inflate with vacuum cleaner or auto air hose; or locally available helium for high rise.
Stock No. 60,568EH
(8' diam.) . . . \$2.00 Ppd.
Stock No. 60,632EH
(16' diam.) . . . \$7.00 Ppd.

NEW SURPLUS NI-Cd BATTERIES

Save more than 50% Long life—accept 300 charge and discharge cycles. 1.25 Volts per cell—750 milli-ampere hours capacity. Excel. charge retention. Hermetically sealed. Indefinite storage life. Multiple cells welded in series—easily cut. Combine to form battery. 7/8" dia. x 1-5/8" high. Spec. price for 100 up. Low-cost charger separate.

Order #	Cells	DC Volt.	Price Ppd.
40,986EH	1	1.25	\$ 1.50
40,987EH	2	2.50	2.75
60,633EH	3	3.75	3.60
60,634EH	4	5.00	4.80
70,812EH	Trickle Charger (1.10 cells)		10.95

DUPONT PLASTIC LIGHT GUIDE KIT



Experiment with amazing new plastic fiber optic light guides. 1001 uses for mfrs., experimenters, hobbyists. Use for exciting new projects and products. Guides transmit light same as wire conducts electricity. Use to illuminate remote areas, multiple locations from single source, confine light to small areas, conduct sensing and control systems. Inc. two 2' guides, source, lens, dyes, connectors.
Stock No. 70, 855EH . . . \$10.00 Ppd.

Order by Stock No. Check or M. O.—Money-Back Guarantee.
EDMUND SCIENTIFIC CO., Barrington, N. J. 08007

CLIP AND MAIL COUPON TODAY

SEND FOR FREE CATALOG "EH"

Completely new 1967 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many surplus items: for hobbyists, experimenters, workshop, factory. Mail coupon for catalog "EH".



NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Circle 144 on reader's service card

SILICON RECTIFIER SALE

IMMEDIATE DELIVERY
FULLY GTD NEWEST TYPE
AMERICAN MADE FULLY TESTED



1 AMP SILICON "TOPHAT" & EPOXY DIODES
LOW LEAKAGE FULL LEAD LENGTH

PIV/RMS 50/35 .05 ea.	PIV/RMS 100/70 .07 ea.	PIV/RMS 200/140 .10 ea.	PIV/RMS 300/210 .12 ea.
PIV/RMS 400/250 .14 ea.	PIV/RMS 500/350 .19 ea.	PIV/RMS 600/420 .21 ea.	PIV/RMS 700/490 .25 ea.
PIV/RMS 800/560 .30 ea.	PIV/RMS 900/630 .40 ea.	PIV/RMS 1000/700 .50 ea.	PIV/RMS 1100/770 .70 ea.

ALL TESTS AC & DC & FWD & LOAD

SILICON POWER DIODE STUDS

D.C. AMPS	50 PIV 35 RMS	100 PIV 70 RMS	150 PIV 105 RMS	200 PIV 140 RMS
3	.08 ea.	.12 ea.	.16 ea.	.22 ea.
12	.27	.35	.45	.60
35	.65	.90	1.25	1.40
100	1.00	1.20	1.50	1.75
160	2.50	3.00	3.40	3.75

D.C. AMPS	300 PIV 210 RMS	400 PIV 280 RMS	500 PIV 350 RMS	600 PIV 450 RMS
3	.27 ea.	1.30	.37 ea.	.45 ea.
12	.90	1.40	1.40	1.65
35	2.00	2.35	2.60	3.00
100	2.50	3.50	4.00	5.00
160	4.25	4.75	5.10	Ask

"SCR" SILICON CONTROLLED RECTIFIERS "SCR"

PRV	AMP	AMP	AMP	PRV	7 AMP	16 AMP	28 AMP
25	.50	.75	1.00	250	1.75	2.15	2.50
50	.60	.90	1.25	300	2.00	2.40	2.75
100	.80	1.25	1.50	400	2.40	2.75	3.25
150	.90	1.60	2.00	500	3.20	3.40	3.80
200	1.25	1.80	2.25	1000	3.40	4.00	4.50

SPECIALS! SPECIALS!

Westinghouse 160 AMP, 500 PIV SILICON HI-POWER STUD RECTIFIER IN1666.
Limited quantity. \$5.10 ea. 10 for \$45.00

100 Different Precision Resistors
1/2—1—2 Watt 1/2%—1% TOL \$1.25

Asst transistor Kit. P.N.P.—N.P.N.
All popular types. Unchecked
100 for \$2.95 500 for \$9.95

Computer Grade Condenser 15,500 MFD
12 VDC American Mfg. .75 ea.

Type IN34 DIODE GLASS .07 ea. 100 for \$5

Money Back guarantee. \$2.00 min. order. Include additional \$ for postage. Send check or money order. C.O.D. orders 25% down.

Warren Electronic Components

230 Mercer St., N. Y., N. Y. 10012 • 212 OR 3-2620

Circle 145 on reader's service card

MARKET CENTER

TUBES. "Oldies", latest. Lists free. STEINMETZ, 7519 Maplewood, Hammond, Indiana 46324

RECEIVING & INDUSTRIAL TUBES, TRANSISTORS, All Brands—Biggest Discounts. Technicians, Hobbyists, Experimenters—Request FREE Giant Catalog and SAVE! ZALYTRON, 469 Jericho Turnpike, Mineola, N.Y. 11501

Discharge IGNITION, PHOTOFLASH. Free catalog parts, kits. TRANSPARK, Carlisle, Mass. 01741

ELECTRONIC PARTS! Components, transistors, diodes, kits, relays, and many special items. Guaranteed. Send 25¢ for 100 page catalog. GENERAL SALES CO., P.O. Box 2031C, Freeport, Texas 77541

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, California 92105

MESHNA'S TRANSISTORIZED CONVERTER KIT Converts car radio to receive police & fire. 35-50Mc or 100-200Mc. (one Mc tuning) with simple step instructions \$5.00. MESHNA, No. Reading, Mass. 01864

TV CAMERAS: Assembled and kits. Also plans, vidicons, lenses, scan coils, etc. NEW catalog 10¢. ATV RESEARCH, Box 453, Dakota City, Nebr. 68731

GIANT JAPANESE ELECTRONICS CATALOG. \$1. DEE, 10639A Riverside, North Hollywood, Calif. 91602

FREE ARCTURUS CATALOG

A Trusted name in Electronics Since 1925

Electronic parts, tubes. Wholesale. Thousands of items. Unbeatable prices.

ARCTURUS ELECTRONICS CO.

502-22nd St., Dept. RE, Union City, N. J. 07087

88-108 MC F.M. RECEIVER

10 TUBE CRYSTAL CONTROLLED F.M. RECEIVER WITH TUBES VOLUME TONE CONTROLS 4 WATT OUTPUT. 115 V 60 CYCLE. METAL CABINET 8H x 10D x 12W. WITH DIAGRAM LESS CRYSTAL AND SPEAKER. REMOVED FROM SERVICE BY STORECAST OUTFIT THAT WENT SOLID STATE. \$14.50 EA: 2 for \$25.00 PLUS SHIPPING.

LEED'S RADIO, 57 WARREN ST., N.Y.C. 10007

8 PIECE TOOL KIT

69¢
in original mfr's bags and boxes

- 10 Shipping
- contains 4 Bristo Wrenches
- 1 Hex Blade
- 2 Alignment (tuning) Tools

INTERFERENCE TV TRAPPER

SUPPRESS PICTURE INTERFERENCE CAUSED BY:

- AUTO IGNITION
- AIRPLANES
- APPLIANCES
- NEON SIGNS
- OIL BURNERS
- AMATEUR RADIO TRANSMITTERS

159¢ + 10¢ Shipping

TV LIFESAVER!

STOP TUBE BURNOUTS!

179¢ + 20¢ shipping

CORNELL

33¢

PER TUBE

100 TUBES OR MORE: 30¢ PER TUBE

TUBES

1 YR. GUARANTEED

Mutual Conductance Lab-tested, Individually Boxed, Branded and Code Dated. Tubes are new, or used and so marked.

OZ4	6A55	6CD6	6K6	6X4	12BF6
1B3	6AT6	6CF6	6K7	6X8	12BH7
1J3/1K3	6AT8	6CG7	6Q7	7A7	12BL6
1H5	6AU4	6CG8	6S4	7AB	12BY7
1L4	6AU5	6CM7	6SA7	7B6	12C5
1T4	6AU6				12CA5
1U4	6AV6				12SN7
1X2	6AW8				12SQ7
3BZ6	6AX4				25L6
3DG4	6BA6				25Z6
5U4	6BC5				35W4
5U8	6BD6	6CZ5	6SH7	7C5	35Z3
5V4	6BG6	6D6	6S7	7N7	50L6
5Y3	6B76	6DA4	6SK7	7Y4	
6A6	6BL7	6DE6	6SL7	12AD6	24
6A8	6BN4	6D06	6SN7	12AE6	27
6AB4	6BN6	6E06	6SQ7	12AF6	77
6AC7	6BQ6	6E65	6U7	12AT7	78
6AG5	6BQ7	6F6	6U8	12AU7	84/6Z4
6AK5	6BZ6	6GH8	6U8	12AX7	56B7
6AL5	6C4	6H6	6V6	12BA6	6350
6AN8	6C6	6J5	6W4	12BD6	6463
6AQ5	6CB6	6J6	6W6	12BE6	7044

Other tubes at low prices—send for free list

NO SUBSTITUTIONS WITHOUT YOUR PERMISSION

Special! With every \$10 Order

25¢

per tube

(No Limit) from this list:

6AG5 6SN7
6AQ5 6CB6 6S4
6AU6 6J6 6W4

NEW—EASY TO USE

COLOR TV, 395

DEGAUSSER

40¢

1500-M

BARGAIN CORNER

Solder Iron	1.49
Elect Tape	.89
Epoxy (pr.)	.79
Diode Kit	.39
Noise Filter	.89
Neon Tester	.59
Solder	.39
Antenna Coupler	1.89
Battery Charger	4.95

Prestige & Success are yours as an ELECTRONIC EXPERT

FOR CORNELL CUSTOMERS ONLY by special arrangement with the publisher, these amazing bargains are available

COMPLETE RADIO SERVICING AND BASIC ELECTRONICS COURSE ONLY \$3.00 (12.50 + 50¢ shipping)

NEW PRACTICAL TV TRAINING COURSE ONLY \$3.50 (12.50 + 50¢ shipping)

Both above courses \$6.00

SILICON RECTIFIERS

all purpose ELECTRONIC CLEANER

89¢ + 20¢ shipping

TUBE CARTONS

HIGH GLOSS CLAY COATED P.E.T. & OLACIN. A TYPICAL TUBE IN DIAGONAL PARTITIONS

SIZE	PER 10 CARTONS	PRICE PER 100 CARTONS
MINI	6A10	.29 2.59
ST	6B17	.39 3.49
6 ET	6B44	.59 5.29
6	6A46	.89 7.99

TUBE SUBSTITUTES \$1.25

RADIO-TV TUBE TESTER

289¢ + 30¢ shipping

TEST and REPAIR TV & RADIO SETS APPLIANCES

CORNELL ELECTRONICS CO.

Dept. RE 9 4217 University Ave., San Diego, Calif. 92105

TERMS: Add 3¢ per tube shipping. Orders under \$5.00 add 3¢ per tube shipping plus 50¢ handling. Canadian orders add approximate postage. Send 25¢ deposit on C.O.D. orders. No C.O.D. orders under \$5.00 or to Canada. No 24 hr. free offer on personal check orders. 5-DAY MONEY BACK OFFER

SEND FOR FREE CATALOG



RADIO SHACK'S FRANCHISE STORE PLAN: A REAL OPPORTUNITY FOR SELF-RELIANT MEN TO JOIN THE RADIO SHACK FAMILY!

An invitation to you, and men like you who would like to come with us as owners rather than employees. You may be a young man just starting; or one who's already in business; or a retired man who wants to get back into action. With little more than a desire to be "the boss" and the will to work, you can now open a Radio Shack franchise store 100% owned, located, and operated by you under the 45-year-famous Radio Shack name.

If qualified — NO ELECTRONICS EXPERIENCE is needed — you could be in a profitable business of your own in a matter of weeks, having avoided many of the costly pitfalls and waste of starting out from scratch!

If you want to win with a winner, contact Mr. Bruce Russell, Radio Shack, 730 Commonwealth Ave., Boston, Mass. 02215 (Phone: (617) 734-1000). You'll be talking with a mature man who knows the business from every angle, backed by the know-how and resources of a \$60-million corporation.

Radio Shack President and Board Chairman of Tandy Corp.

UNIQUE RADIO SHACK *Science Fair* ELECTRONICS KITS

At last! Electronic kits that let you work the same way engineers do — by "bread-boarding". Designed by Radio Shack's engineers and produced by our new Science Fair Electronics Division, the kit line fea-

tures step numbered construction data, pictorial, schematic and add-on instructions. Each kit includes, as needed, potentiometers, line cords, and other components often left out of kits.

TRANSISTOR RADIO KIT

Tunes standard AM band; use also as a tuner! Battery-operated. Earphone. #28-102

3⁹⁵

TRANSISTOR ORGAN KIT

Each note on the seven note scale is separately tone variable. Battery operated. #28-101

5⁹⁵

WIRELESS AM MIKE KIT

Transmit to any radio up to 20 ft. away! Battery-operated. A real broadcaster! #28-103

3⁹⁵

1-TUBE DC RADIO KIT

Battery Operated! Learn tube theory and build a real working radio. Earphone. #28-100

3⁹⁵



NEW! RADIO SHACK PERFBOX™!

The bloody-knuckle brigade will like Radio Shack's effort to stop chassis cutting and drilling, and make things prettier!

New bakelite chassis box into which is installed (4 screws) a 3 1/2" x 6" perfboard top. The back of the box is pre-drilled for a 2 1/4" or other PM speaker, and there's a pre-drilled 1/4" outlet hole on one side! As an added fillip, there's a com-

panion set, Radio Shack's Experimenter's 5-Piece Panel Set (Cat. No. 270-100) consisting of 3 perfboards and 1 aluminum and 1 bakelite panel board, each 3 1/2" x 6" pre-drilled to fit the PERFBOX™ #270-097. Each 1.69

ORDER NOW FROM YOUR NEAREST RADIO SHACK STORE!

ARIZONA — Phoenix
 ARKANSAS — Little Rock
 CALIFORNIA — Anaheim, Bakersfield, Covina, Downey, Garden Grove, Glendale, Inglewood, La Habra, Long Beach, Los Angeles, Mission Hills, Mountain View, Oakland, Pasadena, Pomona, Reseda, Sacramento, San Bruno, San Diego, San Francisco, Santa Ana, Santa Monica, Torrance, West Covina
 COLORADO — Denver
 CONNECTICUT — Hamden, Manchester, New Britain, New Haven, New London, Orange, Stamford, West Hartford
 FLORIDA — Jacksonville, Orlando
 GEORGIA — Atlanta
 ILLINOIS — Belleville, Chicago, Harvey
 INDIANA — Richmond

KANSAS — Wichita
 LOUISIANA — Gretna, New Orleans
 MAINE — Portland
 MARYLAND — Langley Park, Rockville
 MASSACHUSETTS — Boston, Braintree, Brockton, Brookline, Cambridge, Dedham, Framingham, Lowell, Medford, Natick, Quincy, Saugus, Springfield, Waltham, West Springfield, Worcester
 MICHIGAN — Detroit, Lincoln Park
 MINNESOTA — Minneapolis, St. Paul
 MISSOURI — Kansas City, St. Joseph, St. Louis
 NEBRASKA — Omaha
 NEW HAMPSHIRE — Manchester
 NEW JERSEY — Pennsauken
 NEW MEXICO — Albuquerque

NEW YORK — Albany, Binghamton, Buffalo, New York, Schenectady, Syracuse
 NORTH CAROLINA — Charlotte
 OHIO — Cincinnati, Cleveland, Lima
 OKLAHOMA — Oklahoma City, Tulsa
 OREGON — Portland
 PENNSYLVANIA — Greensburg, Philadelphia, Pittsburgh
 RHODE ISLAND — Providence, East Providence
 TENNESSEE — Memphis, Nashville
 TEXAS — Abilene, Arlington, Austin, Brownsville, Corpus Christi, Dallas, El Paso, Fort Worth, Houston, Lubbock, Midland, San Antonio, Sherman, Waco
 UTAH — Salt Lake City
 VIRGINIA — Arlington, Norfolk, Virginia Beach
 WASHINGTON — Seattle

RADIO SHACK } East: 730 Commonwealth Ave., Boston, Mass. 02215
 } West: 1515 So. University Dr., Ft. Worth, Tex. 76107

- Send me FREE Radio Shack Catalog '68
- #40-922, Wharfedale Speaker Kit
- #40-1908, 4" Speaker
- #21-107, TRC-99 Walkie Talkie
- #21-105, TRC-66 Walkie Talkie
- #22-025, 6 1/2" VTVM
- #22-105, Multitester
- #28-102, Radio Kit
- #28-101, Organ Kit
- #28-103, Mike Kit
- #28-100, Tube Radio Kit
- #270-097, Perfbox

Name _____
 Street _____
 City _____
 State _____ Zip _____

Add 50¢ per item for postage and handling.

Dept. TF



PERMOFLUX . . .
ANNOUNCES A BRAND
NEW HEADPHONE . . .
the "HM" SERIES

The entire audible spectrum, from the resounding bass smoothly thru the soothing middle ranges to the clear tingling highs, is awaiting you in the miniature carspeakers, as these headphones comfortably engulf your ears. Feather-lite in weight, fully adjustable, the superior Permoflux quality is now available at popular prices. A wide selection of impedances.

All ear speakers are fully warranted for life.

STANDARD OF THE WORLD



P.O. Box 6364, Dept. RE 9
 GLENDALE, CALIFORNIA

Circle 140 on reader's service card

U.S. GOV'T ELECTRONIC SURPLUS

• Nationally Known-World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.

ORDER DIRECT FROM AD or WRITE FOR CATALOGS

STANDARD DIAL TELEPHONE

• (ITEM #715) - Standard, commercial telephone name as used throughout U.S.A. Attractive polished black, like new condition. Use as extension phone to private systems or connect several phones together for local intercom system. Full instructions are furnished. Wt. 9 lbs. Original Cost \$24.50.



F.O.B. \$5.95

STEP-BY-STEP AUTOMATIC SWITCH

• (ITEM #738) - Amazing "in-and-around" electro-magnetic telephone switch. Dial any bank pair from 1 to 100. Make your own telephone system. Can also be used to remotely connect up to 100 circuits over a single pair of wires.



• One of our FOUR STAR bargains. Comes complete with data, one dial and one line bank. Size, 5 1/2" x 12 1/2". Wt. 16 lbs. Cost gov't (over \$75.00). Complete! Switch, cover, dial, line bank, instructions..... F.O.B. \$9.95

TYPICAL BUYS FROM OUR 1967 CATALOGS

- \$ 350.00 - Geared 2-hp Battery Golf Car Motor \$24.95
- \$ 15.00 - Westinghouse DC Ammeter, 0 to 300..... \$ 7.11
- \$ 40.00 - Vacuum/Pressure Pump, 12-VDC \$11.95
- - - 80-MW Walkie-Talkies, Per Pair \$19.60
- - - Deluxe, Multi-Range, AC/DC Tester \$ 8.98
- \$4000.00 - Carrier Telephone Amplifier System \$13.91

SPECIAL SALE
Correspondence
Course In
ELECTRICAL
ENGINEERING



Sells For \$10.79 \$8.79 Postpaid Outside U.S.A.

• (ITEM #A181) - Wonderful chance to obtain technical training at Amazing Low Cost! Lincoln Engineering School has suspended its Correspondence Courses because of increased operating costs. We offer a limited number of the school's complete Electrical Engineering Course but without the examination paper grading service. The course consists of 14 lesson unit books, each book has the regular exams, and in a separate section, "Standard Answers" to each exam question.

• Course is well written, easy to understand, profusely illustrated. Reader's Digest size, easy to carry and study in spare time. Many Lincoln Engineering School students holding excellent jobs as a result of E.E.S. training. Course contains latest information on transistors, silicon diodes, etc. Additional book on how to build and operate a "Home Laboratory and Experimental Bench" furnished with each course.

SEND 25c COIN OR STAMPS FOR 3 MAIN CATALOGS
 All Items FOB Lincoln Money Back Guarantee

SURPLUS CENTER

DEPT. RE-097 LINCOLN, NEBR. 68501

Circle 141 on reader's service card

NOTEWORTHY CIRCUITS

AUDIO SWITCHING CIRCUIT

A means of selecting either of two audio signals from a remote locations is a desirable feature not often included in PA, broadcast and other sound-distribution equipment. Here is a circuit, that you can adapt for this purpose.

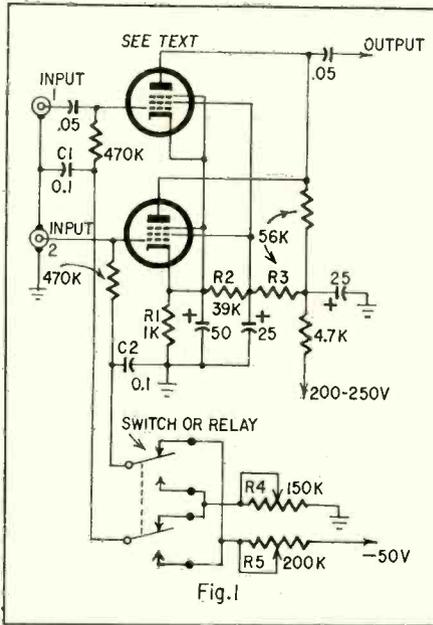


Fig. 1

The circuit in Fig. 1, abstracted from *Radio und Fernsehen* (Berlin), is designed for high-impedance circuits. The tubes are 6X4's but any pentode can be used with minor adjustments in the values of R1, R2 and R3 to provide normal screen and cathode voltages.

The desired signal is selected by a dpdt switch or relay connected as shown. The unwanted channel is biased to cutoff by returning its control grid to -50 volts. C1, C2, R4 and R5 are components in RC networks used to minimize switching transients and clicks.

UNUSUAL SQUELCH CIRCUIT

Here is a novel squelch circuit that you can add to a CB or similar monitoring receiver. It can be inserted between two audio stages in the set.


V1-a is an audio amplifier and V1-b is the squelch control tube. A neon glow lamp is the squelch element. When it is extinguished, it "opens" the circuit and prevents audio from appearing across the output terminals. When the lamp

fires, it conducts and feeds the signal to the following stage. A negative avc voltage that swings from zero to at least -2 is used to switch the lamp on and off.

The neon lamp may be any convenient type with a firing voltage of 90 or less and an extinction voltage of 55 or more. When the switch is open, the 220K plate resistor maintains the plate of V1-a at a level at least 5-10 volts above the firing voltage of the glow lamp. When the switch is closed, the voltage on both plates of V1 is the difference between the supply voltage (250) and the drop across the common plate resistor (R).

If the grid of V1-b is at zero volts, the plate current is at maximum and both plates drop to around 40 volts. At this level the neon lamp is off and the set is squelched. When an incoming signal develops avc voltage, plate current in V1-b drops and both plates rise to around 100 volts. This fires the lamp and conduction continues until the plate voltage drops below the extinction voltage of the lamp.

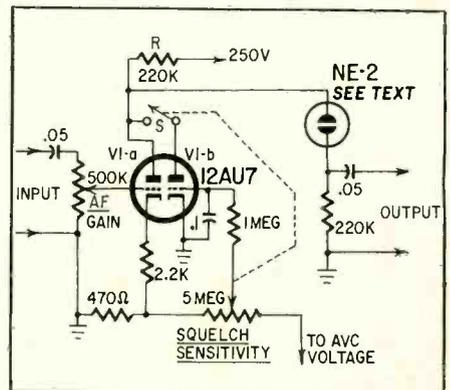The lamp in my circuit operated in an ambient light level of 5 to 50 foot-candles. Increasing the ambient light reduces the firing voltage; lowering the



light level increases the voltages needed to fire the lamp.

The bottom of the 5-megohm squelch control is returned to a tap on the V1-a cathode resistor. This applies a small positive voltage that bucks the negative self-bias on V1-b when the avc voltage is zero.

Within the range of 50 to 4,000 Hz, the distortion caused by the neon lamp is probably less than that caused by some more conventional squelch circuits. —Kendall Collins

END

GOVERNMENT SURPLUS

72 page illustrated Government Surplus Radio, Gadgets Catalog 25¢. MESHNA, Nahant, Mass. 01908

EDUCATION/ INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING. New home study course covering all makes electronic organ including transistors. Experimental kits—schematics—trouble-shooting. Accredited NHSC-GI Approved. Write for free booklet. NILES BRYANT SCHOOL, 3631 Stockton Blvd., Dept. F, Sacramento 20, Calif.

CORRESPONDENCE COURSES—B.Sc., Engineering, Electronics. Catalog \$1. CANADIAN INSTITUTE OF SCIENCE & TECHNOLOGY, 263E Adelaide St. W., Toronto

WANTED! TV-RADIOMEN to learn aircraft electronics servicing. Numerous job openings everywhere. Write: ACADEMY AVIONICS, Reno/Stead Airport, Reno, Nevada

SLEEP LEARNING. Hypnotism! Tapes, records, books, equipment. Details, strange catalog FREE. RESEARCH ASSOCIATION, Box 24-RD, Olympia, Wash.

HIGHLY EFFECTIVE HOME STUDY COURSE in Electronics Engineering Mathematics with circuit applications. Earn your Associate in Science degree. Free literature. COOK'S INSTITUTE OF ELECTRONICS ENGINEERING, P.O. Box 36185, Houston, Texas 77036 (Established 1945.)

HIGHLY EFFECTIVE HOME STUDY REVIEW for FCC commercial phone exams. Free literature. COOK'S SCHOOL OF ELECTRONICS, P.O. Box 36185, Houston, Texas 77036

ASSOCIATE DEGREE IN ELECTRONICS earned, first half by correspondence and second half in residence. Free catalog. GRANTHAM INSTITUTE, 1505 N. Western Ave., Hollywood, Calif. 90027

FCC First Class License in six weeks—nation's highest success rate—approved for Veterans Training. Write ELKINS INSTITUTE, 2603E Inwood Road, Dallas, Texas 75235

"SLEEP-LEARNING." Send for free brochure. "What's It All About." TAPES, Box-190RE, Quincy, Mass. 02169

SERVICES

Transistorized products dealers catalog. \$1. INTERMARKET, CPO 1717, Tokyo, Japan.

WHEN YOU ORDER MERCHANDISE BY MAIL . . .

- Be sure to include your name and address. Include your zip code number.
- Type or print if you can—if not, write clearly.
- Don't send cash! Remit by check or money order.
- Include allowances for postage charges if you know the weight of what you're ordering.
- Mention you saw it in

RADIO-ELECTRONICS

SALE ON ELECTRONICS BOOKS!

5 FOR \$3.98—
\$16.50 VALUE

Guaranteed \$16.50 Value. Grab bag of 5 Gernsback electronics books on testing, test equipment, TV, radio, hi-fi, stereo, etc. Clearance of books which sell for as high as \$4.50. Guaranteed retail value of \$16.50. Retail prices clearly printed on covers. Send check or money order to: GRAB BAG DEPT. D97, Gernsback Library, Inc., 154 West 14th Street, New York, N.Y. 10011.

FIND BURIED TREASURE!

10-DAY MONEY BACK GUARANTEE

TREASURE PROBE

\$18.88 ppd

ALL TRANSISTORIZED

3 ft. portable detector finds buried metal objects, Signals location with loud audible sound. Detects gold, silver, metallic ore and nuggets of all kinds. Find lost coins, jewelry, Indian artifacts, Civil War souvenirs. Treasureprobe guaranteed to equal detectors selling to \$150 or your money back. Absolutely complete, sensitive earphone, 9V battery, nothing else to buy.

TO ORDER: Send check, cash or money order, \$5.00 deposit for COD in Calif. Add 76¢ tax. TREASUREPROBE Dept. RBA P.O. Box 3446, Granada Hills, Calif. 91344

FREE!

PLUS CHOOSE ANY \$100 ITEM FREE

\$25

WORTH OF
TRANSISTORS
RECTIFIERS
RESISTORS
CONDENSERS
DIODES ETC.

Add 25¢ for handling

BOTH FREE WITH ANY \$10 ORDER

FACTORY TESTED **\$1 SEMI-KON-DUCTORS**

- 2-85 WATT 2N424 PLANAR, silicon. TO-53 npn \$1
- DUAL TRANSISTORS PNP (2N2807) NPN (2N2060) \$1
- 3-40W NPN SILICON MESA 2N1648, transistor \$1
- 4 2N170 TRANSISTORS, by GE, npn for gen'l rf. \$1
- 10 3 Amp RECT's, studs, silicon, to 800 V no test \$1
- 4-2N255 POWER TRANSISTOR EQUALS. \$1
- 10 PNP SWITCHING TRANS'RS. 2N104. no test \$1
- 2N3088 "N" Channel FET'S Very High Input Z. \$1
- 5 2N107 TRANS'RS, by GE, pnp, pop, audio pak \$1
- 3-2N1613 3W NPN SIL. 120 mc, by "Rheem" \$1
- 3-45 AMP POWER RECTIFIERS, stud, silicon. \$1

1 AMP SILICON RECTIFIERS

TESTED	PIV	Sale	PIV	Sale	PIV	Sale
	50	5¢	800	23¢	1800	99¢
	100	7¢	1000	40¢	2000	1.50
	200	9¢	1200	59¢	3000	1.90
	400	11¢	1400	69¢	4000	2.50
	600	19¢	1600	89¢		

- 5 2N706 500MW, 300MC NPN trans, TO18 \$1
- 10 PNP SWITCHING TRANSISTORS. no test. TO5 \$1
- 4 2N43 OUTPUT TRANSISTORS, by GE, pnp, TO5 \$1
- 1-IGNITION SWITCHING TRANSISTORS, 10 AMP \$1
- 25 GERMANIUM & SILICON DIODES. no test \$1
- 25 TOP HAT RECTIFIERS, silicon, 750 ma, no test \$1
- 2-1000 MC-TRANSISTOR 2N918 NPN SILICON \$1
- 4 2N333 NPN SILICON transistors, Silicon \$1
- 4 BIDIRECTIONAL TRANSISTORS, 2N1641 \$1
- 10 NPN SWITCHING TRANS'RS, 2N338 no test \$1
- 15 NPN TRANS'RS, CK722, 2N35, 107, no test \$1
- 15 NPN TRANSISTORS, 2N35, 170, 440, no test \$1
- 30 TRANSISTORS, rf, if, audio osc-ifs, TO5 no test \$1
- 10 FAMOUS CK722 TRANSISTORS. pnp no test \$1
- 30 TRANSISTORS, rf, if, audio, no test. TO5 no test \$1
- 4 35-W TRANS'RS, 2N1434, CRS, TO10. stud. \$1

SILICON POWER STUD RECTIFIERS

AMPS	Factory Tested	50 PIV	100 PIV	200 PIV
3		7¢	11¢	17¢
15		22¢	40¢	65¢
45		75¢	90¢	1.25
160	All Tests	2.50	2.95	4.05
250		4.50	5.50	6.89

AMPS	400 PIV	600 PIV	800 PIV	1000 PIV
3	22¢	31¢	40¢	59¢
15	90¢	1.35	1.59	1.79
45	1.59	1.90	2.50	2.95
160	5.75	7.50	9.25	10.95
250	9.59	12.53	15.00	19.95

Factory Tested	SILICON CONTROLLED RECTIFIERS	SILICON TUBE SPECIALS
50	7 48¢ 16 70¢ 25 80¢	5U4GB 2.39
100	70 1.05 1.20	5R4 4.39
200	1.05 1.30 1.70	OZ4 2.39
300	1.60 1.90 2.20	6AU4GT 2.39
400	2.10 2.30 2.70	866A 11.19
500	2.80 3.00 3.30	2 Amp 39¢ EA
600	3.00 3.30 3.90	1000 PIV

Special! MOVIN' sale

6-MONTHS' GUARANTEE

Poly Paks, the only company of its kind in the world due to its tremendous purchasing power, quality and factory testing procedures, GUARANTEES all items AS ADVERTISED for 6 months or your money back. A 'FIRST' ANYWHERE

1 AMP ZENER RECTIFIERS

Actual Size

PIV	Sale	PIV	Sale
50	5¢	600	19¢
100	7¢	800	25¢
200	9¢	1000	45¢
400	12¢		

2N1100 \$1.99

VCB (volts) 120

GLASS AMP ONE AMP

PRV may be exceeded without the rectifier breaking down.

PIV	Sale	PIV	Sale
50	5¢	600	19¢
100	7¢	800	29¢
200	9¢	1000	45¢
400	13¢	1200	59¢

WORLD'S MOST POPULAR \$1 PARTS PAKS

- 10 TRANSISTOR ELECTROLYTICS: 10mf to 500mf \$1
- 40 "TINY" RESISTORS, 1/10W, 5% tol! \$1
- 10 TRANSISTOR SOCKETS for pnp-npn transistors \$1
- 30 MOLDED COND'S. mylar, porc, black beauty \$1
- 10 TRANSISTOR ELECTROLYTICS: 10mf to 600mf \$1
- 50 COILS & CHOKES, if, rf, ant, osc, & more \$1
- 35 TWO WATERS, asst incl: A.B., 5% tol! \$1
- 30 "YELLOW" MYLAR CONDENSERS, asst val \$1
- 60 CERAMIC CONDENSERS, discs, npo's, to .05 \$1
- 60 TUBULAR CONDENS'RS, to .5 mf, to 1 Kv, asst \$1
- 40 DISC CONDENSERS, 27mmf to .05mf to 1Kv \$1
- 60 TUBE SOCKETS, receptacles, plugs, audio, etc. \$1
- 30 POWER RESISTORS, 5 to 50W, to 24K ohms \$1
- 65 HALF WATERS, asst incl: A.B., 5% tol! \$1
- 60 HI-Q RESIST'RS. 1/2, 1, 2W, 1% & 5% values \$1
- 10 VOLUME CONTROLS, to 1 meg, switch too! \$1
- 10 ELECTROLYTICS, to 600mf, asst FP & tubulars \$1
- 50 RADIO & TV KNOBS, asst. colors & styles \$1
- 4 TRANSISTOR TRANSFORMERS, asst. worth \$25 \$1
- 40 PRECISION RESISTORS, 1/2, 1, 2W; 1% values \$1
- 40 CORNING "LOW NOISE" resistors, asst. \$1
- 10 PHONO PLUG & JACK SETS, tuners, amps \$1
- 50 TERMINAL STRIPS. 1 to 8 solder lug types \$1
- \$25 SURPRISE PAK: transistors, rect. diodes, etc. \$1
- 10 TUBULAR ELECTROLYTICS, to 500 mf \$1


10¢ FOR OUR XMAS' BARGAIN CATALOG ON:

Semiconductors Poly Paks Parts

POLY PAKS

TERMS: send check, money order, include postage—avg. wt. per pak 1 lb. Rated, net 30 days. CODs 25%

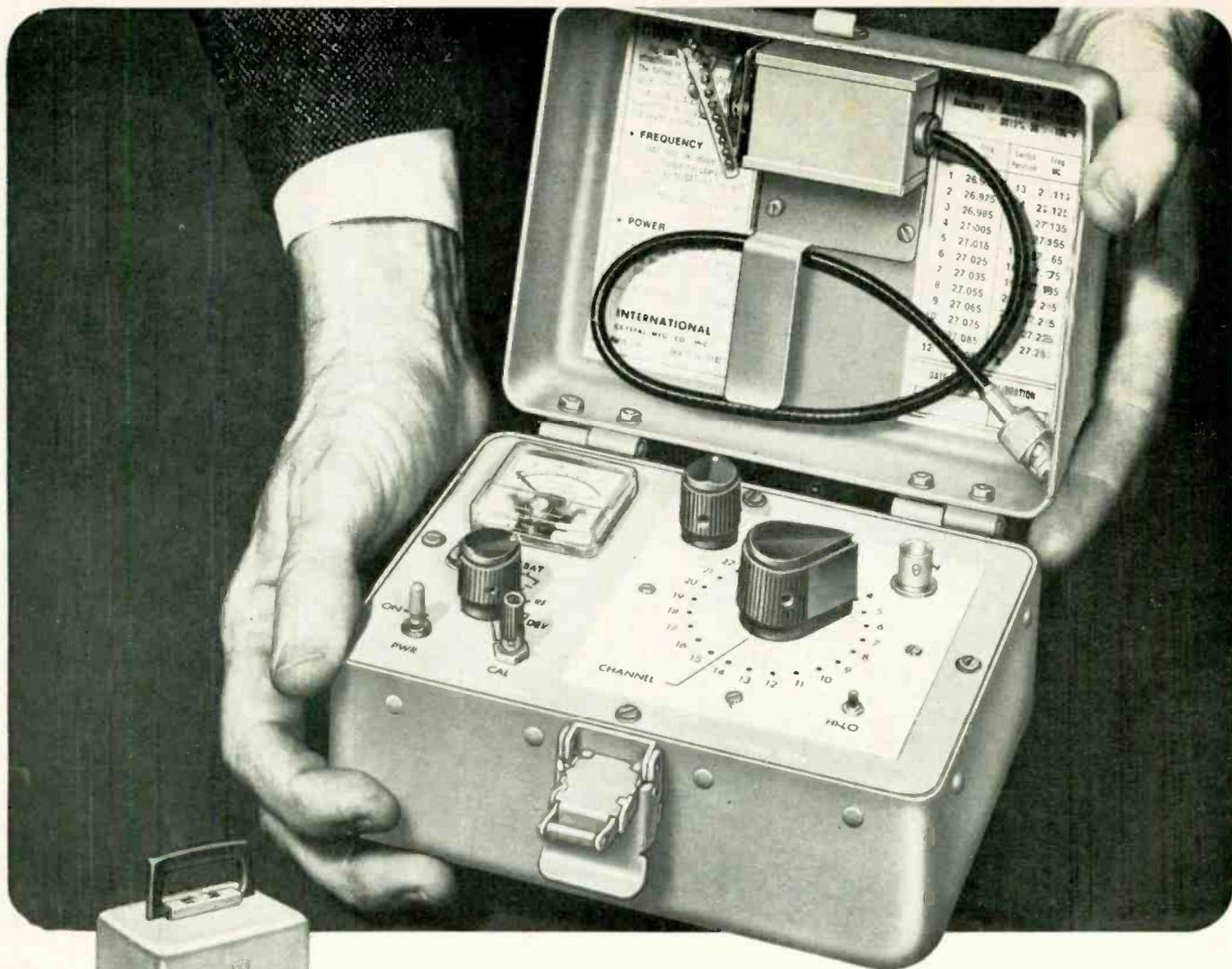P.O. BOX 942 R
SO. LYNNFIELD, MASS. 01940
"PAK-KING" of the World



...THREE IN ONE


INTERNATIONAL'S 6024 FREQUENCY METER

- SECONDARY FREQUENCY STANDARD
- SIGNAL GENERATOR
- POWER METER

The all new 6024 packs three test instruments into one small package for fast, professional servicing on all makes of Citizens Radio transceivers. You have at the flick of a switch, a SECONDARY FREQUENCY STANDARD, range 26.965 to 27.255 MHz with Counter Circuit, zero to 2500 Hz; SIGNAL GENERATOR, 26.965 to 27.555 MHz and DUMMY LOAD/POWER METER up to 5 watts. Order your International 6024 today! It's all new.

Complete with connecting cable, dummy load, rechargeable battery and charger. **\$345⁰⁰**

Circle 148 on reader's service card

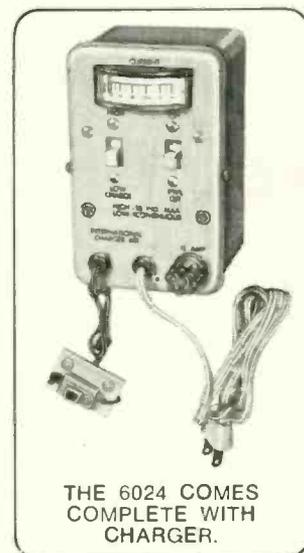

THE 6024 COMES COMPLETE WITH CHARGER.

WRITE FOR CATALOG



CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

RADIO-ELECTRONICS

NO REWARD THE EXACT KID



Be on the lookout for the Wide Ranger. He represents CDE's wide-range electrolytic program in the TV serviceman's never ending fight for easier, faster, more profitable service calls.








It doesn't pay you to go looking for the Exact Kid—any Exact Kid.

The Wide Ranger's 200-plus replacement electrolytics do the job of the Exact Kid's thousands. So your distributor always has the wide range electrolytic you need, in stock.

That's why everybody calls the CDE **WIDE RANGER*** a Good Guy.

CDE CORNELL-DUBILIER

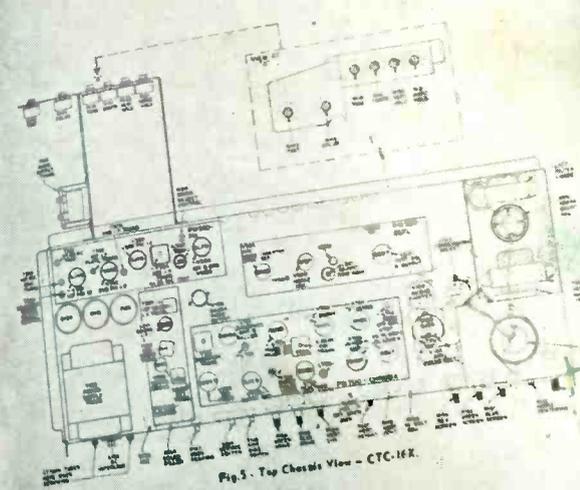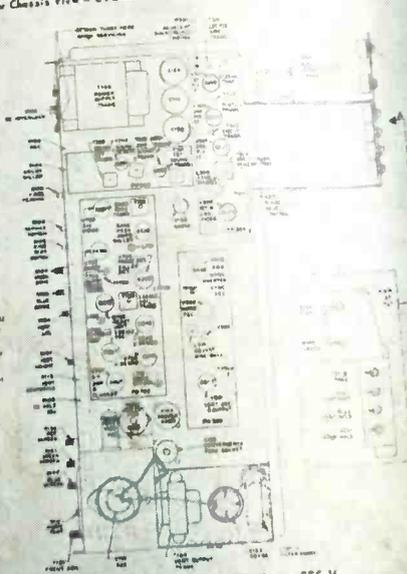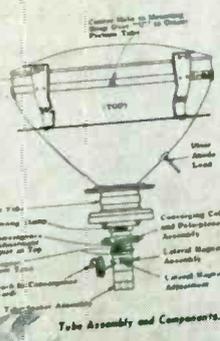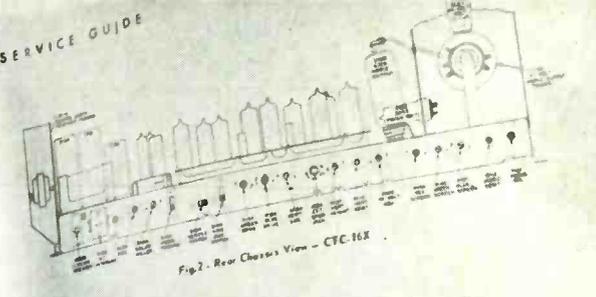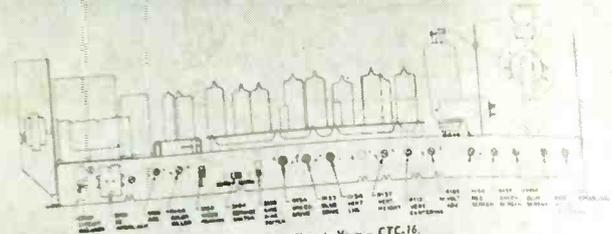

You need this guide for RCA Color Home Service Calls!

RCA'S NEW FIELD SERVICE GUIDE, ERT-200 helps you make all adjustments on all RCA color sets from 1955 to 1966 that can be performed in the home... including step-by-step procedure for replacing a color picture tube.

Three part index lets you look up the set you are working on by model number, name or chassis number. You'll find the ERT-200 Field Service Guide indispensable. There's nothing like it on house calls for RCA color sets.

WHAT THIS GUIDE CONTAINS:


- Schematics on all RCA color sets from 1955 to 1966
- Field service adjustments (AGC, linearity, centering, etc.)
- Convergence, purity and black and white setup adjustments
- Parts lists
- Wave forms keyed to test points for majority of chassis
- Top and rear chassis views
- Photos of typical receivers
- Index of models from CTC2 through CTC20
- Separate section on tuner schematics
- Separate section on remote tuner schematics



FIELD-SERVICE GUIDE

RCA COLOR-TV RECEIVERS

1955-1966

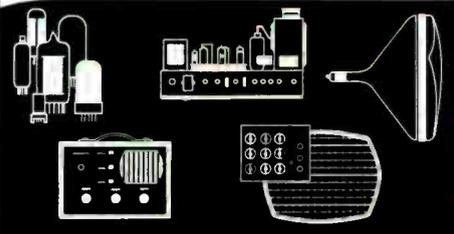

FEATURES:

- Field Service Adjustments - CTC-16 through CTC-20A
- Top and Rear Chassis Views
- Schematic Diagrams
- Vacuum Waveform Chart for Test Points
- Secure Section on Test Schematics
- Parts Lists
- Comprehensive Index of Model Numbers, Model Names and Chassis Numbers

See your RCA Tube Distributor today and arrange to get your copy.

RCA Electronic Components and Devices, Harrison, N.J. 07029



The Most Trusted Name in Electronics